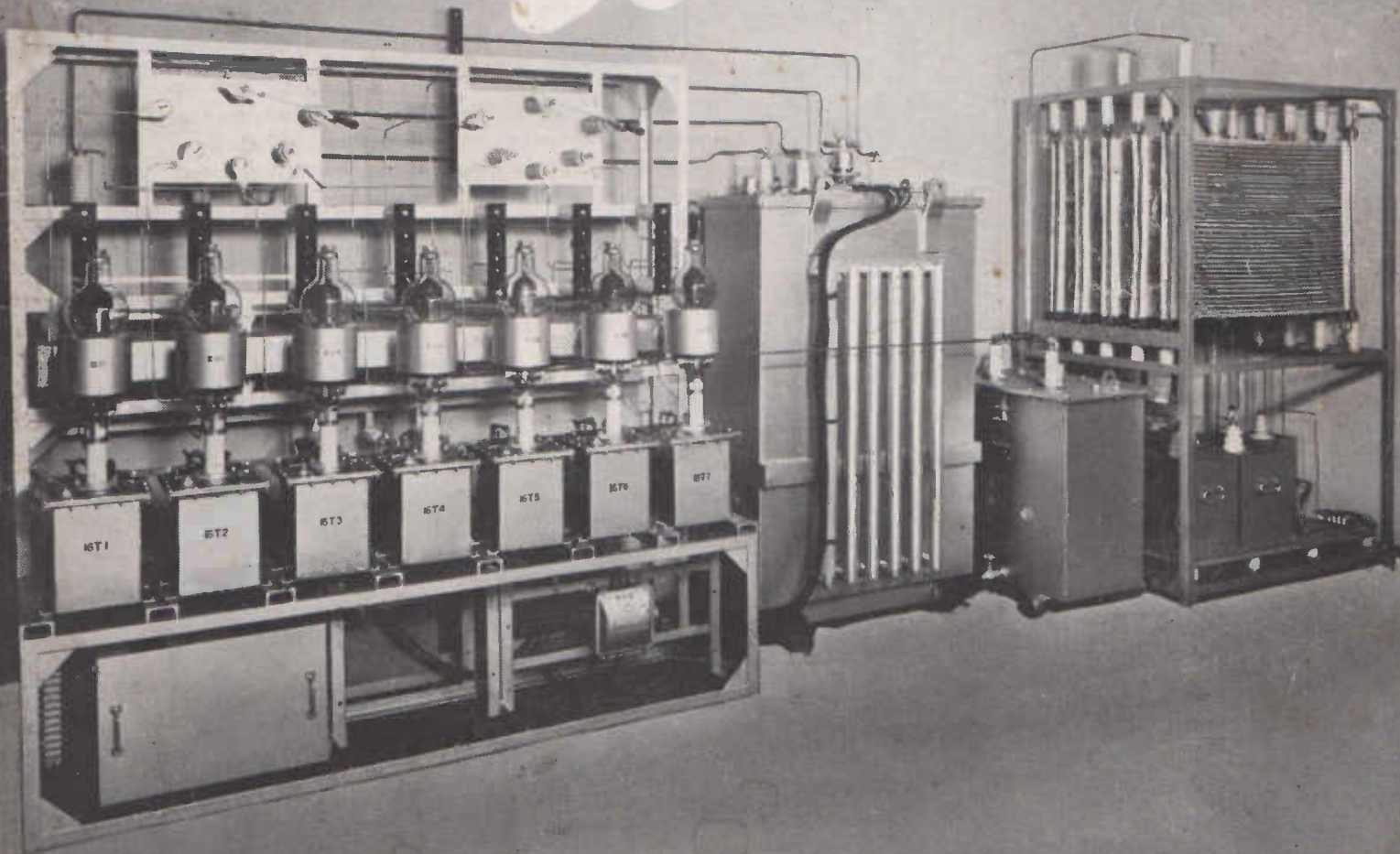


THE
AUSTRALASIAN

DECEMBER 10, 1938
VOL. 3 — NO. 8
PRICE, 1/-

Radio World

Registered at the G.P.O.,
Sydney, for transmission
by post as a periodical



—See Page 8

- "1939 SKY-KING DUAL-WAVE FIVE" USES LATEST 6K8-G CONVERTER:
- HOME RECORDING FOR THE AMATEUR: DIRECT-READING RESISTANCE AND
- CAPACITY BRIDGE: FIVE-BAND TRANSMITTER: "HI-FI" SPEAKER BAFFLE.



OUT BACK *BUT* UP TO DATE..

WHEREVER you go in Australia you will find Ever Ready Batteries. In outback areas, for example, it will be Ever Ready "Superdynes" in the farmer's radio, keeping him in touch with the world, keeping him up-to-date. Or if his set is a recent model, the chances are that it will be operated by an Ever Ready Air Cell, the new type battery that has replaced the accumulator because it needs no recharging and no attention for twelve months (with normal use). Even if there isn't a radio set within ten miles, there will be an Ever Ready Torch, powered with Ever Ready Torch Refills, somewhere handy, ready for use "after dark"

In the city, too, Ever Ready batteries and torches serve you in a thousand different ways. For maximum power, long life and better value, there is nothing to equal an "Ever Ready" product.

The Ever Ready Co. (Aust.) Pty. Ltd.
SYDNEY



EVER READY

TORCHES, TORCH REFILLS, RADIO BATTERIES, AIR CELLS


"1939 SKY-KING DUAL-WAVE FIVE" Makes Kit-Set History!

Features New . . .


FOXRADIO COIL KIT!

The secret of the outstanding success of this new "Sky-King" is the special FOXRADIO Coil Kit developed to match the recently-released 6K8G mixer oscillator.

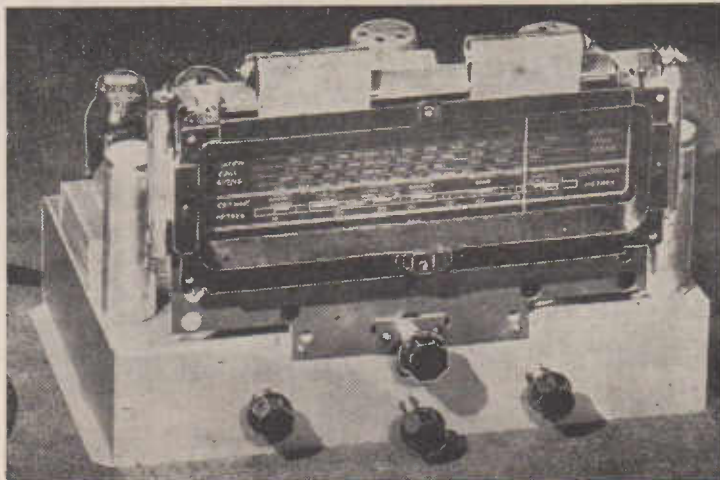FOXRADIO Type DK-465 k.c. coil kit comprises dual-wave, aerial and oscillator coils, two high-gain iron-cored 465 k.c. intermediates 65/-



Superior even to last year's model—which broke all records for ease and economy of construction, coupled with amazing all-round performance—this new 1939 version of the "Sky-King Dual-Wave Five" is a set anyone can build with perfect results. For DX work on both broadcast and short-wave, for volume and for tone, it is the finest and most up-to-date 4/5 yet offered to the set-builder. Only finest quality parts supplied with each kit—ORDER YOURS NOW!

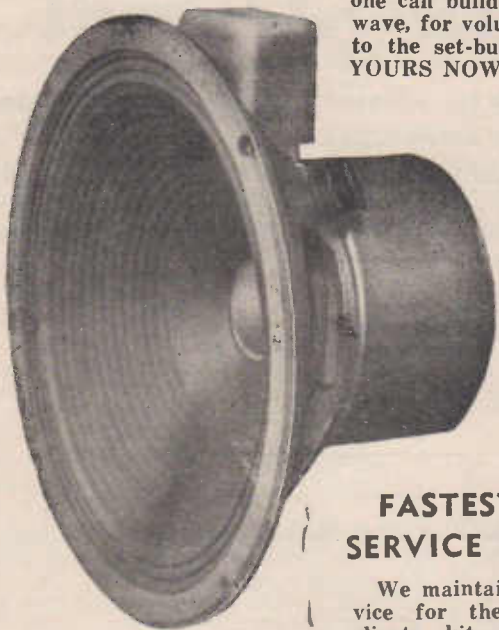

Complete Kit with Valves and **£16-6-9**
new Amplion "V" type speaker

We supply this latest Amplion Type "V" 12-inch speaker with every kit. Write for pamphlet describing its many new features.

FASTEST MAIL ORDER SERVICE IN AUSTRALIA!

We maintain a special mail-order service for the convenience of country clients—kits packed and despatched within 24 hours of receipt of your order. Complete kits of parts are available for any receiver described in "Radio World."


FOXRADIO

COILS AND COIL KITS

FOX & MacGILLYCUDDY LTD.

MERINO HOUSE, 57 YORK STREET, SYDNEY.

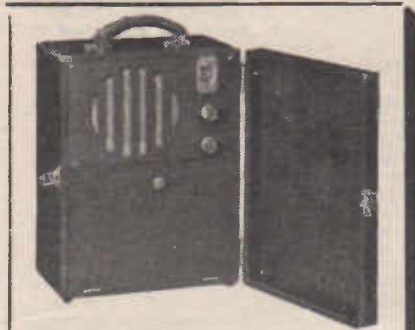Telephone : B 2409-19 - - - Telegrams : Foxradio



BUILD AN "OUTDOOR PORTABLE" FOR CHRISTMAS!

More compact, powerful and efficient than ever, this year's "Outdoor Portable Four" is the greatest portable in years. Outstanding features are full automatic volume control, automatic grid bias, special reflex circuit, exceptionally high sensitivity giving excellent inter-State reception.

Write for our list of parts and price for complete kit, including valves, batteries, speaker and cabinet.

Boost your Signals from R4 to R9+

"NOISEMASTER"
Aerial Kit drags up
signals out of the mush
to overload your speaker

DO mush and hellish noise drown these sought-for, rarely heard distant stations? Let the "NOISEMASTER" Engineered All-Purpose Aerial Kit drag them in and boost up signals to overload your speaker. "NOISEMASTER" wipes out noise and local static, and boosts up signals, even as much as from R4 to R9 plus!

No one else would ever dare make such a claim — no other aerial of ANY TYPE can give you such incredible performance, because "Noise-master" is the only Aerial Kit authorised to use the wonderful American invention "ANTENNEX." It acts like a purifier and cleans out every trace of locally created noise, leaving all stations beautifully clear at astounding volume.

Besides, you get in the "Noise-master" Kit 200 feet of special aerial wire, 12 specially designed transposition blocks, earth clamp, lead-in strip, screws, lightning arresters, etc. Easy to-follow instructions and drawings with each Kit enable you to set up your aerial in a very short time. No testing. No doubt. No delay. Once "Noise-master" is fitted, your noise-troubles end! Send this special form for your "Noise-master" Aerial Kit NOW, and have revealed to you a glorious new thrill in reception that makes you feel your set is new again.

**Send for yours
without Delay**

Antennex (A'sia.) Corporation
Box 3868 T, G.P.O., Sydney.

Send me right away your "Noise-master" Kit. I enclose 52/6 in postal notes, money order, cheque. (Add exchange to country and interstate cheques.)

NAME

ADDRESS

A.R.W. 7/38.

THE AUSTRALASIAN RADIO WORLD

Incorporating the
ALL-WAVE ALL-WORLD DX NEWS.

Managing Editor:
A. EARL READ, B.Sc.

Vol. 3

DECEMBER, 1938.


No. 8.

CONTENTS:

The "Sky-King Dual-Wave Five"	3
Resistance And Capacity Checker	6
Tasma 1.4-Volt Valve Receiver Gives Outstanding Results	7
More About The 5-Metre Super-Gainer	10
"Hi-Fi" Speaker Baffle	12
Radio For Bush Search Parties	14
Waverley And Hurstville Radio Club Notes	16
Improved Performance From 6K8G Converter	17
Home Recording (1)	21
World Shortwave Stations	23
5-Band 10- To 160-Metre 'Phone And C.W. Transmitter	29
What's New In Radio	34
All-Wave All-World DX News	41
Shortwave Review	42
Hourly Tuning Guide	46
5- And 10-Metre Transmitter Next Month	48

The "Australasian Radio World" is published monthly by Trade Publications Proprietary, Ltd., Editorial offices, 214 George Street, Sydney, N.S.W. Telephone BW 6577. Cable address: "Repress," Sydney. Advertisers please note that copy should reach office of publication by 14th of month preceding that specified for insertion.

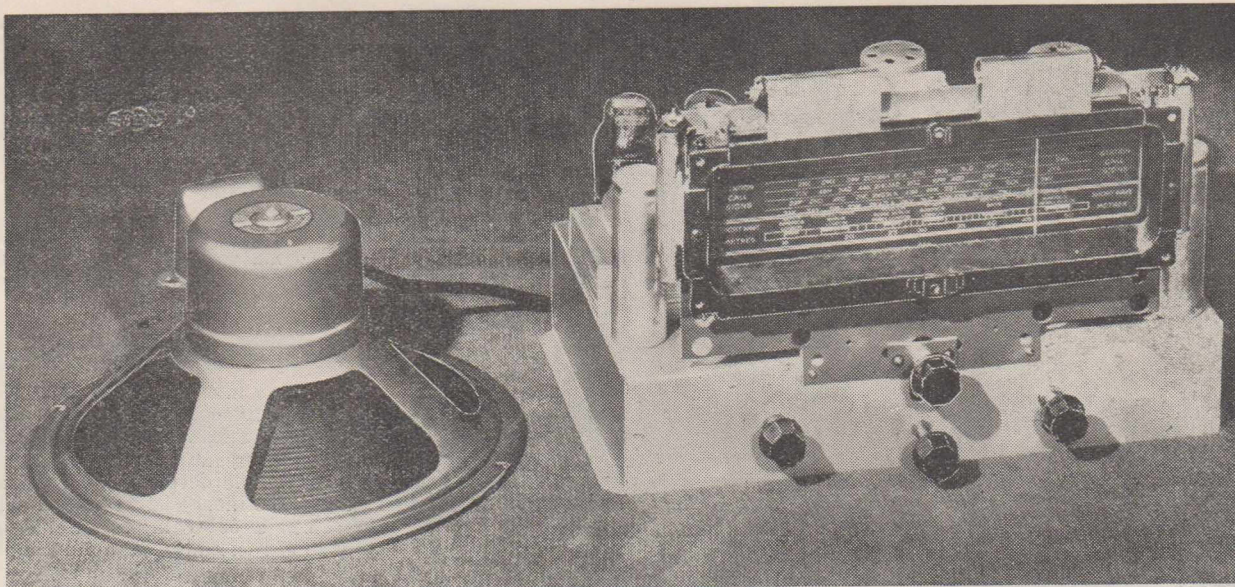Subscription rates: 1/- per copy, 10/6 per year (12 issues) post free to Australia and New Zealand. Subscribers in New Zealand can remit by Postal Note or Money Order.



This view shows the completed "1939 Sky King," with a Rola K12 speaker on the left.

The . . . 1939 Sky-King Dual-Wave Five

This latest improved version of last year's "Sky-King D.W. Five" uses the new 6K8G mixer oscillator. Designed for maximum performance from five valves, this receiver gives high gain on both bands, while excellent tone is ensured by the use of inverse feedback.

two high-gain iron-cored 465 k.c. i.f. transformers, were made available specially for this receiver by "Fox-radio" (Messrs. Fox and MacGillycuddy Ltd., of Sydney).

Other important improvements on last year's model comprise the use throughout of octal-based "G" type valves, and the substitution of a 6V6G beam output tetrode for the 42 in the original receiver. Inverse feedback has been applied, giving a fidelity of

FOR some years now valve design engineers have been concentrating their attentions towards improving mixer-oscillator valve performance, particularly on short waves. The latest important advance in this direction has been the recent release of the 6K8G (to which a separate article is devoted elsewhere in this issue).

special coil kit is required to suit the 6K8G. The dual-wave unit used in the original model, together with the


Main features of this new converter valve include greatly-improved oscillator stability on all bands, overcoming frequency drift and flutter, coupled with excellent sensitivity and particularly good all-round performance on the highest frequencies of the shortwave band.


Special Coil Kit Required.

The "1939 Sky King Dual-Wave Five" is a five-valve version of a special six-valve receiver recently developed by A. W. Valve Co.

A particular point to note is that a

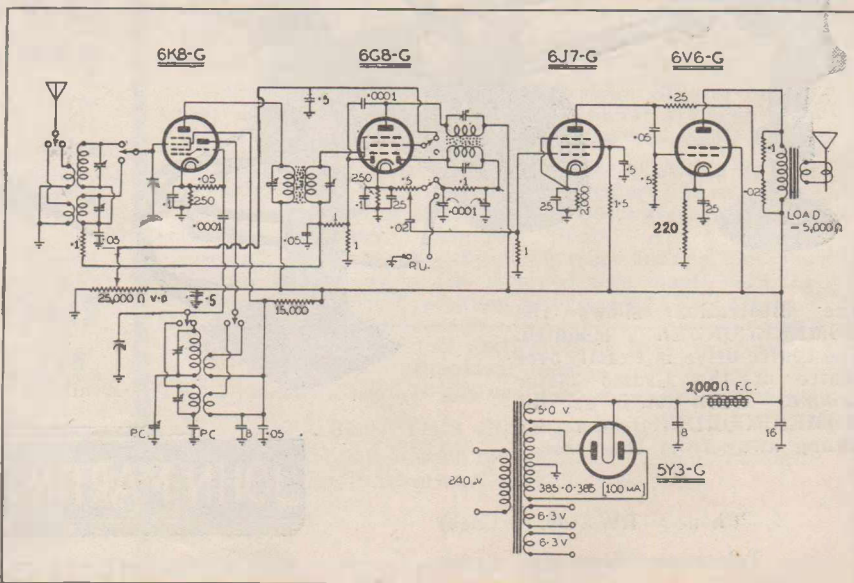The circuit of the "1939 Sky King," which uses the recently-released 6K8G mixer oscillator.



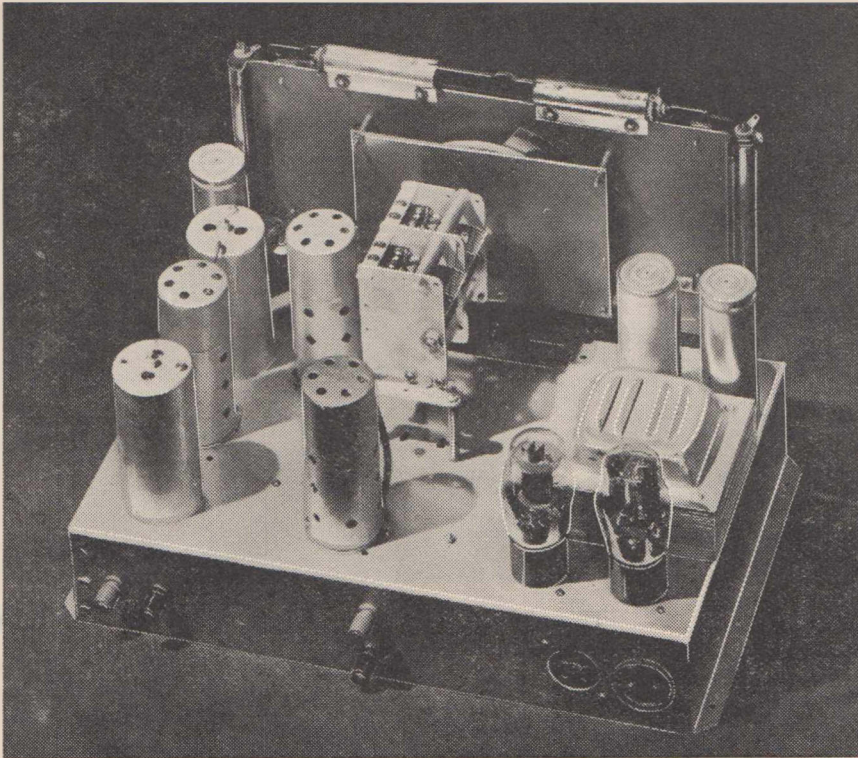

A rear view of the completed receiver, showing the aerial and earth terminals (left), pick-up terminals (centre), and speaker and output sockets (right).

The Foxradio coil kit supplied is colour-coded and is simple both to mount and wire. The dual-wave unit has been designed to employ a minimum amount of shielding, consistent with stable performance, thus keeping the efficiency high.

Further Circuit Details.

The valve line-up of this new "Sky King" comprises the 6K8G mixer, followed by a 6G8G, with the pentode section acting as i.f. amplifier, one diode as second detector and the other as a.v.c. rectifier. The audio channel comprises a 6J7G high-gain pentode as driver, resistance capacity coupled to a 6V6G beam output tetrode. A 5Y3G is used as rectifier. No tone control is used, as the inverse feedback supplies all the correction that is necessary.

The list of parts published on page 48 will enable builders to assemble the components needed in readiness for the article that will appear next month outlining the assembly, wiring and alignment. A complete under-chassis wiring diagram, together with a separate sketch showing coil unit connections, will also be published, together with further photographs.


reproduction that is comparable with that obtainable from a power triode. Other alterations made are minor, and have been included only to conform with the circuit developed by A. W.

Valve Co. The shortwave band coverage chosen can be from either 16 to 51 metres or from 13 to 39 metres, coil data being supplied for both.

MAKE YOUR OWN RECORDINGS

You can make your own recordings inexpensively and simply with the "MAYNARD" HOMERECORDER. Just hook up the cutting head terminals to the output of your radio and record on a "MAYNARD" HOMERECORDER blank.

- | | | | |
|-----------------------|--------------|------------------------|--------------|
| 6in. blanks | 1/9 plus tax | 10in. blanks | 3/6 plus tax |
| 8in. blanks | 2/6 plus tax | 12in. blanks | 5/6 plus tax |

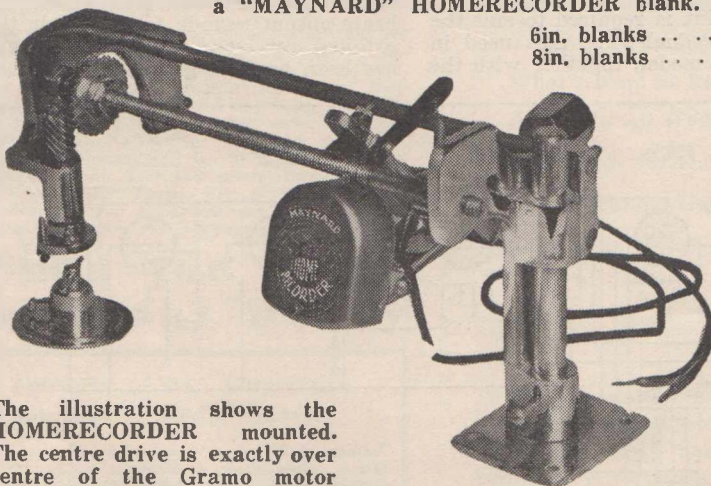

The illustration shows the HOMERECORDER mounted. The centre drive is exactly over centre of the Gramo motor spindle. When not in use the HOMERECORDER can be swung away from the table.



Complete with cutting head.

Available from "The Friendly Wholesale House."

'Phone : BW 3109 (2 lines)
Telegrams : "Jonmar," Sydney.



116-118 Clarence Street, Sydney.

A Wonderful Record . . . BREVILLE WINS AGAIN !

Two of the first three International DX (long distance) Contests conducted by the "Australasian Radio World" were won by Breville users. The First Contest was won by Mr. Ern Neill, of Ipswich, Queensland, with the wonderful record of receiving 1825 stations on his Breville Receiver.

Now BREVILLE Receives Over 80 COUNTRIES



Winner of the Third DX Contest, Mr. R. G. Cook, with his Breville receivers.

PERFORMANCE COUNTS

The Breville sets used by Mr. Cook were Model 109—8-Valve Triple-Wave A.C. Electric priced from 38 Guineas, and Model 85—5-Valve Broadcast Vibrator, price 25 guineas.

YOU TOO CAN BREAK RECORDS WITH BREVILLE.

Manufactured and fully guaranteed by :

**BREVILLE RADIO
Pty. Ltd.**

Head Office and Factory :
67-73 Missenden Road, Camperdown,
N.S.W., Australia.

Phone : L 3688 (4 lines).
Telegrams & Cables : "Breville," Sydney.
And at Brisbane and Newcastle.

Distributors in all States and New Zealand.

First place in the Third Contest goes to Mr. R. G. Cook, of Bowen, Qld., who writes as follows:—

"My main receiver is the latest eight-tube triple-wave Breville, using Radiotrons 6U7 (2), 6A8, 6B6, 6U6, 6C5, 5Y3, 6U6, coupled to a 12in. Rola speaker. This set gives me all the power that is required. I find that it is 100 per cent. efficient, and may add that the climatic conditions of North Queensland are not the best for DX on account of the heat and the heavy atmospheric conditions that prevail at all times of the year. At the present time I can bring in any of the southern commercial stations at R6-7 at mid-day, which is good for this part of the globe.

"My second set is a five-valve Breville vibrator broadcast model, with which I do all broadcast DX and have picked up many foreign stations in the wee small hours.

"Catching the elusive DX is a matter of sitting up late or early, and by doing this I have logged over 80 countries, giving me a total of 500 odd cards, which include Alaska, U.S.A., Germany, Belgium, South Africa, India, England, Scotland, Ecuador, Panama, Malaya, Manila, Hawaii, and others, which, if typed here, would take the entire page. My best reception was from K7ANQ, Alaska."

Send the coupon for full particulars of Breville "Record-Breaking" Sets.

POST THIS COUPON NOW !

Without obligation, send me FREE illustrated Catalogue of Breville Radio Receivers.

NAME

ADDRESS

.....

TEST EQUIPMENT No. 4

Resistance And Capacity Checker

“C” And “R” Checker : Main Applications.

Measures resistance from 10 ohms to 10 megohms with 1 per cent. accuracy; measures capacity from 10 mmfd. to 10 mfd. with 1 per cent. accuracy; gives rough check over ranges from 5 ohms to 100 megohms and from 5 mmfd. to 100 mfd.; measures power factor up to 60 per cent. of poor condensers from .1 mfd. upwards; compares components, including large inductances, with any suitable standard; provides a continuously variable 50-cycle signal up to 50 volts; provides a continuity test, with neon indication; gives approximate merit test of all condensers from .05 mfd. upwards, including electrolytics.

THE main capabilities of the instrument described in this article are tabulated above, and it will be seen that it is an exceptionally useful piece of gear. It is not intended for extreme accuracy over a narrow range of measurements, but rather for moderate accuracy over the greater part of the whole range of components that have to be dealt with in radio work generally, and experimenting particularly.

Such an instrument is indispensable in the workshop, and in the experimental laboratory encourages the sound practice of checking every component before putting it into use.

The basic circuit is shown on page 8. The component to be tested is connected at “res. cap.”, and is compared with any one of the six standards selected by the range switch.

To avoid the need for continuously variable standards, the ratio arm is made variable, and is composed of an ordinary potentiometer which is calibrated to read ratios directly. The bridge is supplied with a 50-cycle voltage and the balance or “null” point is shown by the 6E5 cathode ray indicator tube.

The reading of the potentiometer at balance, multiplied by the value of the standard in the circuit, gives the

A view of the completed instrument, which is mounted in a crackle-finished steel cabinet. The special scale illustrated will be reproduced full size next month.


The fourth of a series of articles on test equipment for servicemen, amateurs and experimenters, designed and described by . . .

W. McGOWAN (VK2MQ)

Further Circuit Features.

Referring to the circuit again, some of the other features are as follows: The special mains transformer supplies, as well as 50 volts for the bridge, 150 volts for “B” supply of the indicator tube. The value of the filter resistor should not be increased,

value directly, and as in this instrument the standards are all multiples of 10, this process demands only the simplest of mental calculation. For instance, if the potentiometer reading is .4 and the range switch is on 100, the result is 40 ohms, or if on the 10,000 range is 4000 ohms. and so on.

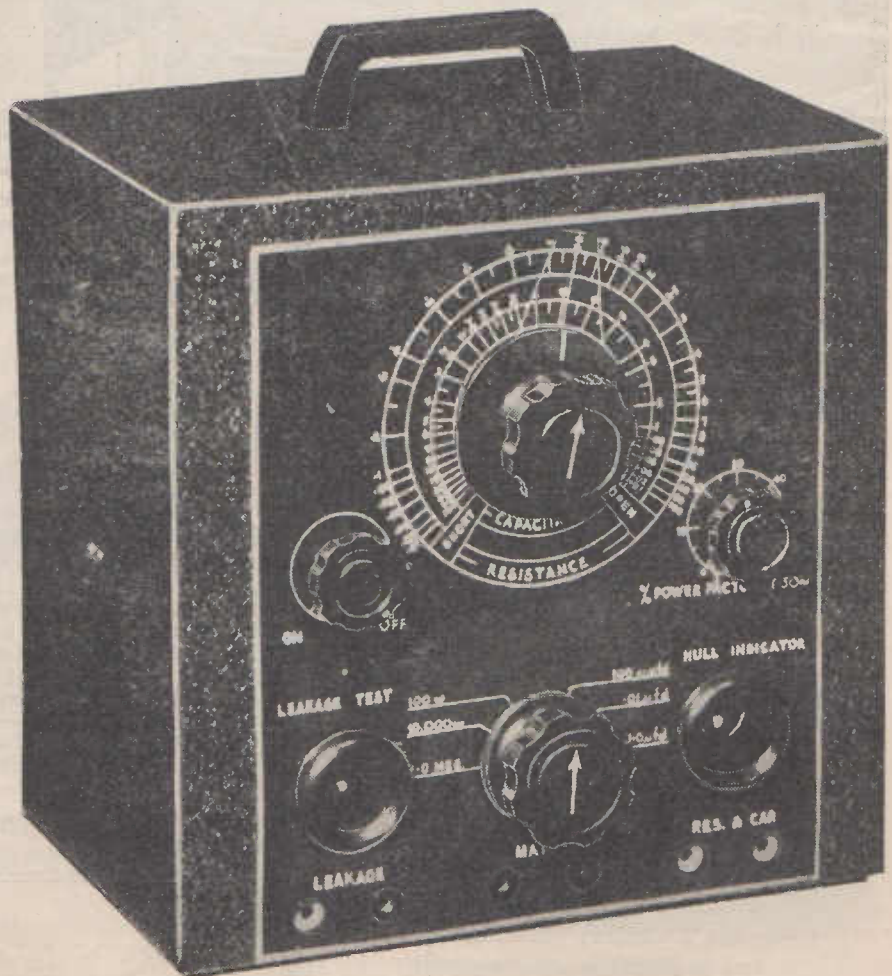

TASMA 1.4-VOLT VALVE RECEIVER GIVES OUTSTAND- ING PERFORMANCE

Special Ever Ready "A" Battery Available Shortly

The three views shown alongside were taken during field tests conducted in Sydney on what is probably the first commercial model receiver using the new 1.4-volt valves to be released. It is a Tasma five-valve dual-wave superhet, using 1N5G's in the r.f. and i.f. amplifier valve sockets, 1A7G pentagrid converter, 1H5G second detector, a.v.c. voltage rectifier and first audio stage, and a 1C5G power pentode in the output socket.

In the top photograph is Mr. Chas. Hart (left) Queensland manager for the Ever Ready Co., and Mr. G. K. Herring, Commonwealth sales manager.

EXCELLENT PERFORMANCE ON BOTH BANDS.

In the brief field and laboratory tests conducted by "Radio World," the receiver put up an excellent performance—actually far better than was expected from these unusually low consumption valves. As regards both selectivity and sensitivity, the receiver compares favourably with some "fives" on the market using two-volt valves throughout. Shortwave sensitivity is excellent—during the evening London on 16 metres could be brought in at full volume using only a dozen feet of wire attached to the aerial terminal.

DEMONSTRATION TRIP TO QUEENSLAND.


The receiver illustrated was taken to Queensland early this month by Messrs. G. K. Herring, Ever Ready sales manager, and D. B. Knock, radio editor of the "Bulletin," for the purpose of demonstrating it to the radio trade in Brisbane and surrounding districts, and also to conduct comprehensive field tests on its performance. It is hoped that a complete report will be available for publication in next month's "Radio World."

SPECIAL EVER READY BATTERY.

Incidentally, the Ever-Ready Company have announced that a new 1½-volt battery, designed to give over 900 hours of service from a five-valve receiver using 1.4-volt valves, is being developed, and will be released shortly.

"R. W." RECEIVER NEXT MONTH.

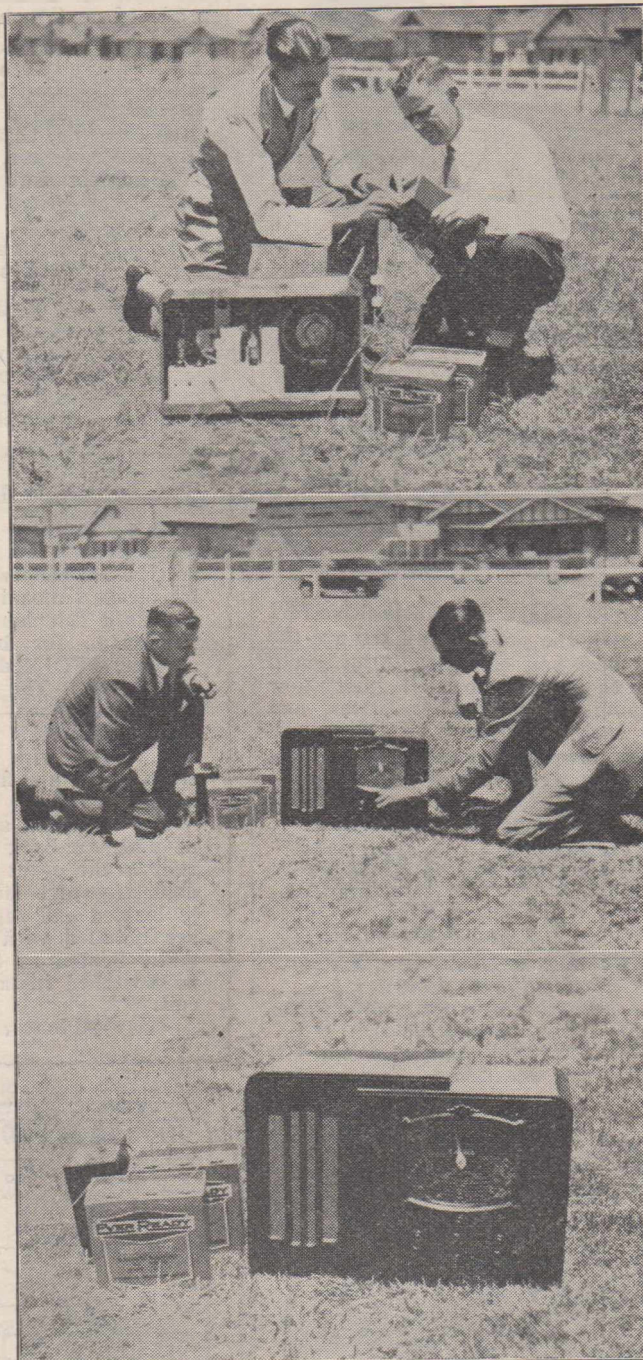In the meantime, a five-valve receiver using these new valves is nearing completion in the "Radio



World" laboratory, and a full description of its assembly and alignment, accompanied by photographs and diagrams, will be published in next month's issue, which will be a Special 1.4-Volt Valve Number.

for this would appreciably drop the voltage. The bridge voltage should be graduated to suit the impedance being measured, and this is done automatically by the 1000-ohm 3-watt resistor in series with the transformer winding and the ratio potentiometer.

For high impedance such as grid leaks and small condensers, which would be difficult to balance sharply without a high signal voltage, practically the full 50 volts is available, but for low impedances, which at 50 volts would pass too much current for

themselves and for the transformer, the voltage is reduced to a suitable value.

The 1000-ohm potentiometer should be a reliable one. In this case it is a Radiokes, and if the panel supplied is to be at all accurate, this make should



I BUY
RADIO PARTS
AND I WANT
THEM GOOD

YOU can take it for a positive fact that the products we sell are the very best you can get. But you'll have to see for yourself just how pleasingly low are our prices, and how snappy our service! If you have not yet seen how far you can make your money go, and what good service you can get, for your next radio requirements, come to

**MARTIN DE LAUNAY
PTY. LTD.**

Cr. Clarence & Druitt Sts., Sydney.
M 4263 (4 lines).
Cr. King & Darby St., Newcastle.
New. 959 (2 lines).
86 Keira St., Wollongong. Woll. 681.
Telegrams, "Martindel," Sydney and
Newcastle.

WE CAN GIVE
YOU THAT
AND PLENTY
BESIDES.



be used. (The scale shown in the front view of the instrument will be reproduced next month.—Ed.)

The input resistance to the 6E5 indicator is kept high; otherwise it would not be possible to get defined results with such a high impedance as, for example, that possessed by a 10 mmfd. condenser, which at 50 cycles is no less than about 300 megohms.

Accuracy Of Condensers And Resistors.

The accuracy of the instrument is no better than that of the standards used, but if one is not so particular about expensive shunts and has no chance of getting standards checked, condensers and resistances of the or-

This Month's Front Cover

This month's front cover photo shows the power supply section of the two 10-kilowatt broadcast transmitters built by Standard Telephones and Cables Pty. Ltd., for installation at stations 2FC Sydney and 3LO Melbourne. The power supply equipment shown comprises hot cathode mercury vapour rectifier valves, with high tension transformer and filter choke and condenser unit.

The rectifiers are all provided with arc-back indicators, so that in the event of failure the defective valve may be instantly located and replaced. Spares are installed, with cathodes normally heated so that they can be switched instantly into circuit.

—Photo courtesy S.T.C.


The Editor and Staff of "Radio World" join in wishing every reader the Compliments of the Season.

inary receiver type would do, provided they are within 5 per cent. limits. IRC precision type resistances can be had with 1 per cent. tolerance, which is excellent for most practical purposes.

Standard condensers are more difficult, and apart from the question of measuring their values, the type most commonly used are liable to vary with age, temperature, etc.

The smallest (.0001 mfd.) should be one of the new 1 per cent. T.C.C. silver-plated ceramic, the .01 mfd. a good quality mica and the largest (1 mfd.) a paper type. It is convenient for them to be slightly low, as the distributed capacity of the wiring will add a certain amount. Incidentally, the calibration of this instrument was done by a series of IRC 1 per cent. precision standards, and is substantially accurate.

(Continued on page 47.)

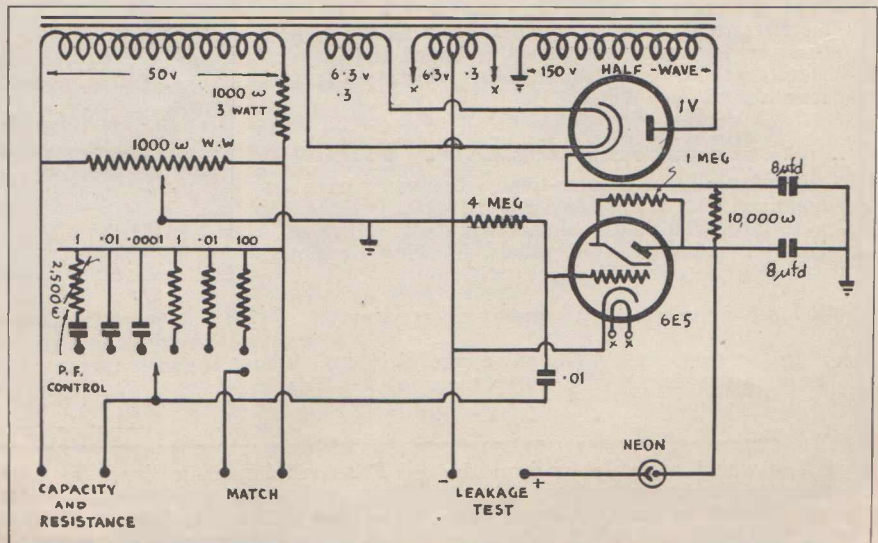

Circuit of the resistance-capacity bridge described in the accompanying article.

MICRO "ALL WAVE AUTOMATIC FIVE"

This is not just another radio receiver—look over its many features! All-wave coverage from 16 to 150 metres and 200 to 550 metres. Automatic tuning of six broadcast stations. Ultra-modern circuit employs an entirely new output tube. Attractive oval four-colour dial (dial shown is for descriptive purposes only). Dial is accurately calibrated, and all main shortwave bands clearly indicated.

Truly an ideal low-priced kit for the "ham," DX enthusiast or for a second set in the home.

Complete with valves and speaker . . . £11/18/6

Complete with speaker less valves . . . £9/17/6

(Freight paid to your nearest railway station)



The kit comes to you with the complete r.f. tuner, dial, gang condenser, and first tube socket ready wired and tested.

THE "MICRO" VIBRATOR POWER UNIT.

Special design allows for entirely hash-free operation on any battery receiver using 2, 4 or 6-volt valves. The new "Electronic" synchronous vibrator ensures long, trouble-free performance. Cut out expensive dry batteries now, and give your radio new life.

Complete Kit of Parts £4/1/6

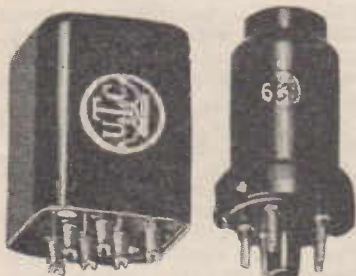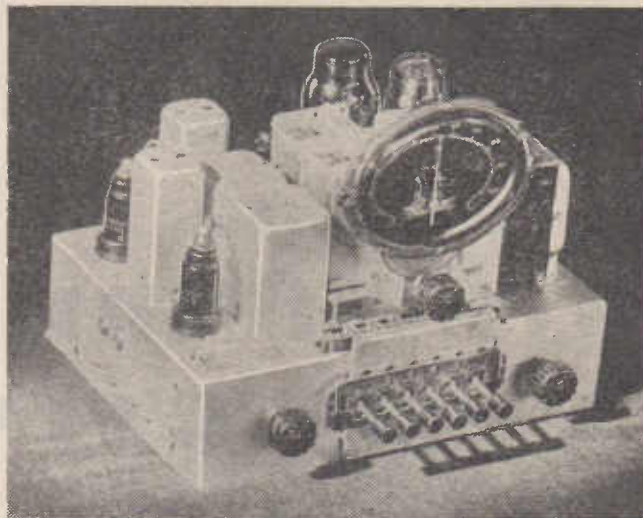Complete Kit, assembled and tested . . . £4/17/6



U.T.C. HIGH FIDELITY AUDIO UNITS.

Designed for broadcast and all quality amplifiers—the frequency range is flat from 30 to 20,000 cycles—series L.S., H.A. and "A."

WRITE FOR FULL PARTICULARS.

HEADPHONES.

FROST, definitely the most popular 'phones in N.Z. . . . 15/-

MICRO, high-grade English 'phones, used extensively in British Government departments, 18/6

British Post Office pattern, heavy brass morse keys. Here's the key you have tried hard to procure 52/6

"MEISSNER ALL-WAVE SEVEN."

Modern in every respect. Band

coverage 7.5 to 550 metres. Four colour dial; tone control, etc.

Complete kit with valves and speaker £19/10/-

HERE'S VALUE!

- Best quality electric jugs, 3 pint 27/6
- Speedee Toasters 18/6
- Speedee Jugs 21/6
- Spiral Indoor Aerial, with two insulators 1/9
- Enamelled Aerial Wire, 100ft. coil 4/9
- "Lektrite" Aerial, 100ft., 4/3
- Push-button Aerial Earth Switches 2/-

FIVE-BAND TRANSMITTER

Described this month. Write for our special price list. All components as specified.

MIKES FOR AMATEURS.

Now—a high-grade dynamic microphone for amateur or P.A. work. Frequency response 50 to 9000 cycles £5/5/-

ASTATIC, acorn model, T-3, crystal mike. Quality reproduction, ideal for dance band or studio work £6/10/-

ASTATIC, model D-104—the "hams" favourite £5/10/-

SHURE, model 70 SW, crystal, with modern desk stand . . . £6/10/-

U.T.C. AGAIN LEADS THE FIELD WITH TWO NEW SERIES TRANSFORMERS.

Series "R" transformers are designed for radio set replacement and manufacture. They are entirely universal and specially treated for long service under adverse humidity conditions. The range includes input, line, microphone, output, and many other types of transformers.

Series "S" transformers consist of a range of very attractive and efficient units for amateur and P.A. service. Varimatch modulation and driver transformers—universal output units to line and voice coil, and also power transformers and chokes.

U.T.C. manufacture the most complete range of transformers in the world. WRITE FOR DETAILS



COMPLETE AUDIO AMPLIFIERS

Ideally suited for all P.A. or modulator service. Power outputs from 15 to 120 watts. Provided with high and low gain input channels.

F. J. W. FEAR and CO.

31 WILLIS STREET, WELLINGTON, N.Z.

Telegrams

"FEAR"


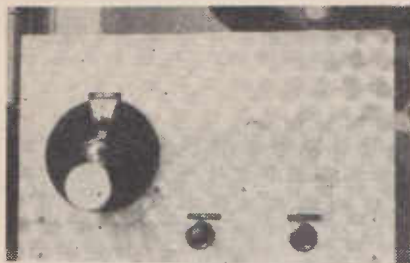


Fig. 1 (left): Front view of the receiver. The two small knobs are for i.f. gain and second detector regeneration.

Fig. 2 (right): End-on view, showing the tuning assembly.

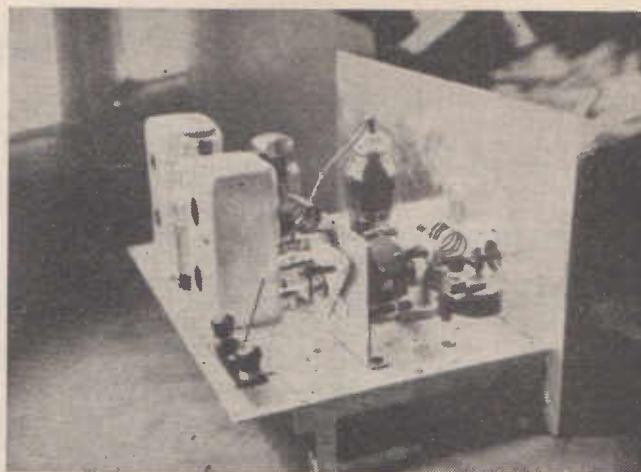

More About The . . . FIVE - METRE SUPER - GAINER

1600 k.c. I.F. Channel Is Of Vital Importance ★ Operational Data

By DON B. KNOCK (VK2NO)

Radio Editor, "The Bulletin."

THIS ultra-short-wave superhet, outlined in "Radio World" for October last, has since been put through its paces by the writer, and a few tips on construction should be of value.

The circuit diagram, with all resistor and capacity values, is again reproduced as a guide. Although the 6H6 twin diode is used as a noise-limiter across the audio output, this is not absolutely essential, unless the receiver is in a particularly bad location for interference from motor-car ignition. Fundamentally, this is a three-valve superhet, but, despite this apparent paucity of valves, it gives the precise results that Jones claimed in his original description in "Radio" (U.S.A.).

There are two important features which need watching, the intermediate frequency channel is provided by high-gain iron-cored I.F.T.s. at 1600 k.c., and the high-C oscillator section is used with a low-C detector. If an attempt is made to use anything but a very small tuning capacity in the detector portion of the 6J8G mixer, results will be indifferent, with lack of the essential sensitivity. Although a sensitive I.F. amplifier is provided with the special I.F.T.s. now available, the mixer plays an equally important part in the overall gain. Hence the necessity for tracking the high-C and low-C tuning circuits. This is by no

means difficult, as the receiver is designed to cover only 56 mc. to 60 mc.

Figure 2 shows the receiver from the oscillator-mixer end, the oscillator section being nearest to the front panel. The coil for the oscillator consists of four turns of 14-gauge copper wire, $\frac{1}{2}$ in. inside diameter and spaced to take up $\frac{3}{4}$ in. This is tuned by a Raymart 15mmfd. variable condenser. Normally this low-C ratio would fall short of 56mc., so, in order to cover the band with this small coil and to provide high-C tuning, a 50 mmfd. midget variable condenser is used as a padder or "band-setter" in shunt with the coil and 15mmfd. tuning condenser. This padder can be seen mounted vertically alongside the oscillator coil in Figure 2.

Once the padder is set for the band it must be locked in position, and the

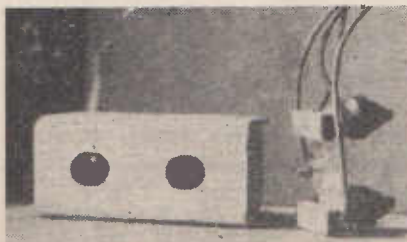


Fig. 3: The new 1600 k.c. i.f. transformers made by Tasma Radio. These are now available to experimenters.

shaft can be fixed by running sealing-wax or Chatterton's compound around the spindle where it enters the bearing. Because of the high frequency, it would hardly be possible to set this padder condenser accurately by knob-control, owing to hand-capacity. The condenser spindle is therefore cut short and slotted with a metal saw for bakelite screwdriver operation. As with the tuning condensers, good insulation must be used in the padder condenser. There are several older types of 50mmfd. midgets which can be suitably revamped by using WT/22 insulation material; they are likely to be stiff in action, an advantage in this case.


Ganged with the oscillator-tuning condenser, and with its coil on the other side of the small vertical screening partition, is the detector-tuning condenser, which is also a Raymart of originally 15mmfd. capacity. This condenser is doctored to provide a spacing of 3-16 in. between rotor and stator, the capacity then being in the vicinity of 7 mmfd. The grid coil is of 14-gauge copper with seven turns of $\frac{1}{2}$ in. inside diameter, with turns spaced a little more than the diameter of the wire. Although on paper it may appear impossible to get detector and oscillator circuits to track with such widely different constants, this is not so. The aerial is coupled through a 3-30mmfd. trimmer condenser, and in practice it is found that variation of this small capacity in series with the aerial has quite a bearing on the tracking.

To ensure that the receiver is covering the band, switch on the crystal oscillator of a 40-metre or 20-metre transmitter near by, and use the harmonic, which should be readily picked up in the receiver. The harmonic will be heard strongly at two points, differing by the intermediate frequency. In the case of the receiver illustrated the circuits were found to track better by using the lower-frequency harmonic. A calibrated absorption meter

can be used as a rough guide to the band in proximity to the oscillator coil.

I.F. Transformers.

The 1600 k.c. I.F.Ts. were made specially by Tasma Radio, and are particularly well designed. Trolital low-loss material is used for the assembly and the coils are wound with Litz wire on a new type of iron core. Only a small shunt capacity is used, and the windings are peaked at the frequency by the variable permeability screws, which are reached through the holes in the shield can. Remarkable high gain is obtained with these

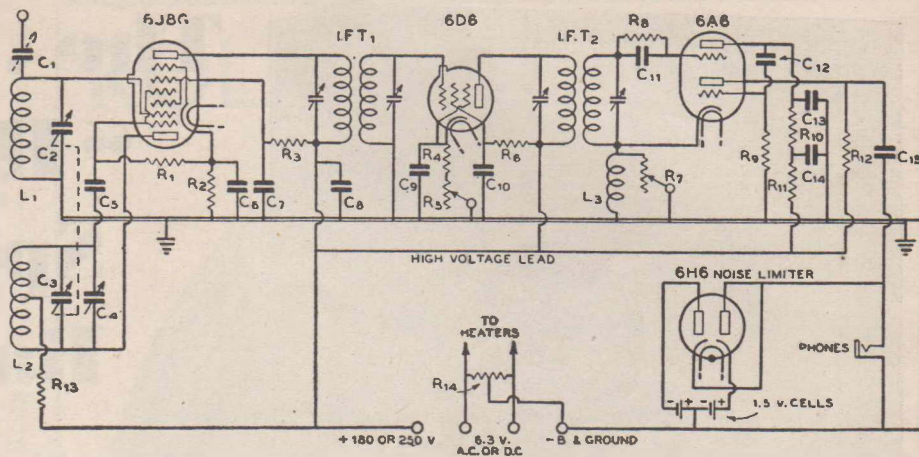

- C₁—3-30- μ fd. coupling condenser
- C₂—8- μ fd. tuning condenser Revamped 15- μ fd. midget
- C₃—15- μ fd. midget tuning
- C₄—50- μ fd. osc. tank condenser
- C₅—0.001- μ fd. mica coupling

- C₆, C₇—0.05- μ fd. mica by-pass
- C₈, C₉—0.1- μ fd. 400-volt tubular
- C₁₀—0.1- μ fd. mica by-pass
- C₁₁—0.001- μ fd. mica coupling
- C₁₂—0.1- μ fd. 400-volt tubular
- C₁₃—0.002- μ fd. 400-volt tubular

- C₁₄—0.5- μ fd. 400-volt tubular
- C₁₅—25- μ fd. 400-volt tubular
- R₁—50,000 ohms, 1/2 watt
- R₂—300 ohms, 1/2 watt
- R₃—100,000 ohms, 1/2 watt
- R₄—300 ohms, 1/2 watt
- R₅—50,000-ohm rheostat
- R₆—100,000 ohms, 1/2 watt
- R₇—1000-ohm rheostat
- R₈—5 megohms, 1/2 watt

- R₉—500,000 ohms, 1/2 watt
- R₁₀—50,000 ohms, 1/2 watt
- R₁₁—20,000 ohms, 1/2 watt
- R₁₂—50,000 ohms, 1/2 watt
- R₁₃—25,000 ohms, 1/2 watt
- R₁₄—50-ohm c.t. resistor
- IFT_{1, 2}—Midget 1600-kc. iron-core i.f. transformer
- L₁, L₂—See text
- L₃—40 turns, 1/2" dia., no. 28 d.s.c. jumble wound

I.F.Ts., and since the first pair was obtained for experimental work on this receiver Tasma has made them available to experimenters at a very reasonable price per pair.

Such I.F.Ts. open up a new field, not only in the construction of ultra-shortwave superhets, but in superhets for general short-wave reception. Main advantage is the freedom from image interference in comparison with 460kc.

Although these 1600kc. I.F.Ts. are lined up accurately in the factory, it must be realised that there will be a difference in the peaking when they are wired into a receiver. This is because of the effect of wiring and valve capacities at the higher frequency. They will, however, be near enough to obtain some kind of a signal from a modulated oscillator, and if any signal is heard at all with the receiver they can easily be lined up. Where there is a somewhat noisy reception background, the I.F. channel can be lined up on the background noise quite easily. First thing to do after completing the receiver to the details given in the October issue of "Radio World" is to get the I.F. channel "on the nose."

BFO and Noise-limiter.

The noise-limiter described by Jones is very effective, but it must be understood that this is not essential to the performance of the receiver. Where there is little or no interference from electrical circuits or car

ignition, the noise-silencer can be omitted. In any case, it is found that this form of limiter definitely cuts down on the audio gain, but this would be immaterial if an extra audio stage is incorporated for speaker reception. Without the limiter, local 56mc. signals are so strong that a permag. speaker can be operated comfortably straight from the output of the 6A6 second detector-audio.

No trouble should be experienced with the regeneration in the second detector portion, provided that the I.F. amplifier is correctly peaked. Regeneration here is very important, as it contributes materially to the overall sensitivity of the receiver.

A 1000-ohm potentiometer is specified across the cathode coil, but this can be any value from 400 to 2500 ohms. Advancing this potentiometer should put the second detector into oscillation for c.w. reception just as smoothly as with any conventional oscillating detector. Unless this control is smooth, the performance of the receiver will suffer. With the detector oscillating for c.w. the advantages of the high-C oscillator are at once apparent. Crystal-controlled stations show a T9 carrier of rock-steady nature fully comparable with lower frequencies.

Figure 1 shows the front of the receiver, and it will be obvious that a tuning dial completely free from backlash or slip must be employed. Indifferent dials can be used with super-regenerators owing to the broad


frequency characteristics, but not with a receiver of this kind. As may be seen in Figure 2, the dial is insulated from the tuning gang by a length of erinoid rod. This is good practice with any short- or ultra-short-wave receiver, as noises from metal dial mechanisms can be eliminated. The 6J8G mixer-oscillator valve is mounted on a Raymart ceramic octal socket on stand-off pillars 1 1/4 in. above the chassis. By this means, wiring can be kept very short and rigid.

It is planned in the near future to build another version of this receiver employing an R.F. stage with an 1851 or 1852 valve, plus extra audio for loudspeaker operation. Such a receiver should represent the last word in modern 56m.c. receiver practice.

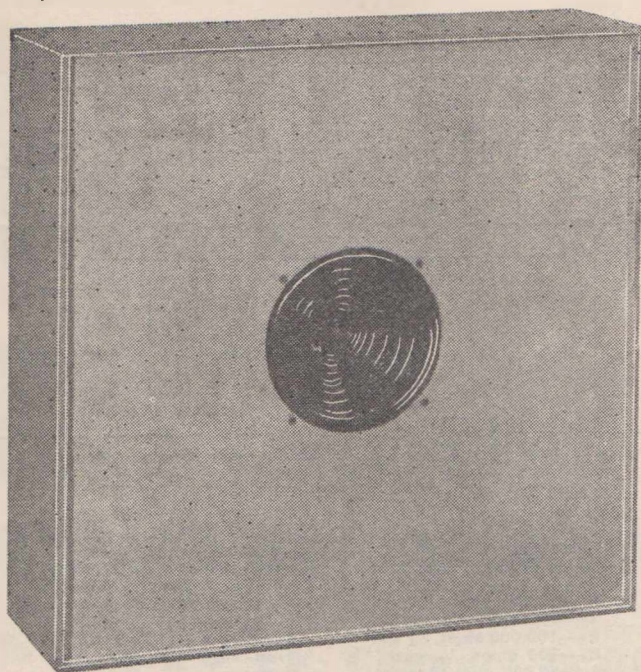D. B. K.

ROUND THE SHACKS

Amateur operators desirous of having their transmitters and activities featured under this heading are requested to forward details to "Reporter," C/- "Radio World," 214 George St., Sydney. Articles should be similar in style to those already appearing in the series, and should, where possible, be accompanied with photographs of operator and transmitter.



The . . . “HI - FI” Speaker Baffle

A special and highly-successful application of the infinite baffle principle, designed and described by . . .

W. McGOWAN (VK2MQ)

TOO few experimenters have experienced the thrill of wide range musical reproduction, principally because there are limitations set up by speaker and baffle. Apart from the acoustical labyrinth and similar type of baffle, very little is available except in the most expensive receiver, and even then, reproduction cannot be classed as true wide range. It is next to impossible to obtain wide range reproduction unless the equipment has been specifically designed for that purpose.

What Wide Range Means.

The use of the term wide range includes more than mere reproduction from radio or record source of the complete band of musical frequencies. It includes as well as a comparatively flat reproduction of the frequencies, so that certain tones are not amplified out of proportion to others, a high safety factor to guard against distortion due to mechanical or electrical overloading, and lastly provision for eliminating the bad effect of both tone and volume level of the “back-door” acoustics of the average loud-speaker when used in the conventional way.

By using a special type of cabinet, uniform and flat response is obtainable, irrespective of where the speaker is located.

A radio transmitter is best design-

ed working backwards from the antenna. This also applies to any audio system, the speaker system being constructed first. A determination of the required output is necessary, and it was decided that for ordinary home use, eight watts is simple.


Rola K-12 Chosen.

The speaker is one of the new Rola K-12 electro-dynamics. It is rated to handle ten watts, so does the job without any overloading, and the frequency response is comparatively flat from 40 to 9000 cycles.


The speaker is used in conjunction with an infinite baffle as illustrated in the photographs.

This is merely an enclosed space, airtight except for a one-inch percussion hole at rear centre. The greater the volume of air space contained in the infinite baffle, the greater the low frequency response. The baffle illustrated cuts off at approximately 45 cycles.

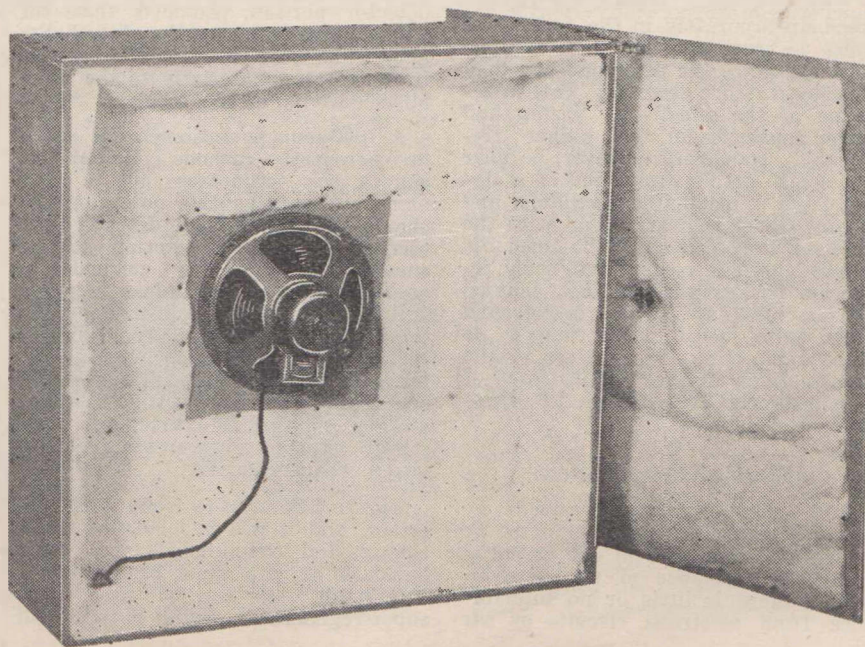The idea of the one-inch percussion hole at the rear, incidentally, is to relieve the cushioning effect that results as the speaker diaphragm moves backwards.



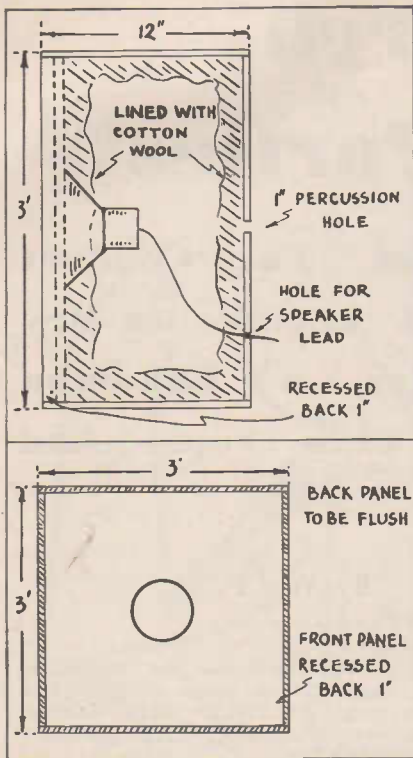The view above shows the appearance of the baffle from the front, while the photo on the right shows an internal view, with back removed. The baffle is assembled using 1in. screws, spaced approximately 4in. apart.



Full dimensions of the baffle are given in these sketches, showing front and side views.

The material utilised in the infinite baffle is a recently-released cane fibre material which is called "Caneite" and is marketed here by the Colonial Sugar Refining Co.

Cotton Wool Padding Absorbs Sound


It has excellent absorbing qualities so far as sound is concerned, and provides a really good response. As the infinite baffle is for all practical purposes airtight, means must be provided to prevent reflection of the sound waves from the inside walls back to the speaker diaphragm.

While the "Caneite" absorbs an appreciable amount, due to its porous, non-resilient nature, some sound does find its way reflected back. To prevent this, the entire cabinet was lined with cotton wool, fastened to the inside walls with drawing pins. Other material available would do just as well, such as hair felt or rock-wool obtainable from any upholsterer.

Results both on radio and records far exceeded expectations, and more than compensated for the time and cost involved in making the baffle. The most striking feature of the quality of reproduction is the realism obtained—piano and organ records being startlingly life-like, while on orchestral selections and dance band music, every instrument appears to stand out in what can be termed "audioscopic" relief.

ROLA . . . First

Choice Of Experts

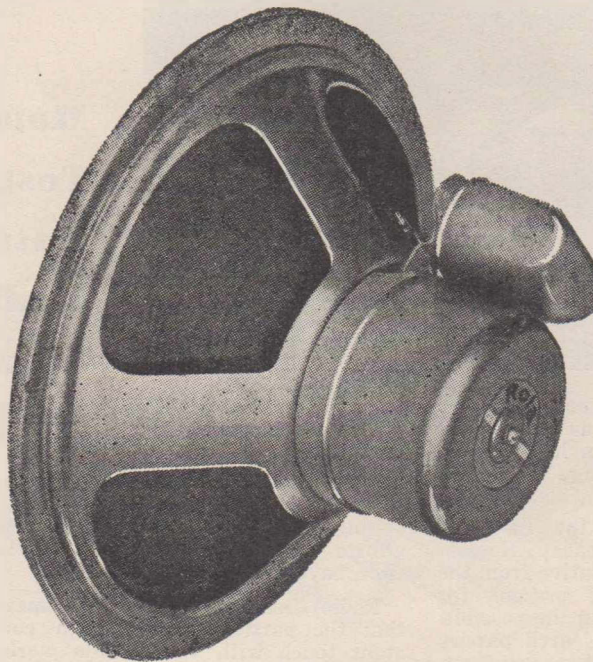

Illustrated alongside is the Rola K12 de luxe reproducer as specified exclusively in this month's issue for the "Hi-Fi" speaker baffle and the "1939 Sky King Dual-Wave Five."

RAUDIO engineers the world over always insist on ROLA for quality receivers. They know that the speaker is the vital link between station and listener, and hence that the speaker chosen can make or mar the performance of the finest chassis ever designed. The Rola Model K12, illustrated above, is specified exclusively this month for the "Radio World" "Hi-Fi" Speaker Baffle. It was also chosen for the "1939 Sky King Dual-Wave Five" . . . sure proof of the superiority of Rola. You too can ensure faultless reproduction by following the designer's lead and insisting on ROLA.

THREE NEW PERMAGS. BY ROLA

Rola now announces the release of three new permanent magnet models of revolutionary design—the 8-42, 10-42 and 12-42. These new speakers embody many latest developments, including 42-ounce alnico magnet, 1-inch voice coil, special graded moisture-resisting diaphragm, patented dust-proofing, Isocore transformer, and, most important of all, EXCEPTIONALLY HIGH SENSITIVITY, COUPLED WITH GREATLY IMPROVED OVERALL RESPONSE.


Rola reproducers are standard with the world's radio and amplifying systems . . . proof positive of Rola Quality !

DISTRIBUTORS AND FACTORY SERVICE FOR N.S.W.

Geo. BROWN AND CO. PTY. LTD.

268 Clarence Street, Sydney . . . (Phone M 3437)
Sole Australian Agents for ULTIMATE RADIO

Radio For Bush Search

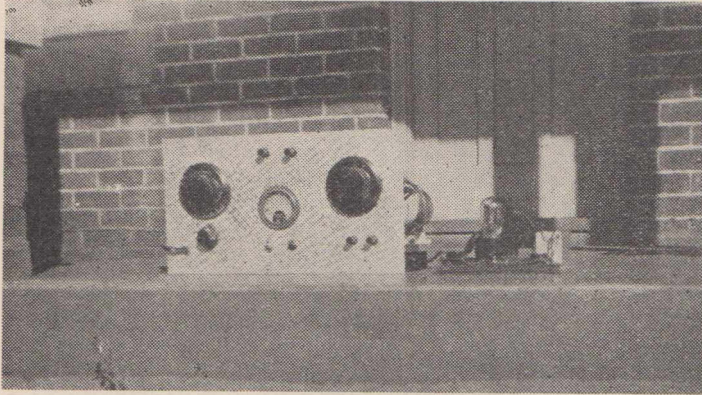

The rig at VK2YA, consisting of a 2A5 crystal-oscillator with either one or two 46's as p.a. Originally riddled with holes, the aluminium panel shown has been rejuvenated according to the process described on page 16 by owner-operator R. C. Black.

Parties

Members To Conduct Tests ★ Lecture On Dry Batteries ★ Lakemba Radio Club Notes And News.

By W.J.P.

AT the meeting of the Lakemba Radio Club on Tuesday, November 22, a representative from the Bushwalkers' Club was present for the purpose of discussing the possibility of equipping bush search parties with radio receivers and transmitters. In the course of his address, Mr. W. G. Morris stated that during past years the Bushwalkers' Clubs have rendered valuable assistance to the police and community by sending out parties of their own members to search for persons who have become lost in treacherous and mountainous country.

These organisations are entirely voluntary, and the members are expert bushmen who have an excellent knowledge of the country in general. Parties from their ranks may be summoned within 24 hours, the members being prepared to stay away a week or more if necessary, at no small cost to themselves.

The main difficulty in the past has been the matter of communication between the parties and civilisation. Smoke signals, fires and homing pigeons have been tried, and although pigeons have provided a link from the search parties to headquarters, there has still been no satisfactory means of getting return messages to the searchers.

It will be obvious what a saving of time and expense would result from direct two-way communication. At the present time many parties continue their search for a week or so before returning. It very often happens that the missing persons are located perhaps a day after the commencement of the search. The other inland searchers being unaware of this, often go through unnecessary hardships, privations and useless tra-

velling, only to return and find their efforts for the greater part of the time have been wasted.

Radio communication would mean that the parties could keep in constant touch with the outside world, and at the same time receive instructions from headquarters. Immediately the lost persons were located an order would be issued for all parties to return, thus effecting a considerable saving in time, energy and expense.

Test Suggested By President.

Having outlined all details, Mr. Morris was given an assurance by the Lakemba Club that apparatus of this nature was a practical possibility, as in the past satisfactory communication had been obtained by members from extremely difficult mountain locations. The Club President, Mr. E. P. Hodgkins, then suggested that a test be conducted early in February under actual working conditions, before any permanent apparatus is installed.

The arrangements will be as follows: A fairly rough stretch of country will be selected where a party will become "lost"; three search parties will go out each equipped with small receivers and transmitters or transceivers; a semi-portable unit using as high power as possible will be driven as near as possible to the area being searched; and this unit will endeavour to maintain communication with the search parties and also with another station in a populated area connected with the telephone, thus completing the link between headquarters and the inland parties.

Obviously, the apparatus will be as simple, compact and light as possible.

Those who have had the experience of carrying their packs over some of the rough country for which Australia is renowned will readily appreciate this necessity.

Past tests have revealed that wavelengths from 40 to 5 metres are useless for this type of work, due to skip effects and absorption. For reliability over short distances, 80 and 160 metres appear to be the most satisfactory, these wavelengths permitting a signal to travel a few miles from the depths of some mountain gully. The maximum distance of transmission and reception under normal conditions probably will not exceed 10 miles, and if necessary the mobile unit could change its location as the search progresses.


However, the test early in February should prove most interesting, and no doubt many difficulties will be encountered, as conditions will be entirely different from those existing on ordinary field day or portable work.

★

Lecture On Dry Batteries

In keeping with its policy of presenting a series of interesting lectures, a talk will be delivered by Mr. A. Luciano, chief chemist of the Ever Ready Battery Co., at the clubrooms early in the new year. Lectures of interest during the past month have included the talk by Mr. Morris (detailed above) and a lecture on crystal oscillators, by Mr. J. Read, VK2JR.

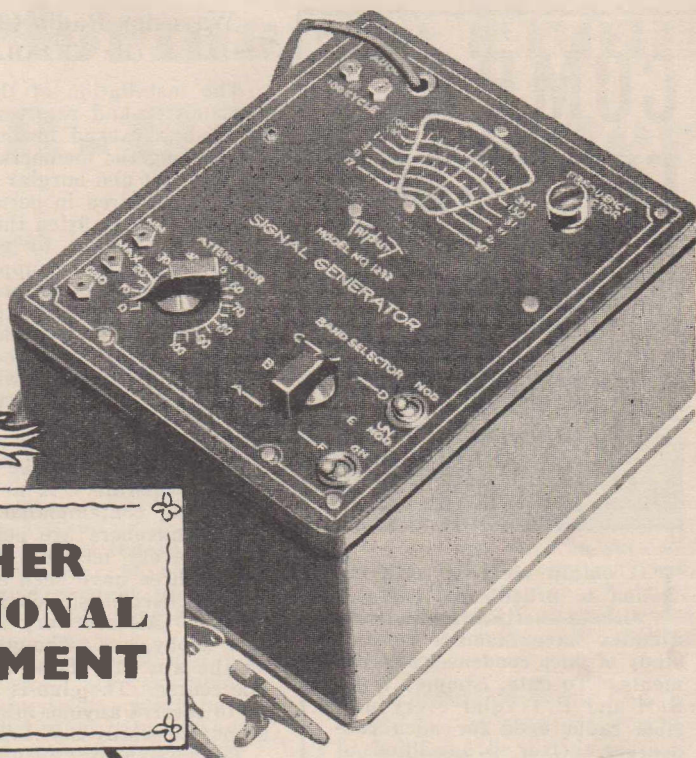The club would welcome offers to deliver talks or demonstrations of general interest, and those interested are invited to communicate with the Secretary, 14 Park Avenue, Burwood, or Publicity Manager, 14 Watkin Street, Canterbury.



**ANOTHER
SENSATIONAL
DEVELOPMENT**

TRIPLETT SIGNAL GENERATORS With Built-in Trimmer Calibrated Coils

★ 120-30,000 k.c. ★ Direct reading on Six Bands, all fundamentals ★ Completely shielded ★ Guaranteed accurate to 1% for broadcast, intermediate and short-wave bands.

MODEL 1231 All-Wave Direct Reading D.C. Signal Generator now has built-in trimmer calibrated coils for accuracy of 1% on broadcast, intermediate and short-wave bands. Six bands cover 120-30,000 k.c.—all fundamentals. Fully stabilised. Extra-long 12" vernier type direct reading scale. Improved band selector switch. 400 cycle audio signal available. Includes batteries and two type '30 tubes. Price £10/10/-
1232 unit (same as 1231, but for A.C. operation. Price . . £10/15/-

MODEL 1230.


MODEL 1230 Unit is an All-Wave Signal Generator supplying a continuously variable signal. Frequencies controlled on six fixed positions, from 100-18,000 k.c. batteries, tubes and six individually calibrated graphs supplied. Price £6/10/-

VOLT-OHM MILLIAMMETER

MODEL 1200-A.

Has two instruments (A.C. and D.C.) in moulded case. Can be tilted to any reading angle. Scale readings: D.C., 10-50-250-500-1000 volts at 2000 ohms per volt; 1-10-50-250 M.A.; low ohms, .5-500; 1500 ohms, 1.5 and 3 megohms. A.C., 10-50-250, 500-1000 volts. Resistance measurements have individual zero adjustments. Selector switch for all readings includes 22½ volts and 1½ volt batteries.


Price, £9/-/-

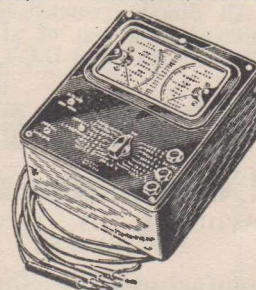

W. G. WATSON & CO. PTY. LTD.

Head Office: 279 Clarence Street, Sydney. Newcastle branch: King and Bolton Streets, Newcastle. Branches at Melbourne, Adelaide, Hobart, Launceston and Perth.

COMPACT EFFICIENCY

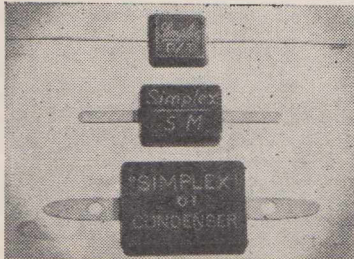

TO obtain ideal performance and to provide compactness without sacrificing efficiency, Simplex have made a detailed study of mica condenser requirements. To date, Simplex types S/M and P/T fulfil every possible radio need for mica condensers. Over two million of them are now in use, proof positive that they are superior in design and in actual operation. Notable features include:—

- High resistance to moisture.
- 1000 volt A.C. & D.C. test.
- Triple-strength contacts
- High accuracy of calibration.

Type S/M, available in capacities from .000005 microfarads to .01 microfarads.

Type P/T (Pigtails) measuring only $\frac{5}{8}$ " x $\frac{5}{8}$ "—capacity range .000005 microfarads to .001 microfarads.

(All Simplex condensers are subjected to a test of at least 1000 volts A.C. and D.C.)

SIMPLEX Condensers

"FAVORED BY FAMOUS
FACTORIES"

Manufactured by Simplex
Products Pty. Ltd., 716
Parramatta Road,
Petersham, N.S.W.

'Phone LM 5615.

AGENTS IN ALL STATES.

Waverley Radio Club Notes

(By VK2AHJ.)

The installation of the new club transmitter and receiver in the club-room has caused much interest of late among the members. The remote control unit and burglar alarm system have been wired in permanently, and the rig itself is fitted throughout with protective devices to guard against overload of power supplies and also against grid bias failure.

The rig is mounted to one side of the operating table and is enclosed in a beautifully-polished maple cabinet. Control of the switching of the power supplies is effected by a key switch on the table. There remain still a few details to be completed. The new station will be a pleasure to see and operate. A new antenna is also being contemplated.

New members are being welcomed almost every meeting, and quite recently three have been elected, namely, Dick Griffiths, Bob Ball and Geo. Preece. All are very keen on their new hobby, and although are not yet on the air, they hope to be there in due course. The club is always pleased to receive anyone interested in the game, especially S.W.L.'s and "hams."

The absence of 2FJ and 2ABS from the air lately is explained by the fact that the former has been rebuilding and the latter holidaying at Orange. Jack reports having a good holiday and a very interesting visit to 2CR, Orange.

2MQ has also been rebuilding, but Bill's attention is centred on five metres, and he is never heard on the lower frequencies.

2TN is making firm friends around the neighbourhood by tying antennas to the neighbours' chimneys!

The half-yearly election of officers took place on November 15, and most of the office-bearers were returned to their positions. The offices of President, Secretary and Treasurer were again filled by Gordon Wells, Jack Howes and Eric Johnson, with Ivan Bailise (2TN) as W.I.A. representative and the writer as publicity officer. Bill Stanley has accepted the task of getting and keeping the club's books in shipshape order, and has made a good start at doing so.

Code practice is to be held at 7.30 p.m. every Tuesday evening, and it is hoped that this will encourage anyone interested in getting started in their code to come along and do so "en masse." The clubroom is situated at the rear of "Almont," 13 Macpherson Street, Waverley, and meetings are held every Tuesday night.

★

The Hurstville Amateur Radio Club.

By VK2MZ.

During November two members of the club received notification from the R.I. that they had passed the

A.O.C.P. exam. held in October. They are J. Ackerman and V. Nugent. Well done, Joe and Vince! Both have made application for call signs and hope to be on the air very shortly.

The club transmitter (2MZ) has been rebuilt and is now on 40 m., the line up is 46 C.O., 46 doubler, 46 buffer, 210 in the final, and is working very well. 2MZ is on the air regularly every Thursday night.

A visit was paid to the club by Mr. F. Carruthers (2PF) on behalf of the W.I.A., and he told very interestingly the story of the Cairo Convention of how the amateurs were represented there, and how the results affected the amateur bands. He also urged all amateurs to support the W.I.A. and thereby help to keep the amateur bands as they are at present.

Lectures and Morse code classes are given every Thursday night, and visitors and intending members are always welcome. The clubrooms are situated above 316 Forest Road, Hurstville; entrance is at rear. Any information can be had from the secretary, J. Ackerman, 34 Park Road, Carlton, or G. Calvert, 4 Jolleys Arcade, Hurstville.

New Panels For Old

Most experimenters and "hams" acquire a considerable number of discarded aluminium panels during the years, and frequently a piece of sheet aluminium of the dimensions desired for a new piece of gear is discarded because of the large number of holes resulting from previous experiments.

Even the most "sieve-like" piece can be restored to service by filling the holes with "Tarzan's Grip"—the silvery type, not the colourless, of course. Gum a piece of paper at the rear of each hole, and apply the "Grip" from the front of the panel, until the hole is completely filled and an outward bulge is left.

After all holes have been treated like this, allow to dry, and then sandpaper to level.

At this stage the repairs will be most painfully obvious, but the mottled effect as seen in the photo of my own rig will effectively conceal this. This effect is secured by placing a small piece of medium sandpaper on the thumb and rotating on one spot of the panel until circular scratches appear. Admittedly, it takes considerable time, but to unfinancial persons like myself the expenditure of some time and energy is preferable to the outlay of five or six shillings.

For the benefit of those who may be interested, the rig is a two-stage job, with 2A5 crystal oscillator and either one or two 46's as P.A.

No, that's not the family rat-trap next to the rig, it's the power supply!

—R. C. Black (VK2YA), Trangie, N.S.W.

Improved Performance From 6K8-G Converter

Increased Gain --- Excellent Stability

THE advent of Radiotron 6K8-G has made possible the construction of receivers of quite a simple character which nevertheless have extremely good performance, particularly on short waves (states "Radiotronics" No. 92, published by A. W. Valve Co. Pty. Ltd.). The special characteristics of the 6K8-G which have the greatest appeal are the stability of the oscillator frequency on all bands, and the sensitivity and general satisfactory performance on the highest frequencies of the short wave band.

As a result of these good characteristics, it is possible to apply a.v.c. to the 6K8-G without suffering from frequency drift due to fading and without any likelihood of flutter, provided that reasonable precautions are taken.

Valves of the pentagrid type such as the 6A7 or 6A8-G have high sensitivity and good performance on the broadcast band, but when a.v.c. is applied to the converter on the short-wave band it is usually necessary to employ a fairly expensive filter in the anode-grid circuit in order to prevent flutter and, while this is reasonably effective as an anti-flutter device, it does not assist in any way towards preventing the receiver from coming off-tune when the signal fades severely.

This effect on the short-wave band

is well known to all who have handled such receivers, and in the past, good performance could only be achieved by removing a.v.c. from the converter for short waves. For satisfactory receiver performance this would necessitate the use of an r.f. stage, not only as an amplifying stage, but also for the a.v.c. control. The stability of the 6K8-G makes the r.f. stage no longer essential in this regard, since ample a.v.c. action may be obtained on the short-wave band by applying the controlling voltage to the grid of the converter.

Receivers of the five-valve variety, having no r.f. stage, are very popular in spite of the defects which have been enumerated, but the 6K8-G avoids the most serious of these defects, and therefore makes a considerable contribution to the performance of a typical small receiver.

At the same time it must be realised that the addition of an r.f. stage to any receiver improves its performance very markedly in many directions such as the reduction of back-


ground noise for a given sensitivity, improved a.v.c. characteristic, improved image ratio, and lessened liability to suffer from cross modulation. The receiver which is described in this issue is therefore shown with an r.f. stage using Radiotron type 6U7-G as the r.f. amplifier.

This r.f. stage may, however, be omitted entirely and the remainder of the receiver will have an excellent performance when compared with other receivers having no r.f. stage. No additional circuit diagram has been shown, since the parts to be omitted are so obvious.

Tuning Indicator.

A Magic Eye tuning indicator has been included in the circuit for ease of tuning and may be either type 6U5 or 6G5 as may be desired. Radiotron 6U5 is fitted with a space-charge grid in the target section which provides better uniformity of performance and longer life due to the elimination of excessively high target currents.

The newer types of Radiotron 6G5

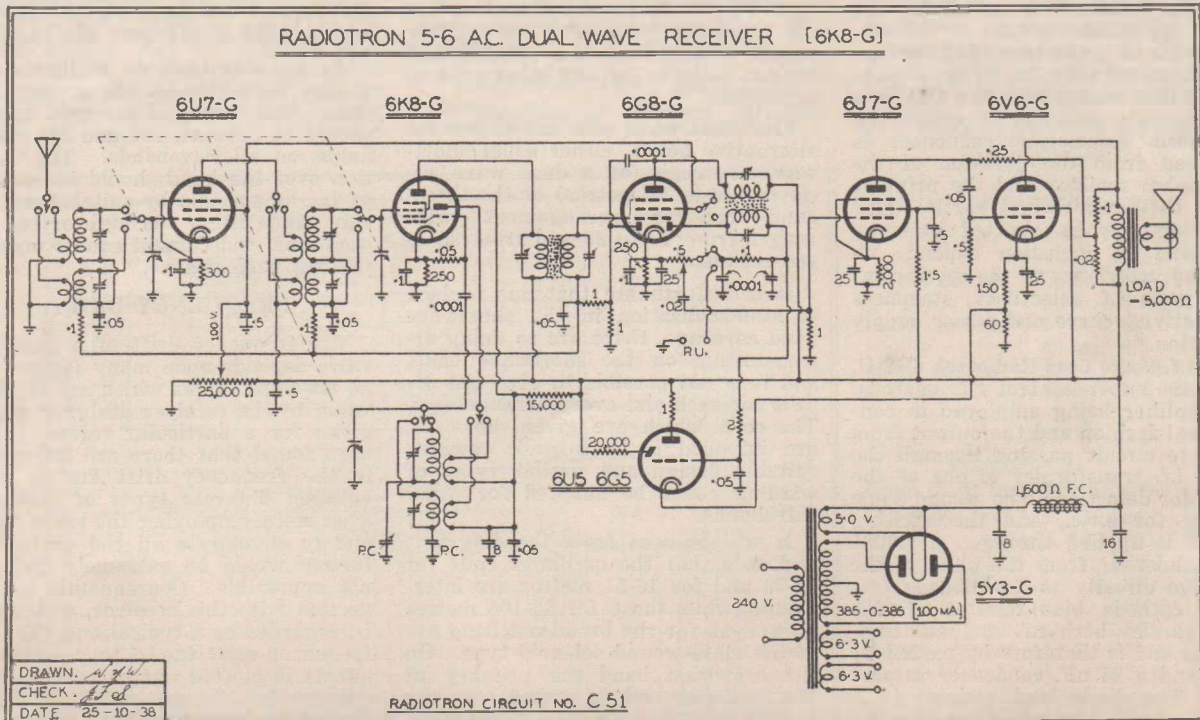

The six-valve circuit developed by A. W. Valve Co. Pty. Ltd., and discussed in the accompanying article.

are also fitted with a space charge grid, but the earlier construction 6G5's will not have such a satisfactory performance. A resistor of 20,000 ohms has been shown in the target circuit of the tuning indicator and this is intended only for use with the more modern type of tuning indicator employing a space charge grid.

With the older type of tuning indicator it is advisable to decrease this resistance to 10,000 ohms, and to decrease the target supply voltage to about 200 or 220 volts.

Circuit Arrangement.

Radiotron 6U7-G is used as the r.f. amplifier and its screen supply is obtained from a 25,000 ohm voltage divider having a tapping at 100 volts, which is used to supply the screens of the r.f. and i.f. stages.

Radiotron 6K8-G converter is operated with normal voltages on all electrodes. As recommended in the published data on this valve type, the screen grid of the mixer and the plate of the oscillator are supplied through a common 15,000 ohm dropping resistor from "B+."

The reason for this particular arrangement is that there is a slight frequency drift in one direction with a change of voltage applied to the oscillator plate, and in the reverse direction with the same change of voltage applied to the mixer screen. Consequently by combining these two in a common dropping resistor the tendency to drift is very much reduced and, since the drift in each section is of approximately the same dimensions, the net drift very closely approaches zero.

In order to make sure that no flutter occurs even with the slight amount of drift that occurs with the 6K8-G, a comparatively small filter employing an 8 mfd. electrolytic condenser is connected from the junction of the 15,000 ohm resistor and the primary of the oscillator coil to earth. This condenser may be omitted in many cases and its inclusion depends on such characteristics of the receiver as audio gain, i.f. selectivity, steepness of selectivity curve and power supply regulation.

The i.f. stage uses Radiotron 6G8-G, duo-diode super control r.f. pentode, the amplifier being employed in conventional fashion and the output from the plate circuit passing through the second i.f. transformer to one of the diodes for detection. The second diode is used for a.v.c., and the exciting voltage is applied through a .0001 mfd. condenser from the plate of the i.f. valve directly to the diode.

The cathode bias resistor of this stage carries both r.f. and a.f. components and is therefore by-passed by a 0.1 and a 25 uF. condenser in parallel. The diode load resistor is .5 megohm, and the r.f. filter consists of a .1 megohm resistor and .0001 mfd. filter as with preceding Radio-

tron circuits.

Due to the special a.v.c. arrangement which has been adopted, the increase of distortion due to the operation of a.v.c. is quite small, and occurs only at a very low input voltage to the aerial. There is no shunting of the diode load by the a.v.c. network, although there is a slight loading due to the 2-megohm resistor to the grid of the tuning indicator.

The audio system comprises Radiotron 6J7-G as a resistance coupled pentode feeding into the grid of a 6V6-G beam tetrode, with negative feedback applied by the series method. Although the percentage of output voltage which is applied to the plate circuit of the 6J7-G is 16.6

per cent., the effective percentage at the grid of the 6V6-G is 10.7 per cent., giving a gain reduction factor of 2.93.

The cathode of the 6U5 is returned to a tapping on the 6V6-G cathode bias resistor in order that the deflection of the tuning indicator may occur even with small signals and on short waves. The same effect could be obtained quite readily by returning the cathode to a suitable point on a separate voltage divider.

The power supply comprises a standard 385-385 volt 100 m.a. transformer and Radiotron 5Y3-G rectifier. The filter system incorporates a 1600-ohm field coil and condensers of 8 and 16 mfd. capacitance.

B. C. AND S. W. COIL DATA

THE coils which were used in this receiver are of conventional pattern, and are regarded merely as examples of average design. It is not claimed that the highest possible efficiency has been obtained, especially since this might result in difficulties in other directions.

In order to assist designers in obtaining a satisfactory conventional type of coil for use with the Radiotron 6K8-G, the data on the coils is tabulated in full and two diagrams are shown, illustrating the aerial and r.f. coils on one and the oscillator coils on the other diagram. The aerial and r.f. coils may be used with any type of converter or r.f. valve, but the oscillator coils are particularly suited to the Radiotron 6K8-G and are not suitable for any other type of converter.

The short wave coils are shown for alternative bands, either usual short-wave coverage for a dual wave receiver (16 to 51 metres) or the three-band receiver arrangement with ranges from 13 to 39 and from 35 to 105 metres.

It is unfortunate that due to lack of standardisation in the shortwave band coverage, there are so many arrangements on the shortwave band, and it is not possible to give coil details for each and every arrangement. The coils which are given, however, are intended to be a guide towards suitable design and similar types of winding could be adopted for other wavebands.

It will be seen from the diagrams and data that the oscillator coils for 13-39 and for 16-51 metres are interwound, while those for 35-105 metres as well as for the broadcast band are of the close-wound solenoid type. On the broadcast band the primary of the oscillator coil is wound over the bottom end of the secondary winding. The aerial and r.f. coils on the broadcast band employ high impedance pri-



maries and sectional Litz-wound secondaries. The aerial coil for the 35-105-metre band is also of the high impedance type, although the secondary is a single layer close-wound solenoid. In all cases where high impedance primaries are employed a capacitance turn is added to improve the gain at the high frequency end of the band.

In the design of the coils for the receiver it is necessary to consider the effects of variation of gain over the wave band, the coil gain, and the necessity for matching the high impedance primary to an aerial; also for the oscillator coil the production of the desired oscillator grid current within fixed limits over the band.

As a guide towards oscillator coil design with the 6K8-G, it may be stated that the oscillator grid current should be between 100 and 200 microamps. on all wavebands. The variation over the band should be reduced as far as possible by suitable coil design, since either too high or too low oscillator grid current causes unsatisfactory performance.

FREQUENCY DRIFT.

The frequency drift of a converter valve depends upon many factors and no absolute curves which are of much value to the receiver designer can be given for a particular valve. It has been found that there are differences in the frequency drift due to a.v.c. between different types of receivers, even when employing the same valve, and to enumerate all the controlling factors would be extremely tiring if not impossible. Consequently in connection with this receiver, which may be regarded as a typical one, the total frequency drift due to a.v.c. and other effects is plotted against aerial input voltage for the receiver as a whole. On the diagram are shown two curves giving the upper and lower limits of individual 6K8-G valves and any

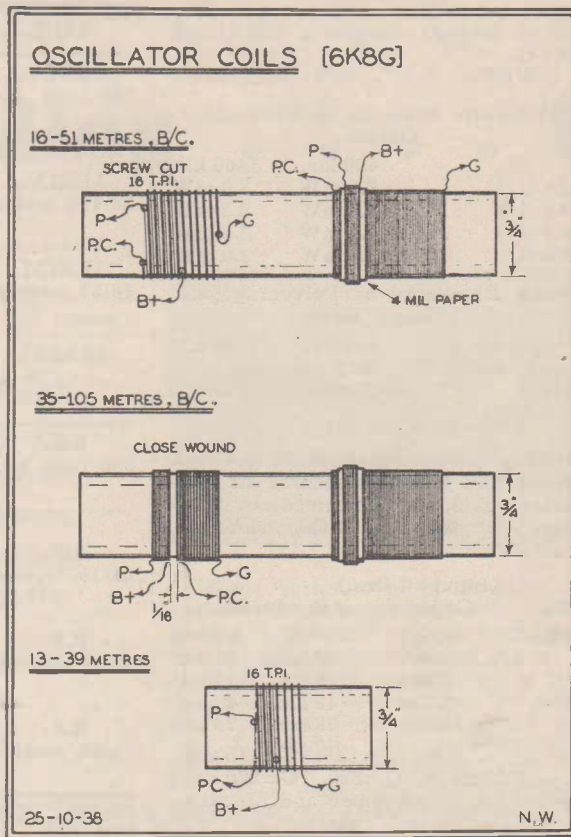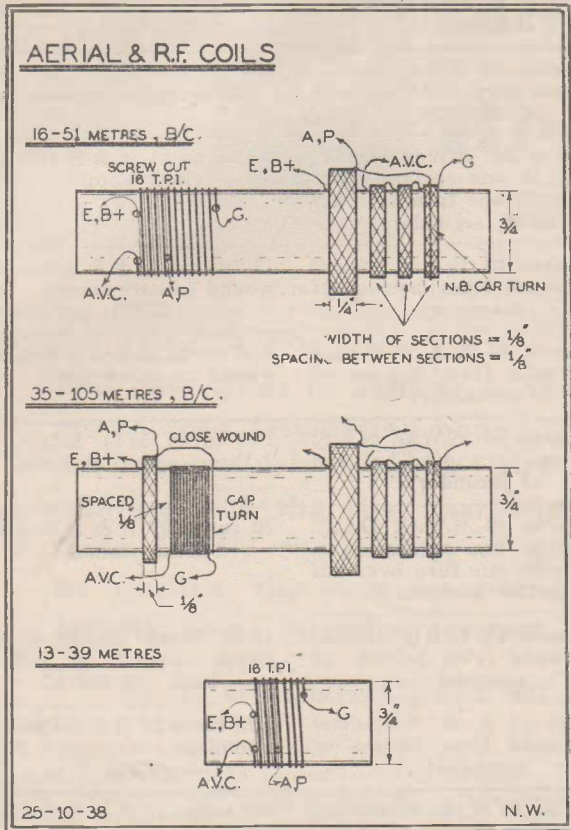

Radiotron 6K8-G should be within these limits. It will be seen that the upper limit is +2.5 k.c. and the lower limit -1.8 k.c. For the purposes of comparison the curve for an average 6A8-G is shown and the improvement

due to the use of the 6K8-G is evident. These curves were taken at a frequency of 18.6 megacycles.

RECEIVER TEST RESULTS.

Comparison of receiver measure-

ments at the Aerial Terminal, using Radiotron receiver No. C51 with representative samples of 6K8-G and 6A8-G, both working under optimum voltage and oscillator conditions.

ABSOLUTE SENSITIVITY. FREQUENCY OR


BAND.	W'LENGTH	6K8-G	6A8-G
550-1500 k.c.	1400 k.c.	1.5 uV	1.0 uV
	600 k.c.	1.3 uV	1.1 uV
35-105 metres	37.5 m.	6.0 uV	3.0 uV
	90 m.	6.5 uV	4.5 uV
16-51 metres	17 m.	6.3 uV	9.0 uV
	45 m.	8.5 uV	6.0 uV
13-39 metres	14 m.	3.5 uV	22 uV
	35 m.	6.4 uV	7.5 uV

IMAGE RATIO.

Band.	W'length.	6K8-G.	6A8-G
550-1500 k.c.	1400 k.c.	10,000:1	10,000:1
	600 k.c.	100,000:1	80,000:1
35-105 metres	37.5 m.	260:1	190:1
	90 m.	1,560:1	1,200:1
16-51 metres	17 m.	100:1	80:1
	45 m.	330:1	240:1
13-39 metres	14 m.	22:1	12:1
	35 m.	330:1	260:1

NOISE LEVEL.

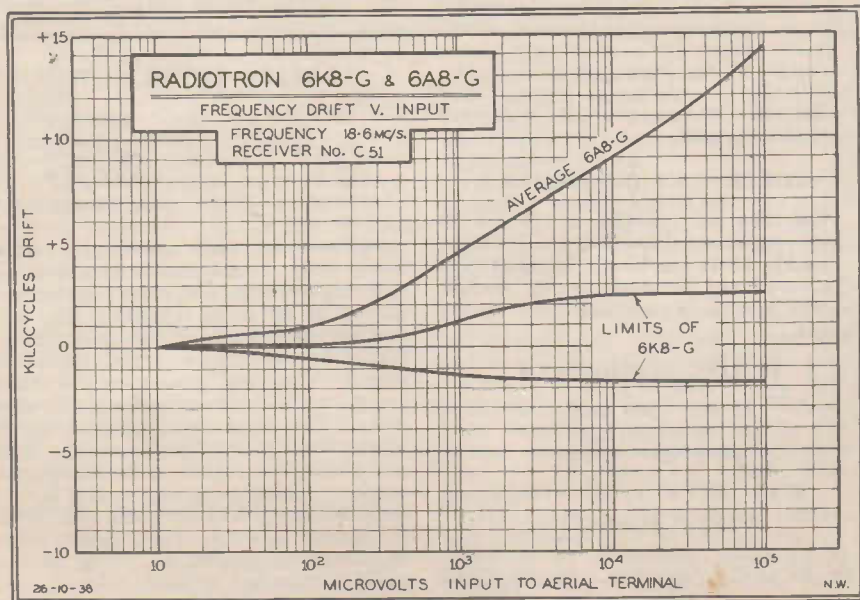Measurements made in Radiotron receiver No. C51 with signal fed to



aerial terminal at 600 k.c. and 1400 k.c. on average samples of 6K8-G and 6A8-G.

INPUT = 5 uV., 30% Modulation.

Milliwatts Noise in 50 Milliwatts Output.

	600 k.c.	1400 k.c.
6A8-G/1	3.5 mW	3.0 mW
6A8-G/2	3.8 mW	3.2 mW
6K8-G/1	3.8 mW	3.5 mW
6K8-G/2	4.5 mW	4.0 mW

Noise Expressed as Percentage on Voltage Basis.

	600 k.c.	1400 k.c.
6A8-G	27.2%	24.8%
6K8-G	28.6%	27.3%

BANDWIDTH.

Comparison of Bandwidth between 6K8-G and 6A8-G measured at converter grid, at Intermediate Frequency = 465 k.c., with various i.f. transformers.

(Input off Res.)

I.F.	(Input at Res.)	Bandwidth.	
Transf.		6K8-G	6A8-G
A	1,000	47 k.c.	65 k.c.
	10,000	120 k.c.	117 k.c.
B	1,000	42 k.c.	43 k.c.
	10,000	69 k.c.	76 k.c.

A.—Zd=0.25 m., Q=125. C=115 uuF.
 B.—Zd=0.25 m., Q=220. C=200 uuF.
 Second i.f. transformer and i.f. stage identical in each case.

OSCILLATOR GRID CURRENT.

Oscillator Grid Current of average sample 6K8-G having Oscillator Gm = 3000 umhos. over the four bands and using coils as specified.

BAND.	Point	Osc. Grid Current.
550-1500 k.c.	550 k.c.	130 uA
	1000 k.c.	150 uA
	1500 k.c.	150 uA
35-105 metres	35 metres	*250 uA
	50 metres	*210 uA
	90 metres	130 uA
	105 metres	110 uA
16-51 metres	16 metres	180 uA
	30 metres	180 uA
	51 metres	110uA
13-39 metres	13 metres	180 uA
	20 metres	190 uA
	39 metres	110 uA

* Although these values are above those normally recommended, no appreciable loss of sensitivity or other defect was found in this particular case.

Frequency Drift.

The frequency drift of a converter valve depends upon many factors and no absolute curves which are of much value to the receiver designer can be given for a particular valve. It has been found that there are differences in the frequency drift due to A.V.C. between different types of receivers, even when employing the same valve.

(Continued on page 46.)

COIL.	PRIMARY.	SECONDARY.
AERIAL. 550-1500 k.c.	375 turns 40 S.W.G. S.S.E. with one turn over hot end of secondary.	120 turns 5/44 Litz in three equal sections.
AERIAL. 35-105 metres.	55 turns 40 S.W.G. D.C.C. wound in one section 1/8 in. wide, with one turn over hot end of secondary.	20 turns 27 B & S Enam. close wound.
AERIAL. 16-51 metres.	4.25 turns 34 B & S enamel interwound from bottom of secondary.	11.7 turns 22 B & S Enam. wound in screw cuts. 16 T.P.I.
AERIAL. 13-39 metres.	3.2 turns 34 B & S enamel interwound from bottom of secondary.	7.75 turns 22 B & S Enam. wound in screw cuts. 16 T.P.I.
R.F. 550-1500 k.c.	950 turns 40 S.W.G. S.E.E. with one turn over hot end of secondary.	120 turns 5/44 Litz. in three equal sections.
R.F. 35-105 metres.	110 turns 40 S.W.G. D.C.C. wound in one section 1/8 in. wide, with one turn over hot end of secondary.	20 turns 27 B & S Enam. close wound.
R.F. 16-51 metres.	8.75 turns 34 B & S enamel interwound from bottom of secondary.	11.45 turns 22 B & S Enam. wound in screw cuts. 16 T.P.I.
R.F. 13-39 metres.	6 turns 34 B & S enamel interwound from bottom of secondary.	7.75 turns 22 B & S Enam. wound in screw cuts. 16 T.P.I.
OSCILLATOR. 550-1500 k.c.	10 turns 34 B & S enamel wound over bottom of secondary.	100 turns 31 B & S Enam.
OSCILLATOR. 35-105 metres.	8.5 turns 34 B & S enamel wound 1/8 in. from cold end of secondary.	18.25 turns 27 B & S enam. Close wound.
OSCILLATOR. 16-51 metres.	4.5 turns 34 B & S enamel interwound from bottom of secondary.	10.9 turns 22 B & S enam. wound in screw cuts. 16 T.P.I.
OSCILLATOR. 13-39 metres.	3.25 turns 34 B & S enamel interwound from bottom of secondary.	7.5 turns 22 B & S enam. wound in screw cuts. 16 T.P.I.

COIL FORMERS.

All coils wound on 3/4 in. diameter bakelite former.

SHIELD CAN DIMENSIONS.

550-1500 k.c., 35-105 m.: SHIELD CAN—Internal diameter 2 1/2 inches.
 16-51, 13-39 metres: NO SHIELD CAN—Placed between gang switch shield plates, which are 2% inches apart.

TUNING CONDENSER.

A: 10 — 390 uuF
 or B: 9 — 398 uuF
 (See note below)

MAX. EFFECTIVE STRAY CAPACITANCES.

A: 34 uuF. Including valve input,
 B: 35 uuF. trimmer, wiring, and coil capacitances.

PADDING CONDENSERS.

550-1500 k.c. . . . 410 uuF
 35-105 m. . . . 2000 uuF
 16-51 m. . . . 4000 uuF
 13-39 m. . . . 4500 uuF

N.B.—Note that these coil data apply only to particular conditions, and adjustment will normally be required in differing layouts. The effective inductance of the coils is affected by the length of the leads, the shield cans, and proximity to other components in the case of unshielded coils. The band coverage is affected by the total stray capacitances as well as by the capacitance of the gang condenser. Using gang condenser B, the band-coverage will be wider than with condenser A. Any minor adjustment in the coils should be made in the same proportion to both primary and secondary.



Home Recording . . . I

Above: One of the early Edison phonographs, which played a cylindrical recording. Right: Some of the experimental equipment used by the authors in making home recordings.

This new series of articles is devoted to home recording—a fascinating hobby that is rapidly becoming widely popular with radio experimenters. In the first instalment the authors trace briefly the history of sound recording an outline the main requirements of a satisfactory home recording system.

By T. O'DONNELL and W. J. PHELPS.

IN December of the year 1877, Thomas Edison obtained patent rights for the first direct sound recording machine, known as the phonograph. This machine used a revolving cylinder covered with thick tinfoil. It was moved sideways past a fixed cutting head, this head in turn being utilised to reproduce the recorded sounds.

Shortly afterwards, the phonograph was placed on the market as a reproducing instrument using wax cylindrical records. (A photograph of such a machine is shown on this page.) As will be evident, this type of phonograph with its associated records had many disadvantages, and some years later was superseded by the flat disc type of machine, later known as the gramophone.

It must be remembered that purely mechanical methods of recording and reproducing were employed during these early stages; that is, the sounds were concentrated by means of a large horn upon a diaphragm, which in turn directly activated the cutting needle. When placed on the phonograph or gramophone, the sounds were then reproduced from the records by reversing the process.

These methods of necessity restricted the frequency quite considerably, and in spite of gradual improvements over a number of years, no great advance was made in this regard until the advent of electrical amplification.

Methods of Present Day Recording.

The three main methods of recording in present day commercial practice are (i) the disc method, (ii) the

steel tape method, and (iii) the film method.

The sound-on-film system requires very costly recording and reproducing equipment, although its frequency range is extremely good. The steel tape system, which, incidentally, is a fairly old one, has a much more restricted frequency range, and also requires special equipment. In both cases the initial cost would prohibit their use as a home recorder.

The Disc Method.


The disc method is available in several different forms. In the manufacture of commercial gramophone records, the sound is cut upon a soft, warm wax disc, after which the impression on the wax disc is transferred through a number of involved processes to a negative metal disc, which in turn presses the plastic into the finished article.

Of much greater interest to home recording enthusiasts, however, are the instantaneous play-back recordings cut on aluminium or soft acetate discs.

Types of Discs.

Probably the cheapest recording blank is the plain aluminium disc, which is generally used in the soft, polished state. This type of disc has been found to be restricted in frequency range, but is satisfactory when used for recording at speech frequencies.

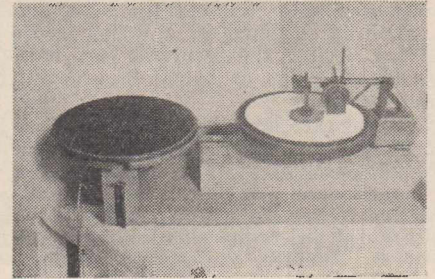Instead of using a sharp cutting point ploughing a furrow in the material of the disc, it has been observed that a more rounded cutting point



produces better results, because it pushes the material to either side, leaving a better-shaped groove from one to two thousandths of an inch deep. Because of the softness of the material, fibre needles must be used when playing back this type of record, but despite this precaution the playing life is comparatively short.

Another material which has also been tried as a recording blank is copper, and when recording on this material (or aluminium), the cutting is materially assisted by lubricating the blank before recording.

Search For Ideal Disc.

Realising the serious disadvantages of the metal type disc, considerable research has been conducted the world over to develop a disc surface material having three essential qualities, e.g., the property of being easily cut, long playing life and wide frequency range.

Undoubtedly, the most suitable materials of this nature are those of the synthetic resin group. There are numerous variations of this synthetic resin group, many being quite suitable for sound recordings. Some of these materials, however, while being quite satisfactory in all other respects, have the unfortunate disadvantage of either hardening too quickly when exposed to the air, or a tendency to partial disintegration of the material itself into other compounds with disastrous effects upon the sound track.

In blanks of this nature, the compound is deposited by various means upon a suitable base, generally of aluminium, although glass, zinc and other materials have been used. For the production of first grade discs, it is essential that the base should be perfectly finished, as the slightest flaw or imperfection upon it will cause corresponding imperfections on the surface of the finished blank, and

will definitely increase the scratch level.

These synthetic resin or soft acetate discs, while possessing a frequency range which is slightly inferior to the present day gramophone record, have the great advantage of a scratch level which is definitely below that of the commercial wax product.

The "Baked" Disc.

Another type which is perhaps not yet available in Australia, is one which is supplied in a rather soft form. After the recording has been made, the disc is baked in order to harden it.

Great care must be exercised before conducting the baking process. All small particles must be removed from the grooves, as, should they be allowed to remain behind, they will be hardened in conjunction with the rest of the surface, and their presence will be revealed in the output of the amplifier as scratch and other objectionable noises.

Certain American discs are supplied with a special liquid which is

applied after recording in order to harden the surface without affecting the frequency characteristics.

In America for some time there was also available a pre-grooved disc on which the track or groove was already cut with smooth (unmodulated) sides. Its advantage was that it obviated the necessity for a special tracking device such as is required with all other types. However, it had the great disadvantage of possessing a very limited frequency range.

Playing Time Considerations.

Before concluding the subject of discs, their playing period is of special interest. Operating the turntable at the standard speed of 78 r.p.m., the 8" disc runs for 2½ minutes, the 10" for 3½ minutes, and the 12" for 5 minutes for each side.

The Stylus.

At this stage it would be as well to deal with the cutting needle or stylus, which plays an extremely important part in the quality of the finished recording.

Two types are generally available for recording purposes, namely, the steel and the jewel. The latter type, which is generally a sapphire, produces a slightly better recording, and in addition has a much longer life than the steel needle, although the initial cost is proportionately high. The steel type is comparatively cheap, and reproduction is quite good, but the needle must be given constant attention to ensure that its cutting edges remain sharp and clean.

As an example of the care necessary with the steel stylus, in the course of experiments an unused stylus which was left exposed to moist air conditions, was found on examination under a powerful magnifying glass to have acquired a considerable amount of rust on its cutting edges. This oxidation was proved to have a definite detrimental effect on the quality of the recording as well as increasing the scratch level. The sapphire, of course, is unaffected by atmospheric conditions, its disadvantage being in its brittle nature.

The direct recording stylus has a very sharp point, as the two sides meet at about 90° and the set-off angle (from the point to the back of the needle) is about 45°. (See sketch). In order to maintain the cutting needle in first-class condition an essential piece of equipment is a powerful magnifying glass, with which each cutting edge is carefully examined for the detection of any imperfections.

Before any important recordings were cut, an additional check was also made by cutting an unmodulated track in a test disc. This was then played back through the amplifier with the gain control well advanced. In this way any scratch or other defect was readily discernible, and as only about a quarter of an inch of disc was used, many such tests could be made on each side of the blank.


The Swarf.

When an immediate playback blank is being cut correctly, the stylus scoops out a thin shaving or thread, known as the swarf. This thread should be continuous from the beginning of the disc to the very end, and any break should be regarded as a definite indication of either an inferior disc, a cutting needle incorrectly inserted, or faulty tracking mechanism. Whatever the cause, the results will inevitably be disappointing until the trouble is rectified.

When the swarf is being removed correctly in an unbroken thread, it tends to follow the disc and collect around the stylus. By using a soft brush this swarf may be caused to collect around the centre of the record, it being quite important to keep the cutting point clear, as the action

(Continued on page 40.)

PALEC Model "M5" VOLT-OHM-MILLIAMMETER

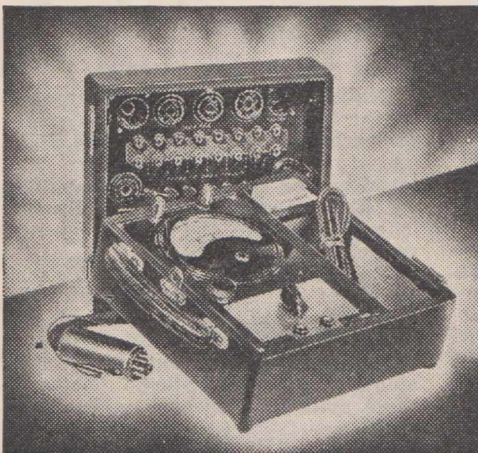

"The Palec" Model M5 is a reliable and accurate multi-range instrument equipped with our large 5 in. type meter. RANGES:—D.C. volts, 10-100-500-1000 (at 1000 ohms per volt).

Ma's, 1-10-50-100.

Ohms, 0-2,000-20,000-200,000-2,000,000.

The latter range is obtained by connecting an external 45 volt battery to the terminals provided. The instrument is supplied in a well fitted leatherette case complete with test prods.

MODEL M5, Trade price, £5/17/6, plus tax.

MODEL MA5, has four additional ranges of A.C. and Output volts. Trade price, £7/19/6, plus tax.

TERMS AVAILABLE

Manufacturers of Cathode Ray Equipment, Meters and full range of testing equipment.

ANALYSER SELECTOR

A special Analyser Selector which is easily fitted into the removable lid of Model M5 (see illustration) can be supplied. This unit enables voltage and current readings to be readily taken at all points of American or Octal type valves, without removing the chassis from the cabinet. Price, £2/15/-, extra.

PATON ELECTRICAL PTY. LTD.

90 VICTORIA STREET, ASHFIELD, SYDNEY. 'PHONE UA 1960.

Leading Distributors in all States.

World Shortwave Stations

Below is published a comprehensive list of world short-wave stations, giving call-signs, locations, frequencies (and wavelengths) together with schedules in East Australian Standard Time. NOTE: To convert kilocycles to megacycles shift the decimal point three places to the left (e.g., read 21,540 k.c. as 21.54 m.c.).

Compiled By ALAN H. GRAHAM
(SHORT-WAVE EDITOR, "RADIO WORLD")

Call.	Kc.	M.	Location.	Schedule, etc.
W9XUY	35,600	3.42	Omaha, U.S.A.—Unknown.	
W1XKA	31,600	9.49	Boston, U.S.A.—Relays WBZ 9 p.m.-4 p.m.; Sundays, 11-4 p.m.	
W1XKB	31,600	9.49	Springfield, U.S.A.—Relays WBZ as W1XKA.	
W9XHW	31,600	9.49	Minneapolis, U.S.A.—Relays WCCO midnight-3 p.m.	
W2XDV	31,600	9.49	New York, U.S.A.—Relays WABC daily, 9 a.m.-2 p.m.; Sun. & Mon., 4.30-9 a.m., 10 a.m.-1 p.m.	
W3XEY	31,600	9.49	Baltimore, U.S.A.—Relays WFBR daily, 7 a.m.-3 p.m.	
W3XKA	31,600	9.49	Philadelphia, U.S.A.—Relays KYW daily, midnight-1 p.m.	
W4XCA	31,600	9.49	Memphis, U.S.A.—Relays WMC. Schedule unknown.	
W5XAU	31,600	9.49	Oklahoma City, U.S.A.—Mon., 3-4 and 9-10 a.m.; also irreg. other days.	
W8XAI	31,600	9.49	Rochester, U.S.A.—Relays WHAM daily, 10.30-3 p.m.	
W8XWJ	31,600	9.49	Detroit, U.S.A.—Relays WWJ daily, 9-3.30 p.m.; Sun., 11-3 p.m. (Mon.).	
W9XPD	31,600	9.49	St. Louis, U.S.A.—Relays KSD. Schedule unknown.	
DGE	27,400	10.95	Nauen, Germany. Phone; irregular.	
W9XH	26,800	11.19	South Beno, U.S.A.—Relays WSBT, WFAM irreg.	
DGX	26,800	11.19	Nauen, Germany. Phone; irregular.	
W9XTA	26,500	11.32	Harrisburg, U.S.A.—Will be on air soon.	
W9XA	26,450	11.33	Kansas City, U.S.A.—Testing.	
W9XAZ	26,400	11.36	Milwaukee, U.S.A.—Relays WTMJ from 4 a.m.	
W2XJI	26,300	11.4	New York, U.S.A.—Relays WOR, 11 p.m.-4 p.m.	
W9XJL	26,100	11.49	Superior, U.S.A.—Relays WEBC daily.	
GSK	26,100	11.49	Daventry, England.—Irregular.	
W9XTC	26,050	11.51	Minneapolis, U.S.A.—Relays WCTN, midnight-4 a.m., 10 a.m.-3 p.m.	
W6XKG	25,950	11.56	Los Angeles.—Relays KGFJ 24 hours daily.	
W9XUP	25,950	11.56	St. Paul, U.S.A.—Relays KSTP, mornings.	
W3XAU	25,750	11.65	Philadelphia, U.S.A.—Experimental.	
DGV	24,300	12.35	Nauen, Germany. Phone; irregular.	
DGT	23,350	12.35	Nauen, Germany. Phone; irregular.	
DGS	22,800	13.16	Nauen, Germany. Phone; irregular.	
DJK	21,640	13.88	Berlin, Germany.—New station.	
DJJ	21,565	13.91	Berlin, Germany.—New station.	
PCJ	21,550	13.92	Hiuzen, Holland.—Evenings.	
JZM	21,520	13.94	Nazaki, Japan.—Irregular.	
W2XE	21,515	13.94	New York, U.S.A.—New freq.	
W2XAD	21,500	13.95	Schenectady, U.S.A.—Daily 11 p.m.-3 a.m.	
GSH	21,470	13.97	Daventry, England.—8.45 p.m.-3 a.m.	
W1XAL	21,460	13.98	Boston, U.S.A.—Irregular.	
OLR6A	21,450	13.99	Prague, C-slovakia.—Irregular.	
DJS	21,450	13.99	Berlin, Germany.—Daily 3.05 p.m.-2 a.m.	
WKK	21,420	14.01	Lawrenceville, U.S.A.—Phones S. America, 10 p.m.-10 a.m.	
WBU	21,260	14.11	Rocky Point, U.S.A.—Phone; irregular.	
WQA	21,220	14.14	Rocky Point, U.S.A.—Phone; irregular.	
LSL	21,160	14.19	Buenos Aires, Arg.—Phones Europe.	
KBI	21,140	14.19	Manilla, P.I.—Tests irregular.	
PSA	21,080	14.23	Rio de Janeiro, Brazil.—Phones WKK.	
KWN	21,060	14.25	Dixon, U.S.A.—Phones irregular.	
WKA	21,060	14.25	Lawrenceville, U.S.A.—Phones England.	
LSN6	21,020	14.25	Buenos Aires, Arg.—Phones New York, 10 p.m.-10 a.m.	
PSB	20,910	14.35	Rio de Janeiro, Brazil.—Phones New York irreg.	
EHY-				
EDM	20,860	14.38	Madrid, Spain.—Phones S. America.	
PFJ	20,830	14.40	Kootwijk, Holland.—Phones Java, p.m.	
KSS	20,820	14.41	Bolinas, U.S.A.—Phones Far East.	
LSY	20,700	14.49	Buenos Aires, Arg.—Tests irregularly.	
DGQ	20,500	14.63	Nauen, Germany.—Phones irregular.	
GAA	20,380	14.72	Rugby, England.—Phones Argentine and Brazil.	
DGW	20,140	14.90	Nauen, Germany.—Phones irregular.	
OPL	20,040	14.97	Leopoldville, Belgian Congo.—Phones ORG.	
DHO	20,020	14.99	Nauen, Germany.—Phones S. America.	
CFA	19,987	15.01	Drummondville, Canada.—Phones U.S.A.	
KAX	19,980	15.02	Manila, P.I.—Phones KWU, JVE and DFC.	
DLO	19,947	15.04	Rehmate, Germany.—Phones irregular.	
LSG	19,900	15.08	Buenos Aires, Arg.—Tests irregularly.	
WKN	19,820	15.14	Lawrenceville, U.S.A.—Phones England.	
JIB	19,820	15.14	Taihoku, Taiwan.—Relays JFAK, midnight.	
DFJ	19,700	15.23	Nauen, Germany.—Phone irregular.	
CEC	19,680	15.24	Santiago, Chile.—Phones Colombia and Argentine.	
LSN5	19,650	15.27	Buenos Aires, Arg.—Phones Europe.	
VQG4	19,620	15.28	Nairobi, Kenya Colony.—Phones London, 10.30-11 p.m.	
LSF	19,600	15.31	Buenos Aires, Arg.—Tests irregularly.	
EDX	19,530	15.36	Madrid, Spain.—Phones S. America.	
IRW	19,520	15.37	Rome, Italy.—Phones S. America; tests irregularly.	
LSQ	19,500	15.40	Buenos Aires, Arg.—Phones irregular.	

Call.	Kc.	M.	Location.	Schedule, etc.	Call.	Kc.	M.	Location.	Schedule, etc.
GAD	19,480	15.41	Rugby, England.—Phones VQG4, 10.30-11 p.m.		W9XAA	17,780	16.87	Chicago, U.S.A.—Irregular.	
DFM	19,460	15.42	Nauen, Germany.—Phones irregular.		PHI-2	17,770	16.88	Huizen, Holland.—Daily, 10.40-11.40 p.m.; Tues., Thurs., 10.25-11.40 p.m.	
FTM	19,855	15.5	St. Assise, France.—Phones S. America.		DJE	17,760	16.89	Berlin, Germany.—Daily, 3.05-8.50 p.m., 9-10.50 p.m., 11 p.m.-2 a.m.; Sun., 2.10-3.25 a.m.	
PMA	19,345	15.51	Bandoeng, Java.—Phones Holland, 8.30 p.m.-2 a.m.			17,760	16.89	Buenos Aires, Argentine.—"Radio Splendid." Schedule unknown.	
PPU	19,260	15.58	Rio de Janeiro, Brazil.—Phones France.		W2XE	17,760	16.89	New York, U.S.A.—Irregular.	
WKF	19,220	15.6	Lawrenceville, U.S.A.—Phones England and France.		ZBW5	17,755	16.9	Hong Kong, China.—Irregular, 7 p.m.-1 a.m.	
ORG	19,200	15.62	Ruysselede, Belgium.—Phones OPL, Belg. Congo.		IAC	17,750	16.91	Pisa, Italy, Phones ships.	
GAP	19,161	15.66	Rugby, England.—Phones Australia 4-11 p.m.		HSP	17,741	16.91	Bangkok, Siam.—Phones Germany, 11 a.m. and 6 p.m.; phones JVE, 2 p.m.	
LSM	19,140	15.68	Buenos Aires, Arg.—Phones Europe.		CJA3	17,710	16.94	Drummondville, Canada.—Phones Australia and Far East.	
HS6PJ (or HSSPJ)	19,020	15.77	Bangkok, Siam.—Mon., 11 p.m.-1 a.m. (Tues.).		IAC	17,699	16.95	Pisa, Italy.—Phones ships.	
GAQ	18,970	15.81	Rugby, England.—Phones S. Africa.		XGM	17,650	17.00	Shanghai, China.—Phones London, 10 p.m.	
WQD	18,960	15.82	Rocky Point, U.S.A.—Tests with LSY; irregular.		IBC	17,620	17.03	San Paolo, Italy.—Phones irregular.	
JVA	18,910	15.86	Nazaki, Japan.—Irregular tests; phones Europe.		VVY	17,545	17.10	Poona, India.—Phones England (GAU, GBC, GBU).—	
ZSS	18,890	15.88	Klipheuveel, S. Africa.—Phones KAAQ, midnight.		DFB	17,520	17.12	Nauen, Germany.—Phones S. America, 12.15 a.m.; phones Siam, 11 a.m. and 6 p.m.	
PLE	18,890	15.93	Bandoeng, Java.—Phones Holland, p.m.		VHY2	17,480	17.16	Poona, India.—Phones England, 10.30 p.m.	
TYD3	18,776	15.98	Paris, France.—Phones Madagascar.		HIIX	17,400	17.24	Ciudad Trujillo, D.R.—Relays HIIX.	
DFQ	18,700	16.04	Nauen, Germany.—Phones irregular.		DGR	17,341	17.30	Nauen, Germany.—Phones irregular.	
OCI	18,680	16.06	Lima, Peru.—Tests with Bogota, Colombia.		W2XGB	17,310	17.33	Hicksville, U.S.A.—Tests exc. Sun, Mon., 12:30-2:30 a.m.	
PSC	18,640	16.09	Rio de Janeiro, Brazil.—Phones N. York & B. Aires.		W3XJU	17,310	17.33	College Park, U.S.A.—Experimental station for Washington Institute of Technology.	
GAU	18,620	16.11	Rugby, England.—Phones New York.		FZE8	17,280	17.38	Djibouti, Fr. Somaliland.—Irregular.	
PCM	18,540	16.19	Kootwijk, Holland.—Phones Java.		DAF	17,263	17.38	Norddeich, Germany.—Phones ships.	
HHB	18,480	16.23	Geneva, Switzerland.—Mons., 1.45-2.30 a.m.		CMA5	17,260	17.39	Habana, Cuba.—Phones and tests irregularly.	
HBH	18,480	16.23	Geneva, Switzerland.—Mons., 1.45-2.30 a.m.		DAN	17,260	17.39	Nordenland, Germany.—Phones ships; p.m.	
HBH	18,450	16.26	Geneva, Switzerland.—Irregular.		DJG	17,185	17.46	Berlin, Germany.—New station.	
HJY	18,440	16.27	Bogota, Colombia.—Phones CEC and OCI.		WOO	17,120	17.52	Ocean Gate, U.S.A.—Phones ships.	
PCK	18,405	16.30	Kootwijk, Holland.—Phones Java (PLE and PMC).		GBC	17,080	17.56	Rugby, England.—Phones ships.	
FZS	18,345	16.35	Saigon, Fr. Indo-China.—Phones Paris.		JZD	16,910	17.59	Nazaki, Japan.—Phones ships.	
WLA	18,340	16.36	Lawrenceville, U.S.A.—Phones England.		DJH	16,810	17.84	Berlin, Germany.—New station.	
GAS	18,310	16.38	Rugby, England.—Phones New York.		ITK	16,385	18.32	Mogadiscio, It. Somaliland.—Phones IAC around 12.30 a.m.	
YVR	18,299	16.39	Maracay, Venezuela.—Phones Germany.		PCL	16,305	18.39	Kootwijk, Holland.—Special relays & phones irreg.	
IUD	18,270	16.42	Addis Ababa, Ethiopia.—Irregular.		WLK	16,270	18.44	Lawrenceville, U.S.A.—Phones S. America.	
FTO	18,250	16.43	St. Assise, France.—Phones S. America.		WOG	16,270	18.44	Ocean Gate, U.S.A.—Phones England.	
KUS	18,220	16.46	Manila, P.I.—Phones U.S.A.		KTO	16,240	18.47	Manila, P.I.—Phones Japan and U.S.A., 8 a.m.	
GAW	18,200	16.48	Rugby, England.—Phones New York.		FZB3	16,233	18.48	Saigon, Fr. Indo-China.—Phones Paris.	
JVB	18,190	16.49	Nazaki, Japan.—Phones Java and U.S.A.		GBA	16,140	18.59	Rugby, England.—Phones S. America.	
CGA	18,180	16.51	Drummondville, Canada.—Phones GBB, Rugby.		IRY	16,177	18.62	Rome, Italy.—Phones IDU, ITK.	
PMC	18,135	16.54	Bandoeng, Java.—Phones Holland.		JVC	16,050	18.69	Nazaki, Japan.—Phones Hong Kong.	
LSY3	18,115	16.56	Buenos Aires, Arg.—Tests; broadcasts Sat., 8-9 a.m.		KKP	16,030	18.71	Kahuku, Hawaii.—Phones Dixon, U.S.A., 6 a.m.	
TYE1	18,090	16.58	Paris, France.—Phones New York.		FIK	15,880	18.90	St. Assise, France.—Phones Saigon, 11 p.m.	
PCV	18,070	16.60	Kootwijk, Holland.—Phones PLE.		CEC	15,865	18.91	Santiago, Chile.—Phones Lima.	
KUN	18,060	16.61	Bolinas, U.S.A.—Phones Manila.		JVD	15,860	18.91	Nazaki, Japan.—Phones Shanghai and U.S.A.	
GAB	18,040	16.63	Rugby, England.—Phones Canada.		LSL	15,810	18.98	Buenos Aires, Argentine.—Phones London & Paris.	
KQJ	18,020	16.65	Bolinas, U.S.A.—Phones irregular.		XOJ	15,800	18.99	Shanghai, China.—Phones London & U.S.A.	
WQB	17,940	16.72	Rocky Point, U.S.A.—Phones LSY, Arg.		JYT	15,760	19.06	Kemikawa-Cho, Japan.—Tests with Dixon, U.S.A.	
WLL	17,900	16.76	Rocky Point, U.S.A.—Tests with Geneva and Berlin.		JIA	15,740	19.06	Chureki, Japan.—Tests irregular.	
LSN	17,850	16.81	Buenos Aires, Arg.—Phones irregular.		WJS	15,700	19.11	Hicksville, U.S.A.—Phones Africa.	
DJH	17,845	16.81	Berlin, Germany.—New station.		JVE	15,650	19.16	Nazaki, Japan.—Phones Java & Siam, 6-8 p.m.	
HVJ	17,840	16.82	Vatican City, Italy.—New freq.						
PCV	17,810	16.84	Kootwijk, Holland.—Phones Java, 9-11 p.m.						
TPB-3	17,810	16.84	Rome, Italy.—Relays 2RO, till 9 a.m., irreg.						
TGWA	17,800	16.84	Paris, France.—Daily 12.30-2 a.m.						
GSG	17,790	16.86	Guatemala, City, Guat.—Irregular.						
			Daventry, England.—Daily, 3.20-7 a.m., 8.45 p.m.-3 a.m.						
JZL	17,785	16.87	Tokyo, Japan.—Irregular.						
W3XAL	17,780	16.87	Bound Brook, U.S.A.—Daily mid.-11 a.m.						


Call.	Kc.	M.	Location.	Schedule, etc.	Call.	Kc.	M.	Location.	Schedule, etc.
OCJ	15,625	19.20	Lima, Peru.—Phones CEC.		GSO	15,180	19.76	Davenport, England.—Daily, mid.-3 a.m., 5-7.15 a.m., 7.15-9 a.m., 9.20-11.30 a.m.	
JVF	15,620	19.21	Nazaki, Japan.—Phones Dixon, 11 a.m. and 8 p.m.		TGWA	15,170	19.77	Guatemala City, Guat.—Daily, 1.45-2 a.m.; Mon., 1.45-9 a.m.	
CO9XX	15,550	19.29	Tuinucu, Cuba.—Broadcasts irregularly, mornings.		I2RO5	15,170	19.77	Rome, Italy.—Testing.	
HSC2	15,530	19.32	Bangkok, Siam.—Phones JVE.		XEWW	15,165	19.78	Lima, Peru.—Testing: "Radio National."	
HS8PJ	15,530	19.32	Bangkok, Siam.—Broadcasts occasionally Mon.		OLR5C	15,160	19.79	Mexico City, Mexico.—Irregular, 3 a.m.-3 p.m.	
CMA3	15,505	19.37	Habana, Cuba.—Phones and tests irreg.		JZK	15,160	19.79	Prague, Cz-Slovakia.—Irregular.	
KEM	15,490	19.36	Bolinas, U.S.A.—Phones Java and China.		VPD	15,160	19.79	Nazaki, Japan.—Irregular.	
KKL	15,475	19.39	Bolinas, U.S.A.—Phones Manila and Japan.		VU-3	15,160	19.79	Suva, Fiji.—New freq.	
KKR	15,460	19.41	Bolinas, U.S.A.—Phones Far East.		XEBR	15,160	19.79	Delhi, India.—Daily, 4.30-7.30 p.m., 11.30 a.m.-1.30 p.m.	
IUG	15,450	19.42	Addis Ababa, Ethiopia.—Phones Rome, 12.15 a.m.		SM5SX	15,155	19.79	Hermosillo, Mexico.—Irregular.	
XEBM	15,440	19.43	Mazatlan, Mexico.—Irregularly 10 p.m.		YDC	15,150	19.80	Stockholm, Sweden.—Daily 2 a.m.-8 a.m.; Mid. Sun., 8 a.m. Mon.	
KWE	15,430	19.44	Bolinas, U.S.A.—Phones Far East.		GSF	15,140	19.82	Bandoeng, Java.—Daily, 9-10.30 a.m., 1.30-5 p.m., 8.30 p.m.-1.30 a.m.; Sat., 10.30 a.m.-5 p.m.	
KWO	15,415	19.46	Dixon, U.S.A.—Phones Japan and Hawaii.		TPB-6	15,130	19.83	Davenport, England.—Daily, 8.45 p.m.-3 a.m.	
HAS3	15,370	19.52	Budapest, Hungary.—Sundays mid.-1 a.m. (Mons.).		W1XAL	15,130	19.83	Paris, France.—Irreg.	
DZG	15,360	19.53	Zeesen, Germany.—Irregular.		SP19	15,120	19.83	Boston, U.S.A.—Tues.-Sat., 1-2 a.m.	
KWU	15,355	19.53	Berne, Switzerland.—Irreg., 9.45-10.45 a.m.		HVJ	15,120	19.83	Warsaw, Poland.—Relays SPW, SPD, 9 a.m.-noon.	
DJR	15,340	19.56	Dixon, U.S.A.—Phones Pacific Isles and Japan.		DJL	15,110	19.85	Vatican City, Italy.—Wed., Thurs., Fri., 1.30-1.45 a.m.	
W2XAD	15,330	19.56	Berlin, Germany.—Daily, 7.50 a.m.-1.45 p.m.; 11 p.m.-mid.		WNC	15,055	19.92	Berlin, Germany.—Daily 1.40-7.25 a.m., 3-5 p.m., 11 p.m.-mid.; Sun., 9 p.m.-11 p.m.	
W6XBE	15,330	19.56	Schenectady, U.S.A.—Daily, 3.15-9 a.m.		RKI	15,038	19.95	Hialeah, U.S.A.—Calls Central America.	
OLR5B	15,320	19.58	Belmont, Calif., U.S.A.—New G.E. station soon in use		HIR	15,038	19.95	Moscow, U.S.S.R.—Broadcasts 3.15 p.m. (Mon.); phones Tachkent, 10 p.m.	
GSP	15,310	19.60	Prague, Cz-Slovakia.—Tues., Wed., Fri., Sat., 9.55 a.m.-12.55 p.m.; Sun., Mon., Thurs., 8-8.15 a.m.		EALAV	15,000	20.00	Ciudad Trujillo, D.R.—Phones WNC.	
XEBM	15,300	19.61	Berlin, Germany.—Daily, 7.50 a.m.-2 p.m., 3.5 p.m.-7.30 a.m.		YSL	14,985	20.02	Salas, Spain.—Nationalist station.	
YDB	15,300	19.61	Mazatlan, Mexico.—Irreg. midnight-1 a.m., 4-5 a.m., 11 a.m.-1 p.m.		KAY	14,980	20.03	San Salvador, Salvador.—Phones irregular.	
LRU	15,290	19.62	Rome, Italy.—Relays 2RO till noon, irreg.		LZA	14,970	20.04	Manila, P.I.—Phones Pacific Isles.	
VUD-4	15,290	19.62	Soerabaya, Java.—Daily 10.30 a.m.-5 p.m.		PSF	14,960	20.05	Sophia, Bulgaria.—Tues., Wed., Fri., Sat., 2.30-5.45 a.m.; Thurs., 2.30-7.45 a.m.; Sun., 2.30-8 a.m., 9-9.30 p.m.	
H13X	15,280	19.63	Buenos Aires, Argentine.—Daily, 10 p.m.-midnight.		HJB	14,950	20.07	Rio de Janeiro, Brazil.—Phones Buenos Aires.	
DJQ	15,280	19.63	Delhi, India.—New 5KW station soon on air.		HII	14,940	20.08	Bogota, Colombia.—Phones WNC.	
W2XE	15,270	19.65	Ciudad Trujillo, D.R.—Relays HIX, 3.10-4.10 a.m. Sundays, 10.40 p.m.-1.40 a.m. (Mon.).		HJA3	14,940	20.08	Ciudad Trujillo, D.R.—Phones WNC.	
GSI	15,260	19.66	Berlin, Germany.—Daily, 7.50 a.m.-2 p.m., 3.5 p.m.-7.30 a.m.		PSE	14,935	20.09	Barranquilla, Colombia.—Phones WNC.	
RIM	15,252	19.67	New York, U.S.A.—Daily, 3.20-7 a.m., 12.20-2.25 p.m., 5-7.15 p.m.		KQH	14,920	20.11	Rio de Janeiro, Brazil.—Phones U.S.A. and Madrid.	
W1XAL	15,250	19.67	Davenport, England.—Daily exc. Sun, Mon., 4-9 a.m.; Sun., Mon., 5.30-9 a.m.		JVG	14,920	20.12	Kahuku, Hawaii.—Tests irreg.	
TPA2	15,245	19.68	Tachkent, U.S.S.R.—Works Moscow 10 p.m.		OCJ2	14,845	20.21	Lima, Peru.—Phones other S. American stations.	
HS8PJ	15,230	19.70	Boston, U.S.A.—Mon., 1-3 a.m.		WQU	14,800	20.27	Rocky Point, U.S.A.—Phones Europe.	
OLR5A	15,230	19.70	Paris, France.—Daily, 9 p.m.-2 a.m.		ROU	14,790	20.28	Omsk, Siberia, U.S.S.R.—Phones Moscow, 10 p.m.-	
PCJ-2	15,220	19.71	Bangkok, Siam.—Irregularly Mon., 11 p.m.-1 a.m.		WEB	14,770	20.31	Rocky Point, U.S.A.—Phones Europe.	
			Prague, Cz-Slovakia.—Irreg. at 11 a.m.		IPA	14,730	20.37	Rome, Italy.—Broadcasts 9-11 a.m.	
			Huizen, Holland.—Daily exc. Sun., 9.15-9.45 a.m.; Sun., 10.15-10.45 a.m.; Tues., 5-6.30 p.m.; Thurs., 12.30-2.30 a.m.		PSF	14,690	20.42	Rio de Janeiro, Brazil.—Phones Arg. and U.S.A.	
			Pittsburgh, U.S.A.—Daily, 11 p.m.-9 a.m.		DFD	14,665	20.46	Nauen, Germany.—Phones irreg.	
W8XK	15,210	19.72	Berlin, Germany.—Daily, 3.05 p.m.-2 a.m., 7.50-1.50 p.m.; Sun., 2.10-3.25 a.m.		GBL	14,653	20.47	Rugby, England.—Phones JVH, 4-10 p.m.	
DJB	15,200	19.74	Ankara, Turkey.—Daily, 4.20-8 a.m.		TYF	14,640	20.49	Paris, France.—Phones Saigon and Cairo, 3 a.m., 6 p.m.	
TAQ	15,195	19.75	Rome, Italy.—Relays 2RO till 9 a.m., irreg.		EHY-			Madrid, Spain.—Phones S. America.	
	15,190	19.75	Lahti, Finland.—Daily, 3.5 a.m.; Mon., 3-4 p.m.		EDM			Nauen, Germany.—Phones irreg.	
OER-5	15,190	19.75	Vienna, Austria.—New freq.		DGZ				
ZBW4	15,190	19.75	Hong Kong, China.—Irregular, 2.30 and 6 p.m.						
RV26 (or RV96)	15,183	19.75	Moscow, U.S.S.R.—Irregular.						

Call.	Kc.	M.	Location.	Schedule, etc.
JVH	14,600	20.55	Nazaki, Japan.—Broadcasts irreg., 8 a.m.-2.30 p.m.; phones Europe, 7 p.m.	Lawrenceville, U.S.A.—Phones England.
WMN	14,590	20.56	Lawrenceville, U.S.A.—Phones England.	Asmara, Eritrea.—Phones Rome, p.m.
HBJ	14,536	20.64	Geneva, Switzerland.—Mon., 4.45-5.30 a.m.; Tues., 10-11.30 a.m.	Hialeah, U.S.A.—Phones irregular.
LSN	14,530	20.65	Buenos Aires, Arg.—Phones New York.	Maracay, Venezuela.—Phones WNC.
	14,500	20.69	Asmara, Eritrea.—Phones Rome and Addis Ababa, 9.30 p.m.	Drummondville, Canada.—Phones London and ships.
LSM2	14,500	20.69	Buenos Aires, Arg.—Phones Rio and Europe.	Norddeich, Germany.—Phones ships.
TIR	14,485	20.71	Cartago, Costa Rica.—Phones C. America & U.S.A.	Manila, P.I.—Phones Tokyo, 8 p.m.-mid.
YSL	14,485	20.71	San Salvador, Salvador.—Irregular.	Rome, Italy.—Phones irregular.
YNA	14,485	20.71	Managua, Nicaragua.—Phones WNC.	Nauen, Germany.—Phones irregular.
HPF	14,485	20.71	Panama City, Panama.—Phones WNC.	Suva, Fiji Is.—Not in use at present.
HRF	14,485	20.71	Tegucigalpa, Honduras.—Phones WNC.	Nazaki, Japan.—Phones ships.
HRM	14,484	20.71	Tela, Honduras.—Phones WNC.	Lobito, Angola.—Sun. and Thurs., 5.45-7.30 a.m.
TGF	14,485	20.71	Guatemala City, Guat.—Phones WNC.	Paris, France.—Phones CNR, Morocco.
HLR5	14,485	20.71	Nacaome, Honduras.—Phones WNC.	Fisa, Italy.—Phones ships.
PLX	14,480	20.72	Bandoeng, Java.—Phones Europe.	Reindeer Pt., Greenland.—Phones WEL.
WMF	14,470	20.73	Lawrenceville, U.S.A.—Phones London and Paris.	Elgin, U.S.A.—Testing.
DZH	14,460	20.75	Rugby, England.—Irregular.	Novosibirsk, U.S.S.R.—Phones daily, 10 p.m.
GBW	14,440	20.78	Malaga, Spain.—Nationalist station; relays Sala- manca, 5 a.m. and 11.15 a.m.	Ocean Gate, U.S.A.—Phones ships.
RAEM	14,410	20.82	North Pole Base U.S.S.R. Scientists.—Irregular.	Barranquilla, Colombia.—Phones HJB, HPF & WNC.
DOT	14,410	20.82	Koenigs Wusterhausen, Germany.—Phones irregu- lar.	Barranquilla, Colombia.—Phones WNC.
IBC	14,410	20.82	San Paolo, Italy.—Phones irregular.	Rabat, Morocco.—Phones Paris.
EAYBA	14,284	20.96	Cadiz, Spain.—Nationalist station.	Pisa, Italy.—Phones ships.
WIOXDA	14,250	21.00	Schooner "Morrissey".—Irregular.	Rugby, England.—Phones ships.
FETS	14,200	21.13	Burgos, Spain.—Nationalist station.	Ciudad Trujillo, D.R.—Broadcasts, exc. Mon, 2.40 and 10.10 a.m.
PIJ	14,166	21.15	Dordrecht, Holland.—Sundays, 3-3.30 a.m.	Quito, Ecuador.—New Freq.
EABAE	14,080	21.30	Las Palmas, Canary Is.—Nationalist station.	Norddeich, Germany.—Phones ships.
EAB2A	14,031	21.38	Jaca, Spain.—Nationalist station.	Bandoeng, Java.—Phones Sydney.
E9AH	14,004	21.4	Tetuan, Sp. Morocco.—News at 7.30 & 10.15 a.m. Relays Salamanca 8.40 a.m.	Santiago, Chile.—Daily 2-4 and 7-11 a.m.; Mondays, 7 a.m.-1 p.m.
GBA	13,990	21.44	Rugby, England.—Phones Buenos Aires.	Wellington, N.Z.—Irregular.
LSB	13,950	21.5	Buenos Aires, Arg.—Testing around 10.30 a.m.	Rugby, England.—Phones New York.
SUZ	13,820	21.71	Abou Zabal, Egypt.—Phones Europe, 2 a.m.	Manila, P.I.—Phones irregular.
KKW	13,780	21.77	Bolinas, U.S.A.—Special relays.	Paris, France.—Phones Far East and ships.
TYE-2	13,760	21.80	Paris, France.—Phones U.S.A.	Reykjavik, Iceland.—Broadcasts Mon. 4.40-5.30 a.m.; phones England.
CGA-2	13,745	21.83	Drummondville, Canada.—Phones Europe.	Paris, France.—Phones ships.
RIS	13,738	21.84	Tiflis, U.S.S.R.—Phones Moscow.	Trujillo, Peru.—Irregular.
OX2QY	13,700	21.90	Reindeer Pt., Greenland.—Irregular.	Rugby, England.—Phones New York.
KKZ	13,690	21.91	Bolinas, U.S.A.—Irregular.	Zeesen, Germany.—Tests irregularly.
HJY	13,667	21.98	Bogota, Colombia.—Phones CFC.	Algers, Algeria.—Phones Paris, 3-9.30 p.m.
SPW	13,635	22.00	Warsaw, Poland.—Daily 9-11 a.m.; Sun., Mon., 9 a.m.-noon.	Drummondville, Canada.—Phones Australia (VY).
JYK	13,610	22.04	Kemikawa-Cho, Japan.—Irregular.	Kootwijk, Holland.—Phones D.E.I.
ZMBJ	13,600	22.06	TSS "Awatea".—Daily around 4 p.m.	Moscow, U.S.S.R.—Daily, 3.15-4 a.m., 6-9 a.m., 11 a.m.-12.15 p.m., 1-2 p.m., 9-10 p.m.; Sun., 9 p.m.-4 a.m.
GBB2	13,595	22.07	Rugby, England.—Phones Canada.	Nauen, Germany.—Phones irregular.
GBB	13,585	22.08	Rugby, England.—Phones Egypt and Canada.	Rockbank, Australia.—Phones Canada.
JVI	13,560	22.13	Nazaki, Japan.—Phones Manchukuo.	Saigon, Fr. Indo-China.—Phones Paris.
WKC	13,465	22.28	Rocky Point, U.S.A.—Tests and relays irreg.	Ciudad Trujillo, D.R.—Relays HIX Wed., Sat., 11.10 a.m.-1 p.m.
WKD	13,435	22.33	Rocky Point, U.S.A.—Tests and relays irreg.	Addis Ababa, Ethiopia.—Phones IAC around 3 p.m.
GJ	13,415	22.36	Rugby, England.—Phones Japan (JVH) and China.	Victoria, Spain.—Around 7 a.m.
WCT	13,410	22.37	San Juan, Porto Rico.—Phones Miami, U.S.A.	Bolinas, U.S.A.—Tests irregularly.
YSJ	13,410	22.7	San Salvador, Salvador.—Phones WNC.	

Call.	Kc.	M.	Location.	Schedule, etc.	Call.	Kc.	M.	Location.	Schedule, etc.
FTA	11,940	25.13	St. Assise, France.	Phones Morocco & Argentine.	TGWA	11,760	25.51	Guatemala City, Guat.	Irregular at 1 p.m.; Mon., 9 a.m.
YNA	11,935	25.14	Managua, Nicaragua.	Phones C. and S. America.	OLR4B	11,760	25.51	Prague, Cz-Slovakia.	Irregular.
TI2XD	11,920	25.19	San Jose, Costa Rica.	Daily 2-5 a.m., 8 a.m.-2 p.m. (exc. Mon.).	GSD	11,750	25.53	Daventry, England.	Daily, 3.20-9 a.m., 9.20-11.30 a.m., 12.20-2.20 p.m., 5-7.15 p.m.
CB1190	11,910	25.20	Valdivia, Chile.	Relays CB69, 1-4 a.m., 5 a.m.-2 p.m.	COCX	11,740	25.55	Habana, Cuba.	Relays CMX, 11 p.m.-4 p.m.
XEWI	11,900	25.21	Mexico City, Mexico.	Sun., noon-3 p.m.; Tues., Thurs., Sat., 6-7 a.m.; noon-3 p.m.; Wed., Fri., 10.30 a.m.-3 p.m.	HVJ	11,740	25.55	Vatican City, Italy.	Testing.
	11,900	25.21	Hanoi, Fr. Indo-China.	Daily, 3-5 a.m., 9 p.m.-1 a.m.	HP5L	11,740	25.55	David, Panama.	Daily, 7-10 a.m.
IUY	11,900	25.21	Rome, Italy.	10.30 a.m.-noon.	W1XAL	11,730	25.57	Boston, U.S.A.	Daily exc. Sun., Mon., noon-2 p.m.; see also 11790 k.c.
OLR4D	11,900	25.21	Prague, Cz-Slovakia.	Irregular.	PHI	11,730	25.57	Hiuzen, Holland.	Not in use at present.
XEXR	11,895	25.22	Mexico City, Mexico.	Daily, 9 a.m.-2.30 p.m.	CJRX	11,720	25.60	Winnipeg, Canada.	Daily, 9 a.m.-3 p.m.; Mon., 8 a.m.-1 p.m.
VPD	11,895	25.22	Suva, Fiji.	New freq.	TPB-9	11,720	25.60	Paris, France.	Heard around 1 p.m.
HP5G	11,895	25.22	Panama City, Panama.	Daily 12.30-4 a.m., 9 a.m.-2 p.m. (see 11780 k.c.).	CR7BH	11,718	25.60	Laurencio Marques, Port East Africa.	Daily, 3.5-7 a.m., 3.5-4 p.m., 7.30-9.30 p.m., mid-2 a.m.; Sun., 8-10 p.m.; Mon., 1-4 a.m.
TPB-7	11,885	25.23	Paris, France.	Daily 10 a.m.-12.15 p.m., 12.30-3 p.m.	TPA4	11,715	25.61	Paris, France.	Daily, 10 a.m.-12.15 p.m., 12.30 p.m.-3 p.m.
TPA3	11,880	25.23	Paris, France.	Daily, 2.15-9 a.m., 5-8 p.m.	SBP	11,710	25.63	Motala, Sweden.	Daily, 2-4 a.m., 4.20-5.05 p.m., 9 p.m.-mid.; Sat., 4.20-5 p.m., 9 p.m.-4.30 a.m.; Sun., 6 p.m.-4.30 a.m.; Thurs. and Sun., 11 a.m.-noon.
XEXA	11,880	25.23	Mexico City, Mexico.	Not in use at present.				Saigon, Fr. Indo-China.	Daily 9 p.m.-12.15 a.m.
OLR4C	11,875	25.26	Prague, Cz-Slovakia.		XEWB	11,710	25.63	Guadalajara, Mexico.	Irregular.
W8XK	11,870	25.26	Pittsburgh, U.S.A.	Daily, 9-11.45 a.m.	DJZ	11,710	25.63	San Salvador, Salvador.	Irregular, 4.30-5.30 a.m.
YDB	11,865	25.28	Berne, Switzerland.	Irreg. at 11 a.m.	SP25	11,700	25.65	Berlin, Germany.	New station.
	11,860	25.29	Soerabaia, Java.	Daily, 1.30-5 p.m.; Sun., 10.30 a.m.-5.30 p.m.	HP5A	11,700	25.65	Warsaw, Poland.	Relays SPW, SPI, 9 a.m.-noon.
GSE	11,860	25.29	Daventry, England.	5-7.15 p.m.	CB1170	11,700	25.65	Panama City, Panama.	Daily, 1 a.m.-1 p.m.
DJP	11,855	25.31	Berlin, Germany.	Not in use at present.	XGJ	11,691	25.67	Santiago, Chile.	Relays CB89 daily, 9 a.m.-3 p.m.
CB1185	11,850	25.32	Santiago, Chile.	Relays CB138.	KIO	11,680	25.68	Hankow, China.	
KZRM	11,840	25.34	Manila, P.I.	Irregular, noon-1 a.m.	IQY	11,676	25.7	Kahuku, Hawaii.	Phones Far East.
CSW-4	11,840	25.34	Lisbon, Portugal.	Daily, 9-11 a.m.				Rome, Italy.	Relays ZRO, 4.35-5.25 a.m., 9 a.m.-noon.
OLR4A	22,840	25.34	Prague, Cz-Slovakia.	Daily 3.55-7 a.m.; Mon., 8.55-11.55 a.m.; Tues., Wed., Fri., Sat., 10.55 a.m.-1.55 p.m.	PPQ	11,670	25.70	Rio de Janeiro, Brazil.	Phones U.S.A. & Argentine.
W9XA	11,830	25.36	Chicago, U.S.A.	Irregular, 10 p.m.-9 a.m.	JVL	11,660	25.73	Nazaki, Japan.	Irregular.
W2XE	11,830	25.36	New York, U.S.A.	Daily, 9.30 a.m.-2 p.m.	VRRI	11,595	25.87	Stony Hill, Jamaica.	Phones WNC.
XEBR	11,820	25.38	Hermosilla, Mexico.	Relays XEBH, 4-7 a.m., noon-3 p.m.	HH2T	11,570	25.93	Port-au-Prince, Haiti.	Irregular.
GSN	11,820	25.38	Daventry, England.	Not in use at present.	CMB	11,560	25.98	Habana, Cuba.	Phones New York.
12RO4	11,810	25.40	Rome, Italy.	Daily, 1 a.m.-noon, 7.40-11.45 p.m.	VIZ3	11,560	25.98	Fiskdale, Australia.	Tests irregularly.
COGF	11,805	25.41	Matanzas, Cuba.	Relays CMGF daily, 5-6 a.m., 7-8 a.m., 9 a.m.-2 p.m.	XGR	11,538	26.00	Shanghai, China.	Phones irregular.
OZG	11,805	25.41	Skamleboak, Denmark.	Irregular.	SPD	11,530	26.01	Warsaw, Poland.	Daily 9 a.m.-noon.
OFR3	11,801	25.42	Vienna, Austria.	Irregular 1-8 a.m.	XAM	11,500	26.09	Merida, Mexico.	Irregular around 4 a.m.
JZJ	11,800	25.42	Tokyo, Japan.	Daily, 5.30-7 a.m., 7.30-8.30 a.m., 11-11.30 a.m., 3.30-4.30 p.m., 10-10.30 p.m., 11 p.m.-12.30 a.m.	PMK	11,500	26.09	Bandoeng, Java.	Tests irregularly.
DJO	11,795	25.43	Berlin, Germany.	Not in use at present.	CJA4	11,413	26.28	Drummondville, Canada.	Phones Australia.
OAX5B	11,795	25.43	Ica, Peru.	Daily, 2-3 a.m., 7 a.m.-2.15 p.m.	HBO	11,402	26.31	Geneva, Switzerland.	Mon., 10-10.45 a.m., 4-4.15 p.m.; Tues., 10-11.30 a.m.
W1XAL	11,790	25.45	Boston, U.S.A.	Daily, 7.45-9.30 a.m.; Wed., Fri., 7.40-9.30 a.m.; Sun., 4.45-9 a.m.; Mon., 8-9.30 a.m. See also 11730 k.c.	DAF	11,340	26.46	Nordeich, Germany.	Phones ships.
HPSG	11,780	25.47	Panama City, Panama.	Testing; see also 11895 k.c.	HIN	11,280	26.60	Cuidad Trujillo, D.R.	Irregular.
OFD	11,780	25.47	Lahti, Finland.	Daily, 4.05-5.05 p.m.	ZLT4	11,050	27.15	Wellington, N.Z.	Phones Australia and England.
DJF	11,780	25.47	Berlin, Germany.	New transmitter for Africa.	CSW-7	11,040	27.17	Lisbon, Portugal.	Daily, 4.30-6 a.m.
DJF	11,770	25.49	Berlin, Germany.	Daily, 1.35-7.35 a.m., 7.50 a.m.-1.45 p.m.	PLP	11,000	27.27	Bandoeng, Java.	Relays YDB, 9-10.30 a.m., 1.30-5 p.m., 7.30 p.m.-1.30 or 2 a.m.
XETA	11,760	25.51	Monterrey, Mexico.	Relays XET, 4-6.30 a.m.	ZLT-4	10,980	27.33	Wellington, N.Z.	Phones Australia & England.
					OCI	10,970	27.35	Lima, Peru.	Phones Bogota.
					JZB	10,960	27.36	Nazaki, Japan.	Irregular.

Call.	Kc.	M.	Location.	Schedule, etc.	Call.	Kc.	M.	Location.	Schedule, etc.
—	10,960	27.36	Tanarive, Madagascar.	Daily, 1-2 a.m., 3.30-3.45 p.m., 6.30-7.30 p.m.; Sun., 5.30-7. p.m.	OPM	10,140	29.59	Leopoldville, Belg. Congo.	Phones ORK 4-7 a.m. and around 6 p.m.
HSG	10,955	27.38	Bangkok, Siam.	Irregular.	RJR	10,080	29.76	Tiflis, U.S.S.R.	Phones Moscow.
FTH	10,940	27.43	St. Assise, France.	Phones S. America.	EDM-	10,070	29.79	Madrid, Spain.	Phones S. America.
KTR	10,910	27.50	Manila, P.I.	Phones Berlin.	EHY	10,065	29.81	Shinkyo, Manchukuo.	Phones Tokyo, 9.30-10 p.m.
DFL	10,850	27.66	Nauen, Germany.	Tests irregularly.	J/B-	10,055	29.84	Hamilton, Bermuda.	Phones New York.
KWV	10,840	27.68	Dixon, U.S.A.	Phones Hawaii.	ZFB	10,055	29.84	Abou Zabal, Egypt.	Phones Europe.
GCL	10,795	27.79	Rugby, England.	Phones Japan.	SUV	10,050	29.85	San Jose, Costa Rica.	Irregular, a.m.
YNA	10,790	27.80	Managua, Nicaragua.	Phones S. America.	TIEM	10,042	29.87	Zeesen, Germany.	Irregular.
GBP	10,770	27.85	Rugby, England.	Phones Australia.	DJB	10,040	29.87	Barranquilla, Colombia.	Tests irregularly.
JVM	10,740	27.93	Nazaki, Japan.	Phones U.S.A., 5-10 p.m.	HJA3	9,990	30.03	Manila, P.I.	Phones Java.
—	10,700	28.04	Milan, Italy.	"Radio Milano"; till 9 a.m.	KAZ	9,980	30.04	Habana, Cuba.	Relays CMBC 9.55 p.m.-3 p.m.
PLQ	10,680	28.09	Bandoeng, Java.	Phones Malaysia and D.E.I.	COBC	9,966	30.08	Rome, Italy.	Tests irregularly.
WNB	10,675	28.10	Lawrenceville, U.S.A.	Phones Bermuda.	IRS	9,950	30.15	Habana, Cuba.	Relays CMCU 10 p.m.-3 p.m.
CEC	10,670	28.12	Santiago, Chile.	Daily, 10-10.15 a.m.	COCU	9,950	30.15	Rugby, England.	Phones New York.
PSG	10,660	28.14	Rio de Janeiro, Brazil.	Phones U.S.A., Arg. & Eur.	GCU	9,940	30.18	San Juan, Porto Rico.	Phones Miami.
JVN	10,660	28.14	Nazaki, Japan.	Broadcasts daily, 5-11 p.m.; phones Europe irreg.	WCU	9,940	30.18	San Jose, Costa Rica.	Phones irregular.
—	10,630	28.22	Salamanca, Spain.	Nationalist station.	TIZ2	9,940	30.18	Panama City, Panama.	Phones irregular.
WEF	10,620	28.25	Rocky Point, U.S.A.	Tests irregularly.	HPF2	9,940	30.18	Tegucigalpa, Honduras.	Phones irregular.
EHX	10,620	28.25	Madrid, Spain.	Phones S. America.	HRF5	9,940	30.18	San Salvador, Salvador.	Phones irregular.
ZIK2	10,600	28.27	Belize, BR. Honduras.	Wed., Fri, Sun., 4.30-5 a.m., 11.30 a.m.-noon.	YSG	9,930	30.21	Bogota, Colombia.	Phones Rio de Janeiro.
WOK	10,550	28.44	Lawrenceville, U.S.A.	Phones S. America.	HKB	9,930	30.21	Lisbon, Portugal.	Daily, 8-10 a.m.
JIB	10,535	28.48	Taihoku, Taiwan.	Broadcasts, relaying JFAK, mid-1.25 a.m., 4-5.30 p.m.; phones Japan.	CSW	9,920	30.24	Nauen, Germany.	Phones irregular.
VLK	10,520	28.51	Sydney, Australia.	Phones England, 4-9 p.m.	JDY	9,920	30.24	Nauen, Germany.	"Radio Chuquisaca," 2 a.m.-3 a.m.
CF4	10,480	28.51	Mogadiscio, It. Somaliland.	Phones U.S.A.	DGM	9,892	30.33	Sucre, Bolivia.	Phones New York.
ITK	10,480	28.53	Drummondville, Canada.	Phones U.S.A.	CP-1	9,890	30.33	Buenos Aires, Arg.	Phones New York.
DGH	10,440	28.74	Nauen, Germany.	Phones Rome; irreg.	LSN	9,870	30.40	Lawrenceville, U.S.A.	Phones England.
YB3	10,430	28.76	Medan, Sumatra.	Daily, 8.30-9.30, 10.30-11.30 p.m.	WON	9,860	30.43	Madrid, Spain.	Irregular around 11 a.m.
TYE3	10,430	28.76	Paris, France.	Phones U.S.A.	EAQ	9,840	30.49	Kemikawa-Cho, Japan.	Irregular.
XGW	10,420	28.79	Shanghai, China.	Phones Japan, 3 p.m.	JYS	9,835	30.5	Rome, Italy.	Relays 2RO 9 a.m.-noon; phones Egypt.
PDK	10,410	28.80	Kootwijk, Holland.	Phones Java, 10.30 p.m.	IRF	9,833	30.51	Habana, Cuba.	Relays CMCM, 11 p.m.-4 p.m.
KES	10,410	28.80	Bolinas, U.S.A.	Phones S. America and Far East.	COCM	9,830	30.52	Rome, Italy.	Phones Egypt.
YSP	10,400	28.82	San Salvador, Salvador.	Around 1.30-2 p.m.	IRM	9,810	30.58	Rome, Italy.	Irregular around 11 a.m.
WCG	10,380	28.90	Rocky Point, U.S.A.	Tests irregularly.	IRF	9,800	30.61	Nanking, China.	Reported off air.
JVO	10,370	28.93	Nazaki, Japan.	Broadcasts irreg. around 8 p.m.	XGOX	9,800	30.61	Buenos Aires, Arg.	Tests irregularly.
EAJ43	10,370	28.93	Teneriffe, Canary Is.	Relays Salamanca, 5-7 a.m., 8 a.m.-12.45 p.m.	LSI	9,800	30.61	Rugby, England.	Phones New York.
LSX	10,350	28.98	Buenos Aires, Arg.	Tests irregularly.	GCW	9,760	30.74	Sydney, Australia.	Phones Java and New Zealand.
ZFD	10,335	29.03	Hamilton, Bermuda.	Phones U.S.A.	VLJ-	9,760	30.77	Saigon, Fr. Indo-China.	Testing 9 p.m.-12.15 a.m.
ORK	10,330	29.04	Ruyssselede, Belgium.	Daily, 4.30-6 a.m.; works OPM 6 a.m. and 4 p.m.	VLZ2	9,750	30.72	Lawrenceville, U.S.A.	Phones London and Paris.
PPM	10,310	29.10	Rio de Janeiro, Brazil.	Phones New York and Buenos Aires.	WOF	9,740	30.78	Habana, Cuba.	Relays CMCCQ, 9.55 p.m.-4 p.m.
LSI2	29,300	29.13	Buenos Aires, Arg.	Phones Europe.	COCQ	9,720	30.86	Guatemala City, Guat.	Phones irregular.
DZC	10,290	29.16	Zeesen, Germany.	Irregular.	TGZ	9,710	30.90	Lisbon, Portugal.	Daily, 8-11 a.m.
HPC	10,290	29.16	Panama City, Panama.	Phones C. and S. America.	GCA	9,710	30.90	Rugby, England.	Phones S. America.
JZO	10,270	29.22	Nazaki, Japan.	Relays JZJ, 11 p.m.	LQA	9,700	30.93	Buenos Aires, Arg.	Tests irregularly.
PMN	10,260	29.24	Bandoeng, Java.	Relays JDB, 9-10.30 a.m., 1.30-5 p.m., 7.30 p.m.-1.30 or 2 a.m.	LRA	9,690	30.95	Buenos Aires, Argentine.	Irregular 11 a.m.
LSK3	10,250	29.27	Buenos Aires, Arg.	Phones U.S.A. and Europe.	TI4NRH	9,690	30.94	Heredia, C. Rica.	Sun., 10-11 p.m., noon-1 p.m.; Wed, Fri, noon-1 p.m.
CEB	10,230	29.33	Antofagastan, Chile.	Tests 10 a.m.-12.30 p.m.	TGWA	9,685	30.96	Guatemala City, Guat.	Daily 1-2.30 p.m.; Mon., 9 a.m.-2.30 p.m.
PSH	10,220	29.35	Rio de Janeiro, Brazil.	Broadcasts 9 a.m.-noon.	FZF6	9,680	30.97	Fort de France, Martinique.	Daily, 2.30-3.30 a.m., 9.15-10.50 a.m.
DGD	10,210	29.38	Nauen, Germany.	Phones irregular.	—				
RIO	10,170	29.50	Bakou, U.S.S.R.	Phones Moscow, 1-8 p.m.					

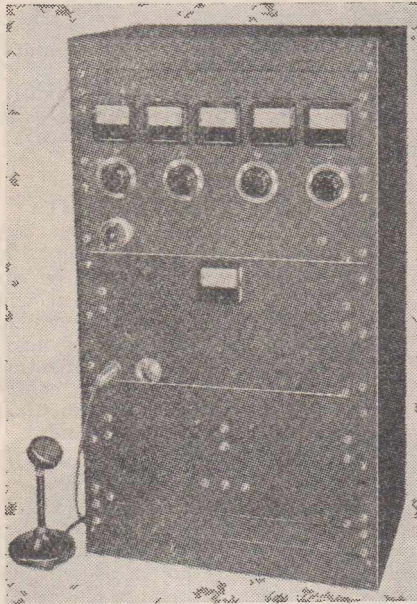Five - Band 10 To 160-Metre 'Phone And C.W. Transmitter . . .



Modern American Design Will Appeal To VK And ZL Amateurs.

★

Left: Neat and compact, the completed transmitter looks like a commercially-built job. Below: A rear view, showing the three racks—r.f. unit on top, modulator next, and power supplies below.

★

The crystal microphone shown has a high output level, greatly simplifying the problems of hum and r.f. feedback so often encountered in amateur transmitters.

THIS transmitter was designed to be as small and compact as possible. The panels on the power supply and modulator are 8 3/4" x 19" relay rack panels. The power supply chassis is set down 2" below the lower edge of the panel and the modulator chassis is set down 1 inch below the lower edge of the panel, to take advantage of all the space available in the smaller rack. The r.f. panel measures 12 1/4" x 19". The small 1 3/4" x 19" panels at top and bottom fill in the additional space in the larger rack.

The meters are the new Triplett Series mounting in a 2 1/4" hole, but having the same scale length as a 3-inch meter. From left to right, the meters are oscillator plate, buffer plate, buffer or final grid, final plate, and r.f. feeder current. The toggle switch in the lower right hand corner of the r.f. panel is the D.P.D.T. switch shown in the r.f. diagram for reading grid current on either the buffer or final with only one meter. The meter in the audio panel is in the Class "B" plate circuit.

Three-Stage Transmitter Unit For 1.75 to 30 M.C. Output.

By far the greatest problem in the design of an all-band amateur transmitter is that of maintaining suitable L/C ratios in the final stage. Insufficient capacity results in high harmonic content and poor linearity if modulated. Too much capacity results in poor efficiency.

Because most transmitting condensers have a capacity ratio of about 4-1, a maximum of 3 adjacent bands may be covered with proper ratios. Operation on any other bands will leave a great deal to be desired. The transmitter to be described approaches the ideal condition over the full range from 1.75 to 30 m.c. Actually, the L/C ratio on 30 m.c. is slightly lower than the optimum value, but the performance should be entirely satisfactory. On 1.75 m.c. the L/C ratio is slightly higher than is desirable


This article is published by courtesy of F. J. W. Fear & Co., of Wellington, N.Z., and the Taylor Tube Company, of America, in whose latest tube manual the design appeared.


A rack and panel design, the three racks comprise the r.f. unit (top), modulator unit (centre), and power supply unit (bottom). The transmitter unit comprises a 6L6G (or 6F6) as crystal oscillator, followed by a T20 buffer driving a T55 in the final. (For those who desire to use them, Radiotron equivalents of the last two valves are types 809 and 808).

The modulator unit employs a 6C6 resistance-capacity coupled to a 76, transformer-coupled to a pair of 76's in push-pull. These in turn drive a pair of push-pull 6A3's in a class "B" driver stage that easily loads the push-pull TZ20's in the output. (Radiotron type 809's can be used here, with the addition of a 1.5-volt cell for negative bias, inserted between the centre-tap of the driver transformer secondary and earth.

for 'phone operation, but is adequate for reasonable harmonic suppression.

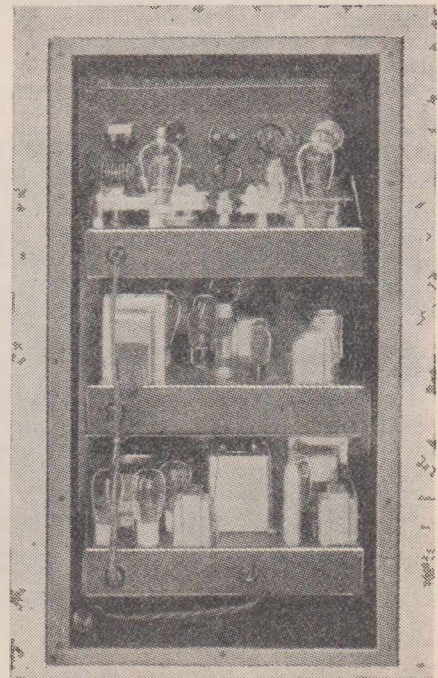Only 3 stages are used, a 6L6G or 6F6, a T20 and a T55. Using a 20 or 40-metre crystal, more than enough excitation to the final may be obtained on 30 m.c., and on the lower fre-



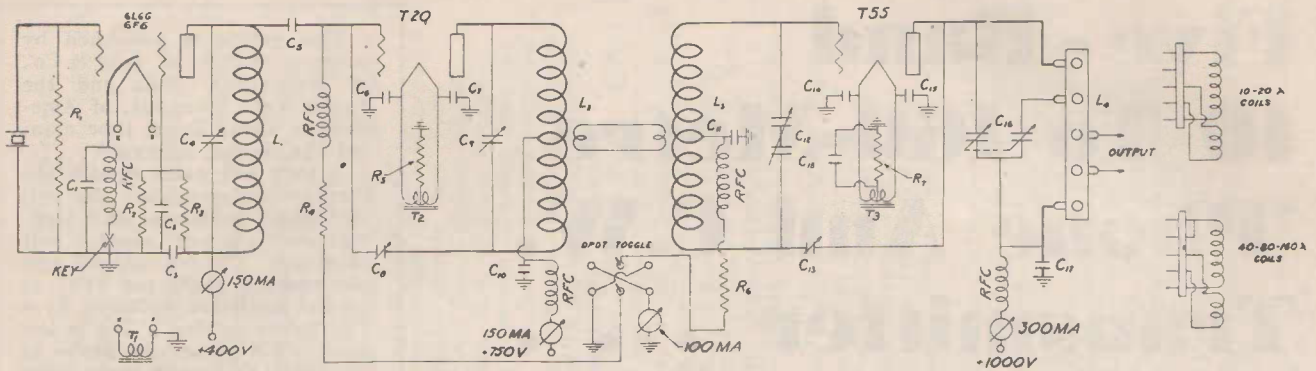

TRANSMITTER CIRCUIT

- R1—100,000 ohm 1 watt (Centralab).
- R2—35,000 ohm 2-watt (Ohmite).
- R3, R4—10,000 ohm 10 watt (Ohmite).
- R5—400 ohm 10 watt (Ohmite).
- R6—5000 ohm 10 watt (Ohmite).
- R7—400 ohm 10 watt (Ohmite).
- C1—00015 mica 600v. C.D.
- C2, C3—.01 paper 600v. C.D.

- C4—.0001.
- C5—.0001 mica 2500v. (Sangamo).
- C6, C7—.006 mica 600v. C.D.
- C8—8 mmfd. max.
- C9—100 mmfd. (Hammond).
- C10—.002 mica 2500 (Sangamo).
- C11—.002 mica 600v. C.D.
- C12—Double section 100 mmfd.
- C13—8 mmfd. max. (Hammond).

- C14, C15—.006 mica 600v.
- C16—Double section 100 mmfd. (Hammond).
- C17—.002 mica 5000v. (Sangamo).
- C18—8 mfd. 450v. electrolytic. C.D.
- RFC—2.5 mr. R.F. chokes (Micro).
- T1—6.3v. (Micro).
- T2—7.5v. (Micro).
- T3—7.5v. (Micro).

quencies the T20 loafs along delivering only about a quarter of full output when exciting the T55.

In order to obtain the necessary high capacity ratio, grid neutralisation, permitting an unbalanced output circuit, is used in the final stage. The plate tuning condenser is a Cardwell MT-100-GD, selected because of its high maximum to minimum capacity ratio (100 mmfd. maximum, 13 mmfd. minimum per section). By using only one section or both sections in parallel, the ratio is 15.4 to 1. The final stage voltage and current were then selected to fit the L/C ratios available and the condenser spacing. The T55 should be operated at a 1000 volts and 150 m.a. or less. Operation over so wide a range cannot be achieved without some compromises. One section of the condenser is used on 28 and 14 m.c., and

both in parallel on 7, 3.5 and 1.75 megacycles.



In one respect, grid neutralisation is rather a bad actor at the higher frequencies. The grid of the tube puts a resistive load across half of the input coil, which results in the opposite end of the coil being other than 180° out of phase, the condition necessary for neutralisation, if the coupling is less than unity. Unity coupling is never realised in actual practice, but satisfactory results are obtained if the coil is made as short as possible with the minimum spacing between turns. The best cure, that of putting a resistor across the neutralising half of the coil equal to the grid of the tube, wastes too much driver power on 10 metres, but could be used on the lower frequencies if desired.

The 10 and 20 metre grid coils should be wound as shown, with the


turns as close together as possible. If this is done, no difficulty will be experienced. The neutralisation will hold from 20 to 160 metres and only a slight re-adjustment need be made for 10 metres. The neutralisation seems to be better with the centre of the coil grounded as shown, than with the condenser rotor grounded.

The T55 stage operates normally with grid currents of 20 m.a. or more. In no event should the rectified grid current exceed the maximum rated value of 40 m.a. No improvement in performance is noted if the grid current exceeds 25 m.a., and it is recommended that the stage be operated with 25 m.a. of grid current under load.

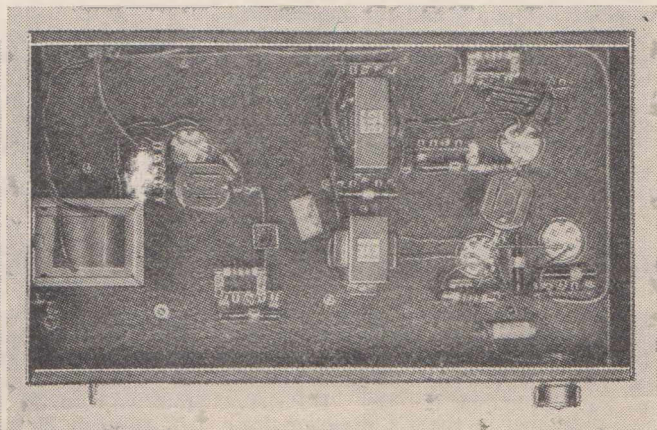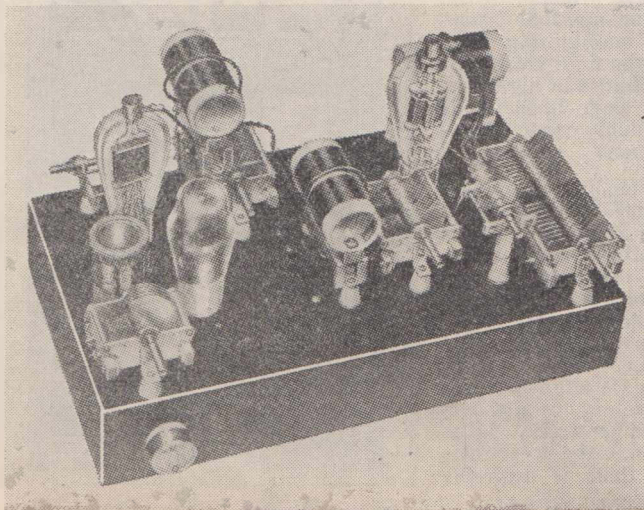Condenser C14 may be used as the excitation control. If tuned to exact resonance, particularly on the lower frequencies, the grid current may be



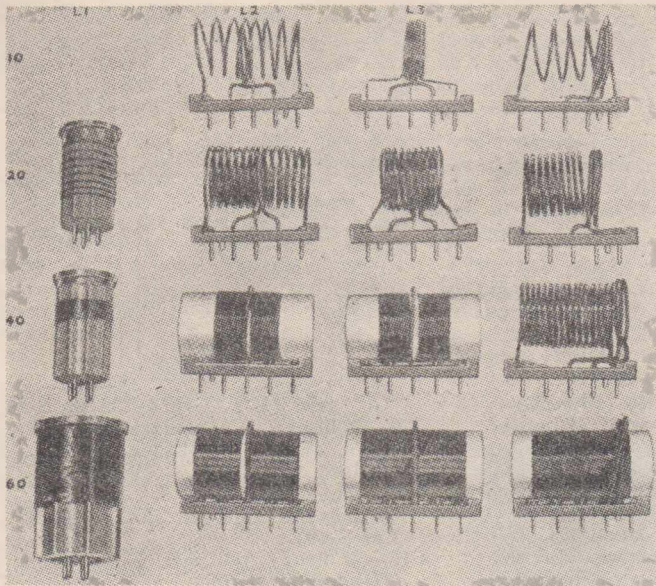These above, and under-chassis views of the transmitter illustrate the layout adopted. This should be followed as closely as possible to ensure duplicating the excellent results given by the original.



COIL DATA

Band	L ₁	L ₂	L ₃	L ₄
1.75 Mc	45 t. No 18 2 1/4" dia. close wound	72 t. No. 20 1 3/4" dia. close wound	78 t. No 20 1 3/4" dia. close wound	46 t. No 16 1 3/4" dia. close wound
3.5 Mc	26 t. No. 18 1 1/2" dia. close wound	36 t. No. 14 1 3/4" dia. close wound	44 t. No. 16 1 3/4" dia. close wound	19 t. No. 14 1 3/4" dia. close wound
7 Mc	12 t. No 18 1 1/2" dia. close wound	22 t. No 14 1 3/4" dia. close wound	24 t. No. 14 1 3/4" dia. close wound	16 t. No. 10 1 3/4" dia. 2 1/2" long
14 Mc	8 t. No. 18 1 1/2" dia. 1 3/4" long	14 t. No. 10 1 3/4" dia. 2 3/4" long	10 t. No. 10 1 3/4" dia. short as possible	10 t. No. 10 1 3/4" dia. 1 7/8" long
28 Mc		8 t. No 10 1 3/4" dia. Approx. 3" long	6 t. No. 14 1 3/4" dia. short as possible	5 t. No. 10 1 3/4" dia. 2 3/4" long

This view shows the four sets of coils required to cover the 10, 20, 40 and 80-metre amateur bands. The table on the right gives complete coil specifications.

as high as 80 m.a. C14 should be tuned on the low frequency or high capacity side of resonance until the 25 m.a. optimum value of excitation is obtained. Operation on the high capacity side of resonance is advan-

tageous because it helps to make the driving voltage more sinusoidal.

The unit is very flexible, and may be used in four different combinations on 20, 40, 80 and 160 metres, and in two-combinations on 10 metres.

1. The unit may be operated straight through on the crystal frequency. A 6F6G should be used in place of the 6L6G on 20 and 40.

2. The crystal may be one half the output frequency, doubling in the




A.C. Model 223 will test every valve used in Australia, including American and European P. and V., and in addition to the emission test a Neon leakage indicator is fitted for individual electrode selection. Eleven steps for filament voltage from 1.5 to 30 volts is provided. The Multitester range is:—A.C. and D.C. VOLTS: 5, 10, 50, 250, 1250. MILLIAMPERES: 5 Ranges, 1, 5, 25, 100, 250. OHMS: 5 Ranges, from 1 ohm to 5 megohms. This is also an excellent instrument for lining up sets and as a "Multimeter" operating in conjunction with the Power Supply an electrolytic condenser leakage test is available, and condensers may be checked at 10, 25, 100, 150, and 250 volts, and a "GOOD"—?—"BAD" meter scale provides the necessary indications.

FREE! For a limited period to purchasers of the AC223 Multitester a new 6-v. Vibrator Unit to convert the Multitester to a General Purpose Instrument for 240-v. A.C. or 6-v. battery operation. This Vibrator, which is separate from the Tester, is a general utility converter, strong, light in weight, and is easily portable. Will run a Mantel Model 5-valve A.C. Set from a 6-volt accumulator, drive an Electric Shaver, and generally act as a universal unit between the battery and the A.C. device. By the use of this New Vibrator Unit, which is plugged into a six-volt battery, the AC223 Multitester now becomes a universal A.C. Tester. The plug on the other end is an A.C. outlet, and the multitester may then be hooked up in the usual manner.


Released by SLADE'S RADIO PTY. for the discriminating Radio Dealer and Serviceman who appreciate and practise the finer points of efficient Radio Service, this is an outstanding instrument for all-round perfection, combining the multiple functions of a Valve Tester and Multitester. This instrument is a boon to the Radio Serviceman and Dealer, and needed by ALL who rely on RADIO SERVICE as an effective means of building up a MODERN RADIO BUSINESS.

the Ideal Portable Testing Laboratory

*... the AC223
Calstan Multimeter*

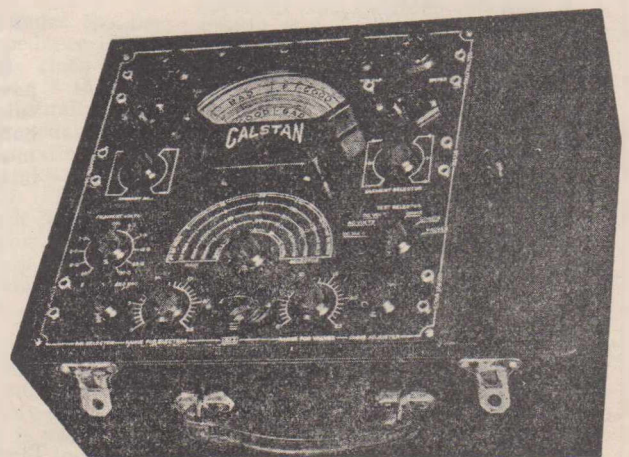

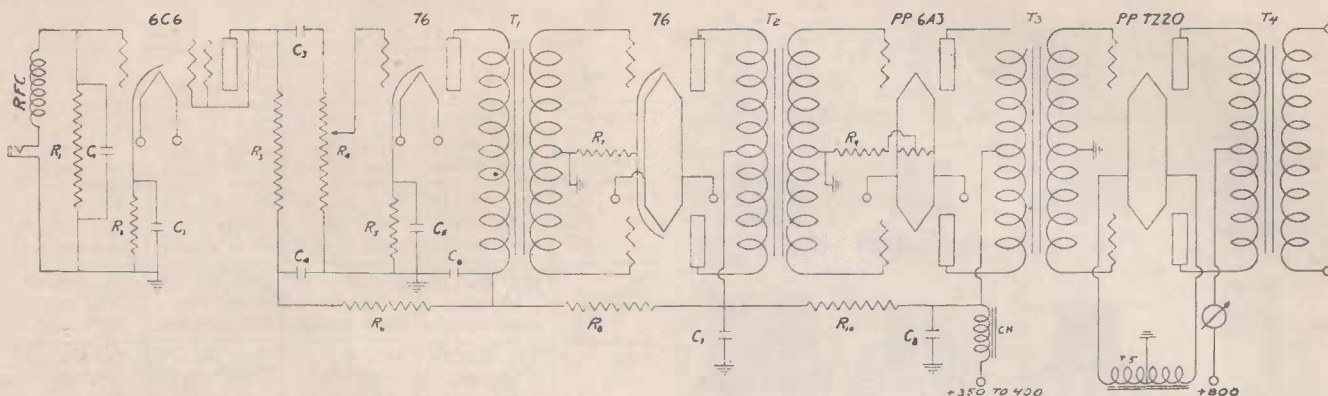MADE BY
SLADE'S RADIO PTY. LTD.
LANG ST., CROYDON, N.S.W. Telephones: UJ5381, UJ5382



MODULATOR.

- R1—5 meg. 1 watt (Centralab).
- R2—2500 ohm 1 watt (Centralab).
- R3—250,000 ohm 1 watt (Centralab).
- R4—250,000 ohm variable (Centralab).
- R5—2500 ohm 1 watt (Centralab).
- R6—50,000 ohm 1 watt (Centralab).
- R7—1500 ohm 1 watt (Centralab).
- R8—20,000 ohm 1 watt (Centralab).

- R9—800 ohm 10 watt (Ohmite).
- R10—10,000 ohm 10-watt (Ohmite).
- C1—.0001 mica.
- C2—10 mfd. 25v. electrolytic.
- C3—.01 600v. paper.
- C4—2 mfd. 450v. electrolytic.
- C5—10 mfd. 25v. electrolytic.
- C6—2 mfd. 450v. electrolytic.
- C7, C8—8 mfd. 450v. electrolytic.
- T1—Single plate to push-pull class

- “A” grid (U.T.C.—PA-132 or S-2)
- T2—Push-pull 76's to class “A” prime 6A3's. (U.T.C. PA-233 or S-8).
- T3—Class “B” input. (U.T.C.—PA-53AX or S-8).
- T4—Class “B” output. (U.T.C.—VM-3 or S-19).
- CH—30 henry 100 m.a. filter choke (Henderson C-100).
- R.F.C.—2.5 mh. R.F. choke (Micro).

crystal oscillator and working straight through in the buffer and final. This is recommended for 20 and 40.

3. The crystal may be one fourth the output frequency, doubling in the crystal stage and again in the T20 stage.

4. The crystal may be one half the output frequency, working straight through in the crystal stage and doubling in the T20 stage. The 6F6G should be used in place of 6L6G when using 20 and 40-metre crystals.

Combination 3 or 4 is necessary for ten-metre operation, 3 with a 40 metre crystal and 4 with a 20-metre crystal. It was not found feasible to use a 20-metre crystal and double to 10 in the crystal stage with this os-

cillator circuit, because the 20-metre crystal appeared to be a 60-metre fundamental type which operated on its third harmonic. With this circuit, the 10-metre output apparently was the sixth harmonic of 60, and was too low to be usable.


For c.w. operation the transmitter may be keyed in the cathode of the crystal stage, or in any other conventional manner. If keyed in the crystal stage, the key should be in series with the r.f. choke and the following stages should be biased to cut-off with some source of fixed bias.

The 10-metre T20 and T55 plate coils should be wound as shown. The inductance of each should then be varied by compressing or expanding


the coils (reducing or increasing the spacing between turns) until resonance is achieved with the minimum amount of capacity in the circuit which will permit proper tuning. In other words, the highest L/C ratios possible are necessary for best efficiency. The coils for all other bands will be correct if duplicated mechanically.

All of the grounds for each stage should connect together and to the chassis at a common point near the mechanical centre for that stage to make all leads as short as possible. The chassis measures 10 x 17 x 3 inches, and the layout should follow that illustrated as closely as possible.

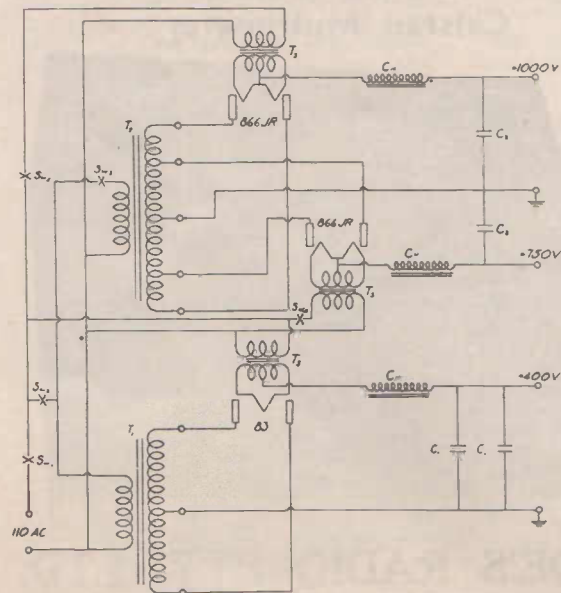The number of turns in the output coil coupled to L4 will depend upon



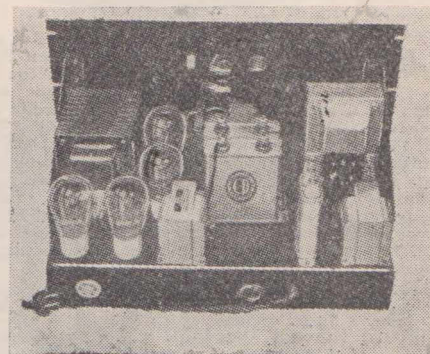Right: A view of the power supply rack (circuit on left), which is built on a steel chassis measuring 10 x 17 inches.



POWER SUPPLY.

- T1—400v. D.C. after filter, 150 m.a. or more; T2—1000v. and 750v. D.C. after filter, 250 m.a. or more; T3—5v. 3a.; CH—swinging input choke 150 m.a. or more; C1—4 mfd. 600v.; C2—2 mfd. 1500v.; X1, X2, X3, X4, X5, toggle switches.

the impedance of the feeders and the coupling method used. Coupling should always be to the cold end of the coil. All link coils coupled to L2 and L3 are one turn each.

The first two stages, the 6L6 and T20, make a satisfactory lower-power transmitter with an output of 40 to 45 watts from 20 to 160 metres and 15 to 20 watts output on 10. With suitable power supplies this would make an excellent portable transmitter. For 'phone work, the excitation to the T20 is sufficient for plate modulation.

AUDIO.

The speech amplifier shown was designed to have sufficient gain for any of the crystal microphones commonly used by amateurs, and to have enough power to drive any Taylor class "B" tube. In addition, the cost was kept as low as possible consistent with good performance, and all fancy circuit arrangements were avoided to assure best results with a minimum of complications.

6A3's were selected for use in the class "B" driver stage because low impedance triodes make the best class "B" drivers. Incidentally, pentodes and tubes with pentode characteristics such as 6L6's make the poorest class "B" drivers. The ideal class "B" driver tube would be a constant voltage tube. The 2A3 or 6A3 is the closest approach to a constant voltage tube available to the amateur today.

On the other hand, tubes with pentode characteristics are substantially constant current tubes, and are just exactly the opposite of what is necessary for best results. Where tubes of this type are used as drivers, it is common practice to load the driver tubes with resistance to improve the regulation. Such resistance, if used to improve voltage regulation, should be across the primary of the input transformer and not across the secondary. It is recommended that tubes be used with the correct characteristics for the job, rather than tubes be employed with inferior characteristics, and an attempt made to compensate for these deficiencies with degeneration or other methods.

Cathode bias is used, since the output is adequate with the tubes operating class "A," and therefore fixed bias is not necessary.


It was decided to use a push-pull 76 stage and a low ratio transformer ahead of the 6A3's, so that if under unusual conditions the grids of the driver stage were driven positive, the resulting distortion would be limited to that caused by bias shift only, instead of the far more serious distortion which would result if a high impedance class "A" input circuit were used.

The 6C6 and 76 furnish the desired amount of voltage gain. The filter

choke, decoupling resistors, and bypass condenser filter the plate supply so that even a fairly-high percentage of ripple in the power supply will not introduce hum in the amplifier.

The power supply voltage must be equal to the desired plate voltage, plus the bias voltage. A supply voltage of approximately 350 should be adequate.

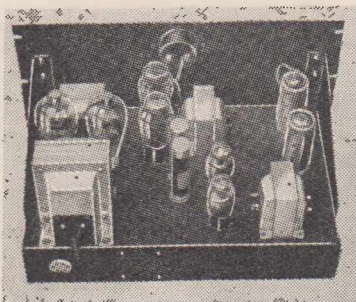The R.F. choke and C₁ are a filter to prevent R.F. from reaching the first grid. It invariably does so to an entirely satisfactory degree. Although a crystal microphone has high internal impedance, the .0001 mfd. condenser does not have any appreciable



A view of the modulator unit, which uses a pair of 6A3's in the class B driver stage, driving a pair of TZ20's.

effect on frequency response because of the characteristics of the microphone. If R.F. is still present another .0001 mfd. condenser from grid to ground of the second stage may help.

In the speech amplifier-driver, the 6A3's are capable of far more output than is necessary to drive a pair of TZ20's, but a large ratio of available power to required power is desirable for best results.

Many amateurs are under the impression that a low impedance line is necessary between the class "B" driver and the modulator if they are some distance apart. Actually, class "B" grids are of low impedance, and the grid leads may be extended the necessary distance in shielded wire. A properly designed class "B" input transformer will be built so that the coupling between windings will be as tight as possible, to keep leakage reactance at the absolute minimum. This is extremely important.

If two transformers are used with a low impedance line connecting them, the leakage reactance must necessarily be higher than if only one transformer of equal quality is used. Consequently the use of a low impedance line may result in inferior results. If the use of a low impedance line is essential, best design would be to put at least the driver stage with the modulator and use the line where the

design requirements are not as stringent.

Power Supply.

For the r.f. and modulator units three different voltages are necessary, 400 volts, 750 volts, and 1000 volts. The audio amplifier and crystal oscillator operate from the same 400-volt supply. Both the T20 buffer and TZ20 Class "B" stage operate at 750 volts, and the final stage at 1000 volts. In the smaller rack in which the transmitter was mounted originally, space was at a premium, and the largest chassis which could be accommodated was 10 x 17 inches. In addition, the height of the unit had to be kept to the absolute minimum. The 400-volt transformer is tapped for 400 or 500 volts at 175 m.a. The total drain for both speech amplifier and crystal stage is a maximum of about 150 m.a.

For the modulator, buffer, and final stage, one power transformer designed to deliver 750 and 1000 volts from the filter with choke input at a total of 250 m.a. is used to obtain both voltages. The final operates at 150 m.a., and the buffer at about 50 m.a. The no-signal plate current to the modulators is about 25 m.a. and swings to 60 or 70 m.a. for 100 per cent. modulation, so the average drain is about the maximum rating of the transformer.

The buffer could be operated from the 750-volt supply with the modulator, or from the 1000-volt supply through a dropping resistor. It was not operated from the 750-volt supply because of the inevitable fluctuation of voltage with change in modulator plate current. In the average amateur transmitter, the meters form the only method of checking performance, so the change in meter readings under modulation is extremely undesirable. As a result, the T20 buffer is operated from the 1000-volt final stage supply through a 5000 ohm 20-watt resistor. As a result all of the meters except those in the modulator plate and feeder stand still as they should under modulation.

Wherever possible, the Class "B" modulator power supply should not furnish power to any R.F. stage. If the same transformer is used for modulator and r.f., it is advisable to use separate filters for each. The same mercury vapor rectifier tubes may be used for both.

At the time this unit was built, no transformers to deliver 2.5 volts at 5 amps. for a pair of 866 Jr. were available. Because 5v. 3a. transformers for 83's are more reasonable than 2½ v. 10a. transformers for 866's, they were used. The 866 Jr. filaments are connected in series. This is entirely permissible if the centre tap of the winding is connected to the common connection between the two tubes.

What's New In Radio

A monthly review of latest releases
in sets, kit-sets, and components

Mr. R. K. Stokes Now Managing Director Radio Suppliers Pty.

Mr. Keith Stokes, well known for many years as Managing Director of Radiokes Pty. Ltd., advises that he will trade in future as Radio Suppliers Pty. Ltd. His Sydney address is Third Floor, Wingello House, Angel Place. Telephone B 4557.

The new company will continue to control the manufacture and distribution of all Radiokes products, and as well will also be handling the selling rights of certain raw materials in which many of the trade will be interested.

According to Mr. Stokes, this new arrangement will mean that very early in the New Year large stocks of all Radiokes lines will be available in all main centres throughout the Commonwealth. With the new company specialising entirely in sales, excellent service with immediate deliveries can be expected.

★

Three New Permags. By Rola

Rola (Aust.) Pty. Ltd. recently announced a new range of three


Rola permanent magnet speakers. These are known as the models 8-42, 10-42, and 12-42, and have overall dimensions of 8, 10 and 12 inches respectively.

These speakers embody the latest developments in permanent magnet assemblies, which include 42 ounce alnico magnets, providing a higher flux density in the air-gap than has ever before been attained in commercially produced loud-speakers in Australia.

This high flux density in conjunction with 1in. voice-coils and special moisture resisting diaphragms has resulted in speakers of high sensitivity that will give the utmost sound output from economical battery operated tubes, and weak distant programs.

The high flux density also makes possible an improved transient response so necessary for the clear intelligible reproduction of words and syllables, this is considered of the utmost importance to the country listener who relies on his radio for news, market reports, etc.

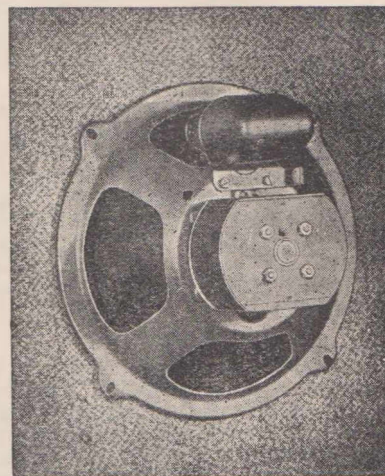Long and trouble-free service is assured due to the use of the well-known "Rola" patented methods of dust-proofing the vital working parts of the units. This is far more effective



The new Rola 10/42 permanent magnet model.

than the older method of enclosing the speakers in bags and has the added advantage that it does not impair the performance of the units.

The speakers are also fitted with "Rola" Isocore transformers which embody a combination of electrical and mechanical principles that are new to loud-speaker transformers and are designed to eliminate electrolysis. This valuable feature makes Isocore transformers especially suitable for humid climates when efficient trouble-free performance depends so much upon protection of such vital parts from moist atmospheric conditions.

In addition to their application to battery receivers these speakers will no doubt be found very desirable for public address installations where a high quality unit is desired, because

Make sure of
maximum efficiency
and longest life—

ADOPT AS YOUR
STANDARD—

Mullard

M A S T E R

RADIOVALVES

MULLARD (AUST.) PTY. LTD., 63-67 WILLIAM STREET, SYDNEY. 'PHONE: FL 5188 (3 lines)

apart from the fact that the field coil leads, which would be necessary in the case of electro-dynamic units, are dispensed with, a higher flux density is available in these units than is possible with similar electro-dynamic models.

The retail prices of these units are:

- Model 8/42 61/-
- Model 10/42 65/-
- Model 12/42 72/-

A point worthy of mention here is that these new speakers are ideal for use with receivers employing the new 1.4-volt valves. The larger of the output pentodes in this series has an output of 250 milliwatts. Though this is a fairly low figure, the extremely high efficiency of these new speakers enables more than sufficient volume to be obtained for all ordinary domestic purposes.



Raymart Variable Selectivity I.F.'s. Now Available

Up to the present it has been impossible to design a receiver which gives high fidelity reproduction, coupled with a high degree of selectivity when required, without incorporating expensive variable selectivity transformers with coils moved mechanically. The new Raymart i.f. transformer kit overcomes this by using the latest American development in this field.

It now becomes possible to obtain two band-widths at the flick of a switch, one giving full 9 k.c. acceptance and the other 2 k.c. acceptance only for reduction of interference. The iron core provides an extremely high i.f. gain, while the price is less expensive than that of many straight i.f. transformers.

A new line of Raymart air-trimmed i.f. transformers is also now available. These high "Q" transformers have latest pie windings of litz, treated to prevent moisture absorption. Their absolute stability makes them ideal for communications receivers.

Full details of these and other Raymart lines are obtainable free on request from Messrs. John Martin Pty. Ltd., 116-118 Clarence Street, Sydney. Incidentally, this firm has just announced their appointment as distributors for the well-known American United transmitting valves. The following types are available from stock:—303A, 305D, 310, 311, 311T, 342B, 914, 911CH, 930, 930B, 938, 941, 942, 945, 949, 952, 966, 966A and 972A.



In "Radiotronics" No. 92.

The release of Radiotron 813—a beam power tetrode for transmitting purposes—is announced in the latest issue of "Radiotronics" (Technical Bulletin No. 92), published by A. W. Valve Co. Pty. Ltd.

Having a maximum plate dissipation of 100 watts, the 813 is in class "C" telegraphy capable of an output of 260 watts, while as a plate-modulated amplifier it may be used to give a carrier output of 175 watts.

A further article (re-printed elsewhere in this issue) gives details of the new 6K8G converter, and discusses its use in a typical six-valve circuit.

Other articles include "Calculation of Grid Bias for Resistance-Coupled Amplifiers," and "Low Voltage Operation of Radiotron 913—a Trouble and Its Cure."


It is also announced that limited stocks of the new 1.4 volt series valves are expected early in December. Incidentally, a receiver using these valves will be described shortly in "Radio World."

A new metal-envelope series of valves has also been announced, in which the grid connection normally taken to the top cap is taken to one of the base pins. This series comprises the 6SF5 high-mu triode, 6SJ7 r.f. pentode, 6SK7 super control r.f. pentode, and 6SQ7 duo-diode high-mu triode. These valves have applications similar to those of types 6F5, 6J7, 6K7, and 6Q7, the addition of the "S" being to indicate the single-ended construction.



Vidor "Show Boat" Portable

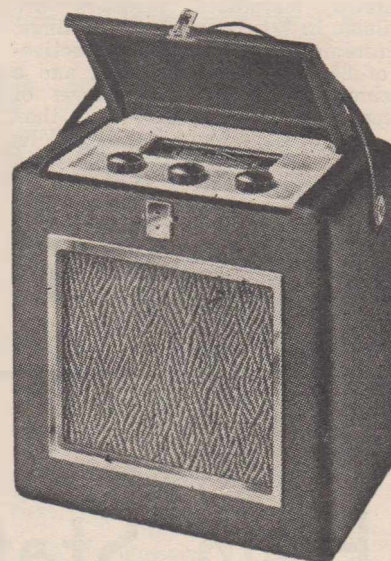Illustrated below is the new Vidor "Show Boat" portable radio briefly reviewed in last month's "Radio World." A four-valve broadcast superhet, it is extremely compact, measuring only 11½ x 10½ x 7 inches



overall, and weighing only 20lbs. complete with batteries.

This portable is handled in New Zealand by Messrs. F. J. W. Fear & Co., of 31 Willis Street, Wellington, from whom further details are available free on request.



Eight-Page IRC Resistor Catalogue

Perhaps the widest range of fixed and adjustable resistors carried in any one make in Australia is the LRC range, handled by W. J. McLellan & Co., of Bradbury House, 55 York Street, Sydney. Type "BT"



RADIOKES

The Name Known to Radio

The trade will be interested to know that full supplies of the popular RADIOKES lines are now available through Radio Suppliers Pty., Ltd., Wingello House, Angel Place, Sydney. The distribution is under the personal direction of Mr. Keith Stokes, who will ensure that all items are up to the famous RADIOKES standard.

Enquiries are also solicited for raw materials.

RADIO SUPPLIERS Pty. Ltd.
WINGELLO HOUSE, ANGEL PLACE, SYDNEY. B 4557

insulated metallised resistors are available in ½-, 1- and 2-watt ratings, with minimum resistances, respectively, of 250, 500 and 750 ohms, and a maximum resistance in all cases of 20 megohms. For ranges lower than the minimums quoted, types BW½, BW1 and F2 can be supplied.

Other IRC resistors available for special applications are the type "WW" multipliers and shunts, type "M" motor noise suppressors, and the power wirewound resistors in ratings ranging from 5 to 200 watts, and de-

signed to fulfil all radio, industrial and electrical requirements.

Types of IRC resistors available, with complete characteristics, are listed and illustrated in an 8-page catalogue that is available, free and post free, to "Radio World" readers from the address given above.

★

New Ever Ready Calendar

The reputation that the Ever Ready Co. (Aust.) Pty. Ltd. has built up

over recent years for artistic calendar productions is fully maintained for 1939 by the particularly striking design reproduced in miniature below.

Printed by the offset process in natural colours, and depicting a typically Australian girl against a background of sunshine and surf, there is no doubt that it will be received by the trade as enthusiastically as its predecessors.

Over 7000 of these calendars will be mailed to radio and electrical retailers in Australia during December.

A Plain Statement Of Fact

TO THE THOUSANDS OF HOLDERS
OF COMMONWEALTH BONDS MA-
TURING IN DECEMBER, 1938.

The Australian Loan Council invites all holders of Commonwealth Inscribed Stock and Bonds maturing on 15th December, 1938, to convert their holdings.

The interest rate on the new Loan is 3% per cent. Price of Issue, Par. Repayable in 1954, the Treasurer reserves the option of redeeming the Loan on or after 15th December, 1952.

Cash may be invested in this new Loan and will be employed for urgent Defence purposes to the extent of £4,000,000, and for paying off those who are unable to convert their present holdings.

Applications may be lodged with any Bank, Savings Bank, Money Order Post Office, or member of a recognised Australian Stock Exchange.

LOAN CONVERSION

Commonwealth Treasury,
Canberra, A.C.T.

R. G. CASEY,
Treasurer.



★

New N.Z. Technical Radio Mag.

The first issue of a new technical radio magazine—"Fear's Radio Review"—is now off the press, and is being distributed free to set-builders and amateur transmitters throughout New Zealand.

The first issue contains complete constructional details, with photographs, of a five-band 'phone and c.w. transmitter, covering from 10 to 160 metres. Details are also given, with prices, of latest American lines.

Messrs. F. J. W. Fear & Co. advise that this issue is presented to readers with the assurance that it is merely an introductory number. It is hoped to make succeeding issues more attractive—of double and treble the number of pages, and with a much wider variety of constructional articles.

Readers wishing to obtain this and future issues free of charge are invited to forward their names and ad-



GIVE RADIO and ELECTRICAL GIFTS THIS XMAS

Write for a copy of Vealls Big Xmas Gift Folder, illustrating dozens of radio and electrical lines suitable for Xmas gifts—gifts that last a lifetime and act as a daily reminder of the good taste of the giver.

ELECTRIC CYCLE LIGHTING OUTFITS from 9/11

Complete outfits, generator, headlamp and tail lamp, 9/11. Other heavier duty types up to 32/6. Spare headlamps, 9/9; twin chrome headlamps, 17/6; tail lamps, 3/9.

MORSE KEYS & SOUNDERS

Solidly constructed brass sounders, English made. Usually 35/-. Special Xmas Price, 17/6, or complete with key and battery, 40/-.
MORSE KEYS, 12/6, 15/6, 19/6 and 37/6. Ultra High-tone BUZZERS, 5/9.

GILBERT ELECTRIC DRILLS

Gilbert B144 light-duty type. Takes 0-1/4" drills, 52/6; also the Gilbert Senior for radio mechanics and light workshop use, £5/12/6.

DIORA "PANTONOS" GRAMO UNITS

Complete gramo unit, comprising silent running A.C./D.C. motor complete with Diora Pick-up and Volume Control. Usually £7/2/6. Special Xmas Price, 72/6

1/4 H.P. ELECTRIC MOTORS

For home workshops, lathes, etc. Economical (only 2.5 amps) and powerful. 230-volt, 50-cycle, split phase. 1425 revs. per minute. Repulsion start. Price only 99/6.

ELECTRIC APPLIANCES

Household Electrical Irons, 12/6 each; Electric Toasters, 17/6; Electric Grillers, 34/6; Boiling Water Jugs, 17/6; Reading Lamps, 12/6.

The 1939 SKY-KING Dual Wave 5

Build the Sky-King Dual Wave A.C. 5 described in this issue. Experience the thrills of all Australian and overseas reception. Look at the price and remember, Vealls supply the complete kit, including valves and speaker, at no extra cost. Get the habit—try Vealls first.

Complete Kit £12-15-0

SEE FULL CONSTRUCTIONAL DETAILS ELSEWHERE IN THIS ISSUE.

ENJOY REAL SHAVING COMFORT - with a "SCHICK"

Over 2,000,000 men are enjoying the comfort of dry shaving. No soap, no water, no brush, no nicks or cuts. Buy a Schick—the pioneer dryshaver—the

best that money can buy. Priced at only £5/10/- cash or on Easy Terms. Write for free literature, learn what the Schick can do—for you.

ARTHUR J. VEALL PTY. LTD.

EVERYTHING RADIO AND ELECTRICAL.

490 Elizabeth St., Melbourne. F 3145.
168 Swanston St., Melbourne. C 10524.
3-5 Riversdale Rd., Camberwell. W 1188.

243 Swanston St., Melbourne. C 3059.
299 Chapel St., Prahran. Wind. 1605.
99 Puckle St., Moonee Ponds. FU 7822.

ADDRESS ALL CORRESPONDENCE TO BOX 2135T, G.P.O., MELBOURNE.

dresses to Messrs. F. J. W. Fear & Co., 31 Willis Street, Wellington, N.Z. ★

Philips "Chair-side" Radioplayer Has Many Striking Features

Lately there have been quite a few departures from the conventional in radio receiver design, but few of



Philips Model 1362 "Chair-side" Radioplayer.

these have proved such a qualified success as the Philips Radioplayer "Chair-side" model 1362, submitted recently to "Radio World" for test.

The design, construction, and finish throughout both receiver and cabinet are excellent, the general appearance as shown in the illustration above being most attractive.

While primarily designed for placing alongside a lounge chair, the 1362 can equally well be located against the wall, as with the more

conventional console. The four controls—tone, tuning, volume and wave-change—are located along one edge of the cabinet, of which the centre portion is recessed to accommodate a sheet of plate glass.

The tuning dial is the well-known Philips "Twilight," carrying zoned broadcast calibrations and shortwave calibrations over the band from 13.5 to 43 metres. The dial, which is of the edgelit type, has a scale measuring approximately 8in. x 6in., the pointer moving through 270 degrees.

Valves used in the chassis comprise one 6D6 r.f. amplifier, one EK2 octode frequency converter, one 6D6 i.f. amplifier, one 75 second detector, a.v.c. rectifier and audio amplifier, one EL3 high gain output pentode with inverse feedback, and one 80 rectifier.

Separate Power Pack Unit.

Considerable amount of attention has been paid to ensuring permanence of alignment of the coil assembly. Another noteworthy feature is the chassis assembly and mounting that has been evolved to suit the cabinet employed. The main receiver chassis is vertical, and when the cabinet back is removed the under-chassis wiring is exposed, a detail that should greatly facilitate any service adjustments. The power pack is mounted on a separate chassis located at some distance from the receiver proper, and is joined to the latter by a four-wire cable.

As might be expected from the valve line-up, and from the obvious care that has been taken in the engineering of this receiver, its performance is exceptional. Sensitivity is high and noise level low, resulting in an unusually good effective sensitivity. As well, both selectivity and stability are of a high standard, while the quality of reproduction obtained (the output pentode employs the well-known Philips "audioscopic" system of inverse feedback), is comparable with that obtainable from a receiver using power triode output.

Bright Xmas Souvenir Issue Of "Vesta Vamp"

The "Vesta Vamp," published monthly by Vesta Battery Pty. Ltd., is well known throughout the radio trade as one of the brightest and most informative of house organs in Australia. The Christmas number just published is a special souvenir issue planned to commemorate the tenth birthday of the organisation.

The Vesta company commenced operations ten years ago as a two-man business in a shed in Sydney, and its phenomenal growth is illustrated in the centre two-page spread of this latest issue of the "Vamp." Here the ramifications of the company are shown on a map of Australia and New Zealand, the portraits of branch managers and key executives being included in the localities where they operate.

Wrapped around this central feature is an enlarged "Vesta Vamp," built up with special features appropriate to a Christmas souvenir issue designed for permanent reference. Jokes, cartoons, and a fine Christmas story strike the seasonal note, while as well there are articles on the growth of the company, and dealing with Vesta products and policy.

Altogether, the admirable combination of workmanlike advertising and publicity features, with lively entertainment items and artistic production, in this special issue of the "Vamp" make it a rare and highly successful one. It should be certain to achieve the results aimed at by the progressive organisation which has proposed it.

★

New Ever-Ready Managing Director

Mr. Albert Jewell has been appointed managing director of the Ever Ready Co. (Aust.) Pty. Ltd. as from November 17, in lieu of Mr. R. P. Walter, who resigned on that date.

★

Acorn Shift To New Premises

Acorn Pressed Metal Pty. Ltd. announce that during the Christmas holidays their business will be transferred from the present address to larger and more convenient premises situated in Marshall Street, Surrey Hills (phone FL 5191).

★

"Schick" Shaver Has Exclusive Patented Head.

Amid the increasing number of electric dry shavers appearing on the Australian market, there are only one or two shavers with sufficient organisation and experience behind them to really ensure the buyer of a guaranteed time-tested product.

Colonel Schick, the inventor of the Schick dry shaver, spent more than

RADIO TEXT BOOKS — PRICES SLAUGHTERED

	Sale Price.	Usual Price.	Postage.
Jones Radio Handbook, 1937	3/6	9/6	9d.
Jones Radio Handbook, 1938	5/-	8/6	9d.
A.R.R.L. Handbook (Q.S.T.), 1938 ..	5/-	7/6	10d.
A.R.R.L. Handbook (Q.S.T.), 1937 ..	3/9	7/6	10d.
Jones Ultra H/F	1/9	3/9	3d.
Jones Amateur Radiotelephony ..	3/6	5/-	3d.
Jones Antenna Handbook	1/9	3/9	3d.

Approximately 50 copies only of each—Rush your order.

McGill's Agency

183-185 ELIZABETH STREET, MELBOURNE. Cent. 8113-8114.

twenty years in study and experiment with skin, hair and shaving, and developed literally dozens of shearing heads (the most important part of the electric shaver) before he evolved the shearing head now embodied in Schick shavers.

After putting in hand the patents on the shearing head, machines and methods were found to produce Schick shavers in large quantities, and now after seven years of successful marketing there are 2,000,000 Schick shavers in use all over the world.

★

Maynard Homerecorder Unit.

Messrs. John Martin Pty. Ltd., of 116-118 Clarence Street, Sydney, an-

nounce that they have been appointed distributors for the Maynard Homerecorder unit which is illustrated overleaf, mounted on the motorboard of a compact radiogram combination.

This new recording unit has a high impedance cutting head, and can be connected to any radio receiver employing either single or push-pull output valves. In the first case, one lead from the cutting head is connected to the plate through a 1 mfd. condenser, and the other is connected to earth, while in the case of push-pull output, a lead is connected to each of the two plates through a .5 mfd. condenser.

The unit is particularly simple to

mount and operate, and gives very successful results. An important feature is that the angle of cutting head is adjustable to any desired degree.

Larger models for cutting up to 12in. and 17¼in. records are also available, with a range of recording blanks in diameters extending from 6in. to 17¼in. Other accessories carried include a variety of cutting heads, and steel, sapphire, and diamond cutting needles.

Full details of the complete range of Maynard recording equipment are available free on request from Messrs. John Martin Pty. Ltd. at the address given above.



QUALITY!

THERE'S nothing old-fashioned about S.T.C. design or appearance — for modern engineering has kept S.T.C. Headphones in step with modern development. But S.T.C. still insists on the old-fashioned idea that "good enough" is not good enough. You can depend upon S.T.C. to be enough better than the letter of the specification to provide a safe margin of performance ability. S.T.C. competes with all comers in terms of what you get in headphone value.

Standard Telephones and Cables Pty. Limited

258-274 Botany Road, Alexandria, N.S.W.

DISTRIBUTORS THROUGHOUT AUSTRALIA & NEW ZEALAND

NEW SOUTH WALES: Standard Telephones and Cables Pty. Ltd., 258-274 Botany Rd., Alexandria.

S.T.C. Radio Sales and Service, 389 Hunter St., Newcastle.

Wagga Wireless Distributors, Fitzmaurice St., Wagga.

QUEENSLAND: Edgar V. Hudson Pty. Ltd., 284 Edward St., Brisbane, Townsville, Cairns, Warwick, and Rock-

hampton.

Fields Cycles, Mackay.

VICTORIA: Standard Telephones and Cables Pty. Ltd.,

Bourke St., Melbourne.

Noyes Bros. (Melb.) Pty. Ltd., 597-603 Lonsdale St., Melb.

SOUTH AUSTRALIA: Lenroc Ltd., 211-215 Pulteney St., Adelaide.


WESTERN AUSTRALIA: M. J. Bateman Ltd., 12 Milligan St., Perth.

TASMANIA: W. & G. Genders Pty. Ltd., 69 Liverpool St., Hobart; 53 Cameron St., Launceston; also Burnie.

NEW ZEALAND: Standard Telephones and Cables Pty.

Ltd., Auckland, P.O. Box 1897; Wellington, P.O. Box

638; Christchurch, P.O. Box 983.

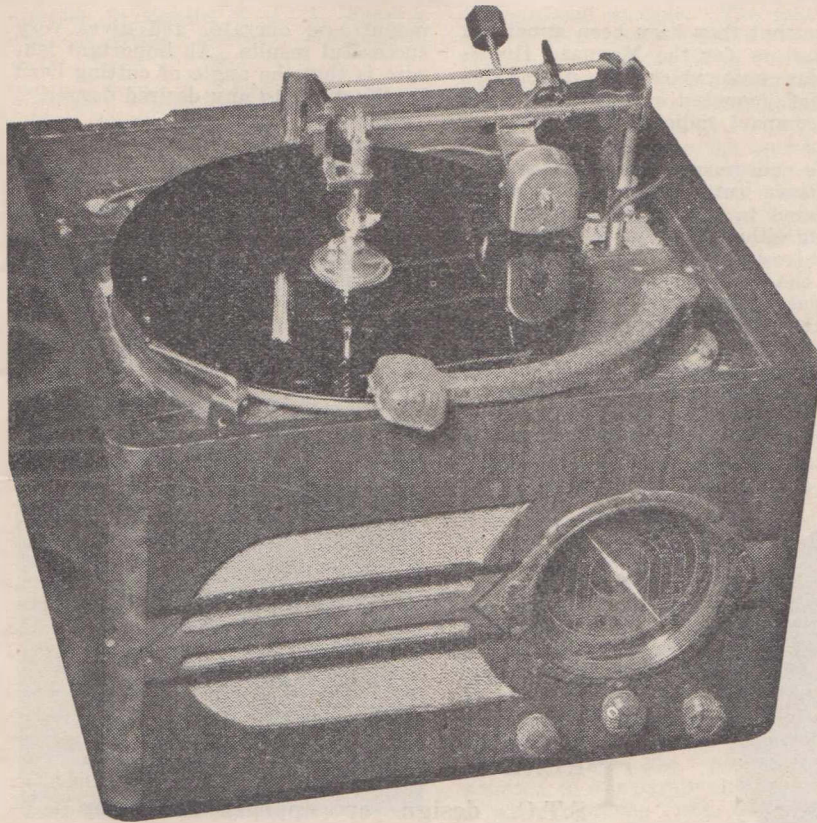

The Maynard home recording unit (reviewed on the previous page) is shown here mounted on the motor-board of a compact table model radiogram.

VK2ME, 3ME And 6ME — Schedules For December

The following transmission schedules will be observed by shortwave stations VK2ME, VK3ME and VK-6ME during December.

VK2ME (31.28 m., 9590 k.c.).
 Sydney Time. G.M.T.
 Sundays: 4-6 p.m. 0600-0800
 8 p.m.-midnight. 1000-1400
 Mondays: Midnight-2 a.m. 1400-1600

VK3ME (31.5 m., 9510 k.c.)
 Melbourne Time. G.M.T.
 Nightly
 Monday to 7 p.m.-10 p.m. 0900-1200
 Saturday (inclusive)

VK6ME, Perth (31.28 m., 9590 k.c.).
 Perth Time. G.M.T.
 Nightly
 Monday to 7 p.m.-9 p.m. 1100-1300
 Saturday (inclusive)

Home Recording

(Continued from page 22.)

of the stylus may be considerably impeded by the mass of thread.

Except for the rare pre-grooved type, all discs require some form of mechanical control over the cutting head so that the stylus may be moved sideways over the surface of the blank, the spiral groove thus formed beginning at the outside of the disc and finishing at a point about 2½" from the centre.

It may well be noted, however, that is reversed, and is done from the inside of the blank towards the edge. It is claimed that in these machines the thread collects itself around the centre, and also that the play-back pick-up will stay in the final groove and will not run over the record as it may in the edge-started type.

The head is generally moved sideways by a threaded rod, which may be driven in various ways—directly by the motor, from the edge of the disc, or from the centre of the spindle. Whatever system is used, no slip is permissible, as any speed variation will cause an off-frequency effect which is particularly noticeable in recordings consisting mainly of single


instruments or voices.

Most direct recorders are arranged to cut about 80 to 90 grooves to the inch at the standard turntable speed of 78 r.p.m., although many will also cut the larger discs (16") at 33½ r.p.m.

Enlarged sketches of a steel cutting stylus are shown in "A" and "B," while "C" and "D" show corresponding views of a typical sapphire stylus.

At the slower speed a much longer playing time is available, although many troubles may be encountered, and the enthusiast would be well advised to master the 78 r.p.m. speed first.

(To be continued next month)

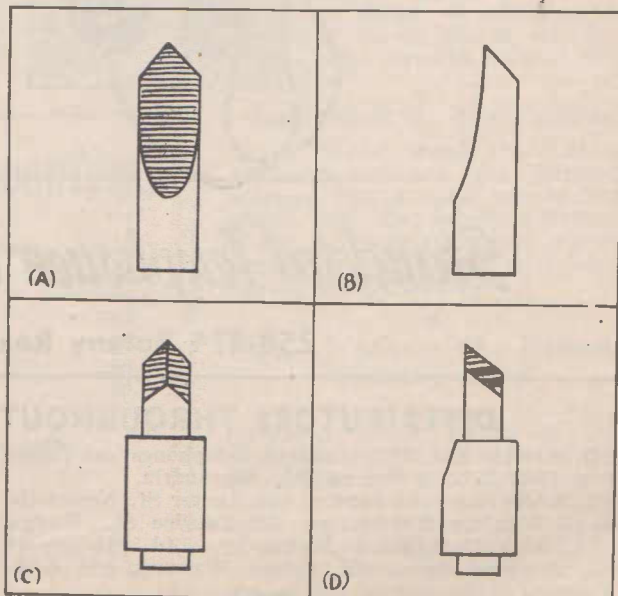




The All-Wave All-World

Official Organ of the
All-Wave All-World DX Club

DX News

 

QSL Exchange Bureau.

The following readers would like to exchange QSL cards with members of the DX Club:—

Leonard D. Hubbard, 17 Patten Road, London, S.W.18, England.

Oscar Westman, 24 Lawrence Road, Maitland, Cope Town, South Africa.

Ben Follrath, 1419 Pearl Street, Alameda, California, U.S.A.

Emily Griswold, 326 No. Main, West Hartford, Connecticut, U.S.A.

Malcolm N. Wicks, "Elmsdale," Balhannah, South Australia.

O. G. Washfold (AW257DX), 59 Radnor Street, Camberwell, E.6, Melbourne, Victoria; O. D. Marks (AW-428DX), 30 Scott Street, South Fremantle, Western Australia.

Mrs. M. M. Anselme (AW307DX), B. Christofferson (AW361DX), Poole Messrs. G. M. Anselme (AW250DX), 16 Hartley Street, Rozelle, Sydney; 16 Hartley Street, Rozelle, Sydney; Street, Bowen, Nth. Queensland.

Syd. E. Molen (AW213DX), Box 8, Kingaroy, Queensland.

Mr. F. J. Rooke (AW429DX), c/- G.P.O., Box 219, Fremantle, W.A.

Mr. R. E. Lee Hunt, 1105 N., Harman Avenue, Danville, Illinois, U.S.A.

Mr. F. Bluett (AW167DX), P.O. Box 8, Midhirst, Taranaki, New Zealand, writes that owing to illness some SWL's did not receive his card. He now has a new card and QRA's would be appreciated.

Mr. B. Christofferson (AW361DX) advises that his new QRA is C/- Garbutt's Flats, Stoke Street, Townsville, Queensland.

DX Notes And News

304 New Loggings In Two Months.

During October and November I logged 304 s.w. stations: 201 VK's, 35 W's, 30 K6's, KA1AP, KA1AT, KA1JM, VR6AY, GSO, PCJ, FIQA, TPA2, LV4BC, PK2AY, PK2WL, PKDJJ, K7FFT, VEQFI, G2AI, JZK, VU3AR, ZL4BK and others.

I have just received a veri. in the form of a letter from Radio Tananarive, Madagascar. Their frequency is shown as 6063 k.c., and it appears as

if their call sign is not FIQA but TSF. The letter was written on October 7, and bears the Chief Engineer's signature.

My receiver is a two-tube a.c. using a 6C6 impedance coupled to a 6F6 in the final. The antenna is a 1/2-wave 20-metre. — D. Newton, Castlemaine, Victoria.

Amateur Verie. From Indo-China.

Verifications lately received are from Hawaii Isles, U.S.A., Peru and Indo-China, the latter being from Rene Lebon, Box 13, Hanoi. He is the operator of F18AC. There are only a few amateurs in Indo-China, so details of his station should be of interest. Receiver H.R.O., transmitter being four-stage crystal-controlled 50 watts input to final, and the antenna

half-wave Zepp. With this rig F18AC has worked 93 countries, 36 zones and W.A.C.

Reports were sent this month to Argentine, Chile, Fed. States of Malay, British New Guinea, Hawaii, U.S.A., Dutch Indies and Japan, but South Africa is still the "dark continent" as far as my locality is concerned. Loggings this month include K6's LKN, ILW, MTP, DTT, OGN, GQF, K5AF, KGU, W6LYY, W6MYD, W2FAM, KA1JN, J2MI, PK6XX, VK9WL and dozens of VK's. No November 20, RNE, Moscow, came in at the most perfect reception I have yet heard—QSA 5, R max., modulation perfect, and for a wonder no QRM, QRN or QSB.—Gordon Young (AW-245DX), Brisbane, Queensland.

ALL-WAVE ALL-WORLD DX CLUB

Application for Membership

The Secretary,
All-Wave All-World DX Club,
214 George Street,
Sydney, N.S.W.

Dear Sir,

I am very interested in dxing, and am keen to join your Club. The details you require are given below:

Name.....

Address.....

[Please print both plainly.].....

My set is a.....

[Give make or type, number of valves, and state whether battery or mains operated.].....

I enclose herewith the Life Membership fee of 3/6 [Postal Notes or Money Order], for which I will receive, post free, a Club badge and a Membership Certificate showing my Official Club Number.

(Signed).....

[Note: Readers who do not want to mutilate their copies of the "Radio World" by cutting out this form can write out the details required.]



Short-wave Review

CONDUCTED BY
ALAN H. GRAHAM

Ultra-High-Frequency Conditions Good ★ 11 Metre Stations At Good Strength ★ All The Latest Information Regarding New Stations And Schedules ★ Reports From Observers In All States ★ Tuning Guide.

Interesting Month On U.H.F. Bands.
—8.4m. Station Logged.

A feature of reception during the past month has been the splendid reception conditions on the U.H.F. bands. This has been more especially the case with the 11-metre band, on which good signals have been audible on most mornings. The two latest stations to be logged are W9XA and W2XJI. W9XA, located in Kansas City (c/- Commercial Radio Equipment Co.), operates on 11.33 m., and has been putting in a very strong signal at times. W2XJI (Bamberger Broadcasting Service, 1440 Broadway, New York) has only been heard once, on December 3, and on this occasion signals were not very strong, and were a trifle difficult to follow. Other 11 m. loggings include the following:—W9XJL, 11.49 m.; W9XUP, 11.56 m.; and W9XAZ, 11.36 m.

The 9.49 m. channel has not been so interesting, signals failing to come up to expectations. Only W9XPD, St. Louis, has been worth logging.

However, in the last week of November, a really interesting catch was logged on 35,000 k.c., or 8.4 m.—the highest frequency broadcaster reported in this country to our knowledge. This was station W9XUY, Omaha, Nebraska. This station was heard from 10 a.m. till noon at R4-5.

It is reported that there are three new transmitters on the 11 m. band. These are W8XNU, Cincinnati, 25,950 k.c., 11.56 m. (same freq. as W6XKG and W9XUP); W2XKI, Newark, 26,300 k.c., 11.4 m.; and W3XEX, Norfolk, 26,005 k.c., 11.53 m. As yet we have been unable to check the authenticity of this report.

The police bands have been very poor. This is probably on account of the reorganisation of the police transmitters which was hinted at in these columns previously. It is now believed that police transmissions will be conducted on a cross-band system with headquarters stations on 175 or 125 metres, and the mobile transmitters on 8 metres. Just at present a few isolated signals are to be heard on the old 9 metre bands, amongst them being Newark, now using the call WQIE.



Latest Overseas Station Information.

Austria.

OER-2, 49.4 m., and OER-3, 25.4 m., are still on the air relaying programmes from Reichsender Wein. It is also reported that two new transmitters are planned—OER-4, 31.35 m., and OER-5, 19.75 m. All these stations will be using a power of 50 k.w.

Call.	Location.	Old Freq. & W/L.	New Freq. & W/L
HJ7ABD	—Bucaramanga	9630 .. 31.14	4815 .. 62.29
HJ1ABP	—Cartagena	9616 .. 31.20	4805 .. 62.41
HJ6ABH	—Armenia	9520 .. 31.51	4875 .. 61.48
HJ6ABB	—Manizales	6105 .. 49.16	4855 .. 61.8
HJ3ABX	—Bogota	6013 .. 49.8	4795 .. 62.5
HJ5ABD	—Cali	6085 .. 49.3	4825 .. 62.2
HJ3ABH	—Bogota	4900 .. 61.19	4895 .. 61.25
HJ4ABP	—Medellin	4880 .. 61.44	4885 .. 61.38
HJ3ABD	—Bogota	4841 .. 61.95	4845 .. 61.92
HJ7ABE	—Bucaramanga	4820 .. 62.24	4775 .. 62.82
HJ1ABE	—Cartagena	4800 .. 62.46	4835 .. 62.03
HJ1ABB	—Barranquilla	4780 .. 62.72	4785 .. 62.66
HJ2ABJ	—Santa Marta	4660 .. 64.3	4865 .. 61.6

Bechuanaland.

ZNB, 50.84 m., has adopted a new schedule—4-5.30 a.m. QRA is P.O. Box 106, Mafeking.

Burma.

Radio Burma, Rangoon, now transmits simultaneously on 49.9 and 80.6 m. Latest schedules are: Daily exc. Monday, 10.15-1 a.m. and 1-2.30 p.m.; Mondays, 1-2.30 p.m. Power 1-2k.w. At the present moment no call sign has been allotted, although an application has been made to the Bern Bureau for the use of XYZ and XZZ.

Chile.

CB1180, Santiago, operated by the Sociedad Nacional de Agricultura, has been testing in preparation for a change of frequency. At present it is being reported on 25.47 and 25.0 m. All reports verified—there is no need to include an IRC. QRA is Casilla 40-D.

CB946, 31.71 m., will soon go on the air at Santiago. Will be known as "Radio Basquedano." Operated by Markoff Bros. Ltd.

CB1174, Santiago, 25.55 m., is another Chilean station recently reported on the air. Operated by Orlan dini and Taggio Ltd., it uses a power of 1k.w.

CB1190, Valdivia, has shifted from, 11900 k.c. to 11,910 k.c., to eliminate QRM from XEW1.

Colombia.

The gradual process of transferring the Colombian transmitters to the 60 m. band is nearing its completion. The latest list available lists the following frequency shifts:—

The following stations are not included in the above list, and it is not known if they are to be changed to 60 m. frequencies, if they are to leave the air, or remain as shown.

Call.	Location.	Freq.	W/L.
HJU	Buenaventura	9510	31.55
HKV	Bogota	8795	34.1
HJ4ABU	Medellin	8650	34.7
HJ4ABE	Medellin	6145	48.79
HJ3ABF	Bogota	6070	49.42
HJ6ABR	Pereira	6054	49.52
HJ1ABG	Barranquilla	6042	49.65
HJ1ABC	Quibdo	6000	50.0
HJ2ABC	Cucuta	4790	62.59
HJ6ABC	Ibaque	4740	63.25

HJ7EAB, Bucaramanga, is a new transmitter on 63.3 m. It relays **HJ7EAK**, signing at 1.10 p.m.

HJ7ABB, Bucaramanga, is another newcomer, relaying **HJ7ABA**. This station, "Radio Santander," operates on 62.8 m. QRA is Apartado 37.

Costa Rica.

TIEMC, the new station referred to last month, is reported to be operating on 48.87 m., and not 29.8 m. as previously stated.

TI2RS, "Radioemisora Athena," 40.2 m., is the latest Costa Rican. It is on the air daily except Monday from 12.30-2 p.m.

Cuba.

COCM, Habana, has been wandering all over the dial—quite a common characteristic of Cuban stations. Listed on 30.41 m. (9865 k.c.), it has been reported recently on 8780, 9820 and 9855 k.c., or 34.1, 30.5 and 30.44 m.

Dominican Republic.

HIG, Ciudad Trujillo, states that it now operates on 32.29 and 47.67 m. Power 150 watts. Schedule extended one hour, station now closing at 12.40 p.m.

S.W. stations relaying **HIX**, Ciudad Trujillo, are **H13X**, 17.2 m., **H11X**, 47.32 m., **H12X**, 25.08 m., and **H13X**, 19.63 m. **H13X** is not on a regular schedule, being used only for special broadcasts.

Note the following seldom-listed Dominican stations: **H15E**, 31.41 m., Ciudad Trujillo; **H15P**, 45.7 m., Puerto Plata; **H16H**, 45.3 m., Ciudad Trujillo; and **H15G**, 45.1 m., La Vega.

Denmark.

Denmark is being heard on a new frequency near 17,930 k.c., 16.7 m. Copenhagen has been heard over **OZH**, **OZG** and **OZF**.

Ecuador.

HCJB now has a wide range of frequencies. Usually it operates on 33.5 and 72.99 m. It also transmits religious programmes on 48.13 m., 41.4 m., 24.1 m., and 20.8 m. These latter broadcasts are made at irregular intervals.

HC2CW, Guayaquil, has changed frequency from 9280 to 9300 k.c. Address is P.O. Box 1166.

Ethiopia.

The latest frequency on which Addis Ababa is operating is 9520 k.c., 31.51 m. Heard from 4-6 a.m.

Fiji Islands.

VPD, Suva, has added a number of new wavelengths. In addition, its power is up to 10 k.w. Watch for it on 19.79, 25.22 and 48.94 m.

Guatemala.

TGWB, Guatemala City, 46.2 m., is a new relay station for **TGWA**.

TG2X, Guatemala City, 50.47 m., is reported off the air.

TG-2, Guatemala City, has shifted to 48.48 m.

TGS has completed a long period of testing, and is now carrying out a regular schedule on 51.81 and 25.9 m.

Haiti.

HH2S, Port-au-Prince, has shifted to 50.4 m. Schedule is from 10 a.m.-1 p.m. daily except Monday. From 11.30 a.m.-12.45 p.m. the programme is entirely in English.

Hungary.

HAS-6, Budapest, 13.8 m., is a new station in this country.

Switzerland.

Switzerland now has a short-wave broadcasting station and therefore will not need to transmit its overseas programmes over the League of Nations' stations. The new station is in charge of the Director-General of Posts and Telegraphs, Radio Division, at Bern. At present experimental broadcasts are being carried out

on 31.46 m. from 4-5 a.m. (except Mondays and Tuesdays). In addition it is thought that 19.53 and 25.27 m. channels are being tested. No identification signals are employed, and as yet no call letters have been assigned. Power is about 300 watts.

Lithuania.

Information from the Chief of Radio Section, Director-General of Posts and Telegraphs, Kaunas, Lithuania, indicates that irregular tests are being conducted over **LYR** on 32.2 m.

It is believed that four new stations are being planned—**LYZ**, 48.98 m.; **LYZ-2**, 31.5 m.; **LYZ-3**, 25.21 m.; and **LYZ-4**, 19.61 m.

Mexico.

XEGW is the new call of the station previously known as **XEPW**, 49.1 m.

XEW1 has increased its power on 25.2 m. Also uses 49.84 m. allocation on occasions.

New Zealand.

ZL2ZB testing on 43.1 m. is being heard well. Address is Hope Gibbons Building, Dixon Street, Wellington C1.

New transmitters to be installed at Wellington with the calls **ZLT 1** to **6** inclusive will operate on 49.3 m., 31.45 m., 25.47 m., 19.63 m., 16.88 m., and 11.6 m., respectively.

Paraguay.

ZP-14, Villarrica, is now transmitting on 49.8 m. Is on the air from 5-8 a.m. Tuesdays and Thursdays,

Have Your "RADIO WORLD" Posted To You Direct

Readers who want to take the "Radio World" on a subscription basis and have their copies posted to them direct each month are invited to complete the coupon below (annual sub. 10/6). New readers are advised that all back numbers in Volumes 1 and 2 are still available, price 9d., post free for copies in Volume 1 (May 1936 to April 1937) and 1/-, post free, for copies in Volume 2 (May 1937 to April 1938).

Enclosed please find remittance for 10/6, in payment for an annual subscription to the "Australasian Radio World," commencing with the..... issue.

Name.....

Street and No.....

City..... State.....

Country.....

Note.—N.Z. Subscribers can remit by Money Order or Postal Note.

THE AUSTRALASIAN RADIO WORLD,
214 George Street, Sydney,
N.S.W., Australia.

and 2-8 a.m. Sundays and Mondays. Known as "Radio Cultura."

Spain.

Radio Nacional, Salamanca, key station of the Nationalist network is relayed by EHZ, Tenerife, on 28.93. (N.B.—Call is definitely EHZ, not EAJ43 as sometimes thought, as the Tenerife station is not a broadcasting station, but a radio telephone transmitter used for relay purposes.) The Salamanca programme is relayed by a large number of 40 m. transmitters located chiefly at Valladolid.

Turkey.

Radio Ankara on 31 m. now uses the call TAO, as also does the 19 m. transmitter.

United States.

A new 11-metre station is W9XH, South Bend, Ind., relaying WSBT/WFAM on 11.3 m.

Los Angeles will soon have another 9.49 transmitter. The CBS station W10XE at Boston will be transferred to the West Coast.

W3XAL will use new allocations on 31.02 and 13.9 m. at once.

Venezuela.

Following is the very latest list of Venezuelan stations available.

Call.	Location.	Wavelength. (metres)
YVQ	—Caracas	44.95
YV4RB	—Valencia	45.98
YV1RN	—Maracaibo	46.13
YV6RC	—Ciudad Bolivar	46.73
YV5RH	—Caracas	46.88
YV5RF	—Caracas	46.99
YV1RH	—Maracaibo	47.19
YV4RD	—Maracay	47.62
YV5RP	—Caracas	47.79
YV5RJ	—Caracas	47.88
YV1RG	—Valera	48.13
YV1RI	—Coro	48.28
YV5RC	—Caracas	50.27
YV1RL	—Maracaibo	50.52
YV4RE	—Valencia	50.71
YV3RA	—Barquisimeto	51.0
YV1RB	—Maracaibo	51.3
YV5RR	—Caracas	51.4
YV1RE	—Maracaibo	51.46
YV5RM	—Caracas	59.9
YV6RU	—Ciudad Bolivar	61.44
YV2RN	—San Cristobal	61.55
YV3RN	—Barquisimeto	62.24

Reports From Observers

Mr. A. R. Payten (Coff's Harbour, N.S.W.).

Although there is nothing really startling to report this month, conditions are certainly better than they have been, despite the fact that QRN is nearly always troublesome in this locality. Generally speaking, there has been a definite improvement on the 16 and 19 m. bands, and an equally definite falling off on 49-50 m.

Interesting loggings of the month include the following. On 31.3 m. a description from Philadelphia of a

football match between Army and Navy was logged at good strength (QSA5, R9). This was heard on November 27 between 5 and 6.50 a.m. The match was played in the snow, before a crowd estimated at 102,000. After 6.55 a.m. signals faded rapidly and no station announcements were heard, but the station would almost certainly be W3XAU.

Also Radio Ankara, TAO, on 31.7 m.; DZC, 29.16 m., and DZB, 29.87 m.; and Vatican City, HVJ, on 49.75 and 19.83 m.

Following are the regular broadcast stations heard:—

- 16 m.: W3XAL (improving daily), GSG and DJE.
 - 19 m.: JVF, W2XE, YDB, GSI, GSO, DJQ, HVJ, GSF and RKI.
 - 25 m.: VLR-3, OLR4A, JZJ, GSD, DJD.
 - 27 m.: PLP, CSW-2.
 - 28-29 m.: JVN, PMN, DZC, DZB.
 - 30 m.: EAQ, COCM, COCQ.
 - 31 m.: 2RO, PCJ, 2ME, VLR, W3XAU, JZI, HS8PJ.
 - 44 m.: PMH.
 - 49 m.: Vatican City, HVJ.
- Amateur loggings between 4 and 5 a.m., and during the early evenings

Slogan.

- "Radiodifusora del Gobierno Nacional"
- "La Voz de Carabobo"
- "Radio Maracaibo"
- "Radio Bolivar"
- "Ondas Populares"
- "La Voz de Venezuela"
- "Ondas del Lago"
- "La Voz de Aragua"
- "La Voz de la Philco"
- "La Voz de la Esfera"
- "Radio Valera"
- "Radio Coro"
- "Radio Caracas"
- "Radio Popular"
- "Radio Valencia"
- "La Voz de Lara"
- "Ecos del Zulia"
- "Estudios Universo"
- "Radiodifusora Maracaibo"
- "Radiodifusora Venezuela"
- "Ecos del Orinoco"
- "La Voz del Tachira"
- "Radio Barquisimeto"

include the following on 20 m.: F8XT, ZS6EB, VQ4KTB, PK6XX (Portable), OA4AI, FB8AD, J2MI, KA1JP, KA1ME, K6OQE, K6DTT, ZS6EO, and TI2FC.

Mr. J. Ferrier (Coleraine, Victoria).

UHF DX has been only fair this month except for one or two days when 10 m. was really good. 11 m. has been fairly good, much better than 9 m.

The amateur band, as mentioned above, was quite good on one or two days. Following are the best loggings:—

Canada: VE- 5VO, 4BF, 4LO, 5AEZ and 5GQ.

Southern Rhodesia: ZE- 1JZ.

Burma: XZ- 2EZ.

Europe: HB9CZ (Switzerland), ON4ZA (Belgium), G- 8MA, 8JV, 6KI., 2IS, 6LL, 6WX (England).

Egypt: SU- 1MW, 1RO.

D.E.I.: PK- 2WL, 1VY.

Philippine Is.: FA1ER (15 watts).

Hong Kong: VS6AO.

(Splendid DX, OM, 10 countries listed on 10 m. phone.—S.W. Ed.)

Mr. W. H. Pepin (Maylands, West Australia).

For a few weeks DX reception has improved on all bands, although QRN has been more troublesome than is usual, extending down as far as 13 m.; whilst above 50 m. reception of even the very strongest signals is all but impossible.

13 m.: GSJ and GSH are the best stations, the former being much the better of the two.

14-15 m.: In this area several good phone stations have been logged:

KAX, 14.01 m., phoning Tokyo; JVA, 15.7 m., phoning Bandoeng; and PLE, 15.9 m., phoning Tokyo.

16 m.: DJE and GSG. Also on 16.87 an American which I believe to be W3XL and not W3XAL. Heard from 7 a.m.-mid-day (Perth time), with frequent announcements in several languages.

19 m.: The usual regulars; also an unknown Hawaiian station on this band around 10 a.m. one Sunday.

25 m.: DJD, GSD, TPA-4, W8XX and JZJ.

27-29 m.: PLP and PMN put in really remarkable signals—remarkable for both strength and clarity.

31 m.: Band has been marred by exceptionally high noise-level at night. In the mornings GSC, GSB, and COCX are best.

The amateur bands are just fair. 10 m. phone loggings include W6MKF, W6GCX, W6LSO, W6ITH, XZ2EZ, PK2WL, VK2GU and VK2HF.

On 20 m.: PK4HS, KA7HB, CO7CX and PK1TT.


Mr. J. K. Sorensen (Gympie, Qld.).

Back in Gympie again, and able to settle down to some DX work. Have found conditions very different. Just at present there are many stations audible during the afternoons, but conditions are poor in the early evenings, only the Australians, JVN and Daventry.

QRN is very heavy and practically prevents any listening on the lower frequencies.

ZLT-1 has been heard a number of times in the early afternoon phoning Sydney and London.

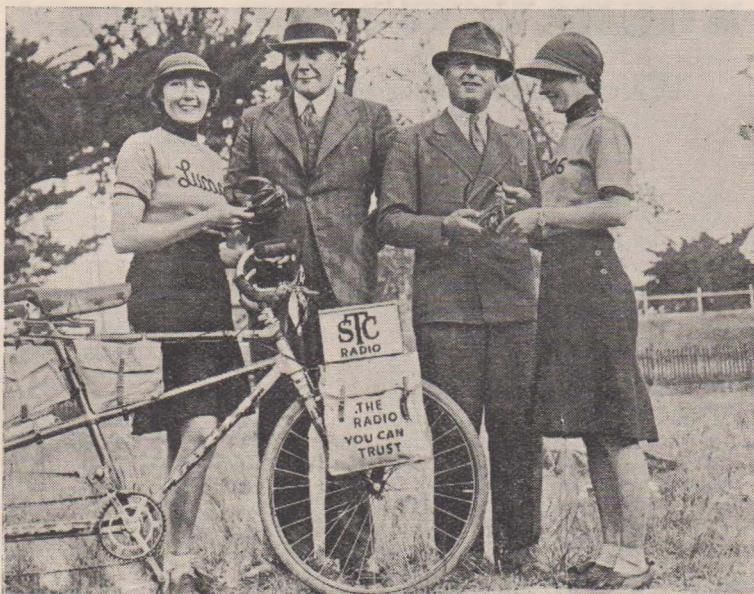On 25 m. of a daytime VLR-3 is very strong, putting in much stronger signals than are heard from the 31 m. transmitter at night.



In happy mood, the Tandem Girls, who have averaged over 100 miles a day on their record-breaking return ride from Sydney to Perth, are here seen with Mr. Tom Court, S.T.C.'s designs engineer (left), Mr. Reg. Mills, S.T.C.'s radio manager in Victoria—and a pair of the new S.T.C. headphones.

The amateur bands are poor; on 20 m. only a few W's and K6's.

Mr. J. C. Linehan (Adelaide, South Australia).

Since writing you last regarding my new antenna (2½ waves in phase, 16ft. 1½ins. aside, feeders 8ft. long and spaced 6ins.) I have found that it gives very satisfactory results when only a ½-wave high—i.e., 36ft. As a matter of fact it is practically as good at that height as it is at 68ft. high, the only difference being that the noise-level is slightly less at the latter height. I have just started work on yet another antenna—a rotary beam using a W8JK beam—this will take some time to complete and will probably not be in use till next year.

DX conditions have not been very good this last month, especially above 40 m., where the noise-level has been exceptionally high. Running through the various bands, I have found the 25 and 31 m. bands very good in the mornings until 8 a.m., when they fade out very rapidly; 10 and 11 m. have been very poor; 13 m. good from 9.30 p.m. till midnight, with GSJ strong; 16 m. only fair; 20 m. very erratic until midnight when a fair number of Europeans and Indians can be logged; 25 m. good from 10 p.m., with CR7BH very good from midnight till 1.15 a.m.; on 31 m. the noise-level has been very high in the early part of the evenings, although later KZRM and VUD are good.

Best amateur loggings are listed below:—

5 metres: VK5JT, VK5LX and VK5HM.

10 metres: ZL1HY, ZL1AJ, J3FJ, KA1ER, W6NWK (portable on board the M.S. "City of Dalhart," 800 miles N.E. of N.Z.), K6LCV, W1HJO, W9FAA, W9DRG, CO2WM.

20 metres: CN1AF, CR7AU, VS2AG, YV4AO, YV5ABQ, VP6TR, VP6R, SU1RD, SU1JM, SU1MW, F18AC, PK6XX, PK4KS, VK9XX, VU2FU, VU2HQ, KA7EF, F8XT, F3JP, G6JL, PAOMZ, OA4AI, HC1FG, VE5AGI.

Mr. C. Anderson (Dumbleyung, West Australia).

Conditions have varied a good deal during the last month. During the last week or so bad QRM has greatly interfered with reception during the afternoons and evenings.

A recent verification from "Radjo Martinique" was a very FB card. No call letters were given. QRA is Box 136, Fort-de-France.

An Italian phone station, IQA, on 20.27 m., was a new logging; as also was W3XAL, using one of their new frequencies on 31.1 m.

An interesting amateur heard this month on 20 m. was PK1RL, using only 4 watts, and putting in a steady R7 signal.

Loggings:—

13 metres: GSJ, GSH and W8XK.

16 metres: GSG, W3XL (not W3XAL), PHI-2, DJE.

17 metres: FZE-8.

19 metres: HAS-3, W2XAD, TPA-2, OLR5A, PCJ-2, W8XK, TGWA, TPB-6, HVJ.

20 metres: IQA, HBJ, DZH.

25 metres: RNE, Saigon (25.2), VLR-3, W8XK, OLR4A, W2XE, 2RO, W1XAL, OLR4B, COCX, TPA-4, Saigon (25.6).

26-30 metres: HBO, CSW (27.27), PLP, PMN, JVN.

31 metres: COBC, JDY, COCM, EAQ, IRF, CSW, COCQ, 2RO, W3XAL, ZHP, ZRK, VUD-3, KZRM, W3XAU, W1XK, W2XAF, HS8PJ, ZBW-3, COCH, HAT-4, KZIB.

39-44 metres: JVP, HBQ, PMH.

49 metres: ZRK, VQ7LO, W8XAL, 9MI, Rangoon, ZRH.

58 metres: PMY.

62 metres: VUD-2, VUM-2, VUC-2, VUB-2.

20-metre amateurs logged are:—

Philippines: KA- 1AF, 1AP, 1ER, 1CS, 1CW, 1ME, 1JM, 2OV, 7EF.

D.E.I.: PK- 1MJ, 1RL, 1VY, 2WL, 3WI, 4KS, 6XX, 6CI, 2AY.

China: XU- 8ET, 8RB, 9W.

Japan: J- 2NF, 2MI.

Indo-China: FI- 8AC.

Hong Kong: VS- 6AG.

India: VU- 2CA, 2CQ, 2BG, 2HQ, 2FU.

Federated Malay States: VS- 2AP, 2AG, 2AJ.

Ceylon: VS- 7GJ.

Burma: XZ- 2DY, 2JB.

Hawaii: K6- MVA, GAS, LKN, OJI, ILW, BNR, DLL, NFY, KGA, OFW, NYD.

Cuba: CO- 2RH, 2JJ, 6OM, 7CX, 2RR, 2WM.

Costa Rica: TI- 2RC, 3AV.

Canal Zone: K5- OF.

Argentine: LU- 4BC.

Great Britain: G- 2TR, 2XN, 2DS, 5DT, 5GO, 5ZG, 6DT, 6WX, 8NJ.

France: F- 8DC, 8XN, 8XL.

Holland: PA- OMZ.

South Africa: ZS- 2X, 4H, 5AB, 5BK, 6CZ, 6DW, 6DY, 6EJ.

Northern Rhodesia: VQ2HC.

★

SWL Card Exchangers' Section

This month we are again including in these columns a list of overseas listeners who are interested in the exchange of SWL cards. All the persons mentioned in these lists guarantee 100 per cent. QSL.

Lewis Sakurada, Box 14, Lanakai, Hawaii; Harold La Pierre, 124 Maithland Street, Halifax, Canada; Sydney Lashley, Box 252, Bridgetown, Barbados, B.W.I.; John Greenbank, 28 Chelmer Street, Oamaru, N.Z.; Peter Koelmans, Zijde, 144, Boskoop, Holland; Dick Merlehan, 5 Valentia Pde., Dublin, Ireland; B. W. T. Cockcroft, "Wanganui," 8 Whetebriidge Road, Onchan, Isle of Man; Doug. C. Johnson, 169 Covurg Road, Halifax, Canada; Meredith Stroth, 172 Queen St., Kitchener, Canada; Maurice L. Hunt, 16 Princess Street, Knutsford, Cheshire, England; George Ludkin, Group D Co., Beachley Camp, Chepstow, England; B. Pearsall, Mount Carmel Cottage, Carmel, near Holywell, North Wales; Ronald Burt, 101 Railway Cottages, Salt River, Capetown, South Africa; Wm. Buchanan, 189 Park Street, Sydney, Canada; George Poulain, 67 Mt. Pleasant Street, Syd-

ney, Canada; John W. Sledge, Jr., 201 West 4th Street, Cisco, Texas, U.S.A.; Hubert L. Martz, Holabird Q.M. Depot, Baltimore, Maryland, U.S.A.; Bill McMullin, 1421 Highland Avenue, Bluefield, W. Va., U.S.A.; Joe Scott, 1718 Berkshire Place, Toledo, Ohio, U.S.A.; H. Bowers, 19 Hubbard Street, Concord, Mass., U.S.A.

On The Ham Bands

More regarding that old question: the "ham" v. SWL controversy. In a current American publication appeared the following extract from a letter of verification received from W9—: "I wish you boys would not send along SWL cards, for I receive so many that I cannot possibly answer them all. Not that I am hard-boiled or anything of that sort, but I simply do not have the time to make them out, and also the expense is quite heavy."

We feel that the above sums up very succinctly the attitude of a good number of amateurs. Possibly SWL's would do well to carry out the following suggestions:—(1) Send only reports which you feel will be of some real interest to the "ham" concerned; (2) always include return postage—strange as it seems there are still SWL's who feel injured if they receive no QSL following a failure to include a reply coupon or unused stamps with their report.

Just at present the ham bands are just fair. 20 m. is not too good at all, and with summer conditions with us we can expect a further falling off. On the other hand, 10 m. should continue to provide something of interest. A glance at Observer Ferrier's report will indicate that there are thrills for even the most blasé DX-er on this band. VE, ZE1, XZ, HB, ON, G, SU, PK, KA and VS6 on 10 m. phone is surely a good month's work. And remember, too, that it is much easier to obtain a QSL for a report on 10 m. signals. From personal experience we can say that 80-90 per cent. of your reports will be acknowledged.

6K8-G Converter

(Continued from page 20.)

Consequently, in connection with this receiver, which may be regarded as a typical one, the total frequency drift due to A.V.C. and other effects is plotted against aerial input voltage for the receiver as a whole. On the diagram are shown two curves giving the upper and lower limits of individual 6K8-G valves and any Radiotron 6K8-G should be within these limits. It will be seen that the upper limit is +2.5 k.c. and the lower limit -1.8 k.c. For the purposes of comparison the curve for an average 6A8-G is shown and the improvement due to the use of the 6K8-G is evident. These curves were taken at a frequency of 18.6 megacycles.

HOURLY TUNING GUIDE

When and Where To Search

Compiled by ALAN H. GRAHAM.

In order to assist beginners and less experienced dxers, it is intended to publish monthly a special tuning guide, setting out at what times to listen for the more easily logged stations. It should be noted that the guide is not intended to cover all stations audible; for full details as to when and where to look for the best catches are given elsewhere. Moreover, the fact that a station is shown as being on the air at a particular time is no guarantee that reception must follow as a matter of course.

All times are given in Australian Eastern Standard Time.

Key to abbreviations used: S, Sundays only; M, Mondays only; T, Tuesdays only; W, Wednesdays only; Th, Thursdays only; Sat, Saturdays only.

Midnight-1 a.m.		1-2 a.m.	
13.93	GSJ	13.93	GSJ
13.97	GSH	13.97	GSH
13.99	DJS	13.99	DJS
16.86	GSG	16.23	HBH (M)
16.89	DJE	16.86	GSG
19.63	DJQ	16.89	DJE
19.68	TPA-2	19.63	DJQ
19.7	OLR5A	19.68	TPA-2
	(exc. M, S)	19.7	OLR5A
19.74	DJB	19.74	DJB
19.76	GSO	19.76	GSO
19.8	YDC	19.8	YDC
19.82	GSF	19.82	GSF
25.29	GSE	19.84	HVJ
25.34	OLR4A	19.85	DJL
	(exc. M, S)	25.0	RNE
25.4	2RO-4	25.24	TPA-3
25.42	ZJZ	25.29	GSE
25.53	GSD	25.4	2RO-4
27.27	PLP	25.34	OLR4A
28.48	JIB		(exc. S, M)
29.24	PMN	25.49	DJD
30.78	COCQ	25.53	GSD
30.96	ZHP	27.27	PLP
31.28	VK2ME	28.48	JIB
	(M)	29.24	PMN
31.3	VUD	31.3	VUD
31.38	DJA	31.35	TPB-11
31.49	ZBW-3	48.7	VPB
31.55	HS8PJ	49.83	DJB
	(F)	49.9	COCO
31.58	XEWW	58.3	PMY
31.8	COCH	60.0	VUD
32.9	COCB	60.6	VUM
33.2	COBZ	61.4	VUC
39.95	JVP	70.2	RV15
48.7	VPB		2-3 a.m.
49.9	COCO	13.93	GSJ
49.98	Rangoon	13.97	GSH
58.3	PMY	16.23	HBH (M)
60.0	VUD	19.71	PCJ (Th)
60.6	VUM	19.74	DJB (M)
61.4	VUC	19.76	GSO
70.2	RV15	19.82	GSF
98.6	YDA		

19.85	DJL	25.42	JZJ
25.24	TPA-2	25.48	DJD
25.29	GSE	25.53	GSD
25.4	2RO-4	27.17	CSW
25.49	DJD	28.93	EAJ43
25.53	GSD	29.04	ORK
31.3	VUD	31.13	2RO-3
31.35	TPB-11	31.28	PCJ
48.7	VPB		(M, T, W)
49.31	VQ7LO	31.35	TPB-11
49.83	DJC	31.46	JZI
60.0	VUD	31.55	GSB
60.6	VUM	39.95	JVP
61.4	VUC	49.1	GSL
		44.94	HBQ (M)
		49.59	GSA
		49.83	DJC
	3-4 a.m.		
16.86	GSG		6-7 a.m.
19.71	PCJ (Th)		GSG
19.85	DJL	16.86	GSG
25.24	TPA-3	16.87	W3XAL
25.49	DJD	19.56	W2XAD
25.53	GSD	19.62	GSP
31.13	2RO-3	19.65	W2XE
31.35	TPB-11	19.67	W1XAL
31.55	GSB	19.72	W8XK
49.1	GSL	19.85	DJL
49.31	VQ7LO	22.0	SPW
49.59	GSA		(T, Th, Sat.)
49.83	DJC	25.0	RNE
60.0	VUD	25.24	TPA-3
60.6	VUM	25.34	OLR4A
61.4	VUC	25.49	DJD
		25.53	GSD
	4-5 a.m.	27.17	CSW
19.62	GSP	30.4	EAQ
19.65	W2XE	31.13	2RO-3
16.86	GSG	31.28	PCJ (W)
19.71	PCJ (Th)	31.28	W3XAU
19.85	DJL	31.35	W1XK
20.64	HBJ (M)	31.35	TPB-11
24.52	TFJ	31.55	GSB
25.24	TPA-3	40.83	DJC
25.49	DJD	43.1	2ZB
25.53	GSD	49.1	GSL
29.04	ORK	49.59	GSA
31.13	2RO-3		
31.3	VUD		7-8 a.m.
31.35	TPB-11	19.56	W2XAD
31.55	GSB	19.65	W2XE
44.94	HBQ (M)	19.72	W8XK
49.1	GSL	19.7	OLR5A
49.31	VQ7LO		(W)
49.59	GSA	19.76	GSO
49.83	DJC	19.82	GSF
		19.85	DJL
	5-6 a.m.	25.0	RNE
16.86	GSG	25.24	TPA-3
16.87	W3XAL	25.34	OLR4A
19.56	W2XAD	25.42	JZJ
19.6	GSP	25.45	W1XAL
19.65	W2XE	25.49	DJD
19.67	W1XAL	25.53	GSD
19.72	W8XK	27.17	CSW
19.85	DJL	30.4	EAQ
20.64	HBJ (M)	31.09	CS2WA
22.0	SPW	31.13	2RO-3
	(T, Th, Sat)	31.28	W3XAU
24.52	TFJ	31.32	GSC
25.24	TPA-3	31.35	TPB
25.34	OLR4A		

31.35 KZRM	31.35 W1XK	25.42 DJZ	7-8 p.m.	31.55 VK3ME	60.0 VUD
31.35 W1XK	31.38 DJA	25.49 DJD	13.99 DJS	34.0 VPD3	60.6 VUM
31.41 OLR3A	31.45 DJN	25.53 GSD	16.86 GSG	43.1 2ZB	61.4 VUC
(T)	31.49 LKJ1	25.61 TPA4	16.89 DJE	44.64 PMH	70.2 RV15
31.46 JZI	31.48 W2XAF	31.28 PCJ (F)	19.63 DJQ	48.7 VPB	
31.48 W2XAF	31.55 GSB	31.32 GSC	19.66 GSI	49.5 W8XAL	11 p.m.-midnight.
31.55 GSB	38.48 HBP (S)	31.38 DJA	19.71 PCJ (Th)	58.3 PMY	13.93 GSJ
43.1 2GB	49.1 GSL	31.48 W2XAF	19.74 DJB	70.2 RV15	13.97 GSH
49.83 DJC		31.55 GSB	19.76 GSF		16.86 GSG
49.92 OLR2A	10-11 a.m.		25.29 GSE	10-11 p.m.	16.88 PHI
(Th, F)			25.52 GSD	13.93 GSJ	16.89 DJE
58.31 OK1MPT	19.56 DJR	2-3 p.m.	25.57 Saigon	13.97 GSH	19.56 DJR
	19.63 DJQ	25.53 GSD	28.14 JVN	13.99 DJS	19.63 DJQ
	19.7 OLR5A	25.61 TPA4	31.38 DJA	16.86 GSG	19.68 TPA2
8-9 a.m.	19.74 DJB	31.32 GSC	31.49 ZBW3	16.88 PHI	19.74 DJB
	19.76 GSO	31.48 W2XAF	31.55 VK3ME	16.89 DJE	19.79 JZK
19.56 DJR	19.8 YDC	31.53 GSB		19.58 OLR5B	19.8 YDC
19.63 DJQ	19.85 DJL			19.63 DJQ	19.82 GSF
19.65 W2XE	25.26 W8XK	3-4 p.m.	8-9 p.m.	19.68 TPA2	19.85 DJL
19.7 OLR5A	25.34 OLR4A	13.99 DJS	13.93 GSJ	19.7 OLR5A	25.29 GSE
(M, S)	25.4 DJZ	16.89 DJE	13.97 GSH	19.74 DJB	25.4 2RO4
19.72 W8XK	25.49 DJD	19.63 DJQ	13.99 DJS	19.8 YDC	25.42 JZJ
19.74 DJB	25.53 GSD	19.74 DJB	16.86 GSG	19.82 GSF	27.27 PLP
19.76 GSO	25.61 TPA4	19.79 JZK	16.89 DJE	19.85 DJI (S)	29.24 PMN
19.82 GSF	26.31 HBO (M)	19.85 DJL	19.63 DJQ	25.29 GSE	30.61 XGOX
25.0 RNE	29.15 DZC	30.04 COBC	19.68 TPA2	25.42 2RO4	30.78 COCQ
25.24 TPA-3	31.13 2RO3	31.28 VK2ME	19.71 PCJ2	25.42 JZJ	30.9 ZHP
25.34 OLR4A	31.25 RAN	(S)	(Sun)	25.57 Saigon	30.96 ZHP
(M, S)	31.28 PCJ	31.38 DJA	19.74 DJB	25.65 HP5A	31.28 VK2ME
25.42 JZJ	(M, T, F)	32.15 OAX4J	19.8 YDC	27.27 PLP	(S)
25.45 W1XAL	31.32 GSC	32.59 COBX	19.82 GSF	28.14 JVN	31.3 VUD
25.49 DJD	31.38 DJA	33.26 COBZ	25.29 GSE	29.24 PMN	31.35 W1XK
25.53 GSD	31.45 DJN	49.18 W3XAL	25.4 2RO4	30.23 JDY	31.38 OAX4T
25.60 TPA4	31.48 W2XAF	49.5 W8XAL	25.57 Saigon	30.61 XGOX	31.38 DJA
28.9 EAJ43	31.49 LKJ1		27.27 PLP	30.78 COCQ	31.49 ZBW3
30.04 COBC	31.55 GSB	4-5 p.m.	28.14 JVN	30.96 ZHP	31.51 HS8PJ
30.31 CSW	49.1 GSL	13.99 DJS	29.24 PMN	31.28 VK6ME	(Th)
30.4 COCM		16.89 DJE	30.96 ZHP	31.28 VK2ME	31.8 COCH
30.43 EAQ	11 a.m.-noon.	19.63 DJQ	31.28 VK2ME	(S)	32.09 COBC
30.7 COCQ		19.74 DJB	(S)	31.3 VUD	32.59 COBX
31.06 LRX	19.56 DJR	19.79 JZK	31.38 DJA	31.35 W1XK	33.2 COBZ
31.09 CS2WA	19.6 GSP	19.85 DJL	31.45 VPD2	31.38 DJA	39.95 JVP
31.13 2RO3	19.63 DJQ	20.64 HBJ (M)	31.49 ZBW3	31.49 ZBW3	44.64 PMH
31.27 HBL (S)	19.7 OLR5A	25.24 TPA3	31.55 VK3ME	31.8 COCH	48.7 VPB
31.28 W3XAU	19.74 DJB	26.31 HBO (M)	34.0 VPD3	32.09 COBC	49.5 W8XAL
31.32 GSC	25.26 W2XK	31.28 VK2ME	43.1 2ZB	32.59 COBX	49.9 COCO
31.35 KZRM	25.42 DJZ	31.35 TPB-11	44.64 PMH	44.64 PMH	49.96 HP5K
31.35 W1XK	25.42 JZJ	31.38 DJA	70.2 RV15	46.8 TIPG	49.98 Rangoon
31.45 DJN	25.49 DJD	49.5 W8XAL		48.7 VPB	58.3 PMY
31.46 JZI	25.53 GSD		9-10 p.m.	49.5 W8XAL	60.0 VUD
31.48 W2XAF	25.61 TPA4		13.93 GSJ	49.96 HPSK	60.6 VUM
31.49 LKJ1	31.13 2RO3	5-6 p.m.	13.97 GSH	49.98 Rangoon	61.4 VUC
31.55 GSB	31.25 RAN	13.99 DJS	13.99 DJS	58.3 PMY	70.2 RV15
31.58 XEWW	31.28 PCJ	19.63 DJQ	16.89 DJE		
31.8 COCH	(M, T, Th, F)	19.74 DJB	19.58 OLR5B		
38.48 HBP (S)	31.32 GSC	25.23 TPA3	19.63 DJQ		
	31.38 DJA	28.14 JVN	19.63 TPA2		
9-10 a.m.	31.45 DJN	31.28 VK2ME	19.7 OLR5A		
19.56 DJR	31.48 W2XAF	(S)	19.71 PCJ (W)		
19.56 W2XAD	31.55 GSB	31.35 TPB-11	19.74 DJB		
19.63 DJQ		31.38 DJA	19.8 YDC		
19.7 OLR5A	Noon-1 p.m.		19.82 GSF		
19.72 W8XK	19.56 DJR	6-7 p.m.	19.85 DJL (S)		
19.74 DJB	19.71 PCJ (W)	13.99 DJS	25.0 RNE (W)		
19.76 GSO	19.74 DJB	16.86 GSG	25.4 2RO4		
19.8 YDC	25.26 W8XK	16.89 DJE	25.29 GSE		
22.0 SPW	25.42 DJZ	19.31 PCJ (Th)	25.57 Saigon		
25.34 OLR4A	25.49 DJD	19.63 DJQ	27.27 PLP		
25.42 JZJ	25.53 GSD	19.66 GSI	28.14 JVN		
25.45 W1XAL	25.60 TPA4	19.74 DJB	29.24 PMN		
25.49 DJD	31.28 PCJ (F)	19.76 GSO	30.23 JDY		
25.51 OLR4B	31.32 GSC	19.82 GSF	30.61 XGOX		
25.53 GSD	31.38 DJA	25.23 TPA3	30.96 ZHP		
25.61 TPA4	31.48 W2XAF	25.29 GSE	31.23 VK2ME		
30.31 CSW	31.55 GSB	25.52 GSD	(S)		
31.06 LRX		28.14 JVN	31.28 VK6ME		
31.09 CS2WA	1-2 p.m.	31.28 VK2ME	31.38 DJA		
31.13 2RO3	19.56 DJR	(S)	31.45 VPD2		
31.27 HBL (S)	19.74 DJB	31.38 DJA	31.49 ZBW3		
31.32 GSC					

"C" And "R" Checker

(Continued from page 8.)

No provision is made for the balancing of the smaller condensers. It is generally enough to observe whether the sample under test (providing it is not defective) gives a reasonably sharp balance at the "null" point.

In the largest size of condenser, however, most of those now used are electrolytic types, and at low frequencies have a relatively large power factor which is not necessarily a reason for rejection. At the same time it should not be too large. Some show a power factor of less than 5 per cent. and are acceptable; others show 30 per cent. or more and cannot be recommended.

The adjustment to exact balance when the power factor or loss factor

is appreciable is done by the 2500-ohm rheostat.

Operational Hints.

In making a measurement, the component to be measured is connected across the "res. cap." terminals and the range switch set to what is believed to be the nearest value.

In all probability the screen of the 6E5 will be completely fluorescent, but if the potentiometer is turned a point is reached at which the "eye" opens to a clearly defined angle. If by careful adjustment, the edges of this pattern cannot be made dead sharp, the power factor of the component must be different from that of the standard. On the largest capacity range this can be cleared up by the power factor control.

If the balance falls outside the readings ".1 to 10" on the ratio scale, a better result will be obtained on another range. If the balance is obtained only at one extreme limit of the potentiometer adjustment, the component must be open-circuited or short-circuited, or at any rate substantially so in relation to the range in use. A 10 mfd. condenser would appear a dead short if tested on the 100 mmfd. range.

When measuring condensers on the 100 mmfd. range, the same sharpness of balance must not be expected as on the higher ranges. It is not that balance is not dead sharp—assuming that the power factor is not exceptionally bad, balance is quite good—but a larger movement of the ratio control is required in order to show an appreciable change in the indicator pattern. The best way is to swing the knob to and fro between positions each side of balance until the exact point can be judged. With this particular instrument measurements can be made as low as 5 mmfd., while the readings around 100 mmfd. are remarkably accurate.

Provision For Matching.

A useful feature is the position marked "Match." For example, it might be necessary to adjust a number of components to the same value or to check their departures from standard. This is available for inductances of not less than 1 henry. Push-pull transformers can be tested for balance in windings.

The leakage and continuity test utilises a Philips neon—the lowest available voltage lamp should be used. When a condenser is connected, the lamp flashes momentarily due to charging, and in a dim light this should be perceptible down to .05 mfd.

If the condenser is a good one it may be necessary to wait quite a while

"1939 SKY-KING DUAL-WAVE FIVE" LIST OF PARTS

1 steel chassis 15" x 9½" x 3", stamped and drilled to specifications (Acorn)	1 50,000 " " "
1 power transformer, 80 mill. 5v. 2a., 6.3v. 2a., 385v., C.T. 385v.	3 .1 megohm " "
1 D.W. coil kit, 2 465 k.c. iron-core I.F.'s. (Foxradio)	1 .25 " " "
1 2-gang condenser (Stromberg-Carlson)	1 .5 " " "
1 dial (Efco)	3 1 " " "
4 knobs	1 1.5 " " "
3 valve shields	
5 octal wafer sockets	
1 4-pin speaker socket	
4 terminals, 2 red, 2 black (Dalton)	
1 power socket and plug	
1 power cable and plug	
3 midjet grid clips	
1 .5 megohm potentiometer (Microhm)	
1 25,000 ohm voltage divider	
1 D.P./D.T. rotary type toggle switch (or 1 6 x 2 single-deck Yaxley switch)	

FIXED RESISTORS:

1 220 ohm 1-watt carbon
2 250 " " "
1 2,000 " " "
1 15,000 " " "
1 20,000 " " "

FIXED CONDENSERS:

4 .0001 mfd. mica
1 .02 " tubular
4 .05 " "
2 .1 " "
3 .5 " "
2 .8 " wet electrolytics
1 16 " " "
3 25 " " "

SPEAKER:

1 dynamic speaker to match single 6V6G, 2000 ohm field (Rola)

VALVES:

1 6K8G, 1 6G8G, 1 6J7G, 1 6V6G, 1 5Y3G

MISCELLANEOUS:

Push back, 2 doz. ⅜" nuts and bolts, solder tags, dial lights, copper shielding

for the next flash, but a poor condenser causes rapid flashing, while one a continuous light. These tests must that has broken down completely gives not be applied too literally to electrolytic condensers, as they always leak to some extent.

Frequency of flashing depends not on resistance alone, but on a factor derived from both resistance and


capacity, providing a truer measure of condenser quality.

With regard to construction, there is scope for individuality, but if the scale is to remain accurate, a close copy of the original wiring and placement of components is essential. Further hints in this direction will be given next month, together with a list of parts.


5- And 10-Metre 'Phone And C.W. Transmitter Next Month

Very little work is being done in Australia at the moment on the ultra high frequency bands, despite the fact that in the future they will be of tremendous importance. Hence, in an effort to stimulate interest in the "ultra - shorts" among amateurs, a 5- and 10-metre 'phone and c.w. transmitter designed and built by Mr. W. McGowan (VK-2MQ) will be described next month.

The exciter uses a 6L6G crystal oscillator followed by an 807 10-metre doubler, in turn followed by an 802 5-metre doubler. The buffer stage comprises a pair of 802's in push-pull driving a pair of 809's in push-pull in the final. Radiotron transmitting tubes have been used throughout. The accompanying photograph of the buffer and final amplifier was taken when the unit was nearing completion in its final form.

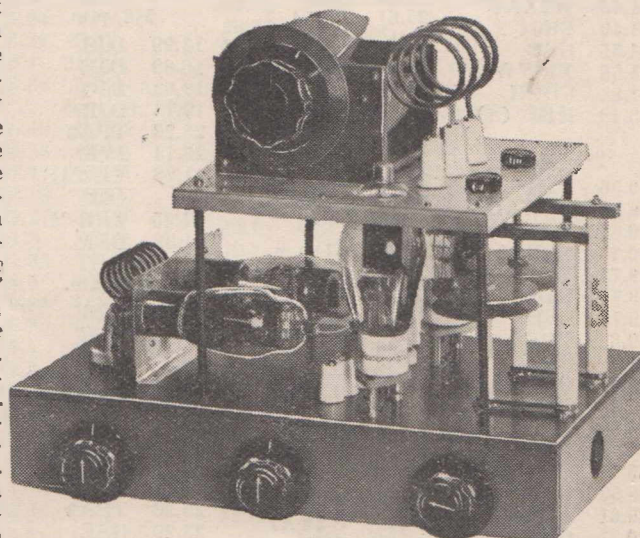

An Amazing Offer on an Amazing Kit

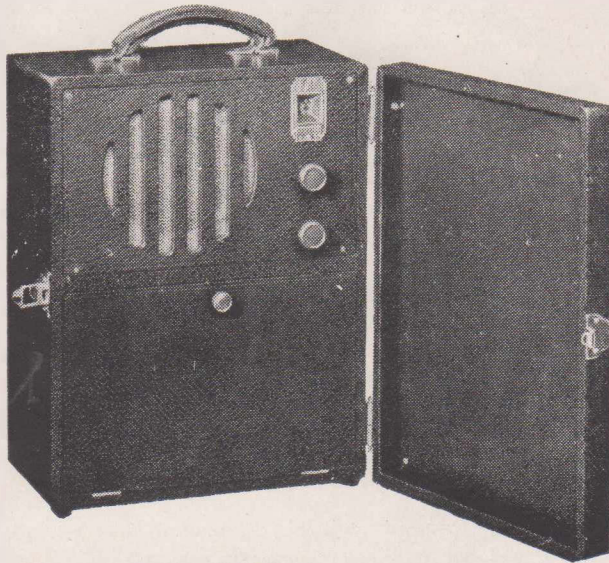

Build the 1938 OUTDOOR PORTABLE 4

During the past three years the "Outdoor Portable Four" has proved to be the outstanding battery receiver of the year. Now the 1938 model with octal-based valves and A.V.C. gives still greater improvement. Read the complete constructional details in this issue . . . see how easily and simply YOU can build this new portable . . . then write to Vealls for details of their special offer, either as a complete kit ready for assembly or as a complete set ready for use.

Complete Kit
11 Guineas

MONEY CANNOT BUY BIGGER
VALUE ——— WRITE TO-DAY

POSITIVELY THE BEST FOUR VALVER EVER
OFFERED IN EASY TO BUILD KIT FORM

Vealls 1938 Radio Catalogue Now Ready

An essential to every Radio Fan and Listener—Vealls Big 60-page Radio Catalogue covers the entire field of radio, including Amplifiers, Radio Gramo units and Test Equipment. Write for your copy to-day—it's Free! Merely enclose a 2d. stamp to defray cost of postage—your copy will be sent by return mail.

THOUSANDS OF RADIO ITEMS
HUNDREDS OF ILLUSTRATIONS

THE MOST COMPREHENSIVE RADIO
CATALOGUE PUBLISHED IN AUSTRALIA



VEALLS 6 BIG STORES

All letters to Box 2135T., G.P.O., Melbourne, C1.

490 Elizabeth Street, Melbourne. F 3145.
168 Swanston Street, Melbourne. C 10524.
3-5 Riversdale Road, Camberwell. W 1188.

243 Swanston Street, Melbourne. C 3059.
299-301 Chapel Street, Prahran. Wind. 1605.
97-99 Puckle Street, Moonee Ponds. FU 7822.



Bring to your home greater enjoyment from radio this Christmas and throughout the New Year by re-valving with

RADIOTRONS

NEW MICRO-SENSITIVE

AUSTRALIAN GENERAL ELECTRIC LIMITED

Sydney, Melbourne, Brisbane
Adelaide, Hobart

AMALGAMATED WIRELESS (A/WA) (A/SIA) LTD.

47 York Street, Sydney
167-169 Queen St., Melbourne

NATIONAL ELECTRICAL & ENGINEERING CO. LTD.

Wellington
New Zealand

(Advertisement of Amalgamated Wireless Valve Co. Pty. Ltd.)