

DECEMBER 1983

\$2.35\* NZ \$2.75

# eti

## ELECTRONICS TODAY INTERNATIONAL

**SPECIAL OFFER**  
Hewlett-Packard Logic Probes

# LOGIC TROUBLESHOOTING

**ROBOT INTELLIGENCE**

**TO BUILD:**

**DELUXE VIDEO  
ENHANCER**

**MICROBEE ANALOGUE  
JOYSTICK PROJECT**

**FULL COVERAGE BEAM  
FOR 6m HAM BAND**

**LINEAR  
TRACKING  
TURNTABLES**  
Six reviewed

**SCANNER  
FREQUENCY  
LIST**  
Part 3



**SPECIAL OFFERS: 'B-ETI' serial terminal • Texas Instruments printers**

# WHEN IT COMES TO PERSONAL COMPUTER SPECTRAVIDEO™ IS BEYOND ANY COMPARE!



To the delight of our customers, and the dismay of our competitors, we now proudly present the most advanced, most capable personal computer system available today: SpectraVideo™'s SV-318 and SV-328. While the SV-318 is "everything home computer users were waiting for," the SV-328 is specially designed "for the small business that doesn't plan to stay that way." These 2 computers, too, are beyond any comparison in their price range.

And they do not stand alone. Seldom, if every, has a new computer been supported by so many peripherals. Of exceptional quality, all this hardware rides into you on the crest of the very last

technology.

Additionally — and importantly —


SpectraVideo™ is very software oriented. With built-in CP/M compatibility, the SV system allows you to take advantage of thousands of pre-existing programs. And with the MSX software compatible standard, jointly launched by SpectraVideo™ and most of Japan's largest electronics firms, SpectraVideo™ can take advantage of all software developed by other MSX participants. Plus, SpectraVideo™ is now producing its own line of top-quality software. Finally, the SV system includes several innovative and interesting accessories that you will want to use.

Because of product depth and ease-of-operation, the SV system will give you

full usage from the moment you unpack it. Yet it is both capable and expandable enough to give you long-term usage, too. That's why SpectraVideo™ is truly, "The computer system you'll grow into, not out of."



software compatible standard

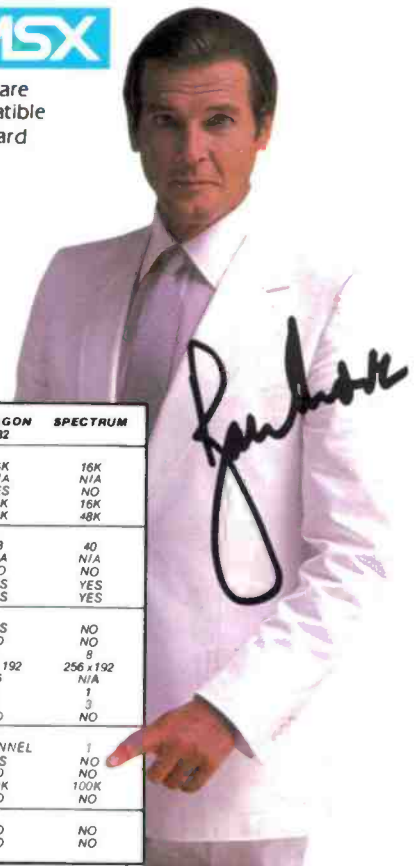

	SPECTRAVIDEO SV 328	SPECTRAVIDEO SV 318	APPLE II E	ATARI 800	COMMODORE 64	BBC MODEL B	DRAGON 32	SPECTRUM
<b>COMPUTING POWER FEATURES</b>								
BUILT-IN ROM	48K	32K	16K	10K	20K	16K	16K	16K
EXPANDABLE TO	256K	96K	N/A	42K	N/A	64K	N/A	N/A
BUILT-IN EXTENDED MICROSOFT® BASIC	YES	YES	NO	YES	NO	NO	YES	NO
BUILT-IN RAM	80K*	32K**	64K	48K	64K	32K	32K	16K
EXPANDABLE TO	256K**	256K**	64K	NO	N/A	32K	64K	48K
<b>KEYBOARD FEATURES</b>								
NUMBER OF KEYS	87	71	83	61	66	73	53	40
USER DEFINE FUNCTIONS	10	10	N/A	4	8	10	N/A	N/A
SPECIAL WORD PROCESSING	YES	YES	NO	NO	NO	NO	NO	NO
GENERATED GRAPHICS (FROM KEYBOARD)	YES	YES	NO	YES	YES	YES	YES	YES
UPPER/LOWER CASE	YES	YES	YES	YES	YES	YES	YES	YES
<b>GAME/AUDIO FEATURES</b>								
SEPARATE CARTRIDGE SLOTS	YES	YES	NO	YES	NO	NO	YES	NO
BUILT-IN JOYSTICK	NO	YES	NO	NO	NO	NO	NO	NO
COLORS	16	16	15	128	16	16	9	8
RESOLUTION (PIXELS)	256x192	256x192	280x160	320x192	320x200	256x640	256x192	256x192
SPRITES	32	32	N/A	4	8	N/A	16	N/A
SOUND CHANNELS	3	3	1	4	3	1	3	1
OCTAVES PER CHANNEL	8	8	4	4	9	3	5	3
A.D.S.R. ENVELOPE	YES	YES	NO	NO	YES	YES	NO	NO
<b>PERIPHERAL SPECIFICATIONS</b>								
CASSETTE	2 CHANNEL	2 CHANNEL	1 CHANNEL	2 CHANNEL	1 CHANNEL	2 CHANNEL	2 CHANNEL	1
AUDIO I/O	YES	YES	NO	YES	NO	NO	YES	NO
BUILT-IN MIC	YES	YES	NO	NO	NO	NO	NO	NO
DISK DRIVE CAPACITY (LOW PROFILE)	250K	250K	143K	92K	170K	100K	100K	100K
	YES	YES	NO	NO	NO	NO	NO	NO
<b>CP/M® COMPATIBILITY</b> (Standard 80 column programs)	YES	YES	NO****	NO	NO****	YES	NO	NO
CP/M 2.2	YES	YES	NO	NO	NO	NO	NO	NO
CP/M 3.0	YES	YES	NO	NO	NO	NO	NO	NO

Specifications are subject to change without prior notice.

\* 64K user addressable plus 16K graphic support

\*\* 240K user addressable plus 16K graphic support

\*\*\* 16K user addressable plus 16K graphic support

\*\*\*\* Apple II can accept modified 40 or 80 Column CP/M

\*\*\*\*\* Commodore 64 accepts 40 column CP/M

70 St. Klida Road, St. Kilda, Vic. 3182. Ph: (03) 537-2000  
 P.O. Box 474, Edgecliffe, N.S.W. 2027. Ph: (02) 328-1190  
 Franklin Agencies, 3 Marie St., Milton, Qld. 4064. Ph: (07) 369-0496  
 Jerdon Agencies, 25 Gladstone St., Perth, W.A. 6000. Ph: (09) 328-5299  
 Dennington Enterprises, 46 Canning St., Launceston, Tas. 7250. Ph: (003) 31-8551



MSX, Microsoft Extended BASIC is a trademark of Microsoft Corporation  
 CP/M is a trademark of Digital Research Inc.

SAD - 83 - 004

© 1983 SPECTRAVIDEO INTERNATIONAL LTD.



**EDITOR**  
Roger Harrison VK2ZTB

**ASSISTANT EDITOR**  
Jennifer Whyte B. App. Sc.

**EDITORIAL STAFF**  
Geoff Nicholls B.Sc./B.E.  
Jane Nicholls

**ASSOCIATES**  
David Tilbrook VK2YMI  
Jonathan Scott  
B.Sc./B.E. (Hons) VK2YBN

**DRAUGHTING**  
David Currie

**PRODUCTION**  
Steve Landon  
Mark Davis

**ADVERTISING SALES**  
Bob Taylor (Group Manager)  
John Whalen (National)  
Steve Collett

**ART STAFF**  
Ali White B.A.  
Bill Crump  
Dean Shirley

**READER SERVICES**  
Carmel Gatt

**ACOUSTICAL CONSULTANTS**  
Louis Challs and Associates

**HEAD OFFICE**  
140 Joynton Avenue, (PO Box 227)  
Waterloo, NSW 2017.  
Phone: (02) 663-9999 Sydney.  
Telex: 74488, FEDPUB.

**ADVERTISING OFFICES  
AND AGENTS:**  
**Victoria and Tasmania:** Virginia Salmon and  
Mel Godfrey, The Federal Publishing  
Company, 23rd Floor, 150 Lonsdale Street,  
Melbourne, Vic. 3000. Phone: (03) 662-1222  
Melbourne. Telex: 34340, FEDPUB.

**South Australia and Northern Territory:**  
The Admedia Group, 24 Kensington Road,  
Rose Park, SA 5067. Phone: (08) 332-8144  
Adelaide. Telex: 82182, ADMEDIA.

**Queensland:** Geoff Horne Agencies, 16  
Bellbowrie Centre, Bellbowrie, Qld 4070.  
Phone: (07) 202-6813 Brisbane.

**Western Australia:** Cliff R. Thomas, Adrep  
Advertising Representative, 62 Wickham  
Street, East Perth, WA 6000. Phone: (09)  
325-6395 Perth.

**New Zealand:** Chris Horsley, 4A Symonds  
Court, Symonds Street, Auckland. Telex:  
260753, TEXTILE.

**Britain:** Peter Holloway, John Fairfax and  
Sons (Australia) Ltd, Associated Press  
House, 12 Norwich Street, London EC4A  
1BH. Phone: (01) 353-9321 London. Telex:  
262836, SMHLDN.

**Japan:** Genzo Uchida, Bancho Media  
Services, 5th Floor, Dai-ichi Nisawa Building,  
3-1 Kanda Tacho 2-chome, Chiyoda-ku,  
Tokyo 101. Phone: (03) 252-2721 Tokyo.  
Telex: 25472, BMSINC.



**ELECTRONICS TODAY INTERNATIONAL**  
Is published monthly by the Electronics  
Division of the Federal Publishing Company  
Pty Limited, 140 Joynton Avenue, Waterloo,  
NSW 2017. Managing Editor: Bob Izzard.  
Typeset and printed by ESN-The Litho Centre,  
Sydney. Distributed by Gordon and Gotch  
Limited, Sydney. Cover price \$2.35  
(maximum and recommended Australian  
retail price only; recommended New Zealand  
price, \$2.75). Registered by Australia Post,  
Publication No NBP0407. ISSN No  
0013-5216.

COPYRIGHT © 1983, THE FEDERAL  
PUBLISHING COMPANY

## FEATURES

NEWS DIGEST .....	8
ROBOT INTELLIGENCE .....	15
<b>SPECIAL OFFER</b> THE 'BETI' TERMINAL .....	51
<b>SPECIAL OFFER</b> TEXAS INSTRUMENTS PRINTERS .....	64
<b>SPECIAL OFFER</b> HEWLETT PACKARD LOGIC PROBES .....	98
THE FREQUENCY LIST, PART 3 — 400-550 MHz .....	154

## SIGHT & SOUND

SIGHT & SOUND NEWS .....	20
SIX LINEAR TRACKING TURNTABLES REVIEWED .....	22

## COMPUTING TODAY

COURT RULES ON COMPUTER SYSTEMS .....	33
COMPUTING TODAY NEWS .....	34
<b>PROJECT 674</b> MICROBEE JOYSTICK .....	40
<b>PROJECT 658</b> RS232 BREAKOUT BOX .....	48
<b>SPECIAL OFFER</b> THE "BETI" TERMINAL .....	51
MICROPROFESSOR SOUND GENERATION BOARD REVIEWED .....	53
MICROBEE COLUMN .....	57
VIC-20 COLUMN .....	60
<b>SPECIAL OFFER</b> TEXAS INSTRUMENTS PRINTERS .....	64
ZX COLUMN .....	68
'660 COLUMN .....	75

## TECHNICAL

EQUIPMENT NEWS .....	79
COMPONENT NEWS .....	85
LOGIC TROUBLESHOOTING .....	90
<b>SPECIAL OFFER</b> HEWLETT PACKARD LOGIC PROBES .....	98
<b>PROJECT 1502</b> SLING PSYCHROMETER .....	102
<b>PROJECT 1518</b> VIDEO ENHANCER .....	112
FURTHER THOUGHTS ON TRAIN CONTROLLER DESIGN .....	120
IDEAS FOR EXPERIMENTERS .....	127
OVER THE COUNTER .....	147
SHOPAROUND .....	148

## COMMUNICATIONS

COMMUNICATIONS NEWS .....	151
<b>PROJECT 750</b> BEAM FOR THE SIX METER BAND .....	152
THE FREQUENCY LIST, PART 3 — 400-550 MHz .....	154

## GENERAL

COMMENT .....	5
ADVERTISERS' INDEX .....	5
MAIL ORDER BOOKS .....	81
LETTERS .....	159
MINI-MART .....	161
DREGS .....	162

**COPYRIGHT:** The contents of *Electronics Today International* and associated publications is fully protected by the Commonwealth Copyright Act (1968). Copyright extends to all written material, photographs, drawings, circuit diagrams and printed-circuit boards. Although any form of reproduction is a breach of copyright, we are not concerned about individuals constructing projects for their own private use, nor by bands (for example) constructing one or more items for use in connection with their performances. Commercial organisations should note that no project or part project described in *Electronics Today International* or associated publications may be offered for sale, or sold in substantially or fully assembled form, unless a licence has been specifically obtained so to do from the publisher, The Federal Publishing Company, or from the copyright holders.

**LIABILITY:** Comments and test results on equipment reviewed refer to the particular item submitted for review and may not necessarily pertain to other units of the same make or model number. Whilst every effort has been made to ensure that all constructional projects referred to in this edition will operate as indicated efficiently and properly and that all necessary components to manufacture the same will be available, no responsibility is accepted in respect of the failure for any reason at all of the project to operate effectively or at all whether due to any fault in design or otherwise and no responsibility is accepted for the failure to obtain any component parts in respect of any such project. Further, no responsibility is accepted in respect of any injury or damage caused by any fault in the design of any such project as aforesaid.





# FREE GAME OFFER

If you own a Commodore home computer,  
here's an offer too good to miss.  
Buy any Computer Classics VIC 20 game  
and get Galactic Defender free.  
Or buy a Computer Classics 64 game and  
get Stratagem free.  
Two explosive games for the price of one.  
Only from Computer Classics.  
Available from all leading software retailers.

**COMPUTER  
CLASSICS**

**THE MINDBENDERS**



## ADVERTISERS' INDEX

ACME .....	86
Altronics .....	46,47,52
94,95,110,111, 149	
Adaptive Elect .....	42,43
Alatron .....	37
All Electronic Components .....	126
Anderson Digital .....	50
Applied Technology .....	54
55,62,63	
Avtek Electronics .....	56
Benelec .....	11
Billco Electronics .....	117
BWD Instruments .....	150
Cashmore .....	19
Centre Industries .....	78
Computer Classics .....	4
Computer Spot .....	32
Convoy International .....	14
Daneva .....	88
Dick Smith .....	6, 7, 38, 39
66,67,100,101	
Electrocraft .....	87
Electromedical .....	
Engineering .....	49
Electromark .....	129
Ellistronics .....	114
Elmeasco Instruments .....	103
Elston Micro .....	45
Emona Enterprises .....	10
Emtronics .....	93
Energy Control .....	45
Esis Pty Ltd .....	70
Essex Laboratories .....	147
Ferguson Transformers .....	98
Flex Electronics .....	37
GFS Electronics .....	117
Hewlett Packard .....	16,17,98,99
Hi-Com Unitronics .....	93
Imark Pty Ltd .....	87
Intermec Australia .....	41
Jaycar/Electronic Agencies .....	58,59,72,73
76,77,88,89,157	
J. H. McGraths .....	122
123	
K-Nar Computer Cards .....	74
Lamron Pty Ltd .....	148
Micro 80 .....	53
Mini Tool .....	70
Mytek .....	71
Parameters Pty Ltd .....	11
Paton .....	104
Power Sonic .....	129
Pre-Pak Electronics .....	158
Prolog .....	35
Pro-Mark Electronics .....	124,125
Pulsar Electronics .....	69
QT Computers .....	32
Radio Despatch .....	93
Rod Irving .....	Catalogue
pps 131 to 146	
Rose Music .....	OBC
Scan Audio .....	31
Scientific Devices .....	80
Scope Elect .....	61
Sheridan Electronics .....	108,109
118,119	
SME Systems .....	40
Software Source .....	47,80
Southern Cross .....	45
Sony (Aust) .....	IBC
SWTPC .....	36
Truscott Elect .....	129
Videocativ .....	IFC
Vidotech .....	87

## COMMENT

### Season's Greetings to all our readers and advertisers from ETI Editor & staff



Roger Harrison  
Editor

## NEXT MONTH

### JAPAN ELECTRONICS SHOW

Dennis Lingane brings you two reports on the All Japan Audio Show and the Electronics Show. Read all about the latest developments in audio, video and home computers.

### LET CALLER

Play tennis, anyone? This unit provides you with clear indication when a ball 'tips' the net in flight — requiring a 'let' call. Our electronic let detector is more reliable than umpires and saves tennis court tantrums. Cheap and simple to build.

### IMPROVING THE '668 EPROM PROGRAMMER

Our popular Microbee EPROM programmer has been improved at the suggestion of a number of readers. Geoff Nicholls combines the best suggestions for the '668 deluxe!

### CIRCUIT SOURCE GUIDE

Our first Circuit Source Guide, published in the Feb. '82 issue, proved a popular feature, so it returns in January. The '84 Circuit Source Guide will contain dozens of practical circuit ideas for experimenters and engineers, tinkers and technicians. Don't miss it — lots of holiday-time inspiration!

### PROGRAM BUG DEBUGGER ▶

Ever burnt a program into an EPROM and found it wouldn't run? Without a logic analyser it's nigh on impossible to debug. This project costs far less than a logic analyser and gets you out of the jam. It provides 'mirror image' RAM (battery-backed, if you like), permits the addition of program breakpoints and removes R/W control. It plugs directly into a 2716/2516 socket. Use also for temporary RAM extension or program storage. Cheap, too.



## SERVICES

**TECHNICAL INQUIRIES:** We can only answer readers' technical inquiries by telephone after 4.30pm Mondays to Thursdays. The technical inquiry number is (02) 662-4267. Technical inquiries by mail must be accompanied by a stamped, self-addressed envelope. There is no charge. We can only answer queries relating to projects and articles as published. We cannot advise on modifications, other than errata or addenda. We try to answer letters as soon as possible. Difficult questions may take some time to answer.

**GENERAL INQUIRIES:** For all inquiries about back issues, subscriptions (\$20.00 for 12 months/12 issues), photocopies of articles, artwork or submitting articles, call (02) 663-9999 or write to: ETI Reader Services, 140 Joynton Avenue (PO Box 227), Waterloo, NSW 2017.

**CONTRIBUTIONS:** Submissions must be accompanied by a stamped, self-addressed envelope. The publisher accepts no responsibility for unsolicited material.





# DICK'S PRICES MAKE GIVING A PLEASURE!



**WARNING!**  
You may see unknown brands at a lower price. They can cause \$\$\$ damage to your video recorder heads as they may be highly abrasive. The wise video enthusiast sticks to the top brand names!

**LOWEST PRICE IN AUSTRALIA**

**FOR QUALITY, TOP NAME POLAROID VIDEO CASSETTES**

VHS 3 hr Cat C-3410  
BETA 3 hr Cat C-3415

**\$12.50**

**NEW**

**NEW 20 MHz**



**HITACHI DUAL TRACE CRO**

Not just a good CRO... a great one! Top brand name with huge 20MHz bandwidth, dual traces... it's got the lot! And all for our low, low price!

**Features:**  
● Extra high bandwidth, ● Extra high sensitivity ● 5 display modes ● 1 touch wave form shifting.  
Cat Q-1243


**ONLY \$699**

**DELUXE FEATURES!**

**200FB BEARCAT SCANNER**

What a beauty! A superb scanner for such a low price, with features like 16ch. memory, direct channel access, auto and manual memory scanning AND it can be used mobile! Cat D-2801

only **\$369**

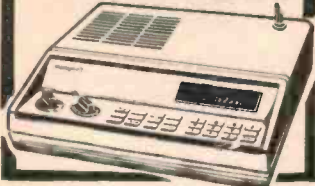

**UNIVERSAL ANTENNA MAGNA BASE**

Ideal for company cars, etc, where drilling holes in the roof is a definite no-no! Extra strong magnet grips any ferrous surface and stays stuck even at high speed!

**\$29<sup>50</sup>**

Cat D-4514

**SAVE**

**SCOOP PURCHASE!**



**Stereo Cassette Player**

**ONLY \$29<sup>95</sup>**


From Bach to Beethoven to Beatles to B-52's, they'll all sound great on this brilliant little stereo cassette player. And at this low, low price, how can you look elsewhere?  
Cat A-4055

**NEW**

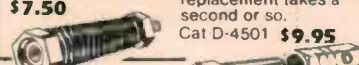**PROTECT YOUR ANTENNA**

**ANTENNA SPRING QUICK DIS-CONNECT**  
Thwunk! You've just hit a low flying bridge - & your antenna is now a dipole. If you had a spring in the base it would have bounced back. Standard thread, suits most antennas.  
Cat D 4500  
**\$7.50**

You didn't realise your antenna was pinched until you saw the smoke coming from your finals... A quick disconnect would let you put the stick in the boot as you leave the car! Removal & replacement takes a second or so.  
Cat D-4501 **\$9.95**




**Metric Conversion Calculator**

Take the hardship out of metric conversion with this pocket sized LCD calculator. Converts to metric and vice versa.

Cat Q-3025

**\$19<sup>95</sup>**

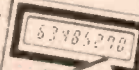

**NOW YOU CAN HANDLE METRICS!**



**RELAYS... RELAYS... RELAYS**



**EXTRA HEAVY DUTY PCB**  
**\$3<sup>50</sup>**

High power rating - but a budget price! Operates from nominal 12V, has double pole, double throw contacts.  
Cat S-7140



**HIGH RATING POWER RELAY**  
**\$9<sup>75</sup>**

A small but high capacity relay ideal for power switching with a massive contact rating of 10A.  
Cat S-7200

**NEW**

**20k/V MULTIMETER**

(inbuilt logic probe)  
Amazing Value! Cat Q-1026

**\$32<sup>50</sup>**



**SAVE \$10**

**AND TIME WITH THE LOGIC PROBE**

This outstanding Logic Probe hooks onto the circuit under test for its power (5V DC), and you can tell at a glance what the logic level is by which of the three LEDs is glowing. It is easily held in one hand - so your other hand is left free! Ideal tool for the hobbyist, technician, engineer etc.  
Cat Q-1272 WAS \$32.50

**\$22<sup>50</sup>**



**Sub Miniature DPDT Slide Switch**

Countless applications - amazing low price!  
Cat S-2010

**45<sup>c</sup>**

**SAVE A FORTUNE!**

**on comparable quality DIE CAST BOXES**

Cat H-2206  
150 x 50 x 80mm

**\$9<sup>25</sup>**



**LOW COST RECHARGE**

**GE Quality NiCad Charger!**

Handles 4 AA NiCads! Great GE brand... full instructions provided!



Cat M-9520

**\$8<sup>95</sup>** WAS \$10.95

**SCOOP PURCHASE!**



**QUALITY PHILIPS Car Speakers**

Twin cone for really thrilling sound! 4 ohms impedance and 20W rating. \$40? No! \$30? No! Thanks to a very special deal, our crazy price is just...

**\$9<sup>95</sup>** ea

**AMAZING!** Cat A-6988

**ILLUMINATED SPST (12V)**

Intended for automotive use. The soft glow from the toggle is not distracting in night driving, the switch can quickly be located. 12V lamp operates from supply being switched.  
Cat S-1214

**\$2<sup>95</sup>**



**NEW**

**Piezo Transducer**

Great for miniature audio alarms. Can be driven by transistor, C-MOS or TTL giving a piercing note around 80dB @ 30cm. Very low power needed - operates from around 3V to 30V peak to peak.  
Cat L-7022

**99<sup>c</sup>**



**Fits your pocket!**

**Mini Sized Multimeter**

A fantastic multimeter for anyone starting out in electronics - & just as useful for the house, car etc. Economic, reliable and simple to operate.  
Cat Q-1010

**\$13<sup>50</sup>**



2kV sens

**DICK SMITH Electronics**




# GREAT SAVINGS, BUILD YOUR OWN

## DICK SMITH SERIES 200

Just cause you haven't got as much space, why skimp on sound quality? Build these superb Dick Smith Series 200 hi-fi speakers and you'll be amazed at the sound quality that could come from such a tiny package! And you'll be amazed at the savings made over built-up speakers! (See ETI September 1983)

Includes:  
Speaker Grille Cat C-2608 \$31.50  
Enclosure Kit Cat C-2636 \$128.50  
Speaker Kit Cat C-2046 \$89.50

Complete 200mm D.I.Y. Speaker Kit

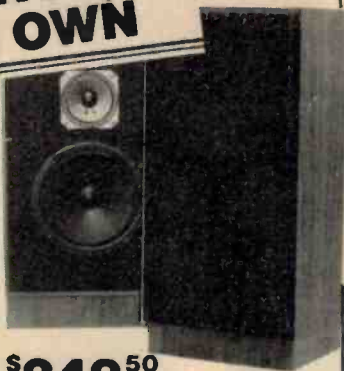

**\$249<sup>50</sup>**



**Fantastic - will not corrode! ALL WEATHER HORN SPEAKER**

At last - a horn speaker you can use anywhere! Until now all horn speakers have suffered a similar problem: corrosion. Now a plastic horn speaker which doesn't sacrifice any of the acoustic qualities of its aluminum counterparts - but doesn't suffer from corrosion!

Cat C-2705

**\$10<sup>25</sup>**

**NEW FROM KAMBROOK!**

**4 WAY POWER BOARD**


Get rid of that ugly piggyback double adaptor with this new-look power-board. 4 outlets. Cat P-5612



**\$12<sup>99</sup>**

ONLY

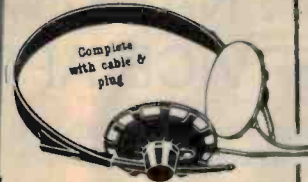**NOW HEAR THIS: FAMOUS SENNHEISER HEADPHONES**



Just look at this! Superb headphones from one of the world leaders in audio products at an unbelievably low price! Check out the quality sound from these phones - you won't go elsewhere. Cat C-4120

**ONLY \$29<sup>95</sup>**

**MOTOROLA QUALITY PIEZO TWEETER**



A magnificent new addition to our range of quality speakers. This excellent piezo-ceramic tweeter is an ideal replacement tweeter. Handles up to 40 watts continuous. Add these to your system and you'll notice the difference. Cat C-2006.

**ONLY \$6<sup>95</sup>**

**Transistor Checker Multimeter**

The ideal test instrument for hobbyists, also great for the serviceman - rugged, low profile 25 ranges, highly visible display. And you now save \$10.00! Cat Q-1136 WAS \$79.95

**\$69 SAVE \$10**

**THE POCKET COM II WALKIE TALKIE**




Great gift for any child! Full 2-way transmission in a unit so compact it could fit into your pocket! Ideal for construction workers on the job or for mothers who want to know what Johnny is up to in the backyard. Makes an ideal Christmas gift! Cat D-1101 Complies with spec. RFME001 of the Australian Dept. Of Communications.

**NO LICENCE REQUIRED!**

**\$9<sup>95</sup>**

**SAVE A FORTUNE!**

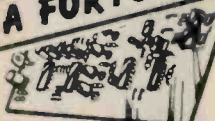

**4 SECTOR ALARM CONTROL MODULE**

**EASY TO INSTALL**

Protect your home and valuables with this alarm control unit. Virtually identical in op. and circuitry to one of the advanced alarm control units you pay \$\$\$ more for! Cat L-5056

**ONLY \$69<sup>50</sup>**

**EASY LISTENING!**

**PHONE AMPLIFIER**

Are you forever sitting with a phone to your ear waiting for the person on the other end of the line to come back to the phone? Well now you can relax because this unit will let you know when there is a person on the other end. Easy to attach via the sucker supplied. Also ideal for conferences or for when those overseas relatives call - now everone can hear the caller. Cat Y-1174



**\$12<sup>50</sup> OVER 8000 SOLD**

**NEW**

**Deluxe Slimline TEAC HI FI at a Dick Smith bargain price!**



**WHAT A BUY!**

Looking for a great hi fi? Check these out: Teac's new A-505 DC integrated stereo Amplifier and the matching T-303 AM/FM Stereo Tuner. 30W plus per channel, full range of inputs and switching for the most demanding audiophiles. And the new slimline appearance looks a million dollars!

**\$249**

**\$209**

**BOOK VALUE**

**GE OPTO BOOK**

Great Value! Cat B-4028 **\$9<sup>95</sup>**

**NATIONAL LOGIC TTL DATA MANUAL**

Contains complete information on the extensive National Semiconductor bipolar logic families. Cat B-4022 **\$11<sup>95</sup>**

**MOS MEMORY**

Data book of Fairchild's MOS memory LSI & VLSI devices! Cat B-4023 **\$5<sup>95</sup>**

**AUST'N RADIO FREQUENCY H'BOOK**

Get into the exciting hobby of scanning with this superb publication. A must for any scanner enthusiast. Cat B-9600 **\$12<sup>95</sup>**



**See Page 101 for full address details.**



# TELECOM-RUN NATIONAL VIDEOTEX SERVICE APPROVED

The Minister for Communications, Mr Michael Duffy has announced the approval for Telecom to establish a national videotex service.

Mr Duffy said that Telecom will soon invite tenders, from selected suppliers, for the supply, installation and commissioning of the necessary equipment. The service is likely to be operating towards the end of 1984.

Mr Duffy said, "There has been strong industry support, especially through the recently formed Australian Videotex Industry Association, for Telecom to provide a national videotex service giving Australians efficient, low-cost access nationally to such a service via the automatic telephone network."

"In effect, therefore, the national videotex service will serve as a decentralised national library, with an extensive range of information being made available via the telephone line."

The service is expected initially to be capable of working with existing Prestel terminals and data bases now operating in Australia. It is anticipated that later it will be able to handle other videotex systems as well.

A national system would boost employment in a variety of fields outside Telecom — manufacture, sale and rental of terminals, operators of data bases, information assemblers, etc.

Mr Duffy emphasised that the


provision of a national videotex service does not preclude other organisations from establishing systems to meet their own special requirements. Telecom will make facilities available for such systems at standard tariff rates.

Meanwhile, the Australian Videotex Industry Association (AVIA) has welcomed the announcement by the Minister for Communications that Telecom will establish a national Videotex service for Australia.

The Association anticipates that several large organisations who have previously lacked confidence in the future of the technology will now become active participants.


The national service will have special attraction for non-metropolitan users as it is understood that Telecom intends to offer the service at a uniform tariff.

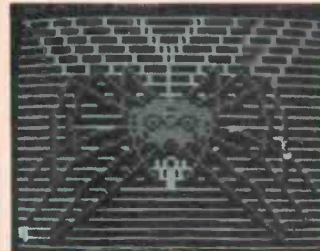The Association believes that Telecom's role as a common carrier — offering information storage capacity only but with no involvement in information ownership, information provision, terminal manufacture or distribution — is the best approach. In this way the private sector will be presented with significant opportunities which will boost activity and employment.



RASSIS DES PYRENEES		PAGE	
ENNEIGEMENT MOYEN LE 5/9/80			
YRENEES OCCIDENTALES	---2000	TOTAL	FRA
	---2700	CM	0
	---1400M	10 CM	0
YRENEES CENTRALES	---1800M	30 CM	0
	---1600M	0 CM	0
YRENEES ORIENTALES	---2100M	60 CM	0
	---1700M	5 CM	0
	---1300M	0 CM	0

COURS JOURNALIERS DES SICAV	
Du 06 MARS 16H30 au 09 MARS 16H30	
Le 09 16H30-16H30 Cours provisionnels	
(coups arrondi au chiffre supérieur)	
- LE LIVRET PORTEFEUILLE	259.8
PRIX FERME PUBLIC	251.8
PRIX FERME PVT	251.8
- LIVRET BOURSE INVESTISSEMENTS	139.1
PRIX FERME PUBLIC	129.8
PRIX FERME PVT	129.8
- SOCIETE NOUVELLE FRANCE DELIATION	331.0
PRIX FERME PUBLIC	327.5
PRIX FERME PVT	327.5
1 A 80 ACTIONS	327.5
1 A 80 ACTIONS	327.5
1 A 80 ACTIONS	327.5

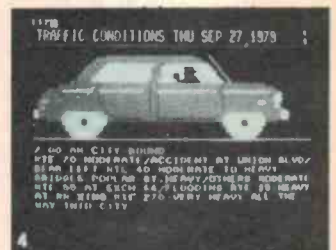

LE QUOTIDIEN DE LA POSTE  
 MONSIEUR ROBERT ESCARPIT, JOURNALISTE ET ECRIVAIN, DONNERA UNE CONFERENCE LE MERCREDI 9 MARS A 16 H AU MUSEE DE LA POSTE BOULEVARD DE VAUGUIER SUR LE THEME LA COMMUNICATION ET LA POSTE

SCOREBOARD THU SEP 27 1979	
NATIONAL	4
NEW YORK	4
CHICAGO	4
ATLANTA	4
LOS ANGELES	2
CHICAGO	2
PITTSBURGH	2
CINCINNATI	1
SAN FRANCISCO	1
HOUSTON	1
MINNAPOLIS	1
PHILADELPHIA	1
INDIANAPOLIS	1



## PORTABLE SOLAR POWER PACK

Since solar cells were first used in outer space, prices have gradually dropped, making them economical for an ever growing range of applications.

Amtex Electronics has released a portable solar power generator in a lightweight carrying case. Called the NV-500M, it can supply up to 5 W of dc power for a variety of appliances. It is especially useful for recharging batteries for portable video cameras which may be taken to the beach, a sports event or anywhere away from main electricity.

The unit produces 12 V at

0.5 A and has a built-in overload protector. It also has outlets for 3 V at 0.5 A, 6 V or 9 V at 1 A. The hinged, molded-plastic, attache-style case measures 330 x 350 x 65 mm and snaps shut to protect the cells during transport.

It simply needs to be opened flat to expose its solar cells, which immediately begin converting sunlight into electricity. The unit is priced at \$389.

For further information, contact Amtex Electronics, 11 Spring Street, Chatswood 2067 NSW. (02)411-1323.



## LASERS COULD AID WEATHER FORECASTING

**W**eather forecasting is a subject that is taken very seriously in Britain and, in a bid to improve results, scientists at a northern England university are to start using data collected by satellite-based lasers.

The University of Hull's Department of Applied Physics has been awarded a grant of almost \$92 000 for work on atmospheric measurements using coherent laser radars. The research has applications for meteorology in examining humidity and wind velocity and in the control of pollution.


Doctors Barry Rye and Eric Thomas are developing a technique for monitoring atmospheric gases which involves the absorption of infra-red laser beams passed

through them.

Dust particles act as the "targets" of the radar system, while wind velocity can be determined from the speed of the dust using methods of measuring doppler shift analogous to those in police radar traps.

The researchers hope that, in the future, it will be possible to develop mobile systems for use on the ground and possibly from aircraft and satellites.

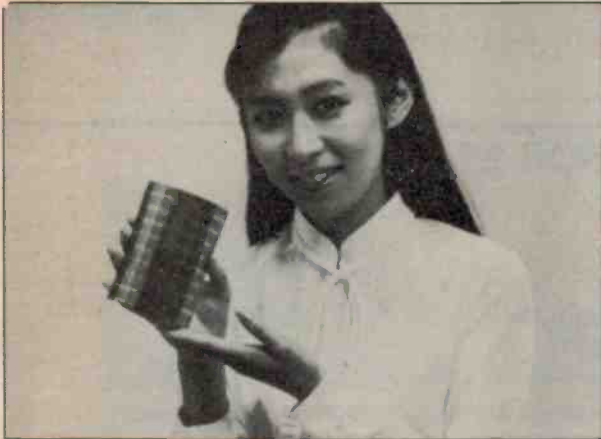As the latter can be used to scan all the earth's surface, the measurements obtained would be far more comprehensive than those available from existing land-based sources, and could lead to a considerable improvement in weather forecasting, it is claimed.



## NEW TYPE OF 'SOLAR BATTERY'

**S**anyo Japan has announced the development of the 'flexible' Amorton — a layered amorphous solar battery which utilises both metal and resin substrates.

In contrast to the existing glass substrate Amorton used in calculators, electronic games and watches, the flexible metal and resin film substrate types are claimed to be superior in their mass production quality.

They are also adaptable to any sort of surface, including bends or curves.

Sanyo says this technology 'breakthrough' is highly significant for the future of applied

solar energy.

New ideas for flexible solar cells include their use in curved-surface electronic products such as headphone radios and adaptation to products which combine energy from both solar light and solar heat.

Now that the Amorton strata can be accumulated on such metal bases as nickel and copper, says a Sanyo spokesman, it is possible to construct solar batteries on the surfaces of all kinds of machinery.

Sanyo Japan expects that a monthly production total of five million units will be reached by the end of the year.

## NATIONAL STRATEGY FOR NEW TECHNOLOGY?

**B**arry Jones, the Minister for Science and Technology, has foreshadowed a national strategy for new technology.

Such a strategy would probably be formulated and discussed at a national technology conference in six months or a year's time. It would incorporate priority actions and ways of putting them into effect.

Mr Jones predicted the move at a three-day technology conference in Canberra in October. The conference was attended by 140 business and union leaders, scientists, academics and politicians from Australia and overseas.

He told the conference delegates in his closing speech that he thought it had been a valuable exercise in conscience raising and he hoped it would serve as a good basis for a national technology strategy.

The general thrust of the Labor Party's science-and-technology had come through the conference "comparatively unscathed", he felt, but he planned to revise the policy before next year's national ALP conference.

The Minister thought the conference had been successful in promoting dialogue between people and interest groups which had not met before and in drawing attention to the central role of technology in economics and politics.

Australia has changed from an industrial society into an 'information society', with more people employed in collecting, processing and disseminating data than farming, mining and manufacturing combined, but politicians and the community have been slow to recognise this shift, Mr Jones said.

## ELECTRONICS INDUSTRY SUPPORTS TRADE MINISTER

**T**he Australian Electronics Industry Association (AEIA) has supported the Federal Trade Minister, Mr Bowen, in his claim that non-tariff barriers would provide more protection for manufacturing industries.

The AEIA represents 50 of Australia's leading electronics and communications companies and pointed out that most developed countries support their technological and strategically significant industries by applying non-tariff barriers.

In many cases, the import tariffs they impose are low compared to Australia, but the non-tariff barriers give their local manufacturing sector adequate protection.

The AEIA executive director, Mr Ed Hodgkinson, says the Australian viewpoint of lowering tariffs the prime objective is one the association does not agree with.

"Too often the initial buying price is taken as the be and end all of the purchasing process. But in many cases, back-up service and support of systems and products are a major cost item,

which can be minimised by having local manufacturing," Mr Hodgkinson said.

The association is keen to see Australian firms follow the example of companies such as Telecom, which buys local equipment and recognises the advantages of having the support of a viable manufacturing industry.

## MARKETING SERVICES

**P**at Daly, the former marketing manager for Dick Smith Electronics, has established a marketing services company.

Over the past few years, Mr Daly has successfully launched many new consumer products, including telephone products, video games, home products and answering machines.

For further information, contact Pat Daly Marketing Services, 6 Chatswood Avenue, Chatswood NSW 2067. (02)411-7707.



## SUNSHINE FOR SUNRISE INDUSTRIES

High-tech 'sunrise' industries are being billed as the growth markets of the future and it seems sunburnt Australia is already embracing some of them with great enthusiasm.

In the solar power marketplace, market growth has been little short of phenomenal during 1983, according to one of the most experienced companies in the field, Amtex Electronics.

At a time when most companies are suffering from the stagnant economic conditions, Mr Jim Kuswadi, the company's general manager, claims sales of solar energy systems, as a replacement for electric and diesel power, have almost doubled since March.

"The major growth has been in NSW, Queensland and Victoria," said Mr Kuswadi.

"Seventy per cent of systems have gone to remote rural communities for domestic applica-

tions such as pumping water from dams and providing electricity for household appliances.

"The remaining 30 per cent are commercial applications such as microwave radio links for communications.

"The technology has been talked about for a long time and is now gaining credibility among the ordinary consumers," he said. "People now accept that it works. It's also economic and our system can be easily installed by a handyman.

"It's a highly innovative market. Every week I'm confronted by somebody who wants to know if solar is the answer to their problems. In many cases it is the perfect solution." Amtex markets the Kyocera brand of solar energy systems. For further information, contact Amtex Electronics, P.O. Box 285, Chatswood NSW 2067. (02)411-1323.

## EXPORT OPPORTUNITY FOR SECURITY SYSTEMS

Sales of security systems in the USA have almost trebled since 1980 as a counter to the increasing rate of crimes against people and property, making it an opportune time for the Australian security industry to increase its penetration of the US market at next year's International Security Conference (ISC) and Expo in New York from 27-29 August.

The Expo is a complete security forum for products, systems, and education, where qualified buyers from all industry segments can see and compare the latest technology available to solve their security problems.

In 1980 the US security equipment market was worth little more than \$7000 million; today it exceeds \$20 000 million; and by 1995 it could reach \$31 000 million. The ISC exhibitors will

have access to 35 000 executives, dealers, installers, end-users, new companies, and security professionals.

The Expo will feature hundreds of displays in all security categories, including alarm systems and components, access control, locking equipment, perimeter and space protection, monitoring equipment, smoke and fire detection equipment, and vehicles and accessories.

The demand exists for high quality, sophisticated security products which Australian firms can supply and Australian participants at the Expo will be exposed to an excellent cross-section of the market, conducive to establishing exports.

For further information, contact The Promotions Officer, Chris Begley, Department of Trade, Canberra. (062)72-2527.

## THE MICROPROFESSOR SERIES



**MPF-IB**  
**\$138**  
**+ SALES TAX.**



**MPF-IP**  
**\$207**  
**+ SALES TAX.**



### COMPLETE Z-80 BASED MICROCOMPUTER SYSTEMS FOR HARDWARE/SOFTWARE TEACHING & DEVELOPMENT

The Micro-professor I gives you all you need to join the growing world of microcomputing.

It's a fully developed, tested and proven system that gives you step by step, start-to-finish hands on instruction.

- Interactive 2K Monitor Enter program in RAM & execute useful debugging functions. Other support functions
- 2K RAM, 4K ROM (expandable to 4K RAM or 8K ROM)
- 6 digit 7 segment display
- 36 keys: 16 Hex, 19 Function & 1 user defined
- Tiny 2K Basic interpreter
- Provision for on-board Z80 PIO & Z80 CTC
- Bread-board/wire wrap area
- Interactive 8K Monitor Two Pass Assembler & Text Editor Line Assembler Disassembler Direct Data Entry (Hex)
- 4K RAM, 8K ROM (Expandable to 16K)
- 20 digit, 14 segment display
- 49 key 'QWERTY' type keyboard
- Optional Languages — BASIC & FORTH
- RAM backup battery

Z80 CPU, Z80 Bus socket for external interfacing, Cassette I/O, Speaker, 3 User's Manuals & Optional Student Work Book.

#### MPF-I OPTIONS:

IOM-MPF-IP, Input Output and Memory Board (MPF-IP only) \$132.00  
PRT-MPF-I, Printer Board \$105.00  
EPB-MPF-I, Eeprom Programming Board (incl. AC/DC adapt.) \$159.00

Synthesizer Board \$159.00  
SGB-MPF-I, Sound Generation Board \$105.00  
AC/DC-Mains Adaptor (for IOM, PRT, SSB & SGB) \$ 11.50

\* ALL PRICES — PLUS 20% SALES TAX, IF APPLICABLE.

\* Micro-Professor is a trade mark of Multitech Industrial Corporation.


\* Z80 is a trade mark of Zilog Inc.



Distributed by:  
**EMONA ENTERPRISES PTY LTD.**  
CBC Bank Bldg,  
661 George St, Sydney NSW, 2000.  
Tel (02) 212-4815. Tlx AA74500

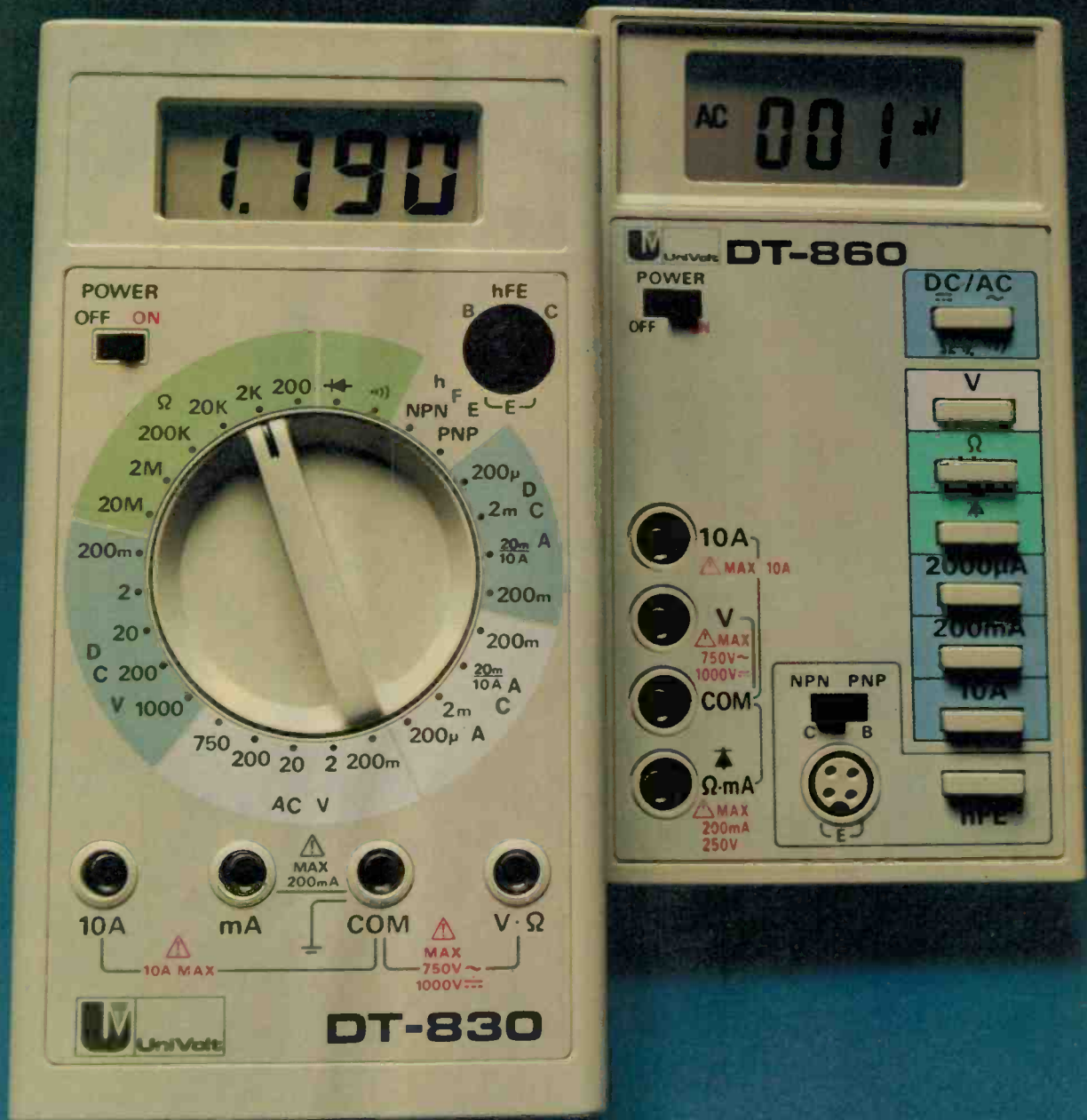Also available from: VIC: Radio Parts Group, 329-7888. SA: International Communication System P/L, 47-3688. WA: HINCO Engineering P/L, 38-4477. QLD: Baltec Systems, 369-5900. TAS: D & I Agencies, 23-1755. ACT: Electronic Components P/L, 80-4654.





**Model DT-830.** The accuracy and functions you need at a sensible price. Extreme electrical and mechanical ruggedness combined with the highest accuracy in its class.

- 30 ranges, including transistor testing, audible continuity test
- Auto zero and auto polarity. Sampling time 0.4sec
- Voltage inputs protected to 1000V, Ohms and Current to 250VAC
- Basic Accuracy  $\pm 0.5\%$

# MEASURING POWER PLUS



**Model DT-860** Autoranging, fast sampling (0.5sec), high resolution and moderate price:

- Continuity buzzer with fast (0.4 sec) response (sampling time other ranges 0.5sec)
- Built-in stand
- Basic Accuracy  $\pm 0.5\%$

For further details and latest prices contact:

**BENELEC Pty Ltd**

1 Greville Street,  
Randwick, N.S.W. 2031


**Phone:** (02) 665-8211

**Telex:** AA20181 BENELEC

## BENELEC



AT-3551C

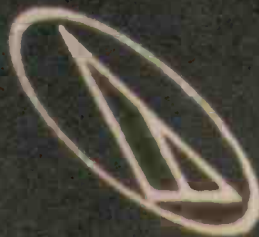

audio-technica



# “We have no quality controllers, just highly critical employees.”

At Audio Technica we reject mindless, conveyer-belt operations.

Instead we encourage our employees to deal with problems on their own initiative. To be responsible for the excellence of their own work.

The result is the world's toughest quality controllers and Audio Technica's unrivalled reputation for precision and reliability in stereo cartridges, styli, microphones, headphones, tone arms and accessories.

And now Australian hi-fi enthusiasts will discover Audio Technica more readily available through an expanded dealer network.

For a free Audio Technica brochure and dealer information, simply clip the coupon below.

Please send me your free Audio Technica brochure and dealer information.

Name \_\_\_\_\_

Address \_\_\_\_\_

Postcode \_\_\_\_\_


Post to: Audio Technica brochure offer, c/- Rose Music Pty. Ltd.,  
17-33 Market Street, South Melbourne, 3205.



**audio-technica®**



# B & W DIGITAL MONITORS

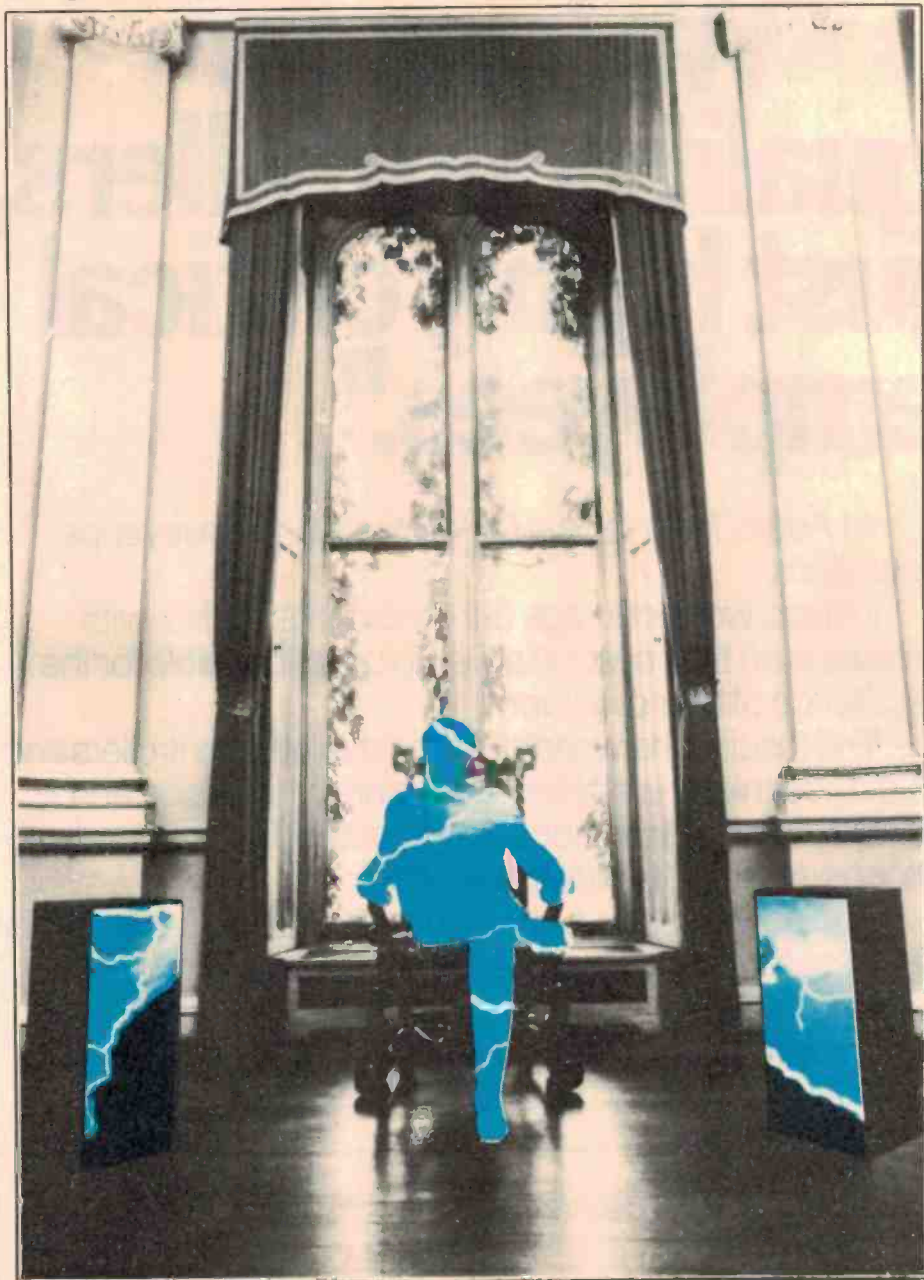

## LISTEN AND YOU'LL SEE

The new DM110 and DM220 are built to the same exacting standards as the monitors we supply to major digital recording studios throughout the world. They are, happily, much more affordable. At around \$399 for the DM110, and \$599 for the

DM220, you now have a perfect excuse to upgrade your equipment to digital standard.

Ask to hear them soon.  
Close your eyes and listen.  
Then you'll see.



AS USED BY DIGITAL STUDIOS WORLDWIDE. AND SOON, WE HOPE, BY YOU.

Distributed by: Convoy International Pty. Ltd.,  
400 Botany Road, Alexandria, NSW, 2015.  
Telephone 698-7300. Telex AA23111.



# Robot Intelligence

The intelligent robots of science fiction and the industrial robots of today may not appear to have much in common. The current trend in robotics is based on principles which are only just being recognised in Artificial Intelligence research.

**D.M.W. Powers**

Department of Computer Science,  
University of New South Wales

## Unintelligent robots

The common understanding of 'robot' is as some sort of humanoid or Dalek-like box of computing tricks. This fantasy being is automobile and intelligent, endowed with human or even superhuman dexterity, language ability and visual acuity, and is typically self-aware, self-motivated and fictitious.

The more informed view of 'robot' will realise that eventually something like such a robot may be achieved. However, now robots are generally just glorified assembly-line or manipulation devices, apart from a few toys and turtles 'running' around research establishments.


When current robots are compared with the 'ideal' robot they are found to be deficient in precision and feedback responsiveness, in pattern recognition ability of a visual and tactile nature, and also in language and speech ability. The principle of self-activation, when a robot makes a decision based on its past experiences, is scarcely more than a dream.

There is, however, one aspect of intelligence that is becoming common in current robot technology. The programming of robots is changing from the familiar pattern of 'programmer and console' to one of 'guidance and learning'. There are still many problems related to the flexibility and tolerance of such systems, but it is clear that guidance, in whatever form it is given, has distinct practical advantages over conventional programming.

Adopting this learning pattern has ramifications far beyond the current usage. Various definitions of what characterises intelligence have been adopted throughout history; e.g. tool-making, language ability and generalisation ability. These features, said to distinguish man from the rest of the animal kingdom, must surely bear some relationship to those which will distinguish the intelligent computer or robot from its unintelligent counterpart.

Each of these characteristics has been disputed, or has been identified in certain other animal species. However, it is clear that the ability to deal with and develop the novel and the intangible is the basis of all these human characteristics. Only a system capable of learning could exhibit such characteristics.

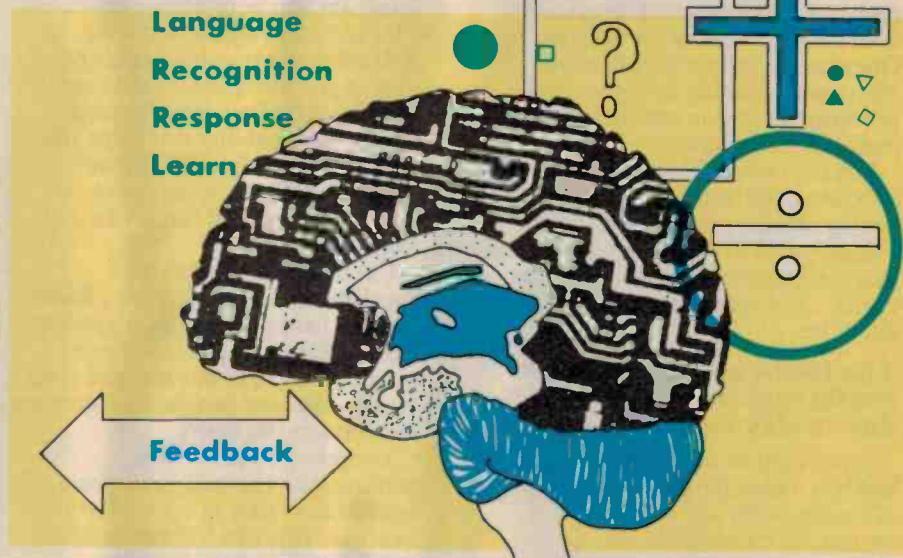It is not really a surprise that learning techniques should be so useful in industrial



robots. What is surprising is that they are not applied more widely. After all, we don't program our children, but they acquire language, knowledge and motor skills naturally without being an intellectual drain on us (Derr77a).

As early as 1959 this technique was applied to draughts (checkers), and the learning program eventually reached master standard (Samu59a, Samu67a). Learning is, in fact, the main activity of our lives — not in a classroom sense, but in terms of everyday memory, in dealing successfully with what is novel, and in tackling a multitude of problems.

The proposition put forward is that it is learning which is the keystone of intelligence.

## Philosophical Robots

As early as 1950, people were wondering about the nature and philosophical implications of this computing machinery they were hearing about. And in that year a paper of continuing significance was written addressing the question 'Can Machines Think?' (Turi50a). This paper has been reprinted a number of times in recent years and is still relevant; the imitation game suggested in it as a test of intelligence and thought has become a focus for argument as well as a goal for research.

The 'Turing Test' tests the ability of a machine to emulate a person and deceive an interviewer into thinking it is human. It is set up so that no communication or hint is conveyed except by typed messages. To fool a person, the computer must not only have language ability and logical inference abil-

ity comparable to a human's, but it must be either provided with or capable of providing a background as a personality in society.

These days the Turing Test is generally accepted as a test of intelligence. However, there are many who argue that it is invalid — that the test does not test for intelligence, but something that looks like intelligence yet is not the real thing (Sear80a). This problem of definitions is precisely what Turing hoped to avoid in defining a test rather than providing a definition of intelligence or thought.

But the philosophical discussion has a useful side-effect. It has focused our understanding of intelligence on purposeful behaviour and on the system of which it forms a part. It denies that an isolated 'black box' of 'intelligent' thought is intelligent; it is only in its involvement and relationships with the environment that intelligence can be construed, if even then. This again forces us to consider how sensory input, motor output, feedback loops and self-awareness, and the intentionality and purpose are involved in human intelligence.

The problem is best characterised in terms of whether a computer that is capable of answering questions, as if it were a person who understands the subject matter and the language, can itself be said to understand. When is it merely manipulating and transforming symbols from one code to another? When does it understand? When is a human merely translating between some sort of input code and some sort of output code? Is the human brain merely a translation program in this sense, translating input data (e.g. sensory) to output data (e.g. motor)?

The best answer that we can come up with ▶



# If you don't find the logic you probably don't need

Meet the logic analyser family that spans a wide spectrum in design. It's a family you can rely on in hardware design, software test and debug and even system performance analysis. One that's equally at home testing and troubleshooting low-cost single processor designs or sophisticated multiprocessor systems.

You can choose from a wide selection of different logic analyser configurations with HP. And when you do, you'll have an analysis solution that can help accelerate your design cycles...and speed your products to market.

## **The 1630A and 1630D...for confidence in tackling the day-to-day logic problems.**

Choose one of these logic analysers and you'll have the combined power of timing, state, and software performance analysis in one convenient, low-cost instrument. The 1630A gives you 35 channels of state/performance analysis (to 25 MHz), or 8 channels of timing (to 100 MHz). In the interactive measurement mode, it delivers 27 channels of state and 8 timing.

The 1630D offers 43 channels of state/performance analysis or 16 timing. In the interactive mode, you have a choice of 35 state and 8 timing or 27 state and 16 timing.

As your primary tool in hardware test and debug, the 1630 provides new triggering power to help you isolate the source of timing errors. This includes pattern triggering ANDed with a transition or glitch, edge or glitch triggering, and time qualification of pattern triggering. This is the capability that helps you quickly solve difficult hardware problems such as timing errors, transient effects and handshake malfunctions.

Use the 1630 in software development and integration phases and you have sequencing, triggering, store qualification, and sequence restart power to isolate targeted areas of code and view just the measurement information you desire.

To optimize your system performance, the 1630 gives you a nonintrusive view of system software in action. One that lets you analyse system activity at the level of procedures and tasks instead of the instruction level. Histogram displays make it easy to spot software bottlenecks and inefficiencies. The result can be improved system performance, and a more competitive product...with minimal additional design effort.

The 1630 also gives you interactive measurement capability for greatly enhanced analysis power. The ability to cross arm and trigger between state and timing analysers helps you get to the problem source quickly when the difficulty could be either a hardware or software malfunction.

Throughout the development cycle, you'll find the 1630 easy to use. That's because menus simplify operation. Label assignments let you view results in your system's terminology. And inverse assembly, via low-cost peripherals, displays listings in familiar target microprocessor mnemonics.

## **The 64110A...a configurable analyser that can handle those complex problems found in multiprocessor environments.**

This logic analyser is, in reality, a number of different analysers, depending on how you configure it. For example, it can be a standalone timing analyser with 8 or 16 channels.

It can also be a standalone state analyser with up to 120 channels. You can combine timing and state with performance overview. Or, combine multiple state or timing analysers in the same station.





# analyser you need here... a logic analyser.

Put the 64110A to work in the hardware test and debug phase and you can allocate high speed timing resources. For example, you might choose sampling speeds to 400 MHz. The resulting 2.5 ns resolution lets you make high-resolution measurements to resolve timing margin problems.

In addition, the timing analyser provides new triggering capability. The dual threshold mode lets you trigger on marginal signal levels, which helps you spot excessive fan-out, bus loading problems, and slow transition times. Other trigger modes include time qualification of pattern triggering, sequential triggering, pattern triggering ANDed with a transition or glitch, glitch triggering, plus other modes that simplify the analysis of handshake problems.

In software test and debug, the 64110A gives you unequalled tracing, triggering, and store qualification power. With its master enable function, 16-level sequencer plus 8 user-definable terms for trigger, store qualification and count functions, you'll have little trouble locating the specific portion of code you want and displaying only the information of interest... even in the most complex multiprocessor software.

For system performance analysis, the 64110A gives you a nonintrusive view of software in action in the form of histogram and graph displays. The histogram modes provide a fast way to locate system bottlenecks and identify inefficient portions of software. These display modes help you identify a processor stuck in a loop, see where software went into the weeds, or spot activity occurring in a forbidden area. A graph mode shows software performance data in chronological order.

Interactive measurements between all analyser subsystems multiplies the power of the 64110A far beyond the capability of other logic analysers. Cross arming and triggering between any of the analyser subsystems helps identify the source of difficult hardware/software interaction problems, and resolves hardware/software fingerprinting issues.

In any phase, the 64110A is a pleasure to use. Directed syntax soft-keys guide you through setups and measurements with a minimum of

keyboard entries. Symbolic tracing means you interface with the analyser using terminology you're familiar with. And preprocessors with inverse assemblers let you view measurement results in familiar processor mnemonics. All of which lets you concentrate on the problem you're trying to solve...not the analyser.

## Choose both and you'll have your analysis needs covered.

When you combine both of these analysers in your lab, you have a cost-effective solution to the day-to-day test and debug tasks, plus the power to deal efficiently with those complex troubleshooting jobs.

So before you buy any logic analyser, be sure you explore the individual power of HP's standalone analysers... and the synergistic effect of a combination of instruments.

For complete details fill in the reply paid coupon overleaf.



HP-IB: Not just IEEE-488, but the hardware, documentation and support that delivers the shortest path to a measurement system.



**HEWLETT  
PACKARD**



here seems to be that understanding is bound up in terms of whether the input, the output and the feedback are all within the compass and purpose of the system. Understanding can then itself be seen as an internal modelling of the world — and from that perspective, modelling of understanding becomes less distinct from understanding per se.

What is the point of this philosophical argument? Merely that 'robot' is the category we must give to the species of composite computer system which is capable of directly sensing and manipulating its environment. And it is only in such a context that we can talk about understanding in the human sense. Of course we can simulate the robot (or the human) and inject the understanding system into a toy world which it is capable of sensing, and this has been done.

The proposition put forward is that it is sensory/motor context which is fundamental to understanding.

### Intelligent robots

The most obvious feature of the computers and robots of science fiction is their ability to converse in English. At first this sort of language ability appears to be necessary, but on second thoughts a number of problems emerge — particularly concerning the accuracy with which we can specify something in a natural language, and the verbosity involved in making sure the meaning is clear. However, language remains one of the greatest barriers to the accessibility of the computer.

Language processing is not the only complex task we must face. If we have taken our language ability for granted, except as contrasted with lower forms of life, we have also taken visual (and tactile, motor, etc) abilities for granted, until coming face to face with the problems of robotics and pattern recognition. Visual processing is giving us just as much of a headache as language. Furthermore, these perennial problems turn out to be not so unrelated as they first appeared to be.

The connection operates both ways. Artists and poets throughout the ages have freely used analogies from each other's art. Our language reflects that 'a picture is worth a thousand words', and today we may claim

that 'a novel is worth a thousand movies'. Philosophers have reflected on the language of art and of vision itself (Turb71a). Psychologists and neurologists have, at a number of levels, reflected on the language of vision and the language of the mind (Prib71a).

Neurologists have found that the mechanisms and transformations they have observed in the study of human vision are identical in nature with the processes used for the other senses. The functions of the brain for the different senses, and therefore for language as well, are the same. But these processes can only be perceived in terms of our visual maps of what occurs in the brain (Ecc167a).

The visual perspective may be characterised as follows. The pattern recognition which takes place in the retina is traced through the cortical layers. Different features of the patterns presented are recognised at succeeding levels; the lower the level, the more complex the feature or 'concept' recognised. The underlying levels use the simpler features recognised by the higher levels. The sequence progresses from specific areas to specific lines, to lines of specific orientation or rate of movement, and eventually to the more complex shapes and 'objects' (Hube79a, Mals73a).

The auditory pattern produced at the cochlea is transformed in a similar way when we perceive visually (if we map the auditory areas of the brain). We simply do not have the mechanism for dealing with musical composition and correlation of concepts derived from different senses are similarly difficult to identify.

Nonetheless, the pattern processing that occurs in the brain, despite our visual perspective, can be employed in a variety of ways — or in computer jargon, applications. We also find this with our more familiar computational tools. For example, the Fourier transform is employed in both vision and speech research.

The Fourier transform, however, is one of those rare techniques; we actually find it easier to think about in auditory terms than visual. Once we have transformed a visual pattern, we lose our orientation and understanding of it at a visual level. But we do understand it in terms of the frequencies (recent patterns) involved.

A more interesting example of a non-visual perspective is the linguistic metaphor employing another major technique of computer science — parsing. A scene may be broken down in the same way as language. Complex structures and concepts may similarly be broken down into simpler ones (Lern80a).

This view is the reverse of the previous transformational one in another sense too. The perspective here is coming from the deepest level toward the external input. But we may reverse this and employ a bottom-up parsing technique; building up the picture. This corresponds with the previous description of cortical layers. Interestingly, we represent parse information visually, using trees.

In fact, theories of the brain can and have been formulated in linguistic terms (Prib71a), and models of the world have been parsed in such a fashion (Powe83a).

It is at this point that the dividend is reached. The parsing technique of an appropriately universal linguistic theory may be applied to the language, the environment and the interrelationships. The hardware associative network or software logical description turns out to bear a close relationship to neurological evidence of linguistic and other sensory and cognitive processes.

The proposition put forward is that it is language which is characteristic of cognitive processes.

### Conclusions

These thoughts have been arrived at after considering research and writings on Artificial Intelligence and Cybernetics. The ideas are based on certain neuropsychological theories which attempt to explain human intelligence. These same ideas are the basis of a research project at UNSW involving the writing on a computer system which relates language input with other modes of input in a simulated environment (Powe83a).


After thirty years of relatively unsuccessful work on isolated language understanding systems, it appears that an acquisitive approach, placing the onus of the computer, or robot, is required. In this way the language of the world and the natural language used may be correlated; semantics actually has a real meaning.

### References

- (Derr77a) Derrick, J., *The Child's Acquisition of Language*, National Foundation for Education Research, Windsor, Berkshire, UK (1977).
- (Ecc167a) Eccles, J.C., Ito, M., and Szentagothai, J., *The Cerebellum as a Neuronal Machine*, Springer-Verlag, Berlin-Heidelberg-New York (1967).
- (Hube79a) Hubel, D.H. and Wiesel, T.N., 'Brain Mechanisms of Vision', *Sci. Amer. Vol.* 241(3), pp. 130-145 (September 1979).
- (Lern80a) Lerner, E.J., 'Computers That See', *IEEE Computer Vol.* 17(10), pp. 28-33 (October 1980).
- (Mals73a) Malsburg, C. von der, 'Self Organisation of Orientation Selective Cells in the Striate Cortex', *Kybernetik Vol.* 14, pp. 85-100 (1973).
- (Powe83a) Powers, D.M.W., *Neurolinguistics and Psycholinguistics as a Basis for Computer Acquisition of Natural Language*, Departmental Report 8301, Department of Computer Science, EECS, University of New South Wales, Sydney, NSW, Australia (February 1983).
- (Prib71a) Pribram, K.H., *Languages of the Brain*, Prentice-Hall, Englewood Cliffs, NJ (1971).
- (Samu59a) Samuels, A.L., 'Some studies in machine learning using the game of checkers', *IBM Jour. R&D Vol.* 3, pp. 211-229 (1959). Reprinted in Feigenbaum and Feldman, 'Computers and Thought', McGraw-Hill (1963).
- (Samu67a) Samuels, A.L., 'Some studies in machine learning using the game of checkers II — recent progress', *IBM Jour. R&D Vol.* 11(6), pp. 601-617 (1967).
- (Sear80a) Searle, J.R., 'Minds, Brains and Programs', *The Behavioral and Brain Sciences Vol.* 3 (1980). Reprinted in Hofstadter and Dennett, 'The Mind's I', Penguin (1982).
- (Turb71a) Turbayne, C.M., *The Myth of Metaphor*, University of South Carolina Press, Columbia, South Carolina (1971). 2nd Ed.
- (Turi50a) Turing, A.M. 'Computing Machinery and Intelligence', *Mind Vol.* 59, pp. 433-460 (1950). Reprinted in Feigenbaum and Feldman, 'Computers and Thought', McGraw-Hill (1963) and in Hofstadter and Dennett, 'The Mind's I', Penguin (1982).



**\$650**

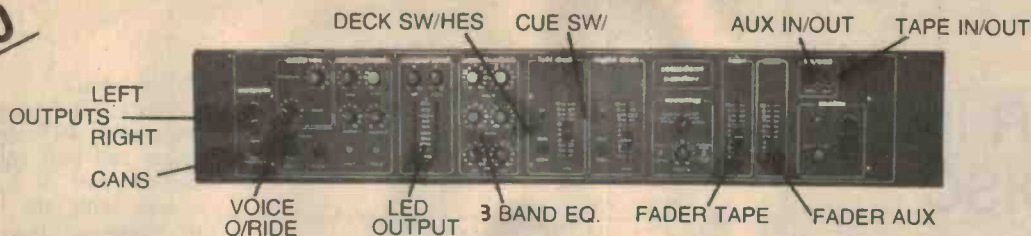

INTRODUCING THE PANTHER. SUPERB QUALITY DC SW/G. STEREO DISCOTHEQUE MIXING CONSOLE. THE ULTIMATE IN DISCO MIXERS INBUILT POWER SUPPLY (TOROIDAL) TRANSFORMER FOR 240 VOLTS +12 VOLT SUPPLY FOR CUE LIGHTS.

**\$220**



**STAGE CONTROLLER**

CHECK THESE FEATURES ON THE BEST CONTROLLER IN THE COUNTRY. ★ 18 SW/BLE FUNCTIONS ★ 1000 WATTS PER CH. ★ ROPE LIGHT EXT. ★ BUILT IN MIC ★ SW/S INDUCTIVE LOADS. MANUAL OR AUTO OPERATION.

**\$170**

ON EVERY PURCHASE OF STAGE CONTROLLER GET ONE ROPE LIGHT FOR \$120.



HOSE TYPE 10 METRE ROPE LIGHT 6 FASCINATING COLOURS. SUPERBLY MANUFACTURED BY OUR COMPANY IN AUSTRALIA. PRACTICALLY UNBREAKABLE — TREAD ON IT/THROW IT IN THE BACK OF YOUR TRUCK.

**\$1390**



**INTRODUCING SCORPION 3.**

18" BASS DRIVER 15" MID RANGE 100 WATT HORN POWER HANDLING 500 WATTS. HEIGHT APPROX 50" x 24" x 24" FREQ FROM 50 HZ TO 16 KHZ USE EITHER PASSIVE OR ELECTRONIC X OVER. THESE CABINETS TESTED AND USED WITH JADE HURLEY. ONE CABINET PER SIDE IN 800 SEATER VENUES.

**\$81**



MID RANGE VOLUME  
HORN VOLUME  
LED + OBM READOUT

THE ONLY 500 WATT PASSIVE X-OVER IN AUSTRALIA DESIGNED BY OUR COMPANY FOR MANUFACTURE BASS X-OVER AT 350HZ. MID RANGE AT 900HZ.

ALSO AVAILABLE ★ MINI MIST FOG MACHINES (CANISTER TYPE) \$800. ★ 4 ARM SPINNERS (SPACE BEACONS) \$220 + PIN SPOTS. \$49. ★ 750 WATT FRESNELS \$180. TEE BAR STANDS \$45. ★ MIRROR BALLS. DECEMBER SALE OF X CONCERT SOUND EQUIPMENT + LIGHTING. ★ DOUBLE W ★ 4560 ★ JBL HORNS. ALTEC 805 HORN DRIVERS, MONITORS. ★ 18FT WINCH UPS. TRUSSES. JANDS. 12x2 DIMMER DESK. ROCK IND. 12x2K BOARDS. ETC. CHECK OUR HIRE DEPT FOR ALL THE ABOVE EQUIPMENT PLUS PARTY HIRE — DISCO'S — STROBES — FLASHING LIGHTS — AMPLIFIERS. GUITAR AMPS MICROPHONES — WALKIE TALKIES — LOUD HAILERS — T/TABLES — CASSETTE REC.

**CASHMORE ENTERPRISES**

HIRE — SALES — INSTALLATION SERVICE.  
356 LIVERPOOL RD., ASHFIELD 2131  
(02) 799-6129 — 798-6732. TLX AA 74549



# PIONEER INTRODUCES NEW LASERDISC

**P**ioneer has finally launched its long-awaited Laserdisc players along with a range of videodisc packages for in-home use.

The Australian launch follows the successful release of Laserdisc in USA and Canada, latterly Japan, the United Kingdom and recently in Germany.

In January, 1981, Pioneer bought out all the interested parties in Discovision Associates in USA to become the sole owner. Pioneer also acquired world wide marketing rights for that optical Laserdisc system. This acquisition included the disc manufacturing facility in Carson, California, which has since been substantially remodelled. Pioneer also owns a disc replication plant in Kofu, Japan.

Les Black, Managing Director of Pioneer Electronics Australia said "response from both consumers and industry during recent shows and exhibitions has convinced Pioneer that this revolutionary product is ready to find a permanent place in the homes and boardrooms of Australia.

"On the home front," he said, "families will be able to enjoy what is a new dimension in home entertainment."

Laserdisc, as Pioneer describes it, 'stereo sound you can see' is poised to become the focal point of the home entertainment situation.

Mr Black went on to say "as an educational and merchandising tool. Pioneer's Laserdisc offers



unique advantages to appropriate business houses and the acceptance of Laserdisc for its industrial versatility had given the company great confidence about its future."

Pioneer will market their domestic Laserdisc LD1100 PAL format model. It is a video-

disc player which uses a laser beam to read the permanently encoded information on a 30 cm acrylic disc providing high fidelity sound of very high quality and a television picture equal to or better than those received from off-air broadcasts when viewed on a television monitor,

Pioneer claim.

The LD1100 can be simply integrated with existing television and hi-fi equipment, or become part of a component system with the result that recording artists covering all shades of musical tastes can be seen whilst they are heard.

A CX noise reduction system is included, which improves the signal-to-noise ratio up to 10 db.

A random access pause facility and ability to link the machine with teletext and interface it with personal or main frame computers makes the LD1100 extremely versatile.

Measuring just 525 mm wide by 143 mm high and 402 mm deep, the player is a very compact unit and it is anticipated that Pioneer will market the concept of a total integrated system consisting of speakers and monitor as they have successfully done in the USA and Japan.

Laserdisc went on sale at the end of October from approximately 100 retail outlets.

The LD1100 player is priced at \$1299 recommended retail and videodiscs will retail between \$35 and \$50 from the Pioneer dealers, depending on the title.

Considering that newly released compact audio disc players are selling in excess of one thousand dollars, the additional feature of colour television to the high quality stereo sound of Laserdisc makes it a most appealing product, according to Pioneer.

For further information, contact Mr Kevin Hoolihan, Manager, Laser Disc Systems, Pioneer Electronics Australia Pty Ltd, (03)580-9911.

## PORTABLE VIDEO SYSTEM

**T**he Dumont Galaxy 2100 video centre, new to Australia, combines a 13 mm VHS video cassette recorder with a 100 mm colour screen.

Aimed at business people who need to show video programmes outside the office, the Galaxy 2100 weighs only 7.2 kg and is no bigger than an attaché case. Both screen and recorder are incorporated in the one unit.

The Galaxy 2100 uses the PAL system and accepts standard 13 mm VHS tapes.

For further details, contact Results Audio Visual/Media-Craft, 7th Floor, 46 Holt Street, Surry Hills NSW 2010. (02)698-8799.



## LOW-PRICE DIGITAL MONITORS

**E**nglish maker B&W Loudspeakers has launched a new pair of digital monitors on to the Australian market, the DM110 and the DM220.

Essentially, the two units are similar in concept. The smaller DM110 is a vented design employing two drive units. The DM220 is a sealed-box enclosure employing three drivers,



## PHILIPS LAUNCH LASERVISION, TOO

Philips plans to release its Laservision video disc system for the educational, industrial and professional audiovisual markets. Laservision is the Philips-developed system based on the same revolutionary laser technology that is the heart of the Compact Disc.

Laservision discs can contain information in many different forms and are enormously versatile in educational, advertising and professional applications.

As well as conventional audio and video signals, Laservision can store complex graphics and text.

Philips Laservision for professional applications will be built around Philips state-of-the-art interactive television monitor which will allow individual users to retrieve single messages from the large array stored on each video disc.

This monitor has a touch-sensitive screen so that cumbersome

keying facilities are eliminated — users simply press the section of the screen displaying their area of interest. In a few seconds, that message is then located and displayed.

Philips will lend its expertise in creating software tailored to each application.

Further information from **Peter Brownlee, Philips Industries Holdings Limited, North Sydney NSW 2060. (02)925-3333.**



## PRAGUE, MADE IN SYDNEY


Sydney's Audiosound Laboratories has developed the Prague 8045 control monitor, a high-performance medium-size two-way loudspeaker system designed for small studios, control rooms and situations where accuracy and high levels are required.

Audiosound claims the 8045, which is fitted with 3 dB precision attenuators for final balance of upper-midrange and treble, has a tonal balance that is close to imported studio monitors.

The 8045's extensive crossover system utilises air-cored coils and polyester capacitors with an 18 dB/oct Butterworth filter.

Efficiency is 91 dB, and the 8045 is suitable for amplifiers from 10 to 100 W (RMS) output.

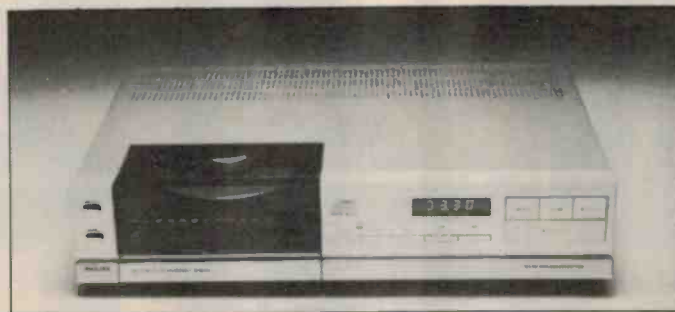For more information, contact **Audiosound Laboratories, 148 Pitt Road, North Curl Curl 2099. (02)938-2068.**



## PHILIPS DROP CD PLAYER PRICES

Philips' new Compact Disc digital audio players will be available at a much lower cost than earlier models.

Mike Orvis, group general manager of Philips Consumer Products, said that the price reduction demonstrated the increasing popularity of Compact Disc worldwide. These "perfect sound forever" disc players are supported by an increasing disc library with more than 500 titles already available and over 1,000 titles expected to be available before the end of 1983.

The new Compact Disc

players are the CD202 (top-loading) and the CD303 (front-loading). These players have the basic features of the earlier Philips models CD200 and CD300 but have an additional digital display facility. An LED digital readout on the front of each player displays either individual track playing time or total elapsed time of the disc currently playing.

The suggested retail prices of the CD202 and CD303 players are \$799 and \$899 respectively. For further information, contact **Philips Industries, North Sydney NSW 2060. (02)925-3333.**

## UHQR's 100-MINUTE TAPE

UHQR Sound Laboratories' new 100-minute cassette tape, the UHQR C-100, features a shell produced by the ULM — ultimate laboratory mechanism — method.

Under this system, the shell is moulded from a polycarbonate material and is so finely tooled that it takes up to 15 times longer to produce than conventional cassette shells.

The principle benefit, says UHQR Sound Laboratories, is

that the shell 'remembers' its initial design form and always returns to its original shape, even after exposure to very high temperature.

The UHQR C-100, which gives 50 minutes of recording on each side, uses a cobalt-formulated tape with an 'amazingly' low residual tape-noise level.

Innovations in the shell, such as specially concave silicon slip-sheets with carbon-sputtered dis-

charge stripes, are designed to provide what UHQR Sound Laboratories believes is perfect tape-spool support as well as being able to dissipate static build-up.

The UHQR C-100 cassettes, in gold packaging, are available as singles and in packs of six. They are priced at \$9.95 for a single cassette and \$59.95 for the six-pack.

For further details, contact **UHQR Sound Laboratories, 421 Forest Road, Bexley NSW 2207. (02)59-4727.**

## TOSHIBA'S FOUR-HEAD VIDEO

Toshiba's V-8700A video cassette recorder, now available in Australia, incorporates a four-head drum to enhance the 'still' and 'slow-motion' modes.

VCRs with two heads inevitably produce bar noise across the screen when in the still or slow-motion modes. This is because the heads must trace two recorded tracks.

Toshiba believes it has solved the problem with its four-head drum, the additional two heads being used exclusively for special-effect playback. These extra heads trace only one track.

Other features of the top-loading V-8700A, which uses the Beta system, include a wire-less remote-control headpiece, 3¼ hours of recording time and an audio dialing system.

For more information, contact **Toshiba Australia, 82-94 Talavera Road, North Ryde NSW 2113. (02)887-3322.**

with greater power-handling capacity and an extension in bass response over the DM110.

B&W Loudspeakers says the design brief for both models had three main requirements: high sensitivity (not less than 90 dB, 1 W at one metre); broad extended and linear frequency response; and a 'dramatic' reduction in production cost.

The end result is an Australian price tag of \$399 for the DM110 and \$599 for the DM220.

For further information, contact **Convoy International, 400 Botany Road, Alexandria NSW 2015. (02)698-7300.**







# Six linear tracking turntables reviewed

More than 60 years ago it was decided that only a linear tracking tone arm system could reproduce recorded sound with minimum distortion. So does a linear tracking system really have better tracking, better dynamics and lower distortion than the conventional pivoted tone arm turntables? Yes it does, but is it worth it?

Louis Challis

SINCE THE FIRST EDISON record player appeared, designers and manufacturers have been involved in developing tangential or linear tracking record players.

The original Edison recorder was the grandfather of the linear tracking record players; it used a mechanical lead screw to control the tracking of the sound head over the tubular recordings. Edison's equipment was far from being high fidelity as it converted the vertical modulation on the waxed tubular recording into a sound that only resembled and never faithfully reproduced the original sound.

Why Edison chose that particular method of tracking the record remains something of a mystery; there were many other ways in which he could have implemented his system.

A different method was used by another equally brilliant gentleman called Berliner who started a revolution with his circular, shellac recording discs. The difference between the two systems was very basic. The Berliner system was more practical and the circular recordings were far easier to mass produce than the Edison Ambirold gold recording system which it later eclipsed.

The trouble with the Berliner concept was that the replay system involved a pivoted tone arm that cannot position the headshell at exactly the same angle as the linear tracking recording head which was, and still is, the basis by which most masters are produced in the studio.

In 1906 that may not have mattered in terms of tracking angle error or even total distortion. But around 1920, and especially later on, a large number of clever gentlemen decided that the pivoted tone arm system was not the correct way to reproduce the sound. They decided that only a linear tracking tone arm system could reproduce the recorded sound with 'minimum distortion'.

Whether you like them or not, pivoted arms have one major attribute — they are very simple and generally inexpensive. More research has gone into their design than the average buff may realise. Even now there are a large number of engineers and scientists working on improving their design, providing better and cheaper tone arms.

But no matter how good you make a pivoted tone arm, it will always suffer one major disadvantage — that of tracking angle error. From 1906 to 1946 that really didn't matter because I do not believe anyone could really tell the difference in sound quality when they were playing a shellac record using a steel-tipped needle, or even a sapphire or diamond stylus.

In 1983, with microgroove records offering superlative performance, it is possible to hear and measure the difference. The tracking error manifests itself as distortion products which purists believe should be removed. So the purists, fadists and technical buffs search for the perfection that the manufacturer's glossy brochures tell you can only be found in a linear tracking turntable.

Since the late 1920s there must have been hundreds of patents taken out in innumerable countries for various versions of linear tracking turntables. Not surprisingly, very few of these ever got into real production. I have only seen a few dozen of the latest generation working, and even fewer of the earlier generations. There were many models produced that never reached this country.

I was fortunate enough to view a number of rare units in the Smithsonian Institute of Washington earlier this year, most of which were developed before the Second World War; the majority were outstanding in their conceptual innovation. I would have liked to have heard them play but these units had been put in glass cases to prevent just that. (If any readers know of such units in Australia I would love to have a look at them and, with the Editor's approval, publish some photographs).

Not surprisingly, the majority of the linear tracking turntables developed between 1920 and 1980 proved to be less than perfect, both technical and financially. (See our review of the Garrard Zero 1000 turntable ETI 1973). Not one linear tracking turntable developed during that 60 year period proved to be a commercial match for the more conventional, and equally imperfect, pivoted tone arm record players.

Many of the best units developed over the last ten years have involved esoteric and expensive concepts which achieved only

slight technical improvements over the best pivoting tone arms. The cheaper units managed to sell the concept but failed to capitalise on the most important attributes of the linear system; better tracking, better dynamics and lower distortion.

With these thoughts in mind I set out to review six units representative of those currently available in Australia: AIWA LX-70, Revox B791, Sony PS-X800, Technics SL-5, Toshiba SR-L7F and the Yamaha PX-3.

These units typify a wide range of units commercially in production at the present time; the marketplace has shown a positive acceptance of both the ergonomic and marketing features by which they are promoted. The major attribute of the smallest units is their physical size which is substantially smaller than that of most conventional record players.

By contrast, the largest units offer a technical performance which is excellent and which partially justifies the concept of linear tracking turntables. More importantly, this creates a niche in the market place which is sorely beset by the new competition from other systems.

These units are strikingly different in just about every possible way; their recommended retail prices range from \$299 to \$1269, their weights range from 5.2 kg to 12 kg and their measured performances were equally diverse.

The objective testing of these units in the laboratory was aimed at assessing their conventional characteristics, as well as the technical improvements achieved through the use of the linear tracking system. The most important parameters were frequency response, wow and flutter, tone arm resonant frequency, bandwidth (the 'Q' of the tone arm), speed stability and, most importantly, improvements in trackability.

The subjective performance of all the players was assessed with two new outstanding records; Verdi's 'La Traviata' featuring Joan Sutherland and Luciano Pavarotti (Decca SXDL7562) and Gustave Holst's 'The Planets' featuring Herbert von Karajan (Deutsche Grammophon 2532019).

I will examine each unit in alphabetical order; many are innovative and technically exciting. ▶



## AIWA LX-70

The AIWA LX-70 is described by the manufacturers as being a computer controlled, linear tracking tone arm system. It features a beautifully designed, lightweight plastic, moulded cabinet with rear-pivoted lid. Only a segment of the lid is clear acrylic, whilst the rest features a matt silver-grey finish, matching the base section of the unit. The lid is removable and the majority of the controls are located on the fascia.

AIWA has chosen to incorporate a host of electronic 'goodies', few of which are conventional in terms of record player control functions, while many are similar to the control features incorporated in the first generation of CD players.

From left to right across the fascia is an enlarged power ON/OFF switch, a row of seven very small programme select buttons, a switch labelled ALL CLEAR by which

one can cancel a previous selection and a novel switch labelled INTRO PLAY/LIST. After all that has been written in the last few months about programme selection, you are now probably familiar with the concept of the user being able to preselect a random choice of tracks on a CD disc. To be able to perform the same function on a minuscule record player the size of this unit may be a little more difficult to grasp.

AIWA has managed to achieve this with a tiny tone arm. On the underside of the arm they have incorporated a track sensor element, duplicating one of the acclaimed advantages of the CD disc system. Obviously AIWA was not the first to offer this capability but it is probably one of the first to achieve it in such a small package.

I believe that the provision of the INTRO PLAY/LIST function is more exciting as this provides the user with the ability to preview the first ten seconds of each track

on the record. You can then determine which tracks you want to listen to on those occasions when you don't want to listen to all of them.

The right-hand side of the fascia incorporates a recessed escutcheon with the main controls. At the centre of the unit is a stroboscope with a speed adjustment knob located immediately adjacent to it. Next to this are three pushbutton switches with illuminated bezel to indicate the function selected. The first button is REPEAT and the second and third buttons facilitate forward or reverse tone arm cueing across the record.

Three larger touch buttons are provided; one is to RAISE the tone arm and lower it, the second is for FORWARD SKIP and the third's for BACK SKIP, moving the tone arm by one track. Last, but not least, is the START/CUT control which is self explanatory.

## Linear tracking

The conventional tone arm moves across the record in an arc of a circle so that the path of the stylus is as shown. When a record is being cut, however, the cutting arm moves inwards along a radius towards the centre of the record. Thus the cutting path is a straight line unlike the arc of the replaying stylus.

This leads to the important point that the direction of the motion of the recording head, relative to the record surface, is a tangent to the recording groove at all times. A conventional stylus cannot move at a tangent to the record groove at more than two places. At all other points there will be a small angle between the direction of relative movement and a tangent to the groove.

Many people feel that a stylus which follows the path of the cutting head across the disc as accurately as possible is likely to achieve a more faithful reproduction of exactly what is on the disc than a stylus which moves at an angle to the direction of movement of the cutting head.


In the linear tracking system the tone arm does not swing in an arc, but moves from right to left along a fixed bar at the back of the record. The stylus moves in a straight line along a radius of the record so that tangential tracking is achieved at all points.

One of the major disadvantages of linear tracking systems is that the arm must be moved across the record surface by some type of motor drive system. This requires very careful design of the tone arm motor, if satisfactory performance is to be obtained.

Most manufacturers employ an optical feedback system to control the tone arm motor.

In the normal or equilibrium position a beam of light from a lamp is blocked off by a shutter of the tone arm so that it cannot reach a photoresistive cell.

If the record now rotates so that the stylus is closer to the centre of the record, the position of the tone arm will be changed by a small amount so that the shutter no longer prevents the beam of light from reaching the photoconductive cell. The current through this cell activates the tone arm motor which moves the arm inwards towards the centre of the record until the shutter again blocks the beam of light.

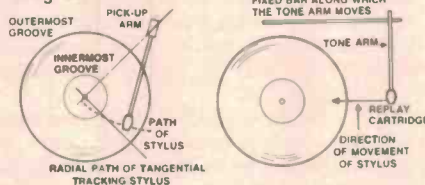

A conventional tracking system.

A linear tracking system.

A successful optical system of this type must be extremely accurate, since the record grooves are very small and close together. The tone arm motor system must also be carefully designed to prevent 'hunting' in which excessive or inadequate movement of the tone arm takes place and the system hunts for the correct position.

Linear tracking systems generally provide tracking angles to within a few tenths of a degree of the desired angle, whereas conventional systems may have angles of up to

a few degrees at some point on the record.

But what is the practical effect? Tracking error angles tend to introduce second harmonic distortion which, while obviously undesirable, is not nearly so objectionable as third harmonic distortion. There seems to be some controversy as to exactly how much distortion is introduced by such tracking angle errors.

The pickup arm of a conventional system will tend to 'skate' towards the centre of a record unless the correct amount of bias compensation is applied. If no bias or an incorrect bias is applied, the inner groove is likely to receive more force from the stylus; this will result in signals of an unequal amplitude in the two channels and is likely to cause the inner groove to wear at an increased rate.

These problems are said not to arise in linear tracking systems, whereas in conventional systems the application of bias is only a compromise; the required bias varies with the position of the tone arm on the record and with the modulation levels.

In a tangential tracking system the effective arm length can be relatively short and the equivalent mass low even if strong materials are used to obtain a highly rigid arm. This can bring the advantages of minimum vibrational levels and small resonance patterns, and hence cleaner reproduction.



In spite of their important advantages, linear tracking turntables must be very carefully designed if they are to be better than conventional systems. The intending purchaser would be well advised to try any linear tracking equipment very thoroughly before making a commitment to purchase.

Make and Model	Recom. Retail Price	Dimensions W x H x D mm	Weight kg	Speed Accuracy %	% Range	Wow %	Flutter Weighted RMS	Rumble dB	Tone Arm Resonance	Rise Rating
AIWA LX-70	\$465 (w/o cartridge)	330 x 88 x 330	5.2		±4.8	0.14	0.04	-60	15 Hz	8 dB
Revox B791	\$1100 (w/o cartridge)	449 x 142 x 395	9.1	0.01	±9.9	0.06	0.03	-61	9 Hz	9 dB
Sony SP-X800	\$1269 (w/o cartridge)	440 x 120 x 445	11.6	0.01	*	0.16	0.036	-62	12 Hz	1.5 dB
Technics SL-5	\$359 (with cartridge)	315 x 88 x 315	4.4	0.34	*	0.02	0.02	-61	13 Hz	9 dB
Toshiba SR-L7F	\$299 (with cartridge)	420 x 110 x 339	5.8	0.05	*	0.16	0.05	-64	14 Hz	7 dB
Yamaha PX-3	\$999 (w/o cartridge)	469 x 149 x 428	12.0	0.01	*	0.02	0.015	-62	7 Hz	10 dB

\* no adjustment



# AIWA LX-70

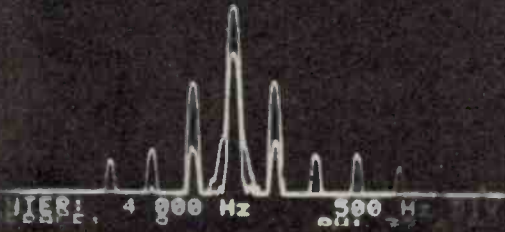
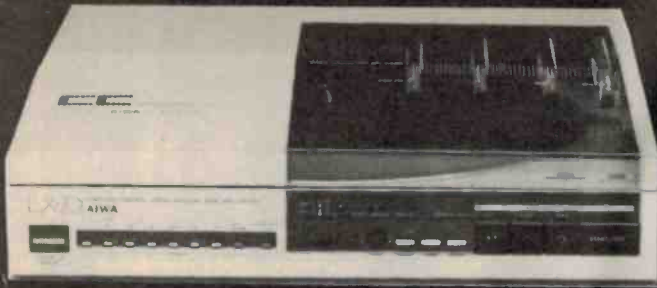


Distortion components of test record and cartridge. At tracked velocities of 15 and 19 cm/s at a pressure of 1.25 g; 10 dB/div; 20 dBV full scale.

## WOW AND FLUTTER

Wow	0.12% peak to peak
Flutter	0.04% weighted R.M.S.
	0.06% unweighted R.M.S.
<b>RUMBLE</b>	-60.0 dB weighted (Band Pass)
(Re 5.42 cm/sec)	
<b>SENSITIVITY</b>	Right Channel 0.86 mV/cm/sec
	Left Channel 0.82 mV/cm/sec

<b>FREQUENCY RESPONSES</b>	20Hz-20kHz (See Curves)
<b>SPEED ACCURACY</b>	Strobe Adjustable
<b>SPEED RANGE</b>	33 1/3 and 45RPM ± 4.8%
<b>tone ARM RESONANCE</b>	15 Hz (see graph) peak + 8 dB
<b>TRACKABILITY</b>	(Using Shure Disc TTR 103 400 and 4000 Hz)

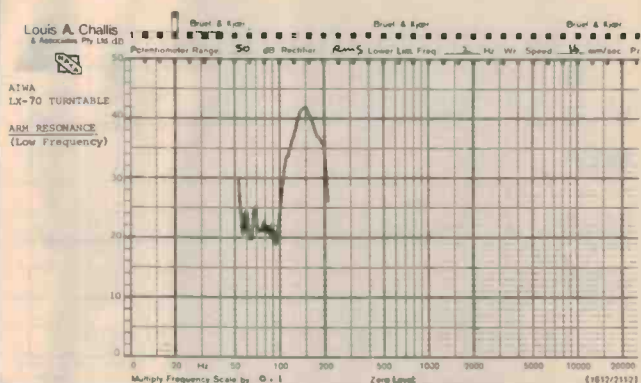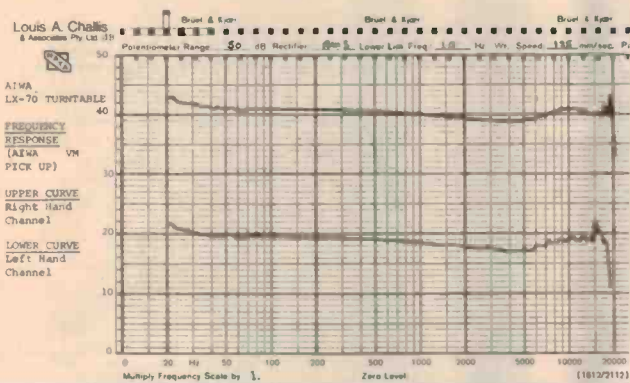

On the forward front edge of the console, inside the lid, are two controls; the tone arm sensor sensitivity control enables the electronics to be optimally adjusted to cope with various record configurations and surface reflectivities.

This control is essential as the record sensor operates on an optical system to detect the presence or absence of grooves. The illumination effect can vary dramatically, depending on the choice of record moulding material. The 33/45 speed control also functions as an auto/manual switch when the 45 rpm position is selected.

The tone arm has a toy-like appearance and uses an extremely lightweight, plastic mounting. On its underside, immediately

behind the fixed cartridge headshell, are a pair of protuberances. One of these incorporates a photoelectric emitter and the other is a matching optical detector. These cleverly sense the lead-in groove as well as the gaps between tracks required for both programme selection and the skip function.

Inside the cabinet at the rear of the unit is a small and cleverly designed motor-driven slide assembly. This runs on two tubular slides and supports the lightweight, plastic tone arm on a solid structure with full diecast gymbal assembly. This slide incorporates the miniature drive motors and electronic optical sensors to provide the parallel tracking function by detecting offset angle between the tone arm and the basic reference.

The most significant difference between this unit and the more expensive units is unquestionably the differences in tone arm and parallel slide design. In this unit they have apparently been designed with size and price, not performance, as the most important parameters.

The unit is, however, innovative and exciting as it contains a host of clever features by which a reasonable performance and some unusual, technical refinements are still achieved. The motor turntable is relatively light, featuring a precision diecast moulding with a total weight of less than one kilogram. With a unit as small as this, a greater platter weight would not really be possible.

The objective testing of the unit revealed a frequency response that is reasonably flat over the frequency range of 20 Hz to 20 kHz, but not quite in the same class as some of the other units that we evaluated. The measured 'wow' is surprisingly good and the 'flutter' is quite acceptable. The measured weighted rumble was -60 dB which is quite good and so the more conventional parameters of the unit are generally acceptable.

The tone arm resonance is relatively high at 15 Hz and it exhibits a resonance curve which is reasonably sharp in terms of its bandpass characteristics. More significantly, the tone arm does not provide facilities for pressure adjustment and was measured with a tracking force of approximately two grams. The cartridge and arm will only track effectively to 19 cm per second on the Shure TTR103 test record and thus could be expected to mistrack on many high velocity sections in some of the most difficult tracks of modern recordings.


However, this unit is better than many other moderately priced conventional record players and features a range of operational attributes which are technically exciting in those situations where space and/or weight are limited.

In the subjective testing the voices on 'La Traviata' came through exceptionally well. However, the transients produced by the music in 'The Planets' was just a little too tough for the trackability of the cartridge. ▶

Cartridge Type	Cartridge Rating	Overall Rating
VM Moving Coil	..	...
Shure TXE-SR Moving Coil	....	....
Sony XL30 Moving Coil	....	....
Technics P24 Moving Coil	...	...
Toshiba C-68M Moving Coil	..	...
Yamaha MC2000 Moving Coil	....	....



# REVOX B791


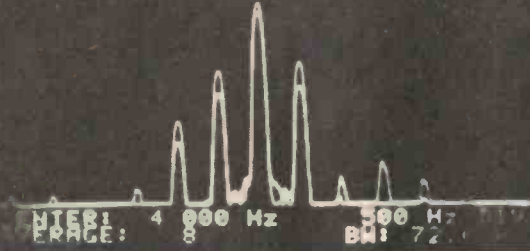


Distortion components of test record and cartridge. At tracked velocities of 19 and 24 cm/s at a pressure of 1.25 g; 10 dB/div; 20 dBV full scale.

<u>FREQUENCY RESPONSES</u>	20Hz-20kHz	(See curves)
<u>SPEED ACCURACY</u>		0.01%
<u>SPEED RANGE</u>	33 1/3 and 45RPM	±9.9%
<u>TONE ARM RESONANCE</u>	9.0 Hz (see graph) peak	±9 dB
<u>TRACKABILITY</u>	(Using Shure Disc TTR 103 400 and 4000 Hz)	

## WOW AND FLUTTER

Wow	0.06% peak to peak
Flutter	0.03% weighted R.M.S.
	0.04% unweighted R.M.S.
<u>RUMBLE</u>	-61 dB weighted (Band Pass)
(Re 5.42 cm/sec)	
<u>SENSITIVITY</u>	Right Channel 0.94 mV/cm/sec
	Left Channel 1.07 mV/cm/sec

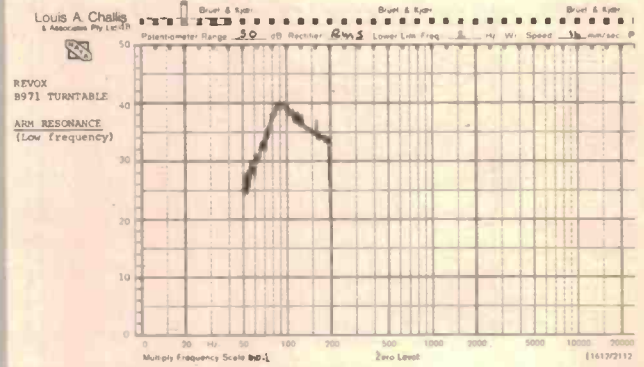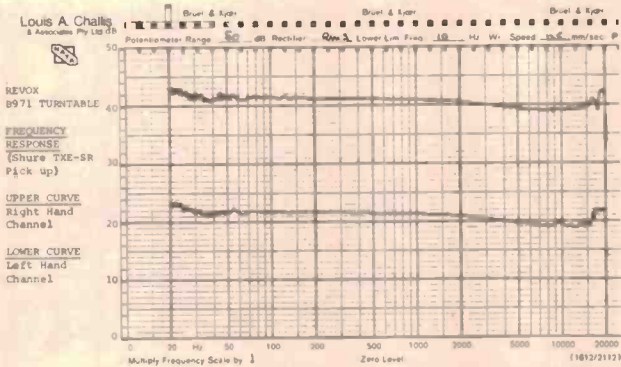

## Revox B791

The Revox B791 direct drive turntable is a completely different unit from the AIWA LX-70. It features a quartz-referenced, direct drive turntable incorporated in a relatively large enclosure with a very high, clear, hinged dust cover. This is required to provide clearance over the unusual linear tracking drive system.

The base of the unit is solid and heavy; the system exudes a solid, expensive feeling which the AIWA unit does not impart. The front of the unit incorporates a sloping fascia with three switches and bezels on the left and three on the right. Two speed control buttons at the centre flanking a digital display are for record speed and percent deviation.

The three switches on the left are the power ON/OFF switch and the other two are for selecting 33 rpm or 45 rpm. The three switches on the right are for cueing, forward and reverse, and raising and lowering the cartridge assembly.

In the centre, the two slides on either side of the bezel allow you to adjust the record speed precisely up or down (by ±9.9%) and shows the exact speed deviation in percent relative to the 33.33 or 45 rpm speeds. These features are, however, far less important than the linear tracking mechanism and its associated features.

Unlike all of the other systems reviewed this assembly pivots on the outer edge, therefore the cartridge assembly does not require a conventional tone arm. The tone arm is a relatively small assembly with which the designers could theoretically achieve any performance and resonance that they may desire. It is interesting that they have chosen to use a special cartridge assembly, designed specifically for this application by Shure Brothers of the USA.

Although the controls are generally simpler than those offered by the other linear tracking turntables, the electronics is still complex. Underneath the turntable cover is a large printed circuit board containing the complex electronic motor and turntable drive systems. This has been designed to provide very precise speed and drive characteristics; the pc board incorporates 31 integrated circuits, 26 transistors and numerous diodes, rectifiers and display units.

The turntable has a mass of 2.1 kg and achieves excellent wow figures of 0.06% and a good weighted flutter of 0.03%. The rumble is low at -61 dB and the general turntable characteristics are excellent.

It is undoubtedly the tone arm characteristics of this particular unit that are its forté. By discarding the conventional tone arm assembly, the designers have been

able to fully optimise the dynamic characteristics of the cartridge assembly which feature a 9 Hz tone arm resonance and an unusually broadband 'Q'.

The breadth of this resonance characteristic is substantially assisted by the use of the brush assembly in front of the cartridge. This also further assists the user by removing some of the dust.

The cartridge appears to be a special version of the V15-IV and this provides a smooth frequency response which is essentially ±2 dB from 20 Hz to beyond 20 kHz.

The Bruel & Kjaer test record which we used for this phase of the testing is not flat at the top end of the range and thus the results are substantially better than indicated on the level recordings.

The cartridge provides good trackability at recorded velocities of up to 24 cm/s, but fails to track perfectly at the highest level on the Shure TTR103 test record.

The subjective performance on both the 'La Traviata' record and 'The Planets' record proved to be outstanding and I believe that most listeners would be just as impressed as I was.

The overall performance of the Revox B971 is excellent, although not markedly superior to the best conventional, pivoting tone arm record playing system.





# SONY PS-X800



## WOW AND FLUTTER

Wow 0.16% peak to peak  
Flutter 0.036% weighted R.M.S.  
0.057% unweighted R.M.S.

## RUMBLE

(Re 5.42 cm/sec) -62 dB weighted (Band Pass)

## SENSITIVITY

Right Channel 1.27 mV/cm/sec  
Left Channel 1.25 mV/cm/sec

Distortion components of test record and cartridge. At tracked velocities of 24 and 30 cm/s at a pressure of 2 g; 10 dB/div; 20 dBV full scale.

## FREQUENCY RESPONSES

20Hz-20kHz (See curves)

## SPEED ACCURACY

Better than 0.01%

## SPEED RANGE



33 1/3 and 45RPM Not adjustable

## tone ARM RESONANCE

12 Hz (see graph) peak + 1.5 dB
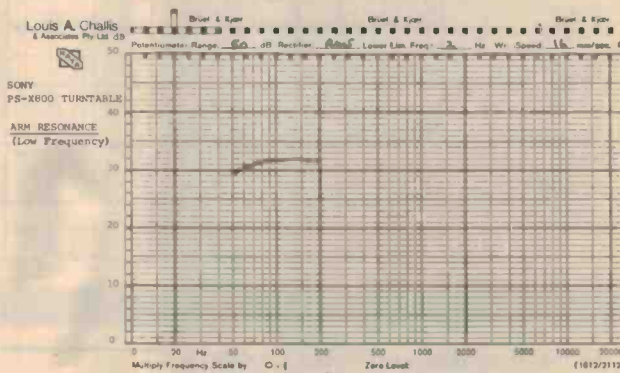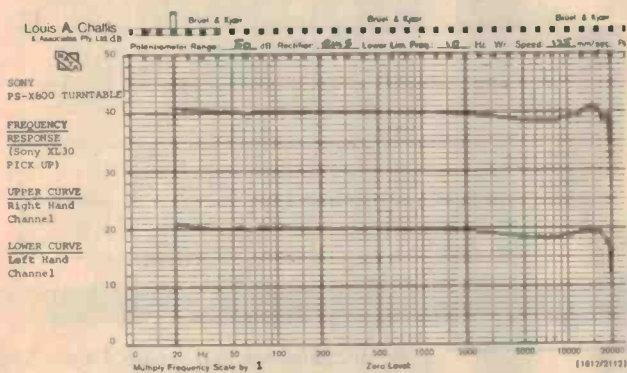
## TRACKABILITY

(Using Shure Disc TTR 103 400 and 4000 Hz)



## Sony PS-X800

The Sony PS-X800 is a very attractive, if somewhat heavy, unit. The appearance of this unit is very different from the first two units in that it features a very large turntable with a heavy, diecast cabinet base and a high upturn at the rear. The high upturn incorporates the unusual parallel tracking tone arm assembly.

The clear plastic cover hinges from the top edge of this upturn and in the well-travelled unit that we received, the lid would stay up only at its uppermost position.

The controls located across the front of the unit consist of a power ON/OFF switch on the left-hand side and the arm transport controls of RAISE/LOWER, FORWARD and REVERSE and a FAST transport control in the middle. This design approach for the controls is sensible as it allows very fine adjustment or, alternatively, by pressing two of the controls, rapid transport at will.

On the right-hand side of the panel is a small inset fascia through which the words LOCKED or the speed, 33 or 45, is displayed. This panel is not particularly well illuminated. You have to be standing directly over the unit, in subdued lighting, to determine whether the speed is locked and to read what the speed is. On the right-hand side of this fascia is a small button which changes the turntable speed

and beside this a REPEAT button by which the full record sequence may be recycled.

On the extreme right-hand side is a green START/STOP switch which, when activated, illuminates a bezel and raises the tone arm from its rest position, traverses it across to the turntable and lowers it onto the record.

The tone arm, labelled a 'Biotracer auto zero balance', allows for stylus forces in the range 0.5-3 gm by means of a control knob placed near the front of the turntable.

The tone arm runs on a single, polished stainless steel rod located at the rear of the unit. The arm and its assembly are relatively short and squat. It is a square section arm with a universal headshell coupling at its end. The unit was fitted with an XL30 moving coil cartridge which gives a very smooth frequency response; effectively  $\pm 1$  dB from 20 Hz to 17 kHz and only 3 dB down at 20 kHz. The cartridge tracked well at 30 cm per second on the Shure TTR103 test record and it provided a performance which was generally better than the majority of the other cartridges reviewed.

Unlike the other arms, this unit's tone arm resonance is low and relatively flat right across the full range of frequencies from 5 Hz to 20 Hz. How they achieve this I don't know, but the results are quite satisfactory. The turntable has a slightly high figure for wow of 0.16%, and an acceptable flutter of 0.036%.

These figures are most probably lower in

a new unit as the unit we received appeared to have been 'kicking around the world' before it got to us, and showed many signs of general abuse. The measured rumble was low at -62 dB and the main objective tests of the unit were excellent.

The turntable rests on four large well-designed pneumatic and rubber shock mounts which seem to work better than those installed on any of the other units.

'The Planets' played very well and came through the test with flying colours. However, the residual record warp in the 'La Traviata' record seemed to worry the tone arm assembly which did not track this particular record as well as most of the other linear tracking turntables. The performance on less warped records was excellent. Provided the records are not badly warped this unit will perform very well.

## Technics SL-5

The Technics SL-5 direct drive automatic turntable is an extremely neat unit with avant garde design features which will endear itself to many users. This is a small unit, even smaller than the AIWA LX-70.

In typical Japanese fashion, this unit is 'something yet again' when compared to any of the other units. It is a more economical unit, based on the design principles developed to such a high degree in the much more expensive SL-10 linear tracking turntable. ▶




# TECHNICS SL-5




Distortion components of test record and cartridge. At tracked velocities of 15 and 19 cm/s at a pressure of 1.5 g; 10 dB/div; 20 dBV scale.

<b>FREQUENCY RESPONSES</b>	20 Hz-20 kHz	(See curves)
<b>SPEED ACCURACY</b>		0.3%
<b>SPEED RANGE</b>	33 1/3 and 45 RPM	Not adjustable
<b>TONE ARM RESONANCE</b>	13 Hz (see graph)	peak = 9 dB
<b>TRACKABILITY</b>	(Using Shure Disc TTR 103 400 and 4000 Hz)	

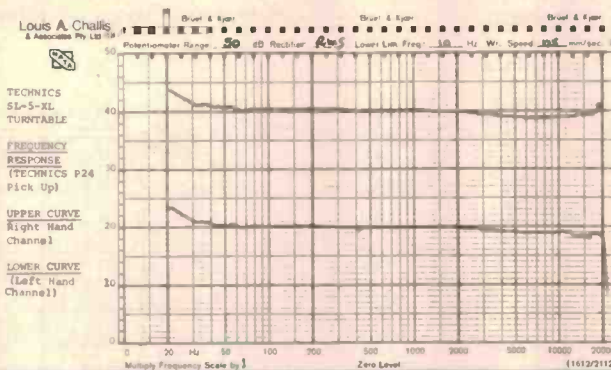

## WOW AND FLUTTER

Wow	0.02% peak to peak
Flutter	0.02% weighted R.M.S.
<b>RUMBLE</b>	0.035% unweighted R.M.S.
(Re 5.42 cm/sec)	-61 dB weighted (Band Pass)
<b>SENSITIVITY</b>	Right Channel 0.83 mV/cm/sec
	Left Channel 0.87 mV/cm/sec

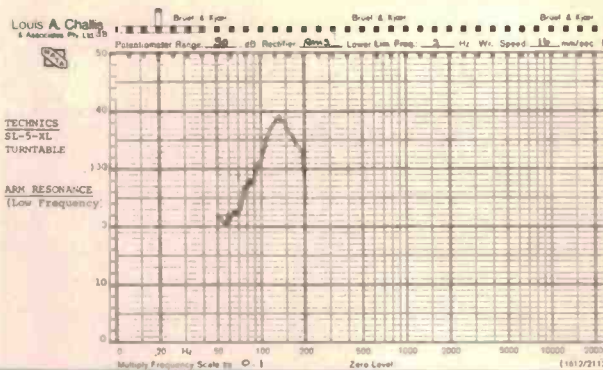

The first thing that catches your eye with this particular unit is the way that the linear tracking mechanism, together with tone arm assembly and cartridge are all attached to the lid of the unit. When the lid hinges up they hinge up with it, achieving what must be one of the smallest and neatest designs of record players (irrespective of type) on the market.

The dimensions of the unit are so small (315 mm x 315 mm x 88 mm) that one must be impressed by the ingenuity of the designers who have put so much into such a small package.

The lid of the unit, unlike the AIWA, is clear right across its front and incorporates a calibrated scale on its rear edge. The tone arm incorporates an illuminated bezel so as to clearly indicate the position of the cartridge, even though you may be unable to see the cartridge below.

The controls are placed on the front edge of the front panel; an ON/OFF switch is on the extreme right-hand side, a small REPEAT button is near the centre, a cueing control switch is adjacent and two large buttons are for START and inward movement, and STOP and outward movement on the right-hand side of the panel. These controls are sensible and ergonomically well conceived.

The other controls are a single three-position switch inside the cover by which the 33 or 45 speeds are selected. There is also a stylus pressure control within the lid of the unit which allows for forces of 1, 1.25 and 1.5 gram.

The rear of the unit features a pair of coaxial sockets so that the signal lead may

## AIWA LX-70

Manufacturer: AIWA in Japan  
Distributor: AIWA (Aust) Pty Ltd, 14 Gertrude St, Arncliffe NSW 2205. (02)597-2388.

## REVOX B791

Manufacturer: Studer Revox, Regesdorf, Switzerland  
Distributor: Syntec International, 53 Victoria Ave, Chatswood NSW 2067. (02)406-4700.

## SONY PS-X800

Manufacturer: Hi-fi audio division of Sony Corp. in Japan  
Distributor: Sony, 33 Talavera Rd, North Ryde NSW 2113. (02)887-6666.

## TECHNICS SL-5

Manufacturer: Matsushita Electric Trading Co, Osaka, Japan  
Distributor: National Panasonic (Aust) Pty Ltd, 95 Epping Rd, North Ryde NSW 2113. (02)887-5333.

## TOSHIBA SR-L7F

Manufacturer: Toshiba Corp, Tokyo, Japan  
Distributor: Toshiba (Aust) Pty Ltd, Cnr Talavera and Alma Rds, North Ryde NSW 2113. (03)887-3322.

## YAMAHA PX-3

Manufacturer: Yamaha Nippon Gakki Co Ltd, Hamamatsu, Japan  
Distributor: Rose Music, 28 Kent St, Belmore NSW 2142. (02)750-8999.

be disconnected and replaced by a longer or shorter pair of leads as required, a feature that some of the other manufacturers would do well to emulate.

The cartridge is one of the new "P" mount units (plug-in) and can be replaced by units from other manufacturers. These include Audio Technica, Shure, Ortofon and others who have cartridges available for this particular headshell configuration.

The wow on this unit is acceptable at 0.022% and the flutter is relatively low at 0.02%. The rumble is reasonably good at -61 dB while the tone arm resonance is only a trifle high at 13 Hz. The tone arm resonance 'Q' is moderately sharp but quite acceptable. The frequency response of the cartridge is excellent and a credit to the designers as it is  $\pm 1$  dB from 30 Hz to 20 kHz, with a 3 dB rise at 20 Hz.

Regrettably, the cartridge trackability only allows it to track satisfactorily at velocities up to 19 cm per second. This robs it of the ability to faithfully track the best and most difficult of modern records which have velocities three times higher than these figures.

Ergonomically, the Technics SL-5 must be one of the neatest, smallest and most attractive record players available anywhere. It is only because of poor cartridge trackability that it cannot be classified as a true all-rounder.

The subjective evaluation of the SL-5 exhibited an excellent performance with 'La Traviata'. However, it failed to achieve a superlative performance with 'The Planets' as the highest velocities on this record caused the cartridge to audibly mistrack.



# TOSHIBA SR-L7F



## WOW AND FLUTTER

Wow	0.16% peak to peak
Flutter	0.05% weighted R.M.S.
<b>RUMBLE</b>	0.07% unweighted R.M.S.
(Re 5.42 cm/sec)	-64 dB weighted (Band Pass)

## SENSITIVITY

Right Channel	0.81 mV/cm/sec
Left Channel	0.80 mV/cm/sec

Distortion components of test record and cartridge. At tracked velocities of 15 and 19 cm/s at a pressure of 2 g; 10 dB/div; 20 dBV full scale.

## FREQUENCY RESPONSES

20Hz-20kHz (See curves)

## SPEED ACCURACY

-0.05%

## SPEED RANGE



33 1/2 and 45 RPM Not adjustable

## TONE ARM RESONANCE

14 Hz (see graph) peak +7 dB
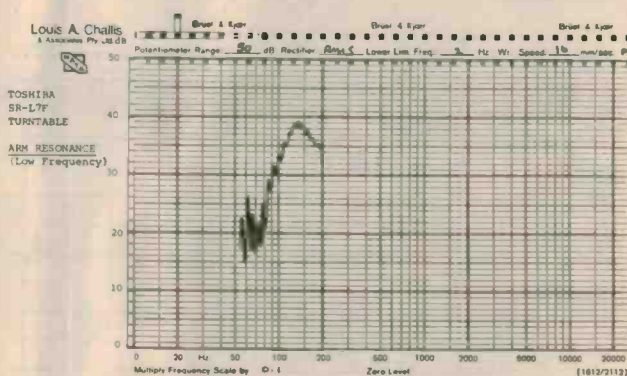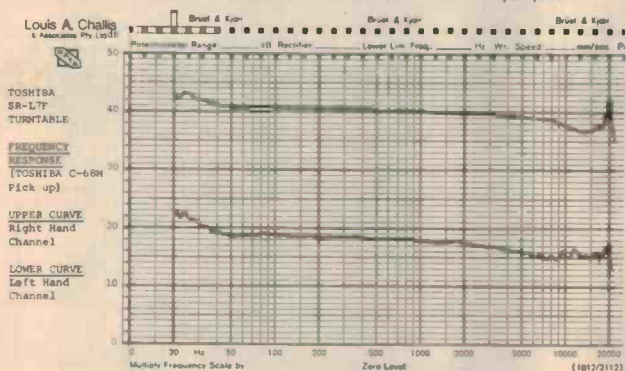
## TRACKABILITY

(Using Shure Disc TTR 103 400 and 4000 Hz)



## Toshiba SR-L7F

The Toshiba SR-L7F is another particularly good example of a fully automated linear tracking turntable. It is a trifle larger than either the AIWA LX-70 or the Technics SL-5, but it resembles both of these units because of the materials from which the plastic cabinet has been moulded.

The lid has a different two-tiered shape which, instead of covering the whole of the plinth, is split five-sevenths of the way across the front. This provides a fixed plinth where the main controls and displays are located. The lid is emblazoned at the front with the letters L7F and is similar to the AIWA player as it incorporates a clear section through which the tone arm may be viewed. This clear section is carried through into the fixed sloping section which contains bezel lights to indicate the selection of the repeat function and also indicates the speed selected.

On the fixed sloping edge on the right-hand side of the unit there are six large rectangular touch buttons. The upper pair are for 33/45 rpm speed selection and REPEAT which allows the entire record to be replayed. The central pair provide the FORWARD and REVERSE cueing functions while the front pair provide START/STOP and CUEING of the tone arm. The only other control is a push-on STAND BY switch located on the very front edge of the plinth.

The turntable automatically detects the size of the records by means of a very simple but effective mechanical switch and

consequently sets the rotational speed accordingly. If the automatic selection function happens to be incorrect then all you have to do is touch the speed selector switch to correct the mistake.

Under the plastic cover, which tilts up clear to the plinth, there is a simple tubular tone arm with a universal headshell assembly. This will accept a wide range of moving coil or moving magnet cartridges. The cartridge supplied is a Toshiba C-68M which is a normal issue with the turntable, however, it fails to optimise the dynamic characteristics or achieve the full performance that the turntable is capable of providing.

The arm and cartridge are attached by means of a rugged, precision assembly incorporating a photoelectric detection system to determine the carriage advance requirements. This part of the system, as we observed with most of the units evaluated, is very effective; it certainly avoids most of the problems which plague the conventional pivoting tone arm.

The short tone arm in this unit has a resonant frequency which is a little high at 14 Hz; it would probably perform better with a slightly heavier cartridge. The tone arm resonance is moderately sharp with an acceptable 7 dB rise in response at the peak frequency.

The turntable is a well machined diecasting, without user adjustment provided for the rotational speeds which were low by -0.5%. The turntable drive system is achieved by use of a direct drive using a dc servo motor with adequate

torque; this produces a moderately high level of wow at 0.16% and a reasonable flutter performance of 0.05% (RMS weighted).

The unit has a rumble figure of -64 dB which is very good and lower than any of the other units.

The moving magnet cartridge type C-68M does not achieve a very good frequency linearity performance as its response is +3 dB high at 20 Hz, ±1 dB from 30 Hz to 8 kHz and -3 dB from approximately 10 kHz to over 18 kHz. This frequency response differs substantially between left and right channels and indicates that either the parallel tracking is not as precise as it should be or that the frictional drag on the slide mechanism is too high.


It is significant that the cartridge does not track particularly well and will only track to 19 cm/s (the third highest velocity) on the Shure TTR103 test records. This is a shame as most of the other parameters are reasonably good and this desultory performance by the cartridge detracts from what would otherwise be a reasonable performance.

Mechanically the Toshiba unit is solid and reliable. It is a joy to use but the cartridge performance detracts from the sparkling sound that this unit should be offering.

During the subject evaluation with 'La Traviata' the performance was outstanding. However, with the highest velocities on 'The Planets', which most certainly exceed 40 cm/s, it failed to track faithfully. ▶




# YAMAHA PX-3

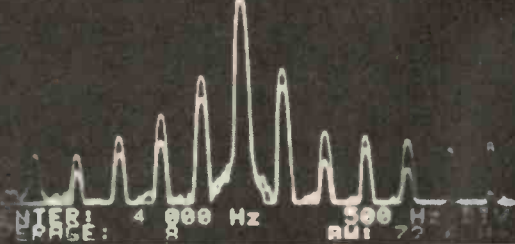


**Distortion components of test record and cartridge.** At tracked velocities of 19 and 24 cm/s at a pressure of 1 g; 10 dB/div; 50 dBV full scale.

<b>FREQUENCY RESPONSES</b>	20Hz-20kHz (See curves)
<b>SPEED ACCURACY</b>	+0.01%
<b>SPEED RANGE</b>	33 1/3 and 45RPM Not Adjustable
<b>TO NE ARM RESONANCE</b>	8.0 Hz (see graph) peak +10 dB
<b>TRACKABILITY</b>	(Using Shure Disc TTR 103 400 and 4000 Hz)

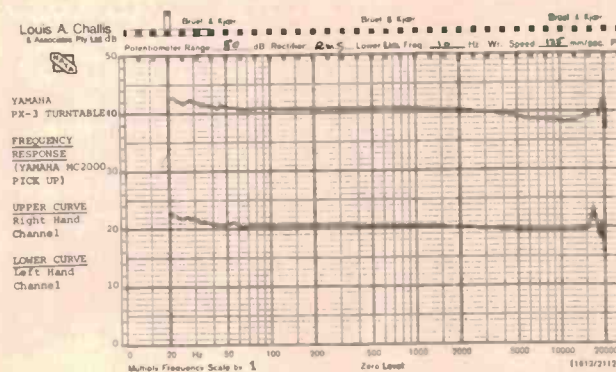

## WOW AND FLUTTER

Wow	0.02% peak to peak
Flutter	0.015% weighted R.M.S. 0.02% unweighted R.M.S.
<b>RUMBLE</b>	-62 dB weighted (Band Pass)
(Re 5.42 cm/sec)	
<b>SENSITIVITY</b>	Right Channel 0.033 mV/cm/sec Left Channel 0.035 mV/cm/sec

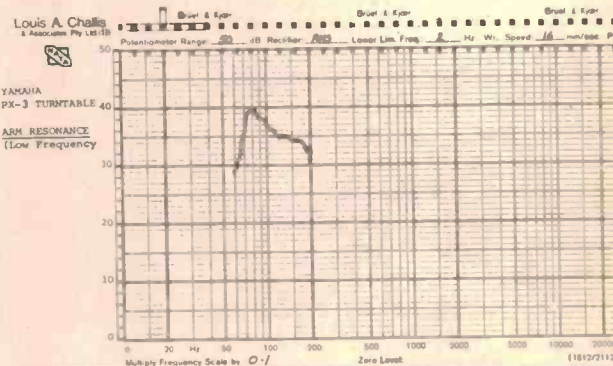

## Yamaha PX-3

The Yamaha PX-3 is the largest of the six units reviewed. This seems to typify one of Yamaha's design philosophies, designing units which are dramatically different to those of their competitors.

The first thing that strikes you about this unit is the unusual shape of the clear acrylic lid. Instead of being rectangular and angular, as are most of the other units on the market, the lid of this unit follows the circular contour of the turntable over one section and incorporates a sloped angular profile over the rest of the front. Surprisingly, the cover incorporates a rectangular notched profile to clear the elevated platform at the rear of the plinth.

The visual impression that this creates is of an expensive and complex form designed to cover the critical sections of the record player. This also frees the controls from the restriction created by the clear dust cover.

The turntable is extremely heavy with a weight of 12 kg, even outdoing the Sony which weighed in at 11.6 kg. Its major attributes include the very clear and large controls on the leading edge of the plinth. On the left-hand side is a power ON/OFF switch and a record speed selector switch; this illuminates on one side or the other to indicate the selected speed. These LED speed indicators are matched on the right-hand side by an illuminated bezel to indicate that the speed has been 'locked' by the crystal-controlled circuitry.

The turntable itself features a 1.6 kg

diecast turntable which is driven by a quartz, phase-locked loop, servo, direct drive system incorporating a four-phase, eight-pole, coreless dc Hall-effect motor. This is a pretty effective drive system and it achieves an excellent wow of 0.02% and an even better flutter of 0.015%. The rumble is -62 dB and so this turntable is right up with the best of the turntables available on the market.

It is the tone arm design and presentation which is the 'piece de resistance'. This must be one of the most technically advanced tone arm support and drive systems available anywhere. The way Yamaha have executed it is unquestionably one of the most complex and advanced that I have seen.

Yamaha's approach to this involves a massive slide assembly with a large and complex machined structure. This incorporates a photoelectric tracking error sensing system by which the servo drive system detects tracking error angles created by the pivoting of the tone arm. These forces are created as a result of forces exerted by the two side walls of the 'V' groove in which the stylus is tracking. The net tracking error achieved by this system is claimed to be less than 0.15° and the tone arm smoothly and effectively traverses any record, provided the record is not damaged.

The tone arm itself features a relatively short tubular structure with a tone arm resonance which we measured at 8 Hz, although the literature indicates that this

should have been at 12 Hz. The difference between our measurement and theirs must be attributed to an incorrect adjustment of either the counter weights or headshell weight and I believe I may have misinterpreted the instructions in the handbook.

The cartridge provides a very smooth frequency response which is ±2 dB on one channel and ±1 dB on the other channel. The cartridge supplied with the unit was a Yamaha MC2000 moving coil cartridge which the manufacturer's literature claims has the lowest equivalent mass of any cartridge in the world. The weight was claimed to be 0.059 mg which is intended to convey the concept that the unit provides superior trackability. Our testing did not fully substantiate this claim as the cartridge did not perfectly track the highest level on the Shure TTR103 test record.

The cartridge uses a 30 μm seven-strand wire for its cantilever suspension and two types of rubber dampers for variable damping of the cartridge assembly.

The subjective testing of the unit with 'La Traviata' and 'The Planets' revealed a particularly smooth performance which indicated that it was better than the objective test measurements showed.

Like the Sony model, this unit features gold plated leads and exemplifies the advanced engineering approaches that need to be applied to linear tracking turntables; optimum performance is based on the design criteria.



## Conclusion

The subjective evaluation of the six record players was an extremely difficult task. The smallest units, the AIWA LX-70, Technics SL-5 and the Toshiba SR-L7F, were in many respects the neatest to use. However, they each suffered from the choice of cartridge in which the low level of trackability impaired their ability to provide the highest performance which most purchasers would be looking for in a linear tracking turntable. Notwithstanding, these three units shine in terms of their compact size, and their cartridge performance disabilities are partially compensated for by user convenience and ergonomic design.

Each of these three units exemplify some of the best features of Japanese innovative design, albeit in slightly different directions. The AIWA LX-70 provides some of the best features of the CD player for those people who are attracted by the advantages of a record player in which you can select the track you want to play. The design of the tone arm limits the dynamic performance and, in particular, trackability and in this unit a better cartridge would not necessarily enhance the quality of reproduction.

By contrast, the Technics SL-5 is the best unit of the six when it comes to avoiding the scratching of your records, as when you lift the lid you also lift the tone arm. The price of this unit is also attractive and it can be easily improved by choosing a better cartridge than that supplied.

The Toshiba SR-L7F is sensibly designed for shelf mounting and provides a striking appearance, excellent ergonomic design and reasonable technical performance. The tracking and trackability of this unit can also be readily enhanced by a better cartridge which would undoubtedly provide a much more exciting result.

The Revox B791 is a particularly large unit; its ergonomic features combined with cartridge trackability make it extremely attractive. Although the controls are simple their major attribute is their 'user friendly' layout, which is superior to that offered by all the other units. This particular unit tracks warped records better than any of the other units and consequently makes it a delight to use with old and badly warped records.

The Sony PS-X800 is an impressive record player and on good or above average records performs admirably well. It failed to perform well on a badly warped record as the vertical dynamics of the tone arm are inferior to the horizontal dynamics. Consequently, the Sony player does not provide perfect tracking on badly warped records. However, I must admit that the test record that I use specifically for warp tests is one that very few self respecting buffs would keep in their collection; it falls outside the limit that most people would regard as acceptable (thus its use for this specific test). The trackability of the Sony cartridge is, however, reasonably good and this record player is a well engineered and well executed piece of equipment.

The Yamaha PX-3 linear tracking turntable is an exciting piece of equipment, although its physical appearance is not as neat as some of the cheaper and smaller units. However, its technical performance is extremely good and it exemplifies the heights to which linear tracking turntables aspire. This particular unit tracks ordinary records very well, tracks warped records reasonably well and tracks difficult, high velocity content extremely well. It is very well engineered for what should be a long and trouble free life. It is also one of the most expensive of the units evaluated, so you tend to get what you pay for.

My overall impression of linear tracking turntables is that properly executed, they require complex engineering far outweighing the complexity of the best pivoting tone arms.

To achieve improvements in distortion and trackability requires superb engineering in the construction of their tone arm assemblies, for which the user must be prepared to pay. The cost of such engineering by and large outweighs the benefits when the final test results and improvements in performance are compared.

Finally, to make a linear tracking tone arm work the way it is intended to calls for skill and attention by the user which may not be achieved by simply following the manufacturer's instructions. With all our laboratory facilities we experienced problems and so it is reasonable to suppose that you might experience more. ●

# "...offer a performance bordering on the superlative."

Louis Challis, ETI.

This statement, made by one of Australia's highly respected hi-fi critics, is no exception.

The Danish JAMO Loudspeakers are acclaimed world wide. Their unique way to solve the problems which plague ordinary speakers have made JAMO one of Europe's best speakers today.

No other speakers on the market feature all these benefits:

- Patented CBR-system (Centre Bass Reflex) which eliminates cabinet resonances and decreases distortion to an absolute minimum.
- Acoustically dead insert around tweeter and midrange ensures perfect stereo image.
- Optimum phase linearity assured by slightly curved front panel which position the drivers on axis.
- Acoustic attenuators.
- Electronic overload protection.

If you are considering spending from \$400-\$2000 on a pair of loudspeakers make sure that you arrange an audition of the incredible JAMO Professional loudspeakers.

Please contact us for brochures, reviews and your nearest dealer.

SCAN AUDIO PTY LTD  
P.O. Box 242,  
HAWTHORN, VIC. 3122.  
Phone (03) 819 5352

**JAMO** HI-FI

CBR-1304  
130 watt RMS  
\$1095.00 incl. stands





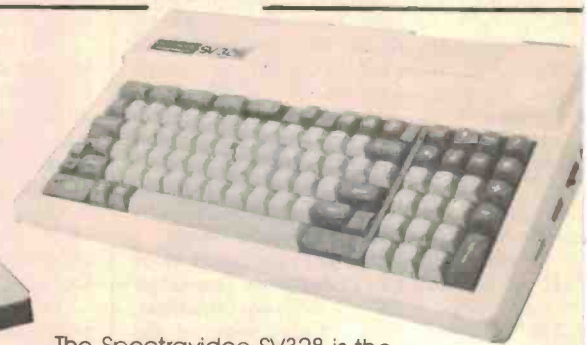
# Where to go for Spectravideo?

Sydney's largest stockist of VIC 20 and C64 utilities and software are proud to announce that a complete range for Spectravideo is now available ex-stock.

The remarkable Spectravideo SV318 is packed with features with a comprehensive range of state-of-the-art software available \$499\*



The Spectravideo SV328 is the computer for the small business that doesn't plan to stay that way. It offers so many features and advantages we couldn't start to mention them. Come in for a demonstration. \$799\*

The Commodore 1541 Disk Drive. Uses standard 5 1/4 Inch floppy disk and stores up to 170,000 characters of program or data information. Unit includes own microprocessor and memory system. \$499\*



The Commodore 64 needs no introduction and are available ex-stock. \$499\*



## Commodore stocks include:

Commodore 801 Printer	\$399*
Commodore Printer/Plotter	\$299*
Commodore Datasette	\$49.75*
Commodore 1701 Colour Monitor	\$499*

## Programming Aids for C64

Simons Basic	\$80.00*
Hes Machine lang. Monitor	\$59.95*
Ozi Sprite Generators (cassette)	\$19.95*
Ozi Typing Tutor (cassette)	\$19.95*
Ozi Typing Tutor (Disk)	\$24.95*

## Computer Education

Gortek and the microchips	\$50.00*
Introduction to Basic part one and two	\$40.00*

## Business Software for C64

Easy Script (Disk)	\$100.00*
Easy Mail (Disk)	\$80.00*
Easy Spell (Disk)	\$80.00*
Easy Calc Result (Cartridge)	\$319.00*
The Filing Assistant (Disk)	\$144.00*
Personal Finance Assistant (Disk)	\$119.00*
Debtors 64 (Disk)	\$119.95*
Creditors 64 (Disk)	\$119.95*
General Ledger 64 (Disk)	\$119.95*
Masterfile 64 Ozi (Disk)	\$39.95*

## C64/VIC 20 Game Cartridges

Now available

Super Lander	\$39.95
Kickman	\$39.95
Sea Wolf	\$39.95
Bingo Math	\$39.95
Radar Rat Race	\$39.95
Clowns	\$39.95
Visible Solar System	\$39.95
Omega Race	\$39.95
Music Machine	\$39.95

These are just a few of our most popular programmes for Commodore. Come in soon and see the complete range. You still have until Nov 25th to enter Another Winning Spot Competition where you could win a Commodore 64. Entries available in store.

\* All prices listed are recommended retail, including sales tax, which is exempt in some business purchases.

# the Computer Spot

Shop C4 MLC Centre, Martin Place Sydney Tele: 235 297

Shop 35 Gallery Level Eastgate Centre, Bondi Junction  
Tel: 387 5208



## COMPUTER SYSTEMS LEGALLY 'GOODS', RULES JUDGE

**B**uyers and sellers of computer systems will be affected by a judgment of major importance made by the Honourable Mr Justice Rogers in the Supreme Court recently.

Sales of computer systems comprising both hardware and software constitute 'sales of goods' within the NSW Sales of Goods Act (1923), and the Commonwealth Trade Practices Act (1974), ruled Mr Justice Rogers.

The judgement provides ammunition for dissatisfied users faced with suppliers disclaiming responsibility for a system's deficiencies. It should put an end to the practice of selling software (packaged with computers at least) before it is fully developed — and allowing early buyers to sort out the deficiencies. Such products must now be of 'merchandise quality'.

The decision was part of an action brought by Toby Constructions Sales Pty Ltd versus Computer Bar Sales Pty Ltd.

Toby Constructions purchased a computer system which included Executive Five accounting, stock control, payroll, and (Wordstar) word processing software from the Ward Computer Company Pty Ltd — a company which the plaintiff also claims never existed.

It is claimed that the sale agreement included installation,

maintenance, periodic updating, and staff training. The system is claimed to be deficient and the action is against three defendants in respect of losses alleged to have been suffered as a result.

Two of the three defendants sued failed to appear and judgement has been signed against them for want of defence — with damages to be assessed.

The third defendant is Kevin John Morrissey. Mr Morrissey is cited as acting for himself only, or as an agent for the first defendant, and/or the second defendant and the Ward Computer Company.

Counsel for Mr Morrissey claimed that the Deed of Sale did not provide for the sale of goods, but for work to be done, materials to be provided, and perhaps for the transfer of intellectual property. It was alternatively submitted that the agreement embodied in the deed was divisible and in so far as there was a sale of the software, and the claims concerned only the software, software not being 'goods', the legislation did not apply.

In his judgement dealing (solely) with part of the Amended Statement of Claim,

Mr Justice Rogers said, "I come to the conclusion that a sale of a computer system, comprising both hardware and software does constitute a sale of goods within the meaning of both the Commonwealth Act and the State legislation. There is a sale of tangible chattels, a transfer of identifiable physical property . . ."

Mr Justice Rogers went on to note that "It may be a debatable question whether or not the sale of computer software by itself is sufficient to constitute a sale of goods within the meaning of the legislation I am considering. However, I have no doubt that the sale of a system in toto is within the legislation . . ."

Commenting upon whether software alone constituted 'goods', Mr Justice Rogers said, "I do not wish it to be thought that I am of the view that software by itself may not be 'goods' . . . the questions arising here are of considerable importance to the computer industry, and I think it is appropriate that those who attend to matters of law reform should consider whether or not legislative action is required to ensure the matter is put beyond argument."

The balance of the action was remitted to the District Court. Costs for the plaintiff were awarded against Mr Morrissey.



## DICK THROWS DOWN CHALLENGE TO IBM

**A**t a time when the top end of the personal computer market is somewhat saturated, it's a bold move to release yet another new model on to the Australian market.

Dick Smith Electronics has done just that with their latest entry to the computer stakes: the Dick Smith Challenger.

Dick Smith Electronics has been down a similar road a few years ago with the release of the System 80. That computer was made software compatible with the then acknowledged market leader, but sold for hundreds of dollars less.

The Dick Smith Challenger has been designed using exactly the same philosophy. A 16-bit machine, it is software compatible with all known programs for the IBM Personal Computer. IBM PC plug-in hardware is also compatible with the Dick Smith Challenger (even the keyboard).

The Dick Smith Challenger sells for less than half the price of a similarly configured IBM PC. A really usable IBM system costs around \$7000 but the equivalent Challenger sells for \$2990.

The expanded Challenger comes with over a thousand dollar's worth of business software included for no extra charge: famous Wordstar, Calcstar and mailmerge. They're the type of programs every business user needs (some may need not other software at all). The basic Challenger costs \$995.

The Challenger is fully backed up by Dick Smith's technical and service centres. For further information, contact Dick Smith Electronics. (02)888-3200.

## IBM PC TO BE MADE HERE

**I**BM Australia is expected to give a \$100 million-plus boost to local hardware and software manufacturing over the next five years.

Planned projects include: the manufacture of the IBM Personal Computer at Wangaratta, Victoria for export to New Zealand and South-East Asia, sourcing Australian-made components for other IBM equipment in addition to the PC; establishment of a Software Development Support Centre (SDSC) in Sydney to promote Australian software and the transfer of production of PC

software and documentation to Australia early next year.

The software centre will acquire software from local industry, encourage Australian software companies to develop products for marketing overseas and handle contracts awarded by the internal development division of the US parent company and other IBM subsidiaries to Australian software companies.

Mr Finn said, "IBM's plans for the SDSC fall in line with recent government encouragement of selected high technology industries. The largest of

the sunrise industries clarified in the Espie report was the software industry."

In announcing the move, IBM Australia's managing director Mr Brian Finn predicted that the various projects would create more than 200 jobs over the next five years.

The manufacture of IBM PCs will begin at the Wangaratta plant by July 1984. The assembly of IBM Selectric typewriters at the plant will be phased out. The plant will become only the third in the world for manufacture of IBM PCs.



## EPROM-BASED MICROBEE 'TOOLKIT'

**H**obart electronics company, High-Tech Tasmania, has released a new Microbee software package in EPROM (Erasable Programmable Read-Only Memory). The 4K package containing eleven programs was written by Tom Moffat, a software author well known to Microbee users.

Although any of the programs can be called from BASIC, most of the package has been directed at machine code programmers. Included is a debugging routine that freezes a program in mid-run and displays the contents of all the Z80's registers.

There's also a memory dump facility that provides a hexadecimal listing of any memory area, to both the screen and a printer.

A program called "BASCON" provides on-screen conversions among the decimal, hexadecimal, and binary number bases, a task that's usually done from tables in a book.

The largest program in the package, occupying just under half the EPROM, is a disassembler that converts pure machine code into human-readable assembly language. It can also display the meaning of ASCII-coded data sections of a program.

The disassembler allows a user to study the workings of any machine language program, including the latest high-speed games.

And for the ultimate games study, a program called

"SCRDMP" when called from within a program, provides an exact copy of the Microbee's screen to a C-ITOH printer, graphics and all.

For those who use the Microbee's editor/assembler as a word processor, there are some programs to make the task easier.

MANU sends control codes to a C-ITOH printer to set it up in manuscript format... big left margin, and double spacing.

WORDS provides a count of the words written into the EDASM's primary file. There's also a program to initialize the Microbee for use with a parallel printer. The Microbee does not do this itself except under BASIC.

Finally, three general use programs represent a "best of Tom Moffat" collection: The highly popular radioteletype decoding program, the facsimile "picture plucker" program, and the Microbee audio frequency counter.

The memory for the eleven programs, presented individually, would run to much more than 4K. The space saving is achieved by sharing subroutines among several programs. The package is available in a type 2532 EPROM for both the standard (2 MHz clock) Microbee, and the IC model (3.375 MHz clock). The cost, including postage and full instructions, is \$50.00. Inquiries to High-Tech Tasmania, 39 Pillinger Drive, Fern Tree, Tasmania 7101.

## PRO-LOG'S 32K RAM BUFFER

**A** 32K x 8 RAM buffer memory has been added to Pro-Log Australia's M980 and M910A PROM programmer control units. The Melbourne-based company has also announced that a 64K x 8 option will be offered when RAMS become available from memory-device vendors.

According to Pro-Log, the new option makes the M980 and M910A the only PROM programmers on the market to provide 32K memory support using CMOS battery-backed

RAM devices.

Existing M980 and M910A control units with 8K x 8 or 16K x 8 RAM buffer memory configurations can be upgraded to the new 32K option.

In addition to PROM programmers, Pro-Log manufactures and markets microprocessor cards and systems based on the STD bass concept.

For more details, contact Pro-Log Australia, 69 Canterbury Road, East Camberwell Vic. 3126. (03)836-3533.



## QUME TERMINALS

**A**nderson Digital Equipment (ADE) is stocking a line of CRT terminals from Qume, a division of ITT.

Qume terminals boast such features as a menu set-up mode instead of DIP switches, a 25th status line, sculptured keys contoured to fit the fingers, high resolution 7 x 9 character format with descenders for superior readability and separate programmable function keys.

ADE also offers a complete set of line drawing characters so

the user can create charts, graphs and forms.

The QVT 102 terminal combines simplicity with quality. This unit has all the standard Qume features in an 80-column 12" display.

The QVT 108 is a high power, low price terminal with 22 programmable function keys for power and flexibility. For further information, contact ADE, 14 Whiteside Road, Clayton Vic. 3168. (03)544-3444.

## MEGS GINGERS UP BIRTHDAY CELEBRATIONS

**A**ustralia's oldest personal computer club — the Microcomputer Enthusiasts' Group of Sydney (MEGS) celebrates its 7th birthday in January.

Formed in 1977 the objective of the club was (and still is) to provide a meeting place where microcomputer enthusiasts and beginners can get together and discuss all sort of problems about hardware, software or whatever, and to pass information on to other members.

Members of MEGS include engineers, technicians, hardware and software experts, sales personnel and everyone from students to retired people having computers as a hobby.

MEGS is an 'all-systems' club with most types of computers being represented including

Apple, Commodore, MicroBee and homebrew equipment.

MEGS has moved from its original meetings at the WIA Hall at St Leonards following sale of the building, and now meets in the hall at the rear of St Andrew's Presbyterian Church, 37 Anderson Street, Chatswood, on the third Monday of each month, commencing 7pm.

Club membership fees have been held at the 1977 level of \$15 per year. MEGS also has a new mailing address; P.O. Box 1309, Chatswood NSW 2067.

For further information contact the publicity officer Jim Hooke on (02)419-2568 or the president, John Whitlock on (02)628-1142 between 7 and 9 pm, or by coming along to any meeting, preferably the next!



# INVENTING THE STD BUS HAS GIVEN PRO-LOG A LOT TO ANSWER FOR...

And in the great Pro-Log tradition, they're practical, engineering-type answers. STD Bus is for real-world projects like  automation of manufacturing processes  production control systems  data acquisition  microprocessor design and test equipment.

## WHY IS STD BUS AN INDUSTRY STANDARD?

STD Bus has become the standard throughout a wide variety of industries (including education) because it has proved to be:  simple  reliable  flexible  compact size  highly modular  inexpensive. Also because it has a well-defined Bus structure, and because it can be sourced from over 100 independent manufacturers from the USA, plus some excellent Australian manufacturers.

■ **LIKE DOWN-TO-EARTH PRACTICALITY.** So engineers and technicians can design from board level, boosting productivity by implementing solutions much more quickly.

■ **LIKE INSISTENCE ON QUALITY AND RELIABILITY.** Just take a look at the range and capabilities of our products and then look at our client list. Our commitment to doing things thoroughly, really does work!

■ **AND NOW THERE'S SERVICE ACROSS AUSTRALIA!** We promise 7 day delivery of 90% of our product range. And all our products are covered by a 2 year limited parts and labour warranty.

We have representatives and distributors around Australia to help you with equipment selection and engineering advice.

We also hold seminars and courses, and can supply you with superb literature on our products and systems.



# SO WE'VE KEPT THE ANSWERS COMING!

## IT'S ALL PART OF THE PRO-LOG APPROACH:

■ **LIKE NO SECRETS.** That's right, when you buy our products you can do with them what you will. We'll even supply the source code on our software if you want it - including any driver routines for the board. Buy more than \$250 worth of any one board and you get the manufacturing rights to that board free of charge.

■ **LIKE THOROUGH DOCUMENTATION.** We're absolutely fanatical about completely comprehensive documentation and when you buy our equipment, that documentation's yours!

## ■ ANY QUESTIONS?

In the first instance, contact: Mr Mike Nash, Pro-Log (Australia) Pty. Ltd., 69 Canterbury Road, East Camberwell, 3126. Phone (03)836 3533 or STD FREE (008) 338020.

## PRODUCTS INCLUDE:

- Z80 and Z80A Processor Cards
- 8085A, 6800 and 6809 Processor Cards
- Memory Cards
- Digital I/O Cards
- Industrial I/O Cards
- Peripheral Interface Cards
- Miscellaneous Cards
- CMOS STD Cards
- Card Racks
- STD Packaging
- STD Development Systems.

To: **PRO-LOG** (Australia) Pty. Ltd., P.O. Box 1, Canterbury, Vic. 3126.  
Please send me more information on

Name \_\_\_\_\_

Position \_\_\_\_\_

Address \_\_\_\_\_

Company \_\_\_\_\_

Postcode \_\_\_\_\_

Phone \_\_\_\_\_



**PRO-LOG**  
(AUSTRALIA) PTY. LTD.

PRO-LOG (Australia) Pty. Ltd., P.O. Box 1, Canterbury, 3126.  
Phone (03)836 3533 or STD FREE on (008) 338020.

LEXICON ETI NOV '83 2067



## CHIP-8 LANGUAGE FOR THE MICROBEE

**D**reamcards, the Melbourne-based software producer, expects to release the Chip-8 language in EPROM for the 16-32K Microbee before the end of the year.

Chip-8 is a language devised by RCA for its low-cost VIP computer systems and used in such machines as the VP-111 (from RCA), the US-produced ELF series and ETI's popular ETI-660 Learner's Micro.

It is a simple language, ideal for beginners, using a small set of 'mnemonic' style instructions that are easy to learn and use. A huge range of software has been produced for the machines available and a software column for the ETI-660 project has been running for two years in ETI.

Dreamcards' Chip-8 for the Microbee gives 'Bee owners instant access to another large software base for which many fascinating and exciting programs have been produced. (Just look back through the '660 Software columns in ETI!)

It comes in a 4K EPROM, containing an interpreter/coder which can be inserted in the 'Bee's Network ROM space. It can also be custom-loaded into

other locations, if so desired. A detailed book on the Chip-8 language is included.

Dreamcards says the interpreter is fully compatible with earlier Chip-8 dialects. In addition, a number of extensions have been included, giving additional instructions which provide such things as full addressing capability over 64K, high-resolution graphics, standard alphanumeric characters (64 x 16), mixing of alphanumerics and hires with standard Chip-8 graphics, software sound-effects generator, joystick instructions, execution rate control (to speed up or slow down program execution), half-or full-tone cursor for standard graphics and a full-size screen display.

The interpreter is of the 'threaded' variety and is claimed to run four to five times faster than earlier Chip-8 dialects. The encoder/decoder converts the Chip-8 code to BASIC REM statements and back again. Chip-8 can be run from or mixed with BASIC to get the best of both languages.

Further details from **Dreamcards, 8 Highland Court, North Eltham Vic. 3095.**

## HEAD-CLEANING KITS FOR DISK DRIVES

**T**he Allsop 3 computer disk-drive head-cleaning kits are for 5 1/4" and 8" disk drives using ANSI compatible media diskettes.

The cleaning disk will remove deposits and negate static charge that can affect 'read' and 'write' functions, claims Allsop.

These kits can be used on single- or double-sided drives and contain two cleaning disks and a bottle of cleaning solution. Each disk can be used for 13 cleanings, providing up to 26 cleanings per kit.

Many computer owners don't realise that the drive heads should be cleaned regularly. It is recommended that drive heads should be cleaned every 40 operational hours, which implies that a heavily used drive would be cleaned once a week. There-

fore, one Allsop kit will clean one drive for six months.

The cleaning process is based on the use of a porous, non-abrasive cleaning disk and a proprietary cleaning solution. The solution is applied to approximately 40% of the cleaning disk. As the disk rotates against the heads, the wet/dry cleaning process removes contaminants and buffs the surface of the heads.

These kits are recommended by major hardware manufacturers and it is claimed that the cleaning solution and the material used for the cleaning disk is completely safe in all drives.

More information about these drive-head cleaners can be obtained from **Allsop Fidelity Accessories, P.O. Box 246, Double Bay NSW 2028. (02)357-2022.**



## SPHERE SET TO SPEAR TERMINAL MARKET

**A** new low-cost terminal, the Sphere CCT-100, for use with computer systems requiring an RS232C terminal, is available through Paris Radio Electronics.

Features include a low-glare 30 cm green phosphor monitor displaying 80 x 24 lines of text, a high-quality detachable keyboard and selectable baud rates from 75 to 19 200 bits per second.

In addition to its own range of editing and data transmission functions, the CCT-100 can also emulate three of the most commonly used terminal configura-

tions, the Hazeltine 1500, Lear-Siegler ADM-3A and the ADDS Viewpoint.

A sound generator is also provided, responding to the ASCII BEL (decimal 7) code and self-test code which is entered when the terminal is first switched on. This reports errors in the terminal's RAM, ROM, serial interface and keyboard.

The CCT-100 is priced around \$799, plus tax. For further information, contact **Paris Radio Electronics, P.O. Box 380, Darlinghurst NSW 2010. (02)344-9111.**

## LITTLE FLEX BOARD

**F**lex Electronics has released their model FMD-09 'Little Flex Board' single board micro-computer, capable of running an 'off-the-shelf' version of FLEX9 DOS.

The board has a 6809 micro-processor, WD2797 disk controller to handle up to four 5" floppy disks as standard (capable of double or single density operation), two RS232 ports, 56K of dynamic RAM and 4K of ROM with resident monitor and bootstrap routine.

The board measures 185 mm x 118 mm and enables users to construct a small but powerful

FLEX9 computer system.

Most applications software available to run under FLEX9 will run on the board with little or no patches to be made to the code. Several commonly used programs have been run on the board with performance and speed the manufacturers claim is comparable to other systems available.

The Little Flex Board is Australian-designed and made. For further information contact **Flex Electronics, 14 Doonkuna Avenue, Camberwell Vic 3124. (03)830-1668.**



## MOVE FOR LOGIC SHOP

One of Victoria's oldest computer outlets, The Logic Shop, has moved into the heart of Melbourne and the central business district.

New owner and managing director, Tom Zagon, said not only will The Logic Shop have an ideal location at 97 Franklin Street, but it will also have a new business policy — total computer solutions for hobbyists, small business and white-collar professionals.

Apple IIe, Apple III, Tele-Video and BBC personal computers are available from The Logic Shop, along with the NorthStar Advantage small-business computer. A full range of printers and peripherals are also available.

For more information, contact The Logic Shop, 97 Franklin Street, Melbourne Vic. 3000. (03)348-1488.



## DATA GENERAL DESKTOPS

Data General has announced the first four models of a new family of professional desktop computer systems.

The new computer systems provide a unique bridge for users as they range from a small diskette-based entry level system to a large 30 megabyte disk system, believed to be the largest available, according to Data General.

Data General's new Desktop Generation models 10 and 10SP computers run most of the popular 'off-the-shelf' software packages and Data General's own software, too.

Models 20 and 30 are more powerful systems designed to

run the full range of technical and commercial languages and operating systems, such as AOS, RDOS, COBOL and others.

Prices start at \$4500 for an entry-level system comprising a processor, 128K of memory, 380K of diskette storage and a display.

The top of the range is priced around \$17 500 for a four-terminal system with 1.5M of main memory, a 736K diskette system and 30M of Winchester type disk storage.

For further information, contact Data General Australia, 32 Ellingworth Parade, Box Hill Vic. 3128. (03)831-3234.

## COMPUTER TECHNICS


Computer Technics stocks a wide range of computer-related equipment, including the ETI light pen and radio teletype decoder.

This light pen for the Microbee works in the low-resolution graphics mode and connects directly to the I/O port. The kit comes fully documented with software examples and costs \$24.50, including p&p. A built-up 'Optiwand' light pen for the VIC-20 and the Commodore-64 is available for \$39.95.

The radio teletype decoder displays RTTY encoded messages on your monitor. The kit includes a DB15 plug and back-shell for connection to the Microbee and costs \$24.50, including p&p.

Computer Technics are now located at a new address, 123 Clarence Street (G.P.O. Box 4936) Sydney NSW 2000. (02) 29-7244.

NEW!

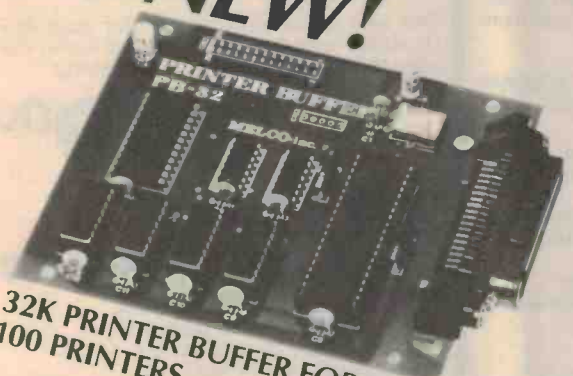

32K PRINTER BUFFER FOR MX 80, 82,  
100 PRINTERS

IMAGINE BEING ABLE TO SEND 32K TO YOUR PRINTER IN SECONDS AND LEAVING THE CPU FREE TO GET ON WITH WHAT IT SHOULD BE DOING.

- PB-32 BUFFER INSTALLS DIRECTLY INTO EPSON MX80, 82, 100 COST: \$144.00
- PB-32X CAN BE USED WITH MOST CENTRONICS INTERFACE PRINTERS COST: \$160.00
- PB-64X GIVES 64K BUFFER COST: \$300.00

**ALFATRON PTY. LTD.**  
**INDUSTRIAL ELECTRONICS**

1761 Ferntree Gully Rd.,  
Ferntree Gully, Vic. 3156  
Ph: 758 9000

Packing & postage  
add \$5.00 extra

### FLEX 9 Single Board Computer



**"LITTLE FLEX BOARD"**

- ★ 6809 Microprocessor
- ★ 2 serial ports
- ★ EPROM with monitor & boot
- ★ WD2797 disk controller
- ★ 64K DRAM
- ★ Runs 'off the shelf' FLEX9

★★ Australian made ★★

The FMD-09 "Little Flex Board" is manufactured in Australia by Flex Electronics. The board is a single board computer measuring 185mm x 118mm, capable of running a standard version of FLEX9. The board contains two RS-232 ports, normally dedicated to VDU and Printer. A Western Digital floppy disk controller WD2797 is used to control 5" disk drives, single or double density. 64K of dynamic RAM is supplied. The ROM socket contains a 2732 with resident monitor and FLEX9 bootstrap routine.

<b>Bare board only</b>	<b>Complete kit</b>	<b>Complete board A&amp;T</b>
<b>FMD-09-B</b>	<b>FMD-09-K</b>	<b>FMD-09-A</b>
<b>\$93</b>	<b>\$396</b>	<b>\$598</b>

Add 20% where sales tax applicable.  
Delivery \$6.50 overnight courier.  
FLEX9 is Trade Mark of TSC.

**Bankcard Welcome**



**FLEX** TECHNICAL SERVICES  
P.O. Box 75 Camberwell 3124  
132 Burwood Hwy Burwood Vic.  
(03) 288-4411.  
N.S.W. — Microbits (02) 89 3145



**LOOK AT THE  
LATEST  
FROM YAESU**



Cat D-2940

**All new, All mode, All powerful . . .  
Computer Aided Transceiver  
FT 757 GX**

Wow! What a transceiver. Everything you could EVER want . . . and then some! Even before its release, Yaesu have over 5000 on back order: that's just from the brochure!

It's the absolute latest state-of-the-art in design - in fact, its CAD/CAM (computer aided design, computer aided manufacture) ensures unbelievable standards of reliability.

LOOK  
AT THESE  
FEATURES:

- All mode - including FM with no optional extras
- All HF bands from 160 to 10m including WARC
- General Coverage Receive - 500 to 29.999MHz
- Computer Aided - use with your micro for external control
- Full 100W PEP/DC at 100% duty cycle
- Tiny 238 x 93 x 238mm (smaller than some 2m rigs!)

**NOT \$1399 AS RUMOURED . . .  
NOT EVEN  
\$1199 - ONLY \$999<sup>00</sup>**

STOCKS DUE IN MID  
TO LATE DECEMBER .  
BUT WILL THERE BE  
ANY LEFT FOR YOU?

Before  
buying  
elsewhere  
check the  
Dick Smith  
'Invisible  
Extras'

- ★ We honour Yaesu's 12 month guarantee: beware of others who may only offer you a 90 day warranty!
- ★ We have the largest service centre to back that guarantee. If anything does go wrong with your Yaesu, we can fix it fastest!
- ★ Dick Smith Electronics: Australia's largest supplier and Yaesu factory approved distributor and service centre.
- ★ Dick Smith Electronics have over 40 stores throughout Australia (with more to come!) plus over 200 approved re-sellers. You're never far from friendly help and service!



**FP 757 GX  
SWITCH MODE SUPPLY**

Neat! Fits under your FT 757 and you'd hardly notice it was there! Designed just for the FT757, makes your base station really look the part. 240V input.  
Cat D-2941

**\$299<sup>00</sup>**

**FC 757 AT  
Antenna Coupler**

The very latest auto coupler for your 757. Great for mobile & contest use - you can almost work into a piece of wet string!  
Cat D-2942

**\$399<sup>00</sup>**

**FIF 232 C  
RS-232C Interface**

Run your transceiver via your micro. Allows external control of VFO, memory functions, etc. 4800 Baud - so it's fast!  
Cat D-2943

Due in stock  
next month! **\$99<sup>00</sup>**



**AMATEURS:**  
CAN YOU MEET  
THE CHALLENGE?

of a  
**'Home Brew'  
UHF Transceiver**

Remember the good old days' of amateur radio? When an amateur built his own gear and was so proud of it! Sadly those days passed! With incredible advances in technology, it became economically and technically impossible to compete with commercially built equipment. **NOW** home brewing is here again! And what's more with the all new Dick Smith UHF Explorer, you'll end up with a transceiver less than the cost of a commercial unit - and not just as good - better! **YES!** A completely up-to-the-minute design featuring phase locked-loop frequency synthesis.

Exclusive  
to Dick Smith  
Electronics

Cat K-6300

**\$199**

**SPECIFICATIONS:**

Freq. Cov. 438.025 - 439.000MHz in 25kHz steps.  
No. of Channels 40  
Mode of Operation FM  
Supply 13.8v DC. Receiver 340mA with full audio output and all options. Transmitter 2A more (5 watt output).  
**Receiver**  
Sensitivity Dual Conversion Superhet  
Selectivity 0.4uV for 20dB quieting  
+/-7.5kHz - 6dB  
+/-15kHz - 60dB  
Better than 80dB  
**Adj. Chan. Reject**  
**Transmitter**  
Power Output 5W (typical)  
Deviation +/-5kHz  
Spurious Emissions Better than -60dB

**OPTIONS AVAILABLE**

**Upgrade Kit** (Cat K-6302)  
(Repeater, S meter, additional xtal filter & new front panel).

**ONLY \$24.50**

**UHF Antenna  
Kit**

Just for your UHF transceiver. Includes deluxe gutter gripper base, UHF co-ax and whip with cutting details. Also suitable for UHF CB.

Cat D-4014

**\$24<sup>50</sup>**

**HFC**

WHY NOT USE HFC FINANCE -  
It's so easy to balance your  
Xmas budget  
No repayments until March  
1984 (Approved applicants  
only)



**DICK SMITH  
HAM SHACK**

**bankcard**  
welcome here

**DICK SMITH Electronics**

See Page 101 for  
address details



**NEW  
70cm H/held**



**YAESU  
FT-708R**

Superb hand-held transceiver for those people constantly on the go! Covers full 438-439MHz band in 25kHz steps, with simplex AND standard 5MHz repeater split.

Look at these features:

● 10 memories ● Low 720g weight ● Switchable 200mW/1W output. NiCad battery (and charger!) and rubber duckie whip are included!

Cat D-2930

and it's only

**\$399**



**ECONOMY  
ALL MODE**

**SAVE \$50**

Cat D-2900

THAT'S THE  
DIRECTLY IMPORTED  
**DICK SMITH SS105S  
HF TRANSCEIVER**

Last chance for a real bargain! All band HF transceiver now reduced to clear - and look at the incredible specs. Where else could you get a transceiver of this type for under \$500? And with optional pcb, it will even do FM (great for 10m and for transverting!). Quick - before they all disappear!

WAS \$549

**\$499**

**AMAZING VALUE  
ONLY**

**ACCESSORIES FOR THE SS105S**

**Noise Blanker**

That really works! Minimise most types of pulse noise. Highly recommended for maximum transceiver capability. Cat D-2901 **\$29<sup>95</sup>**

**FM receive IF unit**

FM receive circuit to convert 9MHz to 455kHz and amplify and detect signals; equipped with a built-in squelch circuit. Cat D-2902 **\$59<sup>95</sup>**

**FM transmit IF unit**

IF circuit for FM transmit, consisting of a modulation circuit & IF amplifier. Cat D-2903 **\$34<sup>95</sup>**

**25 kHz monitor**

Plug-in pcb to give 25kHz for accurate calibration. Cat D-2904 **\$34<sup>95</sup>**

**100W Linear Amp**

100W Linear Amplifier. For when you've got that big ticket! Work the world - and more (more?) Cat D-2905 **\$249**

**Build your own  
Phone Patch**



Cat K-3054

**\$59<sup>50</sup>**

Not Telecom Permitted

Dick Smith Ham Shacks are located in the Dick Smith Stores listed below. You'll find a licensed amateur at each Shack.

● Sydney 125 York St 267 9111 ● Sydney 6 Bridge St 27 5051 ● Gore Hill 162 Pacific Hwy 439 5311 ● North Ryde Lane Cove & Waterloo Rds 88 3855 ● Gosford 315 Mann St 25 0235 ● Melbourne 399 Lonsdale St 67 9834 ● Richmond Bridge Rd 428 1614 ● Springvale Springvale & Dandenong Rds 547 0522 ● Brisbane: Buranda 166 Logan Rd 391 6233 ● Townsville Ingham Rd & Cowley St West End 72 5722 ● Toowoomba Bowen & Ruthven Sts 38 4300 ● Adelaide Wright & Market Sts 212 1962 ● Perth William St & Robinson Ave 328 6944 ● Cannington Wharf St & Albany Hwy 451 8666 ● Hobart 25 Barrack St 31 0800 ● **A621/1991**



# Proportional analogue joystick for the Microbee

The joy of a joystick! A twiddle of the fingers as your spaceship races through the cosmos, zapping space invaders and other various baddies with searing photon torpedoes. Or a tank on a battlefield, dodging the mines. Or your Tiger Moth bucks through the turbulence as your skilful fingers guide it gently towards a landing. Fasten your seatbelts, folks, because with this latest ETI project, you'll be joining the fun.

when you do. Here's where the really subtle control becomes available for such tasks as a precision landing of a lunar module. You can even write your name with it.

All analogue joysticks must use an analogue-to-digital converter. Many computers have them built in but the Microbee doesn't, so we have to supply one. Two, actually, one for vertical values and one for horizontal. Six-bit conversion is used, giving 64 different values each way. The seventh bit tells the joystick whether an X or a Y value is required, and the eighth bit feeds results back into the computer. So, the whole business works through one eight-bit port.

## A bit approximate


Before the joystick can be used, a short driver routine must be loaded into the computer, usually as part of the main program requiring the joystick. The program, and the joystick A/D converter, form a device called a "successive approximation converter". It is a very fast scheme that works in the following way:

Imagine you have a piece of coaxial cable, and some ratbag has stuck a pin in it, and broken the pin off. You know the cable is shorted, but you don't know where. There are two ways to find out . . . first you can cut off a metre at a time until it comes good. If luck isn't with you you will end up with a nice collection of one metre lengths of coax, with the short in the very last one. (Shades of Monty Python's "stringettes" — 3" lengths of string, good for tying small parcels, ideal present etal — Ed.)

In the "sensible" method you cut your losses, so to speak. You first cut your coax in half, knowing that will leave one good bit and one bad bit. You then cut the bad bit in half, leaving half of that good and half bad. You keep on cutting the bad bits in half until you have localised the short. The beauty of this system is that no matter where the short is, it takes exactly the same number of cuts to find it. And it's the fastest way to find the short.

In the joystick we cut its value in half, and then look at a comparator. If the value is above half the maximum it tells the computer to store a bit, and then cuts the upper half in half, looking for a "too high" or "not high enough" indication. And so it goes for all six bits. The result is a binary representation of the joystick value, stored in the computer.

The "halves" are generated by that

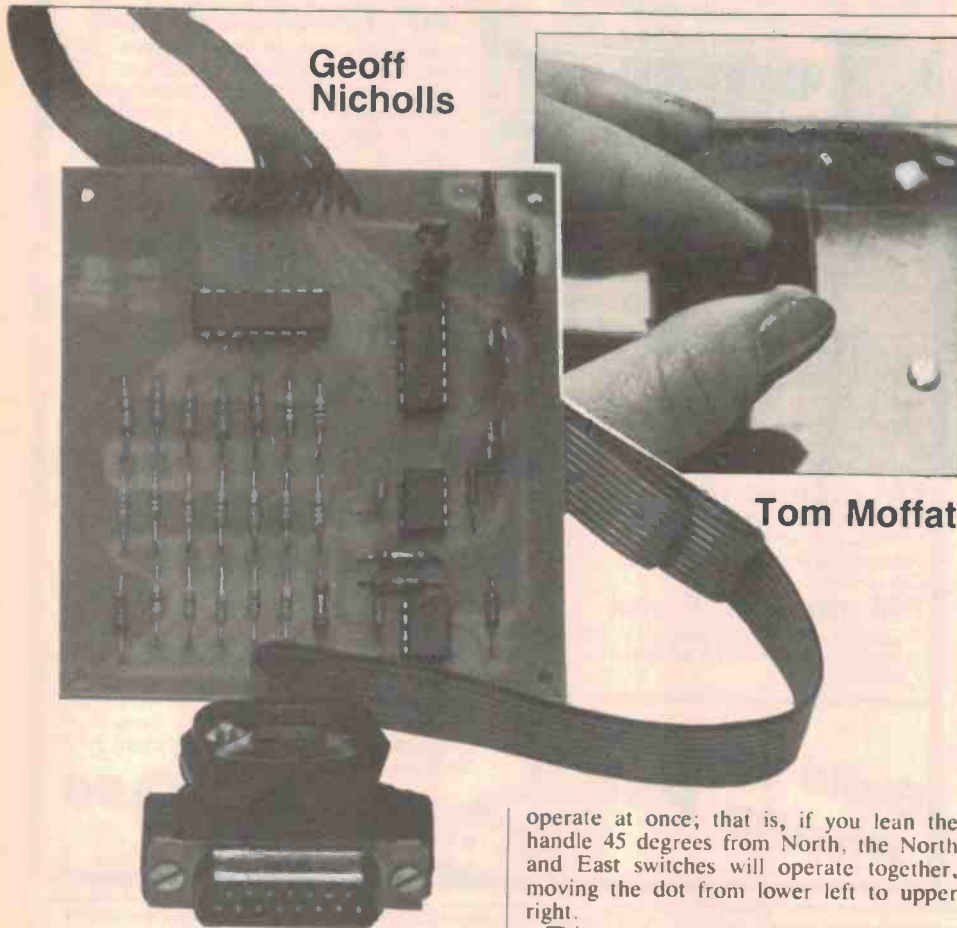

Geoff Nicholls

Tom Moffat

operate at once; that is, if you lean the handle 45 degrees from North, the North and East switches will operate together, moving the dot from lower left to upper right.

This arrangement is quite OK for many applications, but you can only move at one speed, in only eight different directions. Now, consider the true analogue joystick. On the outside it looks the same . . . a vertical handle that can be moved around. BUT . . . when you move the stick say 24 degrees from North, the dot will follow exactly. If you move quickly the dot moves quickly. If you move the stick slowly the dot just creeps along, and it stops or changes direction

MOST COMPUTERS offer joysticks as options. And most of them aren't as snazzy as this one. Your average home computer joystick, or games controller, is nothing more than four switches, actuated by a central handle. Leaning the handle one way or another actuates the appropriate switch, which tells the computer to drive a dot or other shape across the screen in the direction given. Some computers allow two switches to



**HOW IT WORKS — ETI-674**

The circuit includes most of a successive approximation analogue-to-digital converter. The rest of the converter is actually the Microbee!

Resistors R4 to R22 form a binary ladder network, also called an 'R-2R' network. The actual resistance of the resistors in the network is not critical, provided they are closely matched. IC4 is used to ensure that the digital signal levels from the computer's PIO will swing to within millivolts of the supply rails, i.e: 0 or 5 volts. If the six-bit number applied to IC4 is 'n', then the voltage at the junction of R4-R6 will be  $V_{cc} \times n/96$ . Thus, if  $n=0$  the voltage will be 0 and if  $n=63$  the voltage will be 3.28 volts.


Resistors R1, R2 and R3 are chosen to shift the voltage range to match the output voltage range from the joystick. Trimpots RV1-RV4 are used to fine-tune the joystick range.

Comparators IC1 and IC2 compare the voltage from the joystick ports to the voltage from the ladder network; if the latter exceeds the former, then the comparator output is high, and vice versa. IC3 selects either the horizontal or vertical comparator output to feed to the computer, according to the state of bit 6, which is set by the software as required.

To read the joystick, the computer selects the pot (horizontal or vertical), then starts outputting six-bit data via D0-D5, while reading the comparator output. As outlined in the text, this process is done one bit at a time, so only six operations are required, independent of the actual value. This technique is called successive approximation.

ADDR	CODE	LINE	LABEL	MNEM	OPERAND
		00100	;JOYSTICK DRIVER ROUTINES, Tom Moffat, 1/12/82		
		00110			
0400		00120		DEFR	16 ;ASSUME HEX VALUES
0800		00130		ORG	0800
		00140			
		00150	;Initialize the PIO:		
		00160			
0800	3ECF	00170		LD	A,0CFH ;SET FOR CONTROL
0802	D301	00180		OUT	(1),A
0804	3E80	00190		LD	A,80 ;DDR 10000000
0806	D301	00200		OUT	(1),A
0808	C9	00210		RET	
		00220			
		00230	;Joystick routine get X if C=00, get Y if C=40.		
		00240			
0809	79	00250		LD	A,C ;SELECT X OR Y (BIT 6)
		00260		LD	D,20 ;SET "TRY" BIT (BIT 5)
080A	1620	00270	LOOP	OR	D ;COMBINE THE TWO AND...
		00280		OUT	(0),A ;SEND TO A/D CONVERTER.
080F	DB00	00290		IN	A,(0) ;GET THE RESULT.
0811	CB7F	00300		BIT	7,A ;TEST COMPARATOR BIT.
0813	2801	00310		JR	Z,\$+3 ;IF LOW SKIP NEXT INSTR.
		00320		D	;KILL "TRY" BIT IN A REG.
0815	AA	00330		SRL	D ;SHIFT TO NEXT POSITION.
		00340		JR	NC,LOOP ;DO AGAIN UNTIL FINISHED.
081A	E63F	00350		AND	3FH ;CHOP GARBAGE OFF FRONT.
081C	4F	00360		LD	C,A ;LOAD WHAT'S LEFT INTO C.
		00370		RET	;AND RETURN TO BASIC.
0000		00380		END	
00000	Total errors				
LOOP	080C				

LISTING 1

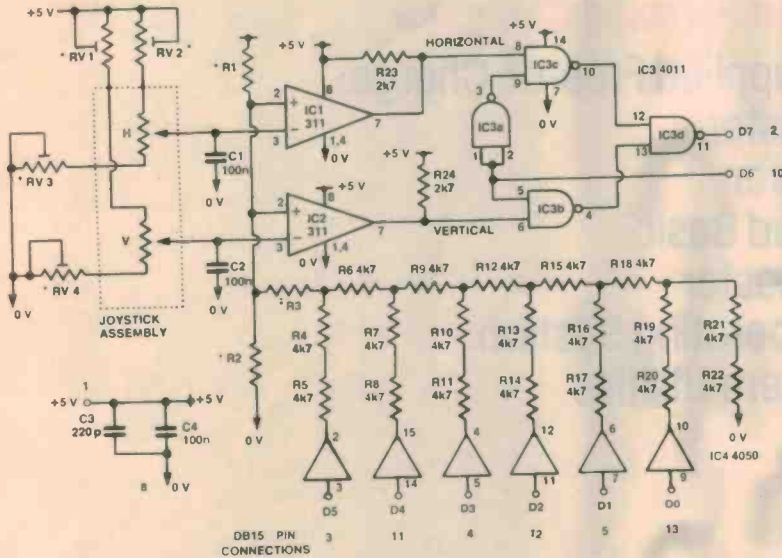


great network of 4k7 resistors, with the output feeding two comparators at once. Each joystick pot, X and Y, goes to one comparator. A series of NAND gates selects which comparator output goes back to the computer. The NAND gate X/Y selector is driven by bit 6 from the computer. An assembly language listing of the A/D converter driver is provided for those interested.

There are actually two subroutines necessary for the joystick to be used in a BASIC program. First the routine at 2048 must be called to set up the parallel port for the joystick. This need be done only once at the start of the program. Then the routine at 2057 is called to get a joystick value. The "USR" function in Micro-World BASIC makes this easy, since you can pass information both to and from a

machine code routine. You send in a "0" to get a horizontal value, or a "64" to get a vertical value. To specify a point on the screen you must do each one.

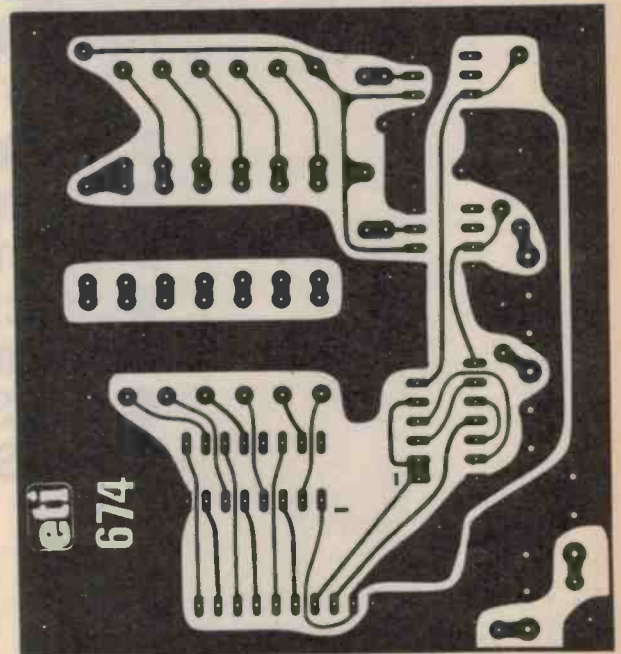The BASIC demonstration program given in Listing 2 shows how this works. The program only writes dots to the screen, leaving a trail of dots behind. Anything more elegant must come from your own imagination.





# WHEN YOU ARE BUYING A SMALL



# *Crom*

**The CROMEMCO C-10.**

**True Value in a Personal Computer.**

Software Supplied Free-of-Charge:

- Writemaster
- Planmaster
- Structured Basic
- Moneymaster
- CDOS Operating System  
and System Utilities

**AE ADAPTIVE  
ELECTRONICS P/L**

418 St. Kilda Rd. Melbourne, 3004. Phone (03) 267 6800  
Sydney: Phone (02) 419 5579. Newcastle: Phone (049) 23 343



# MICRO COMPUTER— THINK BIG

**emco**<sup>®</sup>



## LOW PRICED COMPUTER SYSTEMS for Business—Engineering—Education Manufacturing—Industry

Cromemco Means

- Powerful Z80 and 6800 operating systems for full CP/M compatibility and powerful user programs on the Cromix Multi-user Multi-tasking operating system.
- Pascal, Fortran 77, Macro Assembler and many others.

**Full range of boards and Software  
available.**




## Joystick types

There are a number of different joystick assemblies around, and the type you use affects some components in the circuit. The important parameters are;

(1) Ratio of minimum resistance to total resistance.

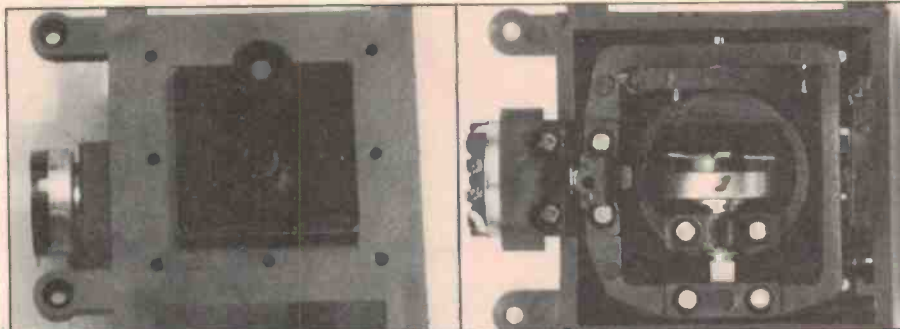(2) Ratio of maximum resistance to total resistance. The project has been built up twice, once by Tom Moffat and once by ETI. Tom used a joystick with pots of about 100k total resistance, with minimum and maximum resistances of 0 and about 90k.

The ETI version used pots with minimum resistances of around 8k and maximums of around 12k out of a total resistance of 20k. We understand that the most common type supplied will be mechanically identical to ours but will have a total resistance of around 5k. This means that the ratios mentioned earlier will be the same as ours, but the trimpots would be reduced from 5k to



Close up. Front and rear views of the joystick used.

2k to give a useful range adjustment.

The table here gives the component values to suit the three types of joystick discussed.

## Construction

First work out where the joystick will mount

in the box, remember that the pc board has to fit as well! Put the joystick right up one end so that a large area is left to rest the wrist on — you don't want to develop an ache after a few minutes use. A square cut-out was required for our stick (obtained from Benelec). Drill lots of holes and file out to exactly fit the flange on the stick. The unit is secured with four self-tappers through the box to bite into the plastic mounts on the stick base. Solder wires to each lug on the pots, around 200 mm allows slack when the pots are moved.

File a bevel to allow the ribbon cable to pass between the box and its lid, and the mechanical stuff is done.

The pc board can be made up now, start with the 4k7 resistors, and be careful not to put them where R2 and R3 have to go. Solder in the remaining resistors and the four capacitors and trimpots. The ribbon cable comes next, if you are using a solder-type DB15 plug then simply follow the overlay diagram. Some suppliers may provide insulation-displacement (ID) plugs, you'll have to carefully work out the wires if you get one — watch the 0 V wire, it is out of sequence.

The wires from the joystick pots can be soldered in now. Next, solder the ICs in place. Take particular care to orient them correctly and avoid touching the pins of IC3 and IC4 — they are static sensitive. Solder their Vcc and 0 V pins first.

The pc board was held in place with double-sided sticky pads, one also being used to secure the ribbon cable to the inside end face of the box.

## Testing and setting up

Having built the unit, the next step is to type in the test program and check that all's well. It is wise to save the program before plugging in the joystick in case a spike stuffs a bit or two. The first test covers the D-to-A converter and you will need a digital multimeter connected to read the voltage at the comparator's positive input. The most convenient place to attach the probes is across R2. Now run the #1 test and type a few different numbers in, noting that the voltage changes with the number, with '0' you should read around 1.8 volts, while a '63' should read about 2.75 volts. If you go through the range from 0 to 63 you should observe an increase with each number. If you get a decrease at some points then either a 4k7 resistor is open circuit or the data is not getting from the port through to the outputs of the 4050, IC4. ●


JOYSTICK	R1	R2	R3	RV1,2	RV3,4
5K	100K	82K	180K	2K	2K
20K	100K	82K	180K	5K	5K
100K	none	91K	91K	20K	none

Note that, when using the 100k version the 0 V wires from the pots have to return to 0 V on the PC board.

```

00100 REM Test programs for ETI 674 joystick project. LISTING 2
00110 REM
00120 REM Initialize
00130 GOSUB 450
00140 REM
00150 PRINT"1 : A-D test"
00160 PRINT"2 : Range test"
00170 PRINT"3 : Drawing"
00180 INPUT"Program no. ?";P
00190 IF P<1 OR P>3 THEN 180
00200 CLS:ON P GOTO 220,300,380
00210 REM
00220 REM #1 : A to D converter test.
00230 PRINT "Measure voltage at pin 2 of IC1"
00240 PRINT "Type test no.s from 0 to 63."
00250 PRINT "To exit type 64"
00260 INPUT A: IF A>63 THEN STOP
00270 OUT 0,A
00280 GOTO 260
00290 REM
00300 REM #2 : Range adjustment program.
00310 CLS
00320 X=USR(2057):REM Get horizontal value
00330 Y=USR(2057,64):REM Get vertical value
00340 IF X=Z THEN 350 ELSE CURS 66:PRINT [14 X]
00350 IF Y=T THEN 360 ELSE CURS 80:PRINT [14 Y]
00360 Z=X : T=Y
00370 GOTO 320
00380 REM #3 : Screen drawing.
00390 HIRE
00400 X=USR(2057)
00410 X=8*X REM Expand to screen width
00420 Y=4*Y REM Expand to screen height
00430 SET X,Y : GOTO 400
00440 REM
00450 REM Machine code loader routine.
00460 REM Pokes subroutines to 0800H
00470 FOR A=2048 TO 2077
00480 READ B
00490 POKE A,B
00500 NEXT A
00510 DATA 62,207,211,1,62,128,211,1,201,121,6,32,176,211,0
00520 DATA 219,0,203,127,40,1,168,203,56,48,242,230,63,79,201
00530 REM
00540 X=USR(2048):REM Initialize the PIO.
00550 RETURN
  
```



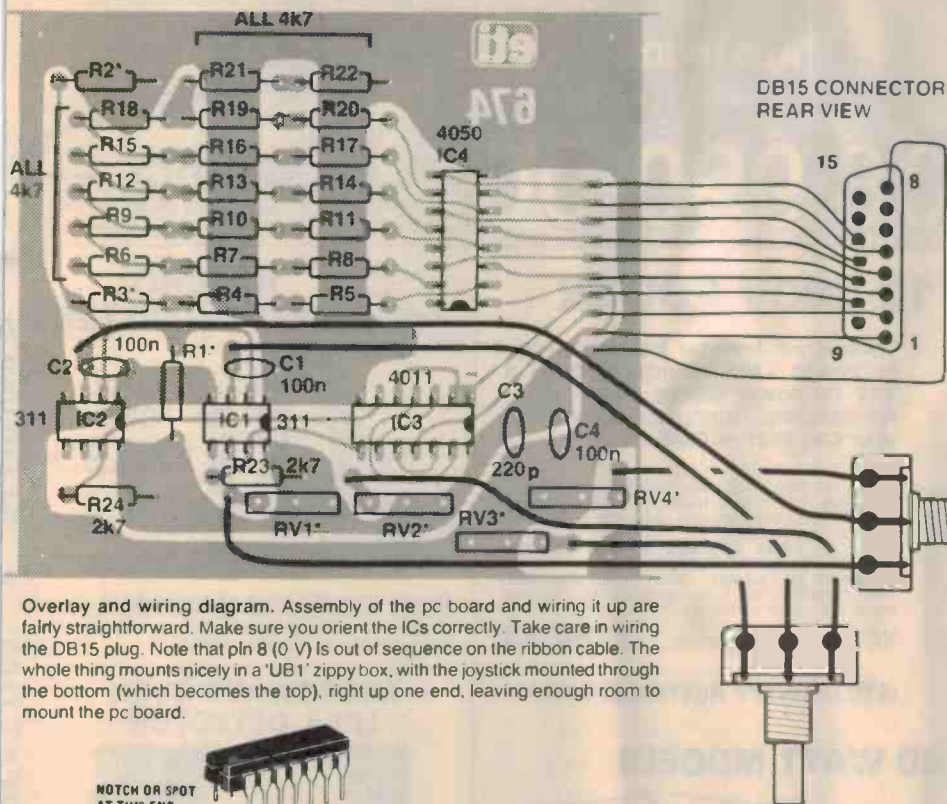

Overlay and wiring diagram. Assembly of the pc board and wiring it up are fairly straightforward. Make sure you orient the ICs correctly. Take care in wiring the DB15 plug. Note that pin 8 (0 V) is out of sequence on the ribbon cable. The whole thing mounts nicely in a 'UB1' zippy box, with the joystick mounted through the bottom (which becomes the top), right up one end, leaving enough room to mount the pc board.

**PARTS LIST — ETI-674**

**Resistors** ..... all 1/4 W or 1/2 W, 5%  
 R1,R2,R3 ..... See table  
 R4-R22 ..... 4k7  
 R23,R24 ..... 2k7  
 RV1-RV4 ..... See table

**Capacitors**  
 C1,C2,C4 ..... 100n ceramic bypass  
 C3 ..... 220p disc ceramic

**Integrated circuits**  
 IC1,IC2 ..... LM311 etc.  
 IC3 ..... 4011B  
 IC4 ..... 4050B

**Miscellaneous**  
 Joystick assembly, ETI-674 pc board; zippy box 155 x 95 x 50 mm; DB15P 15-way subminiature plug; ribbon cable; double-sided adhesive tape; hook-up wire; solder, etc.

**Price estimate:**  
**\$32-\$35**

**The Super 5 Quality Disk Drive from**

**SOUTHERN CROSS RESOURCES**



**ONLY \$448 Tax Paid!**

**PLUS** \* 90 DAY WARRANTY ON PARTS AND LABOUR

\* 14 DAY TRIAL — MONEY BACK IF NOT 100% SATISFIED

\* 7 DAY/24 HOUR ACTION-LINE CALL — (02) 981 1585

\* FREE POSTAGE IN AUSTRALIA

- \* *Super 5* — 100% APPLE COMPATIBLE
- \* LOW NOISE — HIGH PERFORMANCE

Super 5 has the following advantages compared to the normal floppy disk drive.

Characteristics	Normal Type	<i>Super 5</i>
Servo motor/Spindle connection	Belt drive	Direct shaft drive
Head positioning mechanism	Plastic CAM positioner	Metal band positioner
Track to track time	Approx. 40 msec	Approx. 6-12 msec (Fast)
Write-protected sensor	Mechanical switch	Photo coupler (Reliable)
No. of tracks	35 tracks	40 tracks (15% more!)

ALSO AVAILABLE:—

- \* APPLE COMPATIBLE CONTROLLER CARD AND 40 TRACK UTILITY DISC ONLY \$89 EXTRA!
- \* THE RELIABLE COMPUTE MATE CP-80 PRINTER  
 — FAST, 80CPS BI-DIRECTIONAL IMPACT PRINT HEAD  
 — CLEAN, 7 x 8 CHARACTER IN 8 x 9 FIELD  
 — FLEXIBLE, FRICTION AND TRACTOR FEED.  
 ONLY \$618 AND WITH 25 USER SELECTABLE TYPE STYLES!

PAY  MONEY ORDER  CHEQUE  BANKCARD  
 POSTAGE PAID IN AUSTRALIA

BANKCARD NO.

Expiry Date:

Name

Address

Signature

Send to: **SOUTHERN CROSS RESOURCES P/L**  
 P.O. BOX 379 DEE WHY NSW 2099



**BANKCARD HOLDERS —  
PHONE YOUR ORDERS  
TOLL FREE!**

**NEXT DAY DELIVERY**

**AUSTWIDE**

**ALTRONICS**

**008-999-007**

**VIA  
JETSERVICE**  
(CAPITAL CITY & SUBURBAN AREAS)



**GO ANYWHERE 12-240V POWER**



These great Inverter kits enable you to power 240V appliances from a 12V DC power source. Tremendous for camping, fishing etc. Install Into your Car, Boat or Caravan.

A fully regulated and overload protected design, featuring XTAL locked frequency. Use to power hi-fi, TV sets, even electric drills for short time periods.  
**MANY OF THESE KITS ARE NOW IN USE FOR EMERGENCY LIGHTING PURPOSES.**  
ALTRONICS' KIT features: Gold plated edge connector and PCB huss. Low age rate XTAL Sockets for all IC's. High Efficiency Transformer.

K6750..... (EA JUNE '82) ... **\$199.50**

(\$10 DELIVERY AUSTRALIA WIDE)


**TWO GREAT 40 WATT MODELS**



**GENERAL PURPOSE**

Suits small appliances, i.e. Turntables, Tape Decks, Shavers etc. Variable frequency adjustment enables speed control of turntables. Works as a trickle charger when mains power is available.  
EASY CONSTRUCTION VALUE PLUS

K6700..... **\$55.00**

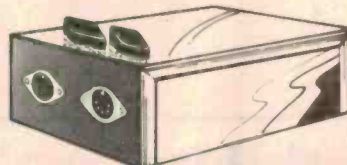

**FLUORESCENT LIGHTING**

Operates above the audible frequency range and is capable of driving one 40 watt or two 20 watt fluorescent tubes to 150% of their normal 240V efficiency. Install permanently into caravans. **COMPLETE BOXED KIT, INCLUDING ALL WINDING WIRE.**

K6505..... **\$37.50**

**ALCOHOL BREATH TESTER**



**K1583  
ONLY  
\$29.95**  
(SEE EA  
MAY 1983)

This Great new Kit from EA will be a smash hit with all the smashed people at your next party. Fun to build. Fun to calibrate and Fun to use. More seriously, this unit could save lives.

**MICROWAVE OVEN LEAK DETECTOR**



**ETI PROJECT**

Completely passive project receives microwaves via an antenna which develops a voltage across a detector diode driving the meter.  
Monitor your microwave oven with this easy to build kit. All components mount on single PCB, including the meter.  
Genuine Hewlett Packard Hot Carrier Diode supplied.

K1724..... (still only) **\$14.50**

**TRANSISTOR ASSISTED IGNITION WITH DWELL EXTENSION**



The Altronics Kit includes all components for the modifications, detailed by Electronics Australia Feb. 1983.

Yes, it's bad enough paying \$2.00 a gallon for petrol without wasting a fortune on an out of tune engine. Fit this transistor assisted ignition kit in minutes and start saving money from the very next petrol stop. Easy to build!

K4010..... **\$35.00**

**POWER DOWN MAINS APPLIANCE TIMER**

(ETI JULY '82)



**NEW KIT**

Clever new design from ETI, mains appliance is turned on at the press of a button and automatically turned off some preset time later.

Use for electric blankets, bathroom heaters, patio light. If your inclined to fall asleep while watching TV late at night — this is the kit for you.

SEC Approved Transformer Screened Front-Panel Complete kit as per ETI article, includes every last part.

K6265..... only **\$32.50**

See EA November, 1982

**POWER UP**

**A MUST FOR YOUR COMPUTER SYSTEM**



This great new Project from EA is the answer to a Maidens Prayer.

**What Does it Do?**

A single 240v mains plug and lead feeds one unswitched master 240v outlet plus 4 switched 240v outlets. With say a hi-fi system, plug your main equipment item (e.g. Amp) into the master outlet and whenever you "switch on" your amp — presto — mains power is applied to the other 4 outlets i.e. simply "turning on" your amp turns on your tape cassette, tuner, turntable, graphic equaliser without mains spikes, plops etc.

Just the shot for your Computer System. The Altronics Kit includes case and all outlets.

K6000..... **\$39.50**



## QUALITY VIDEO KITS

Video has been booming for quite a while, finally a range of video accessories in kit form. Two video amplifiers for both VCR and Computer use, a brand new Video Enhancer and our popular VCR Stereo Synthesizer. All four represent outstanding value for money and all are assembled with Altronic's Extra Care.


### VIDEO AMPLIFIERS



**DISTRIBUTION TYPE**  
Simple, low-cost project will allow you to drive five video monitors from one source, such as a video cassette recorder or a computer. Great for piping video around the house, or for clubs meetings when screening lectures etc, or for computer demonstrations.

\* THE ALTRONICS KIT includes all components as specified by ETI plus all power supply components.

K5830..... Only..... **\$45.00**

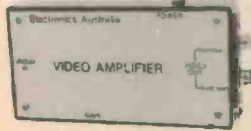

### SINGLE OUTPUT

#### INVERSE AND NORMAL OUTPUT


Brilliant new kit from EA, Super cheap and Super Effective. Whilst our K5830 is suitable primarily for VCR use this video amplifier is best suited to use with computers. The EA documentation supplied is extremely well written and provides details for installation into television sets.

**NO MORE SMEARY COLOURS, SIGNAL BEATS OR RF INTERFERENCE**

NOTE \* NOT SUITABLE FOR USE WITH LIVE CHASSIS TV SETS.

K5850..... **\$14.95**

### FUNCTION GENERATOR

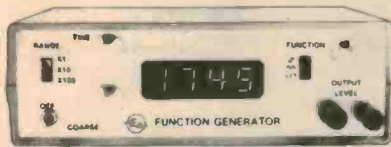

The most essential piece of test gear (second only to a good multimeter) on any hobbyist's bench is some kind of audio signal generator. This design utilizes the latest circuit techniques to produce stable, low distortion waveforms.

A truly versatile unit at a bargain price.

- ☆ 4 digit frequency readout (eliminates tiresome dial calibration) — typical accuracy ± 2% ☆ 3 overlapping ranges x1, x10, x100 ☆ 600 OHM Nominal Output — continuously variable 3MV — 2.5V p-p
- ☆ Distortion — sinewave: less than 0.7% @ 1KHz
- ☆ Linearity — triangle wave: better than 1% @ 1KHz
- ☆ Squarewave rise time — 6V/μs maximum output ☆ Amplitude stability — better than 0.1 dB on all ranges.

With the exception of the display all components mount on a single PCB making this kit suitable for all constructors.

K2505..... **\$85.00**



### VIDEO ENHANCER

Here's a simple but effective Video Enhancer that is super easy to build at a fraction of the cost of commercial models. Unit sharpens picture detail, and can actually improve the quality of a copy by amplifying the top end of the video signal.

AT LAST A VIDEO ENHANCER KIT  
K5825..... **\$35.00**

ENJOY THE PLEASURES OF STEREO SOUND  
(See EA Sept. 1982)



### STEREO SYNTHESIZER FOR VCR'S AND TUNERS


Synthesize realistic stereo from virtually any monophonic source by simply connecting this unit between the source and your stereo amplifier.

- ☆ Quality Phillips MN3001 (not second source dropout).
- ☆ Provision for 2 different signal sources.
- ☆ Selection of either source via front panel switch.
- ☆ Normal or stereo sound selection
- ☆ Complete kit includes all hardware, cables etc., even solar.

Important \* beware of Kitset suppliers who sell this kit for less \* you get less!

K5810..... **\$55.00**

### DIGITAL CAPACITANCE METER

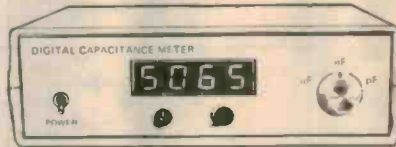

#### NEW DELUXE FINISH

We are pleased to announce the release of the Digital Capacitance Kit housed in our Deluxe HD480 ABS Instrument Case. This superb Test Instrument Kit now complements our top selling Digital Frequency Counter and Function Generator Project Kit. Electronics Australia Project. Measures capacitance of both polarized and non-polarized capacitors from 1 picofarad to 99.99 microfarads in 3 ranges. Check values of unmarked capacitors, especially those little trimmers that are never coded. Select precise values for filters and timing networks within ease.

☆ EXCLUSIVE TO ALTRONICS ☆

Each kit includes precision measured capacitors for accurate calibration of each range.

K2521..... **\$55.00**

## POWER SUPPLIES

If you're thinking of buying a power supply then buy from us, we are the experts on power supply kits and carry a supply to suit most enthusiast and professional requirements. READ ON.



### BENCH STANDARD

- ☆ 3-30v Output @ 1 Amp.
- ☆ Fully Regulated, Fully Protected from Thermal Overload and Short Circuits.
- ☆ Based on EA Design.

K3200..... **\$42.50**

- ☆ All the features of above PLUS Current Limit.
- ☆ ETI Design.

K3205..... (PICTURED)..... **\$49.50**

### DUAL TRACKING

- ☆ ± 1.3 to ± 22v Output @ 2 Amps.: + 5v @ 0.9 Amps.
- ☆ Fully protected.
- ☆ 10 turn pot enables Voltage adj. to within 10mv.
- ☆ EA Design (March '82).

K3220..... **\$89.50**

### HIGH CURRENT

#### MICROCOMPUTER PS

- ☆ + 5 Volts @ 3 Amps. ☆ + 12 Volts @ 2 Amps.
- ☆ - 12 Volts @ 200 millamps.

This universal design has enough grunt to power most disk drives.

K3350..... **\$59.50**

13.8 VOLTS @ 10 AMPS HAM'S & CBER'S  
Save the expense of a Mains Powered Rig.

K3250..... **\$89.50**

### HIGH CURRENT — DUAL METERING

#### EA SWITCH MODE DESIGN

- ☆ 2-50 Volts at massive 175 watts.
- ☆ CLEVER DESIGN — a fully mains isolated supply with a "Switchmode" low voltage circuit.
- ☆ Easy to build.

K3300... (EA MAY, JUNE '83)... **\$139.00**

K3301... (10 TURN VOLTAGE CONTROL OPTION) ... **\$10.00**


K3302... (± 12V OPTION) EA JULY '83... **\$12.50**

### ETI SERIES REGULATOR DESIGN

- ☆ 0-40 Volts @ 5 Amps — that's 200 Watts.
- ☆ Current limiting 0-5 Amps variable.
- ☆ Specifications Second to None.
- ☆ Free from the hum and noise sometimes associated with other techniques.

A PROFESSIONAL SUPPLY

K3325... (PICTURED)..... **\$175.00**

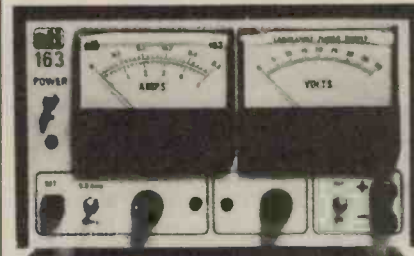

All Altronics prices include Sales Tax. Don't be conned by other advertisers whose seemingly low prices are "plus Tax in fine print". You could well pay up to 32 1/2% more.



# RS232 breakout box



Here's a handy little 'Saturday arvo' project for all those computer hobbyists who've ever wrestled with RS232 cabling, 'sexing' and troubleshooting.

## A. Bendili

CSIRO Division of Applied Physics, Sydney 2070


RECENTLY, there have been a number of articles describing monitors and troubleshooting aids for RS232 communication lines, e.g: ETI Sept. 1982 *RS232 Troubleshooter*. There are also commercially available breakout panels/monitors suitable for use with RS232 equipment. These units invariably require some form of external power either via a battery set or pluggack. It is quite probable that, with infrequent use, the battery will be flat when you least expect it, or you cannot get hold of a double adaptor or a long extension cable for your pluggack.

The recent availability of high efficiency LEDs (e.g: Stanley ESBR-5531) has eliminated the power supply problem. These high efficiency LEDs typically emit 160 mcd at 20 mA; as a result, only 2 mA is needed to obtain the same light output as a standard LED driven with 20 mA.
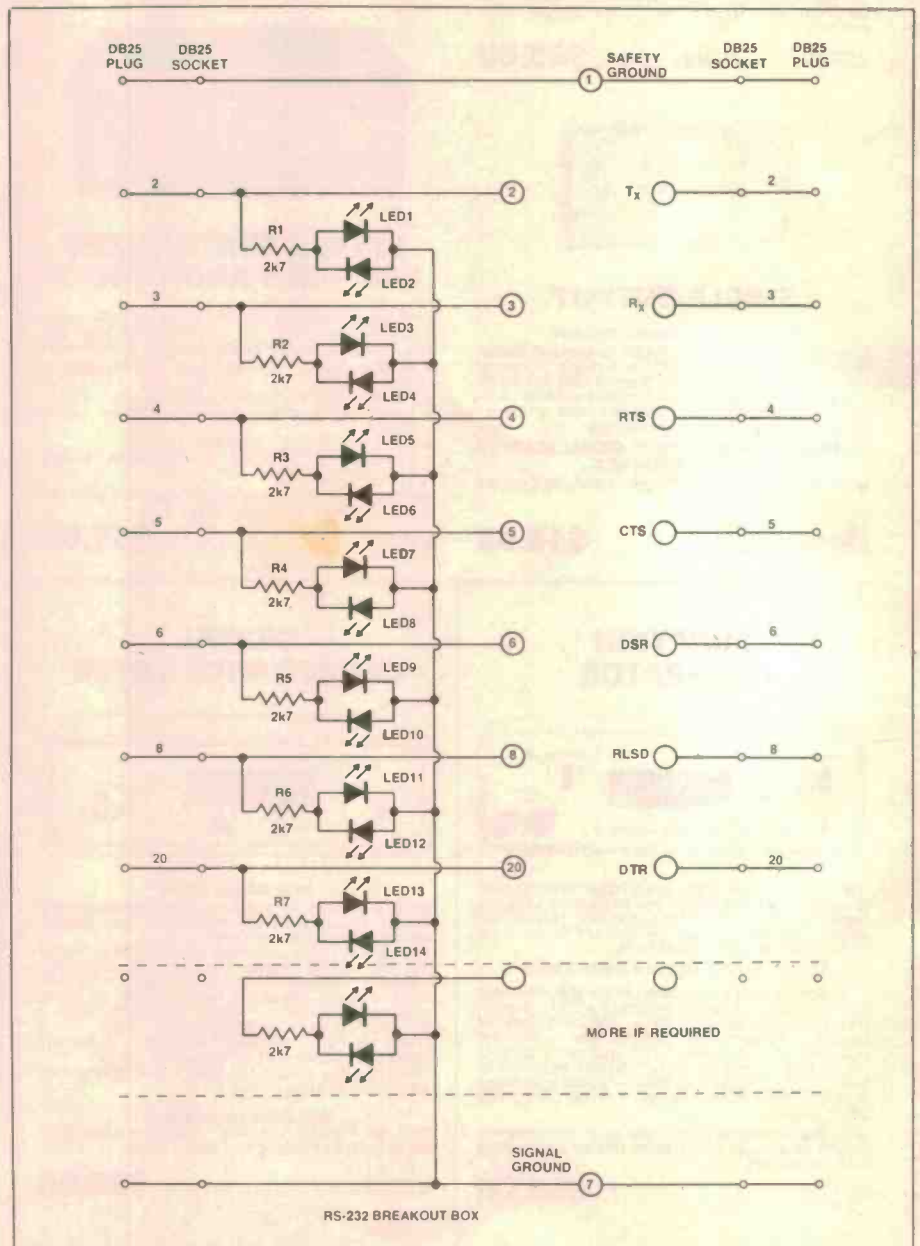
### Description

To eliminate the power supply requirement, standard LEDs were not used since they would require at least 80 mA each. However, the high efficiency LEDs operating at 1 mA emit adequate light to indicate activity. For each signal line shown in the circuit, two high efficiency LEDs are wired back-to-back, not only to indicate whether the signal line is mark/space or disconnected but also to provide reverse bias protection to each other. The 2k7 series limiting resistor is high enough not to adversely load the RS232 lines and low enough so that the LED is still visible (albeit dim) with a 3 V signal through a 500 Ohm combined line and line driver resistor. There is no circuit definition as to which end is the input or output. The input could logically be the side associated with the LEDs.

There are always two permanent connections to be made; these are the safety ground (pin 1) and signal ground (pin 7). The other pins usually depend on the usage, e.g: Tx and Rx could be reversed; some peripherals use RTS instead of DTR.






A spare, unlabelled LED could be connected to any of the 4 mm sockets to monitor its status. I found that a set of eight leads consisting of a flexible (Datwyler) wire about 100 mm long terminated at each end with a stackable 4 mm plug is sufficient to link, stack, strap, crossover, pull up and monitor.

A double row of 4 mm sockets allows the connecting of input to output according to the situation in hand.
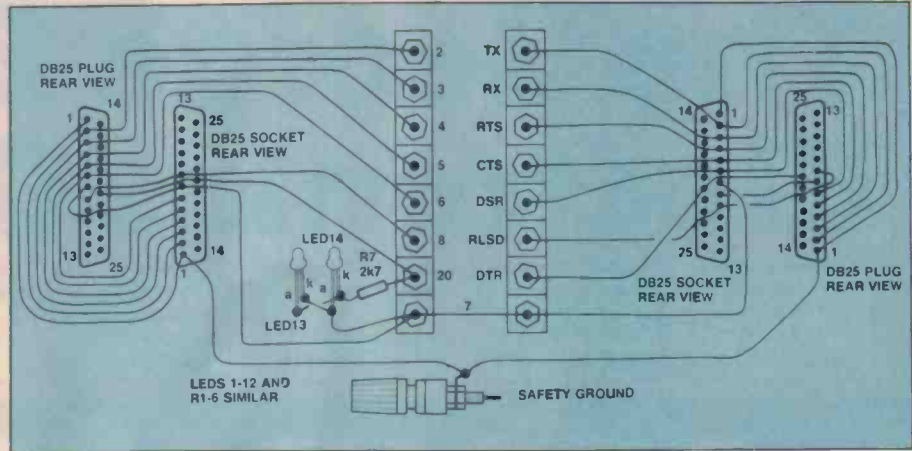
### Construction

As shown in the accompanying photograph, the unit was built in a diecast box. A connector pair consisting of a plug and socket on each side of the box allows for cables with either termination to be connected to the breakout box. A Scotchcal label between the two rows of sockets identifies the pin number and its conventional designation. As it is highly unlikely that all 21 RS232 signals will be monitored, the minimum set of signals shown on the circuit diagram would be adequate for nearly, if not all, situations.

A further improvement to reduce loading would be the use of even higher efficiency LEDs, e.g. the Stanley ESBR-500 which has a light output of 500 mcd at 20 mA. However, the present cost of over \$2 each precludes their use for the time being. ●



### HOW IT WORKS — ETI-658

Back-to-back high efficiency LED pairs, LEDs 1-14, are connected across the RS232 signal lines with a 2k7 current limiting resistor in series. The plug/socket pairs on the left and right can be linked via the central column of sockets, the LEDs indicating the presence or absence of signal and its polarity on the lines.

### PARTS LIST — ETI-658

Resistors	.....all ½W, 5%
R1-7	.....2k7
Semiconductors	
LED1-14	..... Stanley ESBR-5531 or similar
Miscellaneous	
Diecast box to suit; 16 x 4 mm 'banana' sockets;	
1 x 'banana' socket-terminal; 2 x DB25 chassis-mount plugs; 2 x DB25 chassis-mount sockets; 5 mm LED clips; hookup wire, etc.	

# Sendata 300 Modem Direct Connect

A new direct connect 300 bps modem that is no taller than a 50c piece and fits snugly under the base of a telephone, has been released by Australian communications manufacturer, Electromed. Called the Sendata 300 the modem is simple to operate and does not require operator training. It attaches to the existing telephone wall socket plug and becomes fully operational with the flick of a switch by the operator.

- No installation costs.
- Simple operation.
- Fits under telephone base.
- Attaches to existing telephone plug.

## SENDATA

OEM AND DEALER ENQUIRIES WELCOME  
ELECTRO-MED  
ELECTRO-MEDICAL ENGINEERING P/L

69 SUTHERLAND ROAD, ARMADALE,  
VICTORIA 3143, AUSTRALIA  
TELEPHONE: (03) 509 5844.  
TELEX: AA34008



# The George Brown Electronics Group.

## Protronics

SOUTH AUSTRALIA  
(08) 212 3111  
Telex AA88261

## George Brown & Co.

VICTORIA  
(03) 419 3355  
Telex AA35886

## George Brown & Co.

SYDNEY  
(02) 519 5855  
Telex AA21732

## Protronics

WESTERN AUSTRALIA  
(09) 362 1044  
Telex AA93883

## George Brown & Co.

NEWCASTLE  
(049) 69 6399  
Telex AA28461

## George Brown & Co.

A.C.T.  
(062) 80 4355  
Telex AA62128

# REGULATORS

## The more efficient $\mu$ A494.

The  $\mu$ A494 is a monolithic integrated circuit which includes all the necessary building blocks for the design of pulse width modulated switching power supplies, including push-pull, bridge and series configurations. The device can operate at switching frequencies between 1.0kHz and 300kHz and output voltages up to 40V.

## $\mu$ A431 Does it All!

The  $\mu$ A431 is a 3-terminal Adjustable Shunt Regulator with guaranteed temperature stability over the entire temperature range of operation. The output voltage may be set at any level greater than 2.5V up to 36V merely by selecting two external resistors that act as a voltage divided network. Due to the sharp turn-on characteristics this device is an excellent replacement for many zener diode applications.

POWER SUPPLY  
COURTESY OF  
SCIENTIFIC  
ELECTRONICS

FAIRCHILD

A Schlumberger Company



# EXCLUSIVE ETI READER OFFER

## THE "B-ETI" LOW-COST SERIAL TERMINAL

By special arrangement between ETI magazine and Applied Technology, makers of the famous Microbee personal computer, we introduce the B-ETI serial terminal.

Essentially, the B-ETI makes a low-cost "glass teletype". It consists of a 'stripped-down' Microbee. It operates at

300 & 1200 baud transmission speeds in either half duplex or full duplex modes. The B-ETI emulates the popular ADM-3A terminal format and most of the 'Televideo 912' format. This makes it simple to install in CP/M systems as either of these formats can be chosen. Transmission uses eight data bits with one stop bit and no parity. Interfacing is via the serial port on the rear.

The B-ETI has dozens of applications with computer, and computer-related, project and equipment. It is ideal as a low-cost terminal for the ETI-690 Little Big Board computer published in the October '83 issue of ETI for example, or as part of a radioteletype system in an amateur radio station.

The screen format is 80 characters wide by 24 lines. Upper and lower case characters are available and each character key auto-repeats if held down longer than one second.

The video output can be plugged directly into one of the low-cost monitors currently available. Many of these have a 12 Vdc output socket which can power the B-ETI directly. Alternatively, it can be powered

from any suitable 12 V dc source capable of supplying 700 mA. A power pack is not included. As the low-cost monitors available are generally priced at around \$200 or less, you can have a complete serial terminal for less than \$500!

This is an introductory offer. The B-ETI serial terminal has not yet been offered for sale through retail stores. When it is, it is expected to sell in the \$330-\$340 range so you save around 20-25% by taking advantage of this offer.

This offer is made by Applied Technology Pty Ltd (Incorporated in NSW) in cooperation with ETI magazine and ETI is acting as a clearing house for orders. All orders will be despatched by road freight for \$10, insurance included, anywhere in Australia. While deliveries will be generally ex-stock, please allow up to four weeks for delivery to cover order processing and any delays that may occur.

### HOW TO ORDER YOUR B-ETI SERIAL TERMINAL

Fill out the coupon here, or a photostat of it, and enclose a cheque, bank cheque or money order for the amount required, made out to **APPLIED TECHNOLOGY PTY LTD.**

Cut out the coupon and send it to: **B-ETI TERMINAL OFFER**  
c/o ETI Magazine, P.O. Box 21, Waterloo, NSW, 2017.

Please rush me ..... B-ETI Serial Terminal(s)  
@ \$275 each plus \$10 freight. Offer closes 31 December 1983.

I enclose \$..... total.

Cheque or Money Order No.....

Signature .....

Name .....

Address .....

Postcode .....



### INTRODUCTORY PRICE

#### 90 DAY WARRANTY

The B-ETI is manufactured especially for ETI readers by Applied Technology and a full 90-day warranty is available as well as normal backup service.

#### APPLICATIONS

- low-cost computer terminal. Use with ETI-690 Little Big Board.
- use with modem as remote computer terminal.
- use with radioteletype (RTTY) converter/modulator in amateur radio station.

#### FEATURES

- 300/1200 baud operation, software selectable.
- powered from 12Vdc supply.
- low cost — only \$275.
- 80 characters x 24 lines screen format.
- auto-repeat on all character keys and space bar.

**OFFER CLOSES  
31 DECEMBER 1983**







# The Microprofessor Sound Generation Board

The Microprofessor MPF-1 has an optional Sound Generation Board accessory known as the SGB-MPF. This board provides a programmable complex sound generation facility.

Lance Wilson

ANY MUSICAL or non-musical sound has a waveform which varies in a way which can be specified by a series of parameters; that is, a group of numbers which, in the case of a musical sound, describe the pitch and 'quality' of the note. The most fundamental of these parameters is the frequency, which would be the frequency of the fundamental for some complex wave, such as that emitted by a trumpet (look up any good text on electronics under Fourier analysis for more details).


As well as the fundamental there will be the presence of harmonics to affect our perception of the sound; i.e: whether it is raspy or relatively pure, and so such presence requires specification also. When we generate sounds digitally, we are usually working with square waves, which have a high proportion of harmonics.

The way the sounds build up and fall away is also of fundamental importance and other parameters are used to specify these properties, the most important ones being 'attack' — the time to build up to full level, sustain — which is how long it stays at full level, and decay — the time it takes to die away.

The SGB-MPF is a sound generation board designed to operate with the Microprofessor as the controller. It incorporates a complex sound generator chip, the AY-3-8190, to provide sounds of the required parameters as programmed by



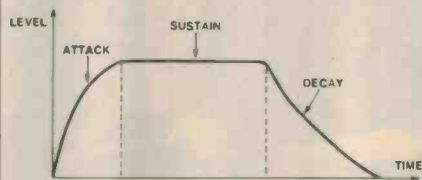The SGB-MPF. You get a board and speaker.



Envelope. The various portions of a sound 'envelope' affect its character.

the MPF-1 CPU board. On-board is an EPROM which contains a demonstration program segment of preprogrammed sounds and many useful subroutines which one may use to obtain certain desired and unusual effects. These include gun shots, explosions, laser-type sounds as well as some PacMan game-type noises. Thus, one may make up a program on the MPF-1 which calls the particular sounds as required.

As well as the unmelodious sounds above, the EPROM has a routine which converts the pushbuttons of the MPF-1 to the keys of a simple 'electronic piano' which has the added provision of a range of rhythm accompaniments, e.g: cha-cha and rock.

However, these preprogrammed sounds are not the only ones available via the board since one may provide a series of bytes to the SGB board which specify the various sound parameters and so you can produce sounds tailored to order.

## Summary

The SGB-MPF provides the facility of sound generation to those users of the Microprofessor who are into the synthesis of various sounds for use in programs or to record for a myriad of purposes. It is fairly easy to operate although the Chinese-English handbook does not facilitate this to a great degree. However, once completely familiar with its use, the serious 'sonophile' would probably find this board a useful tool in investigations into the complexities of sound, before graduating to the delirium (and expense) of a Fairlight Computer Musical Instrument at around 2000 times the price.

The SGB-MPF is available through Emona Computers, CBC Bank Bldg., 661 George Street, Haymarket, Sydney 2000. NSW (02)212-4815.

## For System 80™, TRS-80™ Model I/III and Colour Computer owners:

### ONE BIG ISSUE OF MICRO-80 MAGAZINE FREE!

If you own one of these computers, you should be reading MICRO-80 magazine, the magazine not only written by enthusiasts, but actual owners and operators of the same computers you use.

MICRO-80 understands your needs, is vital reading from cover to cover and features six new programs in each issue with full operating instructions.

An analysis of each program's structure and operation is included to help you improve your own programming capabilities.

Instructional articles on programming techniques, hardware improvements and answers to readers' problems are also published each month.

### ANOTHER MICRO-80 PLUS

Readers can purchase a wide range of software and hardware for their systems at keen prices.

### DON'T DELAY, ACT TODAY

Either telephone your order on (08) 211 7244 (4 lines) or send in the coupon today.

TRS-80 is a trademark of the Tandy Corporation. System 80 is a trademark of Dick Smith Electronics.

Please send me your free issue of MICRO-80

My computer is a: System 80  Model I  Model III  Colour

Commence my MICRO-80 subscription for 12 months.

(a) I enclose a cheque for \$26.00

(b) Please debit my Bankcard

Bankcard No. \_\_\_\_\_ P/code \_\_\_\_\_

Exp. End \_\_\_\_\_

Signature \_\_\_\_\_

To: Micro-80  
P.O. Box 213,  
Goodwood,  
S.A. 5034

ETI





# microbee series 2

## EDUCATOR



### microbee Series 2 EDUCATOR

The microbee Series 2 was specifically designed to serve the needs of the EDUCATION MARKET. Let's face it, the primary non-business use for most personal microcomputers is to increase our learning capabilities either about computers (computer awareness) or about life itself. microbee Series 2 has now been officially approved by Education Departments in NSW, WA and Queensland and is being carefully considered in virtually all other states and by the National Schools Commission at the time this magazine was going to press. Over 5,000 microbees are now in constant use in schools, universities and technical colleges throughout Australia and New Zealand and the number is growing daily.

A large and increasing body of highly creative software has now been written for the microbee by students, teachers and professional programmers. We are aware of up to 6 new programs a day so you are assured of long term support.

The microbee Educator uses BATTERY BACKED NON-VOLATILE CMOS RAM so your programs are saved in the microbee Series 2 after the power is switched off. Students can bring the microbee Series 2 Educator home from

school to complete assignments ready for class the next day. With the optional BEEMODEM you can use your microbee Series 2 Educator to talk to other computers or information networks.

For school classroom use BEENET 1 is available to connect up to 16 or even more microbees on the same classroom network so that the teacher is able to co-ordinate the class with maximum efficiency.

### Specifications:

**PROCESSOR:** Z80A running at 3.375 MHZ  
**KEYBOARD:** 60 key FULL SIZED QWERTY layout with full travel.

**MEMORY:** 44K comprising of 16K user RAM (expandable on-board to 32K), 20K ROM software, 4K character ROM, 4K graphics and screen memory.

**DISPLAY:** Direct video to external monitor or modified TV. 80 by 24 and 64 by 16 character display modes, high resolution PCG graphics to 512 by 256 pixels. Upper and lower case with full programmability at any screen location.

**SOFTWARE:** MICROWORLD 16K BASIC V5.22 in ROM, MICROWORLD Z80 machine code monitor, built-in diagnostics, NETWORKING with programmable baud rates from 110 to 4800 Baud, 7.8 bit formats, half, full duplex transmission and complete file transfer using the 'HOBBY' standard Christensen protocol.

**INPUT/OUTPUT:** Programmable 8 bit input/output parallel port, programmable RS232 port, cassette interface, direct video, 50 way Z80 expansion bus.



### microbee Series 2 EDUCATOR

**\$449**

#### Recommended Options:

- microbee HIGH RESOLUTION MONITOR ..... \$199.00
- BEEMODEM ..... \$149.50
- RGB COLOUR MODULE \$125.00
- microbee PRINTER ..... \$449.00
- BEENET 1 (recommended for school classroom use only).

## Choose your Personal Computer from the all New microbee Series 2 with Guaranteed E-X-P-A-N-D-A-B-I-L-I-T-Y

If your needs are for POWER PACKED computer for the home then the Personal Communicator with its generous 68K Memory comprising of 32K user RAM, 28K ROM Software, 4K Character Rom, 4K Graphics and Screen Memory is the computer for you.

microbee Series 2  
PERSONAL  
COMMUNICATOR

**\$499**

For serious use you can select the microbee Advanced Personal Computer (APC) which can be used with 1, 2 or even more disk drives to provide computing power unmatched by other computers in its class.

microbee Series 2  
ADVANCED PERSONAL COMPUTER

WITH SINGLE 400K DISK DRIVE \$1495  
WITH DUAL 400K DISK DRIVE \$1795





# microbee series 2 EXPERIMENTER



### Specifications:

**PROCESSOR:** Z80A running at 3.375 MHZ.

**KEYBOARD:** 60 key FULL SIZED QWERTY layout with full travel.

**MEMORY:** 36K comprising of 8K user RAM (expandable on-board to 16K), 20K ROM software, 4K character ROM, 4K graphics and screen memory.

**DISPLAY:** Direct video to external monitor or modified TV. 80 by 24 and 64 by 16 character display modes, high resolution PCG graphics to 512 by 256 pixels. Upper and lower case with full programmability at any screen location.

**SOFTWARE:** MICROWORLD 16K BASIC V5.22 in ROM, MICROWORLD Z80 machine code monitor, built-in diagnostics, NETWORKING with programmable baud rates from 110 to 4800 Baud, 7,8 bit formats, half, full duplex transmission and complete file transfer using the 'HOBBY' standard Christensen protocol.

**INPUT/OUTPUT:** Programmable 8 bit input/output parallel port, programmable RS232 port, cassette interface, direct video, 50 way Z80 expansion bus.



microbee Series 2 **\$399**  
**EXPERIMENTER**

### Recommended Options:

microbee HIGH RESOLUTION MONITOR ..... \$199.00

BEEMODEM ..... \$149.50

RGB COLOUR MODULE \$125.00

microbee PRINTER ..... \$449.00

microbee EXPERIMENTER'S 'PROJECT BOARD' (Coming Soon)

## microbee Series 2 EXPERIMENTER

By popular request, the low cost microbee Series 2 Experimenter has been designed for those who are starting out in the fascinating world of computers or those who want to share the fascination of exploring the exciting developments in the fast moving MICRO WORLD.

Demand for projects using the microbee is so great that 'Electronics Today' are now planning to run a microbee project every

month during 1984. So far ETI has described the light pen, EPROM programmer, a radio TTY printer, the World's first home facsimile receiver and ROM expander board for the microbee. Virtually every local computer magazine has run reviews and/or columns devoted entirely to the microbee. If you want to be part of the MICRO-COMPUTER GENERATION in 1984 then microbee Series 2 Experimenter is the ideal starting point.

## microbee computer shops



1 Pattison Ave,  
Waitara 2077.  
Phone (02) 487 2711



729 Glenferrie Rd,  
Hawthorn 3122.  
Phone (03) 818 2244



Coleman Court,  
Weston A.C.T. 2611.  
Phone (062) 88 6384



141 Stirling Highway,  
Nedlands, Perth.  
Phone (09) 386 8250



welcome here

DIRECT ORDERS  
PHONE (02) 487 2711

APPLIED  
TECHNOLOGY  
RETAIL  
PTY LTD

### Authorised Dealers:

**NSW:** Jaycar, (inc. Electronic Agencies)  
117 York Street, Sydney.

115 Parramatta Road, Concord.

121 Forest Road, Hurstville.

Cnr Carlingford and Pennant Hills  
Road, Carlingford.

Compu-K, 7 Casino Street, Lismore.

Comput/Ed, 8 Park Arcade,  
Park Avenue, Coffs Harbour.

**ACT:** Computech, Belconnen Churches  
Centre, Benjamin Way, Belconnen.

**VIC:** Computerland South Melbourne,  
37 Albert Road, Melbourne.

**S.A.:** Key Computers,  
1061 South Road, Edwardstown.  
77 Grenfell Street, Adelaide.

**W.A.:** Altronics, 105 Stirling Street,  
Perth.

**QLD:** Software 80, 105 Milton Road,  
Milton.

Electrographic Office Systems,  
25 Grafton Street, Cairns.

Town and Country Computers,  
CTL Centre, Anne Street, Aitkenvale,  
Townsville.

TAS: Central Data, 14A Goodwin  
Street, Launceston.



microbee  
The world's most popular home computer.



AVTEK in  
the heart of  
"SILICON ALLEY" ★  
★

# MULTIPROM INTERFACE BOARD

A NEW KIT

## ONLY \$99

MICROBEE

The Multiprom board is an extension of the Microbees memory in ROM. It simply plugs into the fifty way bus expansion port on the core board. It fits either neatly inside the Microbee or behind it, using the Microbee's own power supply.

The board takes the EDASM and NET eeprom normally residing inside the Microbee, but allows several different sets to fit in: Editor-Assembler, Wordbee, Logo, MiniPascal, Networkrom, Bemon or your own program. It has room for 4 sets of eeproms in the EDASM location and 3 sets of eeproms in the NET location, a total of 44K of eeprom. The board can be simply daisy chained with up to 6 slave boards (using an outside power supply in this case), allowing a maximum total of 308K in ROM. The EDASM locations accept either type 2532 or 2764 eeproms and they can be mixed. Another powerful feature of the board is the input/output system, 11 outputs, open collector transistor driven. Each can turn ON or OFF a relay under program control, 8 inputs, buffered and protected can read 8 switch status - ideal for computer controlling of model trains, alarm systems, tape recorders, machinery etc. The Avtek kit includes a plated through board plus all components to make this exciting project. There is also provision on the board to change the address of the ports used for eeprom selection and input/output.



SEE ETI NOVEMBER 1983

# MULTI ROM BOARD

XM-1 - This is a totally new product developed EXCLUSIVELY for AVTEK. It takes two sets of EPROMs (e.g. WORDBEE and EDASM) and allows you to choose between them by simple KEYBOARD COMMANDS. It will take a short time to assemble and is simply installed inside the MICROBEE with one DIP plug (supplied) and two solder connections.

XM-1 - suits early model MICROBEE plus models using 2532 type EPROMs. These have serial numbers starting with 8 - ONLY \$19.95  
XM-2 - same as XM-1 but suits the "MICROBEE IC" and is even simpler to fit. Also responds to PAK1 and PAK2 commands. These have serial number starting with 9 - ONLY \$16.95



S-100 SOCKETS  
High quality, gold plated  
\$6.95 ea or 10 for \$65



# LITTLE BIG BOARD



SEE ETI OCTOBER 1983 FOR FULL DETAILS

The Pulsar Series 6000 microcomputer card has been designed to provide a cost-effective general purpose central processor that will find application in a wide range of systems, from stand-alone and dedicated control processors to multi-processing and network configurations. While the 6000 Series is fully compatible with the industry standard STD bus, attention was given to partitioning the circuit so that a complete disc-based computer system could be constructed using just one card. Included on the board is: Z80A processor operating at a full 4MHz, 64kbytes dynamic RAM, single/double density floppy disc controller, two RS232C serial I/O ports, 2kbytes EPROM bootstrap monitor and battery-backed real-time clock and calendar. Interfacing to the STD bus allows systems to include modules from a range of over 1800 cards available from some 80 manufacturers.

Card Includes:

- Power-on automatic bootstrap to CP/M system
- In on-board EPROM
- Real time clock chip with battery backed supply
- Bus Interface
- All signals meet STD Bus electrical specs.
- External Connections


- 50 way edge connector provided for 8" floppy disc connections
- 1 16 pin RS232C for terminal connection
- 1 16 pin RS232C for printer connection
- FULL KIT - PHONE FOR FINAL PRICE
- PCB - MANUAL & ROM ONLY \$149.00

FROM \$149
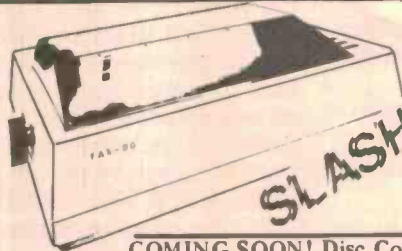
# NEW STORE

172 LIVERPOOL ROAD, ENFIELD  
Phone: (02) 745 2122

DON'T FORGET WE ARE PROBABLY THE LARGEST SELLER OF IC'S, COMPONENTS, IDC CONNECTORS, ALTRONICS KITS ETC. IN SYDNEY



SLASHED

FAX 80  
\$399 INC. TAX!!

That's our price Dec Only  
\$10 P&P - NO Bankcard  
Check the opposition!!

COMING SOON! Disc Controller & C/PM to suit  
32K MicroBee - WATCH OUR ADS!!  
CAR ALARM - WAS \$69.50 SAVE \$10 Dec. Only  
NOW \$59.50 - full featured - easy to install.  
Logic & Voltage testers SAVE nearly 20% \$7.95 Dec. Only


"Reach the  
world"  
FOR AROUND  
\$200

# Multi Modem

Limited Stock

THIS KIT WILL "KILL" ALL OTHER KITS AVAILABLE IN ITS TOTAL COMMUNICATION WITH THE WORLD! READ ON  
Modulation Frequency shift keying, Digital Interface RS-232C, Auto answer and disconnect, Data communication to basic Bell or CCITT specifications giving a world data communications capability. Operates with your normal phone, 300BPS or 1200 BPS with backward channel 75 BPS, indicators and test switch. Auto answer by manual connect. Backward channel standard on 1200 BPS mode. Direct connection, inbuilt isolation unit Operates in the following modes: Bell 103 originate 300 BPS, Bell 103 answer 300 BPS, Bell 202 equalised 1200 BPS, Bell 202 1200 BPS, CCITT V23 mode 2 equalised 1200 BPS, CCITT V23 mode 2 1200 BPS, CCITT V21 originate 300 BPS and CCITT V21 answer 300 BPS.

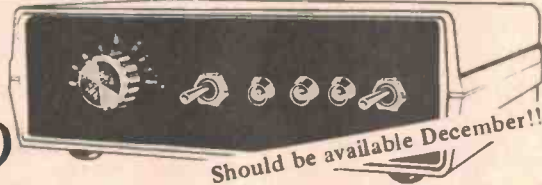AND IT'S COMING SOON!  
THE PRICE? AROUND \$200 - THAT'S HUNDREDS LESS THAN THE NEAREST EQUIVALENT!



Should be available December!!



# AVTEK

(ELECTRONICS) Pty. Ltd.

TWO GREAT LOCATIONS  
119 YORK STREET, SYDNEY 2000  
PHONE: (02) 267 8777  
(Above Charlie Browns Place)  
172 LIVERPOOL ROAD (HUME HIGHWAY), ENFIELD  
PHONE: (02) 745 2122  
All Correspondence to:  
P.O. BOX Q302, QUEEN VICTORIA BUILDING,  
SYDNEY 2000

### POST AND PACKING

Divide the value of your order by 20 (45%) to get post and packing value and then add \$2.00 - it's that simple!  
All Bankcard orders can only be sent to a normal address (NOT a P.O. Box). All Bankcard orders will be sent by registered mail (add \$3 to P&P charges).  
ENFIELD OPEN ON SUNDAY



# MICROBEE COLUMN

The Microbee is a popular computer and we've been encouraging your enthusiasm with special Microbee projects and this column. Some interesting programs have been sent to this column; keep them coming in.

But when you do send in a program make

sure that it has been given a name, describe what it is intended to do, how it works, what the controls are, etc. We will not publish a program which does not have any description with it.

Microbee Column, August '83, page 61. J. Murfet's program 'Typing Tutor' had a few typing mistakes (ironical, isn't it?).

00280 should be for I = K to K + 16 \* 3 - 1

00330 should be Read L: Poke I, L

00410 should be for I = K to K + 16 \* 5 - 1

## TEST PATTERN

D. J. Whyatt, Sth Plympton SA

To set up a monitor it is often useful to fill the screen with a character. This program does this if the 'ESC' key is pressed before another key. To reposition the screen, just press 'ESC' twice before the positioning key.

This may not sound very exciting, but it does illus-

trate the use of the 'ESC' key to run a machine code program directly.

The POKE in the BASIC program sets the Input Device Vector to point to the routine at 15000 instead of the routine in BASIC. The routine then calls the BASIC so that normal operation is possible, but

checks for the 'ESC' key. If found, control is then directed to a call as specified; in this case, the FILL routine.

In the BASIC program the third Data line is the routine to be called. Hopefully, the Assembly listing shown will help to illustrate this technique.

### TEST PATTERN — ASSEMBLY LISTING

ADDR	CODE	LINE	LABEL	MNEM	OPERAND
		00100	; Program to display screen full of test character		
		00110			
0400		00120		DEFR	16
8006		00130	KEY	EQU	8006
A3E9		00140	BASKEY	EQU	0A3E9
001B		00145	ESC	EQU	1BH
3A98		00150		ORG	3A98
		00160			
		00170	; Control directed here on any key entry from BASIC.		
		00180			
3A98	CDE9A3	00190		CALL	BASKEY
3A9B	F5	00200		PUSH	AF
3A9C	FE1B	00210		CP	ESC
3A9E	2B02	00220		JR	Z,ESCKEY
3AA0	F1	00230		POP	AF
3AA1	C9	00240		RET	
		00250			
		00260	; Control directed here if 'ESC' key found.		
		00270			
3AA2	F1	00280	ESCKEY	POP	AF
3AA3	CD0680	00290		CALL	KEY
3AA6	FE1B	00300		CP	ESC

		3AAB	C8	00310	RET	Z
		3AA9	CDAD3A	00320	CALL	FILL
		3AAC	C9	00330	RET	
				00340		
				00350	; Screen is filled with character in A.	
				00360		
		3AAD	010008	00370	FILL	LD BC,800
		3AB0	2100F0	00380	LD	HL,0F000
		3AB3	5F	00390	LD	E,A
		3AB4	73	00400	LOOP1	LD (HL),E
		3AB5	23	00410	INC	HL
		3AB6	0B	00420	DEC	BC
		3AB7	78	00430	LD	A,B
		3AB8	B1	00440	OR	C
		3AB9	20F9	00450	JR	NZ,LOOP1
		3ABB	C9	00460	RET	
		0000		00470	END	
		00000	Total errors			
		LOOP1	3AB4	FILL	3AAD	ESCKEY 3AA2 ESC 001B
		BASKEY	A3E9	KEY	8006	

### TEST PATTERN — BASIC LISTING

```

00100 FOR L=15000 TO 15035:READ D:POKE L,D:NEXT L
00110 POKE 194,152:POKE 195,58
00120 END
00130 DATA 205,233,163,245,254,27,40,2,241,201
00140 DATA 241,205,6,128,254,27,200,205,173,58,201
00150 DATA 1,0,8,33,0,240,95,115,35,11,120,177,32,249,201
    
```

## CONES AND PYRAMIDS

Jason McLaren, Labrador Qld.

This program is designed to draw and calculate the volume of cones and pyramids.

It contains a combination of hi-res graphics and text. The subroutine, lines 470 to 580, is

interesting as this contains a circle drawing routine. The speed and definition may be varied by altering the step size in line 490 e.g.: 0.01,

### CONES AND PYRAMIDS

```

00100 REM PROGRAM
00110 CLS:PRINT
00120 UNDERLINE:PRINT"THIS CALCULATES THE VOLUME OF PYRAMIDS
AND CONES":NORMAL
00130 PRINT:PRINT"DO YOU WANT CONE OR PYRAMID"
00140 INPUT E1$
00150 IF E1$="CONE" THEN 170
00160 IF E1$="PYRAMID" THEN 260
00170 PRINT:PRINT:PRINT:PRINT:PRINT
00180 PRINT:PRINT:PRINT:PRINT:PRINT
00190 INPUT"WHAT IS THE RADIUS"A1
00200 INPUT"WHAT IS THE HEIGHT"B1
00210 GOSUB 470
00220 CURS 1,15:PRINT"THE RULE IS 1/3 AREA OF BASE * HEIGHT"
00230 LET R1=3.14*(A1)^2*(B1)/3
00240 PRINT"THE ANSWER IS "R1
00250 GOTO 330
00260 INPUT"WHAT IS THE SIDE OF BASE MEASUREMENT"D1
00270 INPUT"WHAT IS THE HEIGHT"G1
00280 CLS
00290 GOSUB 370
00300 LET U1=(D1)^2*(G1)/3
00310 PRINT"THE RULE IS 1/3 AREA OF BASE * HEIGHT"
00320 PRINT"THE ANSWER IS "U1
    
```


```

00330 PRINT"DO YOU WANT TO ENTER ANOTHER SUM. YES OR NO"
00340 INPUT L1$
00350 IF L1$="YES" THEN CLS:GOTO 130
00360 IF L1$="NO" THEN PRINT"OK":END
00370 HIRE$
00380 PLOT 150,127 TO 230,110
00390 PLOT 230,110 TO 230,50
00400 PLOT 150,127 TO 150,70
00410 PLOT 150,70 TO 230,50
00420 PLOT 230,50 TO 320,120 TO 150,127
00430 PLOT 230,110 TO 320,120 TO 150,70
00440 CURS 38,11:PRINT"HEIGHT "G1
00450 CURS 13,13:PRINT"SIDE "D1
00460 RETURN
00470 CLS:HIRE$
00480 P1=355/113
00490 FOR T=0 TO P1*2 STEP .1
00500 X=INT(255+25*COS(T))
00510 Y=INT(127+25*SIN(T))
00520 SET X,Y
00530 NEXT T
00540 PLOT 255,152 TO 400,127
00550 PLOT 1 255,102 TO 400, 27
00560 CURS 18,9:PRINT"RADIUS "A1
00570 CURS 40,10:PRINT"HEIGHT "B1
00580 RETURN
    
```



# UHF AMPLIFIER SENSATION

**NEW**

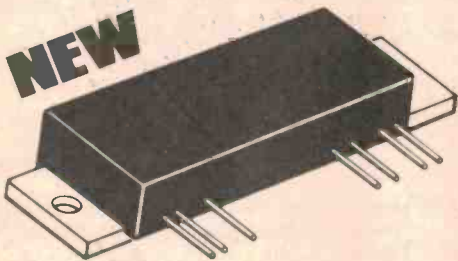

AMATEURS  
PLEASE  
NOTE

**\$39<sup>95</sup>**

**MASSIVE SCOOP PURCHASE! MANUFACTURERS DISTRESS STOCK!**  
Jaycar has purchased a quantity of genuine Brand New MOTOROLA Brand MHW-710-1 UHF Power Amplifier modules. These units are designed for Industrial and commercial FM transmitters!  
The unit (pictured) is a rugged, tuned train of RF Power Amplifier transistors featuring thin-film gold metallization, laser trimmed Nichrome resistors and MOS capacitors. The MHW-710-1 bolts to any flat metal surface to assist heat dissipation.  
**SPECIFICATIONS:**  
- RF POWER OUT @ 12.5V 13 WATTS - RF POWER OUT @ 15V 17 WATTS!!  
(BOTH OF THE ABOVE RATINGS ARE LIKELY TO BE EXCEEDED AS MOTOROLA'S POWER RATING CLAIMS ARE CONSERVATIVE)  
- 19.4 dB (Min) POWER GAIN. TYPICAL DRIVE LEVEL TO FULL POWER 90 - 150mW  
- FREQUENCY BAND 400 - 440MHz. Will work to 450MHz and therefore covers the AUSTRALIAN UHF AMATEUR BAND!!  
**CIRCUIT DIAGRAM INCLUDED**  
Each MHW-710-1 comes individually packaged with full manufacturers data. A manufacturers recommended circuit is included (only a few external components required), as well as a PCB pattern for the circuit. This component makes an ideal base for a "Home Brew" UHF Linear Amplifier! GREAT for UHF Mobile! **SERVICEMEN**

The MHW-710-1 has been used extensively in Australian Manufactured UHF Mobile 2 way radios. If you own or service a UHF radio that uses this part, now is your chance to grab a spare at an unrepeatable price! The MHW-710-1 sells for \$558 plus tax in the USA.  
**QUANTITIES STRICTLY LIMITED**  
To be fair to all, we have limited this offer to 2 per person. Jaycar's Scoop offers are so successful that usually hundreds miss out. Even at 2 per customer we will probably run out quickly. Be early to avoid disappointment!!  
**STAGGERING VALUE! ONLY \$39.95!! - Cat. ZK-8882**

PLEASE RING YOUR NEAREST STORE FOR EXTENDED TRADING HOURS OVER THE CHRISTMAS PERIOD

## Piezo Horns

PH 1005A  
3 1/2" Square Super Horn for PA's, Disco etc. Very efficient. Around 50Wrms equivalent capacity.  
Cat. AS-3100 \$9.95



**\$9.95**

**\$9.95**

Jaycar has broken the price barrier for Piezo Horn Speakers!! We now DIRECT IMPORT a range of piezo horns at prices that will stagger you. Similar units are used everywhere in P.A., Disco and HI FI applications. Only Jaycar, however, can bring you these products at low Jaycar prices!! We now stock the most popular piezo models at new low prices.

PH 1038A  
Hi Fi version of the PH 1005A. Slightly less sensitive but a smoother response.  
Cat. AS-3102 \$9.95

## TWIN SCREENED AUDIO CABLE

Twin screened round audio cable. (Two screened conductors NOT fig '8')  
This cable normally sells for \$0.48/metre or \$42.00/roll.

Cat. WB-1504

\$20.00/roll



SAVE OVER 50%... **\$20<sup>00</sup> PER ROLL**

## BT151-650R

This is the 650 volt version (for extra safety) of the C122E SCR which we use in the popular 'Fluorescent Lamp Starter' Kit as described in October 1982 EA. Normally \$1.50 each. This month only \$0.95 each! (Minimum 5 pieces). Makes the Fluoro starter kit very cheap! (PCB's for the kit) Cat. HP8747


ONLY \$1.95

Cat. ZX7022  
(8 amp 650V SCR)


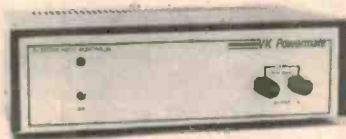
## VK POWERMATE - NEW MODEL \$89.95 comp

Get up to 13.8V @ 10 amps to run those mobile rigs at home!  
The Jaycar kit is complete.




## BD677 DARLINGTON TRANSISTOR

BD677 Popular Philips Darlington Transistor  
The BD677 is an NPN, TO-18, 80 volt 4 amp Darlington transistor. Its gain (hFE at 1.5A) is - would-you-believe 750!  
We have a bulk-buy of this snappy little transistor so you save!

ONLY 75 cents each 10 up 65 cents each



from **65¢**

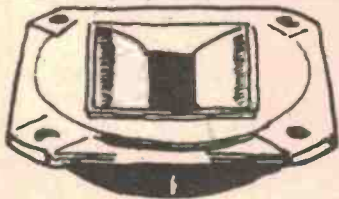

## RIBBON tweeter \$18.95

Unique regular phase design drives the entire diaphragm, uniformly and completely in phase over the full frequency range. The performance of an electrostatic speaker with the ruggedness and ease of use of a dynamic.  
Cat. CE-2042

NORMALLY \$36.50 ea

ONLY \$19.95 - SAVE \$16.95

- 91dB sensitivity
- 5,000-40,000Hz
- 50W system power
- No voice coil

## MAGAZINE BINDER

Keep your precious (and expensive) magazines in order for easy references. Smart blue colour with gold lettering. Heavy gauge and richly chromed metal fittings.  
Cat. BB7000



LOW IMPORT PRICE

NORMALLY \$4.95 ea

\$3.95 each or \$3.50 each 4 up
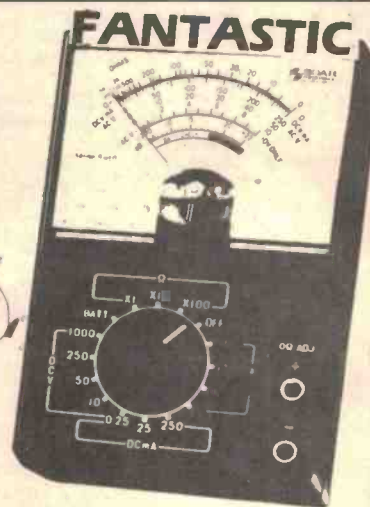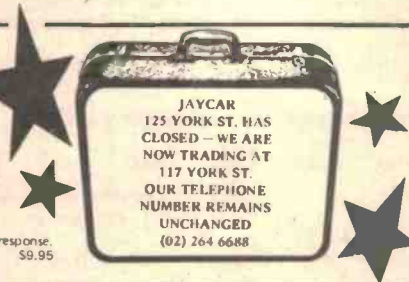
## MARSHALL EQUIPMENT HANDLES

Either for speakers or P.A. Heavy duty.  
Cat. HS-8010  
ONLY \$9.95 ea



## Multimeter

- FUSE/DIODE PROTECTED!
- 4mm BANANA SOCKET PROBES!
- BIFURCATED SELECTOR SWITCH CONTACTS!
- ABS IMPACT-RESISTANT CASE!
- LARGE! MEASURES 90(w) x 135(h) x 45(d)mm

**SPECIFICATIONS:**  
DC 0 - 0.25 AC 0 - 10  
0 10 0 - 50  
0 50 0 - 250  
0 - 250 0 - 1000  
0 - 1000 AT 9,000 ohms/volt  
AT 20,000 ohms/volt

**RESISTANCE DC CURRENT**  
0 - 5K 0 - 0.05  
0 - 50K 0 - 25  
0 - 500K 0 - 250mA

dB: -20 to +22dB  
BATTERY CHECK FACILITY: AA, C & D CELLS  
ACCURACY: DC +/- 3% F.S. AC +/- 4% F.S.  
OHMS +/- 3%

BANANA PLUG PROBES AND BATTERY INCLUDED  
This is an unbelievable meter bargain. Normally this unit would sell for around \$25. Japanese made quality.  
Cat. QM-1005 \$17.95

Wow! **\$17<sup>95</sup>**  
**\$16<sup>95</sup>**

PLEASE RING YOUR NEAREST STORE FOR EXTENDED TRADING HOURS OVER THE CHRISTMAS PERIOD

PLEASE RING YOUR NEAREST STORE FOR EXTENDED TRADING HOURS OVER THE CHRISTMAS PERIOD



PLEASE RING YOUR NEAREST STORE FOR EXTENDED TRADING HOURS OVER THE CHRISTMAS PERIOD

PLEASE RING YOUR NEAREST STORE FOR EXTENDED TRADING HOURS OVER THE CHRISTMAS PERIOD

### METAL TUNING GANG

A scarce commodity now! Made in Australia, 2 gangs (OSC & RF) gangs can be paralalled. (Total approx. 160pF). High quality with 1/2" brass shaft. Measures 30 x 40 x 30mm. Worth well over \$4.00. Cat. RV-5740

**ONLY \$1.00**

### QUALITY PHILIPS (?) 6" ROUND SPEAKER

It says Philips on the back but we're not sure! 8 ohm 4 watt. A bargain whether Philips or not. Cat. AE-8156

NORMALLY \$6.95  
THIS MONTH ONLY \$3.95  
SAVE \$3.00

### DEFINITELY FOSTER BRAND 4" SPEAKER

This wide-range unit is ideal for replacement purposes. Features large magnet, 8 ohm imp. Cat. AE-8146

NORMALLY \$4.95  
THIS MONTH ONLY \$2.95  
ONLY 100 UNITS IN STOCK

### INLINE IGNITION SUPPRESSOR

Inline ignition suppressor. Simply cut HT lead and screw into place.

NORMALLY \$0.75 each  
THIS MONTH \$0.40 each

High quality unit made for the RAAF!!  
Cat. AE-8905

### MATCHING SPARK PLUG ADAPTOR

Matching spark plug suppressor also made for the RAAF.

NORMALLY \$1.00  
THIS MONTH \$0.50 each  
Cat. AE-8909 QTY LIMITED

### MAINS ROTARY SWITCH

WERE \$0.95 EACH  
NOW \$0.50 EACH

Quality Australian made SPDT  
Cat. SR-1260

### QUALITY ENGLISH MADE ARCO TOGGLE SWITCH

GENUINE 250V @ 3A with uncommon (but handy) screw terminals. SPST configuration. Cat. SE-0680

NORMALLY \$1.95 each  
THIS MONTH ONLY \$1.00 each

### GLASS BREAKAGE DETECTOR

High quality unit can be configured either N.O. or N.C. Self adhesive pad attaches to glass. Only 30mm diameter!

NORMALLY \$9.95 each  
THIS MONTH ONLY \$8.95 each

### ALARM STICKERS Buy in bulk and SAVE!

NORMALLY \$1.00 each  
Buy 10 for \$0.75 each and put one on every window in your house or car.

Cat. LE-8500  
1-9 - \$1.00 each  
10+ - \$0.75 each  
Note: No specific alarm system is shown - further confusing potential theft.

### 10" ELECTRIC GUITAR SPEAKER



**\$29.95**

Quality Pioneer brand check the specs! Check the price!!

HURRY

Impedance 8 ohm  
Voice Coil Dia. 1 1/2 (Inch)  
Power Rating 60 WATT (RMS)  
Resonant Frequency 80Hz  
Sensitivity 98 (dB/W)  
Response 80Hz - 7,000Hz  
Total Flux 61,100 Maxwell  
Flux Density 8,300 Gauss  
Net Weight 1,540 gm

### WARNING



# JAYCAR

## Quartz Crystal Clock movement




Cat. XC6000



**\$14.95**

- Very compact and reliable
- Self-starting one second stepping motor has strong torque
- Powered by 1.5V AA battery that lasts for a year
- Supplied with two sets of hands, one short and one long
- ±15 second/month accuracy
- 56mm square, 15mm deep
- Complete with data sheet, instructions and wall hanger bracket.

### WHAT'S UP DOC?

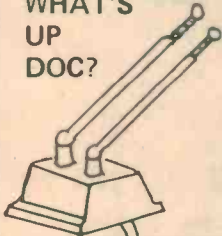

Are the "rabbit ear" antennas on the back of your portable TV broken? You know those ones that are telescopic and have ball-swivel joints.

We have genuine 'HMV' factory spares that will fit other TV's. Apparently they are almost industry-standard components. Each unit comes with a short length of lug-terminated 300 ohm ribbon.

We have a small job lot available at only \$7.95 each.

ONLY 220 SETS AVAILABLE.

Cat. AA2005

**\$6.95**

## low cost IC inserters AND EXTRACTORS

Up until now these have cost a fortune!!

Features:

- CMOS SAFE conductive plastic
- Exclusive bent pin alignment guides in handle . 8 to 40 pins.
- Ground strap can be connected.
- One hand operation.

INSERTERS

Cat. No	Model	Description	Normally	NOW
TH1810	CIT820	8 - 20 pin	\$5.95	\$4.16
TH1812	CIT22	22 pin	\$6.50	\$4.55
TH1814	CIT2428	24 - 28 pin	\$6.95	\$4.86
TH1816	CIT3640	36 - 40 pin	\$8.95	\$6.26

EXTRACTOR


Deceptively simple looking device. One piece metal construction. 8-40 pins

TH1818 ET480

\$2.95

NOW \$2.06

**LESS 30%**

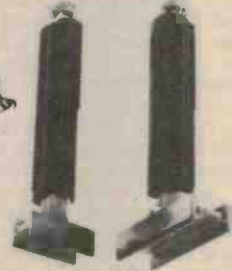

### 115 VOLT COMPUTER FANS


GREAT VALUE!

**\$14.95**



We have made a scoop purchase of computer grade Box Fans. They measure a standard 80 x 80 x 40mm. But there's a catch! They are only available in 115V! Great if you are making equipment for export to the USA - or use 2 in series! No problem! Cat. YX-2508

ONLY \$14.95

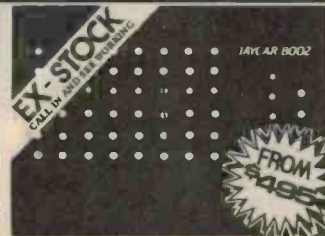

### 8 CHANNEL MIXER KIT

FROM \$95

Ref: EA March/April 1983

This great 8 channel 'live' mixer is perfect for bands, churches, theatre groups, home recording, disco etc.

Each input channel accepts either microphone (balanced) or line (1V) levels. Powerful equalisation foldback effects facilities are provided. The left and right master channels can drive balanced or unbalanced lines with 5 band "graphic" equalisation. Separate foldback and "effects" are provided.

The unit can be rack mounted or housed in a console chassis (which accommodates the power supply). Attractive wooden end-pieces finish the console to form a professional looking unit.

Complete 8 channel mixer (19" rack mount) Cat. KJ6504 \$495.00

Console mount chassis, power supply and wooden end pieces

Cat. KJ6505 \$98.00

You end up with a \$1500+ unit for under \$600

## Jaycar ELECTRONIC AGENCIES

INCORPORATING

SYDNEY

SHOWROOMS

117 YORK STREET - PHONE: (02) 264 6688 and (02) 267 1614

CARLINGFORD

TELEX: 72293

Cnr. CARLINGFORD & PENNANT HILLS ROAD - PHONE: (02) 872 4444

CONCORD

115 - 117 PARRAMATTA ROAD - PHONE: (02) 745 3077

HURSTVILLE 121 FOREST ROAD PHONE: (02) 570 7000

### NUMBER 1 FOR KITS

POST AND PACKING CHARGES

\$5 - \$9.99 (\$1.50) \$10 - \$24.99 (\$3.20)  
\$25 - \$49.99 (\$4.50) \$50 - \$99.99 (\$6.50)  
\$100 - \$199 (\$8.00) Over \$199 (\$10)

\*Free INSURANCE for Road & Registered Post over \$200\*

All heavy or bulky items (over 20kg.) sent Comet Road Freight \$12.00 anywhere in Australia.

SHOP HOURS CARLINGFORD, CONCORD & HURSTVILLE

Mon - Fri 9am - 5.30pm. Sat - 9am - 12pm. Thurs night 8.30pm

SHOP HOURS SYDNEY

Mon - Fri 8.30am - 5.30pm. Sat - 8.30am - 12pm. Thurs night 8.30pm

MAIL ORDERS AND CORRESPONDENCE: P.O. Box 185, Concord, 2137



Mail Order

By



BANKCARD


Via Your Phone







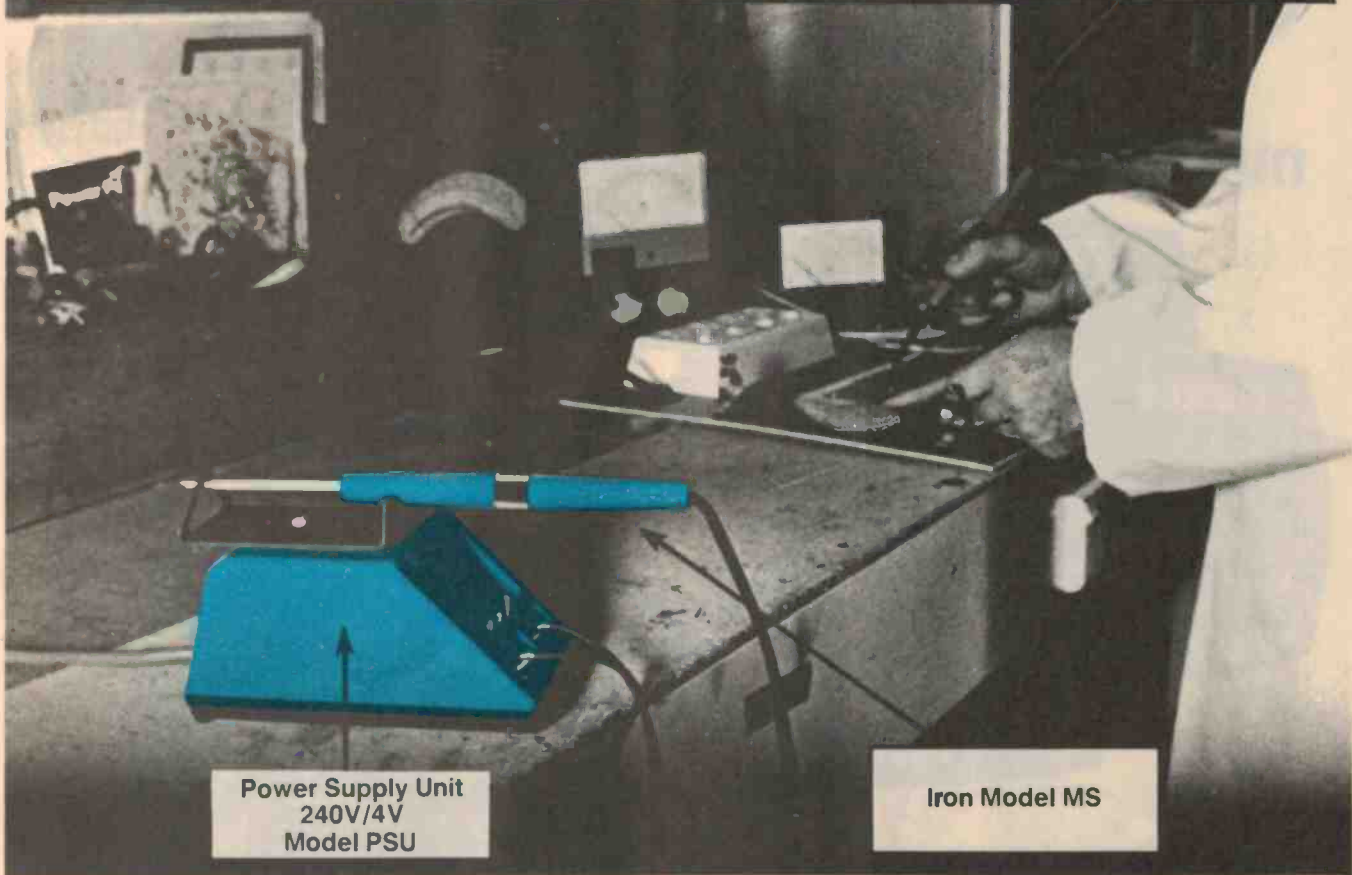**EVER WISHED YOU COULD CONTROL YOUR  
IRON TEMPERATURE ... AS YOU SOLDER  
WITH SCOPES MODEL MS YOU HAVE ANY TEMPERATURE  
200°— 500°C AT YOUR FINGER TIP**



**Power Supply Unit  
240V/4V  
Model PSU**

**Iron Model MS**

## **Adjustable MiniScope 10w ↔ 70w**

**Hobby & Repair Iron**

**...Lets you adjust its wattage and temperature  
....as you solder**

A multipurpose adjustable tool for the professional serviceman. Lets you choose the wattage and tip temperature to suit large or small jobs. Does the work of several fixed heat conventional irons.

- **ADJUSTABLE WATTAGE** : Anywhere between 10W - 70W - you control the output to suit the job.
- **FAST HEATING** : 20° - 200° C in 5 seconds 200° - 400° C in 5 seconds with faster cool down.
- **OWNER MAINTENANCE** : Designed to let you maintain the tool in the field in seconds...for cents.
- **ADJUSTABLE HEAT** : Temperature is controlled by you while soldering to suit the job. Anywhere between 200° - 500° C

**For a  
FREE CATALOGUE**

*send your name  
and address to:*

**FREEPOST No. 2  
SCOPE LABORATORIES  
P.O. BOX 63  
NIDDRIE, VIC., 3042**

**NO STAMP REQUIRED**



**SCOPE**  
(03) 338 1566

**SEND FOR FREE CATALOGUE** ↗






microbee

# TOTAL SOFTWARE SUPPORT



TOP 30 BEST SELLERS

**Survivor**  
Program of the Month!

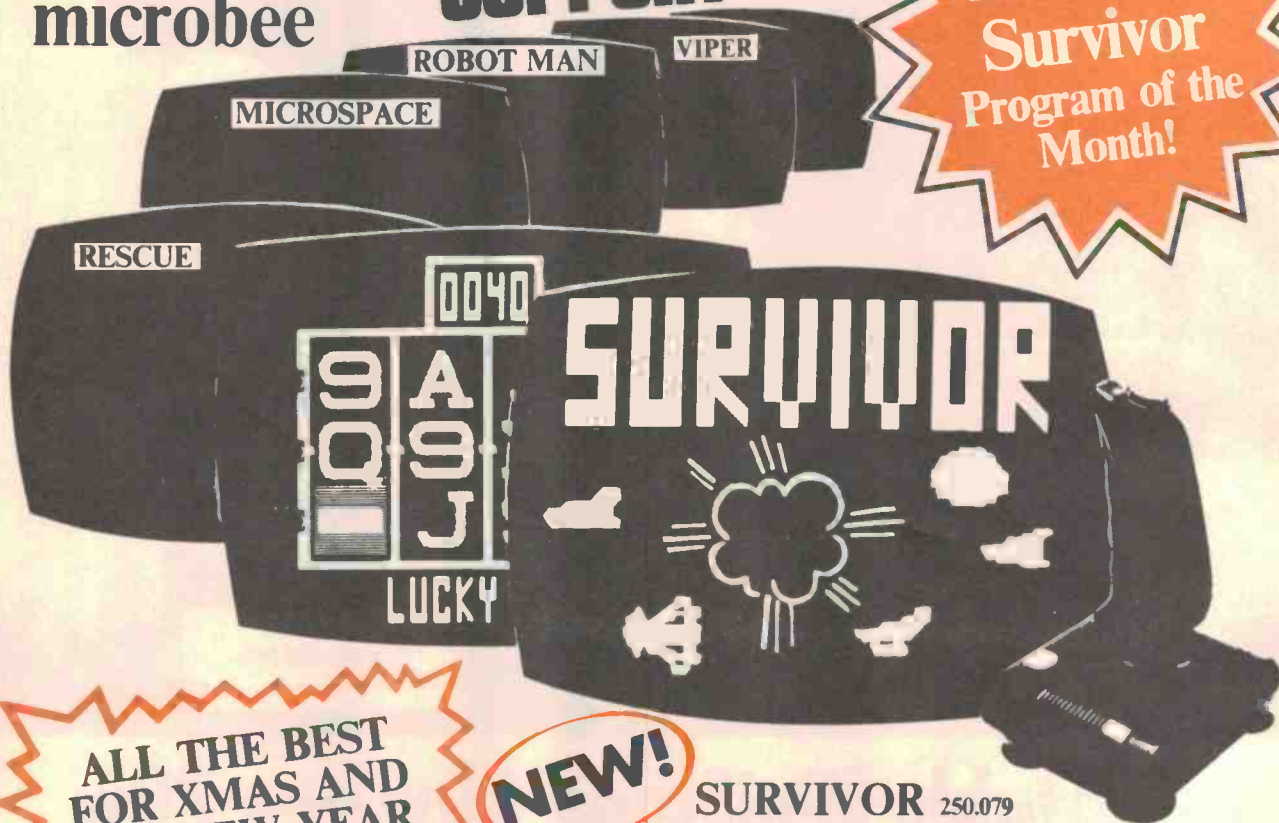

ALL THE BEST FOR XMAS AND THE NEW YEAR

**NEW!**

### GAMES

**VIPER** 250.096  
Rabbits are everywhere and with 4 pet viper snakes, you gobble them up. Careful . . . they grow as they eat and might eat their own tails.

\$14<sup>95</sup>

**REELS** 250.098  
Just like a real poker machine complete with spinning wheels and sound effects. It doesn't eat your money and you won't be caught by the booze bus.

\$14<sup>95</sup>

**CHESS** 250.022  
Try beating the computer at Chess. There are 6 levels of difficulty and a 'help' feature for the computer to make the next best move for you.

\$14<sup>95</sup>

### **SURVIVOR** 250.079

The Aliens are attacking the earth and it's up to you to blast them with your attack fighter before they blast you! With a Joystick . . . you're in control.

\$14<sup>95</sup>

With Joystick . . . . . \$49.95

**MICROSPACE INVADERS** 250.020  
A fast moving Microbee action game. Stop the aliens landing on earth or you will be destroyed.

\$14<sup>95</sup>

**ROBOTMAN** 250.039  
You must eat as much energy pellets as you can and try to escape from the Robotmen before they eat you.

\$14<sup>95</sup>

**CANNIBALS AND MISSIONARIES** 250.084  
Take the cannibals and missionaries across the river but make sure there's not too many cannibals or . . . GULP!

\$14<sup>95</sup>



# AND MANY MORE! . . . .

## EYE OF MIN 250.089 32K ONLY.

The flash of light in the darkness is the Eye of Min Gem and you try to capture it . . . . be careful.

\$14<sup>95</sup>

## CHESS TUTOR 250.076

Now you can study the classic moves of the masters at your own leisure.

\$14<sup>95</sup>

## WONDER WORDS 250.106

You specify the words and the computer then hides them in a matrix. Find them if you can!

\$14<sup>95</sup>

## YAHTZE 250.017

Add this well known dice game to your Microbee. Two versions available on each cassette. A great family game!

\$14<sup>95</sup>

## ESCAPE FROM COLDITZ 250.056

Beat the Hun. Make your break in the big escape. For 32K only.

\$14<sup>95</sup>

## FROG HOP 250.092

Hurry . . . . cross the road before you get squashed. Then you have to cross the stream but look out for the prowling crocodile.

\$14<sup>95</sup>

## EDUCATIONAL

### RESCUE 250.014

You are stranded on an island. To be rescued you must select the appropriate synonym to the word on the screen. Part of Learning can be Fun Vol. 2B.

\$14<sup>95</sup>

### MILLIKAN'S EXPERIMENT 250.087

Now you can deduce the charge of an electron. Graphic demonstration and tutorial for Year 11 and 12 physics students.

\$14<sup>95</sup>

### WORD ADVENTURE 250.086

Follow the path and answer the synonym, antonym or homonym to the word provided or correct the spelling or the serpent will destroy you.

\$14<sup>95</sup>

### KEPLER'S LAWS 250.080

A simulation of planetary orbits enabling physics students to analyse Periods, Ellipses and Areas.

\$14<sup>95</sup>

### WORK-A-BEE 250.062

This program actually helps you write your own educational software. Ideal for teachers. Manual included.

\$19<sup>95</sup>

## UTILITY PROGRAMS

### TYPING TUTOR (Pitmans) 250.078

Typing tutor takes you by the hand and introduces you to typing with the minimum of fuss.

\$14<sup>95</sup>

### PCG TUTORIAL 250.037

Opens up the 'mysteries' of Microbee's programmable character generator to help you to design your own graphics.

\$14<sup>95</sup>

## FORTH 250.302 IN ROM

Now Microbee owners can use the powerful Forth applications oriented program language. Written by a couple of dedicated Forth experts, Microbee Forth is Rom based and comes with an internal dictionary of 200 words. Because the language is interactive, extensible, structured and recursive, the user can readily expand the commands by adding new words. Forth is a very easy language for even a beginner to master and programs written in Forth run only a little slower than in Machine Code.

Microbee Forth can run on 16K and 32K systems. A tutorial is supplied to enable newcomers to master this exciting new development for the Microbee.

\$49<sup>50</sup>

## MICROBEE PASCAL NEW 250.300 IN ROM

A good step into a new language. It incorporates an editor, a p-code single pass compiler and a p-code interpreter.

\$59<sup>95</sup>

## OZ-LOGO 250.301 IN ROM

A remarkable graphics language enabling your Microbee to have outstanding graphics capabilities.

\$49<sup>95</sup>

## SUPER DISASSEMBLER 250.052

This takes a machine code and translates it into Z-80 standard mnemonics to utilise routines in other machine code programs.

\$19<sup>95</sup>

## SKETCH PAD 250.085

Allows you to draw anything you might desire on the Bee. Circles, polygons and boxes. An excellent program.

\$14<sup>95</sup>

## MORSE CODE TUTOR 250.077

Now you can learn the code that you thought was only the domain of the dedicated radio Ham.

\$14<sup>95</sup>

## PROGRAMMING HINTS 250.014

This program consists of a collection of modules which you may use to improve your own Basic programs. To allow you to see the effect of each module, they are all linked together under a menu driven display which allows you to Run each module, or List each to see how they work.

\$14<sup>95</sup>

## BUSINESS

### DATABASE 250.051

The ideal system for keeping lists of all those things you wish to recall during the year. Ideal demonstration of data base techniques.

\$14<sup>95</sup>

### BUSY CALC 250.050

Fed up with constantly having to erase errors from your spreadsheet? Is your spreadsheet giving you a headache? Busy Calc will help solve all your problems for you. Some of the commands available are: Average; Sum; Compute; Format; Recalculate and Load and Save to cassette.

\$14<sup>95</sup>

## microbee computer shops

1 Pattison Ave,  
Waitara 2077.  
Phone (02) 487 2711  
729 Glenferrie Rd,  
Hawthorn 3122.  
Phone (03) 818 2244  
141 Stirling Highway,  
Nedlands, Perth.  
Phone (09) 386 8250  
Coolman Court, Weston  
A.C.T. 2611.  
Phone (062) 88 6384

**DIRECT ORDERS**  
**PHONE (02) 487 2711**

## DEALERS:

NSW: Jaycar, (inc. Electronic Agencies) 117 York Street, Sydney. 115 Parramatta Road, Concord. 121 Forest Road, Hurstville. Cnr Carlingford and Pennant Hills Road, Carlingford. **Compu-K**, 7 Casino Street, Lismore. **Comput/Ed**, 8 Park Arcade, Park Avenue, Coffs Harbour.

ACT: **Computech**, Belconnen Churches Centre, Benjamin Way, Belconnen.

VIC: **Computerland South Melbourne** 37 Albert Road, South Melbourne.

S.A.: **Key Computers**, 1061 South Road, Edwardstown. 77 Grenfell Street, Adelaide.

W.A.: **Altronics**, 105 Stirling Street, Perth.


QLD: Software 80, 105 Milton Road, Milton. **Electrographic Office Systems**, 25 Grafton Street, Cairns. **Town and Country Computers**, CTL Centre, Anne Street, Aitkenvale, Townsville.  
TAS: **Central Data**, 14A Goodwin Street, Launceston.

## APPLIED TECHNOLOGY RETAIL PTY LTD





# UNBELIEVABLE

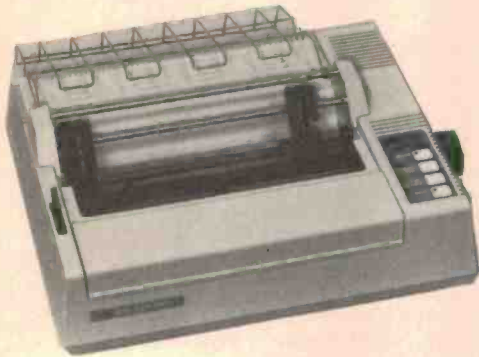

Here is an unbeatable opportunity to purchase a top quality printer from a well known and respected manufacturer, Texas Instruments, at a saving of over 30% on their normal list price.

## TI 850 PRINTER

**\$760 exc. tax**

**\$912 inc. tax**


Normal list price on this printer is \$995 exc. tax; save \$235!

### SPECIFICATIONS TI 850 PRINTER

TI 850 SPECIFICATIONS	
<b>POWER REQUIREMENTS</b>	90-132 Vac, 47-63 Hz, single phase or 187-264 Vac, 47-63 Hz, single phase 100 W maximum
<b>PHYSICAL DIMENSIONS</b>	412 mm (16.2") wide 220 mm (13.0") deep 127 mm (5.0") high 6.8 kg (15lb) excluding options and accessories
<b>CHARACTER SETS</b>	Full US ASCII and 7 international
<b>INDICATORS</b>	Power, on-line, pitch SFL
<b>DATA</b>	Parallel Interface: Line levels Characters per second Line control

<b>Serial Interface:</b>	EIA RS-232-C standard subset -12 or +12 Vdc ASCII and similar international codes
<b>Line levels</b>	Bits per second
<b>Type code</b>	200, 300, 600, 1200, 2400, 4800, 9600
<b>Receive buffer</b>	256 characters, expandable to 4000 characters Printer ready busy
<b>Line control</b>	Printer ready busy
<b>PRINTING METHOD</b>	Wire-matrix impact Print 150 cps 9 x 9 dot matrix (standard print) 15 x 9 dot matrix (enhanced print)
<b>Speed</b>	10 cpi and 16 2/3 cpi (standard) 5 cpi and 8 1/4 cpi (double-wide)
<b>Pattern</b>	Characters per inch

<b>Characters per line</b>	80 characters at 10 cpi (standard), 132 characters at 16 2/3 cpi Full line at 10 cpi or 16 2/3 cpi requires 203 mm (8") 6 lpi and 8 lpi Friction-roller or tractor 76 mm to 254 mm (3 to 10 in)
<b>Line length</b>	Lines per inch Paper drives Paper width
<b>PAPER TYPE</b>	Sheet, roll or fanfold (single or multipart) 254 mm (10in) maximum diameter Single part 0.254 mm (0.01 in) Multipart, 0.34 mm (0.014 in) maximum for original plus two copies (No cards permitted except on last copy)
<b>Width</b>	254 mm (10in) maximum diameter
<b>Roll</b>	Single part 0.254 mm (0.01 in)
<b>Thickness</b>	Multipart, 0.34 mm (0.014 in) maximum for original plus two copies (No cards permitted except on last copy)

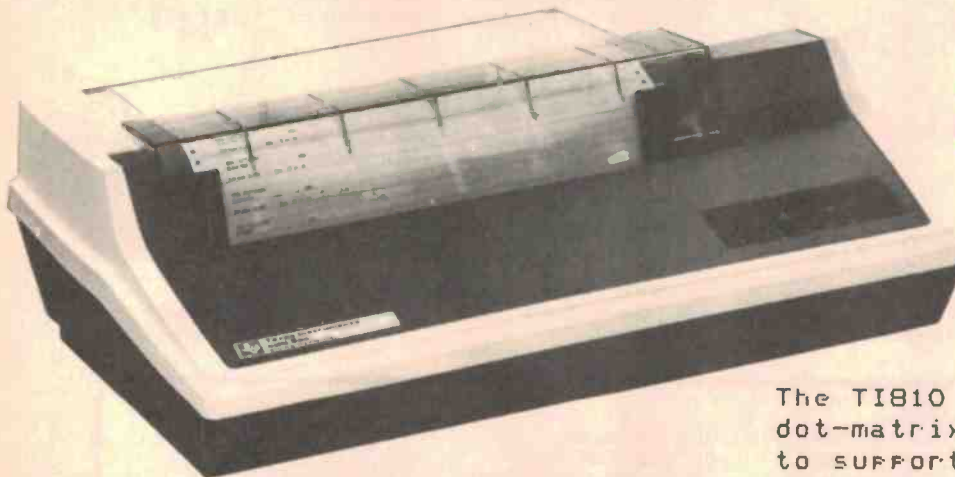

## TI 810 PRINTER

**\$1410 exc. tax**

**\$1692 inc. tax**

Normal list price on this printer is \$1890 exc. tax; save \$480!

The TI810 is a fast, draft-quality dot-matrix printer which is built to support continuous throughput.

### SPECIFICATIONS TI 810 PRINTER

TI 810 PRINTER	
<b>PRINTER</b>	Seven-wire matrix impact 9 x 7 1/8 wide, 7 high dot matrix 64-character limited ASCII 10 132 maximum 8 or 8 (operator — or software — selectable)
<b>THROUGHPUT</b>	150 characters per second 64 at 132 characters per line, and up to 450 at 10 characters per line 33 milliseconds 170 mm per second 16 6/7 inches per second
<b>Line feed</b>	33 milliseconds
<b>Paper slew</b>	170 mm per second 16 6/7 inches per second

<b>PAPER</b>	Adjustable from 76 to 381 mm (3 to 15 inches) Rear or bottom feed One original and five copies
<b>CONTROL SYSTEM</b>	8080 microprocessor system Bidirectional 256 characters Software Programmable Software and operator programmable Prints ASCII characters in a rotating pattern (barberpole) Pulsing audible tone
<b>Self-test</b>	Printer ready busy
<b>Bell</b>	Printer ready busy

<b>COMMUNICATIONS</b>	Serial (EIA RS-232-C) Interface rates 110, 150, 300, 1200, 2400, 4800, 9600 ODD, EVEN or ignore
<b>INPUT POWER</b>	100, 120, 220 or 240 Vac (-10% to 15%) 47 to 63 hertz 200 100 or 120 Vac range, 5 A, 250 V fuse 220 or 240 Vac range, 2.5 A, 250 V fuse
<b>PHYSICAL DIMENSIONS</b>	25 kg (55 pounds) 203 mm (8 inches) 654 mm (25 7/8 inches) 508 mm (20 inches)

### OPTIONS

Serial EIA cable for 810 printer: \$50 exc. tax, \$60 inc. tax.  
Serial cable for 850 printer: \$55 exc. tax, \$66 inc. tax.

4K buffer for 850 printer: \$100 exc. tax, \$120 inc. tax.  
All items carry normal warranty.



# OFFER\*

\* until you've read it through

## TOP QUALITY TEXAS INSTRUMENTS PRINTERS

### TI850 PRINTER

The Model 850 printer is a reliable, versatile dot matrix impact printer featuring 150 cps bi-directional operation and 9 x 9 or 15 x 9 dot matrix characters with true descenders. Mosaic graphics are possible with a squared-off pattern six dots wide by 12 dots high. It is also capable of raster graphics.

It comes with a serial/parallel interface as standard; all you do is change the cable. There is a 256-character buffer inside and a 400-character buffer option is offered, too. The 850 can handle single sheets of paper or fanfold paper up to 254 mm (10") wide and roll paper up to 127 mm (5") in diameter. A comprehensive, copiously illustrated, 108-page manual is supplied with the printer.

This is an example of STANDARD print made by the Model 850 Printer.

This is an example of ENHANCED print made by the Model 850 Printer.

This is an example EMPHASIZED print made by the Model 850 Printer.

This is an example of COMPRESSED print made by the Model 850 Printer.

The Model 850 Printer made this example of DOUBLE-WIDE print.

### TI810 PRINTER

The Texas Instruments Omni 800 Model 810 printer is a receive-only, forms-programmable impact printer. It features a microprocessor system which controls all character recognition, printing and paper movement. Basic operating, data processing and self-test routines for the microprocessor system are stored in ROM.

Random-access memory stores vertical format control routines, which may be locally programmed by the operator or remotely programmed through the communications line.

A single seven-dot-column printhead produces the 9 x 7 dot matrix for character generation. Printing is bi-directional at the rate of 150 characters per second. A full 132-character line is printed in less than one second.

The standard print format is 10 characters per inch (cpi) horizontally and six or eight lines per inch (lpi) vertically. The printer produces one original and up to five copies using sprocket-fed paper in widths from 76.2 to 381 mm (3" to 15").

A detailed, comprehensive, A4-format, 76-page manual is included.

Serial/parallel interface is standard; all you do is change the cable.

There's nothing flash about the Texas Instruments 810 printer — but it's an ideal printer. It prints quickly and cleanly, and it's as close to unbreakable as we've seen. We run three of them in this office — one has been on-line for more than a year without missing a beat. It literally never gets switched off, and runs up to 24 hours a day, all the time.

When we want to move cables in the ceiling, we stand on the printer to get to them! Most printers these days would collapse as soon as you even thought of doing such a thing.

The TI810 is recognised throughout the industry as a reliable, fast workhorse. It's claimed to run at 150 characters a second, and it comes closer to its rating than anything else we've tested. On a solid-text printing test that shows 80 cps machines are actually running at around 34 cps, the 810 comes up just under 130. That's fast.

Its dot matrix typeface is obviously draft quality, without full descenders, but it is clear and readable. If speed and real bullet-proof reliability are what you need, this is the machine.

Normal retail price is around \$2200 before tax, and it's good value even at that price.

This is a sample of the dot-matrix print quality of the high-speed Texas Instruments TI810.

## HOW TO ORDER YOUR TI PRINTER

Fill out the coupon here and enclose a cheque, bank cheque or money order for the amount required made out to **PACSETTER SYSTEMS PTY LTD.**

If you are not paying sales tax, please quote you sales tax number on the coupon, where indicated, or for schools, colleges or other educational institutions, enclose a sales tax declaration on your letterhead.

Delivery will be by freight to anywhere in Australia, fully insured. Shipments will be made ex-stock, but to cover unforeseen delays, please allow up to 4-6 weeks for delivery. This offer is made by Pacsetter Systems (a division of VSI Electronics Pty Ltd, incorporated in S.A.) and ETI is acting as a clearing house for orders. All orders must be via the coupon here, or a photostat thereof if you don't wish to cut the magazine.

### SEND COMPLETED COUPON TO:

### PRINTER OFFER

c/o ETI Magazine  
P.O. Box 227, Waterloo NSW 2017

### Please send me:

- ..... T.I. Model 850 Printer(s) @ \$..... tax free/tax paid\*
  - ..... T.I. Model 810 Printer(s) @ \$..... tax free/tax paid\*
  - ..... Serial EIA cable(s) for 810 printer @ \$..... tax free/tax paid\*
  - ..... Serial cable(s) for 850 printer @ \$..... tax free/tax paid\*
  - ..... 4K buffer(s) for 850 printer @ \$..... tax free/tax paid\*
- plus freight: 850 printer — \$10, 810 printer \$20

\* strike out whichever is inapplicable.

Sales tax no. .... (if applicable)

Name .....

I enclose \$..... total.

Address .....

Cheque or Money Order no. ....

Postcode .....


Signature .....  
(unsigned orders cannot be accepted)

## OFFER CLOSSES 31 DECEMBER 1983



# "I'm certainly going to buy one."
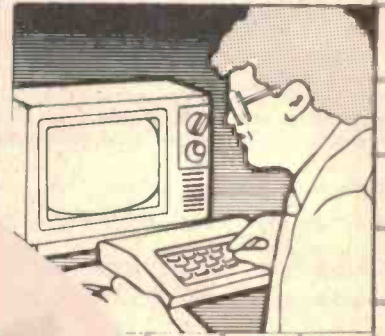
## The brilliant Dick Smith VZ-200 Personal Computer



AMAZING  
VALUE!

# \$199

Cat X-7200

**LIMITED STOCK -  
HURRY DON'T MISS OUT!**

Here it is — the breakthrough you've been waiting for! A personal computer with all the right features: colour graphics, sound, standard Microsoft BASIC for easy programming, a whopping 8K bytes of RAM memory, the ability to work with a standard TV set, and much more. Yet thanks to modern electronics and our buying power, the Dick Smith VZ-200 will cost you only \$199 — far less than any comparable computer (and you get our 7-day money back satisfaction guarantee!). There'll never be a better time to invest in your family's future....

### What the experts say:

"...this is a great machine, and one that is likely to change the face of Australian personal computing." — Editor, APC.

"We are impressed with the excellent implementation of Microsoft BASIC, full on-screen editing, repeat keys and easy-to-use graphics features." — Creative Computing, May 1983.

"If...you want a computer for playing games, for self-education, for learning about BASIC and perhaps for writing your own programs, the VZ-200 has one overwhelming advantage — the number of features for its price." — EA, July 1983.

### Now every family can afford their own personal computer!

Yes, for just \$199, the Dick Smith VZ-200 gives you amazing computing power — far more than many machines two, three or even four times the price. Now you can find out what computers are all about. The kids can use it with their school work. It can keep track of your home budget. It can even help you in your business!

# DICK SMITH Electronics

See page 120 for address details



A614 TH



**& look at these exciting ways to expand your system**

**Technological Breakthrough!**

**Colour Printer/Plotter at an amazingly low price!**



Write & store your own programs/data!

**VZ Datasette**

Get the most from your VZ-200 - store your programs on this deluxe recorder. Made just for the VZ-200 so it's better than any normal cassette unit. Cat X-7207

ONLY \$69<sup>50</sup>

**WANT MORE MEMORY? SIMPLY PLUG IT IN!**

**16K MEMORY MODULE**

Want to write your own programs but find the memory of your computer unable to handle it? This happens with almost every computer, no matter how large its memory! But with the VZ200 the answer is simple - just plug in the memory expansion module and now your VZ200 has a whopping 24K of total RAM! Cat X-7205

\$79



**A great range of games software**

- POKER**  
Straight draw poker - just you and the computer. You can bet, raise, call, bluff and fold, just like the real thing. Cat X-7232
- MATCHBOX**  
A great memory tester! Behind the letters on the grid are pairs of symbols, but you can only see one at a time. Which letters have which pairs behind them? Good colour graphics and sound effects. Cat X-7231
- BLACKJACK**  
Ever wanted to visit Las Vegas? This is the next best thing - OR a good way to practice if you're planning a trip there. Blackjack or '21' is the game and the screen shows all the cards. Cat X-7235
- HANGMAN**  
If you can't guess the mystery word (8 letters) the figure on the screen is hanged - you lose! Based on the popular children's game, this program helps kids with spelling and vocabulary. Cat X-7233

NOTE: Some programs may require 16K memory module.

**ALL ONE PRICE! \$12.50 ea.**

Don't buy just a printer - here's a fantastic NEW 4 colour printer that is an X-Y plotter as well! Use it to produce graphs, pie charts, printing in many different sizes and lots more - all in four colours. Thanks to its built-in microprocessor, all of this can be done easily using simple commands in your BASIC programs.

Look at some of the features:  
 ★ 4 colours! (black, green, red, blue [uses ball pen inserts]) ★ A PLOTTER as well as a printer ★ Standard Centronics-type parallel interface ★ 10 chars. per sec. printing speed ★ Software switching between printing and plotting ★ 40/80 columns per line ★ Resolution 0.2 mm ★ Step size 0.2 mm min. ★ Full 96 char. ASCII set (caps and lower case) ★ Inbuilt microprocessor provides 'intelligence' - plots lines, etc in response to simple commands ★ Plotting speed 52 mm/sec max vertical and horizontal. 73 mm/sec for 45° plotting.  
 ★ & the best feature of all is THE PRICE!

Cat X-7208

**AVAILABLE THIS MONTH**

**ONLY \$299**

Use any Centronics type printer with this **Printer Interface**

Now get a printed 'hard copy' of both your programs and your data with this low cost Printer Interface. This superb compact module simply plugs into the back of your VZ200 alongside the memory expansion module, and lets you connect it to any standard Centronics-type printer, (like the X-7208 above). Includes printer cable.

ONLY \$49<sup>50</sup>

Cat X-7210

**WE'VE GOT NEW BOOKS TOO!**

**VZ-200 Technical Manual**

Want to get the most from your VZ-200? This technical manual explains all the ins and outs, ups and downs. For the real computer enthusiast or the beginner who wants to know more! Cat B-7204

\$9<sup>50</sup>

**Introduction to Computing**

Are you a 'babe in the woods' when it comes to computing? Try this one out - written just for YOU! In a language you can understand, it will have you as VZ-200 expert in just a few days! Cat B-7200

\$9<sup>95</sup>

**First Book Of Programs**

Tried, trusted and true programs for your VZ-200. There's something for everyone - and remember, they're all written in BASIC so you can save these on cassette so you only have to key them in once! Cat B-7202

\$6<sup>95</sup>

**Plus these great financial & educational programs**

- STATISTICS 1**  
A great introduction to the basic principles of statistical analysis. Explains about the Mean, Variance Standard Deviation, different types of Distribution etc. Gives you the opportunity to test your knowledge by working out examples. Cat X-7251
- STATISTICS 2**  
Following on from Stat. 1, this program deals with more advanced concepts. Tests of statistical significances. Students T-test, the Chi Square test and so on. Cat X-7252
- MATRIX**  
Working out mathematical matrices can be a real chore. This program gives you more skill in handling them by practice. Cat X-7253
- TENNIS LESSON/GOLF LESSON**  
Challenge your computer to a game of tennis or golf. It plays by the rules so even if don't win you can learn a quite a lot about the game. Cat X-7254
- PORTFOLIO MANAGEMENT**  
Like to invest in the share market? This program will help you to analyse and manage your portfolio for max. profit and min. risk. It gives you a working model of your portfolio, so you can see the likely effects of any changes. Cat X-7261
- DISCOUNTED CASH FLOW ANALYSIS**  
An ideal working tool for executives, accountants etc, providing a model for market capital budgeting decisions and minimising an investment without prejudicing a project's liquidity. Cat X-7262
- FINANCIAL RATIO ANALYSIS**  
A program for the professional accountant, investment advisor, or small business owner who doesn't want to stay small! Cat X-7263

**ONE LOW PRICE \$12.50 ea**







## SEAFIGHT

C. Huebel, Macquarie ACT

You are in control of an aeroplane circling over a submarine and you have to hit the submarine. You have an unlimited amount of bombs and the bombs are released by pressing any key. But watch out for the battleships because if you hit one of them your five lives will be lost.

The game requires 16K to run it.

### SEAFIGHT

```

1 REM SEAFIGHT
2 REM
3 REM (C) C.HUEBEL 1983
4 REM
50 PRINT "
60
70 NEXT N
80 PRINT "
85 LET H=0
86 PRINT AT 2,0;"
87 PRINT AT 1,1;"SCORE=";S;TAB
11;"HI-SCORE=";H;TAB 24;"LIVES="
;L
90 LET A$=""
100 LET B$=""
110 LET C$=""
120 LET D$=""
130 LET E$=""
140 LET F$=""
150 LET F=INT (RND*5)+1
160 PRINT AT 12,F;A$;AT 13,F;B$
;AT 12,F+7;A$;AT 13,F+7;B$;AT 12
,F+14;A$;AT 13,F+7;B$;AT 12,F+21
;A$;AT 13,F+21;B$
170 LET G$=""
180 LET I$=""
190 LET G=1
200 FOR N=23 TO 1 STEP -1
210 PRINT AT 4,N;D$;AT 3,N,C$;A
T 18,N;I$
220 IF INKEY$ <> ** THEN GOTO 1
000
230 NEXT N
240 LET G=2
250 FOR N=1 TO 23
260 PRINT AT 4,N;F$;AT 3,N;E$;A
T 18,N;G$
270 IF INKEY$ <> ** THEN GOTO 1,
000
280 NEXT N
290 GOTO 190
1000 REM **FIRE ROUTINE**
1005 FOR M=5 TO 13

```

```

: 1010 PRINT AT M,N+((G=2)*4);"V"
: 1020 LET N=N+(G=2)-(G=1)
: 1030 IF N=1 OR N=23 THEN GOTO 20
: 00
: 1040 IF G=1 THEN PRINT AT 4,N;D$
;AT 3,N;C$;AT 18,N;I$
: 1050 IF G=2 THEN PRINT AT 4,N;F$
;AT 3,N;E$;AT 18,N;G$
: 1055 PRINT AT M,N+((G=2)*4)-1)-
((G=1)*2);" "
: 1060 NEXT M
: 1070 IF N+((G=2)*4)=F+4 OR ((G=2
)*4)=F+11 OR ((G=2)*4)=F+18 OR (
(G=2)*4)=F+5 OR ((G=2)*4)=F+6 OR
((G=2)*4)=F+12 OR ((G=2)*4)=F+1
3 OR ((G=2)*4)=F+19 OR ((G=2)*4)
=F+20 THEN GOTO 1080
: 1075 GOTO 3000
: 1080 FOR M=14 TO 18
: 1090 PRINT AT M,N+((G=2)*4);"V"
: 1100 LET N=N+(G=2)-(G=1)
: 1110 IF N=1 OR N=23 THEN GOTO 20
00
: 1120 IF G=1 THEN PRINT AT 4,N;D$
;AT 3,N;C$;AT 18,N;I$
: 1130 IF G=2 THEN PRINT AT 4,N;F$
;AT 3,N;E$;AT 18,N;G$
: 1140 PRINT AT M,N+((G=2)*4)-1)-
((G=1)*2);" "
: 1150 NEXT M
: 1160 GOTO 4000
: 2000 PRINT AT M,N+(((G=2)*4)-1)-
((G=1)*2);" "
: 2005 IF G=1 THEN GOTO 240
: 2010 IF G=2 THEN GOTO 190
: 2999 REM **FIRE FAILED**
: 3000 PRINT AT 10,10;"FAILED...."
: 3005 PAUSE 50
: 3010 PRINT AT 5,N-1;" "
T 6,N-1;" "
: 3020 LET L=L-1
: 3025 IF L=0 THEN STOP
: 3027 LET C=1
: 3028 PRINT AT 10,10;" "
: 3030 GOTO 4010
: 3999 REM **FIRE HIT**
: 4000 PRINT AT 10,10;"HIT....."
: 4002 PAUSE 50
: 4005 LET C=2
: 4010 PRINT AT 18,N;"
: 4020 PRINT AT 3,N;" "
;AT 4
,N;" "
;AT 12,1;" "
;AT 13,1;" "
;AT 10,10;" "
: 4030 LET S=S+((C=2)*10)
: 4040 IF H<S THEN LET H=S
: 4050 GOTO 87
: 9998 SAVE "SEAFIGHT"
: 9999 RUN

```

## NUMBERS

The computer prints a random number and the player must then enter this number. Each time a new number is added to the existing one, and the player has a limited amount of time to recall this number and enter it.

At the end it shows how many times the player guessed the number.

```

5 REM NUMBERS
10 LET A$=""
20 LET Y=1
30 LET X=INT (RND*10)
40 LET A$=A$+STR$ (X)

```

Frank Papadopoulos, Dulwich Hill, NSW

```

50 PRINT A$
60 PAUSE 1000/Y
70 CLS
80 INPUT B$
90 IF A$<>B$ THEN GOTO 190
100 IF Y<5 THEN PRINT "THAT""S
O.K."
110 LET Y=Y+1
120 IF Y=5 AND Y<8 THEN PRINT
"WELL DONE ""
130 IF Y=8 THEN PRINT "THAT""S
EXCELLENT...."
140 GOTO 30
190 PRINT "TOO BAD...."
200 PRINT A$;" WAS THE ANSWER"
210 PRINT B$;" WAS YOUR ANSWER"
220 PRINT "YOU LASTED FOR ";"Y;"
GOES"

```

## THE ZX SPECIALISTS

The Professionals who care!

SPECTRUM HAS ARRIVED!!

Spectrum 48K version  
\$399.00 (add \$7 for p&p)



### HARDWARE



32K D RAM Pack in attractive case .....  
\$125.00 (incl. p&p)

Suitable for ZX81. No extra PSU required. Plugs into Expansion Port. Works also with Printer. Unique wobble free design.

X ROM CARD ..... \$69.95 (incl. p&p)  
Works with ZX 81 only. Compatible with Sinclair 16K RAM Pack. Has built-in Printer interface for centronics type printers and contains EPROM Burner for Basic and machine code programs.

PROGRAMMABLE CHARACTER GENERATOR ..  
\$95.00 (incl. p&p)  
(Fully assembled) Suitable for ZX 81/80 fitted with 8K ROM. Create own character sets, high resolution graphics, etc. FREE supporting software of Demmo, 2 Games and instructions.

For the ZX80 and  
Microace

VIDEO UPGRADE UNIT for ZX 80 .....  
\$38.50 (incl. p&p)  
(Fully assembled). Upgrade to fully animated graphics of ZX81. Will now run in SLOW MODE. Requires 8K ROM—not included.

90 Day warranty on all products



Payment by cheque, money order or Bankcard.  
For further information send a large S.A.E. to

# VENDALE

VENDALE PTY. LTD.,  
Dept. T7, Box 456, Glen Waverley,  
Vic. 3150, Australia. Ph: (03) 232 0444.



## DRILLS FOR PROFESSIONALS

VALUE • QUALITY • RELIABILITY

Use these products and improve efficiency



PISTOL DRILL  
IN STAND  
12V DC

000-62-402 Pistol Drill—\$39.22 incl. S/Tax. Single speed unit ideal for production line board assy. and repairs also modelling and prototypes—7000 RPM.  
000-64-493. Drill Stand—\$39.22 incl. S/Tax



2 SPEED PISTOL DRILL  
12V DC

000-62-251—2 SPEED Pistol Drill \$47.00 incl. S/Tax. 850 and 7000 RPM. Torque plus for the heavier jobs. SUPERB VALUE.

Power supply to suit above—000-62-608 12V. 1A. \$17.40 incl. Tax.  
Workshop Kit—Case, Pistol Drill, Stand, Orbital Sander, Jigsaw, Flexible Shaft and extras—\$200.00 incl. S/Tax.



MD1  
General  
Purpose  
6 Speed  
850 to 3100  
RPM

Compact Bench Drills for volume operations. Fast, reliable. Value plus for production. \$198.00 incl. Vice. S/Tax extra.

240V AC



MD1H  
Printed  
Circuit  
Board

2 Speed  
8000 & 12,000  
RPM

## IS FINISH A PROBLEM?

Trim and Rework whilst Assembling?  
Special shapes? Prototype construction?  
Product need that little touch?

WE HAVE THE ANSWERS



Jigsaw  
12V DC

000-62-108 JIGSAW—\$39.22 inc. S/Tax. Cuts anywhere—1mm radius corners. Wood, plastic, fibreglass, aluminium, PCB's—to 1/4" thick. A MUST!  
000-62-117 Coarse, 000-62-144 Fine  
Blades—\$2.49 Set of 10.



Angle Grinder  
12V DC

000-63-605—ANGLE GRINDER \$47.70 inc. S/Tax. REAL BITE—Dresses boards and parts easily and quickly. Essential for production line—speeds up assembly operations.

Engrave Names and Numbers—Fine finishing 18000 RPM.  
12V power supply. 000-62-608 \$17.40 incl. S/Tax.



Wood  
000-63-669  
\$4.16




Metal  
000-63-678  
\$8.16

Fit these blades to your Angle Grinder—Use it in the Drill Stand—dock those connectors, strips, sockets, etc.



Gravilo  
12V DC

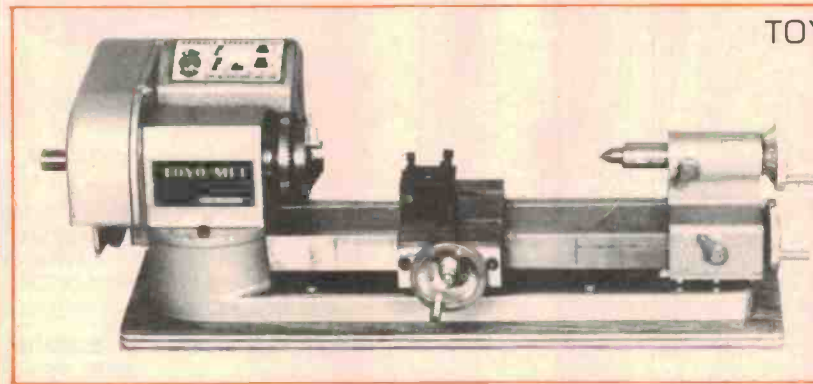


## TOYO MINI-LATHE

\$530 + s/tax

Standard as shown.  
Centre height—50 mm  
Swing (Carriage)—50 mm  
Cast Iron Bed!  
Between centres—250 mm  
Swing (bed)—100 mm  
Thru head—12.5 mm  
Options—  
Taper Turning, Screw Cut, etc.


## MODULE ENCLOSURES

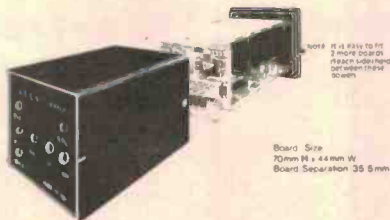

NOTE: If it fails to fit 2 more boards. Place a solder bridge between these 20 pins.

Board Size  
70mm H x 44mm W  
Board Separation 35.5mm

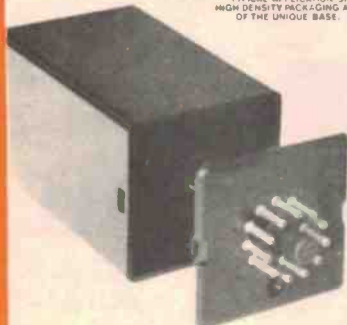
TYPICAL APPLICATION SHOWING HIGH DENSITY PACKAGING AND VERSATILITY OF THE UNIQUE BASE.



Board Connectors Pins, Sockets & Components available.

80 mm H. x 50 mm Sq.  
With 8 Pin (Octal) Base \$4.55  
With 11 Pin Base \$4.65  
Power Supply G.P. P.C.B. \$3.20  
General Purpose P.C.B. \$3.20  
240V—24V AC IVA Trans. \$5.87  
Relay—10A 240V Contacts  
24V DC Coil C/O \$6.30

## HEATSINK EXTRUSION

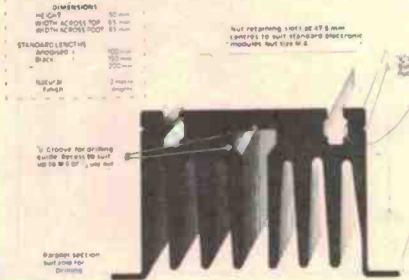

Versatility is the keynote of this extrusion. The incorporated features permit high-speed assembly with minimum use of jigs & fixtures for fitting electronic "pack" & stud mount devices, as well as terminals.  
Performance  
100 mm Black Anodised length—  
Vertical in free air.  
1-4° C/W @ 30W  
Don't forget—this extrusion is compatible with Series II Extrusions—

100 mm flat black \$9.50 + s/tax if applicable

Send Self Addressed Envelope for full price and accessory list! (Accessories include: panels, cutters, blades, turn, brushes, stones, etc.)

NAME .....  
ADDRESS .....  
BANKCARD NO.  
OR CHEQUE .....  
EXPIRY DATE ..... VALUE ..... SIGNED .....

**mintool**  
AUSTRALIA PTY. LTD.  
134A AYR STREET,  
DONCASTER, VIC. 3108  
Tel. 850 9887



Post & Pack  
To \$25+\$3.50  
To \$100+\$5.00  
To \$150+\$7.00  
To \$400+\$10.00  
Over \$400+\$14.00





# MICROBEE

NEW PROGRAMS NOW AVAILABLE FROM MYTEK

**DEFENDER** is our fastest, most involved and challenging arcade game. You must defend earthlings in your territory for earthlings are being captured and turned into mutants. Shoot down the enemy by controlling your craft through air-space. If an earthling is captured, you must destroy the Alien and catch the earthling as he plummets to the ground.

Our version of DEFENDER is complete with Swarms, Space Mines, Baiters, Bombers, Pods, Smart Bombs, Hyperspace and Twin Displays. The MYTEK quality explosions are guaranteed to make you wince!

**\$22.50**

**CHOPPER** is the game that took first prize in our recent competition. Your mission is to rescue stranded allies in enemy territory by helicopter. The enemy has a large fleet of Kamakaze pilots and an inexhaustible supply of missiles.

This high resolution graphics arcade game is very fast. Realism is achieved by a realistic helicopter with spinning blades, people that wave frantically and run into the helicopter. And the explosions are real! Joystick compatible.

**\$20.00**

**KING KONG** is a complete version of DONKY KONG fully equipped with monkey, drums, people and many other animated creations. You owe it to yourself to see true cartoon animation on your MicroBee. Joystick compatible.

**\$20.00**

**KILOPEDE & GHOST MUNCHER** are two super arcade games that were originally to sell for \$17.50 each but a typing error in our catalogue placed them together by mistake! We have decided to leave them together for what must be the best value in this catalogue.

**KILOPEDE** revolves around a nasty Centipede charging down through the garden towards you. When your beetle makes a direct hit, the Centipede breaks into two! Now you have double trouble. Watch out for the flees, bugs and most of all, the gardener's boot!

**GHOST MUNCHER** is the MicroBee version of PAC MAN. Guide your little Chomper around a maze avoiding the Ghosts. Once a Power Pill is eaten, your Chomper can chase the Ghosts. PAC MAN is one of the greats of arcade games and now you can have a true to life version on your MicroBee!

Both games together on the one cassette **\$20.00**

**FROGGER** is modelled after the popular arcade game of the same name. Your frog is in a real predicament. To get home, he must firstly cross a four lane highway, dodging cars and trucks. If he survives, he must then negotiate the flooded river, jumping from log to log until he arrives safely home.

**\$17.50**

**MYTEK WORDPROCESSOR** is the MicroBee's most up-to-date electric typewriter. Although powerful beyond belief, the MYTEK WORDPROCESSOR is quick and simple to use. Handwritten letters and typewriters are a thing of the past. Any member of your family, club or of-

fice will be able to save time and improve the look of their essays, letters, assignments, documents, accounts and all other correspondence. Everybody can benefit from this Wordprocessor.

The MYTEK WORDPROCESSOR is available on both cassette and EPROM chip. If the serial number of your MicroBee starts with nine (9) then your MicroBee takes an 8K EPROM. Otherwise it takes two 4K EPROM. Please specify.

Cassette: **\$35.00**

EPROM: **\$39.00**

**TRSBEE** is a package of three programs that loads TRS-80 Model 1 and 3 program tapes into the MicroBee without any additional hardware. Although some program editing will still be required prior to their running, the majority of program typing time is saved by TRSBEE. The first program loads TRS-80 BASIC programs into MicroWorld BASIC. Most programs may then be edited and run. The second program in the package loads any TRS-80 machine code file into MicroBee memory. The third program loads TRS-80 assembler files into the MicroBee EDITOR/ASSEMBLER. Any TRS-80 Model 1 or 3 tape may be loaded. TRSBEE opens up a whole new world of possible software on your MicroBee!

**\$30.00**

**TAPE DOCTOR** is an easy to use programming aid for loading and saving programmes on tape. TAPE DOCTOR will load nearly any program from tape, regardless of protection system. BAD LOAD files may be loaded also and TAPE DOCTOR will aid in finding the faulty byte. Saving files of any type become a breeze. Create Auto Start BASIC files and files that include both BASIC and machine code subroutines. Comes complete with a monitor. If you use tapes at all, TAPE DOCTOR is a must.

**\$17.50**

**DEBUG** is a utility program to enable the debugging of machine code programs as they are written on the MicroBee using EDASM. The program operates at the assembler level. Break points are inserted in the source code as calls to a subroutine. The source code, with included breakpoints, is then assembled and the resulting code is executed in the normal way. Program execution will halt at the first break point encountered with a display of the internal Z80 registers. With execution halted, registers can be examined and modified as can memory locations. Execution can then proceed until the next breakpoint is encountered. By means of breakpoints inserted in the source code, the programmer can examine all or any part of the operation of the program on a statement by statement basis.

**\$17.50**

**FORTH** is a language that is much more powerful and versatile than BASIC but executes nearly as fast as machine code. We have negotiated with the authors of FORTH to be able to bring you this powerful language with MYTEK quality documentation at a give away price. Never before and never again will you be able to run FORTH on your MicroBee so inexpensively!

**\$29.00**

**LOGO BEE** is a graphics language. Specifically designed to introduce children to computer programming, LOGO BEE is destined to become a standard on the MicroBee. Both simple and intricate designs may easily be drawn on the screen in hi-res through use of short and easy to understand LOGO BEE programs.

LOGO BEE programs are based on an imaginary turtle moving about the screen leaving a trail behind him. The turtle may be moved in any direction for a given distance. He may then be turned any number of degrees and moved again. The trail may also be turned on or off. Each short routine is given a name, such as SQUARE, CIRCLE or TRIANGLE, depending on the shape created. These routines may be used within other routines. In this way, the concepts of programming can be easily introduced to young children and adults who have had no previous computer experience.

LOGO BEE was written specifically for MicroBee graphics. The program is essentially idiot proof and is a joy to use.

**\$22.50**

**COMPOSER BEE II** is an excellent aid in learning music theory. Write your own melody on the screen staff and listen to the result. You may now transpose, add to or modify your tune. The notes on the staffs will change accordingly and you may again listen to the result. COMPOSER BEE II is graphics orientated, has a 2 octave range, handles accidentals, non-standard timing and repeated sections of music. Teachers and students alike will welcome COMPOSER BEE II.

**\$20.00**

## HOW TO ORDER

Fill out the following form and send it to MYTEK Computing:

Program	Price
Postage — Allow \$1 per item	
<b>TOTAL</b>	

Name \_\_\_\_\_

Address \_\_\_\_\_

Suburb \_\_\_\_\_

Postcode \_\_\_\_\_

Method of Payment: CHEQUE/BANKCARD/M O /CASH

Bankcard No. \_\_\_\_\_

Name on Bankcard \_\_\_\_\_

All MYTEK programs come on cassette and will run on any 16K or 32K MicroBee Plus or IC  
We are able to take phone orders if a bankcard is being used



**MYTEK** COMPUTERS


1 Kent Street, Bicton, 6157. W A Telephone (09) 330 7336


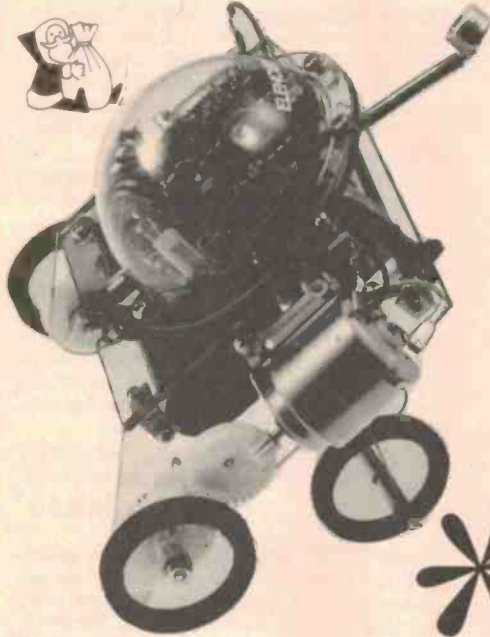
# Special Announcement

Jaycar Electronics is proud to announce a range of very low cost "Turtle" like robot kits. Don't let the low prices fool you — they are not toys.

The units feature solderless connections with explicit illustrations to ease assembly. Only simple tools (i.e. screwdriver, pliers etc.) are needed to assemble.



## PIPER MOUSE

This "microbot" is powered by 2 DC motors that drive wheels. When a special ultrasonic whistle is blown, the unit goes left, right, straight ahead according to your command. Complete, including perspex dome cover!

Be a Pied Piper!  
Cat. KJ-6680

ONLY \$39.95

## AVOIDER (not illustrated)

Similar to the Piper Mouse, but this unit travels on its own. It avoids objects because it has an infra-red beam system. Very clever!

Cat. KJ-6682

\$44.95

## LINE TRACER (not illustrated)

This robot will automatically follow a black line drawn onto a sheet of paper. It uses an infra-red feed back system.

Cat. KJ-6684

\$39.95

## MEMOCON CRAWLER (not illustrated)

This robot is controlled by a keyboard which is supplied. The operation of the unit is programmed by the keyboard and stored in RAM. All movements can be controlled as well by lights (beams) and sound (buzzer). A very sophisticated unit.

Cat. KJ-6686


\$79.95

**FROM \$39<sup>95</sup>**

Note: The "Microbots" work well on their own but can also be used as a platform for robotic development. If you are a robot experimenter you will find them useful as they help resolve the mechanical parts problem.

## 30W + 30W

## STEREO PREAMPLIFIER STEREO AMPLIFIER

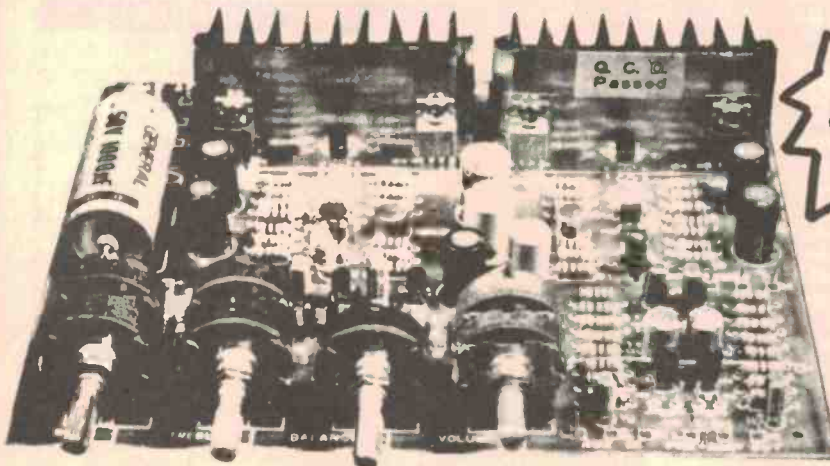

ONLY  
\$34.95

- Fully built and tested
- Separate bass, treble, balance and volume controls
- Less than 0.1% distortion
- Mic, phono and aux. inputs (line)
- Power supply components on board

Back at last! No hassle amplifiers. Just connect a transformer, speakers a signal and you're away!

STAGGERING VALUE

\$34.95!!

## MICRO COMPUTER POWER SUPPLY

All multi-polarity D.C. supply problems solved! This fully built and tested unit provides you with REGULATED power as follows: —

- 5V @ 0.5A, +5V @ 6A,
- 12V @ 0.5A and
- +12V @ 2.5A!!

(You can modify it to give +/-15V)

- Current limit on all outputs
- Heavy duty Darlington Transistors used
- Only power transformer(s) needed

A price breakthrough at —  
\$39.95!!

(Suitable transformers commonly available)

PLEASE RING YOUR NEAREST STORE FOR EXTENDED TRADING HOURS OVER THE CHRISTMAS PERIOD

PLEASE RING YOUR NEAREST STORE FOR EXTENDED TRADING HOURS OVER THE CHRISTMAS PERIOD



# 3 1/2 DIGITAL PANEL METER

(not illustrated)

Low cost unit. Completely self-contained. No longer an expensive proposition! This easy-to-build kit (takes about 1 hour) is self-contained, compact and even comes with a front panel filter/bezel. It can be battery 6V or 12V powered.

- 200mV. Full scale (+/- 199.9mV)
- Input impedance 10 to the twelfth ohms
- Required DC 5-6V @ 150mA
- Guaranteed to reset to zero at zero input voltage
- Automatic reverse polarity indication
- Assembly instructions include notes on using your DPM for: Amp-meter, AC-Volmeter, Anmeter, Thermometer, Frequency Counter, Capacitance Meter (circuits supplied)

STAGGERING VALUE  
Cat. KJ-6670

\$29.95

## MN3001 BUCKET BRIGADE

This has been used in many projects lately and has been very hard to get. They are now available from us at a lower-than-normal price.

NORMALLY \$22.50

ONLY \$19.50 each - Cat. ZK-8001

# SLASHED \$3



## GOLD PLATED WIRE WRAP SOCKETS Incredible Value!




24 and 40 pin quality. A must for high cost LSI  
Cat. PI-6519 24 pin \$4.95 - \$4.50 10+  
Cat. PI-6520 40 pin \$6.95 - \$6.25 10+

# Value!



## IEC Cable Connectors

INCREASED RANGE

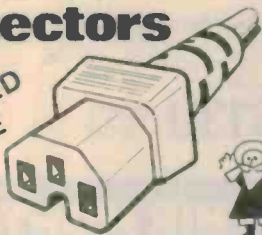

Most imported equipment these days now uses IEC-320 style AC power inlet connectors. Indeed, the electronics mags will soon be specifying these connectors on many of their mains-powered projects to simplify (and therefore make safer) mains wiring. Jaycar now stocks a range of ELECTRICITY AUTHORITY APPROVED mains line cords. We have them in straight entry, left and right entry with and without standard 240V mains moulded plug. Each cord is a generous 2 metres long and is rated at 7.5 amp continuous.

Cat. No	Description	Price
PS4302	LINE CORD STRAIGHT ENTRY 2M	\$3.95
PS4304	LINE CORD R/HAND ENTRY - 2M	\$3.95
PS4305	LINE CORD L/HAND - 2M	\$3.95
PS4306	LINE CORD STRAIGHT ENTRY WITH 240V PLUG - 2M	\$4.95
PP2302	IEC 320 CHASSIS PLUG	\$2.95
WM4530	2 PIN 240V PLUG MOULDED TO 2M FIG. 8 7.5 AMP CORD. BLACK IN COLOUR (Note: the first 5 items are grey in colour)	\$2.95

## FERGUSON TRANSFORMERS

MF-1000	PL9/5VA	PCB	\$7.90
MF-1002	PL12/5VA	PCB	\$7.90
MF-1004	PL15/5VA	PCB	\$7.90
MF-1006	PL18/5VA	PCB	\$7.90
MF-1009	PL24/5VA	PCB	\$7.90
MF-1012	PL30/5VA	PCB	\$7.90
MF-1015	PL40/5VA	PCB	\$7.90
MF-1018	PL18/12VA	PCB	\$8.95
MF-1021	PL24/12VA	PCB	\$8.95
MF-1024	PL30/12VA	PCB	\$8.95
MF-1027	PL15-18/20VA	LP	\$17.95
MF-1030	PL12/20VA	LP	\$14.50
MF-1033	PL15/20VA	LP	\$14.50
MF-1036	PL18/20VA	LP	\$14.50
MF-1039	PL24/20VA	LP	\$14.50
MF-1042	PL30/20VA	LP	\$14.50
MF-1045	PL40/20VA	LP	\$14.50
MF-1048	PL12/40VA	LP	\$17.95
MF-1051	PL15/40VA	LP	\$17.95
MF-1054	PL18/40VA	LP	\$17.95
MF-1057	PL24/40VA	LP	\$17.95
MF-1060	PL30/40VA	LP	\$17.95
MF-1063	PL40/40VA	LP	\$17.95
MF-1066	PL30-9/60VA	LP	\$20.95
MF-1069	PL12/60VA	LP	\$20.95
MF-1072	PL15/60VA	LP	\$20.95
MF-1075	PL18/60VA	LP	\$20.95
MF-1078	PL24/60VA	LP	\$20.95
MF-1081	PL30/60VA	LP	\$20.95
MF-1082	PL40/60VA	LP	\$20.95
MF-1087	PP88/1000 Bell transformer		\$13.95
MF-1092	TS115/125B 115V STEPDOWN		\$79.50
MF-1095	PF3577/JT144 56VCT 2 amp		\$34.50
MF-1098	OP590 Line output transformer		\$45.00
MM-2015	PF4361		\$39.50
MM-2016	PF4362		\$49.50
MM-2017	PF4363		\$49.50

## VIDEO SENSATION

AT LAST  
A Video Enhancer/  
Distribution Amplifier  
designed  
EXCLUSIVELY  
for AUSTRALIA

BACK IN STOCK!!

12 Volt AC  
Adaptor only  
\$12.95



Cat. AV6501

NOT A KIT  
BUILT, TESTED  
AND GUARANTEED  
KIT VERSION  
ONLY \$39.50

# \$49.50

Jaycar has had designed a high quality, high performance Video Enhancer which is specifically for the Australian 625 line 50 frame PAL-D system.

As far as we know it is the ONLY Australian designed, Australian built unit available!!

But, guess what? The Jaycar AV6501 Enhancer is CHEAPER than its inferior imported Asian counterparts!!

This unit is professionally designed and University tested! It works and it works well.

### SPECIFICATIONS

- 1 Maximum enhancement, not less than +8.3dB @ 2MHz
- 2 Enhance disabled (By-pass) response, DC to 5MHz, -0.5-1.0dB.
- 3 Colour Subcarrier 0dB notch frequency, tunable to 4.43 MHz. +/- 0.5dB, all settings.
- 4 Amplifier group delay, less than 0.076us
- 5 Signal handling capability not less than 1.35 volts p.p. (Sync. is clipped first)
- 6 Power 12V AC @ 100mA
- 7 Controls, ON/OFF, ENHANCE, ENHANCE/BYPASS SWITCH, CORE/GAMMA CONTROL
- 8 Input connector, RCA socket
- 9 Output connector, RCA socket x 3

### DESIGN FEATURES

- 1 A unity gain notch at the colour subcarrier frequency, whose purpose is to prevent chrominance to luminance errors at high enhance levels.
- 2 A closed loop configuration with lead lag compensation to achieve stable, well defined gain
- 3 DC coupling, eliminating large capacitors in series with the video signal and achieving DC response for applications requiring it.
- 4 Low output impedance prior to termination resistors, enabling up to three outputs to exist and be used or left unterminated.
- 5 A level dependant closed loop response or Gamma control (Core)
- 6 Clip on negative going signals at -67 volts into 75 ohms to prevent sync errors owing to overshoot.

## NEW ETI JOYSTICK CONTROLLER

Ref: ETI Dec 83  
True proportional control with this kit.  
Includes recommended joystick unit.


ONLY \$24.95



Following the spectacular success of the DP2010 Digital Multimeter kit, we now have an ENGINE ANALYSER KIT! But the spectacular thing is the price! It is ACTUALLY CHEAPER than the DPM 05 Display and Case!! The Minitune will measure voltage, resistance (down to a very low range), RPM and Dwell Angle.  
Cat. KJ-7012 \$42.95

TEST LEADS TO SUIT ONLY \$2.95

Function	F.S.D	Resolution	Accuracy
Voltage (d.c.)	20V	10mV	0.5% - 1 digit
	200V	100mV	0.8% - 1 digit
Resistance	2000	100ohm	0.8% - 1 digit
	20k	100	0.5% - 1 digit
R.P.M.	20,000 p.p.m	10 p.p.m	1% - 3 digits
Dwell	90	0.1	2% - 3 digits

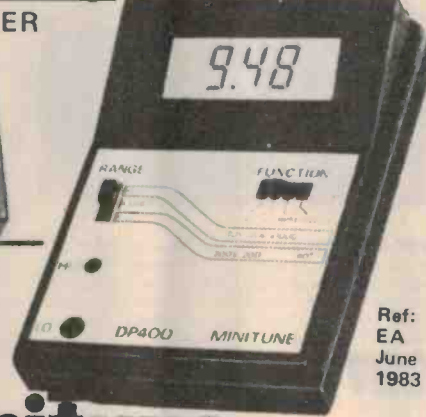

Ref: EA June 1983

# minitune \$42.95



## CX-230 ELECTRONIC CROSSOVER

Cat. AZ-5030 ONLY \$257  
See previous ad for technical data

# Jaycar

Incorporating  
ELECTRONIC AGENCIES

**SYDNEY** SHOWROOMS  
117 YORK STREET - PHONE: (02) 264 6688 and (02) 267 1614  
**CARLINGFORD** TELEX: 72293  
Cnr. CARLINGFORD & PENNANT HILLS ROAD - PHONE: (02) 872 4444  
**CONCORD**  
115 - 117 PARRAMATTA ROAD - PHONE: (02) 745 3077  
**HURSTVILLE** 121 FOREST ROAD - PHONE: (02) 570 7000

## NUMBER 1 FOR KITS

POST AND PACKING CHARGES  
\$5 - \$9.99 (\$1.50) \$10 - \$24.99 (\$3.20)  
\$25 - \$49.99 (\$4.50) \$50 - \$99.99 (\$6.50)  
\$100 - \$198 (\$8.00) Over \$199 (\$10)

"Free INSURANCE for Road & Registered Post over \$200"

All heavy or bulky items (over 20kg.) sent Comet Road Freight \$12.00 anywhere in Australia.

SHOP HOURS CARLINGFORD, CONCORD & HURSTVILLE

Mon - Fri 9am - 5:30pm Sat - 9am - 12pm Thurs night 8:30pm

SHOP HOURS SYDNEY

Mon - Fri 8:30am - 5:30pm Sat - 8:30am - 12pm Thurs night 8:30pm

MAIL ORDERS AND CORRESPONDENCE: P.O. Box 185, Concord, 2137



Mail Order

By



BANKCARD


Via Your Phone

PLEASE RING YOUR NEAREST STORE FOR EXTENDED TRADING HOURS OVER THE CHRISTMAS PERIOD



# K-NAR COMPUTER CARDS

## S100 Z80 System Card Specialists

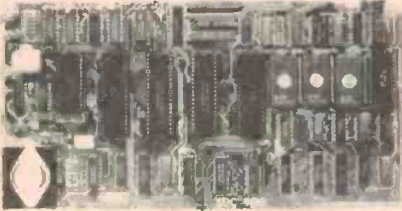

**SBC-800.** 4 Mhz Z-80 CPU, two serial RS232 ports, software programmable Baud rate gen., Centronics parallel port, 22 prog. I/O lines, real time clock (battery backed), 2K CMOS RAM power on reset/power fail detect battery backed as standard, etc. List Price \$495.

**\$415** OUR PRICE



**256 DYNAMIC RAM - DRC-II.**  
 • Companion RAM for SBC-800  
 • Ideal for CP/M plus 3.0. List Price \$865.

**\$795** OUR PRICE




**FDC-II.** Enhanced floppy disk controller, IBM 3740 compatible, operates 5" & 8" and single/density drives, handles up to 4 drives, runs multi-density CP/M2.2 & MP/M 2. Vectored interrupt operation optional. List Price \$465.

**\$389** OUR PRICE



**CRC-64.** Fool-proof memory system. State-of-the-art 64K CMOS memory card with memory protection, on board battery back-up, compatible with DRC-II, write protection enable/disable. List Price \$675. Our Price \$565.

**\$593** OUR PRICE

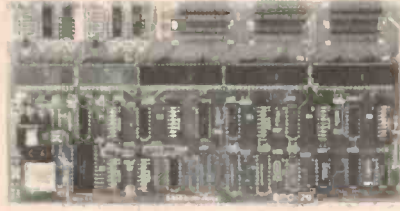


**SPC-29.** High performance dual serial & 9 parallel port I/O CARD, with full I/O address decoding Switch selectable baud rates. Link patch area, programmable modes for strobed/latched I/O. List Price \$295.

**\$247** OUR PRICE



**S-100 WIRE WRAP CARD.** Gold-plated edge connectors, through hole plating, provisions for four regulators, distributed power rails. I/O connector provision on top of card.

**\$33** OUR PRICE

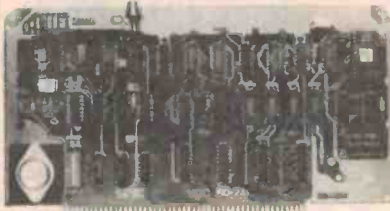


**VDC-8024.** The low cost alternative to stand-alone terminal. Flexible 80 x 24 memory mapped video display board with full ASCII, semi graphics. Inverse and half intensity video, flicker free screen updating. Battery backed option offers diagnosis of system shut downs. List Price \$325.

**\$278** OUR PRICE



**SERIAL MULTICHANNEL I/O MPC-6.** Intelligent 6 channel RS232C communications with I/O buffering and drivers. • Build a multi-user, multi-tasking system.

**\$450** OUR PRICE

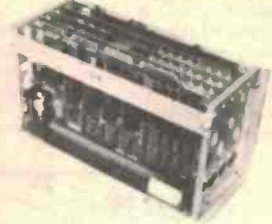

**MINI CARD CAGE.** Compact card cage frame with 5-slot motherboard plated through hole. Five edge connectors. Was \$150.

**\$130** OUR PRICE

### THIS MONTH'S SPECIALS

SAVE  
 \$\$\$\$\$\$\$\$

#### COLOUR GRAPHICS SYSTEM. CMC-100/GDC-512.

Combine one palette mixing card with up to eight display cards. Resolution 512 x 490, up to 256 colours simultaneously, user programmable intelligence, software available.  
 • Build your own CAD/CAM System. • A special low cost for a high performance graphics system. Price plus software.

NOW ONLY **\$450** (each)

#### ES100P OLYMPIC PRINTER INTERFACE CARD

Turn your typewriter into a computer printer.

SLASHED TO **\$180**

# K-NAR

## COMPUTER CARDS

PO Box 412, Dandenong 3175, Phone (03) 795 5858. Authorised distributor of SME Systems products.

\* Prices subject to change without notice. All prices excluding tax. For retail prices add 20%.

All boards fully assembled and tested and backed by 90-day guarantee.



## TOUCHDOWN

In this program I have used the 'Message Maker' program published in ETI March '83.

It is a lunar lander program. Once you have successfully landed on the surface you then have to take off and battle with gravity and Newton's first law to dock with a section on the top of the screen.

There are three modes to the program — Menu, Create Moon and Play Game.

In the Menu mode you are asked what you wish to do, play the game or create a new lunar surface. The appropriate key must be pressed.

In the Create Moon mode, using keys 0, 1 and 4, you construct a landscape on which you must land. Key 4 creates a flat surface for landing. Key 0 moves the dot up, key 1 moves the dot down. Once finished press any key to return to Menu.

When you start the Play Game mode the surface is redrawn with borders around it. Your trusty ship appears on its side and proceeds towards the left of the screen. When you think the ship is above the landing pad press key 4. The ship will then turn and lower itself to the surface, but due to gravity the ship will crash unless you are careful.

Key 0 is your upward thrust and key 4 will cut all engines. Press key 4 when you think you have landed. If you press it when still above the surface then... Wow what an explosion.

If you succeed in landing, the word 'touchdown' will appear. When it disappears a block will appear at

the top of the screen with a hole which is just a perfect fit for the nose of your rocket. Now you've got to get it in there.

When it takes off you have some new key functions: 2-right retro rocket; 3-left retro rocket; 0-upward thrust; 4-neutral retro rockets.

### TOUCHDOWN

```
600 6A19 6B00 6C00 A800 FC1E 272E 7C01 3C04
610 1606 7B06 6A19 602A 2732 2734 2734 2734
620 6C00 6A00 6B0F A804 FC1E 272E 7C01 3C0F
630 1626 7B0A 6A00 6C00 A813 FC1E 272E 7C01
640 3C10 1638 6BA0 FB00 FB18 7BFO 6A00 EAA1
650 168E 6A04 EAA1 1692 1646 6100 6020 6201
660 E2A1 7001 6200 E2A1 70FF 186C F315 F307
670 3300 166E A774 D101 AE00 F11E P055 7101
680 F100 F118 3140 165E F80A 00E0 1600 00E0
690 165A 00E0 6100 AE00 F11E P065 A774 D101
6A0 7101 3140 1696 6000 611F D011 71FF 3100
6B0 16AA AE3F P065 8200 6000 72FF A774 D011
6C0 7001 303F 16BC D021 72FF 32FF 1606 A824
6D0 6130 6203 1127 4F01 1942 D127 71FF 6404
6E0 E4A1 16E6 16D4 D127 2710 D127 A82B D128
6F0 2710 D128 A833 D128 2710 D128 2854 7202
700 D128 4F01 1942 D128 6404 E4A1 171C 1840
710 650A F515 F507 3500 1714 00EE 6F00 D128
720 4F01 1942 7208 D121 3F01 199C 18B2 F000
730 F065 273C DAB5 7A04 FC18 00EE ----
```

73C - 7FF CHARACTER GENERATOR  
MARCH 1983 ISSUE OF E.T.I.

```
800 160E 171E 1C1D CA1B 1D2C 100A 160E 2C29
```

Peter Easdown, Kew NSW

You must remove the upward thrust if you want to go left or right, but gravity also pulls you down. Key 4 simply stops your sideways movement.

If you ever manage to dock you get the message 'success' and that's it. A bit anticlimatic but a hard game requiring skill.

```
810 262C 040C 1B0E 0A1D 0E2C 1618 1817 2C29
820 262C 0000 0508 36DA 3608 0580 6651 3C18
830 5040 2010 1028 3854 AA38 82FE E8EE C6C6
840 6400 E4A1 184A 6500 16FC 75FF 8254 45FB
850 65FC 16FC 7650 F600 F618 7606 F600 F618
860 660A F615 F607 3600 1864 00EE 6404 E4A1
870 1876 6305 166E 6790 A774 D101 AE00 F11E
880 F055 7101 7701 470C 1890 4140 1688 1876
890 6305 166C 1D18 1E0C 110D 1820 172F 6A03
8A0 6B05 6C00 A894 FC1E 272E 7C01 3C0A 184A
8B0 00EE 289E 6F50 FF15 F307 3F00 18B8 289E
8C0 C72F 7705 6801 A91A D786 A833 D121 72F8
8D0 D128 72FC D128 4F01 1942 D128 6402 E4A1
8E0 76FF 6403 E4A1 7601 6400 E4A1 2908 7201
8F0 46FD 66FE 4603 6602 8164 4202 190C 1912
900 9710 1920 1912 00FF 75FF 45FD 65FE 8254
910 00EE 6404 E4A1 6600 18DA FE8E E8C6 C682
920 D128 6A03 6B0F 6C00 A93A FC1E 272E 7C01
930 3C08 1928 F80A 00E0 1600 1C1E 0C0C 0E1C
940 1C2F 00FF A9BE D128 8320 7308 5410 8510
950 7509 74FF 2974 73FF 74FF 7501 820 1954
960 6600 7301 2974 7301 74FF 7501 7601 360A
970 1964 1934 A996 D433 A999 D533 C70F 7780
980 F700 F718 A996 D433 A999 D533 00EE 8140
990 2400 4610 1C3E 9600 2828 C0D2 72F8 1942
```

## CAR RACE

In this program you steer a car to the left and right to dodge the other cars which come down the screen at you.

To one side is your fuel gauge which shows how much fuel you have left. Once you run out you can go on to your next car.

After three cars your score is shown. To play use keys '4' and '6'.

To load this program use 0480 at 0400 and 08FF at 0402.

### CAR RACE

```
0600 172E 6200 A738 D121 7201 322F 1604 6130
0610 6200 D121 7201 322F 1612 613C 6200 630F
0620 F329 D125 622A 630E F329 D125 6206 A73A
0630 D121 7201 3229 1630 615E 6206 D121 7201
0640 3229 163C 6206 613D D121 6228 D121 6208
0650 D121 7201 3228 1650 2762 6220 633D 6408
0660 6500 C70F 7706 6802 690F 7916 6A05 2774
0670 D78A D9AA A746 D12E 4F01 16E6 D12E 6604
0680 E6A1 71FE 6606 E6A1 7102 A73C D78A D9AA
0690 7803 7A02 C802 4E02 77FF 4E00 7701 4E02
06A0 7901 4E00 79FF 4705 6706 4714 6713 4916
06B0 6917 492B 6929 4A2F 16BE 26CC 166E 7802
```

Peter Easdown, Kew NSW

```
06C0 FB00 F618 1662 A73A D341 00EE 7501 6E01
06D0 6DB0 7D40 FDOO FE18 3505 00EE 6500 2606
06E0 7401 3428 00EE A754 630A C42F 7410 F400
06F0 F318 F315 F607 3600 16FA 73FF D12E 3300
0700 16EA 7C01 4C05 170E 1732 00FF 00FF 00E0
0710 6310 6410 A700 FB33 F265 F029 D345 7304
0720 F129 D345 7304 F229 D345 F10A 1600 6C00
0730 6B00 00E0 6100 1602 1800 8000 5A7E 5A18
0740 3C7E 3C99 FF99 185A 7E5A 183C 7E7E 7E3C
0750 BDFE 9918 AA55 AA55 AA55 AA55 AA55
0760 AA55 A786 6118 6200 D124 7208 3220 1768
0770 611F 00EE 6E18 6D00 A786 DE8E 7D08 3D20
0780 177A A73C 00EE 1010 1010 1010 1010 ----
```

## ASTERIODS

Yes, it's another asteroids game but this one is better. In this game your cannon starts in the centre of the screen with three asteroids moving down the screen.

This time your cannon can spin around by hitting keys '4' and '6'; '5' will fire and '8' will send you forward in the direction you are facing.

Your score is shown after five cannons have been destroyed.

To load this program use 0480 at 0400 and 08FF at 0402.

### ASTERIODS

```
0600 6200 6800 6401 6112 00E0 A822 6018 6B00
0610 6C06 6605 C50F C70F 7718 C90F 7920 D566
0620 D7B6 D9C6 2666 4F01 16DA 6D05 EDA1 16DC
```

```
0630 2666 6D06 EDA1 7401 6D04 EDA1 74FF 6D08
0640 EDA1 268A 4409 6401 4400 6408 F600 F418
0650 A822 D566 D7B6 D9C6 7602 7B01 7C03 4C20
0660 160A A822 161E 4401 A7FF 4402 A7F8 4403
0670 A7FE 4404 A804 4405 A70A 4406 A810 4407
0680 A816 4408 A81C D016 00EE 4401 16AC 4402
0690 16B0 4403 16B6 4404 16BA 4405 16C0 4406
06A0 16C4 4407 16CA 4408 16CE 00EE 71FF 00EE
06B0 71FF 7001 00EE 7001 00EE 7001 7101 00EE
06C0 7101 00EE 7101 70FF 00EE 70FF 00EE 70FF
06D0 71FF 00EE 7801 3805 1608 17D2 6D15 FDOO
06E0 FD18 7DFD 3D00 16DE 8200 8310 4401 170E
06F0 4402 1722 4403 173A 4404 1750 4405 1768
0700 4406 177E 4407 1796 4408 17AA 1630 7202
0710 73FF A802 D231 4F01 17BE D231 3300 1710
0720 1630 7206 73FF A802 D231 4F01 17BE D231
```

Peter Easdown, Kew NSW

```
0730 7201 73FF 3300 1728 1630 7204 7302 A802
0740 D231 4F01 17BE D231 7201 323F 1740 1630
0750 7206 7306 A802 D231 4F01 17BE D231 7201
0760 7301 332F 1756 1630 7202 7304 A802 D231
0770 4F01 17BE D231 7301 332F 176E 1630 72FF
0780 7306 A802 D231 4F01 17BE D231 72FF 7301
0790 332F 178A 1630 7302 72FF A802 D231 4F01
07A0 17BE D231 320C 1798 1630 72FF 73FF A802
07B0 D231 4F01 17BE D231 3300 17AA 1630 7E01
07C0 00FF D231 6D40 FDOO FD18 7DFD 3D15 17C6
07D0 1630 00E0 A8F0 FE33 F265 F029 6310 6410
07E0 D345 7304 F129 D345 7304 F229 D345 F10A
07F0 1600 2070 50P8 0000 14A8 4428 1008 80B0
0800 B0B0 8070 0810 2844 A814 P850 7020 0000
0810 4020 5088 54A0 1070 D070 1000 A054 8850
0820 2040 1876 DFED 6E18 ----
```

## NASTIES

This is a game of speed. The aim of the game is to 'run over' all of the black dots with your flashing dot, as fast as possible.

At the bottom of the screen your score is shown along with the time left. The maximum time is about two minutes and twenty seconds.

To move your dot use these keys: 4 — left; 6 — right; 8 — up; 2 — down.

To load this program use 0600 at 0400 and 07FF at 0402.

### NASTIES

```
0600 26E4 64FF 6E64 A60E C8FF C91F 16FC 80E0
0610 6A10 6B28 2626 80E0 6A10 6B28 2626 7E9F
0620 3E02 1606 1644 A7F0 F033 F265 F029 DAB5
0630 7A04 F129 DAB5 7A04 F229 DAB5 6501 FE00
0640 F518 00EE 6E00 80E0 6A10 6B28 2626 C83F
0650 DCD1 6A00 6B27 A70A DAB6 A710 7A06 DAB6
0660 6A1F 6B27 A716 DAB6 7A06 A71C DAB6 6A30
0670 6B28 8040 2626 A616 DCD1 4F01 26BE 6504
0680 E5A1 7C1F 6506 E5A1 7C01 6508 E5A1 7DFD
0690 6502 E5A1 7D01 4CFF 6C00 4C40 6C3F 4DFD
```

Peter Easdown, Kew NSW

```
06A0 6D00 4D20 6D1F DCD1 6A30 6B28 8040 2626
06B0 7701 4704 16DA 166E 00FF 00FF 00FF 80E0
06C0 6A10 6B28 2626 7E01 80E0 6A10 6B28 2626
06D0 4E64 1706 A616 DCD1 00EE 6700 74FF 3400
06E0 166E 1706 A722 6A00 E0E0 DAB8 7A08 3A40
06F0 16EA 6A00 7B08 3E20 16EA 00EE D891 4F01
0700 160E D891 1608 F10A 172A 7088 4030 8870
0710 7088 8080 8870 P820 2020 2020 P820 2020
0720 20P8 FFFF FFFF FFFF FFFF 00E0 1600 ----
```



# UNBEATABLE KIT VALUE

## Jaycar & Electronic Agencies

### "Blueprint" 5000 preamp



- FUNCTIONS**
- MOVING COIL INPUT
  - MOVING MAGNET (DYNAMIC CART)
  - INPUTS (2 OFF)
  - TUNER INPUT
  - AUX INPUTS (2 OFF)
  - TAPE INPUTS (2 OFF)
  - INPUT LEVEL CONTROL
  - TAPE OUTPUTS (2 OFF)
  - 400Hz CALIBRATION OSCILLATOR
  - LED AVERAGE (VU) & PEAK
  - LEVEL METERS -48dB TD +9dB
- MODE SWITCH, STEREO BALANCE CONTROL**  
**LINE OUT, MONITOR OUT, MONITOR VOLUME CONTROL**
- FEATURES**
- EXTREMELY CLOSE TRACKING TO RIAA PHONO EQ.
  - GOLD PLATED CONNECTORS ON ALL INPUTS
  - ENGLISH 'LORLIN' LOW NOISE SELECTOR SWITCHES
  - BLOW NOISE 1% 50ppm METAL FILM RESISTORS USED
  - TINNED FIBREGLASS PCB'S
  - LOW CAPACITANCE SCREENED CABLE USED THROUGHOUT
  - QUALITY I.C. SOCKETS
  - SPECIAL REAR PANEL
  - MULTICOLOURED RECTANGULAR LED'S USED

**\$299**

### 5000 POWER AMPLIFIER



Cat. KE4200 **BLACK MONOLITH**

unbeatable value  
**ONLY \$319**

### 5000 SERIES GRAPHIC EQUALISERS



**SPECIFICATIONS**  
Signal to Noise: -102dB with respect to 1 Volt  
Frequency Response: 12Hz 105dB to 10dB  
Slope/Cut: 14dB (18dB total)  
Distortion: 100Hz @ 0.7%  
1kHz @ 0.007%  
10kHz @ 0.0008%  
Responsibility: 100% free of cut or boost!  
Current consumption (DC) Approx 100mA @ 110V (Requires 30V AC CT)  
Output short circuit proof.

**\$199 each**

### Lyrebird Piano Kit



- GREAT NEW FEATURES!**
- FREE! A stand like the one illustrated but not exactly the same. Worth around \$50 but yours at no extra charge with each 73 or 88 note kit.
  - FREE! A soldering iron (worth around \$19). Yours to keep to give years of faithful service after you have completed your Lyrebird. (88 note only)
  - FREE! A 200y roll of solder. You will need some to build the Lyrebird but there will be plenty left over for other projects. (73 & 88 note versions).
  - FREE! Quality IC sockets provided in both kits.

REF: EA 11/81-1/82

73 NOTE VERSION \$589  
88 NOTE VERSION \$589



**REMEMBER!! THE LYREBIRD OUTPERFORMS READY BUILT PIANOS COSTING UP TO THOUSANDS OF DOLLARS MORE. WHY PAY MORE WHEN YOUR CONSTRUCTION KNOWLEDGE CAN SAVE YOU A FORTUNE?**



The stand that we provide for the piano kit is not the same as the one shown in the illustration.

**88 NOTE VERSION \$589**  
**73 NOTE VERSION \$475**



**MUSICOLOUR IV**

### Musicolor IV

KE3025 \$89.90

**JAYCAR KITS ARE THE BEST AND COST NO MORE**

## Digital Delay Line

The Digital Delay Line is designed to produce a huge variety of electronic effects. It works very well but the amazing thing is the low price! The effects depend on the time delay selected and some of those included are: Phasing, Flanging, Chorus, ADT (Automatic Double Tracking), Echo, and Vibrato. The delay time can be varied from 0.32ms to 1.6 seconds! Because the signal is stored in digital form there is, unlike analog systems, no degeneration of the signal with time and unlimited repetition is provided by use of the freeze control.

All the controls mount directly upon PCB's to eliminate wiring and to further simplify construction the main board is 'plated through' i.e. there are no wire links or link-through pins. The whole of the memory whether for the basic 400ms machine or the fully expanded 1.6 second model all fits on the main board. The cabinet which is free standing but also suitable for 19" rack mounting, is fully finished to a very high standard. The panel is deep blue whilst the cover is sprayed with a durable black enamel. The kit is available for only \$449 - compare that with inferior units that can cost over \$2,000!

Cat. KJ6621

**ONLY \$449**  
**COMPLETE KIT**

400ms VERSION



**NOW IN STOCK!!**

### BBD EFFECTS BOX

Fantastic low-cost instrument using the versatile MN3001 Bucket Brigade Delay Line to achieve brilliant sonic effects. Now you can emulate the commercial rock groups with Phasing, Flanging, Reverb and Echo. The Jaycar kit includes all components INCLUDING IC sockets and the TU 04 box. (Not cut down but this is easily done). Jaycar has a specially built cabinet for this kit with all holes pre-punched etc., at only \$10 extra but only if you buy the original kit from us. Available as a separate item for \$29.50. WHEN THE KIT IS PURCHASED WITH THE DE-LUXE CASE THE TU 04 CASE WILL NOT BE SUPPLIED.



Special cabinet to suit \$10.00  
Cat. HB6445

**COMPLETE KIT**


Cat. KE1522 \$79.00

PLEASE RING YOUR NEAREST STORE FOR EXTENDED TRADING HOURS OVER THE CHRISTMAS PERIOD

## SAVE A FORTUNE!
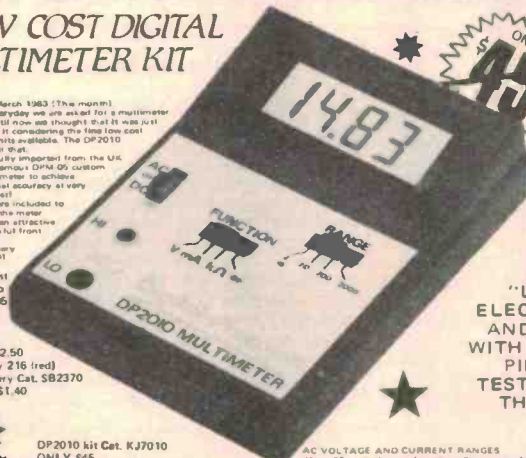
### LOW COST DIGITAL MULTIMETER KIT

From EA March 1983 (7th reprint) All test gear today we are asked for a multimeter kit. Up until now we thought that it was just not worth it considering the fine low cost turn-up units available. The DP2010 changed all that. This kit fully imported from the UK, uses the famous DPM DP custom LCD Voltmeter to achieve phenomenal accuracy at very modest cost. All parts are included to complete the meter including an attractive and colourful front panel. (a 9V battery is required). Set of test probes to suit \$2.95 Probe to suit Cat. WTS312 ONLY \$2.50 Eveready 216 (red) 9V Battery Cat. SB2370 ONLY \$1.40



"LEARN ELECTRONICS AND END UP WITH A USEFUL PIECE OF TEST GEAR IN THE END"

DP2010 kit Cat. KJ7010 ONLY \$45

**SPECIFICATIONS**


Function	Volts (d.c.)	Resolution	Accuracy	Protection
Volts	2V	1mV	1%±1 digit	500V for one minute
	20V	10mV	1%±1 digit	one minute
	200V	100mV	1%±1 digit	one minute
Current	500V	1V	1%±1 digit	1A/250V
	2mA	1uA	1%±1 digit	1A/250V
	20mA	10uA	1%±1 digit	1A/250V
Resistance	200V	100mV	2%±5 digit	260V r.m.s.
	500V	1V	2%±5 digit	260V r.m.s.
	20mA	1uA	2%±5 digit	1A/250V
Volts (a.c.)	200mA	100uA	3%±1 digit	260V
	2000mA	1mA	5%±1 digit	260V
	2V	1mV	2%±5 digit	500V for one minute
Diode Test	20V	10mV	2%±5 digit	one minute
	200V	100mV	2%±5 digit	one minute
	500V	1V	2%±5 digit	one minute
Current (a.c.)	20mA	1uA	2%±5 digit	1A/250V
	200mA	10uA	2%±5 digit	1A/250V
	2000mA	1mA	2%±5 digit	1A/250V
Resistance	2K	1	1%±1 digit	260V
	20K	10	1%±1 digit	r.m.s.
	200K	100	1%±1 digit	r.m.s.
Diode Test	2000K	1K	1%±1 digit	r.m.s.
	20K	10	1%±1 digit	r.m.s.
	200K	100	1%±1 digit	r.m.s.

**AMAZING VALUE**

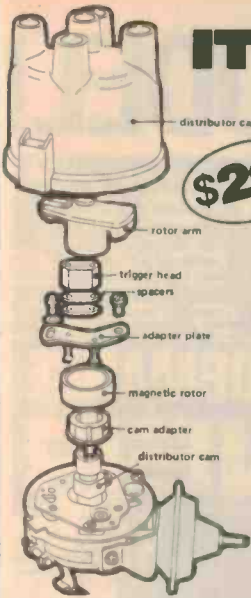**\$39.95**

PLEASE RING YOUR NEAREST STORE FOR EXTENDED TRADING HOURS OVER THE CHRISTMAS PERIOD





# IT HAD TO HAPPEN

**\$29<sup>95</sup>**

**PLEASE NOTE**  
this system must be used in conjunction with an electronic ignition. The Hall Effect device will not switch enough current to replace the contact breaker points on their own!

A professionally engineered electronic ("breakerless") contact breaker system. Yes, only Jaycar has a complete Hall-effect triggerhead assembly designed to adapt to an extensive number of cars. Each kit contains the following:  
 - HALL EFFECT TRIGGER HEAD  
 - MAGNETIC ROTORS FOR BOTH 4 & 6 CYLINDER CARS  
 - OVER 6 CAM-LOBE ADAPTORS  
 - OVER A DOZEN DIFFERENT ADAPTOR PLATES FOR YOUR PARTICULAR DISTRIBUTOR  
 - OTHER HARDWARE (i.e. SCREWS etc.)  
 - YOU CAN REMOVE THIS SYSTEM AND RE-EQUIP YOUR CAR WITH THE ORIGINAL  
 - BREAKER POINTS WHEN YOU SELL THE CAR!  
 - AS EASY TO INSTALL AS A SET OF POINTS!  
 - INSTRUCTIONS (SIMPLE-TO-FOLLOW) INCLUDED!  
 This set is designed to fit most European and Japanese cars. In fact it will also fit many Australian cars fitted with Lucas, Bosch, Motorcraft, AC Delco or Autolite electrics. If you wish to check first, please send SAE for car/distributor list.  
 Because we have no way of knowing, you get the fitting set for ALL of the distributors available. Basically you end up with a jar full of parts that you don't need to use! (Perhaps for your next car?)  
 Quite frankly, we are amazed that we can supply such a comprehensive kit for this price. To produce a kit that will adapt to the dozens of different distributors around is amazing!  
 Remember, once you have installed a breakerless system it will never wear out and that part of your system will remain in tune FOR EVER.  
 We expect this kit to sell well. To ensure that you receive one, check with us early!  
 Cat. KJ6655

With this kit and the interface electronics you can forget about contact breaker point problems!  
 Cat. KJ-6655 \$29.95

New PCB for TAI Kit includes Hall Effect interface. Cat. HP-8786 ONLY \$3.95


# Call Us

Jaycar and Electronic Agencies have the largest range of kits in Australia. We stock kits for most of the projects described by the magazines over the last few years. Space does not permit us to include ALL kits in our ads, all the time. So if you are after a specific kit - call us first. We can probably help you!!


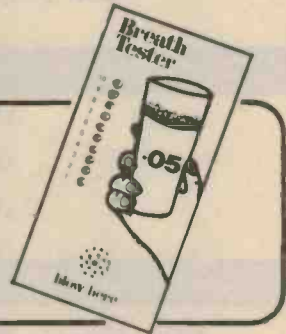
## ETI 492 Sound Bender

Ref: ETI Feb 1982  
 Short form kit of a device to give either your voice, musical instrument or other source that Dalek, metallic sound - as well as other sounds!  
 \$24.50



**QUALITY BLANK COMPUTER CASSETTES**

	1-9	10-19	20 or more
XE3530 C10	1.10	99	90
XE3540 C20	1.20	1.08	99
XE3545 C30	1.40	1.26	1.15

The quality tapes are supplied to us in boxes of 20, so to make it easier we've got a special price for 20.

# Breath Tester

## \$29<sup>95</sup>

In all states and territories in Australia it is an offence to drive a vehicle with an alcohol/blood concentration above a certain limit. In most states it's 0.05 others 0.08. Either way it's only a relatively small number of alcoholic drinks. Because it's only a small number of drinks, many people (quite wrongly) believe that they remain below the statutory limit.  
 The KA1522 Breath Tester can help here. A unit with the same circuit diagram was featured in May "Electronics Australia". It CANNOT give you an actual blood/alcohol content reading, however it can go close. And it can give you a relative reading between inebriated friends!!! Great at parties!!!  
 Grab the whole kit now for only \$29.95. You never know, it may save your licence or your life!

Cat. KA1522

## VIDEO ENHANCER

Ref: EA Oct 1983  
 Get improved performance from your VCR.  
 Cat. KE-7016

**ONLY \$35**



**TRANSISTOR TESTER KIT**  
 Check your transistors in circuit. Saves removing them.  
 Ref: EA sept. 1983.  
 Cat. KA-1532 ONLY \$15

## TV Crosshatch/Dot Hatch Generator

Ref: EA Nov. 1983  
 Great new version of this handy piece of test gear. Now you can generate Crosshatch, Dots and Blank (white) video signals. This is handy for TV/Video alignment.  
 Cat. KA 1530 Basic (short form) kit inc. Jiffy box ONLY \$24.95  
 Cat. LT-3800 Video Modulator to suit \$8.95  
 Power Supply to suit \$9.95

**ONLY \$24<sup>95</sup>**



## ETI15000 METAL DETECTOR

The Performance of a \$500 metal detector for only \$219! This is a fully discriminating VLF T/R instrument (yes! the same principle as those expensive American ones) with ground balance. Control facilities are comprehensive - including an "auto tune" button. This kit includes all parts including a fully built search head and handle assembly and special meter and case.  
 Cat. KE-1460 \$219.00

SEE ETI DEC 1980 and JAN/FEB 1981



**EQUIVALENT TO \$500 units**

**\$219**

## Touch Sensitive Light Dimmer


Ref: EA April 1983  
 Cat. KA1508

Complete kit including quality HPM wall plate with attractive brushed metal insert. The Jaycar kit is absolutely complete including a small dial spring which can be used to connect the PCB to the wall plate. (Beware of other kits that do not include this). In addition to the above, we supply the High Voltage Resistors ALREADY SOLDERED in as a foolproof safety feature!



**only \$19<sup>95</sup>**

## build your own speakers & SAVE!

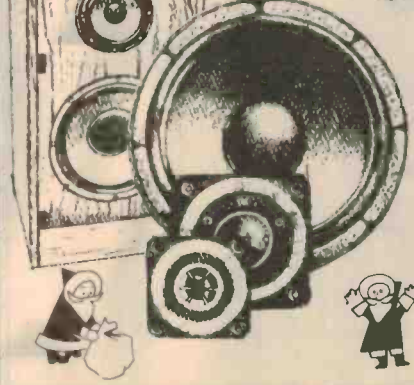

4000/1 4-way System  
 Cat. CE-2430  
 Speakers only \$525 (set of 8 spkrs with x/overs)

**\$525**

4000/2 3-way System  
 Cat. CE-2440  
 Speakers only \$397 (set of 6 spkrs with x/overs)

**\$397**

# Jaycar

Incorporating ELECTRONIC AGENCIES

**SYDNEY** SHOWROOMS  
 117 YORK STREET - PHONE: (02) 264 6688 and (02) 267 1614  
**CARLINGFORD** TELEX: 72293  
 Cnr. CARLINGFORD & PENNANT HILLS ROAD - PHONE: (02) 872 4444  
**CONCORD**  
 115 - 117 PARRAMATTA ROAD - PHONE: (02) 745 3077  
**HURSTVILLE** 121 FOREST ROAD - PHONE: (02) 570 7000

## NUMBER 1 FOR KITS

POST AND PACKING CHARGES  
 \$5 - \$9.99 (\$1.50) \$10 - \$24.99 (\$3.20)  
 \$25 - \$49.99 (\$4.50) \$50 - \$99.99 (\$6.50)  
 \$100 - \$198 (\$8.00) Over \$199 (\$10)

"Free INSURANCE for Road & Registered Post over \$200"  
 All heavy or bulky items (over 20kg.) sent Comet Road Freight \$12.00 anywhere in Australia.  
**SHOP HOURS CARLINGFORD, CONCORD & HURSTVILLE**  
 Mon - Fri 9am - 5.30pm; Sat - 9am - 12pm; Thurs night 8.30pm  
**SHOP HOURS SYDNEY**  
 Mon - Fri 8.30am - 5.30pm; Sat - 8.30am - 12pm; Thurs night 8.30pm  
 MAIL ORDERS AND CORRESPONDENCE: P.O. Box 185, Concord, 2137



Mail Order By **BANKCARD** Via Your Phone

PLEASE RING YOUR NEAREST STORE FOR EXTENDED TRADING HOURS OVER THE CHRISTMAS PERIOD







## UNIVERSAL COUNTER-TIMER FEATURES VERSATILITY

**G**lobal Specialties Corporation has introduced a new universal counter-timer, the Model 5001, which offers a very versatile combination of time and frequency-measuring capabilities plus signal-conditioning facilities.

Operating at up to 10 MHz as a frequency counter, the 5001 also provides the functions of period and multiple-period averaging, time-interval and multiple-time-interval averaging, frequency-ratio measurement, and unit or event counting.

The Model 5001 has two decoupled BNC inputs both of 1M plus 20 pF input impedance and having a sensitivity of 20 mV RMS.

Each has a three-position attenuator (x1, x10 and x100), a positive/negative-going slope selector and a variable trigger-level control. Maximum frequency at the 'A' input is specified as 10 MHz and at the 'B' input as 2 MHz.

An 8-digit, 7-segment filtered LED display with 11 mm high digits is used to ensure easy readability in all ambient light conditions.

For ease in noting or recording displayed readings a variable-delay control is provided to add between 75 ms and 7.5 sec to the usual display time of one gate period (which can be 0.01, 0.1, 1 or 10 sec); subsequent measurements are also postponed by this variable delay, and a 'hold' position is provided if it is required to maintain the displayed reading indefinitely.

Power consumption is 10 W and the unit operates from 105-130 V<sub>ac</sub> or 210-250 V<sub>ac</sub> supplies with full performance over the supply frequency range 47-63 Hz. The Model 5001 measures 76 mm high x 254 mm wide x 178 mm deep.

Further information can be obtained from the Australian distributors, Vicom International Pty Ltd, Head Office, 57 City Road, South Melbourne Vic. 3205. (02)62-6931. ▼



## CAVITY GENERATORS NOW COVER TO 18 GHz

**T**he HP8683D (2.3 to 13.0 GHz) and HP 8684D (5.4 to 18 GHz) cavity-tuned signal generators now include an internal doubler band to extend frequency range and provide doubled FM deviation.

With their dc-to-10 MHz modulation rates and +/- 10 MHz deviation, the generators now can be considered for satellite-video modulations.

Both generators also feature high-performance pulse modulation in the main and doubled bands for use in radar and EW applications (less than 10 ns rise/fall times and greater than 80 dB on/off ratio.)

The internal pulse generator has pulse rates of 10 Hz to 1 MHz, pulse widths of 100 nanoseconds to 100 milliseconds and pulse delays of 50 nanoseconds and 100 milliseconds. Amplitude modulation is available at depths to 70% and rates to 10 kHz.

One of the main advantages of cavity-tuned generators remains their excellent non-harmonic spurious characteristics at less than -80 dBc. Single-sideband phase noise is less than -72 dBc/Hz at 10 kHz offset in S-band. Cavity technology also allows a broadband noise floor from -135 to -150 dBc. ▶



## LOW-COST A-D-A CONVERTER

**R**oland Corporation has released the ADA-200, a low-cost general purpose analogue-to-digital converter that reconfigures under software to digital-to-analogue.

The unit is highly portable and may be configured to act as a controller for equipment having a voltage control facility, including audio equipment, machine tools and laboratory equipment, and electronic musical instruments.


It may also be configured as a joystick/paddle interface, and software is available for its use as a data logger in scientific applications, as a wave form generator, to produce digital oscilloscope displays, and as a waveform analyser in voice

recognition and synthesis.

The Roland ADA-200 is compatible with a wide range of CPU chips and buss structures. Connection to the host processor is made via 50-ribbon cable, and interfaced processor chips include 8080, Z80, 6800, 6502 and 6809.

The A-D and D-A modes are selected by software switch, and the convertor produces an 8-bit parallel binary stream at a maximum sampling rate of 44 kHz. The unit is fitted with input and output filters to prevent aliasing and for smoothing the staircase wave output.

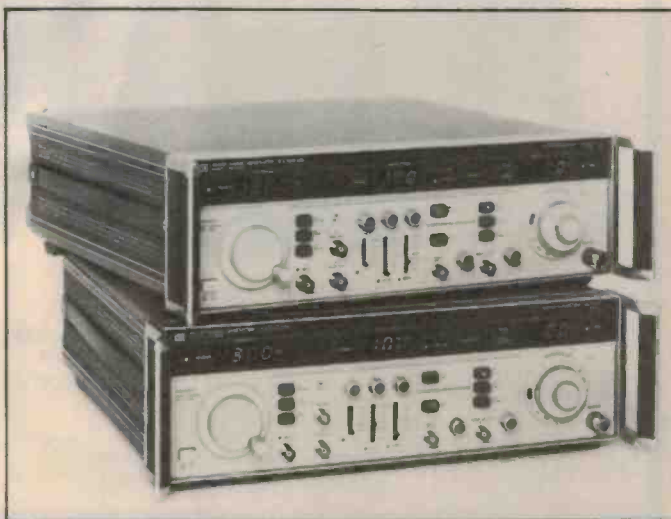The Roland ADA-200 Converter is available from Roland, 23 Cross Street, Brookvale 2100. (02)938-3911.






► Output power in the doubled bands is calibrated from -3 to +130 dBm. Pulsed power is peak-leveled and can be corrected for connecting cable loss vs frequency.

According to HP's Instrument Group Marketing Manager, John Schmidt, the HP 8680-series generators are proving very popular with defence and communications users because of their unique combination of performance, reliability, ruggedness and serviceability.

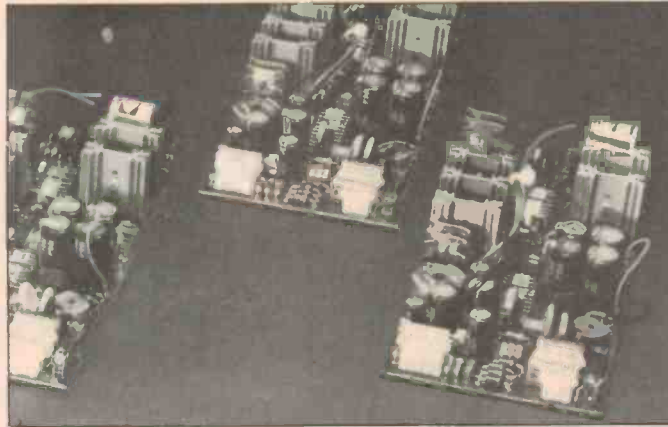Contact Hewlett-Packard, 31-41 Joseph St, Blackburn Vic. 3130. (03)890-6351.



## CURRENT AND POWER GUNS

Elmesco Instruments is now handling F. W. Bell's range of six hand-held current and power/power factor gun products.

Two models, CG100A and CG103A measure current to 200 A and 500 A and ac and dc with a frequency response to 1 kHz on conductors up to 19 mm diameter. They are fitted with output jacks to connect to a multimeter, 'scope or chart recorder.

Next in the range is the model PG200D digital power meter which will measure real power to 199.9 kW, dc or ac (to 400 Hz).

The latest addition is the model PFG360D. This unit measures power factor in all quadrants plus phase angle from 0-360° over the frequency range of 45 to 65 Hz.

For more information please contact Paul Twigg at Elmesco on (02)736-2888.

## OPEN-FRAME POWER SUPPLY FAMILY ▲

The SM80 series of power supplies from Australian manufacturer, Scientific Electronics, offers all of the features needed by the micro designer — low cost and small size coupled with high performance and reliability.

These open frame power supplies — the SM80AE1, 2 and 3 have all been designed and manufactured by Scientific Elec-

tronics in Australia to meet Telecom specification 1302.

All are rated at 80 watts, the model 1 being five rail, model 2, four rail and model 3, six rail. All three units offer standard output rails as well as output rails to customer specifications.

All outputs are short circuit protected and total allowable power is 80 watts continuous, at greater than 3.5 kV and effi-

ciency greater than 60% at full load.

All models measure 108 x 240 x 45 mm and are fully supported by a five year warranty and complete local technical back-up from Scientific Electronics.

For further information, contact Scientific Electronics, 6 Holloway Drive, Bayswater Vic. (03)762-5777.

### MODEL 175 AUTORANGING BENCH/PORTABLE DMM

## KEITHLEY INSTRUMENTS



For more information on the Model 175 Autoranging DMM, or on a variety of other industrial electronic testing and measurement equipment, contact:



SCIENTIFIC DEVICES AUSTRALIA PTY. LTD.  
 VIC. 2 JACKS RD., SOUTH OAKLEIGH, 3167  
 PHONE (03) 579 3622 TELEX AA 32742  
 N.S.W. OFFICE 2, 35-37 HUME ST., CROWS NEST, 2065  
 PHONE (02) 43 5015 TELEX AA 22978  
 S.A. 31 HALSEY RD., ELIZABETH EAST, 5112  
 PHONE (08) 255 6575 TELEX AA 88125

The new Model 175 Autoranging Bench Digital Multimeter, from Keithley Instruments, Inc., combines the measurement capabilities of much higher-priced system DMMs with several new features to extend its utility, yet retain simplicity of use. Ideal for use as a bench meter in production or lab work, this 4-1/2 digit autoranging DMM also has a field-installable battery option, making it fully portable. Fast autoranging (up to 200ms per range change on DCV) enables the user to concentrate on getting the reading without worrying about choosing the appropriate range.

The Model 175 features digital calibration for reduced cost of ownership, as many users can now calibrate the meter in-house. With the Model 1753 IEEE-488 (GPIB) option, the 175 is the lowest-priced IEEE-interfaceable DMM available. Model 175's 100-point data logger monitors drifts, determines rates of change, and collects response curve data without a printer, output cables, or complicated hook-ups. The data logger has six different store rates from one reading/400ms to one reading/hour, and data recall is "push-button" easy.

Other features of the Model 175 include:

- 4-1/2 digit LCD display with annunciators for function, range, and feature indication
- 10µV/10mΩ/10nA sensitivity
- 0.03% basic DCV accuracy
- True RMS AC
- 10A capability
- 100kHz bandwidth in AC
- dBm/relative function
- Relative reference
- Max/Min reading hold
- Safety input jacks
- Front panel accessible amps fuse



# ETI Book Sales

## electronics textbooks

**ELECTRONICS: IT'S EASY — VOL 1**  
**A0001E** \$5.95  
 Meters, resistance, capacitance and inductance, emitter followers, op-amps, power supplies, electronic filters.

**ELECTRONICS: IT'S EASY — VOL 2**  
**A0002E** \$5.95  
 Digital sub-systems, counters and shift registers, A-D and D-A conversion, digital instruments and test equipment, computers, transmission links, oscilloscopes.

**ESSENTIAL THEORY FOR THE ELECTRONICS HOBBYIST**  
**A0013B** \$5.95  
 Supplies the electronics hobbyist with the background knowledge which will exactly suit his specific requirements. Minimum maths.

**INTRODUCTION TO AUTOMOTIVE SOLID-STATE ELECTRONICS**  
**A0015P** \$14.95  
 For the professional as well as the home mechanic — explains the functions of most on-board automotive black boxes and logic systems, including anti-skid braking, electronic spark control and diagnostic systems.

**ELECTRONICS: IT'S EASY — VOL 1**  
**A0016E** \$12.95  
 Meters, resistance, capacitance and inductance, emitter followers, op-amps, power supplies and electronic filters. Hardcover.

**ELECTRONICS: IT'S EASY — VOL 2**  
**A0017E** \$12.95  
 Digital sub-systems, counters and shift registers, A-D and D-A conversion, digital instruments and test equipment, computers, transmission links and oscilloscopes. Hardcover.

## reference and data handbooks

**INTERNATIONAL TRANSISTOR EQUIVALENTS GUIDE**  
**B0018B** \$9.95  
 Contains a huge amount of information on modern transistors produced by more than 100 manufacturers. Wherever possible, equivalents are subdivided into European, American and Japanese types.

**WALL CHART — HOW TO IDENTIFY UNMARKED ICs**  
**B0019B** \$2.95  
 This chart shows the reader how, with just a test-meter, to go about recording the particular 'signature' of an unmarked IC which should enable the IC to be identified with reference to manufacturers or other data.

**WALL CHART — RADIO, ELECTRONICS, SEMI-CONDUCTORS AND LOGIC SYMBOLS**  
**B0020B** \$2.95  
 Identify those symbols at a glance. A must for beginners and advanced enthusiasts alike. Professionals can always hide it in their desks!

**WALL CHART — RADIO AND ELECTRONIC COLOUR CODES AND DATA**  
**B0021B** \$2.95  
 This chart covers all colour codes in use throughout the world. For all radio and electronic components made in Britain, United States, Europe and Japan.

**CONTEMPORARY MATHEMATICS FOR ELECTRONICS**  
**B0024P** \$35.95  
 This book is split into three sections. Direct current maths introduces the student to the calculator, fractions and dimensional analysis. Alternating current maths covers phasors, quadratics and RMS in both sine and digital waveforms. Active device maths introduces number systems and boolean.

**PRACTICAL ELECTRONIC CALCULATIONS AND FORMULAE**  
**B0027B** \$9.95  
 For the practical person's workbench. Bridges the gap between technical theory and cut-and-dried methods which work but leave the experimenter unfulfilled. There's a strong practical bias. High maths avoided where possible.

**INTERNATIONAL DIODE EQUIVALENTS GUIDE**  
**B0339B** \$6.95  
 Includes zener diodes, LEDs, diacs, triacs, thyristors, OCIs, photo diodes, display diodes and simple rectifier diodes.



**FIRST BOOK OF PRACTICAL ELECTRONIC PROJECTS**  
 Normally \$4.95; this month only, \$3.70

Full constructional data, circuits, components lists for many practical projects including audio distortion meter, guitar amp, metronome, etc. To order, quote book number CX0358.  
 Limited supplies

**RESISTOR SELECTION HANDBOOK**  
**B0348B** \$2.95  
 Shows how to combine two preferred values of resistor to obtain virtually any required value of resistance. Includes information about fixed resistors, standard ranges, colour codes and markings, power ratings and resistor calculations.

**REACTANCE/FREQUENCY CHART FOR AUDIO AND RF**  
**B0381B** \$2.95  
 Enables the reactance of any capacitor or resistor to be read off immediately, from 10 Hz to 100 MHz. Also applies to resonant frequencies of LC networks. Limited supplies.

## electronics for beginners

**HI-FI LOUDSPEAKER ENCLOSURES**  
**C0028B** \$4.95  
 Data for building corner reflex, bass reflex, exponential horn, folded horn, tuned port, Klipschorn labyrinth, tuned column, loaded port and multi speaker panoramics. Clear dimensioned diagrams included.

**BEGINNER'S GUIDE TO DIGITAL ELECTRONICS**  
**C0029B** \$4.95  
 Covers all essential areas including number systems, codes, constructional and sequential logic, analogue/digital/analogue conversion.

**BEGINNER'S GUIDE TO BUILDING ELECTRONIC PROJECTS**  
**C0030B** \$6.95  
 Enables total beginners to tackle electronic projects. Includes component identification, tools, soldering, building methods, cases, legends, etc. Practical basic projects are included.

**HOBBY ELECTRONICS PROJECT BOOK**  
**C0031E** \$4.95  
 Fifty projects, ranging from very simple ones for complete beginners to more elaborate ones for those with more experience.

**HOW TO BUILD ELECTRONIC GAMES**  
**C0032E** \$3.95  
 Alien invaders, electronic die, sound effects, two-slot car controllers, electronic poker machine and lots more.

**HOW TO BUILD GOLD AND TREASURE DETECTORS**  
**C0033E** \$3.95  
 Tells you how metal detectors work and how to construct the different types of detectors: discriminating, BFO, induction balance and a professional deep-seeking unit.

**ETI PROJECT ELECTRONICS**  
**C0269E** \$4.95  
 Twenty-six projects for beginners, including battery saver, electronic siren, Morse practice set, FM antenna, etc. etc. Fifth edition.

**HOW TO BUILD YOUR OWN METAL AND TREASURE LOCATORS**  
**C0036B** \$6.95  
 Electronic and practical details on the simple and inexpensive construction of heterodyne metal locators.

**ELECTRONIC PROJECTS FOR BEGINNERS**  
**C0038B** \$6.95  
 This book gives the newcomer to electronics a wide range of easily built projects. Actual components and wiring layouts aid the beginner. Some of the projects may be built without using soldering techniques.

**POPULAR ELECTRONIC PROJECTS — BOOK 1**  
**C0039B** \$6.95  
 A collection of the most popular types of circuits and projects to interest most electronics constructors. The projects cover a wide range and are divided into four basic types: radio, audio, household and test equipment. ▶

Save time and trouble with mail order — simply fill out the reply-paid coupon!

140 Joynton Avenue, Waterloo, NSW 2017, Australia. Phone (02) 663-9999 Sydney. Telex 74488.  
 Postal Address: ETI Book Sales, PO Box 227, Waterloo, NSW 2017.



**EASY ELECTRONICS: CRYSTAL SET CONSTRUCTION**  
C0041B \$6.75

For those who wish to participate in the intricacies of electronics more through practical construction than by theoretical study. The circuits are based on those from earlier publications but have been modified to use modern components and home-wound coils.

**IC PROJECTS FOR BEGINNERS**  
C0042B \$6.75

Especially written for the less experienced hobbyist, and offers a range of fairly simple projects based around a number of popular and inexpensive linear and digital ICs. Complete layout and point-to-point wiring diagrams.

**SOLID-STATE NOVELTY PROJECTS**  
C0043B \$4.95

A number of novelty projects using modern ICs and transistors. Includes a musical instrument played by reflecting a light beam with your hand, water warbler for pot plants, music tone generator, LEDs and ladders game, touch switch, electronic roulette wheel, etc.

**SOLID-STATE SHORTWAVE RECEIVERS FOR BEGINNERS**  
C0044B \$5.95

Design and construction of several solid-state shortwave receivers giving high level of performance yet utilising few components.

**constructional projects**

**ELECTRONIC PROJECTS FOR YOUNG SCIENTISTS**

D0045E \$3.95  
PH meter, geiger counter, helium-neon laser, sound-level meter, solar cells, negative ion generator and more.

**REMOTE-CONTROL PROJECTS**

D0046B \$6.95  
Covers radio, infra-red, visible light, ultrasonic controls. Full explanations are provided so that the reader can adapt the projects for domestic and industrial use.

**POWER-SUPPLY PROJECTS**

D0047B \$5.95  
Gives a number of power-supply designs, including simple unregulated types, fixed-voltage regulated types and variable voltage stabilised designs. The designs are all low-voltage types for semiconductor-circuits.

**ELECTRONIC HOUSEHOLD PROJECTS**

D0048B \$5.95  
Most useful and popular projects for use around the home. Includes two-tone buzzer, intercom, smoke and gas detectors, baby alarm, freezer alarm, etc. etc.

**ELECTRONIC PROJECTS USING SOLAR CELLS**

D0049B \$6.75  
Includes a number of projects that benefit from solar power and obviate the problems encountered with batteries, such as weight and bulk, frequency of replacement, and failure when batteries are exhausted.

**DIGITAL IC PROJECTS**

D0050B \$6.75  
The projects included in this book range from simple to more advanced projects — some board layouts and wiring diagrams included.

**BUILD YOUR OWN HI-FI AND AUDIO ACCESSORIES**

D0052B \$4.95  
Essential for keen hi-fi and audio enthusiasts. Projects include stereo decloder, three-channel mixer, FET preamp for ceramic pick-ups, mic preamp with adj. bass, stereo dynamic noise limiter, loudspeaker protector, etc.

**ELECTRONIC SECURITY DEVICES**

D0059B \$6.95  
Besides including both simple and more sophisticated burglar alarm circuits using light, infra-red and ultra-sonics, this book also gives circuits for gas and smoke detectors, flood alarms, fire alarms, doorphones, etc. Limited supplies.

**POPULAR ELECTRONIC CIRCUITS — BOOK 1**  
D0060B \$6.75

Includes audio, radio, test gear, music projects, household projects and many more. An extremely useful book for all hobbyists, offering remarkable value.

**POPULAR ELECTRONICS CIRCUITS — BOOK 2**  
D0061B \$7.75

A wide range of designs for electronics enthusiasts who are capable of producing working projects from just a circuit diagram without the aid of detailed information.

**MINI-MATRIX BOARD PROJECTS**  
D0062B \$6.75

This book provides a selection of 20 useful circuits which can all be built on a mini-matrix board which is just 24 holes by 10 copper strips in size. Simple and easy for those with not much experience in electronics.

**MULTI-CIRCUIT BOARD PROJECTS**  
D0063B \$6.75

All circuits are based on one specially designed pc board. Recommended to the less experienced hobbyist.

**AERIAL PROJECTS**  
D0064B \$6.75

Practical aerial designs including active, loop and ferrite which are relatively simple and inexpensive to build. The complex theory and mathematics are avoided.

**MODERN OP-AMP CIRCUITS**  
D0065B \$6.75

A collection of widely varying circuits and projects based on the op-amp ICs.

**ELECTRONIC TIMER PROJECTS**  
D0066B \$6.75

These may have a high degree of accuracy with quartz control or they may be quite simple designs, using only a few components. A number of specialist timer projects are car windscreen-wiper delay unit, darkroom timer, metronome, etc.

**ELECTRONIC PROJECTS FOR CARS AND BOATS**  
D0067B \$6.75

Fifteen fairly simple projects designed for use with 12 V electrical systems but in some cases can also be employed with 6 V and/or positive earth systems.

**ELECTRONIC PROJECTS FOR CARS**  
D0261E \$4.95

Projects include car alarm, reversing alarm, over-rev alarm, twin-range tachometer, breakdown beacon, intelligent battery charger, etc.

**THIS MONTH'S SPECIAL**

**LEARNING TO WORK WITH INTEGRATED CIRCUITS**  
Normally \$2.35; this month only, **\$1.75**

Discover the basics of integrated circuits while building a simple and useful electronics project. A complete collection of the popular American QST series.  
To order, quote book number EX318R.  
Limited supplies

**ETI TOP PROJECTS — VOL 5**  
D0263E \$3.00

Includes photographic strobe, bucket brigade audio delay line, white line follower, house alarm, etc. etc.

**ETI TOP PROJECTS — VOL 6**  
D0264E \$4.95

Revised second edition. Projects include theatrical lighting controller, simple intercom, electromyogram for biofeedback use, Series 4000 four-way loudspeaker, etc. etc.

**ETI TOP PROJECTS — VOL 7**  
D0265E \$3.95

Includes geiger counter, AM tuner, laser, simple metal detector, discriminating metal detector, dc power supply, etc. etc.

**ETI TOP PROJECTS — VOL 8**  
D0266E \$4.95

Includes UHF to VHF television converter, universal process timer, sound bender, percussion synthesiser, etc. etc.

**ETI TOP PROJECTS — VOL 9**  
D0267E \$4.95

Includes a radioteletype-computer decoder, model railway points controller, universal dc-dc converter, MicroBee EPROM programmer, etc.

**SECURITY SYSTEMS**  
D0294P \$14.95

Step-by-step instructions show you how to carry out a security survey of your home and then plan, install and maintain an alarm system.

**ELECTRONIC SCIENCE PROJECTS**  
D0413B \$5.95

Twelve electronic projects with a scientific flavour — each project includes details on how it works, construction and use. Includes a simple infra-red laser, a low-cost solid-state oscilloscope, a pH meter, and electronic stethoscope and an electronic seismograph.

**circuit techniques and design**

**50 PROJECTS USING RELAYS, SCRs AND TRIACS**  
E0068B \$6.95

Practical working circuits using silicon controlled rectifiers, relays and bi-directional triodes. With a minimum of difficulty you can use them in motor control, dimming and heating control, timing and light sensitive circuits, warning devices and many others.

**ETI CIRCUITS — BOOK 1**  
E0070E \$2.95

Many of these circuits have been published in the 'Ideas for Experimenters' Section of ETI.

**ETI CIRCUITS — BOOK 2**  
E0071E \$2.95

See Book 1.

**ETI CIRCUITS — BOOK 3**  
E0072E \$2.95

See Book 1.

**ETI CIRCUITS — BOOK 4**  
E0073E \$2.95

See Book 1.

**DESIGN OF PHASE-LOCKED LOOP CIRCUITS, WITH EXPERIMENTS**  
E0074P \$16.95

An excellent introduction to the theory, design and implementation of phase-locked loop circuits using various TTL and CMOS devices. Includes manufacturers' data sheets and describes the use of breadboarding aids in laboratory-type experiments.

**RF CIRCUIT DESIGN**  
E0079P \$36.95

A practical approach to the design of RF amplifiers, impedance-matching networks and filters. Uses a minimum of complex maths.

**50 CMOS IC PROJECTS**  
E0080B \$5.95

Projects include multivibrators, amplifiers and oscillators, trigger devices and other special devices.

**SECOND BOOK OF CMOS IC PROJECTS**  
E0081B \$5.95

Leading on from 50 CMOS IC Projects, this second book provides a further selection of useful circuits of a simple nature. Contents have been selected to ensure minimum overlap between the two books.

**COUNTER DRIVER AND NUMERAL DISPLAY PROJECTS**  
E0082B \$5.95

Author F.G. Rayer features applications and projects using various types of numeral displays, popular counter and driver ICs, etc.

**ELECTRIC CIRCUITS AND NETWORKS**  
E0091P \$18.75

Comprehensive explanation of the theory, with numerous examples and solved illustrative problems.



## HOW TO USE OP-AMPS

**E0092B** \$7.75  
Design notes and applications on many topics including basic theory, amplifiers, power supplies, audio circuits, oscillators, filters, computers and control engineering. It's written around the 741 IC but includes design notes for most of the common op-amps.

**50 PROJECTS USING CA3130 ICs**  
**E0101B** \$4.50

The CA3130 is an advanced operational amplifier capable of higher performance than many others: circuits often need ancillary components. Audio projects, RF projects, test equipment, household projects.

**PRACTICAL INTRO TO DIGITAL ICs**  
**E0102B** \$5.95

Introduction to digital ICs (mainly TTL 7400). Besides simple projects, includes logic test set to identify and test digital ICs. Also includes digital counter-timer.

**50 CIRCUITS USING GERMANIUM, SILICON AND ZENER DIODES**  
**E0103B** \$5.95

Fifty interesting and useful circuits and applications using the germanium and silicon signal diodes, silicon rectifier diodes and zener diodes, etc.

**DESIGN OF VMOS CIRCUITS, WITH EXPERIMENTS**  
**E0104P** \$17.75

The authors look at the technology which makes dramatic advancements possible with VMOS, and show how these components can easily be integrated into common circuit designs to enhance their responses.

**UNDERSTANDING CMOS INTEGRATED CIRCUITS**  
**E0105P** \$9.95

This book tells you what CMOS ICs are, how they work, and how they can be used in electronic circuit designs. Practical circuits, with parts values, are included.

**GUIDE TO CMOS BASICS, CIRCUITS, AND EXPERIMENTS**  
**E0107P** \$14.95

If you are already familiar with TTL devices and are ready to examine the benefits of CMOS, this book is your complete source. It tells you what CMOS devices are, their characteristics and design rules. Experiments demonstrate the concepts discussed.

**50 SIMPLE LED CIRCUITS — BOOK 1**  
**E0108B** \$4.50

Fifty interesting circuits and applications using the LED. Includes circuits for the 707 common anode display for the beginner and advanced enthusiast.

**IC 555 PROJECTS**  
**E0109B** \$6.75

One wonders how life went on before the 555! Included are basic and general circuits, car and railway circuits, alarms and noise makers plus section on subsequent 556, 558 and 559s.

**LM 3900 IC PROJECTS**  
**E0110B** \$4.75

Unlike conventional op-amps, the LM 3900 can be used for all the usual applications as well as many new ones. It's one of the most versatile, freely obtainable and inexpensive devices around. This book provides the groundwork for simple and advanced uses — it's much more than a collection of projects. Recommended.

**50 CIRCUITS USING 7400 SERIES ICs**  
**E0111B** \$5.95

Fifty interesting and useful circuits and applications using these versatile devices.

**VMOS PROJECTS**  
**E0112B** \$6.75

Though primarily concerned with VMOS power FETs and their applications, power MOSFETs are dealt with, too, in a chapter on audio circuits. Projects include audio circuits, sound generator circuits and signal circuits.

**IC CONVERTER COOKBOOK**  
**E0139P** \$22.75

Written for the practising engineer, technician, hobbyist or student, this book will be an invaluable working guide to the understanding and use of IC analogue/digital and digital/analyse converters.

**HOW TO DESIGN AND MAKE YOUR OWN PCBs**  
**E0284B** \$6.95

Covers the practical aspects of printed-circuit board design and construction.

**50 SIMPLE LED CIRCUITS — BOOK 2**  
**E0346B** \$4.95

Fifty useful circuits and applications using the LED to complement Book 1 (ETI Book Sales No. E0108B). Includes diode tester, unijunction LED flasher, car voltage probe, SCR tester, fuse tester and simple timer.

## test equipment and fault-finding

**HOW TO GET YOUR ELECTRONIC PROJECTS WORKING**  
**F0114B** \$6.95

Helps you to overcome the problems of a circuit that doesn't work by indicating how and where to start looking for many of the common faults that can occur when building up a project.

**WALL CHART — TRANSISTOR RADIO FAULT-FINDING**  
**F0115B** \$2.95

Used properly, this chart should enable the reader to trace most common faults quickly. Across the top of the chart are four rectangles containing brief descriptions of the faults. Selecting the appropriate fault, the reader simply follows the arrows and carries out the suggested checks until the fault is cleared.

**PRACTICAL REPAIR AND RENOVATION OF COLOUR TELEVISIONS**  
**F0116B** \$6.55

This book shows how to obtain a working colour television for very little outlay by repairing and renovating a set that has been 'written off' by a dealer. Includes practical details of how to construct your own CRT tester/rejuvenator and cross-hatch generator.



**THE 6809 COMPANION**  
Normally \$6.95; this month only,  
**\$5.15**  
A discussion of the features of the 6809 and a reference guide. Don't be deceived — it's more than just a beginner's guide to microprocessors. To order, quote book number JX154B.  
Limited supplies

**TEST GEAR — METERING AND POWER-SUPPLY PROJECTS**  
**F0118E** \$3.00

Includes many types of meters, audio noise and signal generators, CMOS tester, oscilloscope calibrator, etc.

**TEST GEAR — VOL 2**  
**F0119E** \$3.95

Projects include audio oscillator, transistor tester, true RMS voltmeter, RF signal generator, versatile logic test probe, microwave oven leak detector, etc.

**TROUBLESHOOTING WITH THE OSCILLOSCOPE**  
**F0121P** \$16.95

Excellent for the professional service technician or the serious hobbyist, as it combines step-by-step procedures for using the scope with the specific nuts and bolts of television receiver troubleshooting.

**ELECTRONIC TEST EQUIPMENT CONSTRUCTION**  
**F0122B** \$5.95

Describes construction wide range of test gear, including FET amplified voltmeter, resistance bridge, field strength indicator, heterodyne frequency meter, etc.

**TEST GEAR — VOL 3**  
**F0255E** \$4.95

Projects include RF attenuator, op-amp tester, tachometer, transistor tester, mains cable seeker, electric fence tester, portable core-balance relay, etc.

**ELECTRONIC TROUBLESHOOTING HANDBOOK**  
**F0257P** \$10.50

This workbench guide shows you how to pinpoint transistor troubles in minutes, how to test almost everything electronic and how to get the most out of low-cost test equipment.

**USE OF THE DUAL-TRACE OSCILLOSCOPE**  
**F0259P** \$23.75

This programmed text breaks down the process of operating a scope into a series of logical steps, starting with the deflection of the electron beam and continuing through proper use of the triggering controls to measure the phase difference between two waveforms.

**HOW TO BUILD YOUR OWN SOLID-STATE OSCILLOSCOPE**  
**F0282B** \$6.95

This book comprises a project divided into sections for builder to individually construct and test — then assemble into complete instrument. Includes short section on scope usage.

## electronic music and audio/video

**MOBILE DISCOTHEQUE HANDBOOK**  
**G0093B** \$4.95

Most people who start mobile discos know little about equipment or what to buy. This book assumes no preliminary knowledge and gives enough info to enable you to have a reasonable understanding of disco gear.

**AUDIO CYCLOPEDIA**  
**G0125P** \$71.95

A complete in-depth look at the art of audio — from the basic principles of sound to solid-state and integrated circuits. More than 3000 entries and hundreds of illustrations and circuit diagrams cover acoustics, amplifiers, recording, reproduction, test equipment, audio measurements, and much more.

**ELECTRONIC MUSIC CIRCUITS**  
**G0126P** \$26.95

How to build a custom electronic music synthesiser, outlines numerous other circuit designs and then shows you how to modify them to achieve particular responses. Many of the circuits can be used as special-effects boxes for guitars and other musical instruments.

**INTRODUCTION TO ELECTRO-ACOUSTIC MUSIC**  
**G0127P** \$15.95

This book assumes no previous technical knowledge. It discusses the relationship between the technology and the composition of electro-acoustic music.

**MODERN RECORDING TECHNIQUES**  
**G0128P** \$21.95

Explains the equipment controls and techniques found in a modern recording studio and how to use them creatively and correctly to produce a desired result. Numerous photographs, diagrams and charts.

**SOUND-SYSTEM ENGINEERING**  
**G0129P** \$35.50

Dealing with audio systems as a whole, it includes installing and equalising the sound system and interfacing the electrical and acoustic systems. Instrumentation, the acoustic environment and designing for acoustic gain.

**TUBE SUBSTITUTION HANDBOOK**  
**G0130P** \$8.75

Complete, accurate, up-to-date guide to direct substitutes for receiving and picture tubes. Contains more than 6000 receiving tube substitutes, 4000 monochrome and colour picture tube substitutes, and 600 communications substitutes. Also includes pinouts for quick operational checks.



## HOW TO BUILD SPEAKER ENCLOSURES

**G0131P** \$8.75  
A guide to the 'whys' and 'hows' of constructing top-performance loudspeaker enclosures.

## VIDEO TAPE RECORDERS

**G0132P** \$21.25  
In this completely revised second edition, the author tells in simple language how helical VTRs work and how to operate and service them. Includes numerous examples of circuits and mechanical systems.

## computers for beginners

### COBOL FOR BEGINNERS

**H0140P** \$30.95  
It is a solid text for introductory programming courses in Cobol, using a format that is easy to understand, yet comprehensive enough to make supplementary readings unnecessary.

### THE PET PERSONAL COMPUTER FOR BEGINNERS

**H0141P** \$20.95  
This handy guide is written for use with all varieties of PET computer, from the original 2001 to the 8032 Super PET. It is suited to novices with no practical experience and provides advice and practical examples.

### BIG THINGS FROM LITTLE COMPUTERS

**H0142P** \$19.25  
A layperson's guide to personal computing with all the basic information and lots of examples of how personal computers can be used.

### BEGINNER'S GUIDE TO MICROPROCESSORS AND COMPUTING

**H0143B** \$6.95  
Introduction to basic theory and concepts of binary arithmetic, microprocessor operation and machine language programming. Only prior knowledge assumed is very basic arithmetic and an understanding of indices.

### A MICROPROCESSOR PRIMER

**H0144B** \$5.95  
Learning about microprocessors is easy with this book, written in a style that is easy to follow. The shortcomings of this basic machine are discussed and the reader is shown how these are overcome by changes to the instruction set. Relative addressing, index registers follow as logical progressions.

### AN INTRODUCTION TO BASIC PROGRAMMING TECHNIQUES

**H0145B** \$6.75  
Ideal for beginners seeking to understand and program in BASIC. Includes program library for biorhythms, graphing Y against X, standard deviations, regressions, generating musical note sequences, and a card game.

### BEGINNING BASIC

**H0146A** \$24.95  
Intended for beginners with no computing experience, one should be able to intelligently program in BASIC in a short time.

### BEGINNING FORTRAN

**H0147A** \$25.50  
Starts with simple elementary examples and proceeds to intermediate level programs. Also includes references, tutorials, flow charts, deck set-ups and matrix algebra.

### UNDERSTANDING COMPUTERS

**H0148A** \$20.95  
For people who use small computers, this book starts with the most elementary gates and works up to the complete computer. Gives an understanding of the languages and how they operate in the computer.

### NAILING JELLY TO A TREE

**H0149A** \$25.50  
This guide to software teaches you about machine language, assembly language programming and BASIC. The emphasis is not on learning to write programs but on learning to use the thousands of available programs that have already been written.

## DON'T (OR, HOW TO CARE FOR YOUR COMPUTER)

**H0153A** \$19.95  
A guide to computer and peripheral preservation. Specific advice for the computer, floppy disks, hard disks, the CRT terminal, the printer, tape units, the computer room, software and documentation.

## COMPUTERS FOR EVERYBODY

**H0270A** \$8.95  
In this easy-to-understand book it is explained how a computer can be used at home, in the office or at school. Includes a consumer's guide to computer equipment that will help the reader decide what to buy and who to buy it from. Second edition.

## YOUR FIRST COMPUTER

**H0271A** \$15.25  
An easy-to-understand beginner's book to small computers. Understanding them, buying them and using them for personal and business applications.

## MICROCOMPUTERS: A PARENTS' GUIDE

**H0275J** \$13.75  
In clear, non-technical language, the authors explain what micros are, what they can do and what to expect in the future.

## computer hardware and techniques

### MICROCOMPUTER DESIGN AND TROUBLESHOOTING

**J0161P** \$26.75  
Tells you how to design microcomputer systems and make them work without an expensive commercial development system or the need for costly test instrumentation. Includes a complete description of two microprocessors — the 8085 and the 6502.

### MICROPROCESSOR INTERFACING TECHNIQUES

**J0167A** \$29.95  
Teaches you how to interconnect a complete microprocessor system and interface it to the usual peripherals. The hardware and software skills needed to effectively interface peripheral devices are covered along with various buss standards and A/D conversion. Third edition.

### EXPERIMENTS IN ARTIFICIAL INTELLIGENCE FOR SMALL COMPUTERS

**J0168P** \$13.25  
Artificial intelligence is the capability of a device to perform functions normally associated with human intelligence. With this book, a small computer with extended BASIC and some knowledge of BASIC language, you can conduct experiments in artificial intelligence.

### PET INTERFACING

**J0169P** \$25.25  
Demonstrates how to build numerous interfacing devices for PET hardware. BASIC language programs are used throughout, and the book includes a discussion of the microprocessor's internal architecture and general hardware/software interfacing.

THIS MONTH'S SPECIAL

### FIFTY BASIC EXERCISES

Normally \$17.95; this month only,

\$13.25

Designed to teach BASIC through actual practice, this book contains graduated exercises in maths, business, operations research, games and statistics. The programs were designed to run directly on a TRS-80 but will run on any system with MicroSoft BASIC. To order, quote book number KX188A.

Limited supplies

## USING THE IBM PERSONAL COMPUTER

**J0319P** \$21.50  
This all-purpose beginner's book is a complete guide to the IBM-PC.

## Z8000 HANDBOOK

**J0341P** \$18.95  
Provides a complete and clear description of the function and operation of the Z8001 and Z8002 16-bit microprocessors. Includes information on data types, memory management, interfacing and peripheral devices and the Z8000 instruction set.

## computing software

### THE CP/M HANDBOOK (WITH MP/M)

**K0173A** \$24.95  
Contains a step-by-step description of all the CP/M command features. Designed for the beginner, the book progresses to detailed explanations of the file transfer, debugging and CP/M text-editing programs.

### HOW TO GET STARTED WITH CP/M

**K0174A** \$22.95  
This practical book eases the reader into the essentials of the system, giving an overview of the operating system, an idea of what it will be like to use and what it can do for the reader.

### THE 68000: PRINCIPLES AND PROGRAMMING

**K0176P** \$19.95  
An easy-to-read, systematic approach to the 68000 advanced 16-bit microprocessor. The book guides you through the complex architecture, instruction set, pinouts and interfacing techniques. Written for design engineers, programmers and students.

### COMPUTER GRAPHICS PRIMER

**K0180P** \$21.95  
Almost every page has a colour drawing, photograph, picture or a schematic to help you learn computer graphics quickly and easily. Programming concepts apply to all microcomputers, and examples are given in BASIC for the Apple II.

### PASCAL PROGRAMS FOR SCIENTISTS AND ENGINEERS

**K0181A** \$23.50  
More than 60 of the most frequently used scientific algorithms, with program implementation in Pascal.

### HOW TO WRITE AN APPLE PROGRAM

**K0182P** \$23.25  
Very much a 'how-to' book. Author assumes only a minimal familiarity with computer and BASIC. The book covers every aspect of simple program writing from initial concepts to final debugging — wittily illustrated.

### HOW TO WRITE AN IBM-PC PROGRAM

**K0184P** \$23.25  
Virtually identical to *How to Write an Apple/TRS-80 Program*. Changes have been made to allow for differences in the two machines and variations in BASIC.

### THE UCSD PASCAL HANDBOOK


**K0197P** \$23.75  
Language descriptions organised in a quick and easy reference are given in this book for readers with no prior experience of Pascal programming.
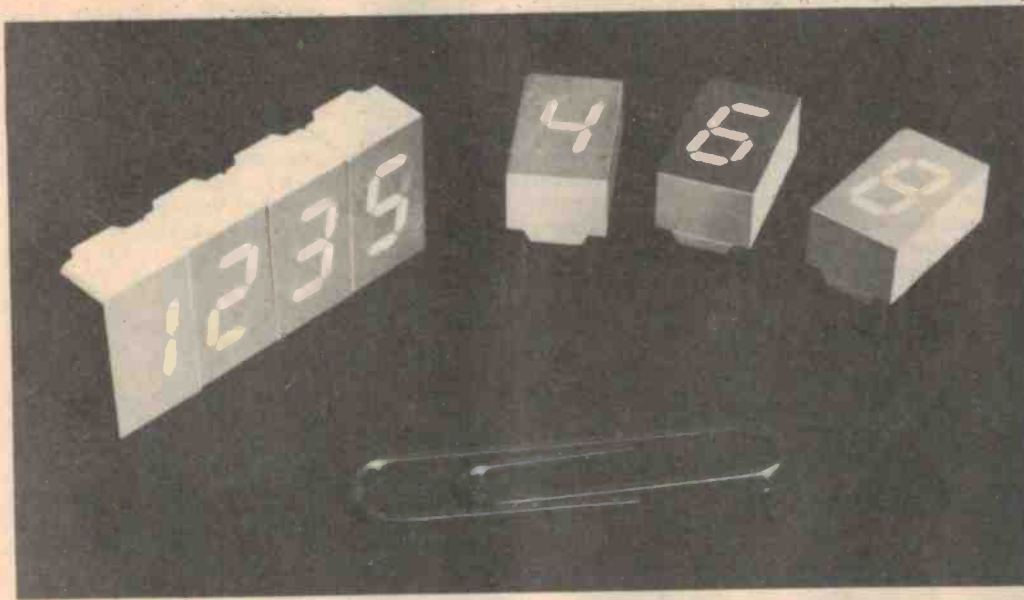
### PASCAL

**K0199A** \$21.95  
For people with little or no programming experience, this book gives lots of examples that clearly explain proper usage of language features. Discusses top-down programming, debugging, self-documentation, etc.

All prices of publications in this catalogue listing are subject to change without notice.





## HEWLETT-PACKARD INTRODUCES SUPER-BRIGHT, SEVEN-SEGMENT DISPLAY FAMILY, PIN-FOR-PIN COMPATIBLE WITH FND 35X/36X

**A** new 7.6 mm (0.3") seven-segment LED display available in standard red, high-efficiency red, yellow and green has been announced by Hewlett-Packard featuring pin-for-pin compatibility with Fairchild's FND 35X/36X display.

Fairchild quit the opto and display market earlier this year and inventories of most Fairchild opto products are currently run out or very low.

Features such as bright, evenly lighted segments for high ambient-light viewing, a low forward-drive current, a small, space-saving package and an attractive character font characterize these new HDSP Series

displays.

The displays require a lower drive current to achieve the same brightness as HP's existing family of 7.6 mm LED displays. This new family requires up to 25% less current and can still be viewed at distances up to three metres.

Increases up to 50% in viewed brightness are possible when the displays are driven at typical

drive currents of 6 to 10 mA. This makes the displays well suited for high ambient-light applications.

The display package measures 7.62 by 12.7 mm. Their Mitred Segments and categorisation for luminous intensity assure an attractive front-panel appearance. Yellow and green displays are also categorized for colour.

Price and delivery information are available through authorised HP components distributors, or contact **Hewlett-Packard, 31-41 Joseph St, Blackburn Vic. 3130. (03)890-6351.**

60 dB, while the volume control range is -80 to +21.5 dB.

The TDA1524 is suitable for car radios, stereo television receivers and low-cost mains-fed stereo audio equipment. It will operate from supply voltages between 7.5 V and 16.5 V, over a temperature range of -30 to +80°C.

For further information, contact **Philips Electronic Components and Materials, 67 Mars Road, Lane Cove NSW 2066. (02)427-0888.**

## NEW CONTROL IMPROVES S/N OUTPUT BY 20 dB

**P**hilips' new TDA1524 active tone/volume control for stereo audio systems incorporates its own internal gain to give a signal-to-noise ratio up to 75 dB. This is 20 dB higher than similar devices.

The four functions of this bipolar integrated circuit are bass and treble control, volume

control with built-in loudness (which can be switched off) and balance, all of which are controlled by dc voltages from potentiometers or a D/A converter.

Bass and treble boost is up to 15 dB and is set by one external capacitor each per channel. Channel separation is typically

## TELEDYNE'S CONVERTER WITH A DIFFERENCE

**T**he Teledyne TSC800, a 15-bit plus sign-integrating analogue-to-digital converter, is designed to improve the conventional two-cycle dual slope conversion cycle by incorporating systems zero and integrator output zero phases.

Offset error sources are automatically zeroed, and overrange recovery time is reduced. The integrating conversion technique is immune to the noise spikes that introduce errors in successive approximation converters.

The externally adjustable clock allows integration periods which are integral multiples of 50 Hz or 60 Hz for maximum power-line noise rejection. By using the 2.4576 MHz crystal oscillator mode, 50, 60 and 400 Hz signals are rejected.

Microprocessor interphase signals support eight- or 16-bit parallel data transfers.

For further information, contact **Promark Electronics, Suite 102, 6-8 Clarke Street, Crow's Nest NSW 2065. (02)439-6571.**

## A SHARP SHUNT

**F**airchild has announced the availability of the  $\mu$ A431 precision adjustable three-terminal shunt regulator with guaranteed temperature stability over the entire temperature range of operation.

The output voltage can be set at any level greater than 2.5 V (V ref.) up to 36 V by selecting two external resistors that act as a voltage divider network.

The sharp turn-on characteristics make the device an excellent replacement for many zener diode applications.

Other features include low output noise, programmable output voltage and an average temperature coefficient of 50 ppm/°C.

For further information, contact **Fairchild Australia, 366 Whitehorse Road, Nunawading Vic. 3131. (03)877-5444.**



# Cut your computer installation time.

We carry Belden®...the most comprehensive line of computer cable available.

If you want to move data a few feet or a few miles, we can help you get clean, clear signals regardless of how difficult the operating environment. We have cable for local area networks plus plant and office interconnect applications. We also stock Belden's Bit-Driver™ line drivers and multiplexers for replacing short-haul phone lines with long-term savings. Plus, RG-62 coax, twin-ax from 78 to 200 ohms, Datalene™ and individually shielded pair cables. Ask for them in Belden's time-saving, convenient, self-dispensing UNREEL® packages. Many are also in stock for direct air plenum installations. Plus, we carry fiber optic cable for total interference immunity. You won't find a more complete line anywhere to cover your needs.



There is no equal.

**ACME®** **ACME ELECTRONICS**  
A Division of James Hardie Electrical (Hardie Trading Ltd. Inc. in Vic.)



## SPEED DATA. Datalene™ data cable.

Belden® Datalene is the answer to your high-speed data transmission requirements. Datalene insulated cables offer lower capacitance and signal dissipation so you can send distortion-free data at higher speeds and for longer distances. It's crush-resistant, lightweight and has a temperature range of -40°C to +80°C. We have this high-performance Belden product—plus a huge selection of other Belden data transmission cables—in stock, ready for delivery. Just give us a call.

There is no equal.

**ACME®** **ACME ELECTRONICS**  
A Division of James Hardie Electrical (Hardie Trading Ltd. Inc. in Vic.)

**VIC.** 2-18 Canterbury Rd, Kilsyth 3137. Tel: 729 6211  
**N.S.W.** 120 Beaconsfield St, Auburn 2144. Tel: 648 2255  
**QLD.** Actrol Parts P/L Tel: 358 2011 Brisbane  
**A.C.T.** Electronic Components Tel: 80 4654  
**S.A.** Neil Muller P/L Tel: 272 8011  
**W.A.** J.G. Thomas & Assoc. Tel: 272 7122  
**TAS.** W.P. Martin P/L Tel: 34 2811 Hobart, 31 5545 Laun.

## Component **NEWS**

### QUICK MOS

Philips has released samples of the new PC54/74 high-speed CMOS logic circuits. The total program includes 240 devices, including a full range of TTL-compatible circuits, and is being alternate-sourced with RCA.

The devices have the low power dissipation, high input noise immunity and wide operating temperature range of CMOS devices and the TTL attractions of high speed and high drive capability.

The low power dissipation of the high-speed CMOS series improves reliability, simplifies power supplies, can eliminate heatsinks and fans and allows components to be packed more

densely. This makes for a substantial reduction in equipment size and weight.

The new devices dissipate negligible power due to leakage when they are not switching. Dissipation is still extremely low under operating conditions. With a 5 V supply, typical gate operating current is 3  $\mu$ A at 10 kHz, 30  $\mu$ A at 100 kHz and 300  $\mu$ A at 1 MHz. This compares with the currents of 400  $\mu$ A (up to 100 kHz) and 560  $\mu$ A (at 1 MHz) of LSTTL gates.

Encapsulations are plastic and ceramic DIL and plastic SO (mini-pack). For further information contact Philips Electronic Components and Materials Division, 67 Mars Rd, Lane Cove NSW 2066. (02)427-0888.

### NEW VARISTORS

General Electric has released a new high-energy MOV-varistor to protect heavy duty industrial motors and machines against damage caused by high-energy transients.

Rated at 70 000 amps and 10 000 joules, the newly designated 'B' Series is packaged in a new pyramid-shaped epoxy package that is easily mounted through two base screw holes.

They are designed to work in multiple parallel and series configurations where necessary.

G.E. claims the new varistor

out-performs existing technology at lower cost, has lower  $V_c$  (clamping voltage) than Silicon Carbide and a faster response and lower  $V_c$  than spark gaps.

Major applications include ac/dc motor control, traction/transportation, induction heating, mining, welding (high-energy), power supplies and oil drilling rig systems.

For further information, contact General Electric, P.O. Box 174, Willoughby NSW 2088. (02)888-8111.

### INTEL'S TOP-SECURITY MICROCONTROLLER

Intel has announced that it is making the erasable PROM version of its 8051 single-chip microcontroller in the HMOS (high-performance metal-oxide semiconductor) technology.

The new version, called the 8751H, matches the 8051AH's architecture and speed, and is primarily for the prototyping of systems that are based on the 8051.

A key feature of the 8751H is that it provides software security. When a program has been developed and finalised, a security bit can be programmed to make it virtually impossible to access the internal program. This capability is used for pro-

tecting proprietary software from unauthorised examination and copying.

During prototyping and production ramping, users can program the EPROM program memory in the 8751H. These programs can be erased and modified until a final version is developed.

During that phase, it is both efficient and economical to use the 8751H. Once users have developed and debugged their programs, factory-programmed 8051AHs can be ordered in large volumes.

For further details, contact Total Electronics, 9 Harker Street, Burwood Vic. 3125. (03)288-4044.





# ELECTROCRRAFT

## THINKING OF TV AERIAL INSTALLATIONS

We can help you with the largest stocks of Antennas and all associated equipment in NSW, from six manufacturers. Austenna — Channel-Master — Ecraft — Hills — Kingray — Matchmaster. Plus all the Technical information of 40 years experience in the aerial business.

### HILLS ANTENNAS

Gutter CM5 Kit 5EL	\$ 31.80
3-5/0 8EL 0-10 High Gain	\$ 46.13
EFC3/03S 12EL 0-10 Top of Line	\$113.16
EFC3/03S 3EL add on kit = 15EL	\$ 31.85
TL3/0 Log Periodic 10EL Ch 0-11	\$ 71.14
TL4/0 Log Periodic 12EL Ch 0-11	\$ 82.55
215 8EL Ch 2-10 300Ω	\$ 41.33
CA16 Phased array Outer fringe	\$ 86.57
2010 Ch's 2-10 (Airways) 300Ω	\$101.67
PF7 Anti ghost 7EL 300-75Ω	\$ 55.90
Y4 Ch's 6-11 4EL Yagi	\$ 20.49
Y6 Ch's 6-11 6EL Yagi	\$ 23.81
Y10 Ch's 6-11 10EL Yagi	\$ 37.36
Y14 Ch's 6-11 14EL Yagi	\$ 56.88

### CHANNEL MASTER BROAD BAND 0-10

3110A Coloray 300Ω-75Ω	\$ 51.00
3112 Super Coloray 7EL 75-300Ω	\$ 65.00
CX7 7EL Crossfire 300Ω	\$ 44.00
CX13 13EL Crossfire 300Ω	\$ 70.68
CX17 17EL Crossfire 300Ω	\$111.00
CX21 21EL Crossfire 300Ω	\$176.00
CX28 28EL Crossfire 300Ω	\$210.00
428 Airmaster Anti ghost 300Ω	\$106.00
1113 Quantum Anti ghost 300Ω	\$109.00

### FM ANTENNAS

Hills DIY FM Kit 75Ω	\$ 59.54
Hills Y3/FM 3EL 300Ω	\$ 28.00
Channelmaster FM700 7EL 300Ω	\$ 32.00
Matchmaster FMG/2 5EL 300Ω	\$ 38.98
Matchmaster FMG/6 10EL 300Ω	\$ 73.83

### HILLS UHF ANTENNAS

TC10/B5 10EL 75Ω 11dB/G Kings X	\$ 37.42
TC18/B5 18EL 75Ω 13.5dB/G Kings X	\$ 54.15
TC10/B4 10EL 75Ω 11.7dB/G Gore Hill	\$ 42.25
TC18/B4 18EL 75Ω 15.5dB/G Gore Hill	\$ 60.50

### CHANNEL MASTER UHF ANTENNAS

M2 13EL Wide Band B4-5 10dB/G	\$ 53.13
M3 22EL Wide Band B4-5 11.5dB/G	\$ 61.93
M4 27EL Wide Band B4-5 13dB/G	\$ 37.57
4225 Bowtie Wide Band B4-5 13dB/G	\$ 52.85
4194 Corner reflector B4-5 9dB/G	\$ 43.51
4193 Corner reflector B4-5 11dB/G	\$ 62.58

### INDOOR & CARAVAN ANTENNAS

Austenna AL1/10 1EL 2 Dipoles	\$ 19.93
Standard Spiral Indoor	\$ 6.93
Hills Tenna Trakka Indoor	\$ 15.00
Hills CV1 Caravan aerial	\$ 31.81
Matchmaster GGR Caravan	\$ 26.66

### MAST HEAD AMPLIFIERS

MH22 Ecraft 22dB/G 75Ω VHF	\$ 89.94
MH26 Ecraft 26dB/G 75Ω VHF-UHF	\$ 96.61
Hills MH4 25dB/G 300-75Ω VHF	\$ 89.93
Hills MH6 36dB/G 300-75Ω VHF	\$105.39
Kingray MH20 20dB/G 300-75Ω VHF	\$ 88.28
Kingray MH20WN 20dB/G	
Selective filter attenuates	
Ch's 3 to 5A	\$94.95
Ca. amp 12V AM-FM	\$ 9.00
Radioamp: SW-MW-LW-FM 240V	

### 50 Types of amplifiers in stock

Down converters UHF-VHF	
Kingray UV1 V for VCR's	\$ 82.50
Hills set top converter tuneable	\$105.50
ROTATORS IND. ROT. TORQUE VERT LOAD	
KR250 Pre set 200KG CM 50KG	\$114.38
KR400 Meter 400KG CM 200KG	\$206.25
6-Core Cable per metre	\$ 0.76

Good stock of Channel 28 aerials.  
Phone for Technical Information.  
Hours 8AM to 5PM Monday to Friday.

All prices plus freight or postage.

## ELECTROCRRAFT (MANUFACTURING) PTY LTD.

68 WHITING STREET, ARTARMON 2064  
(PO BOX 398, ARTARMON 2064)

TELEPHONE 438 4308, 438 3266

OFF-STREET PARKING

# Just for Listening!!!



## SAIKO SC7000

Computerized Programmable Scanning Receiver



## AMAZING FUNCTIONS ..

- 70 Memory channels.
- Scans the Aircraft Band, the UHF Band and the VHF (High and Low) Band.
- 2.5 KHz channel steps on VHF and Aircraft Bands.
- 240 volt and 12 volt operation.
- Tape Recording Connections.

You may want to listen for many reasons whatever the reason, the SAIKO SC7000 offers a truly "state of the art" receiver with micro-processor technology and far more features than competitive receivers.

# IMARK

PROPRIETARY LIMITED

167 RODEN STREET, WEST MELBOURNE,  
VIC. 3003, AUSTRALIA.  
PHONE: (03) 329 5433. TELEX: AA37753 IMARKO

## APPLE® 100% COMPATIBLE PRODUCTS

(R) Trade Mark of Apple

### SLIMLINE DISK DRIVES

Includes patent switch that allows recording on both sides of disk.

(6 months guarantee) **\$365**

**BUY 2 DRIVES \$345**

And get the second drive for BI-DOS Disk control card: \$75

### AMBER HI-RES MONITORS

20 MHz 1000 Lines Res

Best Buy in Australia.

(12 months guarantee) **\$199**

MONITOR STANDS .....\$30  
(Will tilt, swivel and hold any monitor)

COOLING FANS .....\$50

(JUST CLIP ON, FRONT ON/OFF LIGHT SWITCH FOR TOTAL SYSTEM CONTROL)

JOYSTICKS .....\$35

(SELF CENTERING AND ADJUSTABLE)

PRINTER CARD .....\$80

(INCLUDES CABLE AND WILL RUN ANY PARALLEL PRINTER)

WILD COPY CARD .....\$90

(ULTIMATE IN PROGRAM BACKUP)

SPEECH SYNTHESISER

CARD .....\$65

(UNLIMITED VOCABULARY COMPLETE WITH SPEAKER & DISK)

EPROM CARD .....\$95

(PROGRAM 2764, 2732, 2716, 2708)

HOBBY CARD .....\$20

(DESIGNERS OR TECHNICIANS DELIGHT)

16K RAM CARD .....\$75

ALL PRICES INCLUDE SALES TAX AND COURIER CHARGE.

PLUS 80 COLUMN, PAL, PRINTER.

R.G.B. GRAPPLER, PRINTER BUFFER, 8088 (WILL RUN IBM SOFTWARE), CLOCK, 128K RAM, KEYBOARD & FUNCTION CARD, PRAXIS TYPEWRITER TO PRINTER CARD, POWER SUPPLIES CASES & KEYBOARDS.

PLUS SOMETHING SPECIAL FOR ALL CURRENT BUSINESS USERS!

\*\*LIMITED STOCK ON SOME ITEMS.

ALL PRODUCTS COVERED BY OUR 6 MONTHS GUARANTEE.

FOR FREE CATALOG SEND S.A.E. FOR CATALOG MEMBERSHIP, IE (RC 12 ISSUES DETAILING UPDATE PRODUCT INFORMATION BARGAINS (SEND \$5 AND ALSO RECEIVE OUR \$10 DISCOUNT VOUCHER FOR ANY FUTURE PURCHASE.

DELIVERIES — FAST. NO C.O.D.

PERSONAL CHEQUES ACCEPTED, BANKCARD, BANK CHEQUE AND MONEY ORDERS RECEIVE SHIPPING PREFERENCE. ALL GOODS EXPRESSED VIA T.N.T. AIR. 14 DAY MONEY BACK GUARANTEE. SEND ORDERS AND ENQUIRIES TO:

## VIDEO TECHNOLOGY

Computer Peripheral Mail Order Division

P.O. BOX 217, PETERSHAM  
NSW 2049 AUSTRALIA  
TELEX: AA71115 ANBETA  
TELEPHONE: (02) 568-3423

DEVELOPERS & WHOLESALEERS OF VIDEO-COMPUTER TECHNOLOGY PRODUCTS. WE SUPPLY TECHNICAL SUPPORT AND ENGINEERING BACK-UP FOR ALL PRODUCTS BUT DO NOT OPERATE A RETAIL OUTLET.

### BANKCARD ORDER FORM

Name .....  
Address .....  
Postcode .....  
B/card No. .... Exp/Date .....  
Signature .....





# SUPER DEALS

JAYCAR ELECTRONICS &  
No. 1 FOR COMPUTERS,

## MicroBee features:

- 16K and 32K.
- Non-Volatile CMOS RAM.
- Programmable RS232 Serial Port.
- Programmable 8 Bit I/O Port.
- Display 64 x 16 and 80 x 24 screen format.
- 6545 Programmable VDU Driver.
- Cassette Interface, 300 and 1200 baud.



Australia's leading  
personal  
Computer  
Now with  
Jaycar  
Dealer  
Support

## BRILLIANT!

DIRECT CONNECT MODEM

- KEY FEATURES
- DIRECT ATTACH AUTO ANSWER MODEM
  - 300 BPS FULL DUPLEX (CCITT V21)
  - 1200 BPS HALF DUPLEX (CCITT V23)
  - 75 BPS BACK CHANNEL (FULL V23)
  - AUTO DIAL
  - BELL FREQUENCIES INCLUDED
  - TELECOM APPROVED
  - 1 YEAR WARRANTY
  - NO ADJUSTABLE CIRCUITRY
  - DESIGNED IN AUSTRALIA
  - MADE IN AUSTRALIA
- THIS IS NOT A "TOY"



\$399

Includes 1 year subscription to  
the Australian Beginning

Jaycar has made a bulk purchase to bring them to you at the incredibly low price of \$399. Amazing value for a FULL DUPLEX unit. Cat. YC 1350

### "Y" ADAPTOR LEAD

You could simply plug this adaptor lead into your telephone socket if you were allowed to. It plits to two sockets. One for the YC-1350 Modem (special fitting) and the other for a telephone. No need to disconnect the phone ever! ONLY \$29.95

### MICROBEE CARRY CASE

Carry your MicroBee around without risking damage!  
Glittering brown vinyl rigid enclosure measures  
355(W) x 245(D) x 75(H)mm. Incorporates the  
MicroBee logo emblem on box.

FANTASTIC VALUE AT \$12.50

## pricing information

Cat. XE-5000	MicroBee 16K Plus	\$469.00
Cat. XE-5050	MicroBee 16K IC	\$499.00
Cat. XE-5100	MicroBee 32K Plus	\$559.00
Cat. XE-5150	MicroBee 32K IC	\$599.00
Cat. XE-5200	MicroBee 64K Plus	\$699.00
Cat. XE-5250	Single Disc System	\$1099.00
Cat. XE-5255	Add-on Disc	\$559.00
Cat. XE-5260	Dual Disc Drives	\$1599.00
Cat. XE-1205	Printer Cable Interface	\$49.95

## MICROBEE

### KITS—KITS—KITS—KITS—KITS—KITS—KITS—

ETI 733 RTTY Converter. Ref: ETI April 1983. This simple project allows you to hook up your MicroBee to a HF receiver and print radio teletype messages on a monitor screen. Listen to world news for FREE!!  
Cat. KE-4654

ONLY \$17.95

ETI 649 MicroBee Light Pen. Ref: ETI August 1983. This simple, low cost device plugs into the Bee's 8 bit port. The "pen" gives you an entry into the world of light pens and interactive software.  
Cat. KE-4656

SHORTFORM \$19.50

SPECIAL PROBE CASE TO SUIT (as specified in ETI article) Cat. HB-6400 \$19.95  
ETI 668 MicroBee EPROM Programmer. Ref: ETI February 1983. This simple, low cost EPROM programmer just plugs into the Bee's I/O port and enables you to save programs in any of the 5 different common EPROMs available (2716, 2532, 2732, 2732A, 2764). Kit comes complete with 'Personality' plug and all IC sockets.  
Cat. KE-4650

\$39.95

Parallel Interface Kit for the MicroBee. Includes 15 pin 'D' plug - add \$15.00 if Centronics plug required.  
Cat. KE-7017

\$15.00

PLEASE RING YOUR NEAREST STORE FOR EXTENDED TRADING HOURS OVER THE CHRISTMAS PERIOD

PLEASE RING YOUR NEAREST STORE FOR EXTENDED TRADING HOURS OVER THE CHRISTMAS PERIOD

PLEASE RING YOUR NEAREST STORE FOR EXTENDED TRADING HOURS OVER THE CHRISTMAS PERIOD



# FOR COMPUTERS!

## ELECTRONIC AGENCIES SOFTWARE & PERIPHERALS



**DISASSEMBLER** By Dreamcards  
Some may say "Not another Disassembler". But this one has a difference. It allows you to set out where the data fields are so the computer is saving time, not trying to disassemble data. A program you shouldn't be without.  
Cat. XE-6915 \$15.00

**CHEAPIE** By Dreamcards  
Two top quality programs for the price of one. The best Hangman we've seen yet on side A and a superb version of Battleship on side B. Both have excellent graphics.  
Cat. XE-6920 \$15.00

**CANNIBALS AND MISSIONARIES**  
The old logic problem game of transferring 3 Cannibals and 3 Missionaries from one side of a river to the other in a boat that holds two. If there are more Cannibals than Missionaries on either side at any time the Cannibals revert to their favourite form of feeding.  
Cat. XE-6925 \$14.95

**COMPOSER BEE**  
This is a very well written program for music. This program allows you to compose, play, edit, transpose as well as being able to load and save your music. A program that has been a long time in the writing and well worth buying.  
Cat. XE-6930 \$22.50

**WORD ADVENTURE**  
A program with very good graphics using little characters to entice the user to think what word is either a synonym, antonym or homonym of the word they are showing. Everytime you get it wrong you are given more clues. After the clues run out you must face the Dragon when you must spell the word he is holding correctly before you.  
Cat. XE-6935 \$14.95

**PONTOON**  
A quality fast moving card game where up to 6 players can play against the computer who is banker.  
Cat. XE-6940 \$14.95

**MUSIC - B - MYTEK**  
MusicB is a music Composer/Editor that lets you create and save music and sound effects with a flexibility that makes chopsticks of the Basic PLAY command. MusicB is a great way to learn and play music! Comprehensive instructions are included.  
Cat. XE-7010 \$20.00

**TRSBEE - MYTEK**  
TRSBEE is a package of three programs that loads TRS-80 Model 1 and 3 program tapes into the MicroBee without any additional hardware. Although some program editing will still be required prior to their running, the majority of program typing time is saved by TRSBEE. The first program loads TRS-80 BASIC programs into MicroWorld BASIC. Most programs may then be edited and run. The second program in the package loads any TRS-80 machine code file into MicroBee memory. The third program loads TRS-80 assembler files into the MicroBee EDITOR/ASSEMBLER. Any TRS-80 Model 1 or 3 tape may be loaded. TRSBEE opens up a whole new world of possible software on your MicroBee!  
Cat. XE-7005 \$30.00

**HOUSEHOLD REGISTER**  
This program will simplify the task of determining the value of your home's contents for insurance purposes, as well as providing descriptions of all listed items in the event of their loss or destruction. Effects are catalogued by name, description and value. Nine separate rooms are provided, and up to 28 items may be listed in each.  
Cat. XE-7000 \$15.95

**STAT PACK - STATISTICS**  
This program is a general purpose graph plotting, linear regression, line of best fit and correlation program. It features a t-test of significance for the correlation coefficient and, if no evidence of correlation is found, a determination of minimum sample size is performed.  
Cat. XE-6999 \$14.95

**BASIC TUTORIAL**  
Is a super teaching aid for any classroom. Basic Tutorial is a set of 9 interactive exercises designed for teaching Basic to the computer novice. No previous knowledge is assumed. Basic Tutorial uses a unique double screen technique to display both the normal computer output and the tutorial exercises at the one time. This allows the student to use the MicroBee in the normal way, while the tutorial instructions appear in the lower half of the screen.  
Cat. XE-6860 \$20.00

**MACHINE CODE TUTORIAL - MYTEK**  
Consists of 8 interactive exercises designed for teaching machine code programming and related topics as they apply to the MicroBee computer. Only a general knowledge of the BASIC language is assumed. Machine Code Tutorial is designed to bridge the gap between BASIC programming and being able to understand and use typical Z80 manuals.  
Cat. XE-6855 \$25.00

**BUDGET - SPREADSHEET**  
This program is designed to speed up and simplify the task of framing a usable financial budget. Applications range from personal or household to small business finances. A quality program.  
Cat. XE-6850 \$15.95

**DECODE**  
Basic decoder and listing formatter  
This programme will be an invaluable aid to any one taking first steps in understanding machine code or wants to expand their library of proven machine code routines. Decode will (a) print imbedded machine code routines fully and accurately (b) print all unprintable characters (c) provide a clearer, easier to read listing and send all output to a printer if so required. ED ASM is not required.  
Cat. XE-6765 \$15.95

**DATABEE**  
This program is a well written data base management system that utilised the MicroBee to its fullest to provide a Data Management System similar to those found on larger and more expensive systems. This comes complete with large bound manual.  
Cat. XE-6945 \$19.95

**ASTEROIDS PLUS - MYTEK**  
Asteroids Plus is one of the finest high resolution graphic arcade games available for the MicroBee computer. It features 3-D point by point resolution graphics, shields, sound effects, intelligent objects, guided missiles, black holes and a score board. If you enjoy playing computer games, you will be captivated by Asteroids Plus.  
Cat. XE-6297 \$22.50

**BEEZ 80 - MYTEK**  
This secret code disassembler will disassemble any code sequence. Nothing is illegal. It will allow you to program with codes that no other disassembler can decipher!  
Cat. XE-6298 \$20.00

**SPACE INVADERS**  
One of the most popular programs ever released. This version was written especially for the MicroBee.  
Cat. XE-6030 \$14.95

**FORTH**  
A new language for the MicroBee. Comes complete with interpreter on one side of the tape and supporting programs on the other side. As well as this it includes a very well written, bound manual.  
Cat. XE-6965 \$45.00

**PSYCHOTEC** By Dreamcards  
Psychotec provides a striking example of artificial intelligence, allowing a dialogue in English between computer and operator, the computer playing the role of psychiatrist and the operator being a "patient" on the couch. Leaves other "similar" types for dead.  
Cat. XE-6875 \$15.95

**MERLIN** By Dreamcards  
Merlin is a 32K adventure set in England during the dark ages. Your task is to search through the dark forest inhabited by robbers, outlaws and creatures with awesome magic powers to find a legendary sword. An excellent adventure.  
Cat. XE-6870 \$25.00

**PROGRAMMING HINTS**  
Consists of a collection of modules which you may use to improve your own BASIC programs. They are all linked together under a menu driven display which allows you to RUN or LIST each module to see how they work.  
Cat. XE-6895 \$14.95

**LOG - GENERAL PURPOSE INDEX**  
This program is designed to suit a wide range of records where indexing (and later searching) can be on one or two words, or on a string of up to 15 characters. Each record consists of its index heading, plus up to 12 lines of text. Each line can contain up to 41 characters.  
Cat. XE-6890 \$15.95

**MINE DROP**  
You are a tank running around a maze gathering all the supplies you can. It sounds easy, but you have a guided missile hot on your trail. Your only defence is a remote controlled mine which you drop and explode at will. A very fast joystick or key controlled game.  
Cat. XE-6960 \$14.95

**PENETRATOR**  
A low resolution graphic version of the popular game "Scrambler". You must defeat the rockets and bomb the radars in an effort to get to the next stage which is even harder. This game can be either controlled by a Joystick or by keys. Being in Lores graphics it is a very fast game. If you are bored with the same land pattern you can devise your own.  
Cat. XE-6955 \$19.95

**SPACE PATROL**  
A lot like Penetrator but in high resolution graphics. You must battle your way through four chances of blowing up a neutron bomb shelter. If you are successful, the next round is a lot harder.  
Cat. XE-6950 \$16.95

**METEOR RESCUE - MYTEK**  
Your mission is to rescue stranded astronauts. You are the commander of the Landing Module docked in space with the mother ship. It is your responsibility to guide the landing module through a meteor field, down to the surface of the planet, to land safely on a landing pad. An astronaut will then run to your landing module and you will blast off. You must use your lasers if necessary and dock with the mother ship again. A total of six astronauts must be shuffled to the mother ship.  
Cat. XE-7020 \$17.50

**CORVILLE CASTLE**  
Corville Castle is an adventure which will take you to a far away place of mystic castles, fierce monsters and evil warlocks. You must enter the warlocks castle and find some dark secret which will help you to destroy the warlock. But remember, you only have until dusk.  
Cat. XE-6285 \$16.95

# DEFENDER

for the  
MicroBee Computer

## Fast Furious Action Game

**NEW GAMES FOR MICROBEE**

<p><b>DEFENDER - FROM MYTEK</b> This long awaited program is finally available. Defender needs no introduction. The Defender arcade game is one of the most popular ever produced and the Mytek version is brilliant, a rival for Asteroids Plus. Cat. XE-7036 \$22.50</p> <p><b>DESTROYER</b> You are the UFO and you must destroy the enemy city buildings before you can land. You have no control over the UFO except for the three bombs on every pass you make over the city. But beware the UFO gets lower with every pass. Good graphics and sound. Cat. XE-7048 \$14.95</p> <p><b>COULOMBS LAW</b> This program is another in the series of Physics simulations. The first part is a tutorial and the second is a simulation of the experiment. Cat. XE-7049 \$14.95</p> <p><b>BACKGAMMON - FROM MYTEK</b> This game conforms exactly to that set down in the official rules of the International Backgammon Association, including the rules of doubling and scoring. Cat. XE-7050 \$17.50</p> <p><b>POOLS AND LOTTO</b> Two programs to help make life easier for the Pools and Lotto enthusiasts. The first program chooses your numbers for the week and the second program allows you to input your numbers into a program and when Lotto night arrives you can input the winning numbers and the computer will check your Lotto for you. Cat. XE-7045 \$14.95</p> <p><b>WONDER WORDS</b> This program allows you to input 20 words and the computer will create a Wonder Word puzzle. This can be either sent to a printer or solved on the screen, or let the computer solve it. Just the program for Wonder Word enthusiasts. Cat. XE-7046 \$14.95</p> <p><b>GEO-TECH DRAWING</b> This is the first tape in a series to assist students in grasping the fundamentals of geometric and technical drawing. It uses good graphics with excellent explanations. Cat. XE-7047 \$14.95</p>	<p><b>DEFENDER - FROM MYTEK</b> This long awaited program is finally available. Defender needs no introduction. The Defender arcade game is one of the most popular ever produced and the Mytek version is brilliant, a rival for Asteroids Plus. Cat. XE-7036 \$22.50</p> <p><b>DESTROYER</b> You are the UFO and you must destroy the enemy city buildings before you can land. You have no control over the UFO except for the three bombs on every pass you make over the city. But beware the UFO gets lower with every pass. Good graphics and sound. Cat. XE-7048 \$14.95</p> <p><b>COULOMBS LAW</b> This program is another in the series of Physics simulations. The first part is a tutorial and the second is a simulation of the experiment. Cat. XE-7049 \$14.95</p> <p><b>BACKGAMMON - FROM MYTEK</b> This game conforms exactly to that set down in the official rules of the International Backgammon Association, including the rules of doubling and scoring. Cat. XE-7050 \$17.50</p> <p><b>POOLS AND LOTTO</b> Two programs to help make life easier for the Pools and Lotto enthusiasts. The first program chooses your numbers for the week and the second program allows you to input your numbers into a program and when Lotto night arrives you can input the winning numbers and the computer will check your Lotto for you. Cat. XE-7045 \$14.95</p> <p><b>WONDER WORDS</b> This program allows you to input 20 words and the computer will create a Wonder Word puzzle. This can be either sent to a printer or solved on the screen, or let the computer solve it. Just the program for Wonder Word enthusiasts. Cat. XE-7046 \$14.95</p> <p><b>GEO-TECH DRAWING</b> This is the first tape in a series to assist students in grasping the fundamentals of geometric and technical drawing. It uses good graphics with excellent explanations. Cat. XE-7047 \$14.95</p>
---	---

PLEASE RING YOUR NEAREST STORE FOR EXTENDED TRADING HOURS OVER THE CHRISTMAS PERIOD

PLEASE RING YOUR NEAREST STORE FOR EXTENDED TRADING HOURS OVER THE CHRISTMAS PERIOD

**Jaycar** Incorporating  
**ELECTRONIC AGENCIES**

**SYDNEY** SHOWROOMS  
117 YORK STREET - PHONE: (02) 264 6688 and (02) 267 1614  
TELEX: 72293

**CARLINGFORD**  
Cnr. CARLINGFORD & PENNANT HILLS ROAD - PHONE: (02) 872 4444

**CONCORD**  
115 - 117 PARRAMATTA ROAD - PHONE: (02) 745 3077

**HURSTVILLE** 121 FOREST ROAD - PHONE: (02) 570 7000

**NUMBER 1 FOR KITS**

POST AND PACKING CHARGES	Mail Order
\$5 - \$9.99 (\$1.50)	By
\$25 - \$49.99 (\$4.50)	Bankcard
\$100 - \$199 (\$8.00)	Via Your Phone
Over \$199 (\$10)	

\*Free INSURANCE for Road & Registered Post over \$200\*

All heavy or bulky items (over 20kg.) sent Comet Road Freight \$12.00 anywhere in Australia.

**SHOP HOURS CARLINGFORD, CONCORD & HURSTVILLE**  
Mon - Fri 9am - 5:30pm; Sat - 9am - 12pm; Thurs night 8:30pm

**SHOP HOURS SYDNEY**  
Mon - Fri 8:30am - 5:30pm; Sat - 8:30am - 12pm; Thurs night 8:30pm

MAIL ORDERS AND CORRESPONDENCE: P.O. Box 185, Concord, 2137



# Logic troubleshooting tools and techniques

Digital circuitry has had an explosive growth over the past decade and now pervades virtually every facet of electronics. Whilst the reliability of devices and equipment has improved dramatically during that period, things still do go wrong and equipment still needs servicing when it breaks down. 'Board level' servicing can solve problems quickly in the field, but economics demands those removed boards be repaired and recycled. This article details the problems encountered and the tools and techniques employed to fix them.

DIGITAL integrated circuits range from simple buffers and two-input gate packages through to complex purpose-built controllers and microprocessors. Finding faults in digital equipment requires a *fundamentally different* approach from fault-finding in analogue circuitry, where the multimeter and oscillator are the prime tools and component characteristics can be individually measured. In digital electronics, most 'components' are contained within the ICs — which are often multi-functional. Thus there is need for a different troubleshooting approach to be developed, and different tools used, based on the type of faults that develop and the 'signatures' they leave. Of necessity, this article does not cover microprocessor-based equipment — *that's a whole subject on its own!*

## Faults & effects

When fault-finding circuits built from discrete components, the task is one of verifying relatively simple characteristics such as resistance, capacitance, or turn-on voltages of components with two or at most three nodes. (A 'node' is an active junction in a circuit, usually an input or an output.) While the function of the total circuit may be quite complex, each component in that circuit performs a relatively simple task and proper operation is easily verified.

In Figure 1, each diode, resistor, capacitor and transistor can be treated using a signal generator and a voltmeter, ohmmeter, diode checker or oscilloscope — the traditional servicing tools. But when this circuit is built in integrated circuit form, these components are no longer accessible. It now becomes necessary to test the operation of the complete circuit function.

Thus an important difference between discrete circuitry and circuits built from digital ICs is in the complexity of the functions performed by these 'components'. Unlike the resistor, capacitor, diode or transistor, which must be interconnected to form a circuit function, digital ICs perform complete, complex functions. Instead of observing simple characteristics, it is now necessary to observe complex digital signals and decide if these signals are correct according to the function the IC is meant to perform.

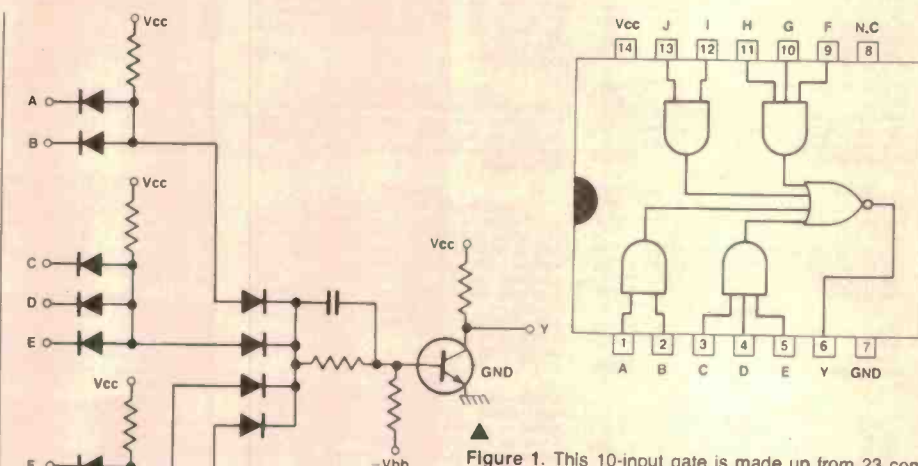


Figure 1. This 10-input gate is made up from 23 components. An IC to do the same job is shown at right. With discrete components, finding faults is easy with conventional meters, etc. When it's all inside an IC, where you've only got access to inputs and outputs, the job can be much harder. But there are ways.

Verifying proper component operation now requires 'stimulating' and observing many inputs (in Figure 1 there are 10 inputs) while simultaneously observing several outputs (up to two or three and at times as many as eight).

Thus another fundamental difference between circuitry built from discrete components and digital ICs is the number of inputs and outputs associated with each component, and the need to stimulate and observe these simultaneously.

In addition to the problems of simultaneity of signals and complexity of functions at the component level, the digital IC has introduced a new degree of complexity at the circuit level. Circuits which perplex all but their designer are commonplace. Given enough time, these circuits can be studied and their operation understood, but this is not an affordable luxury for those involved in troubleshooting electronic circuits. Without understanding a circuit's intricate opera-

tion, it becomes necessary to have a technique of quickly testing each component rather than attempting to isolate a failure to a particular circuit segment by testing for expected signals.

In order to solve these problems and make fault-finding of digital circuits more efficient, it is necessary to take advantage of the digital nature of the signals involved. Tools and techniques designed to service analogue circuits do not take advantage of this digital nature and thus are less efficient when used to troubleshoot digital circuits.

Figure 2 shows a typical TTL (Transistor-Transistor-Logic) signal. This might as well be any analogue signal when viewed on an oscilloscope. The oscilloscope displays absolute voltage with respect to time, but in the digital world absolute values are unimportant.

A digital signal exists in one of two or three states — high, low and undefined or in-between level — each determined by a threshold voltage. It is the relative value of the signal voltage with respect to these thresholds that determines the state of the digital signal, and this digital state determines the operation of the IC, not absolute levels.



In Figure 2, if the signal is greater than 2.4 volts, it is a high state and it is unimportant whether the level is 2.8 or 3.0 volts. Similarly for a low state the voltage must be below 0.4 volts. It is not important what the absolute level is as long as it is below this threshold. Thus when using an oscilloscope, the serviceman must over and over again determine if the signal meets the threshold requirement for the desired digital state.

Within a digital logic family, such as TTL, the timing characteristics of each component are well defined. Each gate in the TTL logic family displays a characteristic propagation delay time, rise time and fall time. The effects of these timing parameters on circuit operation are taken into account by the designer. Once a design has been developed beyond breadboard or prototype stage and is into production, problems due to design have (hopefully) been corrected.

An important characteristic of digital ICs is that when they fail, they fail catastrophically. This means that timing parameters rarely degrade or become marginal. Thus, observing on an oscilloscope and making repeated decisions on the validity of timing parameters is time consuming and contributes very little to the fault-finding process. Once problems due to design are corrected, the fact that pulse activity exists is usually enough indication of proper IC operation without further observation of pulse width, repetition rate, rise time or fall time.

Figure 3 shows a problem created by the TTL logic family. The output stage of a TTL device is a transistor totem pole. In either the high or low state, it is a low impedance. In the low state it is a saturated transistor to ground. It thus appears as 5-10 ohms to ground. This presents a problem to in-circuit stimulation.

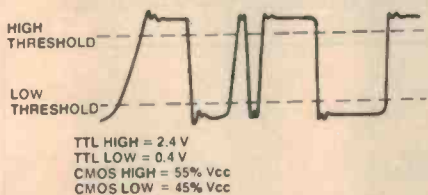


Figure 2. Digital circuits work on 'thresholds', and signals must be 'above' or 'below' the given high and low thresholds, which are different for the different 'families' — CMOS and TTL. ▲

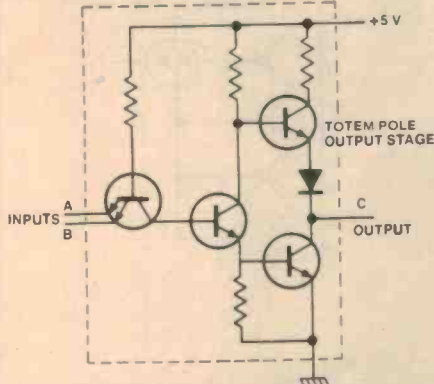


Figure 3. TTL ICs have 'totem pole' output stages, as shown above. When attempting to 'stimulate' an output node, such as C above, it is necessary to override the low impedance output stage, which consists of a saturated transistor. ▲

A signal source used to inject a pulse at a node which is driven by a TTL output must have sufficient power to override the low impedance output state. If you use a square-wave signal generator for fault-finding it must provide this capability, otherwise it is necessary either to cut printed circuit traces or pull out IC leads in order to stimulate the circuit being tested. Both of these practices are time consuming and lead to unreliable repairs.

Thus the use of the traditional oscilloscope and the traditional signal sources is inefficient. Since the diodes and transistors are packaged in the IC, use of diode checkers is also marginal, if not impossible.

These tools are general purpose tools that can be applied to any situation if you have enough time. But with the quantity and complexity of today's electronic circuits, it makes sense to find the most efficient solution to the problem at hand. This suggests using the oscilloscope, diode checkers and voltmeters on analogue circuits where they really shine, and using instruments that take advantage of the digital nature of signals on the digital circuitry to be repaired. We'll get to them a little later.

In order to repair digital equipment efficiently, it is important to understand the type of failures found in digital circuits. These can be categorised into two main classes — those caused by a failure internal to an IC and those caused by a failure in the circuit external to the IC.

Four types of failures can occur internally to an IC. These are (1) an open bond on either an input or output, (2) a short between an input or output and Vcc or ground, (3) a short between two pins (neither of which are Vcc or ground), and (4) a failure in the internal circuitry (often called the steering circuitry) of the IC.

In addition to these four failures internal to an IC, there are four failures that can occur in the circuit external to the IC. These are (1) a short between a node and Vcc or ground, (2) a short between two nodes (neither of which are Vcc or ground), (3) an open signal path, and (4) a failure of an analogue component.

Before showing how to detect each of these failures we will discuss the effect each has upon circuit operation.

The first failure (internal to an IC) mentioned was an open bond on either an input or output. The failure has a different effect depending on whether it is an open output or an open input bond. In the case of an open output bond (Figure 4), the inputs driven by that output are left to float. In TTL circuits a floating input rises to approximately 1.4 to 1.5 volts and usually has the same effect on circuit operation as a high logic level. Thus an open output bond will cause all inputs driven by that output to float to a bad level since 1.5 volts is less than the high threshold level of 2.0 volts and greater than the low threshold level of 0.4 volt. In TTL a floating input is interpreted as a high level. Thus the effect will be that these inputs will respond to this bad level as though it were a static high signal.

In the case of an open input bond (Figure 5), we find that the open circuit blocks the signal driving the input from entering the IC

Figure 4. An open output bond allows all inputs driven by that output to float to a 'bad level', usually interpreted as a high. Signals at points A and B illustrated below. ▼

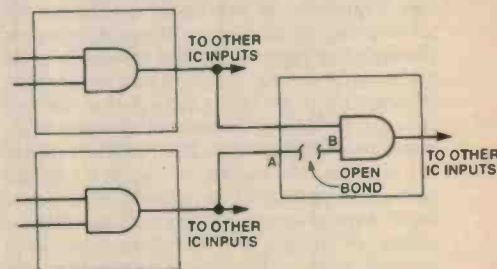
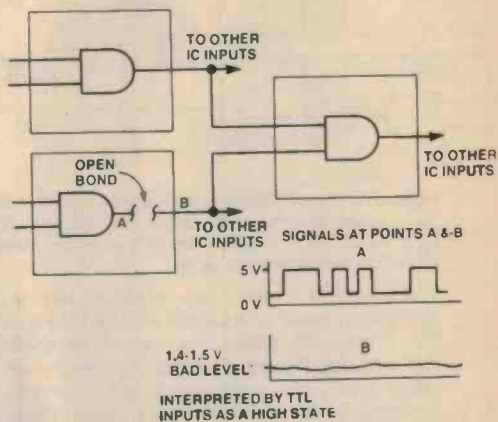


Figure 5. An open input bond blocks the incoming signal, allowing the input to float to a 'bad level' — interpreted as a high. Signals at points A and B illustrated above. ▲

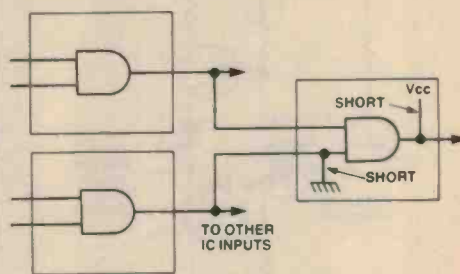


Figure 6. When you get an internal short to ground, the affected node is always pulled low. When shorted to Vcc (supply), the affected node is always pulled high. ▲

chip. The input on the chip is thus allowed to float and will respond as though it were a static high signal. It is important to realise that since the open circuit occurs on the input inside the IC, the digital signal driving this input will be unaffected by the open circuit and will be detectable when looking at the input pin (such as at Point A in Figure 5). The effect will be to block this signal inside the IC and the resulting IC operation will be as though the input were a static high.

A short between an input or output and Vcc or ground has the effect of holding all signal lines connected to that input or output either high (in the case of a short to Vcc) or low (if shorted to ground) (Figure 6). In many cases, this will cause expected signal activity at points beyond the short to disappear, and thus this type of failure is catastrophic in terms of circuit operation. ▶



# Logic troubleshooting

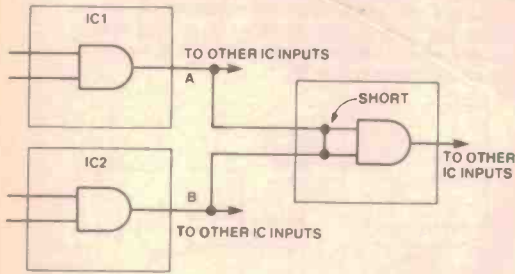


Figure 7. A short between two inputs makes a low-going driver pull the other driver low too. In IC2 at right, if B is low, it is pulled low by a saturated transistor, which pulls A low too. ▲▶

A short between two pins is not as straightforward to analyse as the short to Vcc or ground. When two pins are shorted, the outputs driving those pins oppose each other when one attempts to pull the pins high while the other attempts to pull them low (Figure 7). In this situation the output attempting to go high will supply current through the upper saturated transistor of its totem pole output stage, while the output attempting to go low will sink this current through the lower saturated transistor of its totem pole output stage. The net effect is that the short will be pulled to a low state by the saturated transistor to ground. Whenever both outputs attempt to go high simultaneously, or to go low simultaneously, the shorted pins will respond promptly. But whenever one output attempts to go low the short will be constrained to be low.

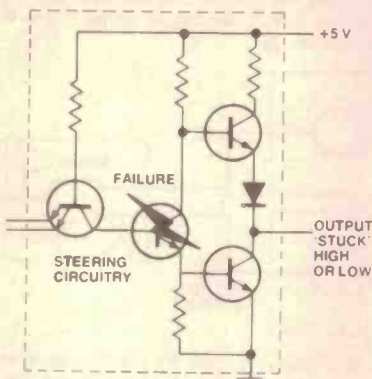



Figure 8. An internal failure of the steering circuitry will either cause the output to be 'stuck' high or low. ▲

The fourth failure internal to an IC is a failure of the internal steering circuitry of the IC (Figure 8). This has the effect of permanently turning on either the upper transistor of the output totem pole, thus locking the output in the high state, or turning on the lower transistor of the totem pole, thus locking the output in the low state. Thus this failure blocks the signal flow and has a catastrophic effect on circuit operation.

A short between a node and Vcc or ground external to the IC is indistinguishable from a short internal to the IC. Both will cause the
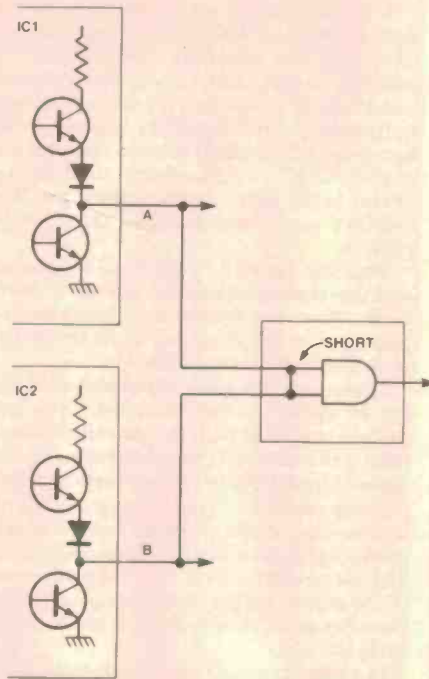
## ACKNOWLEDGEMENT

We would like to acknowledge the assistance kindly provided by the Instrument Group of Hewlett-Packard Australia Limited.



signal lines connected to the node to be either always high (for shorts to Vcc) or always low (for shorts to ground). When this type of failure is encountered a very close physical examination of the circuit may reveal if the failure is external to the IC, but it can be determined using 'pulsing' and 'tracing' tools, as explained later.

An open signal path in the circuit has a similar effect to an open output bond driving the node (Figure 9). All inputs to the right of the open will be allowed to float to a bad level and will thus appear as a static high level in

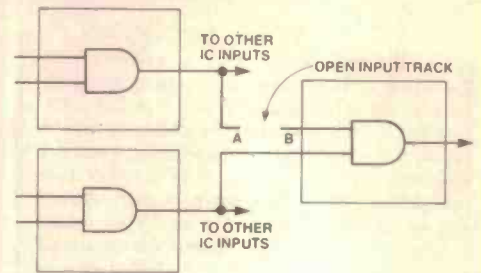


Figure 9. An open input track (external to the IC) has a similar effect as an open driver output bond. B will float to a bad level while A will still have signal on it. ▲

circuit operation. Those inputs to the left of the open will be unaffected by the open and will thus respond as expected.

The problem of open-collector outputs — 'wired-ANDs', 'wired-ORs' — is different from the other cases described. Open-collector outputs differ in that they do not have an active logic-high current source. Instead, the output stage collector (Q3 in Figure 10a) is left unconnected. Thus the output stage can sink current in a logic low state, but cannot source any current in the high state. This is provided by the 'pullup' resistor  $R_L$ . Generally, you will find several open-collector gates are interconnected in parallel, as shown in Figure 10b.

So long as every output stage is turned off, the voltage at the common connection node is near Vcc, but when any one gate output is driven on, the node voltage drops to the low state (near 0 V). The common node thus acts as an AND gate in itself (hence 'wired-AND'). This circuit is 'wired-NAND' in TTL circuits if the inputs and outputs are active low. In other families, it's an OR function. When looking for faults here, the output has to be looked at in conjunction with the input. ▶


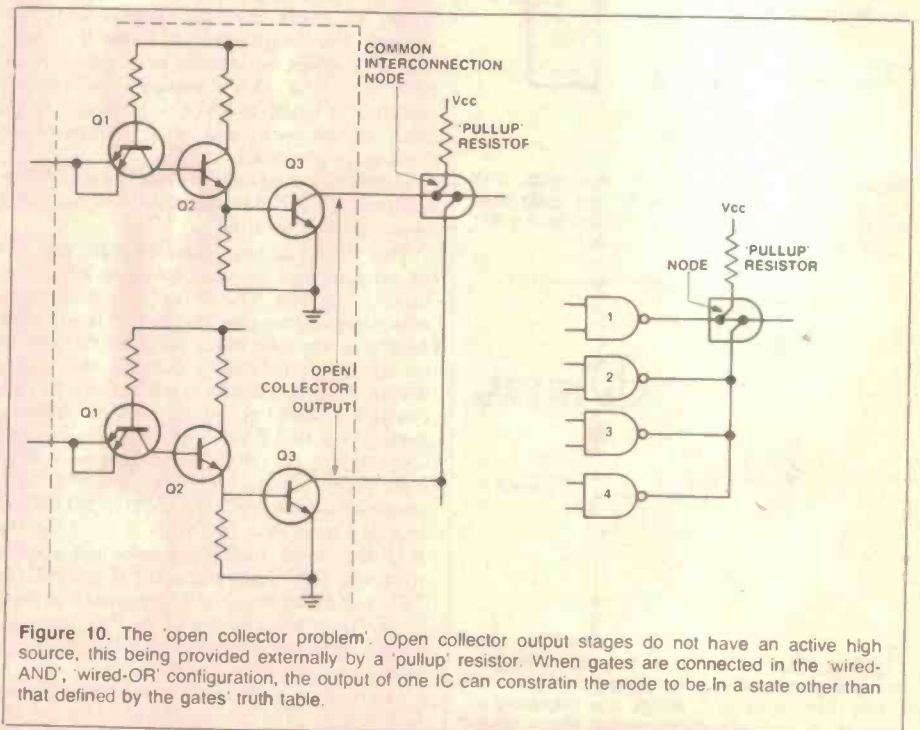


Figure 10. The 'open collector problem'. Open collector output stages do not have an active high source, this being provided externally by a 'pullup' resistor. When gates are connected in the 'wired-AND', 'wired-OR' configuration, the output of one IC can constrain the node to be in a state other than that defined by the gates' truth table.

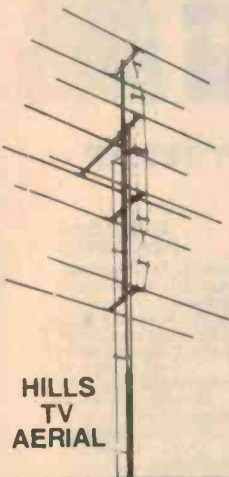

# TO THE ELECTRONICALLY MINDED. (Professionals, Hobbyists, Students & Enthusiasts.)

We carry a wide range of Multimeters, Calculators, Soldering tools, Transformers, Cables, Instrument boxes, Computer Connectors, TV Aerials, Components and just about anything you may require.




HILLS TV AERIAL



### MULTI-METERS

- UNIVERSITY
- FLUKE

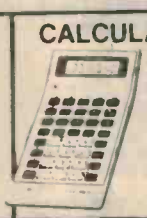

### CALCULATORS

- CASIO
- HEWLETT PACKARD
- TEXAS INST.



### SOLDERING TOOLS

- WELLER
- ROYEL

## RADIO DESPATCH SERVICE


869 George St., Sydney NSW 2000 (Near Harris St.)

Tel. 211 0816  
211 0191

Open: Mon-Fri 8.15am to 5.30pm  
Thursday night late shopping till 8.30pm Sat 8am to 11.45am

"QUALITY COMES FIRST" has been our trading principle for many years. This enables us to give you the best in service and the best in products...ensuring durability in what you buy and your own guaranteed satisfaction.

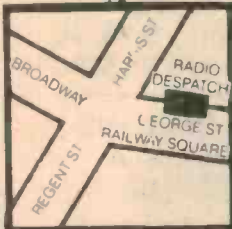**MAIL ORDERS TO RADIO DESPATCH SERVICE**  
869 George St., Sydney 2000 Tel. (02) 211 0191 • 211 0816



## CHRISTMAS SPECIAL OFFERS!

### PLUG ADAPTORS

You might need them today or tomorrow! A must for every HOBBYIST!

CAT. NO.	PLUG/SOCKET/ADAPTOR	UNIT PRICE
PA0010	3.5mm plug/6.5mm socket	\$ 1.20
PA0030	6.5mm plug/RCA socket	\$ 1.20
PA0040	RCA plug/3.5mm socket	\$ 1.40
PA0050	RCA plug/6.5mm socket	\$ 1.40
PA0060	3.5mm plug/RCA socket	\$ 1.20
PA0080	3.5mm stereo P/6.5mm st.S.	\$ 1.60
PA0100	3.5mm mono P./3.5mm st.S.	\$ 1.20
PA0130	2.5mm S./3.5mm socket	\$ 1.30
PA0140	RCA socket/RCA socket	\$ 1.10
PA0090	6.5mm st.plug/3.5mm st.S.	\$ 1.60

CHRISTMAS ADAPTORS BAG SPECIAL 10 \$13.20

**FOR ONLY \$10.00 INCLUDING POST & PACK RING FOR OTHER ADAPTORS/PLUGS/SOCKETS.**

**PT2209** TV antenna INPUT SELECTOR between computer/game or 75 ohm TV antenna. WAS \$5.40  
**NOW \$4.50 ea.**

**PA3005** Aust. plug to USA/European socket will suit most overseas hi-fi & equipment.  
**ONLY \$1.60 each.**

### NEW - FIRST TIME OFFERED TOP QUALITY HIGH PERFORMANCE PCB RELAYS

#### SPECIFICATION:

Contact material: Silver (Cadmium Oxide added on SR4011)  
Contact resistance: less than 50mΩ

Insulation resistance: more than 100M at DC500V  
Mechanical life: more than 10 million times  
Electrical life: more than 100,000 times

Cat. No.	SR4001*	SR4003*	SR4011
Operating power	12V/30ma	12V/37.5ma	12V/60ma
Contact Capacity (resistive)	SPDT	DPDT	SPDT
Price:	\$2.95	\$3.95	\$5.95
<b>This month only</b>	\$2.65	\$3.65	\$5.60
10 up	\$2.50	\$3.50	\$5.40

Other operating voltage available at quantities

mount directly on to 14 pin IC sockets

**Numerical keyboards, 12 & 16 keys, ideal for Alarm, combination lock etc.**

**MEMBRANE KEYBOARDS 4, 12, 16 and any other combinations. Full price details in November ETI '83.**

We stock over 300 EA & ETI circuit boards, ALTONICS kits and some fully imported kits including the ECHO & REVERBERATION AMPLIFIER KIT (\$158.00) and a STEREO PRE-AMP & GRAPHIC EQUALISER KIT (\$144.20). Full details on EA November '83 issue.



MAIL ORDER ADD POST & PACK CHARGES				
under \$ 25	\$2.00	\$50 —	\$100	\$4.50
\$25 — \$ 50	\$3.00	over	\$100	\$6.00

HI-COM UNITRONICS INTERNATIONAL PTY. LTD.  
Shop 7, 45 President Ave., CARINGBAH NSW 2229  
MAIL ORDER: P.O. Box 20, SYLVANIA NSW 2224  
PHONE: (02)524-7878







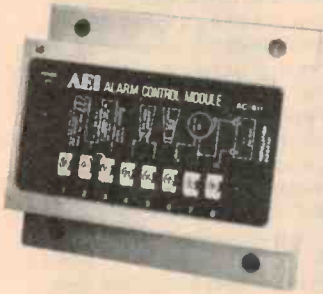
## ALARM CONTROL MODULE

EASY TO INSTALL ★ BUILT IN SIREN DRIVER — DIRECTLY DRIVES LOW COST 8 OHM HORN SPEAKERS, SIREN HORNS AND MECHANICAL BELLS ★ LOW POWER 12V DC OPERATION.



The AC-811 is a low cost professional burglary protection system which detects the presence of an intruder who breaks into your home, office or business. The system also allows connection of emergency panic buttons, wall vibration switches, smoke and heat sensors, as well as freezing or flooding detectors to form a complete protection system.

EXIT / ENTRY DELAY  
BOTH N/C AND N/O CONTACTS  
**Ideal for homes, offices, factories, shops, caravans, any area requiring protection.**

S5042. Only **\$39.50**

## DELUXE ABS INSTRUMENT CASE

Case color light grey front-rear panels black. Our superb new instrument case will give your projects the professional appearance they deserve.




- ★ Internal mounting posts enable a wide combination of PCB's, Transformers, etc. to be accommodated (screws supplied).
  - ★ PCB guide rails provided internally allow vertical PCB positioning to several locations.
  - ★ Removable front and rear panels. Attractive textured finish one side and plain the reverse side. (Enables direct engraving, silk screen printing etc. to plain side.)
  - ★ Great for test instruments and other high grade projects.
- Overall Size: 200W x 160D x 70mmH

HO480..... only **\$13.50** ..... 10 UP \$11.50

**OEM'S — Manufacturers — Bulk Users:** Your product will look like it's straight out of "Hewlett Packard's" factory with this brilliant low cost case. Contact our wholesale Department for Bulk Prices.
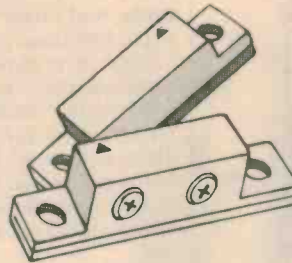
## FULLY ENCAPSULATED REED SWITCH & MAGNET SETS



Powerful Magnet  
Self-Adhesive or Screw Mount.

N/C Reed & Magnet  
S5055..... **\$2.50**  
10 up..... **\$2.10**

N/O Reed & Magnet  
S5056..... **\$2.95**  
10 up..... **\$2.75**

## LOW COST WEATHERPROOF HORN SPEAKER

5 WATT 8 OHM  
Fully weatherproof. New unique voice coil construction ensures high dependability on full drive. Suitable for PA intercom and security systems etc.

C2010..... **\$9.50**  
10 Up..... **\$8.90**



## WEATHER PROOF SIREN HORN

12V DC operated — Deafening Siren Wall. Super handy for audio signalling, security systems etc. Current drain 500MA approx. Completely weatherproof. Attractive off-white PVC finish.

S5058..... **\$22.50**  
10 Up..... **\$20.00**



# ALTRONICS

105 STIRLING ST. PERTH — FOR INSTANT SERVICE

**008 999 007** TOLL FREE

**(09) 328 1599** PERTH METRO AREA & AFTER HOURS RECORDED SERVICE

All Mail Orders: Box 8280, Stirling St, Perth WA 6000.

### ALTRONICS RESELLERS

Please note that resellers may not have all the items advertised in stock, and as resellers have to bear the cost of freight, prices may be slightly higher than advertised. ALTRONICS reseller prices should however represent a considerable saving over our competitors' prices.

#### VICTORIA

**CITY**  
All Electronic  
Components..... 662 3506  
Ellstronics..... 602 3499  
MaGraths  
Electronics..... 347 1122

**SUBURBAN**  
**BENTLEIGH**  
Absolute Electronics 557 3971  
**BOX HILL SOUTH**  
Eastern  
Communications..... 288 3107

**CHELTENHAM**  
Talking Electronics 550 2388  
**FOOTSCRAY**  
Acron Electronics 689 1911  
**SOUTH CROYDON**  
Truscott Electronics..... 723 3860

**COUNTRY**  
**BENDIGO**  
Lindrea & Johnson..... 41 1411  
**MILDURA**  
Electronic and  
Digital Services..... 23 3380  
**SHEPPARTON**  
GV Electronics..... 21 8866  
**WODUNGA**  
A & M Electronics..... 24 4588

#### QUEENSLAND

**CITY**  
Delsound P/L..... 229 6155  
**SUBURBAN**  
**BIRKDALE**  
Wholesale Sound  
Accessories..... 207 2502  
**FORTITUDE VALLEY**  
St. Lucia Electronics..... 52 3547  
**PADDINGTON**  
ECO Technics..... 369 1474  
**SALISBURY**  
Colourview Wholesale 275 3188  
**SLACKS CREEK**  
David Hall Electronics..... 208 8808

**COUNTRY**  
**CAIRNS**  
Thompson Instrument  
Services..... 51 2404  
**GLADSTONE**  
Purley Electronics..... 72 4321  
**IPSWICH**  
P & P Electronics..... 281 8001  
**NAMBOUR**  
Nambour Electronics..... 41 1604  
**PALM BEACH**  
The Electronics Centre..... 34 1248  
**ROCKHAMPTON**  
Purley Electronics..... 2 1058  
**TOOWOOMBA**  
Hunts Electronics..... 32 9677  
**TOWNSVILLE**  
Soles..... 72 2015

#### WESTERN AUSTRALIA

**COUNTRY**  
**ALBANY**  
BP Electronics..... 41 2681  
**ESPERANCE**  
Esperance  
Communications..... 71 3344  
**GERALDTON**  
Geraldton TV and  
Radio..... 21 2777  
**KALGOORLIE**  
Todays Electronics..... 21 5212  
**MANDURAH**  
Kentronics..... 35 3227  
**WYALKATCHEM**  
D & J Pease..... 81 1132

#### NT

**DARWIN**  
Radio Parts Darwin..... 81 8508  
Ventronics..... 81 3491  
**ALICE SPRINGS**  
Ascom Electronics..... 52 1713  
Farmer Electronics..... 52 2967

#### TASMANIA

**CITY**  
D & I Agencies..... 23 2842  
**GEORGE HARVEY**  
Hobart..... 34 2233  
Launceston..... 31 6533

Phone toll free 6am - 8pm (EST) for personal service, or take advantage of our 24 Hour 7 day p/week Bankcard phone order service. Give your name address with postcode, phone number, bankcard number and expiry date then your order — and presto your order will be processed and back to you in a flash. — Please nominate Jetservice if you want overnight delivery.

**\$2.50 DELIVERY AUSTRALIA WIDE** We process your order the day received and despatch via Australia Post. Allow approx. 7 days from day you post order to when you receive goods. Weight limited 10kgs.

**\$4.50 DELIVERY AUSTRALIA WIDE** We process your order day received and despatch via Jetservice for delivery next day.

**BANKCARD HOLDERS CAN PHONE ORDERS UP TO 8PM (EST) FOR NEXT DAY DELIVERY — SOUNDS INCREDIBLE DOESN'T IT?** Alright you cynics just try us! Weight limit 3.3kgs. Jetservice cannot deliver to P.O. box numbers (Australia Post would have a fit).

**\$10.00 HEAVY HEAVY SERVICE — AUSTRALIA WIDE** All orders over 10kgs must travel on the heavy service, that is — road express. Delivery time 7 days average.

#### SOUTH AUSTRALIA

**CITY**  
ADN Electronics..... 212 5505  
Protronics..... 212 3111  
**SUBURBAN**  
**CHRISTIES BEACH**  
Force Electronics..... 382 3366  
**ELIZABETH GROVE**  
A.E. Cooling..... 255 2249  
**KESWICK**  
Freeway Electric  
Wholesalers..... 297 2033  
**PROSPECT**  
Jensen Electronics..... 269 4744

**COUNTRY**  
**PORT PIRIE**  
G.F. & J.A. Pointon..... 32 5141  
**ACT**  
**CITY**  
Electronic  
Components..... 80 4654  
Sentronics..... 54 8334

#### NEW SOUTH WALES

**CITY**  
Avtek Electronics..... 267 8777  
David Reid Electronics 267 1385  
Electronic Agencies..... 29 2098  
Jaycar..... 264 6688  
Radio Despatch..... 211 0191

**SUBURBAN**  
**CONCORD**  
Electronic Agencies..... 745 3077  
**DEE WHY**  
David Ryall  
Electronics..... 982 7500  
**ENFIELD**  
Avtek..... 745 2122  
**LEWISHAM**  
PrePak Electronics..... 569 9770  
**MATTRAVILLE**  
Creative Electronics..... 666 4000

**COUNTRY**  
**ALBURY**  
Webb's Electronics..... 25 4066  
**BATHURST**  
Sound of Music..... 31 4421

**BROKEN HILL**  
Crystal TV..... 4803  
**COFFS HARBOUR**  
Coffs Harbour  
Electronics..... 52 5684  
**GOSFORD**  
Tomorrows  
Electronics..... 24 7246  
**KURRI KURRI**  
Kurri Electronics..... 37 2141  
**NEWCASTLE**  
D.G.E. Systems..... 69 1625  
George Brown & Co..... 69 6399  
**NOWRA**  
Vimcom Electronics..... 21 4011  
**PENRITH**  
Acorn Electronics..... 21 2409  
**PORT MACQUARIE**  
Hall of Electronics..... 83 7440  
**RICHMOND**  
Vector Electronics..... 78 4277  
**TOUKLEY**  
TES Electronics..... 96 4144  
**WINDANG**  
Madjenk Electronics..... 96 5066

RESELLERS WANTED IN ALL AREAS (Including WA).

Phone: STEVE WROBLEWSKI (09) 381 7233 for details.



## Logic troubleshooting

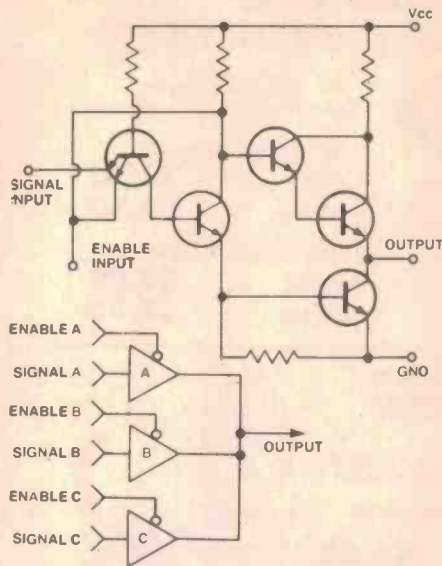


Figure 11. The internal circuitry of a 'tri-state' driver is shown above. The output can be high, low or open-circuit. Outputs are generally wired in parallel, as in the wired-AND circuit. ▲

A now widely used logic type, known as 'tri-state' logic, is a development of this idea. It is found extensively in microprocessor equipment. It is particularly used in *bussed* systems where a multitude of devices might share a common, multi-track buss. Figure 11a shows the general internal circuitry of tri-state logic. The output can be high, low or (virtually) open circuit. The control input determines whether the output is 'enabled' (i.e. operative) or not. The outputs of tri-state logic are wired in parallel, sharing the same line. Only one driver is enabled at a time. It operates in a similar fashion to the wired-AND, the difference being that an 'enable' signal *must* be present for a particular gate's output to be active, otherwise the outputs remain in the open state.

### Tools

There are two fundamental classes of tools employed in logic troubleshooting — 'stimulators' and 'indicators'. A stimulator is nothing more than a relatively simple pulse signal generator that is used to 'stimulate' sections of a faulty circuit into action. Hence the generic name. However, they are often called simply 'pulsers'. An indicator is just that — a device that will indicate the state of a point in a digital circuit, whether it's high, low, sitting at a bad level or pulsing. Generally a LED or other light indicator is used to signal the condition, some makes using several, coloured indicators.

There are two types of indicators — the *contact* type, where a connection is actually made to the circuit, and the *non-contact* type which picks up currents flowing in the circuit interconnections (generally called 'current tracers').

For user convenience, these tools are generally built into handheld, pen-sized cases with a sharp 'probe' point at the business end. Hence they are generally known as probes — *pulsers probes* for the stimulators, *logic probes* for the indicators (because they

indicate logic states). Actually, the use of the word 'probe' here is a misnomer. A probe is in fact a blunt instrument. Examine a logic probe, and except for the current tracer type you'll find they have sharp points!

Since it is necessary to observe dynamic signal activity, as well as the static levels, logic probes usually have pulse stretching circuitry that can detect pulses as narrow as 10 ns and stretch them so that a readily visible blink can be seen. Thus if a low signal pulses high, the logic probe will blink 'on'. If a high signal pulses low, the probe will blink 'off'.

With some logic probes, a pulse memory may be provided. This enables the probe to monitor a signal line for single shot or low frequency pulses over extended periods of time. If a pulse occurs, this will be indicated by the device, which will remain 'on' until reset by the user.

The existence of a pulse train is indicated by flashing the lamp indicator at a constant rate (typically 10 Hz) when a pulse train is present.

Thus a logic probe enables you to view static (high or low) logic levels, single-shot pulses and pulse trains. Automatic threshold detection is generally included as it eliminates the need to determine repeatedly whether a signal is above or below the threshold, and can be employed to show open-circuit conditions also. A TTL/CMOS switch is a necessity so that a probe can be used on both device families. Some makes work on both families, without a switch.

Current tracer logic probes require no contact with the circuit at all. At the business end of a current tracer probe is a small magnetic pickup, generally consisting of a coil wound on a tiny core which has a split, permitting any external field to induce currents into the winding. Of necessity, it works on pulse (ac) signals, detecting *current change*, not dc levels. Pulses are stretched so that the display, usually a LED, can be easily seen. Sensitivity can be arranged so that the current tracer will detect the current it takes to charge the gate input capacitance of CMOS devices.

Current tracers are very useful in sorting out 'stuck' nodes, particularly where there are many elements common to the node and too few ways to isolate the one bad component. It can be done, too, without cutting pc board tracks or lifting IC pins. They are also very useful in tracing signals on multi-layer boards.

### Poke & peek

The mainstay of all digital troubleshooting is stimulus-response testing. It is necessary to apply a signal and observe the response to determine if the device is operating properly. As was pointed out earlier, this can sometimes be very difficult to do in TTL circuitry.

A logic pulse provides the solution. It is used to inject into the circuit a single pulse of proper amplitude and polarity — *forcing* something to happen. If the node happens to be low, it will be pulsed high, and if high, it will be pulsed low.

Generally, logic pulsers are capable of supplying both continuous pulse trains and single-shot pulses.

A logic pulser used in conjunction with a current tracer probe is particularly useful in tracing supply rail short circuits and stuck nodes having many common elements.

These tools are useful in troubleshooting both sequential logic circuits (counter, timer and simple control systems, etc) and parallel bit circuitry (microprocessor systems, etc). However, in parallel systems which are partially working it becomes necessary to see the simultaneous action of many lines or nodes, and a more complex technique, called *signature analysis*, is necessary. A signature analyser is the appropriate tool here, and they come in many forms. Signature analysis, though, is a whole subject in itself and we'll have to leave that to another time.

### Techniques

Your first 'port of call' should *always* be the power supply, particularly in the case of total collapse. If the power supply itself proves OK, but the rails on the pc board show a volt or less, then shorted rails should be suspected. If the supply rails are healthy, then the very next step is to attempt to narrow down the malfunctioning area as much as possible by examining the observable characteristics of the failure. Try to localise it to a circuit section or to as few sections as possible. Then you can proceed to eliminate circuit components step by step by looking for improper key signals between circuits — which is where the logic probe and current tracer come into their own. Table 1 details the general run of faults and how to detect them using the stimulus-response technique.

Dependence upon a well-written service manual is the key to this phase of troubleshooting. Isolating a failure to a single circuit requires knowledge of the instrument or system and its operating characteristics. A well-written manual will indicate key signals to be observed. The logic probe will provide a rapid means of observing the presence of these signals.

Once a failure has been isolated to a single circuit, the tools described can be used to observe the effect of the failure on circuit operation and to locate the failure to its cause (either an IC or a fault in the circuit external to the IC).

The logic probe is used to observe the signal activity on inputs and to view the resulting output signals. From this information, a decision can be made as to the proper operation of the IC.

For example, if a clock signal is occurring on a decade counter and the enabling inputs (usually reset lines) are in the enabled state, then the output should be counting. A logic probe will allow the clock and enabling inputs to be observed, and, if pulse activity is indicated on the outputs, then the IC can be assumed to be operating properly.

As stated before, usually it is not necessary to see the actual timing of the output signals, since ICs fail catastrophically. The occurrence of pulse activity is often enough indication of proper operation.

When more detailed study is desired, or when input signal activity is missing, the logic pulser can be used to inject input sig-



**TABLE 1.**

FAULT	INDICATOR	STIMULUS	TEST METHOD
Shorted node	Current tracer	Pulsar or circuit signals(1)	<ul style="list-style-type: none"> <li>• Pulse node</li> <li>• Follow current pulses to short</li> </ul>
Stuck data buss	Current tracer	Pulsar or circuit signals(1)	<ul style="list-style-type: none"> <li>• Pulse buss line</li> <li>• Trace current to device holding the buss line in a stuck condition.</li> </ul>
Signal line short to Vcc or ground	Logic probe and/or current tracer	Pulsar	<ul style="list-style-type: none"> <li>• Pulse and probe test point simultaneously</li> <li>• Short to Vcc or ground cannot be overridden by pulsing</li> <li>• Pulse test point, and follow current pulses to the short with tracer</li> </ul>
Vcc to ground short	Current tracer	Pulsar	<ul style="list-style-type: none"> <li>• Remove power from test circuit</li> <li>• Disconnect electrolytic bypass capacitors</li> <li>• Pulse across Vcc and ground</li> <li>• Trace current to fault</li> </ul>
Suspected internally open IC	Logic probe	Pulsar or circuit signals(1)	<ul style="list-style-type: none"> <li>• Pulse device input</li> <li>• Probe output for response</li> </ul>
Solder bridge	Current tracer	Pulsar or circuit signals(1)	<ul style="list-style-type: none"> <li>• Pulse suspect line(s)</li> <li>• Trace current pulses to the fault (Light goes out when solder bridge passed)</li> </ul>

1. Use the pulser to provide stimulus, or use normal circuit signals, whichever is most convenient.

nals, and the probe used to monitor the response. This technique is especially good when testing gates and other combinatorial devices. A logic pulser can be used to cause the inputs to go to a state which will cause a change in the output state.

For example, a three-input NAND gate which has high, low, low inputs will have a high output. By pulsing the two low inputs high using a logic pulser, the output will pulse low, and can be detected by a logic probe. This then indicates that the IC is operating properly.

A logic pulser is also valuable for replacing the clock in a digital circuit, thus allowing the circuit to be single-stepped while the logic probe is used to observe the changes in the circuit's state.


The first step might be called the 'mapping' step, since the effect is to map out the problem areas for further investigation. It is important to do a complete 'mapping' of the circuit before proceeding to analyse each of the indicated failures. Prematurely studying a fault can result in overlooking faults which cause multiple failures, such as shorts between two nodes. This often leads to the needless replacement of a good IC and much wasted time. With a complete trouble-area 'map' you can begin to determine the type and cause of the failures. This is done by systematically eliminating the possible failures, as discussed earlier.

The first failure to test for is an open bond in the IC driving the failed node (the Figure 4 problem). A logic probe provides a quick and accurate test for this failure. If the output bond is open, then the node will float to a bad level. By probing the node, the logic probe will quickly indicate a bad level. If a bad level is indicated, then the IC driving the node should be replaced and retested.

If the node is not a bad level, then a test for a short to Vcc or ground should be made next (the Figure 6 problem). This is best done using a logic pulser and current tracer. The problem is to determine if the driver is dead, or if a shorted input is clamping the node to a fixed value.

Use a logic probe and pulser to test the node's logic state and to see if the state can be changed (shorts to Vcc or ground cannot be

**Figure 12. Tracing a supply rail short.**

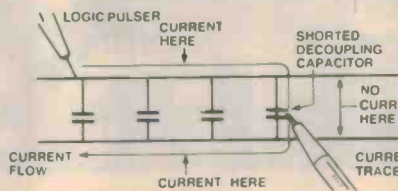


Use the probe and pulser to test the node's logic state and to see if the state can be changed (shorts to Vcc or ground cannot be overridden by pulsing). By pulsing the node you can follow the current directly to the faulty input using a current tracer (Figure 13).


If the node is shorted to Vcc or ground there are two possible causes. The first is a short in the circuit external to the ICs and the other is a short internal to one of the ICs attached to the node. The external short should be detected by an examination of the circuit. If no external short is found, then the cause is equally likely to be any one of the ICs attached to the node. The only suggestion that can be made (based on experience) is to first replace the IC driving the node, and if that does not solve the problem try each of the other ICs individually until the short is eliminated. (It might be noted that on occasion analogue components such as resistors or capacitors attached to the node have shorted.)

If the node is not shorted to Vcc or ground, nor is it an open output bond, then we should look for a short between two nodes. This can be done in one of two ways. First the logic pulser can be used to pulse the failing node being studied, and the logic probe can be used to observe each of the remaining failing nodes. If a short exists between the node being studied and one of the other failing nodes, then the pulser will cause the node being probed to change state (i.e. the probe will detect a pulse). To ensure that a short exists, the probe and pulser should be reversed and the test made again.

If the failure is a short there are two possible causes. The most likely is a problem in the circuit external to the ICs. This can be detected by physically examining the circuit, but shorts are not always obvious if only

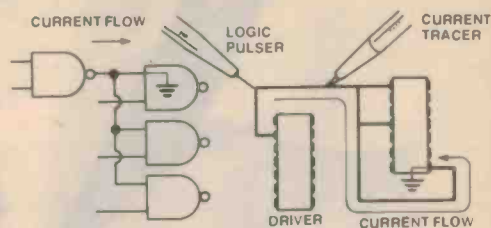

**Figure 13. Tracing a stuck node.**

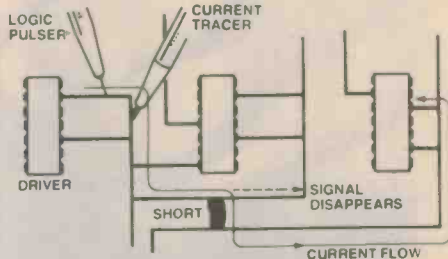

**Figure 14. Tracing a track short.**

traced down to an area. A current tracer is best to pinpoint a short between tracks by tracing current from the pulser. When the short is passed, the signal disappears (see Figure 14).

If the two nodes which are shorted are common to one IC, then the failure must be internal to that IC (the Figure 7 problem). If after examining the circuit no short can be found external to the IC, then the IC should be replaced.

If the failure is not a short between two nodes, then there are only two possibilities left. They are that the failure is an open input bond or a failure of the internal circuitry of the IC (Figures 5 and 8 problem). In either case, this IC should now be replaced. Thus by systematically eliminating the IC failures, the cause can be located.


An important step at any point where an IC is replaced is the retesting of the circuit. If the testing again indicates a failure, then more study of the problem must be made with the knowledge that the failure is not in the IC that has just been replaced.

An open track on the pc board (the Figure 9 problem) is best located with a logic probe, using either circuit signals or a pulser to provide the stimulus. The logic probe provides a rapid means of not only detecting but also physically locating the open.

Since an open signal path allows the input to the 'right' of the open to float to a bad level, the logic probe can be used to test the input of each IC for a bad level. Once an input floating at a bad level is detected, the logic probe can be used to follow the circuit back from the input looking for the open. This can be done because the circuit to the 'left' of the open will be a good logic level (either high, low or pulsing), while the circuit to the 'right' will be a bad level, precisely locating the open. The open can then be repaired and the circuit tested.

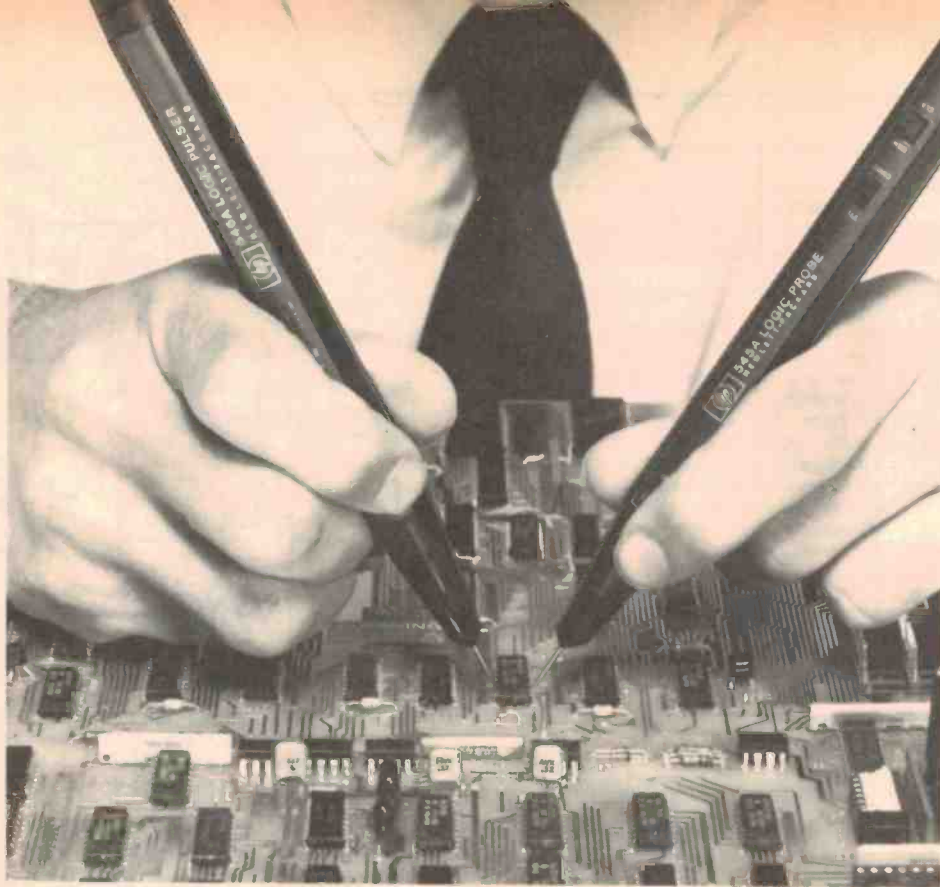This systematic elimination of possible failures in digital circuits by the use of such special tools will ensure a rapid and accurate repair. Because these instruments provide a digital solution to the digital problem, improvements in servicing time of at least 4:1 are easily achieved over the use of analogue instruments.






# Hewlett-Packard IC Troubleshooters to show it like it is:



1

2

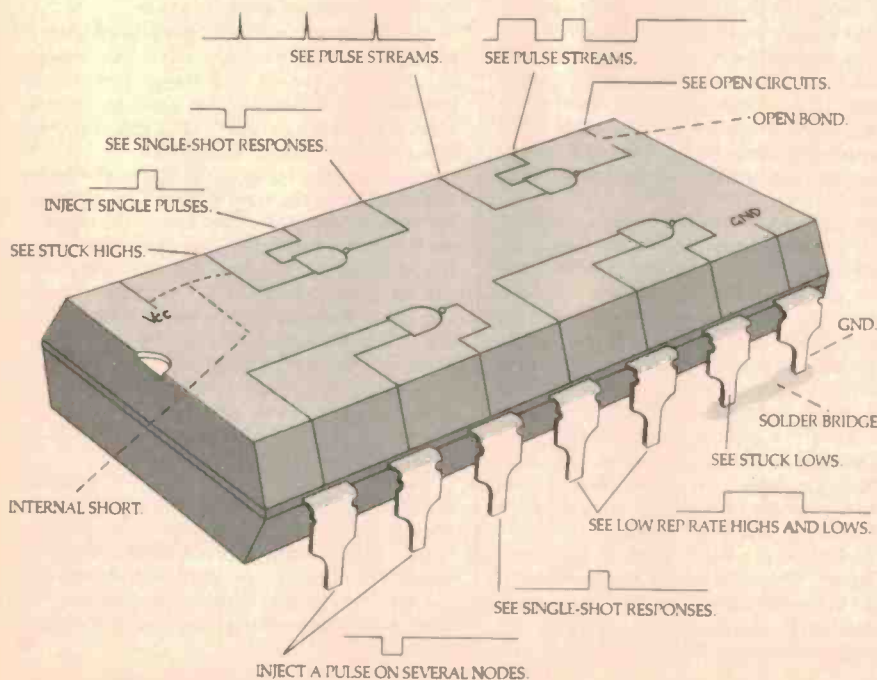

**The Model 545A Multi-Family Probe.** See logic highs, lows, bad levels and open circuits with logic probes. Capture one-shot pulses. See pulse streams.

**The Model 546A Pulser.** Inject a pulse or pulses into a circuit without trace cutting or unsoldering. Automatically drives low nodes high or high nodes low. The Model 546A Logic Pulser creates your programmed number of logic pulses and has multi-family capability.



**ETI**  
**READER OFFER**  
**20% OFF! SAVE UP TO \$197**

3

**The kit puts it all together.** The HP5024A Kit puts the logic tool kit all together in a convenient carrying case. In addition to the Multi-Family Probe and Pulser, the kit contains the model 547A Current Tracer. The 547A will trace current when you reach

a node where the logic probes cannot work because the node is stuck low and you don't know which bus component of many is faulty. No pc board trace cutting or good component removal is necessary.

**INSPECTION.**

You are welcome to inspect the Logic Troubleshooters during office hours at the following locations:

**SYDNEY**

ETI Offices,  
 Federal Publishing Company,  
 140 Joynton Avenue, Waterloo.  
 OR  
 Hewlett-Packard Australia Limited,  
 17-23 Talevera Rd., North Ryde.

**MELBOURNE**

Federal Publishing Company,  
 150 Lonsdale St., Melbourne.

**BRISBANE**

Hewlett-Packard Australia Limited,  
 10-14 Payne Rd., The Gap.

**ADELAIDE**

Hewlett-Packard Australia Limited,  
 153 Greenhill Rd., Parkside.

**PERTH**

Hewlett-Packard Australia Limited,  
 261 Stirling H'way, Claremont.

**HOW TO ORDER YOUR TROUBLESHOOTER.**

Fill out the coupon here and enclose a cheque, bank cheque or money order for the amount required made out to HEWLETT-PACKARD AUSTRALIA LIMITED. If you are not paying sales tax, please quote your sales tax number on the coupon or use an official order. Schools, colleges, etc. should enclose a tax declaration on official letterhead. The completed coupon, together with your payment should be sent to:

Hewlett-Packard Troubleshooters Offer  
 C/- ETI,  
 140 Joynton Avenue, Waterloo, N.S.W. 2017

**Delivery.** Hewlett-Packard will endeavour to deliver your Troubleshooters in less than four (4) weeks from receipt of payment.

**Nothing else quite measures up.**



**HEWLETT  
 PACKARD**

**ORDER NOW! OFFER CLOSING JANUARY 31, 1984**

Please supply, on the terms outlined in this offer and the Terms and Conditions of Sale of Hewlett-Packard Australia Limited.

Qty. \_\_\_\_\_ HP545A Logic Probe @\$139 (normally \$176 ) each.  
 Qty. \_\_\_\_\_ HP546A Logic Pulser @\$215 (normally \$275 ) each.  
 Qty. \_\_\_\_\_ HP5024A Logic Kit @\$790 (normally \$987 ) each.

Sales Tax No. \_\_\_\_\_  
 (if applicable)

All prices excluding tax. Add 16% if applicable

Name \_\_\_\_\_ Position \_\_\_\_\_

I enclose \$ \_\_\_\_\_ total

Address \_\_\_\_\_

Postcode \_\_\_\_\_

Cheque or Money Order No. \_\_\_\_\_ Signature \_\_\_\_\_

Send completed coupon with payment to: Hewlett-Packard Troubleshooters Offer.


C/- ETI,  
 140 Joynton Avenue, Waterloo, N.S.W. 2017





**DICK'S PRICES  
MAKE GIVING  
A PLEASURE!**

LATEST  
TECHNOLOGY

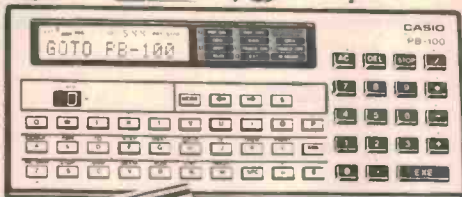

**Hand Held Computer**  
Casio quality - Dick Smith price

A brand new hand held computer from one of the world's leading manufacturers. The Casio PB100 - learn as you go computer with VLSI CPU equivalent to 150,000 transistors! 544 program steps, 94 data memories (expandable), 5 x 7 dot matrix 12 digit display and a standard 53 key keyboard. Cat X-5110

**NEW MODEL ONLY**  
**\$79.95**

**'WEDGE' CAR SPEAKERS**

Latest wedge style speakers for the ultimate in car hi-fi sound. 3 way system, 4 ohms impedance (suits most car systems), handle a huge 50 watts max. Ideal for vans, trucks, 4WD's etc. too - real home hi-fi quality as you drive. Cat A-7082

**\$79.50 WAS \$89.50**  
pr



\$40

**240V CANNON PLUG & SOCKET**

Mains rated! Don't take chances with mains! If you haven't got room for normal 3 pin plugs and sockets, these genuine Cannon brand fittings are the safest.

Line Plug Cat P-1627 **\$6.95**  
Panel Socket Cat P-1630 **\$5.95**



**NEW Balanced Mic Cable Complete**

Huge 20m length of quality mic cable fitted with Cannon-type plugs & sockets. Intended for balanced type microphones, ideal for other types too. Cat W-1100



**\$29.95**

**TOP VALUE**

**Bosch Digitimer**

Unbelievable! Microprocessor controlled flexibility for all timing and switching functions - like burglar alarms, industrial processors, even swimming pool filters! Cat Y-1121



**DON'T MISS OUT \$99.50**  
IT'S JUST



**ADHESIVE BACKED**

**Invisible Speaker Cable System**

Huge scoop purchase of unique home speaker wiring system. Under carpet, wallpaper, etc - 10m cable tape plus four plugs and sockets. Cat W-1288

Below manufacturers cost! **ONLY \$2.95**

**Extra high grade Ferrite Rods**

Keep a couple of these in the junk box! Small (40 mm) lengths top grade ferrite, suitable for a huge range of inductors, chokes, etc. Cat K-6036 **60c ea.**

**NEW**

**1K RAM PACK** Expands the PB100's memory to 1K, programming to 1,568 steps. A must for the serious user. Cat X-5112

**AND NOW FOR FUN WAY 3!**

**10 exciting new projects using Integrated Circuits**

At last - the latest addition to our Incredibly popular 'Fun Way' series. And this one gets right into the big time using both digital and linear integrated circuits in a variety of projects. Yes, there are still projects for the beginner - and there are projects for the more advanced. And we're sure you'll find the projects even more satisfying, more fun to both build and use. PLUS, like the other 'Fun Way' books, special cut-out labels to give your projects a real professional finish.

- Over 100 pages
- 10 brand new and exciting projects to build and use.
- Every project fully explained with printed circuit layouts etc.
- Especially written to suit all ages and experience levels. Schools, Re-sellers etc.

We offer discounts to quantity (above 10) purchasers. Call our wholesale division on (02) 888 3200.

**HURRY! Get your copy now!**  
**Makes an ideal Xmas gift!** **ONLY \$6.95**

Cat B-2610

**Kits from a low \$7.95**

**Minder** (Cat K-2660) A multi-purpose project for the car. **\$7.95**

**Two-Up** (Cat K-2661) Electronic version of Australia's national game! (Beats trying to find King George pennies!) **\$9.95**

**Lil Pokey** (Cat K-2662) You can't lose your shirt on this game! **\$19.95**

**Nocturnal Stridulus Gryllidae**

(Cat K-2663) In English that means Cricket, and no not the game either! Hide it in a dark room and it starts chirping, turn the light on and it stops. It's infuriating! **\$9.95**

**OTHER KITS INCLUDE:**

Mini Colour Organ (K-2664 \$12.95); Combination Time Lock Switch (K-2666 \$12.95); Binary Bingo (K-2668 \$19.95); Mini Synthesiser (K-2669 \$19.95); and more!

Educational & Safe

**ONLY \$6.95**

**DICK SMITH'S FUN WAY INTO ELECTRONICS Volume 3**

**INTEGRATED CIRCUITS**

- 10 exciting projects including a mini Synthesizer, Night Cricket, Stereoph. Amplifier and Combination Time & Lock Switch.
- Masses of information - you can't go wrong!
- PLUS pre-printed labels to give your projects a professional finish.





A PRO  
SOLDER  
STATION AT A  
HOBBYIST'S PRICE!

## Dick Smith SOLDER STATION



**\$69<sup>00</sup>**

Serious about soldering? Do it the right way - with a temperature controlled soldering iron! Dick Smith Auto Temp!

• Fully variable temperature control (approx 200C to 500C) • Lightweight iron • Instruction manual • Full Energy Authority approval Cat T-2000

### YOU SAVE SOLDER

1.25mm (18g) 200 grams Cat N-1619 **\$5<sup>50</sup>** 0.71mm (22g) 200 grams Cat N-1623 **\$5<sup>50</sup>**




The last word in  
pocket calculators

## CASIO FX-602 P ADVANCED PROGRAMMABLE CALCULATOR

88 memories - 512 steps - full memory retention. An amazing 33 parenthetical levels, up to 9 sub-routines and nestings. Cat Q-3110

NEW LOW  
PRICE!

NOW ONLY **\$139** WAS \$199.00

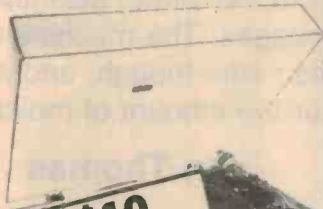

SAVE \$10

## Semi Automatic Belt Drive Turntable

WAS \$169

Complete with base, perspex lid and quality magnetic cartridge. Belt drive for superb speed control, low 0.06% WRMS wow and flutter. Suits all modern hi fi amplifiers.

Cat A-3080 **\$159<sup>00</sup>**  
ONLY

NEW  
IMPROVED  
MODEL



## Microwave Detector

An alarm sensor that doesn't rely on opening doors, broken beams etc. It traps thieves in the act - as soon as they move, they're gone!! A brilliant 21st century alarm system that's almost impossible to beat. Cat L-5000

ONLY **\$95<sup>00</sup>**

# DICK SMITH Electronics

NSW ALBURY 21 8399  
AUBURN 648 0558  
BANKST. SQ. 707 4888  
BLAKEHURST 546 7744  
BONDI JUNCT. 387 1444  
BROOKVALE 93 0441  
CHULLORA 642 8922  
GORE HILL 439 5311  
GOSFORD 25 0235  
HORNSBY 477 6633  
LIVERPOOL 600 9888  
NORTH RYDE 88 3855  
PARRAMATTA 689 2188

PENRITH 32 3400  
RAILWAY SQ. 211 3777  
SYDNEY 27 5051  
SYDNEY 267 9111  
TAMWORTH 66 1961  
TIGHE HILL 61 1896  
WOLLONGONG 28 3800  
ACT Fyshwick 80 4344  
VIC COBURG 383 4455  
FRANKSTON 783 9144  
GEELONG 78 6766  
MELBOURNE 67 9834  
RICHMOND 428 1614

SPRINGVALE 547 0522  
QLD BRISBANE 229 9377  
BURANDA 391 6233  
CHERMSIDE 359 6255  
TOOWOOMBA 38 4300  
TOWNSVILLE 72 5722  
SA ADELAIDE 212 1962  
DARLINGTON 298 8977  
ENFIELD 260 6088  
WA CANNINGTON 451 8666  
PERTH 328 6944  
PERTH 321 4357  
TAS HOBART 31 0800

# The story of a most incredible Journey!

## Dick Smith's Solo helicopter flight The Earth Beneath Me

In a word... magnificent! See the world as it's never been seen before in this day-by-day account of one of the aviation events of our time. From the scorching deserts of the Middle East to the frozen wastes of the Arctic, Dick has captured every incredible moment for all to share and enjoy. And even more, a 'guided tour' of Dick's helicopter VH-DIK, showing all the controls, what they do - even how to fly it! A beautifully hard-bound edition for years of enjoyment - you must read 'The Earth Beneath Me'. Cat B-9105

A wonderful collector's item and  
great Xmas gift idea! Only  
WAS \$24.95

**\$19<sup>95</sup>**

Also Available on Video Cassette

Contains three one hour commercial documentaries of the flight, as seen on John Laws' World. Available in either VHS or Beta formats ONLY AVAILABLE THROUGH MAIL ORDER. Pay by cheque, postal order or bankcard FREE POSTAGE AND PACKAGING. Send \$69.50 to PO Box 321 North Ryde NSW 2113.



AS  
SEEN ON  
JOHN LAWS'  
WORLD

## SPEEDY PHONE/BANKCARD ORDER SERVICE

Just phone your order and Bankcard details - it's so simple!

(02) 888 2105

ORDER ONLY ON THIS NUMBER  
ENQUIRIES: (02) 888 3200

HEAD OFFICE AND MAIL ORDER CENTER:  
P.O. Box 321, NORTH RYDE, NSW 2113.  
TEL. (02) 888 3200

### POST & PACKING CHARGES

ORDER VALUE	CHARGE	ORDER VALUE	CHARGE
\$5.00-\$9.99	\$2.00	\$50.00-\$99.99	\$5.00
\$10.00-\$24.99	\$3.00	\$100.00 or more	\$6.50
\$25.00-\$49.99	\$4.00		

Charges are for goods sent by post in Australia only. Not apply overseas or road freight.



Terms available to  
approved applicants  
through...



DSE/A653/PA1





# An electronic sling psychrometer

‘What in the name of Beelzebub’s left horn is a sling psychrometer?’  
I hear you ask. The very name itself conjures up images of smug mid-Victorian (era, not state) scientists airing their knowledge of classical languages. The machine is nowhere near as complicated as its name though, and all it does is measure humidity, or the amount of moisture in the air.

Ian Thomas

TO MOST OF US humidity is a rather poorly understood quantity and we are only aware of it when we are hot and sticky and our cold tinny leaves wet rings all over the place. The measurement and control of humidity, however, has a host of applications in industry and research as well as at home. For example the growing of a lot of exotic plants requires that the humidity where they are raised be kept under some sort of control.

Before we go on to the actual construction of the project and how to use it, it is interesting to look at the phenomenon of humidity itself and how it is defined and measured.

## Humidity

Humidity is simply the amount of water vapour that is present in the air, but this seemingly straightforward quantity can be


measured in many ways. Probably the easiest to understand is *Absolute Humidity* which is simply the amount of water vapour, expressed as either a mass or volume, that is contained in a given amount of air. This can be expressed as parts per million on a volume basis or mass basis, or grams per kg of air (or, in all probability in days gone by, decigrains per cubic rood — please don’t ask me to define it). These units are nice and easy to understand but don’t directly relate to the subjective feeling of how comfortable or uncomfortable we feel.

Another way of expressing Absolute Humidity is to measure the Dewpoint of the air. Air at a given temperature is only capable of holding so much water and the hotter the air the more water it will hold. If air that contains a certain amount of water is cooled to below its Dewpoint then the water will come out as a liquid (fog, rain or

dew) or solid (snow or frost). The relationship between the Dewpoint temperature and absolute humidity is very well known and tables are published giving the exact amount of water vapour that is present for a given Dewpoint.

Measuring the Dewpoint is an accurate way of determining humidity but it’s a bit clumsy as you have to have a method of cooling the air to see when mist or frost starts to form. This is usually done by cooling a mirrored surface in the air until it starts to mist over, then measuring the temperature of the surface. Another way is to expand the air to cool it and measuring the temperature of the air when fog starts to form. Either way is ‘fiddly’ at best and can give rather variable answers depending on how things were set up.

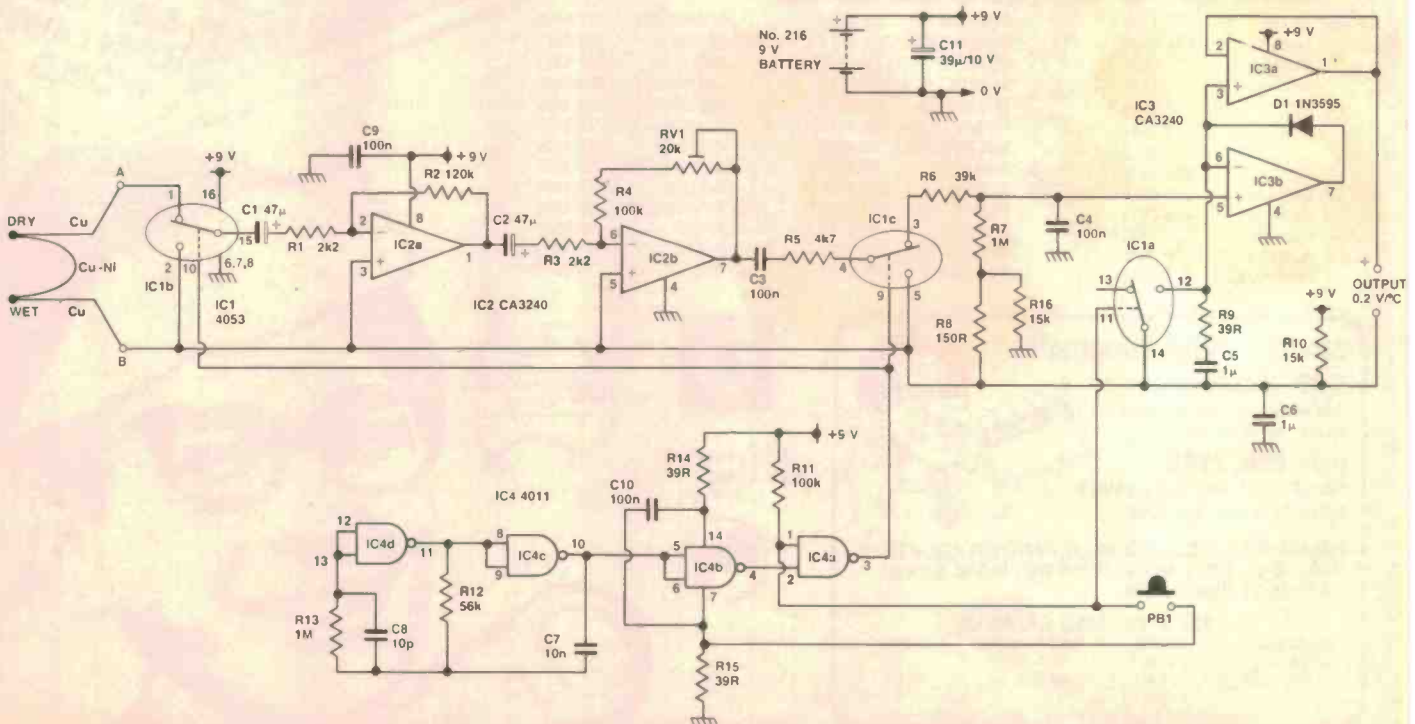By far the most common way of expressing humidity is *Relative Humidity*





and this is how you see it on the weather forecasts. Relative Humidity is the ratio of the amount of water vapour present in a given volume of air to the amount of water vapour that would be present if the air had its Dewpoint at the same temperature. It shows how much water is in the air as a ratio of how much water the air will carry before mist starts to form and is a very good indication of how we feel (sticky and uncomfortable means close to 100% and sore throat and eyes hurting means close to 0%). The measurement of relative humidity can be done in many ways also, depending on whether the readings are wanted

continuously for control purposes or just spot readings. This brings us to the project for this article; the psychrometer.

We're all aware that if a surface is wet and air is blown over it then the surface is cooled (the fact is drawn to our attention when we get out of a swimming pool on a windy day).

This principle is used to make measurements of Relative Humidity.

Normally, two mercury-in-glass thermometers are used with one thermometer's bulb surrounded in water-soaked cotton.

The two thermometers are mounted in a 'sling' so they can be whirled around

in the air to create a draught.

The dry bulb thermometer records the ambient air temperature and the temperature difference between the two thermometers gives the so-called Wet Bulb Depression or the degree of cooling caused by the water on the wet bulb. Using these two figures it is possible to look up the Relative Humidity from tables.

The whole assemblage of thermometers, sling, water reservoir and wick to cover the wet bulb, is called a *slings psychrometer* and so long as the wick is kept clean and pure water is used, will give reliable and accurate humidity readings.

## — HOW IT WORKS — ETI-1502 —

The circuit can be divided into six separate stages which will be described separately. They are:

(1) The temperature difference sensing thermocouple. Thermocouples have been used for many years and can give very accurate temperature measurements. Even today they are still used to calibrate semiconductor diffusion furnaces where the temperature must be correct to about  $\frac{1}{4}^{\circ}\text{C}$  at  $1100^{\circ}\text{C}$ , a remarkable feat of control. Our needs are not quite so dramatic but as the voltages out of a thermocouple are very small, care must be taken.

The couple used is copper-constantan one which gives, for small temperature differences, about 38.5 microvolts per  $^{\circ}\text{C}$ . Constantan is an alloy of 60% copper and 40% nickel and the copper constantan couple is normally used between  $-200^{\circ}\text{C}$  and  $+300^{\circ}\text{C}$ . The thermocouple consists of two pieces of copper wire which are soldered onto the printed circuit board close together. The two free ends of the wires are connected together by a piece of constantan wire. About five millimeters of the copper and constantan wire are twisted together tightly to form the actual couple and may be soldered if the same solder is used for both junctions. The junction whose copper side is connected to the low voltage terminal is the cold junction (in our case the junction which is covered with wet cotton wool) and the junction whose copper side is connected to the amplifier input is the hot junction.

(2) The input chopper. This is a simple CMOS analogue switch which, in this case, is a CD4053BE. The integrated circuit consists of three separate single-pole double-throw semiconductor switches, all of which have separate control inputs. The thermocouple is connected to one input of the switch and the other input is connected to a reference voltage which is common to the whole circuit. The control line for the switch is driven from a 500 Hz square wave so that the output from the switch is a 500 Hz square wave with an amplitude equal to the thermocouple voltage (plus a few bonus spikes from the switching).

(3) The ac amplifier. The low level signal from the input chopper is then amplified up through two stages using common or garden operational amplifiers. C1 ensures that the first stage of gain has unity gain for dc and the two resistors R1 and R2 set the gain for ac signals. It is about 54.5 for the stage, which is still well below the open loop gain for the op-amp at the chopping frequency so the gain will be stable with temperature and

power supply voltage. The output from the first stage is ac-coupled to the second stage through C2 and the second stage gain is set by R3, R4 and RV1. RV1 is used to calibrate the gain of the whole amplifier so the output of the complete circuit is  $0.2 \text{ volts}/^{\circ}\text{C}$ . The output of the amplifier is a square wave whose peak-to-peak voltage corresponds to the dc voltage we want.

(4) The synchronous switch for dc recovery. In order to convert the square wave out of the amplifier into a dc voltage again a second section of the CMOS analogue switch is used. The ac signal from the amplifier is coupled through a capacitor C3 (and resistor R5 to prevent any large currents from flowing and upsetting the op-amp output) to the 'pole' of the analogue switch. One switched output from the switch is connected to the common reference voltage. The other output is connected to a simple RC low pass filter formed by R6 and C4. The control line for the analogue switch is driven from the same signal that drives the input chopper. When the input chopper connects the reference voltage to the amplifier input the amplifier output is also connected to the same voltage and C3 is charged to any residual dc voltages that may exist due to op-amp offsets.

When the input is connected to the thermocouple input the amplifier output is switched to R6 and charges C4 to the amplified thermocouple voltage. The overall effect is that the output analogue switch acts as a very accurate fullwave rectifier and converts the ac output from the amplifier back into a dc voltage referred to the common reference voltage.

Because the two amplifier stages together have a gain of about 2500 as well as amplifying the thermocouple voltage, a lot of noise and switching spikes are amplified as well. R6 and C4 filter these out so the dc signal on C4 is an accurate representation of the dc input. Resistors R7 and R8 form a bleed so that when the whole circuit is reset C4 is discharged to the reference voltage (more about this later).

(5) The output peak hold circuit. The dc voltage on C4 will vary as the temperature changes on the thermocouple input and, as we want to measure the largest voltage we can generate by whirling the whole thing around in the air, we need a way of capturing the peak output so it can be measured at leisure. This is done by IC3 and C5.

The varying dc voltage is connected to the non-inverting input of the op-amp, pin 5 and feedback is connected around the op-amp through a low leakage diode, D1. When the non-inverting input (pin 5) moves more

positive the op-amp output also moves positive and charges C5 to the same voltage. If pin 5 moves slightly more negative, then the output also swings negative and reverse biases the diode. In fact, the op-amp output immediately swings to ground as the diode breaks the feedback loop. Capacitor C5 therefore holds exactly the peak dc voltage that is applied to the non-inverting input to the op-amp. R9 is in series with C5 so, once again, the op-amp output does not have to drive directly onto a large capacitor (if it is left out the op-amp will oscillate when the diode is turned on and the peak detector accuracy falls to pieces). The second op-amp of IC3 is used as a very high impedance input unity gain buffer.

The peak dc voltage is only held as a charge on a capacitor so, in order to be able to take measurements with any voltmeter, the capacitor voltage must be buffered. It is very important to use FET-input op-amps for this part of the circuit and MOSFET input op-amps such as the RCA CA3240 are about the best cheap ones available.


As the voltage on C5 can only go more positive, a way is needed to reset the peak detector when the reading has been taken. The last section of the analogue switch is used as a reset circuit. The common input to the analogue switch is connected to the reference voltage and the input which is off. When the control line is high it is connected to C5. The control line is pulled high by R11 and the analogue switch is off when measurements are being taken. When the reset switch, SW1 is operated C5 is shorted to the reference voltage and at the same time the filter capacitor C4 is allowed to discharge through R7 and R16. The oscillator driving the two synchronous switches is also disabled by SW1 so C4 will not be charged through R6 when the circuit is being reset.

(6) The switch drive oscillator. The 500 Hz square wave which drives the two synchronous analogue switches is generated by a simple CMOS oscillator formed by IC4, R12 and C7. This circuit is used so commonly that it doesn't really need to be described. Two extra gates, the last of which is also used to gate off the output when the circuit is being reset, square up the drive so the analogue switches are switched cleanly. The whole chopper stabilised amplifier is not sensitive to drive mark-space ratio so no attempt is made to ensure that the drive output is symmetric.

Resistors R14 and R15, together with C10, filter the supply for IC4, preventing supply rail switching pulses from being coupled into the rest of the circuitry.



# Project 1502

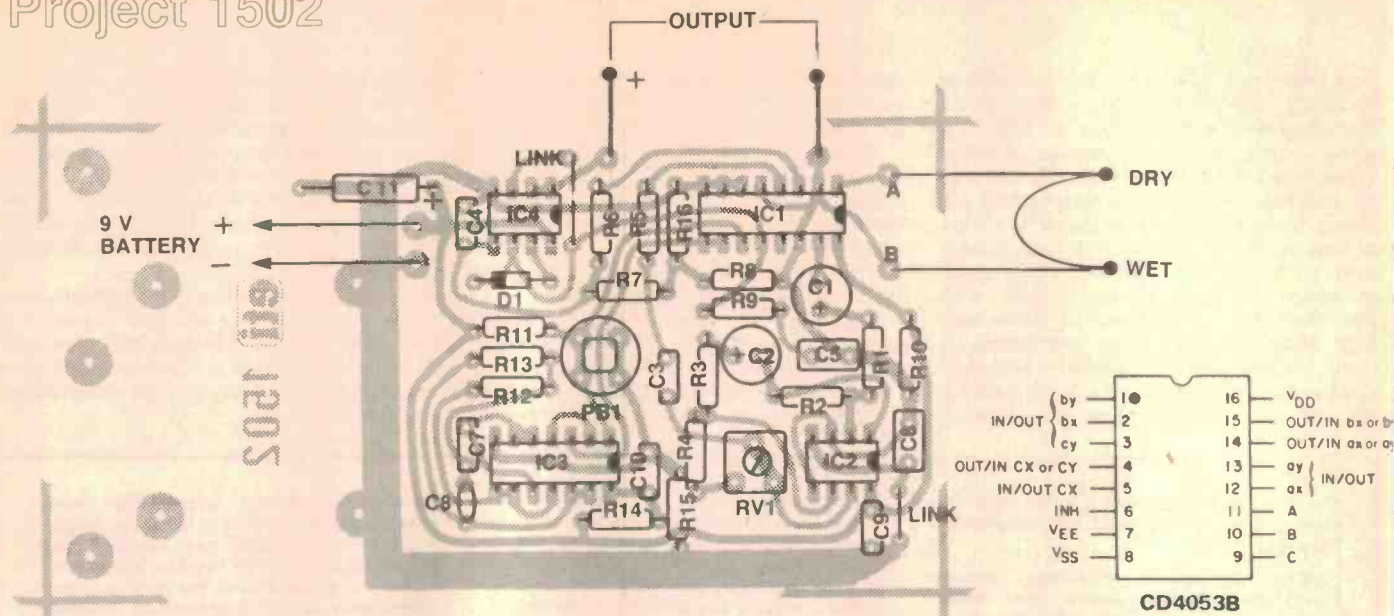

Component overlay. Assembly is pretty straightforward. Watch the orientation of the 'polarised' components — diodes, ICs and electrolytic capacitors.

## Doing it with wires

The project reads wet bulb depression directly by using a copper-constantan thermocouple to measure the temperature difference between ambient and a junction covered with wet cotton. For the temperature differences we're interested in, the potential difference generated by the thermocouple is a linear function of temperature and is approximately 38.5 microvolts per °C. This gives us our first problem as amplifiers which have input dc offset voltages much less than one microvolt are pretty thin on the ground and usually cost a bomb. The answer to this is to use a chopper-stabilised amplifier so all the gain is produced for ac signals only where offsets are no problem (see How It Works).

The next problem was that the thermocouple responds very fast to temperature changes and stopping whirling the device around and attaching the probes to the amplifier output terminals gave the thermocouple time to change its reading considerably. A simple peak hold circuit had to be incorporated to keep the peak value of the output voltage until it could be read. Even with this peak hold included it was necessary to use a low leakage diode in the peak charging feedback path as diodes such as the old favourite 1N914A have a reverse leakage of about 20 nA at room temperature and this caused the output temperature reading to drift by about 0.1°C per second. (This may not sound like much but it was nigh on impossible to connect the DVM probes and get a good reading in time). The 1N3595 that I used has a reverse leakage of only 1 nA and made things much more manageable but unfortunately the better performance costs — these diodes are not cheap.


## Construction

If you are using the artwork supplied then building up the project will give no trouble.

First assemble all resistors and capacitors. This is a good general rule when using CMOS integrated circuits as it makes it harder to zap the IC with static charge. Then insert the integrated circuits, making very sure that they are all in the right way (everyone harps on this but its an embarrassingly easy mistake to make as I can personally testify). The orientation of the two coupling electrolytic capacitors, C1 and C2, is not important as the only dc voltage that ever appears across them is the offset voltage of the operational amplifiers and this voltage is very small and can be of either polarity. It's bending the rules a bit to reverse bias an electro but the 10 mV or so doesn't really matter. The polarity of the power supply filter capacitor C8 *does* matter though, so take care.

After all the components except the pushbutton PB1 have been inserted and neatly soldered, it is necessary to thoroughly clean and deflux the board. Parts of the circuit (mainly the node connecting IC3 pins 3 and 6 to C5, D1 and IC1 pin 12) are very sensitive to leakage and if dirt or flux is left on the board you will waste the money you spent on the 1N3595. The best way to thoroughly deflux the board is to use an el-cheapo 25 mm paint brush, whose bristles have been cut to about 10 mm long, and acetone solvent. Both can be purchased at the local hardware store.

Tip some of the acetone out into a shallow glass dish (if you use a plastic dish its bottom will immediately dissolve and you will have acetone everywhere dissolving everything in sight — it's a very good solvent!) and thoroughly wet the short bristles of the brush. Scrub the soldered side of the board and immediately mop the board dry with a clean rag or paper towel. The board must be patted dry as if you try to wipe it the towel will catch on all the cropped component leads but it is important that the board be dried off completely and quickly as if the acetone is left to dry on the

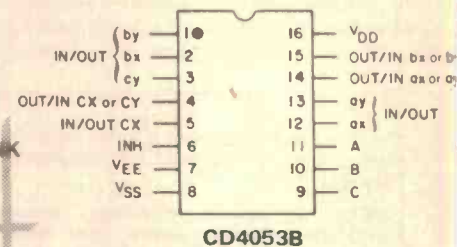

## PARTS LIST — ETI-1502


Resistors	
R1, R3	all 1/2W, 5% unless noted
R2	2k20, 0.4W, 2% metal film
R4	120k 0.4W, 2% metal film
R5	100k 0.4W, 2% metal film
R6	4k7
R7, R13	39k
R8	150R
R9, R14, R15	39R
R10	15k
R11	100k
R12	56k
RV1	20k cermet trimpot, Allen-Bradley type E or similar.
Capacitors	
C1, C2	47µ/10 V electro, radial leads
C3, 4, 9, 10	100n/63 V metallised film, Wima type RS-21 or similar
C5, C6	1µ/50 V metallised film, Wima type RS-21 or similar
C7	10n/63 V metallised film, Wima type RS-21 or similar
C8	10p ceramic
C11	39µ/10 V electro, axial leads
Semiconductors	
D1	1N3595
IC1	4053B
IC2, IC3	CA3240E
IC4	4011B

**Miscellaneous**  
 ETI-1502 pc board; length of copper-constantan thermocouple (about 150 mm); Spintate nut driver (with 4" or 5" shaft); small cable clamps (5 mm i.d. or to suit Spintate shaft); battery snap and battery clamp for No. 216 9 V battery; No. 216 9 V battery, piece of cotton wool.

board the dissolved flux will be deposited on the board again and can be seen as a white deposit, usually in the spaces between tracks and IC pins. Repeat the scrubbing and mopping dry until the board appears completely clean when the acetone is dried off completely (this usually takes several applications).



What a whizzer! The completed Sling Psychrometer. Some of the capacitors (C3, 4, 5, 6, 7, 9 and 10) are small, low voltage, metallised film types with 5 mm pins spacing, not run-of-the-mill 'greencaps'. See Shoparound in this issue for supplier details. The copper-constantin sensors should be secured to the board at points A and B with a generous 'glob' of a plastic sealing compound such as 'Silastic'.

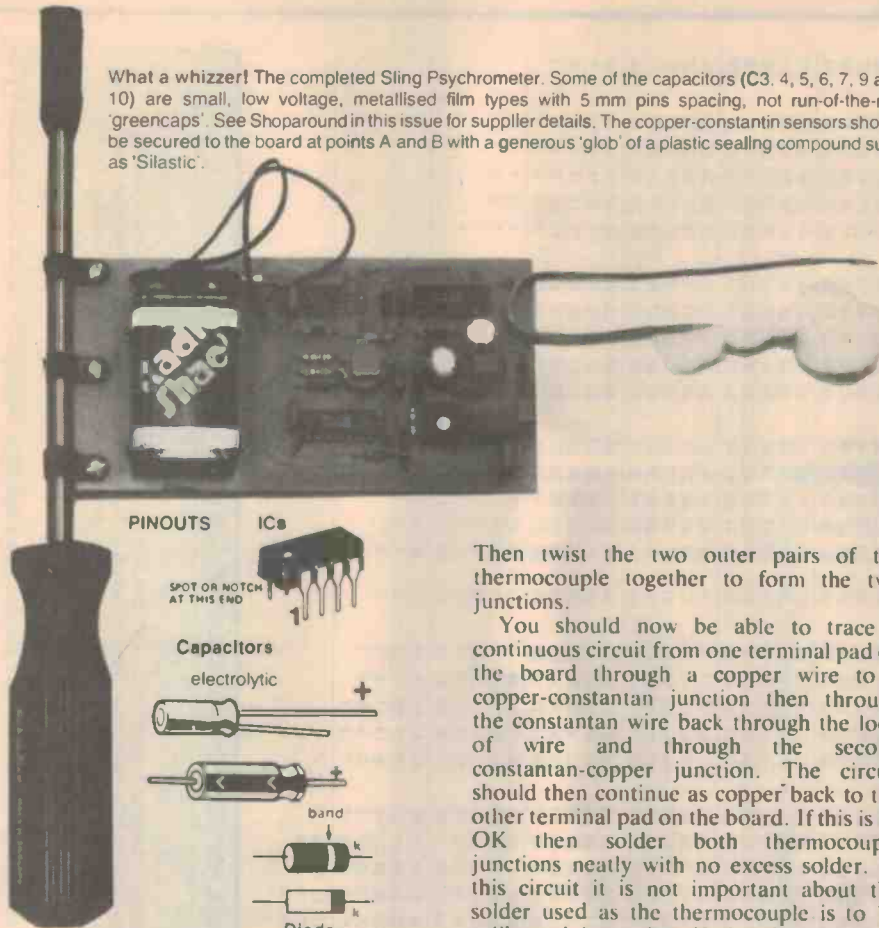

Do this out in the open or in a well-ventilated room. Acetone is flammable, so do not smoke or have anyone smoking nearby while you're doing it and keep away from possible arcs and sparks. Avoid getting the acetone on your skin.

The pushbutton can be soldered in when defluxing is finished. If you insert the switch before cleaning the board there is a very good chance that some flux will be deposited in the contacts and give unreliable operation.

The next step is to attach the thermocouple wire. I used standard copper-constantan insulated thermocouple wire that is available from most scientific supply houses (i.e.: Selby Scientific). Only about 150 mm of the pair is needed for the psychrometer, but if you want to use the project for remote temperature sensing as discussed later, much longer runs can be attached with no ill effects.

To prepare the short thermocouple as shown in the photograph, first take about 150 mm of the pair and bare both ends of both wires for about 10 mm. Then lay the pair flat on the table and very carefully trace the copper wire back to the centre of the pair. Separate the two insulated wires for about 10 to 15 mm from the centre and cut the copper wire (if you cut the constantan wire you've ruined it). Bare the two ends of the copper wire that you've just cut for about 5 mm and solder them into the printed circuit board. The insulated constantan wire should form a neat loop between the two terminated copper wires.

Then twist the two outer pairs of the thermocouple together to form the two junctions.

You should now be able to trace a continuous circuit from one terminal pad on the board through a copper wire to a copper-constantan junction then through the constantan wire back through the loop of wire and through the second constantan-copper junction. The circuit should then continue as copper back to the other terminal pad on the board. If this is all OK then solder both thermocouple junctions neatly with no excess solder. In this circuit it is not important about the solder used as the thermocouple is to be calibrated later, but if the thermocouple was to be used directly into a meter then care would have to be taken to use the same solder for both junctions.

All that remains now is to solder in the battery clip-lead and the circuit is ready for test and calibration.

### Amplifier calibration

To calibrate the thermocouple-amplifier combination you will need two kitchen drinking glasses, some ice from the freezer and a reasonably good thermometer. While thermometers expounding the virtues of Bert's Big Ends or Clives Clutches are all good and fine in their place they really aren't accurate enough here. I bought a  $-10^{\circ}$  to  $+510^{\circ}\text{C}$  mercury-in-glass thermometer from Selby Scientific at North Ryde (Sydney, NSW) but most scientific supply houses stock them (see your local 'phone book). The thermometer is also used when actual humidity readings are taken and you will find it quite useful round the house as well, and I found the \$8.40 really well spent.

Calibration is done by establishing an exactly known temperature difference between the two junctions of the thermocouple and adjusting RV1 until the voltage difference at the output terminals reads correctly. The cold junction is set to  $0^{\circ}\text{C}$  by immersing it in water with plenty of ice in it and the hot junction is immersed in ordinary tap water.

The temperature of the hot junction must be between  $18^{\circ}\text{C}$  and  $20^{\circ}\text{C}$  to give accurate calibration and if the water out of the tap is

hotter or colder than this a judicious admixture of ice or hot water will be necessary. Fill one of the tumblers with ice from the freezer then fill it up with water to create a  $0^{\circ}\text{C}$  reference and fill the other glass with water mixed as described. If you have no faith you can check that the ice-water mixture is really at  $0^{\circ}\text{C}$  (alternatively, this could be considered to be a check on your thermometer). Then measure the temperature of the warmer water and note it down. Make sure that the thermometer is left in the water long enough for the reading to stabilise (60 seconds or so is long enough).

Connect the battery to the amplifier and, as a quick check to make sure that all is working, your DVM to the output terminals. If you hold the hot junction with your fingers the output voltage should climb to about 0.5 V in a few seconds (unless it's a very hot day in which case your fingers may actually be cooler than ambient). This test just measures the temperature difference between your fingers and the air temperature and ensures that the amplifier is working correctly.

When the hot junction (the junction whose copper side connects to pin 1 of IC1) is released the output voltage should very slowly drift towards zero. In the prototype, the drift was about 1 mV every two or three seconds but if you used a 1N914 in place of the 1N3595 the drift will probably be about 20 mV per second.

After you are satisfied that the amplifier and peak hold circuit are working OK, press PBI and make sure that the output voltage goes to zero. There will be a slight residual offset due to the input offset voltages of the two op-amps of IC3 but if the output is within  $\pm 20$  mV of zero all is well.


The final step is to adjust RV1. Place the two tumblers of water that you've prepared close side by side and immerse the hot junction in the warmer water and the cold junction in the iced water. Both junctions should be about 20 mm below the surface. The DVM reading should rapidly climb to about 1.8 to 2.0 volts. Adjust RV1 fully clockwise to set the amplifier to its lowest gain and operate the zero switch for a few seconds to start adjustment from the lowest voltage. Then, slowly adjust the potentiometer until the output voltage equals the thermometer reading ( $2.000$  volts =  $20.00^{\circ}\text{C}$ ). If you overshoot the desired reading and want to come back, then you must operate the zeroing switch after every clockwise adjustment because the peak hold circuit will not allow a gain reduction to be displayed. Make sure that the cold junction is right in the middle of the ice in the tumbler and not at the bottom of the glass as the water at the bottom is probably not at  $0^{\circ}\text{C}$ .

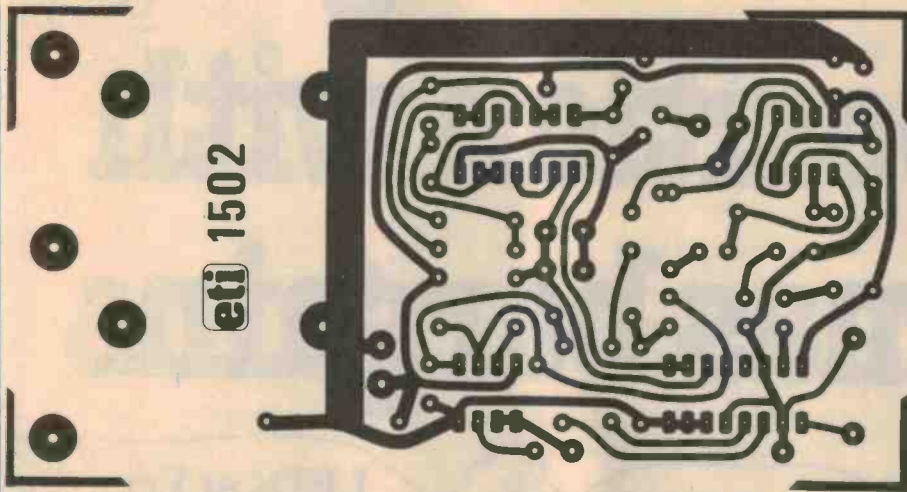It is a good idea to check this adjustment several times as a  $1^{\circ}\text{C}$  error by misplacing the two junctions in the tumblers or incorrectly measuring the temperature of the hot junction is easy to make and gives a 5% error. Once this adjustment is made the psychrometer is ready to be assembled onto its sling handle. ▶









Printed circuit. Full-sized artwork for the printed circuit board.

Tie the battery down to the printed circuit board with twist ties (the things you use to close garbage bags) as firmly as possible as it would be most embarrassing to sling the battery through a window, and mount the whole assembly on a suitable handle. I used a spare 'Spintite' nut driver that I had or you could use a screwdriver but make sure that the tip of the spintite is bigger than the clamps that you use to attach the board to the handle (it would be just as embarrassing to sling the whole lot through a window).

Mount the board to the handle using three 'P' cable clamps and the three holes marked on the board so the board can rotate freely around the shaft of the handle. Wrap a piece of cotton wool around the cold junction of the thermocouple and tie it on securely with cotton thread. It is a good idea to bend the last 5mm of the thermocouple wire back on itself and bury it in the cotton wool to make sure that it remains covered at all times with the wool. You sling psychrometer is now ready to try out.

### Making measurements

In order to take a humidity reading, the first thing to do is wet the cotton wool around the cold junction. Drip tap water on the cotton wool until it is thoroughly wet but not completely dripping. You must be extremely careful not to get any water on the board itself as you've spent a lot of money on low leakage diodes and water would not improve the leakage properties of the board surface one little bit. Allow the wet cotton wool to stand a while to allow the water to reach room temperature, five minutes or so should be enough, then connect the battery and whirl the psychrometer around in the air for 60 seconds or so.

If you had too much water on the cotton wool this will get rid of it most effectively

and at the same time creates the necessary draft over the wet wool to cool the cold junction of the psychrometer. After it has been spun for the required time place the psychrometer on an insulating surface (a formica tabletop for instance) taking great care not to touch the back of the board at all and connect your DVM to the two output terminals.

The *wet bulb depression temperature* can be read off directly by multiplying the volts by 10 and calling them degrees Celcius. Next, measure the actual air temperature with the accurate thermometer used to calibrate the amplifier. Finally, look up the tables given at the end of this article to determine the actual relative humidity.

First use the air temperature to find the correct row in the tables then use the psychrometer reading to find the column which has the actual humidity value. As an example, I took a reading and found that the air temperature was 23.7°C and the wet bulb depression from the psychrometer was 7.63°C (it is interesting to note that the electronic psychrometer is a great deal more accurate than the normal wet and dry bulb so we must round the wet bulb depression reading off to 0.2°C). Rounding the temperature off to the nearest degree gives an ambient temperature of 24°C and rounding the wet bulb depression off gives 7.6°C.

Referring to the tables we have a row of humidity values which start with 49% on the left (wet bulb depression = 7.0°C) and go to 10% for a wet bulb depression of 14.0°C on the right. The fourth value in from the left corresponds to our wet bulb depression of 7.6°C and gives the result of 46%. As is always the case when using tables to work anything out it is not possible to find the exact value, but even so the humidity readings obtained this way are accurate to about 1% (if you calibrated the amplifier accurately!).

### As a thermocouple amplifier

The psychrometer can also be used as a straightforward thermocouple amplifier to measure temperature in differences from ambient temperature. The peak hold function can be left in, or removed in the following way. First remove C5 and R9 then replace D1 with a piece of wire. This converts the op-amp IC3 pins 5,6 and 7 to the simple unity gain buffer and allows the amplifier output to follow temperature differences continuously. The thermocouple wire connected to the amplifier input can be as long as necessary to monitor the desired temperatures, but as there is no input filtering care should be taken to avoid gains hum pickup.

If the wire is very long and you want the reference temperature to be the ambient then it is not necessary to have both thermocouple junctions remote from the amplifier. Simply use a length of copper-constantan wire pair with one end of the pair bared and twisted together to form a junction and the other end of the pair bared and soldered onto the two amplifier input terminals. The terminal where the constantan wire is soldered onto the board becomes the second junction of the thermocouple and temperature differences are measured from the temperature of this connection.

Calibration of the amplifier is a bit more complicated in this case as you can't very well immerse the whole amplifier in a glass of water to establish a reference temperature. I calibrated the setup in the following way. First power up the amplifier and connect the DVM to the output terminals. Make up a 0°C reference again with ice and water in a tumbler as was done to calibrate the psychrometer and immerse the sensing junction in it (once again, make sure that the junction is right in the middle of the ice and not at the bottom of the tumbler). Rest the mercury-in-glass thermometer on the amplifier and leave the whole lot to stabilise for 15 minutes or so. The amplifier should be away from any draughts or direct sunlight as the thermometer is supposed to measure the temperature of the printed circuit board and any outside sources of heat or cold will create temperature gradients which will destroy the accuracy of the reading.

When everything appears to have settled down adjust RV1 until the amplifier output reads the same as the mercury-in-glass thermometer. As the peak hold circuit is no longer functioning you can adjust either way with no trouble. As the sensing junction is at 0°C the temperature difference for the thermocouple is the temperature of the board (and reference junction) directly. If you want to reverse the polarity of the output readings then reverse the two thermocouple wires connected to the amplifier input; both input terminal pads and copper and the amplifier will work just as well.



# Sheridan's sleigh

# the opposition with

# Christmas bargains



## EPROM Price Blowout!!

Top quality EPROMs at rock bottom prices.



2716 EPROM \$4.00 each \$3.70 10+  
 2532 EPROM \$7.00 each \$6.30 10+  
 2732 EPROM \$7.00 each \$6.30 10+  
 2764 EPROM \$11.00 each \$10.00 10+

## Hitachi 2114AP2

Fantastic price on brand new Hitachi 2114AP2. These are low power 200nS devices going for a song!! But stocks are limited so you'll have to be quick.

~~\$1.30~~ 10up **\$1.50**

## Microprocessor Tick Tocks

Enthusiasts, get out your soldering irons. Santa Sheridan has got these amazing OKI MSM5832RS microprocessor controlled clock, calendar ICs in stock. You'll spend hours learning about all its functions. And look at this tiny price.

**only \$8.00**

Fantastic 14 page applications and technical manual: **\$2.00**




Crystal to suit (32.768 kHz) **\$2.00 each**


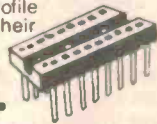
## 14 and 16 pin IC sockets

Never again at these prices. High quality AMP low profile sockets at a fraction of their usual price.



**10 for \$1**  
**100 for \$9**

## Colorburst Crystals

Going for a song!! These crystals are used in many projects and timing circuits. at these prices you can use them for experimenting etc. Solder type 4.43619MHz



Were \$3.00 **only \$2**

## LEDs at Very Light prices!!

Scoop purchase of high quality Stanley 3mm red LEDs. Packs of 200 only at this price!!



**200 for only \$16.00**

## Centronics Plug

This is the most common plug of all on Centronics printers, computers etc. Amphenol type 57/303/60. Most of our opposition are charging around \$18.00 for these connectors. Look at our Knockout Price!!



**only \$9.50**

ONLY 1,000 available

## The Pulsar

## Little Big Board at a Better Price!!

You've seen the specs (or see October ETI for the full article). So you know its fantastic value. Now buy at a better Sheridan price!!



**SAVE**

Kit 1: PC Board, MP7A Monitor PROM, Users Manual and setup sheet. List price is ~~\$149.00~~

**Sheridan Price: \$135.00**

Kit 2: As above but with full component set and LB00T6 boot PROM. List price is ~~\$499.00~~

**\$429.00**

**Sheridan Price:**

## Pushbutton Telephone

We've sold thousands of these superb phones from PYE/TMC. With 10 memories and 'try again' facility its not surprising!! But we're clearing them out at massively reduced prices. You reap the benefit!!



were ~~\$59.00~~ **now \$29.00**  
 50 only. First come, first served!!



# Super Deal on Super Tomcat!

Now you can afford this superb AM/SSB CB radio. With Pearce Simpson quality you know you can trust - the most advanced mobile of its type. Full 40 channel phase locked loop design. Fully approved by D.O.C. Telecom Australia.

Normally ~~\$299~~  
**Sheridan Price:**  
**\$229**



Fill up your sleigh at Sheridans - best prices in Australia



**SAVE**

**SANTA SHERIDAN!**

## Scope PH20 soldering iron

This superb 20W iron is normally \$17.50. We've reduced the price to only:

**\$15<sup>95</sup>**

## Matching STS2 safety stand and sponge

Normally \$15.95  
**\$14<sup>50</sup>**



## Weller WTCPN Soldering Station

The best costs less at Sheridans. Protect valuable components with this low voltage 'closed loop' soldering

iron. Now with redesigned wiper pad, case and quick disconnect for iron.

**only \$75<sup>00</sup> inc. tax**



**SAVE**

## ST-100 Multimeter

These meter features ultra high 100,000ohms/volt sensitivity and a superb 3 1/2" 10uA movement. A mirrored scale ensures reading accuracy and OF position protect the movement during transit.

**Brief Specifications**  
 Ranges: 28 in total  
 DC Voltage: 0-0.5 -5 -50 -100 -250 -500 -1000V  
 AC Voltage: 0-5 -10 -50 -200 -500 -1000V  
 DC Current: 0-10uA -2.5mA -5mA -500mA  
 Resistance: 0-10K -1M -10M -100M  
 Decibels: -20 to 63dB in 6 ranges  
 Accuracy: within 4%  
 Size: 6" x 4 1/4" x 2"

**\$26.00**



normally ~~\$52.00~~

## Mains Line Filters

Cure problems with mains interference to you TV, HiFi or computer with these incredible filters.

Reduces both line to line and line to ground interference dramatically. 3A and 5A types.


Reduced \$1.00 for Xmas!!

**PLF-2V-3RA-501(3A)**

**only \$9.50**

**PLF-2V-5RA-501(5A)**

**only \$10.50**

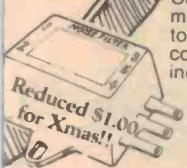

## FAX80 Printer at a knockout price!!

**Only \$429<sup>00</sup> inc. tax!!**

We set the price when it comes to computer printers. And we intend to keep on offering the best deals in Australia. So for Christmas only, we've further reduced the price on the incredible FAX80 printer. Now you can own this superb high resolution/graphics printer with tractor and friction feed, 80 characters per second and detachable print head for the lowest price in Australia. But only at Sheridans!!

**RS232 Interface only \$79.95**  
**Spare ribbons only \$13.00**

**Don't pay \$499**


## Superb FET Meter

Ideal for the hobbyist needing an instrument with a constant high input impedance. A balanced FET amplifier ensures high stability. Both movement and input section are diode protected.

**Brief Specifications:**  
 Input Resistance: 12 megohms on all DC ranges (except 0.3V, 1.2 megohms)  
 DC Voltage : 0.3 1.2, 12, 60, 300, 1200V  
 AC Voltage: 3, 30, 120, 300  
 DC Current: 60uA, 600uA, 600mA  
 Resistance Ranges: RX1, RX100, RX10K, RX1M  
 Accuracy: Within 3%  
 Decibel Scale: -20 to 63dB

**only**

**reduced from \$74.00 \$38.00**

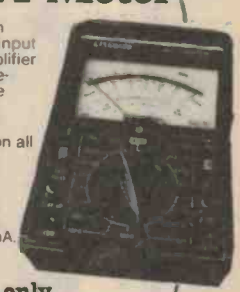

**NB: All Prices include tax**

# SHERIDAN ELECTRONICS

164-166 Redfern St., Redfern NSW 2016  
 Phone (02) 699 6912, (02) 699 5922. Mail Orders to PO Box 229 Redfern NSW 2016

**Trading Hours:**  
 Mon-Fri 9am-5:30pm  
 Thursday 9am-7pm  
 Saturday 9am-12noon

**Credit Cards:** We accept both BankCard and American Express

**Mail Charges:**  
 \$5.00-\$9.99 \$3.50  
 \$10.00-\$24.99 \$4.00  
 \$25.00-\$49.99 \$6.00  
 \$50.00-\$99.99 \$7.00  
 \$100.00 or over \$8.00



**MINIMUM ORDER \$6.00**

We regret we cannot give quantity discounts on credit card purchases



**BANKCARD HOLDERS -  
PHONE YOUR ORDERS  
TOLL FREE!**

**NEXT DAY DELIVERY**

**AUSTWIDE**

**ALTRONICS**


**008-999-007**

**VIA  
JETSERVICE**  
(CAPITAL CITY & SUBURBAN AREAS)

**MICRON SUPER 80**

80 CPS - 80 COLS  
BIT IMAGE GRAPHICS  
FRICTION FEED AND  
ADJUSTABLE SPROCKET FEED

MADE IN JAPAN  
QUALITY

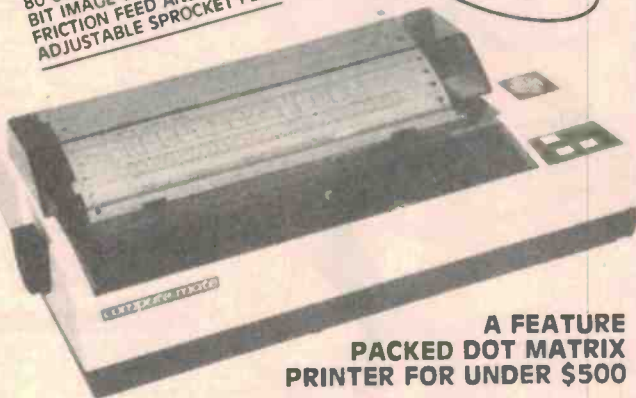

**A FEATURE  
PACKED DOT MATRIX  
PRINTER FOR UNDER \$500**

Your "Super 80" printer will enable you to print letters, reports, graphics generated pictures, etc and importantly for the programmer, Hard Copy of program listings. Operating under software control from any general purpose micro-computer the Super 80 features 13 different print types including emphasized (LETTER QUALITY). Bidirectional print action ensures smooth, quiet operation.

**228 ASCII Characters, Handles 4" to 10" Paper  
STANDARD CENTRONICS INTERFACE**

VALUE PACKED AT D1174..... **\$499.50**  
INTERFACE CABLE TO SUIT MICROBEE D1190..... **\$45.00**  
SPARE RIBBON D1175..... **\$12.50**

ALTRONICS • BANKCARD JETSERVICE DELIVERY NEXT DAY • ALTRONICS

**DC PLUG PACKS**

**AT LAST . . . DIRECT IMPORT  
PRICES ON FULLY APPROVED  
PLUG PACKS**

Great for powering  
small Micro's, TV  
Games, Slot Car  
Sets, etc.

Eliminate the need  
for batteries, when  
testing or operating  
new projects.



**M9000**  
240v AC - 3, 4.5, 6, 7.5, 9,  
12v DC @ 300mA  
ONLY..... **\$14.95**  
4 OR MORE..... **\$13.50**

**M9005**  
240v AC - 6, 9, 12v DC  
@ 500mA  
ONLY..... **\$14.95**  
4 OR MORE..... **\$13.50**

Both Plug packs come with  
Instructions and a 4 way  
multiplug 1.6m lead.

**INSULATED  
TO  
ASC 126**

★

TOP QUALITY  
LINED  
PRINTER  
PAPER  
TRACTOR FEED

AT LAST AT  
AN AFFORDABLE  
PRICE


TO SUIT SUPER 80  
240mm WIDE  
D1160 **\$47.50**  
380mm  
D1165 **\$39.50**

2000 SHEETS  
PER BOX

★

**CENTRONICS  
PLUG**

36 WAY  
D1192  
**\$14.95**

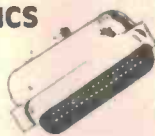

When you buy one of our printers  
you'll need a centronics plug. If you are  
**MICROBEE USER**, have a look at our **IN-  
TERFACE KITS** on the opposing page.

**UK MADE, GOLD PLATED  
D RANGE CONNECTORS  
SAVE 25% ON BULK QUANTITIES!**



	ea.	10 +	25 +
P 0880 DB9 Male 9 Pin	2.50	2.20	1.95
P 0881 DB9 Female 9 Pin	2.95	2.70	2.50
P 0885 DB9 Backshell	2.85	2.50	2.50
P 0890 DB15 Male 15 Pin	2.95	2.50	2.29
P 0891 DB15 Female 15 Pin	3.50	3.00	2.80
P 0895 DB15 Backshell	2.85	2.50	2.50
P 0900 DB25 Male 25 Pin	4.30	3.95	3.60
P 0901 DB25 Female 25 Pin	4.95	4.50	3.98
P 0905 DB25 Backshell	2.85	2.50	2.50

**THE SENSATIONAL  
MICROBEE IC**



**NEW 3.375 MHz  
CLOCK SPEED**

SCREEN FORMAT 64 x 16 OR  
80 x 24 WHILE NETWORKING  
EG. USED AS A TERMINAL



The all new Microbee IC has got to be the  
most value packed ROM based personal  
computer available today. New enhanced  
basic enables 64 x 16 or 80 x 24 screen for-  
mat while networking and the clock speed  
is now a zippy 3.375 MHz and over \$110  
worth of software integrated in ROM i.e.  
the absolutely delightful Wordbee word  
processor package or Editor Assembler

plus all the other exciting Features that  
have made the Microbee famous

D1020..... 16K IC..... **\$499.00**  
D1035..... 32K IC..... **\$599.00**  
ARCADE GAMES, PERSONAL, BUSINESS AND  
EDUCATIONAL APPLICATIONS.

**SOFTWARE**

JUST PHONE OR WRITE & ASK  
WE'LL SEND YOU OUR SOFTWARE CATALOGUE  
HONEYSOFT • MYTEK • DREAMCARDS

FOR DESPATCH P&P CHARGES AND ADDRESS DETAILS PLEASE REFER TO OUR AD. ON PAGE 95







# 'Deluxe' video enhancer features three controls

This simple to build project features three controls for curing video 'image ills' — *floor* which cuts off the low-level noise that causes snow; *ceiling* — which ensures that high-level signals are not enhanced, causing ringing; and *enhancement*, which really 'crisps up' those soggy signals, providing up to 8 dB of boost.

John Power




THIS PROJECT has been designed to team with the ETI-1517 Video Distribution Amplifier (September issue), but can be used 'stand alone' if you wish. It's easy to build, low in cost and effective in use.

The problems one meets with video signals, particularly when recording and replaying, have been explained by Jonathan Scott in 'The ins and outs of video enhancers', in the October issue. This project has been designed to avoid the problems that can arise in trying to compensate for video bandwidth degradation. I have included a 'notch' at the 4.43 MHz colour subcarrier so that it will not be 'enhanced' — to the detriment of the picture! — and have provided controls that set the limits of enhancement so that noise at one extreme, and high-level signals at the other, are not boosted, which can also further degrade a picture.

Many 'economy' video enhancers I've seen simply provide a single control, which sets the level of boost in the 2-5 MHz region. From experience, this is only effective on certain signals which have not suffered much degradation at all. Too many cases occur where you need to have some control of the signal level range over which the boost is applied. Thus, you see some commercial enhancers with a 'gamma' or 'core' control, which is there for just this purpose.


After some experimentation, I hit on a scheme that provided controls to adjust separately the minimum level from which boost is applied and the maximum level beyond which enhancement ceases. The minimum level I have dubbed *floor* and the maximum level control I have dubbed *ceiling*. Their function is obvious from the names. I prefer to work on the KISS theory ('Keep It Simple, Sam') and avoid jargon. Between the floor and ceiling, the amount of boost or enhancement can be varied from none to maximum with a control simply labelled *enhancement*. See? Simple, but 'deluxe'.

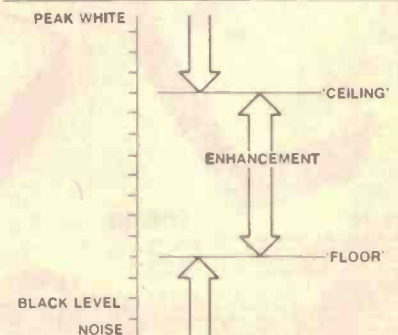I notice that some VCRs have a direct-coupled output which sits at a mean dc level



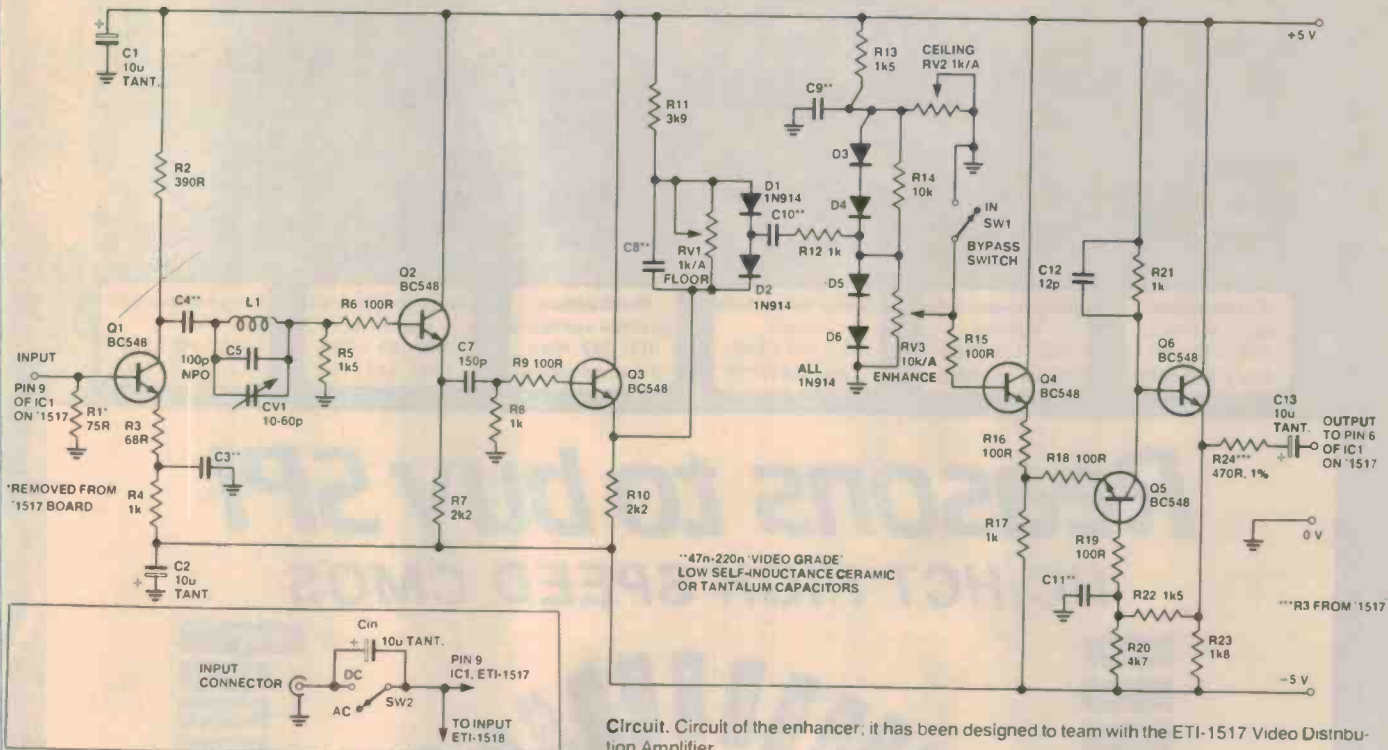Controls. The enhancement control works between the limits set by the floor and ceiling controls.





Circuit. Circuit of the enhancer; it has been designed to team with the ETI-1517 Video Distribution Amplifier.

HOW IT WORKS — ETI-1518

I will assume you are familiar with the operation of the ETI-1517 Video Distribution Amplifier. You will recall that it consisted of a differential amplifier with the signal applied to the non-inverting input and equal value resistors placed from output to inverting input and inverting input to ground, giving a gain of exactly two from input to output before termination loss, and a gain of exactly one after.

The enhancer section of this project takes the input signal, removes the low frequency part of it, inverts it, processes it according to the control settings, then adds it (out of phase) to the original signal by applying it to the inverting input of the differential pair in the '1517. By maintaining the output impedance of the final processing stage at the value of the lower leg of the feedback divider in the '1517 (470R) the original signal path gain remains unchanged.

The effective addition of the processed high frequency content of the signal to the unaltered original is equivalent to boosting that high frequency information, which is enhancing.

Referring now to the circuit of the enhancer section, Q1 is a buffer stage with a gain of -4 approximately. Here the inversion necessary to reverse the eventual inversion of the differential pair is introduced. Q1 is biased in such a manner as to clip off sync pulse tops without saturating. This prevents them being fully enhanced, which is desirable.

It may be necessary to remove dc from the incoming signal to ensure that no video is clipped as well. For this reason, provision to ac couple the whole system is included. Most VCR inputs are expecting only ac coupling, and most outputs are not dc offset, so maintenance of dc levels is not as crucial as it sometimes is in circuits not equipped to 'dc restore' off the sync waveform.

Coil L1 and surrounding components form a 'trap' which excludes from the circuit the colour subcarrier. This should not be enhanced,

so a notch is introduced at 4.43 MHz. The subcarrier thus passes only through the distribution amp and remains unaltered.

Transistor Q2 is a common collector buffer stage, giving a low output impedance for C7/R8, which form a low cut filter which is 3 dB down at 1 MHz. This selects only the high frequencies for further processing. Q3 is another buffer stage to prevent different processing steps interacting. The base decoupling resistors prevent possible buffer instabilities in the face of reactive loading.

Potentiometer RV1 and surrounding components form the floor or gamma processing stage. The aim of this stage is to make it possible to selectively pass higher amplitude signals. The motivation for this is that noise, particularly 'snowy' effects, is predominantly present in the high frequency part of the signal, but needs to be minimally enhanced. The noise is also predominantly lower in amplitude than brightness transitions in the video signal, which it is desirable to enhance. Hence it is possible to apply more enhancement to higher-amplitude components without enhancing noise. This function is sometimes referred to as 'core'. However, I think the label 'floor', for its obvious connection, or 'gamma' (less obvious) are more descriptive of its function.

Potentiometer RV2, plus D3-6 and associated components, provide the reverse function, which I labelled 'ceiling'. This section basically permits the setting of a level above which enhancement is reduced, by smoothly limiting the signal. I am not entirely convinced of the utility of the function, but include it for purists on the theory that winding the control clockwise removes it anyway. The idea behind this process is that the problem when enhancing certain signals is that ringing on full amplitude transitions induces nasty shadow lines; thus there is something to be gained by limiting enhancements of the high end of the amplitude range.

Both floor and ceiling circuits work in a similar way. Diodes, two in the former case and two

pairs in the latter, are subjected to varying forward dc bias conditions.

To proceed further down the signal path (to the right on the circuit diagram), the video signal must get through the diodes in the floor case, and not get shorted out through the diodes in the ceiling case. If the difference between the dc bias present on the diodes and that necessary to make them conduct is larger than the instantaneous signal amplitude, the signal will not pass without attenuation. Of course, the effect is not that sharp, as the levels are chosen to make use of the diodes' turn-on characteristics to produce no gross discontinuities in the waveform.

In the floor circuit, RV1 sets the bias on D1 and D2. Adjusted for maximum resistance, RV1 permits current to flow in the diodes (turning them) on sufficiently to pass all the signal. At zero resistance only signals exceeding about half a volt pass, and then only their high-amplitude parts. These two extremes bound the useful region where mild selectivity of response is applied.

Signals not limited by the ceiling circuit are passed to RV3, which acts as a level control, setting the amount of signal passed back to the differential amplifier and hence the degree of enhancement. Transistors Q4-6 form a dc-coupled amplifier (in the form of a long-tailed pair and an emitter follower) which provides a gain of eight and a low output impedance. C13 and R24 pass the signal out and provide a precise 470 ohm impedance to ground for the feedback signal from distribution amplifiers.

The video amplifier output stage in the '1517 was designed to limit negative-going signals to an amplitude of about a volt. Thus, any gross overshoot on the partially limited sync pulses will be limited at that point. This occurs because the voltage gain is entirely vested in the differential pair, further stages providing only current gain. Q3 in the '1517's differential pair will saturate at a voltage corresponding to an output voltage of -2 V before matching loss.



# The George Brown Electronics Group.

**Protronics**  
SOUTH AUSTRALIA  
(08) 212 3111  
Telex AA88261

**George Brown & Co.**  
VICTORIA  
(03) 419 3355  
Telex AA35886

**George Brown & Co.**  
SYDNEY  
(02) 519 5855  
Telex AA21732

**Protronics**  
WESTERN AUSTRALIA  
(09) 362 1044  
Telex AA93883

**George Brown & Co.**  
NEWCASTLE  
(049) 69 6399  
Telex AA28461

**George Brown & Co.**  
A.C.T.  
(062) 80 4355  
Telex AA62128

## Reasons to buy SPI HC/HCT HIGH SPEED CMOS

1. 74HC00  
2. 74HC02  
3. 74HC04  
4. 74HC08  
5. 74HC10  
6. 74HC11  
7. 74HC12  
8. 74HC14  
9. 74HC20  
10. 74HC27  
11. 74HC30  
12. 74HC42  
13. 74HC73  
14. 74HC74  
15. 74HC75  
16. 74HC76  
17. 74HC77  
18. 74HC80  
19. 74HC82  
20. 74HC83  
21. 74HC85  
22. 74HC86  
23. 74HC86  
24. 74HC90  
25. 74HC90  
26. 74HC93  
27. 74HC107  
28. 74HC108  
29. 74HC112  
30. 74HC112  
31. 74HC125  
32. 74HC125  
33. 74HC132  
34. 74HC132  
35. 74HC133  
36. 74HC133  
37. 74HC138  
38. 74HC138  
39. 74HC139  
40. 74HC139  
41. 74HC147  
42. 74HC148  
43. 74HC151  
44. 74HC151  
45. 74HC153  
46. 74HC153  
47. 74HC157  
48. 74HC157  
49. 74HC158  
50. 74HC158  
51. 74HC160  
52. 74HC160  
53. 74HC161  
54. 74HC161  
55. 74HC162  
56. 74HC162  
57. 74HC163  
58. 74HC163  
59. 74HC164  
60. 74HC164  
61. 74HC165  
62. 74HC165  
63. 74HC166  
64. 74HC166  
65. 74HC167  
66. 74HC167  
67. 74HC168  
68. 74HC168  
69. 74HC169  
70. 74HC169  
71. 74HC170  
72. 74HC170  
73. 74HC171  
74. 74HC171  
75. 74HC172  
76. 74HC172  
77. 74HC173  
78. 74HC173  
79. 74HC174  
80. 74HC174  
81. 74HC175  
82. 74HC175  
83. 74HC176  
84. 74HC176  
85. 74HC177  
86. 74HC177  
87. 74HC178  
88. 74HC178  
89. 74HC179  
90. 74HC179  
91. 74HC180  
92. 74HC180  
93. 74HC181  
94. 74HC181  
95. 74HC182  
96. 74HC182  
97. 74HC183  
98. 74HC183  
99. 74HC184  
100. 74HC184  
101. 74HC273  
102. 74HC280  
103. 74HC298  
104. 74HC365  
105. 74HC367  
106. 74HC373  
107. 74HCT373  
108. 74HC374  
109. 74HCT374  
110. 74HC393  
111. 74HCT502  
112. 74HC533  
113. 74HC534  
114. 74HC540  
115. 74HCT540  
116. 74HC541  
117. 74HCT541  
118. 74HC573  
119. 74HCT573  
120. 74HC574  
121. 74HCT574  
122. 74HC670  
123. 74HC4002  
124. 74HC4017  
125. 74HC4020

**101.**  
**WE DELIVER  
THE FIRST 100  
REASONS.**

**SPI** Solutions in Silicon



of one to two volts or so. In a direct-coupled enhancer/distribution amp, this dc level can wreak havoc, clipping the video signal. Hence, I have provided the option of switching between ac and dc coupling. With ac coupling, some low frequency roll-off can be expected, but it's only slight.

## Construction

For the purposes of this discussion, I assume you have already built, or at least are prepared to build, the ETI-1517 Video Distribution Amplifier. The circuit presented here is designed to be used in conjunction with the previous circuit, as indicated in the article which accompanied that project.

The first thing to do is locate a suitable position within the box to locate the new pc board and the new switches and potentiometers. There are three pots and one switch directly related to the enhancing section, and one additional switch to be added to permit ac coupling of the incoming signal.

The dc/ac coupling selection switch is

ideally located near the input connector. The other controls may be laid out as you see fit or according to the front panel design reproduced here. If you're using a different layout, the controls should be as close as practical to each other and the location of the Video Enhancer board. The new enhancer is best located adjacent to the distribution amp board, but a few centimetres of spacing can be tolerated if required.

Once the layout is decided and the appropriate holes drilled in the case and panel, the board may be assembled according to the overlay diagram. As I anticipate that a number of our constructors will be basically video enthusiasts, not electronics enthusiasts, I will take the liberty of stressing how vital it is not only that each component be inserted the correct way around, but that each solder connection be clean and neat. Only the resistors and ceramic capacitors may be put in either way around without impairing the operation of the circuit. It is best to put in only half a dozen items at a time, starting with the resistors and capa-

citators, and then solder these into place, cutting the component leads after soldering. Resistors R2 and R24 should be left out for now.

Next, two modifications need to be made to the ETI-1517 board, or the whole must be constructed with these two variations taken into account. The first consists of removing the termination resistor from the input side of the ETI-1517 circuit. A termination resistor, nominally of 75 ohms and preferably a 2% type, is provided in the enhancer (R2), and hence the one in the distribution amp is unnecessary. It may be used as R2 in the enhancer circuit if you wish. A wire may then conveniently convey the input signal from the ETI-1517 to the ETI-1518, using the hole vacated by the resistor you have just removed or transferred.

The second modification also consists of transferring a resistor. This time it is R24 in the enhancer circuit. Resistor R3 in the ETI-1517 (nominally 470R), running to ground from pin 6 of IC1, should be moved to R24 on the enhancer board. Recall that this resistor was a 1% or 2% type, or at least a selected value resistor. This is why it is transferred; the precise gain of the distribution amp is not disturbed. A wire is again run, using a vacated hole, this time from pin 6 of IC1 on the ETI-1517 to the output of the ETI-1518 enhancer board.


Now, apart from any beautification process you may wish to use, such as a Scotchcal panel fascia, the only remaining job is to hook up the flying leads to the ETI-1518 board. There are the leads to the pots and bypass switch, an earth and +/-5 volt leads, which may be run from underneath the ETI-1517 board, as well as the two signal leads already mentioned. My prototype layout is shown in the overlay/wiring diagram. Note that the various earth returns from connectors and boards, etc. all run to *one* convenient point. It is important to avoid any excessive lengths or tortuous paths in the signal and earth return leads, as this can easily provoke instability in a wide bandwidth circuit such as this.

At this point it seems appropriate to indicate that the compensation capacitor in the distribution circuit, the 27 pF capacitor in parallel with the collector resistor in the differential pair (C1), may require increasing to 33 or even 39 pF. Depending upon layouts and component tolerance, it appears that some units could exhibit unstable behaviour, especially on black-to-white transitions in the video signal. While my prototype was quite happy in a 'clean' environment, mismatches and other variations have subsequently been found to upset it. If super-video frequency ringing is evident on square-wave transitions with short risetimes, proper matching will cure it.

Finally, the video subcarrier trap must be adjusted. This entails adjusting the variable capacitor (CV1) to produce a 'notch' in the enhancer amplifier train at 4.43 MHz.


Connect a generator, set to deliver a sinewave signal at 4.43 MHz of about 200 mV p-p into a 75 ohm load. Viewing the output with the bypass switch closed so as to pass unenhanced signal, verify that the output is the same as the input when terminated correctly. Switch in the enhancer part of the

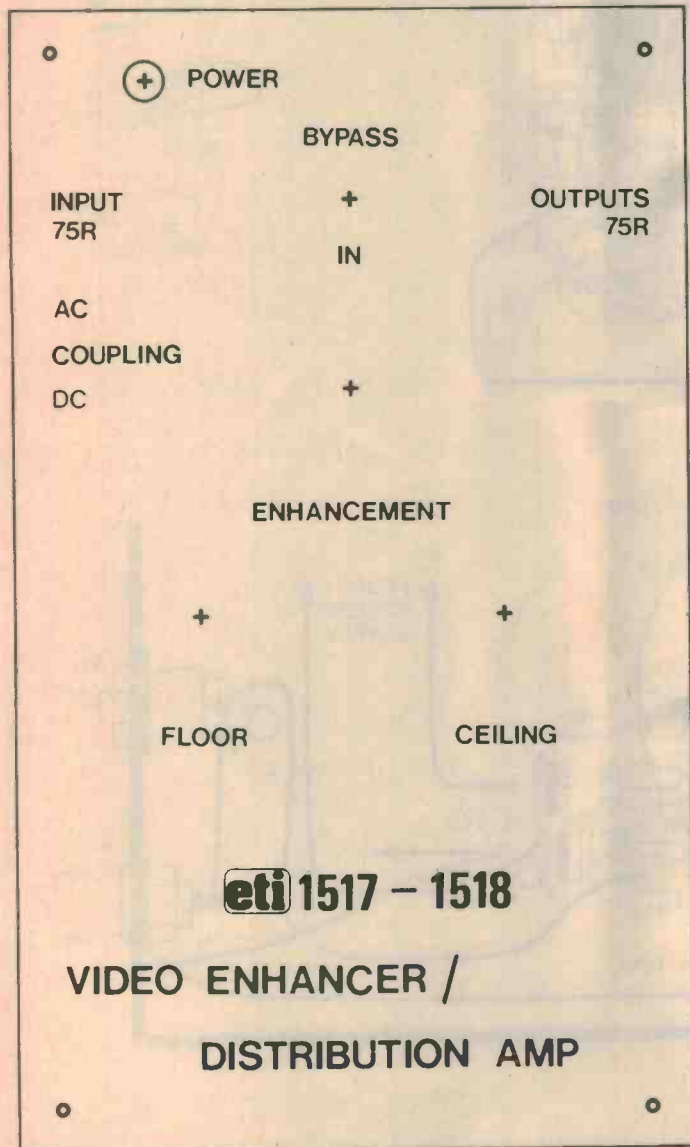Front panel. Full-size reproduction of the front panel artwork.






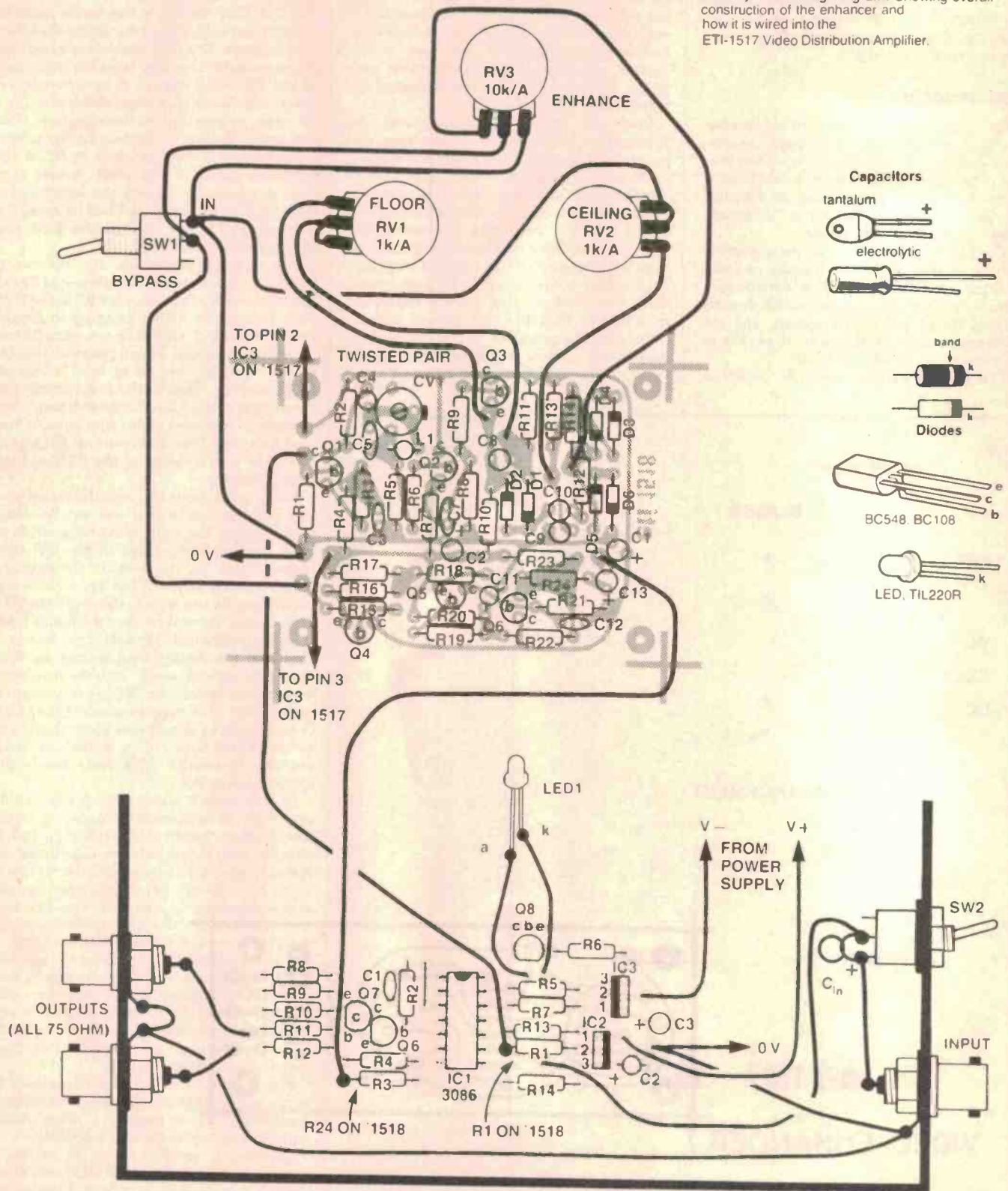Overlay and wiring diagram. Showing overall construction of the enhancer and how it is wired into the ETI-1517 Video Distribution Amplifier.





Using it. Typical setup for using the enhancer when dubbing from tape to tape. The monitor can either be plugged into a spare output on the project (as shown) or plugged into the video output of the recording VCR. Always run the playback VCR for a few minutes to initially set up the enhancer, with the recording VCR off, before commencing dubbing. Return the tape to start before commencing dubbing and only monitor results as recording proceeds. Try to avoid adjusting the enhancer during recording, unless absolutely necessary.

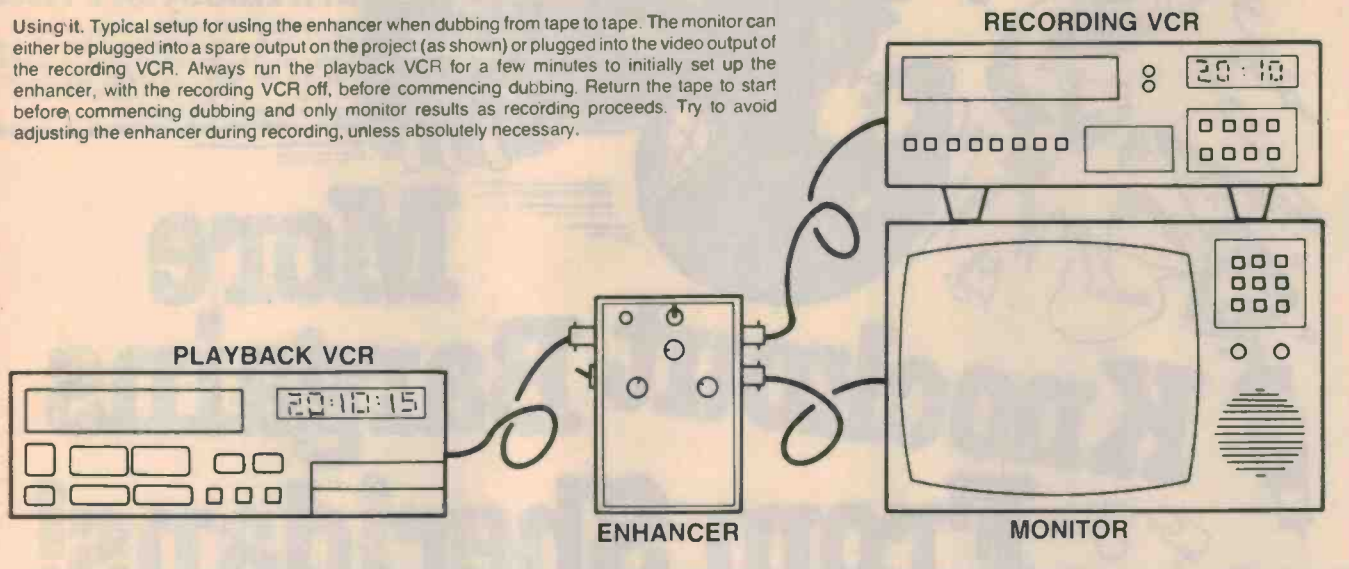

**PARTS LIST — ETI-1518**

- Resistors** ..... all ¼ W, 5% unless noted  
 R1 ..... 75R, 1%\*  
 R2 ..... 390R  
 R3 ..... 68R  
 R4, 8, 12, 17, 21 ..... 1k  
 R5, 13, 22 ..... 1k5  
 R6, 9, 15, 16, 18, 19 ..... 100R  
 R7, 10 ..... 2k2  
 R11 ..... 3k9  
 R14 ..... 10k  
 R20 ..... 4k7  
 R23 ..... 1k8  
 R24 ..... 470R, 1%\*  
 RV1, RV2 ..... 1k/A pots.  
 RV3 ..... 10k/A pot.  
 \*may be taken from ETI-1517 board

- Capacitors**  
 C1, 2, 13 ..... 10u/35 V tant.  
 C3, 4, 8, 9, 10, 11 ..... 47n-220n ceramic (low inductance)  
 C5 ..... 100p ceramic NPO  
 C7 ..... 150p ceramic  
 C12 ..... 12p ceramic  
 CV1 (C6) ..... 10-60p trimmer  
 Cin ..... 10u/35 V tant.

- Semiconductors**  
 D1-D6 ..... 1N914  
 Q1-Q6 ..... BC548, BC549 etc.

- Miscellaneous**  
 L1 ..... 10 uH RF choke (Q of at least 50)  
 SW1, SW2 ..... SPST or SPDT min. toggle switches

ETI-1518 pc board: power supply +/−5 V (can come from ETI-1517); ETI-1517 (if you wish); Scotchcal front panel.

**Price estimate**  
 \$18-\$24 (alone)  
 \$45-\$50 (with ETI-1517)

circuit, setting the floor low and the ceiling high (RV1 to maximum and RV2 to minimum resistance). Adjust RV3 to mid-position. Now adjust C6 for a minimum of output signal. This will be near, though not necessarily exactly at, the original output level before enhancement.

If you do not have access to the equipment needed to do this adjustment, you will not be able to set the enhancer trap correctly, but a setting satisfactory to your recorder should be obtainable simply by selecting that setting of CV1 which leaves the *colour* of the picture minimally disturbed throughout the travel of the enhancement control. If a range of settings fits this bill, leave the trimmer at the centre of the range.

**Operation**

Operation of the enhancer is quite straightforward, though some experience is necessary in optimising the control settings. The effects are subtle, but worthwhile if you do a lot of viewing and recording of video material.

Connect the enhancer between the video source you wish to enhance and the monitor or receiving VCR. If possible, choose some material with plenty of contrast and colour — commercials are good for this, if little else.

Initially, adjust the floor *down* and the ceiling *up*. Wind up the enhance knob. You will observe that the image first gets 'crisper', with fine print and signs, labels etc becoming more easily read. Eventually the snow and general noise gets significant, or perhaps the bright/dark transitions get shadowy, indicating too much boosting.

The noise problem can often be improved with judicious fiddling with the floor level. You will find that the floor and enhance functions are interactive to some extent. This is really a very fine point, because the amount of extra boost you can squeeze in with the use of the floor level control is usu-


ally minimal, but it is there.

Likewise, the transition overshoot problem, manifesting itself as rippled edges, can be improved with the ceiling function. This function may be rarely useful, but seeing the logic behind it, I included it for you to try out.

This control is also interactive, so the adjustment of all may be finicky. I had better results by adjusting the enhance and floor controls until just too much enhancement was evident, then 'backing off' ceiling to just correct it.


A further check can be made by immediately playing back the copy. It is possible that over-enhancement to the immediate viewer can be just right when the signal has gone through another record-replay stage: sort of pre-enhancement.

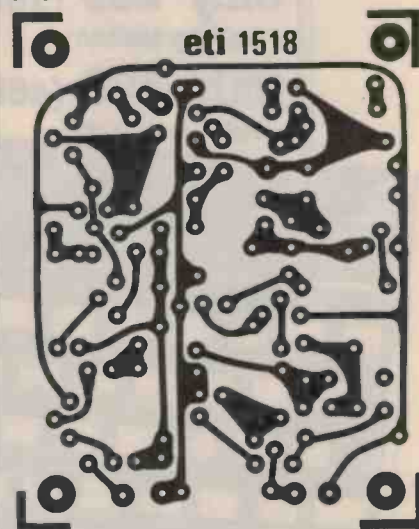About here is where the written advice is superseded by on-the-job fiddling with the knobs. I wish you all the best with your new project.



Board. Full-size pc board artwork.



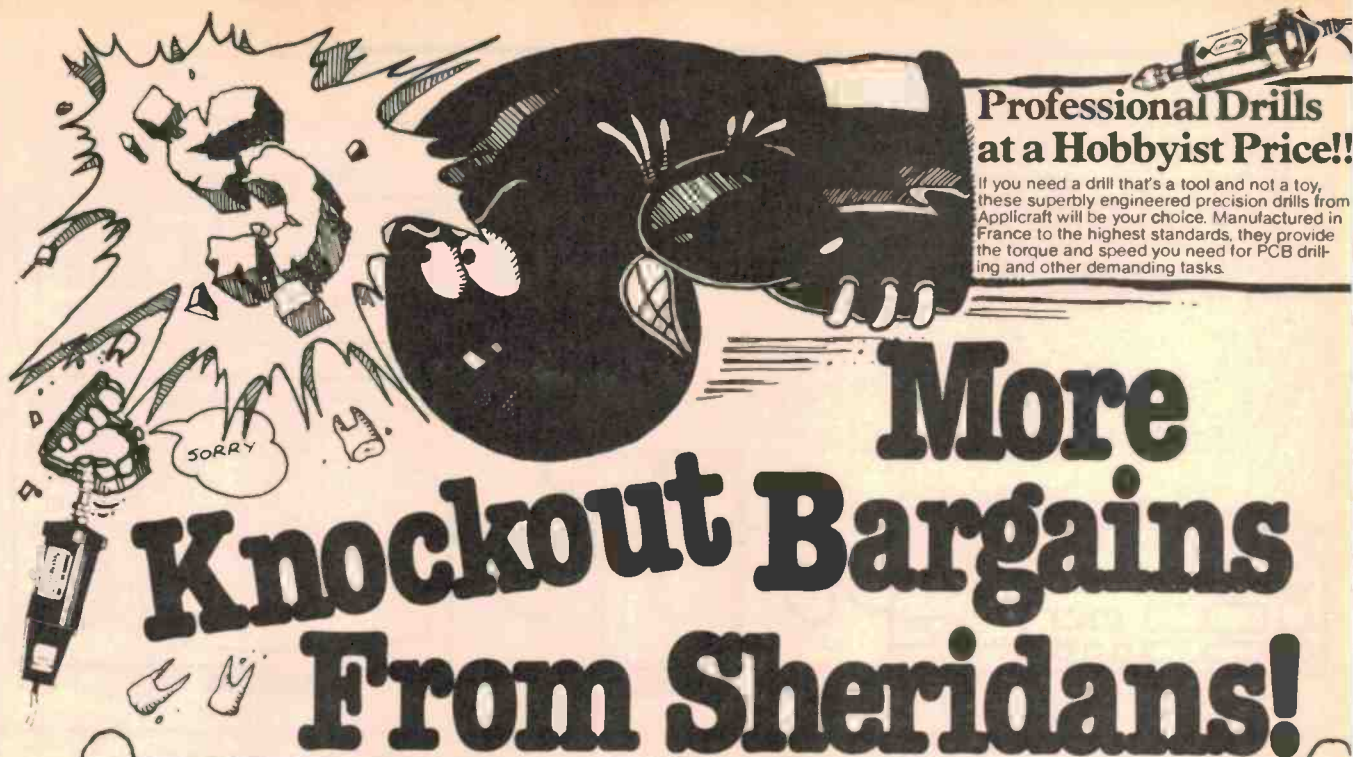

## Professional Drills at a Hobbyist Price!!

If you need a drill that's a tool and not a toy, these superbly engineered precision drills from Applcraft will be your choice. Manufactured in France to the highest standards, they provide the torque and speed you need for PCB drilling and other demanding tasks.

# More Knockout Bargains From Sheridans!

## The Sinclair Spectrum – the World's Finest Home Computer. Now at Sheridans

If you've seen ads for the incredible Sinclair Spectrum colour computer, you'll know it pounds the opposition to a pulp!!:

- Full colour
- Sound with variable pitch and duration
- Intensity control
- Up to 48K of RAM
- Full sized moving keyboard
- High resolution – 256 x 192
- ASCII character set with upper and lower case
- Teletext compatible
- Super powerful 16K extended BASIC
- Compatible with ZX81 programs and printer (but now gives upper case and high res graphics)

**Only \$289 (16K)**

– don't pay \$299.00

**Only \$379 (48K)**

– don't pay \$399.00



## Software:

(Note: a few of these programs require 48K, please phone or write if in doubt)

All are supplied on cassette.


Biorythm	\$22.50
Space Radar	\$19.50
Chess	\$24.95
Planetoids	\$19.50
Flight Simulation	\$24.95
Backgammon	\$19.50
VU File	\$27.50
VU Calc	\$24.95
VU 3D	\$24.95
Inca Curse	\$22.50
Ship of Doom	\$22.50
Espionage Island	\$22.50
Reversi	\$24.95
Collectors Pack	\$22.50
Club Record Controller	\$22.50
Embassy Assault	\$19.50
Cyrus/IS/Chess	\$27.50
Small Business Account	\$39.95
Hungry Horace	\$19.50
Horace goes skiing	\$19.50
Horace and the Spiders	\$19.50
Planet of Death	\$22.50

(Note: stocks more titles available in the New Year plus you can use existing ZX81 programs!)
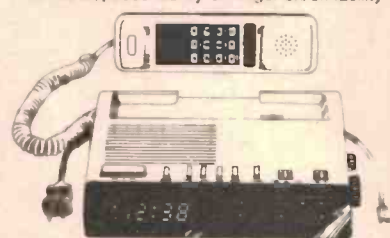
## Rover TR303 Speaker Phone and Clock Radio

This knockout phone/radio/alarm clock has got the works!! Facilities include:

- Pushbutton telephone with loudspeaking facility (condensor mike with volume control and mute facility)
- Redial/pause facility ● Ringer on/off facility



The radio section includes:

- AM/FM radio
- ON/OFF/AUTO facility on radio

**Only \$79.00**

- Alarm facility on clock with sleep button
- Snooze button ● Radio or buzzer on alarm facility ● Large superclear display
- Fully Telecom approved

You can go to sleep with the music, wake to the music and answer the phone without lifting the receiver. And it's all at a Knockout Sheridan Price!!

Provides full upper and lower case plus high resolution graphics. COPY facility lets you print out straight from the screen. Prints at 50 characters per second with 32 characters per line and 9 lines per vertical inch. Supplied with paper and full instruction.





## High Speed Model Deluxe Drill Set

Precision drill with 3 interchangeable collets for sizes from .1mm to 2.4mm. 10,500 RPM 9-16V. Ref 20,000

**\$16<sup>50</sup>**



Includes Drill, stand and flexible drive complete with 30 accessories in carrying case. Includes the High Speed Drill shown above plus the drill stand shown below. Ref 20100

**\$69<sup>00</sup>**



## Drill Stand

Stand for Ref 20,000 drill (above). Ideal for precision drilling of PCBs Ref 20,400

**\$12<sup>50</sup>**




## Improve Your Image

We now stock the most sought after range of video enhancers at the best prices around. If you want to improve the quality of your video without spending a fortune, Sheridans is the place!!
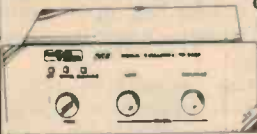
### VP-5030 Video Detail Enhancer

Design to rectify the loss of detail from VCR tapes. Perfect for off the air recording and dubbing. Now you can actually improve on the original. At with Sheridan you save a fortune!!  
Input 1 video  
Output 3 videos  
Enhance 9dB



only **\$79<sup>00</sup>**

don't pay ~~\$89.00!!~~

## AAA Nicads at a stagggggging price

Looking for AAA Nicads at a sensible price. We've got 'em!! 1.2V/180mA

only **\$3.00 each, 10+ \$2.70**



## Illuminated Pushbutton

These superbly made IMO pushbuttons are perfect for car and other alarm situations. SPDT momentary action with 12V long life globe. Available in red, green or yellow lens. Others are asking \$15.00. Put them in the losers corner!!



only **\$8<sup>95</sup>** SAVE!!

## We're out and thumping for Hewlett Packard Opto!!

Now you can afford HP quality. Replacements for Fairchild, National ETC

HDSP5303 .56" Common Cathode equivalent to FND500 (but better) only **\$1.70 each, 10+ \$1.55**



HP 5082-7730 .3" common anode equivalent to MAN71, DL707) only **\$1.50 each, 10+ \$1.35**



HP 5082-7740 .3" common cathode equivalent to MAN74, DL704 etc only **\$1.50 each, 10+ \$1.35**



## Flexible Drive Shaft

Suits the high speed drill above. Complete with chuck and collets. Ref 20,700


**\$10<sup>95</sup>**



## NEW! Precision High Speed Model

Capacity to 3.5mm, 9 to 18 volts. 20,000RPM. A really superb drill that will give years of use.

**\$24<sup>00</sup>**

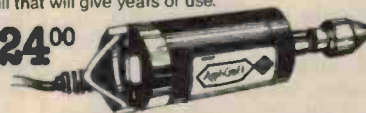

## Drill Set

This fantastic drill set includes the high speed precision drill shown above plus a wide range of 15 accessory drills, brushes and grinders. Ref 40,100

**\$35<sup>95</sup>**

## Heavy Duty Stand

Suits precision high speed drill. Perfect for any hobbyist work. Ref 40,400

**\$20<sup>00</sup>**



## Modutec Car Alarm

This is the most powerful and comprehensive car protection system on the Australian market we have seen. Compare the features. Then you'll know its the best.

- Automatic or Manual start
- When tripped it sounds horn and disables ignition system
- Dash mounted warning light
- Variable entry and exit times
- 12 months warranty
- Protects accessories

only **\$89<sup>00</sup>**




don't pay ~~\$129.00!!~~
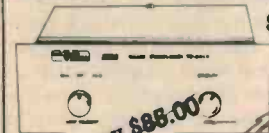
## VP-5010 Video Image Stabilizer

Ensure you don't get vertical rolls or blackouts. With slight adjustment immediately stabilises picture of pre-recorded tapes - removing the copyguard signal.

Power 9V DC  
Input 2 videos  
Output 1 video



Price only **\$71<sup>00</sup>**

## Jawbreaker purchase!!

Top quality English Made by SAE. 10 way .1" DIL DIP switch. Special top quality pushbutton type. At a punchup price!! \$1.30 each 10+ \$1.20



Less than 1/2 price

## Video Tape Knockout

Superb G Tape VHS tape. VHS E180 full spectrum tape at a never to be repeated price. Reduced from our normally low price of \$14.95 to only

**\$13.95 each or 10 for \$135.00**



# SHERIDAN ELECTRONICS

164 - 166 Redfern Street, Redfern NSW 2106. Phone (02) 699 6912, (02) 699 5922. Mail Orders to Dept ETI, PO Box 229 Redfern NSW 2016

Large and heavy items sent Freight On

Trading Hours	Mail Charges	Note:
Mon-Fri ..... 9am-5:30pm	\$5.00-\$9.99 ..... \$3.50	We regret we cannot give quantity discounts on Credit Card purchases.
Thursday ..... 9am-7pm	\$10.00-\$24.99 ..... \$4.00	<b>Credit Cards:</b> We accept both Bankcard and American Express.
Saturday ..... 9am-12noon	\$25.00-\$49.99 ..... \$6.00	
	\$50.00-\$99.99 ..... \$7.00	
	\$100.00 or over ..... \$8.00	

NB: All Prices include tax

Minimum Order \$6.00

An Express 923 1499



# Further thoughts on train controller design

The ETI-1508 Train Controller (December '82 issue) proved a popular design and occasioned much reader comment. Though seemingly elaborate, many readers said we hadn't gone far enough! After many months of experience, some improvements suggested themselves (a clever train controller!). Here they are, plus further thoughts on new design possibilities.



OUR LAST train controller project, the ETI-1508, has stirred above-average comment and enthusiasm, it seems. It was a fairly imaginative design (read oddball if you are one of the school that disapproves of radical steps). In a way, the more sceptical people had a point, for there are two drawbacks with the design, one brought on by lack of experience with different train systems on my part, and the other a purely cost-based one. This article talks about the problems, suggests short term measures to improve the situation, discusses the inherent design problems and points the way to the next generation design — work upon which continues.

The first thing to note from reader responses is that many of the heavy enthusiasts are willing to accept rather high component counts, and hence cost. When the '1508' was designed, a lot of attention was paid to keeping the circuit reasonable in size so that beyond the transformer, the cost could be low. True, the hardware was not cheap, especially if you built it entirely from scratch, but it was cheap if you used a cheap box and an existing power supply. I should have spent more time than I did wandering in model shops, because if you look at how much trains cost, controllers aren't big chips. However, remembering my days of cannibalising old equipment and buying AC127s in ones (oops, dated now) we played Scrooge. At this point, it seems fitting to mention the first inescapable design decision on train controllers.

## Decisions, decisions

There are two radically separate controller designs. The '1508 epitomises one, and perhaps the Hornby 'Zero-One' the other. The Zero-One places 16 volts ac on the tracks at all times and controls engines (plural), points, signals and all accessories using only the two connections of the track. This it does by sending control signals as well as raw available power down the lines, rather like the SEC controlling off-peak systems with control tones. These are

picked up by small switching units in the controlled items which do their stuff, drawing from the rails whatever power is required. This gives ease of wiring and the ability to control several trains separately without isolating track sections.

## Jonathan Scott

In a way, it is quite superior to the '1508 type, which needs on train per circuit and that is all it will handle. However, it sacrifices feedback. This means no 'real train feel', no erratic response to hills, no difficulty in control and no open/short-circuit indication, etc. It is also costly as every item on the system needs an 'implant'; one is likely to pay about \$200 for a starting setup, and each new item added demands another 'implant'. It is also a rather cut-and-dried design; there is little room for tinkering and improvement, because of the lack of feedback. So if you want to go that way, we can see the reason. It probably produces the best effect as far as looking is concerned, in that lights are always on and models always moving in a 'controlled' way. There are far fewer wires and fewer things to twiddle. The professional's system it is, in every way.

## Jerking off

The '1508 is a sensitive analogue approach, for which we pay in complexity and 'fiddliness'. So, back to its problems. Engine takeoffs are often 'unsmooth' and sometimes need the train to be nudged. If you have the throttle up too far the train can jerk off, entirely ruining realism. If the current rises slowly, the train may never shift without a nudge, or may appear to jam for a while and then, when the power is enough to overcome static friction, it takes off at a pace.

These effects are aggravated by the fact that the unit is regulating current rather than voltage. We found that Hornby trains, which are significantly less smooth than

other makes, are particularly susceptible. Airfix or Jouef ones proved quite OK in this regard. Some Hornby pickup systems are virtually the same as they were on their locomotives over twenty years ago! Tradition is nice but often painful. Even Rolls Royce have begun to change their grille design!

A voltage regulation regime gives improvement, but tends to remove the very real (steam era) effect that a locomotive engine develops more power as it speeds up, giving a positive feedback effect, demanding care and concentration from the driver. What is required is voltage regulation in the short term (seconds) and current regulation in the longer term (tens of seconds and up).

The modification shown in Figure 1 can be added quickly to the '1508 and gives this effect. Startup is smoother and far less critical. It has one drawback on the '1508: namely, that the open-circuit sensor uses the fact that there is current drive, and since the current drive is effective only after 5-10 seconds, the o/c light may take up to this long to respond.

In future designs the current sense requirement of the o/c detector can be removed so that the drawback is overcome (at a small cost of increased component count).

The suggested modification requires only three points of connection to the pc board and is thus quickly added in situ, and removed if you do not like it. Startup only requires that you use more throttle than you thought before; the margin for mis-estimation is greatly reduced. In addition, the engine appears to have more inertia when encountering a sudden hill or extra carriages, though the need for attention to the throttle in the long term is still present, which I feel is important.

You may wish to reduce the basic acceleration time constant and the idle-slowdown time constant as well, in order to restore the original feel of inertia, as the circuit here will suggest an increase




The function of the modification is to apply feedback to the main regulation amplifier in order to produce output voltage regulation effects for frequencies in the 0.1 Hz region. It achieves this by converting changes in output voltage in this frequency area into current and adding this to the signal presented to the feedback input of the control operational amplifier.

Clearly, Q301 will be turned off in the quiescent dc state by R302. Together, R302, C301, R303 and C302 form a filter which passes frequencies near 0.1 Hz to the base of Q301. When load voltage increases, the voltage at the collector of the output transistor falls with respect to the +25 V rail. This is passed on to the base of Q301 which conducts sourcing current, the amount determined by R301. Thus R301 defines the transconductance of the system at the frequency of peak gain.

Although the whole circuit may have a large ripple component because the +25 volt line has large ripple on it, this is not passed down to the op-amp because of the constant current output characteristic of the transistor.

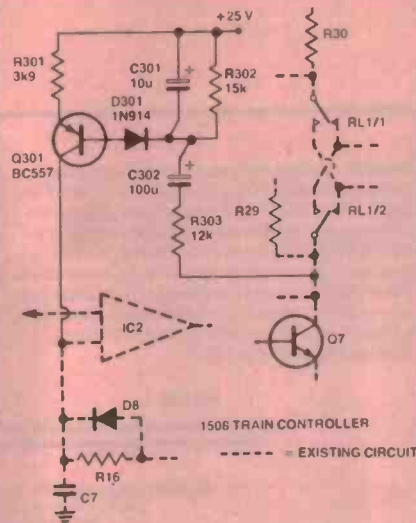The sourced current for a rise in load voltage in turn induces the drive to the output of the controller, effectively holding load voltage constant. Owing to the required Vbe drop of Q301 and that of D301 there is a small dead band before which the regulating action occurs, meaning that there is no effect for small signals. This, plus the bandwidth limitation of C301, assists stability and also



reduces the lag before the o/c detector responds. The bandwidth limitation is such that the turn-on pulse is not significantly affected. D301 also protects the transistor b-e junction against reverse biasing when a low load impedance is suddenly added.

Sudden load reductions, as in braking or collecting extra carriages, represent rises in the output transistor collector voltage, which serves only to turn Q301 further off so that its action occurs only at or near acceleration points.

overall. (i.e: reduce R4 and R7 to around half or a little more of the previous values.)

The second half of the problem, the effect of jamming whereby the train does not take off at all without mechanical persuasion, is not solved even by the voltage regulation technique. It was hoped that the initial impulse delivered at the point of acceleration would overcome this to a large extent, which it does, but it still occurs annoyingly often.

The effect occurs because the friction of the gears and engine mechanicals requires more force to be initially applied than is necessary to sustain movement. It is worse in certain designs.\* The Hornby wormgear drive is again not the best way to do it. Also, engines with a higher top speed, and hence usually a lower reduction ratio, are worse. Oiling and cleaning are partially effective, but are not cures. It seems as though applying power in pulses is very helpful. This suggests that a switchmode power delivery scheme would be beneficial. I did not use a switchmode supply in the '1508 because, firstly, it did not seem justified as a power economising measure and because it tends to make engines 'sing' at the switch frequency. As the '1508 applies power, albeit a tiny amount, even when at a standstill, the engine would sing even when standing at a station. To apply the technique while avoiding obtrusive noise, excessive component count and disturbance and s/c and o/c detectors, is tricky. I have not solved this stumbling block as yet.

To summarise the needs and changes


\* This may also be due to demagnetisation effects, especially if you have ever made the mistake of dismantling the engine (motor) itself.

which should be implemented in a next design: (1) The o/c sense will be of an independent type, as is a s/c in the 1508, so that (2) one can use voltage regulation for frequencies above about 0.1 Hz and current regulation below this point. (This constrains the gain and configuration of the feedback loop in order to guarantee stability — for example, the drive must not permit the load impedance to affect gain of the final stage, as does the 1508 where it does not matter.\*\*)

(3) The power delivery mechanism should be switchmode, with a frequency and duty cycle optimised for overcoming friction yet minimising noise. The circuit must apply pulses with a rate comparable to the armature time constant in order to exercise maximum force momentarily to overcome static friction, yet be fast enough to give smooth travel at low speed and hopefully be inaudible. It must also respond to input changes faster than the actual inertia of the train permits it to respond, and also deliver a current which it is practically possible to average out faster than the train can respond. The latter condition is necessary in order to maintain apparently slothful response in the actual model, despite real world effects like dirty contacts, which are instantaneous.

\*\* This is the limitation of effectiveness of the modification suggested earlier. Any tighter regulation of train voltage at higher frequencies (than the circuit offers) gives rise to oscillation when load impedance rises, disabling the o/c indicator totally. Reduction of the BC557's 3k9 emitter resistor would tighten the regulation, smoothing response further, but permitting instability for large load impedance. Curing that by reducing loop gain bandwidth elsewhere defeats the turnon impulse. That resistor may be selected (1k-10k range) to give best train response for stability.

## REDESIGNED AND IMPROVED SK-10

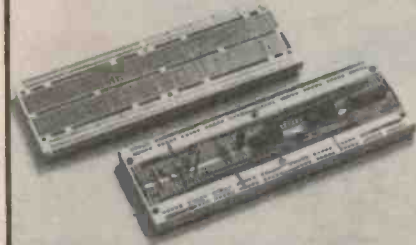

### LIFETIME GUARANTEE!

- New Body Material (capacitance 3.5pF rail to rail)
- Numbered contacts (840 contact points)
- Current capacity 4 amps
- Resistance 2.5 contact to contact
- All component sizes 20-26 AWG
- Also available:
  - SK-50 Halfboard (430 contacts)
  - SK-20 Miniboard (80 contacts)

- Lifetime guarantee

"We will replace, free of charge, any E & L Breadboarding socket which fails to meet specifications or which breaks down in the course of normal usage."

Available throughout Australia from:

VIC: Stewart Electronics (03) 543 3733  
 SA: Graphic Electronics (08) 42 6655  
 WA: Reserve Electronics (09) 328 9755  
 QLD: Fred Hoe & Sons (07) 277 4311  
 NSW: E.D.S. (02) 438 2500  
 MACELEC (042) 29 1455  
 D.G.E. (049) 69 1625



**ELECTRONIC DEVELOPMENT SALES PTY LIMITED**

92 Chandos Street, St Leonards  
 NSW Box 217 St Leonards 2065

Tel: (02) 438 2500  
 Tlx: AA 25963





# MERRY CHRISTMAS FROM MAGRATHS



DISC DRIVES  
M4853



MITSUBISHI

\$378.45

- SLIM-LINE 5.25"
- DOUBLE SIDED
- DOUBLE DENSITY
- 80 TRACKS PER SIDE
- 1.0M BYTES UNFORMATTED

## KIT SUPPORT FOR THE MICROBEE

### EPROM PROGRAMMER

Versatile, low cost and easy to build. Plugs straight into the microbee I/O port. Suitable for 2716, 2732, 2532, 2732A and 2764 Eproms. Burn your games programmes and eliminate cassette loading time. **KIT FEATURES** Sockets for all other IC's 1 x 2716 supplied - get started straight away. Front Panel and Mains (SEC approved transformer 28 pin and 16 pin wire wrap sockets to flush mount personality plugs (2 included) and ZIF socket (included) DB 15 Plug. Complete to last nut and bolt.

K9668 \$55.00

### RADIOTELETYPE DECODER

Display RTTY encoded messages on your video Monitor. Receive up to date weather information, International News before the Papers, all sorts of coded military info. Simple circuit uses PLL techniques Single PCB Construction. Kit includes DB 15 Plug and backshell for connection to microbee. Shielded pretinned PCB.

Great Value!



K9733 \$19.50

### MAGRATHS PRODUCT OF THE MONTH! DIGITAL MULTIMETER



0.1% and 0.25% Basic DCV Accuracy  
Overload Protected on All Ranges  
2,000 and 200 Hour Battery Life  
Current Ranges to 10 Amps  
Hi-Lo Volt Resistance Tests  
Rugged construction  
26 Ranges  
3 1/2 Digits  
Low Cost

ONLY \$100.91



### MICROBEE LIGHT PEN

AT LAST - a light pen for the Bee. This pen works in the low-resolution graphics mode and connects directly to the I/O port  
• Complete kit including DB 15 2m CORD  
• Fully documented with software example.

PROVIDES DIRECT PERSONAL CONTACT WITH YOUR BEE!

K9649 \$19.95

### FAX-DECODER

This project allow you to decode the signals of shortwave stations, transmitting radio facsimile weather maps, satellite pictures etc and then reproduce them on your dot-matrix printer.

- Complete kits of parts includes DB15 Ribbon Cable
- SOFTWARE LISTING

K9733 \$24.50



TC48/  
TC64-IC  
TEST CLIPS

14 PIN	\$7.00
16 PIN	\$7.34
16 PIN LFI	\$13.80
18 PIN	\$15.43
20 PIN	\$17.68
22 PIN	\$19.65
24 PIN	\$20.33
28 PIN	\$22.44
40 PIN	\$29.85
64 PIN	\$43.52

### MULTIPROM INTERFACE FOR THE MICROBEE

- 44K OF PROGRAM STORAGE • FULLY SOFTWARE SELECTABLE • SUITS BOTH IC AND PLUS MACHINES
- 8 OUTPUTS FOR CONTROL APPLICATIONS

A sensational new kit for the MICROBEE. requires no modification to the computer except for the fitting of a 50 pin expansion socket. This project is easy to build and will allow you to store and software select up to 44K of eprom storage - acts like a mini disk drive system with the speed of RAM. Extra units may be added to further increase storage.

- Full set of IC sockets
- Double sided, plated through board
- Assembled connection lead to Microbee
- Fully documented
- Cassette monitor included (plus sourcefile).

K9673

\$99.50

THE MICROBEE KIT OF 1983

### STEREO SYNTHESIZER FOR VCR'S AND TUNERS

Synthesize realistic stereo from virtually any monophonic source by simply connecting this unit between the source and your stereo amplifier.

- Quality Phillips MN3001 (not second source dropout).
- Selection of either source via front panel switch.
- Normal or stereo sound selection.
- Provision for 2 different signal sources.
- Complete kit includes all hardware, cables etc., even solder.

K5810 \$55.00

### ETI SERIES REGULATOR DESIGN

- 0.40 Volts @ 5 Amps - that's 200 Watts
- Current limiting 0.5 Amps variable
- Specifications Second to None
- Free from the hum and noise sometimes associated with other techniques.

A PROFESSIONAL SUPPLY

K3325

\$175.00

### COMPUMUSE

YOUR GAMES WILL NEVER BE THE SAME

A computer music synthesizer that is easy to build and easy to use, connects to any computer with a Centronics-style parallel port and provides music over a five octave range and a wide variety of sound effects.

- EXPERIMENTAL KIT-PCB, COMPONENTS & SOFTWARE

K9834 \$26.50


ALL PRICES INCLUDE SALES TAX

<b>KITS</b>	SOUNDBENDER	\$26.39
	RADIO MICROPHONE	\$6.20
	ELECTRONIC IGNITION	\$31.88
	MICROBEE EPROM PROGRAMMER	\$52.96
	MUSICOLOR IV	\$91.39
	NEGATIVE ION GENERATOR	\$39.28

POWER SUPPLIES K3300

\$139.00

SUPER BARGAINS AT MAGRATHS

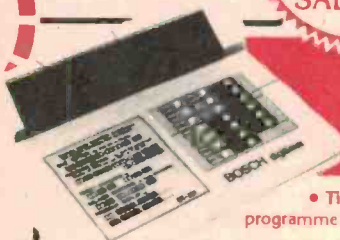

### Bosch digitimer

a fully programmable Digital Computer Clock with 4 independently switched power outlets.

- Time.
- Day of week.
- Calculator-type key entry for programme setting.
- 4 independently switched power outlets.

Equipped with a programmable computer which can switch four power outlets independently to control most appliances up to 10 amps. The computer is programmed via a calculator type key entry facility to perform up to 20 daily or weekly switching functions.

Ideal for both home and industry, the Bosch Digitimer DT201 can be used for:

- Security Lighting.
- Shop Window Lighting.
- Radio/Hi-Fi.
- Electric Blankets.
- Air Conditioners and Heaters.
- Most Kitchen Appliances.

\$86.25

MAGRATHS ELECTRONICS Phone or Mail.  
55 A'BECKETT STREET, MELBOURNE, 3000  
Tele (03) 347 1122, Telex AA31001

Prices subject to change without notice.



— Mail or phone orders add \$2.00 up to 1kg pack post  
Special rates for heavy items on request.





# MERRY CHRISTMAS FROM MAGRATHS



## Books & Magazines.

- COLOUR COMPUTER NEWS • COLOUR COMPUTER NEWS
- SYSTEM 68 - APPLICATIONS • 68 MICRO JOURNAL
- MICRO 80 • APPLE ORCHARD • CREATIVE COMPUTING
- AUSTRALIAN PERSONAL COMPUTER

WE ALSO HAVE A RANGE OF OTHER MAGAZINES IN STOCK!

### FAIRCHILD

Bipolar Memory Databook	
	\$8.00
CMOS Databook	\$9.00
A Linear Databook	\$12.50
MOS Memory Databook	\$8.00

### MOTOROLA

CMOS Databook	\$9.00
Schottky TTL Databook	\$8.00

### PHILIPS

Building Hi-Fi Speaker Systems	\$6.50
Semiconductors, Pt 2	\$10.00
Semiconductors, Pt 3	\$10.00
General Catalogue 81 82	\$10.00

### DATA BOOKS

#### TEXAS INSTRUMENTS

Software Design for Micro Processors	\$14.95
1981 Supplement - TTL Data	\$6.25
Linear Control Circuits	\$3.90
Interface Circuits	\$16.00
MOS Memory	\$8.35
Bipolar Microcomputer Components	\$9.99
TTL Data Book	\$12.50
Understanding Solid State Electronics	\$7.95
Understanding Computer Science	\$7.95
Understanding Communications Systems	\$7.95
Understanding Optronics	\$7.95
Beginners Basic TI-99 4A	\$14.95

### NATIONAL SEMICONDUCTOR

Audio Radio Handbook	\$6.50
Advanced Bipolar Logic	\$6.50
Linear Applications Handbook	\$18.00
Transistor Data Book	\$7.50
Voltage Regulator Handbook	\$8.00
Memory Data Book	\$7.00
Series 80 Board Level Computer	\$6.00
Hybrid Products Databook	\$9.00
Logic Data Book	\$9.00
MM 54HC 74HC High-Speed CMOS	\$2.50
The Reliability Handbook	\$16.00
NEW Databook 2Vol	\$14.00



## CENTRONICS INTERFACE FOR THE MICROBEE

A simple kit to build—takes about 20 minutes. K9671  
save on the cost of a built interface and save the cost of a serial printer. **\$29.95**

## TTY TYPE INTERFACE FOR THE MICROBEE

Teleprinters are cheap, so is this kit. If you've got an old teleprinter, this is for you. K9672 **\$17.50**

## SEMI-CONDUCTOR SPECIALS

\$68A21P 1.5 MHz PLA	\$3.68
\$6800P CPU	\$5.75
\$6821P 1 MHz PLA	\$2.88

## POWER UP - A MUST FOR YOUR COMPUTER SYSTEM

This great new Project from EA is the answer to a Maiden's Prayer. What Does It Do? A single 240V mains plug and lead feeds one unswitched master 240V outlet plus 4 switched 240V outlets. With say, a hi-fi system, plug your main equipment item (e.g. amp.) into the master outlet and whenever you "switch on" your amp. - presto - mains power is applied to the other 4 outlets, i.e. simply "turning on" your amp. turns on your tape cassette, tuner, turntable, graphic equaliser without mains spikes, plops, etc. Just the shot for your computer system.

K6000 **\$39.50**

## SUPER SPECIALS

3 Pin Din Plugs	Only 12 cents each
3mm T1 3/4 Red LEDs	Only 8 cents each

## INTER-VIDEO

VP-5030 VIDEO ENHANCER \$74.64

## SENNHEISER QUALITY HEADPHONES -

RUGGED, LIGHTWEIGHT

HD40 Dynamic 20 Hz-18KHz	\$25.03
HD410 Dynamic 20 Hz-18KHz	\$36.11
HD 414 Dynamic 20 Hz-18KHz	\$65.67
HD425 Dynamic 18 Hz-20KHz	\$80.49

## MORE KITS

K5001 ETI - Series 5000 Pre-amp. Kit	\$275.00
K5005 ETI - Series 5000 Mosfet Power Amp.	\$319.00

## SPHERE CCT-100 TERMINAL AS REVIEWED IN EA JULY '83

### SPECIFICATIONS

COMMUNICATION	• Code:	128 ASC 11 characters
	• Baud rate:	75, 110, 150, 300, 600, 1200, 1800, 2400, 4800, 9600, 19,200
	• Parity:	odd, even, mark space
	• Operating Mode:	full duplex, half duplex or block mode
	• Interface:	EIA RS-232C or 20mA Current Loop
EMULATION	• LEAR SIEGLER ADM-3A, HAZELTINE 1500, ADDS VIEWPOINT	
SCREEN PRESENTATION	• Display format:	24 lines x 80 characters
	• Display unit:	12-inch, non-glare CRT
	• Character type:	7 x 9 dot matrix
	• Character set:	96 ASC 11 characters, 15 graphic symbols, 32 control character symbols
	• 5 screen attributes	blink, underline, blank, reverse, dual intensity
	• Cursor type:	selectable slow, fast blinking or steady cursor, block, underline or invisible cursor

PLUS MANY MORE FEATURES!

**\$1029.25**  
ONLY

## WILDCARDS MAGAZINE VOL. 1

100 pages of application notes and tips for the Microbee Personal Computer. **\$15.00**

## MULTIMETERS

BECKMAN RB153030	\$346.30
BECKMAN HD100	\$290.95
SANWA M501	\$157.55
SANWA M301	\$109.25
SANWA 460ED	\$110.40
SANWA EM300	\$105.80
SANWA CX50511	\$81.65
SANWA LD510	\$144.90
SANWA AX303	\$66.70
SANWA LD530F	\$263.35
SANWA BX808M	\$92.00
SANWA CP-7D	\$36.80
SANWA U-60D	\$43.70
SANWA LD520H	\$240.35
SANWA BX505	\$69.00
SANWA ZX505	\$101.20
SANWA CP7D CASES	\$4.60
SANWA TB-2 CASES	\$5.75
SANWA CX505 CASES	\$17.25
UNIVERSITY MVA50	\$46.00
UNIVOLT DT1314	\$41.40
UNIVOLT DT840	\$65.67
UNIVOLT DT830	\$115.00
UNIVOLT DT860	\$125.10
KAISE SK244	\$27.03
K.W TS2000	\$158.70
ARLEC 200H MULTIMETER	\$18.63

## POWER TRANSISTORS

MJ4502	PNP - 100 Volt - 30 Amp	\$4.35
MJ802	NPN - 100 Volt - 30 Amp	\$5.85
BUX80	NPN - 400 Volt - 10 Amp	\$4.63
BU126	NPN - 750 Volt - 3 Amp	\$2.49
BDV65B	NPN - 100 Volt - 10 Amp	\$3.11
BDV64B	NPN - 100 Volt - 10 Amp	\$3.11
MJ2955	PNP - 60 Volt - 115 Watt	\$1.62
MJ15003	NPN - 140 Volt - 20 Amp	\$5.10
MJ15004	PNP - 140 Volt - 20 Amp	\$5.10
2N3055	NPN - 60 Volt - 15 Amp	\$1.12

## ALL PRICES INCLUDE SALES TAX

## CENTRONICS CONNECTORS

### MAGRATHS THE RIGHT CONNECTION (AMPHENOL)

SOLDER TYPE	D' CONNECTORS	FLAT CABLE TYPE
25 PIN PLUGS	\$2.13	24 WAY PLUGS \$3.65
25 PIN SOCKETS	\$2.82	24 WAY SOCKETS \$5.37
9 PIN PLUGS	\$1.98	36 WAY PLUGS \$7.98
9 PIN SOCKETS	\$2.97	36 WAY SOCKETS \$7.98
15 PIN PLUGS	\$2.32	50 WAY PLUGS \$8.74
15 PIN SOCKETS	\$4.12	50 WAY SOCKETS \$9.66

### CENTRONICS CONNECTORS

### FLAT CABLE 'D' CONNECTORS

9 PIN PLUG	\$10.47
9 PIN SOCKET	\$6.90
15 PIN PLUG	\$7.84
15 PIN SOCKET	\$9.34
25 PIN PLUG	\$10.51
25 PIN SOCKET	\$11.71
37 PIN PLUG	\$15.53
37 PIN SOCKET	\$17.66

## GREAT BUYS ON COMPUTER PRODUCTS

BMC - BX 80 - Dot Matrix Printer	\$460.00
BMC - BM - 12EG 18 MHz 12" Monitor, Green	\$195.50
BMC - BM - 12EY 18 MHz 12" Monitor, Yellow	\$225.00
BMC - BM - 12A 15 MHz 12" Monitor, Green	\$173.56
BMC - PA900 Swivel & Tilt Base	\$28.75
Cicada 300 Data Modem (Telecom approved)	\$212.75
Mitsubishi M2896 - 63 8" DSDD Disk Drive	\$588.80
Mitsubishi M4854 - 5 1/4" DSDD Disk Drive	\$442.75

## TEXTOL ZERO INSERTION SOCKETS FORCE

16 PIN	\$10.83	28 PIN	\$14.49
24 PIN	\$10.06	40 PIN	\$17.83

## T.I. PERSONAL HOME COMPUTER TI-99/4A

Call us for the best price in town!



**EX STOCK**

You can buy just a video game - or you can get a full colour Home Computer

- Typewriter Keyboard
- 16K bytes RAM
- Expandable to 52K bytes RAM
- Easy to follow instructions
- Extensive range of programmes
- Educational
- Add-on expandability



# Mail Order... Promark Distributors... Mail Order

Your First Choice for High Technology Electronic Components  
(Founded 1976)

## COMPUTER GRADE ELECTROLYTICS

Metal can top screw terminals, High Current includes clamp and screws. Made by Siemens and Marcon.



10,000/16V...\$ 5.75	3,300/40V...\$ 5.50	4,700/63V...\$ 6.50
47,000/16V...\$13.25	4,700/40V...\$ 6.45	10,000/63V...\$12.25
100,000/16V...\$18.50	10,000/40V...\$ 8.85	10,000/100V...\$18.50
10,000/25V...\$ 6.60	15,000/40V...\$12.25	880/350V...\$15.85
22,000/25V...\$11.25	22,000/40V...\$14.25	3,100/450V...\$75.85
33,000/25V...\$13.50	47,000/40V...\$25.50	
47,000/25V...\$17.50	22,000/50V...\$13.50	

## TELEDYNE I.C.'S.

3 1/2 digit LCD DVM IC TSC7106...\$16.50	Superlow power 3 1/2 digit LCD DVM TSC7126...\$19.50
3 1/2 digit LED DVM IC TSC7107...\$16.50	Dual power MOSFET driver TSC450...\$ 4.95
12 bit CMOS A/D for uP TSC7109...\$19.50	15 bit CMOS A/D TSC800...\$35.50
4 1/2 digit CMOS DVM IC TSC7135...\$22.50	Ultra linear VCO TSC9400...\$ 6.45
4 digit LCD driver TSC7211...\$10.50	Stable VRef 1.22V TSC9491...\$ 2.45
4 digit LED driver TSC700...\$ 8.65	Super stable VRef 5V TSC9495...\$ 7.70

## OPTO ELECTRONICS

Siemen's and Optron

### LED'S, PHOTOTRANSISTORS & DIODES

HI-Power IR LED LD271A...\$0.75 (A)
Super-Power IR LED 600mw Peak OP290...\$2.25 (A)
Narrow Beam 6° IR LED SFH400...\$3.35 (A)
Submin IR LED LD261...\$1.00 (C)
Phototransistor BP103...\$1.10 (A)
Submin Phototransistor BPX81...\$1.65 (C)
IR Photodiode Flat Pack BP104...\$2.35 (F)
Photodiode VIS + IR with lens OP903...\$9.85 (D)
Luxmeter Photodiode BPW21...\$12.75 (B)
4 Quad Photodiode for optical trackers SFH204...\$25.50 (E)

### DISPLAYS

4 digit + driver DL1416...\$36.00 (M)
4 digit lge. + driver DL2416...\$45.00 (M)

### 7 SEGMENT HI-BRIGHTNESS 13.5 MM

Red common anode HD1131R...\$1.70 (O)
Red common cathode HD1133R...\$1.70 (O)
Green common anode HD1131G...\$2.05 (O)
Green common cathode HD1133G...\$2.05 (O)

### OPTOCOUPLERS

Telecom modem type SFH601...\$2.30 (J)
Gen. purpose 4N25...\$0.95 (J)
Gen. purpose 4N26...\$0.95 (J)
Darlington 4N32...\$2.15 (J)
Darlington 4N33...\$1.50 (J)
Darlington 4N35...\$1.10 (J)
Dual ILD74...\$2.75 (K)
Quad ILQ74...\$6.35 (I)
200V collector OPI6100...\$1.65 (J)
10KV isol OPI110...\$4.85
Triac driver OPI3020...\$1.95 (J)


### OBJECT SENSORS

Interruptor OPB813...\$3.50 (P)
Reflector OPB708...\$3.75 (H)
Mirror reflector B141...\$0.25 (L)

## SIEMENS MICROPROCESSOR & MEMORY

HYB4164P2 64K DRAM...\$8.50	SAB8155 RAM + 10...\$9.00
SAB8085 CPU...\$8.50	SAB8086 CPU...\$28.50
SAB8031 CPU...\$36.00	

## PACKAGES

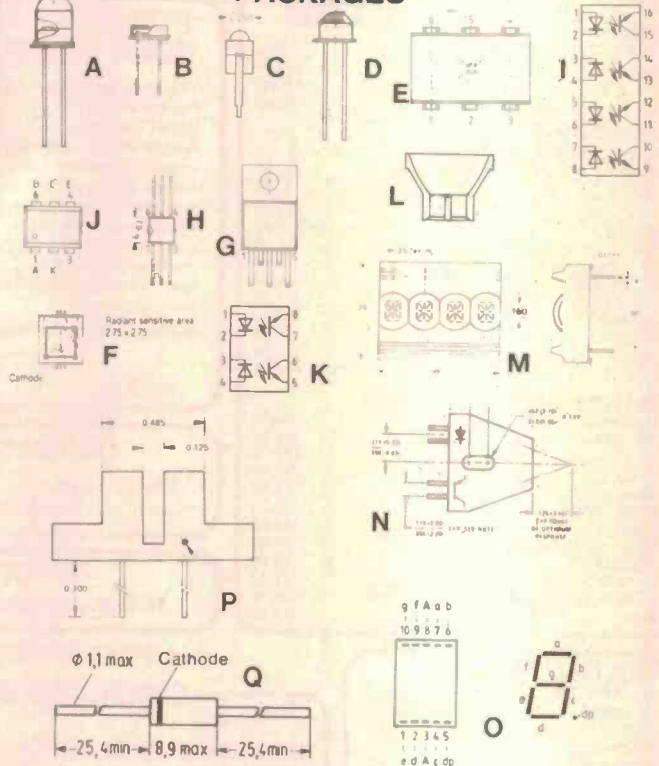

## SIEMENS COMPONENTS DATA BOOK 1983

This fantastic book has 600 pages of data on the SIEMENS range of semi-conductors, capacitors, ferrites, relays, thermistors, magneto detectors and all manner of exotic devices.

Really GREAT value at \$10.00 (includes postage)


## SUBMIN R. F. CHOKES



ALL VALUES 50c

2.2 Microhenry	100 Microhenry
3.3 Microhenry	220 Microhenry
4.7 Microhenry	330 Microhenry
10 Microhenry	470 Microhenry
22 Microhenry	1 Millihenry
33 Microhenry	3.3 Millihenry
47 Microhenry	4.7 Millihenry
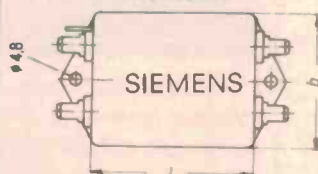
## PROTECT YOUR DATA WITH THE PROMARK PULSE PRUNER



The PROMARK PULSE PRUNER is a high energy metal oxide varistor and a multi-element balanced LC line filter which work together to clip spikes and hold back RF interference. These are a must for computer power inputs — Also great for Hi-Fi's to keep out taxi's, CB's, etc., from your Wagner & Strauss.

Rated 240V — 4 AMP  
\$22.50

## SIEMENS T092 TRANSISTORS SPECIAL!

All 10c each

BC547	BC556
BC548	BC557
BC549	BC558
BC550	BC559



## SPECTROL TRIMMERS, POTS AND DIALS

- 3/4" rectangular 20 turn cer. met type  
43P 100R, 200R, 500R, 1K,  
2K, 5K, 10K, 20K, 50K, 100K,  
200K, 500K, 1M ..... all \$1.50
- 3/8" single turn cer. met type 63P, 50R,  
100R, 500R, 1K, 2K, 5K,  
10K, 20K, 100K, 1M ..... all \$0.85
- Precision 10 turn wire-wound  
pot type 534, 500R, 1K, 2K,  
5K, 20K ..... all \$10.50
- 100K ..... \$17.50
- 3 digit dial to suit 534, mod 15 ..... \$25.50



### I.C. SOCKETS

- Burdndy type DILB pcb mounting tin plated mil. spec.
- |                  |                  |                  |
|------------------|------------------|------------------|
| 8 pin ..... 13¢  | 18 pin ..... 28¢ | 24 pin ..... 36¢ |
| 14 pin ..... 20¢ | 20 pin ..... 30¢ | 28 pin ..... 40¢ |
| 16 pin ..... 25¢ | 22 pin ..... 33¢ | 40 pin ..... 60¢ |

## E.C. POWER FERRITES

Includes 2 corehalves, bobbin and clamp

- |                   |                   |
|-------------------|-------------------|
| EC35 ..... \$2.95 | EC52 ..... \$5.35 |
| EC70 ..... \$8.45 |                   |



## FUJI POWER RELAY — SPECIAL!

2 changeover, 10 amps per contact — 240 AC.

- |                                |                                |
|--------------------------------|--------------------------------|
| 12V type HH62P12V ..... \$4.45 | 24V type HH62P24V ..... \$4.45 |
|--------------------------------|--------------------------------|

## SIPMOS N CHANNEL POWER FETS

- |                               |                               |
|-------------------------------|-------------------------------|
| BUZ10-50V/12A ..... \$9.25    | BUZ15-50V/37A ..... \$32.50   |
| BUZ20-100V/12A ..... \$9.25   | BUZ23-100V/10A ..... \$12.35  |
| BUZ30-200V/7A ..... \$7.30    | BUZ24-100V/32A ..... \$23.70  |
| BUZ80-800V/2.6A ..... \$15.50 | BUZ84-800V/5.3A ..... \$33.75 |
| BUZ40-500V/2.5A ..... \$7.30  | BUZ18-50V/37A ..... \$37.95   |

- |                              |                    |                              |
|------------------------------|--------------------|------------------------------|
| <b>SCR'S</b>                 | <b>TO 220 PACK</b> | <b>TRIACS</b>                |
| C1053M 800V 6A ..... \$1.32  |                    | XD10K70 8A 700V ..... \$1.68 |
| D1046M 700V 10A ..... \$1.32 |                    | XC10H70 6A 700V ..... \$1.44 |


## SIEMENS LEDS

We have an enormous range of SIEMENS coloured LEDS, red, yellow, green, orange, from 1 mm diameter to 3 mm and 5mm types, round, square, rectangular, triangular, arrow, pointer, bar graph, two-colour, auto-flashing. Too numerous to list here. Send large S.A.E. for LED catalogue.

### TUBULAR SOLID TANTALUM CAPS

#### MILITARY GRADE CSR13


- |                        |
|------------------------|
| 2.2µF/35V ..... \$0.50 |
| 3.3µF/35V ..... \$0.50 |
| 6.8µF/35V ..... \$0.50 |
| 47µF/6V ..... \$0.50   |
| 100µF/10V ..... \$1.75 |

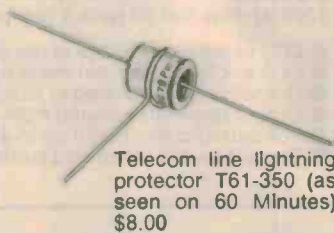

## SIEMENS MINIATURE PCB RELAYS 1 AND 2 CHANGE OVER

Contacts 1 Amp, max voltage 120AC, plugs in IC socket.

- |                                    |
|------------------------------------|
| 1 c/o 6V type 6V103 ..... \$2.10   |
| 1 c/o 12V type 12V103 ..... \$2.10 |
| 1 c/o 24V type 24V103 ..... \$2.10 |
| 2 c/o 6V type 6V104 ..... \$3.25   |
| 2 c/o 12V type 12V104 ..... \$3.25 |
| 2 c/o 24V type 24V104 ..... \$3.25 |

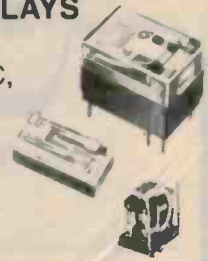

## SPECIAL IC'S FROM SIEMENS

- |  |   |
|--|---|
| Light spot driver 16 LEDS<br>UAA170 ..... \$3.85           | IGHZ divide by 64 prescaler<br>SDA2101 ..... \$7.95 |
| Light band driver 12 LEDS<br>UAA180 ..... \$3.85           | Photo sensitive amp<br>TFA1001W ..... \$4.85 (H)    |
| 3 Tone chime SAB0600 ..... \$6.60                          | IR photo-preamplifier<br>TDA 4050 ..... \$4.85      |
| Touch dimmer IC S576A ..... \$7.65                         | Metal detector IC<br>TCA205A ..... \$4.65           |
| AC motor speed controller<br>TLB3101 ..... \$5.50          | Pot core + bobbin for<br>TCA205A ..... \$0.85       |
| Long period timer<br>SAB0529 ..... \$7.00                  | 14 Watt audio amp<br>TDA2030 ..... \$5.95 (G)       |
| Linear magnetic field<br>detector SAS231W ..... \$7.00 (H) | AM radio IC mw-sw<br>TDA1046 ..... \$8.75           |
| Switch-mode driver IC<br>TDA4718A ..... \$9.95             | FM radio control RCVR IC<br>S1469 ..... \$9.20      |
| 8 Chan remote control<br>TX SLB 3801 ..... \$7.35          | FM IF + demodulator<br>TDA1047 ..... \$5.60         |
| 8 Chan RX SLB3802 ..... \$9.95                             |   |
| VHF mixer S042P ..... \$4.65                               |   |

## !SPECIALS!

- 5W ZENERS  
5.6V \$0.50  
12V \$0.50 (Q)

- Super Bright Red LED  
CQV51-H (150 mcd) \$0.40 (A)

- Hi-Power IR LED  
LD242 (30mW output) \$0.85 (D)

!SPECIAL!


- Little Big Board  
(Includes sockets for all IC's)  
\$422.00  
No discount on this item.

!SPECIAL!
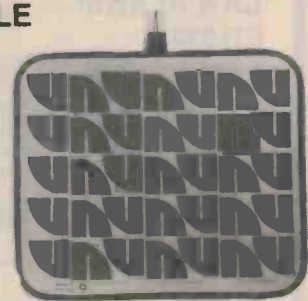
## SOLAR POWER MODULE

The ARCO solar type M82 is a compact 36 cm x 31 cm array providing open circuit 20V and short circuit 600mA. This unit is ideal for 12V battery charging for boats, caravans, etc. It can also be used for powering pumps, radios, electric fences, beacons, etc. Made in U.S.A.

Price . . . \$260.00  
(No discount on this item)



ALL COMPONENTS OFFERED ARE BRAND NEW, PREMIUM GRADE DEVICES. SALES TAX IS INCLUDED FREIGHT CHARGE IS \$3.50 PER ORDER. IF YOU REQUIRE DATA AND APPLICATIONS ON ANY ITEM SEND A STAMPED SELF-ADDRESSED ENVELOPE.

D.I.S.C.O.U.N.T.S. . . . TOTAL ORDER VALUE . . . up to \$50 NETT; \$50 to \$100, less 10%; \$100 and over, less 15%.

**P.O. BOX 381 CROWS NEST N.S.W. 2065. PHONE (02) 439 6571**

BANKCARD WELCOME

(No discount on B/Card Sales)



# ALL ELECTRONIC COMPONENTS


118 LONSDALE STREET, MELBOURNE, VIC. 3000. TEL 662-3506.

MAJOR STOCKISTS OF ALL GENERAL RADIO AND ELECTRONIC COMPONENTS

## KIT SET SPECIALIST

## JOIN THE GOLDRUSH

### ETI 1500 KITSET

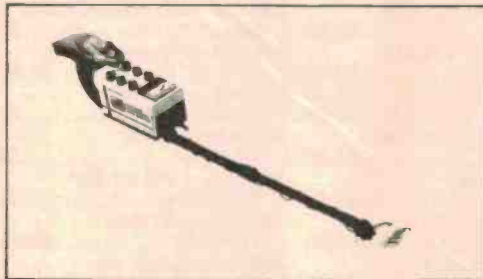

Superb unit featuring:

- Tune and discriminate.
- 4 modes of operation.
- VLF/TR design.
- Ground balance.
- Auto balance push buttons.
- Pre-wound search heads.
- Very professional unit.
- Approximately 1/3 price of many similar commercial built up locators.
- Audio and meter indication. Lets you know when to rejoice.

**PRICE: \$193.50 including pre-drilled and punched case, or \$179.99 including blank case. Plus \$10.50 p&p reg. post.**

### Stac Timer

ETI 650

**\$135.00**

incl. tax

Plus \$6.00 p&p



This unit has four different programmable outputs, clock controlled switch-ons/switch-off times. Selected days from the seven or eight day cycle can be "skipped". Ideal for operating air conditioning, fish tanks, hi-fi systems, tape recorders, slide & movie projectors, laboratory control, video equipment, etc.

### HOUSE ALARM

ETI 582

This complex alarm system is quite easy to construct.

Features: Exit/entry delay: Resets after 10 min: Has multi-loop circuits: Microwave, Infra—red and Ultrasonic devices can be added into the circuit. Includes case. Horn speaker, accessories and detector units available.

**\$87.50 INCL. TAX**



### CAR ALARM

ETI 330

A false-alarm proof unit senses current drop across car battery.

Features exit entry delay: Shorts out ignition coil: Pulses car horn: LEDs indicate when alarm is armed and when it has been triggered: Easy installation: Complete with die-cast case.


**\$35.50 INCL. TAX**



### 'PRO' BENCH POWER SUPPLY

ETI 142  
0-30 VOLTS;  
0-15 AMPS!

\$272.64 plus \$10.50 pack & reg. post.

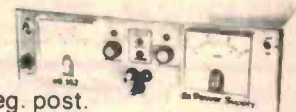

A phenomenal supply with professional finish and professional performance. It features 20 mV regulation from zero to full load, 10 mV ripple and noise, voltage and current metering on separate meters, overload protection and adjustable current limiting. Sturdy metal cabinet with silk-screened aluminium front panel supplied.

### LABORATORY POWER SUPPLY

ETI 163  
0-40 Volts  
0-5 Amps

\$208.47 Plus \$10.50 pack & reg. post.

- LED to indicate voltage made operation.
- LED to indicate current made operation.
- Output switch provided to isolate supply output.
- Output terminals isolated from chassis.
- Full output current right up to 4 ov.
- Current switch for setting current limit value.

**We stock the largest range of ETI and EA Kits in Australia.**


**Call in and see our comprehensive catalogue.**

**EA VIDEO ENHANCER OCT 1983 ELECTRONICS AUSTRALIA**  
Sharpens picture detail when copying from one video tape to another. Can be used between two VCR's—between video camera and VCR—Or between VCR and T.V. This extremely popular kit comes complete with case & front panel. Only \$39.57 incl. tax.


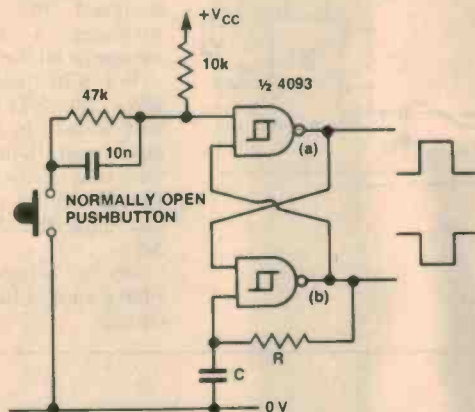
# IDEAS FOR EXPERIMENTERS

These pages are intended primarily as a source of ideas. As far as reasonably possible all material has been checked for feasibility, component availability etc, but the circuits have not necessarily been built and tested in our laboratory. Because of the nature of the information in this section we cannot enter into any correspondence about any of the circuits, nor can we produce constructional details.



## CMOS monostable

Geoff Nicholls, ETI project engineer, designed this circuit which was adapted from the familiar RS flip-flop by adding R and C.

Two gates, (a) and (b) from a 4093 quad Schmitt NAND gate, form a useful monostable multivibrator.

On power up, C ensures that the mono is in the reset state, and is charged up to the rail by R. If the pushbutton is operat-

ed, gate (a) goes high and (b) goes low. R then discharges C to the switching point when the monostable resets, thus charging C back up ready for the next period.

The recharging may be sped up by adding a diode across R, with the cathode to the capacitor side. The timing period, with R = 1M and C = 100n, was 100 ms.

## Two mode light show


This light show circuit was designed by A. Taylor of Glen Forrest, WA. It has two modes — chaser and pulser.

In the first mode, two inverters are set up as an oscillator with a frequency which varies from about 3 Hz to 300 Hz (adjustable by VR1). This clocks a 4017 and flashes the LEDs in sequence; if set up in a line or a circle they appear to chase each other.

In the 'pulse' mode a 555 timer is used to provide an output pulse whenever the input goes above 0.5V. The input could be an audio signal or an output from a solar cell; it could be used to respond to other flashing lights like this.

The sensitivity control VR3 sets the voltage which the input must exceed in order to trigger the device. VR2 sets the length of the output pulse and hence sets the number of pulses that the circuit can respond to in a given period. It cannot trigger again until pin 3 has gone low. By adjusting this control a variety of different effects can be obtained.

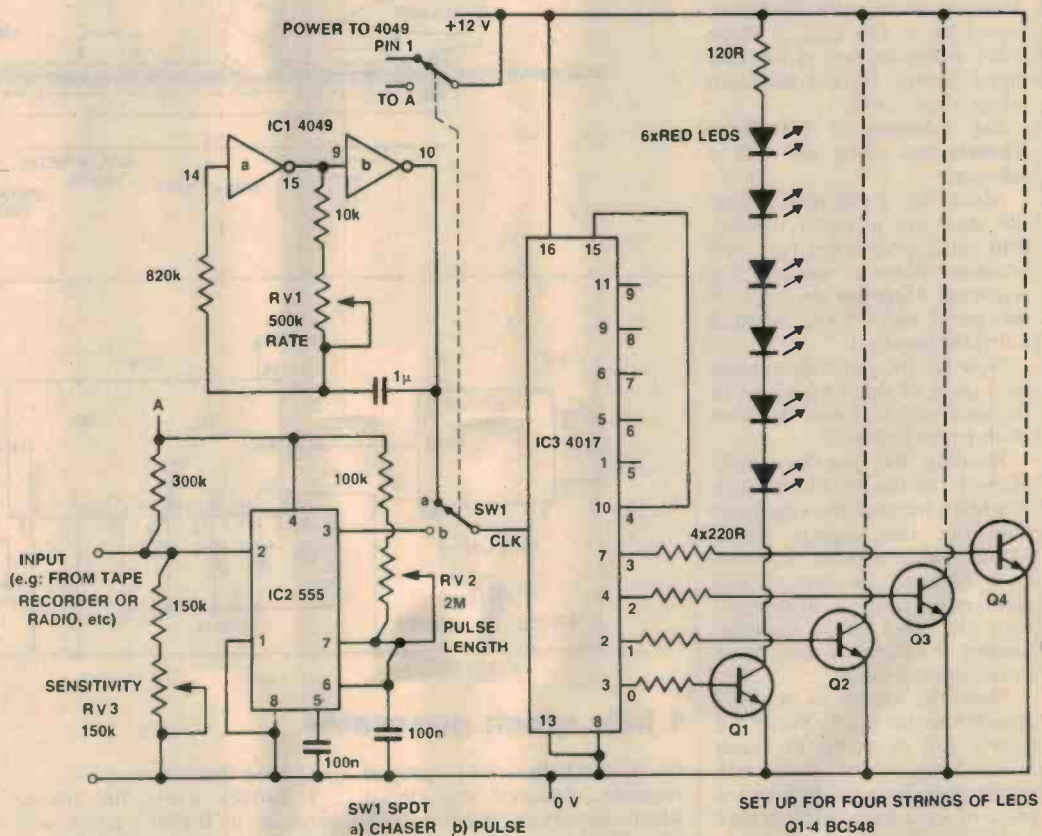Up to 10 LED strings can be used off the 4017. One pin, the next highest in the sequence,



must go to reset, unless all 10 output pins are used, to prevent an annoying pause in the sequence.


With a 12 volt supply up to six

LEDs (1.6V drop each) can be used per transistor unless two strings of LEDs are paralleled, each with its own limiting resistor, per transistor.

The 120R resistor limits the current to about 20 mA per string and therefore two strings per BC548 can be used without exceeding its ratings.



## Novel position for pilot light

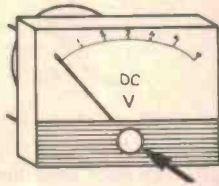

LED REPLACES THE ADJUSTING SCREW

When V. Starr of Higgins, ACT was finishing the ETI Dual Power Supply project he was trying to decide on the best place to put the pilot light

and came up with this idea.

The LED was placed into the hole used to adjust the needle movement, after removing the adjusting screw. In my case a 5 mm LED fitted almost perfectly.

The plastic case on most meter movements is easy to prise off. You can adjust the movement before replacing the plastic front and after fitting in the appropriate LED.


Take care in running wires or the appropriate dropping resistor from the LED.

## Mosquito imitator

Matthew Sorrell of Clarence Park SA is 10 years old and designed this circuit which produces a sound like a mosquito buzzing.

For Christmas 1978 I was given the ETI-062 AM tuner with which I had a great deal of enjoyment. Since then I have built other projects from Project Electronics on a SK-10 board including the Morse Practice Set.

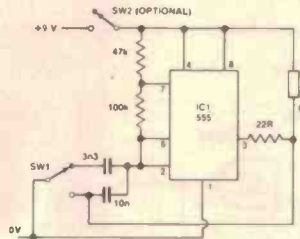My dad brings home ETI and I have a lot of fun trying out the circuits.



## Drilling Scotchal 8005 panels

Scotchcal 8005 panels (black on Aluminium) are difficult to drill, especially in the case of large holes where tearing of the thin metal occurs. Burred and torn edges often result.

Ian Johnston of Mt Eliza, Victoria has come up with a solution.



Mount the panel material on the sheet metal panel surface, drill small pilot holes (say 1/8") wherever holes of any size are required. Mark on the back of the panel surface the finished hole size required.

Now lay the panel face down on a piece of sheet metal cut to the same size with two layers of plain paper between.

Keeping the panels exactly aligned, run the 1/8" drill through two holes (near to the edge) and bolt the two panels firmly together with 1/8" bolts. Now drill each hole to its correct size (preferably using a drill-press) with the heel of a G-clamp holding the panels firmly down to the drilling table.

Place the clamp as close as possible to the drill. Move the panel, and re-clamp for each hole. Neat, clean holes will result. It is best to drill into a piece of scrap metal plate placed under the work.

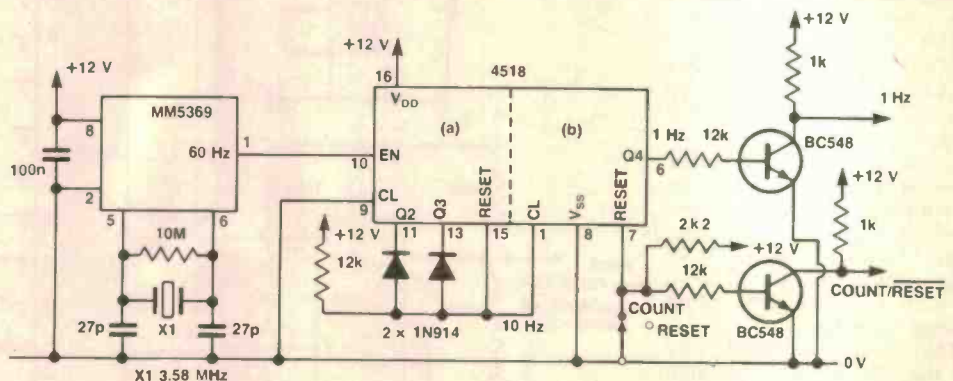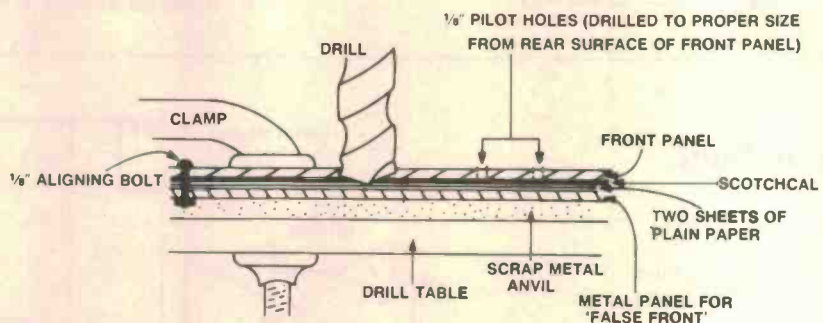When drilling is finished the extra plate can be used for a 'false front', which many instrument panels require anyway.



## 1 kHz clock generator

Geoff Nicholls, ETI project engineer, designed this circuit which has been used with a Microbee to get lap times at sporting events.

The 1 kHz and COUNT/RESET signals were connected to CLK and CTS of the serial port, and the port supplied the

+12 V to the circuit.

I initially wrote the timing program in BASIC, which was able to poll the serial port fast enough to work alright. However, the latest program is, in machine code and takes advantage of the Z80 PIO's control mode interrupt feature.

The COUNT/RESET switch resets the last decade divider, so the overall timing is accurate to within 0.1 second of switching to COUNT. The other half of the dual decade divider is set up to divide by six by resetting the counter to zero when Q2 and Q3 are high.



## ELECTRONIC HOBBYIST!

Do You Live In ...

Ringwood

Lilydale

Boronla

Wantirna

Bayswater

Croydon

Mooroolbark

etc ...

We can supply your components  
at city prices

**Ian J. Truscott  
Electronics**

Cnr Eastfield & Bayswater Roads,  
South Croydon, Vic.  
Telephone (03) 723-3860

FROM THE PUBLISHERS OF  
ELECTRONICS TODAY INTERNATIONAL

# ETI CIRCUITS No 4

\$2.95\*

contains a wide range of circuits, ideas and data for the electronics enthusiast, arranged in 15 categories, including: Alarms, Audio, Computers, Games, Triggering & Switching, Techniques, RF and Test & Measurement.

**\$2.95**

Available from newsagents, selected electronic suppliers or direct from ETI Magazine, P.O. Box 227, Waterloo NSW 2017. Please add \$1.00 for post and handling if buying by mail.

## Engineered With Vision



## Built With Care


**POWER-SONIC**, a leading manufacturer of rechargeable batteries, offers a complete line of both sealed lead-acid and nickel-cadmium batteries, engineered to meet the toughest specifications. State-of-the-art design, meticulous quality control and time-proven performance are the reasons why engineers are specifying **POWER-SONIC** batteries; competitive prices and an outstanding track record for product reliability and on-time delivery have convinced buyers. For more information or a copy of our catalog, contact:

**POWER-SONIC**

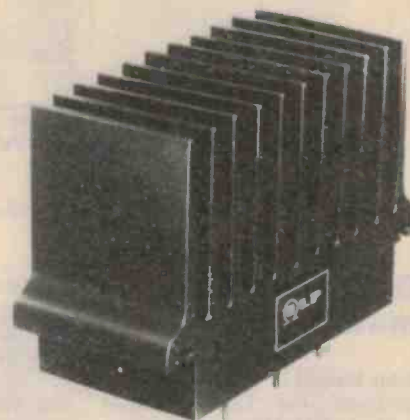**SEALED RECHARGEABLE BATTERIES**

100-102 Buckingham Street,  
Surry Hills, 2010,  
P.O. Box 171, Darlinghurst, NSW 2010.  
Ph: (02) 699 2722, 699 2521.

Electromark are pleased to present the third generation of I.L.P. Modular Amplifiers.



This new range of Bipolar and Mosfet Modules offers optimum convenience and flexibility to the constructor and manufacturer.

A choice of Bipolar Amps from 15 watts to 180 watts (4 or 8 ohms) or Mosfet Amps of 60 and 120 watts (4 or 8 ohms) or 180 watts into 4 ohms are available.

Matching these amplifiers are the range of 19 types of pre-amp or mixer modules in the well known I.L.P. compact plug-in case.

★New to the range are the HY-6060 Stereo 30 watt amplifiers and the C1515 Stereo Car booster amps.

★Electromark also stock the whole range of I.L.P. Toroidal transformers. (240 V Primaries)


**ELECTROMARK  
Pty. Ltd.**

Write for information on any of these products to:

**Electromark Pty. Ltd.,  
43 Anderson Road,  
(P.O. Box 184)  
Mortdale, NSW 2223**




# IDEAS FOR EXPERIMENTERS

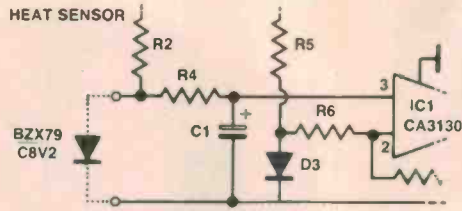
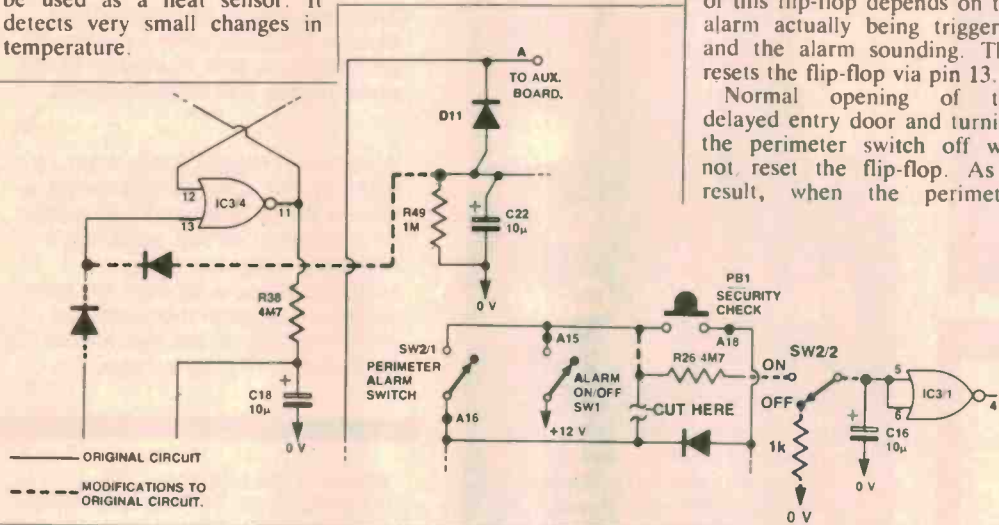
## GSR monitor modification

John Russell of Whyalla SA has modified the GSR monitor project, ETI-546, so that it can be used as a heat sensor. It detects very small changes in temperature.

The circuit diagram illustrates the input section of the GSR monitor with the necessary modification shown dotted in. It can be mounted in a probe or in situ with the GSR monitor.



## ETI-582 House alarm modification

This goes way back to one of the early projects. Lloyd Davies of Paddington NSW had a few problems when constructing the house alarm project, ETI-582, published in ETI July 1977.

I found that the unit was extremely unreliable when switching the perimeter/internal switches on and off, this action alone being sufficient to cause the alarm to trigger. The fault lies in the way the flip-flop IC3/3 and 4 is reset. The reset of this flip-flop depends on the alarm actually being triggered and the alarm sounding. This resets the flip-flop via pin 13.

Normal opening of the delayed entry door and turning the perimeter switch off will not reset the flip-flop. As a result, when the perimeter

switch is again turned on the alarm will sound because the circuit of R38 and C18 is at 1 rather than 0.

This fault was corrected by the addition of a reset facility from A17 and a diode (see the modified circuit).

Another problem arose because the time delay of 30 seconds on leaving the house is taken from the time the security button is depressed. This is not a serious difficulty, but could cause erratic operation and I decided to use a double-pole switch for SW2; this caused the time delay to start when the perimeter switch is turned on. The 1k resistor was added to discharge the delay circuit of R26 and C16, allowing the house to be entered and exited in quick succession.

I also found the use of NiCd batteries and a constant current charger to be very useful.

## C'MON, ALL YOU EXPERIMENTERS!

You'll have to do better than the last lot of entries — we couldn't find a decent idea worthy of the prize. It's holiday time, so redouble your efforts and get those entries in!

## 'IDEA OF THE MONTH' CONTEST

### COUPON

Cut and send to: Scope/ETI 'Idea of the Month' Contest, ETI Magazine, P.O. Box 227, Waterloo NSW 2017.

"I agree to the above terms and grant *Electronics Today International* all rights to publish my idea in ETI Magazine or other publications produced by it. I declare that the attached idea is my own original material, that it has not previously been published and that its publication does not violate any other copyright."

\* Breach of copyright is now a criminal offence.

Title of Idea .....


Signature .....

Name .....

Date .....

Address .....

Postcode .....

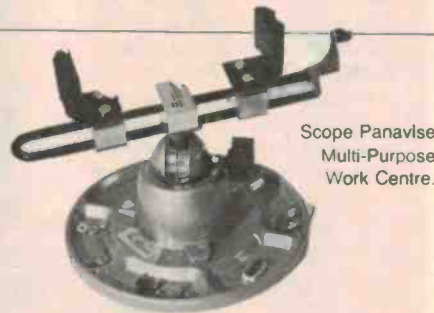

Scope Panavise Multi-Purpose Work Centre.

Scope Laboratories, which manufactures and distributes soldering irons and accessory tools, is sponsoring this contest with a prize given away every month for the best item submitted for publication in the 'Ideas for Experimenters' column — one of the most consistently popular features in ETI Magazine. Each month, we will be giving away a Scope Panavise Multi-Purpose Work Centre, Model 376/300/312, comprising a self-centering head (376), standard base (300) and tray base mount (312), all worth about \$90! Selections will be made at the sole discretion of the editorial staff of ETI Magazine. Apart from the prize, each winner will be paid \$10 for the item published. You must submit original ideas of circuits which have not previously been published. You may send as many entries as you wish.

### RULES

This contest is open to all persons normally resident in Australia, with the exception of members of the staff of Scope Laboratories, The Federal Publishing Company Pty Limited, ESN, The Litho Centre and/or associated companies.

Closing date for each issue is the last day of the month. Entries received within seven days of that date will be accepted if postmarked prior to and including the date of the last day of the month.

The winning entry will be judged by the Editor of ETI Magazine, whose decision will be final. No correspondence can be entered into regarding the decision.

The winner will be advised by telegram the same day the result is declared. The name of the winner, together with the winning idea, will be published in the next possible issue of ETI Magazine.

Contestants must enter their names and addresses where indicated on each entry form. Photostats or clearly written copies will be accepted but if sending copies you must cut out and include with each entry the month and page number from the bottom of the page of the contest. In other words; you can send in multiple entries but you will need extra copies of the magazine so that you send an original page number with each entry.

This contest is invalid in states where local laws prohibit entries. Entrants must sign the declaration on the coupon that they have read the above rules and agree to abide by their conditions.

PRIZE WORTH \$90!



# OVER THE COUNTER

This occasional column introduces readers to those people on the other side of the counter in the electronics retail business — where you buy your equipment and component requirements. It serves to 'put a face' to the people who own and run the businesses you may deal with in the course of your job or pursuing your hobby, and to give some background on the business itself.

## Sheridan Electronics

164-166 Redfern St, Redfern NSW 2016  
(02)699-6912, 699-5922

MIKE SHERIDAN is something of an institution in the Sydney electronics retail scene. He's been in the business now for 13 years, first as M.S. Components, latterly as Sheridan Electronics, and has always been located in Redfern; in Regent St until 1976 then moving to the present location in Redfern St, the suburb's 'main drag'.

If location counts for much, then Sheridan Electronics seems well located. Many major commercial customers are nearby — Sydney University, Wormalds Security, various Telecom inner-city establishments etc. The store is located a short block away from Redfern station and Redfern post office is less than 100 metres further on — very handy for mail order customers. Sheridan Electronics has 'commanded' the locality ever since opening. Indeed, a certain multinational electronics retail chain opened a branch in Redfern Street almost opposite them some years ago, but after a year or so of desultory trading, they closed up and sought greener pastures.

Sheridan Electronics is a family business; Mike and his energetic son Barry, managing it between them. You can meet the proprietors behind the counter almost any day you care to pop in. They pride themselves on low prices and a huge range of components.

"Customers tell us we have the widest range of components they've ever seen," Mike reports. "We keep our prices low, always stock a wide range of just about every type of component and offer friendly personal service."



Apparently, Barry was instrumental in stocking a huge range of component data books recently. "If you sell components, you've got to have data," Barry says. On a


set of floor-to-ceiling shelves about three metres wide you'll find data books from major semiconductor manufacturers like Fairchild, General Electric, National Semiconductor, Motorola and others.

The Sheridans have never produced a catalogue because, as Mike and Barry say, "price movements — both up and down — make a catalogue obsolete almost as soon as you produce it."

"Also, the cost of a catalogue raises prices and we like to keep our prices low."

Sheridan Electronics' business has greatly expanded in the past four years, they say, largely as a result of broadening the product range offered. Apart from the 'run-of-the-mill' components, you'll find all sorts of power devices, opto-devices, RF components and ferrites in the store. They also specialise in manufacturers' surplus components — and it's possible to pick up some top bargains almost any time. Whilst a major customer group is the hobbyist, industry and government instrumentalities represent a significant slice of their sales. Current turnover is reported to be around the \$1 million mark. ●

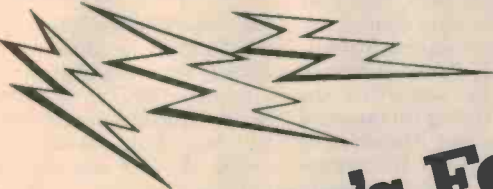

  
**If Athlete's Foot has got your  
toes in a shocking state...**  
Try Tinacidin. Pull the plug on the burning,  
itching, prickly pain of Athlete's Foot... fast!  
At pharmacies everywhere.

SCHERING CORPORATION U.S.A., AUSTRALIAN SUBSIDIARY  
— ESSEX LABORATORIES PTY. LTD., BAULKHAM HILLS, N.S.W.  
Health Care is our business

PM6067/82 SX 8914/3



# SHOP AROUND

## Newcomers

We are happy to welcome two newcomers to the Sydney electronics scene, one in the inner city, the other out west.

If you're looking for ready-made printed circuit boards for your projects, or if you want boards made up from your own artwork, then try **Better PC Boards**, 112 Robertson Road, Bass Hill 2197. (02)645-1241.

Sydney's latest electronics retail outlet is called **Geoff Wood Electronics**, and is located in historic downtown Rozelle at 656A Darling St, just off Victoria Road, opposite the 105-year-old school and near the corner of National Street. What a coincidence, G.W. specialises in National semiconductors! Proprietor is the affable Geoff Woods, who has been in the trade around 30-odd years (some of them very odd!); a familiar face behind the counter at a certain long-established electrical/electronic despatch house and previ-

ously known on the 600 ohm line as 'radio despair'! (Not a broadcast station.) Geoff's knowledge of the business and his contacts are legion. His semiconductor inventory has to be seen to be believed.

Meanwhile, **Avtek** now has a second store, located in Sydney's south-western suburbs. If Avtek's York St store could be described as 'adequate', the Enfield store is positively palatial! It's located at 172 Liverpool Rd, Enfield, and is open Sundays. Check your requirements by phone on (02)745-2122.

## ETI-1502 psychrometer

Be your own weatherman! This project will likely be stocked as a kit by Jaycar in Sydney and **Rod Irving Electronics** in Melbourne, for starters. You might also try **Altronics** in Perth and **All Electronic Components** in Melbourne.

Components for the project

should be generally available, with the exception of the metallised film capacitors used. This is where we put in a plug for low-voltage metallised poly capacitors. They are high-quality, have low self-inductance and are packaged with a 5 mm pin spacing in values right up to 1u! They are good for all applications from bypassing to coupling (dc to MHz), timing to... whatever. And they're cheap. Because of their small size, you can fit them where you can't fit greencaps. And they're cheap.

Wouldn't it be a good idea if your favourite electronics store stocked them? Low-voltage metallised poly capacitors made by **Wima** are distributed by **Semikron** (02)745-4533. The same sort of capacitor, with 5 mm pin spacing, made by **Ernst Roderstein**, are distributed by **Mayer Kreig** (02)684-1900. Values from 150n to 1u are type MKT 1826, values below that are type MKT 1817.

The temperature sensors for this project employ copper-constantin thermocouple wires which can be obtained from scientific supply houses — see your local phone directory (Selby Scientific carry it).

If you want to etch and drill your own pc board, positive or negative film artwork can be obtained from 'ETI-1502 Artwork', ETI Magazine, P.O. Box 227, Waterloo NSW 2017, for the positively low price of \$2.80, post paid. Make sure you request positive or negative, according to your requirements.

## ETI-1518 deluxe video enhancer

Put the 'punch' back into your pictures with our deluxe enhancer. At time of going to press, the following firms indicated they would be supporting the project: **Rod Irving Electronics** in Melbourne and **Altronics** in Perth. Try also **All Electronic Components** in Melbourne. In any case, all parts should be available over the counter virtually anywhere.

If you're making your own pc board and/or front panel Scotchcal, positive or negative film of the artwork is available from us. The pc artwork costs \$1.20, the front panel artwork \$3.40, post paid. Send your orders to: 'ETI-

1518 Artwork', ETI Magazine, P.O. Box 227, Waterloo NSW 2017. Make sure you ask for the artwork you want (pc board or front panel, or both) and specify positive or negative film according to what you require.

## ETI-674 Microbee joystick

Bound to be a popular project! We understand that kits will be available from **Altronics** in Perth Jaycar in Sydney (four locations), plus **Rod Irving** and **Magraths** in Melbourne — just for starters. Try **Avtek** in Sydney, too. They're an Altronics agent. With the exception of the joystick itself, components are generally available. The joystick, though, will likely be stocked by several firms as a standard component.

Making your own pc board and want film of the artwork? Just send \$2.70 in rust-proof money or its equivalent to: 'ETI-674 Artwork', ETI Magazine, P.O. Box 227, Waterloo NSW 2017.

## Project 658 RS232 breakout box

Every computer hobbyist should have one! Occasions will inevitably arise when you need to sort out that 'standard' RS232 interface. All the bits are 'bog standard', as they say, available virtually anywhere. Most stores stock super-bright LEDs these days, but the Hewlett-Packard types specified are recommended. Shop around.

## ETI-750 6 m beam

Get amongst the long-haul DX on 50 MHz or slide on up to 53.450 MHz for a chat on the FM channel — you can do it with this beam. Specialist aluminium supply houses (i.e. Alcan centres) stock the 9.5 mm aluminium tube, and some will even cut it to length for you. See your local phone directory. Some hardware stores stock 9.5 mm aluminium tube, too. Wood and screws can be purchased from hardware stores. If you're into the 'plumber's delight' construction, try **Dick Smith Electronics** for element-to-boom clamps (catalogue no. D-4652).

## DIGITAL MULTIMETERS THAT MEASURE CAPACITORS



Ranging in size from 650 Watts with single or multiple outputs. Prices start from \$85.00

### \$100 COMPUTER PRODUCTS

- 64k static Ram Boards, 150ns Chip access time, 32 x 2k windows switch selectable anywhere in 64k. \$420.00 + Tax.
  - 512k Disc emulator expandable to 4 megabytes. Includes software + print spooler. Battery back-up available. \$1299.00 + Tax.
  - I/O Board 8 Serial & 2 x 8 bit parallel ports. Real time clock. Battery back up. 8 level interrupt controller \$564.00 + Tax.
  - 6 Mhz Single Board computer. 128k Bank select memory WD2793 Disc controller. Suitable as bus master for multiuser systems. \$845.00 CP/M 3.0 & Turbo-Dos available (extra)
  - CP/M & MP/M Software Utilities. 8" ss/d IBM format \$29.50.
- cp/m & mp/m are trade marks of Digital Research Inc.

## LAMRON PTY. LTD.

P.O. Box 438, 20 Stamford Ave., Ryde, N.S.W. 2112 Ermington, 2115 85-2599, 85-6228 Thx. AA71551 Lamron.

### BANKCARD

Name .....  
Address .....  
Card No. ....  
Expiry date .....  
Signature .....

MODEL	7601	7605	7901	7905
Test measure	Transistor		Capacitors	
DC Volt	100µV-1000V		100µV-1000V	
Basic Accuracy	.1% .5%		.1% .5%	
AC Volt	100µV-750V		100µV-750V	
Basic Accuracy	.5% 1%		.5% 1%	
DC Current	1µA-10A		1µA-10A	
Basic Accuracy	.5% 5%		.5% 5%	
AC Current	1µA-10A		1µA-10A	
Basic Accuracy	.5% 5%		.5% 5%	
Resistance	.1-20Meg		.1-20Meg	
Basic Accuracy	.2% 5%		.2% 5%	
Hfe @ 10µA	0-1000			
Capacitance	## ##		1pF-20µF	
Basic Accuracy	## ##		5%-1.5%	
Diode test	1mA 1mA		1mA 1mA	
PRICE	112.50	89.50	125.50	101.90

6 month warranty. Test leads, carry case and instruction manual supplied. P/P NSW \$3.60 VIC \$4.50 All others \$5.50

### SWITCHING POWER SUPPLIES

The latest state-of-the-art switching technology in twenty five off the shelf models, from fan cooled types to open frame types. Nine major sizes are available.



**BANKCARD HOLDERS -  
PHONE YOUR ORDERS  
TOLL FREE!**

**AUSTWIDE**

**NEXT DAY DELIVERY**

**ALTRONICS**

**008-999-007**


**VIA  
JETSERVICE**  
(CAPITAL CITY & SUBURBAN AREAS)

**TOP QUALITY  
XTALS**

			ea.	10 +
Y 1000	1.0000 mHz	Parallel	\$11.50	\$10.25
Y 1003	1.8432 mHz	Parallel	9.50	8.75
Y 1006	2.0000 mHz	Parallel	7.50	6.75
Y 1010	3.5875 mHz	Series	3.00	2.75
Y 1012	4.0000 mHz	Parallel	5.00	4.50
Y 1015	4.1940 mHz	Parallel	5.00	4.50
Y 1017	5.0000 mHz	Parallel	5.00	4.50
Y 1018	6.0000 mHz	Series	5.00	4.50
Y 1019	8.0000 mHz	Series	5.00	4.50
Y 1020	10.0000 mHz	Series	5.00	4.50
Y 1025	12.0000 mHz	Series	5.00	4.50
Y 1030	16.0000 mHz	Series	5.00	4.50

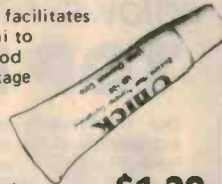**HEATSINK COMPOUND**

Heat conducting paste facilitates heat transfer from semi to Heatsink. One tube good for up to 30 T03 package semiconductors.



H 1600...7.5g Pack..... **\$1.20**  
New trade pack  
H 1610...150g Pack..... **\$7.50**  
SAVE UP TO 33%

**VELOSTAT**

Non-static sheeting for storing CMOS IC's, LSI's etc. 1000 times better than aluminium foil. Will store up to 150 IC's on one 225 x 150mm sheet.

H 0500..... **\$3.50 per sheet**

**DIL SWITCHES**


GOLD PLATE SELF WIPING CONTACTS



	EA	10UP
S 3050		
4 Way	\$1.50	\$1.35
S 3060		
8 Way	\$2.00	\$1.75

**NEW HITACHI F SERIES  
SQUARE SCREEN DUAL BEAM CRO**

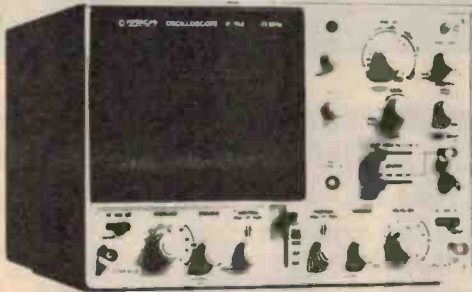SUPERB NEW MODEL V152F DC TO 15 mHz 1mV/DIV DUAL TRACE



**FREE DELIVERY  
ANYWHERE IN  
AUSTRALIA THIS  
MONTH**

CAT 00152  
PRICE ONLY  
**\$579** TAX EXEMPT  
**\$649** TAX PAID

Features \* X-Y Operation \* Vertical sensitivity 1mV/div. \* 10 x Sweeptime magnification with 1-touch operation \* Convenient CH1 signal DVM output \* Z-axis input provided - possible to use as CRT display \* 0.2us to 0.2s - wide sweep range setting \* Five modes of vertical operation \* Panel layout with colour coding of respective functions.

**SPECIFICATIONS**

Vertical deflection	5mV/div to 5V/div 5%
Sensitivity	10 calibrated steps 1mV/div to 1V/div -5% (When using x5 amplifier) Uncalibrated continuous control between steps 1 - 2.5 (provided with click positioning function)
Bandwidth	DC to 15MHz -3dB (at 4div) DC to 7MHz -3dB (at 4div) (When using x5 amplifier) 74ns, (for x5) 70ns typ
Rise time	
Signal delay time	
Max. input voltage	600Vp-p or 300V IDC - AC peak, at 1kHz
Input Coupling	AC, GND, DC
Input impedance	Direct 1M ohm approx 30pF
Operating modes	CH1, CH2, DUAL, ADD, DIFF
X-Y operation	CH1 X axis, CH2 Y axis
Sensitivity	5mV/div to 5V/div (When using x5 amplifier - 1mV/div)
Phase difference	DC to 10kHz within 3
X bandwidth	DC to 500kHz -3dB
Dynamic range	4div or more
CH1 output	20mV/div or more
Output voltage	(terminated into 50Ω)
Band width	50Hz to 5MHz -3dB
Output impedance	Approx 50Ω

Horizontal deflection	AUTO, NORM TV (1-), TV (1-)
Trigger modes	CH1, CH2, LINE, EXT
Trigger source	AC
Trigger coupling	TV synchronization circuit
TV sync	1div or more TV sync-signal
Internal	1Vp-p or more TV sync-signal
External	
Trigger sensitivity	Frequency Internal External
	20Hz to 2MHz 0.5div 300mV
	2 to 15MHz 1.5div 800mV
	30Hz
AUTO low bandwidth	
Trigger slope	Input impedance approx 1M ohm
External trigger input	30pF or less
Sweep time	Max. input voltage 100V (DC - AC peak, at 1kHz)
	0.2us/div to 0.2s/div -5%
	19 calibrated steps
	Uncalibrated continuous control between steps 1 - 2.5 (provided with click positioning function)
Sweep time magnifier	10 times (-7%)
Max. sweep time	100ms/div 120ms/div and 50ms/div, not calibrated
Amplitude calibrator	
Waveform	Approx 1kHz - 10% (typ)
Voltage	square wave 0.5V ±5%
Power requirements	100/120/220/240V ±10%
	50 to 60Hz approx 40W
Dimensions	Approx. 275(W) x 190(H) x 400(D)mm
Weight	Approx. 9.5kg

**Powerful New  
6000 RPM  
Mini Drill  
for PC  
Work**



Tons of Torque. Just the shot for PCB work. 12V DC operated from external Power Pack 1.2mm chuck capacity. Supplied c/w 1mm drill bit.

T2302 ..... **\$12.95**

Drill Bits:  
T2320 (0.8mm) ... **\$1.25**


T2325 (1.0mm) ... **\$1.25**

**ALTRONICS JIFFY BOXES**

**Incredible offer!**

Black plastic body with 22 g. aluminium lid and 4 st. screws supplied. Unique horizontal PC "Snap In" mounts as well as vertical card guides. Order your PC Boards pre-sized and dispense with costly stand offs, screws etc. These utility boxes are used in dozens of E.T.I. and E.A. projects.

Box	Dimensions	Board Width		Price this month
		Vertical	Horizontal	
H 0101	150 x 90 x 50	90	87	<b>\$1.90</b>
H 0102	195 x 113 x 60	106	103	<b>\$2.90</b>
H 0103	130 x 68 x 41	62	60	<b>\$1.80</b>
H 0105	83 x 54 x 28	50	47	<b>\$1.20</b>

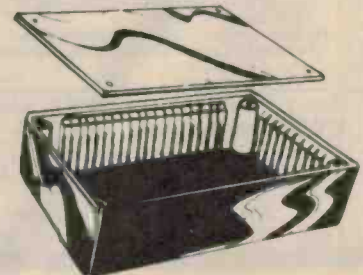




**eti** ELECTRONICS  
TODAY  
INTERNATIONAL

\$4.95\*

## TOP PROJECTS Vol. 8

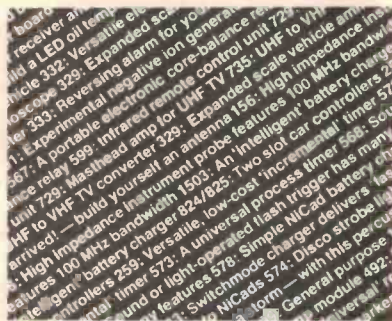

# THE VERY LATEST

This great new book from ETI is so 'hot off the press' that the cover literally *glows red!*

## TOP PROJECTS VOL. 8

Our 'Top Projects' series have always been very popular with hobbyists, containing as they do a collection of the best projects from the past year or so's issues of ETI Magazine. Here we have 25 projects, ranging from the ETI-1501 Negative Ion Generator, to the ETI-499 General Purpose 150 W MOSFET Power Amp Module, from the ETI-574 Disco Strobe to the ETI-469 Percussion Synthesiser, from the ETI-735 UHF TV Converter to the ETI-563 NiCad Fast Charger. Also included are the ETI-599 Infrared Remote Control Unit, the ETI-567 Core Balance Relay, the ETI-259 Incremental Timer, the ETI-156 100 MHz High Impedance Instrument Probe, the ETI-328 LED Oil Temperature Meter for cars, the ETI-257 Universal Relay Driver Board, the ETI-492 Sound Bender, the ETI-1503 Intelligent Battery Charger, the ETI-729 UHF Masthead Amp & more, & more.

Top Projects Vol. 8 is available at newsagents, selected electronic suppliers or directly, by mail order, from ETI Magazine, P.O. Box 227, Waterloo 2017 for \$4.95 plus \$1 post and handling.


# BWD

## Instruments.
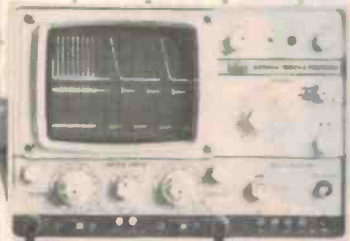
### THE INNOVATIVE AUSTRALIAN BACK AUSTRALIA — BUY AUSTRALIAN

**No. 1 FOR VALUE AND  
PERFORMANCE**

**FOR MORE SOPHISTICATED  
APPLICATIONS**



**821 50MHz Mix-Mag  
Oscilloscope**

**835 50MHz Dual Sweep  
Oscilloscope**



TO COMPLEMENT OUR  
COMPREHENSIVE RANGE  
OF OSCILLOSCOPES, BWD  
ALSO MANUFACTURES  
AND DISTRIBUTES THE  
FOLLOWING ITEMS . . .

- ★ SIGNAL GENERATORS
- ★ POWER SUPPLIES
- ★ PULSE GENERATORS
- ★ SPECTRUM ANALYSER
- ★ DIGITAL MULTIMETERS
- ★ FREQUENCY COUNTERS
- ★ PLUS MANY MORE

Dual Trace, DC-60MHz at 1mV and 50MHz at 2mV  
20 MHz Bandwidth limiter  
Delayed trigger or sweep with A + B display  
5nsec sweep speed  
Phase corrected identical X-Y to 300kHz  
90 to 264V, 48-440Hz AC or DC operation  
A full complement of triggering facilities  
High Intensity finely focused internal graticule CRT  
Completely portable, small and lightweight  
Extremely simple operation  
Universal power input provides 'go-anywhere' freedom of use  
High performance, high quality at low cost  
Manufactured to IEC 348 safety and reliability standards  
Sales and service around the world

Dual Trace — 50MHz at 5mV-20MHz at 1mV  
75MHz Triggering — 20ns/div max. Sweep speed  
X10 or X100 magnification — identical X-Y 1mV — 20V/div  
TV line & frame triggering — internal graticule CRT — 6kV EHT  
3% Calibration — amplifiers & time base  
Unique MIX-MAG one knob control of X1 & X10 magnification  
High sensitivity amplifiers for analog, digital, video and audio measurements  
Wide band communication monitor including modulation detector  
High calibration accuracy maintained from +5° to +40° C and over a 195 to 264V of 98 to 132V power line range  
Portable, compact, easy to use, wide range facilities and built to IEC 348 safety standards

— FOR FURTHER INFORMATION CALL OR WRITE —

Designed and manufactured in Australia by  
**BWD Instruments Pty. Ltd.**  
PO Box 325, Springvale, Vic 3171  
Miles Street, Mulgrave, Vic. 3170 Australia  
Phone National (03) 561 2888  
International 613 561 2888  
Telex 35115. Cables "OSCOPE" Melbourne

**NSW BRANCH**  
10 Euston St., Rydalmere  
N.S.W. 2116 Australia  
Phone: (02) 684 1800  
Telex: AA22523  
Ans. Bk.: BWDNSW

**NATIONAL DISTRIBUTORS**  
QLD.: L. E. BOUGHEN ..... (07) 369-1277  
S.A.: WERNER ELECTRONICS ..... (08) 268 2766  
W.A.: WARBURTON FRANKI ..... (09) 277 7000  
TAS.: D & I AGENCIES ..... (002) 23 2842



## RADIO COMMUNICATIONS BILL TABLED

**T**he Radiocommunications Bill and its associated Bills, which will provide modern administrative machinery to manage use of the radio frequency spectrum, were introduced into Parliament on 22 September.

The Minister for Communications, Mr Michael Duffy, said that the legislation would replace the outdated *Wireless Telegraphy Act 1905* and its associated Regulations which, because of technological advances, were now inadequate to control use of the spectrum.

Mr Duffy said that at first sight the Radiocommunications Bill hardly seemed to concern the average person. But the spectrum was a limited natural resource and without proper control over its use much of the business of daily life could not run smoothly.

"Most people make frequent use of the spectrum in one way or another as many services commonly used are dependent on it," Mr Duffy said.

Mr Duffy said the major intent

of the legislation was to control interference to and between radiocommunications services.

The Bill was made available for public comment earlier this year. Initial comment received was favourable and the Government incorporated many of the ideas received into the Bill. This was evidence of the Government's general commitment in policy-making to consultation with interested parties, the Minister said.

Mr Duffy said the associated Bills dealt with transitional matters and radiocommunications licence fees. These licence fees were currently set as taxes under the Radiocommunications Licence Fees Act. The associated minor tax Bills would replace this Act and have a similar legal effect.

## AMATEUR LOG-KEEPING OPTIONAL

**T**he Department of Communications has announced that, following consultations with the Wireless Institute of Australia, it has agreed to amend requirements for log-keeping by amateur radio operators.

A spokesman said that, in future, log-keeping would be optional with these exceptions; every amateur station is required to have a log-book in which to record distress and emergency traffic. In a case of a network carrying emergency

traffic, a log is to be kept by the control stations and a log is to be kept by an amateur if requested to do so by an officer of the Department of Communications.

Club stations are still required to maintain a log of all transmissions in accordance with the format detailed in paragraph 6.11 and Appendix 15 of the 'Amateur Operator's Handbook'.

The changes were made under the provisions of the Wireless Telegraphy Regulation 31(1).

## NEW PHILLYSTRAN AGENT

**H**igh-performance Phillystran non-metallic flexible rope is now available from Antenna Engineering Australia.

Used increasingly throughout the world for guying radio masts, Phillystran is an electrically transparent rope that provides excellent resistance to severe

corrosive environments, plus a high strength-to-weight ratio.

It offers the strength of steel with the advantages of synthetic fibres.

For further information, contact Antenna Engineering Australia, P.O. Box 191, Croydon Vic. 3136. (03)728-1777.



## IMARK TAKE SAIKO

**T**he Saiko SC7000 scanning receiver is now imported by Imark. The Saiko SC7000 uses a Z80 microcomputer chip and is ideal for listening to CFA, MFB, SES, police, public authority, ambulance, taxis and airport frequencies.

The scanner covers the VHF lo-band (60-90 MHz), the VHF hi-band (140-180 MHz), the UHF band (380-520 MHz) and the air band (108-138 MHz). It also has 2.5 kHz steps on the VHF and air bands and 25 kHz channel steps on the UHF band.

The unit's operator convenience functions include; scan between limits, scan 70 memory frequencies, scan any memory bank of 10 frequencies, scan

with the ability to capture, monitor and automatically store frequencies for later recall and a priority channel feature. There is also a tape recording facility, a digital 24-hour clock and a 'memory keep alive' option.

The Saiko SC7000 boasts solid-state design, a double conversion superheterodyne receiver, two monolithic crystal filters and a ceramic filter to provide excellent receiver sensitivity and selectivity.

The Unit weighs 3.1 kgs and measures 270 mm x 90 mm x 230 mm. For further information, contact Imark Pty Ltd, 167 Roden Street, West Melbourne Vic. 3003. (03)329-5433.

## GROUP TO EXAMINE MOBILE LICENSING

**T**he Australian Electronics Industry Association Mobile Radio Product Division (AEIA MRPD) and the Australian Business and Industrial Radio Association (ABIRA) have established a joint working party to examine the basis of mobile radio licensing and structure of licence fees.

This follows the Budget announcement to substantially raise licence fees for more than 150 000 Australian users of mobile radio.

Mr Harry Court, Chairman of

ABIRA said, "We believe that there must be a balance between the requirements of users of the radio communications spectrum, industry supplying these users, and the policies of Government regulating the use of the radio spectrum."

"We are very concerned that fees have been increased without addressing this fundamental point."

For further information, contact Harry Court, Chairman, ABIRA, c/- Taxis Combined Services (02)331-2124.



# A full coverage beam for the six metre band


With the 50 MHz end of the six metre band now available to Australian amateurs, a beam to cover the full band is a natural requirement. This log-periodic yagi design does it, and then some!

Roger Harrison VK2ZTB

AS HAS BEEN long observed, long-distance (DX) propagation on the six metre amateur band is definitely frequency sensitive, particularly with regard to ionospheric F-layer modes that take advantage of the equatorial F-layer 'anomalies' sited north and south of the geomagnetic equator. Afternoon-type or Class I transequatorial propagation being the favourite for contacts to the US, Japan and other Pacific regions. And the lower the frequency, the longer and more frequent the openings. Amateurs in countries across the 'big pond' (Pacific Ocean) are permitted to operate over 50-54 MHz whereas, until recently, Australian and New Zealand amateurs have been permitted to use only 52-54 MHz. That 2 MHz has caused some difficulties. The popular segment of the band in the Australasian region is around 52.000 MHz to 52.500 MHz, whereas, in other countries it's around 50.000-50.300 MHz or so. Most of the local area beacons, widely used to indicate improving propagation conditions, are spread between 51 MHz (ZL1UHF, Auckland 51.020 MHz) and 52.500 MHz (VK7RNT, Launceston 52.470 MHz and ZL2MUF, Mount Climie 52.510 MHz).

The most popular antenna on six metres is the Yagi, generally of four to six elements. These generally have a bandwidth of around 5-6%, which gives adequate coverage of part of the band if cut at an appropriate centre frequency, but when narrow bandwidth matching methods (like the common gamma match) are used, overall bandwidth may drop to 1% — 500 kHz! A Yagi like this, cut and matched for best performance at 52 MHz, does poorly at 50 MHz as many frustrated operators will attest.

A better bet is the log-periodic Yagi array, or log-yagi as it has been dubbed in some quarters. This design is based on the ETI-714 VHF Log-Periodic Antenna published in the February 1978 issue of ETI. It comprises a three-dipole log-periodic array with passive reflector and director elements added. It has been cast to cover 45-55 MHz and should yield a gain of some 6-7 dB over a dipole. Balanced feed is necessary and a

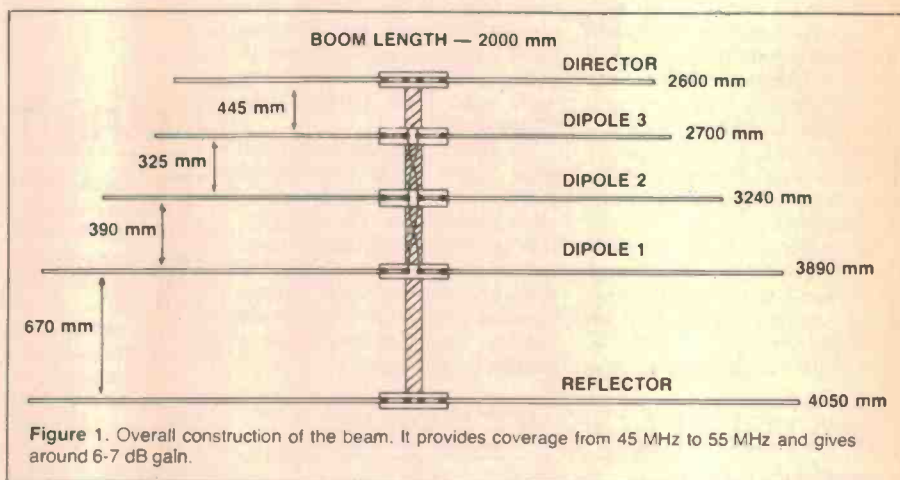

simple coax feedline balun is all that's necessary for matching. Feedpoint impedance is in the 60-70 Ohm region and VSWR across the band should remain below 1.5:1 which is quite acceptable, there being generally little point in trying to better that.

## Construction

The beauty of log-periodic designs is that they're tolerant of construction variations. At these frequencies, tolerances of  $\pm 10$  mm can be accommodated without serious (if noticeable) effects on performance. Figure 1 shows the overall construction dimensions. Each of the dipole halves must be insulated so an insulated boom is required, along with some convenient method of mounting the dipole elements on it. There are two basic ways of achieving this — using a wooden boom and wooden element support brackets; or using a boom of high density water pipe of a suitable diameter and conventional element-to-boom brackets.

The boom for the model illustrated in Figure 1 is a two metre length of 25 x 50 mm (dressed size) wood such as maple, though western red cedar is also good. It must be a straight-grained and knot-free and suitable for outdoor use if sealed with a stain or Estapol. Wattle 'Forestwood' or one of the

Cabot outdoor stains are fine and will ensure a long life.

The elements consist of two halves screwed to a wooden support block which is affixed to the boom. These blocks are cut from a length of 42 x 19 mm (dressed size) timber of the same type as used in the boom. The element halves are 10 mm diameter aluminium tube which is generally available from hardware stores or specialist aluminium suppliers (look them up in your local 'phone book). The measurements for element length given in Figure 1 are tip-to-tip dimensions. Cut the element halves 5 mm shorter than required to leave a 10 mm gap in the centre. The reflector should be made from a single length, if you can possibly do it, otherwise, use two, two-metre lengths and bond them thoroughly in the centre to get electrical contact. (If it has to be 50 mm short, it won't hurt all that much). Figures 2 and 3 show the general assembly details for the dipoles.

The position of each dipole support block should be marked out on the boom before assembling the dipoles. Drill the two bracket-to-boom screw holes in the brackets a little oversize so that the elements can be lined up parallel and at right angles to the boom, for appearance's sake. Note that the







# VHF LISTENERS' GUIDE

## Part 3 400-550 MHz

This last part of our listing covers the ultra-high frequency (UHF) region from 400 MHz up to the limit where the coverage of most receivers available seems to stop. As in Part 2, the National listing includes some New Zealand frequencies which may be observed under enhanced propagation conditions, but reception would probably be limited to the Australian eastern seaboard.

Note also that, where several services are listed on the one channel, they are likely to be geographically separated.

A large number of public authorities and emergency services have moved or expanded their communications to the UHF bands in recent years and the crowded taxi channels on VHF have spilled over to the UHF.


The complete list, parts 1, 2 and 3, has been compiled from generally publically available material and sorted using a computer. We make no claims regarding its accuracy or completeness and welcome any additions, deletions or corrections readers may wish to submit so that a revised edition may be compiled and published at a later date.

In Parts 2 and 3, the amateur 2 m and 70 cm band listings in the 'National' section indicate the nationally agreed-upon 'band plans' and specific usage will vary from area to area. The Radio Amateurs' Callbook, published by the Wireless Institute of Australia, includes listings of repeater channels in use in various areas and this will give you an idea of which channels may be heard from your locality. We did not include UHF CB repeater listings as we have incomplete information on activity and repeater locations as yet. Very few have been approved to date. The Public Automatic Mobile Radio Telephone Service frequencies have been left out as we have been advised it is an offence to monitor these frequencies (see Scanners World, page 159, September '83).

## NATIONAL

433.025	FM	NATIONAL	REPEATER INPUT	70 CM AMATEUR BAND
433.050	FM	NATIONAL	REPEATER INPUT	
433.075	FM	NATIONAL	REPEATER INPUT	MOBILE VOICE
433.100	FM	NATIONAL	REPEATER INPUT	
433.125	FM	NATIONAL	REPEATER INPUT	
433.150	FM	NATIONAL	REPEATER INPUT	
433.175	FM	NATIONAL	REPEATER INPUT	
433.200	FM	NATIONAL	REPEATER INPUT	
433.225	FM	NATIONAL	REPEATER INPUT	MOBILE VOICE SECONDARY
433.250	FM	NATIONAL	REPEATER INPUT	
433.275	FM	NATIONAL	REPEATER INPUT	RTTY

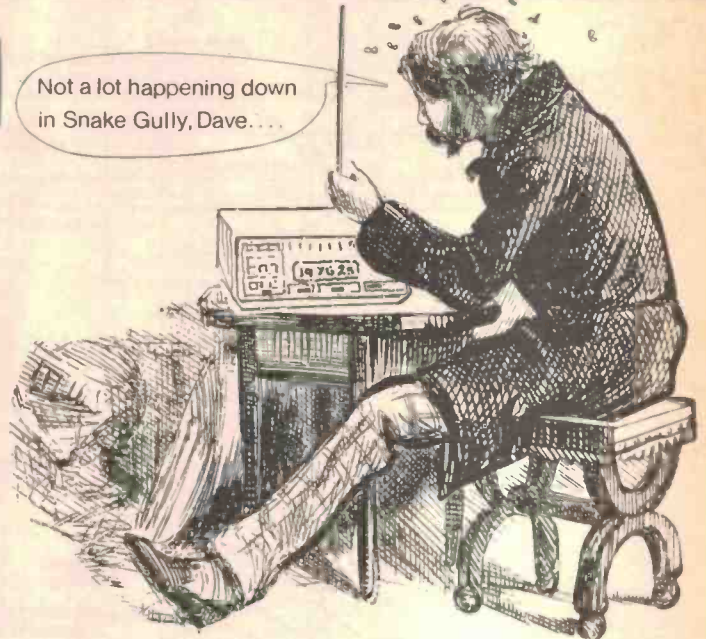Not a lot happening down in Snake Gully, Dave...



433.300	FM	NATIONAL	REPEATER INPUT
433.325	FM	NATIONAL	REPEATER INPUT
433.350	FM	NATIONAL	REPEATER INPUT
433.375	FM	NATIONAL	REPEATER INPUT MOBILE VOICE
433.400	FM	NATIONAL	REPEATER INPUT
433.425	FM	NATIONAL	REPEATER INPUT DATA
433.450	FM	NATIONAL	REPEATER INPUT
433.475	FM	NATIONAL	REPEATER INPUT
433.500	FM	NATIONAL	REPEATER INPUT
433.525	FM	NATIONAL	REPEATER MOBILE VOICE PRIMARY
433.550	FM	NATIONAL	REPEATER INPUT
433.575	FM	NATIONAL	REPEATER INPUT DATA
433.600	FM	NATIONAL	REPEATER INPUT
433.625	FM	NATIONAL	REPEATER INPUT WICEN
433.650	FM	NATIONAL	REPEATER INPUT
433.675	FM	NATIONAL	REPEATER INPUT MOBILE VOICE SEC
433.700	FM	NATIONAL	REPEATER INPUT
433.725	FM	NATIONAL	REPEATER INPUT SSTV
434.275	FM	NATIONAL	REPEATER INPUT MOBILE VOICE
434.300	FM	NATIONAL	REPEATER INPUT
434.325	FM	NATIONAL	REPEATER INPUT RTTY
434.350	FM	NATIONAL	REPEATER INPUT
434.375	FM	NATIONAL	REPEATER INPUT
434.400	FM	NATIONAL	REPEATER INPUT
434.425	FM	NATIONAL	REPEATER INPUT MOBILE VOICE
434.450	FM	NATIONAL	REPEATER INPUT
434.475	FM	NATIONAL	REPEATER INPUT
434.500	FM	NATIONAL	REPEATER INPUT
434.525	FM	NATIONAL	REPEATER INPUT
434.550	FM	NATIONAL	REPEATER INPUT
434.575	FM	NATIONAL	REPEATER INPUT MOBILE VOICE
434.600	FM	NATIONAL	REPEATER INPUT
434.625	FM	NATIONAL	REPEATER INPUT
434.650	FM	NATIONAL	REPEATER INPUT
434.675	FM	NATIONAL	REPEATER INPUT
434.700	FM	NATIONAL	REPEATER INPUT
434.725	FM	NATIONAL	REPEATER INPUT MOBILE VOICE
434.750	FM	NATIONAL	REPEATER INPUT
434.775	FM	NATIONAL	REPEATER INPUT
434.800	FM	NATIONAL	REPEATER INPUT
434.825	FM	NATIONAL	REPEATER INPUT



434.850	FM	NATIONAL	REPEATER INPUT
434.875	FM	NATIONAL	REPEATER INPUT MOBILE VOICE
434.900	FM	NATIONAL	REPEATER INPUT
434.925	FM	NATIONAL	REPEATER INPUT
434.950	FM	NATIONAL	REPEATER INPUT
434.975	FM	NATIONAL	REPEATER INPUT
435.025	FM	NATIONAL	UOSAT AMATEUR SAT DATA DOWNLINK
438.750	FM	NATIONAL	SIMPLEX
438.775	FM	NATIONAL	SIMPLEX RTTY
438.800	FM	NATIONAL	SIMPLEX
438.825	FM	NATIONAL	SIMPLEX VOICE SECONDARY
438.850	FM	NATIONAL	SIMPLEX
438.875	FM	NATIONAL	SIMPLEX DATA
438.900	FM	NATIONAL	SIMPLEX
438.925	FM	NATIONAL	SIMPLEX SSTV
438.950	FM	NATIONAL	SIMPLEX
438.975	FM	NATIONAL	SIMPLEX
439.000	FM	NATIONAL	SIMPLEX VOICE NAT PRIMARY
439.025	FM	NATIONAL	SIMPLEX
439.050	FM	NATIONAL	SIMPLEX
439.075	FM	NATIONAL	SIMPLEX
439.100	FM	NATIONAL	SIMPLEX
439.125	FM	NATIONAL	SIMPLEX VOICE SECONDARY
439.150	FM	NATIONAL	SIMPLEX
439.175	FM	NATIONAL	SIMPLEX
439.200	FM	NATIONAL	SIMPLEX
439.225	FM	NATIONAL	SIMPLEX
439.250	FM	NATIONAL	SIMPLEX
476.425	FM	NATIONAL	UHF CB CHANNEL 1
476.450	FM	NATIONAL	UHF CB CHANNEL 2
476.475	FM	NATIONAL	UHF CB CHANNEL 3
476.500	FM	NATIONAL	UHF CB CHANNEL 4
476.525	FM	NATIONAL	UHF CB CHANNEL 5 EMERGENCY
476.550	FM	NATIONAL	UHF CB CHANNEL 6
476.575	FM	NATIONAL	UHF CB CHANNEL 7
476.600	FM	NATIONAL	UHF CB CHANNEL 8
476.625	FM	NATIONAL	UHF CB CHANNEL 9
476.650	FM	NATIONAL	UHF CB CHANNEL 10
476.675	FM	NATIONAL	UHF CB CHANNEL 11
476.700	FM	NATIONAL	UHF CB CHANNEL 12
476.725	FM	NATIONAL	UHF CB CHANNEL 13
476.750	FM	NATIONAL	UHF CB CHANNEL 14
476.775	FM	NATIONAL	UHF CB CHANNEL 15
476.800	FM	NATIONAL	UHF CB CHANNEL 16
476.825	FM	NATIONAL	UHF CB CHANNEL 17
476.850	FM	NATIONAL	UHF CB CHANNEL 18
476.875	FM	NATIONAL	UHF CB CHANNEL 19
476.900	FM	NATIONAL	UHF CB CHANNEL 20
476.925	FM	NATIONAL	UHF CB CHANNEL 21
476.950	FM	NATIONAL	UHF CB CHANNEL 22
476.975	FM	NATIONAL	UHF CB CHANNEL 23
477.000	FM	NATIONAL	UHF CB CHANNEL 24
477.025	FM	NATIONAL	UHF CB CHANNEL 25
477.050	FM	NATIONAL	UHF CB CHANNEL 26
477.075	FM	NATIONAL	UHF CB CHANNEL 27
477.100	FM	NATIONAL	UHF CB CHANNEL 28
477.125	FM	NATIONAL	UHF CB CHANNEL 29
477.150	FM	NATIONAL	UHF CB CHANNEL 30
477.175	FM	NATIONAL	UHF CB CHANNEL 31
477.200	FM	NATIONAL	UHF CB CHANNEL 32
477.225	FM	NATIONAL	UHF CB CHANNEL 33
477.250	FM	NATIONAL	UHF CB CHANNEL 34
477.275	FM	NATIONAL	UHF CB CHANNEL 35
477.300	FM	NATIONAL	UHF CB CHANNEL 36
477.325	FM	NATIONAL	UHF CB CHANNEL 37
477.350	FM	NATIONAL	UHF CB CHANNEL 38
477.375	FM	NATIONAL	UHF CB CHANNEL 39
477.400	FM	NATIONAL	UHF CB CHANNEL 40

425.750	TV	NZ	ATV VIDEO 2 70 CM AMATEUR BAND
431.350	FM	NZ	ATV SOUND 2 70 CM AMATEUR BAND
432.200	SSB	NZ	SSB SIMPLEX CALLING 70 CM AMATEUR BAND
433.300	FM	NZ	FM SIMPLEX CALLING 70 CM AMATEUR BAND
433.350	FM	NZ	FM SIMPLEX 70 CM AMATEUR BAND
433.400	FM	NZ	FM SIMPLEX 70 CM AMATEUR BAND
433.450	FM	NZ	FM SIMPLEX 70 CM AMATEUR BAND
443.250	TV	NZ	ATV VIDEO 1 70 CM AMATEUR BAND
448.750	FM	NZ	ATV SOUND 1 70 CM AMATEUR BAND

## ACT

468.400	FM	ACT	POLICE
468.425	FM	ACT	POLICE
468.475	FM	ACT	POLICE
468.700	FM	ACT	POLICE
470.250	FM	ACT	HERALD
491.750	FM	ACT	TV CH7

## NSW

432.420	CW	NSW SYDNEY	VK2RSY AMATEUR BEACON
445.775	FM	NSW	SERVICE COMPANY
453.925	FM	NSW	HEALTH COMMISSION
454.000	FM	NSW	MARITIME SERVICES BOARD
454.175	FM	NSW	ANSETT AIRLINES
454.275	FM	NSW	MARITIME SERVICES BOARD
454.700	FM	NSW	ANSETT AIRLINES
455.200	FM	NSW	RAILEX
458.050	FM	NSW	TECH EDUCATION
463.150	FM	NSW	UTA AIRLINES
463.300	FM	NSW	TWO WAY CONTAINER DEPOT
463.400	FM	NSW	SINGAPORE AIRLINES
464.200	FM	NSW	UNIVERSITY OF NSW
465.300	FM	NSW	PAN AM AIRLINES
465.625	FM	NSW	TAXI
465.825	FM	NSW	THAI AIRLINES GROUND
467.300	FM	NSW	TAXI
468.250	FM	NSW	POLICE
468.275	FM	NSW	MARITIME SERVICES BOARD
468.300	FM	NSW	POLICE WOLLONGONG
468.355	FM	NSW	TAA AIRLINES
468.400	FM	NSW	POLICE SYDNEY CITY
468.425	FM	NSW	POLICE SYDNEY WEST
468.450	FM	NSW	POLICE SYDNEY NORTH
468.475	FM	NSW	POLICE BATEMANS BAY NTH
468.500	FM	NSW	POLICE SYDNEY CENTRAL
468.525	FM	NSW	POLICE
468.550	FM	NSW	POLICE
468.555	FM	NSW	POLICE SYDNEY EAST
468.625	FM	NSW	HEALTH COMMISSION
468.700	FM	NSW	POLICE SYDNEY CENTRAL
468.725	FM	NSW	POLICE SYDNEY NORTH
468.750	FM	NSW	POLICE HERIMBULA BEGA
468.775	FM	NSW	POLICE LICENCE CHECKS
469.725	FM	NSW	MARITIME SERVICES BOARD
469.800	FM	NSW	AWA MARINE

## QLD

432.440	CW	QLD BRISBANE
---------	----	--------------

VK4RBB AMATEUR BEACON
-----------------------



# SA-NT

468.450	FM	SA	POLICE
468.475	FM	SA	POLICE
468.500	FM	SA	POLICE
468.700	FM	SA	POLICE
468.725	FM	SA	POLICE
468.775	FM	SA	POLICE

# VIC

406.750	FM	VIC	DINHOL PTY LTD
406.750	FM	VIC	COLORSHIELD
415.415	FM	VIC	PORT EMERGENCY
415.475	FM	VIC	PORT EMERGENCY
416.075	FM	VIC	PORT EMERGENCY
416.250	FM	VIC	COLORSHIELD
416.250	FM	VIC	DINHOL PTY LTD
429.000	FM	VIC	ESSO OIL RIGS
432.450	CW	VIC	MT BUNUNYONG
450.675	FM	VIC	VK3RMB AMATEUR BEACON
450.800	FM	VIC	FOREST COMMISSION CENTRAL
453.450	FM	VIC	FOREST COMMISSION CENTRAL
454.300	FM	VIC	MFB CHANNEL 4 HAND HELD UNITS
454.875	FM	VIC	ALBERT SMITH & STAFF - TX MOBILE
455.900	FM	VIC	GOLDEN MESSENGERS
456.250	FM	VIC	CROWN CONTROLS TX MOBILE
456.350	FM	VIC	AWA
457.775	FM	VIC	ASSOCIATED OWNER DRIVERS TX
459.300	FM	VIC	MUTUAL AID EMERG FIRE SERV ALTONA
460.000	FM	VIC	MOTOROLA MOBILE TX
460.200	FM	VIC	FOREST COMMISSION FIRE TOWER
461.575	FM	VIC	FOREST COMMISSION CENTRAL
463.150	FM	VIC	TV STATION GTV9 HAND HELDS
463.150	FM	VIC	MFB CHANNEL 3 MLC BUILDING
463.175	FM	VIC	CHANNEL 9 UHF
463.225	FM	VIC	DONNELLY SAND SUPPLY
463.225	FM	VIC	MFB CHANNEL 2 MLC BUILDING
463.275	FM	VIC	MFB CHANNEL 1
463.275	FM	VIC	MFB CHANNEL 1 REPEATER
463.275	FM	VIC	MFB CHANNEL 2
463.450	FM	VIC	EPA
463.800	FM	VIC	ALBERT SMITH & STAFF - RX
464.375	FM	VIC	GOLDEN MESSENGERS
465.200	FM	VIC	ERRAND MESSENGERS BASE RX
465.400	FM	VIC	CROWN CONTROLS RX MOBILE
465.700	FM	VIC	ERRAND MESSENGERS BASE TX
465.750	FM	VIC	AWA VH3HS
465.850	FM	VIC	ASSOCIATED OWNER DRIVERS RX
467.200	FM	VIC	WESTGATE BRIDGE CONTROL
467.275	FM	VIC	MUTUAL AID EMERG FIRE SERV ALTONA
467.275	FM	VIC	PETRO CHEMICALS ALTONA
467.625	FM	VIC	CRB
468.050	FM	VIC	PETRO CHEMICALS ALTONA
468.300	FM	VIC	VICTORIAN RAILWAYS
468.400	FM	VIC	POLICE HAND HELDS
468.425	FM	VIC	POLICE HAND HELDS
468.450	FM	VIC	POLICE HAND HELDS
468.475	FM	VIC	POLICE HAND HELDS
468.525	FM	VIC	SES REPEATER DOWNLINK
468.600	FM	VIC	SES REPEATER DOWNLINK COUNTRY
468.625	FM	VIC	SES REPEATER DOWNLINK COUNTRY
468.650	FM	VIC	SES REPEATER DOWNLINK
468.675	FM	VIC	SES REPEATER DOWNLINK
468.800	FM	VIC	MOTOROLA MOBILE RX
468.925	FM	VIC	POLICE HAND HELDS
469.525	FM	VIC	ST JOHNS AMBULANCE SIMPLEX

470.075	FM	VIC	SECURITY SERVICES
470.125	FM	VIC	SECURITY SERVICES
470.550	FM	VIC	SECURITY SERVICES
470.850	FM	VIC	SECURITY SERVICES
480.865	FM	VIC	MMBW CHANNEL 10
483.000	FM	VIC	YELLOW CABS
483.300	FM	VIC	SILVER TOP TAXIS
483.325	FM	VIC	SILVER TOP TAXIS
483.350	FM	VIC	SILVER TOP TAXIS
483.375	FM	VIC	SILVER TOP TAXIS
483.425	FM	VIC	SILVER TOP TAXIS
483.525	FM	VIC	SILVER TOP TAXIS
483.575	FM	VIC	SILVER TOP TAXIS
483.600	FM	VIC	SILVER TOP TAXIS
483.675	FM	VIC	YELLOW CABS
483.700	FM	VIC	YELLOW CABS
483.725	FM	VIC	YELLOW CABS
483.775	FM	VIC	YELLOW CABS
483.900	FM	VIC	BLACK CABS
483.925	FM	VIC	BLACK CABS
484.000	FM	VIC	EASTERN GROUP TAXIS
485.375	FM	VIC	BANK SECURITY
486.650	FM	VIC	BOX HILL COUNCIL
486.975	FM	VIC	SECURITY SERVICES
487.175	FM	VIC	MMB
487.325	FM	VIC	WORMALDS
487.775	FM	VIC	STATION JMP
488.500	FM	VIC	SILVER TOP TAXIS
488.525	FM	VIC	SILVER TOP TAXIS
488.550	FM	VIC	SILVER TOP TAXIS
488.575	FM	VIC	SILVER TOP TAXIS
488.625	FM	VIC	SILVER TOP TAXIS
488.725	FM	VIC	SILVER TOP TAXIS
488.775	FM	VIC	SILVER TOP TAXIS
488.800	FM	VIC	SILVER TOP TAXIS
488.875	FM	VIC	YELLOW CABS
488.900	FM	VIC	YELLOW CABS
488.925	FM	VIC	YELLOW CABS
488.925	FM	VIC	VICTORIAN RAILWAYS
488.975	FM	VIC	YELLOW CABS
489.000	FM	VIC	YELLOW CABS
489.100	FM	VIC	BLACK CABS
489.125	FM	VIC	BLACK CABS
489.200	FM	VIC	EASTERN GROUP TAXIS
490.125	FM	VIC	RACV CHANNEL 5
490.150	FM	VIC	RACV CHANNEL 6
490.175	FM	VIC	RACV CHANNEL 7
490.200	FM	VIC	RACV CHANNEL 8
490.550	FM	VIC	TELECOM
490.725	FM	VIC	DEPT EDUCATION
490.735	FM	VIC	SECURITY SERVICES
492.275	FM	VIC	STATION 3AW
493.475	FM	VIC	SEA PILOTS RX
494.150	FM	VIC	METROPOLITAN SECURITY SERVICES
495.325	FM	VIC	RACV CHANNEL 1
495.350	FM	VIC	RACV CHANNEL 2
495.375	FM	VIC	RACV CHANNEL 3
495.400	FM	VIC	RACV CHANNEL 4
496.100	FM	VIC	MMBW CHANNEL 11
496.100	FM	VIC	FOREST COMMISSION FIRE TOWER
498.675	FM	VIC	SEA PILOTS TX
500.175	FM	VIC	TELECOM

# WA

432.410	CW	WA	CARNARVON	VK6RTT AMATEUR BEACON
---------	----	----	-----------	-----------------------



PLEASE RING YOUR NEAREST STORE FOR EXTENDED TRADING HOURS OVER THE CHRISTMAS PERIOD

PLEASE RING YOUR NEAREST STORE FOR EXTENDED TRADING HOURS OVER THE CHRISTMAS PERIOD

# JAYCAR FOR VALUE!

Cat. BM-9000



**Merry Christmas**

**\$2<sup>95</sup>**

**MUSICAL CHRISTMAS CARD**


Incredible but true. Send a friend a card that plays a tune!

Each card is fitted with an electronic watch module, battery and flat transducer. An appropriate seasonal tune plays when the card is opened. Now no more expensive than ordinary high quality Xmas card.

ONLY \$2.95

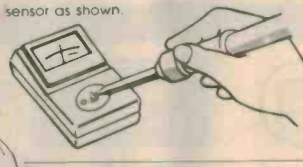**EASY TO USE!**

Apply solder to the tip of soldering iron and then press the temperature sensor as shown.



**SOLDERING IRON TEMP. TESTER**

**READS TEMP IN DEGREES CENTIGRADE!**

**\$29<sup>95</sup>**

**NEW**

Cat. QT-2100

Temperature is the most important factor for soldering!

Prevent precision parts from burning intermittent connection.

When you solder electronic parts to the printed circuit board, you should know the proper temperature.

Improper temperature can cause damage to parts or cold soldering.

**Ideal for all temperature controlled irons**

**UNIDIRECTIONAL ELECTRET MICROPHONE INSERT**



Just out in time for the new EA Parabolic Microphone project! (Ref: EA Nov. '83). This brand new direct import unit has an average sensitivity around 7dB BETTER than the common low cost Electret insert.

The unit (Cat. AM-4012) has a front-to-back ratio of 1.5:1. The power requirements are the same as for the low cost mic. insert.

Each insert is supplied with a comprehensive data sheet which includes connection details, specs. and frequency response graph.

Be early as they may be in short supply around Xmas.

Cat. AM-4012

**NEW only \$3<sup>95</sup>**

ONLY \$3.95

**Amazing Value**

**PROFESSIONAL COMPUTERISED CAR ALARM WITH FLASHING LIGHT**

**\$69.95**



This alarm has all the features of those expensive types. These include:—

- \* Flashing light for visible protection
- \* Automatically switches on when ignition key is in off position and switched off with same key — no switches
- \* Exit and entry delay and unit chirps when exit delay begins
- \* Sounds for one minute, then resets
- \* Pulsating or steady alarm tone selectable
- \* Can be used with optional N.O. Motion sensor
- \* Bonnet, boot, car stereo and CB protected
- \* All hardware, wire and two warning decals supplied

Cat. LE-8600 \$69.95

**16 bit computer KIT**

**Slashed**



**WAS \$1299**

**SAVE \$500!!**

**NOW \$799**

**Comp. Kit**

Cat. KJ-6630

**KAISE**



**DIGITAL MULTITESTER**


**THE ALL SINGING ALL DANCING MULTIMETER**

Scoop purchase of quality "KAISE" Japanese 3 1/2 digit LCD digital multimeter.

- Manual range override (Normally auto-range)
- A must. Zero adjust button. Calibrates meter if you change test probes
- Virtually "open circuit" input impedance
- Magnificent clear LCD readout
- Most significant digit flashes if out of range
- Tone beeper for status identification
- 4V-1000V DC. 600V AC
- Resistance & Current ranges (AC & DC)
- Lo ohms range for checking semis
- 4mm banana plug leads on industry standard 19mm centres
- High current shunt available
- Fuse protected. Spare fuse provided — inside case.

Cat. QM-1525

**NEW \$59<sup>95</sup>**



**MACHINED PIN GOLD CONTACT IC SOCKETS.**

Expensive. But the best for professional work. Each pin is machined out of solid material (not punched out of a flimsy sheet). High quality heavily gold plated inserts form the socket end of the pin. The pins are then precision moulded into a high quality plastic housing. Ideal for use in equipment where high field service costs are a distinct possibility or where high reliability is essential.

Cat. No.	Description	1-9	10+
PI-6452	8 WAY SOCKET	\$0.90	\$0.84
PI-6454	14 WAY SOCKET	\$1.15	\$1.10
PI-6456	16 WAY SOCKET	\$1.25	\$1.15
PI-6458	18 WAY SOCKET	\$1.45	\$1.35
PI-6460	20 WAY SOCKET	\$1.60	\$1.50
PI-6462	22 WAY SOCKET	\$1.75	\$1.60
PI-6464	24 WAY SOCKET	\$1.95	\$1.80
PI-6466	28 WAY SOCKET	\$2.25	\$2.10
PI-6468	40 WAY SOCKET	\$2.95	\$2.75

**Amazing WE'VE GOT THE EDGE!**

Quality Australian made cabinets. Aluminium and Marvplate construction with handles.

Cat. No.	Description	1-9
HE-1452	84/6V 203(D) x 102(H) x 153(W)	\$18.50
HE-1454	84/8V 203(D) x 102(H) x 203(W)	\$20.00
HE-1457	84/10V 203(D) x 102(H) x 254(W)	\$21.50
HE-1458	84/12V 203(D) x 102(H) x 305(W)	\$23.00
HE-1459	84/17V 203(D) x 102(H) x 432(W)	\$28.00
HE-1461	93/8V 228(D) x 76(H) x 150(W)	\$16.50
HE-1462	93/8V 228(D) x 76(H) x 203(W)	\$18.00
HE-1463	93/10V 228(D) x 76(H) x 254(W)	\$19.50
HE-1467	93/12V 228(D) x 76(H) x 305(W)	\$22.00
HE-1469	93/17V 228(D) x 76(H) x 432(W)	\$25.50

**Horwood Instrument Cases**

**Jaycar** Incorporating **ELECTRONIC AGENCIES**

**SYDNEY** SHOWROOMS  
117 YORK STREET - PHONE: (02) 264 6688 and (02) 267 1614  
TELEX: 72293

**CARLINGFORD**  
Cnr. CARLINGFORD & PENNANT HILLS ROAD - PHONE: (02) 872 4444

**CONCORD**  
115 - 117 PARRAMATTA ROAD - PHONE: (02) 745 3077

**HURSTVILLE** 121 FOREST ROAD - PHONE: (02) 570 7000

**NUMBER 1 FOR KITS**

POST AND PACKING CHARGES  
\$5 - \$9.99 (\$1.50) \$10 - \$24.99 (\$3.20)  
\$25 - \$49.99 (\$4.50) \$50 - \$99.99 (\$6.50)  
\$100 - \$198 (\$8.00) Over \$199 (\$10)

"Free INSURANCE for Road & Registered Post over \$200"  
All heavy or bulky items (over 20kg.) sent Comet Road Freight \$12.00 anywhere in Australia.

**SHOP HOURS CARLINGFORD, CONCORD & HURSTVILLE**  
Mon - Fri 9am - 5.30pm. Sat - 9am - 12pm. Thurs night 8.30pm

**SHOP HOURS SYDNEY**  
Mon - Fri 8.30am - 5.30pm. Sat - 8.30am - 12pm. Thurs night 8.30pm

MAIL ORDERS AND CORRESPONDENCE: P.O. Box 185, Concord, 2137

Mail Order By **BANKCARD** Via Your Phone





# Christmas Values



**2K/VOLT MULTIMETER**  
Ideal toolbox or beginners multimeter, 15 useful ranges.

**\$14.95**

Full specs available on request, SAE please.



**20K/VOLT MULTIMETER**  
Handy and servicemen's bench type multimeter, 19 useful ranges incl 10A DC and buzzer.


**\$26.50**

90 day warranty included.



**DIGITAL LCD MULTIMETER**  
Professional 3 1/2 digit meter with carry case, overload protected, 10m (0.4m) readout, 14 useful ranges.

**\$69.90**

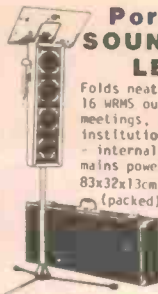


**Portable PA SOUND COLUMN LECTERN**  
Folds neatly into carry-case. Big 16 WMS output, ideal for lectures, meetings, educational, religious institutions - use indoors/outdoors - internal batt, 12V car batt or AC mains power  
83x32x13cm (packed)

**\$330**

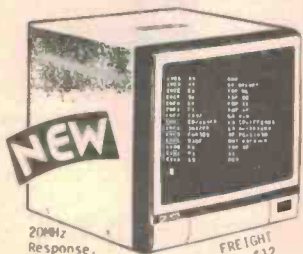**Affordable PA SYSTEMS**

AMPLIFIERS SPEAKERS ADAPTERS MIXERS STANDS MIKES HORNS  
OUR RANGE OF ECONOMY-PRICED PA SYSTEMS AND ACCESSORIES IS SECOND-TO-NONE! OUR NEW PA CATALOGUE IS AVAILABLE FREE: PLEASE SEND SAE.



## ORANGE SCREEN COMPUTER MONITORS

LIMITED STOCK AT THESE PRICES

ORANGE SCREENS GIVE A CLEAR, HONEST IMAGE! Computer data and graphic displays never looked better, brighter, sharper. ORANGE SCREENS ARE 'NOT A SIGHT FOR SORE EYES!' Positive research indicates that orange causes least eye fatigue.

**High Resolution \$199**

1000 lines at centre resolution, Display characters: 1920 (80x24) incl 5/16x

MONEY-BACK OFFER IF NOT FULLY SATISFIED

BRING YOUR OWN COMPUTER FOR A FREE DEMONSTRATION. BANKCARD ORDERS OK.

## APPLE® 100% COMPATIBLE PRODUCTS

Speech Synthesizer Board... UNLIMITED VOCABULARY COMPLETE WITH SPEAKER AND DISK... \$75

Printer Board... FOR PARALLEL PRINTERS... \$95  
Wild Copy Card... ULTIMATE DISK BACK-UP... \$99  
Prototyping Board... DESIGNERS HELP... \$25  
Joysticks... SELF-CENTERING, ADJUSTABLE... \$40  
New 80 Column card, Z80 CPU card, 16K RAM card, PAL Colour card, etc now available.



**\$365 SLIM-LINE DISK DRIVE**

WITH READ/WRITE DISK PROTECT SW! Price does not include disk drive card, Disk Drive Controller Card. Plugs into an expansion slot and will run up to 2 disk drives. Limited quantity avail at... \$79  
Bring your APPLE for a free in-store demonstration. Bankcard OK.

## S100 SYSTEMS MAINFRAMES


QT COMPUTER MAINFRAMES ARE PROFESSIONALLY BUILT AND TESTED AND GUARANTEED.  
incl 8 slot M/board A&T... \$592  
incl 12 slot M/board A&T... \$632

**S100 CARD FRAMES**  
8 slot... \$37 12 slot... \$44  
Card guides to suit above... each 50c

**S100 MOTHERBOARDS**  
QT 'Silence 1' NOW RATED NUMBER ONE!  
6 slot... BB \$34... A&T \$84  
8 slot... BB \$37... A&T \$107  
12 slot... BB \$43... A&T \$142  
S100 bus connectors... ea \$6.20



## Disk Drive Cabinets

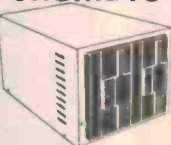

WE ARE A COMPLETE S100 SOURCE FOR ALL SYSTEM BUILDERS AND DEM'S.

OUR 1984 CATALOGUE IS AVAILABLE FREE TO GOVT DEPARTMENTS, COMPANIES ETC, OTHERWISE SEND \$1 TO COVER POSTAGE. SENT FREE WITH MAIL ORDERS. ON REQUEST.

## 64K S100 STATIC RAM BOARD



BARE BOARD... \$95  
KIT (NO RAM)... \$149  
ASSEMBLED 64K... \$390  
Plus Sales Tax 20% if applic.


256K S100 DYNAMIC MEMORY BOARD BARE BOARD... \$195 ASSEMBLED... \$995 PLUS SALES TAX 20% EXTRA

SBC 2/4 Z80 CPU BOARD BB... \$66 2 or 4 MHz option, 1K RAM, serial/parallel I/O ports A&T... \$199

## EX-COMPUTER G'TEED ELECTROS

10,000uf 15v	\$ 3.00	10,000uf 25v	\$ 4.00	70,000uf 15v	\$ 9.00
100,000uf 15v	\$ 5.00	10,000uf 75v	\$ 4.50	3,000uf 50v	\$ 3.00
100,000uf 35v	\$ 6.00	17,000uf 75v	\$ 4.50	4,000uf 50v	\$ 3.50
17,000uf 10v	\$ 2.00	17,000uf 75v	\$ 5.00	5,000uf 50v	\$ 4.00
25,000uf 10v	\$ 3.00	18,000uf 75v	\$ 5.50	6,000uf 50v	\$ 4.50
25,000uf 10v	\$ 3.00	18,000uf 75v	\$ 5.50	7,000uf 50v	\$ 5.00
42,000uf 10v	\$ 4.00	19,000uf 75v	\$ 6.00	8,000uf 50v	\$ 5.50
42,000uf 10v	\$ 4.00	19,000uf 75v	\$ 6.00	8,000uf 50v	\$ 5.50
42,000uf 10v	\$ 4.00	25,000uf 75v	\$ 7.00	9,000uf 50v	\$ 6.00
76,000uf 10v	\$ 5.50	32,000uf 75v	\$ 7.50	12,000uf 50v	\$ 8.00
80,000uf 10v	\$ 6.00	48,000uf 75v	\$ 8.00	15,000uf 50v	\$ 9.00
100,000uf 10v	\$ 8.00	48,000uf 75v	\$ 8.00	15,000uf 50v	\$ 9.00
100,000uf 10v	\$ 8.00	48,000uf 75v	\$ 8.00	15,000uf 50v	\$ 9.00
150,000uf 10v	\$ 10.00	50,000uf 75v	\$ 9.00	29,700uf 50v	\$12.00
150,000uf 10v	\$ 10.00	50,000uf 75v	\$ 9.00	34,000uf 50v	\$14.00
184,000uf 10v	\$ 12.00	50,000uf 75v	\$ 9.00	20,000uf 60v	\$11.00
200,000uf 10v	\$ 13.00	74,000uf 30v	\$ 7.00	20,000uf 60v	\$11.00
21,000uf 15v	\$ 3.75	37,000uf 30v	\$ 9.00	30,000uf 40v	\$12.00
30,000uf 15v	\$ 5.00	40,000uf 30v	\$10.50	25,000uf 62v	\$12.00
31,000uf 15v	\$ 5.25	45,000uf 30v	\$11.00	4,500uf 64v	\$ 9.00
44,000uf 15v	\$ 5.50	50,000uf 30v	\$12.00	9,000uf 75v	\$ 8.00
47,000uf 15v	\$ 5.75	100,000uf 25v	\$14.00	10,000uf 75v	\$ 9.00
60,000uf 15v	\$ 7.00	15,000uf 30v	\$ 6.00	12,000uf 75v	\$10.00
63,000uf 15v	\$ 7.50	25,000uf 30v	\$ 8.00	16,800uf 75v	\$12.00
73,000uf 15v	\$ 8.50	30,000uf 30v	\$ 9.00	20,000uf 75v	\$14.00
80,000uf 15v	\$ 9.00	40,000uf 30v	\$10.00	20,000uf 75v	\$14.00
83,000uf 15v	\$ 9.50	40,000uf 30v	\$10.00	20,000uf 75v	\$14.00
100,000uf 15v	\$ 12.00	12,000uf 40v	\$ 6.50	20,000uf 100v	\$13.00
100,000uf 15v	\$ 12.00	12,000uf 40v	\$ 6.50	20,000uf 100v	\$13.00
140,000uf 15v	\$ 16.00	20,000uf 40v	\$ 7.50	20,000uf 100v	\$13.00
48,000uf 20v	\$ 6.00	21,000uf 40v	\$ 8.00	3,000uf 200v	\$ 6.00
10,000uf 20v	\$ 2.50	21,000uf 40v	\$ 8.00	2,000uf 200v	\$ 6.50
25,000uf 20v	\$ 6.00	31,000uf 40v	\$ 9.00	4,000uf 200v	\$10.00
76,000uf 20v	\$ 7.50	32,000uf 40v	\$ 9.50	5,000uf 200v	\$11.00
90,000uf 20v	\$10.00	33,000uf 40v	\$10.00	5,000uf 200v	\$11.00
7,000uf 25v	\$ 3.50	44,000uf 40v	\$12.00	7,000uf 250v	\$ 8.50

## WHAT'S IN SANTA'S SACK?

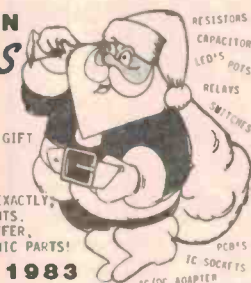

LOT'S OF CHRISTMAS GIFT BOXES.  
WHAT'S IN THE GIFT BOXES?  
WE CAN'T TELL YOU EXACTLY, BUT WE'VE GIVEN HINTS. IT'S A ONCE-ONLY OFFER. OVER 1,000 ELECTRONIC PARTS!

**Gigantic 1983**

## Christmas

**GIFT BOXES \$25.00**

## BURGLAR ALARMS

WE SUPPLY THE BEST LOCALLY-MADE AND IMPORTED BURGLAR DETECTION SYSTEMS.

12V CAR ALARM ENTRY/EXIT DELAYS, AUTO RESET... \$59.95  
HOME ALARM CONTROL MODULE ENTRY/EXIT DELAYS \$19.50  
R.D./A.C. CONTACTS, RESETS AUTOMATICALLY, ON/OFF SWITCH  
DE-LUXE CONTROL MODULE AS ABOVE, INCL SIREN \$55.00  
DRIVER, VARIABLE DELAY TIMES, VIBRATION DETECTOR CIRCUIT  
RACAL PASSIVE INFRA-RED DETECTOR... \$109.00  
ASTROL MIDI MICROWAVE DETECTOR... \$139.00  
12V ELECTRONIC SIREN HORN SPEAKER... \$27.50  
STROBE WARNING FLASHER ORANGE, BLUE, RED... \$29.50  
12V RECHARGEABLE BATTERIES  
1.2Ah \$19.50 2.6Ah \$29.50 4.8Ah \$39.50 SEALED LEAD-ACID GEL TYPE BATTERIES  
WE ALSO SUPPLY METAL BOXES, REED SWITCHES, POWER SUPPLIES, KEY-SWITCHES, VIBRATION SWITCHES, ULTRASONIC, RADAR AND SATELLITE ALARMS, ALL ACCESSORIES. ALARM CATALOGUE AVAIL. SOON - SEND SAE.

## DISCO STROBE

**\$29.50**

FLASH RATE 0-12/Sec  
Mains operated, ideal for parties, discotheques, etc, variable flash rate, teak finish wood cabinet, NEW IMPROVED MODEL!



## MOVING COIL CARTRIDGE

MODEL MC100

Was \$49.50

- Standard 3" mounting.
- Maximum coil signals for high output transformer not needed.
- Freq. response 15Hz-35KHz.
- High 2" output (18W/50mA/s)
- Tracking Force: 7-0 gram.
- 0.5m Diamond stylus.
- Complete mounting kit incl.
- Stylus easily replaced (\$15.00)

**NOW ONLY... \$24.95**

## 3 CORE MAINS LEADS

3 METRES usually \$3.30

**\$2.00 EA.**

10-24 \$1.75  
25-49 \$1.50  
50-99 \$1.35

## PAKS OF ASSORTED POTS

20 MIXED VALUES \$3  
100 MIXED VALUES \$10  
250 MIXED VALUES \$20

PACK/POST \$2 PLUS 5% OF ORDER VALUE.



**PRE-PAK electronics p/l**

**1a WEST ST, LEWISHAM, NSW**

**569-9797**  
24 HR PHONE ORDER SERVICE

**Phone or mail order BANKCARD accepted**




# LETTERS

Dear Sir,

In the course of my job I design (nothing spectacular), construct and commission electronic equipment. I recently built a power supply for an IMPATT microwave source. It actually consisted of three separate supplies, one of which was to supply 31 V at a current of up to one amp; regulation was not critical.

I opted to use a 30 Vac, 40 VA Ferguson low profile transformer (PL30/40 VA), with a fullwave bridge rectifier, two 2200  $\mu$ F capacitors followed by an LM317M high voltage, three-terminal adjustable regulator. The LM317M was a bit of an over-kill but it was easy to use.

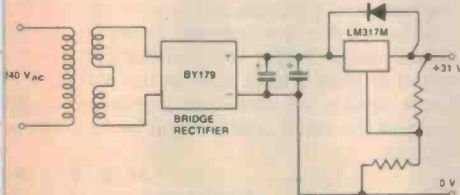I thought that it was all pretty ordinary, simple and effective. So you can imagine my surprise when the circuit started to sag around 700 mA. I checked the capacitors and the bridge rectifier diodes, replacing them, etc, etc.



However, the problem was with the transformer, which I also replaced but to no avail. The problem was saturation. The oscillographs in Figures 1, 2 and 3 illustrate this clearly. The supply was isolated from ground so there was no hassle in plugging a CRO into the secondary winding.

The 31 V stated supply did give 31 V (31.5 V in fact) unloaded, and the 30 Vac secondary seemed to be alright. The dc input voltage to the regulator was about 46 V.

However, when the transformer was loaded the story was totally different. The ac waveform was badly clipped, shown in Figures 1 and 2. The load voltage was 30.5 V and the current, measured with a Fluke multimeter, was 738 mA.

The dc input voltage to the regulator dropped to 32 V and the secondary ac voltage was 32 V, measured with the Fluke multimeter, a true RMS model. The peak voltage, as shown in the photographs, was only about 35 V. The RMS secondary current (again measured with the Fluke) was 1.04 A.

So for a dc output of 24.5 W from the filter circuit, the output from the transformer was 33.3 VA. It seemed to me that this 40 VA transformer was hard pushed, although it was technically within the specifications as the RMS output voltage is rated at 30 V with a full load.

For comparison, Figure 3 shows a similar oscillograph for another supply which is also part of the original IMPATT supply. It uses a PL15/20 VA, BY179 bridge, 5600  $\mu$ F capacitor (about 4400  $\mu$ F for the 31 V) and a 7815 IC. The problem is not quite so bad. The load current for the 15 V supply was 738 mA at 14.7 V which is comparable to the 31 V supply, without the same sogginess.

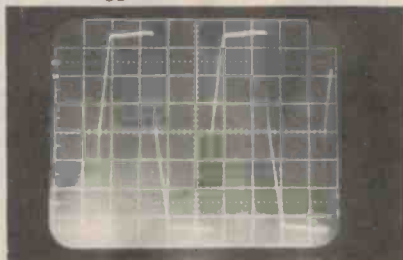


Figure 1. 30 Vac: 10 V/div; 5 ms/div.

As it turned out, the 31 V supply has only to supply 200-300 mA. The specified 1 A was an over-kill, so I was saved from trying to shoehorn a larger transformer into the available space.

All this tends to vindicate my thoughts on the design of power supplies. My measurements also back up certain statements made in several editions of the National Semiconductor Voltage Regulator Handbook i.e.: if a transformer (and hence a power supply) is intended to run near its rated maximum output current for a reasonable length of time (which would be as low as one second in my particular case) then the VA rating of the transformer should be at least 50% higher than the dc power taken off at the filter capacitors.

National quote figures more like 80%. This is not surprising at all, considering that the peak secondary current of the transformer can easily be five to ten times greater than the dc output current, due to the highly nonlinear nature of the rectifier/filter capacitor circuit.

Two points should be made.

1. The problem was mainly that the peak voltage of the secondary dropped quite drastically when loaded. I have been told that Ferguson transformers can be good at this sort of sogginess.
2. The reluctance of the 20 VA transformer's core is probably less than that of the 40 VA; the core cross-section appears to be the same but the magnetic path length for the 20 VA is shorter.

I am bringing this to your attention because I think you may find it valuable in your work, and ETI readers may wish to know. I have criticised statements published in ETI before, with respect to transformer rating and supply output power.



Figure 2. 30 Vac: 20 V/div; 5 ms/div.

Let me state my case clearly. It is not sufficient to use a transformer where the secondary is rated as E volts RMS at I amps, for a dc output of  $\sqrt{2} \times E$  volts dc at I amps dc (neglecting diode drops and other considerations).

I am not saying that ETI magazine is guilty of this, but it does seem to be a pervading idea that I have often come across. In fact, I do not think that it would be wise to choose a transformer that has a VA rating on the secondary equal to the expected dc power drawn.

A full analysis of the operation of a power supply would be extremely tedious due to the non-linear nature of rectifiers and transformers (I have seen some bizarre capacitors too) and I do not think that it is necessary.

In most cases power supplies can be built by 'rule-of-thumb'. However, I have come across so many poorly designed power supplies that I am convinced that many people have short thumbs when it comes to designing simple power supplies.

Overspecifying transformer and rectifier ratings (say 50%-100% over) is not as ludicrous as it may appear to be. Large devices operating at a low power usually run cooler than small devices operating at the same power. Therefore, the larger devices are probably more efficient and certainly more robust.

I wonder how many hobbyists consider the effects of the hot Australian summer on circuits they construct. A transformer in its case, running at the full rated VA, can easily reach a temperature of 40°C-50°C in a room which is only at 20°C-25°C.

Phillip Dennis  
Chippendale NSW


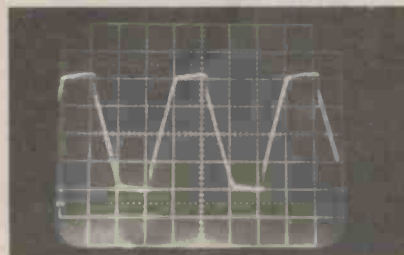


Figure 3. 15 Vac: 10 V/div; 5 ms/div.

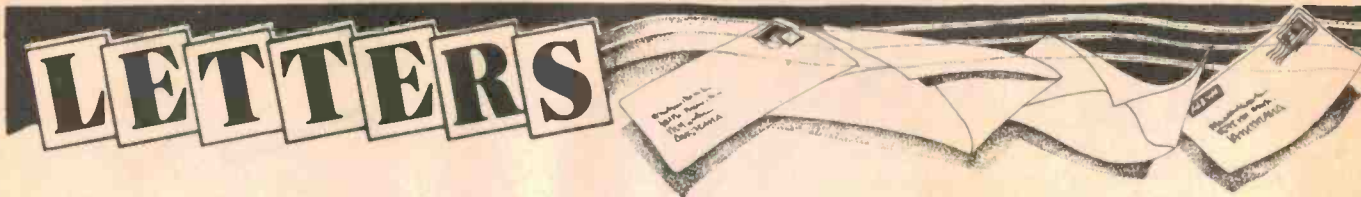

# LETTERS



The following comments are listed in order to assist your readers in choosing suitable transformers, rather than being disappointed, as was Phillip Denniss.

1. If the results achieved by Phillip Denniss are compared with the literature on Choke Input Filters it will be seen that, in effect, the PL30/40 VA is acting as both a transformer and a choke. Whilst a choke input filter requires a higher applied voltage to produce the same output voltage as that of a capacitor input filter it has the advantages of cheaper rectifiers and filter capacitors. Filtering requires less capacitance of lower ripple rating.

2. The leakage inductance of the PL30/40 VA is in the order of 30 mH when referred to the secondary. The PL20/40 VA is in the order of 10 mH and a tightly coupled transformer could be less than 1 mH.

3. The 'PL' range of Ferguson transformers has been designed to meet the requirements for a low profile transformer, achieving outputs that could not be obtained with conventional transformers meeting the same limiting dimensions. The design, with separate bobbins or separate bobbin sections, provides the ultimate in electrical safety.

4. The 'PL' range is designed with Class 'E' (120 °C) materials which allows a 90 °C rise on 25 °C ambient (75 °C and 40 °C). Since the case is designed to dissipate heat (the copper/case differential can be as low as 15 °C) the transformer runs much cooler in a metal case acting as a heat sink. Generally the limiting temperature will be that which the associated electronic componentry can tolerate.

5. If a 30 V stock transformer is required, the Ferguson Selection Guide lists types from 0.17 A to 4.0 A. Phillip Denniss answers his own question when he says "The specified 1 A was 'overkill', so I was saved from trying to shoehorn a larger transformer into the available space".

**Roy Robinson,**  
Senior Design Engineer.  
Ferguson Transformers

(Ferguson Transformers are only too willing to discuss any problems you may have with their transformers, so don't hesitate to contact them. — Ed.)

Dear Sir,

As you may be aware there has been sold a large quantity of radiocommunications equipment, including scanners, capable of being used to intercept radiocommunications.

While the court ruled in the *Golds v Comerford* case that the operation of a receiver for interception purposes without a licence is not an offence under the Wireless Telegraphy Act, I understand that its use to monitor communications carried on Telecom's public automatic mobile radio telephone system (AMTS) would constitute an offence against Section 7 of the Telecommunications (Interception) Act 1979.

Furthermore, if a person prints or publishes any writing which incites, urges, aids or encourages any person to commit the above offence, it may constitute a breach of Section 7A of the Crimes Act 1914. That Section creates the offence of incitement to break Commonwealth or Territory laws.

I feel it is my duty to draw the above matters to your attention, and also to point out the need for care in publishing technical articles and advertisements for radiocommunications equipment in your magazine to ensure that you do not encourage the unlawful use of receivers.

In particular, references in advertising material to the ability of certain receivers to intercept radiocommunications carried on Telecom's public automatic mobile radio telephone system should be carefully considered.

**M. R. Ramsay**  
First Assistant Secretary,  
Radio Frequency Management Division

Many thanks for your letter regarding the use of receivers to monitor communications on Telecom's public automatic mobile radio telephone system (AMTS).

I would like to know how the various acts relate to a person using a scanning receiver, or some other type of receiver covering the appropriate frequencies, monitoring (intercepting, if you like) channels used by State and Federal Police, Customs and government or non-government security services?

I would be interested in a reply, not only with regard to how it affects my publication, but how it affects readers who use scanners, as well.

**Roger Harrison**  
Editor, ETI

Dear Mr Harrison,

The following discussion is presented in response to your request for information on how current legislation affects the use of receivers to intercept communications on various other services.

In accordance with Sections 4 and 5 of the Wireless Telegraphy Act a person may not establish, erect, maintain or use stations and appliances for the purpose of transmitting or receiving messages by means of wireless telegraphy, unless he has been granted a licence by the Minister.

As I mentioned previously, the Court of *Golds v Comerford* decided that receiving within the meaning of the Wireless Telegraphy Act does not include interception, and the operation of a receiver for interception purposes without a licence is, therefore, not an offence under the Wireless Telegraphy Act.

It should be remembered, however, that the judgement in question was handed down by a single judge of the Victorian Supreme Court. It is, therefore, only binding on Victorian District and Magistrates' Courts. As far as other Courts are concerned it has persuasive authority only.

Assuming the law to be as laid down in *Golds v Comerford*, the interception of communications on services other than AMTS would not constitute an offence against Commonwealth law.

Regarding relevant State legislation, I understand that the New South Wales Government is planning to legislate against the use of devices for bugging. However, as my knowledge of the subject at this stage is limited to what I have seen in the media, it is not clear to me how such legislation would affect the interception of radiocommunications.

**M. R. Ramsay**  
First Assistant Secretary,  
Radio Frequency Management Division

## Australians are dying younger from heart disease.



National Heart Foundation.



# MINI-MART

Where readers can advertise —  
For Sale/Wanted/Swap/Join

● We'll publish up to 24 words (maximum) totally free of charge for you, your club or your association. Copy must be with us by the 1st of the month preceding the month of issue. Please — please — print or type adverts clearly, otherwise it may not turn out as you intended! Every effort will be made to publish all adverts received; however, no responsibility for so doing is accepted or implied. Private adverts only will be accepted. We reserve the right to refuse adverts considered unsuitable:

● Conditions: Name and address plus phone number (if required) must be included within the 24 words. Reasonable abbreviations, such as 25 W RMS or 240 Vac, count as one word. Adverts must relate to electronics, audio, communications, computing etc — general adverts cannot be accepted. Send your advert to:  
ETI Mini-Mart,  
4th Floor, 15 Boundary St,  
Rushcutters Bay NSW 2011.

FOR SALE: LOW LOSS coax cable, RG34, black, 16 mm dia, loss 1.4 dB/100 ft at 100 MHz, 300 ft drum, \$100. Coax PT29M, 10 mm dia, 70 ohm 70 c/yd. VK2ASZ, 179 Rusden Rd, Blaxland NSW 2774.

## AUDIO

FOR SALE: CASIO MT70 Polyphonic Keyboard, as new, \$225 ono. Steve (02)663-9999 ext 241.

FOR SALE: QUAD 2 A, pair KT66 valves, GWO, \$40. AWA 100 W PA amp, pair KT88 valves, GWO \$100. VK2ASZ, 179 Rusden Rd, Blaxland NSW 2774.

FOR SALE: KRIESLER turntable/tuner, \$350. (No speakers). Matthew Croft, 31 Addison Rd, Black Forest SA 5035.

FOR SALE: HAFLER DH200 MOSFET power amplifier, 100 WRMS per channel, excellent condition, \$525 ono. Peter Prava, 60 the Esplanade, Wagga Wagga NSW 2650. (069)21-3692.

SELL: Series 5000 preamp and power amp, Blueprint. Black Monolith. T200 speakers, 150 WRMS, 400 W p-p. Aurex (Toshiba) deck, Dolby/Adres. Akai turntable, direct drive, quartz lock and Ortofon Concord cartridge. All new with warranties, reasonable offer. (02)646-4662.

## MISCELLANEOUS

WANTED: ONE job. I am currently doing the COT (electronics) at Boxhill TAFE. I am enthusiastic to learn. G. Anastasi, 37 Churchill Way, Kilsyth Vic. (03)723-1988.

WANTED: TALKING ELECTRONICS Nos 3, 6, 7, 8 and 9. Will buy or swap magazines for same. Sell DX160 speaker, \$10. T. Dodsworth, P.O. Box 917, Ingham Qld 4850.

CRYSTAL OVENS: SIEMENS, two only, 100 kHz, ex ABC, valve. One fixed output, \$55, the other variable output, \$75. Mark (02)816-1498 bh.

FOR SALE: 103 assorted new and near new TV valves, approx. value \$300, including popular EHT valves, sell for \$95 ono. C. Chapman, 15 Merinda Cres, Koorlingal NSW 2650. (069)22-4305.

SELL: PAST issues of ETI, EA, WW, PW and PE. Over 250 magazines, Kevin Wilson, P.O. Box 208, Applecross WA 6153. (09)364-2843 ah or (09)420-6901 bh.

MICROBEE: 32K, EDASM, Wordbee, Ritron monitor, Sharp cassette player. Heaps of games, etc, on tape, \$650 ono. Andy Hardy (045)70-2184 bh.

MICROBEE: MYTEK Machine Code and BASIC tutorials. Brand new and still in original packaging. Works on pre-IC models only. \$12.50 each. (02)713-9473 ah.

FOR SALE: PRINTER for TRS80-PC1 and Sharp PC1211 pocket computer. All the accessories included, \$95. Frank Rees, 27 King St, Boort Vic. 3537.

WANTED: DGZ80 CPU board. Terry Smith, Lot 77, Jeffrey Ave, St Clair NSW 2232. (02)670-4110.

COMPUTER TERMINAL: GE Termlnet 30" with paper and magnetic tape accessories. Photos and specifications available, \$1500. H. Johnson, 47 Wahroonga Rd, Kanwal NSW 2259. (043)53-2274 bh.

SELL: ZX81 as new, leads, manual, 1.2 A power pack, tapes etc. Also 16K RAM pack, \$80. Many constructional projects. Write to F. Papadopoulos, 13 Kroombit St, Dulwich Hill NSW 2203.

FOR SALE: 8" floppy disk drive, single sided. No controller, box or power supply. Ex IBM370 Microcode loader, \$150 ono. Stever (03)573-2266 bh.

SELL: ETI-660, colour, 3K modulator, hex-keyboard, transformer, step-repeat function, cassette software, fibreglass case, \$120 ono. TV game, two cartridges, joysticks, \$20. M. Samerski (02)542-1365.

MICROBEE: FOUR reel poker machine plus free copy of Battleships, only \$9.95 plus \$1 postage. Send mail order to David Peters, 190 Bourke Rd, Umina NSW 2257.

VIC-20 COMPUTER: Excellent condition, great games machine and home computer, still in box, \$240. Mr Begg (08)31-0310 after 5 pm.

ACT VIC-20 bimonthly magazine: Many interesting articles and programs. December issue \$1.50. Bimonthly \$8 per year. Write to Chris Groenhout, 25 Kerferd St, Watson ACT 2602.

NORTH STAR HORIZON: Z80A, 64K RAM, two 340K disks, 12-slot S100 motherboard, two serial, parallel ports, considerable software, perfect condition, \$3300 ono. (07)30-1460.

SELL: ETI-660, 8K RAM, case, articles, programs, cassette included, \$100. (03)743-5129.

FOR SALE: EXIDY SORCERER computer, 56K RAM, two disk drives, 610K storage, word processor and heaps of software. Must sell, only \$1800. Many extras. Tony (02)449-4163 after 6 pm.

FOR SALE: MEMORY board, S100 buss, 16K static RAM with manuals, \$115. Gordon (07)369-8013.

WANTED: 8" disk drives, either one or two with power supply. Prefer SS SD but will consider better drives. Paul Shields, 2/39 SMQ, Dampier WA 6713. (091)83-1724 ah or (091)83-1000 bh.

FOR SALE: PRINTER terminal, GE Termlnet 30, with magnetic tape accessory, little used, excellent condition, \$350 ono. (043)92-6838.

FOR SALE: ZX81 software, ZX Monopoly (two players), \$12 Tape copier, \$9. Shape table plotter, \$9. The lot, \$25. N. Kefford, 120 Church St, Yass NSW 2582.

## COMMUNICATIONS

FOR SALE: CREED 7B teleprinter with loop supply, manual, supplies, etc, 240 Vac. Can deliver to city, VGC, \$50. D. Hutchinson, 69 Bulla Rd, Bulla Vic. 3047. (03)307-1368.

FOR SALE: FREQUENCY meter, 1 GHz, ETI. Built and tested by professional engineer, modified and improved, \$250 ono. A. Lay, 44 Swales St, Mundingburra Qld 4812.

WANTED: TELETYPE Model 15 or ASR33. E. Plunkett, Hill St, Eugowra NSW 2806. (068)59-2472.

FOR SALE: TWO No. 14 teleprinters, one three-head TD sender, \$40. Teletype power supplies contain 240/115 V, 400 W transformer, swinging choke, etc, \$10. VK2ASZ, 179 Rusden Rd, Blaxland NSW 2774.

FOR SALE: STEEL tower, self supporting, 15 ft at base, 70 ft high, brand new in box, ready to assemble, ex DCA with plans, \$1200 ono. VK2ASZ, 179 Rusden Rd, Blaxland NSW 2774.

FOR SALE: NATIONAL DR-31 SW/MW/FM receiver, only 16 months old. Bargain at \$240. John (03)363-7773 ah.

## COMPUTERS


FOR SALE: DGZ80, S100, 32K, PCG, documentation, Software: Dissem Edtasse, games, level II BASIC (ROM). Card case (10-slot), PSU, fan, STD keyboard, \$700 ono. Michael (002)44-4148.

WANTED: SYM-1 with monitor 1.0 or 1.1, working or not. Write Glenn Dabrera, c/- 8/11 Walsh St, Ormond Vic. 3163. (03)578-9045.

WANTED: MISCELLANEOUS and game programs to suit Commodore Vic-20. M. Kenschaw, 4/141 Hotham St, Saint Kilda East Vic. 3183.



# DREGS

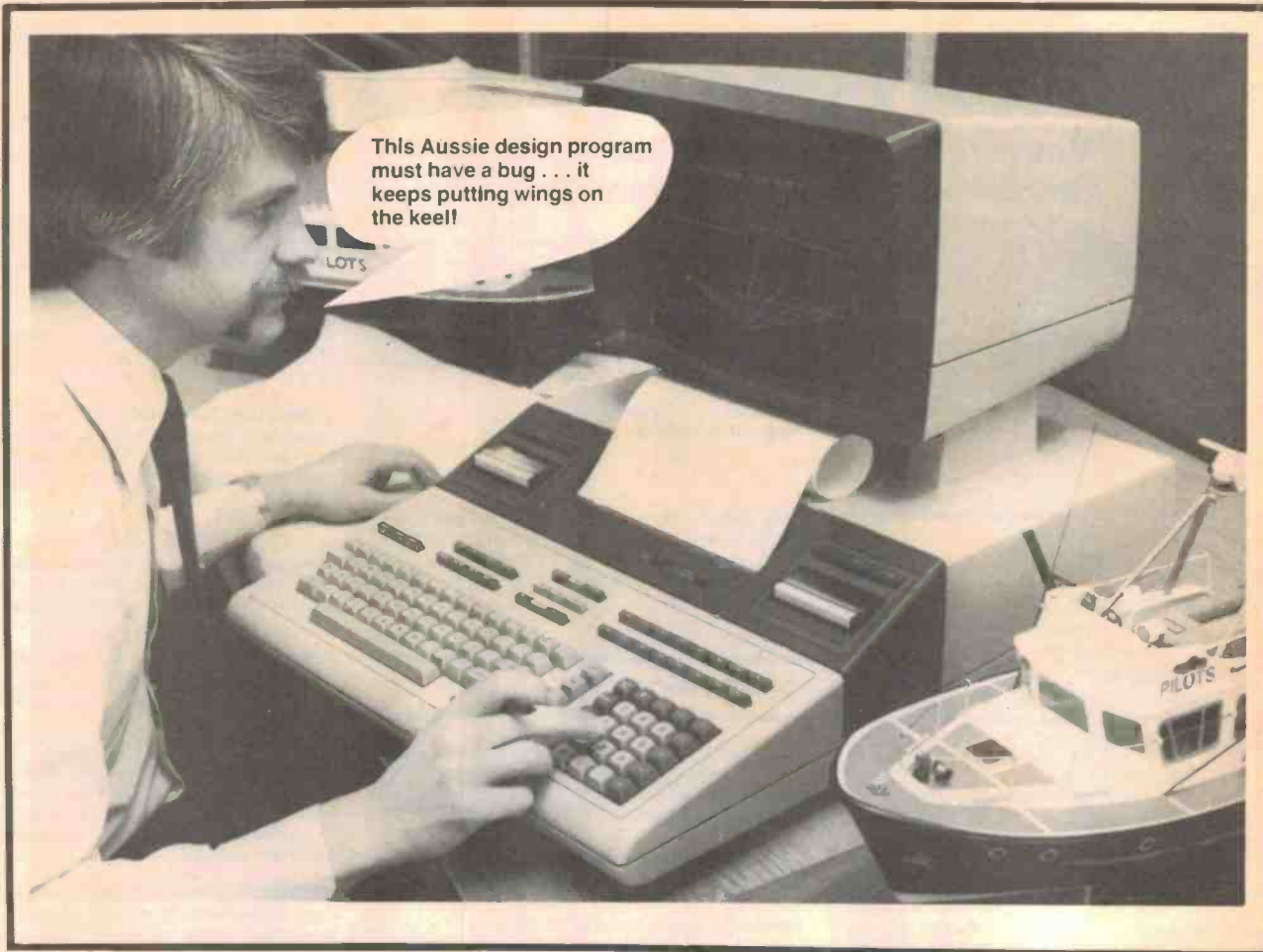

NOW THE STORY can be told. Now, that is, since David Tilbrook is no longer here to look over the Dregs editor's shoulder and censor what I am about to divulge.

Just so you all know who I'm talking about, that's him below.



As has been our practice over many years, when the engineers needed a few tools and components for the project laboratory from time to time, they would go out and pur-

chase their requirements, submitting the store's docket to our Accounts Department along with a Petty Cash Claim form for a refund of the amount spent. Standard business practice.

Every now and then some pretty substantial purchases were made (to an accountant, any purchase over \$10 is 'substantial'). As is their wont, the Accounts Department would occasionally send someone down to the ETI lab to query randomly chosen claim dockets. Fair enough I suppose, accountants can't really be expected to know or understand a docket that says "10 x SCI41, 30 x 100k/5%, 6 x 4011BE . . . etc". It would be duly explained, the objects paraded for viewing and the delegated Accounts Department person would go away with a quizzical facial expression, mollified, but believing.

Then, one day, an Accounts Department person who had never previously been delegated the job, wandered into ETI's office area with a docket in hand, with a very

puzzled expression, and enquired who might be the David Tilbrook person who had submitted the docket in question. Said Accounts Department person was pointed toward David Tilbrook who happened to be standing nearby.

Accounts Dept. person's expression turned from one of puzzlement to *thunderous disbelief* on sighting the famous D.T.

"What seems to be the problem?", David enquired in his characteristic gentle manner.

"What are *you* doing putting in a claim for a *hair dryer*?", blurted out Accounts Dept. person!

Amid the uproar of mirth that swept the office, much to the embarrassment of Accounts Dept. person, David, in his characteristic calm, logical manner, explained:

"It's for drying pc boards after they've been etched."

Accounts Department person slunk out amid hoots, laughter and general chyacking.

We haven't had a visit from them since.





CDP-101

COMPACT  
disc  
DIGITAL AUDIO

# Hear digital perfection.

## Introducing the Sony Compact Disc Player

When we used our long experience in digital technology to create the CDP-101 Compact Disc Player, we wanted to give you something more than the world's clearest sound.

**WIRELESS REMOTE CONTROL** Full-function remote control.

**3-WAY MUSIC SEARCH**  Instant direct access to any selection with the 10-key pad on remote control unit.  AMS (Automatic Music Sensor) allows access to the beginning of next or previous selection.  2-speed bi-directional search to find any desired music passage.

**REPEAT FUNCTION** Program to repeat the entire disc, one selection, or a specific portion of music.

**3-FUNCTION DIGITAL READOUT DISPLAY**  Selection number.  Time lapse of selection being displayed.  Remaining time on the disc.

**LINEAR SKATE DISC LOADING** Just press the button, platter control and cueing are automatic.

Get even more perfect sound with the Sony Digital Audio Component System, "Precise Series".



**SONY**

AUD 0391



# Ladies and gentlemen, be seated. (While you tune your rec

The best place to tune your receiver is where you listen to it, sitting down.

And with the new Yamaha R100 you can do exactly that.

Its unique remote control gives you push button command over the R100's Computer Controlled Sound System which allows you to select from five different preset frequency response curves.

And that's in addition to all input functions like phono, video auxilliary, tuner and both tape monitors as well as remote selection of any one of ten preset AM and FM stations.

The tuner itself has Computer Servo Lock Tuning to automatically select the optimum signal, a Dynamic Noise Canceller for exceptionally quiet, noise free reproduction from tape, disc or tuner and a Stereo Spatial Expander to broaden the total stereo sound field.

The new Yamaha R100 is literally the 'state of the art' in stereo receivers, a phrase often used by others but a level of perfection only Yamaha builds to.

And as with all Yamaha audio equipment, the R100 is covered by Yamaha's unique 5 year full parts and labour warranty.

For a free brochure on the remarkable Yamaha R100, see your Yamaha dealer or clip the coupon below.

Post to: Yamaha R100 Receiver Brochure,  
Rose Music Pty. Ltd. 17-33 Market Street,  
South Melbourne, Vic 3205.

Name .....

Address .....

.....

Postcode .....

# YAMAHA

UCRRM 5155

