 


COMMUNICATIONS QUARTERLY

THE JOURNAL OF
COMMUNICATIONS
TECHNOLOGY

Spring 1994


\$9.95



- HF Radio On Mars
- A Gyator Tuned VLF Receiver
- Arcs And Sparks: Part I
- Solar Spectrum
- Technical Conversations

- TX High-Pass Filter Application
- Quarterly Devices
- Comparing Mininecs
- Surface Acoustic Wave Technology
- A New Method For Measuring Cable Loss

DEMAND THE BEST

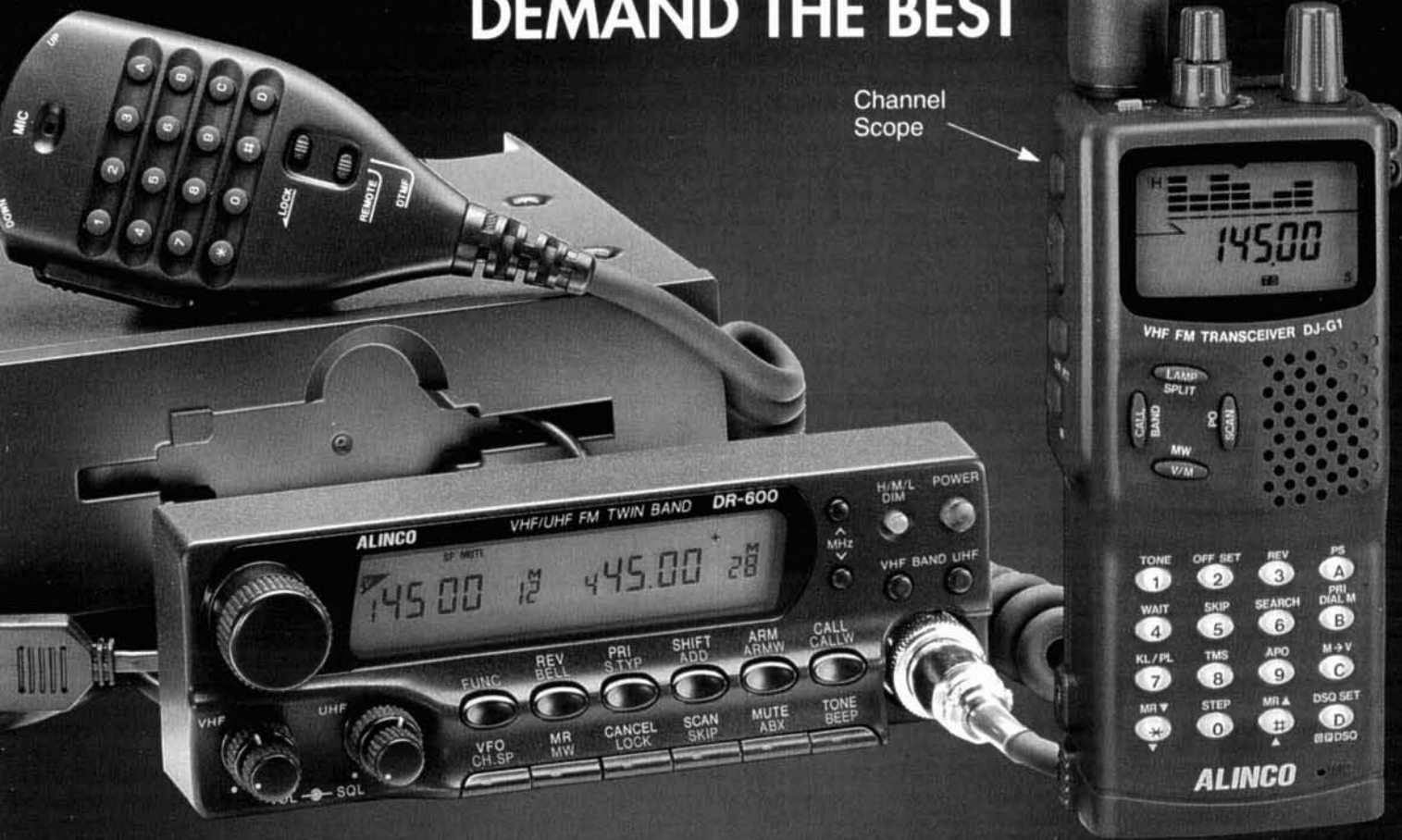

DR-600T (144 MHz/440 MHz)

The outstanding abilities of the DR-600T set it apart from every other radio. Features like Wide Frequency Coverage, Excellent Intermod Rejection, Direct Frequency Entry from the microphone, Three Output Power Selections, Autopatch Memories, and 6 Scanning Modes make the DR-600T the radio of choice for demanding users. The Remote Mount Head allows for custom installation in most any vehicle, and also helps to deter theft.

This road-ready rig can also be remote controlled by any radio that transmits DTMF tones. This remarkable feature allows the DR-600T to act as a full-featured Cross-Band Repeater. For added control, a security code can be programmed that will allow control only by the control operator (you).

DJ-G1T

The DJ-G1T 2m HI from ALINCO scores another "First" for Amateur Radio technology. Our new "Channel Scope" feature opens new doors for Ham operators. Now it is possible to visually monitor up to 7 memory channels at once with just a glance at the display.

Also, the Channel Scope feature can be used to show band activity in the frequency domain, much like a Digital Spectrum Analyzer. Hunting for band activity just got easier.

Other outstanding features include 440 Receive, 80 Memory channels, AM Aircraft receive, 5 Autodialer channels, DSQ for private paging, Cross-Band Semi-Duplex, 6 Scan Modes, and Odd Splits on all Memory Channels.

Better Products, Better Service.
See for yourself why people are coming to ALINCO.



438 Amapola Ave., #130,
Torrance, CA 90501
Phone: (310) 618-8616
Fax: (310) 618-8758

— Other Great Products from ALINCO —



No Matter What Scanner You Have It's Not Complete Without a DC440



With the DC440 We bring you a Complete Scanning System

Scanning the busy VHF/UHF communications bands has always been exciting. Now monitoring enthusiasts are discovering that adding a DC440 to their Scanner or Communications Receiver* adds a new dimension to listening. Virtually all commercial, industrial, business and governmental two-way radios are now using sub-audible tones or codes and being able to display them provides valuable insight into who is talking or being called. Keep tabs on individuals and monitor repeater access codes.

Computer Aided Scanning

Use the DC440 with Scan-Star™ Software to monitor 50 CTCSS Sub-Audible Tones & DCS Codes and the TouchTone™ (DTMF)

The DC440 is small in size and has an exceptional back lit 2x16 character LCD display. In addition to it's all mode decode, there are 5 other operating modes and convenient front panel controls.



Ideal For Testing Two Way Radios can be directly connected to the Model R10 Interceptor* for checking CTCSS, DTMS, Deviation, Signal Strength and Audio. **Update older service monitors.**

Unique features such as an actively decoding indicator, squelch connection, a serial communications

interface and ToneLog™ software data logging for PC. There is a scrollable 126 character DTMF display of actual characters to prevent lost data.

For Communications Monitoring, Two Way Radio Test, Security & Surveillance, the DC440 is the Most Capable Decoder available today.

*Will likely require internal connection to scanner or receiver.

DC440 - 3.1 Decoder	\$259.
CX12 RS-232C Interface Converter	\$ 89.
ToneLog™ Software for the PC	\$ 49.
NiCad 44 Battery Pack	\$ 39.

Order Line **1-800-327-5912**
Fax 305-771-2052

OPTOELECTRONICS

305-771-2050 • 5821 NE 14th Avenue., Ft. Lauderdale, FL 33334

5% Ship/Handling (Max \$10) U.S. & Canada. 15% outside continental U.S. Visa, Master Card, C.O.D., Cash or Money Order only
All specifications and prices are subject to change without notice or obligation.

Kenwood's TM-942A/742A/642A— Triple Triumph

NEW
TM-642A

TM-942A



TM-942A/742A/642A
FM MULTIBANDER

Features

- Max. 50W output (144MHz), 25W (220MHz), 35W (440MHz), 10W (1200MHz)
- 101 memory channels & memory bank system
- Independent SQL & VOL controls for each band
- Automatic band change
- Built-in DTSS selective calling feature with page
- Selectable frequency step ■ 8 scan modes per band
- Time Operated & Carrier Operated scan stop modes
- Direct frequency entry with supplied microphone
- Tone alert with elapsed time indicator
- S-meter squelch, noise squelch & auto squelch
- Cross-band repeater ■ Muting for sub-band circuit
- Multiple lock functions ■ Wireless remote control function
- Built-in CTCSS encoder & optional TSU-7 decoder
- Date & time display, stopwatch, alarm & on/off timer
- 3-position RF output power control
- Auto power-off with warning beeper ■ Time-out timer
- Separate control & display units (optional cable kits)

Good things come in threes. Like Kenwood's distinctive TM-942A (144MHz/440MHz/1200MHz), TM-742A (144MHz/440MHz), and new TM-642A (144MHz/220MHz)—high-performance FM multibanders that demonstrate the best in mobile communications technology. Besides offering triple receive and display capability, the TM-942A can even receive all three bands simultaneously. For the TM-742A and TM-642A, you can choose one of several optional band units, enabling triple band operation with the same triple simultaneous receive. Top-notch features include 101 memory channels (all available for split operation), automatic band change, DTSS with page, and S-meter squelch. There's even a wireless remote control function. Yet operation is remarkably simple, thanks to sophisticated microprocessor control, high-visibility illuminated keys, and clear status displays. You wouldn't expect any less from Kenwood. But there's more: you can mount the controls and display separately from the main unit (requires optional kit) for unique 3-way convenience.

KENWOOD COMMUNICATIONS CORPORATION
AMATEUR RADIO PRODUCTS GROUP
P.O. BOX 22745, 2201 East Dominguez St., Long Beach, CA 90801-5745
KENWOOD ELECTRONICS CANADA INC.
6070 Kestrel Road, Mississauga, Ontario L5T 1S8

KENWOOD

COMMUNICATIONS QUARTERLY

THE JOURNAL OF
COMMUNICATIONS
TECHNOLOGY


CONTENTS

Volume 4, Number 2

Spring 1994



Fry, page 13

 

Littlefield, page 94

- 6 Tech Notes**
Peter Bertini, K1ZJH
- 13 HF Radio On Mars**
Craig D. Fry, WL7C and Robert J. Yowell, KC5BRG
- 24 A Gyrator Tuned VLF Receiver**
Arthur J. Strokes, Sr., N8BN
- 27 Arcs And Sparks: Part 1**
W.J. Byron, W7DHD
- 44 The Solar Spectrum**
Peter O. Taylor
- 49 TX High-Pass Filter Application**
Marv Gonisor, W6FR
- 53 Comparing Mininecs**
L.B. Cebik, W4RNL
- 73 Technical Conversations**
Richard E. Franklin, W2EUF; John S. (Jack) Belrose, VE2CV; and David M. Barton, AF6S
- 83 Surface Acoustic Wave Technology**
Byron Bergeron, NU1N
- 94 Quarterly Devices**
Rick Littlefield, K1BQT
- 98 A New Method For Measuring Cable Loss**
A.E. Popodi, AA3K/OE2APM

Cover Photo: In this issue, Bryan Bergeron, NU1N, explores Surface Acoustic Wave (SAW) technology. The cover illustrates facets of this subject. In the upper left, we see a SAW schematic, the grid represents the semiconductor wafer before etching, and the rectangular object in the foreground is a SAW filter/delay showing transducers and wave propagation. Photo by NU1N.

EDITORIAL

From The Future To The Past, And Back Again.

The operator looked out the window at the stark rose-colored horizon. He returned his attention to the radio in front of him and spoke into the microphone . . .

"KA1STC, KA1STC, KA1STC, this is K1ZJH calling from Mars Station Alpha. QSL?"

On Earth, KA1STC crouched close to the speaker of her transceiver. She heard a loud crash of static, then out of the ether came the faint, but audible, call . . .

"KA1STC, KA1STC, KA1STC, K1ZJH."

She eagerly replied:

"K1ZJH, KA1STC, you are 5-by-2 on Earth."

After several minutes delay came the reply:

"5-by-2 Mars, Roger?"

KA1STC sent her final message into space, "Roger, 73," and awaited a final call from K1ZJH. "73," came the faint reply.

With that final 73, K1ZJH and KA1STC could lay claim to the first two-way QSO between Mars and Earth, and a special award—"The Planet Mars QSO Cup."

In fact, The Planet Mars QSO Cup is a real award that awaits the first two amateurs to complete a two-way amateur radio contact between Earth and the Red Planet. The Mars QSO Cup was the brainchild of two hams—Fred Johnson Elser, K3AA, and Stanley M. Mathes, K1CY—who created the award in 1928. The trophy is on display at The American Radio Relay League Headquarters in Newington, Connecticut, waiting to be claimed by the winners.

During the same decade that Elser and Mathes were designing their "heavenly" award, a group of prominent scientists were devoting their time to the design, construction, and operation of arc and spark transmitters. Many of you have probably heard of these types of transmitters; articles about them have appeared in the *AWA Journal* and *QST*. But perhaps you are not aware that, while arcs and sparks were developed within five years of each other and their fundamental circuits were almost identical, their operational characteristics were quite different. Bill Byron, W7DHD, has performed a detailed study of these transmitters, and presents his findings in this issue of *Communications Quarterly*. He begins his discussion by comparing arcs and sparks, and continues with an in-depth look at spark transmitters. A more thorough treatment of arc transmitters will appear in a later issue. To bring his work into the present, Bill uses a Fourier

Analysis program written in BASIC to calculate the frequency spectra of spark transmitters.

While the editorial staff of *Communications Quarterly* tends to concentrate on publishing information about current state-of-the-art technologies, we like to include historical material with present-day applications periodically. It is interesting to note that a lot of the technologies we think of as recent developments in the communications field, have roots reaching back to the earliest days of radio. A case in point: You may assume that wideband RF transformers were developed to meet the needs of broadband matching circuits for semiconductor-based circuits. Yet as early as 1924, companies such as Acme Aparatus Company were marketing wideband untuned transformers covering the 200- to 500-meter range. Intended for broadband interstage RF amplifier stages in reflex radio designs, today's broadband baluns and interstage transformers.

But let's return to Mars, and our intrepid radio operator. While it may seem far-fetched to even consider two-way communications with Mars, who's to say that it won't be a part of our future? After all, how many of us thought we'd be exchanging QSOs with space stations and shuttles orbiting the Earth? It's quite possible, that sometime in the future (granted it probably won't be in our lifetimes), men will visit Mars. Already, NASA and the European Space Agency (ESA) have plans to launch missions to the Red Planet at the end of this decade. These unmanned missions, the Mars Environmental Survey (MESUR) and MARSNET, would involve orbiting satellite relays gathering data from Mars-based rovers and fixed land stations for retransmission back to Earth. In their article, "HF Radio On Mars," Craig Fry, WL7C, and Robert Yowell, KCSBRG, discuss these missions, and put forth their own theory that HF radio would be a viable communications mode for future Mars explorers.

In all scientific endeavors, a knowledge of the past and the present intertwine allowing projections for future technologies. The dreams of the past are often the realities of the future. We must always bear in mind that what is past is prologue.

Terry Littlefield, KA1STC
Editor
Peter Bertini, K1ZJH
Senior Technical Editor

EDITORIAL STAFF

Editor

Terry Littlefield, KA1STC
Consulting Technical Editor
Robert Wilson, WA1TKH
Senior Technical Editor
Peter Bertini, K1ZJH
Assistant Editor
Nancy Barry

EDITORIAL REVIEW BOARD

Forrest Gehrke, K2BT
Michael Gruchalla, P.E.
Hunter Harris, W1SI
Bob Lewis, W2EBS
John Marion, W1QM
Walter Maxwell, W2DU
Jim McCulley, P.E.
William Orr, W6SAI

BUSINESS STAFF

Publisher

Richard Ross, K2MGA

General Manager

John Dorr, K1AR

Advertising Manager

Arnie Sposato

Sales Assistant

Tracy Parbst

Controller

Frank Fuzia

Circulation Manager

Catherine Ross

Operations Manager

Melissa Nitschke

Data Processing

Carol Licata

Customer Service

Denise Pyne

PRODUCTION STAFF

Art Director

Elizabeth Ryan

Asst. Art Director

Barbara Terzo

Artist

Susan Reale

Electronic Composition Manager

Edmond Pesonen

Production Manager

Dorothy Kehrwieler

Production

Emily Kreutz

Tracy Parbst

Photographer

Pat Le Blanc

A publication of

CQ Communications, Inc.

76 North Broadway

Hicksville, NY 11801-USA

Editorial Offices: P.O. Box 465, Barrington, NH 03825. Telephone/FAX: (603) 664-2515.
Business Offices: 76 North Broadway, Hicksville, NY 11801. Telephone: (516) 681-2922. FAX: (516) 681-2926.

Communications Quarterly is published four times a year (quarterly) by *CQ Communications, Inc.* Subscription prices: Domestic—one year \$29.95; two years \$56.95. Foreign—one year \$39.95; two years \$76.95. Foreign Air Mail—one year \$60.95; two years \$118.95. Contents copyrighted CQ Communications, Inc. 1994. *Communications Quarterly* does not assume responsibility for unsolicited manuscripts. Allow six weeks for change of address. Second-class postage paid at Hicksville, NY and additional mailing offices.

Postmaster: Please send change of address to *Communications Quarterly*, CQ Communications, Inc., 76 North Broadway, Hicksville, NY 11801. ISSN 1053-9344.

0 to 9600



With Packet Transmission

Satisfy your need for speed with the new PK-96 9600 baud packet controller from AEA.

This high-performance machine comes standard with 1200 baud AFSK tone signaling, as well as 9600 baud K9NG and G3RUH compatible direct frequency modulation. The PK-96 makes an excellent terrestrial or satellite data controller. It can be used for high-speed data links to eliminate bottlenecks and increase system capacity.

Big capability in a small package is what

you get from the PK-96. Under the hood, there is a 18K battery-backed MailDrop which is easily expandable to 100K. MailDrop allows you to automatically control third-party traffic and receive and reverse-forward messages.

Bring your system up to speed. Call AEA's Literature Request Line at (800) 432-8873 for more information, or call us direct at (206) 774-5554. Contact your favorite ham radio equipment dealer for the best pricing.



Connect with us

Of lawnmowers, sail boats, and radio equipment

We lead off this issue's Tech Notes with a project by Ron Mather, ZL2AXO: "A 230-Volt Generator from Scrap." Ron's generator, with its 230-volt, 50-cycle output lends a "down-under" air to this note. More importantly, the main components for this project are almost universally found taking up valuable space in a diminishing resource—our landfills. Our American readers will, of course, probably opt to use a junker 60-Hz, 115-volts AC induction motor for this project, along with suitable pulley ratios to match the optimum engine rpm to the induction motor's rated speed.

Peter Bertini, K1ZJH
Senior Technical Editor

A 230-Volt Generator from Scrap

Ron Mathers, ZL2AXO
Reprinted with permission from the September 1993 issue of Break-In.

A 230-volt, 50-Hz, 500-watt generator has been constructed primarily from discarded parts which would not be difficult to find for the keen homebrewer.

This generator is large enough to power relatively constant loads such as lighting, radio receivers, a TV set and, for instance, a 20-watt transceiver. However, it is not capable of supplying a 100-watt SSB/CW set, as the rapid fluctuations of load which the transceiver presents result in unacceptable swings in the generator terminal voltage. As well, the capacity is insufficient to run a refrigerator or an electric chain saw, though it will drive a 10-mm electric drill without problems.

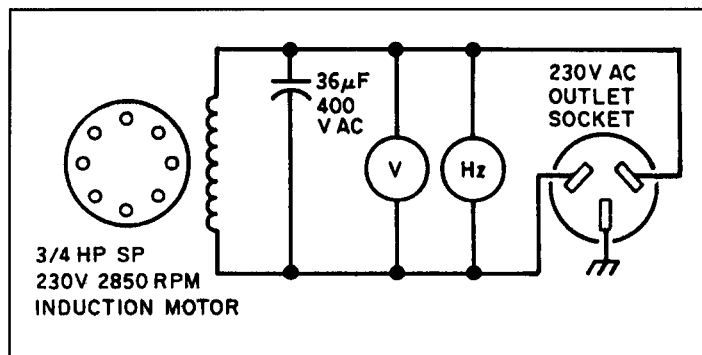


Figure 1. The induction generator.

A 3 HP lawnmower motor was brought out of retirement to play the part of the prime mover. This was coupled by a belt drive to a 3/4 HP single-phase induction motor used as an induction generator. The 3/4 HP motor was an old 2850 rpm pump motor salvaged from the local rubbish tip. Both bearings in the motor were renewed as it was found one tended to run warm. No modifications of any sort were done to the induction motor.

Capacitive excitation is used in the induction generator. Referring to **Figure 1** it can be seen that the connections are very simple indeed. It was found that a capacitance of 36 µF was a suitable size to give 230 volts, 50 Hz at no load. This was made up of three 12 µF, 400 volts AC condensers. The size of the capacitor required for capacitive excitation is approximately that which gives unity power factor when the motor is driven from the AC mains. Final adjustments to this figure can be made to give an output of 230 volts, 50 Hz at no load.

Changing the size of the capacitor changes the no-load frequency with the output voltage being kept at 230 by adjusting the throttle of the petrol motor.

Induction generators with capacitive excitation rely on the residual magnetism of the rotor to initiate the buildup of magnetic field in a somewhat similar way a DC shunt generator relies on the residual magnetism of its field poles. The magnetic field eventually rises to a value limited by the saturation curve of the machine. In earlier tests using a 1/4 HP induction motor as a generator it was found that if the generator was overloaded or short circuited, the residual magnetism was lost and, consequently, the generator was unable to restart unaided. The residual magnetism could be restored in one of three ways:

1. Connecting the generator to the AC mains and running it as a motor for a short period.
2. Discharging a charged condenser across the generator terminals while the machine is in operation.
3. Momentarily connecting a 6 or 12-volt battery across the generator terminals with the machine at rest.

The third method would probably be the most practical in most circumstances. As it turned out, the 3/4 HP motor gave no problems losing residual magnetism with short circuits or overloading. However, the possibility that a short circuit could result in the loss of residual magnetism must be kept in mind, and a proce-

ture for dealing with it available.

In operation, as load is applied to the generator, the terminal voltage needs to be kept constant by opening the throttle of the petrol motor. This increases the speed and results in an increase in the frequency. The frequency is proportional to the rotor speed minus the slip speed, which at full load is about 150 rpm. With a load of 500 watts, the frequency rises to 56 Hz. This rise in frequency is unlikely to be a problem in normal use apart from electric clocks running fast. To assist in the setting up of the generator, a frequency meter was built up using an old Jonan automobile tachometer driven by a 9-volt transformer.

The speed of the generator at no load is just over 3000 rpm. This needs to increase with load until at 500 watts output an estimated 3500 rpm is reached. On the petrol motor shaft, a pulley of 95 mm (3-3/4 inches) diameter drives a 1/2-inch vee belt to a 76 mm (3-1/2) diameter generator pulley.

The advantages of an induction generator include:

1. Low maintenance—no brushes, commutator, or slip rings to wear.
2. The output voltage is a sine wave.
3. The generator cannot be damaged by a short circuit.

Lights powered by the generator produce a noticeable flicker at a frequency equal to that of the power strokes of the petrol motor. It is caused by the low flywheel mass of the motor. However, it is not a serious problem and did not show up on the TV screen or affect the operation of other appliances.

BIBLIOGRAPHY

J. E. D. Basset and F. M. Potter, "Capacitive Excitation for Induction Generators," *Trans. AIEE*, May 1935, Vol. 4, page 540.

Moving on from lawnmowers to sail boats, Richard Cortis, VK2XRC, tracks down a mysterious electrical problem.

Beware of Dissimilar Metals

Richard Cortis, VK2XRC

Reprinted with permission from the October 1992 issue of Amateur Radio.

Apart from being an amateur radio operator, I occasionally attempt to pass myself off as a yachtsman. I am also the owner of a small sailing boat that's called "Mistress." Over the past year or so, my boat has been suffering from a lot of electrolysis.

Some electrolysis is always expected in boats, and zinc anodes are installed in various locations in an attempt to control the problem. However, the rate of loss of the sacrificial zinc anodes was particularly rapid on *Mistress*. Anodes can normally be expected to last in excess of 12 months. However, mine were lasting only about 6 months, requiring the installation of additional costly anodes and, even more importantly, the slipping of the boat, which is particularly costly. The problem was critical because the boat has an aluminum "sail drive" leg which protrudes through the bottom of the boat and looks somewhat like the bottom end of the leg of an outboard motor. This aluminum leg is particularly susceptible to corrosion when electrolysis is present. Accordingly, urgent action was required.

Possible Causes

All the usual things were investigated first. Stray currents from electric cables laid in the bilge were investigated and no likely cause was visible. A number of cables were replaced as a precaution. However, the electrolysis continued unabated. Further research was undertaken and there were suggestions that the copper based anti-fouling paint on the boat beneath the waterline may have had some effect. However,

CABLE ASSEMBLIES



Soliton/Vector builds flexible and semirigid cable assemblies to meet the most demanding procurement requirements. ■ The combination of MIL spec qualified connectors and over twenty years of cable assembly expertise produces the highest quality product at the lowest possible cost to the customer.

Soliton/Vector
MICROWAVE PRODUCTS, INC.

3301 Electronics Way • West Palm Beach, Florida 33407 Tel: (407) 840-1800 • Fax: (407) 844-8551


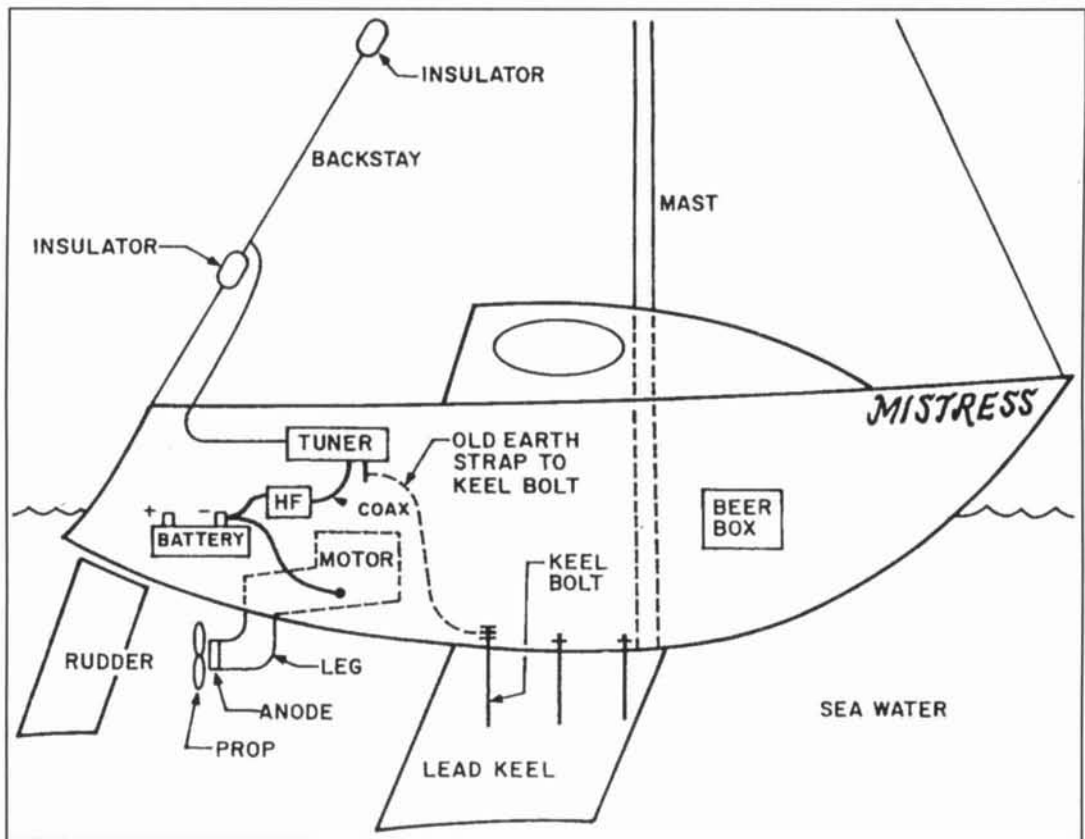


Figure 1. The radio installation setup aboard the *Mistress*.

FILM PRODUCTS

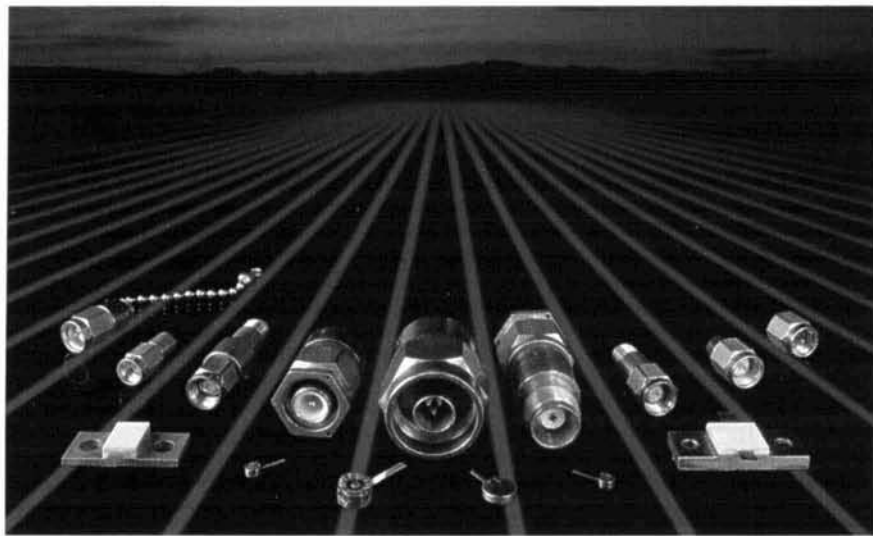

Soliton/Vector manufactures a complete line of custom and standard attenuators and terminations. Coaxial devices are available in connector series from micro-miniature to type N with superior performance to frequencies of up to 40 GHz. Stripline and chip devices are made to handle a wide range of power. S/V is fully qualified under MIL-D-39030 and MIL-A-3933 in N and S versions.

Soliton/Vector
MICROWAVE PRODUCTS, INC.

3301 Electronics Way • West Palm Beach, Florida 33407 Tel: (407) 840-1800 • Fax: (407) 844-8551

the area on the leg and on the bottom of the boat around the leg had been coated with a different anti-fouling, and the general opinion was that this was not affecting the electrolysis. I continued my search.

Recently I had the thought that the electrolysis problem first appeared at around the time the new HF marine radio was installed. **Figure 1** shows the radio installation on the *Mistress*. I commenced further investigation of the problem using my trusty salt-encrusted multimeter. The usual installation for an HF marine radio in a sailing yacht involves the linking of the ground connection from the tuner to a keel bolt using a heavy copper strap. This provides a substantial and effective connection to earth either by capacitance if the keel is encased in fiber glass, or by direct connection if not encased. During my investigation, the diver who cleans the marine growth from the bottom of the boat from time to time advised me that large areas of anti-fouling paint had become detached from the side of the lead keel. As this area had been carefully prepared and primed prior to the last anti-fouling, my suspicions were raised.

High Voltage Keel?

My investigation started at the accessible end of the earth strap between the tuner and the

keel. The earth strap was detached from the ground connection of the tuner and I used the multimeter to measure the voltage between the earth strap and the tuner. Initially, I set the multimeter to the lowest DC voltage setting, 0.25 volts, in order to get a meaningful reading. To my surprise, the needle on the meter swung across full scale. The next scale was selected and a reading in excess of 0.5 volts was indicated. I cannot give a more accurate reading than that as the multimeter is a cheap but robust item which lives on the boat and, because of salt spray and rough service, requires replacement quite regularly. Accordingly, I cannot afford a more sophisticated device. However, I find this meter provides a satisfactory level of service between replacements.

Having discovered this large potential difference, I then switched the meter from the voltage setting to the current setting, first selecting the 50-mA range. Again, the needle swung to full-scale deflection, and a higher range was selected. It appears that a DC current in the order of 250 mA was flowing between the ground connection of the tuner and the keel. This initiated further investigation and it was found that the negative connection on the battery was continuous through the HF radio and onto the outer braid of the antenna connection on the back panel. I also discovered the tuner was continuous from the outer braid connection of the coax from the HF through to the ground connection on the back of the tuner. The negative on the battery is connected by a heavy starter cable to the engine block, which is bolted to the gearbox, which is in turn bolted to the engine leg, which protrudes through the bottom of the boat into the sea water. I will not go into the details of the sealing of this engine leg through the bottom of the boat but, suffice to say it is durable and very flexible. The zinc anode is attached to the engine leg near the propeller.

Connections

So now we have it. The zinc anode is connected to the aluminum engine leg, which is connected to the gearbox, which is connected to the engine, which is connected to the negative of the battery, which is connected to the HF, which is connected to the tuner, which is connected to the earth strap, which is connected to the keel bolt, which is connected to the lead keel. And there we have it, a zinc anode at one end of a piece of wire connected to a lead cathode at the other end of the piece of wire. So why didn't I see it earlier? Well, thereby hangs a tale. The original HF radio installation in the boat had a different tuner which contained a capacitor in the ground connection. In the earlier radio, the negative from the battery was iso-

lated from the ground connection by this capacitor, which effectively blocked any DC current. So there was no electrolysis problem.

Now, having found the source of the problem, how do I remove the electrolysis? Happily, the solution was fairly simple and, perhaps, somewhat obvious. As the metal engine leg is of quite substantial dimensions beneath the water line, it was tried as a dyna-plate and proved to be generally satisfactory. No serious degradation in the level of the HF signal was detected. Accordingly, I made a more permanent connection between the ground connection of the HF tuner and the engine block. The connection between the tuner and the keel bolt was disconnected and removed.

Messages

There are a number of messages to amateurs and yachtsmen in this problem I have suffered. Firstly, one must never assume that items of equipment which look similar and provide the same function are actually constructed in a similar manner. The second and most important moral is that one must always avoid connections between dissimilar metals where any form

(Continued on page 104)

RF CONNECTORS



Soliton/Vector is an industry leader with over twenty years of proven reliability in precision components for major aerospace and defense programs. We have unlimited capability to provide custom and standard coaxial connectors and are fully qualified under MIL-C-39012, MIL-A-55339, MIL-C-83517, and DESC products. Whatever your need, Soliton/Vector can perform.

Soliton/Vector
MICROWAVE PRODUCTS, INC.

3301 Electronics Way • West Palm Beach, Florida 33407 Tel: (407) 840-1800 • Fax: (407) 844-8551

When we talked to technicians about servicing radios, they told us they were too busy to talk.

Now the new HP 8920A RF Communications Test Set solves test problems in less time, so you have more.

- Easy-to-use front panel
- Optional full-feature spectrum analyzer
- Rugged portable package
- Built-in computer with optional software for FM, cellular mobile and base station testing.
- Price \$13,800



Keeping you ahead in communications.

For more information call: **1-800-344-3802** and ask for Charlie or Ken.



1994 Equipment Buyers Guide



There's Nothing Else Like it . . . And It's Here Today!!

The New CQ 1994 Equipment Buyer's Guide



Completely updated, the CQ 1994 *Equipment Buyer's Guide* has once again defined what a Ham Radio reference guide should be. This all-new edition is loaded with photos, product descriptions and specs on practically every piece of amateur equipment and accessory on your "wish list." And the Guide's listing of manufacturers and dealers is the only one of its kind. It's the best place to find out who makes and sells the latest in amateur products.

And, There's More in This Issue!

CQ continues its long-standing Buyer's Guide tradition of providing practical feature articles for almost every area of amateur interest. Written by some of our hobby's leading experts, such as Lew McCoy, W1ICP, Buck Rogers, K4ABT, Fred Maia, W5YI, Gordon West, WB6NOA, and John Dorr, K1AR, you'll be sure to learn valuable information from these articles. Enjoy all the insightful information on packet radio, operating amateur satellites, contesting, improving your morse code skills, the many facets of radio for the new ham, and an overview of this year's "milestones" in our hobby. Whether

you're a newcomer or have been a ham for 50 years, this is a line-up you won't want to miss. And, it's all for the low, low price of only \$4.95.

You'll want to keep this issue handy for day-to-day reference.

The CQ 1994 *Equipment Buyer's Guide*—there's simply nothing else like it. Order your copy today!



For Fastest Service, Order Toll Free **(800) 853-9797**

Or Fax 516-681-2926, CQ Communications, 76 North Broadway, Hicksville, New York 11801 Also available through your local dealer!



ELIMINATES SEARCHING, SCANNING, TUNING INTERCEPTOR™

INTERCEPT, DETECT & CAPTURE
Near Field Transmissions with
Optoelectronics' New
INTERCEPTOR™



MADE IN THE U.S.A.

NEW TECHNOLOGY

- Follows & Locks on even when frequency changes.
- Intercepts ALL FM Two-Way Transmissions without gaps in coverage.
- Does Not have to tune through RF Spectrum to find signals.

FCC Classified as Communication Test Instrument for:

- Deviation, FM, FMN
- Relative Signal Strength
- Signaling Tones (CTCSS)
- Modulation Monitor
- Great for testing VHF, UHF & Cellular transmitters

A New Dimension in Recreational
Monitoring – Intercept the Two-Way
Communication that Surrounds You.

Increase Your RF Security.



Hand Held/Shirt Pocket Size

Interceptor™ R10 FM Communications
Interceptor (Includes NiCads, AC/Charger
Adapter, Antenna, Earphone)

Special
Price
\$299

OPTIONS

Headphones (Lightweight personal headphones).....	\$ 15.
Antenna Pak 2 (Five assorted rubber duck antennas – save \$32.).....	\$ 99.
TC200 Tone Counter (CTCSS signalling tones).....	\$ 179.
APS-104 (Extends RF detection distance 10x).....	\$ 995.
CF800 Cellular Band Pass Filter/Amplifier.....	\$ 149.

OPTOELECTRONICS

FACTORY DIRECT ORDER LINE **1-800-327-5912**

305-771-2050 • FAX 305-771-2052 • 5821 NE 14th Ave., Ft. Lauderdale, FL 33334
5% Ship/Handling (Max\$10.) U.S. & Canada. 15% outside continental U.S. Visa & Master Card accepted

R-2600

Bob Wendt of Canyon State Communications

"We take it to the mountain."




"We bought our Motorola R-2600s for features, ease-of-use, and quality. As an independent two-way service business we are always looking for equipment that will help us get the job done right. Computerized, digital accuracy, with an analog feel. Dependable on the job. I particularly like its software upgrades. Our regular use of the R-2600 is on the bench, but when necessary (just about every day) we take it to the mountain."



Bob Wendt

 *Bob Wendt, Manager
Phoenix Technical Operations
Canyon State Communications*



For more information call 1-800-235-9590



MOTOROLA
Test Equipment CBU

Craig D. "Ghee" Fry, WL7C
1308 Shallow Ford Road
Herndon, Virginia 22070
AND


Robert J. Yowell, KC5BRG
14614 Laurel Shadows Court
Houston, Texas 77062

HF RADIO ON MARS

The solution to a difficult communications problem?

Sometime early in the next century, people will travel to Mars. They'll set up base camps and roam across the landscape to explore a new world. The success of their activities will depend upon how free they are to move about on the surface. Astronauts will need an adequate supply of air, water, and food to travel long distances, and they will need to communicate with their base stations.

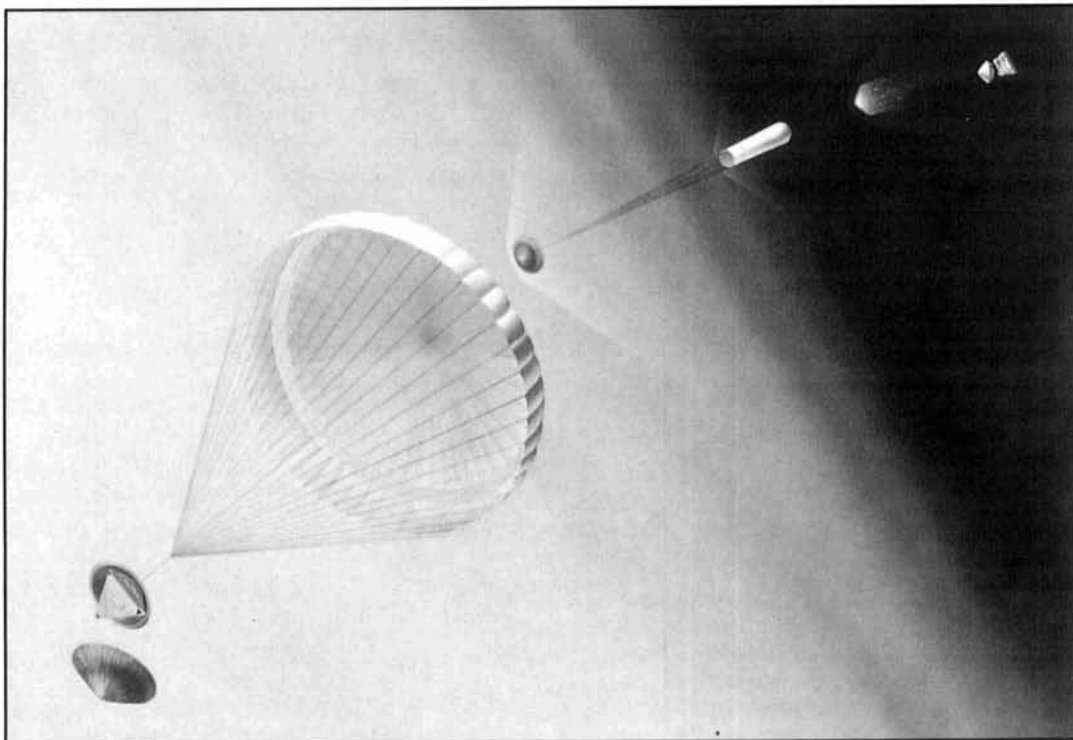Mission planners will have to tackle a difficult communications problem: how do you ensure the astronauts will be able to talk to each other over wide distances, say hundreds or thousands of miles? The typical UHF radio system used by NASA allows line-of-sight communication. Once beyond the horizon, the signal is lost. The visible horizon for a person standing on Earth is about 20 miles, but on



#	Site	Latitude	Longitude	Elevation (km)
1	Valles Marineris	-6.00	58.00	3.50
2	Valles Marineris	-5.00	54.00	3.50
3	Chryse Plan. VL-1	23.00	48.00	-2.20
4	Olympus Mons	13.00	130.00	2.00
5	Valles Marineris	-2.00	54.00	3.50
6	Hadriaca Patera	-32.00	268.00	2.00
7	NW Hellas	-40.00	310.00	-2.00
8	Argyre Planitia	-37.00	44.00	3.50
9	South Pole	-86.00	315.00	4.00
10	Sirenum Terra	-45.00	185.00	4.20
11	Northern Plains	60.00	50.00	-2.70
12	Gusev Crater	-15.00	185.00	0.50
13	Syrtis Major	5.00	295.00	3.50
14	North Arabia	38.00	309.00	2.20
15	North Pole	82.00	55.00	0.00
16	Chasma Borealis	-66.00	66.00	2.50

Table 1. Candidate MESUR observation sites. Latitudes are in degrees North, longitudes are in degrees East, and elevations are in kilometers.

Mars it's about half that far. Radio repeater stations could be set up on the surface to extend the communication range, or orbiting relay satellites might receive the weak signals from the surface and retransmit them over the horizon. A third method of communicating would be to use Earth stations to relay signals between Martian explorers. This idea may not be too practical unless the exploring astronauts have lots of transmitting power and tremendous

patience. Depending on how close the two planets are in their orbits, the travel time for a radio signal from Mars to Earth and back ranges from 9 to 40 minutes!

We'd like to suggest that Mars explorers may be able to communicate with each other by bouncing their signals off the Martian ionosphere, a natural "radio mirror." But before people travel to Mars, robots will first make the trip.

Background

Near the end of this decade, NASA and the European Space Agency (ESA) plan to send unmanned spacecraft to Mars. These spacecraft will carry landers, to be deployed as observing stations on the surface. Remote vehicles, or "rovers," and balloons may also be used to study a larger portion of the Martian surface and atmosphere.

NASA's plans call for placing a chain of small stations on Mars, called the Mars Environmental Survey, or MESUR (pronounced "measure"). This program will collect meteorological, seismological, and other surface and atmospheric data.¹ **Table 1** shows the planned locations of the 16 MESUR landers. These sites were selected to provide extended coverage of the Martian globe, and at the same time, allow the study of intriguing geological sites. A precursor mission called MESUR Pathfinder could head for Mars as early as 1996. **Photo A** shows an artist's sketch of the MESUR Pathfinder lander descending to the surface of Mars. Several of the MESUR landers may carry "microrovers," such as Rocky IV shown in **Photo B**. Rocky weighs in at about

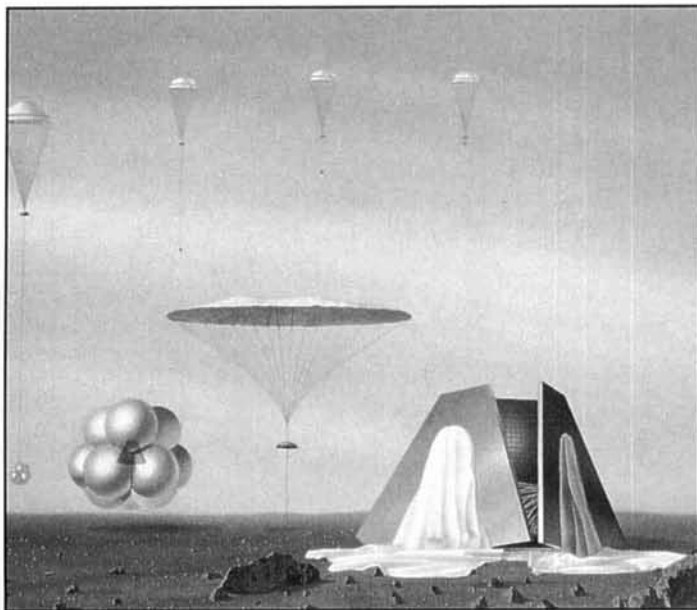


Photo A. NASA plans to send a series of small spacecraft to Mars at the end of this decade. This project, called the Mars Environmental Survey, or MESUR, will place 16 landers and several microrovers on the planet's surface. The details of how MESUR will be linked together to form a network are still being worked out. This artist's conception shows the prototype MESUR Pathfinder descending to the Martian surface.

16 pounds (11 kilograms), and will be smart enough to maneuver on his own. He will carry a visible-light spectrometer and color camera, and tools to chip rocks and scoop soil samples. Rocky will be linked to his lander by low power UHF radio.

The ESA is developing a mission called MARSNET to put three surface stations on Mars at about this same time.² The MARSNET sites form a triangle about 3000 kilometers on a side and will complement the MESUR network. If these missions fly as planned, they'll provide a network to give us a global picture of the Martian environment for the first time.

Both MESUR and MARSNET missions will likely rely upon orbiting relay satellites to send the data collected at the multiple sites back to Earth. It's possible the data may be transmitted directly from each site to Earth instead. But both of these relay concepts present problems. Relay satellites are expensive, require a lot of fuel to send to Mars, and make up a sizable portion of the overall cost of the mission. Direct transmission of data to Earth requires NASA to aim the high-gain antennas of its Deep Space Network (DSN) toward Mars to pull in the weak signals. Considering the large number of sites in the MESUR mission, the requirement to collect data from each site may place heavy scheduling demands upon the DSN.

On the other hand, if the data and telemetry from missions such as MESUR could be forwarded to two or three central sites on the Martian surface, for subsequent retransmission to Earth, a much smaller number of Earth stations would be needed, and would reduce the overall cost of the communication portion of the mission budget. This is where the Martian ionosphere comes in. At the Case for Mars conference in Boulder, Colorado this in June 1993, we proposed using ionospheric refraction for over-the-horizon communication on Mars.³ Here, we look at the feasibility of using short-wave (or HF—high frequency) radio to connect a chain of remote sites on Mars for the relay of collected data. We use typical observed characteristics of the Martian ionosphere and the MESUR site locations for illustration purposes. We'll keep in mind that current HF data communications technology won't support the total data rates required by the MESUR mission—10 MBit per day from 8 sites, and 1 MBit per day from the remaining sites.

Over-the-horizon propagation

First, consider radio propagation here on Earth. People have been using short-wave radio to communicate for over 90 years. An HF radio wave transmitted upward from the surface is refracted back toward the Earth as it travels



Photo B. The MESUR Pathfinder lander and its micro-rover, Rocky IV, on the Martian surface. Room for an HF mobile antenna?

through the ionosphere. The radio wave may eventually travel downward to a distant point on the ground, several hundreds or thousands of kilometers from the transmitter. This mechanism provides a fairly reliable means of communicating. The radio wave may also be reflected off the ground at the distant point and back into the ionosphere to be refracted again. In this way, around-the-world communication occurs via "multi-hop" propagation.

Even with the advent of satellites, short-wave radio continues to play a major role in long distance communication on Earth. This is due to short-wave radio's low equipment costs and fairly consistent performance, at least at low bandwidths (several kHz). Even with low power transmitters and simple antennas, communication usually occurs during part of each day, with the right choice of frequency. Often times, the power needed for good communication ranges down to the 1-watt level.⁴ Also, new technologies are pushing usable bandwidths higher and higher.

It seems reasonable to suspect that the same HF radio propagation might occur in any planetary ionosphere, as long as the electron density is sufficient to refract the radio wave back to the surface, and attenuation due to absorption isn't too great. Early space probes discovered Mars has an ionosphere, with electron densities

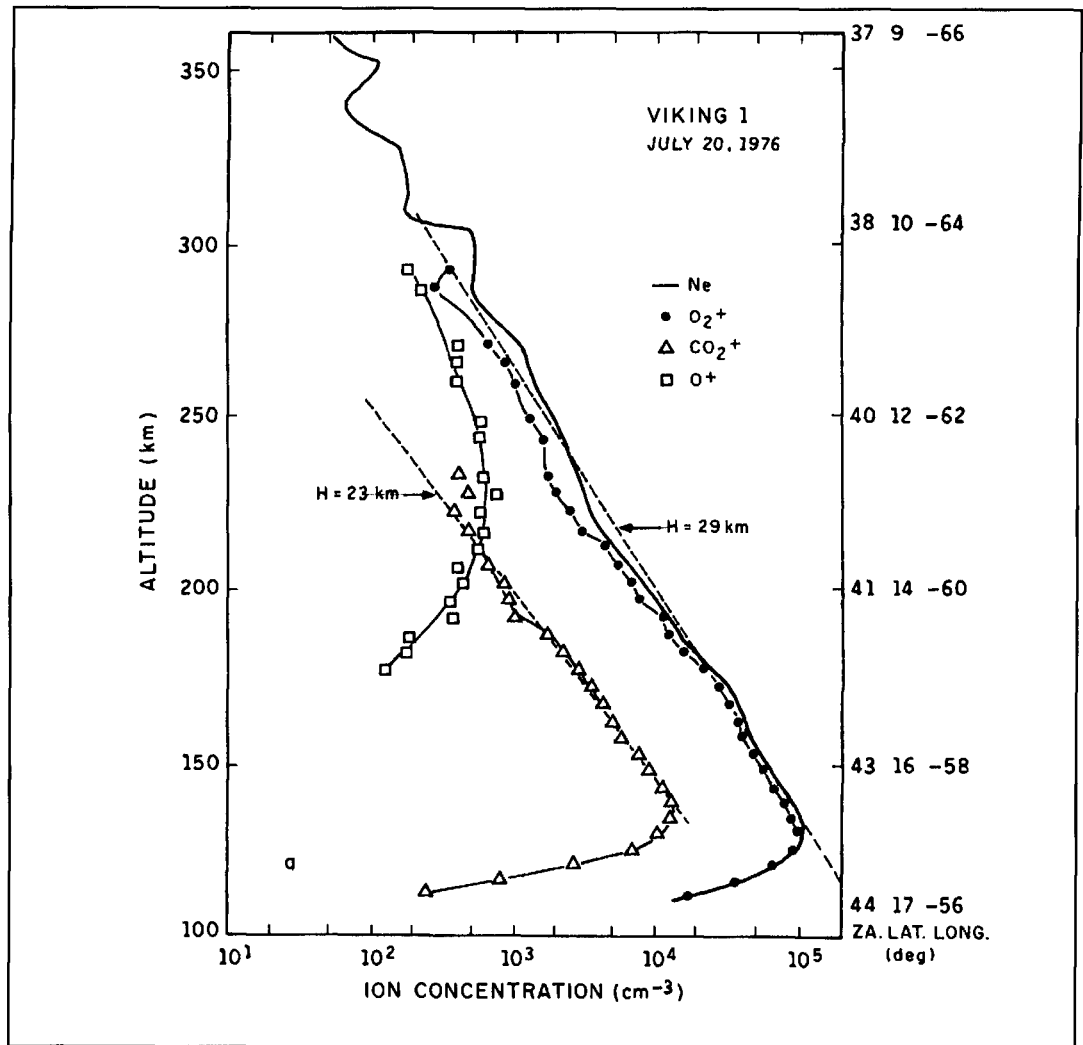


Figure 1. Observations of ion concentrations in the Martian ionosphere during the Viking I lander descent. The solar zenith angle, labeled ZA, ranges from 37 degrees to 44 degrees in this data set. This figure is from Hanson et al.⁵

similar to Earth's ionosphere. This leads us to suspect over-the-horizon communication should be possible on Mars.

The Martian ionosphere

Let's look at the properties of the Martian ionosphere. Peak electron densities are about 1 to $2 \times 10^5 \text{ cm}^{-3}$ during the Martian daytime, and fall to about 10^3 cm^{-3} at night. **Figure 1**, from Hanson et al., shows the data obtained from the Viking 1 lander as it descended to the surface in 1976, during solar minimum.⁵ The neutral Martian atmosphere is mostly CO_2 , and the chief ionized component is O_2^+ , which peaks in density at about 135 kilometers. The electron density equals the sum of the densities of all of the ion species. **Figure 2**, from Zhang et al.,⁶ shows a series of electron density profiles obtained from radio occultation measurements, in this case from the Mariner 9 orbiter, during

the 1971 in the declining phase of the solar activity cycle. The bottomside ionosphere, that portion below the ionized density peak, and of interest to HF communicators, is fairly consistent during the daytime. For an in-depth discussion of our current understanding of the Martian ionosphere, see the review by Kliore⁷ and the papers by Zhang et al.^{6,8}

The Martian ionosphere has an electron density-versus-height profile similar to the so-called Chapman profile, in that it increases steeply in density with an increase in altitude up to the peak density, and falls off more slowly (roughly exponentially) above the peak. Observations from a number of spacecraft have shown the bottomside ionosphere is well established and fairly consistent from observation to observation. Whether the main layer is more like the Earth's E, F1, or F2 layers is still under debate. The Martian ionosphere probably has a D layer, and a thin E layer has been observed, but the details are still undetermined because of

features you want to study, and ray tracing (determining the effects of the ionosphere on the radio wave and its path of travel through this ionosphere). Usual parameters of interest are the ground range, and group and phase delay of the radio wave. In order to study Martian HF propagation, we represented the Martian ionosphere using a “quasi parabolic” ionosphere model as described by Croft and Hoogasian.¹¹ **Figure 3** is from their paper, but modified for the Martian ionosphere. In this model, the electron density profile is defined by the equation:

$$N_e = N_m \left[1 - \left(\frac{r - r_m}{y_m} \right)^2 \left(\frac{r_b}{r} \right)^2 \right]; r_b < r < r_m \left(\frac{r_b}{r_b - y_m} \right) \quad (2)$$

$$N_e = 0 \quad ; \text{ elsewhere}$$

where:

- N_m = peak electron density
- r = distance from the center of Mars
- r_o = radius of Mars
- r_m = height of peak ($=h_m+r_o$)
- y_m = semi-thickness (one half the layer thickness)
- r_b = $r_m - y_m$

Ray tracing is accomplished by integrating the refractive index (related to local plasma density) along the radio ray path, taking the bending due to refraction, and other factors, into account. **Figure 3** shows the ray path geometry used in the calculations. The quasi-parabolic equation has the advantage of yielding an exact solution when integrated. This means that if the quasi-parabolic model is a good representation of the bottomside Martian ionosphere, the ray tracing should be representative of expected behavior on Mars.

We hand-fit quasi-parabolic curves to observed Martian electron density profiles, and calculated single-hop propagation distances, or ground ranges ($=2\theta_t$), along the Martian surface. **Figure 4** shows the daytime and nighttime electron density profiles for the quasi-parabolic model ionosphere. For the daytime conditions, we used a peak electron density of $1.7 \times 10^5 \text{ cm}^{-3}$, a peak height of 135 km, and a semi-thickness parameter of 35 km. For the Martian night, we used a peak density of $1 \times 10^3 \text{ cm}^{-3}$, a height of 150 km, and semi-thickness of 50 km. **Figure 5** shows the ground range of a refracted radio wave for various take-off angles (β_o in **Figure 3**), and includes curves for several frequencies. Note that for a given frequency, two take-off angles can give the same ground range, and a transmitted signal can arrive at a receiver from two different

angles. This means that multipathing can degrade signal quality, just as on Earth. **Figure 6** shows the results of the nighttime calculations. The daytime and nighttime figures are similar, except that the frequencies that produce the same ground ranges for a given take-off angle are lower at night by an order of magnitude.

Our results indicate that with the right choice of transmitting frequency, HF radio can achieve 2000 km ground ranges during both Martian day and night. Referring to **Table 2**, a number of MESUR sites are within the one-hop 2000 km range. For example, data could be relayed from site 9 at the south pole to site 3 at 28 degrees north via sites 16, 8 and either site 1 or 2 in Valles Marineris. In fact, data could be relayed between sites 1, 2, 3, 5, 8, 9 and 16.

Spacecraft observations indicate the height of peak density rises to 150 km in the daytime near the day/night terminator. This implies that the one-hop ground range might be as much as 2200 km when the sun is low on the horizon. Under these conditions both the north and south pole MESUR sites could communicate with the Valles Marineris sites, and in that way, with each other. The network would look as follows:

$$15 \Leftrightarrow 11 \Leftrightarrow 3 \Leftrightarrow (1,2,5) \Leftrightarrow 8 \Leftrightarrow 16 \Leftrightarrow 9$$

$$6 \Leftrightarrow 7$$

$$10 \Leftrightarrow 12$$

$$13 \Leftrightarrow 14$$

Only site 4 at Olympus Mons would be out of range of all other stations.

If two-hop propagation were possible, the ground range would increase to 4000 km. This would allow all sites to be connected by HF radio and communications would be global.

In this study we ignored small scale irregularities in the Martian ionosphere, and the existence of any D or E layers. We assumed the ionosphere was spherically symmetric and didn't have any horizontal gradients. We also didn't include a Martian magnetic field, and didn't consider the effect of absorption on the radio signal. Signal attenuation should be included in future studies. Although it isn't intuitively obvious, signal attenuation has no effect on ground range, only on the signal strength at the receiver end of the path. In other words, the signal will travel wherever the ionosphere lets it, but it may not be heard at the receiver because it is attenuated below the noise floor of the receiver.

HF communications requirements

For HF communication to be practical on Mars, a number of conditions have to be met. We've listed the important ones here.

1. The peak Martian ionospheric electron

densities have to be sufficient to refract the transmitted radio waves back to the surface at the receiver end of the link.

2. The ionosphere must not cause excessive absorption of the radio signal. On Earth, absorption can cause a 0 to 20 dB attenuation of the signal per hop.

3. The one-hop or multi-hop coverage zones have to allow mutual access between relay sites. That is, every site must be within at least one or two hops of another site to allow relay of data.

4. The upper and lower usable frequencies must be far enough apart in the radio spectrum to allow the entire bandwidth of the modulated signal to propagate.

5. Ionospheric irregularities and traveling disturbances must not cause excessive scintillation, dispersion, or multipathing to such an extent that unacceptable distortion or loss of signal occurs.

6. The ionosphere has to be stable enough to support propagation at a particular frequency for the period of time necessary to allow the transfer of data and telemetry at the rates needed.

7. Radio noise generated by equipment or natural sources must be acceptably low at the receiver sites. That is, signal-to-noise ratios at the receiver sites have to be sufficiently large for reliable communications.

8. Ground reflection losses must not be too great if we're relying on multi-hop propagation to bridge the link. On Earth, the losses from ground reflections can range from 0.5 to 3 dB per hop.

9. The benefits of using HF radio have to outweigh the shortfalls. The required hardware and software complexity, mass, and power consumption must be traded off against other communications options.

Actually, in some ways HF propagation might be better on Mars than on Earth. Most of the observations of the Martian ionosphere were obtained during the declining phase of the solar activity cycle, or at solar minimum. During solar maximum, when MESUR flies, the ionosphere should be more dense than the measured values, and the critical frequencies will be higher. This means radio propagation should be even better than at solar minimum. A short-wave DXer's rule of thumb says that the higher the critical frequency, the higher the allowable transmitter frequency and the better the signal quality will be.

The interaction of the solar wind with the Earth's ionosphere deposits large amounts of energy in the ionosphere, and geomagnetic activity often causes large variations in ionospheric conditions. These "ionospheric storms" can degrade HF communications. The Earth has a strong magnetic field that causes birefrin-

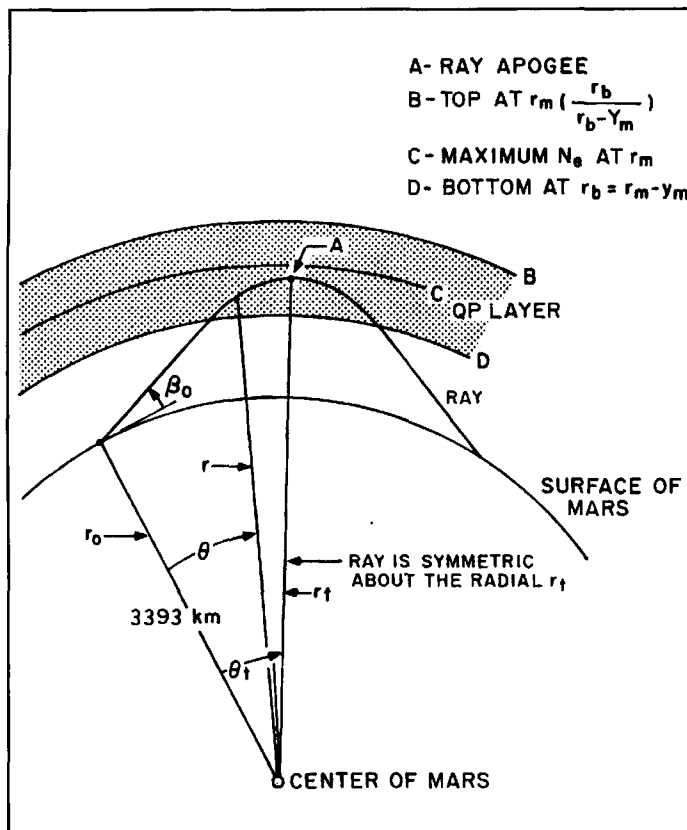


Figure 3. Ray path geometry for the quasi-parabolic Martian ionosphere model, adapted from Croft and Hoogasian's paper.¹¹

gent refraction. This splits radio waves into two components, the ordinary and extraordinary waves, and also complicates terrestrial propagation. The Earth can be a noisy radio environment. Auroral, atmospheric, and equipment-generated sources contribute to the noise. The Earth's HF spectrum is also crowded with many users, and interference can be quite a problem. Ask anyone who's worked a pile-up on 20 meters.

On the other hand, Mars doesn't have a strong magnetic field, and in spite of the top-side ionosphere being exposed directly to the solar wind, the bottomside is fairly stable. The Martian magnetic field is either very weak or nonexistent, so birefringent refraction will be much smaller than on Earth. There are some potential radio noise sources on Mars: extraneous emissions from electronic equipment onboard the landers or rovers, and electrostatic discharge due to wind-driven dust or ice. Noise sources external to the planet, such as solar and galactic radio emissions shouldn't be a problem. However, it's possible that galactic radio noise might pass through the nighttime ionosphere at a low angle and pass over the horizon and be refracted at the bottom of the dayside ionosphere. This could contribute to the received noise at a sunlit site.

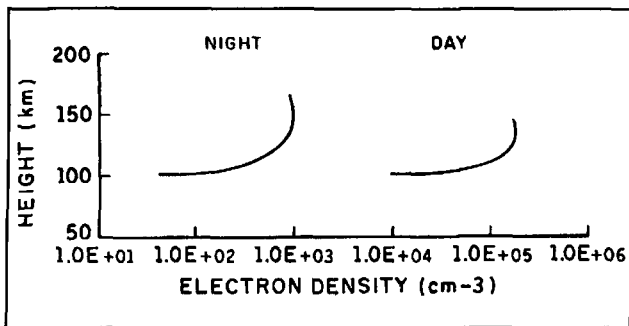


Figure 4. Electron density profile for the quasi-parabolic ionosphere model, with daytime parameters of $N_m = 1.7 \times 10^5 \text{ cm}^{-3}$, $y_m = 35 \text{ km}$, and $h_m = 135 \text{ km}$, and nighttime parameters of $N_m = 1 \times 10^3 \text{ cm}^{-3}$, $y_m = 50 \text{ km}$, and $h_m = 150 \text{ km}$.

Future studies

What kinds of studies would be useful to determine the feasibility of using HF radio as a communications mode on Mars? There are a number of radio experiments that could be included on Mars missions such as MESUR. One extremely low-cost piece of equipment is the relative ionospheric opacity meter, or riometer. This instrument is a self-calibrating HF receiver used to measure absorption by monitoring galactic radio noise that passes through the ionosphere at frequencies above the critical frequency. Absorption is determined from the difference in the received signal and the signal that would have been received if there were no absorption. Active monitoring of the bottomside ionosphere can be accomplished using sounders. A vertical incident sounder, or ionosonde, transmits radio waves over a broad frequency range straight up toward the ionosphere and receives the reflected radio waves.

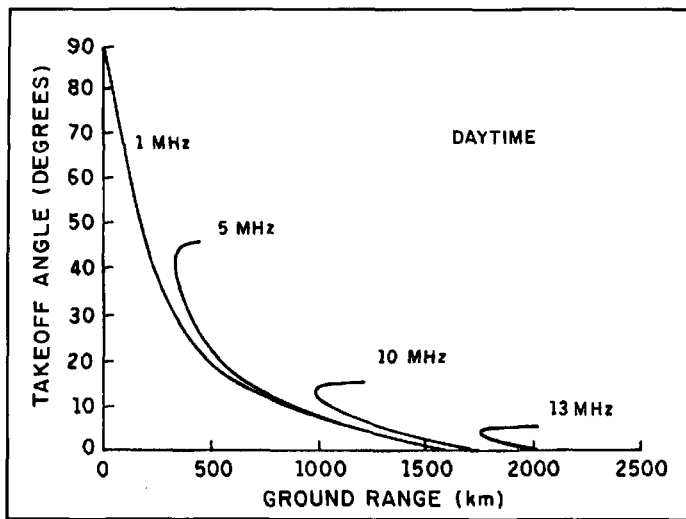


Figure 5. Ground ranges as a function of take off angle (β_0 in Figure 3) for 1, 5, 10, and 13-MHz radio waves, using the daytime electron density profile shown in Figure 4. Peak electron density is 1.7×10^5 at 135 km.

Ionospheric structure can be determined from the returned signal. Oblique incidence sounders such as the chirp sounder are similar to the ionosonde, but use the geometry shown in Figure 3 to probe the ionosphere. Chirp sounders that operate in the 6-watt transmitter power range are available commercially.¹²

Several Earth-based investigations can be conducted before we actually send HF radio experiments to Mars. These include a) HF radio propagation computer modeling and network studies, and b) equivalent terrestrial radio propagation experiments under conditions similar to those expected on Mars. This would give us insight into whether the Martian ionosphere can support reliable long-distance communication.

a. HF propagation simulations. Recent research in the space physics community concerning Mars has focused on several areas: the interaction of the Martian ionosphere with the impinging solar wind; whether Mars has an intrinsic magnetic field or one induced by solar wind interactions; and the structure of the topside ionosphere. However, the bottomside ionosphere is important for HF radio propagation because radio waves are refracted back to the surface only at altitudes below the height of the electron density peak.

An ionospheric model that characterizes the spacecraft measurements and current theoretical understanding of the Martian ionosphere, should be coupled with an accurate radio ray tracing algorithm. Several researchers have developed Martian ionosphere models.^{13,14,15} Realistic studies should use three-dimensional (3-D) ionospheric models, which not only include vertical variations of plasma density, but horizontal changes as well. Zhang et al.,⁶ in their paper on the daytime Martian ionosphere, presented a simple model based upon a modified Chapman layer. This model fit their reanalysis of the Mariner and Viking radio occultation data fairly well. A thorough propagation study should also include a full 3-D numerical or piece-wise analytical ray tracing algorithm. Candidate ray tracing algorithms are described in Jones and Stephenson¹⁶ and Reilly and Strobel.¹⁷

A realistic simulation must account for signal losses due to absorption. Unfortunately, theoretical absorption models based upon collision processes aren't known for accurately predicting observed absorption conditions in the terrestrial ionosphere.¹⁸ Agarwal¹⁹ looked at absorption effects on radio propagation in the Martian ionosphere. He assumed the dominant ion species was O^+ , and looked at radio propagation in the frequency range below 100 kHz or so. We now know that O_2^+ is the main ion species at peak density heights, so his analysis should be reaccomplished, looking at effects of

The Planet Mars QSO Cup

By the end of the 1920s most amateur records had been set, and after the initial smashing of waves upon waves of records, there seemed to be few worlds left to conquer. Technology had evolved in a few short years to the point where arc and spark transmitters were obsolete, and superhet receivers replaced the finicky regenerative in many amateur shacks.

Enter Fred Johnson Elser, W6FB/W7OX and Stanley M. Mathes, ex-7OE and then K1CY, who conceived of the idea of a trophy that would outdistance any short-term advancements in radio communications—the Planet Mars QSO Cup.

In 1928, Elser had just returned home to Manila in the Philippines from a pilgrimage to ARRL headquarters in Newington, Connecticut. While there, he met Percy Maxim, W1AW, ARRL founder and president. During time spent with Maxim, he learned of W1AW's fascination with the planet Mars.

At the same time, Mathes (Lieutenant Commander USN) was stationed in the Philippines, which were then under United States jurisdiction, and also part of the ARRL field organization. After a visit Mathes paid to Elser's shack, the two avid radio hams came up with a unique trophy for the first amateur two-way communication with Maxim's favorite planet, Mars.

After settling on the rules for their award, Elser and Mathes set out to find a suitable trophy. In a store in Baguio, where many examples of Igorot native woodcarving were on display, they found their prize. The trophy is a large curved bowl, standing about 12 inches high. Seated figures on the trophy base, which stands for the planet Earth, signify the people of the Earth. The standing figures holding the bowl, which represents the planet Mars, are amateurs who will bridge the gap between the two planets. The Mars Cup is presently on display at the ARRL headquarters in Newington, Connecticut, where it has resided since 1929.

Two plates are affixed to the base of the cup. One bears the legend "First Amateur Radio Two-Way Communication Earth and Mars,"



The Elser-Mathes cup. This trophy for the first two-way amateur communications between Earth and Mars conceived by Col. Fred Elser, K3AA, and Lt. Comdr. Stanley Mathes, K1CY, while in the Philippine Islands in 1928. Photo courtesy of the Amateur Radio Relay League and *QST* magazine, Newington Connecticut.

with as yet unfilled spaces for the names, calls, and dates for those who would claim the trophy. The other plate simply bears the words [the] "Elser-Mathes Cup." While it was the award creators' fondest wish to see the cup claimed during their lifetime, it seems that was not to be. However, with amateurs routinely active from space, and the surface of the moon long broached, we can only hope that we will all soon see the day when amateurs lay claim to this unique award, and Messrs. Elser and Mathes dream is at last realized.

Peter X, K1ZJH
Senior Technical Editor

Information on the Planet Mars QSO Cup was taken from "That Planet Mars QSO Cup," by Fred Johnson Elser, W6FB/W7OX. The article appeared in QST magazine.

absorption on the HF part of the radio spectrum. Much is yet to be learned about the behavior of the Martian ionosphere, and the roles played by solar wind interactions, ionospheric convection, neutral winds, atmospheric gravity waves, and airborne dust.

b. Equivalent terrestrial HF experiments.

We can run HF radio experiments on Earth to predict the behavior of HF radio propagation

and communication on Mars. These experiments should be conducted at sites and under environmental conditions that match those on Mars as closely as possible. Candidate sites include regions where ground conductivity and dielectric constants are similar to those expected on Mars, and where ionospheric conditions are similar to those observed by previous Mars missions. Antarctica is probably the best match

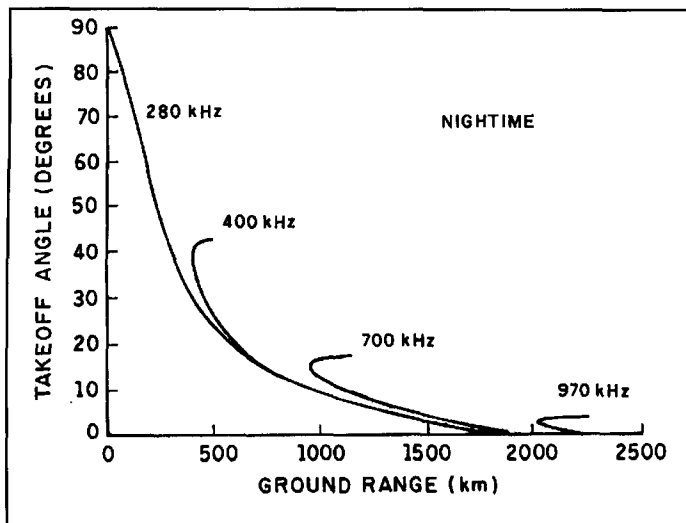


Figure 6. Ground ranges as a function of take-off angle for 280, 400, 700, and 970-kHz radio waves, using the nighttime electron density profile shown in Figure 4. Peak electron density is 1×10^3 at 150 km.

from this perspective. Sites should be selected that support single-hop propagation with geometry similar to those anticipated on Mars. Again, since Mars has half the diameter of the Earth, geometry with 1000 to 4000 km propagation paths on Earth correspond to equivalent Martian separations of 500 to 2000 km.

Recent advances in digital communication capabilities have improved the data rates and performance of HF radio. Adaptive digital modulation techniques have come on the scene, and error-free data transfer rates of 750 Bps are achievable, using modulation techniques such as CLOVER.²⁰ The picture continues to improve. Recently, the Advanced Research Projects Agency issued a Small Business Innovation Research Program Solicitation for the development of an HF network system capable of 64 kbps.²¹ If this research pans out, the new technology would make HF radio a stronger contender for network communications on Mars.

In planetary missions, the average transmitted power must be kept low because electrical power is a limiting factor. This impacts communications because lower power equates to decreased signal quality. However, there is a popular misconception that HF radio requires high power. The low power chirp sounder discussed above supports automatic link establishment and data transfer. Keep in mind that higher power communications systems are still a possibility, as long as the transmission duty cycles can keep power consumption low enough. This should also be investigated further.

Summary and conclusions

This article discussed the concept of using HF

radio for over-the-horizon propagation on Mars. The existence of an ionosphere on Mars implies that HF propagation should be possible. A tentative study using a quasi-parabolic approximation with exact ray tracing shows that one-hop propagation out to 2000 to 2200 km along the Martian surface is possible. We used the MESUR landing site scenario to look at the possibility of conducting radio science experiments on Mars and the possibility of establishing an HF network on the Martian surface. Approximately one-half of the MESUR landers could be connected via HF radio during at least part of the day in the one-hop case. All the landers could communicate if two-hop propagation occurred. Data could then be relayed from remote sites to two or three Earth-link stations. This would reduce or eliminate the need for orbiting relay satellites or the direct transmission of data back to Earth from each site.

The tentative results presented in this paper, using the MESUR scenario of 16 landers, are encouraging. For HF propagation to be practical for network communication on the Martian surface, it must be competitive with other options, such as the option to use relay satellites, or to beam the data directly from each site to Earth. Further investigations and link margin analyses require 3-D raytracing through realistic ionospheric models. Equivalent terrestrial propagation experiments would be beneficial. The results should be analyzed in terms of the implications for Martian radio science experiments, and in terms of HF radio as a viable communications mode on Mars. These studies will help determine the expected ionospheric circuit characteristics for likely sites.

Although we're proposing a low-tech approach to planetary radio experiments and communications, the idea has never been tested on another planet. NASA certainly wouldn't rely on HF radio for their MESUR surface network backbone, but preliminary studies do suggest that HF radio experiments would be useful additions to the manifest on future planetary missions. These types of experiments can provide valuable information about the Martian ionosphere and about signal propagation characteristics. Researchers have been using HF receivers and low power transmitters to study the Earth's ionosphere for over 75 years. It's time we move this proven technology off planet, and support NASA's new direction to do things cheaper, faster, and better. ■

REFERENCES

1. G.S. Hubbard, "Mars Environmental Survey Concept," *Mars: Past, Present and Future*, edited by E.B. Pritchard, American Institute of Aeronautics and Astronautics, Washington, D.C., 1992, pages 141-152.
2. G.E.N. Seoon, "MARSNET—A Mars Network of Surface Stations," *Mars: Past, Present and Future*, edited by E.B. Pritchard, American Institute of Aeronautics and Astronautics, Washington, D.C., 1992, pages 153-168.
3. C.D. Fry and R. Yowell, "Over-the-Horizon Communications on Mars Via

How Are We Alike?

Just how similar is Mars to Earth? In spite of being half the size and 1.5 times farther from the Sun, *in many ways Mars is remarkably similar to Earth*, as the table below shows. The length of a Martian day and the tilt of Mars' rotational axis are nearly the same as Earth's. This means that Mars has seasons as on Earth, but the Martian seasons last twice as long as ours. The Martian air, mostly composed of CO₂, is too thin to breath but dense enough to allow steep temperature changes to kick up strong winds. These winds create global dust storms which can blot out our view of its surface for months on end.

Mars-Earth Comparison

	Earth	Mars
Average distance from Sun (millions of km)	149.6	227.9
Radius at equator (km)	6378	3393
Surface gravity relative to Earth	1.0	0.4
Average density (gm/cm ³)	5.5	3.9
Number of days in a year	365.26	686.98
Length of day	23H56M	24H37M
Tilt of rotational axis (degrees)	23.4	25.2
Atmospheric composition	N ₂ , O ₂	CO ₂
Atmospheric pressure at surface (millibars)	~1000	~6-8
Number of moons	1	2
Temperatures at the surface (°C)	±40	+20/-100
Ionosphere:		
Peak electron densities (day) (cm ⁻³)	~10 ⁵ -10 ⁶	~10 ⁵
Peak electron densities (night) (cm ⁻³)	~10 ⁵	~10 ³
Height of peak densities (day) (km)	~200-300	~130-150
Height of peak densities (night) (km)	~300-400	~150

HF Radio Propagation." *Case for Mars V*. Boulder, Colorado, June 1993, in press.

4. D. Martin and D. Newkirk, "Transmitter Power: What It Is, What It Does and How to Use It," *QST*, March 1993, pages 28-31.

5. W.B. Hanson, S. Sanatani, and D.R. Zuccaro, "The Martian Ionosphere as Observed by the Viking Retarding Potential Analyzers," *Journal of Geophysical Research*, Vol. 82, 1977, pages 4351-4363.

6. M.H.G. Zhang, J.G. Luhmann, A.J. Kliore, and J. Kim, "A Post-Pioneer Reassessment of the Martian Dayside Ionosphere as Observed by Radio Occultation Methods," *Journal of Geophysical Research*, Vol. 95, 1990, pages 14,829-14,839.

7. A.J. Kliore, "Radio Occultation Observations of the Ionospheres of Mars and Venus," *Venus and Mars: Atmospheres, Ionospheres, and Solar Wind Interactions*. Geophysical Monograph 66. American Geophysical Union, Washington, D.C., 1992, pages 265-276.

8. M.H.G. Zhang, J.G. Luhmann, and A.J. Kliore, "An Observational Study of the Nightside Ionospheres of Mars and Venus with Radio Occultation Methods," *Journal of Geophysical Research*, Vol. 95, 1990, pages 17,095-17,102.

9. K. Davies, *Ionospheric Radio*, Peter Peregrinus Ltd., London, 1990, Chapter 6.

10. *The ARRL Handbook*, 66th Edition, American Radio Relay League, Newington, Connecticut, 1989, Chapter 22.

11. T.A. Croft and H. Hoogasian, "Exact Ray Calculations in a Quasi-Parabolic Ionosphere with no Magnetic Field," *Radio Science*, Vol. 3, 1968, pages 69-84.

12. BR Communications, *Tactical Chirpcomm (R) Model 4280 Transceiver Product Brochure*, 1249 Innsbruck Drive, Sunnyvale, California 94089, 1991.

13. A. Tan and S.T. Wu, "Post-Viking Martian Ionospheric Model," *Acta Astronomica*, Vol. 28, 1978, pages 187-194.

14. H. Shinagawa and T.E. Cravens, "A One-Dimensional Multispecies Magnetohydrodynamic Model of the Dayside Ionosphere of Mars," *Journal of Geophysical Research*, Vol. 94, 1989, pages 6506-6516.

15. T.E. Cravens, "Ionospheric Models for Venus and Mars," *Venus and Mars: Atmospheres, Ionospheres, and Solar Wind Interactions*, Geophysical Monograph 66, American Geophysical Union, Washington, D.C., 1992, pages 277-288.

16. R.M. Jones and J.J. Stephenson, *A Versatile Three-Dimensional Ray Tracing Computer Program for Radio Waves in the Ionosphere*, Office of Telecommunications Report 75-76, Department of Commerce, Washington, D.C., October 1975.

17. M.H. Reilly and E.L. Strobel, "Efficient Ray Tracing Through a Realistic Ionosphere," *Radio Science*, Vol. 23, 1988, pages 247-256.

18. L.F. McNamara, *The Ionosphere: Communications Surveillance, and Direction Finding*, Krieger Publishing Company, Malabar, Florida, 1991.

19. D.C. Agarwal, "Electromagnetic Wave Propagation in the Martian Ionosphere," *Institute of Telecommunications Journal*, Vol. 18, New Delhi, India, January 1972, pages 26-28.

20. G.W. Henry and R.C. Petit, "HF Radio Data Communications: CW to CLOVER," *Communications Quarterly*, Spring 1992, pages 11-24.

21. The Department of Defense, *FY 1994 Small Business Innovation Research (SBIR) Program Solicitation 94.1*, Washington, D.C., September 1993, pages ARPA 14.

PRODUCT INFORMATION

Jan Crystals Announces Publication Of Design Guide And Catalog

A new design guide and catalog of frequency control crystals is now available from Jan Crystals, a manufacturer of custom designed quartz crystal components.

The twelve page publication is oriented to electronics designers, engineers, and manufacturers and includes charts, graphs, formulas, and technical information.

The publication is available, by contacting the Design Engineering Department of Jan Crystals, at 813-936-2397.

A GYRATOR TUNED VLF RECEIVER

*This VLF monitoring receiver uses
a gyrator circuit to eliminate
LC-type tuning*

Previously published articles^{1,2} have described two different types of VLF receivers used to monitor very low frequency stations for sudden ionospheric disturbances. These effects have been discussed in **References 1 and 2**. In the spring 1993 issue of *Communications Quarterly*, Peter Taylor and I described a VLF receiver with three separately tuned states using 88-mH toroid coils and air variable capacitors. This arrangement worked well but was somewhat cumbersome.

After publication of the spring 1993 article, I received a communication from Phillip Eide, KF6ZZ, suggesting a gyrator circuit for tuning that eliminated the LC type of tuning used in the previous receivers. I immediately started to experiment with the gyrator approach. This article is the result of my work with a gyrator tuned VLF receiver.

Note that the gyrator directly replaces the cumbersome toroids and slug-tuned coils used in earlier receiver circuits. The Q of a gyrator greatly exceeds that of the iron/copper induc-

tances. Furthermore, the “L” value is easily changed by a resistance. With this type of circuit, it’s easy to construct a complete SID receiver around a single 89 cent IC package. Another advantage of this new design is that there is only one stage of LC tuned circuit as opposed to several in previous designs.

Gyrator circuits

I’ll make no attempt here to get into gyrator theory. It’s sufficient to say that a gyrator is a simple circuit topology that superbly simulates an inductor. The theory is well covered by Moschytz.³ A basic gyrator is illustrated in **Figure 1**.

The inductance is calculated using the following formula:

$$L = \frac{R1 R3 R5}{R2} \text{ for } R2 = R3 \quad L = R1 R5 C4$$

In this circuit, I have chosen R1, R2, and R3 as 3.3 k. R5 is a series combination of 3.3 k fixed and 10 k variable. With C4 as 0.001 μ F, the inductance range of the gyrator is from 43.9 mH to 10.9 mH depending on the setting of the 10 k pot. This, with a parallel capacitance of 0.002 μ F, provides a tuning range of 17 to 34 kHz, a useful range for our purpose. These values will vary somewhat due to the tolerance of the components.

Following the tuned input circuit is a variable gain stage with a gain up to 40 dB feeding into a precision rectifier with another gain of 40 dB. The final capacitor, C6, provides a long time constant to smooth the trace of the Rustrak

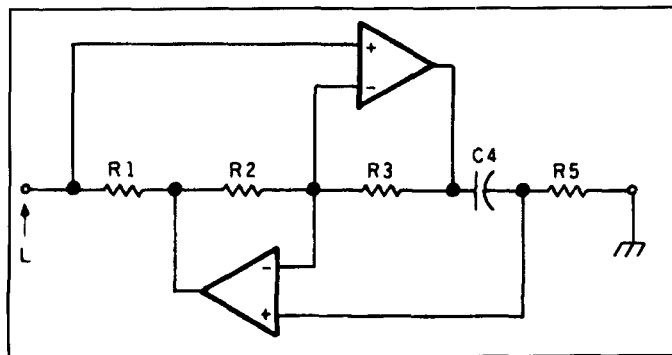


Figure 1. A basic gyrator circuit.

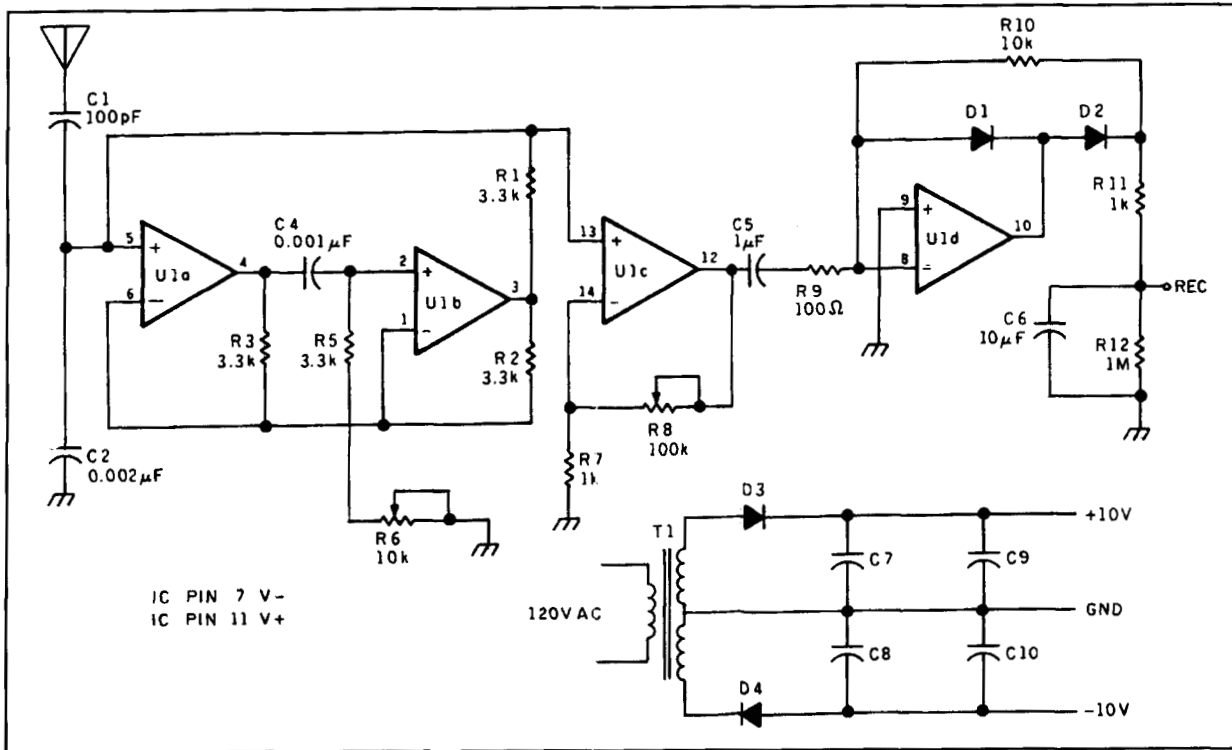


Figure 2. Receiver schematic.

recorder. The schematic is shown in **Figure 2**.

Potentiometer R6 controls the tuning, and overall gain is controlled by R8. A center-tapped 12-volt transformer is used for the bipolar power supply.

Construction

After some experiments with wire-wrapped circuits and a few printed circuit board layouts,

I settled on the arrangement shown in **Figure 3**.

There was some tendency to oscillate in a few of the tests, but I eliminated this problem with bypass capacitors on the power supply leads and shielded leads to the pots. Most of the components are Radio Shack parts. A list is provided with **Figure 4**. I recommend the 4136 op amp as best for this purpose. It's well suited for the gyrator and also the final amplifiers.

The circuit board is mounted on standoffs in


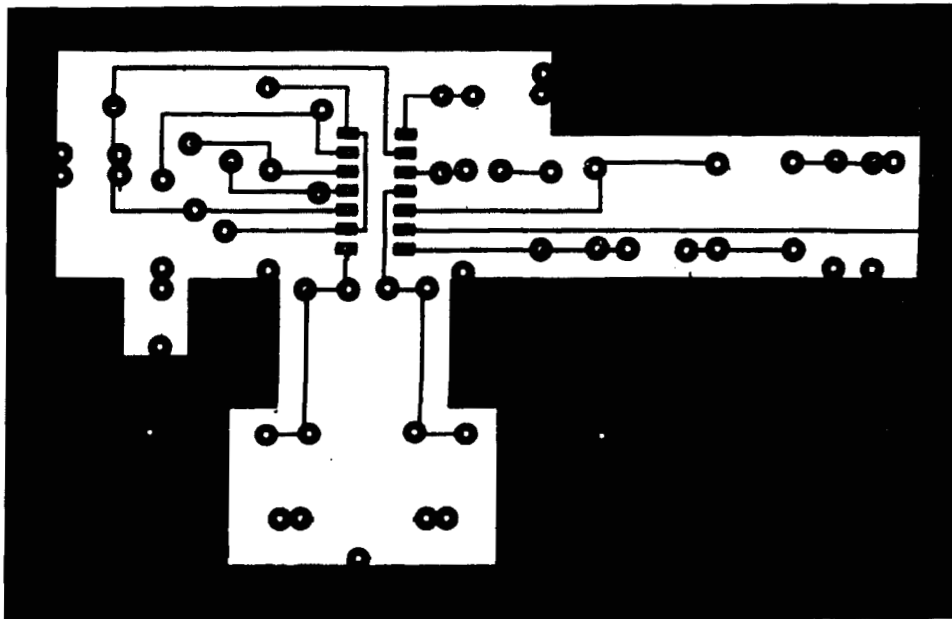


Figure 3. Circuit board layout.

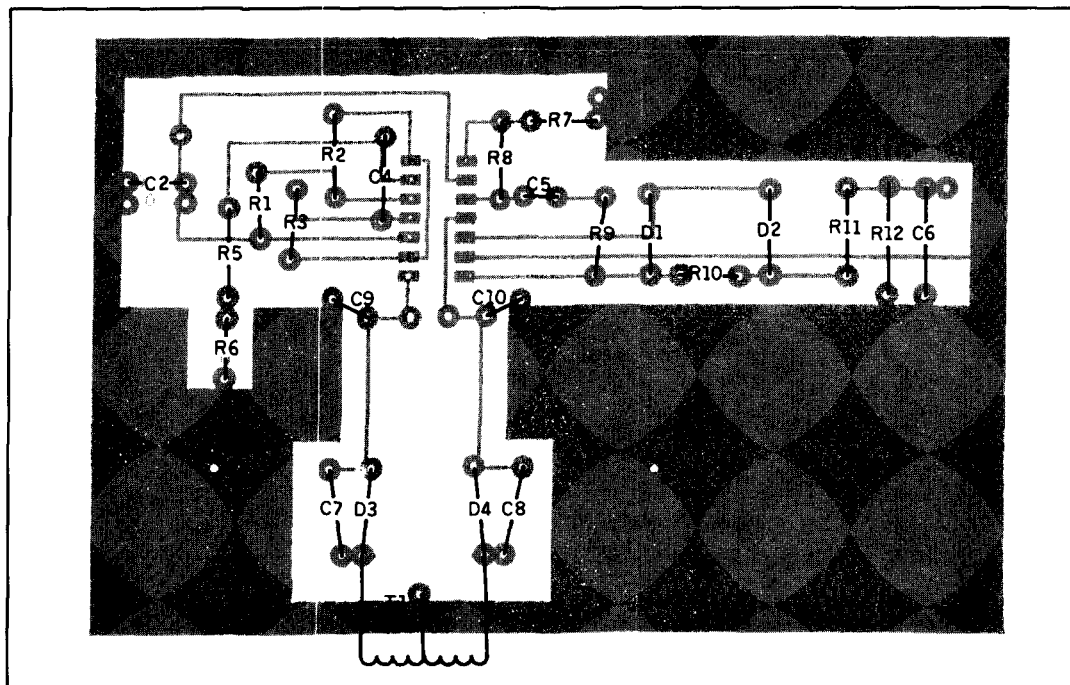

Parts List: VLF Receiver

R1,R2,R3,R5	3.3-k resistors, 1/4 watt	C4	0.001- μ F ceramic capacitor
R7,R11	1-k resistor, 1/4 watt	C5	1- μ F electrolytic capacitor
R9	100-ohm resistor, 1/4 watt	C6	10- μ F electrolytic capacitor
R10	10-k resistor, 1/4 watt	C7,C8	470- μ F electrolytic capacitors
R12	1-meg resistor, 1/4 watt	C9,C10	0.1- μ F ceramic capacitors
R6	10-k linear pot	D1,D2	1N34 diodes
R8	100-k linear pot	D3,D4	1N4001 diodes
C1	100 pF ceramic capacitor	U1	4136 integrated circuit chip
C2	Two parallel 0.001 μ F ceramic capacitors	T1	12-volt CT transformer
			Metal cabinet and miscellaneous hardware.

Figure 4. Parts placement diagram.

a metal box with the potentiometers on the front panel. A BNC connector for the antenna and a 1/8-inch jack for the recorder are mounted on the back panel.

Inasmuch as the receiver was intended to be used for SID monitoring on a continual basis, the output is designed to operate a 100 μ A Rustrak Recorder. The tuning potentiometer is calibrated on the front panel by feeding a signal from a signal generator through a 100-k resistor to the antenna connector.

Summary

I've described my experiments with a somewhat novel method of tuning a VLF receiver. It has performed very well at my location in northern Ohio on 24 kHz and 21.4 kHz signals from NAA and NSS in Annapolis, Maryland and Cutler, Maine, respectively. Various antennas have been described in other articles. I generally use an insulated 24-foot vertical aluminum tube as an antenna. This is connected to the receiver through the center conductor of a coax line. The shield is grounded to an earth

ground. A small diamond shaped loop antenna 14 inches on a side with 100 turns of no. 26 enamelled copper wire has also proved very effective on these stations. The loop was tuned with the proper capacitance in parallel to resonate at each of these frequencies. No ground was needed with the loop.

Acknowledgment

My sincere thanks to Phillip Eide, KF6ZZ, for his basic suggestion of the gyrator and the precision rectifier. Without his encouragement and assistance this project would not have been possible.

Those who wish, may purchase the circuit board for this project from Far Circuits, 18N640 Field Court, Dundee, IL 60118, for \$7 plus \$1 shipping and handling. ■

REFERENCES

1. Peter Taylor and Arthur Stokes, "Recording Solar Flares Indirectly," *Communications Quarterly*, Summer 1991, page 29.
2. Peter Taylor, "The Solar Spectrum," *Communications Quarterly*, Spring 1993, page 51.
3. G.S. Moschytz, *Linear Integrated Networks*, Van Nostrand Reinhold Company, New York, New York, 1975.

ARCS AND SPARKS: PART 1

How Did They Work?

Arc and spark transmitters were exactly contemporary. The techniques for each developed simultaneously, although the origins of spark technology preceded those of the arc by about five years. Even though the arcs got a rather late start, they later surpassed the sparks both in effectiveness and power output. Arcs eventually operated at a power input of over one million watts; two such transmitters (two duplicate converters in one station) were finished and were operated in France, starting in 1920.¹ They ran up until the mid-thirties.

There were always many more spark transmitters operational than arcs, for three main reasons. First, spark transmitters were easier to construct and to operate. Second, sparks could be operated up into the MF range, whereas arcs could not be operated much above 200 kHz, and that was only possible with a special design. The arcs were limited to VLF generally, particularly the high-powered versions—and that precluded their use by hams. The third, and perhaps the most effective reason, was that commercial arc stations in this country were almost entirely manufactured by the Federal Telegraph Company, which possessed the U.S. rights to the patented Poulsen system. Federal made most of the large arc stations in the Western Hemisphere, and also manufactured the most effective (and the most powerful) transmitters in the world. Federal also was “late in the game.” It was perhaps as late as 1910 before the company made much of an impact. A decade later, Federal was out of the arc business; ousted, as all others were, by the imminent appearance of high-vacuum thermionic high-power transmitting tubes.

That the fundamental circuits of arc and spark transmitters are almost exactly alike, belies the fact that their operational characteristics were nearly *diametrically opposite* of each

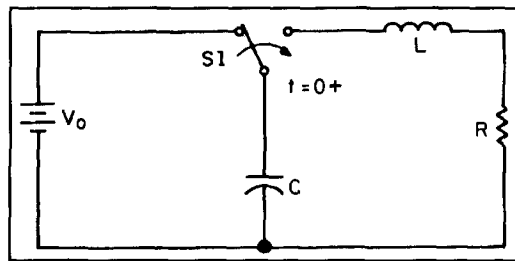


Figure 1. The basic circuit.

other. They didn't look alike, either. Spark transmitters operated from high-voltage, low current supplies, usually AC, and arcs *required* low-voltage high-current DC. The gaps of very large spark transmitters (100+ kW) were always exposed to the atmosphere, and thus were visible and audible: *very* audible. However, the quenched-gap spark transmitters were *relatively* quiet. They were enclosed for a reason other than for noise-reduction. Arc gaps were always shielded—this was necessary for controlling the atmosphere around the arc, which was a hydrogen-rich “fluid” of one kind or another—and they were very quiet. Arcs always required a magnetic field; sparks did not. Sparks could be keyed by interrupting the primary power source; arcs *required an uninterrupted* power source. Spark discharges continued to conduct for many RF cycles; arc gaps were extinguished for a portion of *every* RF cycle. As a matter of fact, there was nothing alike in their operation or appearance except that they both required current to jump across an ionized gap. The following paragraphs describe the main attributes, advantages and disadvantages of each.

Some spark folklore

Heinrich Hertz started it all. The very first

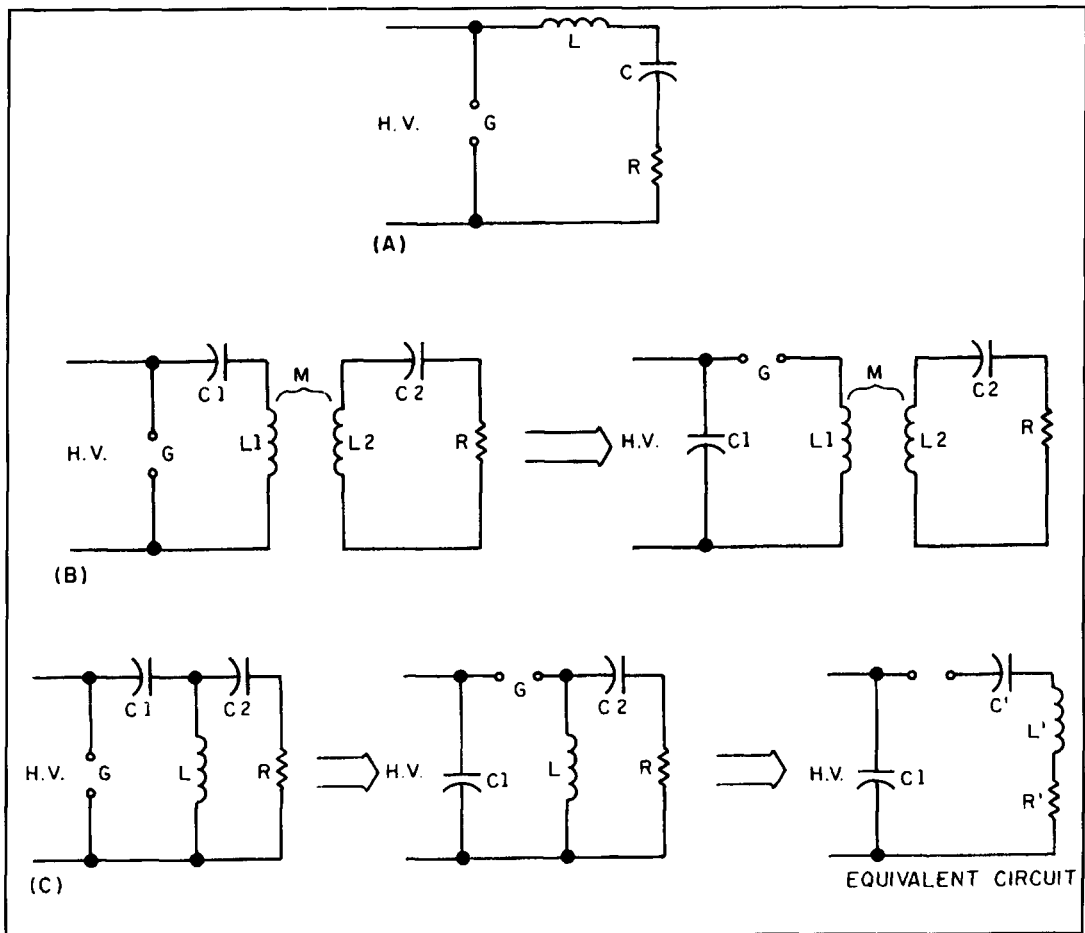


Figure 2. (A) General circuitry for the demonstration of the basic technique. (B) The Braun transmitter. (C) The Wien transmitter.

transmission of electromagnetic waves in what we call the communications band occurred in the latter part of the 19th century. He used the spark, and it produced waves in the HF/VHF part of the spectrum. Hertz was a first-class physicist. His proof of the existence of electromagnetic waves gave confirmation to James Clerk Maxwell's theory, which had been criticized and rejected by his peers for a decade.

There were several experimenters who continued with the art; Popov and Marconi were among them. Gradually, practical techniques were developed. All of them employed the only means of transmission known at the time: *spark generators*. The most effective impetus, of course, was provided by Marconi and his staff in the first trans-Atlantic transmission. The most successful application of spark methods required operation in the LF/VLF bands. The reasons will become obvious later.

The history itself, when not being presented by professional historians, has been massaged over and over by many of us who are really too young to remember; we just pass on the "old wives' tales." Most of the surviving operators

who ran spark transmitters seriously are now easily in their 80s or 90s. Then there are the slightly younger ones (like me) who at one time or another have tried duplicating spark transmitter operation with the most common device available: the Ford Spark Coil. We were aided and abetted by publications (in the '30s, of course), which still carried residual articles and circuits. This was done even though spark transmitters had been unlawful (for hams) since 1926. It didn't bother us, though! We went on about our business of destroying the family receiver's broadcast reception, by connecting a wire "antenna" to one side of the gap, and a ground rod to the other. None of us had any idea what frequency we were on. We didn't even know the theory of operation. We only knew that there was a circuit drawn in a popular publication of some kind, (possibly in one of Hugo Gernsback's magazines) and we duplicated it—"sort of." Looking back on some of those articles, it's apparent that even the *authors* sometimes didn't really understand, either! Fortunately for us, we were fighting a losing battle. Our signals were so wide that the

energy per kHz was minuscule—particularly because the spark coil itself was incapable of more than a few watts.

Could the arrangement described above have been successful? Yes, it could. The hook-up was a simpler version of the Marconi method used for quite a few years. All the absolutely essential parts were there: the spark gap, an antenna, and a ground connection. We just didn't know enough about the procedure to carry it out properly. Had the antenna been properly loaded with an inductance to bring the total resonance into the broadcast band, had the "ground" been composed of a rectangular spider-web-like counterpoise, had the Ford spark-coil been capable of more power, and had the gap been composed of properly adjusted spherical balls, we could have been in a "heap o' trouble." It would have been heard all over town, and over most of the broadcast band.

The professional equipment was quite sophisticated for the time. The mechanical equipment was very complex even by today's standards. It also was effective, and was the *only* practical means of wireless communication for about a decade. Spark transmitters were used on ship-board, in land stations, and even by the military on both sides of the lines in World War I.² Woodrow Wilson's "Fourteen Points"—the terms of German surrender—were transmitted from the United States to Germany (via NSS to POZ, near Berlin) by means of an arc transmitter. POZ, the German receiving station, used the spark. The following paragraphs will explain their operation in considerable detail.

Spark technology

The method of producing an oscillatory wave from a static direct-current source is familiar to all who have studied alternating current circuit analysis.^{3,4} The basic circuit appears in **Figure 1**. With switch S_1 in the left-hand position, the capacitor will charge to the potential, V_0 . If the switch is thrown to the right at $t=0$, it connects the charged capacitor to the series combination of R and L .

If R is too large, the resulting current in the circuit is non-oscillatory, and represents special cases—that of "critically damped" to "over-damped." Below a certain value of R , however, the current wave-shape will follow that of an exponentially decaying sine wave of the form:

$$i(t) = \frac{V_0}{\omega_n L \sqrt{1 - \zeta^2}} e^{-\zeta \omega_n t} \sin(\omega_n \sqrt{1 - \zeta^2} t) \quad (1)$$

where:

ζ = the damping factor (< 1 here) and,

ω_n = the natural resonant frequency of LCR,

which is an *under-damped* case, and it reduces to a general equation:

$$i(t) = a_0 e^{-a_1 t} \sin(a_2 t) \quad (2)$$

That form will appear later in this section. It is the form of one train in a series of such pulses that were transmitted for years by spark transmitters of all makes. Some later modifications of the shape will also be covered; they represent the ultimate development of spark circuitry.

The production of spark transmitter signals followed the principles described above. The main differences between the circuit in **Figure 1** and those of practical transmitters lie in the methods of charging the capacitor and in the magnitudes of the voltages and currents.

The general circuitry for demonstration of the basic technique appears as **Figure 2A**. We start with the power input designated as "H.V." For this explanation, we'll consider it to be direct current. It doesn't make any difference whether it is AC or DC. Both were used. However, the more successful supplies were always AC.

The spark-gap is designated "G." It is "open" (no spark) at the beginning of each pulse. At the time of voltage application, the capacitor "C" is charging, following the voltage of the source. When the charging potential reaches the breakdown voltage of the gap, a spark is produced. Now the gap is conductive with a low intrinsic resistance, and the rest of the circuit is isolated from the source. The circuit GLCR oscillates as in **Figure 1**, decreasing exponentially to a potential too low to sustain the spark in the gap. The energy in the system is dissipated in R .

This circuit was used for several years. The inductance L (**Figure 2A**) included both the inductance of the antenna and whatever loading inductance was necessary for the wavelength in use. C was the capacitance of the antenna itself, and R represented all the losses in the system—including that of the gap, wiring, ground resistance, and the all-important one, *radiation resistance*. The very early Marconi transmitters were of this type.

Power inputs to these early transmitters were limited. The capacitances of even large antennas of the era were usually on the order of 0.01 μF (later antennas were much larger). The maximum charge was thus limited. The actual power input to the system can be computed by:

$$\text{Power Input} = \delta \frac{1}{2} C V^2 \quad (3)$$

where δ is the charging rate (per second), C is

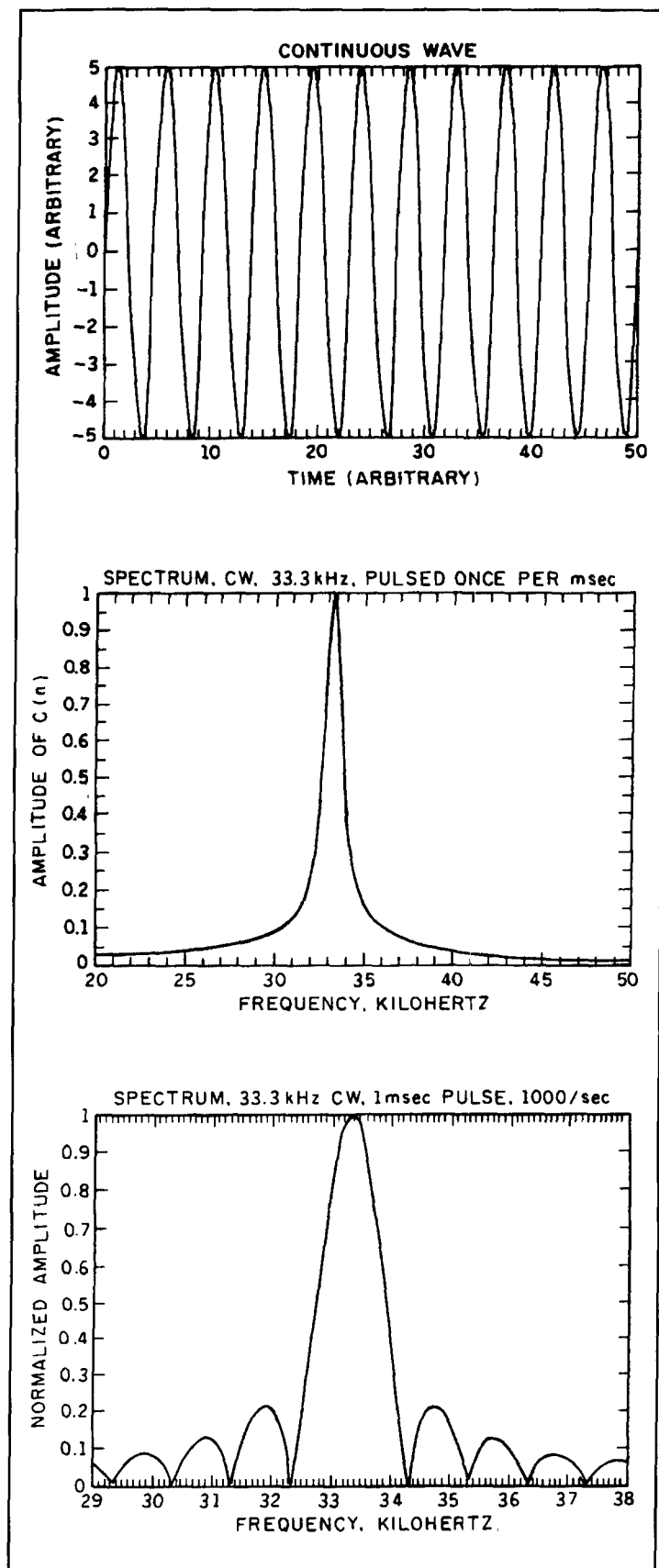


Figure 3. (A) Continuous wave log decrement. (B) CW spectrum, 33.3 kHz, pulsed once per msec. (C) Spectrum, 33.3 kHz 1 msec pulse, 1000/sec.

the capacitance of the antenna in Farads, V is the peak voltage on the capacitor at the instant of gap breakdown, and L and R are as previously defined. It is the small capacitance that limited the power of the early transmitters, even with voltages of 10,000 or more—many, many times more.

The currents in all the circuits of **Figures 1** and **2** decay exponentially, and that created practical problems. If the current doesn't decay, the wave shape is that of a continuous wave, and occupies only one frequency in the spectrum. The shorter the duration, i.e., the higher the damping, the broader the signal. It was recognized early, and the U.S. Department of Commerce (then regulating transmitters) restricted U.S.-licensed transmitters in 1919 to a maximum log decrement of 0.2.

The log decrement (which is related to the damping factor in **Equation 1**) is defined as the natural logarithm of the ratio of any cycle amplitude divided by the amplitude of the next occurring cycle:

$$\text{Log Decrement} = \ln (A_2/A_1) \quad (4)$$

Figures 3, 4, 5, and 6 are waves of several different log-decrements.

Figures 2B and **2C** are the basic circuits of F. Braun (who also invented the Braun Tube, the precursor of the oscilloscope), and Max Wien. The Braun circuit was the more successful; it was patented in 1898.⁴

All the transmitters of the form of **Figure 2A** suffered power limitation because of the relatively low fixed capacitance of the antenna. Voltages as high as 80,000 were applied to those systems; that voltage appeared on all exposed antenna components. It also challenged the insulators. High-voltage RF insulator research and development was necessary because of this problem—which was common to both arcs and sparks.

Braun solved the power limitation problem very neatly. His basic circuit (**Figure 2B**) is the one that nearly all of the subsequent transmitters used—from the lowest-powered ham transmitters to the very large military, governmental, and commercial transmitters. The latter peaked at approximately 350 kW.

There were other advantages in this system; it reduced some harmonic radiation (when properly adjusted; otherwise it could broaden the signal significantly) and further enabled large energy storage in capacitor C_1 . It was critical in adjustment, requiring variable coupling between L_1 and L_2 (a form of what was known as "loose coupling"). Various forms of loose coupling appeared in both transmitters and receivers. The Braun circuit was double-tuned, and could actually produce *two* resonances

simultaneously if mistuned—almost always by overcoupling; hence, various forms of “loose coupling” were developed. Not only did the “double-frequency” reduce the quality of the signal, it was unlawful per U.S. regulations.

M. Wien sought to eliminate the characteristic tuning difficulties in the Braun system by combining the two inductances, L_1 and L_2 , and their mutual inductance into one, while retaining large energy storage. The circuit is shown in **Figure 2C**.

Efficiencies of these transmitters usually were between 60 and 85 percent. Of the power ultimately reaching the antenna circuit, less than a tenth actually was radiated; antenna efficiencies were notoriously poor. They still are. Who has room to lay down more than one hundred radials, each one many kilometers in length? Adequate ground systems were, and are, the most important and limiting factors in the performance of Marconi verticals; particularly VLF Marconis. In general the Wien system was the more efficient, but it suffered a disadvantage because it couldn't divorce the log-decrement of the antenna from that of the storage circuit. Although POZ (a very famous German station) used the Wien system for a while, it reverted to the Braun system until it was shut down after World War I. One of its successors was at Eilwese, which used a Goldschmidt alternator. The Goldschmidt was of the same general power level as the Alexandersons, and was developed to circumvent the Alexanderson-Fessenden patents.

By the time hams were using the Braun circuit, they were under the “200 meters and down” (1,500 kHz and up) dictum. Although the storage capacitance (C_1) enabled much more energy storage than the capacitance of the antenna alone, the power input still followed **Equation 3**. It was difficult, if not impossible, to achieve the one kilowatt maximum allowable input if ordinary 60-Hz line power was used in combination with a single ball-gap or even with the rotary gap. The charging rate δ , had to remain at twice the line frequency (120 Hz). The capacitor could be charged only at that rate.

The circuit was known as the “oscillation circuit”, and the coil in amateur transmitters usually was constructed of quarter-inch copper tubing, and consisted of four or five turns about six or eight inches in diameter. It was a “high-C” combination. The larger was “C,” the smaller “L” had to be—and that meant a correspondingly more difficult energy transfer to the antenna circuit.

The two graphs, **Figures 7 and 8**, were calculated on the bases of the largest practical storage-capacitor (somewhere around 2800 pF for a four-turn coil) and a frequency of 1,500

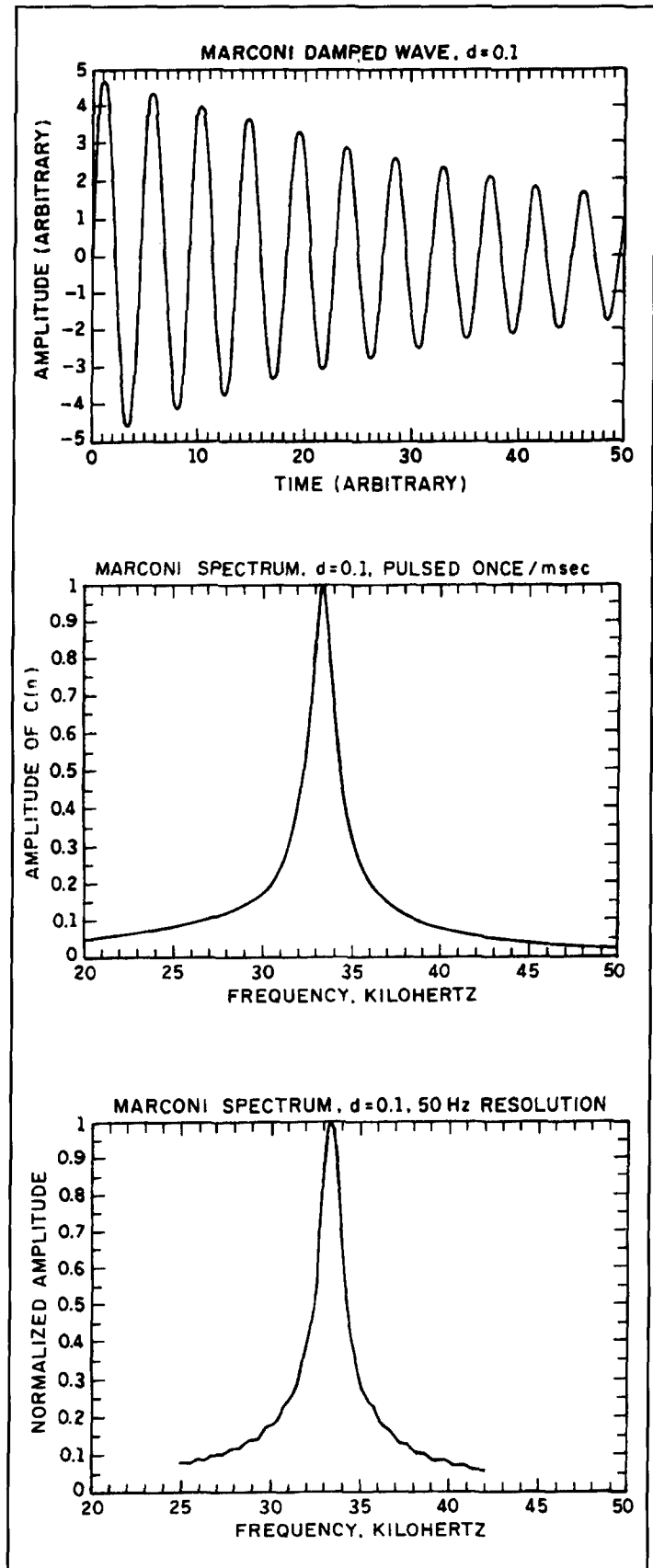


Figure 4. (A) Marconi damped wave, $d = 0.1$. (B) Marconi spectrum, $d = 0.1$, pulsed once/sec. (C) Marconi spectrum, $d = 0.1$, 50-Hz resolution.

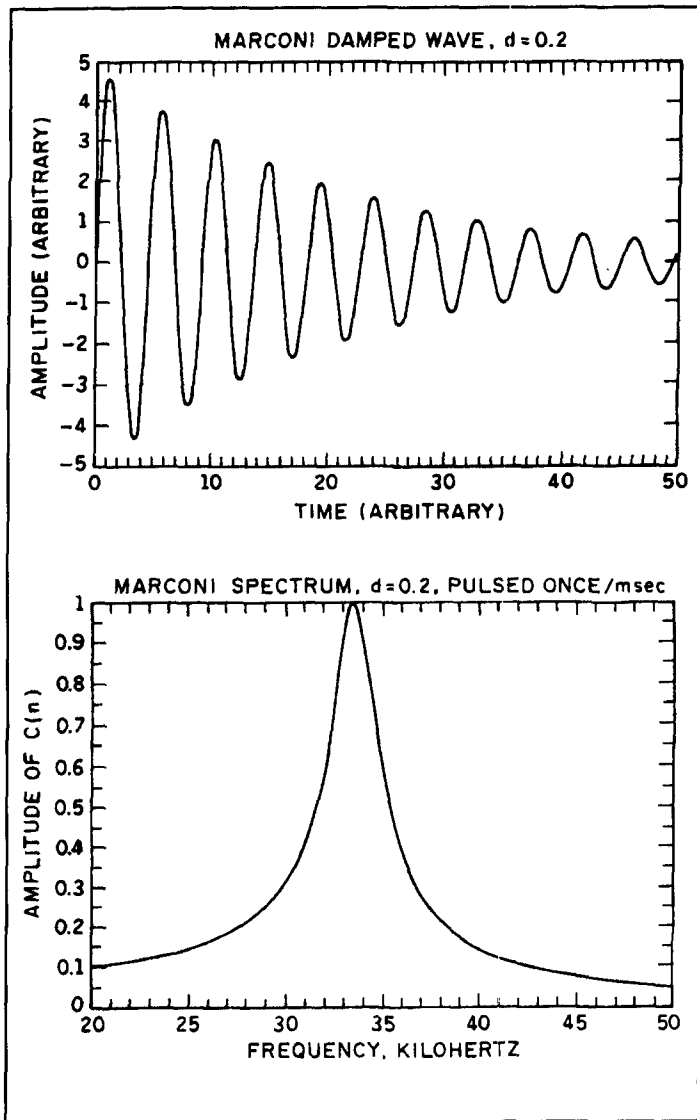


Figure 5. (A) Marconi damped wave, $d = 0.2$. (B) Marconi spectrum, $d = 0.2$, pulsed once/msec.

kHz (200 meters). These were computed for 2,814 pF. The graphs show very well just how difficult it was to achieve the maximum input for amateur transmitters following the forced band-change. It would require approximately 77,000 volts (peak) for a transmitter using 60-Hz line current, and it would require a peak voltage of 27,000 using a synchronous pulse-frequency of 1000/second. Either would be hard to manage in the typical ham's basement or garage. They are hard to manage safely *anywhere*. It would be an unusual ham who could build circuits—and provide insulation—for 27,000-volt systems, and even more unusual for a 77,000-volt transmitter.

That wasn't the end of the effort. There were some hams who reduced the primary inductance to a minimum—and correspondingly increased the capacitance to a maximum. The

practical culmination of this was the construction of *one-turn* primary inductances, and capacitances of about 10,000 pF.

Correspondingly, somewhat lower voltages were required, and some hams were operating this way.

Capacitors in all of the spark transmitters were required to withstand at least 15,000 volts in smaller transmitters, and 80 to 100,000 volts in the largest, while simultaneously containing from 0.1 μF to as much as 1.5 μF capacitance. Remember that the wavelengths usually were *very* long; 12 kilometers was a common wavelength for the very large transmitters, corresponding to a frequency of 25 kHz. They also had to be of high quality, because they were handling large circulating currents.

It would be difficult (at least expensive) even now to produce a single capacitor of 1 μF size at 100,000 volts that would handle several thousand RF amps. On some very large spark transmitters, the initial discharge (first cycle) current was nearly 10,000 amps.

The most common small-transmitter capacitor dielectric was glass. Commercial plate-glass was much used by hams, though other dielectrics were tried—mica being one. Glass was used by many of the commercial-sized units, too. Here, however, the design ranged from actual latter-day Leyden-jar configuration with glass dielectric, to pressurized CO_2 dielectrics in steel pressure-vessels. Both these were used, always in parallel combinations. Oil-immersed glass plate dielectric capacitors were used in latter-day large Marconi transmitters employing the Braun circuit.⁵

Pressurized capacitors can be identified by their flanges and bolts. Internal construction of some of the latter resembled fully-meshed modern-day Jennings vacuum variables. Others were often stacked interleaved parallel plates, insulated from each other and pressurized as were the cylindrical types. High-vacuum techniques were not yet developed to the point necessary for that technology, and techniques that were essential to the soon-to-come high-vacuum thermionic tubes were yet to appear.

It was understood that if the energy per pulse was multiplied by the pulse-rate, higher power would result. It was known also that the ear, as well as the earphones of the day, were most sensitive to frequencies around one kilohertz. Except for an occasional special circumstance (read about station MUU, later) the usual alternator supply frequency was established at 500 Hz, giving the 1-kHz pulse rate. The rotary gap was used in most of these systems, and it was used in *all* of the stations of 100-kW power levels and above.

In those cases where the gap speed was synchronized with the line frequency, a "synchro-

nous gap" was produced. There were hundreds of synchronous ship- and land-based transmitters in use. Most were manufactured by Marconi's companies. Fessenden (and his company NESCO) had several in service, too. The gap rotor was on the generator shaft, assuring synchronism. The note of the signal (actually a sort of "interrupted CW") was therefore one kilohertz, as was δ .

The electric utility system frequency in the United States largely was fixed at 60 Hz. If an amateur wished to use a rotary gap, he was forced to accept either a synchronous pulse-rate of 120 per second (if he were wealthy enough to obtain a synchronous motor) or to use an ordinary motor of relatively high speed. This type of motor invariably produced a "warbling" tone because it would be passing in and out of synchronism continuously. It was a non-synchronous combination. Most hams operated in just this mode.

They also tried to take advantage of increased pulse-rate within the 60-Hz supply restraint. The rationale can be explained partially by **Figure 9**. One cycle of a 60-Hz sinusoid is the solid curve. The hypothetical rotor has ten points, giving a "tooth passage" every 36 degrees in a synchronous sense. They are first labeled A through K, unprimed. K actually represents the "A" of the next cycle. By adding 18 degrees to each point, we have the primed points, A' through J', in which a K' (not shown) would be the A' of the next cycle. The dotted zone is the area in which no spark is possible. The gap is too large, or the voltage too low; either is correct.

No spark is possible at points A, F, and K. However, it is possible at B, C, D, and E, and on the other half-cycle, at G, H, I, and J. The power input for the first case would be four times the energy at the voltage of B, say, plus four times that of point C—all points multiplied by the appropriate δ , of course.

If the phase is shifted just 18 degrees, sparks are possible at all primed points—including two (C' and H') at the highest voltage of the sine. For any other phase-angle, the resultant power input will drift between these values. Either case would theoretically increase the power input over a synchronous pulsing at points C' and H'. And it *did*. Hams were able to achieve the maximum 1-kW input with 60-Hz power. The problem was that the sparks did not occur exactly when they were supposed to, and the voltages did not follow the nice, clean sine wave. In fact, they occurred at considerably lower values than are indicated in **Figure 9**. The increase in power input and output was evident, but the effectiveness of the signal wasn't. It actually decreased.

Hams of the day had a habit of turning the

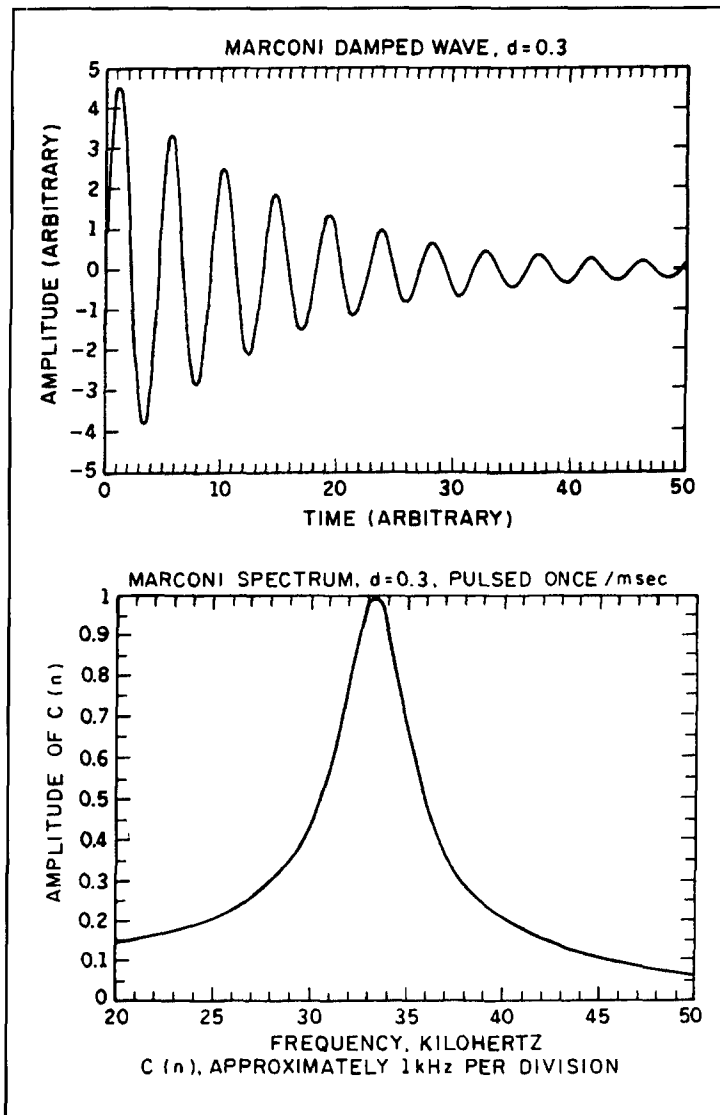


Figure 6. (A) Marconi damped wave, $d = 0.3$. (B) Marconi spectrum, $d = 0.3$, pulsed once/msec.

gap motor off during the "dah-dit-dah" on sign-over, allowing the spark-rate to drift down and through true synchronism at 120 Hz. The signal readability actually increased even though the measured power (real, by the way) was decreasing. What was happening? This question was the subject of at least one *QST* article. The authors' conclusions were essentially correct, but for the wrong reasons.

The transformers in use then would produce many thousands of volts; but a transformer of say, 25,000 volts rms, would deliver only 40 mA at 1 kW! They also possessed many turns of fine wire (necessary for the voltage increase), and much higher insulation requirements. Comparatively large spaces brought about by the insulation requirement also meant decreased flux-linkage. Those transformers suffered from both high ohmic wire resistance and leakage reactance.

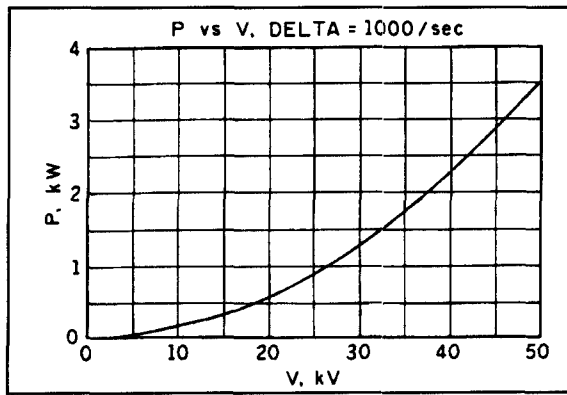


Figure 7. P versus V, delta = 1000/sec.

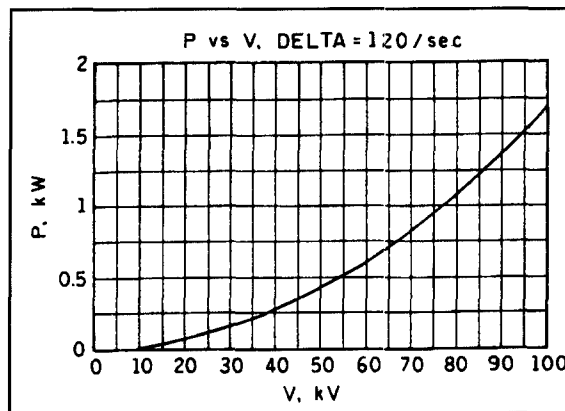


Figure 8. P versus V, delta = 120/sec.

It is not unreasonable to assume that a 10 percent voltage drop occurs in such a transformer when fully loaded by a resistance. One can estimate the combined effects of leakage reactance and resistance (they will appear as a combined resistance) by dividing the voltage change by the current change; $2500 \text{ V}/0.04 \text{ A}$. The resultant resistance, 62,500 ohms, is now the “source resistance” of the transformer. Every pulse in spark transmitters is preceded by a charging cycle. The capacitor must be charged from the source. The voltage on the capacitor follows the usual inverse exponential, $V_c = V_0(1 - e^{-t/\tau})$, where τ is the time-constant, RC , R is the internal dynamic resistance of the transformer, and C is that of the RF primary circuit, in Farads. It is 0.625 millisecond for $C = 10,000 \text{ pF}$ and $R = 62,500 \text{ ohms}$. Referring to **Figure 9**, it is seen that there are only 1.67 ms between pulses. It is also true that three “ τ s” (1.875 ms) are necessary for a capacitor to assume 90 percent of its full charge. In short, the capacitor *never* gets charged. There are enough pulses, though, to achieve the kilowatt average input, but the peak power never reaches the equivalent power of fully-charged capacitors. It is exacerbated by the sinusoidal

shape of the source voltage—or at least it *tries* to be sinusoidal. The only loads those transformers saw were charging surges. They were grossly nonlinear loads. It was difficult duty.

Detectors used in the reception of spark signals were *envelope* detectors. Even regenerative detectors on the verge of oscillation (the most sensitive state) were envelope detectors. They all were sensitive to p.e.p.—*peak envelope power*. Sound familiar? As the spark rate decreased at the signover, more time was available for the capacitor to charge, and its p.e.p. increased. There is a modern lesson here, by the way, for SSB operators infatuated with excessive use of processors. Even product detectors are envelope detectors in the general sense.

Large commercial installations were plagued by the same problems. There were methods of resonating the source (at 1 kHz) simultaneously with the charging voltages. It is an interesting concept, but is not appropriate for systems with 60-Hz supplies. A good description of the principle can be found in **Reference 5**.

The “quenched gap” was devised to prevent “arcing” at the gap. The power sources for transmitters ranged from fractions of kilowatts to hundreds of kilowatts. Once a ball-gap became ionized, it had a tendency to continue conducting long after the oscillating current in the circuit had ceased. Sometimes it did not quench at all. The quenched gap—one of the solutions—was a static device. It was composed of a number of parallel circular plates, each insulated from the next by an annular ring. Eight or ten such plates were common. The overall gap therefore consisted of several shorter ones. One could select just how many stages he desired by tapping onto any particular stage. It had the property of discouraging arcing, but it was limited in its heat-handling capability, so it was used in transmitters of relatively low power. It was quiet in operation, and where there was a choice (switch-selected) mostly in small 2-kW transmitters, like the American Marconi P-4, it was the preferred gap. Quenched gaps were used in some larger transmitters (mostly in Germany) but they were limited in heat-dissipating capability, even with forced-air cooling.

All of the large commercial transmitters used the rotary gap. When the gap is required to pass thousands of amperes at tens of thousands of volts, heat becomes a severe problem. So does noise and (probably) the production of ozone. Rotary gap discharges in the very large commercial transmitters could be heard for miles, and the radio rooms of ship-board transmitters were frequently sound-proofed, particularly on passenger liners.⁶

The motion of the rotor not only quenched the gap, it cooled the rotor points. The stator

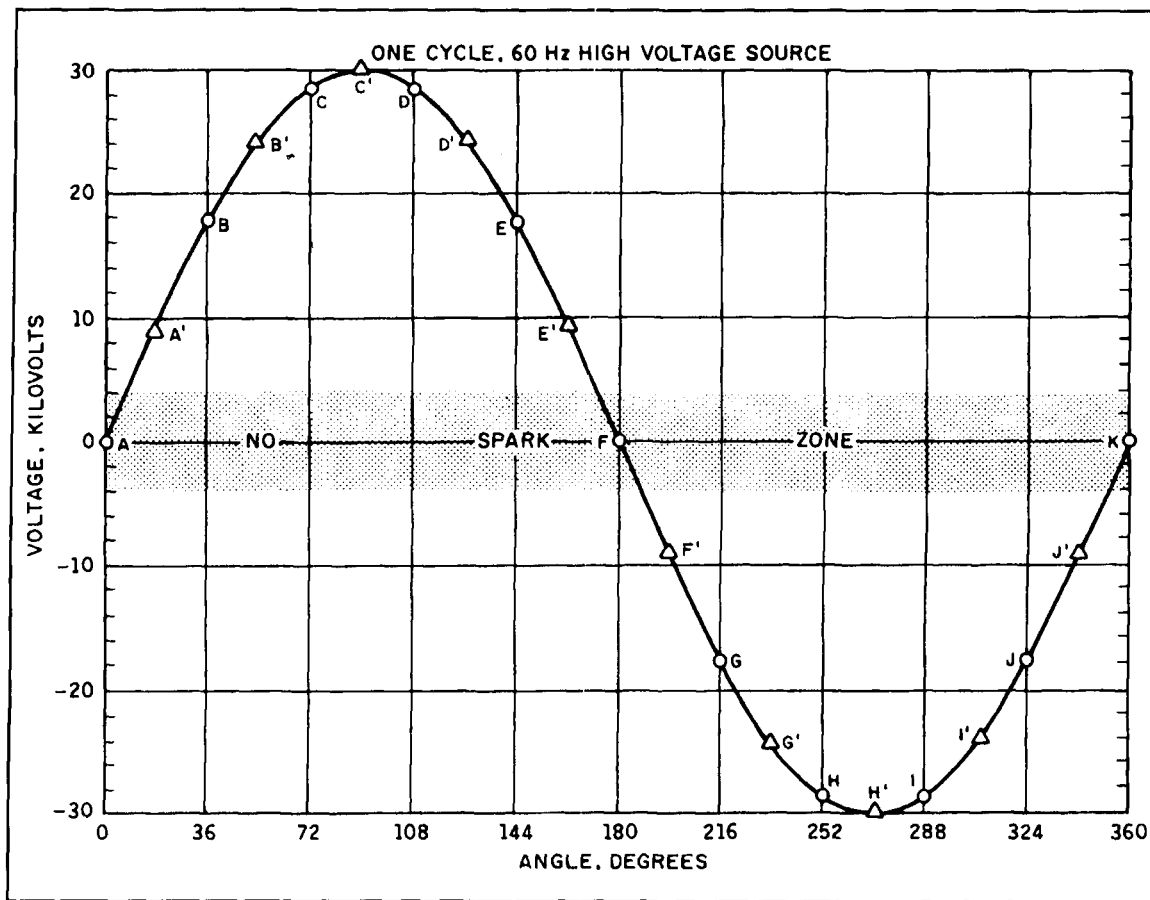


Figure 9. Partial explanation of rationale behind taking advantage of increased pulse-rate within the 60-Hz supply restraint.

points on very large rotaries often were water-cooled; Fessenden used self-contained (and insulated) thermal siphons with small tanks.

Adjustment of the Braun circuit was somewhat tedious. There was a transfer of the energy from the oscillation circuit via the "oscillation transformer"—actually L_1 and L_2 in **Figure 2B**, to the secondary circuit, and the two currents are presented in **Figures 10** and **11**. Note that the antenna current still decays exponentially with the log-decrement of the particular antenna and ground system (beyond $t = 20$) in the figure. The abrupt rise in antenna current (at $t = 0+$) produced by the circuit in **Figure 2A** is missing, and its absence contributes to a narrower signal width.

It was easy to over-couple the Braun "oscillation transformer," and serious degradation of the signal always resulted. It is very easy to see how this happened. All of the total energy per pulse (at $t = 0$) is contained in the primary circuit CGL. That energy is transferred to the secondary system, starting with the first swing of the primary current. If the coupling is too close, the field established by the current in the secondary system is reflected back into the prima-

ry system with enough energy to reignite the spark gap, and the process continues back-and-forth until the remaining energy is too low to reignite the gap.

A simulation of the effect appears as **Figures 12** and **13**. The trick was to adjust the coupling "just so"—far enough apart so that there would not be enough energy fed back to restart the spark, yet close enough to maintain good efficiency. Observation of the currents in real time could occur only with the aid of laboratory instruments; in practice, the operators used what were for the time conventional instruments. "Hot-wire" ammeters, d'Arsonval (dynamic) wattmeters, wave-meters, and regular voltmeters sufficed.

Notice that the currents appear to be "modulated." Indeed, that is just what is happening. **Figure 14** shows the currents in **Figures 11** and **12** recalculated to reveal the decaying sinusoidal (and cosinusoidal) envelopes. Note that when one is at a maximum, the other is at a minimum—right down the line. If the actual signal frequency were in the audio range, it would appear to have "beat-notes"—a not-so-subtle indication of a "second frequency" that

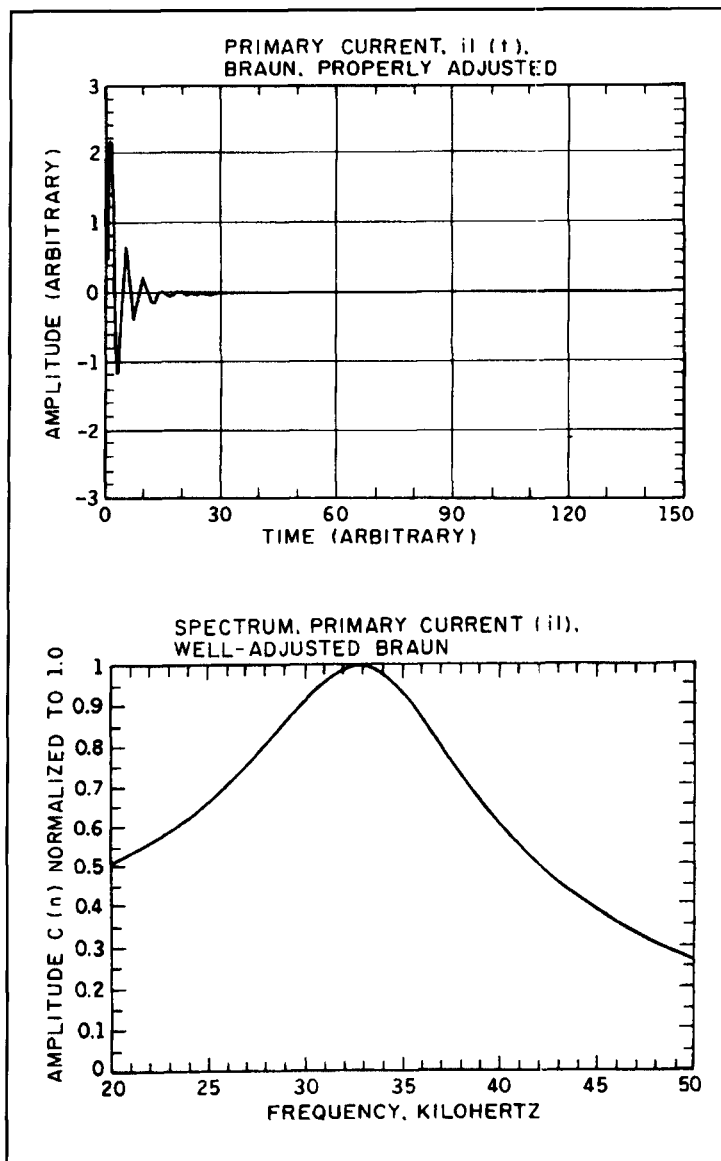


Figure 10. (A) Primary current, $i_1(t)$, Braun, properly adjusted. (B) Spectrum of the primary current (i_1), well adjusted.

was mentioned earlier. The envelopes reflect the combined log-decrement.

The figures show both primary and secondary currents to have a common log-decrement. Zenneck goes into great detail about the differences of decrement between coupled circuits both with and without a spark-gap.⁷ If the primary gap quenches by giving up all of its energy to the secondary, and if the coupling is loose enough so there is no reignition of the spark, the secondary—which is the antenna circuit in this discussion—behaves as if there were no primary circuit at all, and it decays by its own unique decrement. Coupled decrements will not be addressed.

Marconi designed and operated very advanced spark transmitters. There were others,

too, but his are perhaps the most thoroughly documented. Some very exotic electrical designs and equipment were required to overcome certain problems. One of his transmitters at Carnarvon, Wales (callsign MUU), was a 300-kW spark transmitter. Very thorough discussion of the design of this transmitter can be found in the *AWA Review*.⁵ A few characteristics follow.

None of the damped wave-shapes presented later on show a log-decrement of less than 0.1. MUU and several others, however, emitted a damped wave of exceedingly small decrement—0.029 being rather representative of those systems. Such decrements were completely out of the reach of hams. They occurred in large, expensive, professional systems with very good ground setups, and they were for waves of approximately 10,000 meters. Both were beyond the pocketbooks, the knowledge, and later, the law, for hams (“200 meters and down”). The Carnarvon antenna (for 11,000 meters) was a trapezoidal flat-top, varying from 450 to 600 feet wide by 3100 feet long. It was supported at a height of 400 feet by ten masts. Its feedpoint resistance was 1.4 ohms, and the capacitance of the antenna was 0.039 μF .⁵ Its spectrum would no doubt show a lot of the same “fine structure” present in the CW spectrum (Figure 3).

An alternator supplied 150-Hz power to the transmitter. At one spark at each of the positive and negative peaks, the “tone” (spark-rate or δ) was 300 Hz. It wasn’t an arbitrary selection. With a decrement of about 0.03, over seventy oscillations in the antenna current were required to reduce it to 10 percent of its initial value. Thus, there was always a remaining oscillating current in the antenna circuit—and it was present at the next primary pulse. Even though the gap was synchronized at the alternator frequency, there was still “jitter” inherent in all those systems, so synchronizing the primary initial current rise to the desired 90 degree lag with respect to the antenna current was extremely difficult. It was impossible to guarantee. Rather than abuse transformer, gap, and other components, a synchronous pulse rate was selected to assure that the remaining oscillating current in the antenna was reduced to about 10 percent. In this way, the initial pulse phase could vary from +90 degrees to -90 degrees without damaging components. Remember that the initial current in the primary transformer was 9,000 amperes.

The maximum capacitor voltage was 35,000. Primary circuit capacitance was 1.5 μF . Even at 11,000 meters (27.3 kHz) the total primary inductance could not exceed 22.7 *microhenries*. That meant that “interconnecting” conductors could not add much inductance. They were of

copper, quarter-inch thick, 24 inches wide, and several feet long. The primary of the oscillation transformer was three turns, with an inner diameter of about 4 feet. The "turns" were composed of a sheathed 12-inch diameter cable of Litz-wire. The size of components—both electrical and physical—by this time had limited further power escalation of spark transmitters.

There were about 450 spark transmitters of various sizes in operation in the U.S. at the height of their era. This compared with perhaps a dozen large arcs, most of which were in the hands of both the U.S. Navy and Federal's commercial enterprises. The spectrum was crowded. Operation with the minimum log-decrement was sought by everyone, and there were several different practical methods employed by the operators for determining it, which, as stated above, was restricted to 0.2 after 1919. They faced even *another* restriction, also in the Department of Commerce regulations—affecting both arcs and sparks. If the transmitted signal contained more than one frequency (measurable by a sensitive wave-meter), the second (unwanted) signal could not exceed twenty percent of the main signal. An exception was in the transmission of emergency and emergency-related signals. Operation with less-than-lawful signals, by the way, is still permitted under those circumstances.

The problem of crowding was compounded by the fact that the common detectors were envelope detectors, still using tuned circuits of relatively low selectivity. Crystals (Galena, Silicon Carbide, and some others—with "cat's whiskers") as well as electrolytic and thermionic diodes (Fleming Valves) were used most often. Heterodyning detectors were of little use in receiving spark signals, and diode-detectors were equally useless in most cases in the detection of pure CW (then usually arc) signals. All of these detectors were passive. They had no signal amplification. The *transmitters* had to supply the power necessary to actuate operators' earphones—operators who were sometimes 3,000 miles or more away from the transmitter. Improvements brought about by the development of both "gassy" (i.e., De Forest) and high-vacuum triodes (hence regenerative detectors, too) did enable signal enhancement, but much later. They appeared in the latter part of the *spark transmitter era*—principally in its last decade. They were better suited to the reception of CW signals.

Operation of large spark transmitters in the near vicinity of receiving posts using crystal detectors was an incompatible combination. During the several years of development—principally to higher powers—occasional "welding" of cat's-whiskers to the crystals occurred, even with the T/R switch in the "receive" position.

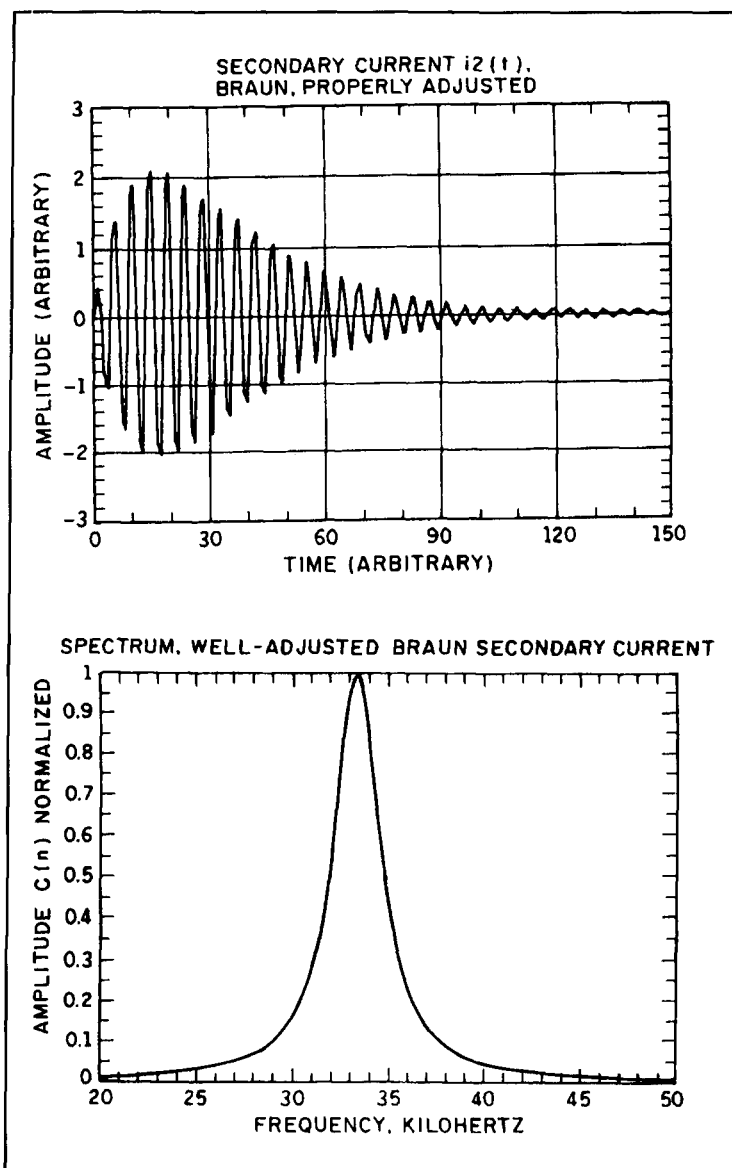


Figure 11. (A) Secondary current $i_2(t)$, Braun, properly adjusted. (B) Spectrum of the well-adjusted Braun secondary current.

That is just *one* of the reasons for high-powered stations placing their receiving locations many miles away from the transmitters. Keying was accomplished by telephone lines—"hard-wired." That was true of all large stations, no matter what type of equipment was used. It was a more efficient use of personnel and facilities, such as telephone and telegraph, to have traffic nets serviced from one location. Often those operators were controlling several transmitters simultaneously on different frequencies.

Some analyses

Fortunately, spark-generated wave-shapes are easy to reconstruct. The correctly-coupled and over-coupled Braun transmitter cases faithfully

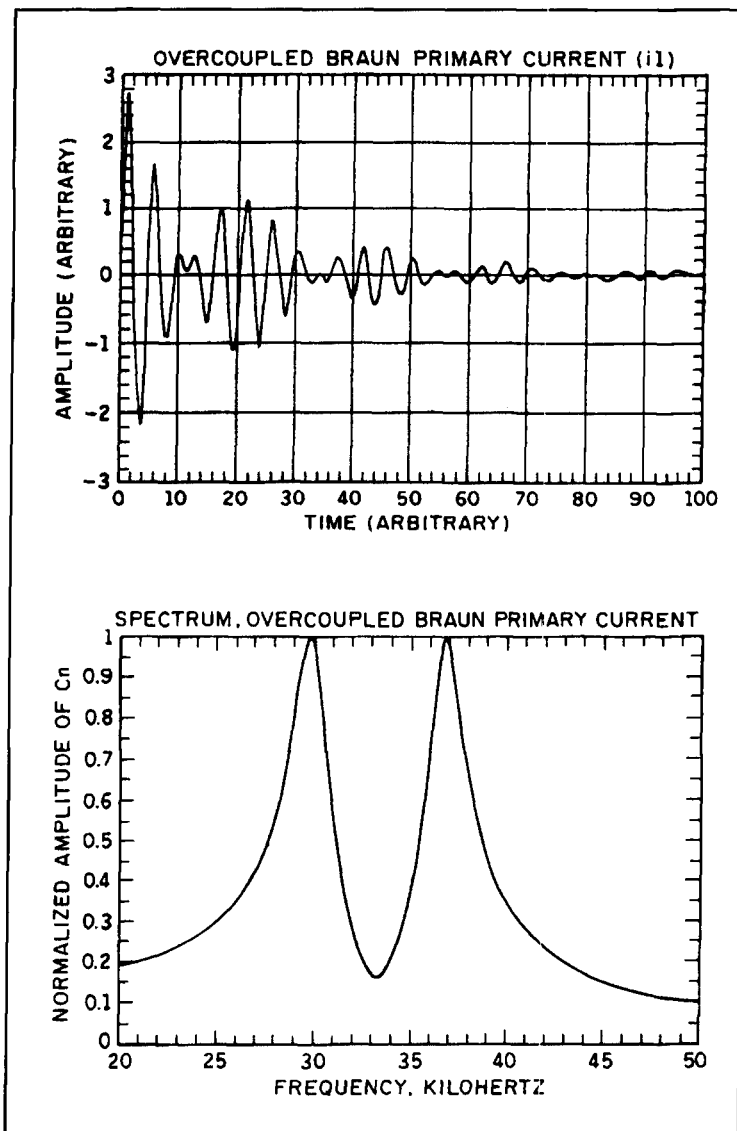


Figure 12. (A) Overcoupled Braun primary current (i_1). (B) Spectrum of the overcoupled Braun primary current.

reproduce the shapes of published wave-shapes from Zenneck, dated 1915. The waves simulated in this paper are adequate for the purpose.

The preceding paragraphs have presented the shapes of virtually all the transmitted waves and some that are not, like the Braun primary currents. They are paired with their frequency spectra, which in turn are related to Federal regulation of the log-decrement of spark signals.

What were these signals like? Since there are few people alive today who actually have operated spark transmitters, we must use other means to evaluate them. One good way is to calculate their frequency spectra. It also removes subjective bias from the evaluations.

We are fortunate to have many tools for bandwidth investigation. The most valuable analytical tool for use in this case is Fourier

Analysis, because we have clear analytical expressions with which to work.

They are:

$$i(t) = a_0 (\sin(a_1 t)) e^{-a_2 t}, \quad (5)$$

$$i(t) = a_0 e^{-a_1 t} (\sin(a_2 t)) (1 - e^{-a_3 t}), \quad (6)$$

$$i(t) = a_0 e^{-a_1 t} (\sin(a_2 t)) (\sin(a_3 t)) (1 - e^{-a_4 t}), \quad (7)$$

$$i(t) = a_0 e^{-a_1 t} (\sin(a_2 t)) (\cos(a_3 t)) (1 - e^{-a_4 t}), \quad (8)$$

and,

$$i(t) = a_0 (\sin(a_1 t)) \quad (9)$$

Equation 5 is identical to **Equation 2**, and is repeated for convenience. It describes both the Marconi wave-shape and the Braun primary current when properly coupled. **Equation 6** is of the form of the Braun Secondary (antenna) Current, properly coupled. **Equations 7 and 8** describe the overcoupled Braun secondary and primary currents, respectively. **Equation 9** is that for a steady-state carrier. One spectrum for a pulsed carrier is included. The programs all yield line-amplitudes (C_n), but the spectra are easier to judge if the envelopes are shown—rather than the individual lines—so most of them show the envelopes.

They all lend themselves well to numerical integration, and that is how the BASIC programs—generated for this paper—did it. The advent of fast personal computers, particularly those with math coprocessors operating on compiled programs, makes it relatively easy. All of the spectra were calculated with a minimum of 1,500 products per point, and most of them encompassed 50+ points (frequencies in this case). For those interested, uncompiled BASIC operation on the (CW) integral required 14 seconds per point; when compiled and with the coprocessor invoked, it probably would require less than a second. All these calculations were performed (uncompiled) by an 80386 microprocessor operating at 25 MHz.

Some standardization was required to put all these spectra on the same footing. I chose a spark operating frequency of 33.3 kHz, for one of the bases. All of the curves reflect that frequency. There's nothing special about 33.3 kHz. It was in the right range, and was selected before this paper was begun. One time unit in all the figures represents 6.6667 microseconds. The repetition rate (δ) was assumed to be 1000/second. That repetition rate is employed in *all* the figures, including the one-ms pulsed CW case. When the integration was first performed on a CW carrier pulsed every millisecond, it did *not* reveal a single thin line; it had

finite width. This solution resulted from my taking 1-kHz “cuts” at the functions; it did not have the required resolution. The two spectra depicting pulsed carriers (**Figures 3 and 15**) were produced by specifying 0.05 kHz steps. Notice the narrowing of the signal width as the pulse length is increased. The spark-generated signals of $d = 0.2$ or more did not show any “fine structure”—they were just plain *broad*!

It is important to remember that the programs automatically start the function from zero at $t=0+$, and at the end of the pulse, if it has not damped out, is similarly dropped again to zero—something that the operating transmitter gap cannot do. The spectra therefore must contain the frequencies necessary to define both the leading- and trailing-edges of the pulses. They have been normalized to 1.0 maximum amplitude for easy comparison. Identification and further descriptions are found within the figure captions.

The preceding paragraphs have been dedicated to the apparatus and techniques of 70 to 90 years ago. Are there any similar signals transmitted today? Certainly! A recent issue of *Communications Quarterly* contains a figure showing the shape of a modern LORAN-C pulse.⁸ It is reproduced here as **Figure 16A**. Notice that it strongly resembles the shape of a “well-adjusted” Braun antenna current. The pulse simulation (**Figure 16B**) is not exact, but is so similar that the analysis probably can be trusted. The equation for the simulated pulse is:

$$i(t) = a_0 (e^{-a_1 t}) (\sin(a_2 t)) (1 - e^{-a_2 t^3}) \quad (10)$$

This equation may look like one of the others, but there is a t^2 in the exponent of the last term. None of the others have it; it was necessary in order to simulate the LORAN pulse.

These are different times, and the LORAN-C system exists for an entirely different purpose. The pulse has been subjected to the same exercises as have all the others in this article—for curiosity’s sake. It would have been “just inside” what the law would have allowed; its log-decrement is about 0.15, and its spectrum is broader than that of the well-adjusted Braun antenna current, which for this paper (and usually in practice, too) had a smaller decrement.

The LORAN pulse carrier frequency has been translated to our 33.3 kHz “standard,” and is pulsed at the 1 kHz rate. Its spectrum can be laid right over that of a Braun secondary current pulse of log-decrement 0.15. There is a small difference, however. The leading edge rise of the LORAN pulse is slightly gentler than that of the Braun. It is reflected in the spectrum, which shows lower-amplitude frequency components away from the carrier. Otherwise they are practically identical.

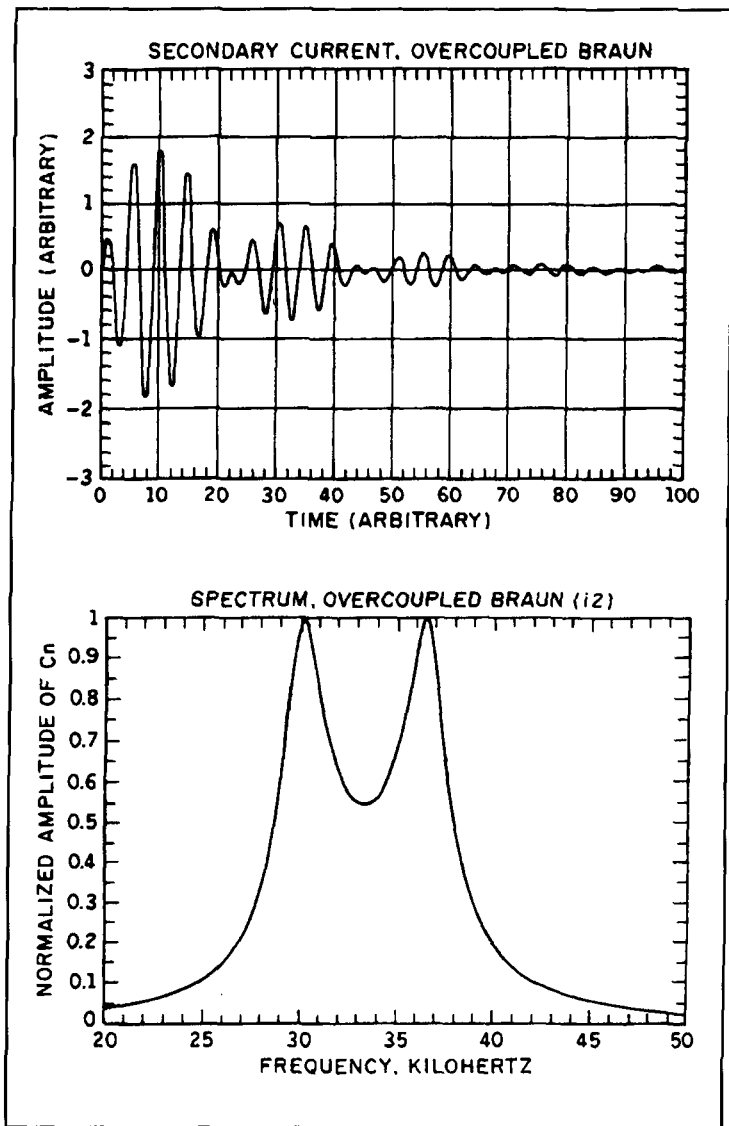


Figure 13. (A) Secondary current, overcoupled Braun. (B) Spectrum, overcoupled Braun (i_2).

One last pulse-spectrum was calculated. To demonstrate just how much of the spectral width results from the steepness of both the leading and trailing edges of the pulse, a wave-shape that has gentle slopes on both ends was synthesized. Its defining equation is:

$$i(t) = 5(\sin(1.3963 t))(\sin(2.068E-2 t))^2 \quad (11)$$

Figures 17A and 17B are the wave and its spectrum. It is the narrowest spectrum reproduced in this article—except for the two “CW” spectra. There are very low-level peaks on either side of the carrier, however, and they occur at multiples of the “modulation” frequency (the simulation required that the carrier be modulated sinusoidally, plus have a repetition rate of the same base frequency—1 kHz). They

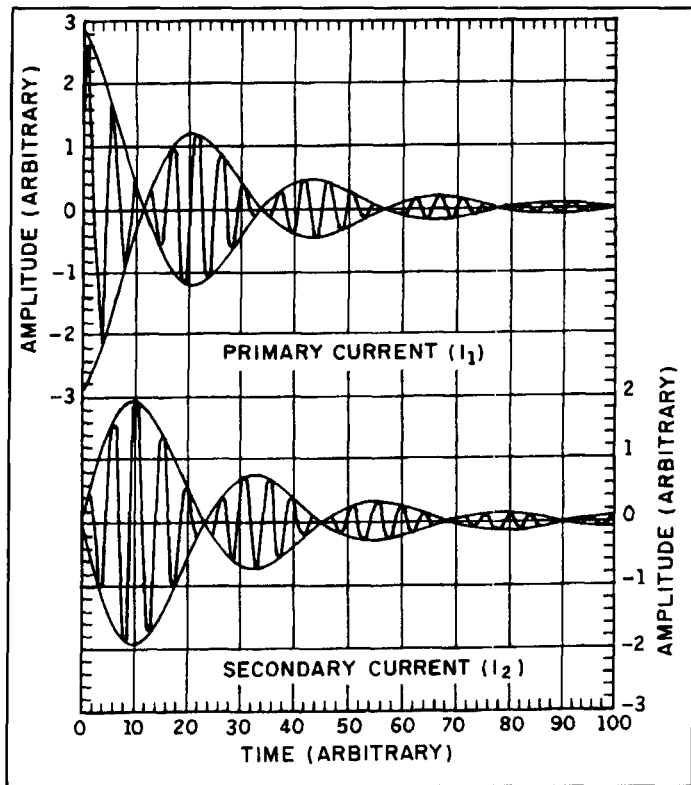


Figure 14. Currents in Figures 12 and 13 recalculated to reveal the decaying sinusoidal envelopes.

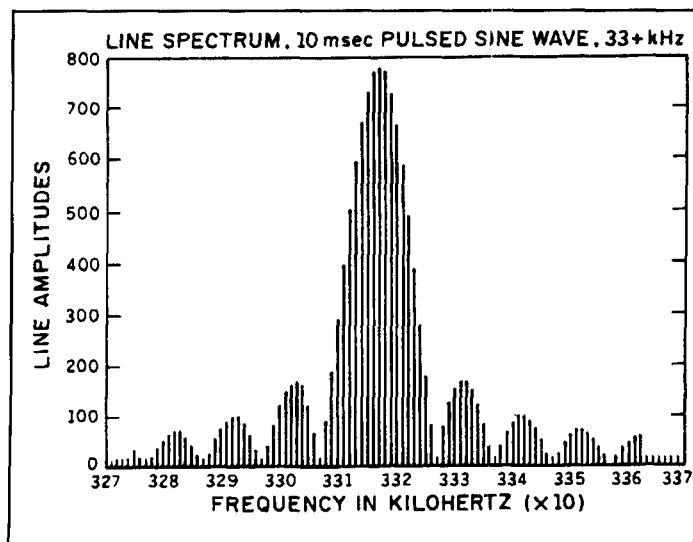


Figure 15. Line spectrum, 10 msec pulsed sine wave, 33+ kHz.

would be much more prominent if the pulse were to last for several cycles of the modulation envelope. The pulse was engineered to use only one full cycle of the envelope, and many cycles of the 33.3 kHz “carrier,” which is therefore much more prominent in the spectrum. Otherwise there would be *three* prominent peaks: one for the carrier, and two for the mod-

ulation—one appearing on each side of the carrier peak. We all have seen that type of spectrum elsewhere.

The BASIC program

A technique often used for determining the Fourier coefficients of unknown functions (such as one that may appear on an oscilloscope face) was adapted for these waves. Where one normally must measure the ordinates of figures recovered from an oscilloscope, we merely calculate the ordinates; we already have the analytical expressions. It is a simple program, containing merely 23 lines, of which only 15 are really necessary to determine the coefficients. It appears as **Figure 18**.

Absolute values of the coefficients are deemed unimportant for this study. All spectra have been normalized to 1.0 maximum, and therefore the original values of the coefficients disappear in the normalization. The magnitudes of A_n and B_n (and thus C_n) are first computed for their peak values (a few points—here, around 33.3 kHz), and then the normalizing factor—unique for each spectrum—is entered as a divisor on Line 171. It is the “/10.01” in **Figure 18**. It is valid only for that spectrum.

The coefficients A_n and B_n in the program descended from the equations contained in any one of several *Circuit Analysis* textbooks.^{3,9} Their defining expressions are:

$$A_n = \frac{1}{\pi} \sum_0^{2\pi} y \sin nx \Delta x, \quad (12)$$

$$B_n = \frac{1}{\pi} \sum_0^{2\pi} y \cos nx \Delta x, \text{ and } (13)$$

$$|C_n| = \sqrt{A_n^2 + B_n^2}, \text{ since } (14)$$

$$C_n = A_n + jB_n \quad (15)$$

A_0 , the DC offset present in an asymmetrical wave-form, is missing in these calculations because of inherent symmetry. C_n and n are the numbers tabulated in the program output. They are labeled “CN” and “N.”

The BASIC program is not universal. Each spectrum requires its describing function be entered manually into the program, along with certain program modifications. As it appears in **Figure 18**, it is set up to calculate the coefficients for a CW wave. It is programmed to evaluate those coefficients *every 50 Hz* (see Line 172: $N = N + .05$). Most of the spectra

were calculated with N set equal to 1.0 or 0.5. It's your choice.

The spectrum for the 1-ms pulsed CW (see **Figure 3B**) reveals much "fine structure." The spectrum of the wave with $d=0.1$ was generated using 50-Hz resolution to see whether there would be similar "fine structure." **Figure 4B** shows that it does, indeed, though it is of limited significance in the overall appearance. This version, by the way, calculated 340 points—at 14 seconds per point. It was done to generate confidence in the spectra calculated for all the other waves in this paper. There is very little significant difference in the spectrum as calculated with 50-Hz resolution compared with that using only 1-kHz resolution—but there *is* some fine detail.

All the wave-shapes were computer-generated, and no doubt are "cleaner" than those generated by an operating transmitter. We can stipulate that they all start precisely at zero when $t = 0$, and end when we want them to. Practical transmitters *all* suffered "jitter;" an uncertainty in the timing of the start of a spark. Arc transmitters exhibited the same phenomenon (for a different reason) that will be revealed when arc technology is discussed in Part 2.

Marconi's CW spark transmitter

The heading seems contradictory; the bulk of this article has covered most of the methods used in spark technology, with emphasis on the damped-wave character of spark transmitters. There was an attempt, partly successful, to produce a transmitter using spark technology, for continuous waves.

Marconi and his very successful companies (several existed, including the American Marconi Company) were all based on the rotary spark, transmitting at very high power levels. It was obvious to all in the late 'teens and early 'twenties, that spark technology no longer stood at the leading edge of radio development. Nevertheless, Marconi's entire career had been in the development of just that technique. He had developed it (nearly) to its practical limit.

The wave of the future was to be in continuous waves, and everybody knew it. Marconi was not idle, however; he had been developing a method of using sparks to generate nearly pure CW, by employing an ingenious idea—the "timed spark."

The transmitter consisted of several disks (rotary gaps) on one shaft, which were arranged to produce a spark discharge in a rigidly timed sequence. The idea was to synchronize the shaft and the gaps so each primary impulse was followed by the next, adding to the coupled currents in sequence, thus producing continuous waves. **Figures 19** and **20** show the method

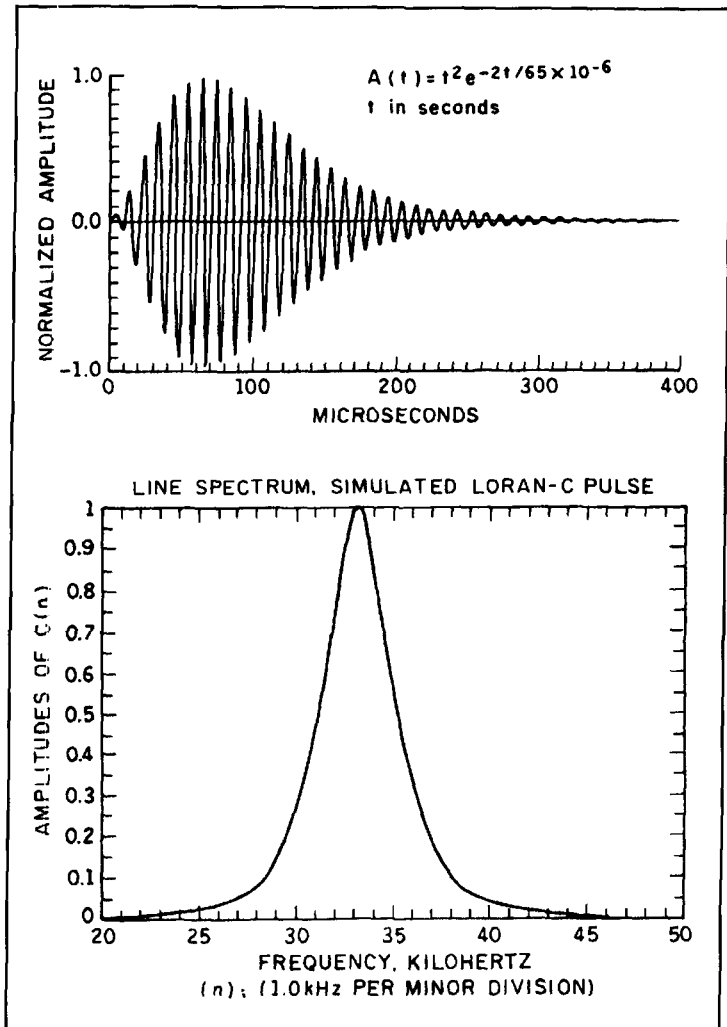


Figure 16. (A) Shape of a modern LORAN-C pulse reproduced from Evans and Evans, *Communications Quarterly*, Fall 1991. (B) LORAN-C pulse simulation.

and its resulting waveforms. Elmer Bucher said that the exact circuits shown in his book and reproduced here were not the final configuration.⁶ At the time of its publication (1921) Marconi was reluctant to divulge design details.

There were apparently two generators. One was operated successfully from station MUU with the excellent antenna system there. The other station was to be at Marion, Massachusetts, Marconi's terminus in the U.S. MUU was using the timed-spark transmitter in daily operation. Bucher wrote, "With a power of less than 100 kW, the author has copied signals from the Carnarvon station in New York City during the daylight hours with an aerial 100 feet in length. The signals were considerably stronger than those obtained from other foreign stations using radio-frequency alternators of greater power. The wave length employed during those tests was close to 10,000 meters."⁶

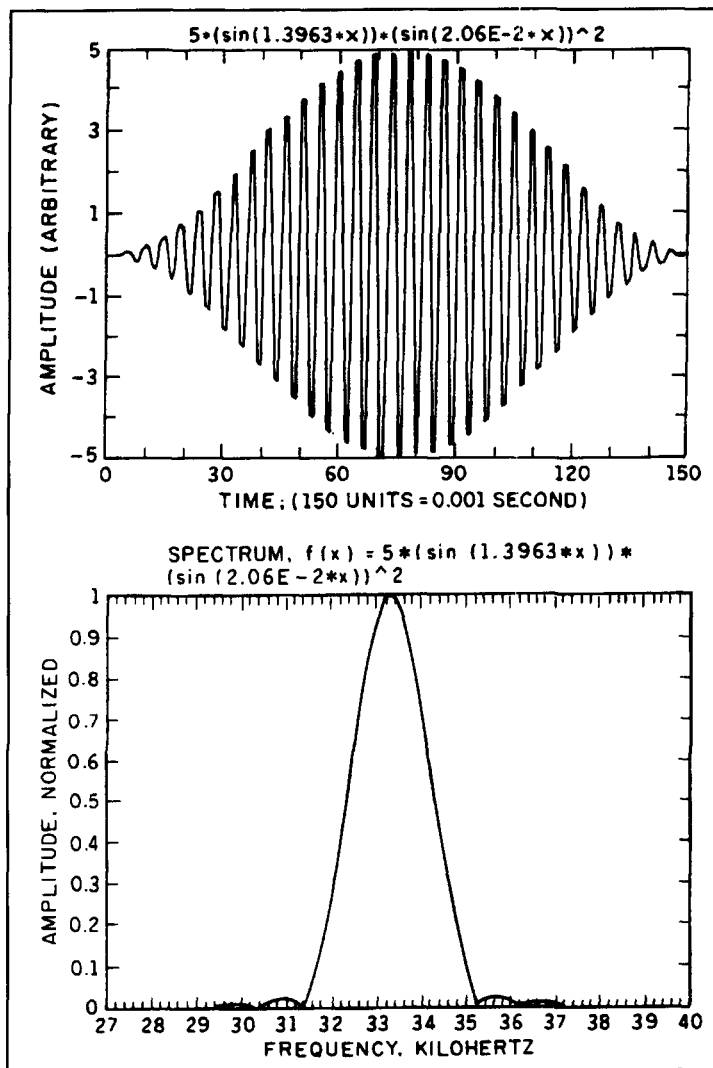


Figure 17. (A) Synthesized wave-shape with gentle slopes on both ends. (B) Spectrum of the synthesized wave.

The other generator was actually installed at Marion, Massachusetts. It never was successful.¹⁰ The antenna at Marion was an inverted-L one mile in length. It also used the Alexanderson multiple-tuned feed system. It was that antenna system, when the “star” type grounding system was used earlier, that produced brush fires. The soil underneath the antenna was very sandy, and obviously had a low conductivity, despite the fact that it was within sight of the ocean. Many transmitting sites, by the way, were built on shorelines, or actually on the beaches themselves.¹¹ The antenna system could very well be the reason for failure of the spark CW transmitter; that would seem to be the only difference between the two sites. MUU has a system that operated with a log-decrement of 0.029. By examining **Figure 19** again, it seems obvious that if the oscillation transformers (P_1 , C_1 , S_1 , etc.) had a large combined log-decrement, the currents could not combine properly to produce a good continuous wave. High ground resistance has the *strongest* influence on the log-decrement of VLF antennas.

The CW generator was the last major development using the spark. It was developed as a possible answer to the other competition—several alternator types, and of course, the very high-power arc transmitters, and the thermionic vacuum-type, which was destined to obsolete them *all*. It was the spark’s last gasp.

REFERENCES

1. Captain L.S. Howeth, USN, *History of Communications-Electronics in the United States Navy*, Washington, U.S. Government Printing Office, 1963.
2. David Kahn, *The Codebreakers—The Story of Secret Writing*, Macmillan Publishing Company, Inc., New York. (Tells of intercepts of field transmitters on both sides in World War I and their decryption.)

```

20   A1 = 0: B1 = 0
30   CTR = 0
40   DEFDBL A, B, Y, W
50   INPUT "ENTER STARTING N" ; N
51   LPRINT "Y = 2*(SIN(1.3963*X))
60   PRINT "WAIT - PROGRAM RUNNING." : PRINT:
61   PRINT TIMES$
70       FOR X = 0 TO 150 STEP .1 ' (Asks for 1,500 computations)
80           Y = 2* (SIN(1.3963*X))
90           W = (6.2832*X)/150
100          Y1 = Y*SIN(N*W)/150
110          A1 = A1 + Y1
120          YY = Y*COS(N*W)/150
130          B1 = B1 + YY
140          CTR = CTR+1 ' (This is to keep track of 1,500 integration steps)
150       NEXT X
160       LPRINT USING "###.###" ; N
161       PRINT USING "###.###" ; N
170       LPRINT "CN = " ; SQR (A1^2+B1^2)/10.01: LPRINT
171       PRINT "CN = " ; SQR (A1^2+B1^2)/10.01
172       A1 = 0: B1 = 0: N = N+.05
181       PRINT CTR-1 ' (Erases the last incrementing in line 140)
190       CTR = 0: IF N <= 38 THEN GOTO 60 ELSE END

```

Figure 18. Program listing.

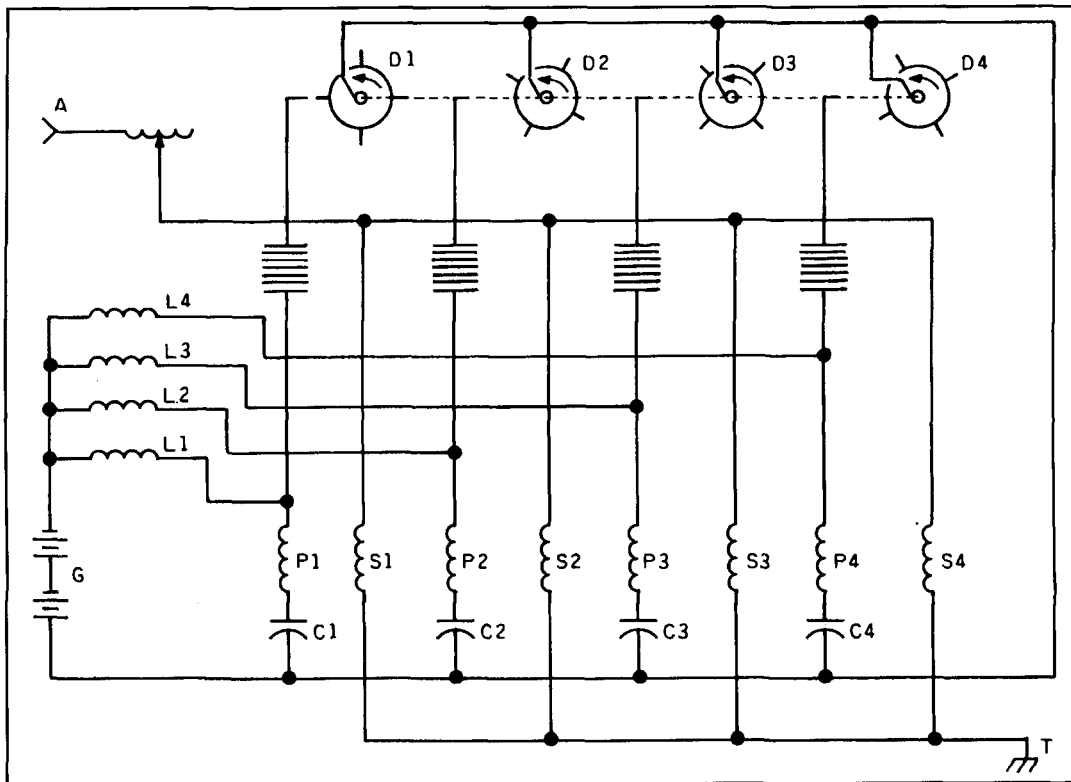


Figure 19. Marconi's method of generating continuous oscillation. (From Bucher).

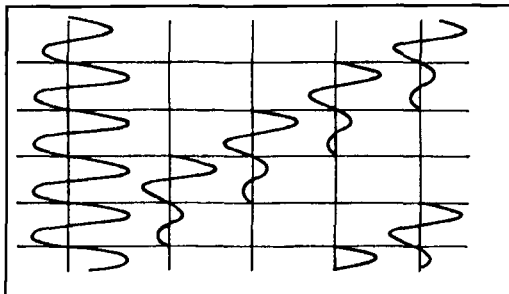


Figure 20. How groups of damped oscillators can be made to overlap one another. (From Bucher).

3. M.E. Van Valkenburg, *Network Analysis*. Prentice-Hall, Inc., Englewood Cliffs, New Jersey, 1955.
4. J. Zenneck, *Wireless Telegraphy*, McGraw-Hill Book Co. Inc., New York, 1915.
5. A.C. Goodnow, "Across the Gap; An Appraisal of Spark Radiotelegraph Engineering," *The AWA Review*, Vol. 2, 1987.
6. Elmer E. Bucher, "Practical Wireless Telegraphy," *Wireless Press*, New York, 1921.
7. As [4], Article 76 et seq.
8. Randy Evans, KJ6PO, and David Evans, N6UEZ, "Loran-C Frequency Calibrator," *Communications Quarterly*, Fall 1991, page 20.
9. R.M. Kerschner and G.F. Corcoran, *Alternating Current Circuits*, John Wiley and Sons, Inc., New York, 1951.
10. Bruce Kelley, W2ICE, personal communication. Bruce witnessed the final days and the dismantling of this and other stations. He also is Curator of the AWA Museum.
11. Irving Vermilya, W1ZE, "Wireless Cape Cod (WCC)", *QST*, February 1942.

PRODUCT INFORMATION

AEA's PK-96

Advanced Electronic Applications, Inc. introduces the PK-96 Packet Controller. The PK-96 is a high-speed, single-mode data controller offering 1200 baud AFSK tone signalling as well as 9600 baud K9NG and G3RUH compatible direct frequency modulation.

The PK-96 offers amateurs the ability to communicate on existing 1200 baud packet systems, as well as communicating with the 9600 baud systems now coming on line. As a high-speed data link, the PK-96 eliminates system bottlenecks and increases system capacity. These features make the PK-96 useful for terrestrial and satellite communications.

The controller comes standard with 14K of battery backed MailDrop memory that is expandable to 100K. Other features include: a hardware HDLC controller to guarantee accurate protocol conversion at 9600 baud; hardware "true DCD" state machine for open squelch operation; and an enhanced MHEARD function that identifies TCP/IP, NET/ROM, and <The-Net> stations.

Suggested retail price of the unit is \$229. The PK-96 is available from your favorite amateur radio dealer.

For more information, contact Advanced Electronic Applications, Inc., P.O. Box C2160, Lynnwood, WA 98036. Phone: 206-774-5554; FAX: 206-775-2340.

Peter O. Taylor

AAVSO Solar Division

4523 Thurston Lane, #5

Madison, Wisconsin 53711-4738

THE SOLAR SPECTRUM

Another index of solar activity


In a recent issue of the Space Environment Laboratory *User Notes*,¹ Frank Recely of SEL and the National Solar Observatory (NSO) described the solar synoptic program which utilizes the vacuum telescope on Kitt Peak, Arizona. Virtually all active solar phenomena, sunspots, flares, coronal holes, etc., are related to magnetic influences on the Sun (**Image A**), so this work is of interest to a broad range of researchers and scientists. According to Mr. Recely:

"The vacuum telescope, one of twenty-two on the mountain, is a coelostat-fed 76-centimeter aperture reflector with a 36-meter focal length. It was built in 1972, with partial fund-

ing from NASA to support the *Skylab* mission of the early 1970s, and has been collecting data ever since. The telescope was designed by NSO scientist emeritus, William Livingston.

"The current program consists of collecting a daily full-disk, 1 arc-second per pixel solar magnetic map at 868.8 nanometers (nm), and a full-disk helium 1083.0 nm spectroheliogram. (The helium image is a good proxy for an extreme ultraviolet image of the Sun, and allows us to detect coronal holes and mass ejections.) These data are processed daily in real or near-real time and distributed to the solar community.

"Space Environment Services Center (SESC) receives these data in the form of daily 512 x

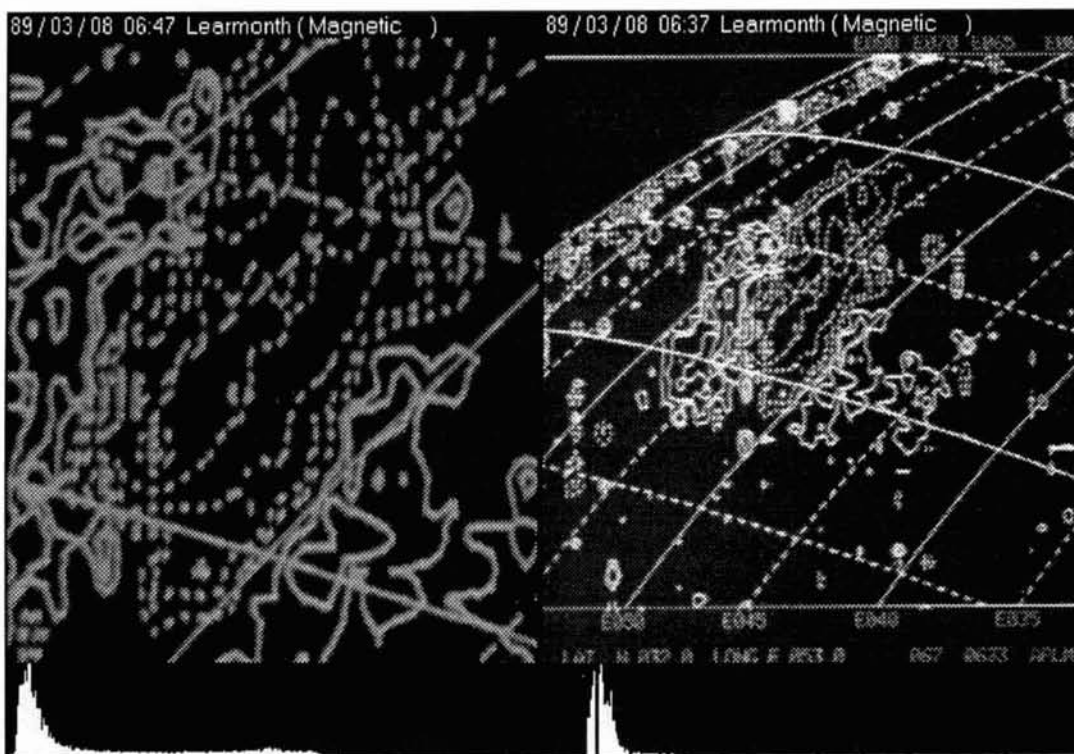

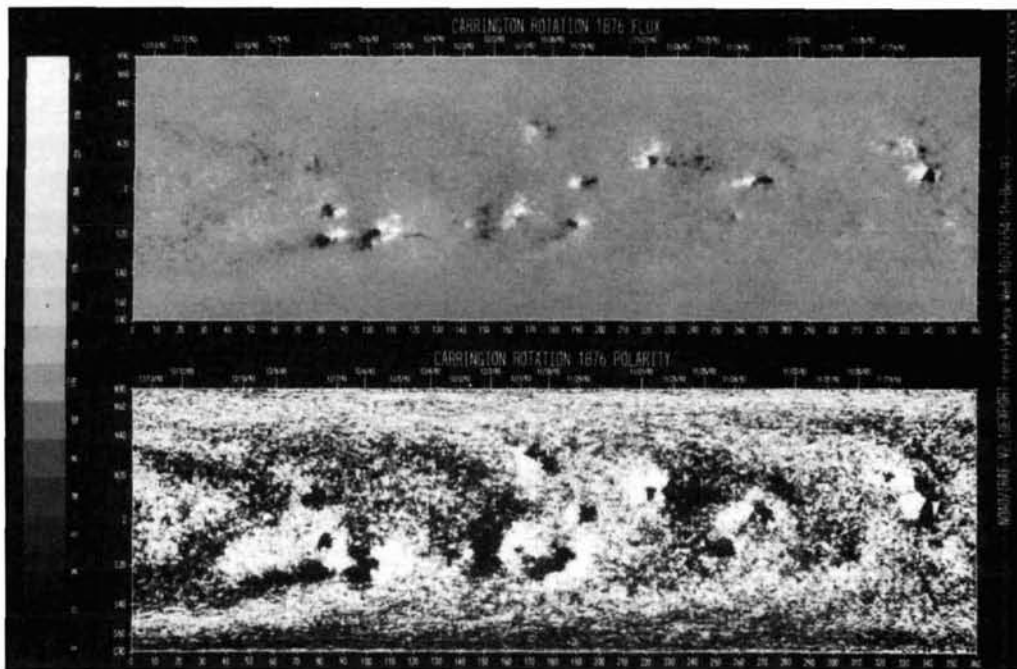


Photo A. Kitt Peak Solar Magnetic Field Synoptic Map. Daily full-disk solar magnetograms can be computer processed into Carrington Rotation maps. Maps such as the one shown here correspond to a single mean rotation of the sunspot zone, according to the method described by Richard Carrington in 1853. In the photo, bright areas represent positive polarities, while dark zones are negative. Note the opposite “leading” (more westerly) polarity for sunspot groups in the Northern and Southern Hemispheres. Northern leaders normally possess positive polarity during odd-numbered cycles, and southern leaders are negative; a feature that reverses each sunspot cycle. (Photo courtesy of Frank Recely, National Solar Observatory—Kitt Peak.)

512 pixel (4 arc-second resolution) digital images, which are sent automatically to Boulder through both Internet and SELSIS along with a line drawing of coronal holes inferred from 1083.0 nm images. These data—from November 1992 to present—also reside on an anonymous ftp disk in Tucson and are available to researchers.

“In addition, we collect a daily full-disk Calcium II K (393.4 nm) image of the Sun from which a *calcium brightness function* is measured as a parameter of solar activity. These data are not available in real time but are furnished at a later date. In the near future, we plan to provide additional images to the Internet community. Our immediate goal is to include the magnetic and 1083.0 nm maps at 1000 x 1000 pixels (2 arc-second accuracy) and to add an 868.8 nm intensity image (a possible first step to deriving sunspot area as a percent of total disk).

“Each month, the daily data are processed into Carrington rotation maps such as that shown in **Photo A**, and distributed to the World Data Center and SESC. These maps are also available on NSO’s anonymous disk for users. Dr. Karen Harvey of NSO computes an average total magnetic flux value from the Carrington map. A plot of the past 18 years appears in

Figure 1, with sunspot maxima and minima indicated.”

A few inferences from **Figure 1**:

- “The magnetic flux increases fivefold from minimum to maximum. This is a far larger increase than in the more common solar activity parameter, 10-centimeter radio flux.
- “The magnetic flux is closer in pattern to the 10-cm flux than to the sunspot number, as both reach a maximum after the sunspot maximum.
- “Cycle 22 is rapidly declining. When it drops below 30×10^{14} Webers, there is a three-plus year period of low solar activity.”

We are indebted to Frank Recely for his explanation of this productive program, and for his description of the variation in magnetic activity that accompanies each solar cycle.

A shielded, tuned-loop antenna with preamplifier

A few contributors to our program of recording ionospheric anomalies caused by solar flares² (myself included) have called attention to problems with interference on the signal to the VLF receiver. Some of this results from

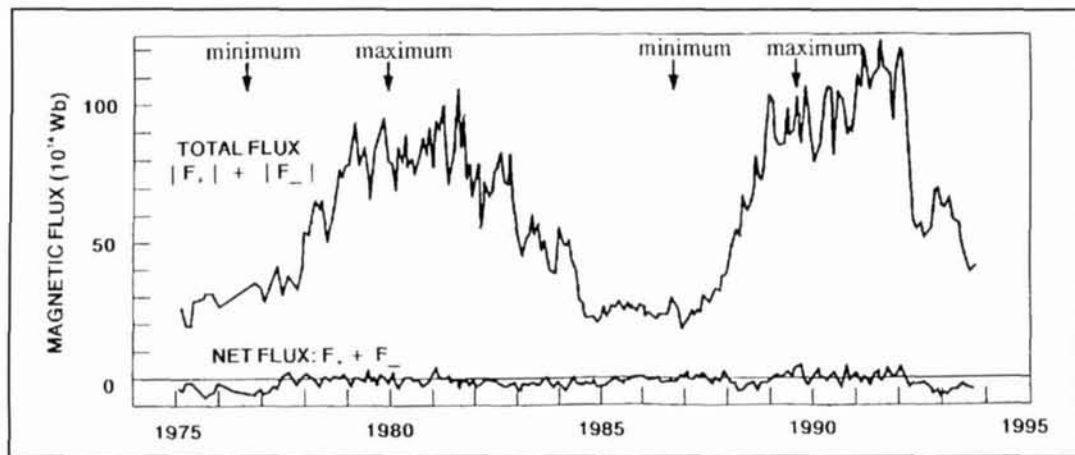


Figure 1. Eighteen-year magnetic flux variation on the sun by Carrington rotation. Sunspot cycle maxima and minima are indicated on the graph. Note that this index appears to peak after the sunspot cycle reaches maximum. The diagram originally appeared in the SEL *User Notes* for January 1994.

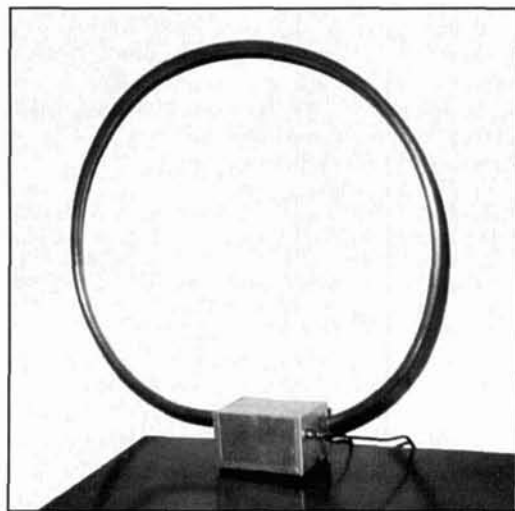


Photo B. Arthur Stokes' new shielded, tuned-loop antenna with preamp. This type of antenna can be helpful in locations where the VLF signal is weak.

exterior electrical noise, but other common sources are television sets and computers—especially older-model computer monitors. This situation can be particularly aggravating if one uses a small loop antenna inside the house. In fact, the noise emanating from some monitors can substantially affect TV reception. When I encountered similar problems, I did as I often do when an electronic difficulty rears its ugly head: I turned to Arthur Stokes for a solution.

Arthur suggested that we try to overcome my dilemma by exchanging my usual loop antenna for a shielded, tuned-loop with preamplifier (Photo B). These units generally incorporate similar design principles, and a number have been described in previous articles. The schematic for our design is shown in Figure 2. A parts list is included. The alert reader will rec-

ognize the circuit as a modification of the new Stokes' gyrator-tuned VLF receiver, which is described elsewhere in this issue. Incidentally, that printed circuit board can also be used for the antenna preamp. Unnecessary parts are simply omitted, and the board trimmed if desired.

This type of antenna is actually comprised of two parts: the shielded loop, and a metal box containing the preamp (Photo C). The first requirement of such a device is to enclose the wire winding of the loop in a nonmagnetic, metallic housing. This pretty much limits the usable material to copper or aluminum.

Soft 1/2-inch copper tubing (the type available in rolls at the local hardware store) was chosen for our unit, since it is always easy to obtain and can be worked without great difficulty. A single turn of the outer diameter of the roll was cut off, leaving a circle of material almost 24 inches in diameter. Next, an aluminum box measuring 3 x 4 x 5 inches was obtained. A box of this size could contain all the wire connections and preamp, and form a base for the shield. These boxes are usually supplied in two sections that fit neatly together. The cover required no modifications, so this part was set aside.

Two 3/4-inch holes were cut into opposite ends of the remaining section, and a 1/2-inch electrical conduit adapter was inserted through one opening. At this point, the loop of copper tubing should be adjusted by carefully shaping the material so that one end fits into the conduit fitting while the other is placed into the opposite opening, leaving about 1/2-inch of tubing extending into the box. The screw on the conduit fitting is then tightened so it clamps the copper tubing securely in place.

A short section of plastic tube about 1-1/2 inches long should be slipped over the free end of the copper tubing in order to insulate it from

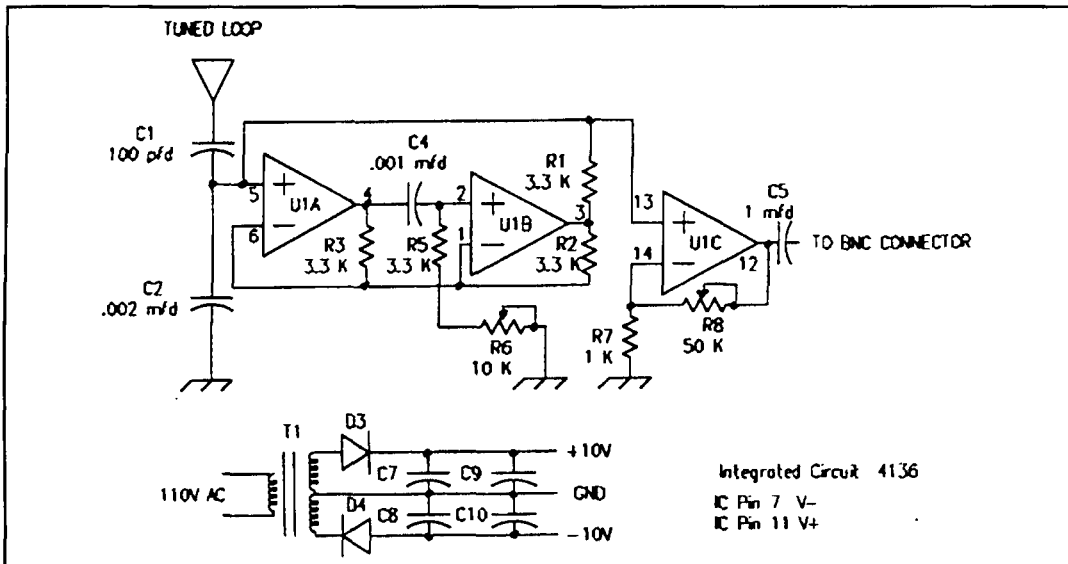


Figure 2. Schematic drawing of the antenna preamplifier. This unit utilizes the same printed circuit as the new Stokes' gyrator-tuned VLF receiver, which is described elsewhere in this issue.

the metal box, since the copper shield must not form a shorted loop! To attach the coil to the box even more firmly, a bit of fiber glass resin can be applied around the seams where the loop joins the box, and allowed to cure.

The next step is to prepare the wire loop and insert it into the copper shield. The material that forms our loop was salvaged from a 50-pair telephone cable. Such cables are comprised of 24 gauge insulated copper wires that are conveniently color coded. Incidentally, a bundle of 50 wires is about all that can easily be pulled through a copper tubing shield of this diameter.

The packet of wire—measuring about 7 feet in length—should be trimmed so that only about 4 inches protrudes from each end of the shield. The wire ends are stripped of insulation and soldered together to form a single 50-turn length, and short pieces of electrical tape are wrapped around the soldered joints. Care must be taken to identify each separate wire during this process, ensuring that a single continuous coil results.

The two ends of the wire loop are connected to a terminal strip, with a fixed capacitor shunted across the coil. The value of this component should be accurately adjusted by using a signal generator and oscilloscope to set the resonant frequency of the loop to that of the desired station. In our case, a 0.016 μF capacitor resonated at exactly 24.0 kHz—the frequency of VLF station NAA located in Cutler, Maine. One end of the loop is grounded to the shield and aluminum box and the other is connected to a 100-pF capacitor input to the preamp.

The pc board was mounted on 1/2-inch standoffs in the bottom of the box. A 12-volt,

Parts List: Preamp/Loop Antenna

R1,R2,R3,R5	3.3-k resistors, 1/4 watt
R6	10-k linear potentiometer or trimpot
R7	1-k resistor, 1/4 watt
R8	50-k linear potentiometer or trimpot
C1	100-pF ceramic capacitor
C2(2)	Parallel 0.001- μF ceramic capacitors
C4	0.001- μF ceramic capacitor
C5	1- μF electrolytic capacitor
C7,C8	470- μF electrolytic capacitors
C9,C10	0.1- μF ceramic capacitors
D3,D4	1N4001 diodes
U1	4136 integrated circuit chip
T1	12-volt CT transformer

Metal cabinet and miscellaneous materials (see text).

center-tapped transformer supplies power to the circuit. Of course the preamp can also be constructed on a small section of perfboard, with a similar placement of components. If that method is chosen, all wiring should be point-to-point with short pieces of fine wire used throughout.

Since only an initial tuning and gain adjustment is necessary, multi-turn trim pots were selected for R6 and R8. A fixed, 10-k resistor can be used for R8 to give a gain of 10, which seems to be a convenient value for my location in Southern Wisconsin.

The only adjustments necessary are to tune R6 of the gyrator for maximum signal strength, and R8 to the desired gain. When the recording system is set up, the loop should be placed a few feet away from the receiver in order to minimize any possible interaction. The two units can be connected with a 4 to 5 foot length

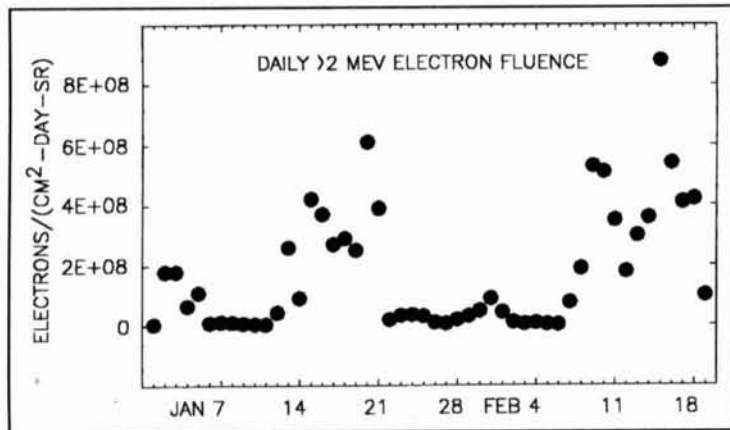


Figure 3. Enhanced electron levels from 1 January through 19 February 1994, as measured by instruments aboard the *GOES* spacecraft. Each of the plotted values has been integrated over the UT day.

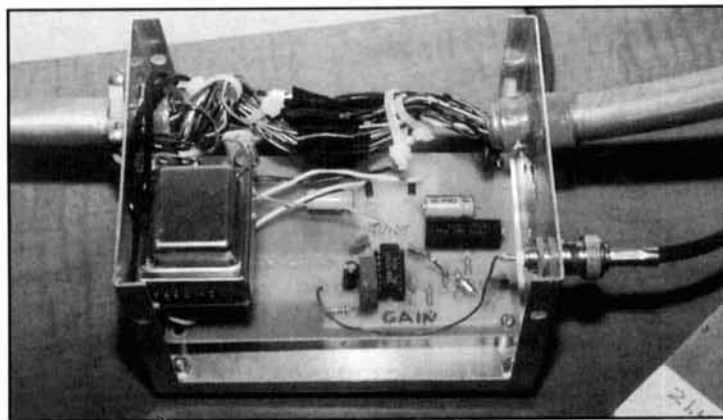


Photo C. The arrangement of copper tubing shield and wire loop in conjunction with the preamp's electronic components.

of coax. If a signal generator is not available, a little patience will be required to tune both the preamplifier and receiver to the exact same frequency. The preamp has a maximum gain of 50; but it is suggested that this be held to perhaps 10 or 20.

The Stokes' loop antenna works beautifully in my location. When I moved to Wisconsin last summer, the VLF signals that I had monitored in the past—NSS in the Washington, D.C. area and NAA—were weak and plagued with local interference. Since implementation of the new antenna systems, both produce excellent recordings allowing me to effectively monitor the ionospheric effects of many solar flares as the eruptions occur.

The January spacecraft anomalies

During mid-January the Canadian communications satellites, Anik E1 and E2, experienced failures and other spacecraft anomalies were reported at geosynchronous altitude. At the time, a number of media and other quasi-offi-

cial reports attributed these problems to a "massive solar flare" or even a "tear in the Sun's surface"! Such statements were erroneous to say the least. No eruptive events (flares, disappearing filaments, etc.) occurred that could have accounted for these difficulties.

In the Summer 1992 issue of *Communications Quarterly*, we discussed some basic features of the solar wind and the low density areas of the Sun's atmosphere known as "coronal holes." To our knowledge the precise mechanism is not fully understood, but after certain of these solar particle streams "connect" with the Earth's magnetosphere, electrons can be accelerated to moderate and high energies. Electrons with energies greater than 2 million electronvolts (MeV) were, in fact, detected by the *GOES* spacecraft during mid-January (Figure 3). Moreover, in this case relatively high energy levels were maintained over an unusually long interval.

Although not certain at this juncture, one explanation for the failure of Anik and the other problems in the near-Earth environment suggests an association with a phenomenon called "deep-dielectric charging," wherein energy penetrates down into the body of a spacecraft. Satellites can slowly discharge such currents, but damage to delicate electronics can occur if energy is deposited at a rate faster than it escapes.

Recurrent coronal holes are not necessarily geoeffective during each appearance, but they do have longer lifetimes and greater stability during the declining phase of a sunspot cycle. The coronal hole(s) that are suspected of involvement in the January incidents, rotated back into a position to affect the Earth's environment at the end of the first week of February. As can be seen from Figure 3, another long period of enhanced electron flux similar to January's high-energy flow was recorded.

A final point: The severe geomagnetic disturbance which began on February 20th-21st and resulted in a complete radio blackout over HF transpolar paths, was not related to the situation described above. Rather, these conditions—including a number of satellite magnetopause crossings, a Forbush decrease, and a sharp surge in reports of aurorae—were caused by the shock wave and plasma cloud from a solar flare and mass ejection that occurred early on the 20th. Protons reached a peak (>10 MeV) of near 10,000 particle flux units shortly after 9:00 UT on the 21st as the fast-moving outflow passed the Earth. This was the first proton event to be recorded since March 1993. ■

REFERENCES

1. SEL *User Notes*, Number 4, January 1994.
2. "Recording Solar Flares Indirectly," *Communications Quarterly*, Summer 1991.

TX HIGH-PASS FILTER APPLICATION

Improve low-pass filters performance by combining them with absorptive high-pass filters

When operating into reactive loads, low-pass filters (LPF) may exhibit degraded characteristics compared to those obtained when working into a pure resistive load. One reason for this is that interaction may take place at harmonic frequencies where the reflection to the input impedance of the LPF causes its performance to deteriorate significantly. This phenomenon can be alleviated, if not cured, with an absorptive high-pass filter (HPF) incorporated in shunt and resistively terminated, so the LPF sees a resistive load in its stopband consistent with its design requirement. Although much has been published regarding the design and application of LPFs, I found very little information about transmitter HPFs used in this application. Two overseas companies are currently manufacturing what I will call a "compound filter" of this nature; one in Japan and the other in Germany. The Japanese filter goes one step further. It consists of a shunt HPF to an LPF to a shunt HPF. The HPFs are terminated in 50 ohms. The company is reputable and claims significant performance specifications. Their power rating is limited to one kW. Unfortunately, I have no data on the filter being marketed in Germany.

In the spring of 1992, I published¹ a survey of LPF performance. While preparing that article, I became aware of previous work on the use of a HPF in a shunt configuration with a LPF.² A brief write-up and schematic of the same application appears in the *The ARRL Handbook*.³ I thought the idea of combining an LPF with an HPF was most intriguing, so it became a goal to learn about this concept and put it into practical application. My results are presented here.

When reviewing the earlier work, I noted that a rather simple four-element HPF was used in conjunction with a four-element LPF. Results were reasonable for 1968, and TV IFs weren't then in the 45-MHz region. Today, it's possible to obtain LPFs with good attenuation at 45 MHz and this is sometimes necessary. In 1968, a rather simple HPF could be used in conjunction with an LPF because its shape was much less demanding from 30 MHz to the first TV frequency of concern—56 MHz. To combine a high-pass and good-quality low-pass filter today, an exceedingly good shape is a necessity. An equal number of elements is required for the two filters to complement each other. It became readily apparent that a high-pass/low-pass combination would necessitate a

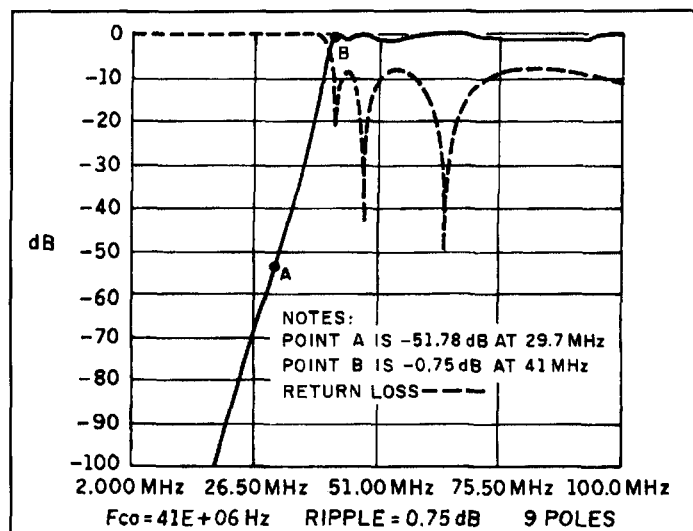


Figure 1. Theoretical HPF performance.

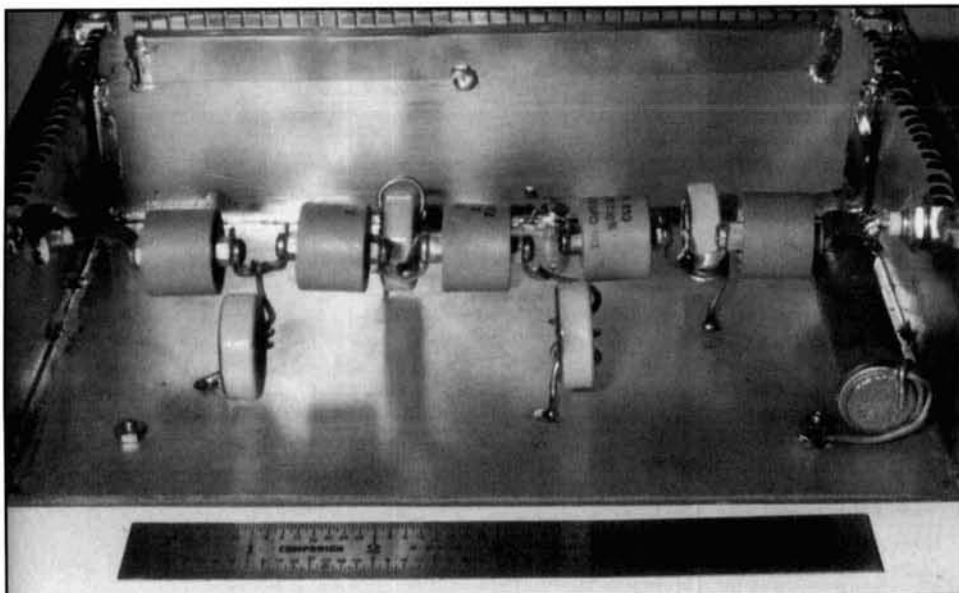


Photo A. High-pass filter configuration.

1:1 element relationship, causing me to quickly progress from a five to a nine-element Chebyshev filter! However, my computer program,⁴ into which I input some very demanding specifications, indicated that a twelve-element filter would be ideal. I compromised by increasing the ripple factor from 0.1 to an insignificant 0.75 dB in the passband, while lowering my sights to nine elements. This design was quite satisfactory. **Figure 1** is taken from the computer program print out of the theoretical result.

The design concept

I wanted to avoid the need to compensate the filter from cover-on to cover-off due to capacitive effects. I looked into the use of toroids to eliminate this problem, which is very dramatic in most LPFs I've measured. If the problem couldn't be resolved, I would need to be able to tune the filter from the outside, and this meant air variables, etc. Also, I wanted to use standard values of relatively high performance, non-inductive capacitors. First, I considered using etched Teflon™ printed circuit board, which would be ideal. Unfortunately, it didn't physically lend itself in the HPF configuration, as it would in an LPF where one side of the capacitors is grounded. I decided to use Centralab type 850/S units because they essentially fulfill all the requirements—including very reasonable current and a large overkill on voltage. (Should you wish, you can substitute high voltage ceramic NPO discs in parallel for the Centralabs.) The results were most gratifying. With the use of an oversize enclosure (more on that later) and the toroid inductors, I found no discernible response change when the filter was

covered, partially uncovered, or totally uncovered when on the breadboard.

The toroids are easy to wind and the entire assembly is very straightforward.

Some construction details

To minimize inductance between the capacitors, I used 1/4-inch wide copper strap. You could substitute 1/2-inch pieces of 6-32 threaded brass stock to interconnect the capacitors. This would make assembly very neat and more simple. Keep all leads short and solder them directly to the enclosure, which is constructed from 1/16-inch thick double-sided printed circuit board whose dimensions are 8 x 4.75 x 2.5 inches. The two copper planes *must* be fully joined together using methods such as screws, connectors, and solder. My results indicate that the enclosure could probably be smaller, but I wasn't going to expend the effort to find out! I included a BNC connector at the terminated end of the filter for two reasons. The first was to allow for testing on the spectrum analyzer and tracking generator; the second was for purposes of adding a detector at that point for some performance evaluation. I leave the use of the connector at the input end up to you. **Photo A** was taken when a BNC was needed at both ends for testing. The 50-ohm terminating resistor wasn't connected in the circuit for spectrum analysis, as the output of the tracking generator to the filter input is 50 ohms. Therefore, the filter is properly terminated in its characteristic impedance at both ends because the HP141T is also a 50-ohm system. Centralab type 850/S capacitors are available at flea markets and some surplus dealers at fairly reasonable prices.

The inductors are made from Micrometals T94-6 toroids (0.942-inch OD and a number 6 mix) that require only three turns of number 14 wire 3-3/4 inches long, including the leads. Micrometals' number 6 iron-powder mix is specified to be most effective in the 10 to 50 MHz range, and is color-coded yellow. The two end inductors are close wound and the intermediate ones are all wider spaced. **Figure 2** gives their dimensional details. I measured the coils on a Hewlett Packard model 4265B Universal Bridge, although I found that high precision inductances weren't mandatory. Consequently, if one wished to duplicate this filter, I feel that only very slight variations would occur with only minor effects on the performance. I tested shielding between filter elements and found no measurable change. This led me to conclude that the use of toroids was reasonable. It's certain that air-wound inductors would have higher Q, but such inductors would result in enclosure effects combined with the probable need for internal shields. As a precaution, I isolated the toroids from each other. This was solely for the purpose of eliminating capacitive coupling, because they are relatively free of inductive coupling due to their inherent self-shielding characteristic. In earlier breadboarding, I noted considerable performance degradation from apparent capacitive coupling. This was eliminated simply by physical isolation.

 


Figure 2. Toroid inductors.

Measurements with the analyzer, I use a -54 dB T notch filter centered at 14,195 kHz. This gives me the ability to place a very large fundamental signal into the analyzer without any risk of overloading its mixer, letting me obtain good harmonic measurements.

I tested the high-pass filter for ten minutes at 1500 watts continuous at 29.7 MHz, without an LPF, in shunt into a 50-ohm Bird dummy load. The carrier was relatively rich in harmonics. It exhibited no temperature rise during this type of operation as measured by a Fluke 8020A meter in conjunction with a Fluke 80T-150

Test results

In all configurations, I used a computer program for modeling. The final HPF calculations and schematic obtained using the program are illustrated in **Figure 3**. My conventional spectrum analyzer and tracking generator test setup is shown in **Figure 4**.

Figure 5 shows the performance characteristics of the HPF. The attenuation at 29.7 MHz is -52 dB—essentially the same value provided by the computer program based upon an infinite Q for all elements. This translates to a power loss of only approximately 9 mW out of 1500 watts. The attenuation at 41 MHz is desirably minuscule, which is consistent with the computer calculation and design objective. Also, note that my capacitors are slightly greater than the theoretical ones due to the manufacturer's standard values. This means the filter is probably over-designed in power capability unless one were to have some very serious harmonics being generated or coupled to the wrong antenna! **Figure 5** demonstrates the result of using a compound filter with a LPF, in this case a Drake TV-3300LP (regrettably no longer in production), that has good rejection at 41 MHz. Both scales on the spectrum analyzer are 10 MHz and 10 dB per division. In all cases of discrete harmonic mea-

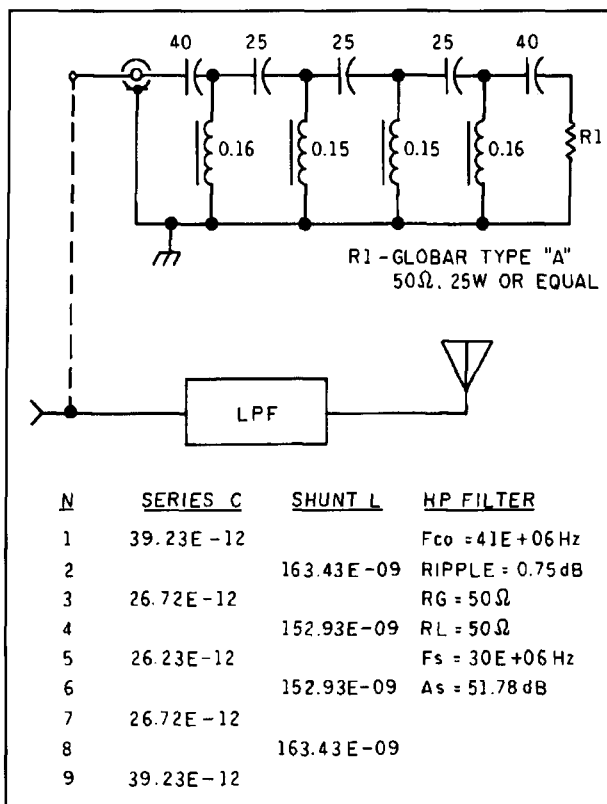


Figure 3. High-pass filter schematic.

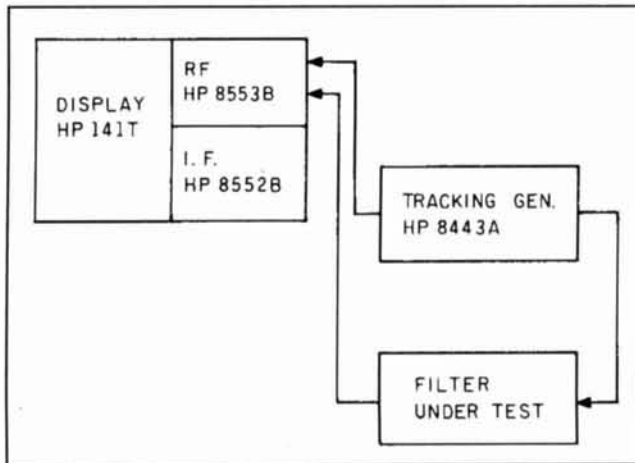


Figure 4. Measurement system. Note: The HP-141T/8443A is a 50-ohm system.

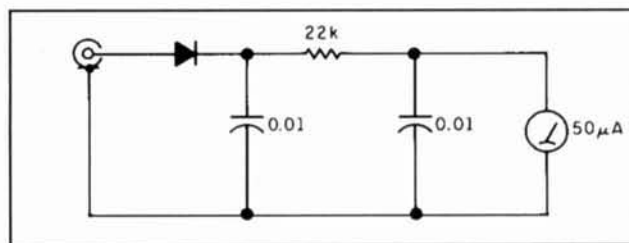


Figure 5. Detector circuit.

temperature probe. While I expected this theoretically from the measured response curve as shown in **Photo B**, it did provide proof that the toroids (I had no doubts about the capacitors!) had sufficient capability for the application. Based upon those results, it would appear that the Micrometals T80-6 (0.80 inch versus 0.96 inch) size would probably be adequate (and save a little money). Of course, this would mean reconfiguring the coils. You could try Micrometals' number 10 mix (black color code) for slightly better Q in the 50 to 100 MHz region. However, their number 6 mix appeared to be reasonable since, from my test results, a higher Q didn't appear necessary.

I then tested the filter under the same conditions, as noted above, but in conjunction with an LPF (a Drake TV-3300LP) into a 2:1 VSWR. I did this by paralleling two 50-ohm Bird dummy loads to simulate what might occur in some real-life situation. There was an increased relative output across the HPF internal dummy load in accordance with the detector schematic, as shown in **Photo C**. There was no measurable temperature rise in the HPF as a result of my tests, but my poor LPF became a bit warm at times!

Conclusions

A compound filter of this type can only yield

 


Photo B. Compound filter response. Note: Scales are 10 MHz and 10 dB/division.

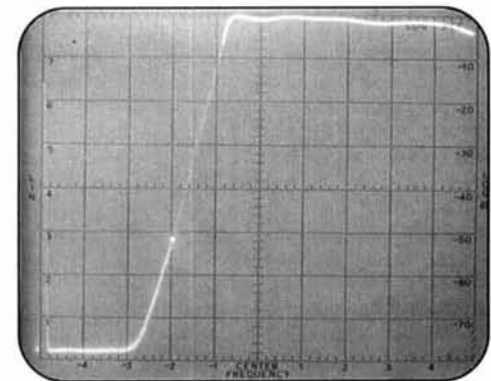


Photo C. High-pass filter response. Notes: Scales 10 MHz and 10 dB/division. 29.7 MHz is -52 dB. The tracking generator marker is at 29.7 MHz.

improved harmonic attenuation by virtue of its nature, because its response curve should provide a good 50-ohm termination to all frequencies above 41 MHz. This prevents significant amounts of that energy in that spectrum from being reflected back to the LPF, potentially degrading its performance. Those who operate in a fringe area, may find that the additional effectiveness from an LPF provided by this HPF, without any modification, will offer a distinct advantage. Relative voltage readings, taken by the detector at the output of the filter, confirm its ability to terminate HF harmonics into a 50-ohm load.

Acknowledgments

I wish to express my sincere appreciation to the Micrometals Corporation, W6NBI, N5AR, and K2SZE for their contributions, which made my work possible.

REFERENCES

1. Marv Gonsior, W6FR, "Low-pass Filter Performance," *Communications Quarterly*, Spring 1992, page 75.
2. Weinrich and Carroll, "Absorptive Filter for TV Harmonics," *QST*, November 1968, page 20.
3. "An Absorptive Filter," *The ARRL Handbook*, 1989 edition, page 40-9.
4. Filter program by Tim Murphy.

COMPARING MININECS

A guide to choosing an antenna optimization program

Although the MININEC code (currently Version 3, revision 13) serves as the basis for available commercial and non-commercial antenna modeling implementations, the resultant programs for amateur use show some significant differences. Consequently, no one program is best for all possible applications. Notices and advertisements for various MININEC enhancements do not give many clues as to which program may be best for an individual ham, regardless of whether he

or she is just exploring the possibilities of antenna modeling or is highly experienced with various forms of computer modeling.

Differences in programming and capabilities are both worth investigating. Ease of use and adequacy of results have no absolute criteria. Rather, each is application dependent. Therefore, in this user examination of three well-advertised versions of MININEC, I shall relate each evaluative remark to one or more applications. This procedure should preclude the

```

Free Space
14.175 MHz

Options

Field      » Total H V RC LC MaxLin MinLin AxialRatio
Segmentation Density      10 segments / halfwave
Auto Segment-Length Tapering  Off On
Frequency-Offset Correction  Off On
Bent-Wire Correction        Off On
X-Axis Pattern Symmetry     No Yes
2-D Pattern Resolution      1° 2° 4°
El Angle for Az Pattern     0.0°
Az Angle for El Pattern     0.0°
SWR Reference Impedance     50.0 Ω
Save Options & Settings     No Yes

Gain & F/B  View  Sources  2-D Plot  Antenna
Far Field  Edit  Frequency  3-D Plot  Options
Near Field Quit  Optimizer  RUN File  Colors

Enter Esc
  
```

Figure 1. AO's main menu with the "Options" menu overlaid.

though MININEC permits the modeling of elaborate ground structures, these models find use in only some of MININEC's calculations. This list of limitations is far from exhaustive.

Implementations of MININEC attempt to correct, compensate for, or overcome only some of these limitations. Thus far in the history of the code, wire segment ratios, angular antenna geometries, close-wire geometries, and frequency-related errors have been most subject to modifications of MININEC or to special antenna description procedures. At present, the remaining limitations appear to have one of two statuses: either they are not correctable within the limits proscribed when running MININEC on a PC, or the errors they introduce fall within the margins of model-to-reality variances inherent in amateur antenna modeling. Indeed, the best amateur antenna situation is filled with objects and conditions whose RF properties remain largely guesswork—even if we could model them.

Some MININEC program basics

MININEC is essentially a three-part program. In the first part, the user describes the antenna within a text editor. Key words and a carefully ordered input permit the second program part to recognize both variables and their values. The second part calculates most of the output values for the model, using the well-known method of moments and its requisite matrix. For a given model, the program calcu-

lates the impedances, mutual impedances, and currents at each pulse, centered on each wire segment junction. Specifying a source position and voltage or current, plus load values and positions, permits calculation of source impedances, SWR figures relative to a standard, and the remaining unknown—either source voltage or source current. Also calculable is gain in any direction in the sphere surrounding an antenna in free space or the hemisphere surrounding the antenna over ground, so long as one uses a standard, usually dBd or dBi. Both near field and far field electrical and magnetic components, along with polarization, are derivable, as well as total field values. From these numbers, one may obtain figures for such usual parameters as front-to-back ratio, front-to-side-lobe ratio, and beam width to the -3 dB points. Grounds may be perfect or may be one of many sets of conductivity and dielectric constant combinations. Antenna material losses for common substances, from copper to steel, can modify the calculations. The results are obtainable from a run or log file that compiles the values.

The third part of the program is a plotting portion that permits the user to obtain a graphic representation of antenna performance. Azimuth and elevation patterns, in either free space or over ground, permit visual inspection of lobe maxima and minima, thus giving an overall view of performance that may escape an inspection of data tables. Possible patterns include the common (sometimes called ARRL) logarithmic polar plot, the linear polar plot, and

```

ELNEC ver. 3.02 / MaxP option
(c) 1993 by Roy Lewallen, W7EL

TI TITLE:                edz yagi 2M 3/4" el
FR FREQUENCY:            144.5 MHz. (wavelength = 6.806721 ft.)

WI WIRES:                2 Wires                WL WIRE LOSS: Aluminum
SO SOURCES:              1 Source              UN UNITS:      Feet
LO LOADS:                1 Load
GT GROUND TYPE:          Real                  LAST FILE SVD/RCLD:
GD GND DESCRIPTION:      1 Medium, 0 Radials    D:\ELNEC\ZEPP\EDZYG2M.EN

PT PLOT TYPE:            Azimuth                AR ANAL RES:   1 Deg.
PA ELEVATION ANGLE:      0 Deg.                RF REFERENCE:  0 dBi
PR PLOT/TABLE RANGE:     0 - 360 Deg. (full)    SZ SWR Z0:     75 ohms
SS STEP SIZE:            5 Deg.
OR OUTER RING OF PLOT:   Automatic scaling
FI FIELD(S) TO PLOT:     Total field only

(BR)rowse file  (DE)lete, (RE)call, (SA)ve desc  (Freq S)wp  <RET> = Plot
(AN)alyze      (CU)rrents  (Load D)ata  (OP)tions  (Print D)esc  (Src D)ata
(TA)ble        (View A)ntenna  (EX)it pgm without saving desc  (QU)it

```

Figure 3. ELNEC's main screen with its network of selections.

 


Figure 4. A sample of AO's 3-D "solid" antenna pattern for a dipole.

a rectangular plot. In descending order, they provide a proportioned notion of maximum antenna achievement; in ascending order, they provide an increased ability to investigate fine detail of small radiation lobes.

The three parts of MININEC yield three different files for each antenna model: a description file, a running file, and a plot file. MININEC accumulates calculated data in successive stages; therefore, the running file may be subdivided into a number of more specific data files. These MININEC components have to a large measure determined the structure of commercial implementations.

AO and MN, for example, retain this structure rigorously. On AO, antenna modeling begins with the main menu. **Figure 1** is a screen print of the menu showing the "Options" screen overlaid in the normally blank space on the operating screen. To create an antenna, one must enter the text editor (TED), either using the "Edit" command or by calling up TED independently, and construct the model. The editor offers no help in ordering the elements or

in employing key words to cue the variable values. The user must keep the manual on hand, make up a cue card, or modify an existing antenna and save it under a new name. The last process is perhaps the most useful in AO, for two reasons. First, AO provides a large collection of models already set and plotted, so most common antennas can be described by changing values. Second, once the user has described either a complex antenna geometry or a complex set of ground conditions, saving these partial model descriptions reduces work with new model elements.

AM also uses a text editor for creating new antenna models. **Figure 2** displays the start of this process by showing the initial screen with the "File" function overlaid. In creating a description, AM's editor feature is bound into the operating and calculating module and does not permit the saving of a revised model under a new name from within the program. However, AM uses a dialogue box to set material, ground, and other basic factors, followed by a template for inserting the remaining values. (If one invokes the editor independently, it lacks the dialogue and template features.) This procedure reduces the need for a reference manual or cue card during the model description phase of the work, but it does not eliminate it—especially if one requires complex sources or loads. Both AO and AM permit the addition of noncalculation-related remarks and end notes for reference.

Both AO and AM keep a running log file (called RUN. in AO and [filename].LOG in AM) for calculations. Both fill and factor the MININEC matrix to produce mutual impedance values. At this point, AM proceeds to generate pattern values. AO prints impedance, wire loss, efficiency, gain, and front-to-back values before entering the pattern generation phase to derive values for angle of maximum radiation, beam width, and side lobe data. AM displays the entire collection at once. From here, both programs are ready to generate rapid antenna plots for viewing or printing. Both contain a command to combine these steps seamlessly, although the plot numbers go into a separate file. Numeric data—including a copy of the antenna description, the segment-to-segment location of pulses, a listing of currents at each pulse, and the noted output data—accumulate in the running log file.

ELNEC has a different method of operation, one that integrates all three MININEC program facets. ELNEC operation involves constant revision of a default file or the last file used in the previous session. **Figure 3** shows the network of data presented to the user. The user can recall from the provided models, or from models saved previously, a description nearest to

Parameter	ELNEC	AM	AO-1	AO-2
Antenna 1: 10 Meter dipole, #18 copper wire, 16.78', 10 segments/wire				
Free Space				
Gain (dBi)	2.050	2.05	2.05	2.04
Source (R±X)	71.8 + 0.01	71.8 + 1.15	71.8 + 0.0	72.4 + 3.2
B/W (degrees)	78	78.7	82	79
Real Ground: Cond.=5 mS/m; Dia. Const.=13; Height = 35'				
Gain (dBi)	7.654	7.65	7.65	7.64
TO Angle (degrees)	14	14	14	14
Source (R±X)	68.7 - 8.3	68.7 - 7.2	68.7 - 8.3	69.3 - 5.2
B/W (degrees)	80	79.9	80	80
Antenna 2: 2 Meter dipole, #18 copper wire, 3.289', 10 segments/wire				
Free Space				
Gain (dBi)	2.087	2.09	2.08	2.07
Source (R±X)	71.0 + 0.05	71.0 + 0.43	71.1 + 0.0	72.3 + 5.2
B/W (degrees)	78	78.7	79	79
Real Ground: Cond.=5 mS/m; Dia. Const.=13; Height = 35'				
Gain (dBi)	8.021	8.02	8.02	8.00
TO Angle (degrees)	3	3	3	3
Source (R±X)	69.3 + 0.61	69.3 + 1.01	69.4 + 0.5	70.6 + 5.8
B/W (degrees)	78	78.8	79	79
Antenna 3: 2 Meter dipole, 6061-T6 Aluminum, 3.196', 10 segments/wire				
Free Space				
Gain (dBi)	2.113	2.11	2.11	2.05
Source (R±X)	71.2 + 0.02	71.2 + 0.5	71.3 + 0.0	77.4 + 10.8
B/W (degrees)	78	78.9	79	79
Real Ground: Cond.=5 mS/m; Dia. Const.=13; Height = 35'				
Gain (dBi)	8.048	8.05	8.04	7.98
TO Angle (degrees)	3	3	3	3
Source (R±X)	69.6 + 0.83	69.6 + 0.86	69.7 + 0.8	75.7 + 11.7
B/W (degrees)	78	78.9	79	78

Table 1. Comparison of EL, AM, and AO for dipoles.

what is required. All variables appear on the main screen or one of the subscreens. Thus, reference manuals or cards are not required except when looking up specific values like the dielectric constant and conductivity for a particular type of soil. ELNEC saves nothing without orders from the user, except the last file of a session. The user specifies a file name within a subdirectory and can choose a new name for a model revision.

Subscreens in ELNEC for antenna wires, sources, and loads permit the deletion of excess items from the present record and the addition of "0" value items into which the user plugs appropriate values. Ground definition is per-

formed on a subscreen of its own. Antenna material, units of measure, and azimuth and elevation angles for plots appear on the main screen. The initiation of calculations produces matrix filling and current calculations, along with the creation of a graphics plot—unless the user specifically chooses a tabular output screen. ELNEC stores calculation results in various files, permitting screen or printer output of data subsets. Plots may be saved separately from the graphics screen. If the user saves an antenna description after calculations are completed, he or she has the option to save the matrix calculation results in a collection of files. However, one must save either all or none

Parameter	ELNEC	AM	AO-1	AO-2
Antenna 1: 3-element Yagi for 14.175 MHz (taken from AO file), 1" 6061-T6 Aluminum				
Free Space				
Gain (dBi)	7.988	7.99	7.97	8.04
Front-to-Back (dB)	25.115	25.24	24.91	28.14
Source (R±X)	27.3 - 1.12	27.3 - 0.98	27.5 - 1.1	26.5 + 4.6
B/W (degrees)	64	63.5	64	63
Run Time (seconds)	12	15	9	9
Real Ground: Cond.=5 mS/m; Dia. Const.=13; Height = 416"				
Gain (dBi)	12.167	12.16	12.15	12.18
TO Angle (degrees)	25	25	25	25
Front-to-Back (dB)	27.413	27.41	27.42	24.36
Source (R±X)	25.40 - 1.58	25.38 - 1.44	25.5 - 1.6	24.8 + 4.6
B/W (degrees)	66	65.7	66	65
Run Time (seconds)	20	40	30	30
Antenna 2: 3-element Yagi for 28.2 MHz; 1" 6061-T6 Aluminum				
Free Space				
Gain (dBi)	7.540	7.54	7.5	7.61
Front-to-Back (dB)	19.595	19.63	19.03	21.07
Source (R±X)	16.24 - 28.63	16.2 - 28.55	17.2 - 29.5	12.9 - 19.9
B/W (degrees)	64	64	65	64
Run Time (seconds)	20	15	15	15
Real Ground: Cond.=5 mS/m; Dia. Const.=13; Height = 35'				
Gain (dBi)	12.842	12.84	12.80	12.88
TO Angle (degrees)	14	14	14	14
Front-to-Back (dB)	24.145	24.19	23.25	25.47
Source (R±X)	15.7 - 27.8	15.7 - 27.7	16.6 - 28.7	12.7 - 19.1
B/W (degrees)	64	64.8	65	65
Run Time (seconds)	34	52	30	30

Table 2. Comparison of EL, AM, and AO for 3-element Yagis.

of these supplementary files. For complex geometries (for example, a fully tapered multi-element quad), this can run to over 100 KB of disk space per model.

These basic program descriptions do not exhaust the lists of program features, but simply give a flavor of the differences in programming style of each developer. AO remains perhaps the most traditionally structured of the MININEC implementations, but adds numerous individual calculation and graphic features. It offers the most field and graphic options, including rectangular coordinates and complete near and far field calculations and views. These even include a slow but impressive three-dimensional view of the total antenna field. See **Figure 4** for an example that plots a dipole in 3-D. K6STI has introduced modifications to the MININEC algorithms to correct for frequency-induced errors, to correct for bent-wire configurations (without the need for segment tapering), and to taper wire junction segments for adjoining

linear segments that surpass the recommended maximum length ratio. Evident is the author's focus upon single source horizontal antennas, as witnessed by recommendations for the use of free space as the fundamental modeling convention, the use of default voltage sources, and the use of dBd(ipole) as the default standard of antenna gain.

In contrast, ELNEC's integrated programming provides easy access to specific data on screen and in print. Additionally, it provides the most data-intensive graphic output. At the user's choice, one may include antenna analysis figures on the graphic itself and in a succinct chart printed below the graphic. ELNEC includes segment tapering for complex antenna geometries; the user can control the maximum and minimum lengths of the segments, but the program then creates the requisite wires automatically. With dB(i)sotropic) the gain standard and current sources the default, W7EL records his own focus upon phased vertical antenna

Frequency	Parameter	AM ¹	AO-2
14.000	Gain (dBi)	12.01	12.03
	Front-to-Back (dB)	19.10	23.63
	Source Impedance (R±X)	25.4 - 14.1	25.6 - 8.5
14.0025	Gain (dBi)	12.03	12.05
	Front-to-Back (dB)	20.40	25.24
	Source Impedance (R±X)	25.5 - 12.3	25.6 - 6.6
14.050	Gain (dBi)	12.06	12.07
	Front-to-Back (dB)	21.86	26.73
	Source Impedance (R±X)	25.6 - 10.6	25.5 - 4.8
14.075	Gain (dBi)	12.08	12.09
	Front-to-Back (dB)	23.37	27.72
	Source Impedance (R±X)	25.6 - 8.8	25.4 - 3.0
14.100	Gain (dBi)	12.10	12.11
	Front-to-Back (dB)	24.92	27.81 ²
	Source Impedance (R±X)	25.6 - 6.9	25.3 - 1.1
14.125	Gain (dBi)	12.12	12.14
	Front-to-Back (dB)	26.33	27.02
	Source Impedance (R±X)	25.6 - 5.1	25.1 - 0.7 ³
14.150	Gain (dBi)	12.14	12.16
	Front-to-Back (dB)	27.28	25.74
	Source Impedance (R±X)	25.5 - 3.3	25.0 + 2.6
14.175	Gain (dBi)	12.16	12.18
	Front-to-Back (dB)	27.41 ²	24.36
	Source Impedance (R±X)	25.4 - 1.4	24.8 + 4.6
14.200	Gain (dBi)	12.18	12.20
	Front-to-Back (dB)	26.70	23.03
	Source Impedance (R±X)	25.3 + 0.4 ³	24.6 + 6.5
14.225	Gain (dBi)	12.20	12.22
	Front-to-Back (dB)	25.52	21.81
	Source Impedance (R±X)	25.1 + 2.3	24.3 + 8.5
14.250	Gain (dBi)	12.22	12.24
	Front-to-Back (dB)	24.20	20.71
	Source Impedance (R±X)	24.9 + 4.2	24.1 + 10.5
14.275	Gain (dBi)	12.24	12.26
	Front-to-Back (dB)	22.92	19.70
	Source Impedance (R±X)	24.7 + 6.2	23.8 + 12.6
14.300	Gain (dBi)	12.26	12.28
	Front-to-Back (dB)	21.74	18.79
	Source Impedance (R±X)	24.5 + 8.2	23.5 + 14.6

Note 1. ELNEC and AM figures are too close to require separate listings.
Note 2. Point of maximum front-to-back ratio.
Note 3. Nearest point to self-resonance.

Table 3. Comparison of 3-element Yagi values from 14.00 to 14.30 MHz.

arrays erected over radial and ground systems requiring accurate specification.

AM shows no focus upon any particular antenna type, but rather a concern for programming itself. It incorporates structured menus in a top bar with "hot" function keys for frequently used operations. Its manual chapter on operations tracks the top bar menus, so the user will find it simple to create a reference card. The program has the operator feel of a spreadsheet

with touches of GUI interfaces. Although AM lacks any of the calculation compensation features of either ELNEC or AO, it includes a special graphics program to permit plotting patterns using the HPGL feature of the HP Laserjet III's PCL5 language, thus improving the printed output quality. It also includes a DOS shell to permit various operations without terminating the program.

Like the brochures for new cars, these basic

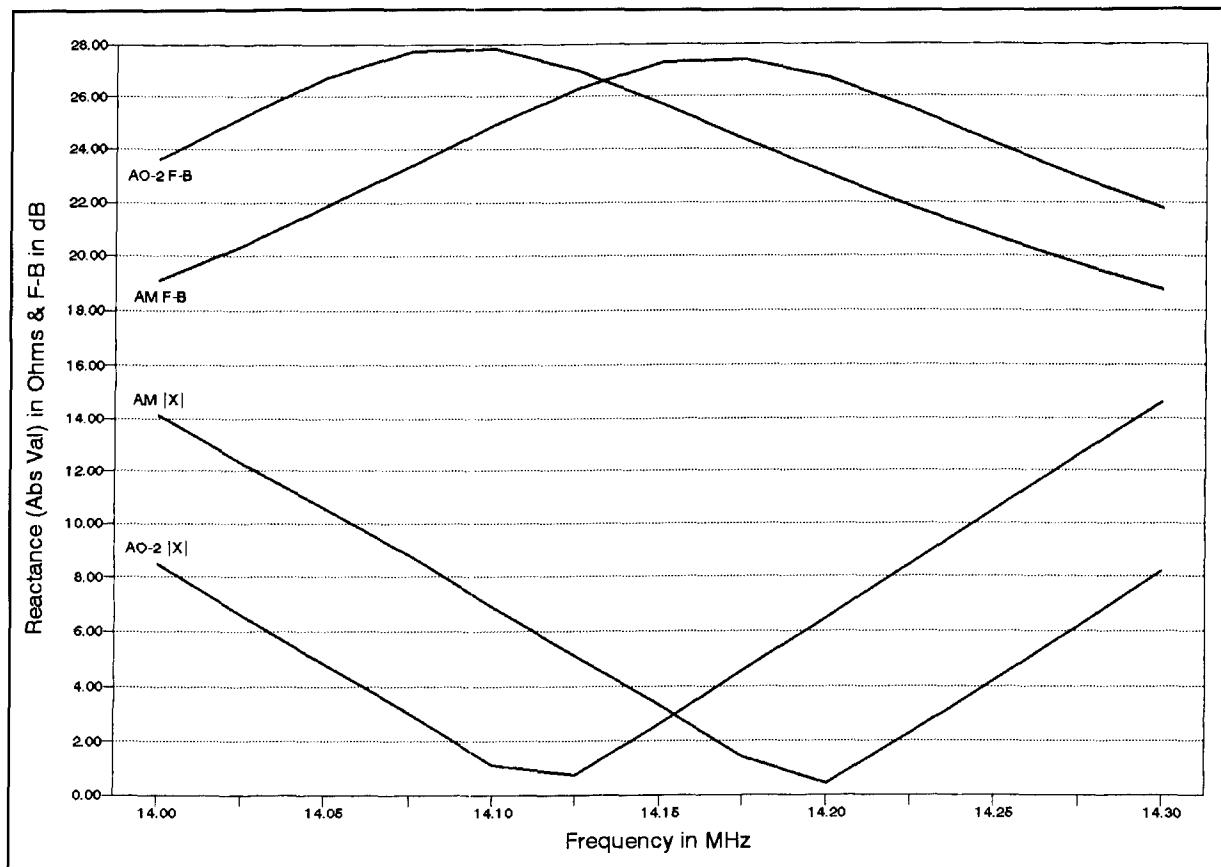


Figure 5. A graph of front-to-back ratios and absolute values of reactance for the 20-meter Yagi between 14.00 and 14.30 MHz as calculated by ELNEC and by AO with frequency correction.

descriptions of AO, ELNEC, and AM may spur some dreams about antenna modeling, but they cannot substitute for a test drive. Therefore, it's important to try out each of the programs: first to assess their technical competencies in various situations, and then to note operational advantages and limitations.

Technical competencies

There is very little the user can accomplish with one program that he or she cannot do with the others. After all, ELNEC, AO, and AM use and are subject to the limitations of the MININEC calculation machine. Technical competency within each program boils down to a matter of how well each performs the basic MININEC functions, and how well each overcomes some of its limits relative to various user tasks. For casual investigation of antenna properties, each produces approximations sufficiently close to empiric reality and the NEC2 standard.

However, many hams wish to study antennas and many wish to build antennas, and a few want to do both. This increases demand for precision. One source of imprecision within MININEC relates to frequency: as frequency increases

and the diameters of wire elements become a more significant percentage of a wavelength, basic MININEC calculations begin to depart from the demands of the real world. AO (and MN) contain correction factors within their calculational schemes to compensate for these errors. ELNEC and AM do not. The significance of the output difference deserved a test. **Tables 1** through **6** contain the results of some initial runs, both in free space and over real ground. All runs were made on a 80386SX computer running under DOS 5.0 at 20 MHz with 4 MB of RAM under QEMM 6.02 control to clear calculation space, with 160 MB of hard disk to absorb created files. Any run times noted are relative to this test set-up.

Table 1 lists three dipoles. The first is a 10-meter wire model, the second a 2-meter wire model, and the third a 2-meter aluminum tube model. The AO1 and AO2 columns represent modeling without and with the correction factors turned on. ELNEC and AM results are consistently close; variations are the result of either the order of operations or the fixed values of certain constants, for example, pi or the speed of "light" (electromagnetic radiation in a vacuum). The wire dipoles, even at 2 meters, show

too little difference under any condition to merit distinction. Attaching the wire to end insulators will likely create more variance from the models than the amount of difference created by the frequency correction factor in AO. Differences of greater significance begin to show up with the 1-inch aluminum tube model. While the gain in dBi and the resistive component of the input impedance fall well within operational margins, the inductive reactance shown in AO2 suggests that raw MININEC may call for unduly long fat elements at VHF.

Table 2 tests more complex antennas, namely, 3-element Yagis. A 20-meter beam, taken from a file supplied by AO and slightly modified for this test, reveals that 14 MHz does not significantly display the frequency error. However, when the design is tested across a span of frequencies (refer to **Table 3** and **Figure 5**), the effects of the difference between corrected AO and raw MININEC begin to appear even at 20 meters. Various parameters

show an approximate 75 kHz displacement, with corrected AO assigning them the lower frequency. Determining whether the displacement precision exceeds amateur construction abilities would require empirical tests beyond the capabilities of my shop.

The 10-meter Yagi also shows little specific frequency effect that goes beyond the margins imposed by building technique, surrounding terrain, and other normally unmodeled effects. However, an interesting arithmetic pattern begins to emerge. Compared to raw MININEC, models optimized initially in corrected AO typically show higher gains, lower front-to-back ratios, lower resistive source impedances, and more inductively reactive source impedances. However, while the results for ELNEC and AM are quite tightly clustered, uncorrected AO begins to depart from the cluster—usually in a direction opposite that of corrected AO.

Nonstandard antennas offer another test of the correction factor. Arrays and parasitic

Parameter	ELNEC	AM	AO-1	AO-2
Antenna 1: 2-element EDZ for 28.5 MHz, 180-degree phase-fed: #18 Copper wire				
Free Space				
Gain (dBi)	7.779	7.79	7.78	7.78
Source (R±X) (x2)	22.51 - 741	22.25 - 736	22.3 - 737	21.9 - 726
B/W (degrees)	30	29.8	30	30
Run Time (seconds)	27	15	35	35
Real Ground: Cond.=5 mS/m; Dia. Const.=13; Height = 35'				
Gain (dBi)	12.894	12.9	12.90	12.89
TO Angle (degrees)	13	13	13	13
Source (R±X) (x2)	23.00 - 740	22.7 - 737	22.8 - 737	22.4 - 726
B/W (degrees)	30	30.4	30	30
Run Time (seconds)	62	94	122	122
Antenna 2: 2-element Yagi EDZ for 144.5 MHz, 0.75" 6061-T6 Aluminum				
Free Space				
Reflector Load (Ω)	305	305	305	280
Gain (dBi)	9.199	9.2	9.23	9.04
Front-to-Back (dB)	22.246	22.27	22.01	22.60
Source (R±X)	50.61 - 289.6	50.63 - 289.6	51.2 - 293	48.7 - 267
B/W (degrees)	32	31.5	31	31
Run Time (seconds)	43	29	45	45
Real Ground: Cond.=5 mS/m; Dia. Const.=13; Height = 35'				
Reflector Load (Ω)	300	300	300	275
Gain (dBi)	15.196	15.19	15.23	15.05
TO Angle (degrees)	3	3	3	3
Front-to-Back (dB)	22.390	22.42	22.11	22.64
Source (R±X)	49.96 - 291.2	49.98 - 291.1	50.5 - 294	48.0 - 268
B/W (degrees)	32	31.4	31	31
Run Time (seconds)	80	90	137	137

Table 4. Comparison of EL, AM, and AO for Multi-Element Extended Double Zepps.

Parameter	ELNEC ¹	AM ²	AO-1 ³	AO-2 ⁴
2-element Quad, 28.5 MHz, #18 copper (Elements: 990/f & 1037/f at 0.25 wavelength spacing)				
Free Space				
Gain (dBi)	7.252	7.45	7.32	7.25
Front-to-Back (dB)	19.580	14.86	18.70	20.87
Source (R±X)	88.61 + 4.68	74.5 - 13.9	85.1 - 1.9	90.1 + 3.5
B/W (degrees)	72	71.9	73	73
Run Time (minutes)	4:03	7:12	1:34	1:34
Real Ground: Cond.=5 mS/m; Dia. Const.=13; Height = 35'				
Gain (dBi)	12.443	12.62	12.50	12.44
TO Angle (degrees)	13	13	13	13
Front-to-Back (dB)	17.924	14.38	17.37	18.82
Source (R±X)	91.89 + 7.69	76.7 -11.71.1	88.2 + 1.0	93.7 + 6.6
B/W (degrees)	74	72.2	73	73
Run Time (minutes)	6:53	11:57	7:31	7:31
Note 1. ELNEC model used fully tapered elements for 104 total segments.				
Note 2. Antenna Model was tested at increasing numbers of segments, with an arbitrary cut-off (due to run times) of 24/side.				
Note 3. AO without bent-wire correction factors used 22 segments per half wavelength.				
Note 4. AO with bent-wire correction factors approached good convergence with ELNEC at 20 wires per half wavelength (10 per side). Over ground calculation time, minus the pattern generation necessary to determine beamwidth and proper angle for maximum gain, was 1:01 minutes. However, the take-off angle was known in advance, precluding the need for a second run, the first to find the proper elevation angle and the second to determine the horizontal bandwidth at that angle.				

Table 5. Comparison of EL, AM, and AO for a 2-element quad.

beams based upon extended double Zepp elements form the basis for **Table 4**. The wire array of the 180-degree phase-fed antenna again demonstrates the minimal effect of frequency upon thin wires: all the antennas are well clustered in every dimension calculated. The 2-element EDZ parasitic beam, however, tells a different story. The principles behind the antenna were first brought to my attention by Brian Egan, ZL1LE. The 3/4-inch diameter aluminum model for potential 2-meter use employs close (1/8-wavelength) spacing for mechanical reasons, and comes in at just over 8 feet from end-to-end. The reflector element requires a loading inductance, hand optimized to the nearest 5 ohms in all the models. Again, ELNEC and AM produce tightly clustered models. Frequency-corrected AO gives results that depart from the original model. Because the EDZ Yagi is purposely nonself-resonant, dimensions could be held constant, and the reflector loading varied for optimum potential performance. Again, corrected AO suggests that this "fat" element antenna is longer than raw MININEC would suggest. The requisite inductive loading to compensate for the capaci-

tive component of the reflector is lower, as is the capacitive reactance at the feed point. (As the length of an EDZ, about 1.25 wavelengths, increases, capacitive reactance at a center feed-point decreases.) Nonetheless, the uncorrected AO shows the minor arithmetical properties noted above relative to the tightly clustered ELNEC and AM results.

Table 5 shows some results for a 2-element quad design. Raw MININEC requires some extensive help to model nonlinear elements. Complex geometries with angles, especially right or acute angles, cut off parts of the antennas at the corners due to the placement of pulses. There are two ways to overcome this difficulty. One is to introduce a bent wire correction factor, as AO has done. The other is to develop a means of tapering the length of wire segments so they are very short (but within the rules) at the apex of the angles. ELNEC has adopted this technique, providing a routine that puts the minimum and maximum length of wire segments under operator control (with suggested default values), but which then performs the tapering automatically.

ELNEC quad models with fully tapered ele-

ments are large—104 total segments in the 10-meter example. The free space model required a bit over 4 minutes to run, while the real-ground model needed nearly 7 minutes. However, without either tapering or a correction factor, AM was still far from convergent with either ELNEC or AO at 24 segments per side or 192 total segments. Even with 24 segments per side, the corner segments were about twice the length of the fully tapered ELNEC corner elements. (However, AM handled 192 segments without need for program supplements.) The AM run took nearly 7 minutes for free space and 12 minutes over real ground. ELNEC's tapering produced a model that appears to agree closely with a similar antenna empirically derived long ago by Bill Orr, W6SAI.⁵ The spacing of this model was increased for greater bandwidth, and the reflector circumference was increased to remove the stub in the original model.

In contrast to ELNEC's provision for tapering segment lengths, AO uses a bent wire cor-

rection factor in the calculations. The manual recommends the use of 16 segments per half wavelength for quads and 20 segments per half wavelength for deltas. However, for this quad model, AO converged most closely with ELNEC's tapered elements at 20 segments per half wavelength, suggesting the use of even more for delta beams. ELNEC's 104-segment model and AO's 80-segment model, although not as tightly clustered arithmetically as linear antenna models, likely exceed the ability of any builder to differentiate.

Whether AO performs its calculations faster or slower than ELNEC depends upon the user's situation. All free space AO quad models run faster than their ELNEC cousins by better than a 2 to 1 margin—even allowing for the pattern generation that precedes calculation of beamwidth. Real ground models, however, will be faster or slower depending upon the data the user needs. Because AO produces an azimuth pattern before an elevation pattern, and since

Parameter:	Gain dBi	F-B Ratio dB	Source 1 R ± X	Source 2 R ± X	Run Time Min:Sec
Antenna #1: 10-meter folded dipole: L = 16.5'; Dipole wire = 1" spacing; Real ground (Cond.=5 mS/m; Dia. Const.=13); Height = 20'					
AM: 40 segments per 1/2 wavelength (84 total segments)	8.18	---	227.5 - 17.7	---	2:00
AO: 4 wires, 34 pulses autotapered	8.09	---	229 + 22	---	2:10*
*Run time doubled to over 4 min, due to requirement for a first run to find elevation angle of maximum radiation.					
ELNEC:					
No taper: 4 wires, 24 segments					
a. Without parallel correction	7.970	---	28.0 -194.0		:19
b. With parallel correction	8.104	---	224.0 + 40.1		:19
Full taper: 24 wires, 38 segments	8.119	---	227.4 + 12.2		:51
Antenna #2: 10-meter W7EL Field Day Special: 2 folded dipoles 135-degree phase-fed; L = 16.16'; Dipole wires = 1" spacing; Elements spacing = 4.27'; Real ground (Cond.=5 mS/m; Dia. Const.=13); Height = 20'					
ELNEC:					
No taper: 8 wires, 48 segments					
a. Without parallel correction	11.182	4.724	29.9 -172.6	- 5.2 -180.2	1:13
b. With parallel correction	11.647	24.231	99.8 + 97.1	80.5 -168.8	1:13
Full taper: 48 wires, 76 segments	11.669	25.328	108.1 + 72.2	69.7 -188.6	3:30

Table 6. Comparison of EL, AM, and AO for a folded dipole.

```

----- WIRBS -----
Wire Conn. --- End 1 (x,y,z : ft) Conn. --- End 2 (x,y,z : ft) Dia(in) Seg
1          -5.230, -8.670, 35.000 W2E1 -5.230, -6.000, 35.000 8.75E-01 2
2 W1E2     -5.230, -6.000, 35.000 W3E1 -5.230,  6.000, 35.000 1.00E+00 8
3 W2E2     -5.230,  6.000, 35.000      -5.230,  8.670, 35.000 8.75E-01 2
4          0.000, -8.310, 35.000 W5E1  0.000, -6.000, 35.000 8.75E-01 2
5 W4E2     0.000, -6.000, 35.000 W6E1  0.000,  6.000, 35.000 1.00E+00 8
6 W5E2     0.000,  6.000, 35.000      0.000,  8.310, 35.000 8.75E-01 2
7          3.490, -8.130, 35.000 W8E1  3.490, -6.000, 35.000 8.75E-01 2
8 W7E2     3.490, -6.000, 35.000 W9E1  3.490,  6.000, 35.000 1.00E+00 8
9 W8E2     3.490,  6.000, 35.000      3.490,  8.130, 35.000 8.75E-01 2
                                         Tot segs: 36

End 1 (x, y, z in ft.; conn.; or length)?

[x],[y],[z] = Coordinates (leave coord blank for no change)
W#E! = Conn. to end ! of wire #      RA# = Rotate azimuth # deg. (+ccw)
L# = Change length to #              RE# = Rotate elev. # deg. (+up)
L+#, L-# = Change length by #

Preserve Connections = OFF                <ESC> = done (terminate entry)

```

Figure 6. A typical wires subscreen from ELNEC, with wire 4 ready for modification.

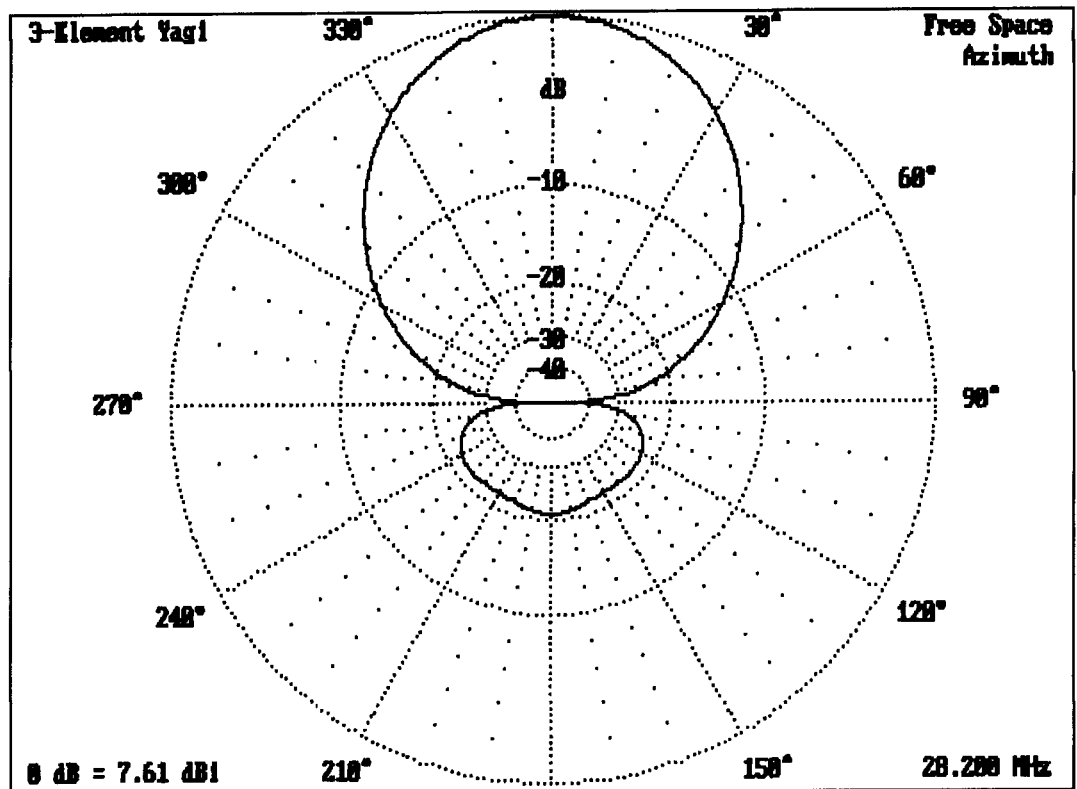


Figure 7. Pattern for a 10-meter 3-element Yagi as plotted by AO.

the latter pattern identifies the take-off angle—that is, the angle of maximum radiation—one often needs to make two pattern runs before obtaining maximum gain and front-to-back figures. The matrix fill and factor task took about a minute, but pattern generation required another five minutes to complete. Doubled, the time

for full data approached the largest run time encountered for AM. (AM, incidentally, precedes the azimuth pattern generation with an elevation run, thus identifying the take-off angle and setting the azimuth pattern to this angle. In ELNEC, one selects the initial pattern, usually elevation over ground, and quickly

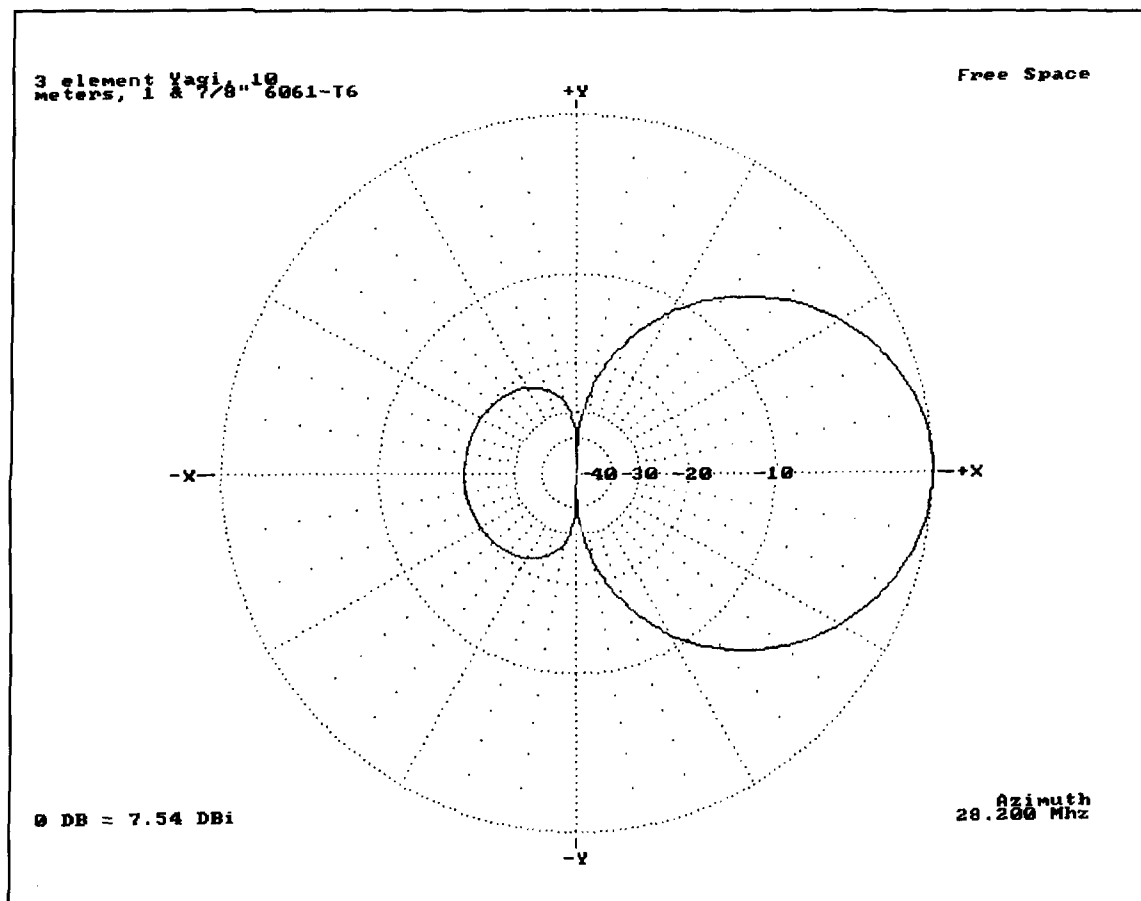


Figure 8. Pattern for a 10-meter 3-element Yagi as plotted by AM.

determines the take-off angle to use for the azimuth pattern from which is derived front-to-back and side-lobe figures.)

One complex geometry problem involves antennas that use closely spaced parallel wires. As a test of the performance of the three programs on this sort of structure, I modeled a 10-meter folded dipole. **Table 6** shows the results. To arrive at a usable result, AM employs the brute force technique of simply increasing the number of wire segments: 84 in all. AO uses an automatic segment-length tapering feature for such geometries. ELNEC provides two methods. One is full element tapering, as used with the quad. This accurate but slow technique is supplemented in the most recent version (3.02) with a close parallel wire correction algorithm that requires no increase in the number of wire segments per half wavelength. Comparative figures are shown in the table with and without the correction feature turned on, along with numbers for a fully tapered version of the same model. The dramatic speed increase allows more efficient model development, with the taper feature available for spot checks to ensure accuracy. Although the feedpoint resistance is similar in all four cases (AM, AO-taper,

ELNEC-wire correction, and ELNEC-taper), the drift in the reactance figure reflects the differences in the techniques used by each program to achieve functional results.

To further test the difference between tapering and close-wire correcting in ELNEC, I modeled a scaled version of W7EL's Field Day Special (a cousin of the ZL Special). The differences in source reactance appear again, along with a difference in the resistive component of the rear element source impedance. Nevertheless, the 3-to-1 modeling speed increase shows the benefits of implementing corrections in calculation algorithms rather than in user modeling techniques.

Calculation speed may not be the decisive factor in overall program performance. While AO calculates the fastest free space complex antennas, with or without the symmetry shortcuts, it requires one to know or guess the take-off angle to match ELNEC over real ground. Without either the tapered element or bent-wire techniques used by its MININEC relatives, AM requires an exceptionally large number of wires in antennas with complex geometries in order to converge with results from the other two programs. Nonetheless, there are a number of

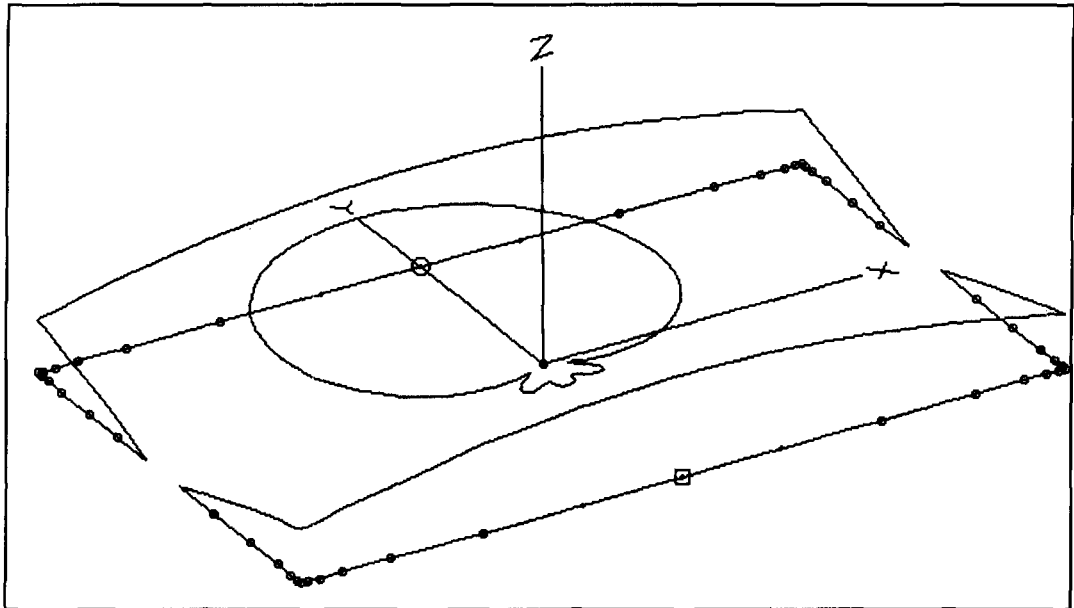


Figure 9. A sample antenna view graphic from ELNEC; AO's graphics are quite similar (without the azimuth pattern). Shown is the antenna, wire segments, source, load, current, and the azimuth pattern. AM supports a 3-D antenna view without current distribution or pattern graphics.

noncalculational factors that contribute to a program's suitability. We might think of these as resulting in an overall efficiency of performance for particular kinds of tasks rather than as raw calculation speed alone. Most of these factors belong in the category of user essentials and conveniences.

Operating conveniences

Program structure features fall into several separable categories. You can skip over those of no relevance to your proposed operation.

Antenna Set-up: There is no single best way to set up an antenna description. However, the three programs do offer some variations that the user can adapt to different situations. With these variations come some limitations.

ELNEC offers a wire subscreen for setting the X, Y, and Z coordinates of the pieces of the antenna elements. All entries are numeric, with some pleasant shortcuts. For example, for a quad, one need only specify a starting point set of coordinates. From there, using wire lengths, angles of rotation, and designators such as "Wire 1, End 2," it is possible to construct the remainder of the antenna. These mechanisms are handy for delta beams and other antennas with complex geometries, where a nonlinear intersection might result in a failure of wires to meet by an imperceptible amount. **Figure 6** shows a typical wire screen in the process of adjusting wire 4. For complex antenna geometries, ELNEC offers a "wire group" feature that permits simultaneous variation of selected para-

meters on a subset of the total number of antenna wires. This feature fulfills essentially the same function as the use of variables in AO and AM, which retain the text-editor antenna description technique of MININEC itself.

ELNEC once used a triple-plane view of the antenna to check one's work, but version 3.02 now offers a three-dimensional graphic view of the antenna, its current pattern, and its total field (if the antenna is viewed after calculations). Antennas can use either the X or Y axis for their lobe of greatest gain without slowing calculations or losing any analytical data.

To take advantage of symmetry in free space to speed calculations by simply mirror-imaging half the antenna, AM and AO require that the main lobe follow the X-axis.⁶ Interestingly, AO plots place the X-axis 0-degree point at the top of the page, while AM places that point to the right, as illustrated in **Figures 7** and **8**. The use of symmetry invokes some antenna set-up restrictions, which are slightly different for each program. The feature shuts itself off over ground. Moreover, both AM and AO permit the use of symbols as variables or place holders in the wire X-Y-Z layout, with a table of equations to tell the program what numeric values to use. Changing antenna element lengths, spacing, and diameters—as well as the number of segments per element—thus becomes a simple matter of changing the value of one or more symbols. AO's symbolic power appears stronger than AM's, because AO allows the use of complex formulae. AO also permits wire rotation for constructing complex geometries. In contrast, AM offers an on-screen calculator whose values can

be spliced into the antenna description, even if the numbers have more significant digits than the display has places to show them. Like ELNEC, both AM and AO offer three-dimensional views of the antenna geometry. **Figure 9** shows a graphic antenna view from ELNEC, but AO is quite similar. AM's geometry view lacks the display of currents.

AO and AM antenna description files can be used with both programs with only minor modifications to satisfy each program's particular limitations and rules. **Figure 10** shows an AO description file set out in symbolic dimensions and fully annotated. Very little change would be needed to run it on AM. In both programs, description files are simple ASCII enumerations of variables and values. Pattern plotting files are fully transportable between AO and AM simply by changing the extensions in the filenames (.PLT vs. .PAT). ELNEC's integration in the form of a compiled BASIC program also puts its description and plot files in non-ASCII form, effectively precluding intercommunication.

Printing: Of all the packages, ELNEC offers the most convenience in producing select printed outputs from various modes of analysis. Its graphic output screen (a "Print Screen" function) prints the selected pattern in one of sever-

al forms chosen either in the options shell or on the fly. One can set the polar patterns for either linear or logarithmic scales and choose to include or exclude border data. One can also let the key analytic factors appear on the pattern for quick reference or appear only in a box below the pattern. In this way, most key data, except the detailed antenna description, appear on a single sheet, as illustrated in **Figure 11**. In addition, separate screen and printer readouts are available for the antenna description, a table of currents, the source data, and the analysis. This selectivity allows the user to commit only needed data to paper. Despite this versatility, ELNEC has one odd shortcoming: no error trapping on print requests. A printer error during a run will crash the program, forcing the user to restart and find the "LAST" file to resume operations.

With the exception of the graphic output, neither AM nor AO offer sophisticated print options. AO requires a batch file containing certain SET functions for printer selection at start-up. Not all the instruction sets work with supposedly compatible printers.⁷ Print control uses no page end instruction, but relies on the operator to control the printer. All data (including a detailed antenna description and the cal-

```

2-Element Yagi for 10-meters
free space symmetric
28.20 MHz
8 wires, feet
sea = 4
seb = 8
dia = .875"
dib = 1"
ht = 0
sp = -4.25'
c = 6'
de = 7.833'
re = 8.750'
sea 0 -de ht 0 -c ht dia
seb 0 -c ht 0 0 ht dib
seb 0 0 ht 0 c ht dib
sea 0 c ht 0 de ht dia
sea sp -re ht sp -c ht dia
seb sp -c ht sp 0 ht dib
seb sp 0 ht sp c ht dib
sea sp c ht sp re ht dia

1 source
Wire 3, endl 1 0

;antenna title
;environment/ground description
;frequency
;# wires, units of measure
;symbol definitions
;sea/b = # segments
;dia/b = element diameters

;ht = height
;sp = spacing
;c = fixed center section length
;de = driven element length
;re = reflector element length
; wire chart

;# sources (default = voltage)
;placement of source, value, phase

;from Bill Orr, "A Compact 2-Element Yagi for 10 Meters,"
CQ, Dec., 1990, pp. 83-84.

```

Figure 10. An annotated AO antenna description with symbolic dimensions, easily modified for use in AM.

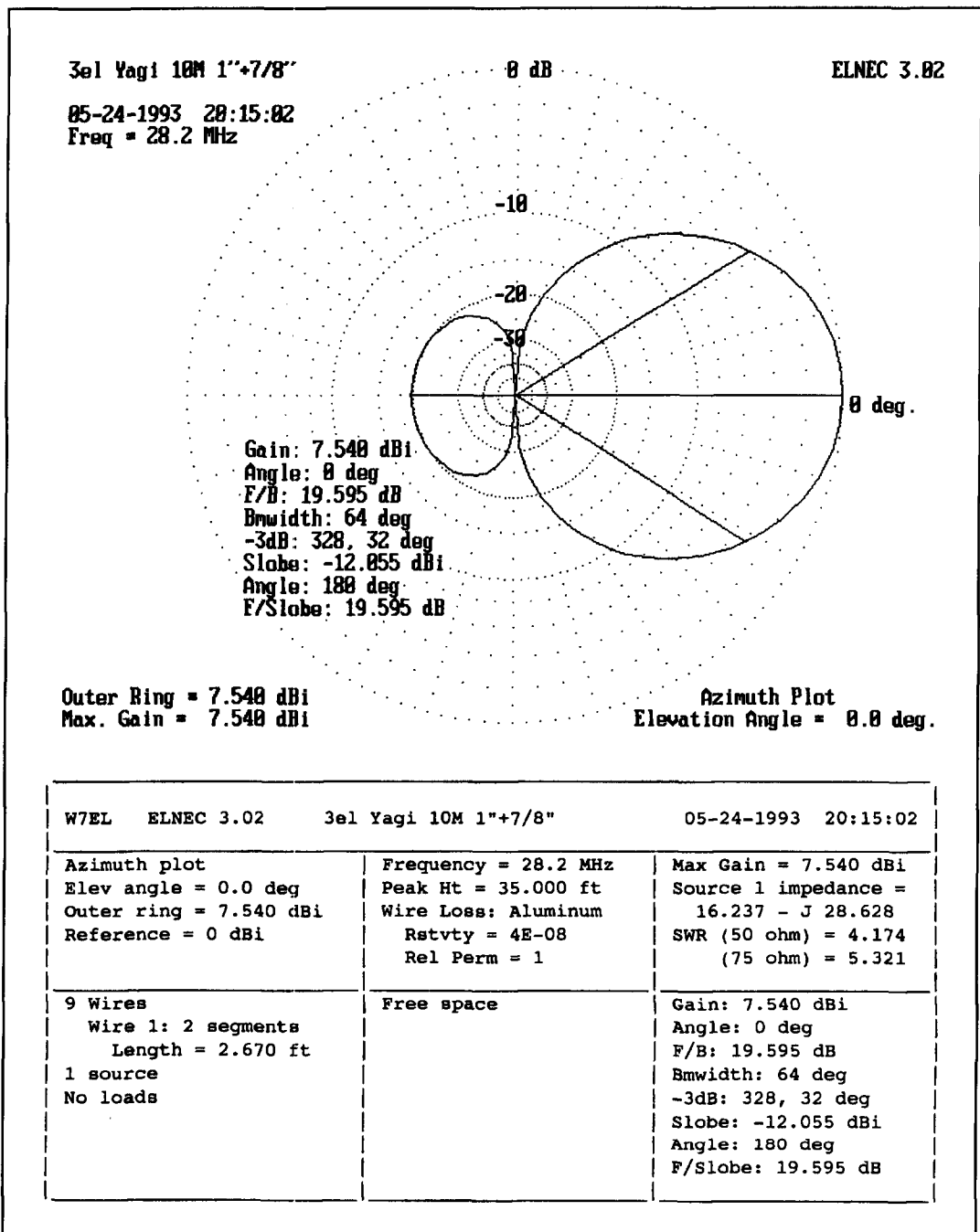


Figure 11. Pattern for a 10-meter 3-element Yagi as plotted by ELNEC.

culations required) appears in the RUN. file. One can print the log screen-by-screen. To save or print the RUN. file as a unit, the user must exit AO and work from DOS. To save collected data, one must print the RUN. file or rename it for disk storage, because the program will overwrite it during the next modeling session. To edit the file to remove unneeded information, one must run the ASCII file through a text editor, such as the TED program supplied for antenna descriptions.

Like AO, AM collects its data in a file with

the extension .LOG. This file is unique to the model and bears the same filename. It can only be overwritten if one uses the same model file in a new session. AM contains a DOS shell that permits copying and printing of the file as a unit without fully departing the program. However, for many purposes, AM log files require extensive manipulation. For example, tables of currents are useful as a check on the sensibleness of the antenna description, but lose their relevance as one makes slight adjustments in various parameters, like element length, fre-

quency, load value, etc. However, AM creates a new current table with every manipulation that requires a refiguring of the matrix, and each dutifully enters into the log. An unreviewed log gave me 17 pages of data that yielded less than 4 pages of needed data after editing within the separately run AE editor that AM uses for antenna descriptions.

If screen review of data suffices for a high percentage of your MININEC use, then the printing inconveniences of AO and AM are at most minor. However, many applications require paper data for study away from the computer screen. With the exception of files generated under frequency sweep, ELNEC offers more efficient generation of select paper than either of the other two programs.

For plot printing, AM offers two methods. Patterns may come from the on-line printing function, which appears to be quicker on a Laserjet than the screen prints of AO and ELNEC. AM also includes a separate program for employing the HPGL feature of the PCL5 HP Laserjet language to produce plotted graphics on Laserjet III's. Plotted outputs free the

printer from dot-to-pixel correlations that produce the inexact curves shown in all the sample azimuth pattern figures. Rectangular plots require less than 1 MB of printer memory, but polar plots require at least 1 MB of added optional memory. **Figure 12** provides an example of the superb, truly camera-ready AM graphics plots. AO plots are also printable in plot form, but require a separate program from another vendor. Both AO and AM offer rectangular graphic plots as well as the more usual polar plots, and are capable of displaying and printing subfields of the total far field usually seen in antenna pattern plots. All three programs offer the potential for overlaying plots for comparison, and the resultant complex graphics are printable.

Parameter Changes: With antenna models, the user almost always wants to modify one or more variables in order to view the resultant pattern or calculated values. The programs offer different methods of performing the changes.

With AO, one may change any factor by revising the antenna description using the edit feature. This results in a permanent file revision

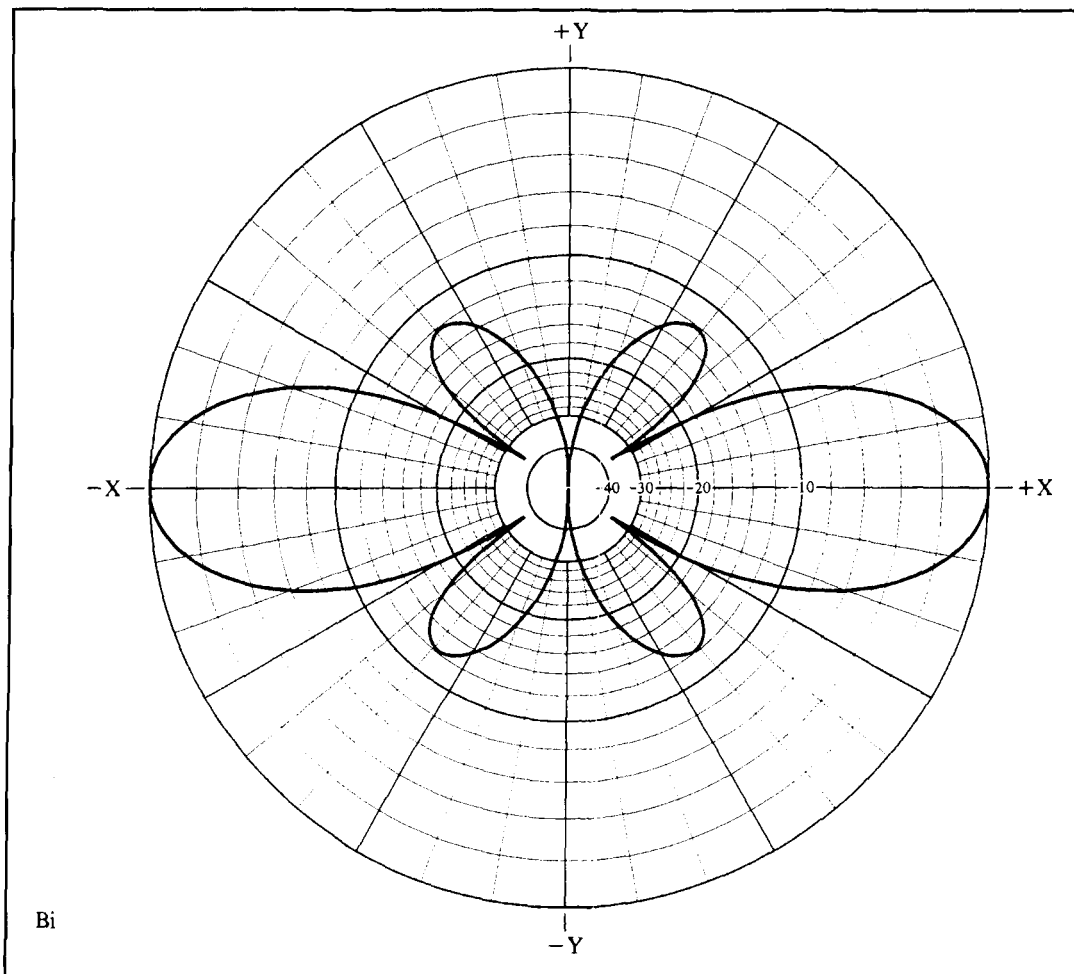


Figure 12. A sample HPGL graphics plot from AM's Antenna Draw.

and a recuing of the RUN. file. From the main menu, the user can perform a frequency sweep over almost any range with any step increment. When run with the "Gain & F/B" instruction, the program produces impedance, efficiency, gain, and front-to-back figures at the current azimuth angle—in other words, prepattern-generation data. The resultant addition to the RUN. file is a compact and easily scanned data collection. In addition, the user can change source specifications from the main menu and also enter into a versatile Options screen, shown with the main menu in **Figure 1**. Among the especially useful options to alter are the segment density to check convergence, the azimuth angle for polar plots and figures, and the toggling of the correction factors built into the program. One caution is necessary: there are 1, 2, and 4-degree options for the generation of patterns. Use the 4-degree setting only in free space. Over real ground, the program will only identify the take-off angle at one of the 4-degree points, without interpolation. Over ground, use the 1-degree selection. (In contrast, unless an elevation pattern has many lobes per pattern step unit, ELNEC will correctly identify the elevation angle, even at 5 degrees per step.)

AM offers a much larger menu of in-flight changes. Without changing the antenna description, the user can modify the sources and loads. One can also move between free space modeling and over-ground modeling by using the menu to change the environment. This can save file storage space by using one free space description per antenna and setting up ground situations, including antenna height above ground, on the go. Or, if the ground model is sufficiently fundamental, one can put it in the antenna description file and make a check run in free space as the final entry in the running log. (AM includes a soil table and calculator in its program for help in setting up both ground conditions and antenna dimensions.) The user can also change frequency, but the AO frequency-sweep provision is not present. Thus, AM creates a new current table in the log for each new frequency, inflating the running log.

Because ELNEC uses a permanent antenna description editor as its menu screen, all changes are quickly accessible. However, as noted earlier, nothing is saved without a save order, but overwritten by subsequent changes. Since select results are available on screen or in print after each run, collecting data for later use requires a different procedure. Instead of letting data accumulate in a running log, the ELNEC user looks at or prints out data on the run. With a dot matrix printer of insignificant memory, this can interrupt operations, but with a laser printer, the interruption is only momentary. For antennas with complex geometries and longer

run times, studying printed output during a subsequent calculation period allows the user to develop modification strategies within a single modeling session.

An exception to this rule is ELNEC's frequency sweep provision, new to version 3. This special subscreen permits the user to select data to be accumulated in the special run files. One can choose to save plot traces, MicroSmith-compatible files, and regular data collections. By dividing the collections into groups, including source data, load data, pattern table, currents table, and antenna analysis, ELNEC lets the user customize data collection to application needs. However, frequency sweep data files may be scanned but not printed from within ELNEC. Paper copies require a return to DOS or other ASCII-printing programs.

Repetitive Operations: Except for the new frequency-sweep feature, ELNEC is essentially a real-time program requiring user keyboard input for each desired change, whether one is moving from one model to the next or merely making changes in the present model. In contrast, AO offers a provision for batch file operation in addition to its frequency sweep feature. A DOS start-up file can specify a number of files to run in a single unmonitored session, including copying the resultant RUN. file under another name before proceeding to the next job.

More versatile are AM's batch or auto-run provisions, which can make use of menu items for each step in a repetitive process. AM's editor contains specific provisions for construction of auto-run controller files. Virtually all the function keys and the submenu selections are available. Most significant for simple but highly repetitive operations may be the "Change" options that include sources, loads, frequency, height, and environment (ground). Applications are numerous. For example, one might run an antenna through a series of height changes in small increments to check performance and source impedance between, say, a half wavelength to one and a half wavelengths in altitude.⁸ The output will be a collection of data that the text editor can boil down into more tabular form. Alternatively, one might change the loading of a given antenna in small increments, seeking out the optimal load for maximum performance (however defined). Or, one might change the source position of an off-center fed antenna in small increments to find the optimal position (again, however that position might be defined). One can simulate AO's frequency sweep through the batch mode operation of AM. As with all unattended operational methods, try a small batch file first to check for smooth operation before starting an all-night run that interrupts itself on an error just as you fall asleep.

These comparisons do not cover anywhere near all the program features available in each of the commercial versions of MININEC. Details regarding the specific attributes of each system require close reading of the manuals. AM provides a 132-page printed manual with excellent illustrations. ELNEC's on-line manual (excluding added pages for the MaxP function), with an excellent starter tutorial, has grown to over 110 pages (over 216 KB on disk) of instruction and information. The 50-page AO manual (excluding additional pages for optimizer operation) also provides good information for the new modeler. If program selection requires attention to more detailed information than is presented here, borrowing manuals for close reading is the next step in the process.

Conclusions

Program efficiency is a far cry from calculation speed alone. To be efficient, a program needs to have at fingertip control all the possibilities required by particular applications. No program designer can anticipate these fully. Moreover, most enhanced versions of MININEC have been produced by amateurs out of their own curiosity and interest, and their main correspondents are likely to have been those with relatively similar interests. Thus, it is natural that the three most commercially advertised versions of MININEC examined here offer a mixture of advantage and disadvantage to the individual user.

Rather than repeat the ups and downs related to diverse tasks, let me close with an exercise every reader can reproduce from his or her own perspective. What would I include in my ideal version of MININEC (had I the ability, which I do not)? From ELNEC, I would take the menu-driven operation. Student learning curves might be steeper with this feature. Also from ELNEC, I would retain the instant and separated data print feature and the possibility for plot prints with maximum data attached. Without doubt, the versatility of element construction would be useful, as would the element tapering and the close-parallel-wire correction provisions. Incidentally, I would also retain the ability to place sources and loads as a percentage of element length, rather than having only end, center, or pulse number options.

Frequency sweep is a must in my ideal program for checking antennas across a band. ELNEC's or AO's version both work fine, although I would like to print the resultant files from within the program. From AO, I would want the calculation correction features at my command. Lest these be slighted by this compact request, they include adjacent wire taper-

Explanation of Parameters in Tables

1. EL = ELNEC 3.02; AM = Antenna Model 1.02; AO = Antenna Optimizer 5.0, an extension of MN. AO1 provides data on AO operation with all correction factors turned off, while AO2 gives data with all correction factors on.
2. Gain figures are in dBi to preclude confusions occasioned by showing dipoles having gain in dBd; that is, gain over a dipole. However, the "dipole" of dBd is a free-space dipole of indefinitely thin wire, whereas the models shown use finitely thick wires, whether in free space or over real ground. Real antenna improvement is always the gain in dBi of the improved model over the gain in dBi of a standard, which is often for horizontal antennas a real wire dipole over the same ground at the same height.
3. Take-off (TO) angle is the elevation angle in degrees showing peak random or maximum gain for antennas over the specified ground conditions.
4. Front-to-back (F/B) are given in dB.
5. Source impedance is given in resistance plus inductive reactance or minus capacitive reactance.
6. Bandwidth (B/W) is given in degrees between points whose gain is down 3 dB from the maximum.
7. Run-time is the total time required from the respective programs to run the MININEC matrix, factor it, and calculate all the data expressed in the tables. For AM and AO, the time does not include putting a pattern on the screen. For ELNEC, the pattern drawing time is included, because some data is most easily obtained by printing the analysis on the pattern screen. Run times are shown only where they exceed a few seconds; that is, where they exceed the time taken to read the results from the screen.

ing, bent-wire correction, and frequency correction. The versatility of plotted outputs is largest, but by only a bit over AM, so I shall choose it. If AO's powerful symbolic dimensioning could be made compatible with ELNEC's group element construction, it would undoubtedly make antenna modification a breeze (as well as enabling the Optimizer feature of AO, which has not been discussed here).

AM offers some powerful programming tools to strengthen my ideal MININEC program. AM's auto-run capabilities are a must (but with control programming from within the overall program and with more selectable and excludable output variables). The large spectrum of "Change" options might be included (in

case the ELNEC menu screen could not be fully preserved). Access to the calculator and to the soil definition table are convenient for empty-lap antenna construction. The use of F-keys to trigger major functions is also an excellent innovation for antenna modeling programs.

This is not everything I want. For example, variables that AM and AO require in a preoperation batch file, such as directory paths, might be placed in an accessible start-up shell. Only ELNEC currently lets you freely specify from within the program a new subdirectory that is not prewritten into a SET command, but you do have to remember where that subdirectory is located. My list could go on indefinitely. And, as noted throughout, convenient running print outputs deserve attention in one or another way by all three programs.

Each program also contains excess capabilities beyond my needs and wants. Those excesses, of course, may not be beyond your needs and wants, as measured by the applications you have in mind. On the other hand, some of my ideal wants will be irrelevant to you. Choosing a program is largely a matter of effectively listing one's needs as dictated by applications and seeing which of the available programs provides the best match. Rather than providing judgments, even about individual features, this exercise in comparative scrutiny demonstrates a method of arriving at the best individual decision. You can rightfully disagree with every evaluative particular and still get something from the exercise, even if only the clarification of your own thinking about MININEC programs.

One thing more: the surplus features of a program offer a challenge. Part of the fun of using these programs is to learn how to turn the excess capabilities into productive output. Ultimately, any tool is only as good as its user. I am now—and always will be—still learning how to use this tool called MININEC.

REFERENCE NOTES

1. ELNEC is available from Roy Lewallen, W7EL, P.O. Box 6658, Beaverton, Oregon 97007. AO and MN are available from Brian Beezley, K6STL, 507-1/2 Taylor, Vista, California 92084. Antenna Model is available from Teri Software, P.O. Box 277, Lincoln, Texas 78948. ELNEC, MN, and AM are in the \$50 price range. However, a MaxPulse option is available for ELNEC, and there are numerous add-on programs for MN, each at extra cost. AO is a separate program that incorporates MN and is in the \$100 price range. The versions of the programs used in this study were current as of May 15, 1993. Improvements after that are not included herein.
2. For example, R.P. Haviland has had a version of MININEC available through Minilab Books, P.O. Box 21086, Daytona Beach, Florida 32019-1086. ACES (Applied Computational Electromagnetics Society) makes available BASIC and FORTRAN versions of MININEC, as well as a version of the parent program, NEC, for the PC. For information on ACES materials and membership, contact Professor Richard Adler, ACES Secretary, Naval Postgraduate School, Code EC/AB, Monterey, California 93943. One or more Macintosh versions are available, including MacMININEC 4.4 from Chris Smolinski, N3JLY, 40 South Lake Way, Reistertown, Maryland 21136. This list is not complete. Indeed, numerous engineers and hams have embellished MININEC for their own personal use, and copies of their work have been distributed. Moreover, the flux of time, economics, and effort makes the MININEC market volatile, even within the space between writing and publication.
3. The basic documentation of MININEC is contained in J.W. Rockway, J.C. Logan, D.W.S. Tam, and S.T. Li, *The MININEC System: Microcomputer Analysis of Wire Antennas* (Norwood, Massachusetts, Artech House, Inc., 1988). For the most recent code, see J.C. Logan and R.W. Rockway, *The New MININEC (Version 3): A Mini-Numerical Electromagnetic Code*, NOSC Technical Document 938, National Technical Information Service document #ADA181682, U.S. Department of Commerce, 5285 Port Royal Road, Springfield, Virginia 22161.
4. Perhaps three of the most significant recent articles in amateur journals are: Roy Lewallen, "MININEC: The Other Edge of the Sword," *QST*, February 1991, pages 18–22; John S. Belrose, "Modeling HF Antennas with MININEC—Guidelines and Tips from a Code User's Notebook," *Antenna Compendium*, Vol. 3 (Newington, Connecticut, ARRL, 1992), pages 156–164; and R.P. Haviland, "Antenna-Structure Interaction: Modeling with MININEC," *Communications Quarterly*, Fall 1991, pages 73–78. In general, some of the best discussions of MININEC's limitations and how to overcome them appear in the manuals for the three programs under discussion.
5. See William I. Orr, W6SAI, *All About Cubical Quad Antennas* (Wilton, Connecticut, Radio Publications, Inc., 1959).
6. This requirement, which may even preclude some data if not followed, is contrary to the preference I once expressed in print for putting element dimensions in the "X" column, where they are most easily inspected for errors. This possibility exists only for ELNEC, or if one accepts the loss of speed or data in the other programs. See L.B. Cebik, "A Beginner's Guide to Using Computer Antenna Modeling Programs," *Antenna Compendium*, Vol. 3 (Newington, Connecticut, ARRL, 1992), pages 148–155.
7. For example, the HP Laserjet options do not function with my Panasonic 4450 in Laserjet in emulation mode, forcing a return to Epsom emulation.
8. See L.B. Cebik, "The Effects of Antenna Height on Other Antenna Properties: A Computer Study," *Communications Quarterly*, Fall 1992, pages 57–79.

PRODUCT INFORMATION

HP introduces new family of precision semiconductor parameter analyzers.

Hewlett-Packard Company unveiled the HP 4155A and 4156A benchtop parameter analyzers, which allow engineers to monitor the electrical performance and reliability of semiconductor devices.

The HP 4155A semiconductor parameter analyzer offers four built-in SMUs, two VSUs, and two VMUs. The HP 4156A adds remote voltage sensing and current ranging.

Three new modes are available in these analyzers. They are: a "stress" mode, which analyzes failure mechanisms; a "standby" mode, which allows continuous circuit bias; and a "knob sweep" mode, which adds a curve tracer.



For prices and additional information, contact Hewlett-Packard Company, Direct Marketing Organization, P.O. Box 58059, MS51L-SJ, Santa Clara, CA 95051-8059.

TECHNICAL CONVERSATIONS

W2EUF wrote in response to the article by Trevor King, ZL2AKW, in the Summer 1993, issue of *Communications Quarterly* ("Build Your Own Direct Reading Capacitance Meter," page 103).

Dear Editor:

The article on the capacitance meter by Trevor King, ZL2AKW, in the summer 1993 issue of *Communications Quarterly* was given me by your subscriber, Al Roehm, W2OBJ, because both of us have constructed similar instruments.

Enclosed is my modification of the meter that Harry Neben, W9QB, described in the January 1983 issue of *QST*, which is mentioned by Mr. King. With a four-section, six-position range switch and 20- μ A meter, there is excellent readout from 2 μ F down to the pF scale. Similar results were obtained with a 50- μ A meter giving a spread of 50 pF to 5 μ F.

All scales are linear and 1 or 2 pF can be determined by subtracting the residual stray capacitance reading of just over 1 pF seen when the 20 pF range is employed. This has been confirmed by using several 1-pF standard capacitors in various parallel and series combinations to get 1, 2, 3, and 4 pF readings on the 20 pF scale. This stray might be less with a non-metal mounting plate, and, of course, no stray shows on other ranges.

It should be noted that only the range switch is needed after power is applied and that damping automatically is provided by the range switch on the 2- μ F scale, which eliminates another control. Also, the sensitive meter is protected automatically when the meter is not being used.

The 23rd edition of *The Radio Handbook*, prepared by William I. Orr, W6SAI, and published by Howard W. Sams & Co., has a similar capacitance meter on page 26-25. This uses

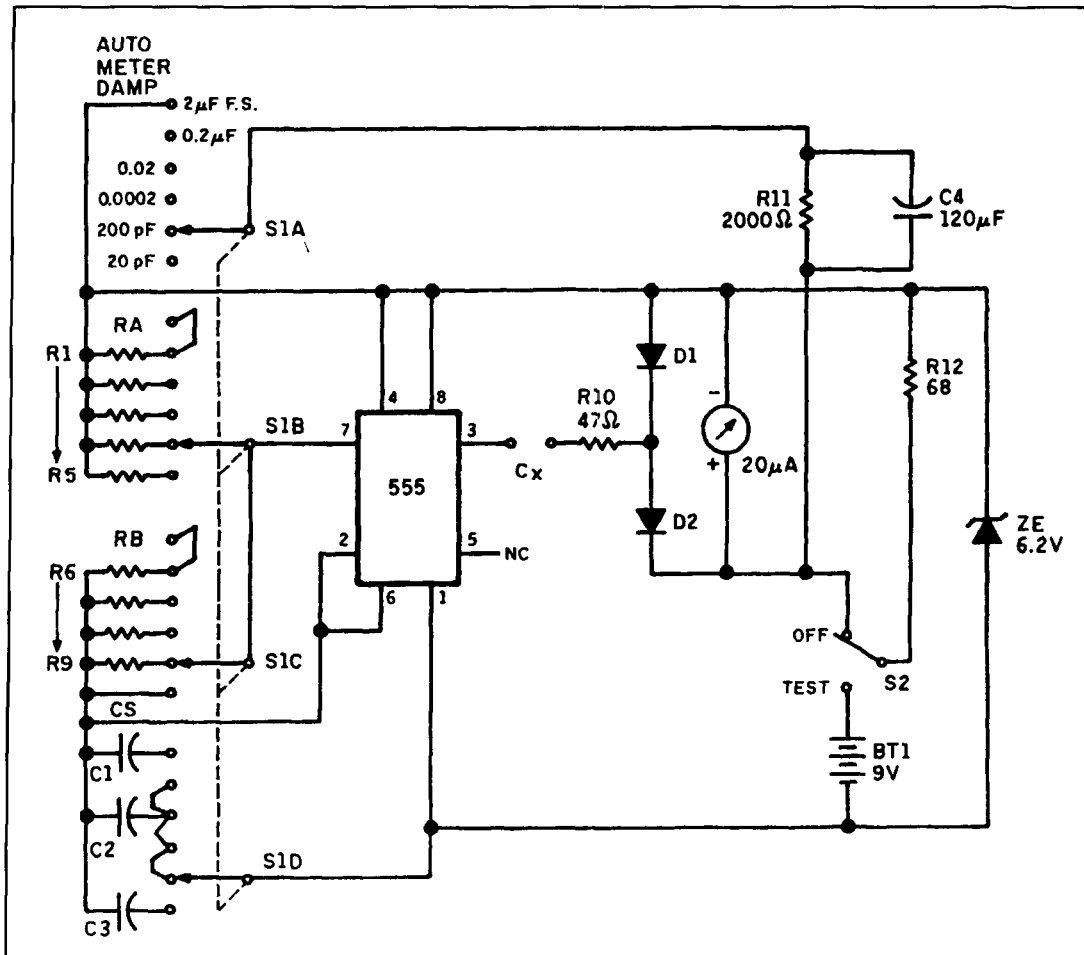


Figure 1. Capacitance meter by Harry Neben, W9QB, from *QST* of January 1983, as modified by R.E. Franklin, W2EUF.

Parts List

R1	3.07 meg
R2	690 k
R3	69 k
R4	6.3 k
R5	4.67 k
R6	1.09 meg
R7	123 k
R8	10.1 k
R9	824 ohms
R10	47 ohms
R11	2000 ohms
R12	68 ohms
C1	30,000 pF mica = 0.03 μ F
C2	10,000 pF mica = 0.01 μ F
C3	1000 pF mica = 0.001 μ F
C4	120 μ F—24 volts DC (100 μ F okay)
Ze	6.2 volts
D1,D2	1N914
S1	4 pole, 6 positions
S2	DPDT (paralleled)
BT1	9-volt transistor battery

Notes:

Subtract 1 pF on 20-pF scale.
 S1 "OFF" protects the meter.
 Battery current: 15 mA.
 Battery volts: 9, no load; 8.6, operating
 20- μ A GE meter type D091 and/or Weston 301.
 50- μ A meter may require different values for RA,
 RB, C1, C2, and C3.

a 556 chip and may be of interest, but I have not sent the circuit as it cannot be reproduced without permission from the publisher.

Richard E. Franklin, W2EUF
 Mountainside, New Jersey

Mr. Franklin's modification follows.—Ed.

Simple Capacitance Meter

In the January 1983 issue of *QST*, Harry M. Nebin, W9QB, describes a capacitance meter of few parts. Results were so good that a 20 pF range was possible with a 20- μ A meter, although a 50- μ A meter worked fine from 5 μ F down to 50 pF. No effort was made to measure larger than 2 μ F. Note the damping applied to the 2- μ F range. Readings are linear on all scales.

One or 2-pF capacitors were measured by subtracting 1 pF stray value on the 20-pF scale. Silver micas and high grade larger capacitors were measured on their respective ranges. After obtaining values for several capacitors, they were connected in parallel and series and the meter read very close to the calculated values of those combinations.

Construction

The circuit is shown in **Figure 1**. Stray capacitance on the 20-pF scale is decreased with short leads and lowest with parts mounted on a plastic plate in a plastic box. Silver micas are needed for C1, C2, and C3. One-watt resistors were from the junkbox and were selected by measuring with a DVM to obtain the schematic values.

C1, C2, and C3 will likely have values different from the prototype, so resistors R1 through R9 may have to be tailored to the circuit, although their values will be within reason. To calibrate, check capacitors of known values, and try resistors R1 through R9 of approximately the listed values until the meter reads the known value of those capacitors.

The test capacitors must be selected to read at the very top of each range, and then double-checked on the next higher scale. Pin 5 of the 555 chip is not needed when the range resistors are tailored to the circuit.

Component values may be determined from these equations:

$$f = I/CV$$

where:

$$C = \text{pF of C1, C2, C3}$$

$$V = \text{applied voltage}$$

$$I = \mu\text{A}$$

$$f = \text{frequency in MHz}$$

RA, RB, with C1, C2, and C3 determine the 555 chip frequency from the equation:

$$f = 1.44/(RA + 2RB)C$$

Note that on the 20 pF range, the frequency calculates twice that measured when operating. On other ranges, the calculated and measured frequency are close.

In the fall of 1991, we ran a reprint of a 1975 Ham Radio article by John True, W4OQ, entitled "How to Design Shunt-Feed Systems for Grounded Vertical Radiators." VE2CV sent us these comments.

I well remember John True, W4OQ's 1975 *Ham Radio* article on gamma matching grounded towers,* with particular reference to feeding radio amateur towers with quad or Yagi beams on top of the tower. I was interested therefore

*I have corresponded with John True, W4OQ, in past years. The reprint of his 1975 article indicates that he now has a new call, N4BA. But that call is not listed in the 1993 callbook, so perhaps John is a silent key? John would have enjoyed seeing the reprint of his article, and to read this correspondence.

 


Figure 1. Antenna model and current distribution for a gamma fed 1.9-MHz tower and Yagi. The heavy black line indicates currents.

to read a reprint of that article in the fall 1991 issue of *Communications Quarterly*, together with Hunter Harris, WISl's comments on implementation.

True's graphical approach to design of gamma match systems was interesting, but not readily adaptable to applications where the spacing between the gamma rod and the tower are quite different from his model. WISl commented on this, since he used a wider spacing for 160 meters. Nowadays, amateurs in radio are using antenna analysis programs like MININEC (or versions of it such as ELNEC or MN), which work on their PCs. Professional antenna engineers use NEC-2/NEC-3, but these programs run on a large computer, and are not user friendly. I was pleased, therefore, when MININEC was developed for the amateur in radio application, since even I can run the program on my PC; and PC versions of NEC-2 are becoming available.

But there are limitations and guidelines in the application of the MININEC code.¹ One of the guidelines is that an antenna, particularly a horizontal antenna, must not be too close to the ground ($h > 0.2$ wavelength), because the initial calculation of mutual and self-impedance of the segments making up the antenna, and hence the current distribution on the antenna, assumes

that the ground beneath the antenna is perfectly conducting. Thus, for antennas at low heights, the gain may not be right, but the far field pattern is correctly predicted, because the program employs Fresnel reflection coefficients for whatever user-selected ground conductivity is desired. However, the program works quite satisfactorily for well-grounded vertical antennas, so we can anticipate that we should be able to model quite successfully the present antenna system. But there is another limitation, in that two wires (or conductors) having different diameters should not be joined. A gamma rod and a tower have quite different diameters. The spacing between conductors, e.g. modeling a 2-conductor transmission line should not be close with respect to the diameter of the wires. For our gamma rod and tower, we are probably right in this respect, but we have to be careful.

The purpose of this correspondence is to give results obtained by numerically modeling WISl's antenna system. For the 160-meter band, he used a gamma rod spacing of 5 feet from one edge of the tower. The length of the gamma rod was the height of the tower. For our model, we assumed that the Yagi was a 20-meter monoband wide-spaced 3-element Yagi on a 50-foot tower. The antenna model and current distribution on the antenna at 1.9 MHz are

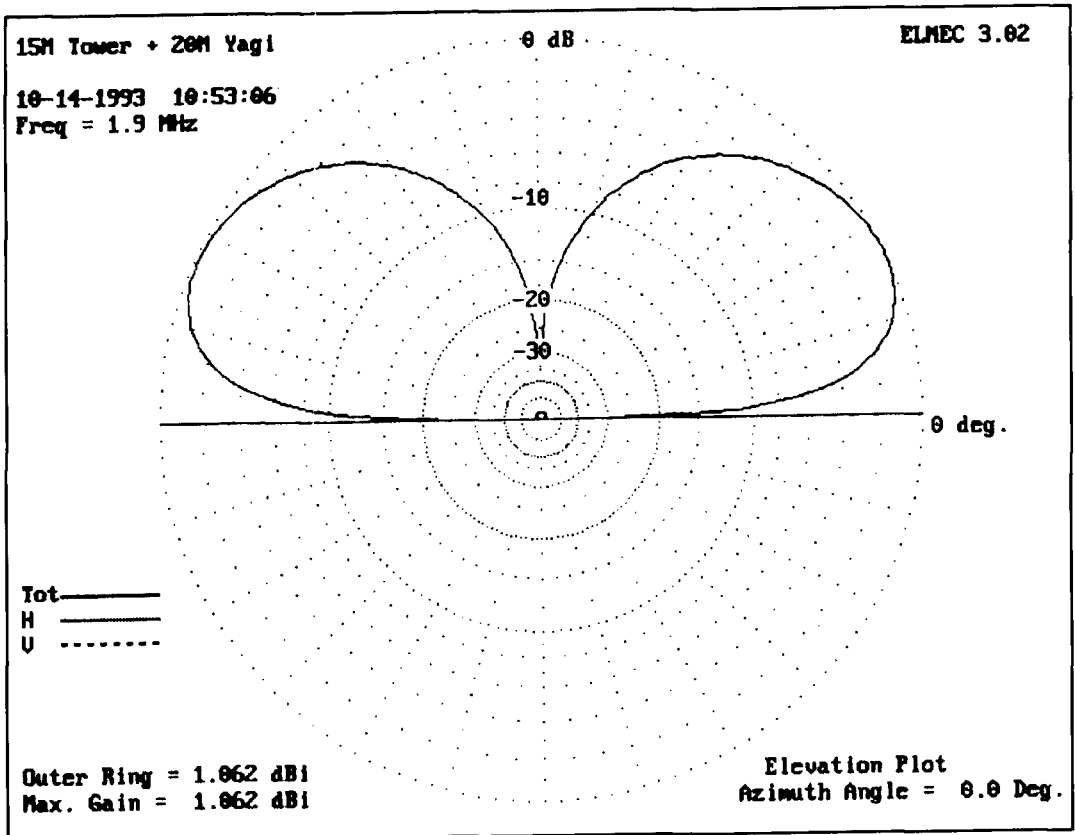


Figure 2. Elevation pattern for Figure 1's antenna, frequency 1.9 MHz.

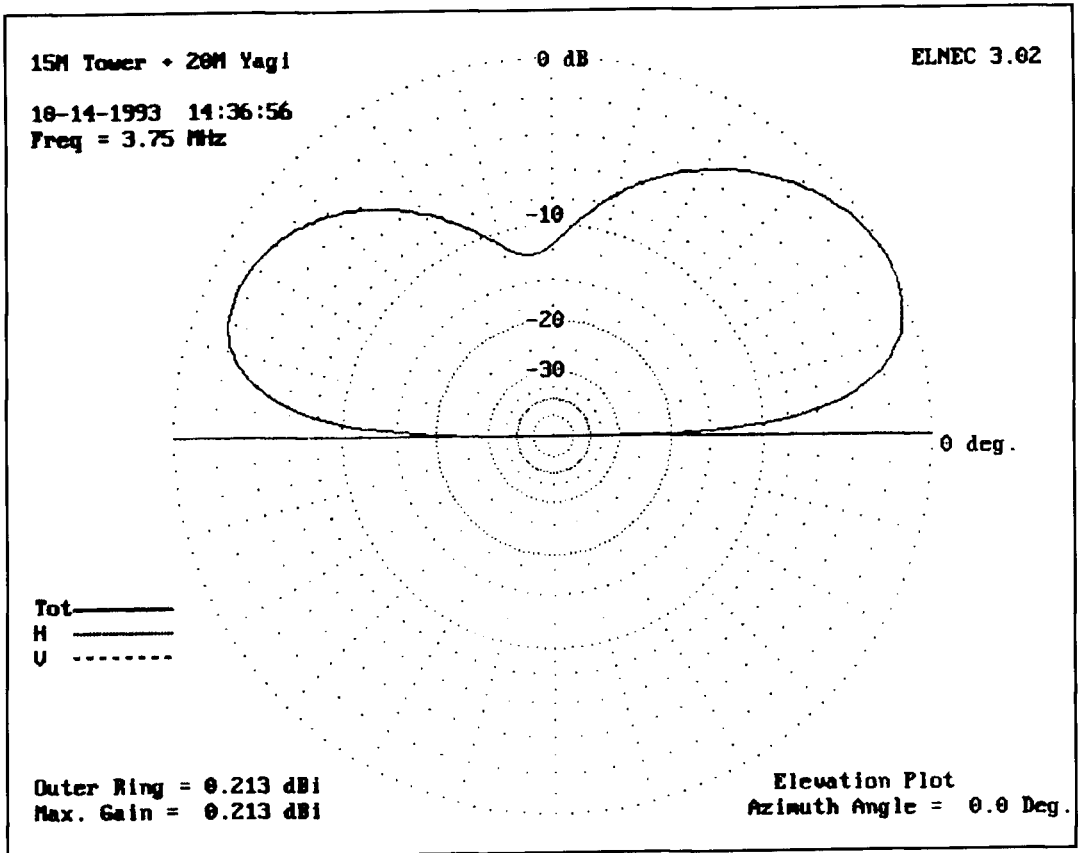


Figure 3. Elevation pattern for 3.75 MHz (see text for details on feed).

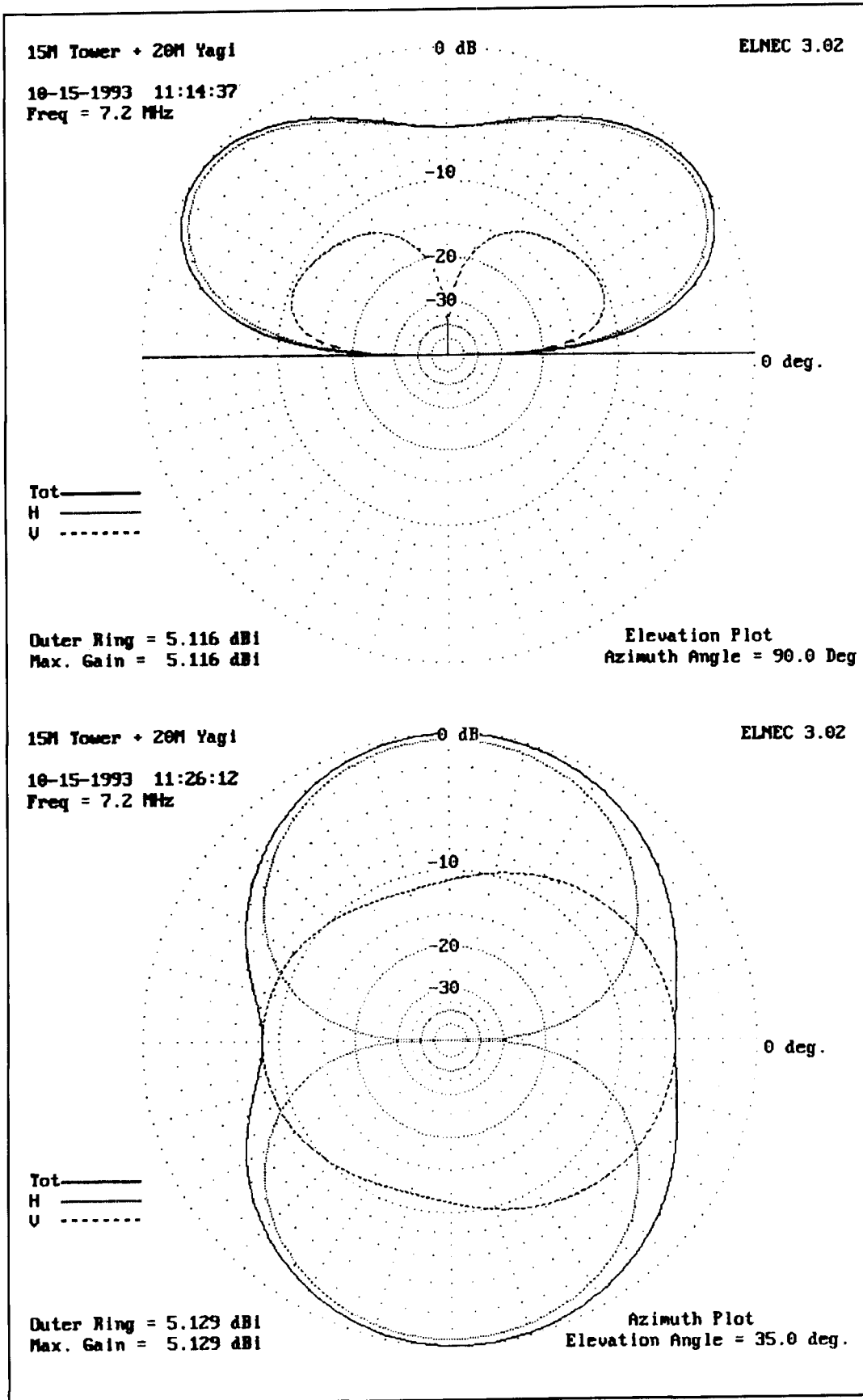


Figure 4. Radiation patterns for 7.15 MHz. A) Elevation pattern at azimuth of maximum gain; B) principal plane azimuthal pattern (at elevation angle of maximum gain).

Method of Gamma Rod Feed	Input Tower Spacing (Feet)	Impedance
Base Fed		12 - j77
Gamma Feed	2.5	26 + j405
Gamma Feed	5	67 + j648

Table 1. ELNEC's antenna system impedance 1.9 MHz.

shown in **Figure 1**, and the elevation radiation pattern in **Figure 2**, for average ground (conductivity 3 mS/m, dielectric constant 13) in front of the antenna. The antenna's impedance base fed (it is easy to lift the base of the tower off the ground for the numerical model, but not so easy at full scale), and for two gamma rod spacings are given in **Table 1**. This confirms W1SI's view that a wider spacing gives better results. As can be seen, the antenna can be tuned by a capacitor to cancel the inductive reactance at the feed point.

For the 80-meter band, W1SI used a gamma rod spacing of about a foot, and the tower was fed about 2/3 the height of the tower from the base of the tower. ELNEC's impedance at 3.75 MHz is 10 + j287 ohms. A wider spacing between the tower and the gamma rod would have been an advantage for this band also. The antenna's elevation pattern is plotted in **Figure**

3. The azimuthal pattern (not shown) is not quite circular at this frequency, but the difference is hardly more than a dB.

The antenna's gain with base feed and gamma match feed are almost the same, indicating that indeed MININEC is modeling correctly the tower and its feed.

The self-resonant frequency of the tower and the Yagi is 2.31 MHz. This is in agreement with experimental modeling I did about 15 years ago. Hence at 1.9 MHz, the electrical height of the tower and Yagi is equivalent to a 0.2 wavelength monopole (or 32.4 meters). On simple reasoning, the electrical height of the antenna system at 3.75 MHz would be 0.4 wavelength; and at 7.15 MHz, 0.77 wavelength. But the radiation pattern at 7.15 MHz is certainly not like that for a 0.77-wavelength monopole (see **Figure 4**). The antenna system exhibits directivity in the plane that contains the elements of the 20-meter beam, and surprisingly the dominant polarization in this plane is horizontal. The boom of the 20-meter beam carries a large current (see **Figure 5**). This is a consequence of my model of the 20-meter beam. Without thinking about it, I modeled a 20-meter wide spaced beam, with reflector spacing of 0.25 wavelength, and director spacing of 0.15 wavelength. The boom connecting to the reflector carries the largest current. Other Yagi dimensions will not give such "good" pattern. By rotating my modeled 20-meter beam,

 


Figure 5. Antenna model and current distribution for a 7.15-MHz tower and Yagi (note I have assumed a base-fed tower for this calculation). The heavy black line indicates currents. I did not bother with a gamma match for this frequency because I was concerned with pattern and currents not with feeding and matching line.

lo and behold we have a directional antenna for the 40-meter band!

In conclusion, MININEC (I used ELNEC) gives results which I believe are about right—in spite of the limitations of the code discussed above. It also, and perhaps not unexpectedly, predicts 40-meter radiation patterns that we certainly could not have guessed intuitively.

John S. (Jack) Belrose, VE2CV
Quebec, Canada

REFERENCE

1. J.S. Belrose, "Modeling HF Antennas Using MININEC: Guidelines and Tips From a Code Users Notebook," *ARRL Antenna Compendium*, Vol. 3, 1993, pages 156–164.

AF6S offers this alternative to the K1CCL propagation velocity method described by George Wilson, W1OLP, in "Tech Notes" (Communications Quarterly, spring 1993, page 83).

Dear Editor:

The K1CCL propagation velocity method that George Wilson, W1OLP, describes in "Tech Notes" (spring 1993, page 83) is clever, but tedious.

The use of separate means to measure dip-frequency accurately brought to mind my MFJ HF/VHF SWR Analyzer, Model MFJ-249, which combines a signal generator, an accurate frequency counter, and an SWR bridge—covering 1.8 to 170 MHz in a hand-held package.

A transmission line that's open at the far end appears as an open at the near end when its length is any *even* number of quarter wavelengths (i.e., *any* number of half wavelengths). A transmission line that is shorted at the far end appears as an open at the near end when the length is any *odd* number of quarter wavelengths. A clear, concise review of transmission theory appears in Caron¹ Chapter 2.

If you connect a small carbon-composition or metal-film 50-ohm resistor directly across the MFJ-249, the SWR meter reads 1:1—except well above 100 MHz, where stray inductance and capacitance enter the picture.

If you connect the end of a transmission line in parallel with the resistor, the total impedance becomes that of the resistor in parallel with the line. At frequencies where the line presents an open, the meter "sees" only the resistor, so SWR reads 1:1.

I soldered the pins of a pair of "four-hole" SO-239s together, and soldered four wires between the opposing holes and a 51-ohm, 1/4-watt resistor between the pins and one of the wires. I connected this "termination" to the MFJ-249 using a UHF double male. As expected, SWR read hardly over 1.00:1 below 150 MHz.

Next, I attached a 24-foot length of RG-8/U (Belden 9267) and put a UHF "bullet" in the PL-259 at the line's far end. **Figure 1A** shows the setup.

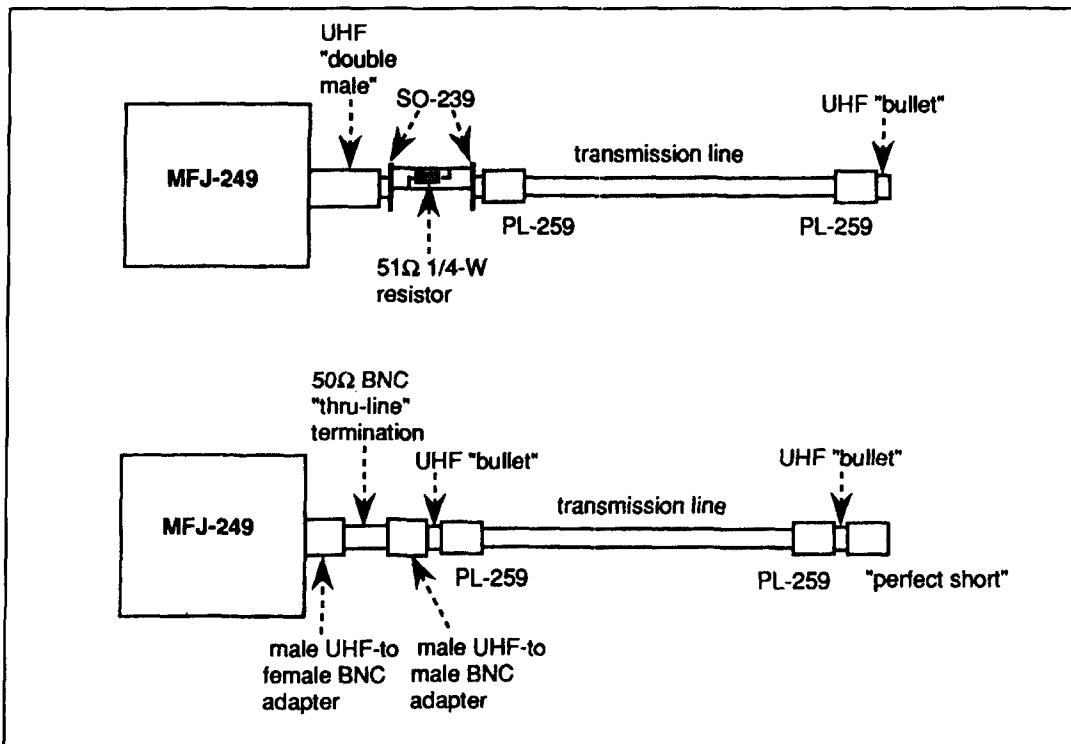


Figure 1. (A) Resistor in parallel with transmission line. (B) With thru-line termination and "perfect short" at far end of line.

	A	B	C	D	E
1	Constants:				
2	Length (meas):	24.1042	ft		
3	Len (physical)=	7.3470	meters		
4	Len (elec.)	F(open)	Vp(open)	F(short)	Vp(short)
5	wavelengths	MHz		MHz	
6	0.25	6.5319	63.99%	6.7226	65.85%
7	0.50	13.3937	65.60%	13.4210	65.74%
8	0.75	20.0468	65.46%	20.2400	66.09%
9	1.00	26.9262	65.94%	26.8830	65.84%
10	1.25	33.6678	65.96%	33.8800	66.38%
11	1.50	40.3875	65.94%	40.3940	65.95%
12	1.75	47.5613	66.56%	47.5095	66.49%
13	2.00	53.9637	66.08%	53.8858	65.98%
14	2.25	60.9219	66.31%	60.9350	66.32%
15	2.50	67.3690	65.99%	67.3350	65.96%
16	2.75	74.3725	66.23%	74.4860	66.33%
17	3.00	80.8952	66.04%	81.0450	66.16%
18	3.25	87.8790	66.22%	88.1200	66.40%
19	3.50	94.5370	66.15%	94.4710	66.10%
20	3.75	101.6320	66.37%	101.5960	66.35%
21	4.00	107.8540	66.03%	107.9500	66.09%
22	4.25	115.3420	66.46%	115.1600	66.36%
23	4.50	121.5980	66.18%	121.4660	66.10%
24	4.75	128.6500	66.33%	128.7590	66.39%
25	5.00	135.1450	66.19%	135.1680	66.21%
26	5.25	142.3170	66.39%	142.4000	66.43%
27	5.50	148.8360	66.27%	148.7200	66.22%
28	5.75	155.9190	66.41%	156.0000	66.44%
29	6.00	162.3000	66.25%	162.1500	66.18%
30		Average=	66.06%	Average=	66.18%
31		Median=	66.18%	Median=	66.19%

Table 1. Measured frequencies and resulting propagation velocities using the commercial termination.

Sure enough, the MFJ-249 showed 1:1 SWR at a series of frequencies in a 1:2:3:4:etc. frequency ratio—where the coax is 1, 2, 3, 4, etc. half-wavelengths long.

I noticed I could also read SWR peaks accurately. The peaks occur at frequencies where the transmission line looks like a short—any odd number of quarter wavelengths from an open. I recorded the frequency of every SWR null and every peak, and measured the coax length to the end of the “bullet.”

Then I made a “perfect short”—a PL-259 with a copper-foil disk with a hole, soldered to the pin and to the surrounding metal body—and put it on the “bullet” at the far end.

I recorded the frequency of every SWR peak and null in the shorted cable. But when I entered all the open and shorted frequency values into an Excel spreadsheet, the variations in calculated propagation velocity seemed excessive. I substituted a commercial “thru-line” termination, with appropriate adaptors, as in **Figure 1B**, and the results improved a little. **Table 1** shows the measured frequencies and

resulting propagation velocities using the commercial termination.

Column A contains electrical length in wavelengths and column B has the corresponding frequency. The following equation for propagation velocity, V_p , in column C works for any electrical line length:

$$V_p = \frac{\text{Len}_{\text{meters (physical)}} \times F_{\text{open (MHz)}}}{300 \times \text{Len}_{\lambda \text{ (electrical)}}$$

Note: this equation gives the result as fraction. Excel can display fractions as percentages, so you don't need to “adjust” your equations for that purpose. But if you prefer an answer in percent, just substitute 3 for the 300 in the denominator.

Column D contains the frequency series measured with the coax shorted, and column E calculates the propagation velocity, using the same equation, but taking its frequency from column D.

The frequencies in both the F(open) and

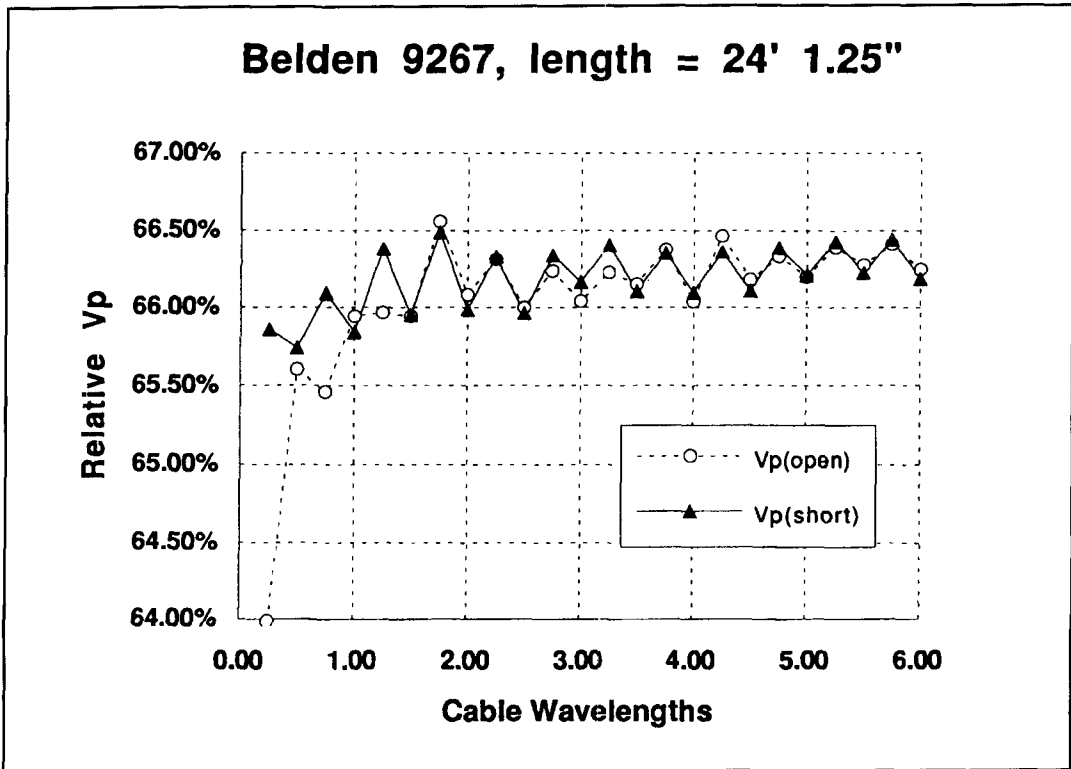


Figure 2. Plot of the results.

F(shorted) columns correspond to alternating SWR readings near 1:1 and infinity. In the 0.25-wavelength measurement, for instance, the F(open) SWR peaks at infinity, while the F(short) SWR nulls at 1:1. In the 0.5-wavelength case, the F(open) SWR nulls and the F(short) reading peaks.

Figure 2 plots the results. Except for the open quarter-wave measurement, all fall within a 1-percent spread. If you ignore readings for lines less than 1.25 wavelengths long, the spread diminishes to 0.6 percent. The values tend to alternate, suggesting some sort of experimental error. Curiously, the higher values are null readings for the shorted line, but peak SWR readings for the open line.

If you can tolerate a half-percent error, this suggests measuring a cable one to six wavelengths long (at its end-use frequency) and considering it accurate enough. But if you are concerned about the variations, as I was, you might want to consider possible causes of error. Here are the ones that occurred to me:

1. The effective position of a simple open, like a "bullet" or a cut-off coax, varies with frequency because of electric field fringing. In their heyday, General Radio supplied calibrated opens (p/n 874-WO3) for their coaxial "trombone lines" used with their Model 1602-B UHF Admittance Meter. The outer conductor extended several of its diameters beyond the inner

conductor, producing an open that did not "move" as frequency changed.

2. An impedance discontinuity at the near end of the cable can also cause errors.

3. Non-uniformity along the length of the coax, dielectric effects, and small "skin effect" caused losses might cause measured propagation velocity to vary slightly with frequency.

What can we do to minimize these effects?

1. It's easier to make a controlled short than an accurate open, so use a "perfect short."

2. To minimize the near-end discontinuity, use a small commercial "thru-line" termination such as Tektronix p/n 011-0049-01 (50 ohms, BNC, \$35)—instead of a resistor.

3. Keep your measurement frequency within a factor of two of the frequency of intended use and, as WIOLP suggested, take your measurements on the piece you intend to use. Cut a piece a bit longer than your application calls for, make the measurement, calculate the exact length needed from the resulting propagation velocity, then trim to that length.

Measure physical length from the middle of the termination to the plane of the shore at the cable's far end. (If you must measure an open-ended cable, add half the cable shield diameter

to the measured physical length and hope for the best.) If the cable is much, much longer than the total of all the adaptors, termination, etc., you need not worry about the propagation velocity in these devices; but for very short cables, the reverse is true.

This method works even if the cable impedance is not 50 ohms, but to measure a balanced transmission line, you need a balun. The Guanella type² is best, because it is made of transmission lines in such a way that its electrical length is constant (ideally) and measurable. Be sure to check a balun's SWR, when it is terminated in its correct output resistance. Balun SWR should be below 1.2 or so in the frequency range at which you intend to measure the balanced line. With the balun in place, proceed as before—but include the electrical length of the balun when calculating propagation velocity.

Another handy use for the MFJ-249 test setup is measuring the length of coax on a spool. An open-far-end measurement should be accurate enough—a good thing, if the far end isn't accessible. Of course, you will measure the electrical length, so you'll have to use the published propagation velocity to calculate the physical length.

On extremely long rolls, the quarter and half-wave frequencies may fall below the lowest frequency of the MFJ-249. No worries! Notice that the frequencies in **Table 1** increase in increments of the quarter-wave frequency. That means you can subtract any adjacent pair of measured frequencies, one peak SWR reading

and the next null, for example, to find the quarter-wavelength frequency. Another bonus: with any long piece of cable, you can always make your velocity measurement near the desired frequency. It's handy and it eliminates one source of error.

You could just as well make MFJ-249 measurements with a terminating resistor in series rather than parallel, duplicating KICCL's results without the coils. The difficulty lies in the impedance discontinuity of the series resistor. If you make a good series terminator using strip-line techniques and a chip resistor on double-sided pc board, it should work just as well as the shunt method. SWR nulls would occur at frequencies where the cable appears as a short instead of an open, so the nulls and peaks would reverse.

I will venture to say that the MFJ-249 is the most useful ham-priced RF instrument to hit the market since the grid-dip meter. MFJ offers it as an antenna-measuring tool, and it certainly handy for that. But the unique combination of generator, counter, and bridge, makes it useful for a far wider range of experimental work than just antennas.

David M. Barton, AF6S
San Jose, California

REFERENCES

1. Wilfred N. Caron, *Antenna Impedance Matching*, Amateur Radio Relay League, 1989.
2. Jerry Seviak, W2FMI, *Transmission Line Transformers*, 2nd Edition, Amateur Radio Relay League, 1990.

PRODUCT INFORMATION

Sipel Multi-Blade Knife From The Tool Resource

The Tool Resource has introduced the Sipel Multi-Blade Knife. Its design allows you to use one handle for many different types of hobby blades. The M34-SA knife is constructed of stainless steel and the blades can be removed or reattached with a three-step process. A scalpel is also included.

The Sipel Multi-Blade Knife (Part number M34-SA) is available for \$19. Scalpel Blades (Part number M9-15C) are available for \$.90 ea.

For more information contact The Tool Resource, P.O. Box 1106, W. Dundee, IL 60118. Phone/Fax: 708-468-0849.

Application Notes From Analog Devices

Analog Devices has published four new application notes.

The AN-203, *Using the AD2S80A-Series Resolver-to-Digital Converters as a Control*

Transformer, for designers of position servo systems.

The AN-369, *Thermocouple Signal Conditioning Using the AD594/AD595*, practical considerations when using these one-chip thermocouple signal conditioners in temperature measurement applications.

The AN-365, -366, and -367, describe in detail evaluation boards for the AD7711, AD7712, and AD7713 24-bit sigma-delta A/D converters (respectively), to provide a complete, high-resolution channel for specific analog signal measurement applications.

And the AN-372, *MDAC Circuit Gives Freedom of Choice for Both Output Span and DC Offset Voltage*, describes use of a multiplying DAC in a configuration which allows independent setting of these two critical parameters.

For more information contact Bill Schweber. Phone 617-461-3821; Fax 617-329-1241; e-mail bill.schweber@analog.com.

SURFACE ACOUSTIC WAVE TECHNOLOGY


*The fundamentals of SAW technology,
how SAW devices operate, and where
this technology is headed*

There's something pleasingly mystical about working at UHF and above.

Materials normally thought of as insulators at HF are routinely used as capacitors and resistors, and component leads become inductors, tuned circuits, or antennas. Hollow metallic tubes serve as RF conduits between transmitters and antennas, the latter often consisting of nothing more than an etched PC board. Yet

another apparent paradox is a class of devices that rely on *acoustic* waves for their operation.

Surface acoustic wave (SAW) devices are so named because, at the most basic level, their operation involves the excitation and detection of minute *acoustic* waves that travel over the *surface* of a substrate in a controlled manner. SAW devices command the attention of communications professionals and amateurs

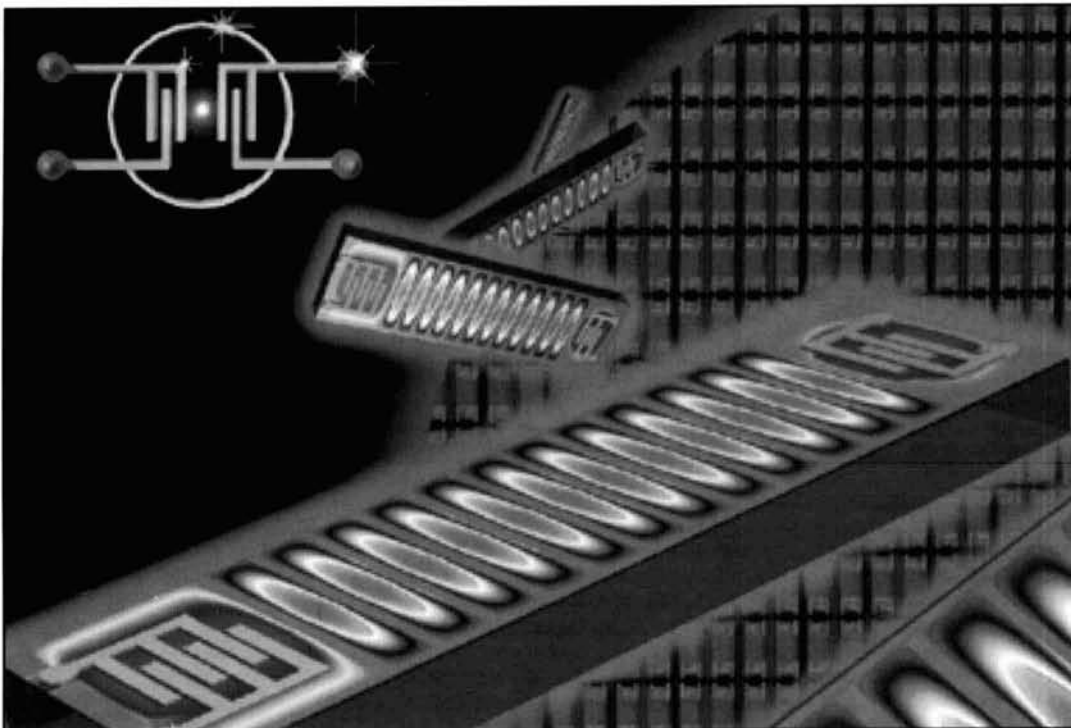

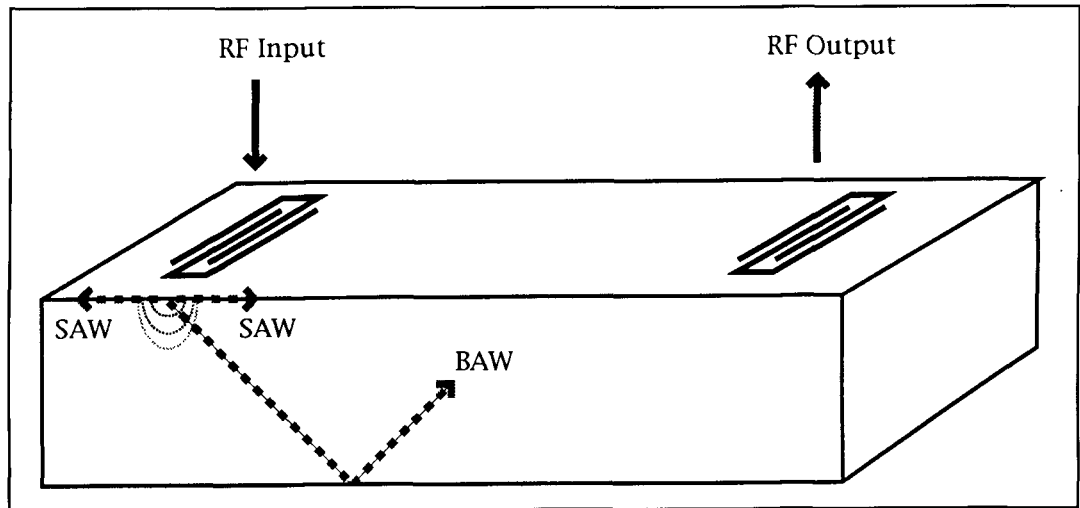


Figure 1. A simplified view of a generic SAW device showing the basic components necessary for operation—a set of RF-acoustic transducers and a substrate capable of conducting acoustic waves. The interdigital transducers produce and respond to both surface and bulk acoustic waves (SAW and BAW, respectively).

Material	Acoustic Impedance
Air	411×10^{-6}
Aluminum	17
Brass	36
Cadmium Sulfide	22
Copper	42
Glass	13
Ice	4
Lead	22
Lithium Niobate	34
Magnesium	10
Mercury	20
Mylar	3
Nickel	54
Nylon	3
Platinum	89
Polyethylene	2
Porcelain	13
Quartz	15
Rubber (Silicon)	1
Silicon	20
Stainless Steel	45
Titanium	27
Tungsten	105
Zinc	30
Zinc Oxide	36

Table 1. Acoustic impedance of both common materials and materials used for SAW device substrates, listed in $10^6 \text{ kg/m}^2\text{s}$.

because these devices provide a unique mix of excellent performance and low cost in an extremely small package. SAW components are found in a variety of applications where low weight, small form factor, ruggedness, and performance are essential—from miniature cellu-

lar phones and secure spread spectrum communications systems to color TV IF filters.

SAW devices have become increasingly important in UHF and microwave communications, where they form the basis of oscillators, amplifiers, bandpass filters, discriminators, and matched filters. SAW devices also have applications in spectrum surveillance systems, RADAR pulse compression and expansion, the generation of long pseudo-random code sequences, and in storing digital information. At the same time, SAW devices are relatively simple and elegant in both their operation and their design.

Fundamental concepts

As electronic components go, those based on acoustic waves are relatively straightforward. A prerequisite to understanding SAW devices, and acoustic wave technology in general, is a grasp of the basics of acoustics, together with a familiarity with piezoelectric transducer operation. To provide a working context for the following discussion, it may be helpful to refer to **Figure 1**. As illustrated in the figure, features common to virtually all SAW devices include metallic electrodes that have been deposited in specific configurations on a suitable piezoelectric substrate. The transducer electrodes generate and receive acoustic waves on the substrate surface in a manner defined by the configuration and relative orientation of the transducers.

Acoustics

Acoustics deals with the propagation of pressure fluctuations in fluid and, of particular importance to this discussion, solid media. The

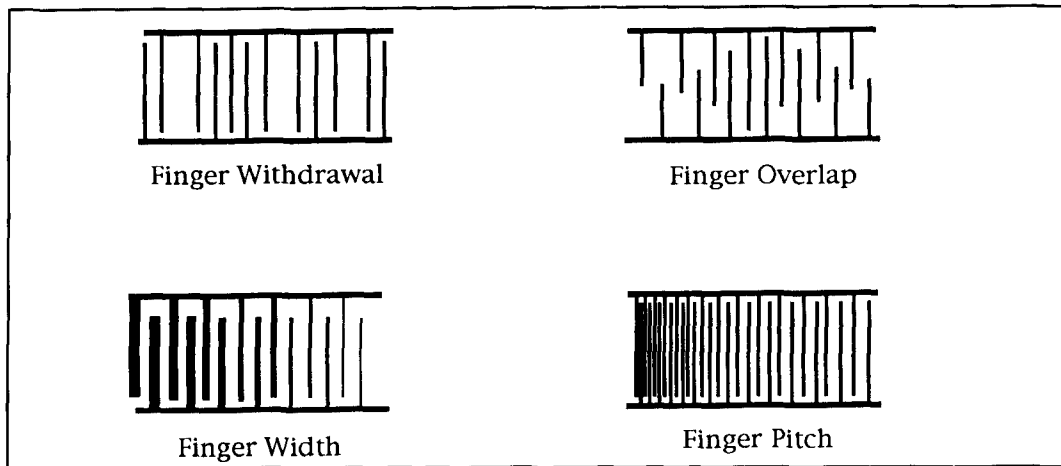


Figure 2. A sample of the more common weighting techniques used to shape SAW transducer amplitude and/or phase response. Weighting techniques allow signal amplitude to be maintained while shaping signal phase. Alternatively, phase can be held constant while shaping signal amplitude. These techniques can be combined in a single device to achieve a variety of transducer response characteristics.

properties of an acoustic wave are typically described in terms of particle displacement, velocity, pressure, and other parameters that have parallels with electronics units and concepts. For example, materials can be classified as either acoustic insulators or conductors, or something in-between. As shown in **Table 1**, materials can also be ranked in terms of acoustic impedance, a term that roughly parallels the concept of electrical impedance.

Acoustic waves propagate with variable loss and velocity in solids, as a function of the media. Furthermore, these properties can be exploited in the creation of a variety of acoustic devices. For example, the relative low velocity of acoustic waves, on the order of 5000 meters/second,¹ makes it possible to construct delay lines that provide significant delays in a minimal amount of physical space.

As illustrated in **Figure 1**, acoustic waves are generally considered as either *bulk waves* or *surface waves*. As its name implies, a *surface wave* follows a path bounded by the surface; greatest particle motion occurs within about one acoustic wavelength of the surface of the substrate.² *Bulk waves* travel, either longitudinally or transversely, through many wavelengths in all directions. As a result, the substrate undergoes motion and stress throughout its volume.

Although acoustic wave devices can be constructed to exploit either bulk or surface wave propagation, surface wave devices are more popular because their construction provides relatively easy access to signal paths for signal sampling. For devices based on surface wave propagation, bulk waves are viewed as undesirable. Not only do bulk waves represent energy loss, but coupling between surface and bulk waves modifies the surface wave radiation. In addition,

bulk waves carry energy to the output transducer, interfering with its response to surface waves. The influence of bulk waves on the output transducer depends on the thickness of the substrate, the parallelism of the bottom and top surfaces, the acoustic impedance match between the substrate and the supporting base, and the distance between transducers (see **Figure 1**).

SAW transducers

Transducers translate energy from one form to another. Like other *electroacoustic* transducers—such as loudspeakers, headphones, and microphones—SAW transducers convert electrical to acoustic energy and vice versa. However, instead of being driven by audio frequency signals, SAW devices operate with RF up to several GHz.

Substrates

The piezoelectric nature of the substrate supports the conversion of electromagnetic into acoustic energy at the input transducer, and acoustic energy back into electromagnetic energy at the output transducer. The coupling of electromagnetic to acoustic energy is commonly achieved through the use of interdigital transducers—metallic electrodes deposited on a piezoelectric substrate. By applying an electrical potential to opposing digits of the transducer, alternating stress patterns are set up in the substrate via the *piezoelectric effect*. As illustrated in **Figure 1**, acoustic waves subsequently created propagate normally to the electrodes on the surface (surface acoustic waves) and at various angles through the substrate (bulk acoustic waves). Acoustic waves that impinge upon the

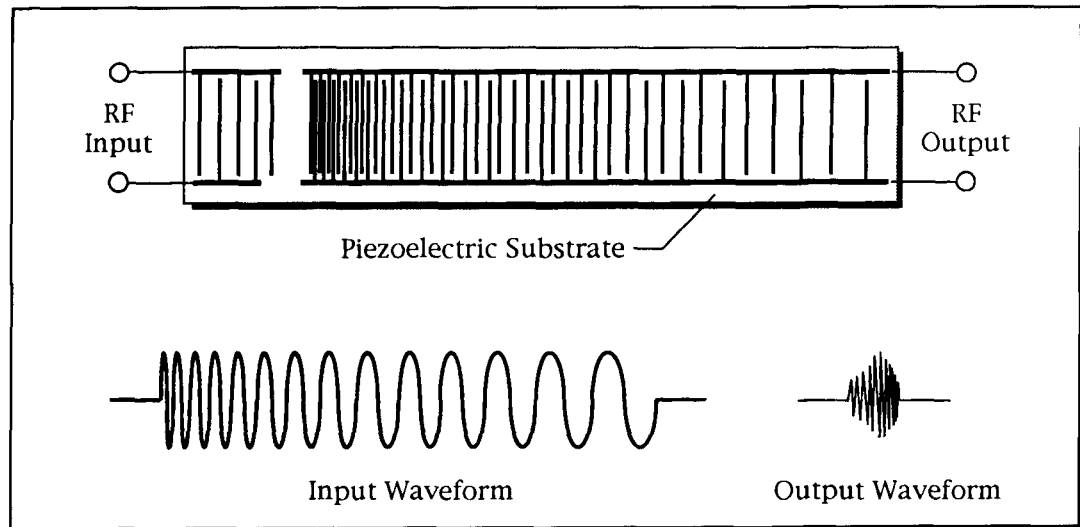


Figure 3. A SAW delay line constructed around a dispersive transducer. In this design, the input transducer (left) launches a signal toward the dispersive output transducer (right). Pulse compression is accomplished by varying the transducer finger spacing in a defined manner. This design can provide moderate compression; i.e., time-bandwidth products on the order of 500. Not shown in this figure are the thin strips of acoustic absorbing materials deposited along the left and right edges of the substrate that minimize acoustic reflections from the substrate edges.

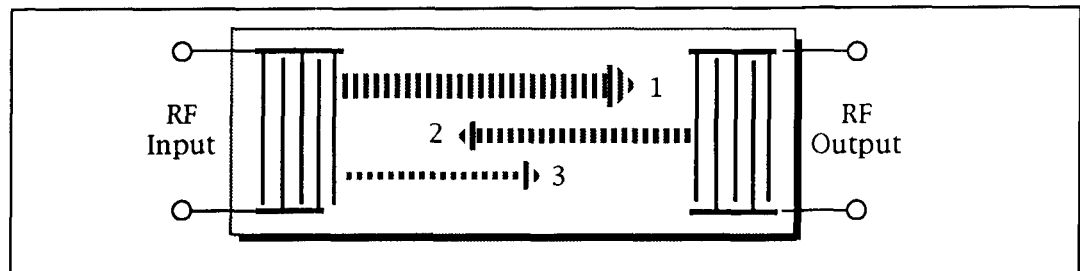


Figure 4. Triple transit echoes arise when the receive transducer reflects energy back into the transducer, thereby causing the generation of a new acoustic wave. This regenerated wave travels to the transmit transducer, where the acoustic signal is similarly regenerated, and returned to the receive transducer. Although this process continues indefinitely, the loss associated with each trip across the substrate renders the higher-order regenerative signals relatively inconsequential. Triple transit echoes limit the useful range of SAW filters.

SAW receiver electrodes establish an electric potential and RF currents in the electrodes, which can be connected to external electronics for amplification and processing.

Piezoelectric substrates are used in the fabrication of SAW devices for the sole purpose of supporting the operation of the input and output transducers. The composition of the substrate places limits on the frequency of operation, bandwidth, and time delay of the SAW device. In selecting a substrate, relevant issues include tradeoffs between high electromechanical coupling versus temperature stability, the availability of large substrates, the compatibility of fabrication techniques, spurious signal rejection requirements, the maximum allowable acoustic loss, and cost. For example, ceramic substrates are associated with severe propagation losses. Quartz, in comparison, has low propagation losses but also a low coupling coefficient. Cadmium sulfide and zinc oxide, which are

both semiconductors, have low loss and show appreciable coupling. Lithium niobate, a synthetic crystal, supports a very high degree of piezoelectric coupling.

The acoustic attenuation associated with SAW devices is a function of the substrate and the conversion loss of the input and output transducers. Acoustic losses in the substrate material can be attributed to relaxation absorption, thermoelastic loss, and scattering.³ *Relaxation absorption*, which can be considered a form of acoustic inertia, occurs when an acoustic wave propagates through a material, but neighboring particles do not move at the same speed. Scattering losses can be attributed to imperfections in the substrate. Since scattering losses are increasingly important at higher frequencies, crystalline substances, which are relatively pure and free of imperfections, are used as substrates at microwave frequencies. In contrast, most piezoelectric ceramics are useful

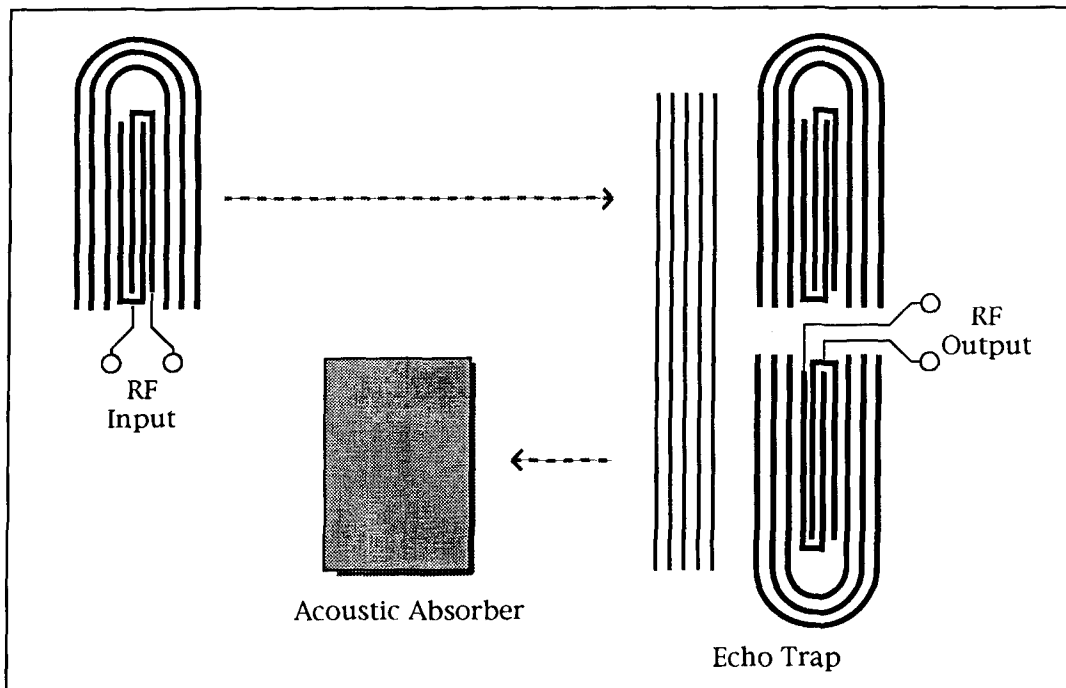


Figure 5. One of the major uses for multistrip structures is the rejection of spurious signals, such as triple transit echoes. In the above example, a delay line is constructed with an echo trap to redirect the signal normally reflected back to the input transducer into an acoustic absorber such as rubber cement.

to only about 20 MHz because of scattering losses. Thermoelastic losses can be considered the result of the compression and decompression of substrate material caused by the acoustic wave, with the result that acoustic energy is transformed into heat. Thermoelastic attenuation is proportional to the square of the acoustic wave frequency.

Transducers

Surface wave transducers typically consist of two sets of interleaved metallic electrodes or fingers deposited on a piezoelectric substrate, such as lithium niobate. The fingers of these interdigital transducers are separated by one half of the acoustic wavelength at the operating frequency. Typical finger spacing for a transducer designed to be driven by a 100-MHz RF signal (or to generate a 100-MHz signal when acting as a receiver) is less than 10 μm .

Whereas the lowest operating frequency supported by a SAW device is limited by the maximum allowable size of the substrate, the upper frequency limits are set by resolution in the photolithographic processes used to form the transducer fingers. Transducers up to about 600 MHz can be constructed with conventional photolithography techniques. Transducers capable of higher frequency operation require scanning electron microscopes to expose the photoresist. With modern fabrication tech-

niques, SAW operating frequency ranges from a few MHz to over 3.5 GHz.

It's often useful to think of acoustic transducers as antennas because the coupling of the transducer to the piezoelectric substrate requires consideration of directivity, acoustic impedance, and radiation resistance. For example, both finger geometry and spacing are dependent on intended operating frequency. Interdigital surface wave transducers have a fractional bandwidth defined by $1/N$, where N is the number of finger pairs. Electrically, surface wave transducers can be thought of as a capacitance shunted by a radiation resistance that depends on finger length as well as the composition of the underlying substrate.

Transducer geometry is often modified to shape the amplitude and/or phase response of the SAW device. These geometric modifications or *weighting* schemes include alterations in finger width, pitch, withdrawal, and overlap (see **Figures 2 and 3**). *Finger width weighting* involves varying the width of successive fingers in an array, while maintaining a constant separation between finger centers. *Finger pitch weighting* varies the separation between finger centers, whereas *finger width weighting* involves modifying the overlap between opposing fingers. *Finger withdrawal weighting* uses selective withdrawal or absence of electrodes, so the average electrode density approximates the desired weighting.

Used alone, each weighting scheme makes it

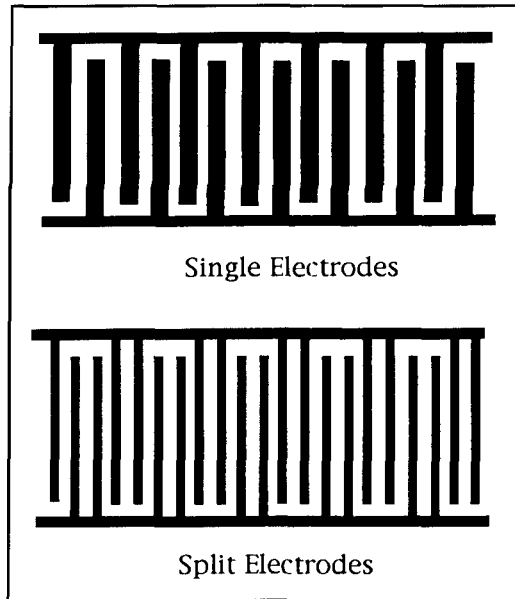


Figure 6. Intra-transducer reflections can be reduced by substituting double or split electrodes (bottom) for single electrodes (top). Transducers with single electrodes have one electrode per half-wavelength, whereas transducers with double electrodes have two electrodes per half-wavelength.

possible to independently define the amplitude and phase responses of a SAW device. Alternatively, these and other weighting techniques can be combined to achieve specific transducer amplitude and phase response characteristics. Variations in electrode width can also be used

to affect amplitude and frequency response.

Transducers have their limitations. Transducer performance is degraded by tight coupling effects, unwanted acoustic waves, electrode resistance, electromagnetic crosstalk, acoustic reflections from terminations and substrate edges, diffraction of the acoustic wave, and electrode interaction. All these factors contribute to distortion, and therefore limit the useful range of SAW devices. *Tight coupling effects* arise because transducer input and output impedances are not fixed, but are a function of frequency, so the generator and load cannot be maintained at the same impedance.

Unwanted acoustic waves include *regenerated waves* (triple transit echoes), *internal reflections* (intra-transducer reflections), and *bulk waves*. Triple transit echoes are due to signals that arrive at the receiving transducer, are reflected back to the input transducer, and then back to the receiving transducer (see Figure 4). The triple transit echo or signal results in part because as an acoustic wave travels under a transducer, it induces a voltage across the bus and external load, which in turn generates another acoustic wave within the transducer. The resulting signal has three times the delay of the original signal. In addition, if the original signal path has a loss of X dB associated with it, the triple transit signal will experience a further loss of $2X + 6$ dB.⁴ Triple transit echoes can be reduced by making one of the transducers unidirectional and tuning it so no energy is available for reflection, or by building a reflect-

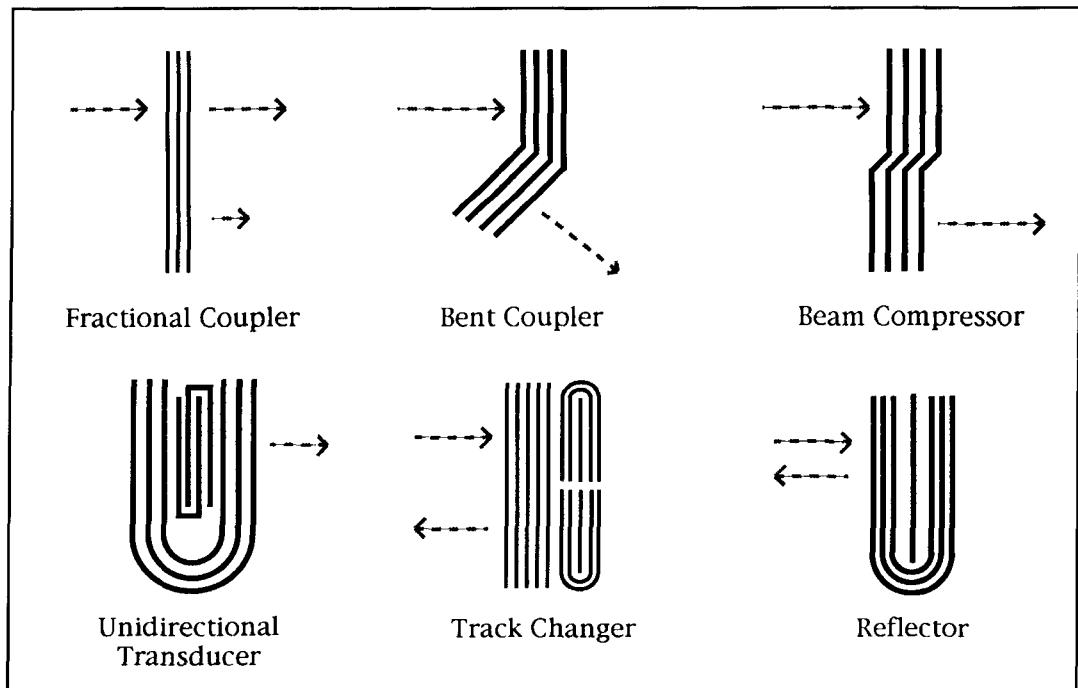


Figure 7. Common multistrip coupling configurations. Multistrip geometry defines how acoustic waves are moved or steered from one region of a piezoelectric substrate to another.

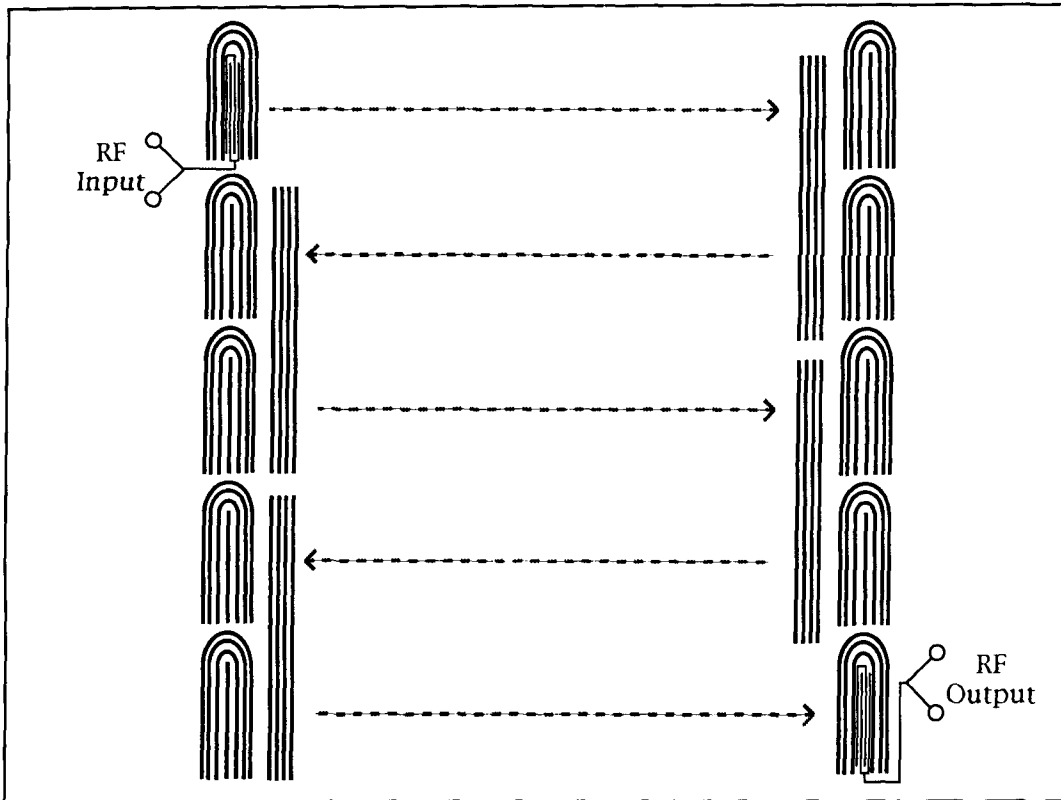


Figure 8. Extended SAW delay times can be achieved on a relatively small substrate by using multistrip structures to fold the acoustic signal, much like the prisms used to extend the light path in binoculars.

ing element that redirects and absorbs the reflection (see **Figure 5**). However, the latter approach has a finite loss.

Intra-transducer reflections, a problem with transducers having many electrodes, can be reduced by using split electrodes, each $1/8$ wavelength instead of $1/4$ wavelength wide (see **Figure 6**). This approach is limited by the resolution of the method used to deposit the transducer patterns on the substrate.

Because bulk waves travel at higher velocities than surface waves, they may reach the output transducer before the desired surface wave signals. As shown in **Figure 1**, bulk waves must pass through the volume of the substrate and then reflect off the back side of the substrate before reaching the output transducer. The intensity of bulk waves reaching the output transducer can therefore be minimized by roughening the back side of the substrate, which has the effect of dispersing the waves throughout the substrate.

Acoustic wave *diffraction* depends on the nature and length of the substrate, the geometry of the transducers, and the wavelength of the acoustic wave. On long paths, diffraction causes *beam spreading*, and therefore amplitude and phase distortion is especially significant in transducers that use a large number of electrodes or weighting

schemes involving variability in electrode overlap. The presence of metallic electrodes on the substrate surface slows the acoustic wave velocity due to shorting of the piezoelectric field. In addition, the mass loading due to the weight of the electrodes results in changes in the local acoustic impedance, which results in acoustic reflections.

In addition to the constraints that are imposed by the acoustic environment, transducers have several purely electrical limitations as well. For example, transducers have a finite electrical resistance, which results in signal loss. Electromagnetic coupling between input and output transducers can also introduce signal distortions. This form of coupling can usually be minimized by proper packaging and shielding, including metalizing and grounding the bottom of the piezoelectric substrate.

Multistrip couplers

Multistrip couplers, in the form of shallow grooves etched in the substrate or strips of deposited metal, are used to extend and enhance the basic performance of SAW devices. Once an acoustic wave has been generated by a transducer, the resulting wave can be modified and redirected in a variety of ways

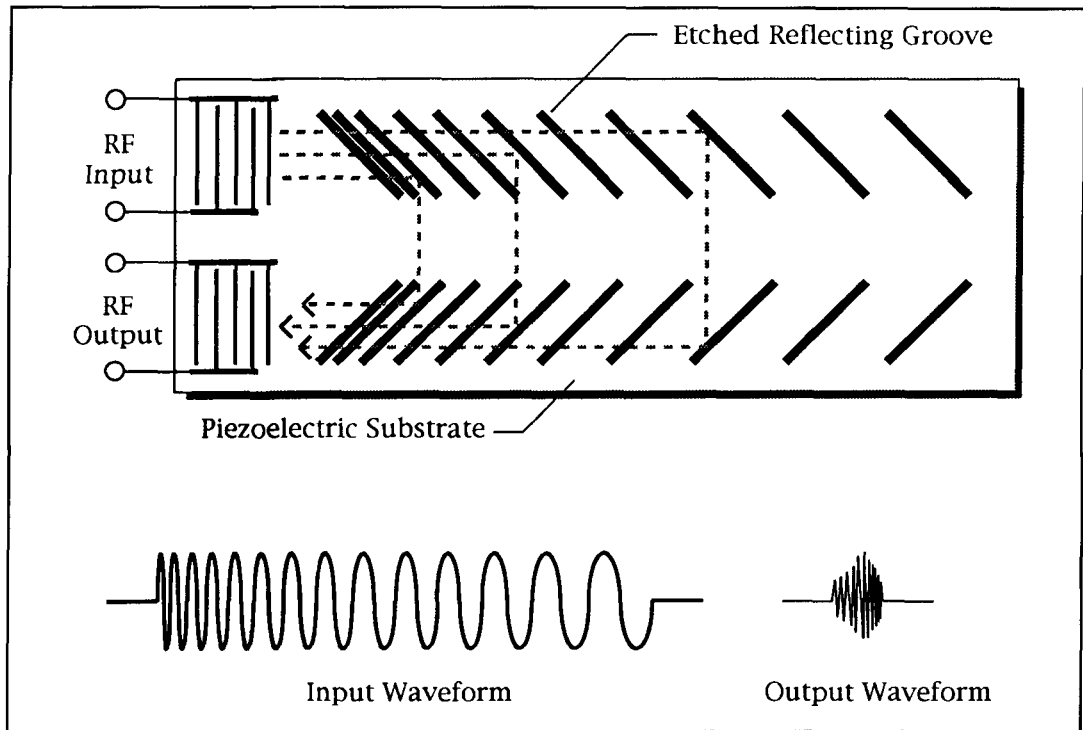


Figure 9. A SAW delay line using reflective array compression (RAC). Signals generated by the input transducer are reflected by shallow grooves etched in the substrate and reflected to the output transducer. This design supports large time-bandwidth applications; i.e., time-bandwidth products up to about 10,000.

on its trip to the receiving transducer (see **Figures 5, 7, 8, and 9**). The applications of multistrip couplers range from rejection of spurious signals, such as triple transit echoes and suppression of bulk acoustic waves, to the creation of filters with delays virtually impossible through alternative approaches.

Grooves are generally considered to be superior to metallic overlays in the construction of multistrip couplers. Not only are grooves more easily reproduced, but metallic overlays are dispersive and introduce phase distortions in the filter response. In addition, the reflectivity of conducting overlays on high coupling piezoelectric substrates is usually excessive. Multistrip grooves, by comparison, are resistant to flaws; a multistrip coupler constructed of grooves can contain a large number of defects and still operate. A small number of flaws in a multistrip coupler constructed of metallic overlays will render the coupler useless. Although multistrip couplers are almost always fabricated on a piezoelectric substrate, the piezoelectric properties of the substrate are required only for the operation of the input and output transducers.

SAW devices

Amplifiers were the earliest acoustic wave devices (see **Figure 10**), and some were capable of providing gain up to 100 dB with band-

widths of up to 50 percent at frequencies of several hundred MHz. Although work in developing acoustic wave amplifiers continues, practical applications of surface wave technology have been restricted to passive delay lines and signal processing components. The most notable acoustic wave components—filters, delay lines, and oscillators—are described in more detail below.

SAW filters

Traditional filter design, normally considered from a frequency-domain perspective, is concerned with the lumped inductance and capacitance values, resonant frequencies, passbands (frequencies that are passed through the filter), and stopbands (frequencies that are not allowed through). When considering SAW filters, it's more intuitive to work from the perspective of a spectrum analyzer; that is, in the time domain. If the incoming signal is considered as a propagating wave, filtering can be viewed as the process by which signals are passed through a number of delay paths, after which the delayed signals are added. Under some conditions, the delayed signals add constructively (the passband), and under other conditions, they add destructively (the stopband). **Figure 11** shows the schematic symbol for a SAW filter device with interdigital electrodes.

SAW bandpass filters are by far the most common form of SAW technology in use today, especially as replacements for the conventional LC filters used in television receiver IF circuits and cable systems. SAW bandpass filters are capable of providing stop-band rejection of at least 60 dB, with a flat in-band response to 0.1 dB, and phase deviation of only a few degrees (see **Figure 12**). Other advantages of SAW bandpass filters include: excellent dynamic range, stability, and linearity in a package that's both rugged and lightweight.

SAW filters are commonly used in applications where it's necessary to pass a very narrow band of frequencies relatively unattenuated, with a sharp dropoff outside the limits of the band. For example, it's not uncommon for the SAW filters used in television receivers and cable systems to have a shape factor (-3 dB to -40 dB bandwidth) as small as 1.1.⁵ In addition to providing excellent performance, SAW filters are extremely space efficient, especially when compared to the multiple resonant LC sections of a conventional filter. Piezoelectric and mechanical resonators, while also providing excellent performance, are relatively expensive.

SAW filters cannot be easily detuned because their properties are established when they are fabricated. However, variations in temperature can affect transducer and substrate geometry through thermal expansion, and therefore affect filter performance. Thermal expansion of the substrate can be minimized by regulating the environmental temperature and avoiding substrates that are sensitive to temperature fluctuations.

Perhaps the major drawbacks associated with SAW bandpass filters are a relatively high insertion loss (about 20 dB)⁶ and a bandwidth limited at the lower end by the size of the substrate (about 100 kHz). Loss can be reduced through the use of special transducer geometries, but not to the point where SAW bandpass filters can be used for the front-end of the IF

where the signal-to-noise ratio would be affected. SAW bandpass filters are better suited for later stages in the IF where loss would not be detrimental to the signal-to-noise performance. Bandwidth can be extended by connecting several SAW transducers in series, each operating at a different center frequency.⁷

Delay lines

Delay lines, traditionally constructed of transmission lines or equivalent components, are used to delay a signal for a predetermined length of time. Delay lines have a variety of applications, from delaying the luminance signal in the luminance channel of a color TV receiver, to compressing a received RADAR signal.

The problem with using transmission lines to delay or compress signals is that the lines must be relatively long to realize an appreciable time delay. A number of conventional solutions have been advanced to address the transmission line length problem. One approach has been the development of a special transmission line in which the center conductor is wound in a helix. Another has been to create the equivalent of a transmission line with lumped capacitors and inductors. However, both of these approaches are limited in the amount of delay that can be practically achieved. For time delays longer than a few pulse periods, SAW delay lines are used.

SAW delay lines, in the form of dispersive filters, are used primarily for pulse compression in applications where significant delays (or pulse compression) must be introduced in an environment where space is at a premium. One SAW approach to achieving pulse delays is to monotonically decrease transducer finger spacing (see **Figure 3**). For greater compression (e.g., time-bandwidth products up to 10,000), a *reflective array compressor* (RAC) design, illustrated in **Figure 9**, can be used. Discretely variable delay lines can be created by electroni-

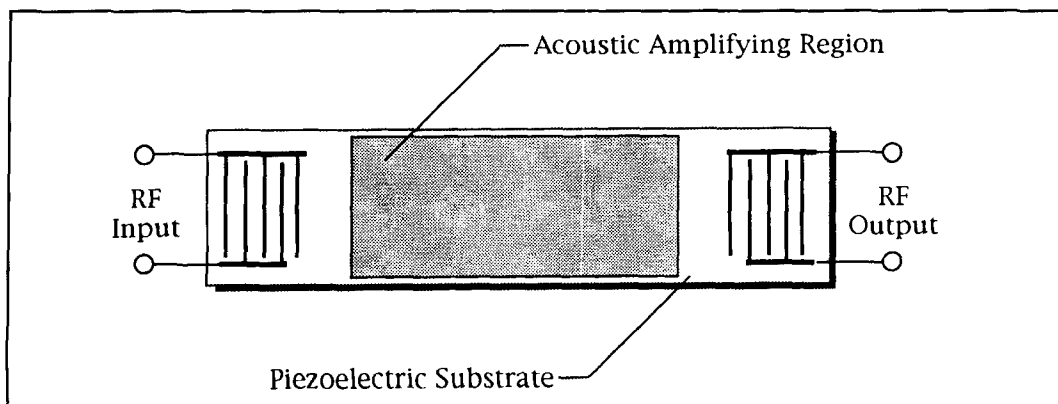


Figure 10. The basic structure of a SAW acoustic amplifier. SAW acoustic amplifiers have yet to reach the popularity of SAW filters and delay lines.

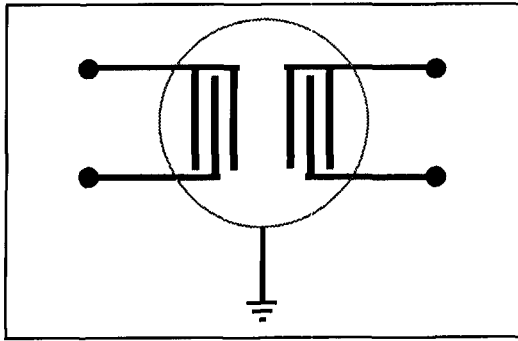


Figure 11. The schematic symbol for a SAW filter device with interdigital electrodes.

cally selecting from a set of transducers spaced along the path of the acoustic beam.

Oscillators

Of the common methods used to generate signals, including those based on phase locked loops (PLLs) and direct digital synthesis (DDS), a quartz crystal oscillator is often used to stabilize or control the frequency of oscillator circuits. However, fundamental frequency crystals are only practical up to about 25 MHz. At higher frequencies, overtone crystals or some sort of frequency multiplier must be used. In addition, quartz crystals are relatively fragile, and often require considerable mounting space.

SAW oscillators, which can be constructed by simply feeding a SAW delay line's output back to its input via an amplifier with excess

gain (see **Figure 13**), provide a number of advantages over quartz crystal and LC oscillators. Because SAW oscillators are planar devices, they are extremely space efficient and can be made mechanically rugged. Secondly, SAW oscillators can operate from about 20 MHz up to over 1 GHz. Qs on the order of 10^5 at 100 MHz and 10^4 at 1 GHz are typical. The frequency of oscillation is a function of the transducer patterns and the relative positions of the input and output transducers, and not the overall dimensions of the substrate. The substrate can therefore be constructed as thick as needed, and bonded to other objects—providing mechanical stability and a thermal sink. Because the oscillation frequency is a function of the relative separation of the interdigital transducers, SAW oscillators can be used as strain gauges, with the frequency output varying in accordance with changes in the SAW delay substrate.

Although SAW resonators can be both smaller and less expensive than traditional quartz or LC resonators, the *long-term stability* of SAW oscillators is less than that of quartz crystal oscillators. The aging rates of SAW oscillators, which can result in slight changes in input and output transducer geometry as well as relative transducer distances, are about an order of magnitude greater than crystal oscillators.

The future of SAW technology

SAW devices are becoming increasingly important in UHF and microwave communica-

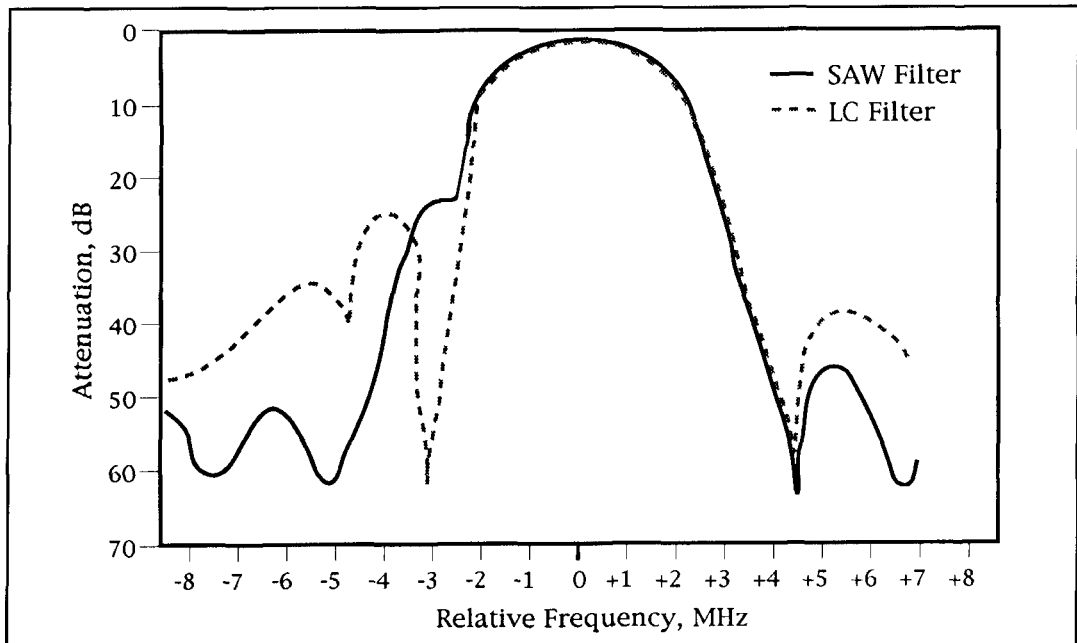


Figure 12. SAW versus conventional LC bandpass filter response. In addition to providing a relatively flat in-band response, properly designed SAW bandpass filters introduce negligible phase deviation.

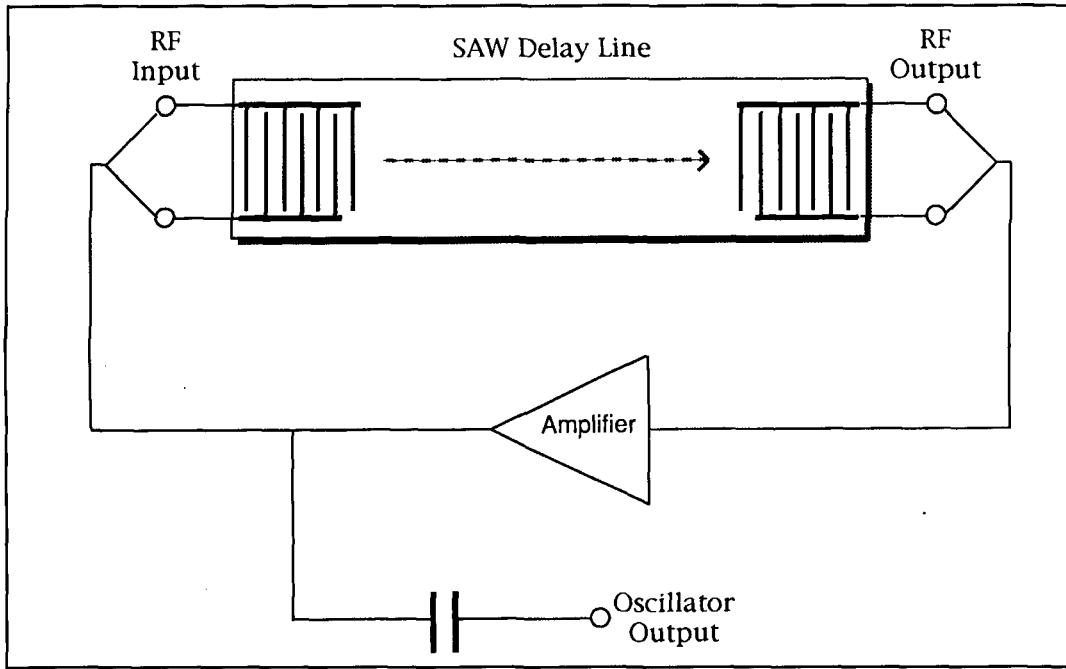


Figure 13. A basic SAW oscillator can be constructed by feeding the output of a SAW delay line back to its input via an amplifier.

tions. They can be used to reduce cost and size, while simultaneously improving reliability of communications systems. SAW technology shows particular promise in spread spectrum communications, owing to the wide bandwidths and high operating frequencies supported by SAW devices.

Although SAW devices are not obviously superior to some competing technologies, like direct digital synthesis, they have the edge in applications requiring ruggedness and reliability over other considerations. In addition, SAW devices have the added advantage of simplicity. Like DDS, one advantage of using SAW filters is that they can be designed and replicated with ease; amplitude and phase specifications can be met by a single filter. Similarly, SAW devices are stable, do not require adjustment, and can be interfaced with standard IC amplifiers. As is the case with all modern electronic components, further size reductions in SAW devices can be expected. Current SAW filters designed for cellular phones are about the size of SMT capacitors and resistors.

SAW devices are finding a variety of applications in electronic warfare. For example, SAW devices are used to provide simple time delay, frequency dependent time delay, discretely variable time delay, bandpass filtering, and generation and recognition of various coded waveforms. SAW devices, in the form of tapped surface wave delay lines, can be used to generate both frequency hopped and pseudo noise phase modulated signals for spread spectrum communications. There are also applica-

tions of acoustic digital memories, similar in operation to charge-coupled devices, but operating at hundreds of MHz.

For those who want to learn more about the SAW technology, there are a number of excellent texts available. The work by Mario³ provides a good introduction to the basics of electromechanical coupling involved in electroacoustic transducers. For more in-depth information on the physics of electroacoustic transducers see the texts by Zdenek,⁸ Merhaut,⁹ and Rosenbaum.¹⁰ The text edited by Matthews¹¹ provides an outstanding description of the physics relevant to the design and construction of SAW filters. ■

REFERENCES

1. J. Feinstein, R. Nelson, G. Farney, D. Preist, A. Scott, and P. Walchli, "UHF and Microwave Devices," *Electrical Engineering Handbook*, Fink and Christiansen editors, 1986, McGraw-Hill, New York.
2. G. Weiss, "Electrical Transducers," *Handbook for Modern Electronics and Electrical Engineering*, Belove, Hopkins, Nelson, Rosenstein, and Shinnars editors, 1986, John Wiley & Sons, New York.
3. R. Mario, *Acoustics and Electroacoustics*, 1988, Artech House, Inc., Norwood, Massachusetts.
4. R. Mitchell, "Surface Acoustic Wave Transversal Filters: Their Use and Limitations," *Component Performance and Systems Applications of Surface Acoustic Wave Devices*, 130-9, 1973.
5. P. Horowitz and W. Hill, "High-frequency and High-speed Techniques," *The Art of Electronics*, 1980, Cambridge University Press, Cambridge, Massachusetts.
6. L. Hoke, "Television Broadcast Receivers," *Electrical Engineering Handbook*, Fink and Christiansen editors, 1986, McGraw-Hill, New York.
7. R. Velimir, *Principles of Acoustic Devices*, 1983, John Wiley & Sons, Inc., New York.
8. S. Zdenek, *Vibrating Systems and Their Equivalent Circuits*, 1990, Elsevier Science Publishing Company, Inc., New York.
9. J. Merhaut, *Theory of Electroacoustics*, 1981, McGraw-Hill, Inc., New York.
10. J. Rosenbaum, *Bulk Acoustic Wave Theory and Devices*, 1988, Artech House, Inc., Norwood, Massachusetts.
11. H. Matthews, *Surface Wave Filters: Design, Construction, and Use*, 1977.

QUARTERLY DEVICES

The Harris Semiconductor HFA3600 Low-noise Amplifier/Mixer

Building a good UHF receiver has always been a challenge. However, the 900-MHz consumer-electronics revolution continues to generate a windfall of special-purpose chips that makes the job easier. In this edition of "Quarterly Devices," we'll look at a new offering from Harris Semiconductors—the HFA3600 Low-noise Amplifier/Mixer.

General description

The HFA3600 is a sensitive 800 to 1000-MHz down-converter on a chip that features a 50-ohm input impedance, 2.3-dB noise figure LNA, and active mixer. By combining these

critical receiver elements into a single 14-pin SOIC package, Harris engineers have lowered the external parts count and removed much of the "touchiness" inherent in UHF front-end design. Combined LNA/mixer intercept performance is a respectable -16.7 dBm (referred to input), and the LO drive requirement is relatively low—around -3 dBm. Like many newer consumer-application chips, the HFA3600 runs on 4 to 5 volts and provides an integrated power-down function to conserve battery life in handheld products. Typical power-on state consumption is just over 11 mA.

Figure 1 shows the HFA3600's internal block diagram. The LNA is internally optimized for direct 50-ohm input. A collector spiral inductor improves stability at lower frequencies while optimizing gain in the 900-MHz range (see **Photo A** for an inside look). In addition to a 2.3-dB noise figure, the LNA section provides nearly 13 dB power gain with a third-order output intercept of $+12.8$ dBm.

The HFA3600's single-balanced active mixer features open-collector output. This gives designers the flexibility to set conversion gain and match the device into a wide range of IF filters. At -3 dBm LO injection, mixer conversion gain is around 7 dB with a third-order output intercept point of $+3.2$ dBm.

To ensure stability and consistent performance, LNA and mixer bias currents are laser-trimmed to hold within 1 percent over the device's temperature range. The bias network is gated to provide a fast-switched power-down mode for battery-powered or TDM (time-division multiplex) applications. Standard TTL-level input controls the gate, reducing current consumption to 250 μ A when logic zero is applied. Although characterized as a 5-volt device, the HFA3600 operates comfortably at 4 volts with minimal degradation in performance.

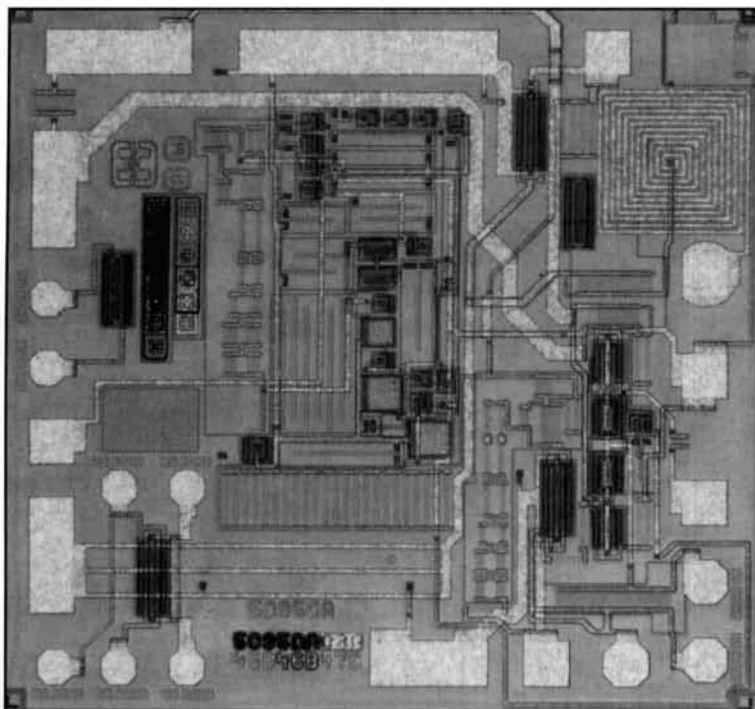


Photo A. Inside the HFA3600.

Detailed operating parameters are presented in **Table 1**.

A typical circuit

Figure 2 illustrates a typical down-converter application circuit. The device's input frequency range, which is established by the LNA's internal network, covers from 800 to 1000 MHz. IF output can range anywhere from 45 to 200 MHz—depending on the frequency of the 1st LO signal. Synthesized or continuously tunable receivers operating in the IF region may be used as tunable IFs.

Supply Vcc for the LNA section goes to pin 1. Appropriate RF and low-frequency bypassing is used to decouple the Vcc line.

Pins 2, 4, 5, 10, and 12 are bonded to the pc groundplane. Ground pins are strategically placed to help isolate the various input and output ports on the device.

Pin 3, the LNA's input port, must be AC-coupled to the 50-ohm antenna line. Note that all AC-coupled inputs and outputs require a minimum coupling capacitance of 100 pF; a value of 1000 pF is suggested in the application note. SMD chips are a must at these frequencies.

Pins 6 and 7 make up the LO port. The bypass capacitor on pin 6 must be positioned as close to the device as possible. LO input goes to pin 7 through a coupling capacitor.

The device's power-down function is controlled at pin 8. This can be driven by TTL or

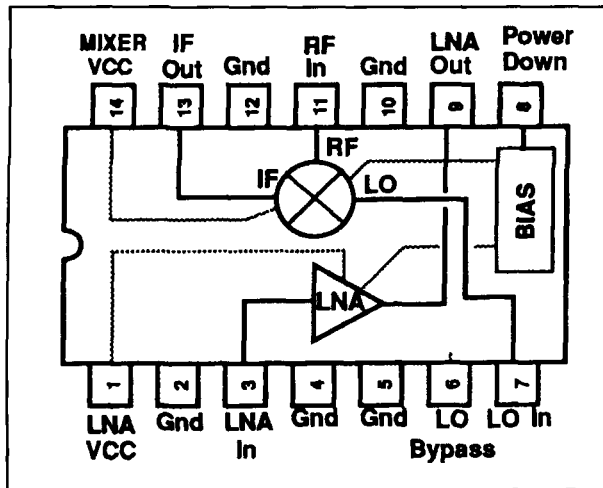


Figure 1. Internal block diagram of the HFA3600.

CMOS-level logic. Logic-low input invokes the power-down mode. An internal pull-up is provided to enable the chip when pin 8 is left open.

Pin 9 is the LNA's output port. In most applications, this will be looped to the mixer's RF-input port at pin 11 through a 50-ohm image filter. The image filter rejects unwanted UHF signals occurring on the image side of the LO, preventing them from entering the mixer. (Note: The image filter is typically of a bandpass configuration.)

Pin 13 is the mixer's IF output port. Because this is an open-collector circuit, Vcc is supplied externally through a resistor. Resistor value

DC Electrical Specifications								
SYMBOL	PARAMETER	CONDITION	TEST LEVEL	TEMP	ALL GRADES			UNITS
					MIN	TYP	MAX	
I _{CC}	Total Supply Current @ 5V	Normal PD= 2V	A	25°C		11.3	12.5	mA
		Shutdown PD =0.8V	A	25°C		250	375	μA
V _{IH}	Shutdown Logic High	Normal Mode	A	25°C	2		V _{CC}	V
V _{IL}	Shutdown Logic Low	Shutdown Mode	A	25°C	-0.3		0.8	V
I _{IL}	Shutdown Input Current	PD = 0.4V	A	25°C	-200	-150	-100	μA
I _{IH}	Shutdown Input Current	PD = 2.4V	A	25°C	-45	-24	-3	μA
V _{LNA-IN}	LNA Input DC Level	Normal Mode	A	25°C		0.79		V
		Shutdown Mode	A	25°C		0.37		V
V _{LNA-OUT}	LNA Output DC Level	Normal Mode	A	25°C		4.9		V
		Shutdown Mode	A	25°C		5.0		V
V _{MX-RF}	Mixer RF _{in} DC Level	Normal Mode	A	25°C		0.79		V
		Shutdown Mode	A	25°C		tbd		V
V _{MX-LO}	Mixer LO _{in} DC Level	Normal Mode	A	25°C		2.1		V
		Shutdown Mode	A	25°C		tbd		V
t _{ON-OFF}	Shutdown On-Off time		B	25°C		10		μs

Table 1. HFA3600 operating specs. (Continued on next page)

AC Electrical Specifications

All characterization results have been obtained with the use of a standard evaluation board.

SYMBOL	PARAMETER	TEST LEVEL	TEMP	ALL GRADES			UNITS
				MIN	TYP	MAX	
LNA ($V_{CC} = +5V$, $T_A = 25^\circ C$, Test Figure 1 and $f = 900MHz$ unless otherwise noted in characterization curves)							
S_{21LNA}	LNA Gain	B	+25°C	11.8	12.8	13.8	dB
S_{12LNA}	LNA Reverse Isolation	B	+25°C		23		dB
S_{11LNA}	LNA Input Return Loss	B	25°C	6.0	7.3		dB
S_{22LNA}	LNA Output Return Loss	B	25°C	10.0	13.0		dB
$P_{-1dB LNA}$	LNA Output 1-dB Gain Compression Point	B	25°C		-2.0		dBm
IP_{3LNA}	LNA Output 3rd-order Intercept	B	25°C	+11.2	+12.8		dBm
NF_{LNA}	LNA Noise Figure	B	25°C		2.30	2.60	dB
MIXER ($V_{CC} = 5V$, $T_A = 25^\circ C$, $f_{LO} = 825 MHz @ -3 dBm$, $f_{RF} = 900 MHz$, $f_{IF} = 75 MHz$ and Test Figure 1 unless otherwise noted)							
PG_C	MIXER Power Conversion Gain	B	25°C	5.9	7.0	8.1	dB
S_{11RF}	MIXER RF Input Return Loss	B	25°C	8.0	11.0		
S_{11LO}	MIXER LO Input Return Loss	B	25°C	18.0	26		dB
NF_{MIXER}	MIXER SSB Noise Figure	B	25°C		12.1	13.9	dB
$P_{-1dB MIX}$	MIXER Output 1-dB Gain Compression	B	25°C		-7.5		dBm
IP_{3MIX}	MIXER Output 3rd-order Intercept	B	25°C	+1.0	+3.2		dBm
C_{OUTMIX}	MIXER IF Output Capacitance	B	25°C		2.3		pF
G_{RF-IF}	MIXER RF-IF Isolation (includes matching network)	B	25°C		25		dB
G_{LO-IF}	MIXER LO-IF Isolation (includes matching network)	B <td 25°C		16		dB	
G_{LO-RF}	MIXER LO-RF Isolation	B	25°C	16	21		dB
$G_{LO-LNAin}$	Mixer LO-LNA _{in} Isolation	B	25°C	42	50		dB
$G_{LNAout-RF}$	LNA _{out} -Mixer RF _{in} Isolation	B	25°C	35	40		dB
(LNA + MIXER) $V_{CC} = 5V$, $T_A = 25^\circ C$, $f_{LO} = 825 MHz @ -3 dBm$, $f_{RF} = 900 MHz$, $f_{IF} = 75 MHz$ and idealized lossless external filters							
CPG_C	Power Conversion Gain	B	25°C		19.8		dB
CNF	Noise Figure	B	25°C		3.97		dB
CIP_3	Input 3rd-order Intercept	B	25°C		-16.7		dBm

Table 1. HFA3600 operating specs.


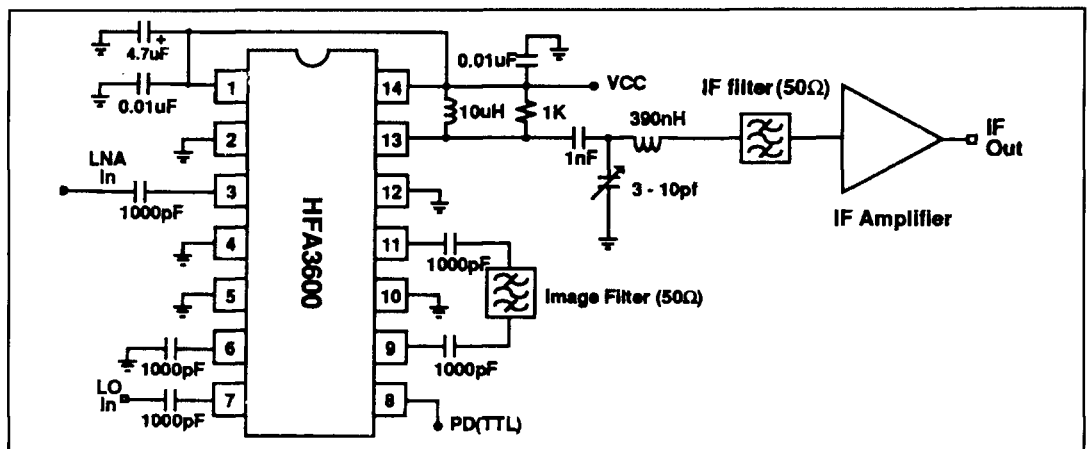


Figure 2. Typical circuit.

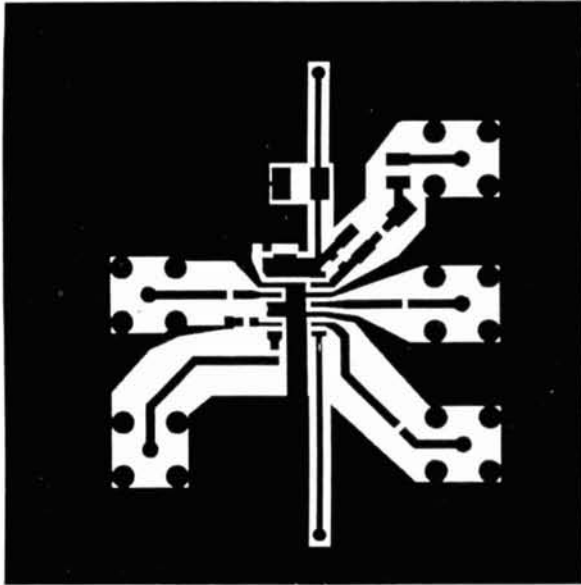Evaluation Board layout. Scale X1 Top View



Component List.

R1 Res, fixed 1KW

L1 Ind., fixed 10uH

L2 Ind., fixed 390nH

C3,C4,C5,C7,C10,C11 Cap, fixed 1nF

C1,C6 Cap, fixed .01uF

C2 Cap, fixed Tantalum. 4.7uF

C8 Cap, var. 3 to 10pF

Cr1 Diode DL4001

Evaluation board Component Placement

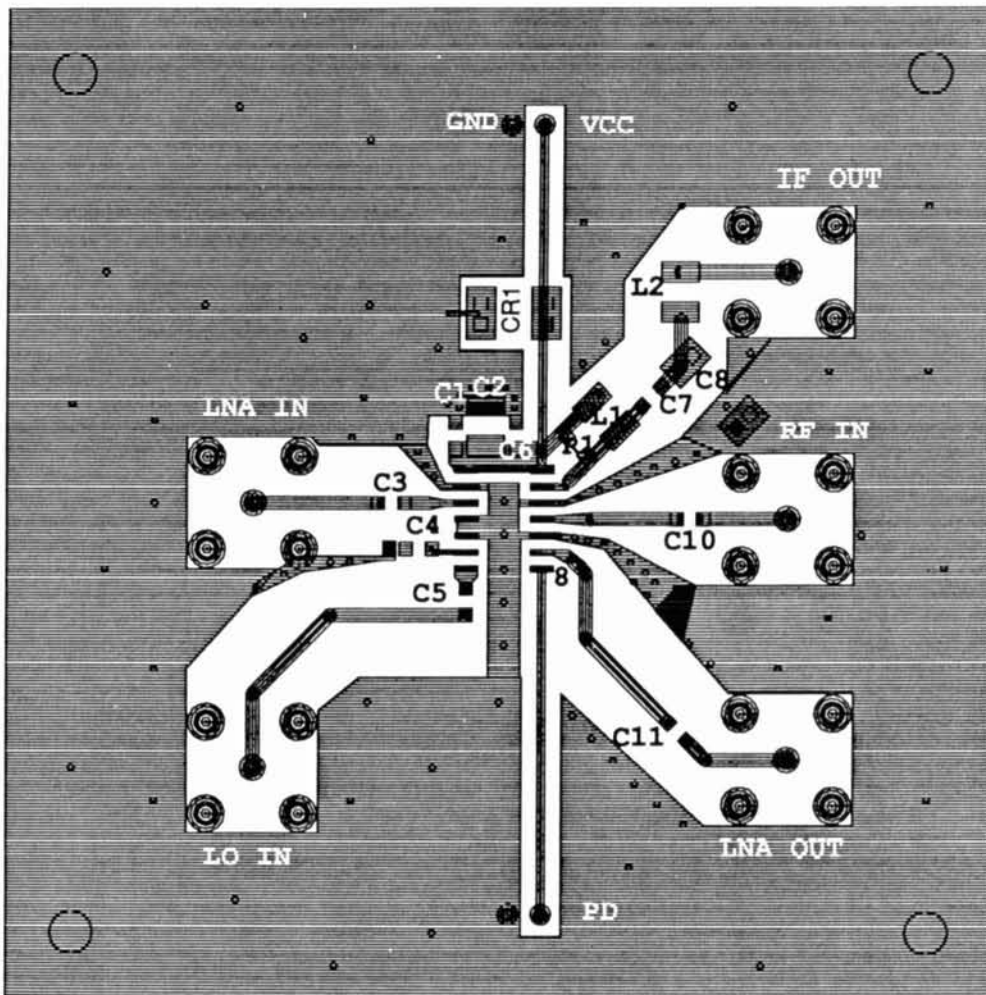


Figure 3. Board layout for experimentation.

will determine mixer conversion gain and IP3. (Acceptable values range from 300 to 1500 ohms, with smaller values providing less gain and a lower output impedance.) An optional 10- μ H RF choke may be installed in parallel with the resistor to lower DC resistance and increase output swing. Some form of impedance transformation is recommended when feeding a 50-ohm IF system.

Vcc to pin 14 powers both the RF mixer and bias network portion of the chip. Note that 0.01 bypasses are shown at *both* Vcc inputs (1 and 14). These must be positioned as close as possible to their respective pins and provide a direct low-impedance path to pc ground.

Although an integrated device like the HFA3600 can greatly simplify UHF construction, you must still adhere to sound 900-MHz RF-design practices. For example, non-stripline traces must be short and direct—with angles or pads shaped or chamfered for minimum parasitic contribution. Chip capacitors and resistors are a must, and pc-board dielectric should be suitable for 1-GHz circuitry. To achieve optimum gain and stability, use two-sided board with abundant feedthroughs to solidify the groundplane. **Figure 3** provides a board layout suitable for general experimentation. When the HFA3600 is used in a single channel application or in conjunction with a tunable IF, a crystal-controlled UHF-transmitter IC like the Motorola MC13176 can provide a simple and stable 700-MHz LO source (see "Quarterly Devices," Fall 1993).

Applications

The HFA3600 is primarily designed for use in portable cellular phones, wireless data transceivers, UHF mobile radios, cordless phones, and wireless telemetry. However, the HFA3600

should work equally well in any specialized communication project that requires a UHF receiver front end. Here are a few possibilities:

- Transverters for 900-MHz SSB service.
- ATV down-converters for TV receivers.
- Repeater control-channel and voice-uplink receivers.
- Packet backbone data receivers.
- Spread-spectrum equipment.
- TDM-multiplexed digital-audio transceivers.
- Block down-converters for VHF-range panadapters or analyzers.
- Simple 800-MHz scanner converters.

HFA3600 price and availability

The HFA3600 is presently available from Harris Semiconductor for \$3.75 each in 100 lots and \$3.56 each in 1000 lots. Application notes, samples, evaluation boards, and referrals for technical assistance are handled through the local Harris sales office in your area (to obtain the number of your local representative, call 1-800-442-7747). Small quantity purchases of the HFA3600 may be made through any Harris authorized distributors, including Newark Electronics (1-800-367-3575).

Conclusion

The 800 to 1000-MHz radio spectrum continues to be a hot area for new RF devices—with plenty of room for exploration and new-product development. If you come up with a unique HFA3600 application or construction project you'd like to share with our readers, please write to *Communications Quarterly*, P.O. Box 465, Barrington, New Hampshire 03825—or call our editorial offices at 603-664-2515. We'd love to put your name in print! ■

PRODUCT INFORMATION

New High Voltage Relay & Contactor Application And Product Guide

Kilovac Corporation has published an expanded 75 page Application and Product Guide for industrial and aerospace applications.

The new guide begins with an introduction to high voltage relays and contactors. It explains the physics of vacuum and gas-filled relays, defines relay and contactor terms, and shows, with cut away type drawings, common high voltage relay designs. It also includes information on various high voltage and power switching relay applications and the criteria that should be used to select the proper relay to ensure trouble-free performance. Special sec-

tions include RF deratings, capacitive discharge loads, power switching loads and high insulation resistance relays for test equipment.

Kilovac's Application and Product Guide introduces some of Kilovac's new 270 Vdc relays and contactors. These include the AP5 and AP10 relays, rated at 5 amps and 10 amps at 270 Vdc, respectively. Also new are the AP90 and the AP350 with 90 amp and 350 amp load switch ratings at 270 Vdc.

If you have any questions about your specific relay application, or would like to obtain Kilovac's Application and Product Guide, call 1-800-253-4560 or write Kilovac Corporation, P.O. Box 4422, Santa Barbara, CA 93140.

A NEW METHOD FOR MEASURING CABLE LOSS

Try this simple technique

In an existing antenna system, it is often necessary to measure the attenuation of the coaxial cable that connects the antenna to the transceiver—especially after many years of outdoor operation. The result can then be compared with data sheet values to see whether any deterioration has occurred. Likewise, if you install a new cable of unknown origin, you undoubtedly would like to know its true condition. However, measuring cable loss can be a frustrating endeavor, especially when the loss is small, the cable is short, or when the frequency is low.

The simplest, though not the best, way to determine the cable loss seems to be to measure the difference between input and output power of the properly matched cable with an RF wattmeter. A more accurate method is to measure the input and output voltages with an RF voltmeter. Both methods require a power source, proper impedance matching, and instruments that, in most cases, the amateur does not have. Ground currents in the test setup and mismatch errors can cause false readings if you consider that the difference between input and output voltage is only 0.89 percent for an RG-213 cable, 2 meters long, at a frequency of 28 MHz. It is not unusual to measure a larger output power than input power.

There is a useful method that is especially suitable for short cables (see **Reference 1**). It is based on the fact that the ratio of input to output voltage of an unterminated, quarter-wavelength cable driven from a low impedance source, is nearly equal to the cable loss in nepers (1 neper = 8.69 dB). However, for this

test you need a power source, a little test fixture consisting of an amplifier and cable driver, and access to both ends of the cable at this fixture.

It is therefore desirable to have a method that does not require costly instruments, cable matching, terminations, and that is simple, fast, and accurate.

The method that meets these requirements is based on the fact that the maximum of the real part of the input impedance of an unterminated or shorted cable is directly proportional to the cable loss in nepers.

Figure 1 is a plot of the real and imaginary part of the cable input impedance $Z_{IN} = R_{IN} + jX_{IN}$ for an unterminated cable, plotted versus frequency. It shows that the input resistance R_{IN} has a maximum value at frequencies that are multiples of the frequency at which the cable is half a wavelength long. The reactive part, X_{IN} , is zero at these points. Calculations show that R_{max} is directly proportional to the cable loss in nepers. The value of R_{max} decreases with successive peaks whereas R_{min} increases with increasing frequency.

How to measure R_{max}

The ideal instrument for measuring R_{max} is the noise bridge. Because the reactive part is zero at R_{max} , the reactance dial must be set to zero. Because R_{max} in most cases exceeds the R range of the bridge, you must shunt the cable input with a resistor to bring it into range. If, for instance, the R range of the bridge is 250 ohms, you can use a noninductive 240-ohm resistor in parallel with the cable. If the resistance reading

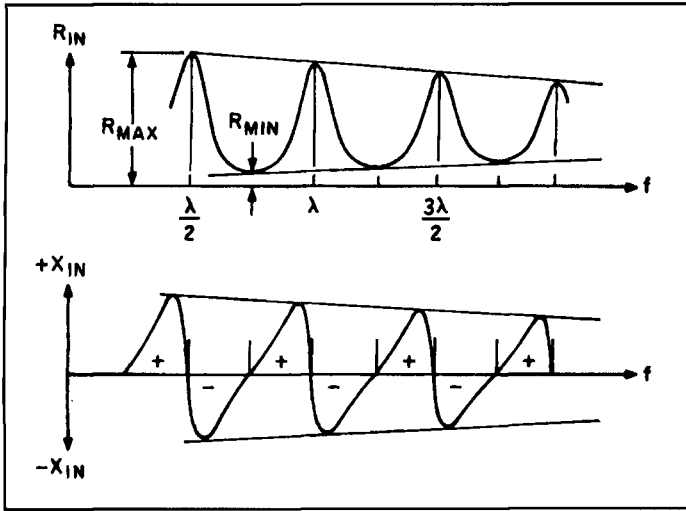


Figure 1. Plot of the real and imaginary part of the cable input impedance $Z_{IN} = R_{IN} + jX_{IN}$ for an unterminated cable, plotted versus frequency.

of the bridge for null then is, for example, 200 ohms, the R_{max} is actually 1200 ohms.

Calculating cable attenuation

Now we must prove that we can calculate the cable loss from R_{max} . The basic transmission line formula for the input impedance is given below and illustrated in **Figure 2**:

$$Z_{IN} = \frac{Z_L + Z_0 \tanh(a + jb)}{1 + \frac{Z_L}{Z_0} \tanh(a + jb)} \quad (1)$$

where Z_L is the load impedance, Z_0 is the characteristic cable impedance, a is the cable loss in nepers, and b is the cable length, expressed in electrical degrees. If we assume $Z_L = \infty$ (open cable output), the formula simplifies to:

$$Z_{IN} = \frac{Z_0}{\tanh(a + jb)} \quad (2)$$

We proceed by using the identity:

$$\tanh(a + jb) = \frac{\sinh 2a + j \sin 2b}{\cosh 2a + \cos 2b}$$

Because the electrical cable length at the half-wavelength frequency is $b = 180$ degrees, $\sin(2b) = 0$, and $\cos(2b) = +1$, the formula simplifies to:

$$\tanh(a + jb) = \frac{\sinh 2a}{\cosh 2a + 1}$$

The formula for Z_{IN} now becomes:

$$Z_{IN} = R_{MAX} = Z_0 \frac{\cosh 2a + 1}{\sinh 2a} \quad (3)$$

This shows that the reactive part of Z_{IN} is zero at the point where $Z_{IN} = R_{max}$ and that the input impedance is a pure resistance that can be measured easily with the noise bridge. Using the known identities:

$$\sinh 2a = \frac{e^{2a} - e^{-2a}}{2}$$

$$\cosh 2a = \frac{e^{2a} + e^{-2a}}{2}$$

Equation 3 now becomes:

$$\frac{R_{MAX}}{Z_0} = \frac{e^{2a} + e^{-2a} + 2}{e^{2a} - e^{-2a}}$$

Multiplying numerator and denominator by e^{2a} , we have:

$$e^{4a} - e^{2a} \frac{2Z_0}{R_{MAX} - Z_0} - \frac{R_{MAX} + Z_0}{R_{MAX} - Z_0} = 0$$

Because e^{4a} is the square of e^{2a} , we have a quadratic equation for e^{2a} that allows us to calculate the cable loss. Its solution is:

$$e^{2a} = \frac{Z_0}{R_{MAX} - Z_0} +$$

$$\sqrt{\left(\frac{Z_0}{R_{MAX} - Z_0}\right)^2 + \frac{R_{MAX} + Z_0}{R_{MAX} - Z_0}}$$

or

$$a = \frac{1}{2} \ln \left\{ \frac{Z_0}{R_{MAX} - Z_0} + \right. \quad (4)$$

$$\left. \sqrt{\left(\frac{Z_0}{R_{MAX} - Z_0}\right)^2 + \frac{R_{MAX} + Z_0}{R_{MAX} - Z_0}} \right\} \text{ nepers}$$

where Z_0 is the characteristic cable impedance and R_{max} is the input resistance as measured with the noise bridge.

Calculating cable loss for the shorted cable

The equation above was derived for the

unterminated cable. However, the principle can also be applied to the shorted cable, as shown in **Figure 3**.

The input impedance of the shorted transmission line is:

$$Z_{IN} = Z_0 \tanh (a + jb) \quad (5)$$

The input resistance maxima now occur at odd multiples of the quarter-wave frequency. In this case, the value of b is 90 degrees and $\sin(2b) = 0$, but $\cos(2b) = -1$. The quadratic equation for e^{2a} now becomes:

$$e^{4a} - e^{2a} \frac{2R_{MAX}}{R_{MAX} - Z_0} + \frac{R_{MAX} + Z_0}{R_{MAX} - Z_0} = 0$$

and the cable attenuation for the shorted cable is:

$$a = \frac{1}{2} \ln \left\{ \frac{R_{MAX}}{R_{MAX} - Z_0} + \right. \quad (6)$$

$$\left. \sqrt{\left(\frac{R_{MAX}}{R_{MAX} - Z_0} \right)^2 - \frac{R_{MAX} + Z_0}{R_{MAX} - Z_0}} \right\} \text{ neper}$$

Although **Equation 6** looks quite different from **Equation 4**, it delivers exactly the same results. You can use either formula, regardless of whether the cable is open or shorted.

Practical example

Let us examine an RG-213 cable 33.238 meters long, unterminated, with a nominal velocity constant of 0.66. This cable will be one wavelength long at 5.957 MHz:

$$f_0 = \frac{300 \times 0.66}{33.238} = 5.957 \text{ MHz}$$

Because the velocity factor may not be exactly 0.66, the measurement frequency may need to be varied to find the exact value that gives R_{max} . (The purpose of this calculation is to aid in finding R_{max} ; the actual frequency is not needed in the formula.) The noise bridge is used to measure R_{max} . Because R_{max} may exceed the range of the noise bridge, a noninductive resistor is placed in parallel with the cable input. I recommend use of the highest possible resistor value that can *just* be measured with the bridge. If, for instance, the bridge potentiometer has 250 ohms, a resistor between 240 and 250 ohms would be best. Here is the measurement procedure:

First, set the reactance dial of the bridge to the zero point, because the reactive part of Z_{IN}

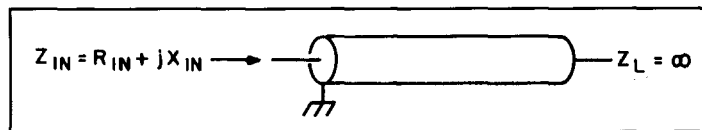


Figure 2. The basic transmission line formula for the input impedance.

is zero for $R_{IN} = R_{max}$. Do this by connecting a 240-ohm resistor at the X terminal of the bridge. Assuming a measuring frequency of 4 x 5.957 MHz, tune the receiver approximately to this frequency and null the bridge. The reactance dial is now set to zero—a setting that does not necessarily agree with the dial.

Second, measure the value of the variable bridge resistor with a digital multimeter. The reading should be 240 ohms, but it will deviate in most cases. If the reading is, for instance, 247.4 ohms, the readings are too high and must be reduced by a factor of $240/247.4 = 0.97$. I recommend this resistance check because most noise bridges are rather inaccurate at the higher resistance values.

Third, connect the coax cable in parallel with the 240-ohm resistor at the X terminal and null the bridge without touching the reactance dial. Do this by adjusting R and, if required, the frequency until you obtain a deep noise minimum. Measure the variable resistor of the noise bridge with the DVM once again. In our example, the reading is 154.6 ohms. The corrected value is then $154.6 \times 0.97 = 150$ ohms.

Fourth, calculate R_{max} . Because R_{max} and the 240-ohm resistor are in parallel, the formula

$$\frac{R_{MAX} \times 240}{R_{MAX} + 240} = 150 \text{ ohm gives } R_{MAX} = 400 \text{ ohm}$$

yields $R_{max} = 400$ ohms

Thus, **Equation 1** becomes:

$$a = \frac{1}{2} \ln \left(\frac{50}{400 - 50} + \right.$$

$$\left. \sqrt{\left(\frac{50}{400 - 50} \right)^2 + \frac{400 + 50}{400 - 50}} \right) = 0.1256 \text{ neper}$$

Because 1 dB = 0.115 neper, the cable loss in dB is $0.1256/0.115 = 1.093$ dB or $(1.093 \times 30.48)/33.238 = 1$ dB per 100 feet. The data sheet value for this frequency is 1.1 dB.

If you want to find the cable loss at another frequency, disconnect the cable briefly and null the bridge with the 240-ohm resistor alone at the new frequency because the zero reactance point may be different. Then proceed as before.

If your receiver does not have continuous tuning, pick one or more frequencies that pertain either to multiples of the half-wavelength frequency or to odd multiples of the quarter-

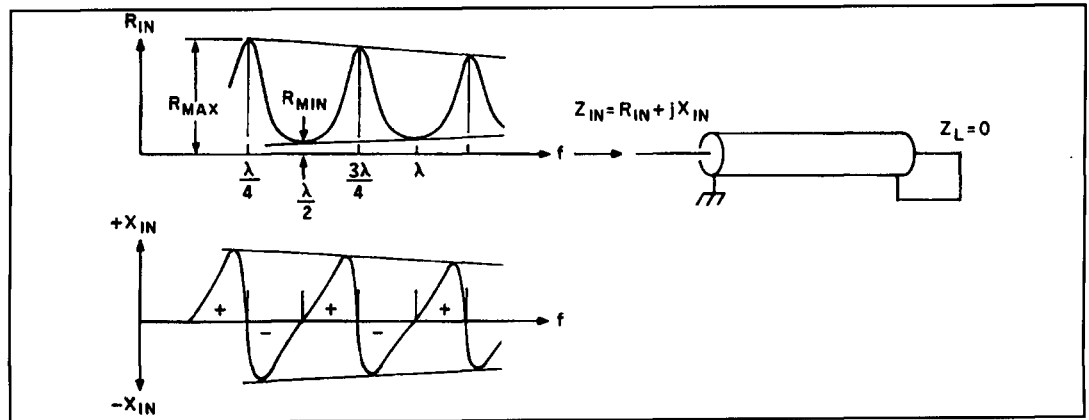


Figure 3. The equation derived for the unterminated cable can also be applied to the shorted cable.

wavelength frequency that will then be covered by the receiver.

Calculating loss at other frequencies

So far we have calculated the loss for only one frequency. But if you make another measurement at another frequency, you will have two sets of attenuations, a_1 and a_2 , and two frequencies, f_1 and f_2 . Using the interpolation method described by K2BT,² you can calculate the loss at any other frequency using the following procedure.

First, calculate two constants m and n :

$$m = \frac{a_1 f_2 - a_2 f_1}{f_2 \sqrt{f_1} - f_1 \sqrt{f_2}} \quad n = \frac{a_2 \sqrt{f_1} - a_1 \sqrt{f_2}}{f_2 \sqrt{f_1} - f_1 \sqrt{f_2}}$$

The cable loss at a_3 at the frequency f_3 is then:

$$a_3 = m \sqrt{f_3} + n f_3$$

Measurement accuracy

Measurement accuracy depends mainly on the accuracy of the R dial readings for large resistance at the operating frequency. Because your noise bridge may not be accurate enough, I recommend measuring the actual value of the noise bridge variable resistor after balancing with a DVM. Because there are several measuring frequencies available for a given cable, I recommend using the highest possible frequencies because the R_{\max} value is lower and therefore easier to measure with the noise bridge.

Calculations and measurements indicate that a 5-ohm error in the noise bridge reading for an 18-meter long RG-213 cable at a frequency of 30 MHz causes an 11 percent error in the loss calculation. However, the resistance error is generally much smaller than 5 ohms if you use a digital multimeter to measure the actual noise bridge resistance.

If you add the parallel resistor with a T-con-

ductor, the added parasitic capacitance has a negligible effect on R_{\max} and the frequency if the reactance dial zero setting is determined with the T-connector in place. Inspection of **Equation 1** shows that an error in the assumed characteristic impedance of 10 percent results in an approximately equal error in a .

Summary

This method of measuring the cable loss is based on the fact that the maximum value of the input resistance is directly dependent on the cable loss and can be used to calculate the latter accurately. Measurements can be made at multiples of the half-wavelength frequency when the cable is unterminated, or at odd multiples of the quarter-wavelength frequency if the cable output is shorted. Both formulas give the same results. The method is simple, delivers excellent results, and doesn't require any instruments on the antenna side of the cable. Measurements can be made from the shack! No impedance matching or terminations are required and only a noise bridge is needed. Even noise bridges with questionable accuracy can give good results if you measure the noise bridge resistance with a DVM after nulling, and if you determine the zero-reactance point with the parallel resistor before the test. Thus, calibration errors of the reactance dial are eliminated.


For very short cables, the accuracy suffers because the noise bridge readings are less reliable when the cable input resistance is very high. In this case, the method described in **Reference 1** is most useful. In general, R_{\max} varies between a few hundred and several thousand ohms.

Practical cable tests, together with the interpolation method, produced excellent agreement with measurements using power meters on both cable ends. The new method is also a very useful application of the noise bridge.

REFERENCES

1. A.E. Popodi, AA3K/OE2APM, "A Novel Method for Measuring Cable Attenuation," *Ham Radio*, May 1989, pages 65-73.
2. Forrest Gehrke, K2BT, "Real Coax, Impedance, and Phase Relationships," *Ham Radio*, April 1987, pages 8-14.

VERSATILITY PLUS +

 

L.L. Grace introduces our latest product, the **DSP-12 Multi-Mode Communications Controller**. The **DSP-12** is a user programmable, digital signal processing (DSP) based communications controller.

FEATURES

- Multi-tasking operating system built in
- PC-compatible (V40) architecture allows development of custom applications using normal PC development tools and languages
- Motorola DSP56001 DSP processor
- Serial interface speeds from 110 to 19200 bps
- Optional 8-channel A-to-D & DAC for voice and telemetry applications
- 12-bit conversion architecture
- V40 source code and schematics available
- RAM expandable to one megabyte. Useable for mailbox feature, voice mail and development
- EPROM expandable to 384k bytes
- Low power requirements: 10-15vdc, 750ma
- 3 analog radio connectors. RX & TX can be split in any combination. Programmable tuning outputs are available on each connector
- Many modems available in the basic unit, including Packet, RTTY, ASCII, and PSK modems for high speed packet and satellite work
- Both V40 and DSP programs can be down-line-loaded from your PC or a bulletin board. You can participate in new development!
- Built in packet mailbox
- V40 and DSP debuggers built in
- Open programming architecture
- Free software upgrades
- Low cost unit
- Room for future growth

APPLICATIONS

- HF Packet
- HF RTTY & ASCII, including inverted mark/space and custom-split applications
- VHF Packet
- 400bps PSK (satellite telemetry)
- 1200bps PSK (satellite & terrestrial packet)
- V26.B 2400bps packet
- 9600bps direct FSK (UO-14)
- Morse Code

CUSTOM APPLICATIONS

- Voice compression
- Telemetry acquisition
- Message Store-and-Forward
- Voice Mail

COMING ATTRACTIONS

(Remember, software upgrades are free!)

- WEFAX and SSTV demodulators
- NAVTEX
- AMTOR and SITOR
- Multi-tone Modems
- ARINC ACARS

Commercial inquiries are welcomed. We offer rapid prototyping of custom commercial, civil, and government applications including intelligent radio, wireline, and telephone modems.

DSP-12 Multi-mode Communications Controller	\$ 595.00
One Megabyte RAM Expansion Option	149.00
Date/Time Clock Backup Option	29.00
8-Channel A-To-D Telemetry/Experimentation Option	49.00
Wall-Mount Power Supply for DSP-12 (110 vac)	19.00

We accept MasterCard & VISA and can ship C.O.D. within the USA. All orders must be paid in US Dollars. Shipping & Handling: \$5 (\$20 International).

L. L. Grace Communications Products, Inc.

41 Acadia Drive, Voorhees, NJ 08043, USA

Telephone: (609) 751-1018

FAX: (609) 751-9705


Compuserve: 72677,1107

1/91

L. L. Grace also manufactures the Kansas City Tracker family of satellite antenna aiming systems. Call or write for more information.

Now from CQ, the Leader in Innovative
Amateur Radio Products . . .

THE CQ 1994 AMATEUR RADIO ALMANAC

 

Get in on the action! With over 500 pages of facts, figures, tables and information on Amateur Radio, the 1994 Amateur Radio Almanac is the authority.

Specially
Priced at Only
\$19.95

The Source for everything you want to know about Amateur Radio!

The Source

- Year in Review
- Rules & Regs • Repeaters
- The Biggest, Fastest, Furthest • Geographic Stats
- Propagation • Awards • Contests • Space
- Postal Regs • Useful Tables • Silent Keys • Thousands of Facts & Figures

OVER
500 PAGES!!

GET YOUR COPY OF CQ'S 1994 AMATEUR RADIO ALMANAC AND FIND OUT . . .

- * Who has the world's largest QSL card collection.
- * What propagation was like in the month and year you were born.
- * Why 1919 was the most important year in the history of ham radio.
- * How many hams live in your town.
- * Where the world's largest amateur antenna systems are located.
- * The location of the world's HF/VHF radio beacons.
- * The names and call signs of famous amateur radio personalities from around the world.

QTY	TITLE	UNIT PRICE	TOTAL PRICE
_____	1994 Amateur Radio Almanac	\$19.95	\$ _____
	Please add \$4 S/H.	Shipping/Handling _____	
	FREE shipping for orders over \$50.	Total _____	

Check/Money Order Enclosed _____ (make checks payable to CQ Communications)

Charge to my: MC VISA AMEX Discover

Account # _____ Exp. Date _____

Name _____ Call sign _____

Address _____

City _____ State _____ Zip _____

Please mail your orders to: CQ Communications, Inc.

76 North Broadway, Hicksville, New York 11801-9962 FAX: (516) 681-2926

ORDER TOLL FREE (800) 853-9797

Also available from your local dealer

TECH NOTES (from page 8)

of electrolyte may be present. Sea water in the sea is a particularly good electrolyte.

The HF radio referred to on the boat is a marine HF radio. It is not an amateur radio, as I don't hold the appropriate license. The radio is used for normal marine communications particularly during long ocean races and return voyages. For the interest of amateurs, the antenna system consists of a ground connection to the ocean, a manual tuner, and an antenna which consists of the back stay which holds the mast up. The length of antenna from the tuner to the top insulator is about 14 or 15 meters, with a further meter or so from the tuner down to the ground connection. The backstay acts as a random radiator and is tuned by the manual tuner. The system is useful up to about 6 to 8 MHz. Above about 6 MHz, the capacitance of the top insulator begins to look like a short circuit to the radio signal, and the system loses efficiency. For 8 MHz and above, I normally use a supplementary whip antenna in amongst the forest of other (amateur VHF and UHF) antennas on the stern rail.

I hope this brief article may be of use to someone, and hopefully it will assist others in the removal of similar problems and save some wastage in materials which would otherwise be destroyed by electrolysis. ■

PRODUCT INFORMATION

New MULTIMEC Switches


SoLiCo/mec introduces a new 1K switch option available in both illuminated and non-illuminated versions.

The square cap measures 14.3 mm and may be complimented by the addition of the 2k bezel which snaps into the designer's front panel. Depending on the position of the pc board behind the front panel, the 1k cap can be extended, flush-mounted, or be recessed within the 2k bezel.

The illuminated 1K option comes complete with high intensity LED illumination, and offers the designer the option of using interchangeable legends or standard printed graphics. The MULTIMEC switch module is totally sealed to IP-67M standards and has a mechanical life rating to 10,000,000 cycles minimum and an electrical rating of 50 mA at 24Vdc. Standard operating temperature is -40°C to +65°C. A high temperature option is available with an operating temperature of -40°C to +160°C.

For more information and/or to receive a MULTIMEC Engineering catalog, contact SoLiCo/mec, 75 Locust Street, P.O. Box 14756, Hartford, CT 06114; or call 1-800-275-7089, Fax 1-800-275-7092.

 TIRED OF PLAYING GAMES?
Finally, a practical use
for your sound card!



Passband monitoring

Signal identification and tuning

3-D surface plots & color spectrogram track frequency changes over time

Multiple open windows

Spectra Vision & Spectra Plus.

Real-time audio spectrum analyzers. Full control over FFT size, sampling rate, scaling, gain, and averaging. Requires 386 or better, Windows 3.1 and any Windows compatible 8 or 16 bit soundcard.

"-A stroke of brilliance...a groundbreaking and valuable program."-Monitoring Times

"-Knock-your-socks-off quality!"- Harold Price, QEX Magazine, Dec. '93

	Spectra Vision	Spectra Plus
Modes		
Real time	●	●
Recorder		●
Post process		●
Price	\$89 ⁰⁰	\$179 ⁰⁰

All display formats included with either package.
 60 day money-back guarantee.

Also available: 'RF Vision'. Ask us about it!

800-401-3472 fax/voice 206-697-3472

Visa, MasterCard, Check or Money Order

Pioneer Hill Software

24460 Mason Rd., Poulsbo, WA 98370
 S & H included, foreign delivery add \$10.00
 Demo disk \$4.00 (credit toward purchase)

In Australia: **ME Technologies**
 PO Box 50, Dyers Crossing NSW 2429, +61 65-50-2200
 In Sweden: **PICS Corporation**
 PO Box 37, 440 41 Nol, +46 303-42995

AMIDON Associates, INC.

W2FMI BALUNS AND UNUNS TRANSFORMERS

How to put MORE power into your antenna and get better and higher signal strength ???

- Use the all new **OUTSTANDING, HIGHEST EFFICIENCY (97% TO 99%),** and the **BEST BROADBAND UNUN (unbalanced to unbalanced) and BALUN (balanced to unbalanced) TRANSFORMERS** exclusively designed and optimized by **DR. JERRY SEVICK W2FMI.** Amidon Associates, Inc. now offers the widest selection of the **W2FMI Baluns and Ununs** to meet all your requirements for better and more consistent communication. Also available in do-it-yourself kits.

Use **UNUN** transformers for matching 50-ohm cable to:

- (1) Vertical antennas, inverted L's and ground fed slopers (all over good ground systems),
- (2) 75-OHM cable,
- (3) A junction of two 50-OHM cables,
- (4) Shunt-Fed towers performing as vertical antennas, and
- (5) The output of a transceiver of class B linear amplifier when an unfavorable VSWR condition exists.

Use **BALUN** transformers for matching:

- (1) Half-waves dipoles and inverted V's
- (2) Quad antennas
- (3) Folded dipoles
- (4) Rhombic and V antennas
- (5) Yagi beams



All designs, when used according to instructions, are guaranteed to give outstanding performances. Comparisons with other matching transformers are invited.

POWER RATING: at least 2KW continuous from 1MHz to 40 MHz.

W2FMI HIGH POWER UNUNS	IMPEDANCE MATCH	COMPLETE UNIT PRICE
2.25-1HU50	50:22.22-OHMS	\$34.95
2-1-HU50	50:25-OHMS	\$34.95
2-1-HDU50	50:22.22-OHMS	\$49.95
	50:25-OHMS	
2.25-1-HU112.5	112.5:50-OHMS	\$34.95
2-1-HU100	100:50-OHMS	\$34.95
2-1-HDU100	112.5:50-OHMS	\$49.95
	100:50-OHMS	
1.78-1-HU50	50:28-OHMS	\$34.95
1.5-1-HU50	50:32-OHMS	\$34.95
1.5-1-HU75	75:50-OHMS	\$34.95
4-1-HRU50	50:12.5-OHMS	\$49.95
4-1-HCU50	50:12.5-OHMS	\$49.95
9-1-HRU50	50:5.56-OHMS	\$49.95
9-1-HU50	50:5.56-OHMS	\$34.95
1.78-1-HDU50	50:28-OHMS	\$49.95
	50:12.5-OHMS	
	50:32-OHMS	
	50:18-OHMS	
1.56-1-HDU50		\$49.95
HMMU50(5 diff. ratios)	MULTIMATCH UNUN	\$69.95
1.78-1-HMMU50	MULTIMATCH UNUN	\$69.95
(8 different ratios)		

W2FMI HIGH POWER BALUNS	IMPEDANCE MATCH	COMPLETE UNIT PRICE
4-1-HB50	50:12.5-OHMS	\$39.95
1-1-HB50	50:50-OHMS	\$39.95
1.5-1-HB75	75:50-OHMS	\$59.95
2-1-HB100	100:50-OHMS	\$59.95
4-1-HBM200	200:50-OHMS	\$39.95
4-1-HBU200	200:50-OHMS	\$59.95
4-1-HBHT200	200:50-OHMS	\$59.95
6-1-HB300	300:50-OHMS	\$59.95
6-1-HBU300	300:50-OHMS	\$119.95
9-1-HB450	450:50-OHMS	\$119.95
12-1-HB600	600:50-OHMS	\$199.95

NOTE: OTHER BALUN & UNUN TRANSFORMERS AVAILABLE. PLEASE CALL OR WRITE FOR ADDITIONAL DETAILS.
 BOOKS: 1) "Transmission Line Transformers Design Handbooks", by Jerry Sevick, W2FMI, Amidon Associates, Inc., 1991, \$8.95 ea., 2) "Transmission Line Transformers", by Jerry Sevick, W2FMI, Amidon, 1986, \$39.95 ea.

ALSO AVAILABLE:

Iron Powder and Ferrite Products

Millions of Parts in Stock for Immediate Delivery.
 Low Cost Experimental Kits.

Call for our FREE tech. flyer.

Toroidal Cores • Shielding Beads • Shielded Coil Forms • Ferrite Rods • Pot Cores • Baluns • Etc.


AMIDON Associates, INC.

Fast reliable service since 1963
 2216 East Gladwick Street, Dominguez Hills, CA 90220
 TEL: (310) 763-5770 • FAX: (310) 763-2250



Unconditional money back guarantee for 1 year on completed unit.
SPECIAL KIT PRICE \$28.00!
CALL TODAY!

Phase 3D Will Bring:

 

Space to virtually every ham through:

- Higher power transmitters
- Higher gain antennas
- Three axis stabilization

More bands:

- Downlinks on 10 Meters, 2 Meters; 70, 13, 5, and 3 Cm.
- Uplinks on 70, 23 and 5 Cm.

Higher Orbit:

- 48,000 km. (29,000 mile), 16 hour orbit for increased coverage, and visibility for many hours each day.

Phase 3D Needs Your Help!

A contribution of just a few dollars from EVERY active amateur will insure that this new marvel gets into orbit.

Make Your Contribution Today!

You are also invited to join AMSAT and receive the AMSAT Journal so that you too, can follow the progress of Phase 3D and other exciting amateur satellite activities. Dues are just \$30 annually in the U.S. and \$36 in Canada and Mexico - \$45 elsewhere



P.O. Box 27
 Washington, D.C. 20044
 (301) 589-6062, FAX: (301) 608-3410

Also Available in PAL format

The Quad Antenna

Hams love antenna books and this book is no exception. Written by world renowned author Bob Haviland, W4MB, *The Quad Antenna* is the authoritative technical book on the design, construction, characteristics and applications of Quad Antennas. Discover how to easily build a quad antenna for your station that will help you fill your logbook with rare DX that you have only dreamed about before.

Order No. QUAD..... \$15.95



Get Started with CQ's New Video Library!

Getting Started in Contesting

Whether you're a newcomer to contesting or an experienced veteran, CQ's **Getting Started in Contesting** is for you! You'll get advice and operating tips from some of contesting's most successful competitors, including Ken Wolff, K1EA, Dick Newell, AK1A, and CQ's own contest columnist, John Dorr, K1AR. Order our contest video and watch your scores begin to climb! **Order No. VCON.....\$19.95**



NEW

Getting Started in Amateur Satellites

Learn with this video how veteran operators set up their satellite stations. Find out how to locate and track ham satellites with ease. Watch operators access current satellites and contact far ranging countries around the world. This video is filled with easy to understand advice and tips that can't be found anywhere else. **Order No. VSAT..... \$19.95**



The Packet Radio Operator's Manual

This book is written by CQ columnist and Amateur Radio Packet authority Buck Rogers, K4ABT. An all new introduction and guide to packet operation, it is the perfect single source, whether you're an advanced user or just starting out. Learn about packet radio without all the technical jargon. Also included are detailed hookups for dozens of radio/packet controller/computer combinations, making this book the definitive resource for the active packet user.

Order No. PROM..... \$15.95



Getting Started in Packet Radio

This video will help de-mystify the exciting but sometimes confusing world of packet radio. Learn how to get started using your computer on the radio. Included are step-by-step instructions on making packet contacts and using packet bulletin boards, networks and satellites. **Order No. VPAC.. \$19.95**



Getting Started in DXing

Top DXers share their experience with equipment, antennas, operating skills, and QSLing. You'll see hams work rare DX around the world. If you're new to DXing, this video is for you! All this valuable information may well give you the competitive edge you need to master the exciting world of DXing.

Order No. VDX..... \$19.95



Ham Radio Horizons: The Book

Written by Peter O'Dell, WB2D, this is a book about ham radio that every beginner can enjoy! If you want to get in on the fun and excitement of Amateur Radio, *Ham Radio Horizons* is the perfect way to get started. HRH is full of tips from expert hams in: DXing, Contesting, Serving the Public, Ham Radio in Space, Experimenting, Digital Communications — you name it! This exciting book is an excellent gift to a prospective ham or for use in your club's licensing classes and library.

Order No. BHOR..... \$12.95



Getting Started in Ham Radio

This is a fast-paced video introduction to the fascinating world of ham radio. CQ's experts show how to select equipment and antennas; which bands to use; how to use repeater stations for improved VHF coverage; the importance of grounding and the basics of soldering. How to get the most out of your station, whether it's home-based, mobile or handheld. **Order No. VHR\$19.95**



Ham Radio Horizons: The Video

This introduction to Amateur Radio is an excellent complement to the *Ham Radio Horizons* book. Enjoy seeing all aspects of ham radio ranging from what it takes (and costs) to get started to how you can get your ham license. Designed for the general public, HRH is ideal for public events, presentations to community groups and as an opening to your club's licensing courses! There's no better way to introduce someone to ham radio. **Order No. VHOR.....\$19.95**



For Fastest Service,
Order Toll Free 1-800-853-9797

Or FAX 516-681-2926 Also available at your local dealer!

CQ Communications, 76 North Broadway, Hicksville, New York 11801

The Vertical Antenna Handbook

Take advantage of the 20 years of research and practical experience of naval communications engineer Capt. Paul H. Lee, USN(ret), N6PL. Learn the basic theory, design, and practice of the vertical antenna. Discover easy construction projects such as a four-band DX vertical or a broadband array for 80 meters. Ever wonder how to build a functional directive vertical system? Paul Lee can get you started today!

Order No. VAH..... \$9.95

The Shortwave Propagation Handbook

There's simply nothing like it — the authoritative book on shortwave propagation. Developed by CQ propagation columnist George Jacobs, W3ASK and Ted Cohen, N4XX, *The Shortwave Propagation Handbook* is your source for easy-to-understand information on sunspot activity, propagation predictions, unusual propagation effects, and do-it-yourself forecasting tips. As an active ham, you can't afford to be without this one!

Order No. SPH\$9.95



1994 Amateur Radio Almanac

If you're like most hams, you'll be fascinated by the thousands of facts, tables, graphs, maps, and other information to be uncovered in the **CQ 1994 Amateur Radio Almanac**. CQ's Almanac puts it all right at your fingertips, providing a resource that you'll refer to over and over again. This is one book you can't be without!

Order No. BALM.....\$19.95

OVER 500 PAGES!!!

CALL

NEMAL FOR RF



- Connectors
- Adapters
- Cable Assemblies
- Coaxial Cable

Manufacturer Of Custom
Electronic Wire And Cable.
• Low Minimums • Quick Delivery

CALL US AT
1-800-522-2253
OR FAX YOUR REQUIREMENTS TO
1-305-895-8178

Call for your copy of our new 44-page
Cable & Connector Selection Guide.
More than 2,500 commercial and QPL
cable and connector products in stock.

NEMAL ELECTRONICS, INC.
12240 N.E. 14th AVE., N. MIAMI, FL 33161
(305) 899-0900

ELNEC Advanced Antenna Analysis Program

Fast to learn and easy to use, ELNEC lets you analyze nearly any type of antenna in its actual operating environment. Describe your antenna with ELNEC's unique menu structure and spreadsheet-like entry system and watch it make azimuth and elevation plots, report beamwidth, f/b ratio, takeoff angle, gain, and more. Save and recall antenna files. Print plots on your dot-matrix or laser printer.

ELNEC uses the full power of MININEC code but makes description, analysis, and changes worlds easier and faster. With ELNEC there's no messing with "pulses" - just tell it where on a wire you want a source or load to go, and ELNEC puts it there. And keeps it there, even if you change the antenna. ELNEC has a host of other features to make analysis fast and easy. The MaxP option extends ELNEC's capability to very complex antennas (up to 260 "pulses").

ELNEC runs on any PC-compatible computer with at least 512k RAM, CGA/EGA/VGA/Hercules, and 8/9 or 24 pin Epson-compatible or HP LaserJet/DeskJet printer. (The MaxP option requires a hard disk, coprocessor, and 640k RAM.)

There's no copy-protection hassle with ELNEC - it's not copy protected. And of course there's extensive documentation.

ELNEC is only \$49.00 postpaid. MaxP is \$25.00. (Please add \$3.00 per order for airmail outside N. America.) VISA and MasterCard orders are accepted - please include card number and expiration date. Specify coprocessor or noncoprocessor type. Order or write for more information from:

Roy Lwallen, W7EL
P.O. Box 6658
Beaverton, OR 97007

ATV CONVERTERS • HF LINEAR AMPLIFIERS

DISCOVER THE WORLD OF
FAST SCAN TELEVISION



AMATEUR TELEVISION CONVERTERS
ATV3 420-450 (GaAs-FET) \$ 49.95 Kit
ATV4 902-928 (GaAs-FET) \$ 59.95 Kit

2 METER VHF AMPLIFIERS
35 Watt Model 335A \$ 79.95 Kit
75 Watt Model 875A \$119.95 Kit
Available in kit or wired/tested

HF AMPLIFIERS per MOTOROLA BULLETINS

Complete Parts List for HF Amplifiers
Described in the MOTOROLA Bulletins
AN758 300W \$ 154.15 AR313 300W \$ 366.00
AN762 140W \$ 95.15 AR305 300W \$ 346.82
AN798 20W \$ 83.79 EB63 140W \$ 89.65
AN799 20W \$ 93.20 EB27A 300W \$ 136.80
EB104 600W \$ 371.65

New! 1K WATT 2-50 MHz AMPLIFIER
POWER SPLITTERS and COMBINERS 2.39MHz
600 Watt PEP 2-Port \$ 69.95
1000 Watt PEP 2-Port \$ 79.95
1200 Watt PEP 4-Port \$ 89.95

100 WATT 420-450 MHz PUSH-PULL
LINEAR AMPLIFIER - SSB - FM ATV
KEB67-PK (Kit) \$159.95
KEB67-PCB (PC Board) \$ 18.00
KEB67-1 (Manual) \$ 5.00

UNIVERSAL DIGITAL FREQUENCY READOUT
TK-1 (Wired/tested) \$149.95

HEAT SINK MATERIAL
Model 99 Heat Sink (6.5 x 12 x 1.6) \$ 24.00
CHS-8 Copper Spreader (8 x 6 x 3/8) \$ 22.00

We stock Hard-to-Find parts
CHIP CAPS-Kemet/ATC
METALCLAD MICA CAPS-Unelec/Semco
RF POWER TRANSISTORS
ARCO TRIMMER CAPACITORS
BROADBAND HF TRANSFORMERS

MINI-CIRCUIT MIXERS
SBL-1 (1-500Mz) \$ 6.50
SBL-1X (10-1000Mz) \$ 7.95

NEW Low Pass Filters
for Harmonics (Up to 300W)
10m, 15m, 20m, 40m, 80m & 160m

For detailed information and prices, call or write for our free catalog.

**CCI Communication
Concepts Inc.**

Add \$4.00 for
shipping & handling

508 Millstone Drive • Beavercreek, Ohio 45434-5840
(513) 426-8600 • FAX (513) 429-2811




ELENCO • HITACHI • B&K PRODUCTS GUARANTEED LOWEST PRICES

TO ORDER
CALL TOLL FREE
1-800-292-7711
1-800-445-3201 (Can.)

AFFORDABLE - HIGH QUALITY
2 YEAR WARRANTY

ELENCO OSCILLOSCOPES

 

STANDARD SERIES
S-1325 25MHz \$349
S-1340 40MHz \$495
S-1365 60MHz \$849



DELUXE SERIES
S-1330 25MHz \$449
S-1345 40MHz \$575
S-1360 60MHz \$775

- Features:
- High Luminance 6" CRT
 - 1mV Sensitivity
 - X-Y Operation
 - Voltage, Time, + Frequency differences displayed on CRT thru the use of cursors (S-1365 only)
 - Plus much, much more
 - TV Sync
 - 2 - x1, x10 Probes
 - Complete Schematic

- Features:
- Delayed Sweep
 - Automatic Beam Finder
 - 2 Axis Modulation
 - Built-in Component Test
 - Plus all the features of the "affordable" series
 - Dual time base
 - Illuminated internal gradicule

Hitachi Compact Series Scopes

- V-212 - 20MHz Dual Trace \$425
- V-525 - 50MHz, Cursors \$1,069
- V-523 - 50MHz, Delayed Sweep \$995
- V-522 - 50MHz, DC Offset \$975
- V-422 - 40MHz, DC Offset \$849
- V-222 - 20MHz, DC Offset \$695
- V-660 - 60MHz, Dual Trace \$1,375
- V-665A - 60MHz, DT, w/cursor \$1,449
- V-1060 - 100MHz, Dual Trace \$1,549
- V-1065A - 100MHz, DT, w/cursor \$1,695
- V-1085 - 100MHz, QT, w/cursor \$2,125

B&K OSCILLOSCOPES

- 2120 - 20MHz Dual Trace \$389
- 2125 - 20MHz Delayed Sweep \$539
- 1541B - 40MHz Dual Trace \$749
- 2160 - 60MHz Dual Trace, Delayed Sweep, Dual Time Base \$949
- 2190 - 100MHz Three Trace Dual Time Base, Delayed Sweep \$1,379
- 2522A - 20MHz / 20MS/s Storage \$869

Digital Multimeter
EDM-828B
\$175.00
Almost every feature available
Bargain of the decade

Digital Multimeter
CM-1500B
\$59.95
DC, AC volts
DC, AC amps
Large 1" LCD display

Digital Capacitance Meter
CM-1555
\$49.95
• Measures capacitors from 1pf to 20,000µf
• 3 1/2 Digit LCD readout with unit indicator

Digital LCR Meter
LCR-680
\$79.95
• 3 1/2 Digit LCD Display
• Inductance 1µH to 200H
• Resistance 1Ω to 20MΩ
• Capacitance 1pf to 200µF

Function Generator
FG-801
\$149.95
Square, triangle sine wave
Freq range 0.2Hz to 2MHz

3-3/4 Digit Multimeter
BK-390
\$139.00
• 0.1% DCV acry
• Analog bar graph
• Auto/manual ranging
• 4,000 count LCD display
• Capacitance meas.
• Temperature probe

Digital Multimeter Kit
with Training Course
By Elenco
M-2655K
\$49.95
• Full function 34 Ranges
• Extra large display • Ideal school project
M-2661 (Assembled) \$55.00

Frequency Counter
F-1225
\$225.00
• 8 Digit LED display
• Wide measuring range
• High sensitivity
• Data hold function
• Input impedance 1MΩ or 50Ω
• 10:1 Input attenuation function

FLUKE MULTIMETERS
(All Models Available Call)
Scopemeters
Model 93 \$1,225.00
Model 95 \$1,549.00
Model 97 \$1,795.00
10 Series
Model 10 \$62.95
Model 12 \$84.95
70 Series
Model 70H \$69.95
Model 77H \$149.00
Model 79H \$175.00
80 Series
Model 87 \$289.00

Triple Power Supply
XP-620
By Elenco
\$75.00
3 fully regulated supplies: 1.5-15V @ 1A, 1.5 to 15V @ 1A or (3-30V @ 1A) and 5V @ 3A Kit XP-620K \$49.95

Quad Power Supply
XP-581
By Elenco
\$79.95
Four supplies in one unit: 2-20V @ 2.5A, 5V @ 3A, 5V @ 5A and 12V @ 1A. All regulated and short protected

High Current DC Power Supply
BK-1686
\$169.95
• 3 to 14 VDC Output
• 12A @ 13.6V
(less current at lower voltages)
• For servicing high power car stereos, camcorders, ham radios, etc.
• Connect 2 or more in parallel or series

Wide Band Signal Generators
SG-9000
\$124.95
RF Frequency 100K-450MHz AM modulation of 1KHz Variable
RF output
SG-9500 150MHz built-in counter \$239

FM Receiver Kit & Training Course
\$44.95 AR2N6 Built
Ideal training aid for beginners. Makes it fun and easy to learn about amateur radio.
• Covers both 2 meter (144-148MHz) and 6 meter (50-54MHz) FM.
• Dual conversion superheterodyne
\$34.95 AR2N6K KIT

ISOTIP #7880
\$24.95
Two tools in one! Perfect, portable tool for hobbyists and technicians

60 Hertz EMF Probe
MP-1
\$89.95
Works with any DMM

Telephone Kit
PT-223K
\$14.95
Available Assembled PT-223 \$15.95

Function Generator
Blox #9600
By Elenco
\$29.95
Kit \$26.95
Sine, Triangle, Square wave

Learn to Build and Program Computers with this Kit
MM-8000
By Elenco
\$129.00
From scratch you build a complete system. Our Micro-Master trainer teaches you to write into RAMs, ROMs and run a 8085 microprocessor, which uses similar machine language as IBM PC.

Electronic Tool Kit
TK-1000
\$39.95
A professional organizer tool kit at affordable prices. Includes 25 high quality tools in a high impact carrying case which includes a pocket for meter.

Digital/Analog Trainer
Complete Mini-Lab For Building, Testing, Prototyping Analog and Digital Circuits
XX-525
\$159.95
Kit XX-525K
\$129.95
Elenco's trainer is designed for school projects, with 5 built-in power supplies. Includes a function generator with continuously variable, sine, triangular square wave forms. All power supplies are regulated and protected against shorts. The case can include a full line of tools and meter of your choice.

WE WILL NOT BE UNDERSOLD
UPS SHIPPING, 48 STATES 5% OTHERS CALL
IL RES add 7.75% TAX
PROBES INCL ALL SCOPES & METERS

C&S SALES INC.
1245 ROSEWOOD, DEERFIELD, IL 60015
FAX: 708-520-0985 • (708) 541-0710



15 DAY MONEY BACK GUARANTEE
FULL FACTORY WARRANTY
WRITE FOR FREE CATALOG

AMATEUR TELEVISION

GET THE ATV BUG



**New 10 Watt
Transceiver
Only \$499**

Made in USA
Value + Quality
from over 25 years
in ATV...W6ORG

Snow free line of sight DX is 90 miles - assuming 14 dBd antennas at both ends. 10 Watts in this one box may be all you need for local simplex or repeater ATV. Use any home TV camera or camcorder by plugging the composite video and audio into the front phono jacks. Add 70cm antenna, coax, 13.8 Vdc @ 3 Amps, TV set and you're on the air - it's that easy!

TC70-10 has adjustable >10 Watt p.e.p. with one xtal on 439.25, 434.0 or 426.25 MHz & properly matches RF Concepts 4-110 or Mirage D1010N-ATV for 100 Watts. Hot GaAsfet downconverter varicap tunes whole 420-450 MHz band to your TV ch3. 7.5x7.5x2.7" aluminum box.

Transmitters sold only to licensed amateurs, for legal purposes, verified in the latest Callbook or send copy of new license. Call or write now for our complete ATV catalog including downconverters, transmitters, linear amps, and antennas for the 400, 900 & 1200 MHz bands.

(818) 447-4565 m-f 8am-5:30pm pst.

Visa, MC, COD

P.C. ELECTRONICS

Tom (W6ORG)
Maryann (WB6YSS)

2522 Paxson Lane Arcadia CA 91007

Looking to challenge your
building skills?

Want to explore beyond
Amateur communications?

Well here's the publication for YOU!

COMMUNICATIONS QUARTERLY, the journal of communications technology. You are invited to become part of an elite group of Radio Amateurs and technical professionals as a subscriber. Circulation will be strictly limited.

Each quarterly has approximately 100 pages of technical material; advertising is limited. Articles flow from page to page, without the interruption of ads placed in the middle. The open layout accentuates each author's work and lets you make notes, calculations, or comments for later reference. Graphs, photos, computer program listings, and charts are presented in an easy-to-use format.

COMMUNICATIONS QUARTERLY is printed on a high-quality stock and "perfect bound" (square backed). It is such a valuable resource, you'll want to file each copy away in your technical archives for future reference. In fact, over time you'll find much of what is presented in COMMUNICATIONS QUARTERLY will become the standard in the Amateur and professional communications field.

Act now. Subscribe today!

1 year - \$29.95

Foreign 1 year - \$39.95

2 years - 56.95

Foreign 2 years - 76.95

Foreign Air Mail 1 year - \$ 60.00

Foreign Air Mail 2 years - 118.95


MasterCard/VISA/American Express accepted

**CQ Communications, Inc., 76 North Broadway,
Hicksville, NY 11801**

Phone: 516-681-2922/FAX: 516-681-2926

Motron
ELECTRONICS

 310 Garfield St Suite 4
PO Box 2748
Eugene, Oregon 97402



This is an actual FingerPrint captured by the TxID-1

TxD-1

Transmitter
FingerPrinting
System

Now Shipping!

FM/AM radio transmitters have a unique frequency versus time start-up characteristic—even radios of the same make and model. This "FingerPrint" can be captured, stored and analyzed. Our exclusive TxID Software and the patented technology of the TxID-1 IBM/Compatible circuit board can help you identify the abusers on your repeater! Or help you keep track of the number of radios per account on commercial repeaters. CTCSS, DCS and DTMF decoding, as well as Deviation measurements and Spectrum Occupancy features further enhance the system.

Call or write for a full brochure with full details, additional examples, and technical specifications

TxD-1 with Software \$699.00

Shipping/Handling LPS Ground USA: \$8.00
Visa/MC and PINXEL and Government Purchase Orders accepted.
COD on Cash or Money Order basis only.

Orders: (800) 338-9058

Info: (503) 687-2118 Fax: (503) 687-2492

DUPLEXERS

★ QUALITY ★ SERVICE

★ PRICE

WE'VE GOT IT ALL!

Our Bandpass-Reject Duplexers with our patented B_pB_r Circuit® Filters provide superior performance... especially at close frequency separation.



PHONE 817-848-4435

FAX 817-848-4209

WACOM

PRODUCTS, INC.

P.O. BOX 21145 • WACO, TX 76702

ANTENNA OPTIMIZERS

AO 6.0 automatically optimizes antenna designs for best gain, pattern, impedance, SWR, and resonance. AO optimizes cubical quads, phased arrays, interlaced Yagis, or any other arrangement of wire or tubing. AO uses an enhanced, corrected MININEC algorithm for improved accuracy and assembly language for high speed. AO features 3-D radiation patterns, 3-D geometry and wire-current displays, 2-D polar and rectangular plots with overlays, automatic wire segmentation, automatic frequency sweep, symbolic dimensions, symbolic expressions, skin-effect modeling, current sources, polarization analysis, near-field analysis, and pop-up menus. NEC/Wires 1.5 accurately models true earth losses and complex arrays with the sophisticated Numerical Electromagnetics Code. Analyze elevated radials, Beverages, delta loops, wire beams, giant quads, LPDAs, or entire antenna farms. 3-D geometry display, 2-D polar and rectangular plots with overlays. Modeling capacity: AO, 225 pulses; NEC/Wires, 1000 segments (450/2000 for symmetrical, free-space designs). AO or NEC/Wires, \$100; both, \$130.

YO 5.0 automatically optimizes monoband Yagi designs for maximum forward gain, best pattern, and minimum SWR. YO models stacked Yagis, dual driven elements, tapered elements, mounting brackets, matching networks, skin effect, ground reflection, and construction tolerances. YO optimizes Yagis with up to 50 elements from HF to microwave. YO uses assembly language and runs hundreds of times faster than NEC or MININEC. YO is calibrated to NEC for high accuracy and has been extensively validated against real antennas. YO is highly graphical and easy to use. NEC/Yagi 2.0 provides reference-accuracy Yagi analysis and easy modeling of large arrays of Yagis. A special feature instantly changes array patterns and gain as you adjust array spacing. 1000 segments (2000 in free space). YO with NEC/Yagi, \$100.

AO and NEC require a 386+387 or better and VGA; YO runs on any PC. Visa, MasterCard, U.S. check, cash, or money order. Add \$5 overseas.

Brian Beezley, K6STI

507 1/2 Taylor, Vista, CA 92084 • (619) 945-9824


ANNOUNCING THE LATEST OFFERINGS FROM . . .



Getting Started in VHF

AND

 The VHF "How To" Book A Guide for All Amateurs



CQ's newest additions to our Video and Book Library bring the world of VHF to you . . .

Get in on the excitement that awaits you in the world of VHF — all with the practical "how-to" format that you've come to expect from CQ.

Send for your video and book today —there's a whole new world of amateur radio awaiting you!

CQ's **Getting Started in VHF** tape offers the visual immediacy that you can only get from video. And, with **The VHF "How To" Book**, you'll have an expanded reference filled with practical advice, tables, pictures, and sources of additional information that you can't be without. Together, there's simply no better resource on VHF!

Whether you're a new Technician or have been an Extra for years, there's plenty of excitement in VHF operating. Our new VHF series can introduce you to a part of our hobby you've never experienced or show you how to have even more fun!

**FOR FASTEST SERVICE CALL OUR ORDER DEPARTMENT AT
(800) 853-9797.**

CQ's VHF series is a fantastic addition to your club's library too!

HERE'S WHAT YOU'LL DISCOVER:

- Descriptions of VHF/UHF bands and operating activities
- How to find and use FM repeaters
- Exotic operating modes like ATV, Meteor Scatter, Aurora, Moonbounce, Satellites and more.
- Helpful operating hints
- Packet Radio basics
- Nets and emergency communications
- Propagation made easy
- VHF Contesting

YES! I want to receive **Getting Started in VHF** and/or **The VHF "How To" Book**. I've filled in the information below.

- copies of **GETTING STARTED IN VHF** video at \$19.95, plus \$3.50 shipping and handling.
 copies of **THE VHF "HOW TO" BOOK** at \$15.95, plus \$4.00 shipping and handling.
 complete video and book set **ONLY \$33.95**, plus \$4.00 shipping and handling.

Name _____

Address _____

City _____

State _____

ZIP _____

Include \$7.00 for overseas shipments. Tapes also available in PAL format.

Payment: Mastercard Visa American Express

Discover Money Order/Check

Card # _____

Exp. Date _____

Mail orders to: CQ Communications, Inc., 76 North Broadway, Hicksville, NY 11801

Fax (516) 681-2926. Club quantity discounts available.

ALSO AVAILABLE AT YOUR LOCAL DEALER.

ORGANIZE AND PROTECT YOUR COPIES OF **Communications Quarterly**

Now there's an easy way to organize and keep copies of your favorite magazine readily available for future reference.

Designed exclusively for **Communication Quarterly** by Jesse Jones Industries, these custom-made titled cases and binders provide the luxury look that makes them attractive additions to your bookshelf, desk or any location in your home or office.

Whether you choose cases or binders, you'll have a storage system that's durable and well organized to help protect your valuable copies from damage.

- Cases and binders designed to hold a year's issues (may vary with issue sizes).
- Constructed of reinforced board, covered with durable green leather-like material.
- Free personalization foil for indexing year.
- Cases V-notched for easy access.
- Binders have special spring mechanism to hold individual rods which easily snap in. This allows magazines to be fully opened for easy readability.
- Title hot - stamped in gold.

Communications Quarterly
Jesse Jones Industries, Dept. Comm--Q
499 East Erie Avenue,
Philadelphia, PA 19134

Quantity	Cases	Binders
One	\$ 7.95	\$ 9.95
Three	\$21.95	\$27.95
Six	\$39.95	\$52.95

Add \$1 per case/binder postage and handling. Outside USA \$2.50 per case/binder. (U.S. funds only)

Please send _____ cases; _____ binders

Enclosed is \$ _____

- Charge my: (Minimum \$15)
- American Express Visa
- Mastercard Diners Club

Card # _____ Exp. Date _____

Signature _____

Print Name _____

Address _____

No P.O. Box Numbers Please

City/State/Zip _____

Zip _____

**PA Residents add 7% sales tax
Call TOLL FREE 7 days,
24 hours 1-800-825-6690**

DOWN EAST MICROWAVE



MICROWAVE ANTENNAS AND EQUIPMENT

- Loop Yagis • Power Dividers • Dish Feeds
- Complete Antenna Arrays • Linear Amps
- Microwave Transverters & Kits • GaAs FET Preamps and Kits • Microwave Components
- Tropo • EME • Weak Signal • OSCAR • FM
- Packet • ATV
- 902 • 1269 • 1296 • 1691 • 2304 • 2400 • 3456 • 5760
- 10,386 MHz

ANTENNAS

2345 LYK	45 el	Loop Yagi Kit	1296 MHz	\$95
1345 LYK	45 el	Loop Yagi Kit	2304 MHz	\$79
3333 LYK	33 el	Loop Yagi Kit	902 MHz	\$95
1844 LY	44 el	Loop Yagi Assembled	1691 MHz	\$105
3B Feed	Tri Band Dish Feed 2.3, 3.4, 5.7 GHz			\$15

Many others and assembled versions available. Shipping extra.

LINEAR AMPS AND PREAMPS

2303 PA	1.2 to 1.3 GHz	3w out	13.8 VDC	\$130
2318 PAM	1.24 to 1.3 GHz	20w out	13.8 VDC	\$205
2335 PA	1.24 to 1.3 GHz	35w out	13.8 VDC	\$325
2340 PA	1.24 to 1.3 GHz	high gain 35w out	13.8 VDC	\$355
2370 PA	1.24 to 1.3 GHz	70w out	13.8 VDC	\$695
1302 PA	2.2 to 2.5 GHz	3w out	13.8 VDC	\$430
13 LNA	2.3 to 2.4 GHz	preamp	6 dB NF	\$140
23 LNA	1.2 to 1.3 GHz	preamp	6 dB NF	\$95
33 LNA	900 to 930 MHz	preamp	6 dB NF	\$95
1691 LNA WP	1691 MHz	mast mounted preamp	8 dB NF	\$140

Kits, Weatherproof Versions and other Frequencies Available

NO-TUNE TRANSVERTERS AND TRANSVERTER KITS

SHF 902K	902 MHz Transverter	40mW, 2m IF	Kit \$139
SHF 1296K	1296 MHz Transverter	10mW, 2m IF	Kit \$149
SHF 2304K	2304 MHz Transverter	10mW, 2m IF	Kit \$205
SHF 3456K	3456 MHz Transverter	10mW, 2m IF	Kit \$205

OSCAR and other frequencies available, also Amps and package versions wired and tested.
Write for more information. Free catalog available.



DOWN EAST MICROWAVE

Bill Olson, W3HQT
RR1 Box 2310, Troy, ME 04987
(207) 948-3741 Fax: 207-948-5157

CAPMANtm

Computer Assisted Prediction Manager

SKYWAVE ANALYSIS

"Use IONCAP⁺ like a pro!"

Package includes:

CAPMAN - Menu driven input & control with context-sensitive help!
Multicolor - Output Graphics display!
Extra or Novice, its EASY to use!

IONCAP⁺ - the same 32 bit tool the pros use to get S/N, MUF, FOT, LUF, Reliability and much More! Special Long-distance model for DXers!

MININEC & ELNEC interface for your custom antenna input!

- + Customize all input parameters for your station!
- + Your contacts and friends may be added to the library and run any time with a few keystrokes.
- + A full featured location database, indexed on country name and call prefix, provides access to over 490 prefixes for quick one-step predictions.
- + The package includes the newest "updated" full commercial version of IONCAP used by over 450 government agencies and commercial depts. in the USA and over 100 other countries.
- + Many more features in a powerful "HF Analysis" package at a fraction of the commercial price.

Entire CAPMAN package — \$89

USA postage paid. Overseas add \$3.50

Order today from:

LUCAS Radio/Kangaroo Tabor Software

2900 Valmont Rd, Suite H

Boulder, CO 80301

(303) 494-4647 (494-0937 fax)

VISA MC CHECK MONEY ORDER



VARI-NOTCH® DUPLEXERS FOR 2 METERS

The TX RX Systems Inc. patented Vari-Notch filter circuit, a pseudo-bandpass design, provides low loss, high TX to RX, and between-channel isolation, excellent for amateur band applications. TX RX Systems Inc. has been manufacturing multicoupling systems since 1976. Other models available for 220 and 440 MHz, UHF ATV and 1.2 GHz.

MODEL 28-37-02A
144-174 MHz
92 dB ISOLATION AT 0.6 MHz SEPARATION
400 WATT POWER RATING




19" RACK MOUNT

TX RX SYSTEMS INC.
8625 INDUSTRIAL PARKWAY, ANGOLA, NY 14006
TELEPHONE 716-549-4700 FAX 716-549-4772 (24 HRS.)



K.V.G. CRYSTAL PRODUCTS

 

9 MHz CRYSTAL FILTERS

MODEL	Appli- cation	Band- width	Poles	Price
XF-9A	SSB	2.4 kHz	5	\$ 75.00
XF-9B	SSB	2.4 kHz	8	105.00
XF-9B-01	LSB	2.4 kHz	8	145.00
XF-9B-02	USB	2.4 kHz	8	145.00
XF-9B-10	SSB	2.4 kHz	10	185.00
XF-9C	AM	3.75 kHz	8	110.00
XF-9D	AM	5.0 kHz	8	110.00
XF-9E	FM	12.0 kHz	8	120.00
XF-9M	CW	500 Hz	4	80.00
XF-9NB	CW	500 Hz	8	165.00
XF-9P	CW	250 Hz	8	199.00
XF-910	IF noise	15 kHz	2	20.00

10.7 MHz CRYSTAL FILTERS

XF-107A	12 kHz	\$105.00
XF-107B	15 kHz	105.00
XF-107C	30 kHz	105.00
XF-107D	36 kHz	120.00
XF-107E	40 kHz	125.00
XF-107S139	100 kHz	175.00

41 MHz CRYSTAL FILTER

XF-410S02 \$199.00

Write for full details of crystals and filters
Shipping \$8.00
Prices subject to change without notice.



si

Spectrum International, Inc.
P.O. Box 1084 Dept. Q
Concord, MA 01742 U.S.A.
Phone: 508-263-2145
FAX: 508-263-7008

ADVERTISER'S INDEX

AEA/Adv. Elec. Applications.....	5
Alinco Electronics	Cov.II
Amidon Associates	105
AMSAT.....	105
Astron Corporation	112
Beezley, Brian, K6STI.....	108
C & S Sales	107
Communications Quarterly	108
Communications Concepts	107
CQ '94 Equipment Buyer's Guide.....	10
CQ Almanac.....	104
CQ Books & Videos	106
CQ VHF Video	109
Down East Microwave.....	110
Hewlett Packard	10
Kenwood	Cov.IV, 2
L.L. Grace Comm. Products	103
Lewallen, Roy, W7EL	107
Lucas Radio/Kangaroo Tabor Software..	110
Motorola.....	12
Motron Electronics.....	108
Nemal Electronics.....	107
OPTOelectronics.....	I, 11
PC Electronics.....	108
Palomar Engineers	111
Pioneer Hill Software.....	105
Solitron/Vector.....	7, 8, 9
Spectrum International, Inc.....	111
TX RX Systems Inc	111
Wacom	108
Yaesu.....	Cov.III

We'd like to see your company listed here too. Contact Arnie Sposato, N2IQO, at (516)681-2922 or FAX at (516)681-2926 to work out an advertising program to suit your needs.

DIGITAL FREQUENCY DISPLAY



- For Classic Transceivers
- ATLAS, KENWOOD, DRAKE, HEATH
- COLLINS, YAESU, SWAN, TEN-TEC

Now you can add digital readout to your older transceiver to get a frequency display more accurate than many of the newer rigs. The dual oscillator system gives 100 Hz accuracy. Six digit LED readout has big .4" digits. Covers complete range 1.5 to 40 MHz.

Model PD-700 \$199.95 + \$6 shipping/handling
U.S. & Canada. Specify transceiver model. For 12-v DC. Model PS-90 AC adapter \$10. California residents add sales tax.



Send for **FREE** catalog showing our complete line: Digital Readout, Noise Bridge, Baluns, SWR Meters and more.

PALOMAR ENGINEERS

BOX 462222, ESCONDIDO, CA 92046
Phone (619) 747-3343
FAX (619) 747-3346

ASTRON POWER SUPPLIES

• HEAVY DUTY • HIGH QUALITY • RUGGED • RELIABLE •

SPECIAL FEATURES

- SOLID STATE ELECTRONICALLY REGULATED
- FOLD-BACK CURRENT LIMITING Protects Power Supply from excessive current & continuous shorted output
- CROWBAR OVER VOLTAGE PROTECTION on all Models except RS-3A, RS-4A, RS-5A, RS-4L, RS-5L
- MAINTAIN REGULATION & LOW RIPPLE at low line input Voltage
- HEAVY DUTY HEAT SINK • CHASSIS MOUNT FUSE
- THREE CONDUCTOR POWER CORD except for RS-3A
- ONE YEAR WARRANTY • MADE IN U.S.A.

PERFORMANCE SPECIFICATIONS

- INPUT VOLTAGE: 105-125 VAC
- OUTPUT VOLTAGE: 13.8 VDC \pm 0.05 volts (Internally Adjustable: 11-15 VDC)
- RIPPLE Less than 5mv peak to peak (full load & low line)
- All units available in 220 VAC input voltage (except for SL-11A)



MODEL VS-50M

SL SERIES



• LOW PROFILE POWER SUPPLY

MODEL	Colors		Continuous Duty (Amps)	ICS* (Amps)	Size (IN) H x W x D	Shipping Wt. (lbs.)
	Gray	Black				
SL-11A	•	•	7	11	2 1/2 x 7 1/2 x 9 3/4	12
SL-11R	•	•	7	11	2 1/2 x 7 x 9 3/4	12
SL-11S	•	•	7	11	2 1/2 x 7 1/2 x 9 3/4	12
SL-11R-RA	•	•	7	11	4 1/4 x 7 x 9 3/4	13

RS-L SERIES



• POWER SUPPLIES WITH BUILT IN CIGARETTE LIGHTER RECEPTACLE

MODEL	Continuous Duty (Amps)	ICS* (Amps)	Size (IN) H x W x D	Shipping Wt. (lbs.)
RS-4L	3	4	3 1/2 x 6 1/2 x 7 1/4	6
RS-5L	4	5	3 1/2 x 6 1/2 x 7 1/4	7

RM SERIES



MODEL RM-35M

• 19" RACK MOUNT POWER SUPPLIES

MODEL	Continuous Duty (Amps)	ICS* (Amps)	Size (IN) H x W x D	Shipping Wt. (lbs.)
RM-12A	9	12	5 1/4 x 19 x 8 1/4	16
RM-35A	25	35	5 1/4 x 19 x 12 1/2	38
RM-50A	37	50	5 1/4 x 19 x 12 1/2	50
RM-60A	50	55	7 x 19 x 12 1/2	60

• Separate Volt and Amp Meters

RM-12M	9	12	5 1/4 x 19 x 8 1/4	16
RM-35M	25	35	5 1/4 x 19 x 12 1/2	38
RM-50M	37	50	5 1/4 x 19 x 12 1/2	50
RM-60M	50	55	7 x 19 x 12 1/2	60

RS-A SERIES



MODEL RS-7A

MODEL	Colors		Continuous Duty (Amps)	ICS* (Amps)	Size (IN) H x W x D	Shipping Wt. (lbs.)
	Gray	Black				
RS-3A	•	•	2.5	3	3 x 4 1/2 x 5 3/4	4
RS-4A	•	•	3	4	3 1/2 x 6 1/2 x 9	5
RS-5A	•	•	4	5	3 1/2 x 6 1/2 x 7 1/4	7
RS-7A	•	•	5	7	3 1/2 x 6 1/2 x 9	9
RS-7B	•	•	5	7	4 x 7 1/2 x 10 3/4	10
RS-10A	•	•	7.5	10	4 x 7 1/2 x 10 3/4	11
RS-12A	•	•	9	12	4 1/2 x 8 x 9	13
RS-12B	•	•	9	12	4 x 7 1/2 x 10 3/4	13
RS-20A	•	•	16	20	5 x 9 x 10 1/2	18
RS-35A	•	•	25	35	5 x 11 x 11	27
RS-50A	•	•	37	50	6 x 13 3/4 x 11	46
RS-70A	•	•	57	70	6 x 13 3/4 x 12 1/2	48

RS-M SERIES



MODEL RS-35M

MODEL	Continuous Duty (Amps)	ICS* (Amps)	Size (IN) H x W x D	Shipping Wt. (lbs.)
RS-12M	9	12	4 1/2 x 8 x 9	13
RS-20M	16	20	5 x 9 x 10 1/2	18
RS-35M	25	35	5 x 11 x 11	27
RS-50M	37	50	6 x 13 3/4 x 11	46
RS-70M	57	70	6 x 13 3/4 x 12 1/2	48

• Switchable volt and Amp meter

• Separate volt and Amp meters

VS-M AND VRM-M SERIES



MODEL VS-35M

• Separate Volt and Amp Meters • Output Voltage adjustable from 2-15 volts • Current limit adjustable from 1.5 amps to Full Load

MODEL	Continuous Duty (Amps)			ICS* (Amps)	Size (IN) H x W x D	Shipping Wt. (lbs.)
	@13.8VDC	@10VDC	@5VDC			
VS-12M	9	5	2	12	4 1/2 x 8 x 9	13
VS-20M	16	9	4	20	5 x 9 x 10 1/2	20
VS-35M	25	15	7	35	5 x 11 x 11	29
VS-50M	37	22	10	50	6 x 13 3/4 x 11	46

• Variable rack mount power supplies

VRM-35M	25	15	7	35	5 1/4 x 19 x 12 1/2	38
VRM-50M	37	22	10	50	5 1/4 x 19 x 12 1/2	50

RS-S SERIES



MODEL RS-12S

• Built in speaker

MODEL	Colors		Continuous Duty (Amps)	ICS* Amps	Size (IN) H x W x D	Shipping Wt. (lbs.)
	Gray	Black				
RS-7S	•	•	5	7	4 x 7 1/2 x 10 3/4	10
RS-10S	•	•	7.5	10	4 x 7 1/2 x 10 3/4	12
RS-12S	•	•	9	12	4 1/2 x 8 x 9	13
RS-20S	•	•	16	20	5 x 9 x 10 1/2	18
SL-11S	•	•	7	11	2 1/2 x 7 1/2 x 9 3/4	12

"200 watts, real cross band receive, even two flywheel-weighted main knobs!"

"Yaesu did it again!"

"Right, there's only one real performer – the FT-1000."

FT-1000 All Mode HF Transceiver

- RF Power Output: Up to 200 Watts
- True Cross-band Dual Receive: Two Large Tuning Knobs
- Front Panel RX Antenna Switch: For Beverage or Loop
- Direct Digital Synthesis (DDS)
- Automatic Antenna Tuner: Built-in, 30 Memories
- Frequency Range: 100kHz-30MHz (RX), 160-10 meters (TX)
- 100 Memories: Independent ATU and Mode/IF Filter Memory
- CW Spot and Two CW Key Jacks for Maximum Convenience
- Dynamic Range: 108 dB
- Optional Digital Voice Recorder (DVS-2): 16 Seconds Each RX/TX
- **Accessories:**
 - SP-5 External Desk-top Speaker
 - LL-5 Phone Patch Unit
 - MD-1C8 Desktop Microphone
 - YH-77ST Stereo Headphones
 - FL-7000 500W Linear Amplifier
 - DVS-2 Digital Voice Recorder

Hear signals you've never heard before.



You're a competitor. You want optimum receiver performance and you want "muscle" on transmit. First with 200 watts – more power than any competing transceiver – and "hand warm" at maximum RF. It's easy to see why the FT-1000 has been judged "best overall" by top DX'ers worldwide.

For elite-class contesting and DX operation, exclusive features maximize your score. Dual Receive – Watch a multiplier or new country on one frequency, run QSOs on another. Diversity Reception – Use two antennas at different heights or opposite polarization. Extensive Cascaded IF Filtering – For "low end" battles.

Dramatic front panel design features two flywheel-weighted tuning knobs, RX antenna selector and two large displays.

A perfect blend of electronics and human engineering, the FT-1000 is the Best of our Best!

To hear signals you've never heard before and get the competitive edge, see your Yaesu dealer today.

YAESU

Performance without compromise.SM

© 1993 Yaesu USA, 17210 Edwards Road, Cerritos, CA 90701 (310) 404-2700

Specifications subject to change without notice. Specifications guaranteed only within amateur bands. Some accessories and/or options are standard in certain areas. Check with your local Yaesu dealer for specific details.

Kenwood's TM-251A/451A/551A Shift into Overdrive!



TM-251A

TM-251A/451A/551A FM MOBILE TRANSCEIVERS

1200
9600
packet compatible

When the going gets rough, Kenwood's mobile FM transceivers show their stuff. For a winning combination of performance and operating ease, nothing beats the TM-251A (144MHz), TM-451A (440MHz), and TM-551A (1200MHz). Despite being single-banders, they have a dual-band receive capability, allowing full-duplex cross-band communications using split-memory channels (TM-251A ↔ TM-451A). Each transceiver is equipped with 41 memory channels (expandable to 200 with the ME-1 option), a digital recording system for messages (max. 16 secs), a dual-menu system, and a 6-pin mini DIN connector for 1200/9600bps packet communications. Built-in DTSS allows 3-digit DTMF selective calling access, and the page function alerts you to incoming calls. There's also a large multi-function LCD with 3 different display modes, as well as a multi-function microphone with 4 programmable keys and 16 DTMF keys. So if you want pole position, choose Kenwood.



TM-451A

Available soon!

TM-551A*

*This device has not been approved by the Federal Communications Commission. This device is not, and may not be, offered for sale or lease, or sold or leased until the approval of the FCC has been obtained.

Features

- Max. 50W output (TM-251A), 35W (TM-451A), 10W (TM-551A)
- 41 memory channels (up to 200 with ME-1 option)
- Dual-menu system ■ DTSS with page ■ S-meter squelch
- Built-in digital recording system
- 6-pin mini DIN connector (1200/9600bps packet)
- Multi-function microphone with DTMF (supplied)
- Fuzzy logic control for tuning
- Selectable frequency step (5, 10, 12.5, 15, 20 or 25kHz)
- Channel number display ■ Auto-lock tuning (TM-551A)
- Band scan, program scan, memory scan, call scan
- Time Operated and Carrier Operated scan stop modes
- Cross-band repeater functions
 - TM-251A — TX: 144MHz band, RX: 440MHz band
 - TM-451A — TX: 440MHz band, RX: 144MHz band
- Auto repeater offset (TM-251A)
- 10 DTMF memory (15 digits)
- Built-in CTCSS encoder and optional TSU-8 decoder
- 5-step dimmer control
- 3-position RF output power control (TM-251A: 50W, 10W, 5W; TM-451A: 35W, 10W, 5W)
- Auto power-off (OFF, 60, 120, 180 min.) ■ Time-out timer (OFF, 3, 5, 10, 20, 30 min.) ■ Wireless clone function

KENWOOD COMMUNICATIONS CORPORATION
AMATEUR RADIO PRODUCTS GROUP
P.O. BOX 22745, 2201 East Dominguez St., Long Beach, CA 90801-5745
KENWOOD ELECTRONICS CANADA INC.
6070 Kestrel Road, Mississauga, Ontario L5T 1S8

KENWOOD