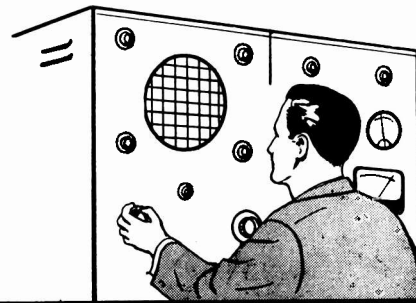


AEROVOX RESEARCH WORKER



Radio Editors of magazines and newspapers will be given permission to reprint in whole or in part, with proper credit to the Aerovox Corporation, the contents of this issue of the Aerovox Research Worker, upon written request.

The Aerovox Research Worker is edited and published by the Aerovox Corporation to bring to the Radio Experimenter and Engineer, authoritative, first hand information on capacitors and resistors for electrical and electronic application.

VOL. 33 NOS. 7-8-9

JULY-AUG.-SEPT., 1963

Subscription By
Application Only

Aids To Timing - Circuit Design

Part 2 RL Circuits

In the resistance-inductance (RL) timing circuit, current increases (on make) or decreases (on break) through R and L in series. Sometimes the inductor is the coil of a relay timed by the process. The current is $I = (E/R)e^{-t/L}$ (where I is the instantaneous current in amperes, E the steady-state d-c supply voltage, t the time interval in seconds from the instant of closing or opening the circuit, R the resistance in ohms, L the inductance in henrys, and e the base of natural logarithms = 2.71828). The time constant of the circuit is given as $t = L/R$ (where t is the time in seconds required for the current to build up (after make) to 0.6321 maximum or to decay (after break)

to 0.3679 maximum, R the resistance in ohms, and L the inductance in henrys).

As mentioned in Part 1 regarding the RC timing circuit, the calculations for determining required values for LR circuits are simple ($t = L/R$, $R = L/t$, $L = tR$), but they can become time-consuming when a number of them must be made. The charts presented in this article will lighten this task. Figure 1 is a graph for determining t or R when $L = 1$ henry. For other values of inductance when t is known, multiply the indicated resistance by L, where L is the desired inductance in henrys. For desired values of t and/or R other than those

shown on the graph, shift the decimal point, as required, by the same amount and in the same direction on resistance and time scales.

For more accurate results, use Tables 1 and 2, which give resistance values required with thirteen common inductances (10 millihenrys to 100 henrys) and for thirty-eight time rates (1 millisecond to 10 seconds for both charts). Resistance values are not carried lower than 5 ohms, since below that figure stray circuit resistance might possibly compete with the timing resistance. Timing rates are not carried lower than 1 msec nor higher than 10 sec, since this range seems most called

AEROVOX - - *The Finest In Electronic Components*



for in I.R. timing practice. However, R, L, and t values other than those given in the tables may be determined by means of interpolation.

The circuit designer must remember that inductors of all kinds have a cer-

tain amount of internal resistance unavoidably resulting from the resistance of the wire with which they are wound. This varies, of course, with type, manufacture, and inductance of the inductor, but usually is low only in those units

which are large in size for a given inductance rating.

This inherent resistance acts in series with the inductance and must be taken into account when determining required resistance for an RL timing circuit.

1 Henry Curve

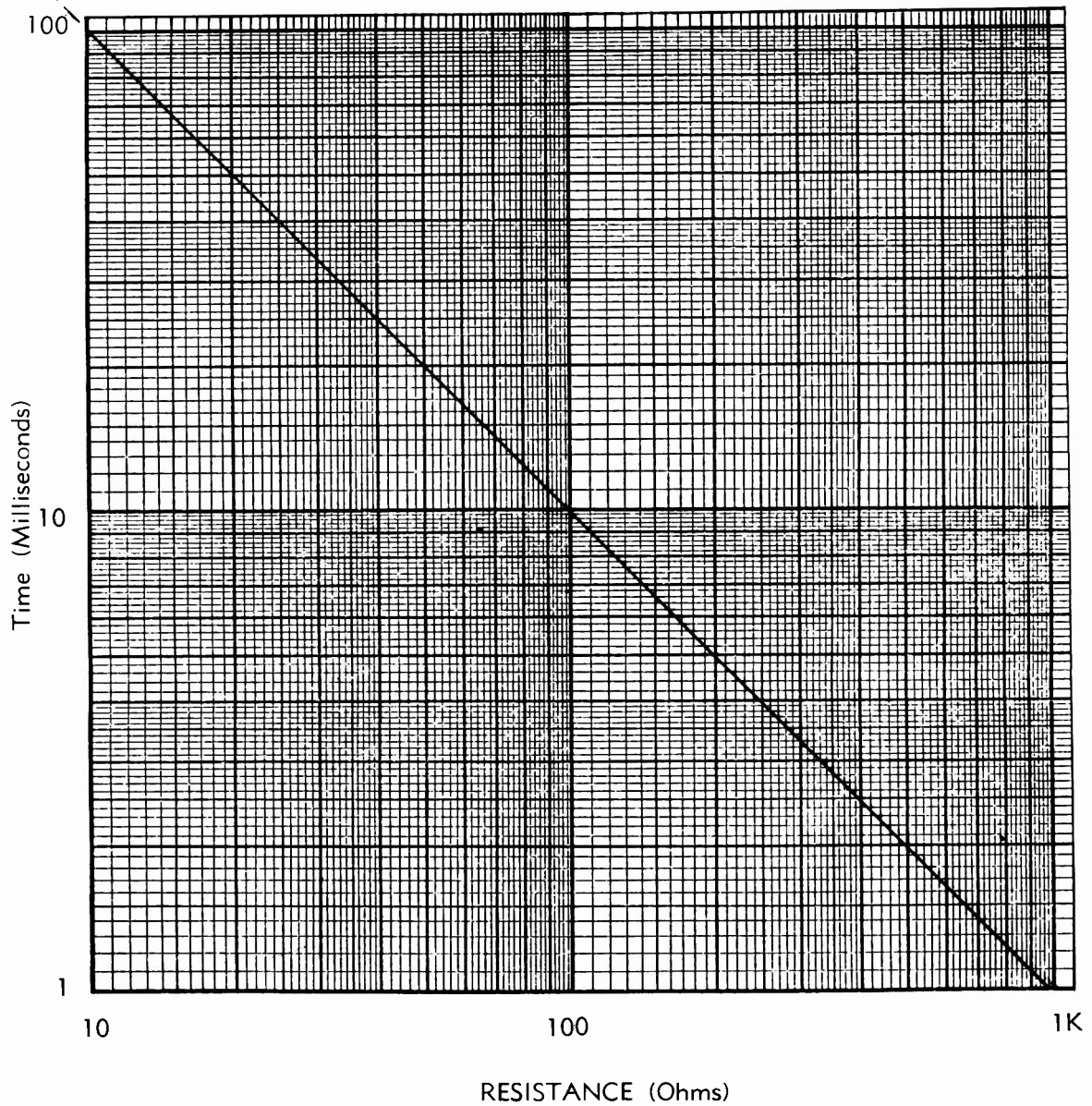


FIGURE 1. RL CIRCUIT CURVE



TIME (t in millisec- onds)	INDUCTANCE (L in henrys)												
	0.01	0.02	0.05	0.1	0.2	0.5	1	2	5	10	20	50	100
1	10	20	50	100	200	500	1K	2K	5K	10K	20K	50K	100K
2	5	10	25	50	100	250	500	1K	2.5K	5K	10K	25K	50K
3		6.7	16.7	33	67	167	330	670	1.67K	3.3K	6.7K	16.7K	33K
4		5	12.5	25	50	125	250	500	1.25K	2.5K	5K	12.5K	25K
5			10	20	40	100	200	400	1K	2K	4K	10K	20K
6			8.3	16.7	33.3	83	167	333	830	1.67K	3.33K	8.3K	16.7K
7			7.1	14.3	28.6	71	143	286	710	1.43K	2.86K	7.1K	14.3K
8			6.2	12.5	25	62	125	250	620	1.25K	2.5K	6.2K	12.5K
9			5.5	11.1	22.2	55	110	222	550	1.1K	2.22K	5.5K	11.1K
10				10	20	50	100	200	500	1K	2K	5K	10K
20				5	10	25	50	100	250	500	1K	2.5K	5K
30					6.7	16.7	33.3	67	167	330	670	1.67K	3.3K
40					5	12.5	25	50	125	250	500	1.25K	2.5K
50						10	20	40	100	200	400	1K	2K
60						8.3	16.7	33.3	83	167	330	830	1.67K
70						7.1	14.3	28.6	71	143	286	710	1.43K
80						6.2	12.5	25	62	125	250	620	1.25K
90						5.5	11	22.2	55	110	222	550	1.11K
100						5	10	20	50	100	200	500	1K

K=kilohms



TABLE 1. RESISTANCE VALUES

TIME (t in seconds)	INDUCTANCE (L in henrys)							
	0.5	1	2	5	10	20	50	100
0.1	5	10	20	50	100	200	500	1K
0.2		5	10	25	50	100	250	500
0.3			6.7	16.7	33	67	167	330
0.4			5	12.5	25	50	125	250
0.5				10	20	40	100	200
0.6				8.3	16.7	33	83	167
0.7				7.1	14.3	28.6	71	143
0.8				6.2	12.5	25	62	125
0.9				5.5	11	22.2	55	110
1				5	10	20	50	100
2					5	10	25	50
3						6.7	16.7	33
4						5	12.5	25
5							10	20
6							8.3	16.7
7							7.1	14.3
8							6.2	12.5
9							5.5	11
10							5	10

K=kilohms

TABLE 2. RESISTANCE VALUES

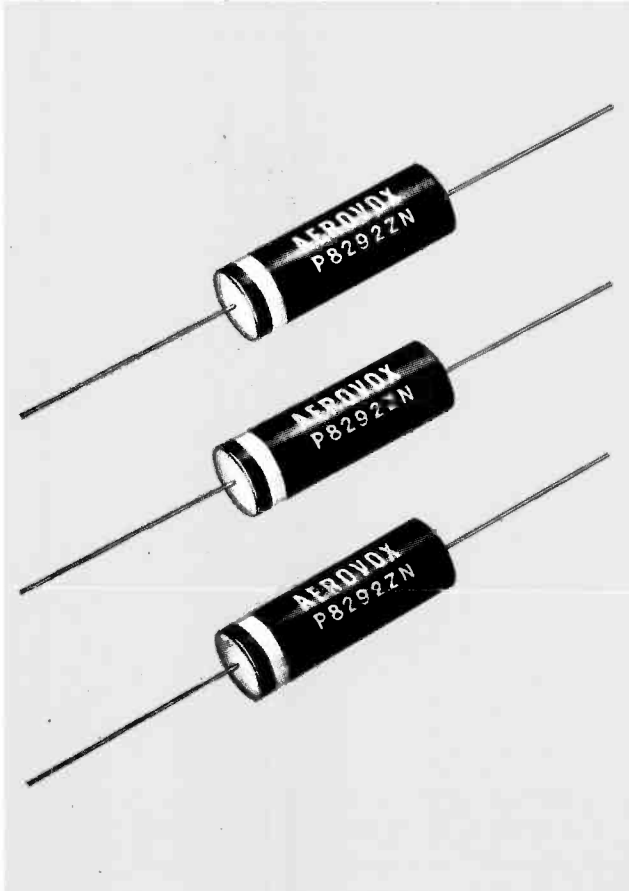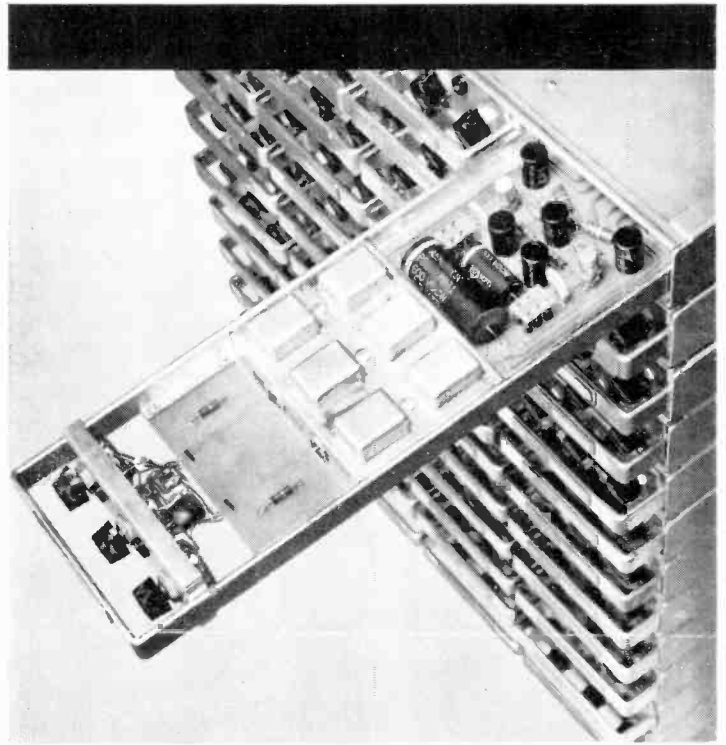Technical Leadership — Manufacturing Excellence



LOW-COST, HIGH-GAIN BUDELMAN VFR EMPLOYS AEROVOX TYPE P8292ZN METALLIZED PAPER CAPACITORS

The Budelman Type 251A VFR, offered as the lowest-cost, high-gain repeater available, incorporates a newly designed transistorized circuitry for uniform speech gain over any telephone line facility. In addition to design economy and compactness, the unit features low power drain and built-in signaling by-pass. ■ This development is another example of teamwork between the product design engineers and Aerovox application engineering... producing the right capacitor answer for a new design concept. Aerovox Type P8292ZN Metallized Paper Capacitors were selected because they satisfied the critical requirements for performance characteristics, reliability, and low cost production... and they could be delivered on time! ■ Aerovox offers a line of metallized paper capacitors in a wide variety of case styles and reduced sizes in types capable of operating to +125 C without voltage derating. All units are manufactured under the strictest quality controls to meet critical operating conditions and the need for high reliability... proven in such demanding applications as guided missiles, computers, airborne receivers, telephone and other equipments. ■ Complete specifications are yours for the asking. Simply contact your local Aerovox Sales Representative today... or write direct. And be sure to ask about the qualified Aerovox application engineering service available for the discussion and analysis of your specific capacitor requirements... absolutely no obligation.



AEROVOX CORPORATION
NEW BEDFORD DIVISION / NEW BEDFORD, MASS.

Other Divisions:
DISTRIBUTOR DIVISION / HI-Q DIVISION / AEROVOX CANADA, LTD.

Aerovox Metallized Paper Capacitors are also available from Aerovox Industrial Distributors in prototype and moderate production quantities.