


73

JUNE 1964

About 40c


Amateur Radio

SECOND ANNUAL

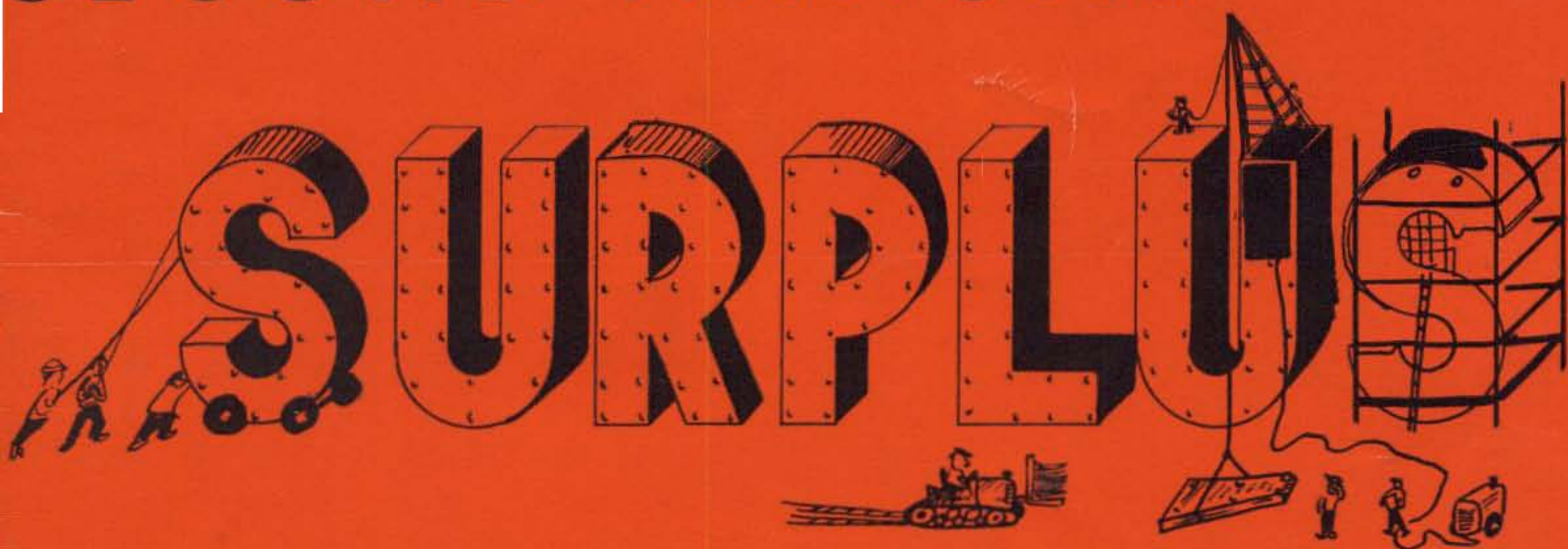

CATALOG ISSUE

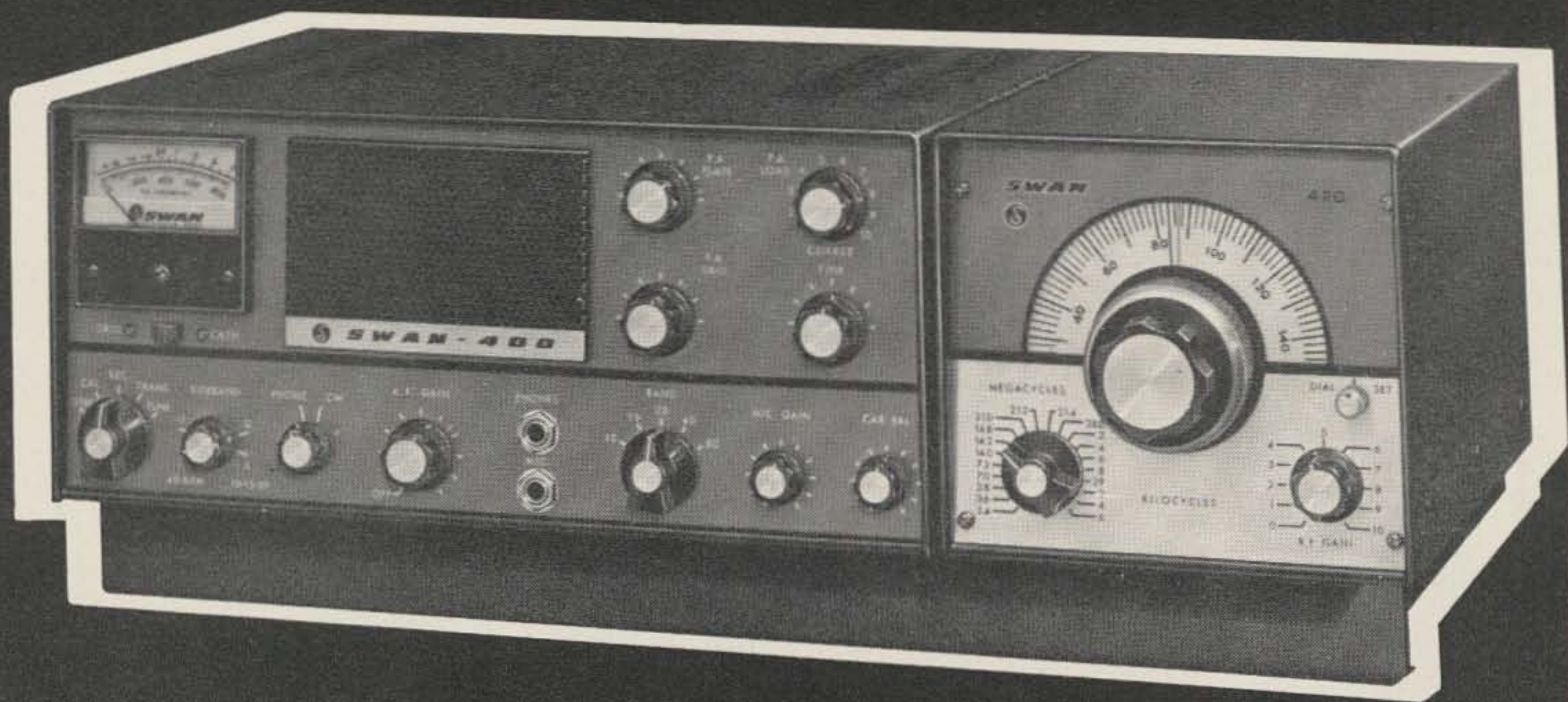HERE IT IS! THE SPECTACULAR NEW SWAN-400 SSB TRANSCEIVER 5 BANDS - 400 WATTS



SWAN-400 SINGLE SIDEBAND TRANSCEIVER 400 watts P.E.P. input, 10 through 80 meters. Fixed station, portable, or mobile. SSB, AM, and CW.

\$375

SWAN-420 FULL COVERAGE FREQUENCY CONTROL UNIT Highly stable transistorized VFO designed for fixed station operation. 20 ranges 200 kc each. Illustrated above as companion to SWAN-400.

\$120



SWAN-406 MINIATURIZED CONTROL UNIT Provides phone band coverage. Designed for mobile installation. May also be used for fixed station. Highly stable transistorized VFO in a compact package.

\$60

ACCESSORIES:

- AC POWER SUPPLY, MODEL 117B.....\$
- MOBILE POWER SUPPLY, MODEL 512.....\$1
- PLUG-IN VOX UNIT, MODEL VX-1.....\$

See your Swan Dealer for complete specifications.

 **SWAN**

ELECTRONICS CORP.
Oceanside, California

Wayne Green W2NSD/1
Editor, etcetera

June, 1964

Vol. XX, No. 1

T-51/ARQ-8: 6 Meter AM and SSB Transmitter	W5AJG	6
Nickel Cadmium Storage Batterys	W4VGS	14
ARB Aircraft Receiver	W1MEG	16
ARR-1: Adding SSB	W6BHR	18
TV-10/A: 220mc Transverter	W5AJG	20
ARR-15	W1MEG	24
R44/ARR-5 Receiver	Ives	26
Surplus Find	Gardiner	30
Propagation	Nelson	31
Really High Gain	K5JKX	33
Smaltz for Semiconductors	Kidder	34
Surplus Circuit Breakers	Pafenberg	39
IP-69/ALA-2 Panoramic Indicator	W8DMR	40
Telechrome 1462-A1 XMTR for 220mc	W5AJG	47
T-28/APT-1: 2 Meter AM and SSB XMTR	W5AJG	52
Correspondence from the Members		58
Using 416B and 8058 Tubes on 432mc	W5AJG	66
Regulated Power Supplies	K5JKX	76
The BC-348	K8ZHZ	88
TS-118A/AP Wattmeter	W1MEG	123
Radar Principles	Gardiner	125

73's Advertising Rates

	1-5 times	6-11 times*	12 times*
2 pages	\$420	\$388**	\$356**
1 page	220	204**	188**
1/2 page	114	106	98
1/4 page	60	56	52
1/8 page	32	30	28
1/16 page	17	16	15

Add fractional page prices for sizes not listed.
 $\frac{3}{8}$ p = $\frac{1}{4}$ p + $\frac{1}{8}$ p.
 *We must have a written contract for frequency discount.
 **No extra charge for second color for full page ads on contract.
 Second color (usually red, but our choice) . . . \$25 per page or fraction.
 Half or full page bleeds are 10% extra.
 No special positions can be promised for color pages.

73 Magazine is published monthly by 73, Inc., Peterborough, N. H. The phone number is 603-924-3873. Subscription rates \$4.00 per year, \$7.00 for two years, \$10 for three years world wide. Second class postage is paid at Peterborough, New Hampshire and at additional mailing offices. Printed in the U.S.A. Entire contents copyright 1964 by 73, Inc. Postmaster: please send form 3579 to 73 Magazine, Peterborough New Hampshire.

Hams in the News	46, 85	Letters	60, 62
Poem	56	Corrections	84
FCC Rule Change	59	New Products	86
Surplus Catalog	98		



de W2NSD/1

never say die

The past few weeks have been eventful for amateur radio. The Institute started mailing its weekly newsletters to every U. S. Senator, U. S. Representative, Governor and government official involved with radio. This has met with an enthusiastic response.

First reports of the ARRL board of directors meeting indicate that it went off remarkably smoothly, considering the serious problems facing them from RM-499, dropping membership, the Coca-Cola scandal, and the disintegration of IARU Region 2. We'll all be watching for the minutes of the meeting in the July QST.

CQ devoted an editorial to me, for which I thank them. A couple letters from IoAR members cover this pretty well . . . see page 62.

The Dayton Hamvention went off smoothly in its new quarters. For the first time since I can remember people weren't jammed like the New York subways trying to get from one exhibitor to another. I've been pretty hard on the ARRL HQ for RM-499 and other things of late and I sort of expected to be taken to task by fellows that hadn't bothered to find out what was really happening. All I got was hundreds and hundreds of compliments for having the courage to bring points of dispute out in the open.

W3NL published a letter that I had sent to all ARRL directors well before the board meeting. I hadn't published this myself for I didn't want to have them think that I was making a grandstand play. The gist of the letter was that all of us will be watching the minutes of this years meeting to see which directors have shown initiative. I explained that I intended to use 73 this Fall to bring more light into the election of directors than they have ever seen before. I want to encourage intelligent dedicated amateurs to run for director and I am willing to devote space in 73 to their qualifications and their platforms. I also mentioned that I knew a simple way for the League to increase its yearly income by from \$250,000 to \$500,-

000. Only one director, Phil Spencer W5LDH from the Delta Division, answered my letter at all. Phil sent me a copy of the results of his ballot on 499, mentioning that Huntoon refused to publish it. No one showed even a slight interest in upping the ARRL income.

Point two of The Amateur's Code has always bothered me a bit. "The Amateur is Loyal . . . He owes his amateur radio to the American Radio Relay League, and he offers it his unswerving loyalty." Back in the early days of amateur radio there is no question that Hiram Maxim did preserve ham radio. But during the 28 years that I've been following the hobby I don't know of any instance where the ARRL saved ham radio. What has the present generation of HQ men done to earn our unswerving loyalty?

Back in 1958 there was growing concern over the 1959 Geneva Conference and ARRL's lack of any program to counter the almost universal demand for a reduction in the amateur bands. When I talked with the heads and important officials of clubs in Europe I found them extremely critical of ARRL leadership. In 1959 I attended the Geneva Conference as a delegate and watched the miracle which saved our skins: the USSR and its satellites supported the U. S. proposal to put off frequency allocation changes until the next conference.

On my visit to Europe last October I did not find any increase in confidence in ARRL. The problem seems mostly to be a lack of any program. First reports of the IARU Region 2 meeting in Mexico City in April tell us that the delegates from South and Central American radio clubs listened to Hoover and Huntoon try to explain the ARRL/IARU "program" and ended up so furious that they refused to join the IARU Region 2 and set up their own separate organization, complete with officers (Antonio Pita, president) the Interamerican Amateur radio Union. They did permit the ARRL to join as long as they picked up 90% of the bill (\$4500 worth of crow eating) for the meeting. Tempers flared and I understand that Hunty had to be shut up by the Panamanian delegate and was told that if he had anything else to say, to say it through his delegate, Mr. Dennison. (If I have any distortion of the actual facts I am most anxious to get corrections.)

73 is still unacceptable as an exhibitor at the Convention. Several manufacturers have written to say that they are going to pass it up as a result. I understand that the ARRL Directors were told that Harry Dannals W2TUK will be the official whipping boy for this one. Good

NEW
FROM
INTERNATIONAL

AOC*

SINGLE SIDEBAND FILTERS

- 9 mc center frequency
- Bandpass 6 db 3 kc (approximate)

ACF-2 Two-crystal filter circuit using low impedance link input and 2K resistive output load. Unwanted sideband rejection greater than 30 db. **\$9.95**

ACF-4 Four-crystal filter circuit using nominal 600 ohm input and output. Unwanted sideband rejection greater than 40 db. **\$18.95**


ACF-6 Six-crystal filter circuit using nominal 600 ohm input and output. Unwanted sideband rejection greater than 55 db. **\$27.95**

MATCHING OSCILLATOR CRYSTALS for the ACF filter series. Recommended for use in OS-4 oscillator.
CY-6-9LO **\$4.40**
CY-6-9HI **\$4.40**

OS-4 Crystal Oscillator **\$6.95**

SE-6F Mounting Case
Special AOC case for mounting filter plates. **\$5.50**

* Add-On-Circuit

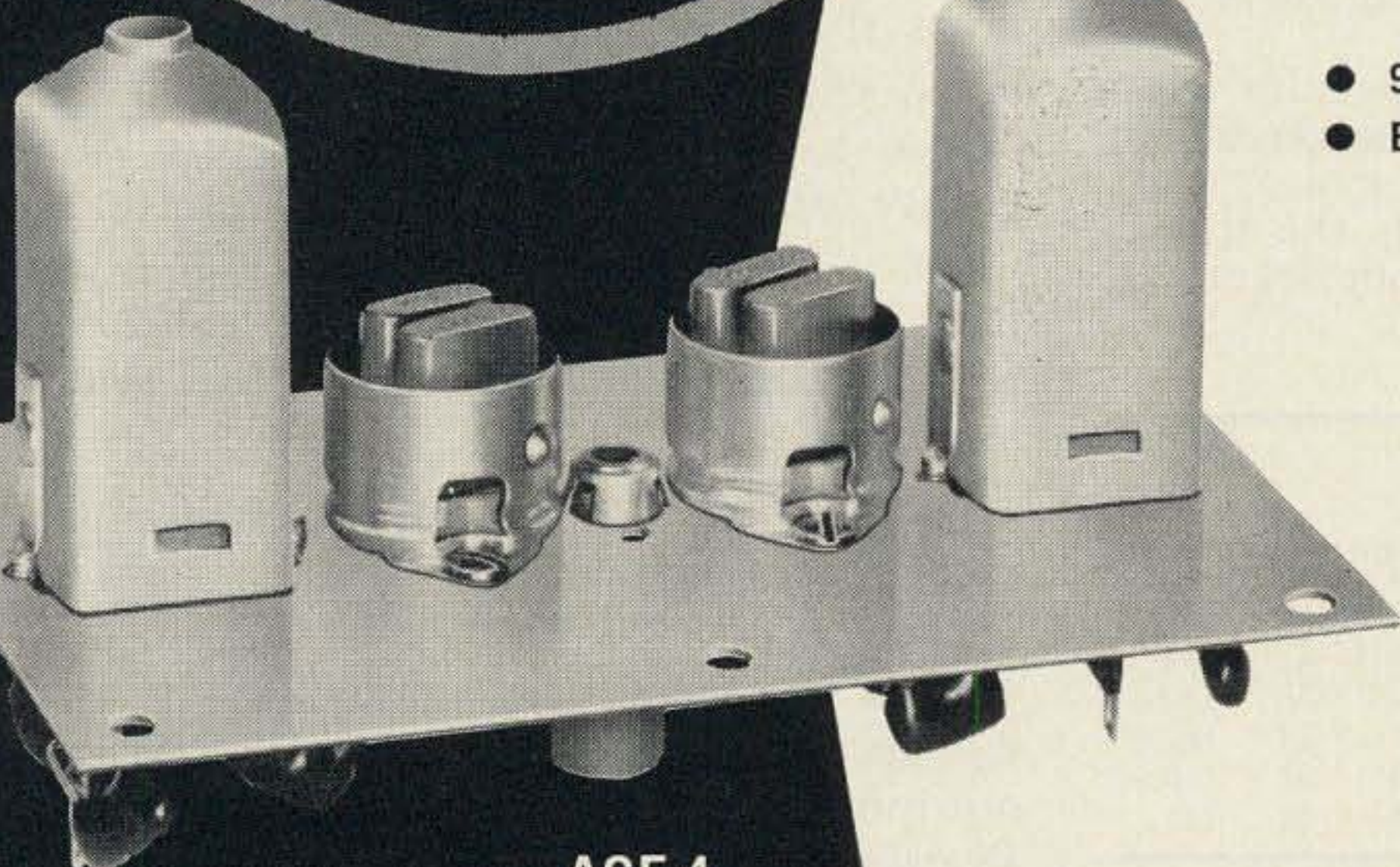

ACF-4



WRITE
TODAY
FOR
YOUR

FREE

1964
CATALOG

International Crystal Mfg. Co., Inc.
18 North Lee, Oklahoma City, Oklahoma
Please rush 1964 catalog.

Name _____

PLEASE PRINT


Address _____

City _____ Zone _____ State _____

**INTERNATIONAL
CRYSTAL MFG. CO., INC.**

18 NORTH LEE • OKLAHOMA CITY, OKLA.

the LEADER in CRANK-UP TOWER DESIGN

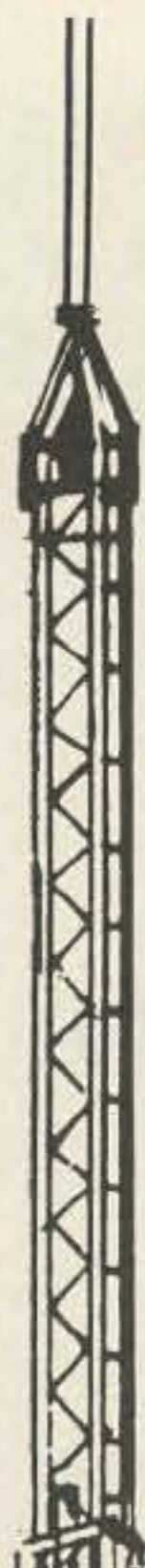

Only
\$955.00

The full-strength Hercules 66-3 has diagonal bracing—a unique feature in all E-Z Way Towers. It's designed to support a large 20 m or 40 m beam; 4 el. Du-band; or 6 el Triband Wind area 22 feet at 66 feet in 60 MPH winds.

The 3 sections of the Hercules telescope from a minimum height of 30 feet to a maximum 62 feet.

A worm gear winch tilts the tower over for easy access to your beam.

MODEL TORBZ 66-3

WIND LOAD CHART

Model	Ant. Wind Area	Full Hgt.	Height MPH	Half Hgt.	Height MPH	Min. Hgt.	Height MPH
TORBZ 66-3	22.2	66	60	50	86	32	125
TORBZ 66-3	13.2	66	75	50	90	32	140
TORBZ 66-3	8.2	66	90	50	100	32	150
TORBZ 75-3	17.0	75	60	55	86	33	125
TORBZ 75-3	10.0	75	75	55	100	33	140
TORBZ 88-3	12	88	60	65	86	38	140

NEW E-Z WAY HERCULES


DELIVERS THE ULTIMATE IN TOWER POWER

HERCULES	Painted	Galvanized
TORBZ 66-3	955.00	1,095.00
TORBZ 75-3	1,055.00	1,240.00
TORBZ 88-3	1,187.50	1,393.50

100' 115' Heights available

MOTOR WINCH

The E-Z Way Motor Winch raises and lowers towers to any height without guys. When towers are motorized a larger beam can be used because the tower is normally lowered to safer elevations. Standard features: Combination worm gear drive; totally enclosed motor and gear box; remote control switch; spiral grooved winch drum; positive crank down and limiter switches. Assembled complete with hardware and instructions, just \$389.50 for TORBZ 66-3; \$399.50 for TORBZ 75-3 and \$495.00 for TORBZ 88-3.

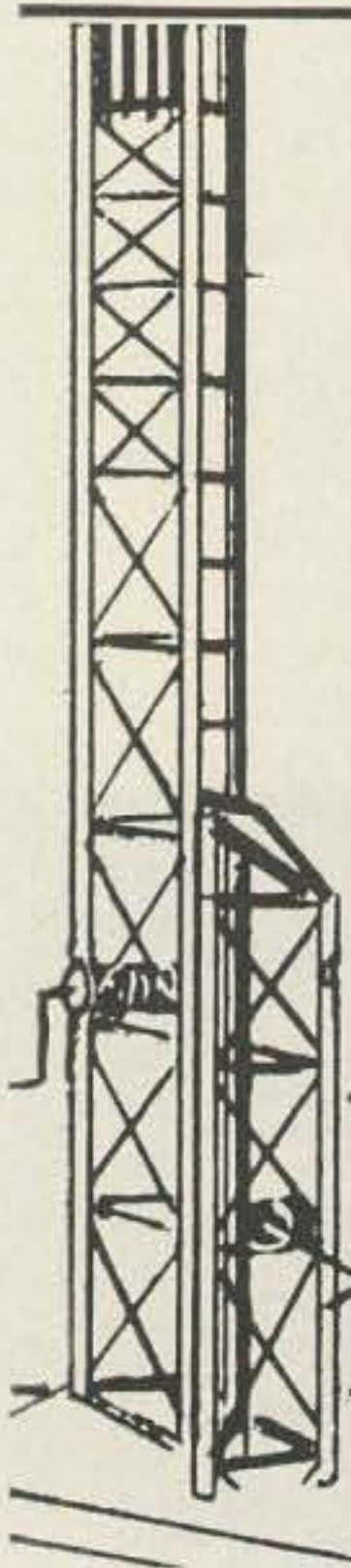

**E-Z WAY
TOWERS, INC.**

**5901 E. BROADWAY
TAMPA, FLORIDA**

choice. Should he decide to run for Hudson Division Director this fall we'll bring you a fascinating resumé of this guy.

Amateurs visiting the Fair will want to see the ARRL Sponsored station K2US in the Coca-Cola pavilion. It is difficult to find without exact instructions for it is well out of the path of the normal Fair goer. When you enter the Coca-Cola pavilion do not follow the main stream of the crowd off to the left, instead look for a stairway over on your right. Go up two and a half flights and then you'll see a small room with a place for a few people to peer through the glass. Only official HARC ops can operate the station, despite the ad in QST that all you have to do is show your ham license and you can operate. It is hard to believe the reports that the \$75,000 a year man for Coca-Cola who made the deal with Hunty was forced to resign as a result. I don't know why Hunty decided that only Hallicrafters equipment could be used at K2US and I don't believe any of the explanations I've heard so far. It is a shame that Hallicrafters had to get stuck in the middle of this.

Enough people got upset over this whole matter so that the Pan American Radio Club in New York got permission to set up a ham station right on the ground floor of the Venezuelan Pavilion. This station, set up with equipment by National, Galaxy, Hammarlund, Waters, etc., will be on view to the millions of Fair goers and should accomplish the purpose of the ill-fated ARRL exhibit. The call of this station is WA2USA. All of us should be thankful for the interest and industry of this club which has resulted in ham radio really being seen at the World's Fair.

I notice that attention is being called to calls other than W2NSD that I have. The big station on 73 Mountain is licensed as W2NSD/1. The station at our HQ building is K1FYP. I also have a CB call of 2W3519 which was used last year in the hunt for a lost boy on 73 Mountain using two Johnson Messengers. I also have NØAOE in Navy MARS and used to have AF2NSD, XEØNSD, W4NSD,, FL8NSD, KC4AF, FØ8AS and others.

Speaking of the Mountain, we got back up there the other day for the first time since the snow melted and found that everything was in good shape. All of the towers and beams were still up in place. With the great emphasis that we are putting on the Institute I didn't see how we would be able to get the shack set up in time for the June QST contest. The 288 element two meter beam still has to have feed-

(Turn to page 75)

**from 2
to 160
meters**



relax...
for the **BEST**
in HF and VHF
listening

HAMMARLUND'S **NEW HQ-170A-VHF** *the only* receiver capturing all popular Ham Bands.*

The exciting HQ-170A-VHF is the **first** and only Ham Band receiver that gives you **everything** you want. Separate NuVistor front ends ($0.3\mu\text{V}$ for 10 db S/N) for both 6 and 2 meters completely eliminates the need for add-on converters or jury-rigged adaptations. Built-in 6 and 2 meter operation employs **matched circuitry** for outstanding performance.

Here is an SSB receiver that combines basic operating excellence with all of the extra features you want to make it a versatile, "fun-to-work-with" unit. Full coverage from 2 to 160 meters, excellent electrical and mechanical stability, expanded vernier tuning and a host of truly incomparable HQ-170A features makes this receiver the new **First Choice** for the amateur fraternity.

The HQ-170A-VHF is the most versatile, and most **complete** amateur band receiver now available on the market—one neat package contains all the flexibility you need—superlative AM, CW and SSB reception on **All** popular amateur bands.

**Coming soon—Matching transmit accessories
for the Fabulous HX-50.**

*Except for the Hammarlund HQ-110A-VHF



HAMMARLUND
MANUFACTURING COMPANY
A GIANNINI SCIENTIFIC COMPANY
53 West 23rd Street, New York 10, New York

I'm interested. Please send HQ-170A-VHF info to:

Name _____
Address _____
City _____ Zone _____ State _____


6 Meter AM and SSB Transmitter from the T-51A/ARQ-8

Leroy May W5AJG
9428 Hobart St.
Dallas 18, Texas

Photo credit: Jim Dungan, Dallas

The T-51A/ARQ-8 transmitter was one of a series of Radar Jamming units used in WWII. Exact operating details of this transmitter are not known to the writer but apparently consisted of a variable self-excited oscillator tube (6V6), driving an 832A mixer stage and this in turn driving the final 832A, or in some cases, an 829B. A noise source was injected into the 832A mixer stage via its grid circuit and mixed with the excitation from the 6V6 oscillator tube.

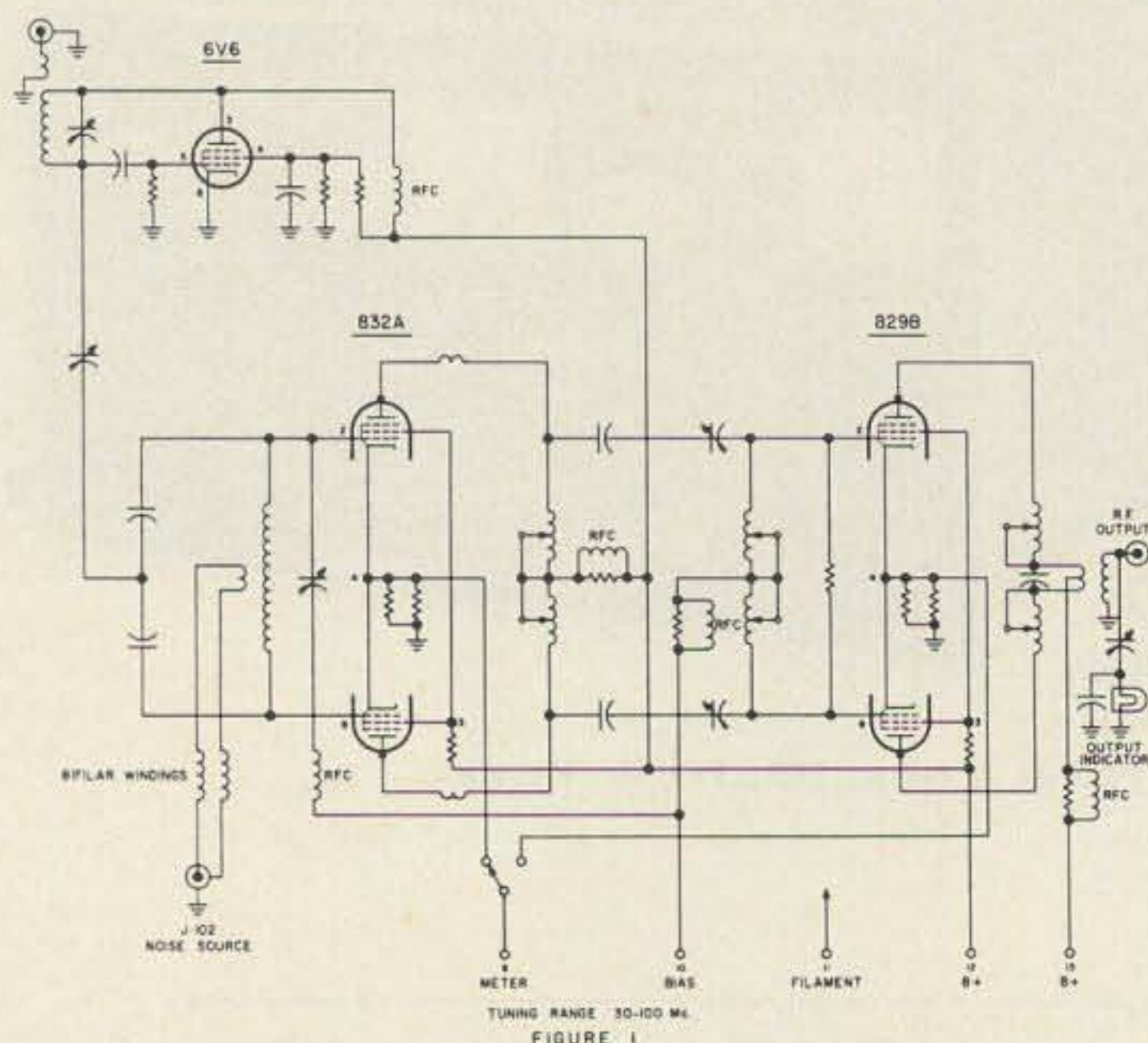The frequency range was from approximately 30 mc to 100 mc, and made use of roller coil inductors (rollo coils), rather than the conventional LC circuits. This enabled the unit to cover this wide range of tuning. Some of the equipment came equipped with an 832A in the final stage and some units contained an 829B tube.



Original schematic

Upon inspection, it was felt this transmitter could be modified into a decent 50 mc unit without too many changes. This was done some four years ago and has since rendered excellent service. Actually, the unit is easily converted into an SSB exciter as well, and this was done at the same time with a second identical unit. The SSB version will be described later.

As an AM transmitter and/or exciter, this modified unit can use either an 832A in the final with an output of about 20 watts, or an 829B, with up to about 60 to 65 watts output. This represents 100 watts or so input power, in the latter case. This is the condition which we will describe.

The original circuit was wire traced and is drawn out in Fig. 1. The modified 50 mc AM transmitter is shown in Fig. 2. On the modified schematic, the original components are left unmarked, while the added or changed parts are so indicated with their values. This modified unit may be modulated, and if so, a modulator of about 50 watts or so will be required. The 829B operates as a Class "C" amplifier. A jack is provided for CW operation—and under such operation, the input can be jacked up a bit higher still, without damage to the 829B. Should the transmitter be used as an exciter to drive something more powerful, the T-51A/ARQ-8 plate voltage may be reduced until the minimum desired power output is reached to properly drive the high powered final.

Modifications

The photograph will show that the T-51A/

ARQ-8 has been mounted on a standard 7 inch rack panel by providing a square cut-out on the left and then fitting in the panel of the unit. It will be necessary to provide some additional enclosure shielding, since the original unit contains nothing in this line—having fitted into another type of case configuration. The rear photograph shows the works, less the aluminum back cover plate, but the shielding requirements may be gleaned nevertheless.

The first step in the modification process will be to scuttle the self-excited 6V6 oscillator tube and insert in its place, a crystal-controlled oscillator-doubler using a type 6AG7 tube in a familiar grid-plate arrangement. The crystal used is the common 8+ mc variety, and the 6AG7 plate coil is resonated to the second harmonic of the crystal, or 16+ mc. From this point, the excitation at 16+ mc is fed into the rearranged 832A tube which formerly was a mixer, but now will function as a push-pull tripler to 50 mc. This tube will in turn drive the final 829B stage as the straight through Class "C" amplifier.

The 832A tripler tube is lightly loaded and easily provides the necessary excitation to the 829B stage. In the grid circuit of the tripler the original grid coil is changed out to another type and the link from the 6AG7 is fed into the middle of this new coil. The 832A tripler plate circuit will use the original rollo coil. About 250 volts dc is ample for this

stage plate supply.

The 829B final stage comes in for a bit more of a change, especially in the plate circuitry. The grid circuit of this stage will again use the original rollo coil for its tuning but the plate circuit makes use of a new LC combination. The reason is this: when the input power to the final 829B is stepped up to around 100 watts or so and the output runs in the vicinity of 65 watts, the original rollo coil in the plate circuit exhibits a bit too much heating and the rather small sliding contacts used in contacting the individual turns of the coil may start arcing when the unit is tuned under power. This condition cuts down on the efficiency of the final stage and prolonged transmission causes excessive heating. It was felt best to provide for something a bit more husky. This took the form of a dual-section, double-spaced variable capacitor and a new tank coil made of No. 12 enamelled wire, with a new two turn output link. If an 832A is substituted in the final, or if the 829B tube is throttled down in power input, this change in the final tank coil will not be necessary. No decrease in efficiency was noted when the power output was in the order of 20 watts or so, nor was heating any problem, so the removal of the original rollo coil will depend on just how far the user wishes to push the final stage.

Referring to the modified schematic, the only other additions of any import would be


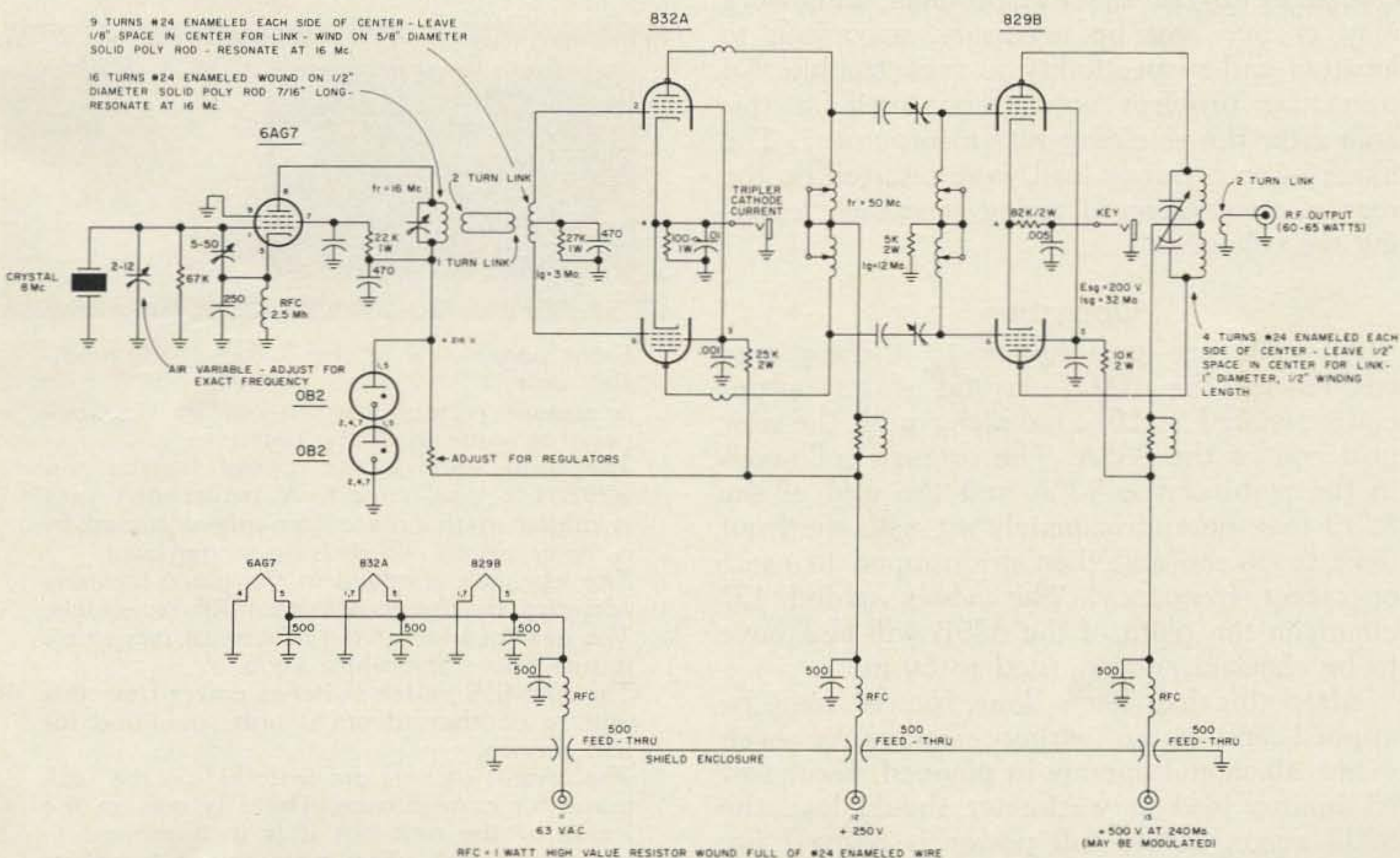


FIGURE 2
Modifications for AM

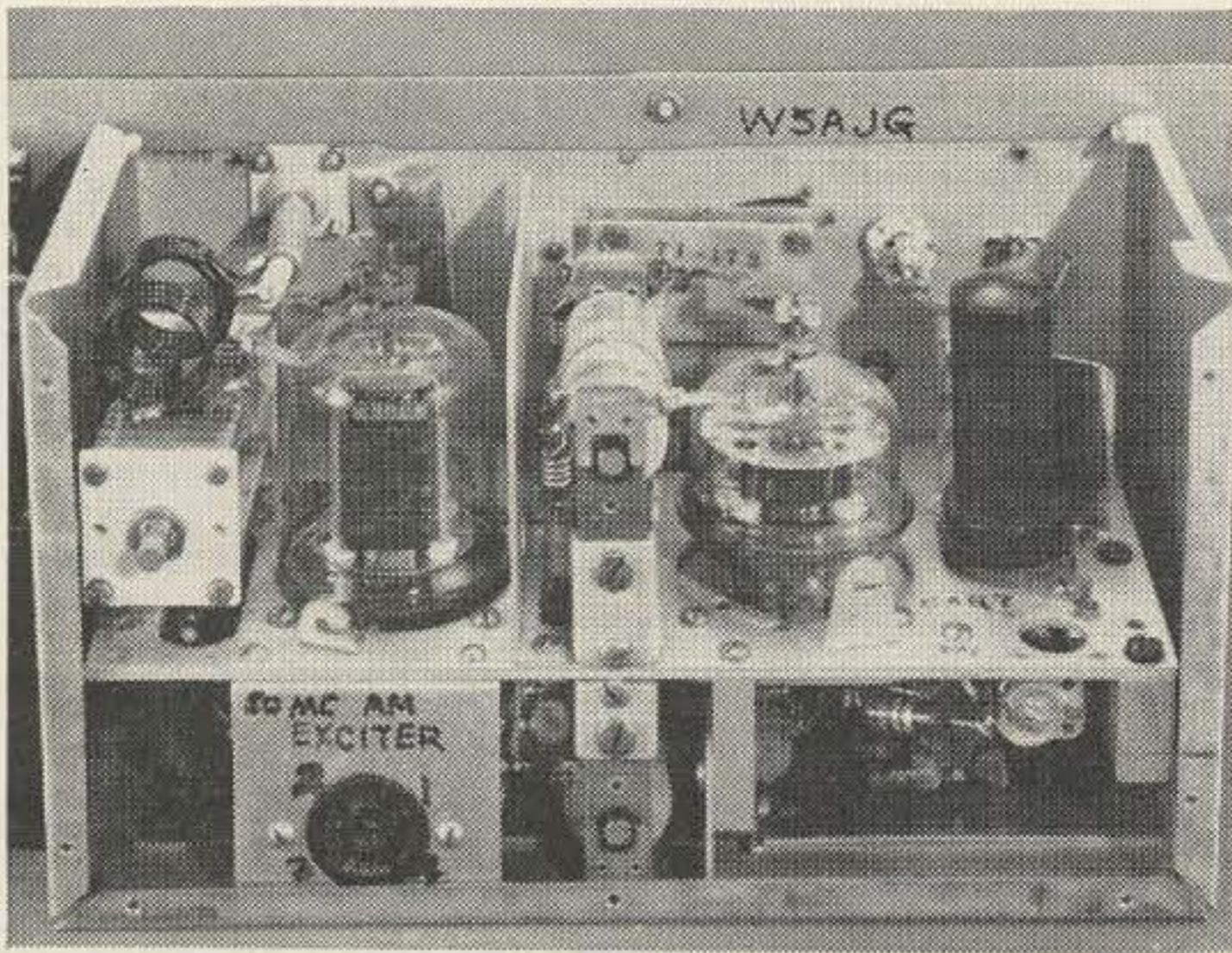

Rear view of T-51/ARQ-8 unit. 829B final on left of partition. 832A tripler and 6AG7 osc-doubler on right. New 829B tank coil and capacitor can be seen, with output link tied into the coax output receptacle. On the right the 6AG7 xtal oscillator and doubler tube replaces the original 6V6 self excited oscillator. The xtal trimming condenser is mounted on the panel. This allows exact freq. operation on nets, etc. (MARS). A box is formed of aluminum for shielding. The back and top plates are removed for the photo. Power is fed in on the 4 prong receptacle.

Note: Since photo was taken, the above 4 prong receptacle has been replaced with a 5 prong MALE receptacle for safety purposes.

the filtering of the power leads. This is, of course, to obviate the TVI problem. This work may or may not be necessary, according to location and susceptibility to such trouble. No particular problem was encountered in this area after the shielding was incorporated. The filters in each power lead were inserted on the rear of an ordinary 4 prong receptacle carrying the voltages.

Operation

All coils are grid-dipped to their proper frequencies—the 6AG7 crystal stage output coil resonated at 16+ mc along with the new grid coil of the 832A. The original rollo-coils in the plate of the 832A and the grid of the 829B may be approximately set with the front dials to 50 mc and then grid-dipped to exact operating frequency. The newly added LC circuit in the plate of the 829B will also have to be checked and adjusted to 50 mc.


After this has been done, power may be applied and if no wiring errors have been made, all should operate as planned. Some sort of dummy load or wattmeter should load the 829B stage, before full power is revived up. The tripler cathode current will measure about 20 to 25 ma, while the final 829B

cathode current (measured in key jack) may be run up to 240 or 250 ma or so with about 500 volts on the plate. This value will include 30 or 35 mills of screen current. Grid current to the final should measure 10 to 12 ma.

The low voltage tap of 250 volts dc should be capable of around 50 ma and may be a separate supply or any other way of providing such capability. Keying may also be accomplished by inserting a key in the "Tripler Cathode Current" jack if cut-off bias is furnished for the 829B final tube. This would be in the order of some 50 volts or so.

Should the unit be used as a complete AM Phone transmitter, the modulation transformer secondary should be inserted between terminal 13 and the power supply. Here at W5AJG this unit is used to drive a push-pull 4X250B final amplifier to 600 watts input when high-level, Class "C" AM operation is desired. The rf drive requirement in this instance is only approximately 10 watts or less so the T-51A/ARQ-8 just loaf along. The actual plate voltage on the final is reduced to 250v and plate current runs about 90 ma for our particular requirements as an exciter.

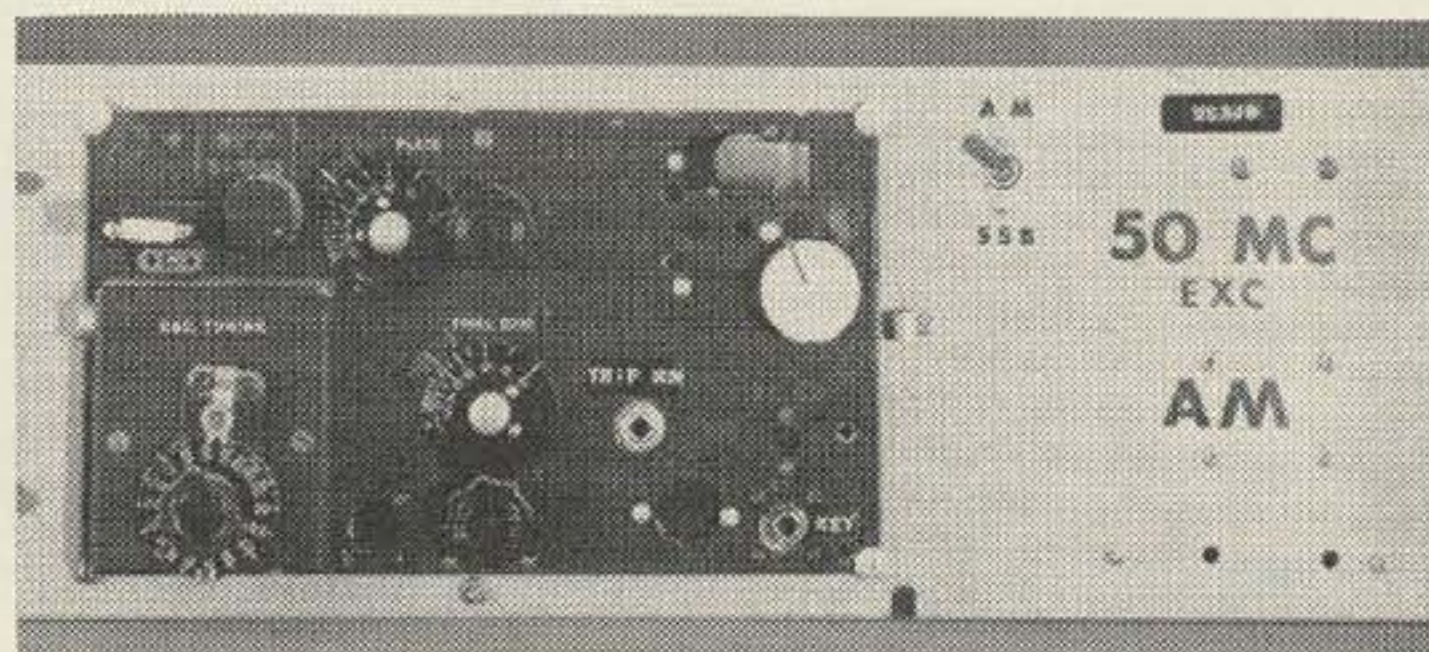When it is desired to use the 4X250B final as a KW PEP linear in SSB service, the second T-51A/ARQ-8 unit modified as an SSB exciter-driver is switched into service in place of the above described AM unit.



Front panel view of the T-51A/ARQ modified unit.

A square rectangular cut-out in the rack panel is made to fit the unit into.

The white knob is the control for the new 829B LC tank circuit. A tripler MA jack is added in the place formerly occupied by a meter switch, which is no longer used.

The key jack is added in the place formerly occupied by the coax output RF receptacle. The new location of the RF output receptacle is just above the white knob.

The AM-SSB switch switches power from this unit to another identical unit, modified for SSB service.

The crystal sockets are installed on the rack panel for convenience. There is one on the inside of the unit but it is inconvenient to change crystals. Two different xtal sockets are wired in parallel so as to accommodate surplus type as well as FT243 type crystals.

BRAND NEW DRAKE MODEL R-4 RECEIVER




Model MS-4 Matching Speaker **\$19⁹⁵**

Model R-4 **\$379⁹⁵** AMATEUR NET

FEATURES

- Linear permeability tuned VFO with 1 KC dial divisions.
- Covers ham bands 80, 40, 20, 15 meters completely and 28.5 to 29.0 Mc of 10 meters with crystals furnished.
- Also covers 160 meters, Mars, Citizens Band, WWV, Marine, and short wave broadcasts. (With accessory crystals.)
- Or will give 5 Mc of continuous coverage (with accessory crystals) for use with VHF converters.
- Or tunes any ten 500 KC ranges between 1.5 Mc and 30 Mc with accessory crystals; 5.0 to 6.0 Mc not recommended).
- Four bandwidths of selectivity (equivalent to 4 filters) are furnished: 0.4 KC, 1.2 KC, 2.4 KC and 4.8 KC.
- Passband tuning
- Noise blanker that works on CW, SSB, and AM; Notch filter; and 100 KC crystal calibrator are built in.
- Crystal lattice filter 1st IF
- Premixed injection — Crystal oscillator and low frequency VFO outputs premixed.
- AVC with fast attack and slow release for SSB or fast release for high speed break-in CW. Also AVC may be switched off.
- Receives SSB, AM, CW, and RTTY with full RF gain, complete AVC action and accurate S-meter indication.
- Product detector for SSB/CW—diode detector for AM.
- Excellent overload and cross modulation characteristics; insensitive to operation of nearby transmitters.
- Compact size; rugged construction.
- Transceive capability; May be used to transceive with the T-4 "Reciter" or T-4X Transmitter.
- 13 tubes and 7 diodes.

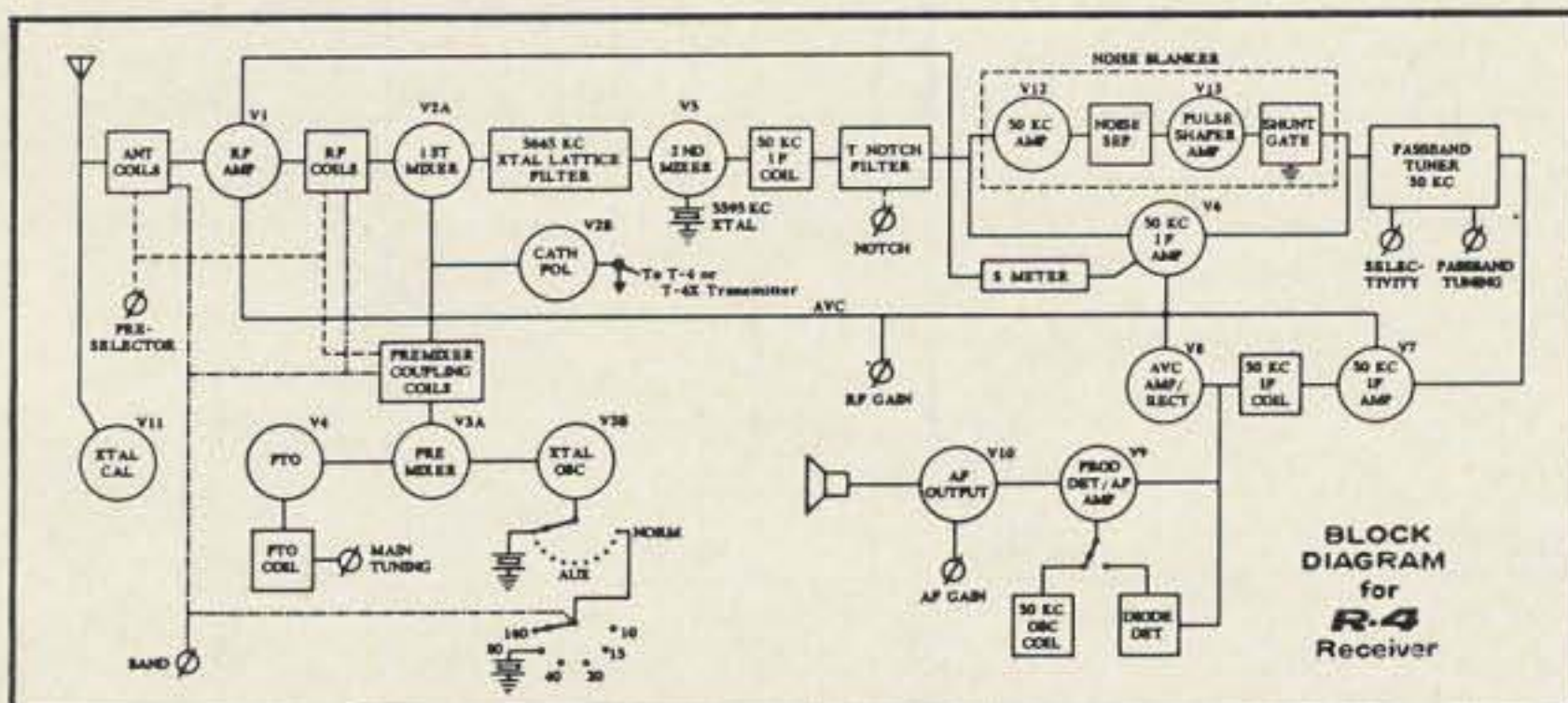

See your distributor or write for free brochure.

R. L. DRAKE COMPANY
MIAMISBURG, OHIO

SPECIFICATIONS — Model R-4

FREQUENCY COVERAGE: 3.5-4.0 Mc, 7.0-7.5 Mc, 14.0-14.5, 21.0-21.5, and 28.5-29.0 Mc with crystals supplied. Ten accessory crystal sockets are provided for coverage of any 10 additional 500 KC ranges between 1.5 and 30 Mc with the exception of 5.0-6.0 Mc.

SELECTIVITY: Drake tunable passband filter provides:

- .4 KC at 6 DB down and 2.6 KC at 60 DB down
- 1.2 KC at 6 DB down and 4.8 KC at 60 DB down
- 2.4 KC at 6 DB down and 8.2 KC at 60 DB down
- 4.8 KC at 6 DB down and 25 KC at 60 DB down

Selectivity switching is independent of detector and AVC switching.

I.F. FREQUENCIES: First I.F.—5645 KC crystal lattice filter; second I.F.—50 KC tunable L/C filter.

STABILITY: Less than 100 cycles after warm up. Less than 100 cycles for 10% line voltage change.

SENSITIVITY: Less than 1/2 uv for 10 DB signal plus noise to noise on all amateur bands.

MODES OF OPERATION: SSB, CW, AM, RTTY.

DIAL CALIBRATION: Main dial calibrated 0 to 500 KC and 500 to 1000 KC in 5 KC divisions. Vernier dial calibrated 0 to 25 KC in 1 KC divisions.

CALIBRATION ACCURACY: Better than 1 KC when calibrated at nearest 100 KC point.

AVC: Amplified delayed AVC having slow (.75 sec.) or fast (.025 sec.) discharge; less than 100 micro-second charge. AVC can also be switched off. 3 DB change in AF output with 60 DB change in RF input.

AUDIO OUTPUT: 1.4 watts max. and .5 watts at AVC threshold.

AUDIO OUTPUT IMPEDANCE: 4 Ohms and hi impedance for anti-vox.

ANTENNA INPUT: Nominal 52 Ohms.

SPURIOUS RESPONSES: Image rejection more than 60 DB. I.F. rejection more than 60 DB on ham ranges. Internal spurious responses in ham ranges less than the equivalent 1 uv signal on the antenna.

FRONT PANEL CONTROLS: Main tuning, AF gain, RF gain, AM-SSB/CW with slow AVC, fast AVC, or AVC off, function switch, band switch, xtal switch, passband tuning and selectivity, preselector, notch, and headphone jack.

REAR CHASSIS JACKS AND CONTROLS: S-meter zero, notch adjust, antenna jack, speaker jack, mute jack, anti-vox jack, accessory power socket, and fuse post.

POWER CONSUMPTION: 50 watts, 120/240 VAC, 50/60 cycles.

DIMENSIONS: 5 1/2" high, 10 3/4" wide, cabinet depth 11 5/8", overall length 12 1/4", weight 16 lbs.


AVAILABLE ACCESSORY: Model MS-4 matching speaker cabinet with high efficiency 5 x 7 speaker. Cabinet also houses the power supply for the T-4 or T-4X matching transmitters.

SSB Conversion: Another identical T-51A/ARQ-8 unit was converted into a 50 mc SSB exciter or transmitter. Using the same technique of changing final amplifier tube types, the PEP SSB input can be anything from about 35 watts to 150 watts. Should the unit be used as a driver for a higher powered AB1 amplifier, the output can be lowered by using the smaller final tube, while the larger tube may be used should the T-51A be utilized as a complete transmitter.

Modifications

Since the requirements at this station dictated the modified unit be used for exciter service to drive a 4X250B push-pull final, running the maximum power, the drive requirements were very modest and the lighter 832A tube was used in the final stage, instead of the heavier 829B tube. However, both conditions will be described and typical characteristics will be listed.

Referring to the two photos and the unmodified schematic as well as the modified schematic (Fig. 3), it can be seen that this conversion, like the previous one, mounts the unit on a standard 7 inch rack panel, in precisely the same way as before. Also followed, is the identical arrangement of enclosure shielding on the rear of the panel. The rear view illustration shows this once again, with the top and back aluminum shields having been removed.

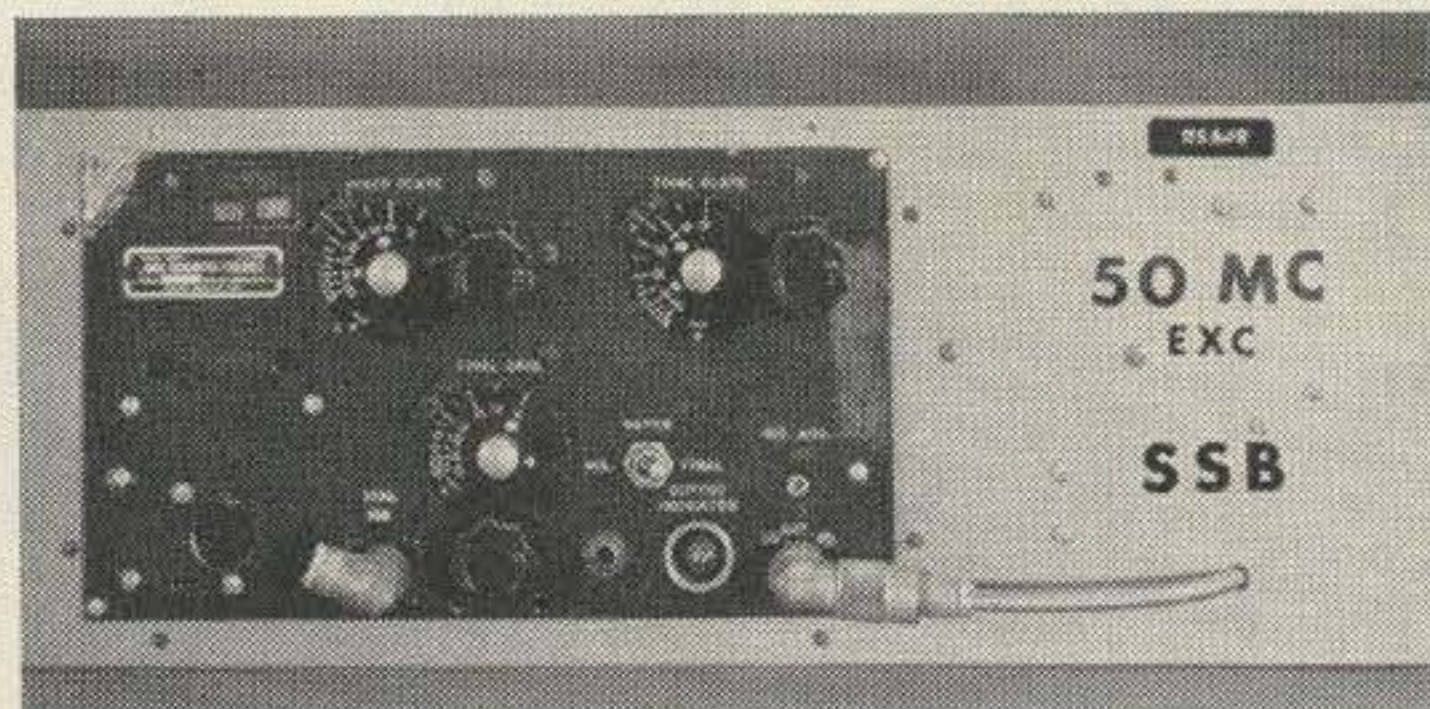

Front panel view of modified T-51A/ARQ-8 unit. Unit is mounted on a standard 7 inch relay rack panel. Original oscillator tuning capacitor dial has been removed. 21 mc SSB input energy goes into the coax receptacle so marked.

The phone jack is for the plugging in of a mill-meter to measure cathode current of the mixer and final.

The first step in this SSB conversion will be to replace the original 6V6 self-excited oscillator tube and substitute a crystal controlled oscillator-buffer stage using a type 6U8 tube. Before we do this however, a word about the proper injection frequency and the appropriate crystal frequency necessary.

All VHF SSB work at this station is done with a basic Central Electronics 20A unit and at an output frequency of 21 mc. Therefore, the wanted crystal injection frequency will be around 29 mc. Since the 50-54 mc band will take in 4 mc and since vfo used with the 20A does not cover but 500 kc, it will be necessary to have more than one crystal to use with the T-51A unit if the full 4 mc range must be

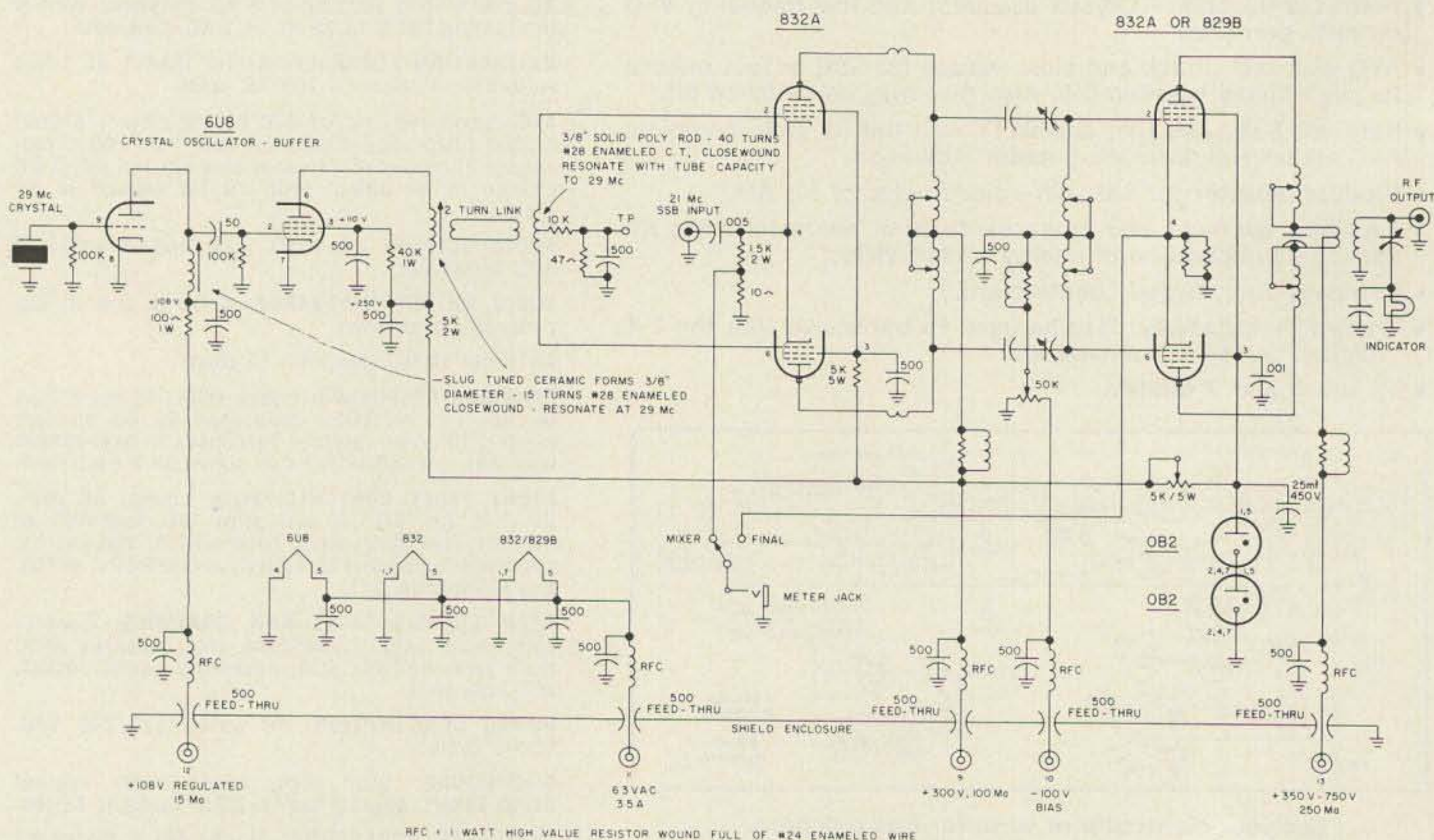



FIGURE 3
Modifications for SSB

covered. This is a common occurrence these days, even with expensive manufactured equipment. One will just have to choose the portion of these wide bands that most appeal to his needs and furnish crystals to cover these segments. Since most side-banders on 50 mc still seem to favor low end operation, it will probably be the most desirable to cover the first 500 kc of the 6 meter band, at least for a start.

This being the case then, a crystal of 29 mc for the injection string will be used. This added to the 21 mc SSB from the 20A will mix in the first 832A mixer tube to produce the desired 50 mc output. The final 829B (or 832A) will then serve as the class AB1 linear output stage.

Other frequencies than 21 mc for the SSB energy may be used, of course. 14 mc is widely employed for this same purpose from the SSB generator and should this frequency be desired, it will merely be necessary to change the crystal string to 36 mc, instead of the 29 mc as shown. This merely involves three coil forms and is of small significance.

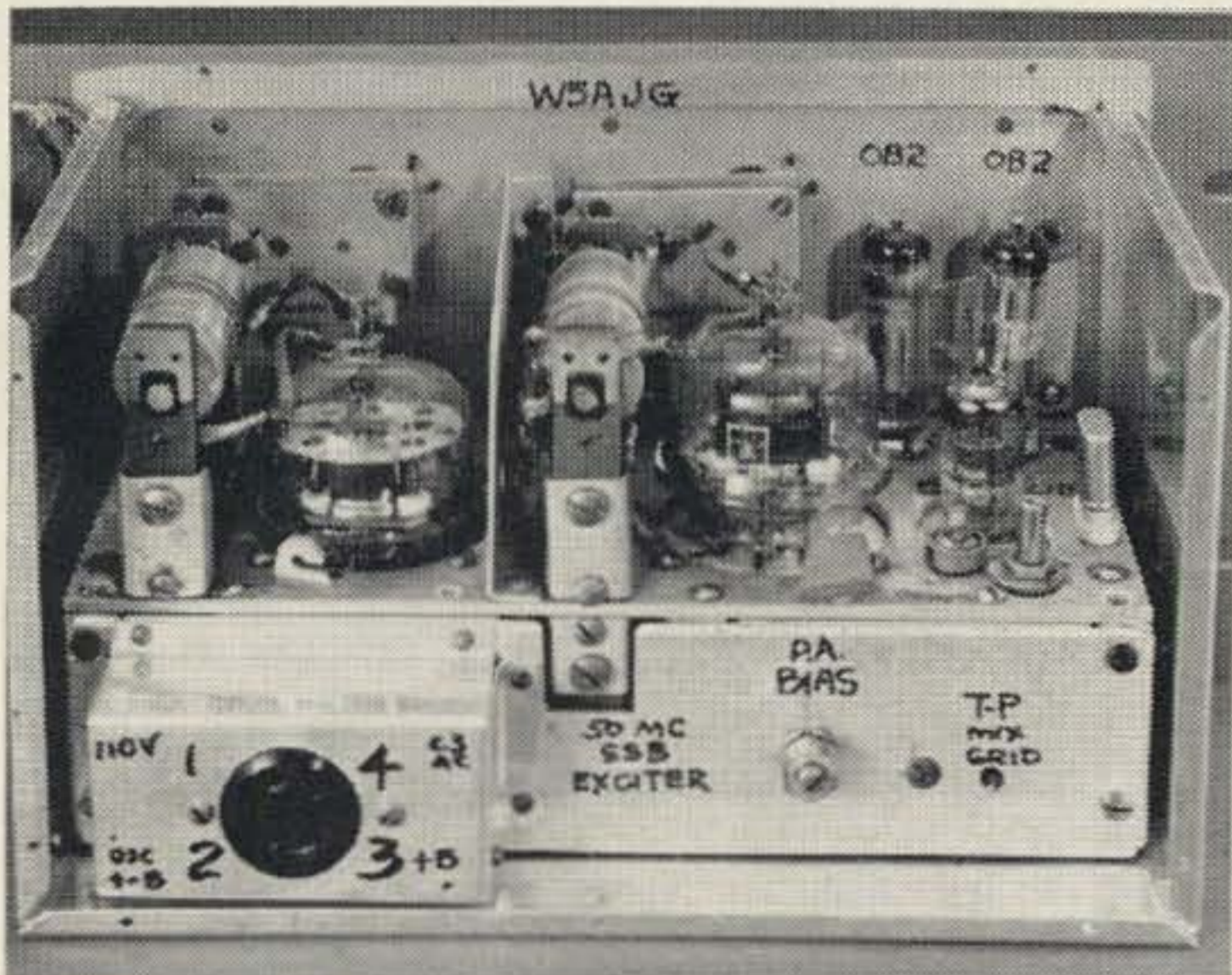Back to the 6U8 oscillator-buffer. For good stability, the oscillator plate voltage supply is regulated at 108 volts. This low voltage is entirely adequate as the pentode section of the 6U8 will furnish sufficient drive for the 832A



Rear view panel photo of the T-51/ARQ modified unit.

Final shows 832A tube in place, but 829B tube may be inserted for additional power output. New 6U8 xtal-oscillator, buffer tube at right. 29 mc xtal also seen. OB2 regulator tubes in series, regulate the final screen voltage. Capacitor with slotted shaft is not used and has no function.

Power input is 4 prong socket at left. Since photo was taken, this female socket has been changed to a male type for safety reasons. The 110V (Pin 1) on this socket is fed from a small 6.3v to 115v transformer reversed. This transformer is located at another point than the unit itself, and is not visible in this photo.

\$59.95
amateur net



Introducing the TR-44, a high-performance rotor system for the Amateur on a budget who's ready to upgrade his antenna installation.

The TR-44 approaches the accuracy and ruggedness of the famous Cornell-Dubilier HAM-M but is designed specifically for intermediate loads.

Check these features:

- Control box contains the HAM-M meter.
- Dimensionally identical to TV rotor types AR-22, TR-2 and TR-4. The TR-44 even fits the same bolt holes!
- End of rotation electrical motor cut-off.
- No mechanical clanking, no electrical pulse noise.
- Increased rotational torque...up to twice as much as TV rotors!
- 48-ball bearing movement.
- New idiot-proof brake system.

If you are now getting marginal results using a TV rotor, the TR-44 is for you! It will give you the increased torque, braking and accuracy that are needed for large VHF arrays and small HF combination antennas. For technical information, contact Bill Ashby K2TKN or your local CDE Distributor.



CDE makes a complete line of the world's finest rotors: the HAM-M; the new TR-44; heavy-duty automatic TV; heavy-duty manual TV; standard-duty automatic TV; standard-duty manual TV; and the industry's only wireless remote control rotor system! Cornell-Dubilier Electronics, Div. of Federal Pacific Electric Co., 118 East Jones St., Fuquay Springs, N. C.

CDE **CORNELL-DUBILIER**

the only Company that makes them all

mixer grid. A couple of ordinary slug tuned coils are utilized in this stage. They should resonate at 29 mc and the output buffer has a link of a couple of turns on its cold end to couple to the new 832A mixer coil. This added coil is also resonated with tube capacity to 29 mc. Normally, no external front panel tuning is necessary on this stage and when the slugs are once set for maximum output, they need not be changed unless one moves a megacycle or so; therefore, the original tuning dial for the old original 6V6 stage is removed from the front panel.

The 21 mc SSB input from the 20A is injected into an existing coax receptacle, marked OSCILLATOR, mounted out front, but it is rewired into the 832A mixer tube cathode instead of into the grid circuit as per the original installation, (J102). An effort was made to use the same type injection scheme as per the original installation—that is, mixing the injection frequency as well as the external frequency (SSB) in a common point through the original bifilar wound coils and J102. While this did work after a fashion, instability was encountered with certain setting of the rolo coils. Apparently a TNT action took place. With cathode injection of the SSB energy, no instability could be made to occur with any setting of the tuned circuits. Control grid as well as screen grid injection of the SSB energy were also tried and all were about on a par with cathode injection, so any method could actually be used. Cathode injection is easy to accomplish. Any SSB exciter like the 10B or 20A with a few watts output is sufficient for driving.

To continue: the 832A mixer plate circuit will use the original rolo coils, as well as the grid circuit of the final tube. Plate and screen voltage on the 832A mixer is derived from a power supply of 300v capable of about 100ma drain. This supply will also furnish power for the pentode section of the 6U8 buffer, and in conjunction with a couple of series OB2's (regulators), the screen voltage for the final tube screen.

The plate circuit of the final tube will likewise use the original rolo coils and as stated in the preceding on the AM version of the T-51A, no heating will be experienced in this low duty cycle SSB work, which is in contrast to the heavy duty cycle of AM type operation. Therefore, the output circuit of the final will remain practically intact, even to the existing indicator (rf) light feature, should you find this is attractive. It will be necessary to provide some fixed bias for the final 832A/829B linear stage. This can be conveniently done with a small

silicon diode rectifying the 115v ac provided by a reversed 6.3 to 115v ac transformer, and providing a variable pot for proper adjustment. This pot is mounted on the rear apron of the chassis and the negative bias of about -90 volts is brought in on terminal 10 of the original terminal strip. The proper adjustment of this control will be covered very shortly.

The original meter switch is left intact on this version of the unit and in conjunction with a jack installed on the panel, is convenient to check the cathode currents of the mixer and PA stage. Other details of construction, such as the necessary shielding and the filtering of the power leads will be identical with the previously described unit.

Operation

Install either the 832A or the 829B in the final stage according to power output required. Plate voltage should be supplied from an external source of from 500 to 750 volts maximum. For full output, the supply should be capable of about 250 ma or so. The only change necessary from using one tube or the other will be the screen grid dropping resistor from the 300 volt supply. This will have to be adjusted a bit to provide proper operation of the OB2 regulators. This variable resistor can take the form of a 5k, 5 watt unit and will allow either tube to be used.

All the coils are grid-dipped to their proper frequency. The two slug tuned coils associated with the 6U8 want to resonate at 29 mc approximately. Same for the grid coil of the 832A mixer. The rolo coils of the mixer plate, the final grid and the final plate, will of course, be set at 50 mc. This can be done fairly closely, for a start, with the front panel dials.

After this has been done, power may be applied and if all wiring is OK, things should start to happen. To begin with, do not apply any SSB energy. With the switch set to check the cathode current of the final stage, set the negative bias pot until the resting cathode current is about 18 or 20 mills. This will do for now. The test point "T-P" in the mixer grid circuit may be checked at this point, and the crystal injection string from the 6U8 peaked up, until a maximum is indicated, as read on a sensitive VOM. Checking the cathode current of the 832A mixer should show around 15 mills or so. No output should be observed from the final as yet.

Now connect the SSB 21 mc input up to the front panel coax-receptacle and turn on the 20A or whatever unit is used. Crank in a bit of re-inserted carrier and trim the three rolo coils until some 50 mc output is indicated in

NEW

Cush Craft

SQUALO*

6-10-11-15-20 or 40 METERS


Cush Craft's continuing research produces another first —THE SQUARE HALO. Squalo is a full half wave, horizontally polarized, omnidirectional antenna. Outstanding all around performance is achieved through a 360° pattern with no deep nulls. Full size and compact dimensions provide a low Q for broad band coverage. Direct 52 ohm Reddi Match feed gives an SWR of 1.5-1 or less from 50 to 51 Mc.

The 6 and 11 meter Squalos are packaged complete with rubber suction cups for car top mounting and a horizontal support for mast or tower mounting. The 10-15-20 and 40 meter Squalos are designed for mast or tower mounting where space does not allow for larger antennas. Squalo is ideal for net control, monitoring, or general ham coverage.


Whether you are a beginner, apartment dweller, or serious DX man the space saver Squalo is for you. You can buy one for each band and build a Squalo Tree!

Model No.	Description	Net Price
ASQ-6	6 meter 30" square	\$12.50
ASQ-10	10 meter 50" square	19.50
CSQ-11	11 meter 50" square	19.50
ASQ-15	15 meter 65" square	23.50
ASQ-20	20 meter 100" square	29.50
ASQ-40	40 meter 192" square	66.50

ON YOUR CAR

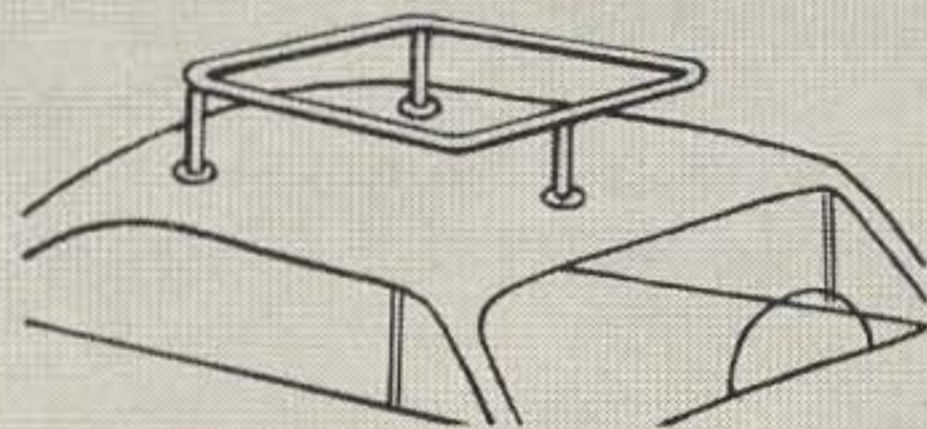

OUT A WINDOW

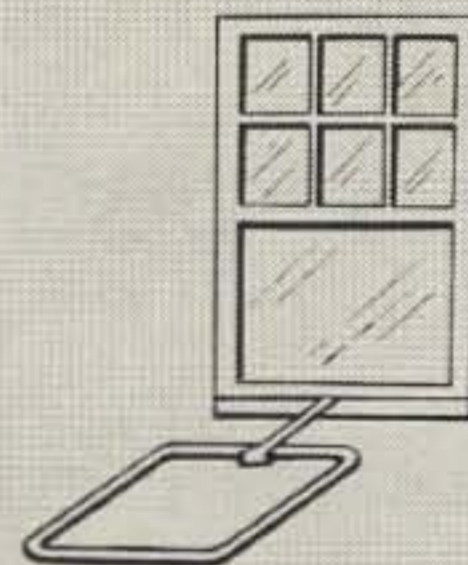

ON A MAST



*Pronounced Squaylo

Cush Craft

621 HAYWARD ST.
MANCHESTER N. H.

BUY FROM YOUR
DISTRIBUTOR OR WRITE
FOR FREE LITERATURE

the dummy load or wattmeter or whatever is hooked on to the unit. At this point, all coil slugs, rolo coils, 20A output circuits, etc., should be peaked for maximum 50 mc output from the T-51A. From here on in, everything should be more or less routine and adjustments of voltages and output may be set as desired. It will be advisable to let the triode oscillator section of the 6U8 tube run continuously between transmission for the best SSB stability.

As for power delivered: should the 832A be used in the final, an input of about 35 to 45 watts may be used. This will result in an output of around 17 to 20 watts PEP and will be more than sufficient to drive any type of grounded cathode final to maximum power. In actual practice, here at W5AJG, the plate voltage on the 832A final is run at about 375 volts and an input of only 10 or 11 watts is needed to produce the 4 or 5 watts PEP output necessary to drive the station final, which is a pair of 4X250B's in push-pull, to more than a KW PEP input.

Should the T-51A be used as a complete transmitter without another higher powered final, then of course the choice would be the 829B tube in the final socket. This tube will allow an input of some 120 to 150 watts PEP and will deliver on the order of 65 to 75 watts PEP output. This unit was checked out with an 829B tube and a plate supply of 600 vdc.

The screen was of course regulated at 216 volts. Final bias was -30v. Resting plate current was 20 mills. With a two-tone test signal driving the final plate current to 100 mills, an output of 40 watts was measured. Speech easily drives the PEP output to the above 65 watt figure, when up to 750 volts is applied to the plates of the final. The rolo coils will hold tuning over a range of about 400 kc before re-adjustment becomes necessary.

A standard Drake transmitting low-pass filter (TV-1000-LP) is used on the output of this transmitter when feeding the antenna. No trouble with TVI in this area was encountered. Channels in use being 4, 5, 8, 11 and 13.

Some workers have reported an interesting variation in the modification process on such a unit as this. Instead of using the 6U8 oscillator-buffer stage as described above, an International Crystal Company ready-made unit, such as the 200-125, or an earlier version, was installed. This was accomplished by removing the 6V6 oscillator tube and all components associated with it, and sub-mounting the assembly under the chassis. The hole left by the 6V6 tube socket removal allows the 6AU8 tube to protrude slightly above the deck.

Many thanks to K5KLU for his help in the modification and the testing of the T-51A/ARQ-8.

. . . W5AJG

The Nickel-Cadmium Storage Battery

Robert MacDonald W4VGS/1
7 Sherman Street
Needham Heights 94, Mass.

You have probably noticed in the surplus columns of various Ham magazines that nickel-cadmium batteries have finally become available at reasonable prices. In case you have been looking for a compact, reliable, portable and re-chargeable source of power, you should consider these devices. The purpose of this article is to supply you with the information you will need to make proper use of these little wonders.

Specifications (For the BB-403 series)

1. Dimensions: Approximately 2" W. x ½" D. x 6" H.
1. Capacity: 4 Ampere hours at 1 ampere rate.

3. Voltage: 1.2 Volts per cell.
4. Venting pressure: 1 to 3 PSI.

While the ampere hour rating is 4 A.H., it might be interesting to note that these cells will supply peak currents up to about 40 amps. Cells are shipped from the manufacturer with shipping plugs installed in the vent wells. However, the cells you will buy should have vent plugs installed. These are in the form of hollow screws, around which rubber sleeves are fitted, and are designed to release gasses produced while charging the cells, and to prevent foreign material from entering the cells, or electrolyte leakage.

Life expectancy of these cells is not precisely known. However, I understand they should

last in excess of 20 years!

Preparation For Service

Carefully examine cells for cracks, and if any are evident, fuse the cracks with a hot soldering iron. Then clean the cells thoroughly with distilled water and a brush. Wipe dry or allow to air dry, remove vent plugs and soak them in distilled water for at least an hour. Check electrolyte level and add electrolyte if necessary to bring level up to $\frac{1}{2}$ " over the tops of the plates. Do not raise level more than $\frac{3}{4}$ " above the tops of the plates, as the solution will rise during charging.

Electrolyte consists of a 33% solution of potassium hydroxide in distilled water and may be purchased from your local pharmacy. This solution is very caustic and will wreak havoc with anything upon which it is spilled; it is also very poisonous and should be kept in a clearly labeled bottle far from the reach of children.

Addition of electrolyte to cells is easily accomplished by filling the vent wells while squeezing the cells and then releasing the pressure applied by squeezing. An eye dropper is very handy for this operation. It is probably wise to discard any eye dropper used for this purpose. After electrolyte level has been adjusted, replace the vent plugs and tighten securely.

Equalization

Equalize cells by discharging at a 4 ampere rate until voltage reaches 0.9 volts. Short cells and leave shorted for at least one hour. Allow cells to cool before charging, then charge according to one of the following procedures.

Charging

If the state of charge of individual cells is not known, always equalize, using the procedure described above. Generally, if cells have been inactive for more than two weeks, or if they have been floating (trickle charging) for more than a month they should be equalized. This is particularly important if you wish to charge cells connected in series.

Method 1: (Constant Current) Charge at 1 ampere for minimum of 5.6 hours.

Method 2: (Constant Current.) Charge at 0.8 to 2.0 ampere until cell voltage reaches 1.55 volts; continue charging at 1.3 amperes for 1 hour.

Method 3: (Constant Voltage.) Charge at 1.5 volts for 1 hour. This method is recommended when cells are completely discharged and rapid restoration is important.

Method 4: (Constant Voltage.) Charge at 1.5 volts for 1 hour. This method is recommended when cells are not completely discharged, are in a questionable state of charge, and when a full charge is not required.

CAUTION: When using constant voltage methods, the charger should be capable of supplying peak currents in the order of 40 amperes and continuous currents of 6 amperes.

Method 5: (Trickle charging or floating.) In order to maintain cells in a fully charged condition, charge at a constant current of 15 to 30 milliamperes, or float by connecting cells to a constant voltage buss which will supply 1.55 volts. These procedures are useful when cells must be used occasionally, and relatively long periods of activity will allow cells to charge back to full capacity at a slow rate. However, after several months of floating or trickle charging, cells should be equalized and recharged, using one of the constant current methods of charging if possible.

Determination of State of Charge

No exact method exists for measuring the state of charge of a Nicad battery. However, the following techniques are reasonably accurate and will indicate the relative state of charge.

Method 1: (Most accurate.) Connect cells to a constant potential buss supplying 1.5 volts. After 5 minutes, connect an ammeter in series with batteries and buss. If current is less than 0.2 amperes, you may assume the cells are fully charged.

Method 2: (Least accurate.) Measure cell voltage. A fully charged cell should produce about 1.3 volts; a fully discharged cell should produce about 1.15 volts.

Periodic Checks and Maintenance

After cells have been in continuous service for 3 months, equalize, clean, adjust electrolyte level and charge as described previously. If electrolyte level was low, try to determine the cause of this condition. If no evidence of leakage is present, low level is probably due to excessive gassing and resulted from charging at high currents. Generally, white deposits *in* the vent wells (potassium carbonate) indicate loose vent plugs or excessive gassing and may be considered normal. White deposits *outside* the vent wells indicate that electrolyte has escaped the vent wells. The point here is simply this: if electrolyte has been lost, *electrolyte* should be used to bring level back to normal. If level is low due to gassing only, add *distilled* water, as the chemicals were not lost and addition of electrolyte will result in exces-

sive electrolyte strength.

You may now test the capacity of the cells by discharging at a 4 ampere rate and observing voltage drop over a one hour period. After one hour, voltage should be at least 1 volt. Any cell which does not pass this test is defective, or possibly does not contain sufficient potassium hydroxide. You may attempt to salvage cells by adding an additional ½" of *electrolyte*, equalizing, charging and testing again. A cell which fails the test three times is not up to par.

It is also important to allow cells to rest for 48 hours between charging and testing; failure to observe this rest period will not damage cells, but will introduce errors into the results of discharge tests.

Following tests, charge cells and return to service, or place in storage.

Storage

These cells may be stored in *any* state of charge, and at temperatures ranging from

minus 55 degrees C. to plus 75 degrees C. Self-discharge will occur at the rate of approximately 10% of the initial charge per week at temperatures below 50 deg. C., and will occur much more rapidly above this temperature. Cells which have been in storage for longer than 2 months should be equalized, inspected and charged before being returned to service.

When cells are to be stored for long periods of time, all metal parts should be coated with vaseline or light grease, and the vent plugs should be tight.

Conclusion

Uses of these cells are countless. I have built at least a dozen gadgets using transistors since my purchase of the cells, and have found them to be the most convenient source of voltage levels I have owned. So, adventuresome souls, dash out and buy a few of these gadgets and take advantage of another "fringe benefit" of the space age.

... W4VGS/1

The ARB Aircraft Receiver

getting it operational

Gordon Hopper W1MEG
75 Kendall Ave.
Framingham, Mass.

The ARB receiver is a superhet capable of AM, CW and RTTY reception in the range of 195 and 9050 kcs. Actually, its performance probably leaves something better to be desired, but it is capable of being a secondary receiver in a ham station.

The easiest way to power the receiver would be to supply 28 VDC to pins 1 and 2 (ground) on J102 (*power*), thereby utilizing the dynamotor furnished with the receiver. Rewiring the filaments for 12 VAC operation will create problems (without major conversion) as there

are 28 VDC relays in the circuit. (If the dynamotor is not to be used, then supply 225 VDC to pins 35 and 36 (ground) on J103 (*accessories*) and 28 VDC to pins 1 and 2 (ground) on J102.) Attach the right angle fitting and tuning knob to the fitting beside the tuning dial window.

Actually it is necessary only to furnish 28 VDC to the receiver, to attach the tuning knob to the receiver, and to make up a simple cable to utilize the remote CW switch and volume control that is contained in the remote head.

Select the pilot's control box (shown in the TM on page 85) and make up one cable to connect the control box to the receiver (J201 *control box*). The cable is a reduced version of W401 on page 113 in the TM. Keep the cable simple. Do the band switching manually at the receiver and thereby reduce the current requirements of the 28 VDC supply. The control box will be used to turn the 28 VDC on or off, to select the mode of reception, to select MVC or AVC, and to control the receivers gain.

... W1MEG

INTERCONNECTING CABLE

FROM P-101	TO P-201 (or P-301)
1	1
2	2
3	3
4	4
5	5
6	6
7	7
12	12
13	13
14	14
15	15
16	16

VLF • LF • MF

OPTIMIZED SOLID STATE RECEIVERS



MODEL VLRC-1



MODEL VLRB-1

10 to 40 KC • 30 to 600 KC
CONTINUOUS TUNED COVERAGE

IN TODAY'S ERA OF ATOMIC WEAPONS, FREQUENCIES AT THE LOWER PORTION OF THE RF SPECTRUM (BELOW 600 KCS) ARE LEAST AFFECTED BY ATOMIC DETONATION AND ARE THEREFORE VERY IMPORTANT FOR COMMUNICATION PURPOSES. THESE FREQUENCIES ARE ALSO PROVEN TO BE A VERY RELIABLE RADIO COMMUNICATIONS MEDIA DURING PERIODS OF HIGH SUNSPOT ACTIVITY.



FOR VLRC-1
REQUEST
TB 3017

- CW, FSK, FAX, AM, AME
- 0.3 MICROVOLT FOR 15db $\frac{S+N}{N}$
- RF, IF and AUDIO OUTPUTS
- VARIABLE SELECTIVITY
- PERMEABILITY TUNING
- AVAILABLE SYNTHESIZED OR UNSYNTHESIZED



FOR VLRB-1
REQUEST
TB 3015

THE TECHNICAL MATERIEL CORPORATION
MAMARONECK, NEW YORK

and Subsidiaries

OTTAWA, CANADA • ALEXANDRIA, VIRGINIA • GARLAND, TEXAS • OXNARD, CALIFORNIA
SAN LUIS OBISPO, CALIFORNIA • LUZERN, SWITZERLAND • POMPANO BEACH, FLORIDA



Adding SSB to the ARR-7

George Marshall W6BHR
554 Westborne Drive
Los Angeles, Cal. 90048

I bought an ARR-7 from R. E. Goodheart after trying in vain to find anything with that complete coverage and overall quality at anywhere near the price. Although Goodheart had already removed and bypassed the re-radiation suppressor, this article on adding SSB will be written for those who have an unmodified receiver. For those already possessing one of these versatile sets, or for those contemplating purchase, the ARR-7 is an extremely simple receiver in which to install a product detector.


Proceeding directly to the heart of the matter, the following steps make it possible to modify the receiver in a few hours' time. First, remove and discard the 6AB7 which precedes the first of the two rf amplifiers. This tube was used only as a reradiation suppressor so don't worry about losing gain or sensitivity in discarding it. The socket is utilized in the modification and the tube is replaced by a 6SN7 Product Detector.

The front-panel screws are loosened sufficiently to get an end wrench between the front panel and the chassis in order to remove the spst bfo switch. When the nut on the switch has been considerably loosened, the switch may be rotated about, so that with a gun-type iron, or other iron with a small tip, the connections may be removed from the terminals.

Replace the old switch with a DPDT and

reconnect the wires removed from the old switch in such fashion that they are switched ON in the bfo "ON" position. Use the uppermost terminals, the ones closest to the top of the receiver, for these connections, the single wire going to the center terminal and the pair of wires going to the other terminal.

Returning to the vicinity of the 6AB7 socket, there is a terminal board immediately adjacent, on which are mounted *79, C80, R54 and R55. Clip off, or unsolder these components so the terminal board can be re-used. Be careful when removing R-55, as this 47K resistor can be re-used as the plate load for the 6SN7. The B lead in the lower corner should also be carefully unsoldered, then the entire board can be removed for ease in installing the new components which consist of a .1 mf capacitor, a 10K ½ w resistor, and the re-installed 47K resistor. The terminal board is modified as follows: Remove the ground connection which runs in the vertical plane and swing it around to the B lug.

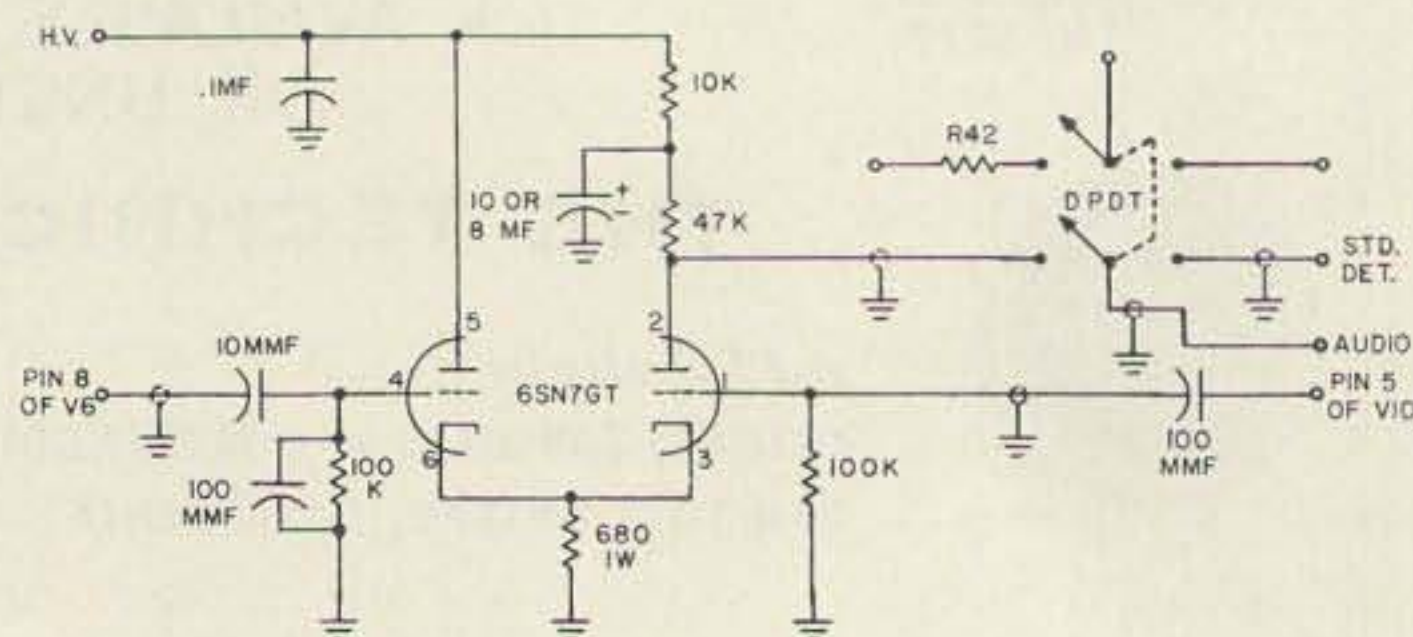

While the terminal board is out of the way, the octal socket may be rewired for the 6SN7 as follows: Remove the antenna lead from pin 4 and the lead connected to pin 8. These two leads may now be directly connected by placing them on the unused lug of the terminal board when it is replaced. The jumper going from pin 3 to pin 5 is removed, carefully, from pin 5 and connected to pin 6. If carefully removed, the ground lead connected to pins 1 and 2 can also be reused. A "soldering aid" tool is an asset for this sort of operation. A piece of spaghetti is slipped over this ground lead and it is then connected to pin 8 which takes care of the heater circuit. The other components are now connected to the socket, the 100K resistor from pin 1 to pin 8, the 100K resistor with a 100 pf capacitor across it, from pin 4 to pin 8 and a 680 ohm 1 w resistor from pin 6 to pin 8. (This is the only 1 w resistor; all others are ½ w.) The terminal board can now be reinserted.

When placing the .1 mf capacitor on the terminal board, leave enough lead on the B end and it can be used to connect directly to pin 5 on the octal socket.

Remove the 3 screws from the bfo compartment and remove the cover. Inside you will notice a "gimmick," two wires twisted together; remove these and replace them with a 100 pf capacitor. Remove the lead going from the lug to the 6H6 for bfo injection. Remove the #6-32 machine screw and place a ground lug under this screw and replace the screw. Replace the cover on the bfo.

Prepare a 7" piece of small coax or shielded lead as follows: Strip one end so that about ½" of shield is exposed and about ¾" of center conductor and its insulation. Strip off about ¼" of this insulation exposing the center conductor. This end of the shield will be connected to the ground lug installed on the bfo compartment and the center conductor connected to the lug which formerly went to 6H6. The other end of the center conductor is connected to pin 1 of the tube socket. The 47K resistor from the terminal board can now be connected to pin 2 of the socket.

An 8½" piece of small coax is stripped in the same manner as the previous piece. With a hot iron, a place can be puddled and tinned with solder on the vertical wall of the bfo compartment nearest to pin 8 of the last *if* tube. The shield of the coax is grounded at this point and the exposed center conductor is connected

through a 10 pf capacitor to pin 8 of the last *if* tube. The center conductor at the other end is connected to pin 4 of the 6SN7.

Now, on the opposite side of the receiver there is a long terminal board. On it, near the rear of the receiver, is the audio coupling capacitor C77; the lead nearest you is removed and transferred to a blank lug which is toward the rear of the receiver.

Now strip 2 26" pieces of small coax exposing the shield and center conductor at both ends. Strip another 26" piece so that the shield and center conductor is exposed only on one end. This end will be connected to the DPDT switch at the front panel. All three shielded leads can be snaked up through the harness along the right side of the receiver when looking at the bottom of the receiver, which will tend to keep things neat.

The center conductor of the coax which is stripped on only one end is connected to pin 2 of the 6SN7. The center conductor at the other end is connected to the lug of the unused section of the DPDT bfo switch is closest to the center of the receiver. The center conductor of the next coax is connected to the center lug of the switch and the other end of the center conductor is connected to C77. The third coax center conductor is connected to the remaining lug on the switch, and thence connected to the point that C77 was removed from.

The 3 shields at the point near the switch are wrapped with bare wire and soldered together. The other end of the two leads going to the audio can be tacked together in similar fashion. Where the lead which goes to the Product Detector, goes by the bfo compartment, about ½" of shield should be exposed and connected to the same point as the lead which went to the last *if* (the solder puddle at the side wall of the bfo compartment).

With all leads now installed on the 6SN7 socket, room can be found to connect the 10 mf decoupling capacitor to the ground lug of the adjacent tube. This completes the modification; plug in a 6SN7, hook up the power and start product detecting whenever the bfo is on. This modification does not affect ordinary CW reception, but makes it easy to tune and receive SSB signals. Either side band can be selected by adjustment of the bfo knob. It works like a charm!

... W6BHR

Leroy May W5AJG
9428 Hobart St.
Dallas 18, Texas

Photo credit: Jim Dungan, Dallas



The ARC Type TV-10 and 10A

Converting them to 220 mc transverters

The surplus unit designed ARC Type TV-10 or TV-10A Transmitter-Converter, commonly known as a Transverter, is built by the Aircraft Radio Corporation and is known generally as ARC Type 12 equipment, or ARC Type 220 UHF Portable Communicator equipment. In the military, it is also designated as a Frequency Converter-Transmitter CV-431/AR.

As used in this instance, a transverter performs in one unit the functions of a transmitter and receiving converter. The transmitter is of course on the desired frequency on which one wishes to send, while the receiving converter translates this frequency to an existing receiver of another frequency.

For instance, these equipments normally transmit on a fixed frequency or frequencies between 228-258 mc, and transforms or converts the reply in this same frequency range, to a new range of 118-148 mc, so as to enable existing receiving equipment to be used. In ham talk, this is a crystal-controlled transmitter combined with a crystal-controlled converter, contained in one case.

Our interest here is to convert the unit to something usable in the 220-225 mc ham range by utilizing the crystal-controlled transmitter and converting the received 220 mc signal to the 144-148 mc range, so as to make use of the existing 2 meter receiver in the station.

There is a little difference between the Model TV-10 and the Model TV-10A. The former has a rated transmitter output of one-half watt, while the latter is rated at a nominal two-watts output. The receiving converter section is identical in both units.

With a few modifications, this little unit will enable one to operate low-power on 220 mc, without installing a separate 220 mc receiver. It is very light in weight and may be worked in a mobile capacity if desired. Although low in power output, several uses suggest themselves—such as CD nets, RACES tie in—and so on.

Modifications

The amateur 1¼ meter band is a rather wide one and different parts of the frequency range are used in different localities. In an effort to split the difference, a design frequency of 225.5 mc was chosen, which represents the midpoint of the assignment.

Transmitter: A schematic diagram of the original TV-10 unit is reproduced and may, for all practical purposes, be used for the Model TV-10A also. The first order of business is the tube heaters. This equipment is designed for 27v dc operation and if either 12v or 6.3v is desired instead, some changes must be made in this wiring. This is rather routine and inspection of the schematic and the actual

Clegg



22'er TWO METER TRANSCEIVER

There is just no better way of getting started in VHF than with the newest of the new in the Clegg line — the 22'er two meter transceiver. This ready-to-go station combines many of the fine features that have made the Clegg name famous in VHF ham circles for years plus refinements to make 2 meter AM phone operation more interesting and challenging. It is realistically priced — your distributor will have complete information.

Amateur Net \$239.50

Features

RECEIVER

1. Dual conversion with crystal controlled first injection oscillator
2. Crystal lattice filter providing selectivity of about 10 KC at 6 db and less than 16 KC at 50 db
3. Freedom from spurious responses, IF leak through and images
4. Panel Meter doubles as calibrated S Meter on receiver and "relative output" meter for transmitter tune up
5. Full 143.8 MC to 148.2 MC coverage with calibrated tuning dial
6. Fine tuning control with approximately 25 KC range
7. Excellent AGC performance
8. NUVISTOR RF stage and low noise first mixer provide $.2 \mu\text{V}$ sensitivity (10 db S + N to N)
9. 3 watts audio output available with self contained high efficiency speaker for operation in high ambient noise associated with mobile operation
10. Effective Automatic NOISE LIMITER


TRANSMITTER

1. Broadband exciter stages to simplify rapid QSY
2. High efficiency straight through final amplifier with crystal controlled 18 WATT input
3. High level plate and screen modulation with speech clipping for typical Clegg "HIGH TALK POWER" performance
4. PUSH TO TALK with provisions to switch external LINEAR and VFO
5. TRANSMITTER frequency SPOTTING SWITCH
6. Self contained universal solid state power supply for 115 volts AC and 12 volts DC
7. Tube line-up


6CW4	Rcvr RF	12AX7	AF Amplifier
6KE8	Mixer/Xmtr Osc	6BQ5	Rcvr Audio Output/ Xmtr Modulator (2)
6KE8	VLO/Buffer	6EA8	Xmtr XLO/1st Multiplier
6BA7	2nd Mixer	12BY7	Buffer Amplifier
6AZ8	IF Amplifier	12BY7	Xmtr Driver
6BA6	IF Amplifier	2E26	Xmtr Final Amplifier
6AL5	Diode Detector/ Noise Limiter		

Squires - Sanders, Inc.


475 WATCHUNG AVENUE, WATCHUNG, N. J.

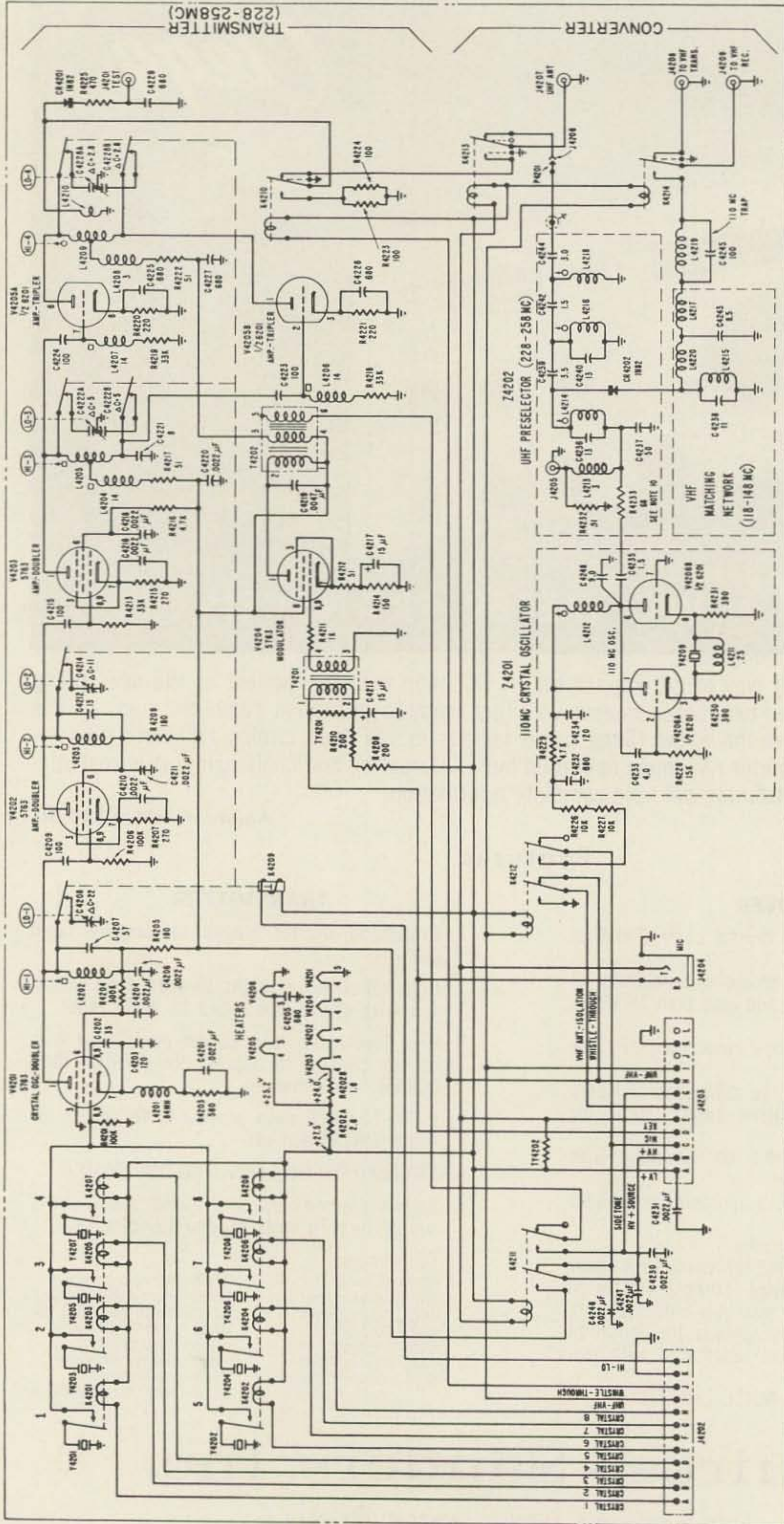

- NOTES:
1. FOR ASSEMBLY SEE DRAWING #14920.
 2. FOR WIRING DIAGRAM SEE DRAWING #14921.
 3. FOR ASSEMBLY AND WIRING DIAGRAM OF PRESELECTOR SEE DRAWING #17040.
 4. FOR ASSEMBLY AND WIRING DIAGRAM OF OSCILLATOR SEE DRAWING #17039.
 5. CAPACITOR VALUES ARE IN MICROMICROFARADS ($\mu\mu\text{F}$) UNLESS OTHERWISE NOTED.
 6. RESISTOR VALUES ARE IN OHMS, MULTIPLES: $k=1,000$ $M=1,000,000$.
 7. INDUCTOR VALUES ARE IN MICROHENRIES (μH) UNLESS OTHERWISE NOTED.
 8. D.C. VOLTAGE VALUES ARE APPROXIMATE AND ARE BASED ON THE FOLLOWING CONDITIONS:
(a) NEGATIVE TERMINAL OF VOLTMETER GROUND TO CHASSIS, EXCEPT WHERE A DIFFERENT CONNECTION IS INDICATED.
 - (b) LV+ AT TERMINAL 'A' OF J4203 SET AT 27.5 VOLTS BY ADJUSTMENT OF LV+ SOURCE.
 - (c) VOLTMETER OHMS-PER-VOLT: EITHER 1,000 OHMS PER VOLT EXCEPT WHERE SPECIFICALLY INDICATED.
 9. ALL RELAYS ARE SHOWN UNENERGIZED. FOR SETTED RELAYS K4211 AND K4213, THIS IS THE STAND-BY POSITION.
 10. AT FINAL ADJUSTMENT, RESISTOR R4233 MAY BE CHANGED TO 47.4K OHMS IF NECESSARY. TO OBTAIN SPECIFIED WIRE CRISTAL CURRENT WITH AVERAGE 6201 OSCILLATION TUBE.

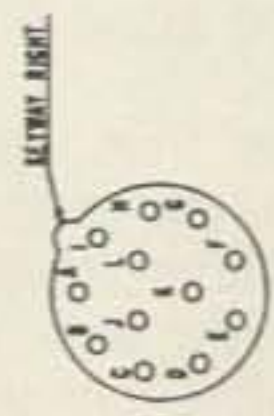

SYMBOL	NUMBER	DESCRIPTION
C	4248	6BE6
C	4249	6BE7
C	4250	6BE8
L	4251	6BE9
L	4252	6BE9A
L	4253	6BE9B
L	4254	6BE9C
L	4255	6BE9D
L	4256	6BE9E
L	4257	6BE9F
L	4258	6BE9G
L	4259	6BE9H
L	4260	6BE9I
L	4261	6BE9J
L	4262	6BE9K
L	4263	6BE9L
L	4264	6BE9M

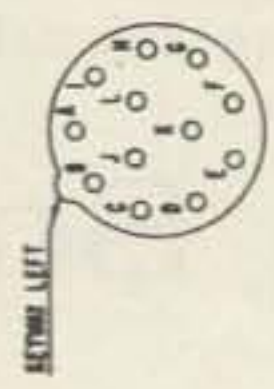

unit will suggest the best way for your case. Of course, the simple way out would be to continue to use the 27v dc. This is not as difficult as it once was—what with all the silicon devices around able to handle a couple of amperes without sweat. If it is desired to use ac however, the mike line will have to be disconnected and rerouted to some source of mike current.

Relays: The next items to be considered are the relays. These are also 24 V dc operated and of course ac will not work here. Fortunately, all of the relays will not be used. Most will remain in the circuit but in their normal un-energized position, and in which case, one side of the coil may be disconnected to keep them from operating. A couple will be used in their energized position. This may be accomplished by blocking the armature closed with a tooth-pick or other suitable means, along with disabling the coil by the disconnect procedure as on the others. Actually, the only relay that would be of value would be the antenna change-over relay. If it is desired to retain this one, it will be necessary to provide 24v dc to operate it. Following is the relay schedule:

Disconnect one or both sides of the coils of every relay in the set, causing them to be disabled, with the exception of the antenna change-over relay K4213. Block in a closed position the two relays marked K4211 and K4214. Further details on some of the individual relays will be given shortly.

Power Supplies necessary: As above mentioned, if 24v dc is available and can be used, much work will be eliminated. Without the relays, about ¼ a will do the job. If 12 volts are used, 1.5 a will be necessary and if 6.3v is used, about 3a will have to be provided. The plates will require 250-275v dc at about 130 mills for the ½ watt output.

On the power receptacle J 4203, the filament heater voltage will go to terminal "A" marked LV+. The B+ will go to terminal "B". The microphone transformer primary T4201 will have to be isolated and fed to the mike being used. Terminal "E" will key the antenna relay by grounding same. When the transmitter is in stand-by position and B+ is not being fed to terminal "B", it will be necessary to get voltage to the receiving converter. This could be accomplished by connecting a wire from the bottom of R4227 to an unused terminal on J4203, such as "L", and feeding the converter voltage at that terminal when receiving and to terminal "B" when transmitting—or perhaps some other arrangement will suggest itself that would fit in better with individual

NEW callbook

**HOT OFF
THE
PRESS!**



**Over 60% of listings
changed in only a year!**

PLUS THESE EXTRA FEATURES:

- Great Circle Bearings
- Great Circle Charts
- Prefixes by Countries
- "Q" and "Z" Signals
- World Time Chart
- Int'l. Postal Rates

United States Listings...\$5.00
DX Listings..... 3.00

**ORDER THESE USEFUL
AMATEUR RADIO AIDS TODAY!**



Radio Amateur DX Guide—62 pages of vital data; 291 Great Circle Bearings for 22 major U.S. cities; Prefix Map, Time Conversion Table, DX Log, plus other features postpaid \$2.00



World Prefix Map—Full color, 29" x 42", shows prefixes on each country . . . DX zones, time zones, cities, cross referenced tables postpaid \$1.00



World Atlas—Only Atlas compiled for amateurs. Polar projection, six continents, prefixes on each country . . . full color, 16 pages postpaid \$1.00

**WRITE FOR
FREE
BROCHURE!**

RADIO AMATEUR

callbook INC.

Dept. B, 4844 W. Fullerton Ave.
Chicago, Ill. 60639



See your favorite dealer or order direct (add 25¢ for mailing)

existing available power supply facilities or switching.

Circuitry: The original frequency range of the transmitting crystals used to cover the 228-258 mc segment was between 9.5-10.75 mc when using a multiplication of 24 times. An alternate multiplication of 36 times could also be used in the gear and in that case the crystal frequencies would be between 6.333 and 7.166 mc. Either arrangement was permissible and satisfactory.

To provide the newly desired output frequency of 222.5 mc a crystal of either 9270.8 kc or 6181.481 kc will be necessary. The latter frequency rock was available at this station and was a surplus one of the type that was used in the old SCR-522 two-meter equipment. Using either crystal, however, no alterations in the rf circuitry are necessary. Merely retune the coils and/or capacitors for maximum rf output at Test Jack J4201 on front of the unit. A small range mill-meter may be used here for the best indication. Also a lamp load could be used for testing and for the tune-up. Select one of the crystal socket positions, insert the 6181.481 kc crystal and block closed the associated relay. The other crystal sockets and relays will not be used.

The 220 mc antenna will connect to J4207 labelled UHF ANT. J4208 labelled to VHF TRANS will not be used. J4209 labelled to VHF REC will be used to go to the 144 mc station receiving equipment. This is the output of the converter section of the TV-10 after the signal has been translated from 220 mc to 144 mc.

Receiving Converter Section: Refer again to the schematic. Note that Z-4201 is an 110 mc crystal oscillator. This 110 mc crystal is actually a 7th overtone type, with inductor L-4212 resonating on the output frequency of 110 mc. Now since the fundamental of this overtone crystal is one-seventh of 110 mc, or about 15.7

mc, we can change the mode over to the 5th overtone, which will be approximately $15.7 \times 5 = 78.5$ mc. Coil L-4212 will have to be padded to resonate at this new frequency. This is accomplished by merely removing capacitor C-4248 (9 mmfd) and replacing with a disc or tubular of 25 mmfd. The coil will now resonate on 78.5 mc and the new *if* frequency will be the difference of $222.5 - 78.5 = 144$ mc, which will work into a 144 mc receiving system very nicely. One other change in the receiving converter section is necessary and that is to change the 110 mc trap circuit labelled L-4219 and C-4245 to the new frequency of 78.5 mc. This is simple to do—merely bridge C-4245 with another capacitor of 150 mmfd. Lastly, after a 222.5 mc signal is received, touch up the slugs on the Pre-selector Z-4202 section for maximum signal. These slugs would be L-4218, L-4216 and L-4214 labelled "Factory Adjusted—Do Not Disturb." (Haven't you always been tempted to do something like this anyway?). This should complete the modifications.

Remember, the converter is a mixer with no rf amplifier stage. It should work well for the stronger signals—do not expect too much on very weak signal reception. Add a nuvistor, or perhaps a 416B 220 mc preamplifier for such work. Also keep in mind that the transmitter output stage on the TV-10 is a tripler with multiplied crystal frequencies probably present to some extent. This is low power certainly, but aircraft line of sight is great and this range of frequencies is hot with such communications. Check carefully with a GDO or sensitive absorption type instruments for such unwanted emissions.

This little set will enable someone mildly interested in 220 mc to talk around town locally and it might even whet the interest to give 220 mc a real shake at some later date.

... W5AJG

Notes on the ARR-15 Receiver

Gordon Hopper W1MEG

The ARR-15 receiver, as received, will function by the addition of the correct voltages and actually requires no major conversion work.

Application of 28 VDC to the connector at the rear of the receiver will operate the dynamotor and it should be applied as follows:

Pins 3 and 20	jumpered
Pin 17	28 VDC
Pin 9	dc return

John Meshna, Inc. in Lynn, Mass., has power supplies which are ideal for the operation of this receiver. They are rated at 24 volts @ 4 amps and can be used on many types of surplus receivers.

In its original condition, the receiver is quite broad. Here is a modification which will select either a sharp or a broad filter: Remove the wire from terminal 2 of Z-122 and tape it out of the way. Remove the ground post.



SEE THE LIGHT?

NEW! NOW! LIGHTED KNOBS

ILLUMINATED KNOB—Model 347

Waters Illuminated Knobs serve as pilot lights and position indicators. The Waters Illuminated Knob projects a light beam on the panel to identify the position, and has a lighted red pointer as a pilot light. It is ideal for applications where the pointer position must be read clearly and where it is desirable to identify position from a distance or under poor lighting conditions. Installation is simple. The knob contains the light and may be mounted on any 1/4" shaft rotary control or switch with no changes required behind the panel. One wire provides the 6 volt source for the light, with the shaft serving as ground.

5⁰⁰
only

ALSO — Please don't forget ▼



DUMMY LOAD WATTMETER

Model 334
2-230 mc 52 ohms
50W continuous
1 KW intermittent
0-10-100-1000W
\$79.75



LITTLE DIPPERtm Model 331

2-230 mc in 7
ranges
Transistorized
Tone mod. built in
\$129.75



PATCH Universal Hybrid Coupler II Model 3002

Patch for phone or tape recorder
Built in compressor
Fine for SSB

\$69.95

UNIVERSAL HYBRID COUPLER Model 3001

Same as 3002 except no compressor
built in **\$49.50**

RETROFIT KIT Model 358

Designed for installation in 3001 Cou-
pler to modify it to 3002 circuit. Also
can be used in your own equipment to
build in a Compreamptm. **\$19.95**



COMPREAMPtm AUDIO PREAMPLI- FIER/LIMITER

Model 359

Connects between
mike and mike in-
put on rig.
Increases effective
speech power up to
four times.

\$27.95



COAXIAL SWITCHES

Model 335 SP6T
\$12.95

Model 336 DPDT
(Transfer Switch)
\$11.45

Model 341 SPDT
\$11.45

Model 351 DPDT
\$12.95




Q-MULTIPLIER NOTCH FILTER

For 75S1 **Model**
337 337-S1A
\$39.95

For KWM2/2A
Model 340A
\$53.75

Fits Collins gear
perfectly

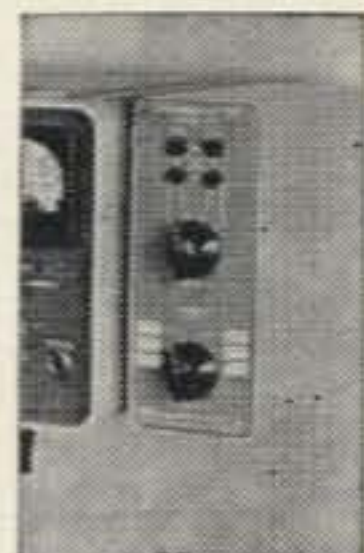

CHANNELATORtm

Crystal frequency
control for
KWM2/2A
Model 349
\$79.95



E V Ttm ELECTRONIC VERNIER TUNING

For KWM2/2A

Model 354 **\$23.95**
KWM2A

Model 355 **\$21.95**
KWM2

WATERS — WAYLAND MASS

Install a SPST bat handle switch in the vacated hole. Run a wire from terminal 6 of J-102 to one switch terminal and run a wire from the other switch terminal to terminal 2 of Z-122.

To make the receiver active when the receiver is off "0" when in MCW-CAL position, remove the wire from terminal 7 of J-102 and install SPST bat handle switch between this wire and terminal. Switch can be located below switch in above modification and labeled CAL. OFF-ON.

To make it possible to calibrate on frequencies whose last two digits are "0," jumper terminals 14 and 22 of J-110.

The addition of a Q5R may be desirable.

Although I have the receiver operational, I have not yet had the chance to try one on it.

If desired, an AC supply for the B voltage (220 VDC at 80 ma) can be connected between pins 3 and 9 (ground) of the dynamotor connector after removing the dynamotor.

To reduce the current requirements of the 28 VDC power supply, it is recommended that the two locks on the front panel be loosened and that the tuning and band switching be accomplished manually.

The original technical manual for the ARR-15 receiver is identified as AN-30ARR15-3. Good luck on locating one.

New Life for the R-44/ARR-5 Receiver

Ronald L. Ives
2075 Harvard St.
Palo Alto, Calif.

Introduction

Many amateurs and experimenters have purchased surplus R44/ARR-5 receivers in the belief that they were military versions of the Hallicrafters S-27. After finding out that the receiver has no power supply, lacks sensitivity, and has headset output only, they have stored the rather well-built equipment in the garage, and have gone on to other things.

Actually, the R44/ARR-5 is a military version of the well-known S-27, and can be made to operate as an S-27 with a very small amount of work. Basically, it is an AM-FM receiver,

with one rf, oscillator, mixer, and two rf stages. Beyond this, there is a limiter and discriminator for FM reception; and an added *if* stage and diode detector for AM reception. Two stages of audio are provided.

Frequency coverage, in three ranges, is from 27 mc to 140 mc. A motor-driven band-scanning device is provided, as well as a fixed tuned bfo. Broad and sharp *if* adjustments are selectable by a front panel switch.

This frequency range covers 10 and 6 meters, a number of radio paging services, the lower frequency TV channels, all of the FM band, and the 110-140 mc aeronautical and

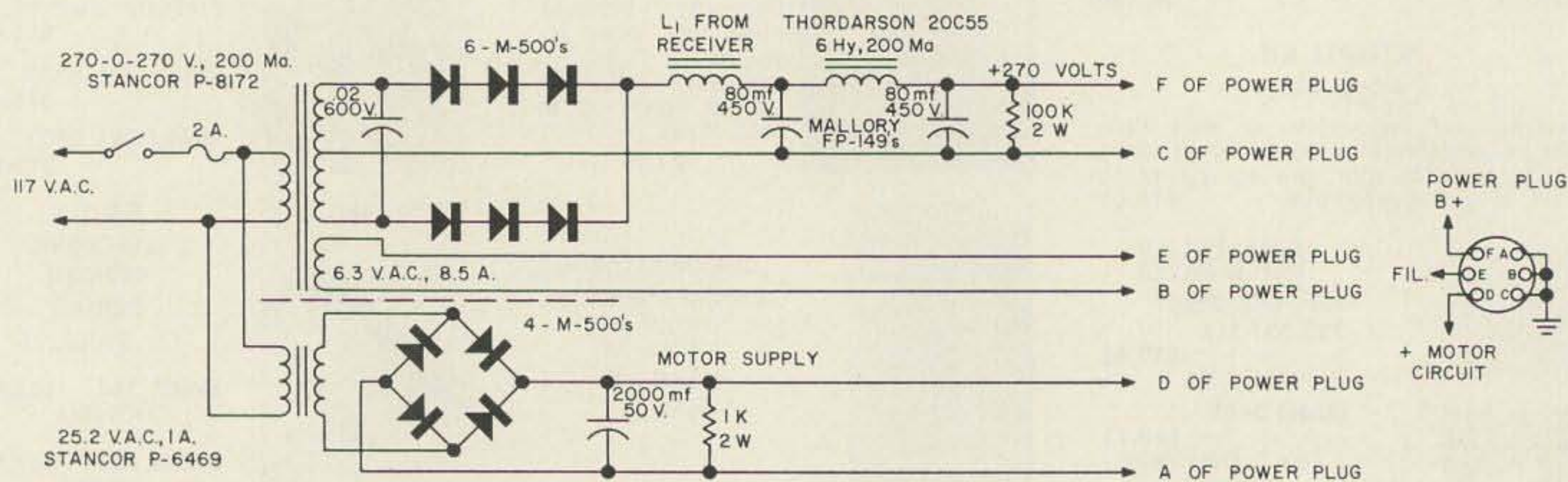


FIGURE 1

Circuit of power supply.

special communications bands. As a general coverage receiver from 28-140 mc it can hardly be surpassed, even though the design is more than 20 years old. It can be put into full service by providing a power supply and by making a few very simple circuit changes.

Power Supply

Operation of the R44/ARR-5 requires 6.3 volts at about 4 amps; 270 volts at about 135 ma; and, if the motor driven scanner is to be used, 24 volts dc at about 135 ma.

The circuit of a more than adequate power supply for this receiver is shown in Fig. 1. Choke input is used here to keep the B voltage low enough. It also reduces surges on the silicon rectifiers. The first choke (L1 from receiver) is an original part of the R44/ARR-5, and is located at extreme left rear of the chassis. Remove both power leads from this and connect them together temporarily, then remove the choke from the receiver.

The .02 mfd capacitor across the high voltage secondary is to absorb rectifier switching transients. If omitted, this power supply may create interference at various multiples of 60 cycles up to at least 60 kc.

Ordinarily good construction is all that is required in the power supply, which is conventional in operation. If you do not want to use the motor-driven scanner, omit the motor supply circuit entirely.


Initial Testing

Once the power supply is complete, connect the receiver in accord with the plug diagram in the inset of Fig. 1, turn it on, and let it warm up for a few minutes. Connect any sort of antenna to the antenna input plug, and plug a headset into the phones jack. Check operation of all functions on all bands, and correct any troubles found.

Most likely troubles are cracked resistors and switches that don't work. Replace resistors found defective by those of like color code. Replace any of the laminated bakelite switches that don't work by good switches, preferably with moulded bakelite cases, so that a second generation of switch failures doesn't develop in a couple of years.

Improving Sensitivity

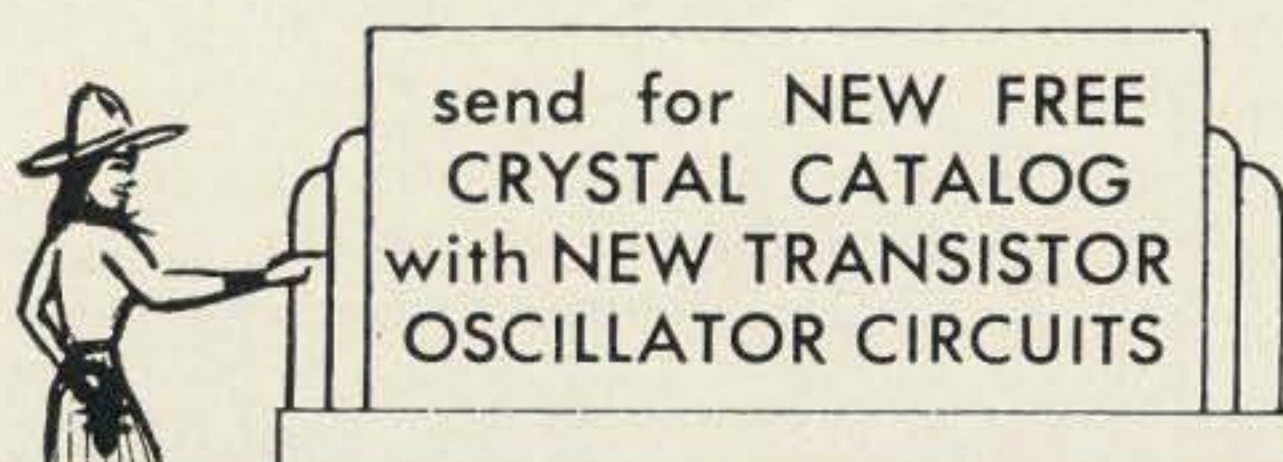When this receiver is in operation, its sensitivity is low, and the signal-to-noise ratio is not very happy. This difficulty is due to the installation of a radiation preventer stage between the antenna and the first tuned rf stage. This is located in a small annex to the main tuner housing, at left rear. The top of this box carries the label "CAUTION, plate termi-



3 BIG MODERN PLANTS TO SERVE YOU BETTER

2 in Fort Myers

1 in Los Angeles



HERMETICALLY SEALED PRECISION GROUND CUSTOM-MADE NON-OVEN CRYSTALS

Top performance assured with quality controlled throughout manufacture. Gold or silver plating acts as electrodes. Crystals are spring mounted and sealed under vacuum or filled with inert gas. Very high frequency stability. Max. current capacity is 10 milliwatts—5 for overtone type. Conformity to military specifications guaranteed.

1000KC to 1600KC (Fund. Freq.)	Prices on Request
1601KC to 2000KC (Fund. Freq.)	\$5.00 ea.
2001KC to 2500KC (Fund. Freq.)	4.00 ea.
2501KC to 5000KC (Fund. Freq.)	3.50 ea.
5001KC to 7000KC (Fund. Freq.)	3.90 ea.
7001KC to 10,000KC (Fund. Freq.)	3.25 ea.
10,001KC to 15,000KC (Fund. Freq.)	3.75 ea.
15MC to 20MC (Fund. Freq.)	5.00 ea.

OVERTONE CRYSTALS

15MC to 30MC Third Overtone	\$3.85 ea.
30MC to 40MC Third Overtone	4.10 ea.
40MC to 65MC Third or Fifth Overtone	4.50 ea.
65MC to 100MC Fifth Overtone	6.00 ea.

DRAKE 2-B Receiver Crystals\$4.00
(All Channels—Order by Freq.)

OVEN-TYPE CRYSTALS

For Motorola, GE, Gonset, Bendix, etc.

Add \$2.00 per crystal to above prices

SUB-MINIATURE PRICES slightly higher

CITIZEN BAND Class "D" Crystals\$2.95
Over 50,000 CB crystals in stock for all sets and channels, both HC6/U and miniature types. To insure proper correlation and correct freq. operation, order by manufacturer model number and channel.

NOW . . . 48 HOUR SHIPMENT

ALL TEXAS CRYSTALS are made to exacting specifications, quality checked, and unconditionally guaranteed!

NEW TWX SERVICE

Fort Myers - 813-334-2830

Los Angeles - 213-737-1315

ORDER FROM CLOSER PLANT

TEXAS CRYSTALS

DEPT. 73-6
1000 Crystal Drive
FORT MYERS, FLORIDA
Phone 813 WE 6-2109
TWX 813-334-2830

Division of

AND
4117 W. Jefferson Blvd.
LOS ANGELES, CALIF.
Phone 213-731-2258
TWX 213-737-1315



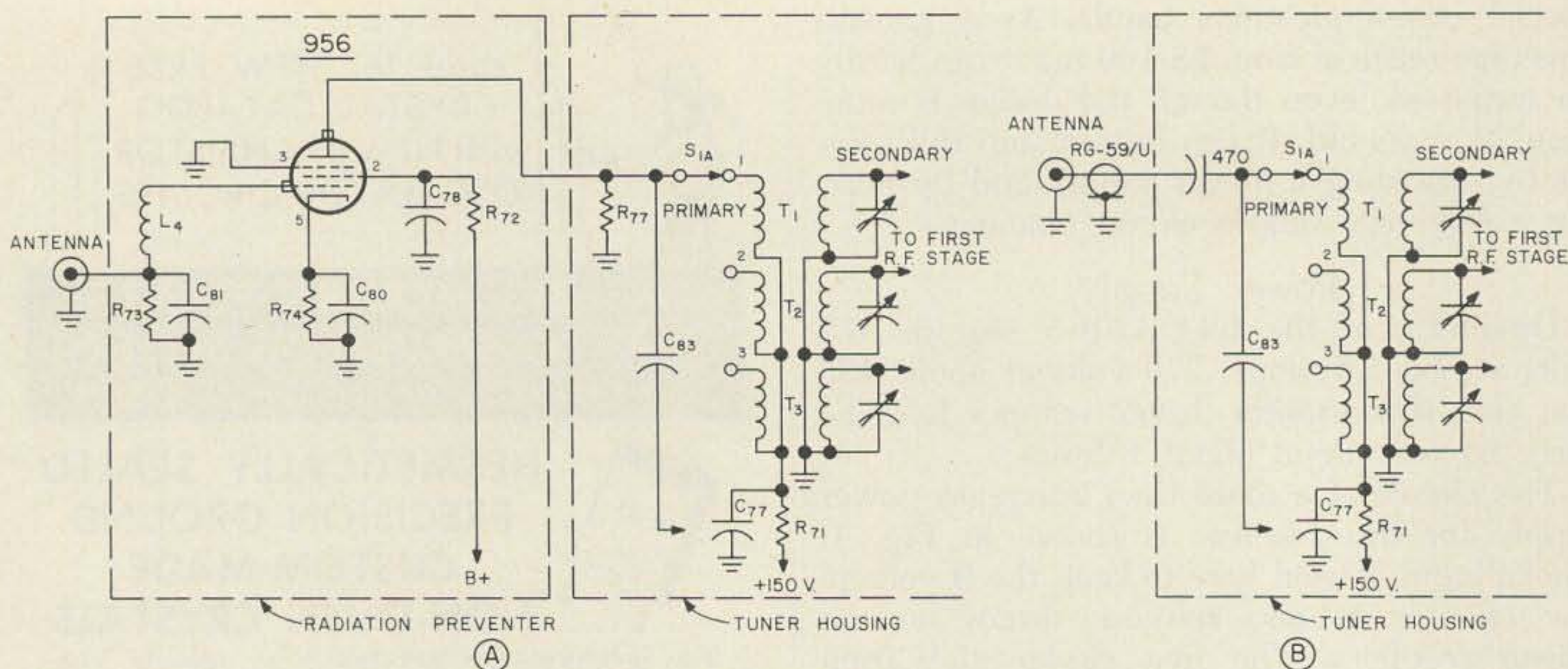


FIGURE 2

Front end revisions.

nal of tube inside projects into R-F stage." This stage is run at low B voltage so that it does not amplify, but unhappily it does contribute to the input noise.

The circuit of the front end of the R44/-ARR-5, as supplied, comprises section A of Fig. 2. To improve the receiver sensitivity, this stage is eliminated. Start by removing the 956 tube from the socket, then remove the small shield box, and finally disconnect the screen and filament supply leads from the connector that goes through the chassis. This will leave a clean circular hole in the back of the main tuner housing, and a clean elliptical hole through the chassis below it.

Remove R-77, a small resistor that connects from the plate lead of the 956 to ground. Center a UG-177/U plug hood over the round hole in the back of the tuner enclosure, mark the positions of the four holes, and drill clearance holes for 4-40 screws at the marked locations. Attach a piece of RG-59/U coaxial cable to the plug hood, leaving about 1½" of clear conductor on the inside. Bolt the plug hood in place, and mount two tie points on the holding screws inside the tuner shield. Connect the free end of the RG-59/U to the one farthest from the tuning capacitors. Connect a 470 mmfd capacitor between them, and connect the plate lead of the removed 956 to the tie point nearest the tuning capacitors. Pass the cable down through the elliptical hole in the chassis, and bring it out to either the front panel SO-239 plug marked ANTENNA or to any other termination that suits your convenience. Check operation, replace the cover on the tuner shield, and the front end changes are completed.

In most instances, this will more than

double the usable sensitivity of the receiver, reducing the "front end hiss" considerably at the same time. Final circuit is shown in Fig. 2, B.

Output Modifications

As supplied to the government, the R44/-ARR-5 was designed for headphone and video output, and no provision was made for speaker operation. The original audio output circuit is shown in Fig. 3, A. All major components are mounted on terminal strips along the chassis skirts, and all are clearly numbered on the bakelite.

To convert the receiver for speaker operation, it is necessary to rip out the video output components and install an output transformer. To start this, cover the large hole at the left rear of the chassis (left when L1 was removed) with a metal plate, bolted in place. On the top of this, mount a small universal output transformer, such as a Stancor A-3877. Provide a grommet hole for the transformer leads. Under the chassis, behind the transformer, mount a tie point. To this connect the two leads removed from L1 previously, and the B+ lead of the output transformer. Connect the plate lead of the transformer to pin 3 of the 6V6 socket. Do not remove the other leads, or disturb the .33 meg resistor between pins 3 and 6 of this socket. This is the feedback resistor, R60 of Fig. 3.

Now find and remove R59, R70, R61, R69, R63 and C64. These are on the terminal strips near the tube socket, except for R63, which is a power resistor at about the middle of the terminal board. These components are best

(Turn to page 32)



12 NEW AMATEUR BEAMS

from

FINCO[®]

**ALL GOLD CORODIZED
ALL GAMMA MATCHED**

- 3 New combination 6 & 2 meter beams**
- 5 New 6 meter beams**
- 3 New 2 meter beams**
- 1 New 1¼ meter beam**

**SEND FOR NEW
TECHNICAL INFORMATION
CATALOG #20-226**

THE FINNEY COMPANY

34 West Interstate • Bedford, Ohio

Another Surplus Find

Among the many thousands of items found on the surplus market, there is one unit that is often overlooked or rejected by the "surplus scavenger." This is the dynamotor set, not to be confused with the dynamotor alone.

The dynamotor set consists of a dynamotor, mounting bracket, chassis, various capacitors, a choke, filter assemblies, resistors, etc. The number and type of components will vary with each type of dynamotor set, but those components listed are generally common to all such sets. Taking the DY-76A/AIC-10 set as an example, the following components were removed and cataloged: one DY-76A dynamotor, (input 27.5 volts dc @ 7 amps, output 175 volts dc @ .6 amps), one filter reactor, (.2 henry @ .65 amps, tested at 1000 volts dc, resistance 7 ohms), two 100 mfd @ 300 wvdc electrolytics, two sealed pi type filters, (one rated at 50 volts dc @ 7.5 amps, and one at 250 volts dc @ 1 amp), and one 5½" x 7½" x 1½" chassis.

The 50 volt pi type filter may be used as an excellent filter for mobile operation of receivers, converters and low powered transmitters. The 250 volt filter may be used as an output filter for low voltage supplies or other such applications. The reactor, or choke, could easily find its way into power supplies, etc. Many applications can be found for the extremely well made, long lasting electrolytics. There is no need to mention the many uses of a strong aluminum chassis of the dimensions listed. In fact, the holes already punched in the chassis will serve most applications without the need of adding others. The holes punched for the mounting of the two electrolytics are perfect for tube sockets. Four permanently attached bolts hold the two chassis halves together quite neatly.

The 27.5 volt dynamotor can be operated from a 12 volt source with its output reduced approximately one half. It can also be operated from a 24 volt marine power source with no apparent decrease in output. If no such use is contemplated, the dynamotor can be converted into a 115 volt ac motor with little trouble and no expense.

The following instructions will enable the dynamotor to be used as an electric motor. First, remove the brushes from the motor end of the dynamotor assembly. The motor end is usually identified on the name plate, or can be found by tracing the yellow input lead. (The red lead is the positive high voltage output lead.) Remove the two field wires from the motor end and connect them in parallel with the generator field winding. Connect a 115 volt line cord across the field coils and generator brushes. If, after applying power, the motor does not run, reverse the motor field connections. There is a fifty-fifty chance of improperly connecting the motor field windings. As the dynamotor shafts are not long enough to attach a pulley, etc., it will be necessary to drill and tap the shafts to attach an extension. The motor that you now have may not deliver as much torque as a standard, commercial motor, but it may be used in many applications. Its low cost more than overcomes any shortcomings it may have. One of these conversions is used by the author to power a small grinding wheel, and another is used to power a blower for cooling of electronic equipment.

The dynamotor sets are found at most surplus dealers and their low cost makes them one of the best buys on the surplus market. Better hurry and get yours before the price goes up!

Propagation Chart

EASTERN UNITED STATES TO:

GMT -	00	02	04	06	08	10	12	14	16	18	20	22
ALASKA	14	14	14	7	7	7	7	7*	14	14	14	14
ARGENTINA	14	14	7*	7	7	7	14	14	14	14	21	21
AUSTRALIA	14	14*	14	7	7	7	7	7	7	7	14	14
CANAL ZONE	21	14	14	7	7	7	14	14	14	14	14	21
ENGLAND	14	7	7	7	7	14	14	14	14	14	14	14
HAWAII	14	14	14	7	7	7	7	7	14	14	14	14
INDIA	14	14	7	7	7	7*	14	14	14	14	14	14
JAPAN	14	14	14	7	7	7	7	7*	7	7	14	14
MEXICO	14	14	7*	7	7	7	14	14	14	14	14	14
PHILIPPINES	14	14	7*	7	7	7	7*	14	14	7*	7*	14
PUERTO RICO	14	14	7	7	7	7	14	14	14	14	14	14
SOUTH AFRICA	7	7	7	7	7	14	14	14	14	14	14	7
U. S. S. R.	14	7*	7	7	7	7*	14	14	14	14	14	14
WEST COAST	14	14	14	7	7	7	7	14	14	14	14	14

Good: 2-8, 14-17, 22-24

Fair: 1, 9-13, 22-21, 25, 28-30

Poor: 18-19, 26-27

Es: 4-8, 13-18

(High MUF and/or freak conditions)

CENTRAL UNITED STATES TO:

ALASKA	14	14	14	14	7	7	7	7*	14	14	14	14
ARGENTINA	14	14	14	7	7	7	14	14	14	14	14*	21
AUSTRALIA	14	14*	14	14	14	7	7	7	7	7	14	14
CANAL ZONE	21	14	14	14	7	7	14	14	14	14	14	21
ENGLAND	14	7	7	7	7	7	14	14	14	14	14	14
HAWAII	14	14	14	14	7	7	7	7	14	14	14	14
INDIA	14	14	14	7	7	7	7*	14	14	14	14	14
JAPAN	14	14	14	14	7	7	7	7*	7	7	14	14
MEXICO	14	14	7*	7	7	7	7	14	14	14	14	14
PHILIPPINES	14	14	14	14	7	7	7	14	14	7*	7*	14
PUERTO RICO	14*	14	14	7	7	7	14	14	14	14	14	14*
SOUTH AFRICA	7	7	7	7	7	7	14	14	14	14	14	7
U. S. S. R.	14	7*	7	7	7	7	7*	14	14	14	14	14

J. H. Nelson

WESTERN UNITED STATES TO:

ALASKA	14	14	14	14	7	7	7	7	7*	14	14	14
ARGENTINA	14	14	14	7*	7	7	7	14	14	14	14	21
AUSTRALIA	14*	21	21	14	14	7*	7	7	7	7	14	14
CANAL ZONE	14*	14	14	14	7*	7	7	14	14	14	14	14
ENGLAND	14	7	7	7	7	7	7	14	14	14	14	14
HAWAII	14	14	14*	14	14	7*	7	7	14	14	14	14
INDIA	14	14	14	14	7	7	7	7*	14	14	14	14
JAPAN	14	14	14	14	14	7	7	7	7*	7*	14	14
MEXICO	14	14	14	7	7	7	7	14	14	14	14	14
PHILIPPINES	14	14	14	14	14	7	7	7	14	7*	7*	14
PUERTO RICO	14	14*	14	7	7	7	7*	14	14	14	14	14
SOUTH AFRICA	7	7	7	7	7	7	7*	14	14	14	14	7
U. S. S. R.	14	14	14	7*	7	7	7	7*	7*	14	14	14
EAST COAST	14	14	14	7	7	7	7	14	14	14	14	14

* Means next higher frequency may be useful...

(Receiver from page 28)

removed by clipping the leads. Because of their age, few of them are worth salvaging.

Now, from pin 5 (grid) of the 6V6 to ground connect a .1 meg resistor, of ½ watt or larger. From pin 8 of the same tube (cathode) connect a 330-ohm 2 watt resistor to ground, and shunt it with a 25 mfd, 25 volt electrolytic capacitor, connected with positive to socket.

Lastly, connect the secondary circuit of the output transformer to the speaker terminals and the phone jack, as in Fig. 3, B. With this connection, the speaker is silent when the headset is plugged in. The load that is switched in when the speaker is disconnected is not critical, any value from 5 to 22 ohms will work well, but its omission will insure that the audio circuit will oscillate powerfully.

When this work is completed and tested, the conversion of the receiver to ordinary use is completed. Appearance of the left rear portion of the chassis, where the changes have been made, is shown in the photo. If, after everything tests OK, you wish to go over the under-chassis wiring, eliminating unnecessary wires and sections of terminal board, appearance of the equipment will be improved slightly, but no changes will occur in the performance.

Automatic Scanning

As previously mentioned, this receiver is equipped with an automatic scanning device, which requires an input of 24 volts dc. The range of the scan is adjustable from the front panel, by means of a pair of switch cams under the hinged cover. The on-off switch for the automatic scan is near top center of the panel. The speed of the scan is adjustable by means of a 250 ohm wirewound rheostat at rear center of chassis. This runs quite hot on continuous scan, as does the motor. The magnetic clutch, which connects the motor drive to the tuning shaft is a rugged device, which will last almost forever. The motor, in contrast, has a nominal life of about 1,000 hours, of which a considerable portion may have been used up in military service.

ACTION REQUIRED

Please send a letter or radiogram to your Representative in Congress asking that he expedite the "International Reciprocity for Radio Amateurs" bill (S.920). This is of immediate importance, do not delay.



Rear chassis view of converted R44/ARR-5.

Performance of this receiver, after conversion, is rather surprisingly good and as consistent as band conditions permit. Tuning gear train operates very smoothly, permitting use of the receiver on the sometimes crowded 10 and 6 meter ham bands. The power supply has enough spare capacity to carry most if not all of the adjuncts that a fertile mind will find interesting with this type of receiver.

... Ives

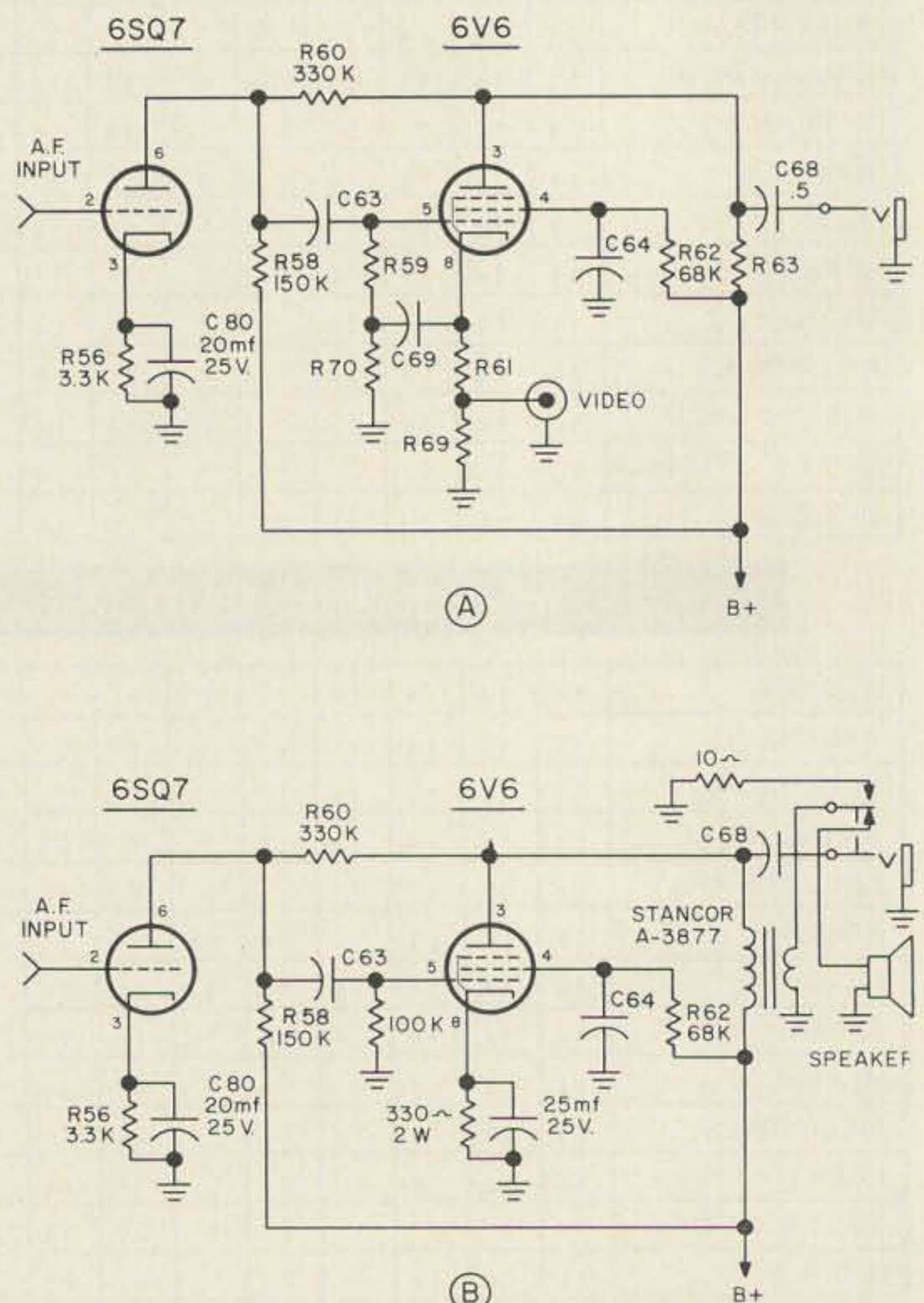


FIGURE 3

Receiver output circuit.

Really High Gain

Jim Kyle K5JKX
1236 N.E. 44th St.
Oklahoma City, Okla.

Gain in an audio amplifier is something you seldom worry about unless you don't have enough—but if you're planning a new portable or mobile rig, you might like either of the two circuits shown here. Both produce voltage gains in excess of 1,000, with an absolute minimum of components.

Using these circuits, a ceramic or dynamic microphone will give you plenty of punch for full modulation—without the worries about audio quality which frequently accompany the use of a carbon mike.

The lead-off circuit, shown in Fig. 1, is a variant on the cascode. The cascode is probably better known as a VHF rf amplifier than as a high-gain audio circuit—but this version gives voltage gain ranging from 1,000 to 2,000, depending on the type of tube used.

Since three triode sections are necessary for best action, this circuit is a natural for Compactrons such as the 6D10 or 6C10. Component values shown are suitable for either, as well as for the three halves of 12AX7, 12AT7, or 12AU7.

Here's how it works. In a normal cascode circuit, the stage gain is actually (very close to) the product of the transconductance of the *input* section multiplied by the load impedance seen by the *output* section. In this version, the load impedance is 4.7 megohms. To keep current flow in the input stage, thus

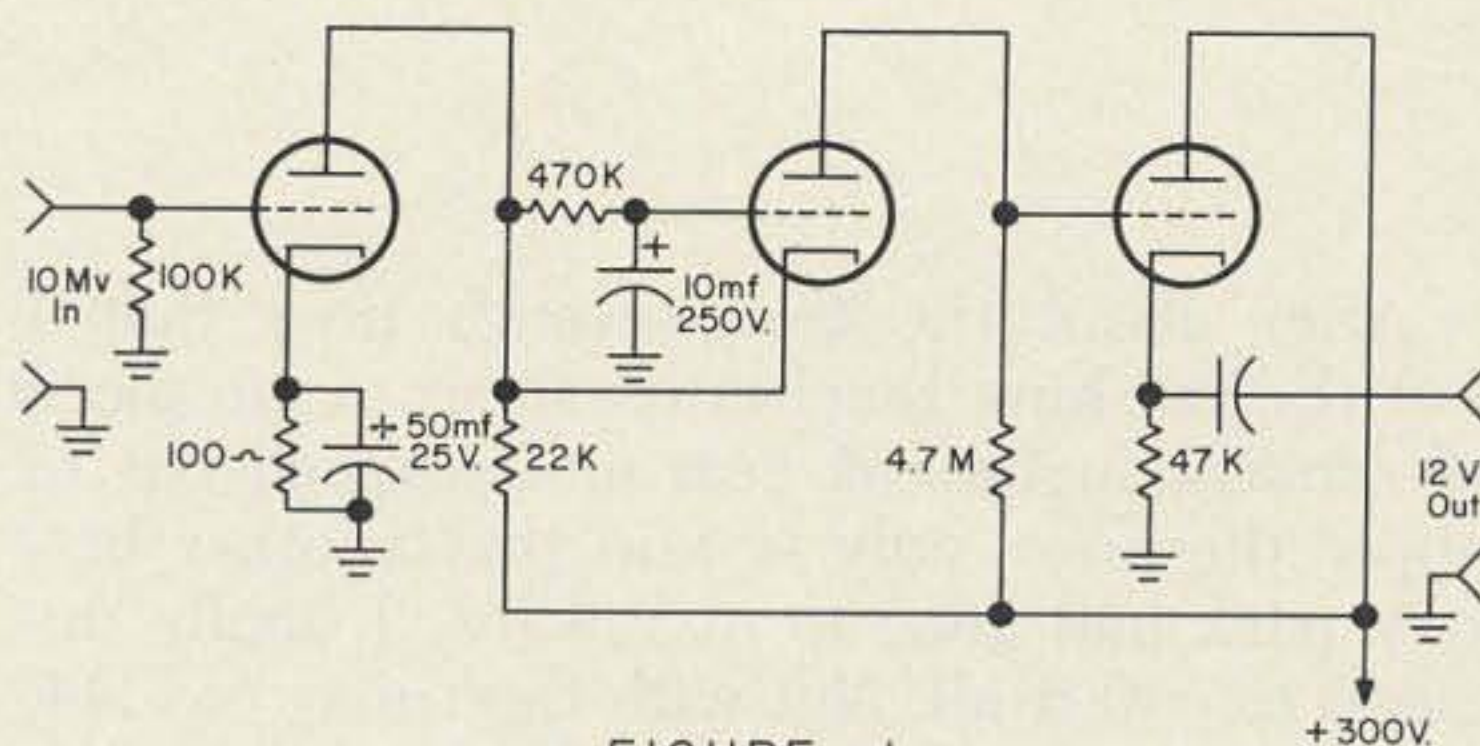


FIGURE 1

keeping transconductance high, the output stage is shunted by a 22K ohm resistor.

Since the input impedance of the output stage is low (usually under 500 ohms), all the signal goes into the output stage. Thus, the stage gain equals the transconductance of the normally functioning input stage times the extremely high plate load resistance in the "output", giving a range of gain between 1,000 and 2,000.

The cathode follower actually used as the output is necessary because otherwise the high output impedance would cause problems above 1500 cps. As shown, response is good throughout the "communication" range up past 3,000 cps, then falls off rather sharply.

The only tricky point to watch in this circuit is to be certain that no heater wires or rf-carrying leads come anywhere near the plate end of the 4.7-meg resistor or the lead connected to the grid of the cathode follower.

While the three triode sections connected as normal amplifiers would provide more actual gain, such connections would also require 3 additional resistors and 3 additional capacitors, as well as introducing phase shifts and attendant possibilities of audio feedback.

But if you're searching for something closer to the ultimate in the "something-for-nothing" department, sneak a peek at Fig. 2. This "starved" amplifier uses only two tubes, four resistors, a single capacitor, and one transformer, to fully modulate a 5 watt transmitter with the output of a ceramic mike!

(Turn to page 90)

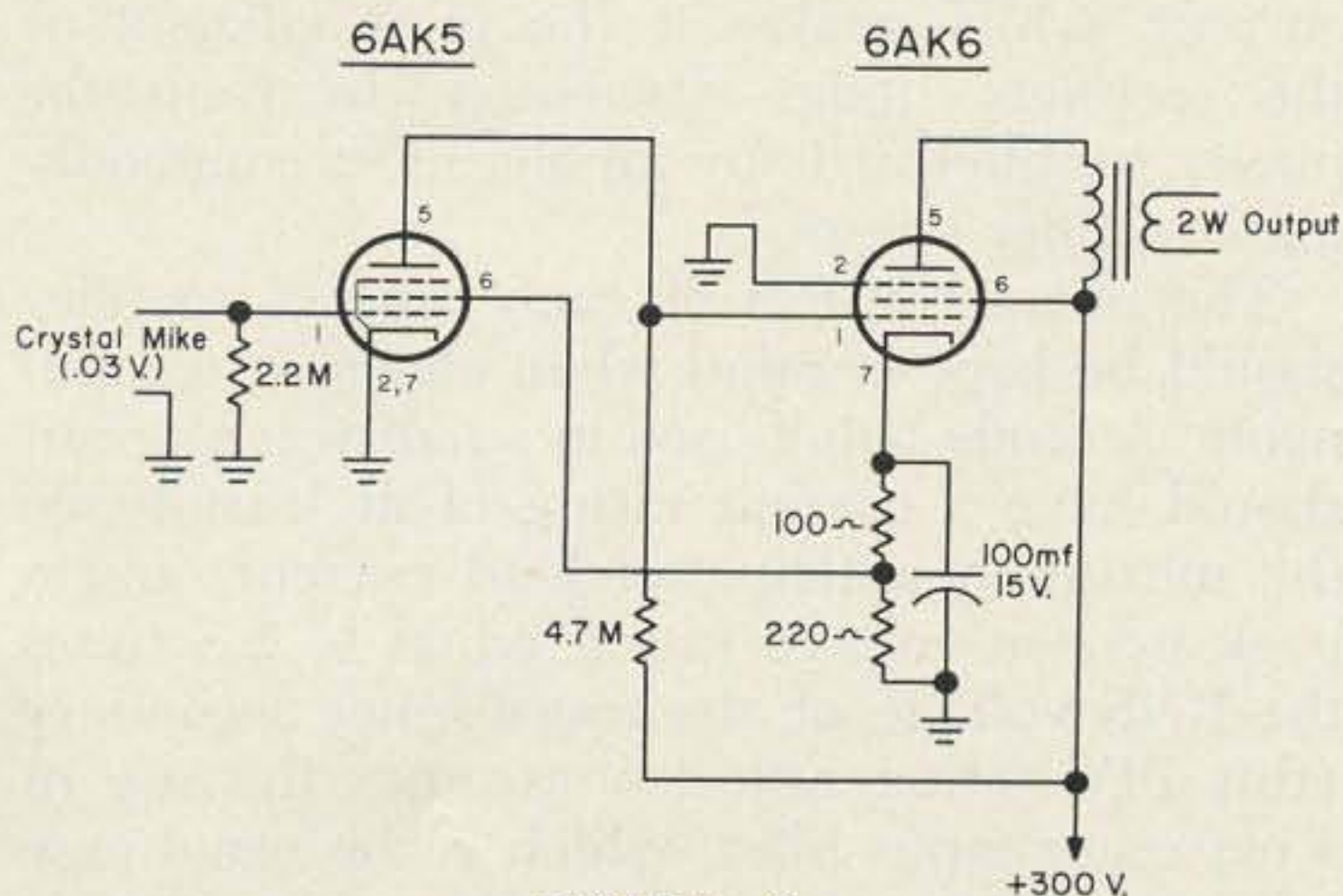


FIGURE 2

Smaltz for Semiconductors

Robert A. Kidder

After about the forty-seventh time that I put the finishing touches on some exotic piece of semiconductorized gear and reached out to apply the juice, only to find that another battery pack had gone to its reward, I finally decided to end it all. Not with the trusty old .44, however, but by hitting the books and engaging in a bit of judicious brain-picking among certain of my cohorts. Herewith follows the results of this research: a treatise on the derivation of low voltage direct current in any reasonable quantity from the ac line.

The biggest difference between vacuum tube plate supplies and transistor supplies is impedance. Tube circuits in general are high impedance affairs and are therefore low current loads. Transistors, on the other hand, are inherently low impedance devices and are heavy loads for power supplies. A typical tube circuit might draw 15 milliamps at 150 volts, or 2.25 volt-amperes, while a similar circuit in transistors might require 15 milliamps at 15 volts, which is also 2.25 volt-amperes. This makes the transistor supply a big, hairy monster, when considered on the basis of the voltage to current ratio. This means that the transistor supply must have very low impedances associated with it. Its output impedance especially must be as low as possible. With this much having been stated, let us now have at these semiconductor feed-bags.

The first thing to consider is the rectifier, because this will have a direct bearing on virtually every other component in the supply. Figure 1 shows a simple, inexpensive, half-wave circuit, which is suitable for light loads (25 milliamps or less). The main reason that heavier current drains from this circuit are not advisable is that the half-wave rectifier is quite inefficient. It delivers to the load less than 50% of the available current. Another point to consider is that the 60 cycle ripple in the

output of a half-wave rectifier is five times harder to filter than the 120 cycle full-wave buzz. This means that hum will increase at a much faster rate with an increasing load than it would in the case of a full-wave circuit. A factor stemming from this is that voltage regulation is inherently poor in a half-wave supply. These faults notwithstanding, half-wave circuitry can be used in compact, low current supplies, especially if very small ripple is not a requirement.

Figure 2 illustrates two basic types of full-wave rectifiers. 2A is the conventional center-tapped configuration which is commonly used in vacuum tube plate supplies. In transistor supplies, however, this circuit is not employed as extensively as in Figure 2B, the full-wave bridge. The full-wave center-tap circuit can be used for loads of any magnitude, but it delivers only about 70% of the available current, and it requires a transformer with a center-tapped secondary. Digging up a center-tapped transformer that will produce 35 to 40 volts of dc could be quite a sporting proposition.

Since suitable rectifiers can be had at very reasonable prices, the full-wave bridge of Figure 2B offers distinct advantages. One is the fact that it will pass 90% of the available current, which makes it the most efficient of the rectifiers under discussion. In transistor power supplies, it is by far the most commonly used rectifier circuit.

The characteristics of each type of rectifier should be kept in mind when choosing components. A diode being used in a half-wave circuit should have a current rating of at least twice the maximum anticipated load current, and a peak inverse voltage rating equal to 2.8 times the RMS voltage of the transformer secondary (this PIV rating criterion assumes the use of a capacitor-input filter, which is the usual case in transistor supplies). Rectifying elements in

a center-tap circuit should have a current rating at least equal to the load current, and the PIV of each diode will be 1.4 times the RMS voltage of the transformer's entire secondary. The minimum current rating for each of the four diodes in a full-wave bridge is equal to one half of the maximum anticipated load current, while the minimum PIV rating is the same as for a center-tap circuit.

Usually the power transformer for a transistor supply is a small filament transformer. These are available in quite a number of secondary voltages, ranging from 2.5 to 26.5 volts, with higher voltages obtainable in other types of power transformers. Other kinds of transformers, such as audio output or interstage types, can be used also, especially in low current supplies, but the word here is "Caution".

(Turn to page 38)



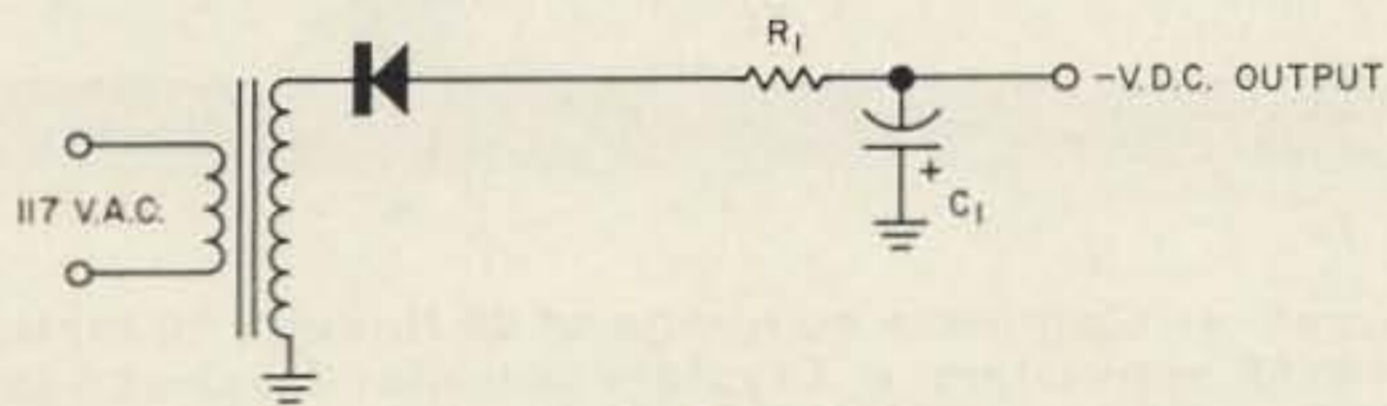


FIGURE 1

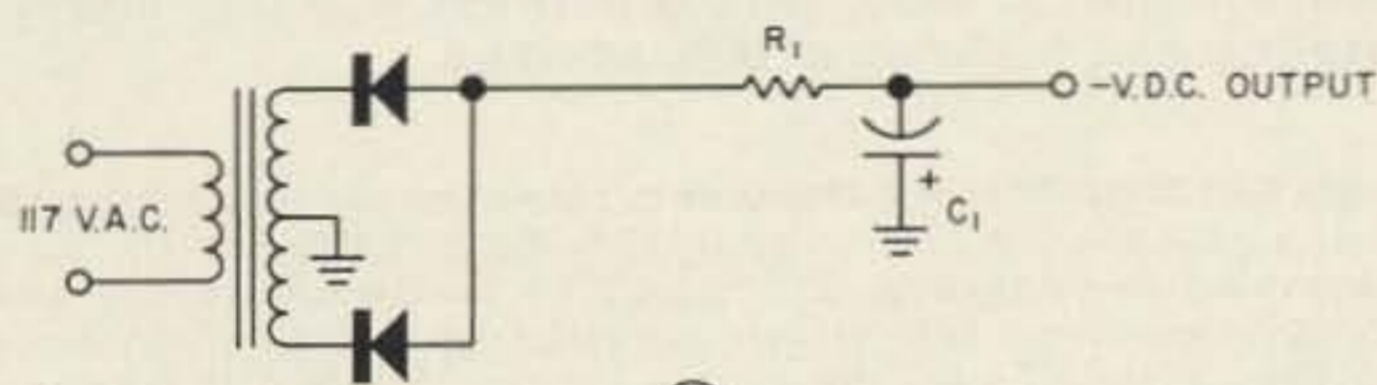


(A)

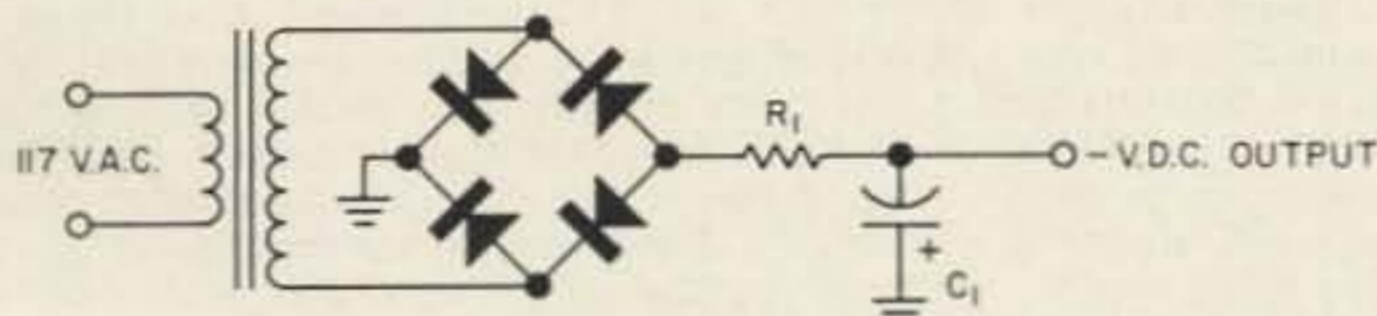


(B)

FIGURE 2

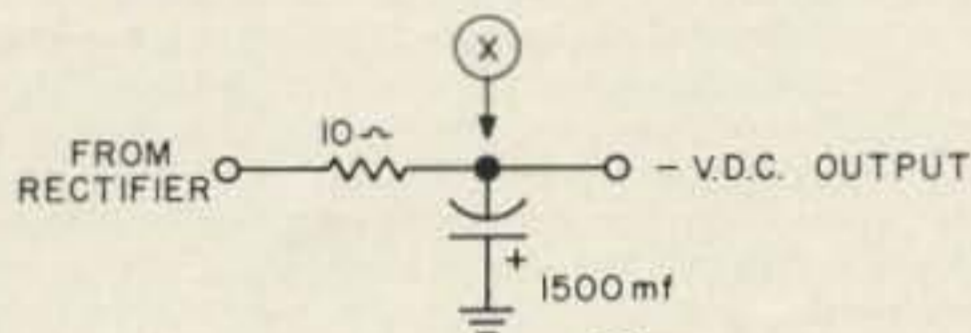

(A)

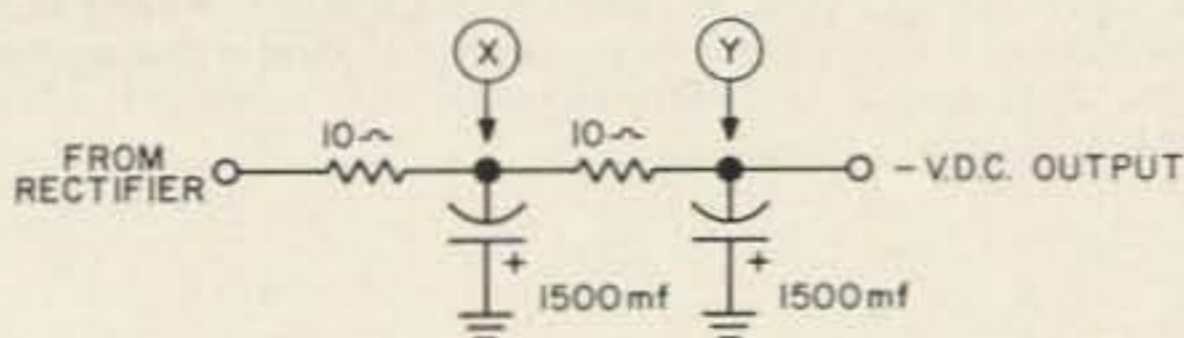

(B)

FIGURE 3


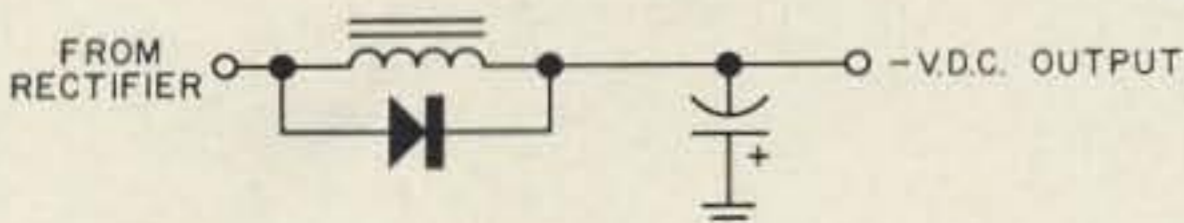


FIGURE 4

2-watt Audio Amplifier

NEW! MITY-AMP

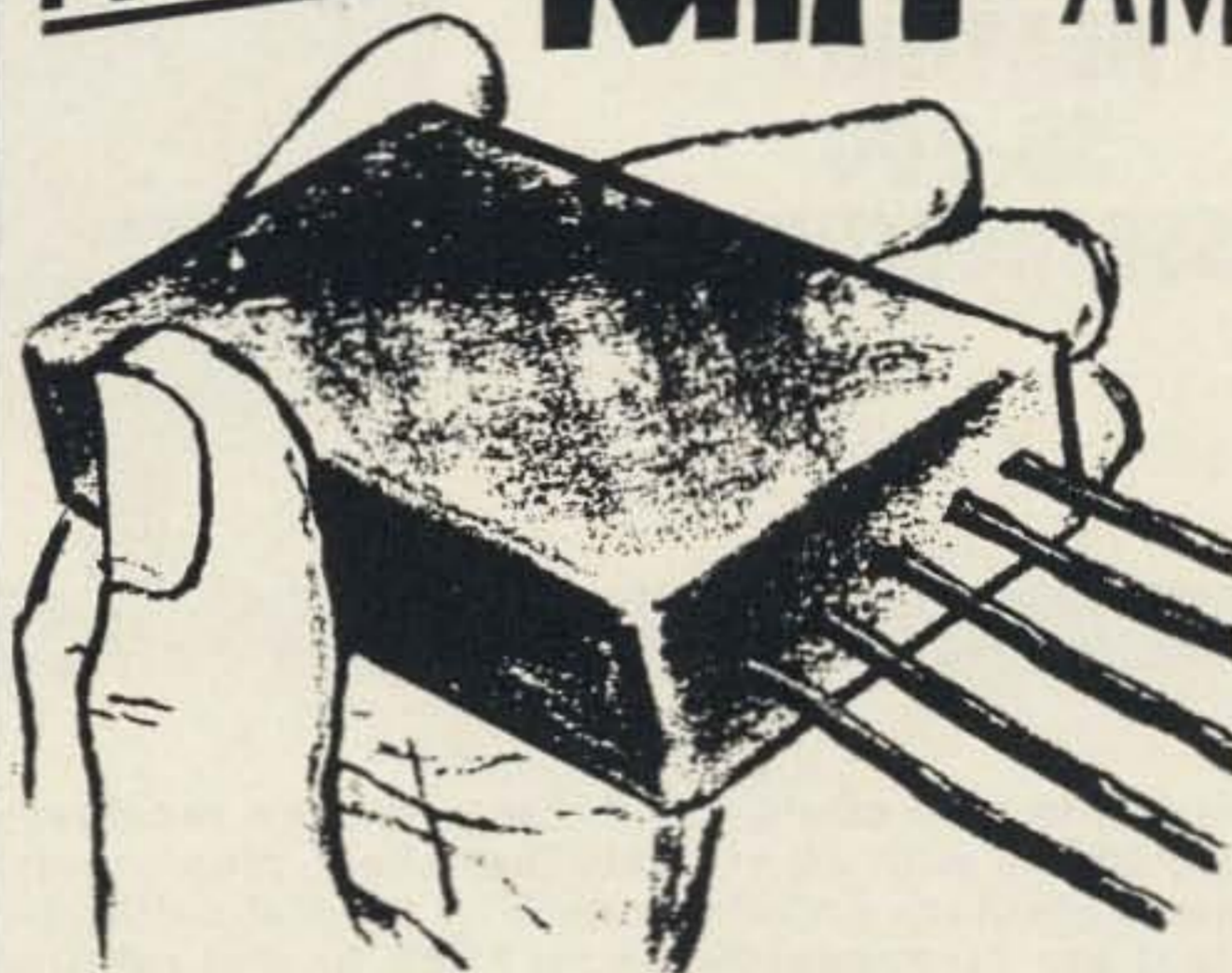

- Completely epoxy encapsulated module
- 20-15,000 cycles \pm 2db
- 2" x 3 1/2" x 7/8", 6 ounces
- 6-12 volts @ 300-700 ma
- 45-50,000 ohms input impedance
- 3.2-45 ohms output impedance
- water, moisture, dirt, dust proof
- guaranteed for one year

USES

- drive loudspeaker from transistor radio
- drive loudspeaker from earphone output
- small modulator
- intercom amplifier
- speech amplifier
- signal tracer
- public address amplifier
- microphone amplifier

(complete with instructions, diagrams, etc.)

ONLY
\$995
No. MA-100

Available from major parts distributors such as Allied, Barry, Electronic Wholesalers, Harrison, Harvey, Lafayette, Olson, Radio Shack, World Radio or direct from

SAXTON PRODUCTS INC.


4121 Park Avenue, Bronx 57, N. Y.

We also make all sorts of wire products; twinlead, coax, open line, etc. Send for our catalog b-24 and see.

Now there are two in

#1

HEATHKIT SB-300 SSB-RECEIVER

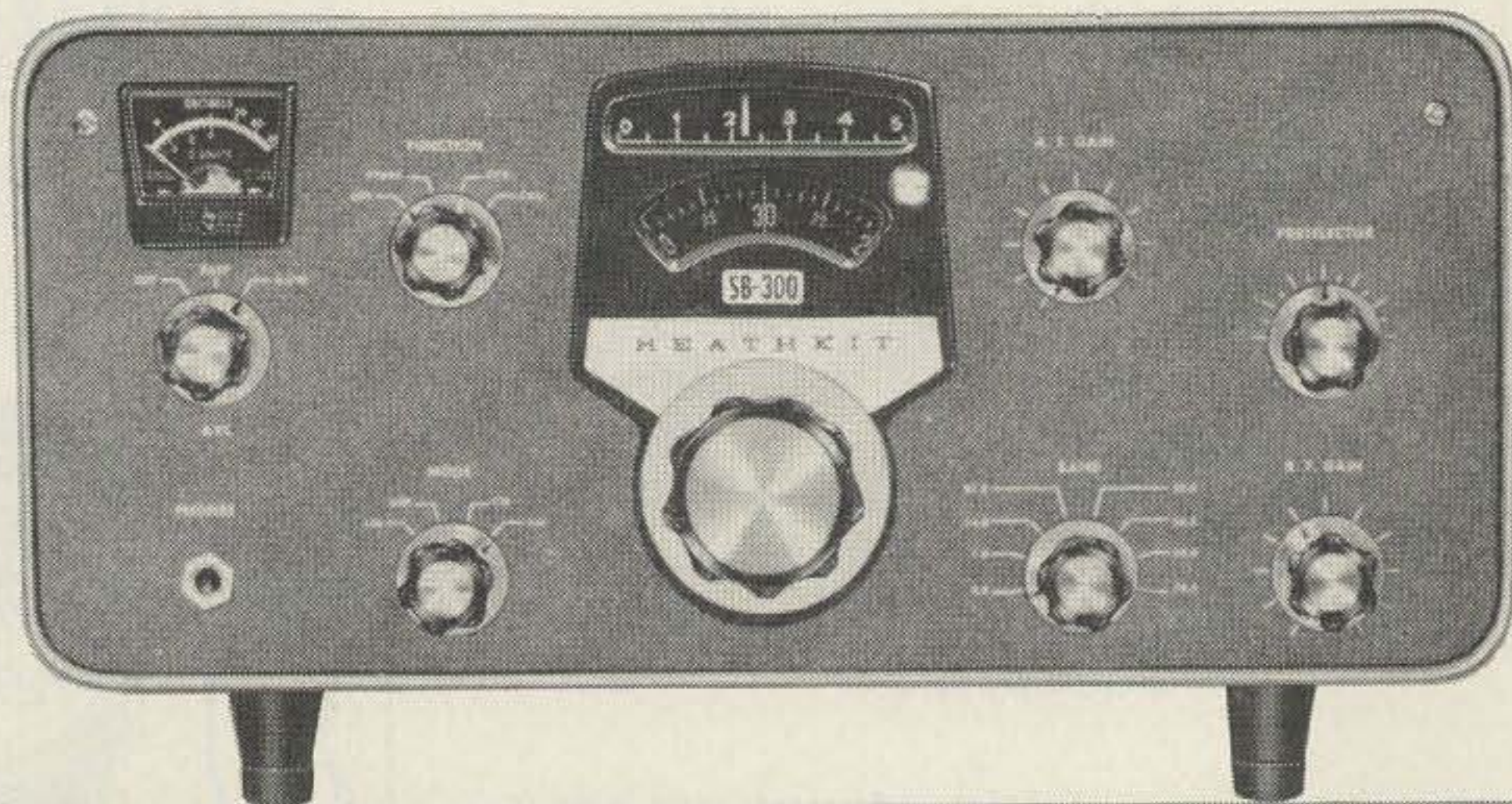

- Everything you could ask for in a deluxe receiver and more!
- Complete coverage of 80 through 10 meter amateur bands with all crystals furnished, plus provision for VHF converters
- Crystal-controlled front-end for maximum stability on all bands
- 1 kc dial calibrations—100 kc per dial revolution provides bandspread equal to 10 feet per megacycle—tuning knob to dial ratio approximately 4 to 1
- Provision for transceive operation with matching SB-400 Transmitter
- Pre-built Linear Master Oscillator (LMO), wiring harness and two heavy-duty circuit boards for fast, easy assembly
- Professional styling and features at 60% savings

Good news travels fast! . . . especially on the amateur airwaves! Since its introduction, the Heathkit SB-300 has set the amateur world on its ear as one of the finest values in the industry! Deluxe styling and features now bring you a new dimension in quality, performance and dependability never before thought possible in kit form! . . . and by doing the easy assembly yourself you'll save 60% the cost of comparable units!

Experienced amateurs will quickly recognize the high standards to which this receiver was designed. Its many superb features include a crystal-controlled front-end for optimum stability on all bands, a pre-built Linear Master Oscillator (LMO) for linear tuning with 1 kc dial calibrations, a built-in crystal calibrator, hermetically-sealed 2.1 kc crystal band-pass filter, smooth non-backlash vernier dial mechanism . . . and many, many more! Order yours today!

Kit SB-300, less speaker
22 lbs., \$27 dn., \$22 mo. \$265.00
SBA-300-1 Optional AM crystal filter
(3.75 kc) 1 lb. \$19.95
SBA-300-2 Optional CW crystal filter
(400 cps) 1 lb. \$19.95
Export model available for 115/230 volts AC, 50-60 cps; write for details.


SB-300 SPECIFICATIONS—Frequency range (megacycles): 3.5 to 4.0, 7.0 to 7.5, 14.0 to 14.5, 21.0 to 21.5, 28.0 to 28.5, 28.5 to 29.0, 29.0 to 29.5, 29.5 to 30. **Intermediate frequency:** 3.395 megacycles. **Frequency stability:** Less than 100 cps per hour after 20 min. warmup under normal ambient conditions. Less than 100 cps for $\pm 10\%$ line voltage variation. **Visual dial accuracy:** Within 200 cps on all bands. **Electrical dial accuracy:** Within 400 cps on all bands after calibration at nearest 100 kc point. **Backlash:** No more than 50 cps. **Sensitivity:** Less than 1 microvolt for 15 db signal plus noise-to-noise ratio for SSB operation. **Modes of operation:** Switch selected; LSB, USB, CW, AM. **Selectivity:** SSB: 2.1 kc at 6 db down, 5.0 kc at 60 db down (crystal filter supplied). AM: 3.75 kc at 6 db down, 10 kc at 60 db down (crystal filter available as accessory). CW: 400 cps at 6 db down, 2.5 kc at 60 db down (crystal filter available as accessory). **Spurious response:** image and IF rejection better than 50 db. Internal spurious signals below equivalent antenna input of 1 microvolt. **Audio response:** SSB: 350 to 2450 cps nominal at 6 db. AM: 200 to 3500 cps nominal at 6 db. CW: 800 to 1200 cps nominal at 6 db. **Audio output impedance:** Unbalanced nominal 8 ohm speaker and high impedance headphone. **Audio output power:** 1 watt with less than 8% distortion. **Antenna input impedance:** 50 ohms nominal. **Muting:** Open external ground at Mute socket. **Crystal calibrator:** 100 kc crystal. **Front panel controls:** Main tuning dial; function switch; mode switch; AGC switch; band switch; AF gain control; RF gain control; preselector; phone jack. **Rear apron connections:** Accessory power plug; HF antenna; VHF #1 antenna; VHF #2 antenna; mute; spare; anti-trip; 500 ohm; 8 ohm speaker; line cord socket; heterodyne oscillator output; LMO output; BFO output; VHF converter switch. **Tube complement:** (1) 6BZ6 RF amplifier; (1) 6AU6 Heterodyne mixer; (1) 6AB4 Heterodyne oscillator; (1) 6AU6 LM osc.; (1) 6AU6 LMO mixer; (2) 6BA6 IF amplifier; (1) 6AU6 Crystal calibrator; (1) 6HF8 1st audio, audio output; (1) 6AS11 Product Detector, BFO, BFO Amplifier. **Power supply:** Transformer operated with silicon diode rectifiers. **Power requirements:** 120 volts AC, 50/60 cps, 50 watts. **Dimensions:** 14 $\frac{1}{2}$ " W x 6 $\frac{1}{2}$ " H x 13 $\frac{1}{8}$ " D. **Net weight:** 17 lbs.



FREE CATALOG

See the wide array of Heathkit Amateur Radio Equipment available at tremendous do-it-yourself savings! Everything you need in "mobile" or "fixed" station gear with full descriptions and specifications . . . Send for Free copy!

the HEATHKIT® SB series

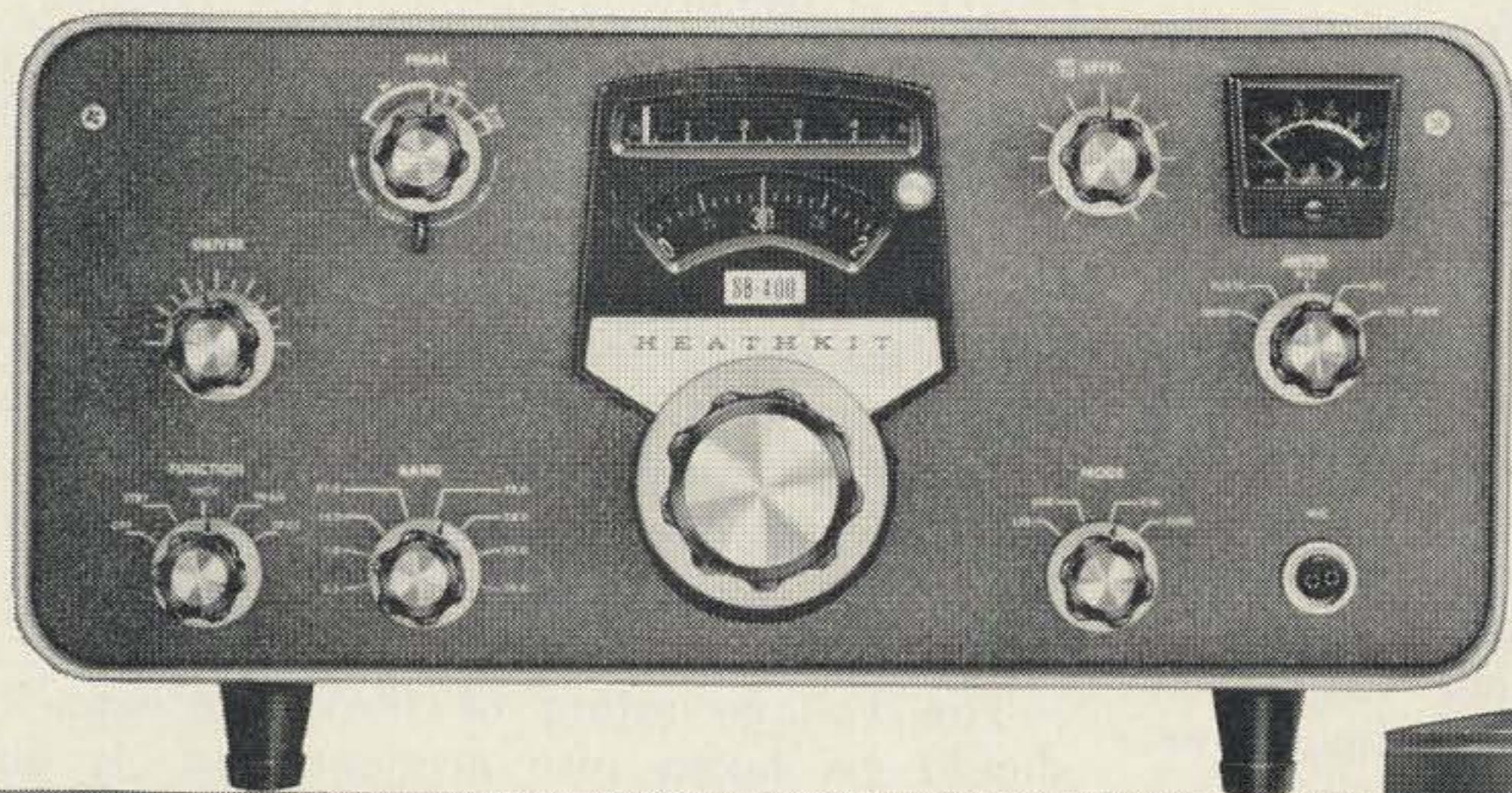

#2

HEATHKIT SB-400 SSB TRANSMITTER

- Built-in power supply • Complete transceive capability with SB-300 Receiver • Linear master oscillator frequency control • Built-in antenna change-over relay • All crystals supplied for complete 80-10 meter coverage • Automatic level control for higher talk power, minimum distortion • 180 watts PEP SSB, 170 watts CW • Crystal filter type SSB generation • Operates SSB (upper or lower sideband) & CW • VOX & PTT control in SSB operation, VOX operated CW break-in using CW sidetone • CW "shift" transceive operation to eliminate transceiver chasing • Crystal controlled heterodyne oscillators • 1 kc dial calibration—100 kc per dial revolution • Dial bandspread equal to 10 feet per megacycle • 500 kc coverage per bandswitch position • Switched 120 V AC for external amplifier antenna relay • Sturdy, lightweight, heavy-gauge aluminum construction throughout • Neat, modern "low-boy" styling

Here it is . . . the new Heathkit SB-400 Transmitter . . . second in the exciting new Heathkit series of Deluxe SSB Amateur gear! Following the same high standards set by the Heathkit SB-300 Receiver, the new SB-400 Transmitter now offers a matching counterpart that permits complete transceive operation with a host of advanced engineering design features for unmatched performance, versatility and operating convenience!

Unique mechanical design . . . prebuilt Linear Master Oscillator (LMO) . . . built-in heavy-duty power supply . . . sturdy chassis construction . . . beautiful modern styling . . . and power-packed performance are just a few of the many features that make the SB-400 your best buy in an SSB Transmitter! Order yours today for "Deluxe" communications at tremendous do-it-yourself savings!

Kit SB-400. . . 33 lbs. . . Write for credit details. \$325.00
Export model available for 115/230 volts AC, 50-60 cps; write for details.

SB-400 SPECIFICATIONS—Emission: SSB (upper or lower sideband) and CW. **Power input:** 170 watts CW, 180 watts P.E.P. SSB. **Power output:** 100 watts (80-15 meters), 80 watts (10 meters). **Output impedance:** 50 to 75 ohm—less than 2:1 SWR. **Frequency range:** (mc) 3.5-4.0; 7.0-7.5; 14.0-14.5; 21.0-21.5; 28.0-28.5; 28.5-29.0; 29.0-29.5; 29.5-30.0. **Frequency stability:** Less than 100 cps per hr. after 20 min. warmup under normal ambient conditions. Less than 100 cps for ± 10% line voltage variation. **Carrier suppression:** 55 db below peak output. **Unwanted sideband suppression:** 55 db @ 1 kc. **Intermodulation distortion:** 30 db below peak output (two-tone test). **Keying characteristics:** Break-in CW provided by operating VOX from a keyed tone (Grid block keying). **CW sidetone:** 1000 cps. **ALC characteristics:** 10 db or greater @ 0.2 ma final grid current. **Noise level:** 40 db below rated carrier. **Visual dial accuracy:** Within 200 cps (all bands). **Electrical dial accuracy:** Within 400 cps on all bands after calibration at nearest 100 kc point. **Backlash:** Less than 50 cps. **Oscillator feed-through/mixer products:** 55 db below rated output (except 3910 kc crossover which is 45 db). **Harmonic radiation:** 35 db below rated output. **Audio input:** High impedance microphone or phone patch. **Audio frequency response:** 350 to 2450 cps ±3 db. **Power requirements:** 80 watts STBY, 260 watts key down @ 120 V AC line. **Dimensions:** 14 $\frac{1}{8}$ " W x 6 $\frac{5}{8}$ " H x 13 $\frac{3}{8}$ " D.

Watch for the new SB-100 All-Band SSB Transceiver and SB-2001 KW Linear Amplifier soon to be released!



Heath Company, Dept. 11-6-1
Benton Harbor, Michigan 49023

Enclosed is \$265.00 plus postage. Please send SB-300 Receiver.

Enclosed is \$325.00 plus postage. Please send SB-400 Transmitter.

Please send Free 1964 Heathkit catalog.

Address _____

Name _____

City _____ State _____ Zip _____

Prices and specifications subject to change without notice.

AM-142

In picking a transformer, you should keep in mind that the input capacitor of the filter will charge up to the peak voltage of the secondary. The peak voltage is equal to 1.4 times the RMS voltage at which the secondary is rated. Thus, a 6.3 volt filament transformer will develop nearly nine volts across the filter capacitor, which, if it is large enough, will maintain that voltage level even in the teeth of a moderately heavy load.

Another factor to consider in choosing a transformer is the rectifying circuit that it will be looking into, because this will affect the current rating of the secondary. The efficiency figures given previously for the various types of rectifier circuits refer to the percentage of a transformer's secondary current capability which can be drawn by the load without overworking the transformer. They are less an indication of how big a wagon a supply is than of how big a horse the transformer has to be in order to move it. If a half-wave rectifier is to be used, the current rating of the secondary should be equal to at least twice the maximum expected load current. In the case of a center-tap circuit, the secondary current capability should exceed the load current by at least 40%. For a full-wave bridge, the current rating of the secondary should at least equal the heaviest anticipated load current.

Now let's take a look at filter circuits. The first component usually encountered is the surge limiting resistor, R1, which is added to protect the rectifier. The reason for this is that when the supply is first turned on, the uncharged filter capacitor is a dead short, and the instantaneous current flow is very high. Without R1 in the circuit, this surge would be limited only by the forward resistance of the rectifier in series with the resistance of the wire in the transformer secondary. The peak surge current could be 20 amps or more, which is enough to wipe out instantly many low current diodes. The value of R1 is picked to keep the maximum possible current flow (effectively the same as a short from the rectifier output to ground with the peak secondary voltage present) less than the one-cycle surge rating of the rectifying element. Typical values for R1 will fall between 5 ohms and 50 ohms, in general. The surge limiting resistor is not always required with medium to heavy duty rectifiers (those rated at 500 milliamps or higher). A quick look at the Condensed Rectifier Specifications sheet in the fourth edition of the G. E. Transistor Manual seems to indicate that the one-

cycle surge rating of any given (G. E.) rectifier is at least 20 times greater than its continuous current rating.

The next component is the filter capacitor. For most light and medium load applications, the B. F. C. (Brute Force Capacitance) approach is usually adequate. This consists of hunting up the biggest, hairiest, electrolytic capacitor you can find and placing it across the output of the supply, such as with C1 in Figures 1 and 2. In general, 250 microfarads should be considered the practicable minimum for loads up to 20 or 25 milliamps. Where loads approach one amp, the filter capacitor may have a value of five thousand microfarads or more, although with loads of this magnitude it's better practice to use a multi-section filter and electronic regulation.

The voltage rating of the filter capacitor should be taken into account, too. It goes without saying that an electrolytic must never be exposed to voltages greater than its rated working level, nor should they be wired up in reverse polarity. They've been known to come apart with explosive force under either condition. The voltage rating of an electrolytic should always exceed the actual voltage present in its working circuit by a small margin, at least 20%, but it can go as high as 100% or more. In any event, if the voltage rating is greater than the working voltage by a large amount, three or four times, for instance, the capacitor may not "form" properly. This condition manifests itself as a loss of rated capacitance, and as a result, the filtering action can be reduced greatly. In choosing a filter capacitor, then, keep its voltage rating higher than, but reasonably close to, the peak voltage of the transformer secondary.

In a previous paragraph, multi-section filters were mentioned. Let us examine them more closely forthwith. Referring now to Figure 3A, suppose the load is such that there is 100 millivolts of ripple at point "X". Assume further that this amount of ripple is intolerable for the desired application, but that 10 millivolts would be acceptable. In order to reduce the hum voltage by a factor of ten, several things can be done. You could increase the value of C1 ten times. Fifteen thousand microfarad electrolytics are available, and they're well within the means of the average working millionaire. A more practicable, and certainly less expensive, solution is to add a second filter section, as in Figure 3B. Since the reactance of a 1500 microfarad capacitor is slightly less than one ohm at 120 CPS (assuming full-wave rectification), the 100 millivolts of ripple pres-

ent at point "X" will see an effective resistance of 11 ohms to ground: the ten ohms of R2 in series with the one ohm reactance of C2. This is a simple voltage divider. Therefore, the ripple to be found at point "Y" will be 1/11 of the ripple at point "X", or just over 9 millivolts, with the remaining ninety-odd millivolts having been dropped across R2. The DC voltage at point "X" will see only R2 in series with the load resistance, with C2 looking like an open circuit. Ripple could be further reduced by increasing the value of R2, but watch out for the DC voltage drop across it. With a one amp load on the circuit of Figure 3B, the DC drop across R2 would be 10 volts. The writer hastens to add that the values given for R1 and R2 in Figure 3 are obviously not advisable in normal practice for a one amp filter circuit.

Chokes are not usually used as filter elements in semiconductor supplies. One of the reasons for this is the fact that the DC resistance is fairly high, as much as two or three hundred ohms. Another reason is that most of the small filament transformers commonly used in transistor supplies can deliver one amp without even trying; if you happen to have a one amp choke lying about, it could be used to far better advantage in your kilowatt vitamin pill. Still other factors to consider are large physical size, magnetic radiation, and dangerously high (for transistors) inductive kickback voltage when the supply is turned off.

It is not the writer's intention to condemn the use of chokes in semiconductor supplies, however. They can be utilized, sometimes to

good advantage, for loads up to a quarter amp or so, if the overall size of the supply is not a factor. The first consideration is that the choke will tend to hold the output voltage at the RMS voltage of the transformer secondary, thereby affording improved regulation. The choke should be positioned with its core at right angles to the transformer core in order to minimize hum radiation, although this is a lesser problem with semiconductor devices than with vacuum tubes, owing to the inherently low impedances of transistors. The inductive kickback can be neutralized by connecting a diode across the choke, as shown in Figure 4. The polarity of the diode should be such that it does not conduct when the supply is in use; it acts to short out the high voltage spike generated by the collapsing magnetic field of the inductor when the supply is turned off, or otherwise suddenly interrupted. One other thing: make sure the capacitor and choke combination that you use is not resonant at either 60 or 120 cps, otherwise you may find that you have raw, wild ac of startling amplitude instead of clean, smooth dc. If you do decide to use a choke, put it ahead of the filter capacitor and omit the surge limiting resistor.

This half of the article has detailed the process of converting the ac line power to low voltage dc which may be used "as is" for many transistor circuits. In the second half we shall examine various ways to regulate the output voltage of these supplies. We'll also look into methods of varying the voltage output. Be sure to tune in again next month.


. . . Kidder

Surplus Circuit Breakers

Large quantities of aircraft circuit breakers are available on the surplus market in a wide range of current values. Typical of those available are the 10 ampere units shown in the photograph. Since the prices are so ridiculously low, you have probably passed them up as unusable for ac and low-voltage dc applications. Such is not the case. These low-cost breakers are usable in most amateur applications.

Before we go into specific applications, a description of the most commonly available units is in order. These breakers, shown in the photograph, measure approximately $\frac{3}{4}$ " wide by $2 \frac{3}{16}$ " high and extend about 2" behind the panel. Mounting is accomplished by two 6-32 screws on $1 \frac{13}{16}$ " centers. A clearance hole of $\frac{1}{2}$ " diameter is required for the actua-

Roy Pafenberg W4WKM

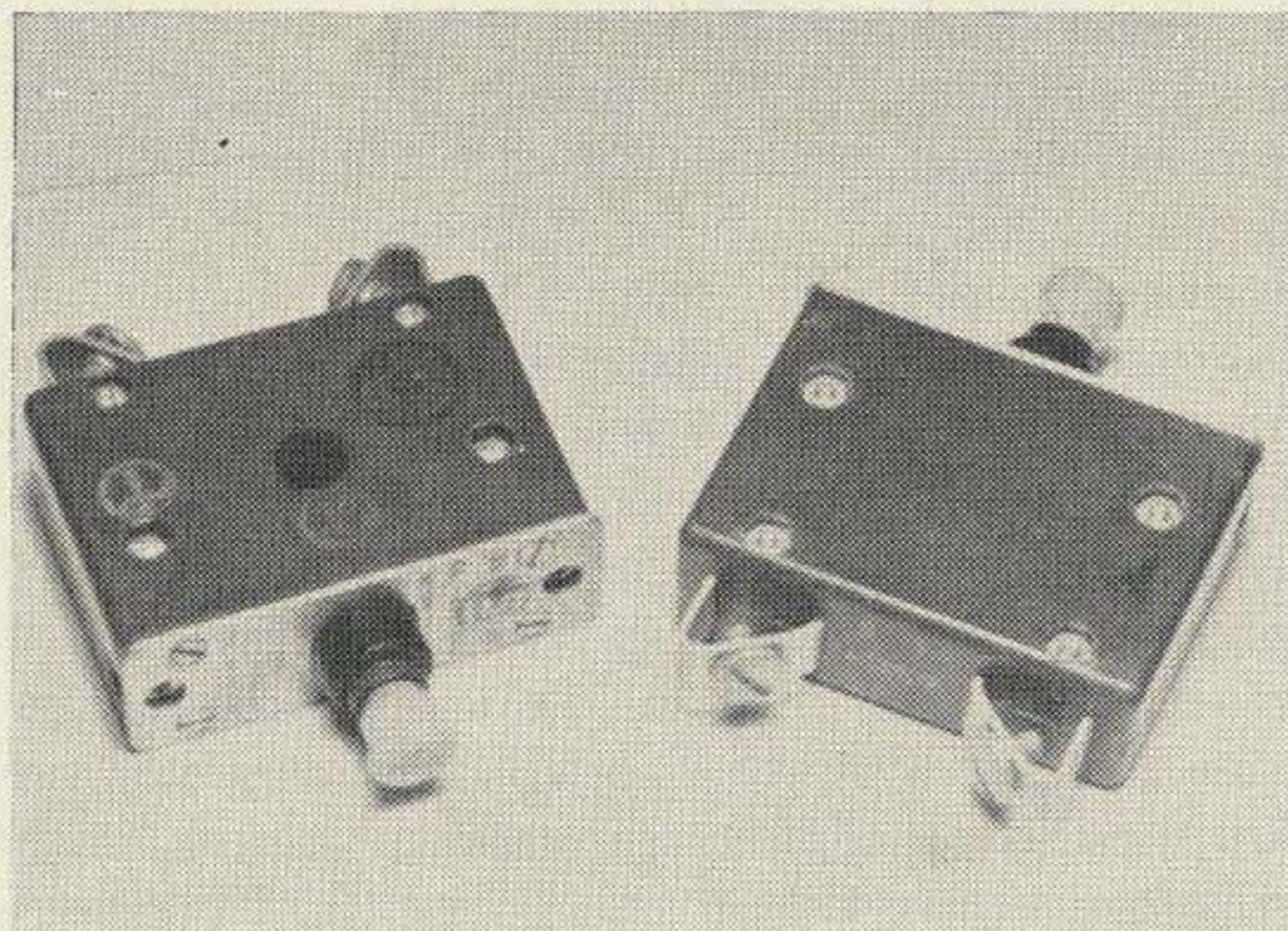

Surplus aircraft circuit breakers, such as these 10 ampere units, have wide amateur application.

tor knob bushing. Terminals consist of metal tabs equipped with 8-32 machine screws. The breaker is closed by pushing in on the front button and opened by pulling it out. In the event the breaker trips, reset is accomplished by simply closing the breaker again.

These breakers are of the thermal trip type so that trip is a function of both percentage and duration of overload. While these units are specifically rated at 120 volts, 400 cycle ac and 30 volts dc, they may be (and have been) successfully used at 120 volts, 60 cycle ac. Current ratings of the standard types range from 5 to 50 amperes and low amperage units are available in the range of 1 to 4 amperes.

These surplus thermal-trip circuit breakers

will carry 100% of their rated current indefinitely and will trip at 125% of their rated current. Trip time at 200% overload ranges, for the various types, from 8 to 25 seconds. Trip time for greater overloads is proportionally shorter. Current interruption capacity varies with voltage and frequency but, in any event, is on the order of several thousand amperes.


Designed to meet military specification requirements, these breakers are *relatively* immune to vibration, shock and temperature variation. Give these low cost, high quality breakers a try in your next construction project. They provide a simple answer to mobile and home station power switching and protection requirements.

... W4WKM

Converting the IP-69 / ALA-2 Panoramic Indicator

William Parker W8DMR
2738 Floribunda Drive
Columbus 9, Ohio

The budget-restricted ham can convert the surplus ALA-2 into a satisfactory panadaptor. Before diving into the conversion, it is best, especially if one does not have understanding of the operation of a panadaptor, to review the functional operation of such a unit. (See block diagram, Fig. 2.) Briefly, the panadaptor is an electronic device that displays on the face of a cathode-ray tube a portion of the radio frequency spectrum. Individual vertical "pips" are panoramically displayed across the horizontal axis of the CRT face. See Fig. 1. An incoming signal (from a receiver) is fed into the broad-band rf amplifier, then into a mixer, the *if* amplifier, and the detector, just as in any conventional superheterodyne receiver. However, the local oscillator voltage supplied to the mixer must vary sufficiently in *frequency* so that it can cover the frequency width carried by the rf amplifier. This is accomplished by the reactance tube which varies the oscillator frequency over the proper

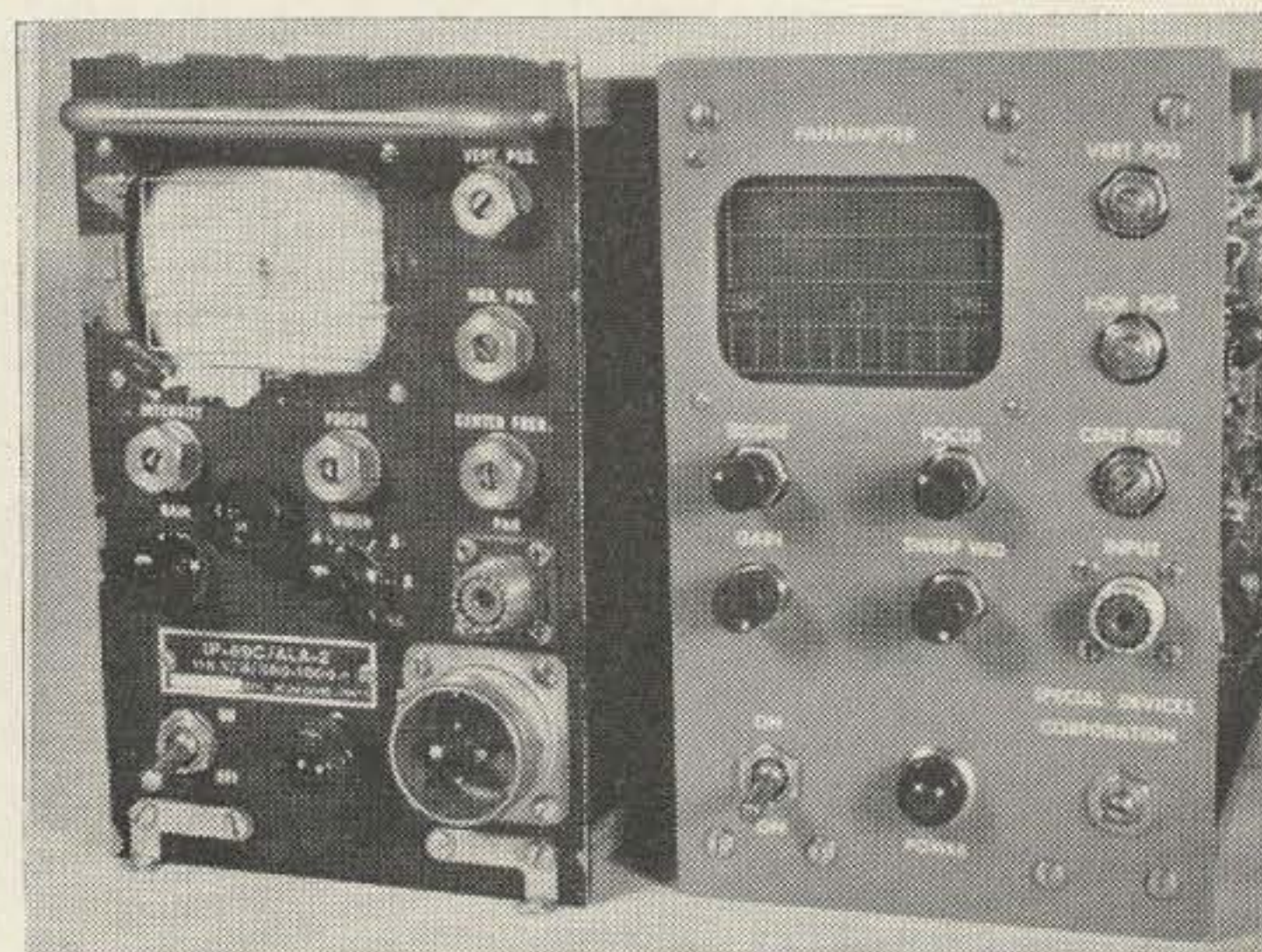

Unit as purchased left, and after conversion right. The power connector hole was plugged with an aluminum disk and liquid aluminum paste.

range. The reactance tube is controlled in turn by the sawtooth generator so that the frequency variation of the oscillator is kept in synchronism with the horizontal deflection. As this deflection occurs, the oscillator beats progressively and periodically with one signal after another to produce an intermediate frequency of 6.5 megacycles. Thus one signal after another is periodically amplified by the *if* amplifiers which are resonant to 6.5 megacycles. Each signal as a signal of the intermediate frequency, in its own order is subsequently rectified by the detector.

The output of the detector is fed to the vertical amplifier and the output of the latter is fed to the vertical deflection plates of the cathode-ray tube.

A signal voltage from the vertical and horizontal amplifiers is used to excite the blanking and intensifier circuit. The output of this circuit is connected to the control grid of the cathode-ray tube and accomplishes two things.

Professional Performance

FOR AMATEURS WITH *Master Mobile* MOBILE EQUIPMENT




Designed for higher "Q" ... with power units and SSB. Use with 3 ft base section and 60" whip. 15 or 20 meter, 6.95; 40 meter, 8.95; 75 meter, 9.95; 160 meter, 14.95



NO. 750 MASTER DELUXE ALL-BANDER
Covers 10 thru 75 frequencies. Silver-plated single turn contact, positive spring. Eccentric cam contact, easy selection of turn. Automatic lock prevents damage to coil.

14⁹⁵ NET

with Field Strength Meter

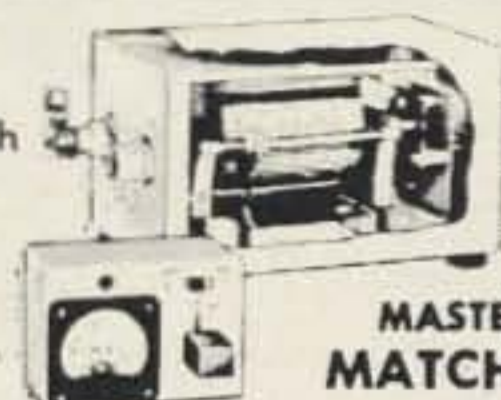

MASTER MATCHER

Automatically tunes Band by remote control. Motor driven variable inductance. All guesswork eliminated.

For 6V Mod. 2495-6 24⁹⁵
For 12V Mod. 2495-12 Complete

No. 925




MICRO-Z-MATCH

Micrometer Impedance - Matching Inductance - Used on all bands with any type coax. cable to match any mobile antenna. Easily adjustable for minimum standing wave ratio (1:1). Complete with Coax. Adp. Kit

9.95 NET

ANTENNAS

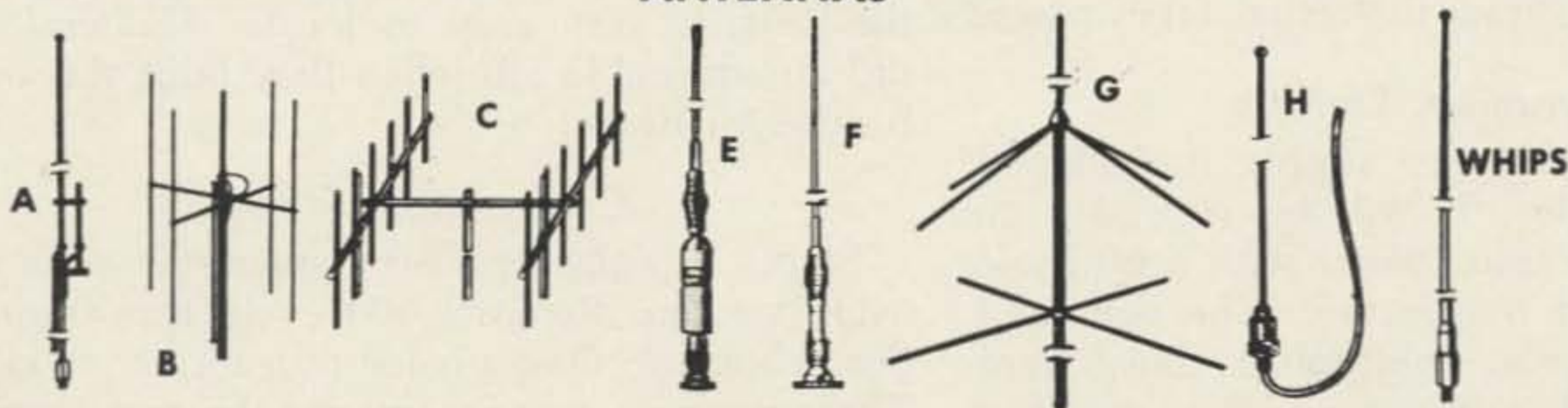

- A** AM-28 2-meter "J" mobile-fixed antenna provides 2 db gain. 86" hght. 14⁹⁵
- B** AM-25 all aluminum "cloverleaf" factory pre-tuned 144-148 mc provides 3 db gain. 12⁹⁵
- C** AM-5 twin six 2-meter beam with 12 db forward gain. Pre-tuned, aluminum, heavy duty. 16⁹⁵
- D** (Not Shown) AM-4 same as above except 6 element beam. 8⁹⁵
- E** AM-7 Sentry "Shorty" 2 meter 1 1/2 wave top loaded fiberglass antenna with mount for CB use. 16⁷⁵
- F** AM-10 "Shorty" as above except it's 6 meter shortened 1/4 wave with mount. 10⁹⁵

G Model 300 ground plane antenna outperforms any type verticle dipole. Ideal for CD and defense nets. 12⁹⁵

H No. 613 Master VHF rooftop antenna for 140-165 Mc. Comes with 10' coax. cable. 4⁹⁵

WHIPS All with Threaded 3/8" stud to fit all mounts. 100-605 60" 4.95; 100-725 72" 4.95; 100-785 5.00; 100-865 86" 5.15; 100-905 90" 5.20; 100-965 96" 5.25; 100-1035 103" 6.95.

FIBERGLASS WHIPS - Flexible, indestructible universal antenna with 3/8" x 24 thread base fitting chrome plated. FG-60 60" 4.95; FG-72 72" 4.95; FG-84 84" 5.15; FG-96 96" 5.25; FG-103 103" 6.95.

E-Z OFF ANTENNA CONNECTOR



Noise-free. Connect or remove loading coils, whips, or mounts without tools. No. E-Z 295.

2.95 NET




No. 10-H

TENNAHOLD
Fits All Cars

1.00 NET

BODY AND BUMPER MOUNTS

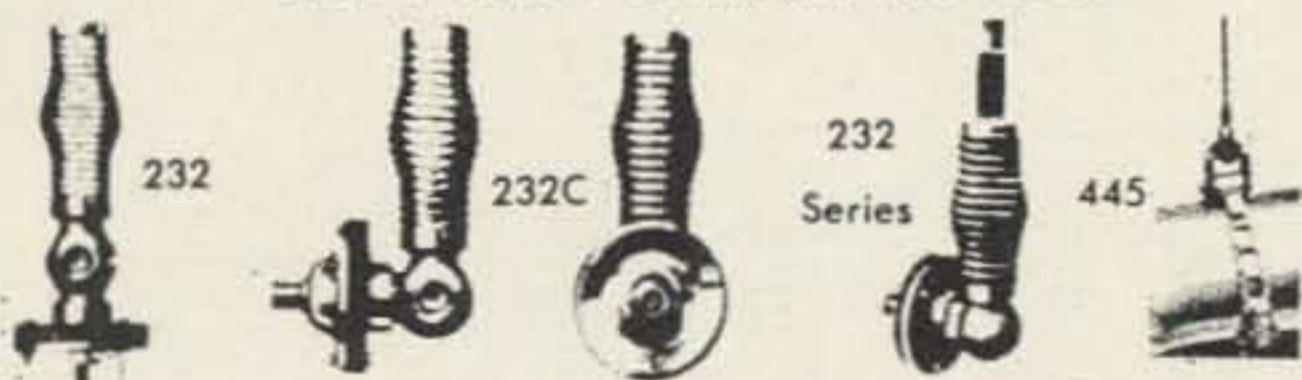

BASE MOUNT	DESCRIPTION	NET
232	D'ble Tapered Spring—Swivel Base	8.75
232C	D'ble Tapered Spring—Swivel Base Coax. Conn.	8.75
232SS	D'ble Tapered Spring—Spec. Stainless	12.95
232SSC	D'ble Tapered Spring—Spec. Stainless — Coax. Conn.	12.95
232X	Heavy Duty—D'ble Tapered Spring—Swivel Base	9.85
232XC	Heavy Duty—D'ble Tapered Spring—Coax. Conn.	9.85
232XSSC	Heavy Duty—D'ble Tapered Spring—Spec. Stainless — Coax. Conn.	14.95
232XSS	Heavy Duty—D'ble Tapered Spring—Spec. Stainless	14.95
232XX	Extra Heavy Duty Spring	10.85
232XXC	Extra Heavy Duty Spring—D'ble Tapered—Coax. Conn.	10.85
232XXSS	Extra Heavy Duty Spring—D'ble Tapered—Spec. Stainless	15.95
232XXSSC	Extra Heavy Duty Spring—D'ble Tapered—Spec. Stainless—Coax. Conn.	15.95
445	Universal Mount—Threaded, 3/8"-24—Chain Mount	7.95

GUTTER MOUNT CG-275



Eliminates hole drilling. Positive locking, retractable and adaptable for any 3/8" 24 thread whip.

7⁹⁵ NET

UNIVERSAL MOUNT



TM-1 is Chrome plated alloy steel mount for any antenna with 3/8" 24 thread.

4⁴⁵ NET

FOR TRUNK LID, COWL MOUNTING



MMM-75 is adjustable for any curved surface. Equipped with coaxial connector.

7⁹⁵ NET

BUMPER MOUNT



MM-520 with shaped links adjustable to any width surface. For spring or whip double mount.

Pat. No. 3,100,241 7⁹⁵ NET
MM-519 S'gle Mt. 4.95

Buy Master Mobile from ALL Leading Dealers
SEND FOR FREE "ANTENNA BUYERS' GUIDE"


Master Mobile Mounts

DIV. OF



4125 W. Jefferson Blvd. Dept. 73-56
AREA 213, 731-2251

LOS ANGELES, CALIF.
TWX 213-737-1315

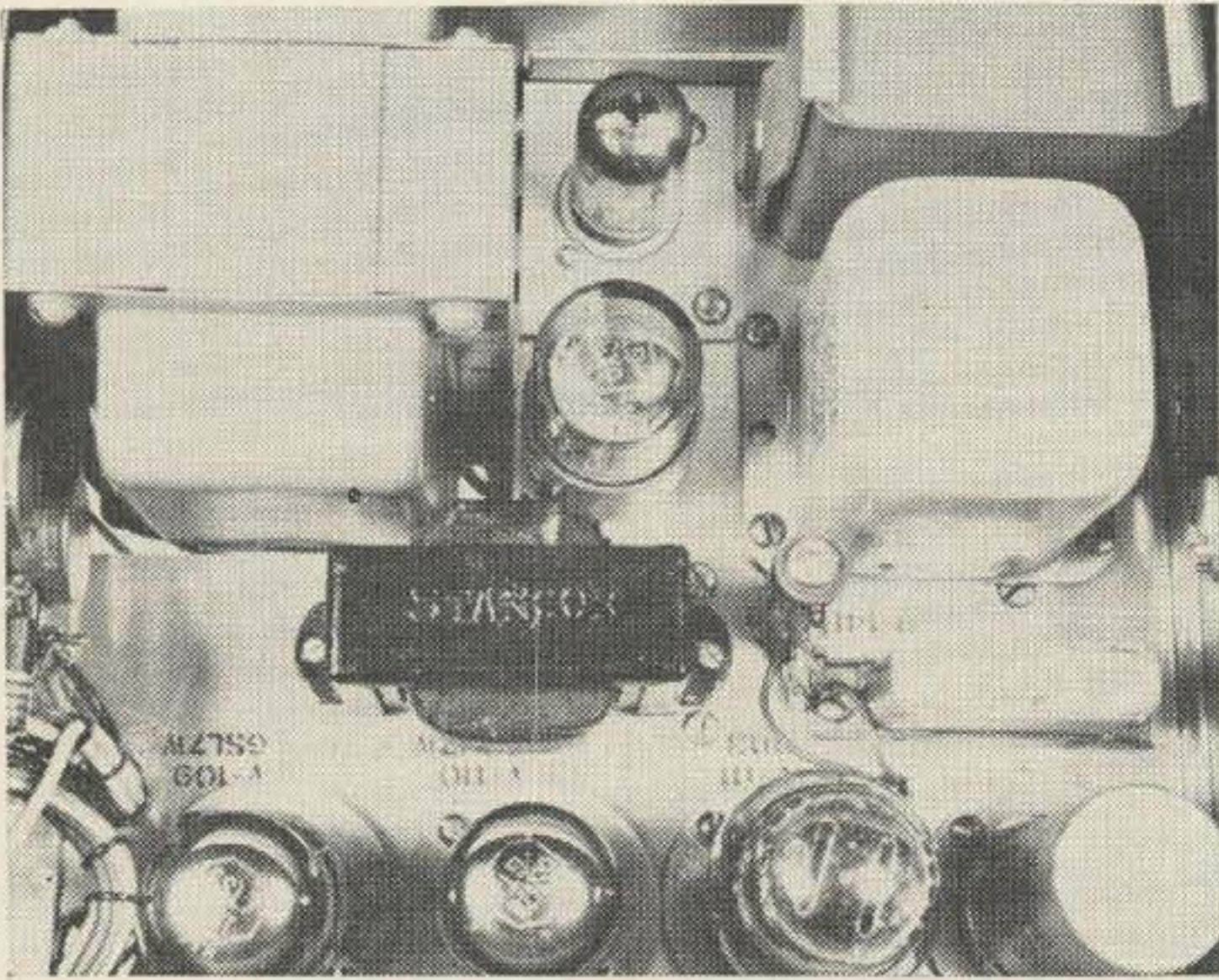

It blanks out the retrace and intensifies the trace whenever a signal deflection takes place.

Conversion Details

The panadaptor power supply is designed for 380-1000 cycles. It will be necessary to replace the power transformer with a 60 cycle oscilloscope power transformer. The one used by the author was a replacement transformer for a Heath 0-11 oscilloscope. See modified schematic diagram. Most transformers do not provide for a 1B3 filament winding. The transformer used in this conversion used a IV3 high voltage rectifier. The author also wished to remove the power connector, name tag, fuse holder, handle and mounting fasteners from the front panel to give the unit a commercial appearance.

Each individual will have ideas that suit his own needs or that utilizes a particular "junk box" part that he wishes to make use of in the conversion of the panadaptor. The steps outlined in the article will serve as a guide to help get started.


A brief reason will be given for the part that was changed or replaced to help in the understanding of the conversion. This will be particularly helpful in the advent of trouble and also help you to determine if the change is unnecessary or fits your particular application.

The unit that was converted by the author was very clearly marked with respect to component identification. Reference to a resistor for example, R125, upon inspection of the unit, is very easy to locate. Hallicrafters did an admirable job when they built this unit for the Air Force.

Conversion Steps

Step 1. Replace power transformer with 60 cycle version. Remove 400 cycle transformer. See schematic diagram for transformer details. The author, in order to mount the transformer he had available, cut a hole in the chassis and mounted the transformer on two small angle brackets.

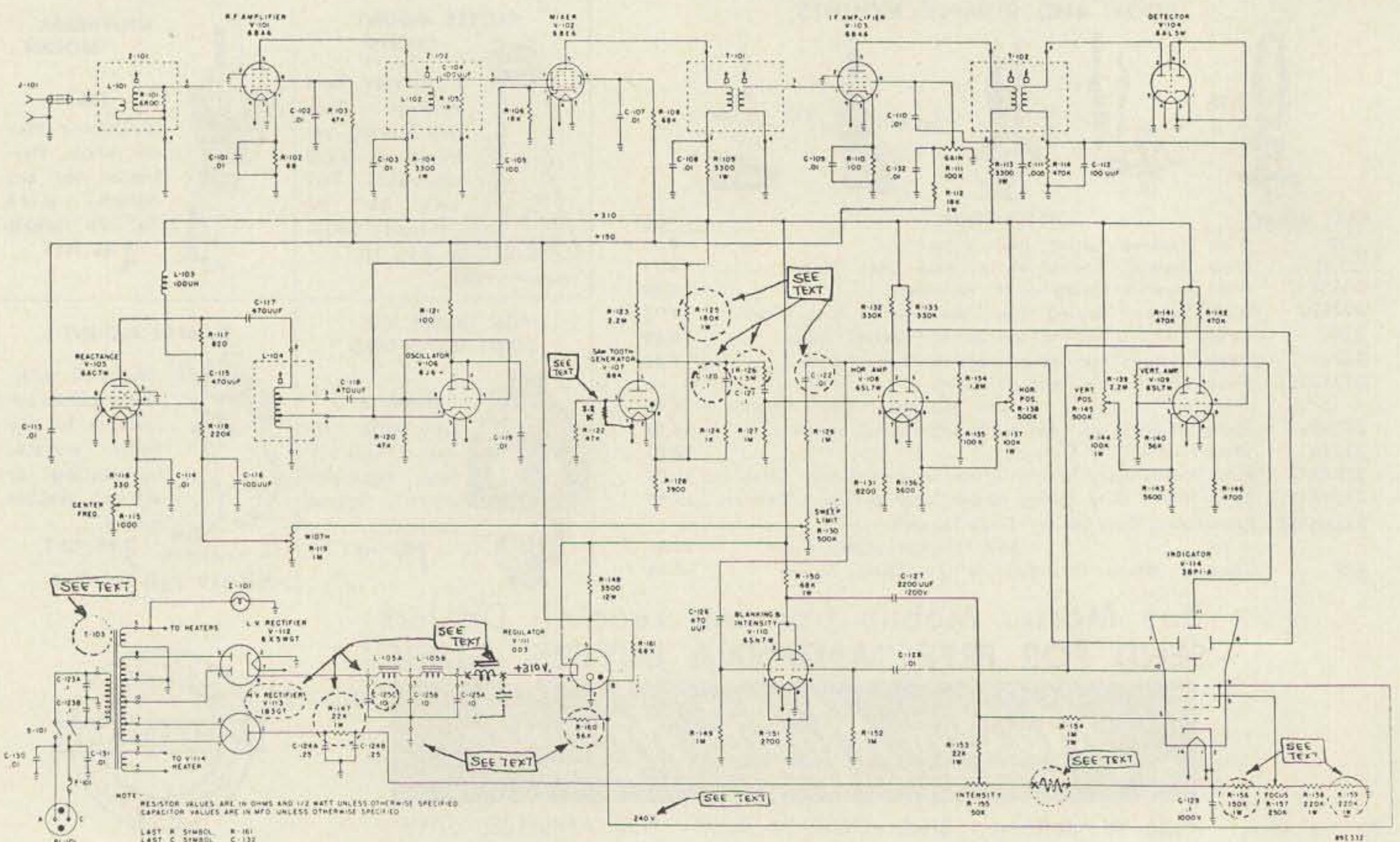Step 2. Replace the 1B3 with a 1V2 tube. This is only necessary if the replacement transformer does not have a 1.25 volt high voltage rectifier filament winding. Most inexpensive oscilloscope transformers have a 0.625



filament winding, and will only operate a IV2 satisfactorily.


Step 3. Replace the following resistors in the high voltage power supply section and accompanying voltage divider circuit. (Note: Throughout the conversion, many of the resistors removed may be used again in the conversion. Therefore treat the leads with respect.) In order to provide the 800 to 1000 volts needed for the high voltage with the ripple component low enough, and still use the high voltage filter capacitors C124A and C124B, it is necessary to:

1. Increase the value of R147 from 22K to 220K 1 watt.

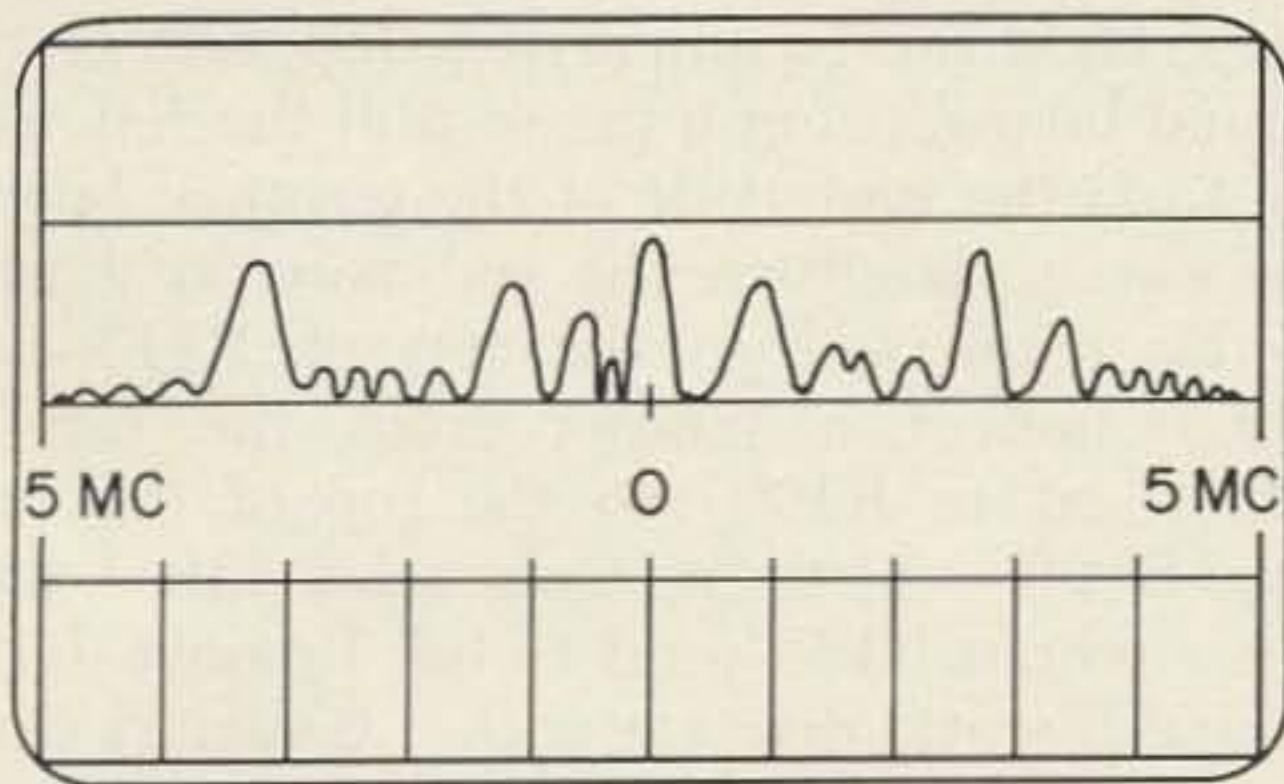2. Increase the value of the high-voltage divider network to limit the current drain.

Remove R159 220K 1 w. Replace with 1.0 meg 1 watt. Remove R147 22K 1 w. Replace with 220 K (use R159). Remove 156 150K 1w. Replace with 680 K 1 watt. Remove yellow wire from R155. Add in series a 22K 1 watt (use R147) between yellow wire and connection of Intensity control. Remove R160 56K ½ w. Replace with 150K (use R156). This improves the astigmatism of the electron beam.

Step 4. In the author's unit, it was found necessary to add a small 8 henry—70 to 100 milliamp choke in series with B-plus. In addi-



LEFT ← CENTER → RIGHT

FIGURE 1

Block diagram less power supply.

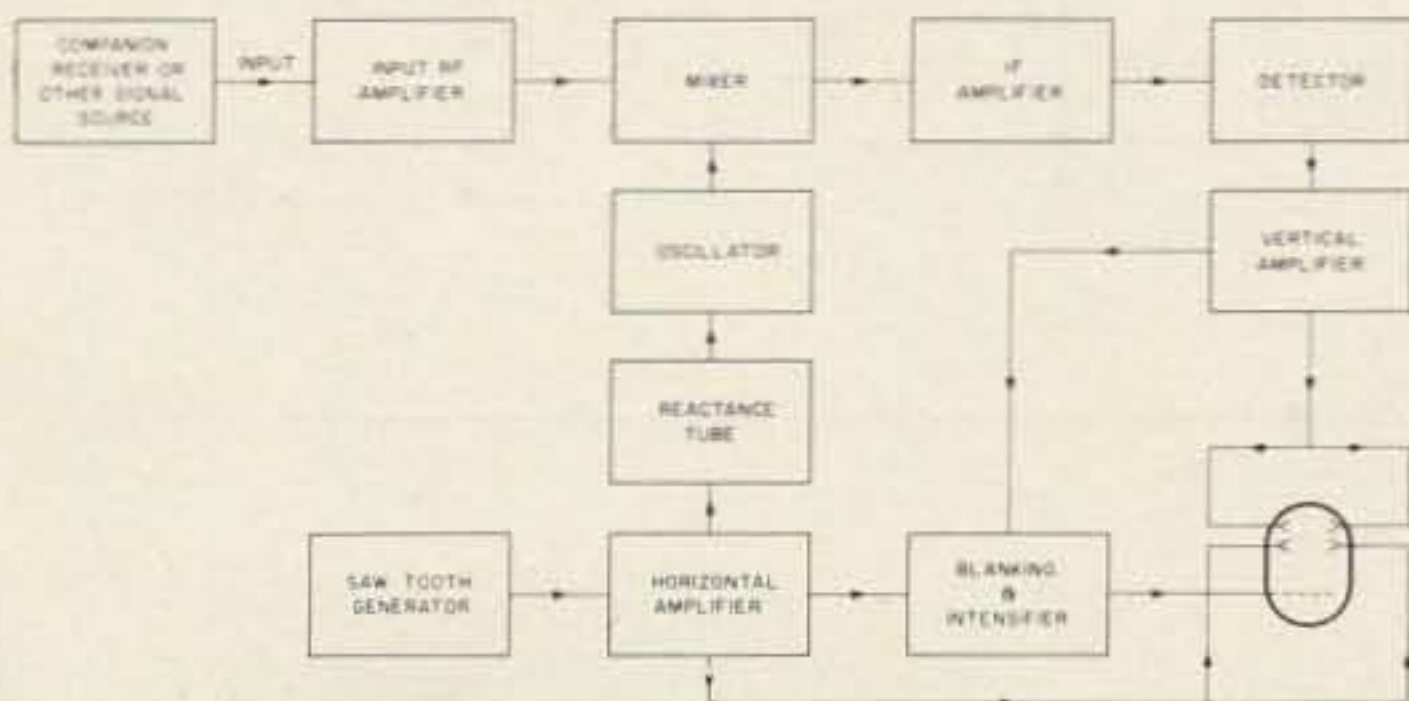


FIGURE 2

Typical display on screen of panadaptor.

ROHN sets the standard

for **CRANK-UP TOWERS**



K7ASK

Why settle for less than the best?

TWO CATEGORIES TO CHOOSE FROM

Standard Duty Guyed in Heights of 37 - 54 - 88 - 105 and 122 feet

Heavy Duty Self Supporting and Guyed in Heights of 37 - 54 feet (SS) 71 - 88 feet (guyed)

ROHN has these 6 IMPORTANT POINTS:

Ease of Operation—roller guides between sections assure easy, safe, friction-free raising and lowering. **Strength**—welded tubular steel sections overlap 3 feet at maximum height for extra sturdiness and strength. Unique ROHN raising procedure **raises all sections together**—uniformly with an equal section overlap at **all heights!** **Versatility**—designed to support the largest antennae with complete safety and assurance **at any height desired!** **Simple Installation**—install it yourself—use either flat base or special tilting base (illustrated above) depending on your needs. **Rated and Tested**—entire line engineered so you can get exactly the **right** size and properly rated tower for **your** antenna. The ROHN line of towers is **complete**. **Zinc Galvanized**—hot dipped galvanizing a standard—not an extra—with all ROHN towers! Prices start at less than \$100.

SEND FOR ROHN TOWER HANDBOOK

—\$1.25 Value

—**ONLY \$100** postpaid (special to readers of this magazine). Nearest source of supply sent on request. Representatives world-wide to serve you. Write today to:



ROHN Manufacturing Co.

P. O. Box 2000

Peoria, Illinois

"World's Largest **EXCLUSIVE** Manufacturer of Towers; designers, engineers, and installers of complete communication tower systems."

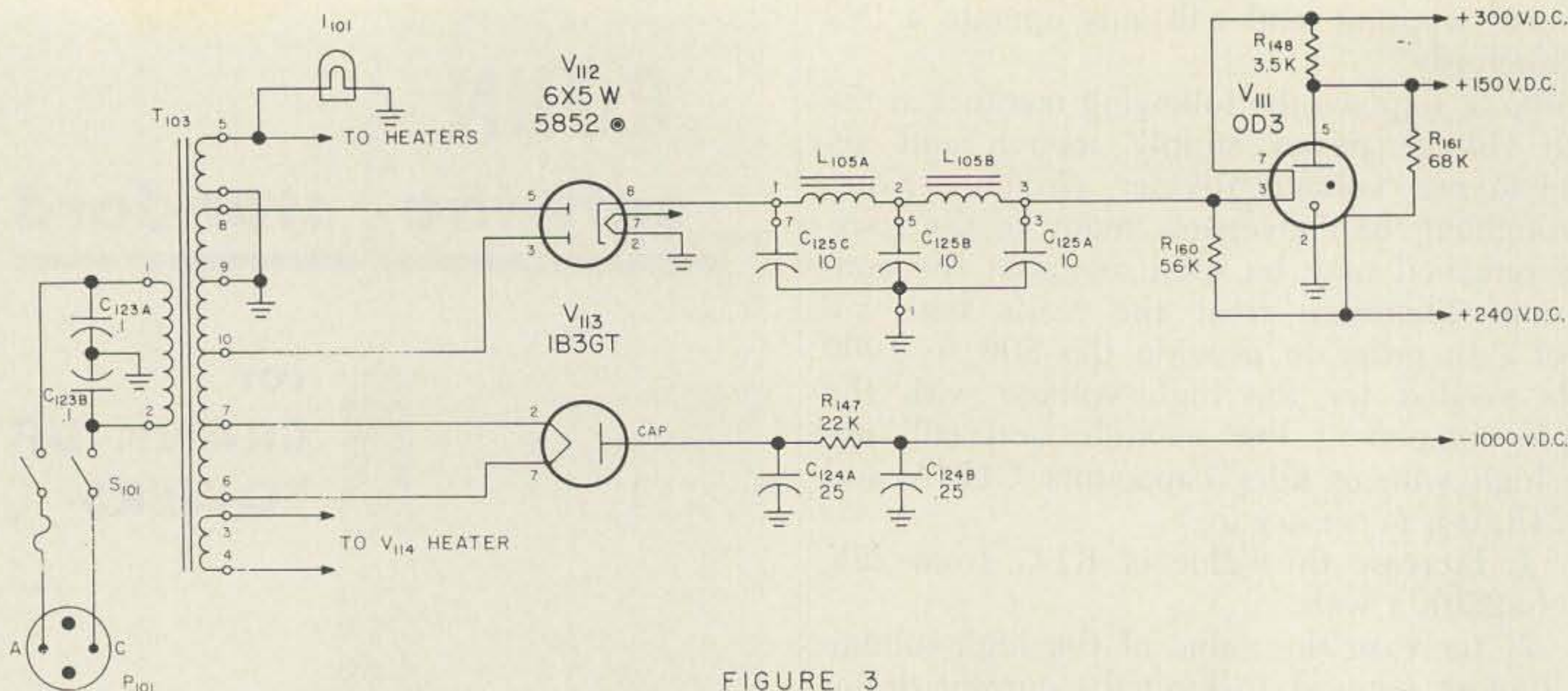


FIGURE 3

Power supply before any changes are made.

tion, B-plus was found to be 350 volts, and needed to be reduced. As opposed to using a series-dropping resistor, choke input to the filter section was chosen. See sketch for this arrangement.

Step 5. The sawtooth generator frequency was original 35 cps. This does not lend itself to 60 cycle operation, because of the beat of the 60 and 120 cycle power supply ripple. Locking of the 884 sawtooth generator to the 60 cycle power line was chosen. The other components in this circuit were changed to improve linearity, amplitude and wave shape. Stability was improved by returning R125 to plus 150 also. It may be necessary to vary R125 from the value used in this article. Capacitor C121 was found to have leakage (0.1 mfd. 400 v) and was producing drift in the horizontal axis.

Connect a 2.2 K ½ watt resistor from pin 5 to pin 7 of the 884 sawtooth generator,

v 107. This locks the oscillator to line frequency. Remove C120 0.1 mfd. Replace with 0.2 mfd. 400 volts. Remove C122 .01 mfd. Replace with 0.1 mfd. (use C120). Added care must be exercised in the next several changes if no errors are to occur. Remove R125 180K 1 watt (a 43K resistor eventually). Remove jumper from top of R113 to top of post where R125 was just removed. A small mirror used to view under the terminal strip will show a red wire (the wire is B-plus that supplies the 310 volt to R113, R109, and R104). Heat the terminal from top side of the terminal board, using a pic to pull the red wire loose from the underside of the terminal board. If necessary, lengthen the red wire so it now may be connected to the top of R113 and R109. Connect a jumper from the top of R121 (next to R109) to the top of the post where R125 used to be. Connect a 43K 1 watt resistor where R125 used to be. Remove R126 1.5 meg ½ watt. Replace with 1.0 meg ½ watt.

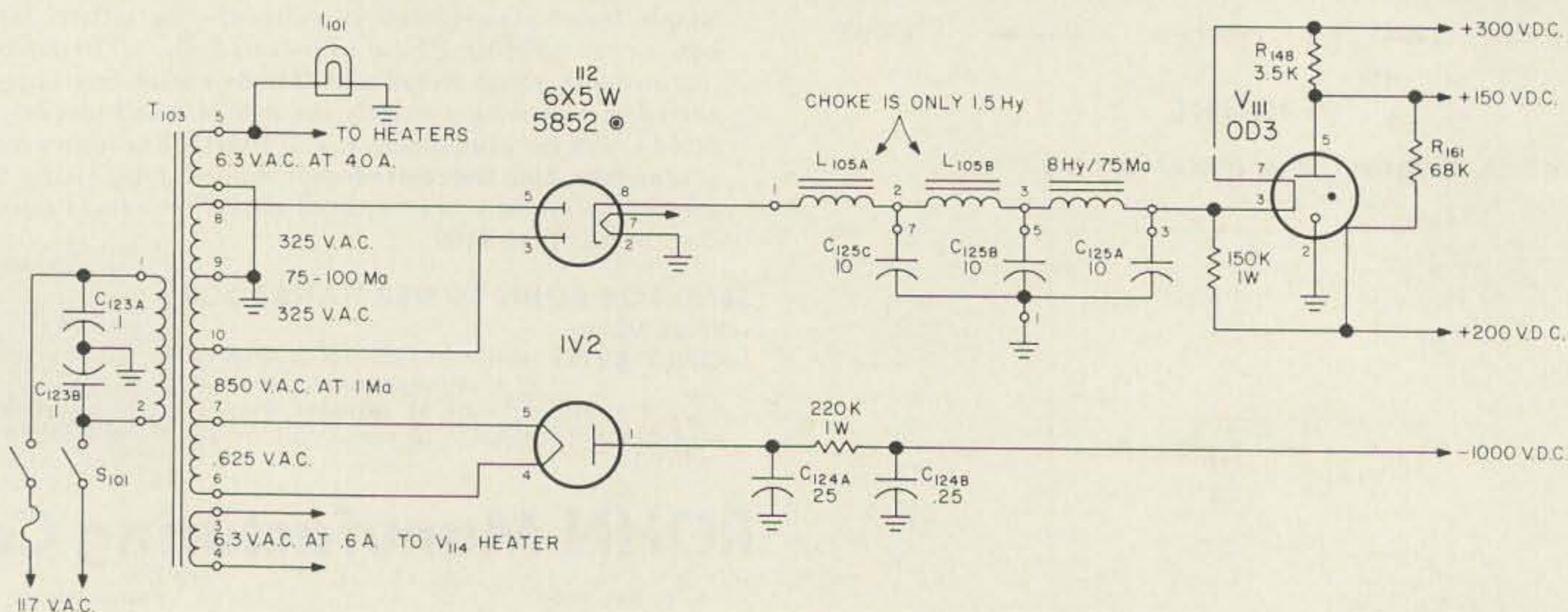


FIGURE 4

Power supply after changes are made. Note T-103 has been replaced with 60 cycle unit (see text).

TRANSMITTER, RECEIVER AND POWER SUPPLY ALL IN ONE HANDY PACKAGE!



GONSET G-50 6 METER Fixed Station COMMUNICATOR

Here's another great GONSET concept in amateur radio communications: Model G-50 with 48 watt transmitter with VFO, ultra-sensitive dual conversion receiver and power supply in a "package" less than one cubic foot! Frequency coverage: 50-54 mcs. Simply connect antenna, microphone and 115 v. AC power and enjoy a new, exciting communications experience in 6-meter DX.

TRANSMITTER: Simple, uncomplicated in operation and adjustment • Husky 48 watt input transmitter uses Type 6146 tube, has pi network output • Modulated by a pair of 6L6GC's • Multiplier stages ganged and tracked with highly stable, calibrated VFO or optional crystal • VFO spotting switch facilitates "zeroing in" on desired stations • Panel meter switchable to read amplifier grid or plate currents or modulator plate current • Built-in low pass filter attenuates transmitter harmonics, spurious emissions above 65 mcs by 80 db or more.

RECEIVER: Contains RF stage for low-signal-to-noise ratio and ultra-high sensitivity • Dual conversion provides excellent image rejection and 7 kcs selectivity • Adjustable squelch • Super-sensitive noise limiter, "S" meter, panel mounted loudspeaker • Calibrated "Full-Vision" dial with planetary vernier for smooth, easy tuning.

POWER SUPPLY: Heavy duty 115 v. AC power supply.

DIMENSIONS: 7½" h., 13" w., 12½" d.; wt. 29 lbs. Finished in attractive Light Gray.

PRICE: \$367.30 Amateur Net; CD Model 3300: \$389.95.

For complete information, visit your Gonset Distributor or write Dept. 73-6



© ALC 1964

GONSET, INC.

ALTEC LANSING CORPORATION

A Subsidiary of Ling-Temco-Vought, Inc.

1515 S. MANCHESTER AVENUE, ANAHEIM, CALIFORNIA

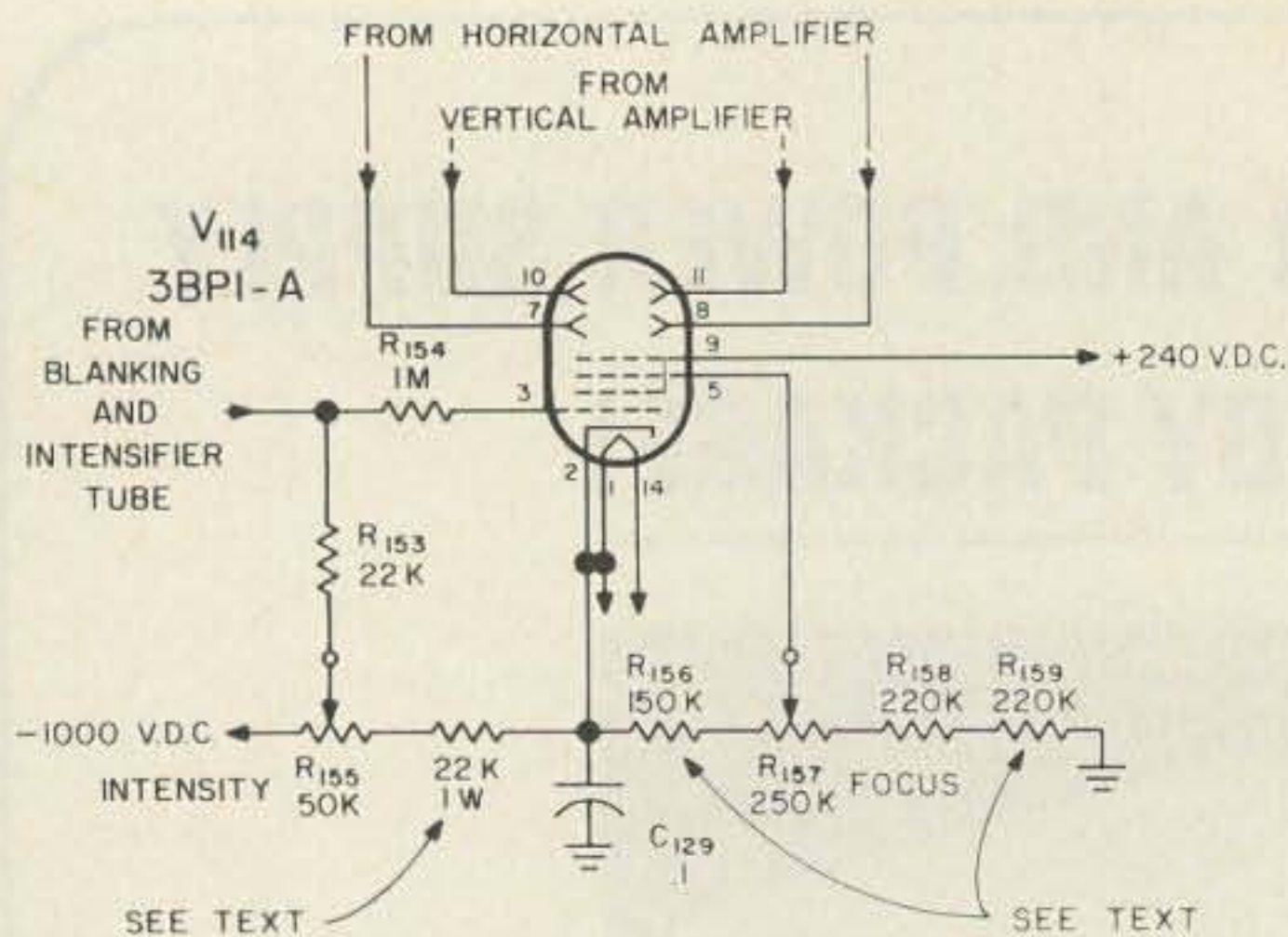


FIGURE 5

Only three resistor changes are required to high voltage divider network.

Step 6. Depending on just what vintage of ALA-2 that you have, you will note some production runs have the fuse holder on the front panel, some have fuse holders mounted inside the unit. The unit described in this article had internal fuse holder clips. They were removed, a fuse holder installed in the rear of the unit, and the ac power cord inserted through a grommet just below the fuse holder. The case was then modified to allow the fuse holder and the power cord with molded plug to freely allow casing and uncasing.

Step 7. Having made the necessary preliminary conversion steps, it is advisable to see if the unit will operate on 60 cycles satisfactorily. The *intensity* should control the brightness of the trace; the *focus* should be able to focus the trace. The *vertical* and *horizontal* controls should be able to position the trace. Before attempting any additional changes, the beam must be operating correctly. Observe if the VR-150 is glowing. Next measure the plus 300 volts dc. Measure the plus 150 volts dc. Do not proceed until these voltages are correct. Carefully measure the CRT high voltage. This should be approximately a negative 850 to 1100 volts. If the high voltage is accidentally shorted to ground, the 1V2 rectifier tube will most probably be permanently damaged. With a low voltage B-plus of 300 volts, the measured current was found to be 75 ma.

Step 8. To test the rf section, connect or couple either an rf signal generator or a grid-dip meter to the *input* connector. Set the *gain*, *sweep limit*, and *sweep width* controls full clockwise position. As the signal generator is tuned from 25 to 35 mcs, a "pip" should roll across the face of CRT. It may be necessary to reduce the level of the signal to keep the pip on the face of the CRT. Set the signal

generator to 30 mcs and adjust the *center freq.* control to position the pip to the center of the screen. If this can be accomplished, then the unit is operating as it was intended to operate.

Applications

To display the VHF or UHF ham bands, a narrow-band panadaptor that is very adequate on the lower frequencies (below 10 meters) will not be adequate for a band like 420-450 mcs. Once the user realizes that the need to tune back-and-forth across several megacycles of VHF-UHF band is no longer necessary, the broad-band panadaptor soon becomes a valued piece of equipment to the ham shack.

After a CQ is called, one merely looks at the display on the panadaptor sees a "pip" rise on the screen, and tunes to that frequency to find out if that station is returning to his "CQ."

Often "CQ's" are missed because they are not observed soon enough. While reading the the mail, one may monitor the rest of the band, ready to take action when a station "appears."

This unit is used with broad band converters having an *if* range of either 26 to 30mcs or 30 to 34mcs. It could be modified for VHF converters with different *if* ranges. A check of the entire band may be made any time, because the signal fed to the panadaptor is from the broad-band crystal controlled VHF-UHF converter. In the case of panadaptors used normally for low frequency operation, the signal is fed to the panadaptor from the *if* output of the receiver and only about 250 kc can be observed. As the receiver is tuned, the signals roll by. Only those signals tuned in the pass-band can be observed.

... W8DMR

Hams in the News

NEW YORK. Charles Green, of Clayton, N. J. got an emergency call from Recife, Brazil for a special drug for leukemia. In a short while Green had cut through a lot of red tape and the drug was on the way by air to Brazil. HOUSTON. Rancher P. C. Coates suffered a heart attack and called for help on his ham rig. Two hams, 500 miles away in Houston, heard the call and gave instructions from a local doctor over the air and got an ambulance to the home. Coates is recovering.



Hallicrafters
SR-160
SSB Tranceiver
\$349.95 !!

Order with confidence
 from Henry, get best
 terms and trades and
 our **FAMOUS**

**Personal
 Service!**

see page 24
 for article
 on this rig.

11240 West Olympic Blvd.
 Los Angeles 64
 Ph. (213) BR 2-0861, GR 7-6701



Henry Radio Stores

Butler 1, Missouri ORchard 9-3127
 931 N. Euclid Ave.,
 Anaheim, Calif.
 PR 2-9200

Using the Telechrome 1462-A1 on 220

Leroy May W5AJG
 9428 Hobart St.
 Dallas 18, Texas

Photo credit: Jim Dungan, Dallas

The Telechrome Model 1462-A1 transmitter is a miniature unit capable of supplying at least 50 watts of rf power into a 50 ohm load, over the telemetry frequency range from 215 mc to 235 mc. The modulation is FM/FM and the deviation sensitivity is such that a 2 volt peak voltage will produce a swing of ± 125 kc. The transmitter is self-contained, except for the necessary power supply. A filter box, including filters for each power input lead, is included to minimize rf leakage from the input power leads.

The model 1462-A1 is readily adaptable to standard rack-panel mounting and an opening in the unit admits power, cooling air and the

modulating signals, with an air seal to prevent air leakage.

Although this unit is capable of FM modulation as is, the application at this station was to be an AM driver for a final using a 4X150A tube as a class "C" modulated amplifier. In such service as this, a total of only 10 or 15 watts rf output were required. However, should one use this little box as a complete AM phone transmitter in itself, with an output of 50 watts rf, on 220 mc, a modulator of about 75 watts audio would be necessary.

The circuit contains a frequency modulated crystal oscillator operating at 1/6 the output frequency, and originally used crystals in the range from 35.53 to 39.17 mc. In order to cover the 220-225 mc band then, the crystal used would have to be between 36.6 and 37.5 mc, and the FM generating portion of the circuitry would be disabled or eliminated, so that the output from the 1462-A1 would be AM instead of FM.

Since crystals of this range are rather hard to come by, except by hard cash, an alternative arrangement was rigged up in the form of a crystal oscillator-tripler box, mounted external to the 1462-A1, and working into it with a short lead. This scheme will allow the use of common 8 mc rocks, the necessary actual

frequencies being 8148 kc to 8333 kc, to cover the band. Also this new crystal oscillator will be much more stable than the original FM crystal circuit of 36 mc. Should FM be desired at a later date, the unit may easily be put back to its original state.

Power requirements for the full 50 watts of 220 mc rf output will require a plate supply of 500v dc at 300 ma for the final tubes, which are a couple of 2C39A's, and a supply of 300v dc at 100 ma will be necessary for the exciter stages. 6.3v ac at 3.5 amps will be required for the heaters of all the tubes.

Modifications

Refer to the photograph of the unit. The external minibox can be seen mounted to the right of the 1462-A1 transmitter. Closer inspection will show the crystal-tripler excitation lead into the main box from the minibox. Now refer to the two schematics. An original unmodified schematic is shown in Fig. 1. In Fig. 2, are shown the modifications to be performed.

The rundown on the original schematic shows V-101 as a modulator-driver. This tube is not used and may be removed. V-102 was originally the crystal oscillator-tripler. This tube will remain a tripler, but the crystal

oscillator function will be performed by the external box oscillator-tripler just described. The diode modulator associated with this stage is disconnected and/or removed. V-103 was originally a doubler. Its operation will become that of a tripler, and no changes are necessary to do this. V-104 and V-105 will remain as is—buffer and driver—as well as the final two tubes, V-107, V-108, performing the function of a straight through amplifier.

In the modification then, we will have the following line up;

New tube 6BH6 as an 8 mc crystal stage (actually 8155 kc for operation on 220.185—the desired frequency)

New tube 5763 as a tripler to 24.46 mc. The above two tubes to be contained in the external minibox.

V-102 as a tripler from 24.46 to 73.35 mc. V-103 as a tripler from 73.35 to 220.185 mc.

V-104, 105, 106, 107 and V-108, as original with no changes.

The multiplication is now 27 times, instead of the original 6 times.

The 8 mc crystal oscillator plate supply is derived from dropping resistors in the common 300 volt line and this is further stabilized by a couple of OB2 gas regulators in series, as shown. The 5763 tripler plate coil, which is to be resonant at 24.46 mc, is a slug-tuned unit, one-half inch in diameter, close wound with 16 turns of no. 20 enamelled wire. A short lead of two-inches is then brought out of the minibox and a hole is drilled in the 1462-A1 adjacent to the original crystal socket. This provides coupling between the two units. Pin jacks are used here.

Rearrange the circuitry of the former crystal oscillator-tripler stage V-102, as per Fig. 2, and insert the 24.46 mc excitation from the minibox into the hot pin of the crystal socket of V-102. The plate coil of this stage, formerly resonant from 106 to 117 mc, is now padded with a 12 mmfd fixed high-quality capacitor to make the coil resonant at 73.35 mc. From this point on, throughout the rest of the transmitter, everything is normal and unchanged. All coils may be grid-dipped to their respective frequencies and peaked for maximum after the unit is fired up. A small blower will be necessary to cool the 2C39A's when running maximum power. This may be conveniently mounted behind the rack panel.

Operation

Using a watt meter rated good at 220 mc on the output of the transmitter, all tuning

AM26/AIC AUDIO AMPLIFIER: \$1.50

Four tube unit in good condition with 28 volt dynamotor. Described in Surplus Conversion Manual with conversion to 9 watt amplifier. Send for catalog of additional items. Amplifiers: F.O.B. Dallas; wt. 8 lbs., or include postage.

J. R. TUCKER, Box 206, Garland, Texas

CONVERTER SALE

New model series 300 with 3 VHF transistors, crystal, and more than 30 high quality parts. Carefully assembled and tested. Measures only 3" x 2 1/4" x 2". Low noise and better than 1 microvolt sensitivity. Made in USA and guaranteed. Available in the following models for 12 volts DC:


Model	Input mc.	Output mc.	Price
300-A	26.965-27.255	1.0-1.255	\$10.95 ppd.
300-B	50-51	.6-1.6	\$10.95 ppd.
300-C	50-54	14-18	\$10.95 ppd.
300-D	144-148	50-54	\$12.95 ppd.
300-E	144-145	.6-1.6	\$12.95 ppd.
300-F	144-146	28-30	\$12.95 ppd.
300-G	14.0-14.35	1.0-1.35	\$10.95 ppd.
300-H	5.0 (WWV)	1.0	\$10.95 ppd.
300-X	Choice of 1 input freq & one output freq between .6 & 160 mc		\$14.95 ppd.

Note: All above converters have a tuned R.F. Stage.

Order now while prices are still low.

All above converters are supplied with Motorola type connectors. For two SO-239 connectors instead, add 75c. N.Y.C. residents add 4% sales tax.

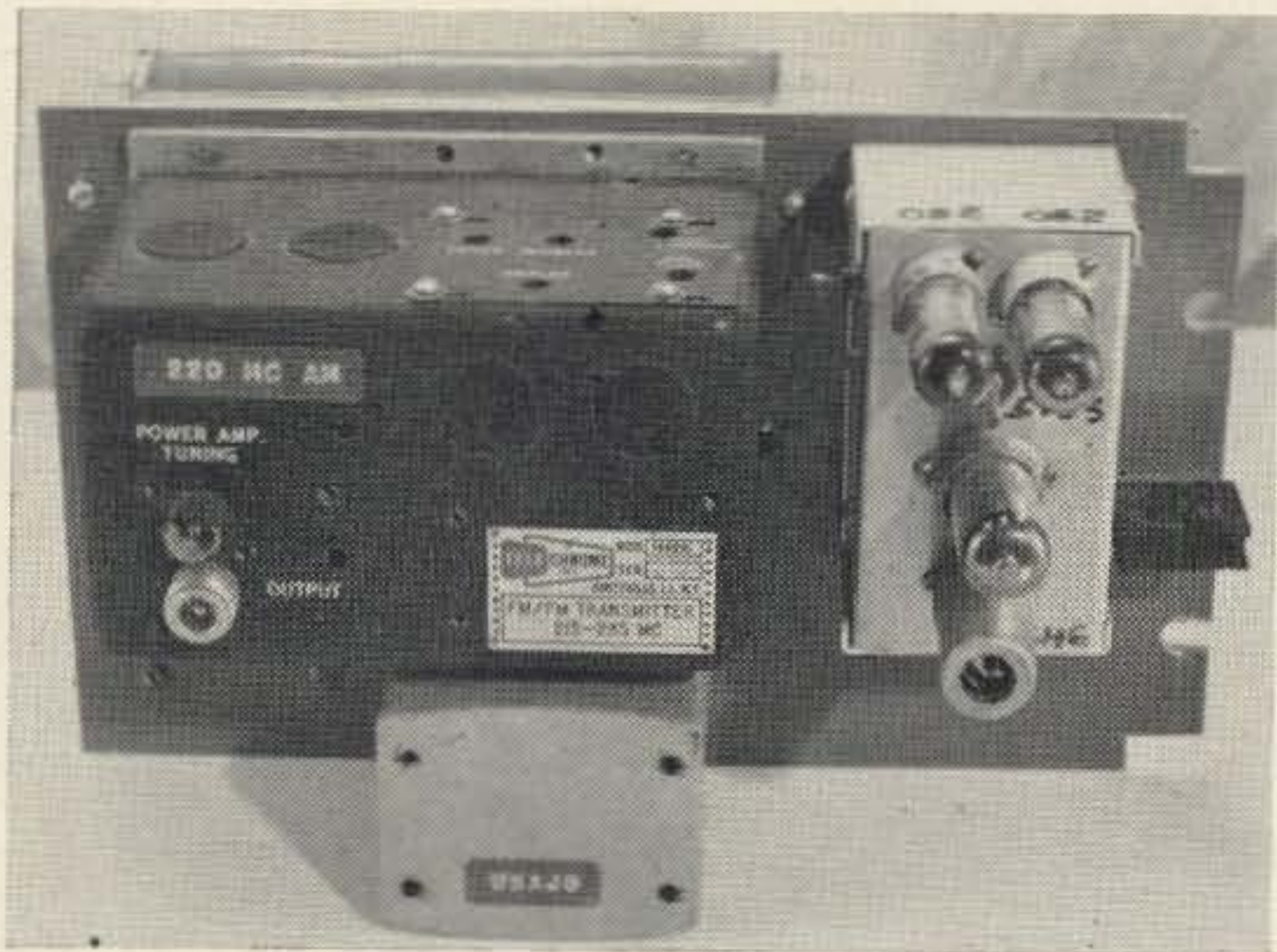VANGUARD ELECTRONICS LABS Dept. H-6
190-48-99th Ave. **Hollis 23, N. Y.**



Front Panel View of the Telechrome 1462-A1 Transmitter.

Minibox at the right of the transmitter contains the 8 Mc xtal stage and the 24 Mc tripler stage. Voltage regulator tubes at top of box.

Short lead couples the 24 Mc component into the Telechrome transmitter at the 24 mc point, which is the former crystal socket. The transformer mounted below the 1462-A1 is a 6.3v ac filament transformer. Tuning controls are on top and on the front of the 1462-A1.

slugs and capacitors should be peaked for maximum output. The input to the final 2C39A tubes will run about 150 watts fully loaded, and at this input, something over 50 watts rf output will result. A properly rated modulator may be inserted into the 500 volt line to the final stage for high level modulation. While this may not be the very best way to modulate a grounded-grid stage, it does work satisfactorily. Should the unit be used as an AM driver for a larger 220 mc final amplifier, as is used at this station, the plate voltage on the 2C39A's may be reduced down to that necessary for the proper rf output. For example, using only 250v dc and drawing a current of 150 ma (37.5 watts dc input) an output of 15 watts is produced. This drives a modified surplus TRA-19 final to 200 watts input, and with an efficiency of 50%, will represent 100 watts rf output into the transmission line. The 1462-A1 unit of course, with its capability of 50 watts plus output, will most certainly drive anything in the way of a 1kw, 220 mc

TRANSTENNA 102A

A PRESELECTOR SECOND TO NONE AND A T-R SWITCH BEYOND COMPARISON

Pat. Pndg. U.S.A. & Canada

MODEL 102A

\$69.45 (Add \$7 for Sidetone — either model)
15 DAY TRIAL

Return For Full Refund If You Burn It Out Or Are Not **FULLY PLEASED**

- Std. coax coupler (xmtr to feedline)
- No TVI or Suck out
- 30 DB Min. Gain (10-80 mtrs)
- No Effect on Transmission
- Monitored switching
- Full Legal Input
- Burnout Proof
- CW Sidetone (optional)

Write for Free Literature

FICHTER ELECTRONICS
33 Myrtle Avenue
Cedar Grove, N. J.
Tel: CEnter 9-6412

Improved 102A Adjustable Mute Circuit Breaks Any Xmtr-Rcvr Between Dots & Dashes Without Clicks. Improved Semi-conductor Through-Position Switch Switches Rcvr Directly to Antenna for Unity Gain 6-80 Mtrs.

102B, \$59.00 like 102A exc. rcvr. muting

NEW — BEAUTIFUL — DISTINCTIVE

PINS • PLATES

ON YOUR HAM-SHACK-YOUR RIG-AT YOUR DOOR



8" X 2"

DESK-STAND SIGNS ON FIRM WOOD STAND in choice of WALNUT or MAHOGANY grain finish with sharp white letters BLACK WITH WHITE LETTERS

Made of finest Laminated Plastic — Permanently engraved with Name, Call-Letters, or both. Stain-proof — weather-resistant — non-corroding — washable — no paint used.

1 line — \$2.50 —

2 lines — \$3.00 —

SEND CASH, CHECK OR MONEY ORDER TO:

M & M ENGRAVING

P.O. BOX 2143 CULVER CITY, CALIF.

WANT TO BUY! KLEINSCHMIDT TT-76 or TT-76A TAPE GEAR

CASH DEAL

Write or phone immediately

BEN WOODRUFF W9UE

Phone: IN 3-3561 (312)

6140 N. Hardng, Chicago, Illinois, 60645

TV CAMERA

We have the lowest prices and complete stock of all components for making your own Ham TV or closed circuit TV camera plus exclusive VANGUARD printed circuits and incredibly low prices on F1.9 lens with focusing mounts. Complete ready-to-operate cameras also available at the lowest prices you'll ever find.

For more information, price list, and photos, send 10c coin or stamps.

VANGUARD ELECTRONIC LABS Dept. H-6
190-48—99th Ave. Hollis, N. Y. 11423

TELREX ROTATOR-INDICATOR SYSTEM MODEL TS238-RIS

Mast Feeds Thru Rotator For Safe, Easier, Installation

- 1300 IN./LBS ROTATION TORQUE
- SELF LOCKING BY STURDY WORM GEARS
- SELSYN AZIMUTH INDICATION
- ACCOMMODATES 2" O.D. MASTING
- MALLEABLE CAST MASTING CLAMP SUPPLIED
- OUTPUT SPEED APPROX. 1 RPM
- WILL FIT INTO OR ONTO A 6" SIDED TOWER

Write for FREE PL64 Describing Rotators and Antennas ASBURY PARK, N.J.

A Really Sturdy
ROTATOR-INDICATOR SYSTEM —
NOT a Modified TV Rotator!
Designed To
Out-Perform, Outlast!

\$238.00 F.O.B.

ALSO:

TB278-RIS \$278.00
TS345-RIS \$345.00
TS435-RIS \$435.00
TS535-RIS \$535.00

TELREX LABS.



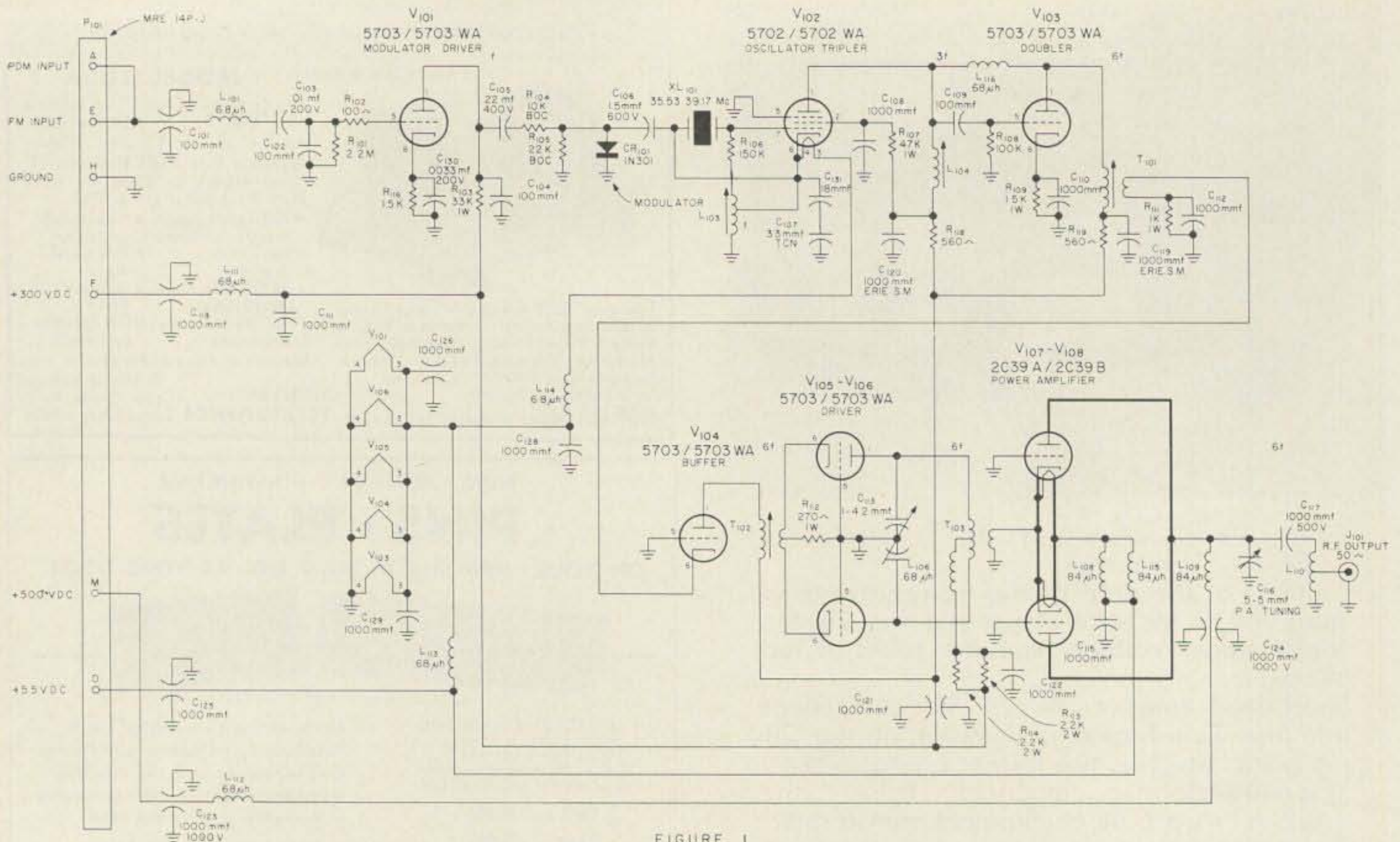


FIGURE 1


final, if desired.

Units such as the 1462-A1 are gradually becoming more available as time passes—actually they are more or less obsolete in telemetry applications, and by regulations, the telemetry business will gradually vacate the

216 mc region during the next few years, moving to much higher frequencies.

This sort of a situation should make quite a few interesting equipments available for 220 mc ham operations.

... W5AJG

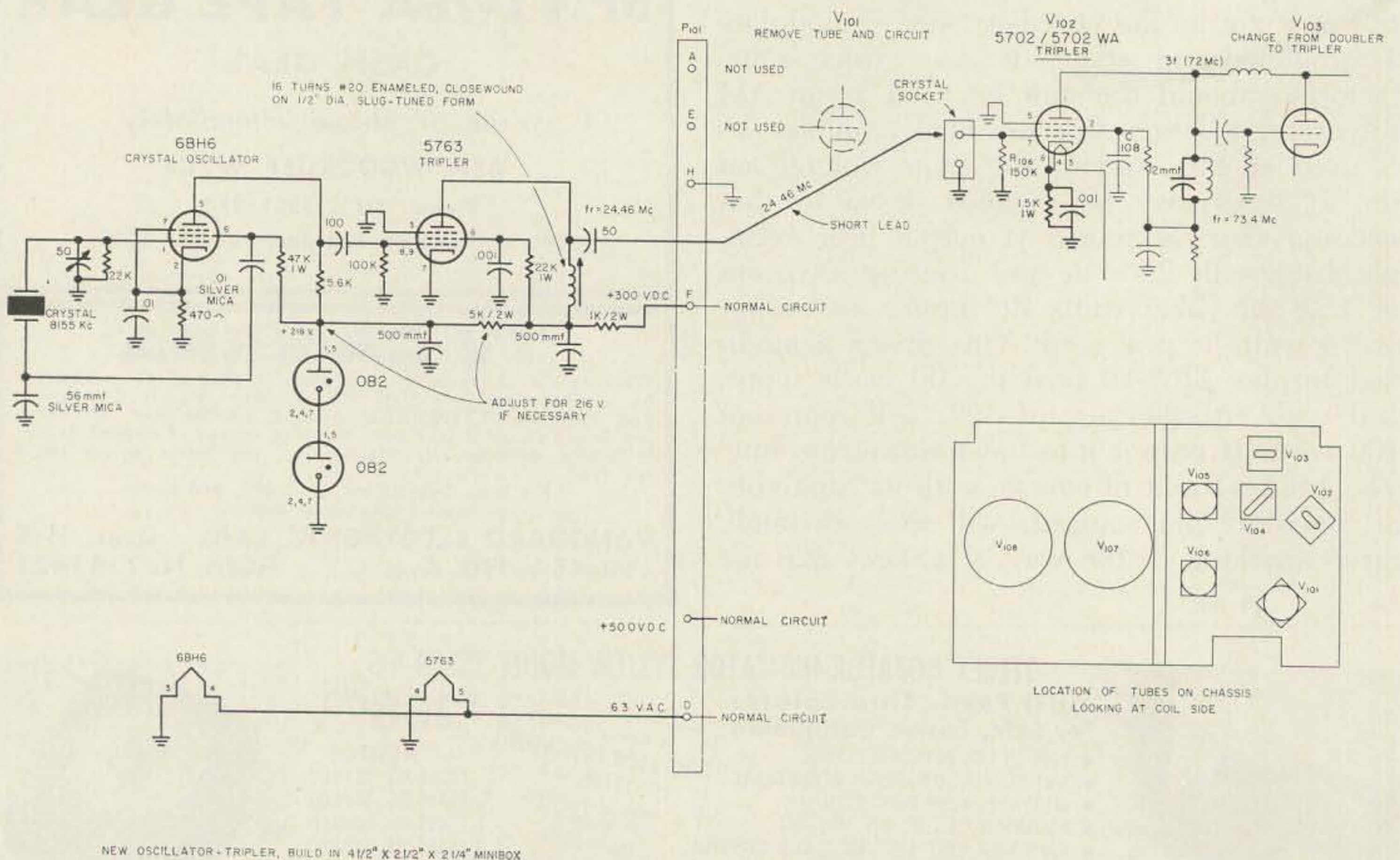

NEW OSCILLATOR+TRIPLER, BUILD IN 4 1/2" X 2 1/2" X 2 1/4" MINIBOX

FIGURE 2
Changes in heavy lines


EVERYONE'S

using the

"CENTURY"

DESIGN CONVERTERS

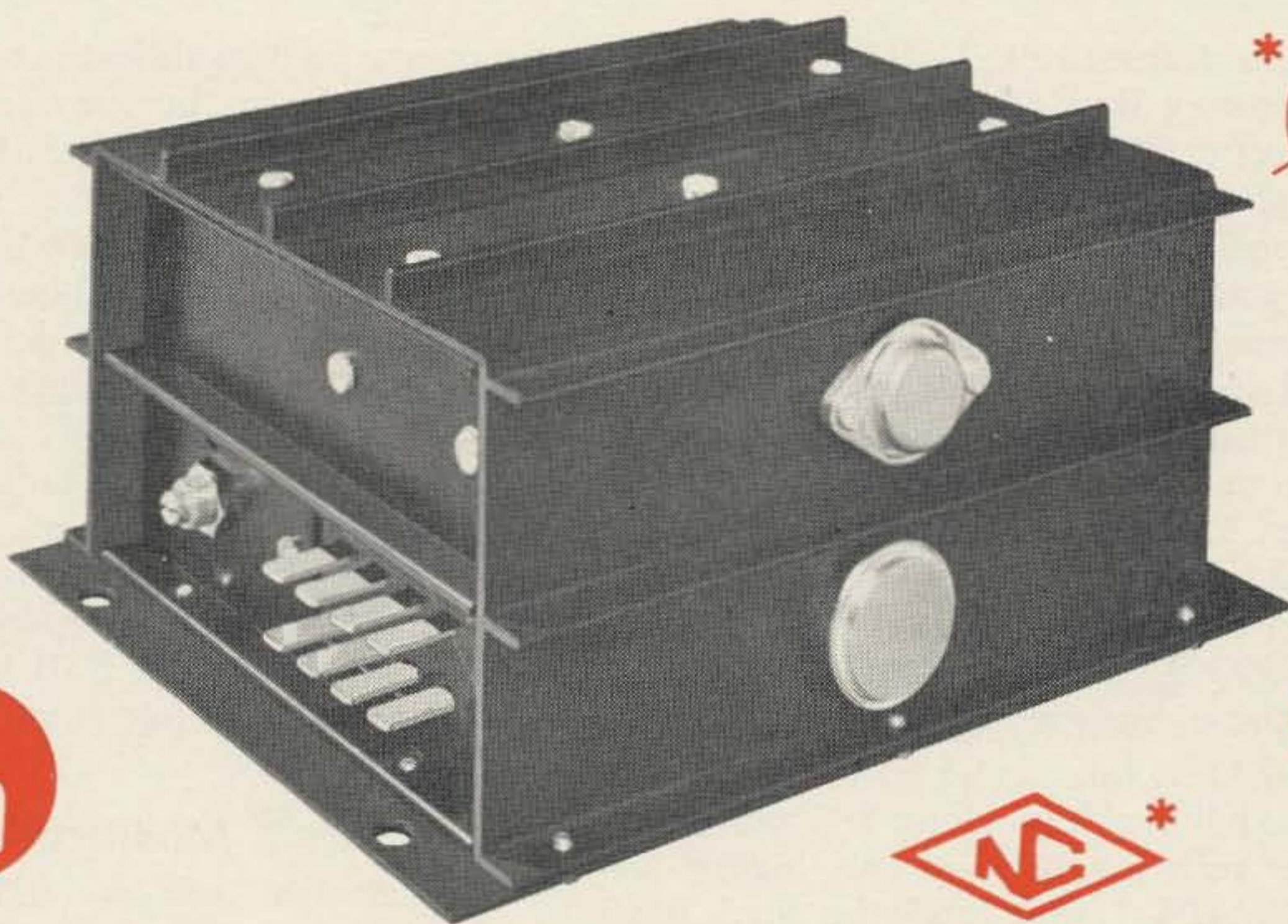(AND INVERTERS) MANUFACTURED EXCLUSIVELY BY LINEAR SYSTEMS, INC.



CUSTOM DESIGN FOR ANY APPLICATION

**the best supply
money can buy**

The
"CENTURY"

is providing the
ultimate in performance
when powering these
fine transceivers in
mobile service.

AVAILABLE THROUGH YOUR
DEALER OR WRITE FOR
FURTHER INFORMATION

605 UNIVERSITY AVENUE
LOS GATOS, CALIFORNIA



**LINEAR
SYSTEMS INC.**

2 Meter AM & SSB Transmitters from the T-28/APT-1

Leroy May W5AJG
9428 Hobart St.
Dallas 18, Texas

Photo credit: Jim Dungan, Dallas

The surplus transmitter T-28/APT-1 is another in a series of Radar Jamming units which were used during WW-II to cover a wide range of VHF-UHF frequencies. It covers the frequency range from approximately 90-220 mc. Since this excursion crosses the 144 mc amateur assignment, approximately the same techniques used in the conversion of the ARQ-8, elsewhere in this issue, may be used to convert one of these units into a 2 meter AM transmitter or driver. Likewise, a second T-28/APT-1 may be used to convert into an SSB transmitter or exciter, in the manner of the two previously described ARQ-8, 50 mc units. Only the rf sections of these equipments are used.

Roller coil inductors (rollo coils) in contact with small wheels riding along the individual turns of the coils are used in this higher frequency T-28/APT-1 unit, and the final stage may again employ either a type 832A tube or an 829B tube, according to the power output desired. Most of the T-28/APT-1 transmitters came equipped with the 832A type installed in the final tube socket.



Fig. 1 shows the original wire traced schematic circuit of the T-28/APT-1. Fig. 2 shows the AM modification—and Fig. 3 covers the

necessary SSB modifications. Since most of the details given in the previous article, concerning 50 mc, will also apply to the present conversions on 144 mc, it is recommended that you read it before starting these alterations. On these two modified schematic diagrams, the original components are left unmarked, while the added or changed parts are so indicated with their new values.

Power outputs of the units will be somewhat similar to the 50 mc versions, that is, the AM transmitter will produce from 18 to 50 watts carrier power output, depending upon the final tube used, while the SSB transmitter PEP input can be anything from about 35 watts to 150 watts.

Modifications

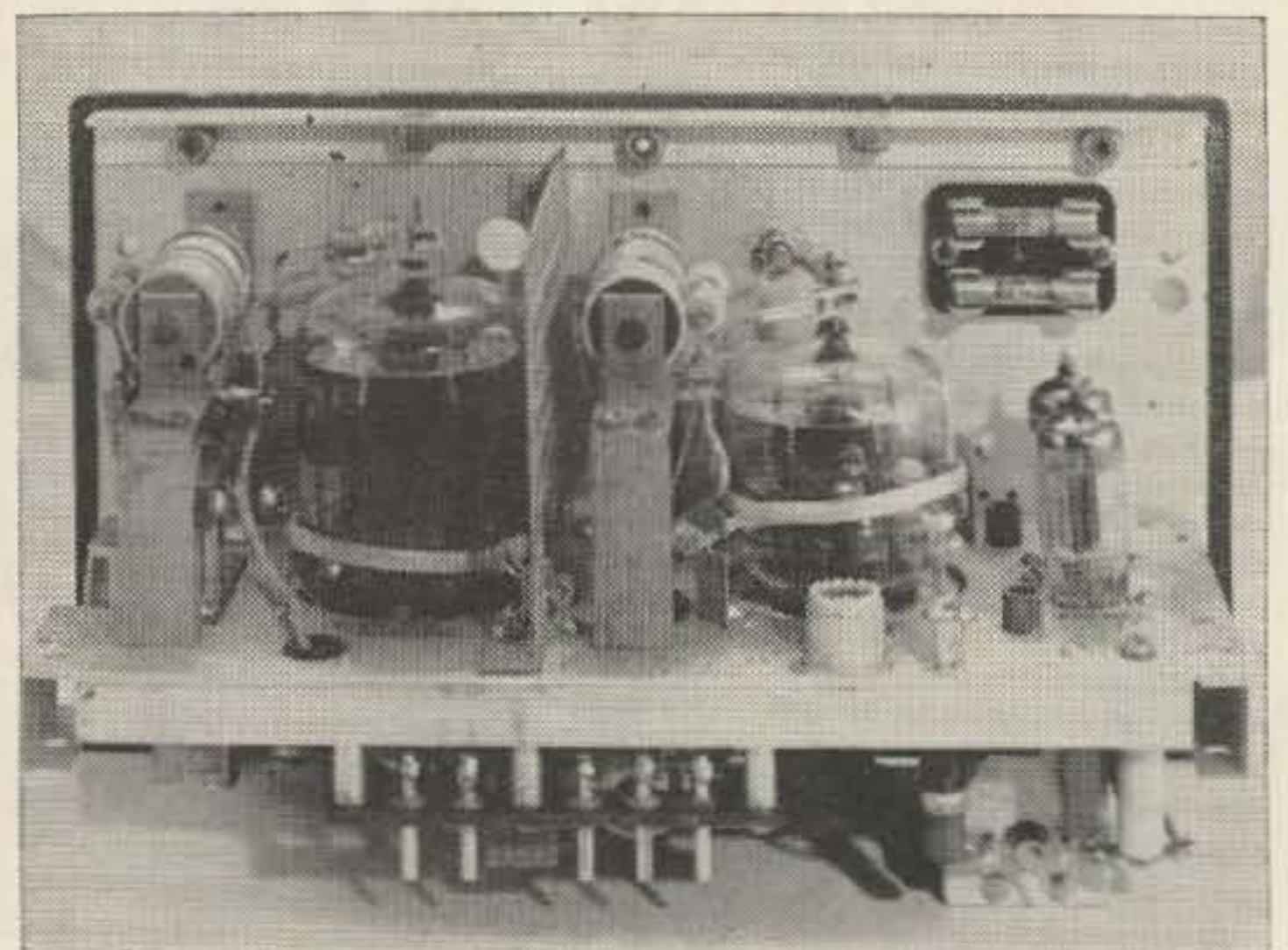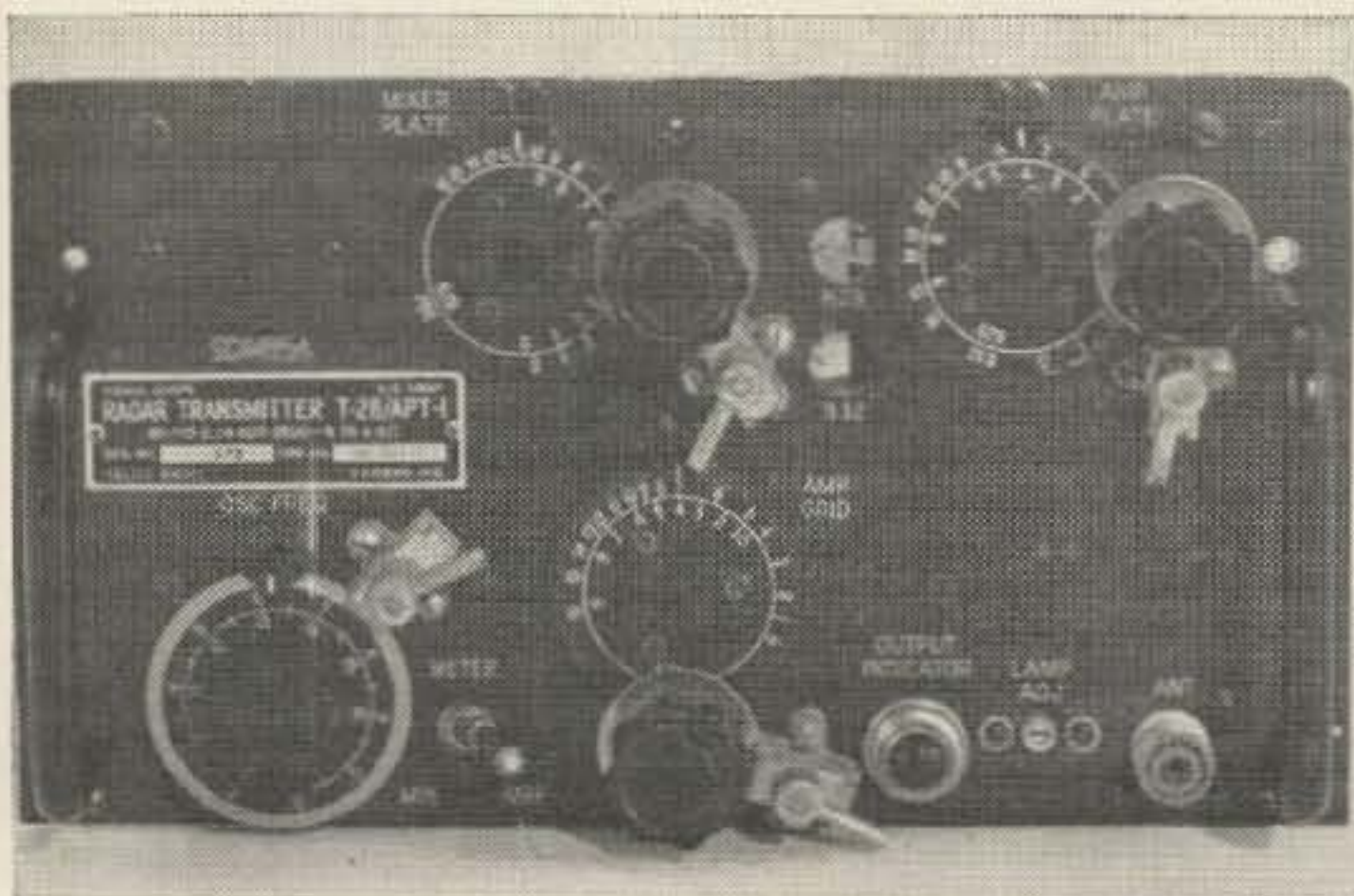To convert into an AM unit: The panel mounting arrangement and shielding requirements are identical to the T-51A/ARQ-8 as modified into a 50 mc AM transmitter. In this case of the T-28/APT-1 modified into a 144 mc AM rig, the first order of business is to eliminate the push-pull, self-excited oscillator using type 6C4 tubes, and insert in their place,



a crystal-oscillator, doubler stage using a type 6BH6 tube. Easily obtained 8 mc type crystals may be used here, with the plate circuit doubling to 16 mc. A second type 6BH6 tube operating as a tripler, will multiply the 16 mc output to 48 mc, and this will then be link coupled to the 1st 832A stage grid circuit. As in the previous transmitters, this 832A stage was originally a mixer, accepting rf drive plus wide band noise. This is no longer needed and the stage in question merely becomes a conventional type tripler, with the grid resonant to 48 mc and the plate circuit tuning the 144 mc frequency.

This 832A tripler will in turn drive the final 144 mc straight-through Class "C" amplifier, which will be either an 832A type or an 829B type, depending upon the power output desired. When changing the final tube type, it will be necessary to change the value of the grid resistor as well as the screen dropping resistor associated with this stage. The schematic of Fig. 1 details such necessary changes. A key jack is indicated on this AM version, and should CW operation be desirable, the power input may be upped a bit more, without damage to the 829B tube.

Now, regarding the plate circuit rollo coils when using this maximum type power input—it is true that the heavy duty cycle type Class "C" operation can very likely cause the roller

contact of the rollo coils to tend towards some arcing, and possibly some heating, if very much tuning is done under such full power. This was mentioned in the previously published 50 mc AM conversion of the T-51A/ARQ-8, and it was there stated, that somewhat better efficiency might be obtained by removing this final plate circuit rollo coil and replacing with an L-C combination specifically resonant to the operating frequency. Such an arrangement can be duplicated in the T-28/APT-1, if desired, by mounting a coil and variable capacitor resonant to 144 mc in place of the original rollo coil and output circuit. A one or two turn link for rf output will replace the original T-28/APT-1 output circuit. A combination that is useable may take the form of a 10 mmfd per section split-stator capacitor in conjunction with a coil of two turns of No. 12 enamelled wire, wound on a 1 3/8 inch diameter, spaced 1/2 inch, tapped in the center for the HV connection.

If an 832A is used in the final or if the 829B type tube is throttled down in power input, this change in the final L-C circuit is hardly worth while, as no decrease in efficiency or unwarranted heating will occur at about the 20 watt output level. In any event, it is recommended that the original rollo coil be left intact even with the higher power, and if trouble is encountered, then corrective steps

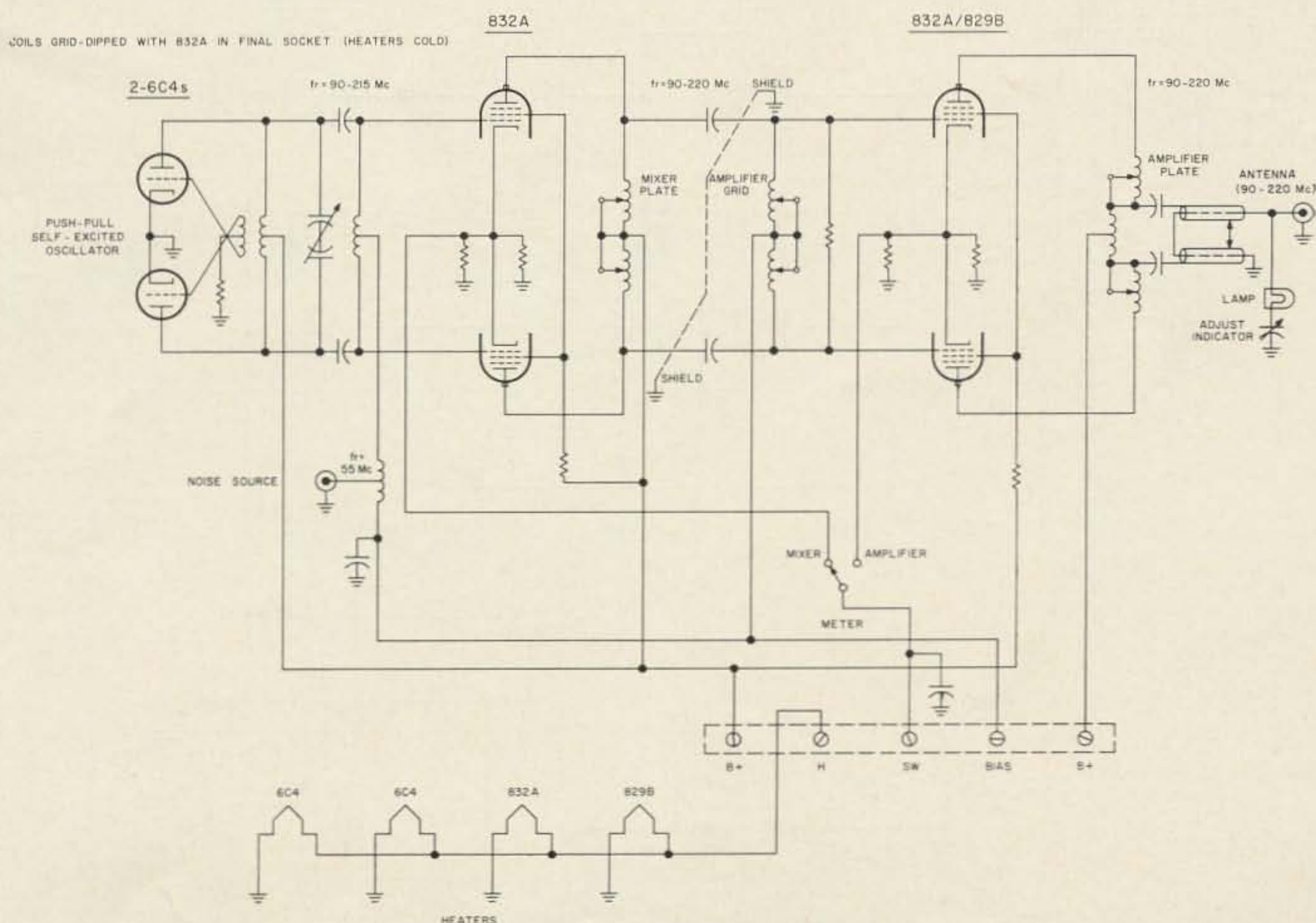


FIGURE 1

can be taken.

Should high-level Class "C" AM modulation be desired, the modulator may be inserted in the high-voltage lead of the final tube. A modulator capable of from 15 to 50 watts audio output will be required, according to the final rf tube selected. Used as an AM transmitter then, one can reasonably expect the following performance; using an 832A in the final, the input for Class "C" AM phone operation will be 32 watts. The efficiency, (dc input to rf output) will run around 55% or so, which will result in an output of about 18 watts carrier power. On CW operation, this input may be raised to at least 40 watts and will result in a 22 watt output carrier. Using an 829B in the final, the input for Class "C" AM phone operation will be 100 watts. The efficiency will run about 50% and will produce an output of at least 50 watts carrier power. On CW operation, this input may be raised to at least 120 watts and will result in a 65 watt output carrier. The screen voltage and current will be about 200v dc and 30 ma. Grid current should run 10 or 12 ma. Keying is accomplished via a closed circuit key jack in the final cathode circuit.

To convert into an SSB unit: Procure a second identical T-28/APT-1 unit and proceed as follows, referring to Fig. 3. The first step here is to replace once more the 6C4's. This

time, the crystal oscillator-tripler tube to be installed is a twin-triode 6J6 type. The crystal frequency will be 41.0 mc, tripling in the second half of the 6J6, to 123 mc. This frequency is then amplified by a new buffer tube (6BH6) and this tube in turn drives the first 832A high level mixer via its new grid coil. All up to this point assumes 21 mc SSB energy available from a 20A or something similar, in order to mix to 144 mc. Should another SSB frequency be desired, such as 14 mc, then the injection string will have to be altered to suit. This was discussed at some length in the original article on the T-51A/ARQ-8 set-up. The plate voltage of the crystal oscillator portion of the 6J6, as well as the plate of the tripler, is regulated for best stability. This is procured from an external +150 volt regulated supply and these two stages should run continuously, coming on with the heaters of all the tubes. The four new coils to be wound will be L-1, L-2, L-3 and L-4. The first three are ordinary slug tune units resonant to either 41 mc or 123 mc. The coil L-4 is to be resonated with the 832A tube input capacitance to 123 mc. Coupling from L-3 to L-4 consists of two-turn links on either coil. A new grid-leak of 10k connects from the center of L-4 to ground.

21 mc SSB energy is fed into the cathode of the first 832A through the 500 mmfd coupling capacitor. The screen voltage on this

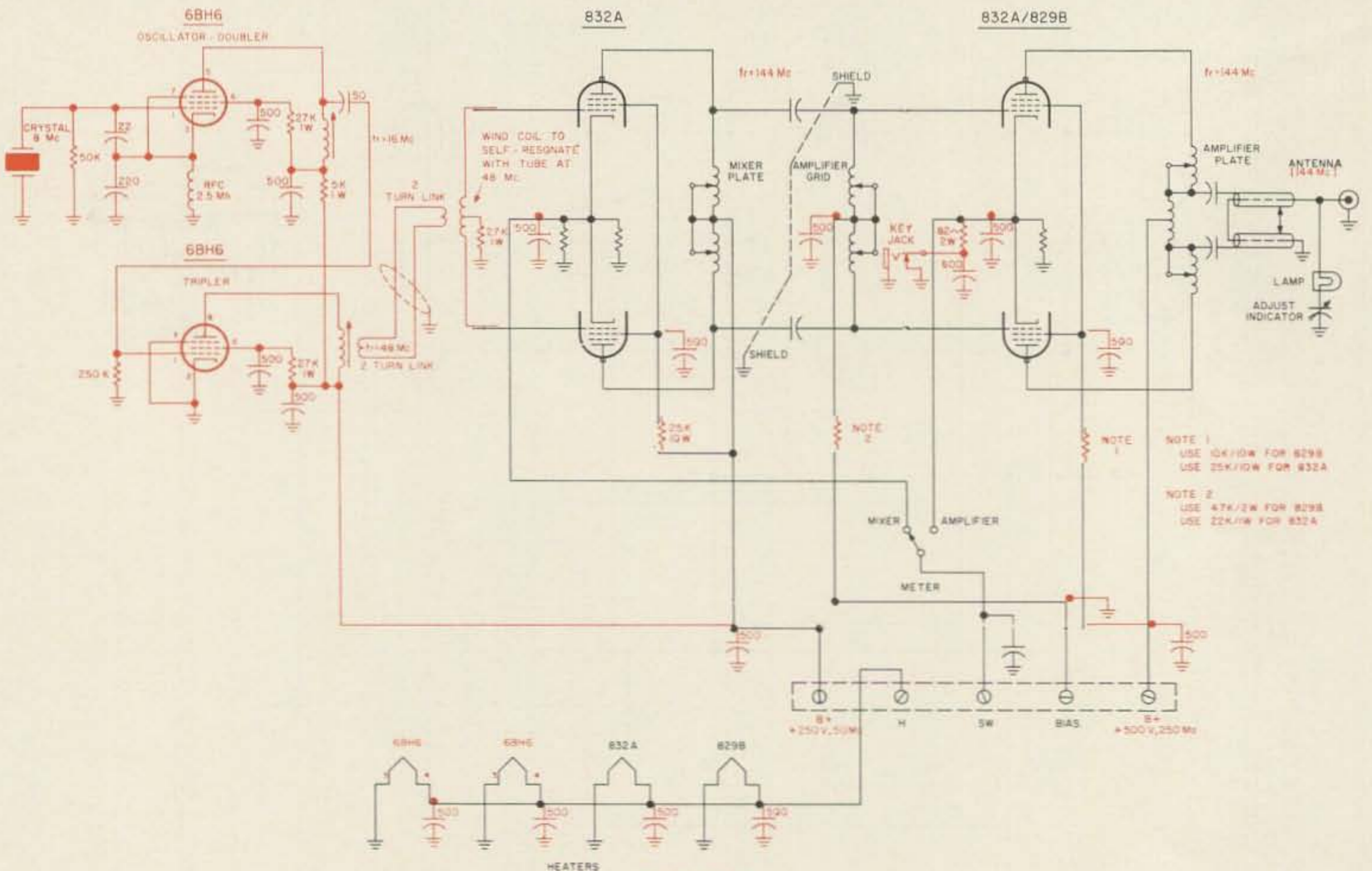


FIGURE 2

Added Components in red

832A mixer tube is derived from a 5k, 5 watt resistor from the 250 volt supply furnishing voltage for the 6BH6 plate and screen and for the 832A mixer plate.

Changes in the final stage to operate in a linear fashion, will first depend on the choice of tubes, either the 832A or the 829B type. The screen grid voltage dropping resistor may be adjusted so that the two OB2 regulator tubes fire properly to provide the regulated 216 volts dc. The rolo coils associated with the plate circuit of the previous 832A mixer stage, the grid circuit of the final and the plate circuit of the final will remain as is. Unlike the AM modification just described using the 829B tube, this SSB version will not require the substitution of a new final tank circuit. This is of course due to the lighter duty cycle of this mode of operation. It will be necessary, however, to provide some fixed bias for the final 832A/829B linear stage to set the proper resting plate current, which will be approximately 10 ma for the 832A and 15 ma for the 829B. This will end up around -15 to -25 volts or so and may be provided by a small silicon supply with a variable pot for exact adjustment.

As for power delivered in the SSB version; Should the 832A be used in the final, an input of from 35 to 45 watts pep may be used. This will result in an output of from 15 to 20 watts pep and will be more than enough to drive any grounded cathode type linear amplifier, such as push-pull 4X250B's to maximum power on 144 mc. Should the T-28/APT-1 be used as a complete transmitter without a following higher power amplifier, then of course, the choice should be the 829B tube (or perhaps an 5894). This tube will allow an input of some 120 to 150 watts PEP and will deliver on the order of from 60 to 70 watts PEP output. Plate voltage may be anything on up to 750 volts.

This particular unit was checked out at this station using an 829B tube with a plate supply of 600v dc. The screen was regulated at the usual 216 volts and the final negative bias was approximately -25 volts. Resting plate current was 15 ma. With a two-tone test signal driving the final plate current to 100 ma, an output of 30 watts average power was measured. Speech easily drives the unit up to the 70 watts pep output mentioned above.

- L_1 = Slug tuned ceramic form $\frac{1}{4}$ " dia—15 turns #24 onem close wound.
 - L_2 - L_3 = Slug tuned ceramic form $\frac{1}{4}$ " dia— 9 turns #22 onem— $\frac{1}{2}$ " long.
 - L_4 = 10 turns #16 tinned $\frac{1}{2}$ " dia.—1" long winding—center tapped.
- (Resonate all coils to frequency with GDO)

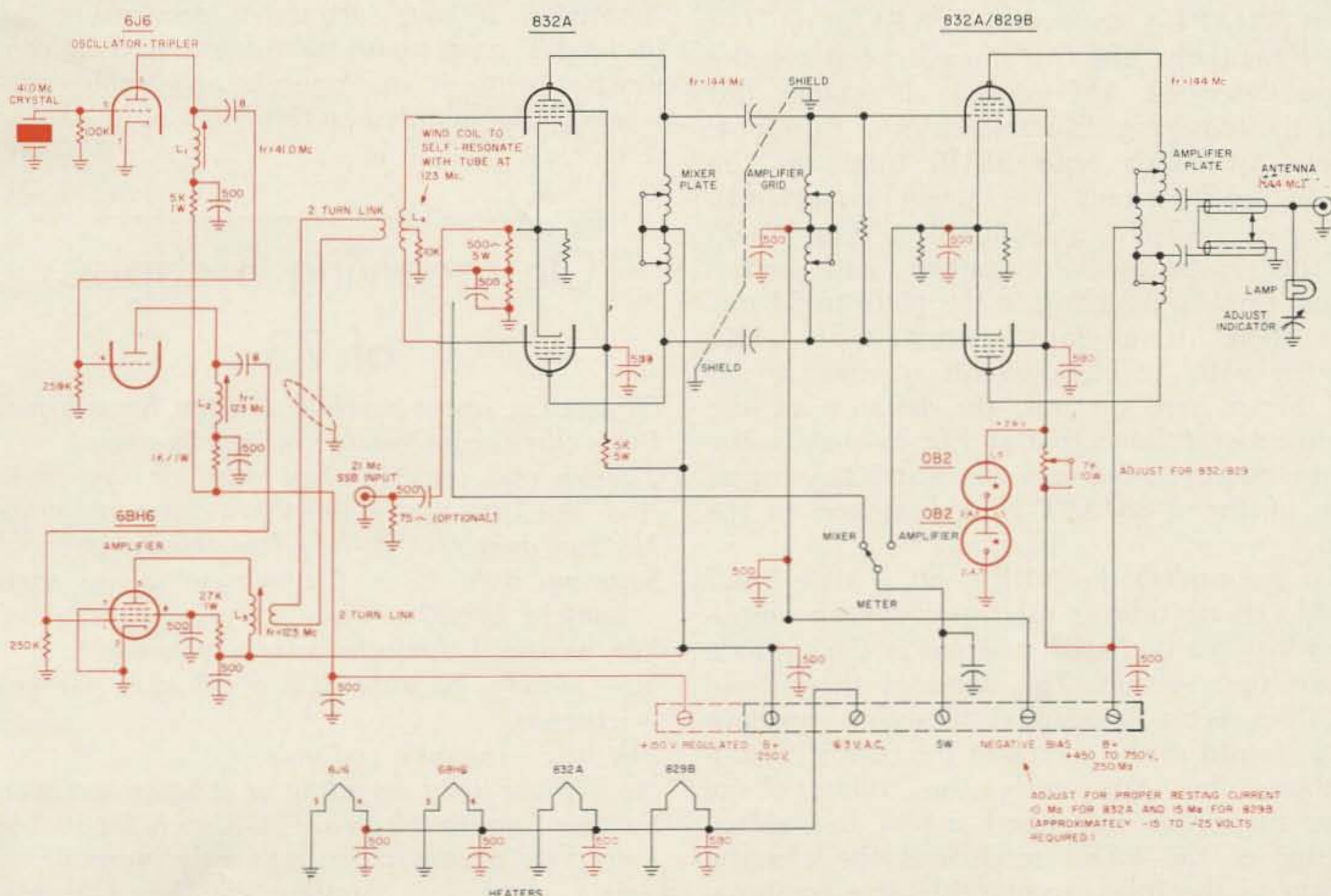


FIGURE 3

Added components in red. The "mixer" lead (shown in black) coming from the meter switch should be connected to the center point of the resistor divider (shown in red) in the cathode of the first 832A.

The rolo coils will not require retuning unless excursions in frequency of more than several hundred kilocycles becomes necessary.

A word about TVI. According to the local situation, it may be necessary in some locations to go to a bit more trouble in the shielding of this unit, as well as filtering of the heater and plate supply leads. Standard de-TVI procedures should be used. Also close attention should be paid to ascertain if any unwanted spurious products are present due to the mixing process. Be very careful to see that the injection frequency used to mix with the SSB energy does not leak through the final. Either 130 mc (used with 14 mc SSB), or 123 mc (used with 21 mc SSB) must not be allowed to radiate. A reentrant cavity filter between the transmitter if feeding the antenna or between this transmitter and the following higher power linear, is excellent insurance towards helping prevent troubles of this nature.

Further Suggestions

The preceding work was an assignment project of the Central Technical Net of A.F. MARS in Texas and as such, several of the units were distributed to different workers for experimentation.

One interesting variation originated with K5JHG Skeets Hogan of Atlanta, Texas, who came up with a very simple modification to put the T-28/APT-1 to work on NBFM on 144 mc. Essentially, this modification follows the above described AM version alterations, but with the following changes referring to Fig. 4, instead of using type 6BH6 tubes in the crystal oscillator-multiplier string as set forth in Fig. 2, K5JHG substituted a type 6AK5 for the crystal oscillator-doubler, and used a 12 mc crystal—doubling in the plate to 24 mc. This then, drives into another type 6AK5 doubler with its plate circuit resonant to 48 mc. From here on out, the balance of the modification follows that of Fig. 2—that is—the 48 mc energy is fed into the first 832A tripler tube of the T-28/APT-1, and thence to the final.

To accomplish the NBFM bit, a type 6SL7 double triode tube is used as a speech amplifier with a carbon mike inserted in the cathode of the first section. The plate of the second amplifier section is coupled through a capacitor of .01 mmfd to the screen of the 6AK5 crystal-doubler tube. Apparently, the audio voltage from the 6SL7 impressed across the screen resistor of the 6AK5 modulates the electron stream of the tube, accomplishing a combination of both frequency modulation as well as

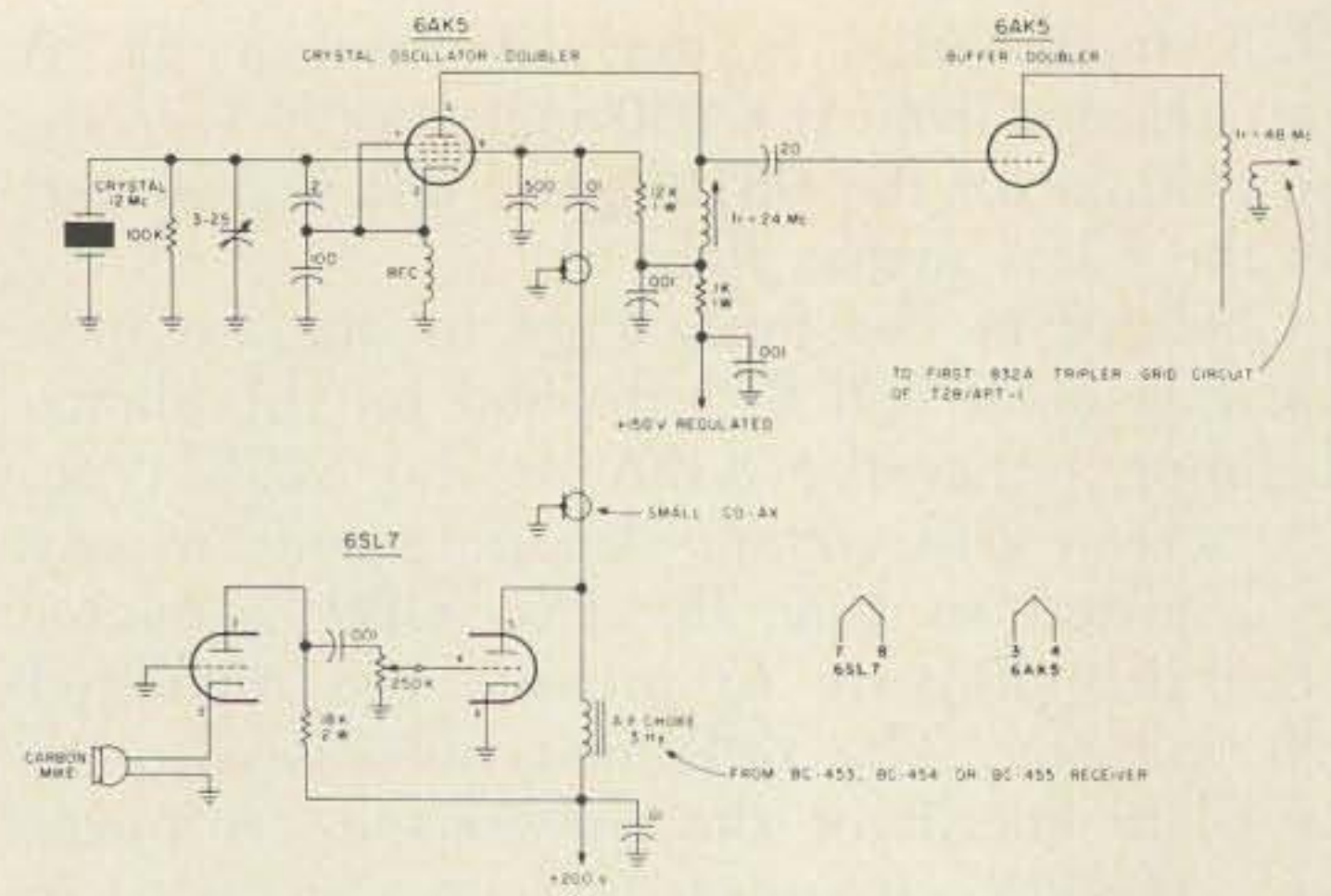


FIGURE 4

some residual amplitude modulation of the crystal-doubler tube. Since the multiplier stages following this tube operate under Class "C" conditions, the AM component is virtually washed out by the FM limiter action, and when multiplied to the final frequency of 144 mc, only NBFM remains. K5JHG uses this T-28/APT-1 NBFM unit as a driver for his 144 mc 4X150A final amplifier as well as a driver for his 432 mc tripler set. This arrangement appears to work very well on both 144 mc and 432 mc and is mentioned as a further example of the versatility of the T-28/APT-1 surplus set.

Other arrangements may also be used to produce frequency or phase modulation in the T-28/APT-1. Several schemes are discussed by Frank Jones in his "VHF For The Radio Amateur." A very attractive scheme is the bridged-T type phase modulator used in conjunction with 8 mc crystals and could conveniently be adapted to this T-28 unit.

... W5AJG

On receiving 3 copies of 73


*Of strange status symbols I often have heard,
But a three copy family's strangely absurd.
There's one for Me, and one for my filius,
And one for my Wife—that's kind of silius.
My son only eats it—he's less than a year, . . .
Says my wife, ". . . Homebrew means some
kind of beer?"
Yet even so, I think the joke is immense,
Not merely because it's at Wayne Green's
expense,
But in 73 humor's endemic,
And 'Twas easy avoiding a lengthy polemic.
So like Egypt's kham-sin-in March invariable,
I need no fourth since that's only buryable*

*Similia Similibus Curantur
Bob Robbins—K3HTB*



TRANSCEIVER HIT PARADE

HALLICRAFTERS

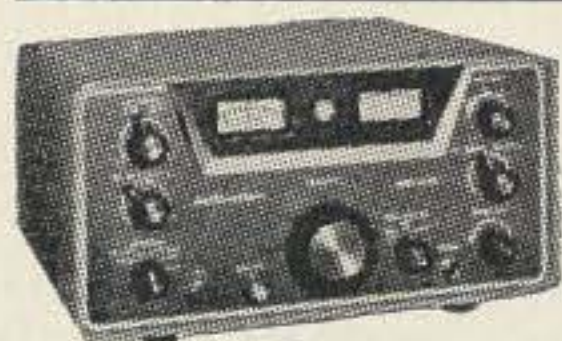

SR160 Transceiver **349.50**

P150 AC Supply/speaker **99.50**

P150 DC Supply **109.50**
MR 160 Mobile Mount **14.50**

COLLINS

KWM 2 Transceiver **1150.00**
516 F2 AC Supply **115.00**
MP 1 DC Supply **198.00**
351 D2 Mobile Mount **120.00**

DRAKE

TR 3 Transceiver **550.00**
AC 3 AC Supply **79.85**
MS 3 Speaker **19.95**
DC 3 DC Supply **129.95**
Mk III **6.95**


NATIONAL

NCX 3 Transceiver **369.00**
NCX-A AC Supply/speaker **110.00**
NCX-D DC Supply **119.50**

SBE

SBE-33 Transceiver **389.50**
SB 2-DCP DC Inverter **79.50**
SB-1 Mobile Mount **12.50**
SB-1 LA Linear **279.50**

SWAN

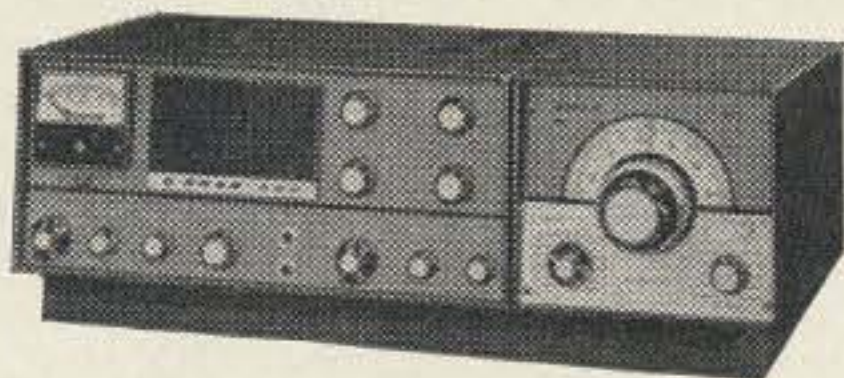

Swan 400 Transceivers **375.00**
Swan 406 VFO **65.00**
Swan 420 VFO **120.00**
Swan 1117B AC Supply **75.00**
Swan 512 DC Supply **145.00**

**Write for our Special
Transceiver Packet**



WE SET THE PACE!

Our realistic, down to earth pricing coupled with full guarantee and good service still leads the field. Remember—We don't claim to be the biggest—only the most reliable. We've been at it a long time—We have the know how. If you are not already a satisfied customer give us a try now.

73

Stan Burghardt WØBJV

These Prices Are Cash—No Trade

BC 221P Frequency Meter	\$ 49.00
CENTRAL ELECTRONICS MM-2 Scope	54.00
CENTRAL ELECTRONICS 600L Linear	179.00
CLEGG ZEUS Transmitter with supply	495.00
COLLINS 30L-1 KW Linear	390.00
COLLINS 32V3 Transmitter	195.00
COLLINS SM-2 Microphone 1/new	32.00
COLLINS 75S3 Receiver, late serial #, 1/new	495.00
DRAKE 2A Receiver	169.00
EICO 722 VFO	44.00
FINNEY A62 2/6 Meter Beam (like new)	19.00
GLOBE Chief deluxe transmitter	44.00
GONSET GSB-100 SSB Exciter	225.00
HALLICRAFTERS HA-2 two meter Transverter with P26 Matching AC Power Supply	249.00
HALLICRAFTERS HA-8 Splatter Guard	15.00
HALLICRAFTERS HT-32 AM/CW/SSB Transmitter	299.00
HALLICRAFTERS HT-32A AM/CW/SSB Transmitter	319.00
HALLICRAFTERS HT-37 AM/CW/SSB Transmitter	279.00
HALLICRAFTERS HT-41 KW Linear	229.00
HALLICRAFTERS SR-150 Transceiver with P-150 AC Supply, P-150 DC Supply and Mobile Mount	549.00
HALLICRAFTERS SX-101-IIIA	189.00
HALLICRAFTERS R-46B Speaker	7.00
HALLICRAFTERS R-47 Speaker	7.00
HEATH VF-1 VFO	15.00
HEATH TX-1 Apache Transmitter	169.00
HUNTER Bandit 2000 linear	390.00
JOHNSON VALIANT II factory wired (like new)	349.00
JOHNSON RANGER I Transmitter	129.00
JOHNSON 122 VFO	29.00
JOHNSON 250-39 TR Switch	19.00
JOHNSON 250-46 Phone Patch	15.00
JOHNSON Valiant fac. wired, exc.	199.00
NATIONAL NCX-3 with AC Supply, Demonstrator with full warranty	399.00
NATIONAL NC-300 with speaker	179.00
P&H LA400C Linear Amplifier (like new)	119.00
SBE33 Late model Transceiver	319.00
SBE1-LA Linear (like new)	229.00
SBE-DC Mobile Inverter Supply	44.00
SWAN SW-120 Transmitter	135.00
SWAN SW-175 Transceiver	179.00
SWAN SW-12 DC 800 volt mobile supply	79.00

SPECIAL HALLICRAFTERS VHF PACKAGE:

HA-2 Two Meter Transverter	Regular	\$349.50
HA-6 Six Meter Transverter	Regular	\$349.50
P-26 AC Power Supply	Regular	\$ 99.50

OUR SPECIAL \$499.00 Cash Only \$798.50

WRITE FOR LATEST REVISED BULLETIN
ISSUED MONTHLY
AMERICA'S MOST RELIABLE DEALER

BOX
37A



PHONE
886
5749

WATERTOWN, SOUTH DAKOTA

Correspondence from the Members

Letters we bet you won't see in QST

Gentlemen:

Thanks for your notice of expiration of my membership in the ARRL.

In reference to the second paragraph on the expiration notice, I have decidedly NOT valued my membership in said organization, inasmuch as it seems they are now making every effort to cause me to lose the Amateur Radio License (Conditional) which they helped me to get.

Over the past omnth I have carefully studied both the pros and cons of the current controversy which your organization has promoted as regards incentive licensnig, and I feel that the ARRL, which through never-tiring efforts, is even today swelling the ranks of Amateur Radio through the media of its organized classes, contests, certificates, etc, has achieved the pinnacle of hypocrisy in submitting, without the concurrence of the membership which it claims to represent, a petition, the results of which must, according to one's viewpoint, either severely curtail the privileges of a large percentage of American radio amateurs or present a minority group of same with unwarranted (not un-earned, but un-warranted) privileges at the expense of the larger group.

I do not write this letter in argument to statistics—you, not I, have the statisticians in employ. I do argue that it is your campaigning which has created the current crowding of the amateur bands which you so deplore; Yet, while the right hand deplores this crowding and solicits legislation to alleviate it, the left continues to campaign for greater memebrship (and crowding) in the ranks of Amateur Radio. Neither do I refute the statements which imply that your fear the "young nations" of the world will have little sympathy for a group of radio amateurs in the United States. I do, however, to a considerable degree listen to the amateur bands in Europe, and at the same time study enough international politics to realize that the elimination of the privileges of a large group of U. S. licensed radio amateurs to the benefit of a minority thereof will not make one iota of difference to these "young nations" in their clamor for more of the radio spectrum.

From the above expression of my opinion, gentlemen, you will perhaps have some inkling of the reason for my failure to renew my membership, and for my campaigning within my modest circle, for others to follow my example.

I have for some years been a member of another organization which claims to represent the desires of its membership, and from experience with it I have become highly critical of organizations which pay lip-service to representation, vowing never again to knowingly maintain connections with an organization which follows the "You boys just keep quiet and do what we tell you—we know what's best for you!" line. I refer to the Air Line Pilots Association, once powerful and with a fanatically loyal membership; subject within the last two years to a devastating internal political shapeup, including a loss of 20% of their paying membership—all as a direct consequence of a ". . . we know what's best . . ." philosophy, and an unwillingness to swallow their pride, back down and follow the will of the membership.

The purpose then, of this letter, is to answer a question and to ask one. The question "Why are you not renewing your membership?" I have already answered. The question I direct to you is: Are you gentlemen of the ARRL board smarter than the deposed politicians of the ALPA—can you learn by their mistakes, or will you, as they did, ignore the clamor of the members until the organization threatens to topple?

Robert G. Gross, Jr.
WA6YGX/DJφIC

Dear Mr. Huntoon:

I received your form letter of welcoming me back to the League for another year. Before you go ahead and use my rejoining the ARRL as part of your statistics of being in favor of the Leagues proposal RM-449, please read on.

At the beginning of this fine mess that the League had started, my first thought was to let my time run out of being a member of the ARRL. Then with a little more serious thought I decided that the right way is to do my best and help (by vote) put a director in office who cannot be "brow beaten" and become a "yes-man", once he returned to the "Home Office". If enough areas would work on this program I believe the League would be in a much better position than it is now.

So my main reason of rejoining the League is to cast my vote for a new Southwestern Division Director and to cast my vote (if we are ever given that privilege by the League) against RM-499. I am sick and tired of reading of the so-called 16-0 voting by the Directors!! The ARRL has torn apart a fine organization and has set it back at least ten years!

Not only am I a member of the ARRL. I have also joined The Institute of Amateur Radio. The ARRL Booster Pin I once proudly wore not sits in the dresser drawer, my efforts now will go to the IOAR to help make it a stronger organization.

Maybe stronger competition will make the ARRL sit up and take notice that they do not control as many of its members they think they do.

The League is a great one for different contests, why don't you put your heads together and come up with some types that would make 10 and 15 meters the MAJOR bands. Help promote these bands now and we stand a great chance of keeping them.

It is very true that the commercial field is looking at our bands for the relief of their crowed bands. But the way you plan is far from the answer.

Donald A. Cofone, W6RDB

Dear Sirs:

I am returning the enclosed notice of subscription expiration I do not wish my subscription renewed.

Since subscribing in 1956 I noted that QST was not aimed at the man who was an "operator" and an "amateur". The articles were consistantly slanted toward the technician who was a semi-professional in the electronics field. Older hams told me at the time I received my license that "you get the deep stuff in QST and useable information in CQ". As CQ in recent years has followed QST the hams now refer novices to a new magazine "73" for the same reason they used to recommend CQ.

There is, of course, the matter of league membership. Yet, to support an organization, one must feel the organization supports the majority of its members. This the league does not do. Whether it is in aiding those defending themselves against a lawsuit aimed at all of us, or in recognizing that the vast majority of its members are general and conditional class (according to the leagues own figures) and setting policies accordingly, the league fails.

Its officers consider themselves a technological elite for whom the FCC must make special provision in its regulations to the detriment of the majority of the membership. No organization can expect to receive membership support on such a self-centered policy.

Even the arguments put forth by the league in its plea for higher technical requirements for licensing are confused. In effect it says: "Because manufactured rigs are better and cheaper than those a ham can make, a ham does not need to know so much—so we propose that he be required to know more." This is certainly moving in a direction opposite to the presented evidence. Another ham's petition giving the lower end of the CW bands to Advanced and Extra licenses for phone would deprive no one and still provide an incentive. These frequencies are empty and the CB's may get them (or commercial interest).

As a conditional licensee I do not appreciate the league's point of view that I hold a "Sears and Roebuck license". An ex-army air corps radio operator-mechanic, I found the examination simple despite a 12 year absence from code operating. I am not only active in many public service projects, but originate many of them (see page 60, June 1961 CQ). Being a freelance writer I see that the local newspapers where I am stationed know we do more than cause TVI. I hold nothing against the hot soldering-iron types, but I make my contribution to ham radio too.

QST has just not kept up with the "state of the art."
 Ross A. Sheldon K4HKD (ex K5UCH)
 Huntsville, Alabama

FCC Rule Changes

215

The following rules changes have been made by the FCC, effective March 18th.

§ 97.13 Renewal or modification of amateur operator license.

(d) Application for renewal and/or modification (change of address, etc.) of an amateur operator license shall be submitted on FCC Form 610 and shall be accompanied by the applicant's license. Application for renewal of unexpired licenses must be made during the license term and should be filed during the last 60 days of such term. In accordance with the provisions of this quarter, made timely and sufficient application for renewal of an unexpired license, no license with reference to any activity of a continuing nature shall expire until such application shall have been finally determined.

e) If a license is allowed to expire, application for renewal may be made during a period of grace of one year after the expiration date. During this one year period of grace, an expired license is not valid. A license renewed during the grace period will be dated currently and will not be backdated to the date of its expiration. Application for renewal shall be submitted on FCC Form 610 and shall be accompanied by the applicant's expired license.

§ 97.47 Renewal and/or modification of amateur station license.

(a) Application for renewal and/or modification (change of address, etc.) of any station license shall be submitted on FCC Form 610. In every case the application shall be accompanied by the applicant's license. Applications for renewal of unexpired licenses must be made during the license term and should be filed during the last 60 days of such term. In any case in which the licensee has, in accordance with the provisions of this chapter, made timely and sufficient application for renewal of an unexpired license, no license with reference to any activity of a continuing nature shall expire until such application shall have been finally determined.

(b) If a license is allowed to expire, application for renewal may be made during a period of grace of one year after the expiration date. During this one year period of grace, an expired license is not valid. A license renewed during the grace period will be dated currently and will not be backdated to the date of expiration. Applications shall be submitted on FCC Form 610 and shall be accompanied by the applicant's expired license.

NOW!

S.W.R. BRIDGE and FIELD STRENGTH METER

9⁹⁵

Allow 50¢ for
packing and
shipping.
California resi-
dents include
4% sales tax.



**THE BEST
VALUE WE
HAVE
EVER
OFFERED!**

An excellent combination unit for either home station or mobile use... as an accurate Standing Wave Bridge and a sensitive Field Strength Meter. 52 ohm impedance. Will take a full kilowatt and can remain in the line all of the time.

Grey metal case, 5 1/4" H x 1 1/4" W x 2 1/4" D, with standard fittings, 1 5/8" Bright-vue meter, and detachable, telescoping antenna which extends to 10 3/4". With instructions and schematic.

QUEMENT ELECTRONICS


1000 SOUTH BASCOM SAN JOSE, CALIFORNIA

"Northern California's Most Complete Ham Store"

SINCE 1933

HEY! WIRE!

OPEN WIRE LINE

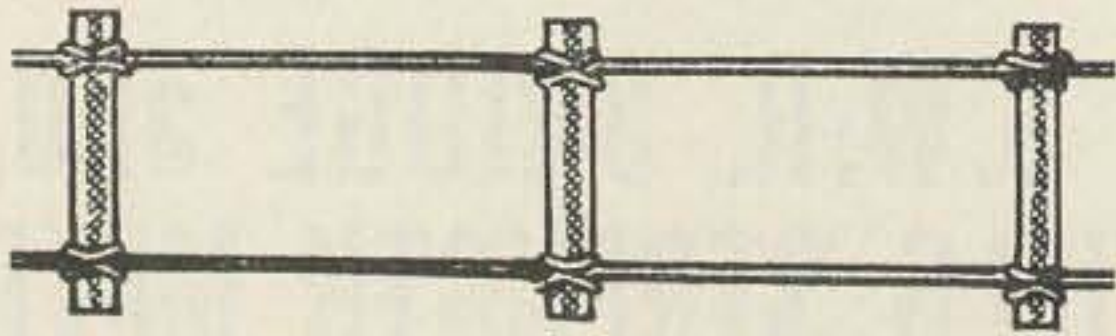

This stuff has about one tenth the loss of coax and costs about half as much. Use this where efficiency is of importance.

300 ohm open line copperweld wires for strength

100'	\$2.15	2 lbs.
250'	\$4.85	4 lbs.
500'	\$9.70	7 lbs.

450 ohm open line also copperweld wire

100'	\$1.90	2 lbs.
250'	\$4.50	4 lbs.
500'	\$8.59	7 lbs.

ORDER DIRECT and save



Standoff Insulators

slots for 300 450 600 ohms	nail end10/\$1.50	1 lb.
	wood screw end ..	.10/\$1.50	1 lb.
	pole clamp end ..	.10/\$1.75	1 lb.

Please include postage — as below.
Minimum order \$5 please, U.S. only

Postage	300 mi	600 mi	1000 mi	1400 mi	1800 mi	beyond
First 2 lbs.	.35	.39	.45	.51	.58	.64
Ea. add'tl lb.	.06	.08	.10	.13	.16	.19

REDLINE

JAFFREY, N. H.

Letters

Dear Wayne,

I have never felt the necessity to write to an editor before, but considering the effect that the ARRL proposal would have on our wonderful hobby of amateur radio I believe it is very necessary for me to express my views on the matter.

When the ARRL first introduced its so-called "Incentive Licensing" program I wasn't very impressed by the idea, since it would mean wasting time memorizing answers to more test questions, time which could be better spent experimenting or increasing operating proficiency; and this to retain what we already have! Other reasons for opposition soon came out, reasons which were consistently more sound than those for its support. For one thing human nature cannot be changed by legislation. Congress tried to do so by amending the Constitution to prohibit the sale of liquor in the United States, thereby hoping to promote temperance among Americans; however it soon became apparent that, if anything, more people were drinking because of this law than less, and the 18th Amendment was soon repealed. The current civil rights controversy is also a good illustration. Thus if amateurs are indeed a lazy lot, as the ARRL seems to think, stiffer tests aren't going to change things one bit.

But I don't think that most of us are so technically ignorant. Many hams here in Moorhead have very well-equipped workshops and spend much time on home construction projects; is there any better way to bring home textbook data than in terms of practical experience with the theory involved? On-the-air discussions also often center around technical problems encountered with transmitters, antennas, etc. Hams lazy? I think not.

Further, if this proposal were placed into effect it would cause a considerable increase in work and expense for the FCC. They would be compelled to spend large sums of money (our money!) devising and printing all of the suddenly required tests; moreover, since there is no difference in calls among the Conditional through Extra classes it would be very easy for the former to continue using the latter's "privileges" unless the FCC hired many more monitors to police us (more of our money). I have always favored minimum government intervention in anything, and this is certainly much more than minimum.

These are all very good reasons for opposing the measure, but the clincher appears, ironically, in QST itself. I am referring to the "Correspondence from Members" columns in several of the recent issues. After close scrutiny it became evident that there was more than chance involved in the order of the letters. One or two would first appear opposing the measure, abruptly followed by one in favor of it arguing on the same points, as if to refute the previous points. This sort of spacing has been too consistent to be mere coincidence. Does the ARRL have so little confidence in the merits of the proposal that it must resort to tactics such as these to win approval of it by us amateurs? Does it, indeed, have any merits good enough to have it forced on us by government decree?

I am sure the ARRL is sincerely interested in improving the technical calibre of amateurs in general; but there are means of doing this that are much better than such drastic proposals. One of these is to change the structure of QST magazine. At present only about a third of the magazines is devoted to technical material; what is there is excellent, but there isn't enough of it. Even the ads lean very heavily toward commercial gear. So why not have QST feature more theory and construction material and solicit more ads concerning parts needed in homebrew equipment, rather than placing so much emphasis on operating and completely commercial gear.

However, if we still must accept more government control there are still better ways of accomplishing it, and much less expensive too. Begin by giving Advanced and Extra class licensees their own distinctive calls; then give each of these two classes phone privileges on small portions of what are now CW only segments. This would be true incentive licensing. The higher grades would then become real status symbols, and be something to work for.

So I believe that this proposal is not only unnecessary but also very unwise. Thank you for giving me this opportunity to express my opinions.

Dave McFarland, WAØDAM

SERVICE TESTED EQUIPMENT

from



HERE IS A PARTIAL LIST OF OUR QUALITY RECONDITIONED HAM GEAR, FULLY GUARANTEED, AND SHIPPED PREPAID WITHIN THE CONTINENTAL U. S. WITH CASH ORDERS.

RECEIVERS

COLLINS 75A-1	\$179.00
COLLINS 75A-4	425.00
COLLINS 75S-1	379.00
ELMAC PMR-6A W/DC POW SUP	39.50
GONSET G66B W/3 way pow sup	89.00
DRAKE 2A	189.00
DRAKE 2B	209.00
HALLICRAFTERS SX101A	239.00
HALLICRAFTERS SX110	119.00
HALLICRAFTERS SX117	269.00
HAMMARLUND HQ110C	139.00
HAMMARLUND HQ145C	179.00
HAMMARLUND HQ170C	219.00
HAMMARLUND HQ180C	299.00
MOSLEY CM-1	129.00
NATIONAL HRO-60 W/5 coils	279.00
NATIONAL NC-107	109.00
NATIONAL NC-173	75.00
NATIONAL NC-183D	165.00
NATIONAL NC-270	139.00
NATIONAL NC-300	189.00
NATIONAL NC-303	289.00
RME 4350A	119.00
RME 6900	189.00

TRANSMITTERS

B&W 5100	149.00
CENTRAL ELECTRONICS 20A	119.00
COLLINS 32V1	129.00
COLLINS 32S1	449.00
ELMAC AF-67	59.00
ELMAC AF-68	129.00
GLOBE CHIEF	29.00
GLOBE SCOUT 680	45.00
GLOBE 755A VFO	39.00
GLOBE SIDEBANDER	59.00
GLOBE MATCHER AT-4	34.00
GONSET COMMANDER	39.00
GONSET GSB-100	225.00

HALLICRAFTERS HT-32A	\$389.00
HALLICRAFTERS HT-32B (like new)	575.00
HALLICRAFTERS HT-37	289.00
HAMMARLUND HX-50	275.00
HARVEY WELLS T-90	69.00
HEATH APACHE	179.00
HEATH WARRIOR	215.00
HEATH DX-35	34.00
HEATH DX-40	39.00
HEATH DX-60	59.00
HEATH DX-100	95.00
HEATH HX-20	199.00
HEATH SB-10	59.00
JOHNSON RANGERS	119.00
JOHNSON VALIANT II	335.00
JOHNSON VALIANT II (new demo)	420.00
JOHNSON NAVIGATOR	119.00
JOHNSON INVADER 200	325.00
JOHNSON INVADER 200 (new demo)	495.00
JOHNSON INVADER 2000 (like new)	750.00

TRANSCEIVERS

COLLINS KWM-2 (with AC pack)	945.00
COLLINS CC-2 Carrying Case	49.00
GONSET G-76 w/DC supply	275.00
HEATH HP-10 pow sup for Swan	44.00
HEATH HP-20 pow sup for Swan	39.00
HEATH HW-12 (75 meters)	125.00
HEATH HW-22 (40 meters)	135.00
SWAN SW-117AC supply	85.00
SWAN SW-120 (brand new)	199.00
SWAN SW-140	165.00
SWAN SW-175	165.00
SWAN SW-240 (near new)	259.00

LINEARS

B&W LPA-1	275.00
HALLICRAFTERS HT-33	325.00
JOHNSON COURIER	115.00
P & H LA-400	85.00

"THE STORE OPERATED BY HAMS FOR HAMS"
K6LOS, K6GCD, K6DXD, K6EF, K1SFQ, W600E

MISSION HAM SUPPLIES

3316 Main Street
Riverside 3, California 92501
Phone 683-0523 (area code 714)

**ORDER
TODAY**

Mission Ham Supplies

3316 Main Street, Riverside 3, Calif. 92501

Attn: Bill Hullquist, K6LOS Ship me the following:

\$ _____ enclosed. Cash orders prepaid within continental United States.

Name _____ Call _____

PLEASE PRINT

Address _____

City _____ Zone _____ State _____

Put me on your mailing list.

Our Readers Answer CQ's Editorial

Dear Wayne:

Well, well, well . . . CQ finally got off the fence. I wonder who pushed them?

I fully agree with the Editor of CQ that one should be a little bit more sure of his facts before running editorials, but I guess he wasn't too worried about this because he was leaving anyhow.

Just for the amusement of it, lets see what he said:

1. "The time "To Be Counted" statistics were written before the ink was dry on the February issue." As you will note this answer to a May editorial appears in the June issue and Wayne did not have to skip a month to answer it. So much for that.
2. "The CQ proposal was warmly received." No argument, it should have been, as it was completely unoriginal and on the only point that was raised, i.e. power increase, they took their lumps. Any active ham would have known this would happen.
3. "They have made no proposal before the FCC", real safe isn't it, to have a proposal and make no proposal.
4. Yes you have more than just one call as do thousands of other amateurs who also possess a citizen's band call, including the editor of CQ and his boss, the son of the publisher of CQ. (By the way Richard, isn't it time you at least tried for your General?)
5. An accounting of the monies of the Institute of Amateur Radio was presented to its Board of Directors and appears in the previous issue of '73' and prior to any requests for same. It clearly shows zero expense reimbursement. How much has CQ spent to benefit anyone but CQ.
6. CQ claims that your petition to the FCC is similar to theirs. Your petition was filed February 20th, before the March issue of CQ was out after having first appeared in the January issue of '73' (you will note that this is the required time, according to CQ to do a copy job) so . . . assuming it is true that the proposal appearing in CQ is similar to yours and yours appeared two months before theirs, I leave it to you as to who is the copycat.

I would suggest that engaging in a name calling contest, you check your own skirts to make sure they are clean. The ARRL was invited to check the count and postmarks on 73's ballot. Neither they, nor CQ requested to do so.

Sounds like the old saying, "Don't confuse me with the facts, my mind is made up."

I sincerely hope the CQ Editor enjoyed his name calling game and "when did you stop beating your wife" type of questions. Every child is entitled to a tantrum once in awhile.

Good luck on his next job.

IoAR Member
New York

By W4RLS

CQ Magazine in its May, 1964 issue, contained an editorial headed "Zero Bias," which was nothing more than

a character attack upon Wayne Green, the editor and publisher of 73 Magazine. Numerous comments have already been made on the air by various amateurs to the effect that character assassination like this has no place in the pages of purportedly responsible publication, and it is certain that the heading of the column is unworthy and untrue, in view of its obviously heavily biased content. This writer would label the column "Zero Potential," because it certainly is totally without voltage in our eyes!

Wayne Green normally needs no help in defending himself, and that is not the purpose of this letter. My purpose is simply to protest this kind of vicious attack in print on anyone.

First, the accusation is made that Wayne tallied the votes on his postcard poll concerning RM-499 before the ballots were distributed. This is the sort of irresponsible approach which Mr. Goebbels used to such good advantage about thirty years ago in Germany. Wayne has offered in the May issue of 73 to allow the ballots to be audited and has assured the A.R.R.L. that every ballot which they have been informed was mailed in favoring RM-499 is definitely included in the group. The entire collection is there, and before anyone hurls the lie at Mr. Green, that someone ought to accept his invitation to audit those ballots! The results of his poll, eighty per cent opposed to RM-499, are borne out in my eyes by virtue of the fact that examination of the file which the FCC has compiled on RM-499, previously reported in 73, showed the same ratio of opposition.

The second accusation is that 73 Magazine changed its attitude on incentive licensing. Whether it did or not is not the question, for certainly CQ did the fastest turn-about on record on its March issue! From a position of abject camp-following, swallowing the A.R.R.L. line hook and sinker, suddenly CQ Magazine discovered that there were possible methods of incentive licensing other than RM-499! Evidently, the editor of CQ has been reading Monitor! Since I originated the so-called W4RLS Plan, which has by far the most support of all the proposals in the FCC file, based on the signatures in that file, I am particularly gratified that both 73 Magazine and CQ Magazine have adopted similar positions. Nevertheless, I do not consider that 73 turned its coat, since the position now occupied by 73 is, to my view, not inconsistent with its previous opposition to the A.R.R.L. form of "Incentive Licensing". The position now adopted by CQ on the other hand, is in direct opposition to its editorial position to which it held through February, 1964, and then suddenly turned 180 degrees out of phase in the March issue of the magazine, with no explanation and no apology for the sudden turn in direction. The editorial in CQ further accused Wayne of deliberately misguiding his reads, of malice, and of himself joining the ranks of "Me Too'ers." Now the CQ editor made his determination of "Deliberately" misguiding his readers, and how he arrived at his conclusion of malice, he does not explain. He offers no evidence. Perhaps he can read minds? Accusations like this have no place in the field of honorable discussion. Nor do I believe Wayne to be guilty of the accusation that he has also become a "Me Too'er." What he advocates in his currently

LAFAYETTE RADIO ELECTRONICS

THE CHOICE OF VALUE-CONSCIOUS AMATEURS THE WORLD OVER



**LAFAYETTE "PRECON"
AMATEUR
PRESELECTOR
CONVERTER**
49⁵⁰

Imported MODEL HE-73

- Crystal Controlled
 - For 80-40-20-15-10 Meter Bands
 - As a Converter—Converts Receiver to Dual Conversion Operation
 - Improves Selectivity
 - Widens Band Spread
- A great 2-in-1 combination. Tuned interstage circuits and 2 stages of RF amplification assures higher signal-to-noise ratio, improved I.F., image rejection. Easy to install.

**PROFESSIONAL-QUALITY 14-TUBE COMMUNICATIONS
RECEIVER MODEL HE-80**



12950

Imported

- Dual Conversion on 6 Meters
- 5-Bands: 550KC-54MC
- Product Detector Circuit for Improved SSB Reception
- Separate BFO and Q-Multiplier Circuits (can be used simultaneously)
- Crystal Calibrator
- Efficient Super-heterodyne Circuit
- Effective Automatic Noise Limiter
- Voltage Regulated Power Supply

Features outstanding sensitivity, Q-Multiplier selectivity and electrical bandwidth, makes a handsome addition to your ham shack. Calibration crystal is sold optionally.

LAFAYETTE MAIL ORDER
& L. I. SALES CENTER
111 Jericho Turnpike,
Syosset, L.I., N. Y.

OTHER LOCATIONS

Jamaica, N. Y. Newark, N. J.
Scarsdale, N. Y. Plainfield, N. J.
New York, N. Y. Paramus, N. J.
Bronx, N. Y. Boston, Mass.
Natick, Mass., Brooklyn, N. Y.

Free!



Send for
Big New
422 page
1964 Catalog

LAFAYETTE RADIO ELECTRONICS

Dent. 73E-4 P.O. Box 10
SYOSSET L. I., N. Y. 11791

- Please send me new 1964 Catalog 640
 Ship Stock No. \$..... enclosed.

NAME

ADDRESS

CITY ZONE STATE

pending FCC petition (RM-577) is closely parallel to the W4RLS Plan, and is greatly different from RM-499. I happen to be in position to refute the accusation that Wayne borrowed his proposal from CQ Magazine. I had been in correspondence with Wayne for several months concerning the W4RLS Plan as opposed to RM-499, and I know that Wayne's own version of this approach to incentive licensing was his own and was not borrowed from the March issue of CQ Magazine. Quite the contrary, I strongly suspect that both plans, that of Wayne's and that of CQ's, were greatly indebted in their inspiration to the W4RLS Plan!

The "Zero Bias" editorial contains an entire paragraph amounting to no more than a character assassination attack, a mere diatribe, and reflects more discredit on its author than it possibly could upon its target. I am also in position to know that the accusation leveled at Wayne of organizing the Institute of Amateur Radio just to grab off \$10.00 donations for his own pocket is utterly false. I am one of the organizing directors of that organization, and am going on record here and now as stating that not only has Wayne offered free space in 73 Magazine to report the doings of the Institute, but that every dime of the money has been accounted for, is in the possession of the Institute, which is duly incorporated, and that Wayne refused payment for the free space in 73 Magazine, despite the fact that the directors did not think it was fair for the Institute to ride free and urged him to accept payment. He stated that he wanted to go "the last mile" in order in every way to show that he had no profiteering motive in connection with the Institute. He wanted to protect the Institute from the sort of false accusation as the one under discussion.

Certainly, a subscription to 73 Magazine is extra. The purposes of the institute are strictly limited to an attempt to benefit amateur radio. It is not the purpose of the institute to boost a magazine. The directors expect to run the institute and try to carry out its program and purposes which are intended to supplement those of the A.R.R.L., and to fill in the areas where A.R.R.L. either

will not or cannot take the necessary action for the benefit of amateur radio.

I do not pretend to agree with any one person fully, nor to claim perfection for anyone, including myself. Nevertheless, I am proud to be associated on the board of IOAR with such men as the following: Bill Ashby, K2TKN; Wells Chapin, W2DUD, Lloyd Haslam, W3AYA; Maurice Hinden, W6EUV; Harry Longerich, W2GQY/4; Ed Schaad, WA4PDX (W9AIY); Howard Pyle, W7OE; Warren Cannefax, K4AQV.

Harry Longerich is already on the ground in Washington, D. C. as the institute's representative, "lobbyist" if you want to call him that. At any rate, amateur radio now has a man in Washington, on the spot, for the purpose of selling amateur radio to our own government. The editor of CQ Magazine ought to spend his time thinking up or at least boosting progressive ideas to help the cause along, rather than wasting his time, words and venom in personal attacks on others.

Foy Guin, Jr., W4RLS

Letter

Dear Wayne:


Just a note in connection with your editorial in April 73. I would like to say that I feel your idea of giving considerable space in 73 to the qualifications of persons running for the position of ARRL director is a fine idea. During the last southwestern election I was fortunate enough to hear equal time speeches given by all candidates at the Los Angeles Council of Radio Clubs. Needless to say only a small fraction of the division's voting amateurs had such an opportunity, and the small biography with the ballot is certainly not enough.

Best wishes in connection with the IOAR and the "man in Washington" project.

Harvey
WA6KZI

USE AS DELUXE FIXED STATION...

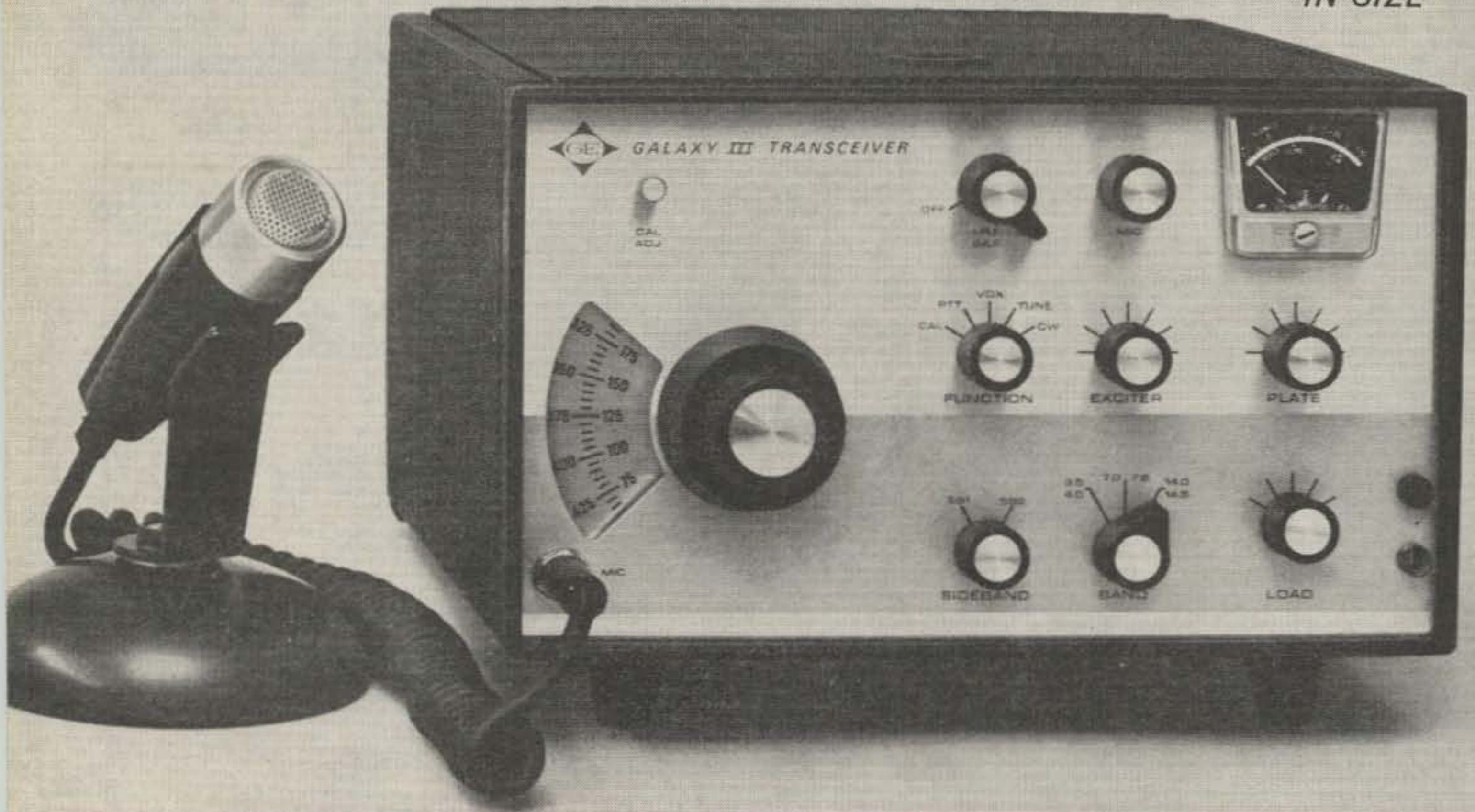
BOTH LESS
THAN ONE-HALF
CUBIC FOOT
IN SIZE



NOW!

TWO NEW
COMPACT
300-WATT
SSB/CW
TRANSCEIVERS

OR HI-POWERED COMPACT MOBILE STATION.

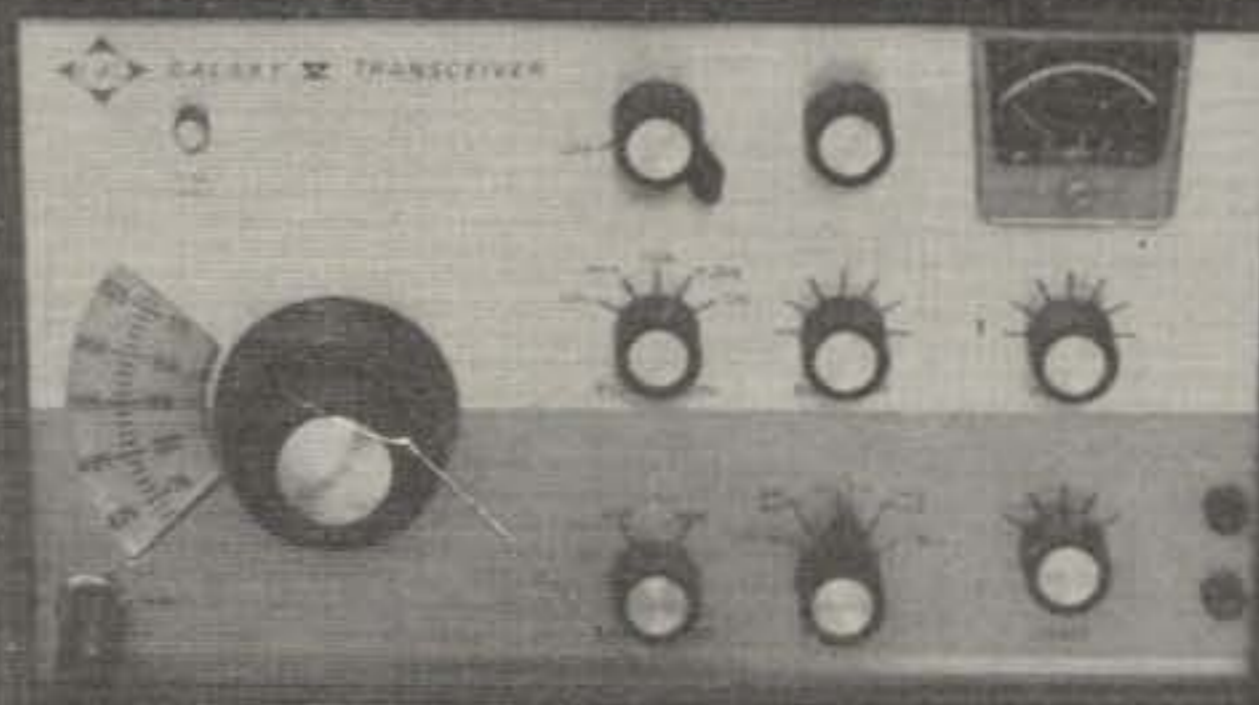

BOTH
TRANSCIVERS
ONLY
6" x 10 $\frac{1}{4}$ " x 11 $\frac{1}{4}$ "

GALAXY V

ONLY \$469.95

80-40-20-15-10 meters

GALAXY V COVERS 3.5-4.0, 7.0-7.5, 14.0-14.5, 21.0-21.5 and 28.0-29.0 *MC

*Factory supplied 28.0-28.5 and 28.5-29.0 MC.

Optional crystals available

GALAXY III

ONLY \$349.95

80-40-20 meters

GALAXY III COVERS 3.5-4.0, 7.0-7.5, 14.0-14.5 MC.

SEE BOTH MODELS AT ALL LEADING HAM DISTRIBUTORS



GALAXY ELECTRONICS

10 SOUTH 34TH STREET COUNCIL BLUFFS, IOWA ZIP 51504

WRITE FOR COMPLETE DETAILED BROCHURE

GALAXY OF FEATURES (For both the V and III)

Handsome styling — functional design. Brushed aluminum panel with 4-color etchings. Flat black knobs and perforated steel cabinet with hinge top.

- ★ 300 WATTS SSB/CW INPUT conservatively rated
- ★ FULL COVERAGE ALL BANDS
- ★ BEST FILTER AVAILABLE exceptional 2.1 KC filter stays 60 db down — with 1.8:1 shape factor
- ★ Suppression better than; unwanted SB 55 db, carrier 45 db
- ★ Highest receiver sensitivity; 1/2 uv @ 10 db S/N
- ★ "Smooth as silk" Dual vernier: fast 12:1, slow 72:1
- ★ Easy reduced-power tune-up
- ★ New advanced hybrid circuitry — transistorized VOX/AUDIO/AVC.
- ★ Highest stability — drift less than 100 cycles in any 15-minute period after warm-up
- ★ Panel selection of VOX/PTT
- ★ Panel calibrator adjustments
- ★ VFO Dial illuminated in three-color, and a well lighted "S" meter. Engineered for convenient mobiling.
- ★ MOST COMPACT 300-WATT TRANSCEIVER — size, 6" x 10 1/4" x 1 1/4". Weighs only 13 lbs.
- ★ SELECTABLE USB OR LSB with illuminated indicators
- ★ ALC CIRCUIT BOOSTS TALK POWER
- ★ Exceptionally good AVC
- ★ Accessory compatability (see below)
- ★ Shifted carrier CW prevents Transceiver "leap-frogging"
- ★ Extra clean CW keying

GALAXY III & V ACCESSORIES

- ★ AC POWER SUPPLY \$79.95
- ★ SPEAKER CONSOLE \$19.95 houses AC supply
- ★ 100 KC CALIBRATOR \$19.95

- ★ VEST POCKET VOX \$24.95
- ★ REMOTE VFO \$59.95 mobile/fixed station use

- ★ DELUXE ACCESSORY CONSOLE \$99.95 speaker, phone patch, SWR bridge, VU meter
- ★ TRANSISTORIZED DC SUPPLY \$119.95
- ★ UNIVERSAL MOBILE BRACKET \$7.95

Using 416B and 8058 Tubes as 432mc Preamps in the CFN-46ADT

Leroy May W5AJG
9428 Hobart St.
Dallas, Texas
Photo credit: Jim Dungan, Dallas

In 73 Magazine for November 1963 there was described a 432 mc converter using the surplus Navy type CFN-46ADT, rf to *if* converter. This was a transponder type military unit as used with a companion radar installation. Towards the last of the article, under "Further suggestions," it was stated that the substitution of W.E. 416B planar triodes, in place of the original 2C40's in the rf stage would improve the operation of the converter in a very substantial way.

It was further stated that the type 8058 nuvistor type had also been substituted for even the 416B's in an effort to evaluate the performance of this newer type RCA tube.

The first thought which will probably come to mind is; which will be the best—the 416B or the 8058? Which route should I go? This is a tough question, and some aspects of the problem will first be discussed, thereby perhaps helping one to decide which road to take.

Here at W5AJG we have modified two of

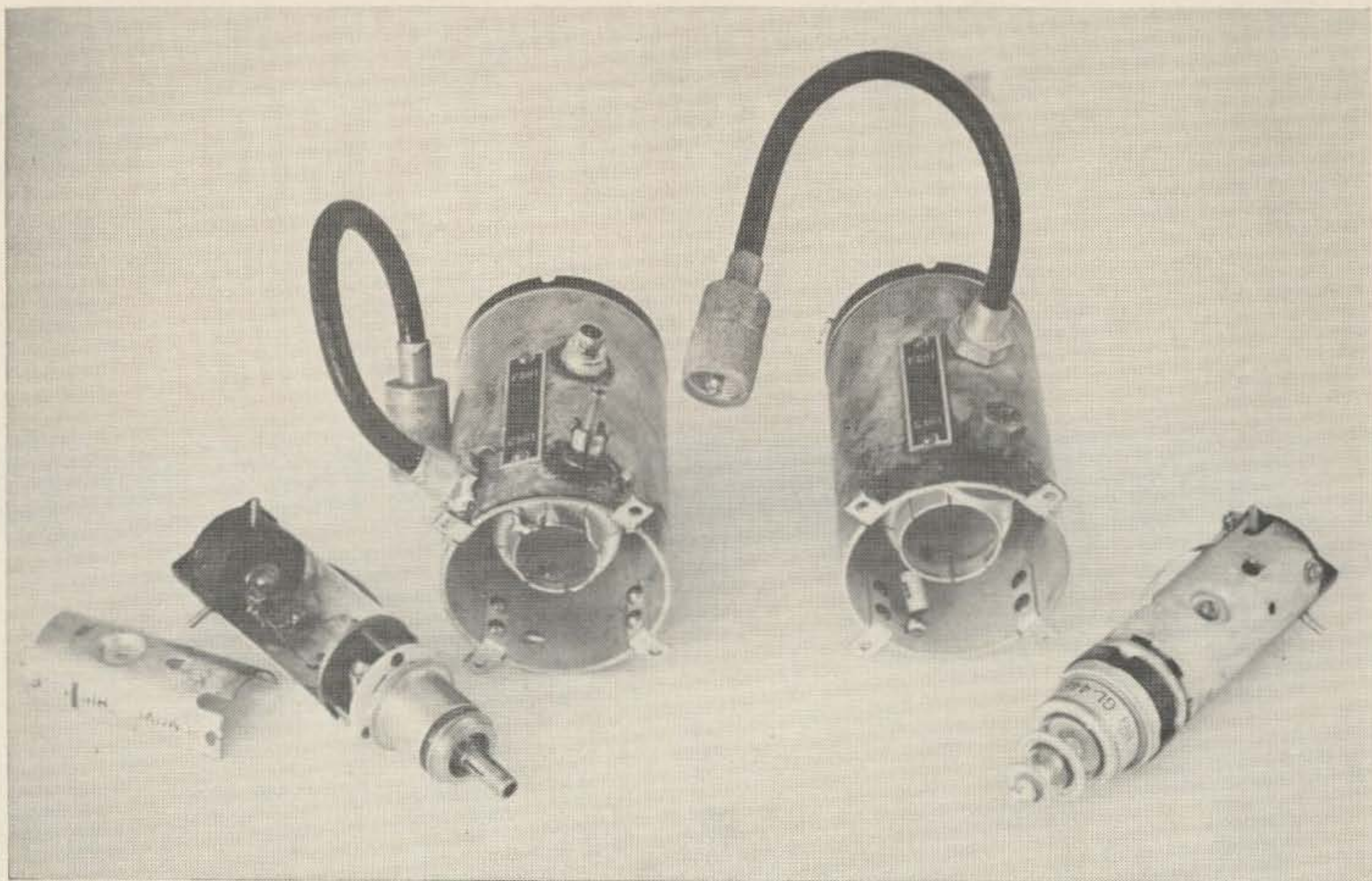


Photo showing modifications to the cathode tanks of the 46ADT to adapt for 416B gold plate planar triodes in place of the original 2C40/446B type tubes. Tank on the left is the modified one. Tank on right is the original unmodified one. Input coax is coupled in to the bottom of the cathode line (at tube) on the left hand line in contrast to the right hand tank where it is coupled in further towards the ground end of the inner conductor. Silver plated fingers on the left hand tank are bent inwards to firmly contact the cathode shell of the 416B tube. A quarter inch copper tube extension of the plate cup makes up for the total length deficiency of the 416B tube version.

TR-3	\$550	GALAXY III	\$249
200V	600	HX-50	325
20A	125	HQ-170C	199
HT-37	325	HQ-180C	299
HT44	395	NC-105	80
SX-43 & speaker	99	NC-140	129
SX-100	125	NC-300	199
SX-101	195	DX-35	25
SR-150	650	DX-40	40
SR-160	369	DX-100	97
RM 4300	99	Cheyenne-Commanche	99
RM 4350	129	Elmac AF-67	35
Viking Challenger	59	Elmac PMR-6A	49
Viking Ranger	125	Globe Chief	29
Eldico SSB 100A	195	75S-1	350
SX-117	379	32V2	195

Madison "Bug Catcher" mobile antenna loading coil 80-10	\$14.95	Madison SWR bridge kit	9.95
Madison 10 element two meter beam-gamma match-13 DB gain	11.95	W2EWL SSB transformers	1.00
Madison 3 position coax switch	\$3.95	Driftless VFO board	1.00
88 mhy toroids80		
Mercury relay for electronic keyer	\$3.95		

Model 15 teletype & table	\$125	Polar relay & socket	\$3.45
Model 14 TD	60	RA87A RTTY power supply	9.00
KY58/GRT RTTY keyer	100	TG30 Terminal repeater	35.00
2" core RTTY tape	8	Large single RTTY paper	12.50

9' AC cords50	TV cheater cords25
TS155C/UP sig. generator	50.00	TS102B/UP range calibrator	25.00
BC605 interphone ampl.	5.00	BD100 switchboard	25.00
ART13 transmitter	39.95	Federal FT102 transmitter	125.00
Throat mikes50	Bristol 6V choppers	5.00
IP69/ALA2 pandaptors	20.00	TS69A/AP freq. meters	20.00

Fresh stock Texas Instrument

IN2069 200PIV 750MA21	2N511 150 watt 25 amp	1.50
IN2070 400PIV 750MA24	2N1046 150 watt 15 amp	1.75
IN2071 600PIV 750MA33	2N1907 150 watt 20 amp	2.00

ALL ABOVE ITEMS FOB HOUSTON, TEXAS. PLEASE INCLUDE SUFFICIENT POSTAGE. EXCESS WILL BE REFUNDED. SEND FOR NEW FLYER!

MADISON ELECTRONICS SUPPLY

CA42668

1508 McKinney
Houston, Texas 77002

JA45298

the 46ADT units. The first allows us to try 416B type tubes in the two rf stages. The second 46ADT chassis allows us to try the two rf stages of 8058 nuvistors. The two units are quickly interchangeable into the same mixer system and thence through the remainder of the receiving setup. In six months of service on the 432 mc band, using out of town signals for comparison purposes, we can truthfully say that we can not tell any practical difference between the two tube types. Therefore, in nearly all cases, we feel the choice would be made for other practical reasons—as to whether it would be 416B's or 8058's on 432 mc.

One or two of these practical reasons might be explored a bit before we proceed. The 8058 nuvistor sells for \$13.25 at the present time. Right off then, an expenditure of \$26.50 must be immediately justified. As against this, the 416B's will cost nothing—in the majority of cases—or at the most, three or four dollars per tube. How important is money, anyhow?


Ease of construction? Well, the 8058's will probably be the easier to get built and plugged in, but there is no great advantage one way or the other. One of the most attractive things about the 8058's will be the absence of any blower—and the low plate voltage required. Using the 416B's at maximum rated electrode

voltages, a blower is definitely necessary. Using them at reduced ratings, both as to plate and heater voltages, blowing is definitely *not* necessary. This latter condition is the arrangement that is used and will be described for the 416B's as used in the 46ADT unit.

To boil it all down then—this means if you have the dough, go 8058's. Even if you are rich (but tight), or if you are plain stinking poor, the 416B's will be the route for you.

K5JHG, Skeets Hogan of Atlanta, Texas, first suggested the feasibility of modifying existing surplus quarter-wave coax-cavity tanks to accept the 416B gold plated triode tube. Many of these WWII surplus units were designed to use the then new 446A/B or 2C40 type planar-triode tube and with small changes, can be made to work excellently with the 416B type, which is of course, much superior in its performance. The majority of these surplus tank circuits are beautifully built, silver-plated and are unusually stable devices with no signs of monkey business, even when used in cascade fashion. The 46ADT is such a unit.

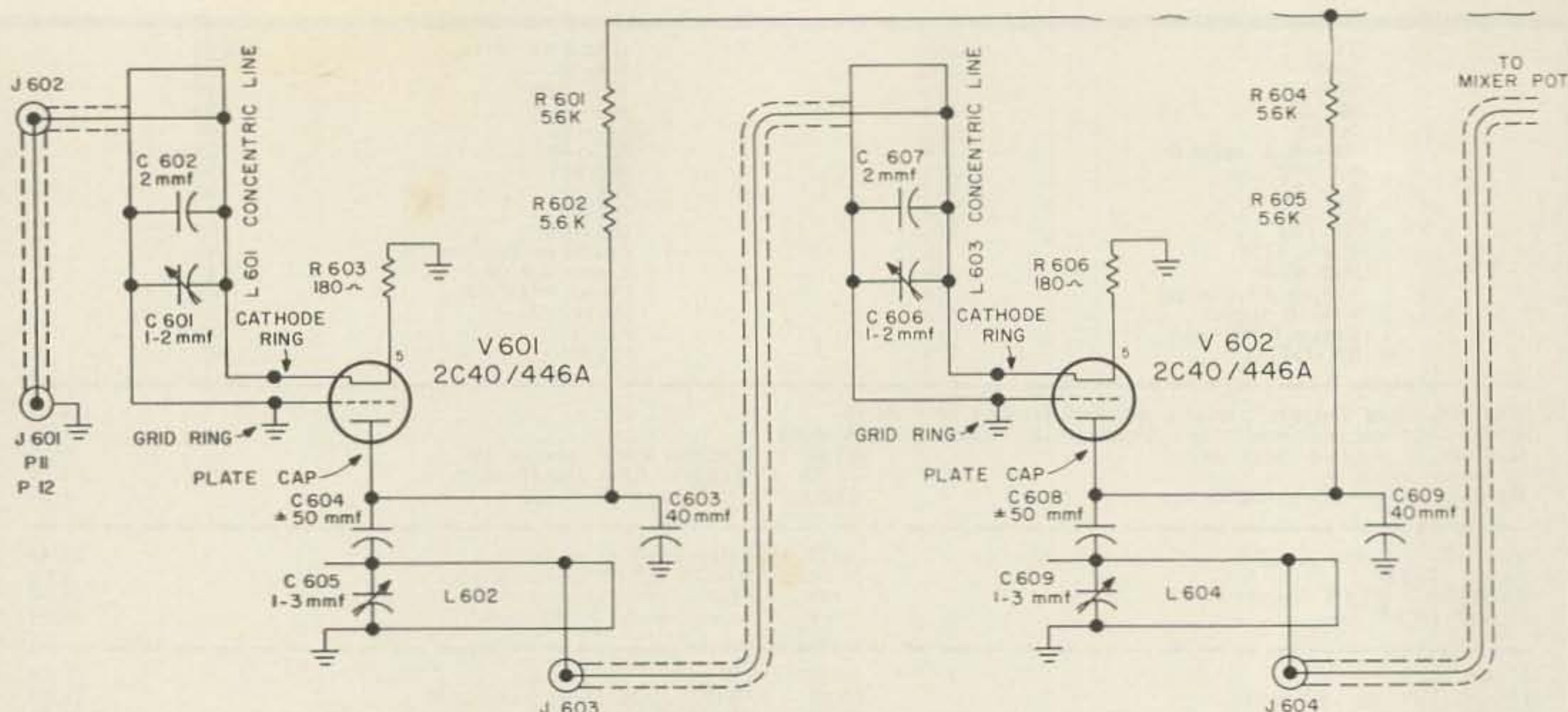
Before going further into details of the conversion, a word about the method of testing. It must be stated that no test equipment was available to actually measure the absolute noise-figure of the units. A simple diode noise generator was on hand and was used to start



Original unmodified schematic of the first 2 rf stages of the 46ADT unit.

with, but as stated earlier, our best method turned out to be actual "on the air" signals, coming from either K5JHG, located about 175 miles distant, or from W5HPT, located 40 ground miles away. On both these test signals, the antenna was nulled for a very weak signal in those cases when the band was treating us well. On other occasions, when signals were

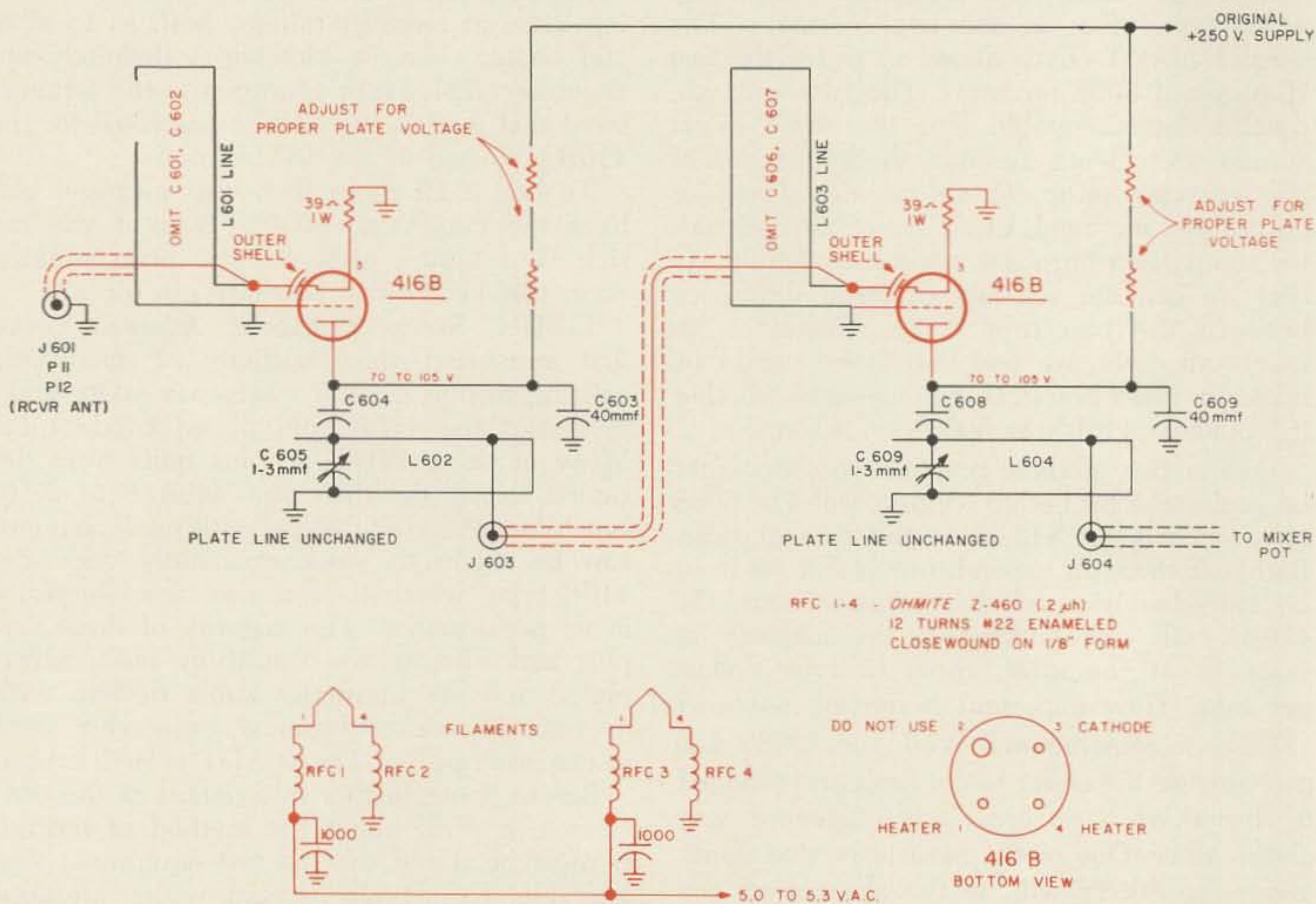naturally weaker, the nulling process was not always necessary on the 175 mile circuit. Both of these stations possess automatic "V" wheels and they would graciously put their transmitters on the air for extended periods while the various pre-amplifier combinations were tried. Ordinary 432 mc signal generators were of little value after one was in the ball park, as



Modifications in red of original circuit to use 416B type tubes.

the signal could never be counted upon to completely arrive via the antenna. These out-of-town signals have only one way to arrive and comparisons were easily made with front-end tuning and tap adjustments easily detectable.


This is admittedly not a very scientific approach, I suppose, but unless one can borrow hundreds of dollars worth of test gear to do the job, this practical S/N method just described will certainly work, and really, all this noise-figure business simmers down to just how good or bad our S/N ratio actually turns out to be on that QSO. At least, this "bonehead" method takes in the antenna and transmission line during the tests—something a noise generator can not very well do. It was definitely found that the proper time to compare anything in the way of rf amplifiers on 432 mc, was when the band was poor—not when the band was hot. Anything works then, and comparison is difficult with extremely strong signals.

Now about voltage and air on the 416B's. As far as electrode voltages go, this unit using the 416B tube was operated at reduced heater and plate potential. The heater voltage was set at from 5.0 to 5.3 volts ac, and the plate voltage

was adjusted from 70 to 105 volts dc. At these values, it was found unnecessary to provide air on the seals of the 416B's, even though the cavity construction bottles up the tubes pretty much. All tubes tried worked well and the average plate current with cathode resistor values of 39 ohms, was on the order of 4 to 6 ma.


Increasing the heater voltage to 6.3 volts ac, and the plate voltage to the recommended maximum of 250 volts dc, did not make any useful difference in the received S/N ratio. Using such increased voltage will necessitate air blowing on the tubes. As previously stated, this may not be the ideal way to measure, but invariably whenever a weak signal was received with the lowered electrode voltages, raising the heater and plate voltage did nothing at all in a practical way of helping the received signal against received noise. Conversely, with the higher voltages and air on the tubes, the received signal was nulled by the antenna to where it was just copyable (CW)—then decreasing the voltages did not put the signal under the noise as might be expected. K5JHG also made this type of test and reports similar results. Only when one gets ahold of a really "flat" 416B does increasing the volt-

DISCARD OLD TANKS (CATHODE) L 601 AND L 603

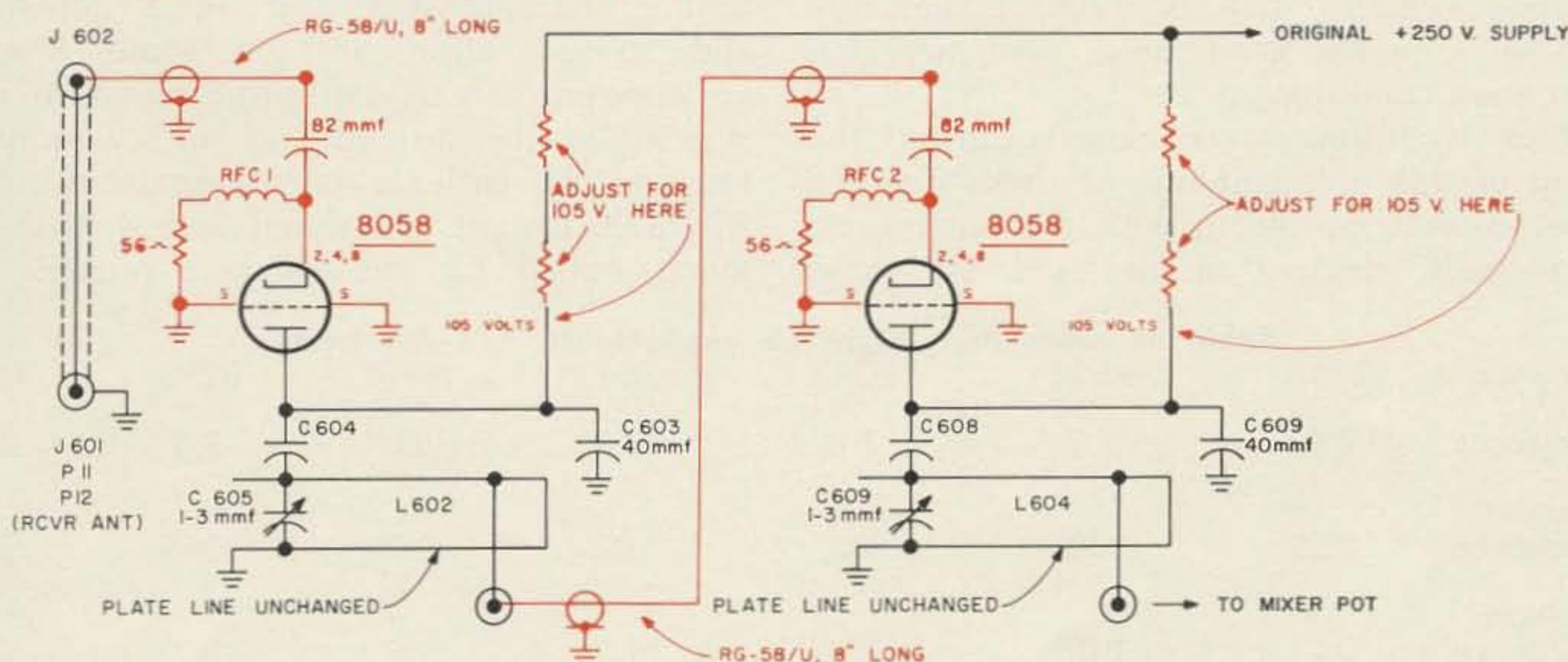


RFC 1-6 OHMITE Z-460 (2.2μh)
12 TURNS #22 ENAMELED
CLOSEWOUND ON 1/8" FORM

8058'S - PLATE, 105 V. at 8-10 Ma.

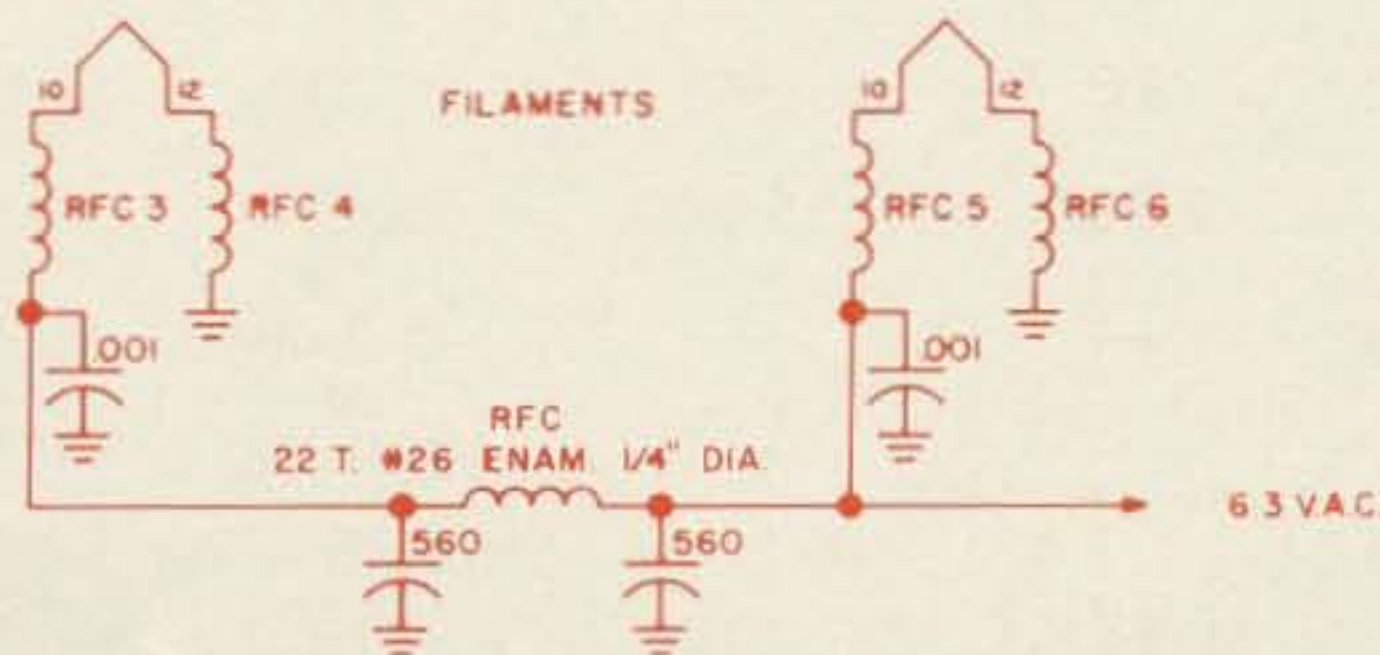

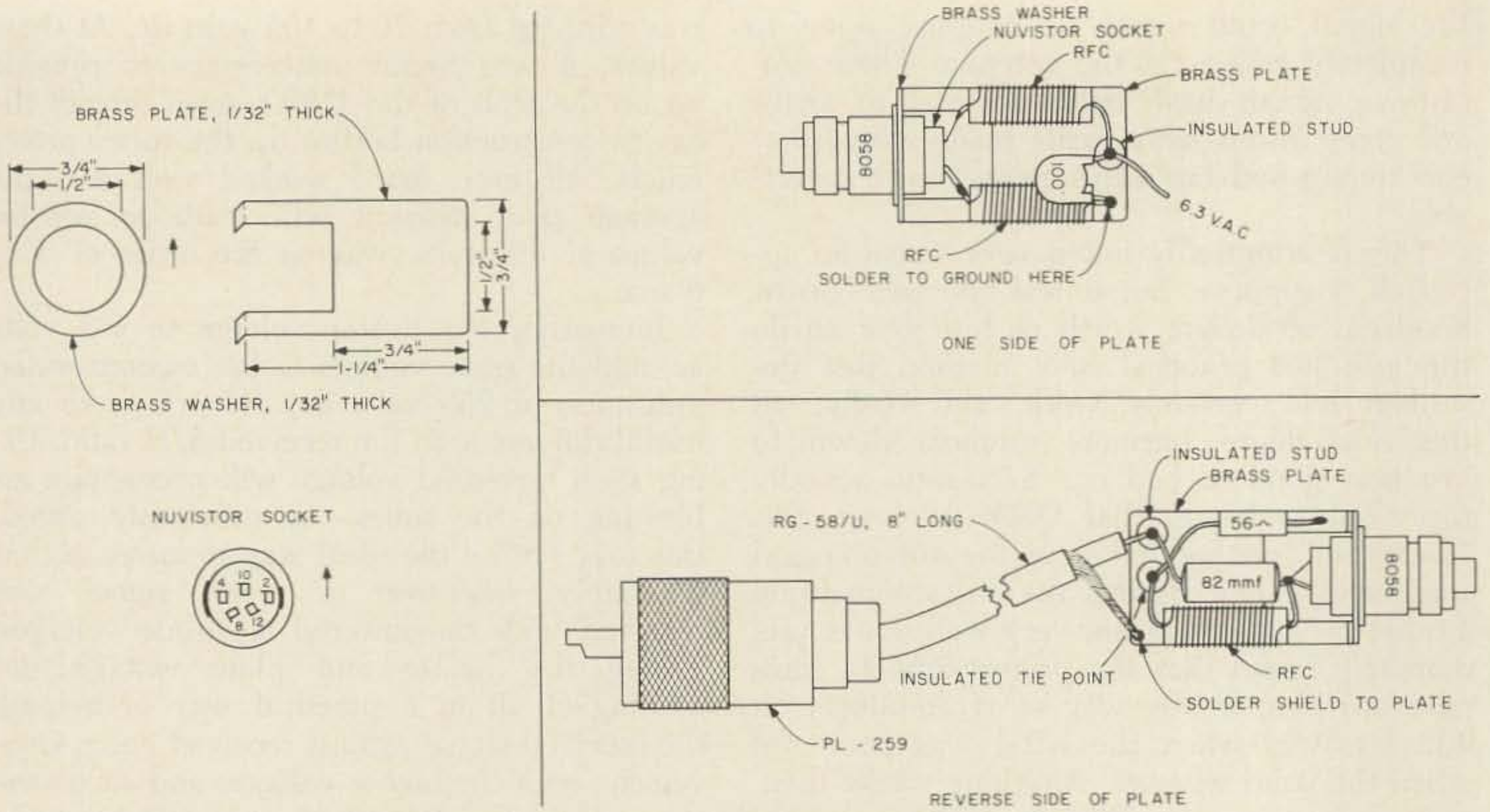Modifications in red of original circuit to use the 8058 Nuvistor tubes.



Details of dimensions to construct the 8058 brass adaptor plates.

ages help the situation. As long as the tubes were drawing from 4 to 6 ma of plate current, the results were always the same as far as a practical QSO was concerned. No doubt the transconductance is lowered with lowered electrode voltages, but as stated earlier, the 416B is a pretty good tube, even working under such conditions.

Other questions were raised during the testing of this unit and one of these was the proper way to couple in with the antenna to the cathode element of the 432 mc tanks

modified for the 416B tube. Checking the specs of the tube, it was found that the input capacity of the 416B is about 7.5 mmfd as against the 2.8 mmfd of the 2C40/446 type. Of course this will alter the original tuning characteristics and input impedance, and in an effort to get some kind of an answer, various tap positions were tried, starting at the ground end and working up towards the cathode point. Again using the 175 mile distant test signal and with the antenna nulled for the weakest possible CW

Table of tubes that might be available to 432 Mc hams

Tube Type	7768	416B	2C40	2C43	8058	6299	7077
Input capacitance in pf	6.0	7.5	2.8	2.8	6.0	3.5	1.9
Output capacitance in pf	.025	.0095	.02	.02	.046	.015	.010
Grid-Plate capacitance in pf	—	1.25	1.3	1.7	1.3	1.7	1.0
Transconductance in umo	50,000	50,000	5100	8000	12,400	15,000	10,000
Amp. Factor	225	300	36	48	70	115	80
Plate Resistance ohms	4500	6,000	6,860	6,000	5,600	9,600	9,000
N/F	4.5 db at 425 mc	3.0 at 400 mc 7.0 db at 1,300 mc	—	—	6.5 db at 450 mc	5.5 db at 450 mc	5.5 db at 450 mc
Freq. rating	—	To 4,000 Mc	To 3,370 mc	To 3,370 mc	To 1200 Mc	To 3,000 mc	To 1,200 mc

— Means unknown

signal, it was found that nothing was gained by tapping down the cathode lines towards the ground end. Invariably, the best S/N input coupling point was found to be right at the rf cathode connection of the tube. It is possible that a small variable capacitor inserted in the antenna lead may help in some cases, especially if some type of interference or spurious signal is present, but such an arrangement really did nothing on the particular antenna and transmission line used at this location. If for some reason, it appears advisable to isolate the antenna, a 50 mmfd or more capacitor can be left in series with the antenna lead, but the system should be checked with and without the capacitor to determine if it degrades the S/N ratio.

Should the vswr of the antenna-transmission line combination not be of the best, a re-entrant type of 432 mc resonant cavity will help in some cases.* This is inserted between the trans-

* See QST, February 1961, page 65.

mission line and the input to the 416B stage and could assist in offering the proper type of load to the input tube.

Under these conditions, then, it would appear that a broadly resonant 432 mc cathode circuit is about as good as one can do. As soon as the antenna is coupled in, attempts to actually tune such a broad input circuit with a small capacity element are of no avail.

Modification to 416B's

The photograph showing the 46ADT cathode tanks will reveal the changes to do the job. First off, the right hand tank is the unmodified component and it can be seen along with the original 446B tube in place in its plug-in-assembly. The tank on the left is the new 416B arrangement. This modification will necessitate a socket capable of accepting the 416B tube, which you will have to acquire along with the tube and presumably from the same source—and this new plug-in arrangement is to be made the same total length of the right hand unmodified unit. A piece of 1/4" copper tubing with the end slit is used to make the difference in total length of the structure and will fit into the contacting fingers of the 446B receptacle. All the necessary rf chokes, cathode resistors, etc. can be fitted in the inserting socket shell as formerly.

Comparing further the two tank pots, it may also be seen that the silver-plated contacting fingers have been bent inwards on the left hand unit to perform a snug fit when the 416B tube is plugged in, and these fingers of course engage the rf cathode shell of the tube. Other changes will be the clipping out of the small

"Your Friendly Supplier"

OFFERS

THE NATIONAL NCX-3 TRANSCEIVER



Here's the hottest sideband rig on the market—a complete SSB/AM/CW station with a conservative 200 watts of SSB punch at a price less than competitive transmitters or receivers only! Complete coverage of the 80, 40 and 20 meter phone and CW amateur bands with everything you need to make operating easy—VOX or push-to-talk operation, SSB/CW fast attack/slow decay AGC, S-meter/cathode current meter, grid-block break-in CW keying with adjustable release time, product detector for SSB and triode detection for AM, adjustable pi-network output and geared planetary tuning drive!

Power input—200 watts SSB PEP, 180 watts CW, 100 watts AM.

NCX-3 Transceiver	\$369.00 NET
NCX-A AC Supply/Speaker	110.00 NET
NCX-D DC Supply	119.95 NET

"Used Equipment June Special"

NATIONAL NC-183D	\$209.95
NATIONAL NC-400	595.00

WRITE FOR LATEST COMPLETE LIST

Evans RADIO

P.O. BOX 312 FONE 603-225-3358 CONCORD, N. H.

... NOW FROM BARKER & WILLIAMSON

"THE Vacationer"

A Portable Antenna for 2 through 20 Meters!



A lightweight, compact telescopic whip . . . mounts anywhere: motel, cottage, trailer, hotel, boat.

Supplied with interchangeable coils and shorting bar for 2 through 20 meters. Furnished with mounting bracket, base and coaxial line (less connector).

The telescopic whip is heavy-duty and chrome plated, the base is high impact polystyrene, a weather-proof boot protects the loading coil.

Low SWR on all bands.

Retracts to 18½ inches, fits into KWM2 carrying case.

COMPLETE UNIT
\$19.95

The Vacationer is ideal for the "ham" who travels—it can be installed and disassembled in minutes.

At leading electronic distributors

BARKER & WILLIAMSON, Inc.
BRISTOL, PA. / Phone 215-788-5581

REDLINE


Though we've advertised hundred-dollar converters, our biggest seller is our HJC-50. This little nuvistor converter is unbeatable for all but the most exacting applications. The circuit is simple . . . so simple you wouldn't expect that it took weeks and weeks of exhausting diddling before we had every aspect of it optimized. The idea is to have just the right amount of gain so you can drive your receiver well, but not enough to run into overload problems. The grounded-grid 6CW4 provides an extremely low noise front end and contributes greatly to the 3 db noise figure which we strive to better with each unit. A 6U8 crystal controlled triode oscillator and pentode mixer keeps the noise low and the gain up.

The 6.3 volts and 1 ampere and 150 volts at 40 ma required to power the HJC-50 can easily be borrowed from your communications receiver . . . or supplied by our HJS power supply which is designed to plug right into the HJC-50 (\$9.95).

The HJC-50 permits you to tune the six meter band by tuning your communications receiver between 14-18 mc.

The HJC-50 is available by direct mail from Redline, Jaffrey, New Hampshire. It is completely guaranteed: your money refunded if you want it back for any reason whatever.

Price: \$31.95.

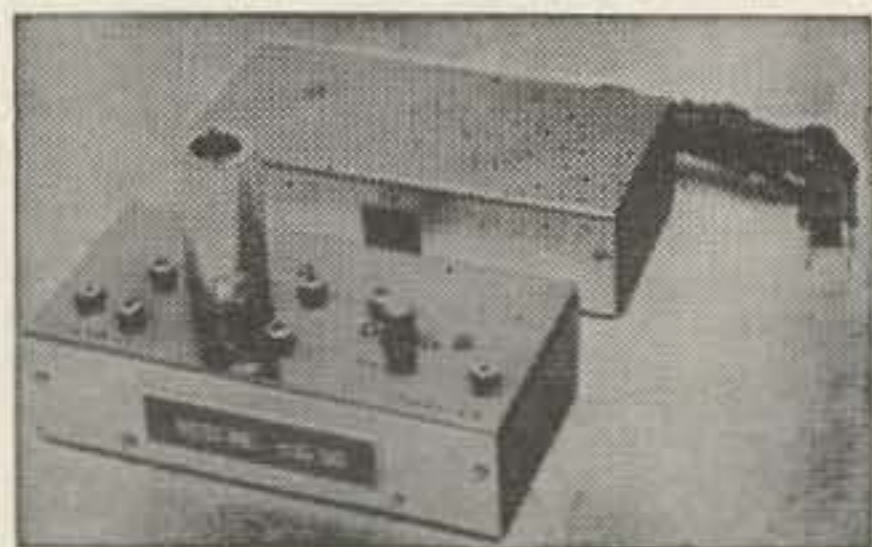

HJS

HJC-50

REDLINE

JAFFREY, N. H.

2.0 mmfd ceramic capacitor from the right hand unit, and the elimination of the two original cathode tuning discs, since the increased input capacitance of the 416B tube renders these unnecessary. Actually the left hand tank shows the variable disc still in but screwed back as far as possible. It is unnecessary and was later completely removed.

The last change concerns the input coupling tap. In the right hand unmodified tank, the antenna is tapped in close to the ground end of the cathode line. In the modified left hand unit, a new opening is drilled in the outer cylinder and the antenna coax input is secured to the rf cathode end of the line, as per the earlier discussion on the subject.

After these changes, the unit is rebolted to the chassis, power applied and plate circuits tuned. Nothing whatever is done to the output plate circuit located underneath the chassis. A slight returning of the plate control is all that is required. The 46ADT may be tested with this one modified rf tank or, if one desires, both rf stage tanks may be modified at one time and then rebolted to the unit for trial. Be sure to adjust the resistors in the plate circuit of the unit to produce the newly lowered plate voltage for the 416B's. Also take means to reduce the heater voltage on the two tubes to the lowered value previously given.

Results

A unit of this sort, using the two modified cathode tanks of the 46ADT was tested on a commercial broadcast STL link operating at 450.15 mc, ahead of a commercial GE receiver which used an 6AJ4 rf stage. The results were remarkable. A gain in excess of 20 db was expected and was achieved, but the improved S/N ratio of the received signal was impressive indeed.

Several hundred kilocycles of the band can be tuned before readjustment of the plate tuning is required. All in all, considerable improvement of the 416B's over the 446's will be immediately apparent.

Modifications Using the 8058's

Should the nuvistor 8058's be available to you and it is desired to utilize this tube type, proceed as follows:

First off, discard the two cathode tanks entirely. On second thought, do not discard but keep around for a quick comparison using the just modified 416B scheme. Merely unbolt from the 46ADT chassis. If you chose to disregard the 416B route, the original 446B tubes and tanks can also be bolted back and

tried at any time to get a comparison with the new 8058's.

W5QOA of Dallas dreamed up the following method for a simple and effective mechanical mounting to replace the 416B's or 2C40A's in the 46ADT. The idea here will be to construct a couple of adapters which will mount the 8058's and their necessary component parts and these adapters to plug into the plate circuit chassis holes left vacant by the removal of the two cathode tanks (L-601 and L-603). Two photographs are shown that should cover the details rather well. One photo shows the adapters before plugging in, and the other photo shows the adapters plugged in and operating.

To build the adapters, refer to the sketch showing details of dimensions. A couple of pieces of flat brass stock, $1\frac{1}{4} \times \frac{3}{4}$ inches and about $1/32$ " thick should be fashioned, as per the sketch, to mount the various components. These plates will then be soldered to brass rings or washers carrying proper dimension to allow the nuvistor sockets to be mounted therein.

The three necessary rf chokes, two capacitors and one resistor will all mount on each brass plate. RF input to the stages will arrive

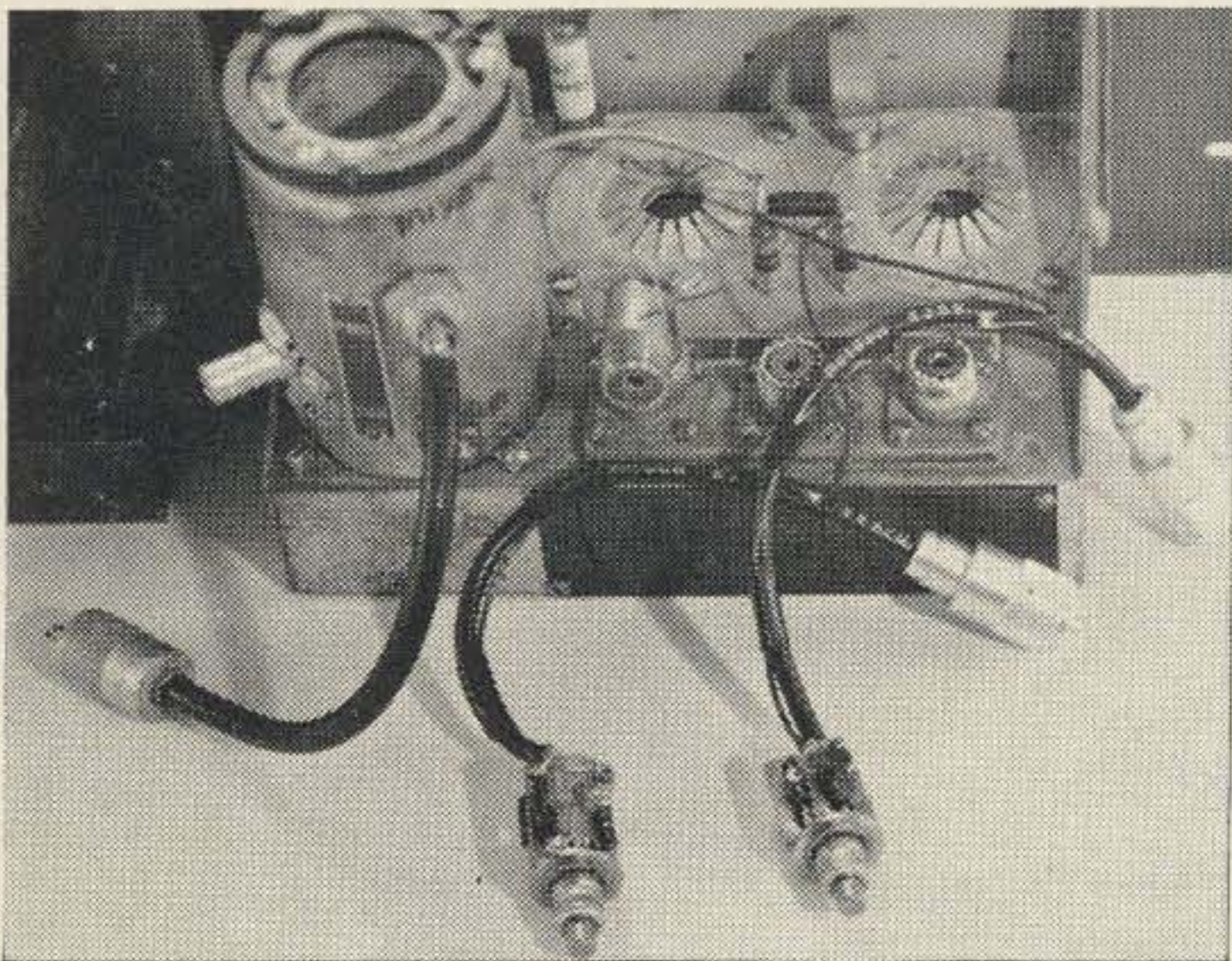


Photo showing the 8058 adapters before plugging in the 46ADT chassis.

The two brass plates carrying the necessary components and the nuvistor sockets are visible. Also the silver-plated fingers on the grid grounding discs on the chassis can be seen to be bent upwards thereby effectively grounding the adapters when they are plugged in.

The rf coming into the 1st stage is via the 8 inch length of RG-58/U and the rf coming into the second stage is via the same sort of deal.

The mixer in this photo is not used. This was to test the 2 rf stages only.

A couple of spring brass clips mounted on stand off insulators (up close to panel) are used to hold down the adapters when they are plugged in.



This photo shows the 8058 adapters plugged into the 46ADT chassis.

The silver-plated fingers of the grounding disc grounds the adapters (which grounds the grids of the 8058).

The spring brass clips or straps hold down the adapters firmly.

via a piece of RG-58/U coax cable about 8 inches long. Ordinary PL-259 type UHF plugs are used to connect to the chassis connectors of the 46ADT, as were the previous used tubes. Insulated tie-points on the brass plates provide means for mounting the parts.

The photograph showing the adapters unplugged will also reveal how the silver-plated fingers of the grid grounding discs on the chassis have been bent upwards a bit to firmly engage and ground the adapters holding the nuvistors sockets. A couple of spring brass strips mounted on the tops of the stand-off insulators are used to hold firmly down the adapters into the chassis holes. No shielding between the two 8058 stages will be necessary. Everything is stable. The two leads taped to the RG-58/U pieces of coax are the heater leads. No changes are necessary in the plate lines L-602 and L-604. The 8058 plate caps are the same diameter ($\frac{1}{4}$ ") as the 2C40's or the copper tube extensions of the 416B's.

The series resistors in the plate supply leads should be chosen to allow 105 volts to feed the 8058 plates. Each tube will draw approximately 10 ma. The heater voltage should be the full 6.3 vac. No air is necessary on the tubes.

After the adapters are plugged in and power applied, retouch the plate tanks L-602 and L-604 for resonance and this will complete the job. The 8058's appear to be slow heaters, so it would be well to allow a few minutes warm

up time to take full advantage of the capabilities of the tubes.

These are smooth working bottles and should have quite long life. No difference in performance has been noted after more than six months service. The RCA tube manual lists the N/F of the 8058's at 450 mc as 6.5db. The only reference to noise figure of the 416B's at this frequency was furnished by W5LUU of San Antonio as 3.5 db. This was

from an article in RCA Review for December 1958. To repeat; No practical difference could be noted between the two rf stages of 416B's and the two stages of 8058's. A listing of several types of tubes that are more or less available to UHF enthusiasts are listed. These are tabulated for rather rough comparisons and the information was collected from here and there. Additions or corrections to the list would be welcome.

Mikes, Handsets, Phones, Speakers

Gerry Stephens W9SLM
RR 2
Sheldon, Ill.

The following Specs were compiled to aid in the selection and use of various pieces of SURPLUS equipment.

Handsets

Type	Cord	Conductors	Plug	Remarks
TS- 9	9 ft.	3	terms	Unit includes PTT switch. Part of telephone EE-8.
TS-10	6 ft.	2	clips	2 sound powered phones in parallel. Impedance is 350-600 ohms. No PTT.
TS-11	6 ft.	4	PL106	Cord equipped with built in rf coil with PTT switch. Part of SCR-195.
TS-12	9 ft.	3	terms	Similar to TS-9 except has hanger to hook on box. Used with EE-91.
TS-13	5 ft.	4	PL-55 PL-68	Similar to TS-11 but has 750 ohm res.
TS-14	5 ft.	4	PL-204	Similar to TS-9 except no PTT switch. Part of SCR-561.
TS-15	5 ft.	4	PL-55 PL-68	Similar to TS-13. Different SW and no resistor. Part of SCR-300.
Type L	4½ ft.	2	—	Similar to TS-10 except impedance is 350 ohms.

Loudspeakers

Type	Impedance	Remarks
LS- 1	—	4" PM type, part of BC-603.
LS- 2	6	6" PM type in walnut cabinet. Part of SCR-13.
LS- 3	8000	6" PM type in 8 x 8 steel box. Part of SCR-299.
LS- 6	—	4" PM type with baffle and horn. Part of PA-4.
LS- 7	4000	4" PM type with input trans. 3 ft. cord.
LS- 9	250	Similar to LS-3 except lower impedance.
LS-11	250	Similar to LS-7 except lower impedance.

Mikes

Type	Res or Imped.	Plug	Remarks
T-17	60	PL-68	Hand held carbon, with PTT switch.
T-21	—	—	Condensor type, with 2 stage preamp built in base. Part of GR-3.
T-24	60	PL-106	Carbon mike, Part of headset SCR 194-195 and 543.
T-26	60	PL-58	Commercial telephone type carbon, with arm. Part of SCR-197.
T-30	120	PL-291	Carbon throat type, 2 units in series on neck piece.
T-32	40	—	Carbon mike on desk stand with PTT sw. Part of SCR-188A.
T-34A	200	PL-179 JK-26	Magnetic type, MC-233 mike. Part of SCR-522 and SCR-542.

T-35	75	PL-51	Similar to T-26. Part of chest set TD-1.
T-36	50	—	Carbon type with PTT SW. Part of PA system PA-4.
T-38	40	PL-58	Carbon mike with PTT SW. Part of SCR-197.
T-42	—	—	REPLACED by ANB-M-CL.
T-44	200	PL-179	Magnetic type for use in oxygen mask.
		JK-26	Part of SCR-522 and SCR-542.
T-45	60	PL-291	Carbon type, anti-noise lip mike.
T-50	21,000	Amphenol	Moving coil type with PTT switch. Part SCR-299, SCR-300
		MC-3M	and SCR-499.
ANB-M-C1	60	PL-291	Carbon type mike MC-254, may be used in T-17 and T-30.
			Replaces T-42.

Headsets (Phones)

Type	Imped.	Plug	Remarks
P -11	24 K	PL-5	Double receiver headset.
P -12	24 K	PL-5	Double receiver headset, will replace P-16.
P -13	512	PL-51	Double receiver headset with cushions.
P -14	24 K	PL-5	Double receiver headset with cushions. Part of SCR-189, 190, and 199.
P -16	24 K	PL-5	Similar to P-12 except has longer waterproof cord. Part of SCR-163.
P -18	24 K	PL-55	Similar to P-16 except different plug.
P -19	24 K	PL-55	Similar to P-14 and P-18 except has PL-55 plug and MC-114 cushions.
P -21	24 K	PL-55	4 Receivers on 2 headbands, one unit each headset in series. For 2 operators to listen to 2 different channels.
P -23	8000	PL-55	Double receiver headset with MC-162 cushions.
HS-16A	520	HB-1	Double receiver headset, used with code practice equipment.
HS-18	8000	PL-54	Fits crash helmets. 2 receivers with cushions. Replaced by HS-30 and HS-38.
HS-20	470	PL-55	Single receiver headset. Part of TG-5A and TG-5B.
HS-22	8000	PL-55	Double receiver headset, with cushions. Part of SCR-194.
HS-23	8000	PL-54	Double receiver headset. Replaced by HS-30 and HS-33.
HS-24	512	PL-58	Sound-powered type double receiver with cushions.
HS-29	256	PL-55	4 rcvrs on 2 headbands, used in DF installations.
HS-30	256	none	Double rcvr insert type. With ear inserts M-300.
HS-33	600	PL-354	Double rcvr headset with cushions MC-162.
HS-38	600	PL-354	Double rcvr for use in Air Corps helmets.

(W2NSD from page 4)

ers attached and be tuned up, plus hundreds of other major and minor details. As I was brooding over the amount of work to be done before the contest and my lack of time to do it, a couple fellows from the Waltham Radio Club dropped in and offered to set everything up in exchange for using the station during the contest. It was a deal.

Later on I hope to have our set up on the Mountain too, furnishing a TV signal of good strength nightly down through New York and New Jersey. We also expect to be set up on wide band FM on six, two and 420 mc. If we have enough visitors to help with hooking things up and operating we should keep the east coast fairly busy this summer on VHF's.

The Institute

While at the Dayton Hamvention I gave a talk about the Institute of Amateur Radio, explaining the basic reasons for its founding. I've expanded a bit on this talk and it will be

found on page 92. One of the values of the Institute is that it puts pressure on the ARRL to do things that it otherwise might avoid. The sudden cooperation shown in the Santa Barbara and Denver legal cases when support was offered by the Institute are cases in point. Everyone has gained as a result of the Institute action.

Membership in the Institute is \$10 per year . . . every cent accounted for and spent carefully for the benefit of amateur radio.

ARRL Board Meeting

The directors and officers of the ARRL gathered at Newington on May first. You'll read it in general in the June QST and in more particular in the extra fine print in July. Perhaps I can save you some time. Of the 52 motions placed before the board 47 were carried *unanimously*, two died of no seconding, one was withdrawn, one was tabled and *one* received one dissenting vote. Fabulous performance gentlemen. I sincerely hope that

(Turn to page 91)

Regulated Power Supplies

Jim Kyle K5JKX
1236 N.E. 44th St.
Oklahoma City, Okla.

As SSB grows in popularity, more and more of us are becoming exposed to regulated power supplies—an item once found only in the very well equipped laboratory. But not too many of us are actually familiar with just how these devices work, and the available literature does little to lift the fog.

Which is, in its way, no small pity—since the regulated power supply is a quite handy device for many purposes other than controlling screen voltage on a high-power linear! Typical characteristics of a good electronically regulated supply include the ability to set output voltage to whatever you want (within reason), fantastically low ripple (usually measured in millivolts), and exceptionally low output impedance. These characteristics make such supplies almost perfect for VFO use, low-level audio, and of course general experimentation where a variable voltage is needed.

The one thing, apparently, which makes a regulated supply a bit difficult for many people to fully understand is simply the way in which they are usually drawn, and the unfamiliar terminology employed in talking about them. Let's start from scratch, building one up as we go, and see if we can't lift the fog.

The starting point is the circuit shown in Fig. 1; as you can see, it's an ordinary cathode follower, but is dc coupled throughout. It's almost obvious that the voltage across R_L ,

denoted on the drawing as E_o , will be equal to the voltage applied to the grid multiplied by the gain of the stage.

Cathode-follower gain, of course, is always less than one. A close approximation to the actual gain figure may be obtained by calculating the gain the tube would have under the same operating conditions but with the cathode resistor in the plate circuit instead, then using this gain figure in the formula: gain/(1 plus gain). The result, which will always be less than 1, will be the gain of the cathode follower. If "conventional gain" is as high as 9, cathode follower gain will be at least 0.9.

The circuit of Fig. 1 allows us to set the output voltage to almost anything we want, within limits. Since the tube gain will always be less than 1, obviously no setting of the grid pot will let us get more voltage out than we put in. Similarly, since the tube cannot be cut off by its own plate current, output voltage can never drop to zero. However, if we assume a constant gain of 0.9 for the tube and adjust the resistor from top (R_a equals zero) to mid-point (R_a equals R_b), and at the same time assume a 300 volt input, we can see that with R_a equal to zero we get an output of 270 volts, while with R_a equal to R_b we get an output of 135 volts.

Note that we are talking about *voltage* rather than power; this has an important additional effect. If our tube V_1 can handle, say, 100 ma, we can control the voltage of this 100 ma current with a tiny replacement-grade volume control which by itself couldn't handle more than 5 to 10 ma!

Since this circuit, as shown, allows us to *vary* the output voltage at will we've dubbed it a "variator." However, it also provides a measure of regulation at the same time. Let's see how this can be:

You will notice that the output voltage is

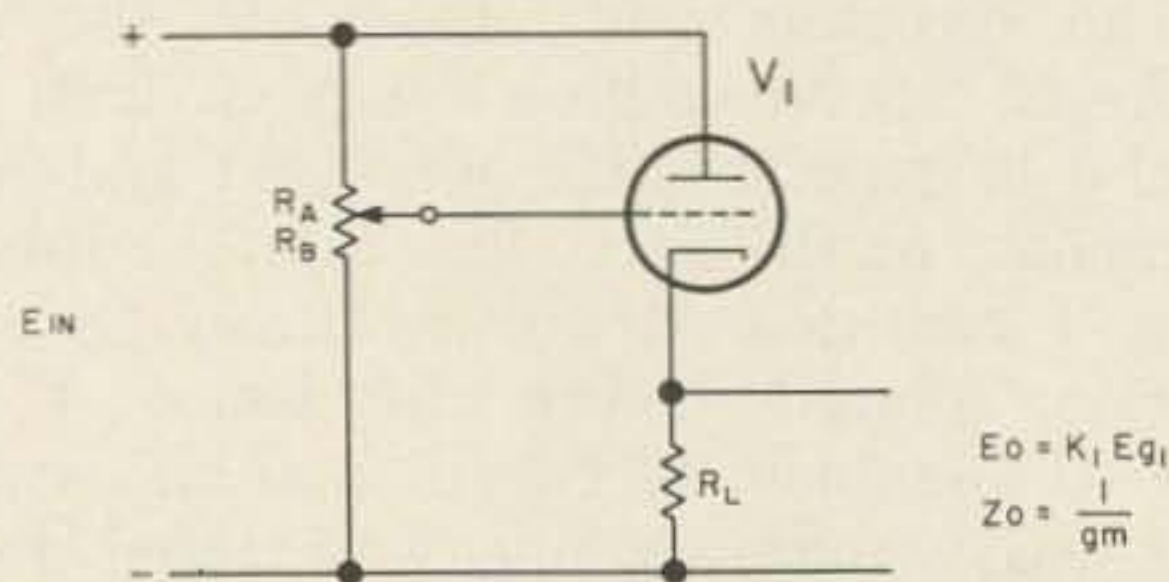


FIGURE 1

Cathode-follower "variator."



DX CHASERS

HEAVY 8X10 QSO RECORDER IS BEST DX AWARD FOR WALL. SIMPLY TURNING SPINNERS ALWAYS SHOWS EXACT NUMBER COUNTRIES QSOED AND QSL'D. ALSO, EXPLAINS DX CHASING TO VISITORS AT A GLANCE. \$2.50 PPD.

VIKING PRODUCTS

DAVE KUHINGOLA **WIHOZ**

ALL HAMS UR CALL AND NAME GOLD EMBOSSED ON HANDSOME PEN AND PENCIL SET. IDEAL GIFT FOR THE CHIEF OP. SPECIFY RED, BLUE, WHITE OR BLACK. REQUEST SPECIAL PRICE ON QUANTITIES WITH DUPLICATE LETTERING FOR GROUP EVENTS. PRINT NAME AND CALL CLEARLY. PEN OR PENCIL ONLY \$2.75 PPD. PAIR \$4.50 PPD.

DEPT. B-3, 196 SO. MAIN ST., ORANGE, MASS.

taken from a cathode follower circuit. One of the major characteristics of a cathode follower is its low output impedance. This, in turn, is a way of saying that changes in load have little effect upon the output voltage of the cathode follower. But that last statement also describes a power supply with good regulation!

One of the more professional ways to measure or specify the regulating ability of a power supply is to specify its output impedance. So far as direct current is concerned, most ordinary supplies have fairly high output impedance. A voltage drop of 100 volts between no-load conditions and 100 ma drain represents an output impedance of $100/0.1$ or 1000 ohms. But in practice, this would be a pretty good HV supply!

The output impedance of the cathode follower, on the other hand, is approximately equal to 1 divided by the tube's transconductance. If the gm of the tube is 4,000 microhms, the output impedance would be $1/0.004$ or 25 ohms. This is only 1/40 as great as the ordinary supply—which means 40 times better regulation.

But, though the simple circuit of Fig. 1 does provide adjustable output voltage and a



FREQUENCY MULTIPLIER

SOLID-STATE

MODELS	1432	2132
\$54.95	144	216
amateur net	to	to
	432	432
	mc	mc

- ★ SMALL SIZE: 3 X 5¼ X 2¾ INCHES.
- ★ NO POWER SUPPLY REQUIRED (varactor is self powered).
- ★ COMPATIBLE WITH AM, FM, & CW.
- ★ 20 WATTS RF IN PRODUCES 12 WATTS OUT (nominal).

VHF ASSOCIATES

P. O. BOX 22135
DENVER, COLORADO 80222

TEST EQUIPMENT

TEKTRONIX, H.P., G.R., MEASUREMENTS,
MILITARY, ETC.

BUY—SELL—TRADE: SEND FOR CATALOG

J. R. Tucker, Box 206 Garland, Texas

6 METER CONVERTER WITH NUVISTOR PRE-AMP

Unbeatable performance at an unbeatable price. Only \$10.00 ppd. Complete with 6U8A, 6CW4 tubes and choice of 36 mc. crystal for 14-18 mc. output or 49.4 mc. crystal for broadcast band output. Fully assembled, tested and guaranteed. Sensitivity .1 microvolt. Noise figure 2.5 db.
VANGUARD ELECTRONIC LABS
190-48—99th Ave.

Dept. H-6
Hollis 23, N. Y.



"BEAMED-POWER" ANTENNAS and ANTENNA SYSTEMS

The Choice of the Discriminating
Communication Engineer . . . the
Man who Never Settles for Any-
thing Less than THE-VERY-BEST!

You too—can enjoy world renowned TELREX performance and value! Send for PL64 condensed data and pricing catalog, describing the lowest priced antennas on the market, in relation to materials and performance! Expanded data sheets—including your favorite band, are also available.

ANTENNAS
SINCE
1921

COMMUNICATION SYSTEMS

telrex LABORATORIES

ASBURY PARK 25, NEW JERSEY, U.S.A.

with a *line*
**MATERIAL DIFFERENCE
—IN USE IN 135 LANDS!**

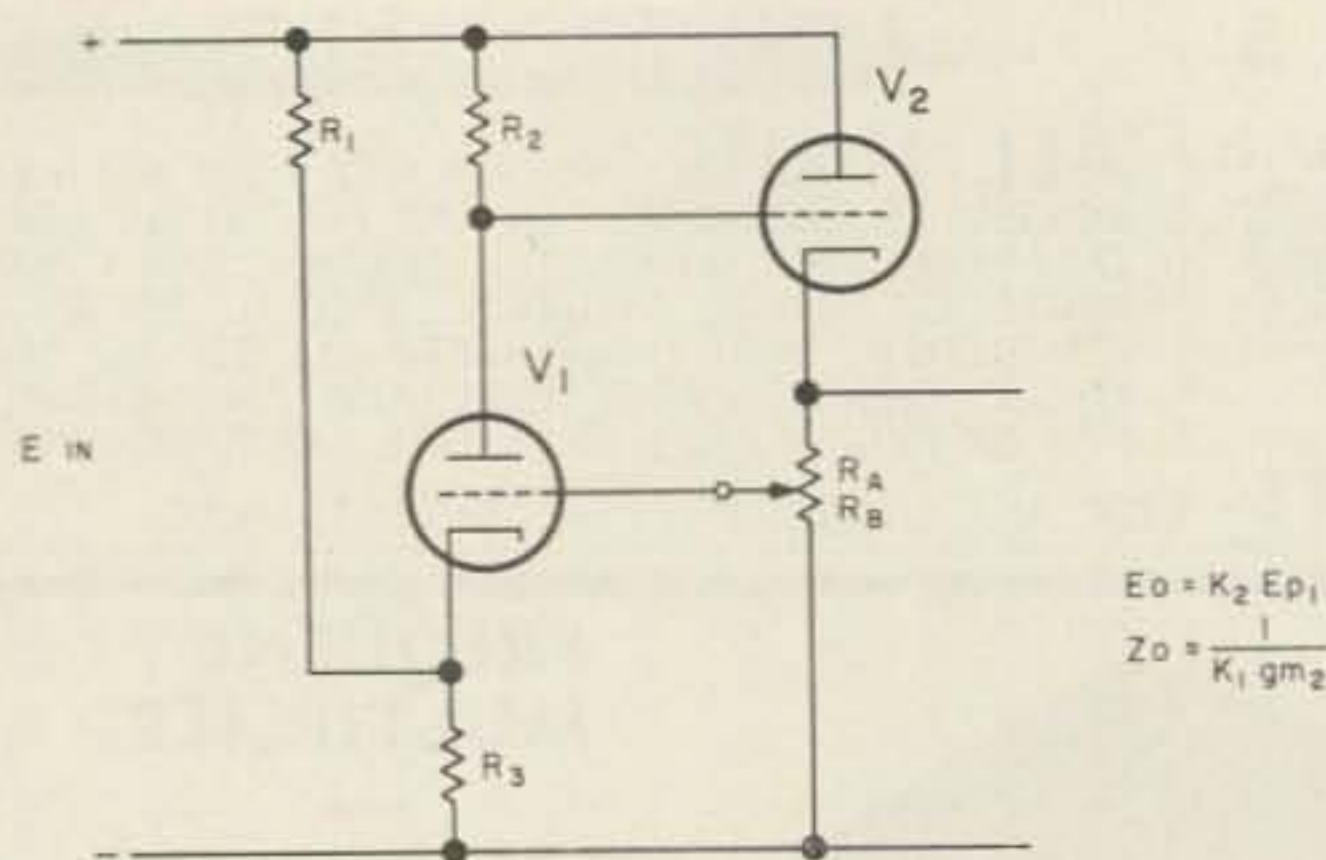


FIGURE 2

Transforming to become automatic "variator."

measure of regulation, it's not a true electronically regulated supply. Let's make it a little more automatic, and progress down the road to the fully regulated version.

A moment's thought will show you that the variable resistor made up of R_a and R_b in Fig. 1 could be replaced by a fixed resistor in series with a vacuum tube; variation of the tube's grid voltage would then change the effective value of R_b , and the result would be an effect identical to twisting the pot.

Fig. 2 shows how this substitution is made. V_1 is substituted for R_b while R_2 replaces R_a . The divider made up of R_1 and R_3 is a "stiff" bleeder designed to hold the cathode voltage of V_1 at an approximately steady value. R_L is now a pot instead of a fixed resistor as in Fig. 1, allowing us to set the standing grid voltage on V_1 to any value we wish.

The output voltage, E_o , is still equal to the grid voltage on V_2 multiplied by V_2 's gain; since the grid of V_2 and the plate of V_1 are tied together, any change of voltage on the grid of V_1 will cause a corresponding change in output voltage.

But since an amplifying stage (V_1) is involved, the direction of the change will be reversed. If V_1 's grid goes slightly positive from its starting value, current flow in V_1 will increase, thus lowering the voltage at V_1 's plate and V_2 's grid, which will in turn reduce the current flow through V_2 , which *reduces* the positive voltage across R_a/R_b , minimizing the change in voltage at V_1 's grid (which started the whole chain).

This is a classic example of error-correcting feedback; any external action which tends to change the output voltage causes the feedback chain just described to become active, and the result is that the actual change in output voltage is held to a minimum.

The purpose of R_1 and R_3 holding the cathode at a fixed positive voltage is to provide a wider range of control. If the ratio of

R_1 and R_3 is such that cathode voltage is, say, 105 volts, then the grid voltage set by R_a/R_b can vary either side of 105 volts. The net grid-cathode voltage, which is what determines current flow in V_1 , will be either positive or negative, depending on which side of 105 the grid voltage lies.

If the grid is at 100 volts, the net bias would be -5 . Let's assume that this is the design point, and that V_1 allows 1 ma of current to flow at a bias of -5 . Let's also assume that we want an output voltage of 200, and that the gain of V_2 is 0.9. E_{in} will be 350 volts.

For the output voltage to be 200 with V_2 's gain set at 0.9, we know the voltage at V_2 's grid must be $222\frac{1}{4}$ volts. For the grid voltage to be $222\frac{1}{4}$, we must drop $127\frac{1}{4}$ volts in R_2 . And we assumed 1 ma of current flow in V_1 at the design point. This means that R_2 should be 127,750 ohms; either a 120K or a 130K resistor would be fine.

For the voltage at V_1 's grid to be 100 when the output is 200, obviously R_a and R_b should be equal.

Now let's see what happens, since we didn't quite hit the proper value for R_2 for practical purposes. If our regulation is working properly, the output should *still* be at 200.00 volts.

We start with 350 volts in, 120K at R_2 , and 1 ma of current through V_1 . This gives us 230 volts at the grid of V_2 , which we then multiply by 0.9 to get 207 volts out. Since R_a and R_b are equal, half of this 207 volts or 103.5 volts shows up at the grid of V_1 .

Subtracting V_1 's fixed cathode voltage of 105 volts from this 103.5 volts gives us a net grid bias on V_1 of -1.5 volts instead of the -5 volts which fixes current through the tube at 1 ma. With less than half the bias, the tube's plate current starts to rise. But as it increases, the voltage drop through R_2 increases also, reducing the voltage at the grid of V_2 and consequently increasing the net bias.

For example, at the instant that V_1 's plate current is 1.01 ma, the drop through R_2 is 121.2 volts, which leaves 228.8 volts at V_2 's grid. This makes the output voltage 205.92; V_1 's grid voltage becomes 102.96 volts, and the net bias on V_1 is $(102.96 - 105)$ or -2.04 volts. The 10 microampere increase in plate current has increased the net bias by 0.54 volts.

As the plate current continues to rise, the net bias rises with it; when plate current is 1.06 ma, the drop through R_2 is 127.20 volts which leaves 222.8 volts at V_2 's grid. Resulting output voltage is 200.52, which results in a net bias on V_1 of -4.74 volts. This value is very close to the design point; in practice, the plate



Here's Steve W9EAN (Manager of our Milwaukee Store) trying out the "Push Button" Tuning feature of the New Squires-Sanders Receiver.

We Carry the Complete Clegg - Squires - Sanders Line

Figures To Right of Prices
Show Monthly Payment After—

\$5 DOWN

DESCRIPTION	PRICE	
SQUIRES-SANDERS, INC.		
SS-1R 3.5 to 30 MC Receiver	\$895.00	\$32.13
SS-1HS Speaker	35.00	
SS-1S Noise Silencer	135.00	4.69
GLEGG LABORATORIES DIVISION		
Zeus, 6 & 2 meter Transmitter, Modulator/Power Supply	\$745.00	\$26.72
Interceptor B, 6 & 2 meter Receiver	495.00	17.69
Interceptor Allbander, HF Frequency Tuner/Speaker	129.95	4.51

DESCRIPTION	PRICE	
99'er, 6 meter Transceiver	179.95	6.31
Thor 6, Transceiver RF	260.00	9.20
Thor 6, model 417 AC Powers Supply/Modulator	139.95	4.87
Thor 6, model 418 DC Power Supply/Modulator	159.95	5.59
Venus, 6 meter SSB Transceiver	495.00	17.69
Venus, Model 416 AC Power Supply	110.00	3.79
Lo-Pass Filter, Model 372	14.95	

GET OUR TERRIFIC TRADE IN OFFER

Find out what your trade in gear is really worth . . . write and tell us what you have to trade and the make and model you want.



AMATEUR ELECTRONIC SUPPLY

MILWAUKEE 8, WIS.

3832 West Lisbon Ave. — Ph WE 3-3262

Hours: Mon & Fri — 9 am to 9 pm
Tues, Wed, Th — 9 am to 5:30 pm
Sat — 9 am to 3 pm



Steve W9EAN

CHICAGO 31, ILL.

6450 North Milwaukee Ave. — Ph RO 3-1030

Hours: Mon, Wed, Th, — 12 pm to 9 pm
Tues & Fri — 12 pm to 5:30 pm
Sat — 10 am to 4 pm



Doc W9HJS

ORLANDO, FLA.

19 Azalea Pk. Shopping Ctr. — Ph 277-8231

Hours: Mon, Wed, Th, — 12 pm to 9 pm
Tues & Fri — 12 pm to 5:30 pm
Sat — 10 am to 4 pm



Phil W9DVM/4

IMPORTANT!

Send all Mail Orders and Inquiries To: Terry, W9DIA at our Milwaukee store, c/o Department (7)
Get Our Quote Today. No Obligation

Terry: I want to buy _____
I have to trade _____ (what's your deal?)

STAY ON THE AIR PLAN

Not only will I give you a terrific trade-in allowance, but you can keep your equipment until you receive your shipment.

Ship Me: _____

I enclose \$ _____ and will pay balance
 C.O.D. 1 Year 2 Years 3 Years
(10% deposit)

If ordering on terms, please list following information on separate sheet and enclose with this order: Name, address, age, married? children? Employed by? Salary? How long? Own or Rent Home? To whom renting? or buying from? Wife employed? Own car?—who buying from? Three to five credit references. The more information you give, the faster we can approve your credit.

EVEN IF YOU'RE NOT ORDERING TODAY, SEND ABOVE INFORMATION FOR ATTRACTIVE CREDIT CARD

NAME _____

ADDRESS _____

CITY _____ STATE _____

Check for latest reconditioned bulletin.

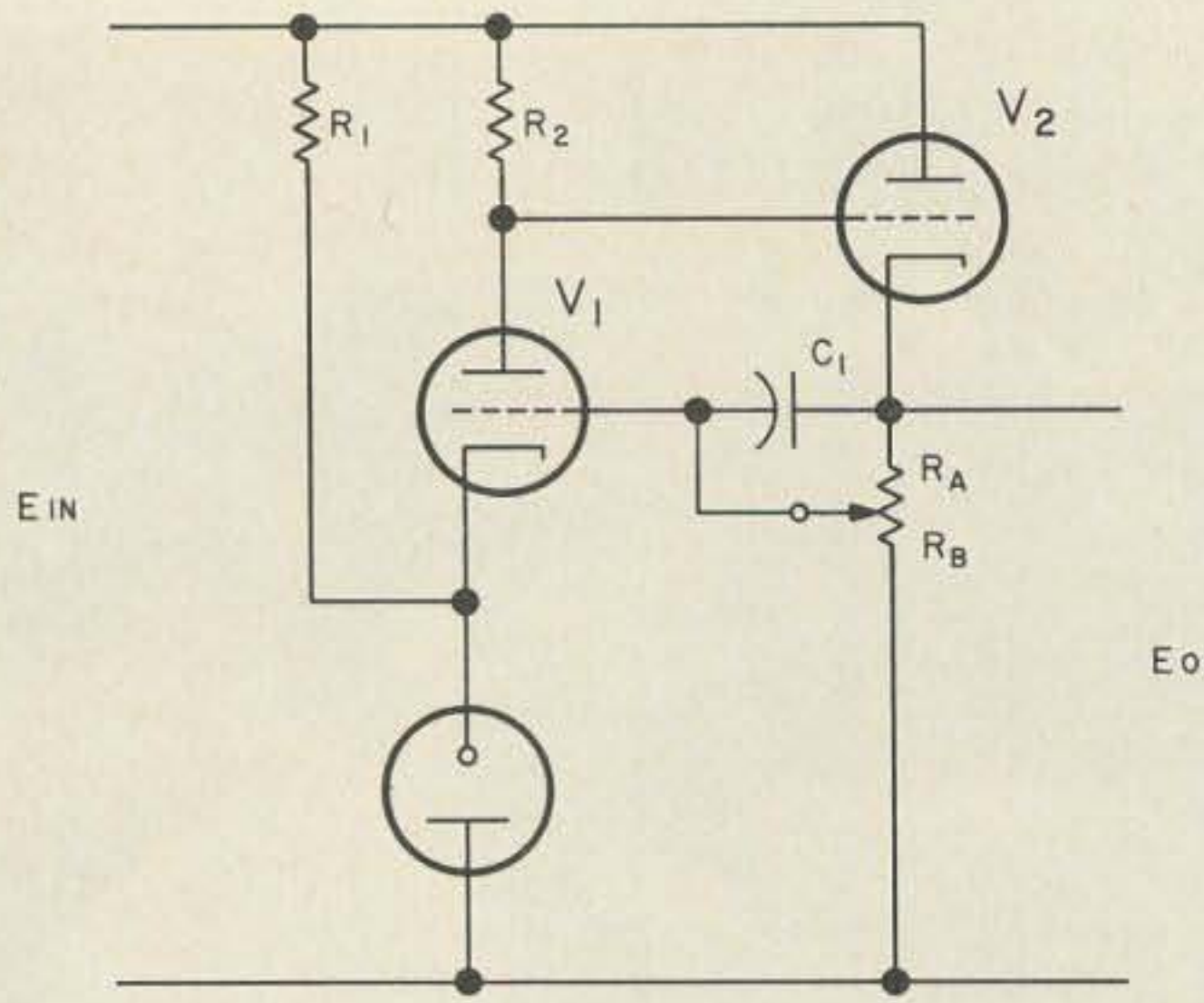


FIGURE 3

Two changes make it a regulator.

current would probably rise on to 1.06458 ma and give an output voltage of 200.01. For all practical purposes, the regulation is complete.

However, even the "automatic" circuit of Fig. 2 is not a fully regulated supply although it does regulate against any changes in load. If the source voltage rises by 10 percent, the output voltage will follow by the same percentage, because the *reference* used to determine net bias voltage on V1 is only a simple voltage divider.

Replacing R3 with a VR tube, to hold the reference voltage constant regardless of changes of line voltage or anything else, turns the circuit into a fully regulated supply. The change is shown in Fig. 3.

Another change is also incorporated in Fig. 3—the addition of capacitor C1. The purpose of this capacitor is to insure that any instantaneous change of output voltage (such as an ac signal or ripple on the line) goes into the correction loop at full strength rather than being attenuated in the voltage divider Ra/Rb.

The two changes together make the power supply output impedance virtually a short circuit so far as ac is concerned. If the output impedance of V2 alone is 25 ohms, and if V1's gain considered as a separate amplifier is 100 times, the output impedance of the circuit of Fig. 3 will be 25/100, or ¼ ohm! Even lower output impedances are attainable by using higher-gain amplifiers at V1; a super-gain cascode with gain of 2,000 here would result in output impedance of 0.0125 ohm.

In case you happen to be familiar with "conventional" feedback amplifiers, Fig. 4 is the circuit of Fig. 3 redrawn to emphasize the similarity with a feedback amplifier. Normally, the "amplifier" has no signal to amplify. If anything tends to change the output voltage,

the change comes to the grid of V1 through Ra or C1 and since cathode voltage is fixed by the VR tube, this change becomes a signal to be amplified.

Amplification through a grounded-cathode amplifier inverts the phase of the "signal," while the cathode follower makes no additional change in the phase. Thus the amplified "signal" is effectively subtracted from the original change "signal" in the cathode circuit of V2; just as the remainder reaches zero, both "signals" disappear. Of course, as soon as they disappear the correction stops, so that the actual result is that the change is reduced by an amount equal to 1 divided by the product of the gains of each stage.

By this point, you should have a working knowledge of the concepts employed in electronically regulated power supplies. Here's how to use it to design one for your own needs.

First, of course, you must decide what output voltage and current you want. Then pick a tube (or tubes) for V2 which will pass the required current. The key characteristics of tubes for this position are high current-handling capability and high transconductance. Low- μ triodes designed for such service, such as the 6AS7 or 6080, are recommended.

Next, add to the output voltage an additional voltage to be dropped across V2, giving it something to work with. The usual allowance for V2 is 100 volts. This determines the supply voltage you need.

Now pick a tube for V1. High gain is wanted here; either triodes or pentodes are suitable. If pentodes are used, the screen-to-cathode voltage should be regulated with additional VR tubes. These VR tubes can be inserted in

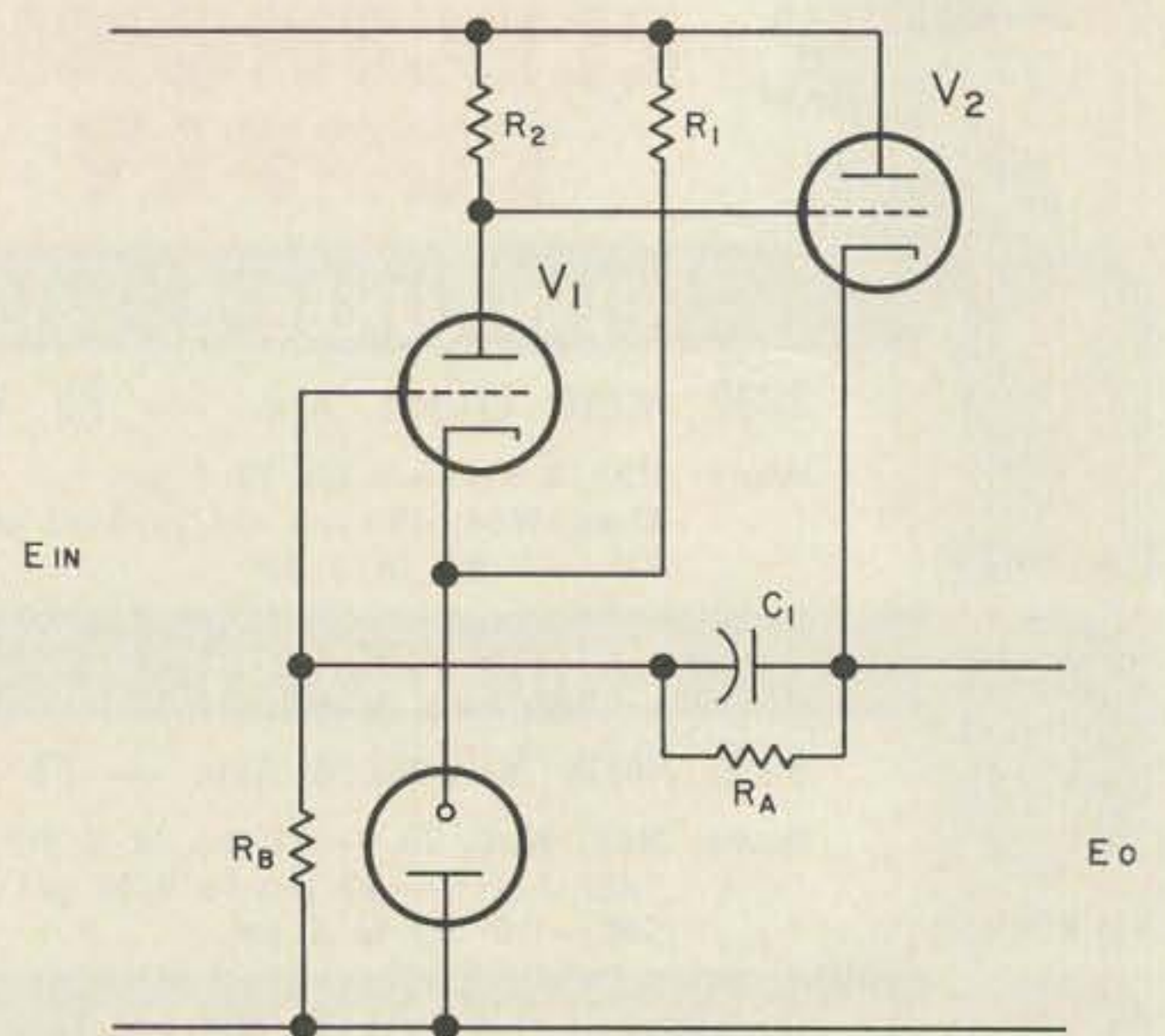


FIGURE 4

Fig. 3 redrawn to emphasize similarity to feedback amplifier.

series between R1 and the cathode in the circuit of Fig. 3.

The next step is to calculate the effective value of the minimum total load resistance for the cathode follower. This will be simply the output voltage (minimum if you're going to adjust it) divided by the maximum output current. Then use this value of R1 to determine the cathode-follower's minimum gain as described earlier.

Now divide the desired maximum output voltage by cathode-follower minimum gain just determined to fix the maximum voltage necessary at V2's grid. Also calculate the minimum voltage necessary at the grid of V2.

Knowing these two voltages, you can now pick a value for R2 which will allow V1 to be acting as an amplifier throughout the effective range. If R2 is calculated on the basis of only one output voltage, there's quite a risk of finding that you lose regulation outside a narrow range of output values!

From the characteristics of V1 and knowing the value of R2, you can quickly determine the net grid bias required on V1 at each end of the output range to produce the desired voltages at V2's grid. Subtracting these net bias values from the voltage of the cathode VR tube gives you the grid-to-ground voltage range for V1, which in turn leads directly to values for Ra and Rb. Frequently the Ra/Rb divider is made up of two fixed resistors with a comparatively small-value pot between, to give a bandspread effect; if you want to do this, calculate the resistors so that each end position of the pot gives you one of the extreme bias values.

And suddenly, at this point, you have completed the design. If you want an example to follow, go back to the sample circuit used to explain Fig. 2 and work it through.

Of course, this explanation and design procedure merely scratches the surface of the subject. A whole book could be—and has been—written about electronically regulated

MINIVERTER

CONVERTS ANY RADIO TO A SENSITIVE SHORTWAVE RECEIVER

★ Crystal Controlled Units Available from 2 to 150 MC.

★ Input Either High Impedance (BC Whip) or Low Impedance (Tuned Whip)

★★★ NOW ★★★



★ ALL Units Transistorized with RF stage and tuned mixer.

★ The following models are available with either high or low impedance inputs (Please specify desired impedance when ordering):

CVA2(160M); CVA4(80M); CVA7(40M-CHU); each \$14.95
CV14(20M); CV21(15M); CV29(10M); CV30(10M); CV50(6M); each \$24.95

MARS Models: 4 to 5 MC (BNC Connectors) 14 to 15 MC output, MARK I \$18.95
4 to 5 MC (BNC Connectors) 6.8 to 7.8 MC output, MARK II \$18.95

CAP Models: 4 to 5 MC (auto radio) .5 to 1.6 MC output \$18.95

FIRE, POLICE: 30 to 50 MC (any 1MC segment) each \$27.95

MARINE: 2 to 3 M (auto or home radio) each \$18.95

★ Brochure available upon request

★ Order direct from

SCIENTIFIC ASSOCIATES CORPORATION
BOX 1027, MANCHESTER, CONNECTICUT

FOREIGN SUBSCRIPTIONS

The foreign subscription rate to 73 is \$4.00 U. S. per year, however we will accept cash or checks in foreign funds at the following rates:

Canada	\$4.35	Germany	16 DM
Mexico	\$50	Hong Kong	\$23
Austria	115 sh	Italy	2500 Lx
Australia	36/	Netherlands	14.50 F1
Belgium	200 BF	Norway	29 NKr
Denmark	27.60 DKr	Portugal	1150 Es
England	28/6	Spain	200 Ptas
Finland	14.2 FM	Sweden	20.80 SKr
France	20 NF	Switzerland	17.50 SFr

power supplies. But the principles described here hold true for any electronically regulated supply, and if you know them you won't have much trouble doping out any unexpected twists you come across. . . . K5JKX

ALUMINUM TUBING

Build your own beam at near half the price of the store bought variety.

- ★ All sizes in stock, the best quality ALCOA 6061-T-6
- ★ Diameters from 1/4" to 3" outside measurements
- ★ Wall thickness from .035" to .125", perfect telescoping.
- ★ Any desired length up to 12 foot, we'll cut to desired size.
- ★ Any size order shipped anywhere.

We also stock all sizes of "U" bolts and sleeve caps for the element ends to finish the job.

These sleeves caps are of polyethelene, will keep out dirt, moisture, and reduce element vibrations.

Write us and enclose a stamp for a complete price chart, or explain your needs for a quote on the entire job.

We also stock Plastic and polystyrene sheets and tubing, and small diameter copper tubing—ideal for tanks or all types of home brew rigs.

PROPAGATION PRODUCTS COMPANY

P.O. Box 242

Jacksonville 1, Florida



DX Titans Meet

Stuart Meyer W2GHK, on the right, talks with Gus Browning W4BPD on the left. Stu, president of Hammarlund, originated the DXpedition of the Month, a non-commercial program that has put on one extraordinarily successful DXpedition after another. It is getting a little difficult to find places to DXpedition these days because Gus has just about covered the entire earth, visiting 327 countries so far, including almost every bare rock sticking out of any ocean and well enough known for the ARRL to Classify it as a country.

Regulated Supply for the LM



Richard Arthur
1924 W. Farwell Ave.
Chicago 26, Illinois

Photo Credit: C. F. Cochran

The LM frequency meter, the Navy version of the BC-221, is still available on the surplus market and is a steal for the price being asked in comparison to the type and quality of instrument therein. John Meshna, Jr. is asking \$49.00, in his current catalog, the lowest I've seen for many a moon.

The LM covers a range of 125 kc thru 20,000 kc with crystal check points throughout its range. Many have used the harmonics with accuracy up to 150 mc. One advantage over some of the BC-221's is the addition of the internal modulation which is standard on all of the LM's.


Once you decide to lay out the fifty bucks or so, you have a nice "black-crackle box" but it isn't doing you any good without a power supply. There are several approaches to the power supply problem but the only right answer is to remember that you have a precision piece of gear, so therefore let's make a decent power supply to go along with it.

As seen in the photograph, the appearance of the attached supply adds to the general design of the LM. That it simply plugs in and out for servicing is a further beauty. No electrical changes were made to the unit itself, and only one mechanical change: that of removing the center guide pin from the power input connector. This is necessary, due to the fact that

the mating plug in the power supply has been drilled out, countersunk, and a 6-32 flat-head bolt passed through it and secured to a metal spacer standing off from the cabinet.

The schematic is straightforward and should not present any problems in construction. If desired, the metering circuit may be left out in order to save a few bucks; however, I felt it was an asset to be able to monitor and know that the supply was delivering a regulated B-plus of 255 vdc.

The transformer is available from GEMCO Electronics, 2415 S. Michigan Ave., Chicago 16, Illinois, for \$2.69. They also carry the 1000 ohm, 2-watt control which is priced at \$0.49. The cabinet is a Bud CB-628 chassis, which is steel in construction and comes with a black-crackle finish. It matches the LM finish closely. The meter is a Calrad CMO-38 which is basically a 1 ma meter with a 0-300 vdc scale. A 300K resistor (R-2) is furnished with the Calrad meter when purchased. R-1 is a shunt across the meter when the slide-switch is put in the left position, thus measuring the current through the voltage-regulator tubes. In my particular case, R-1 turned out to be 2.2 ohms to give a full-scale reading of 30 ma. This value may vary with meters depending upon the internal resistance of the movement. The reading on the meter in this

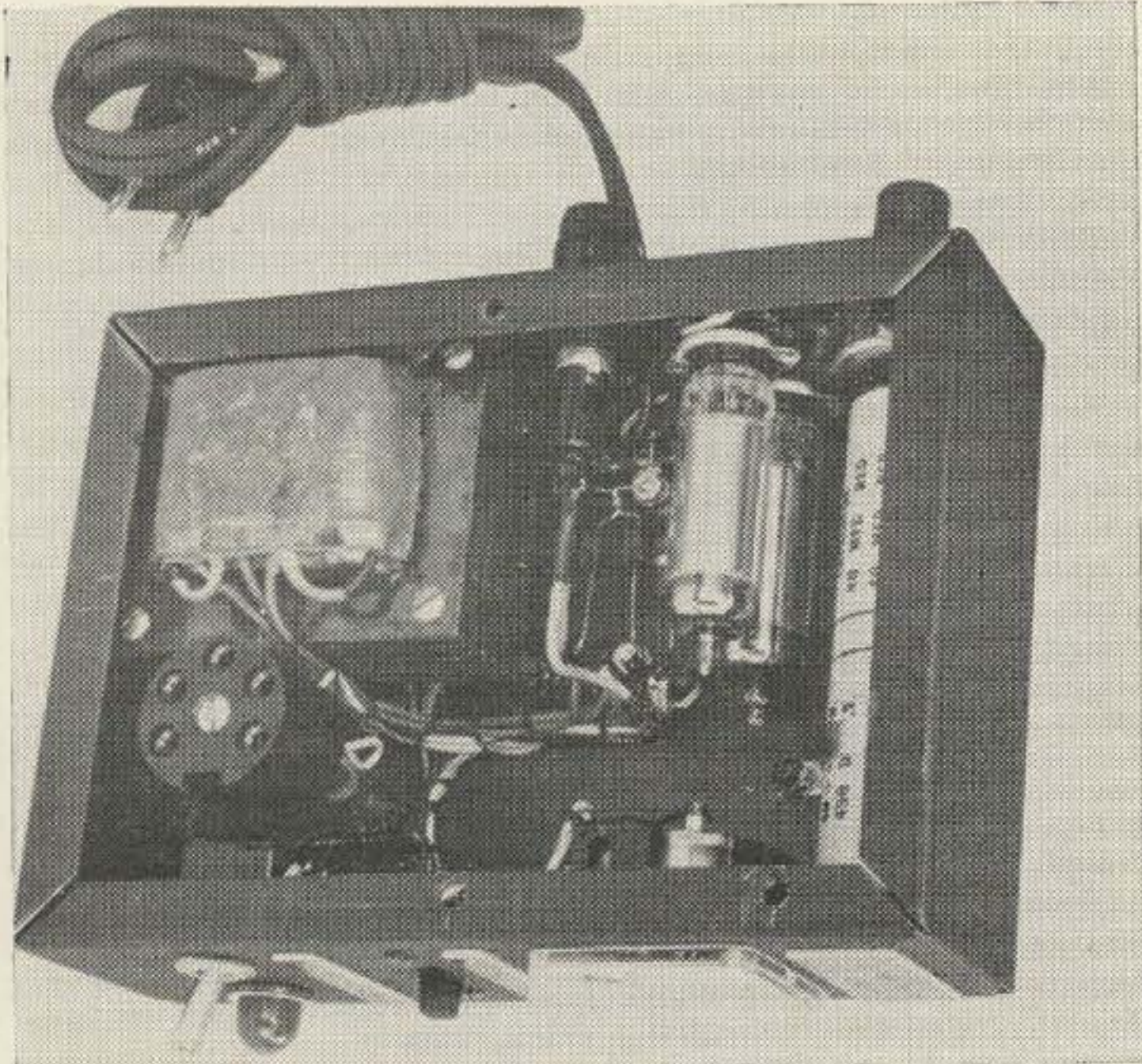


position should be about mid-scale indicating about 15 ma passing thru the VR tubes under load. This can be adjusted by varying the setting of the control mounted on the rear of the chassis.

Two five-lug terminals were mounted to the cabinet to provide connections for the two silicon rectifiers and the 1000-ohm, 2-watt re-

sistor. The VR 7-pin sockets were mounted directly to the cabinet by forcing a 4-40 bolt through the center shield of the socket from the rear of the case. The pins of the socket were bent up to avoid shorts and provide ease in wiring. Three 6-32 \times 2½" bolts were used to secure the power supply to the LM. Clearance holes were drilled through both sides of the power supply case to line up with the existing case holes of the LM. Therefore the long bolts pass through the power supply case and directly into the tapped case of the LM chassis. One additional hole was drilled and tapped into the LM case in order to secure the rear of the power supply. A handle was added to the top of the case. The legs were made by simply bending down the original locking brackets a full 90 degrees and attaching small rubber feet. The original feature of sliding the calibration book under the LM was retained.

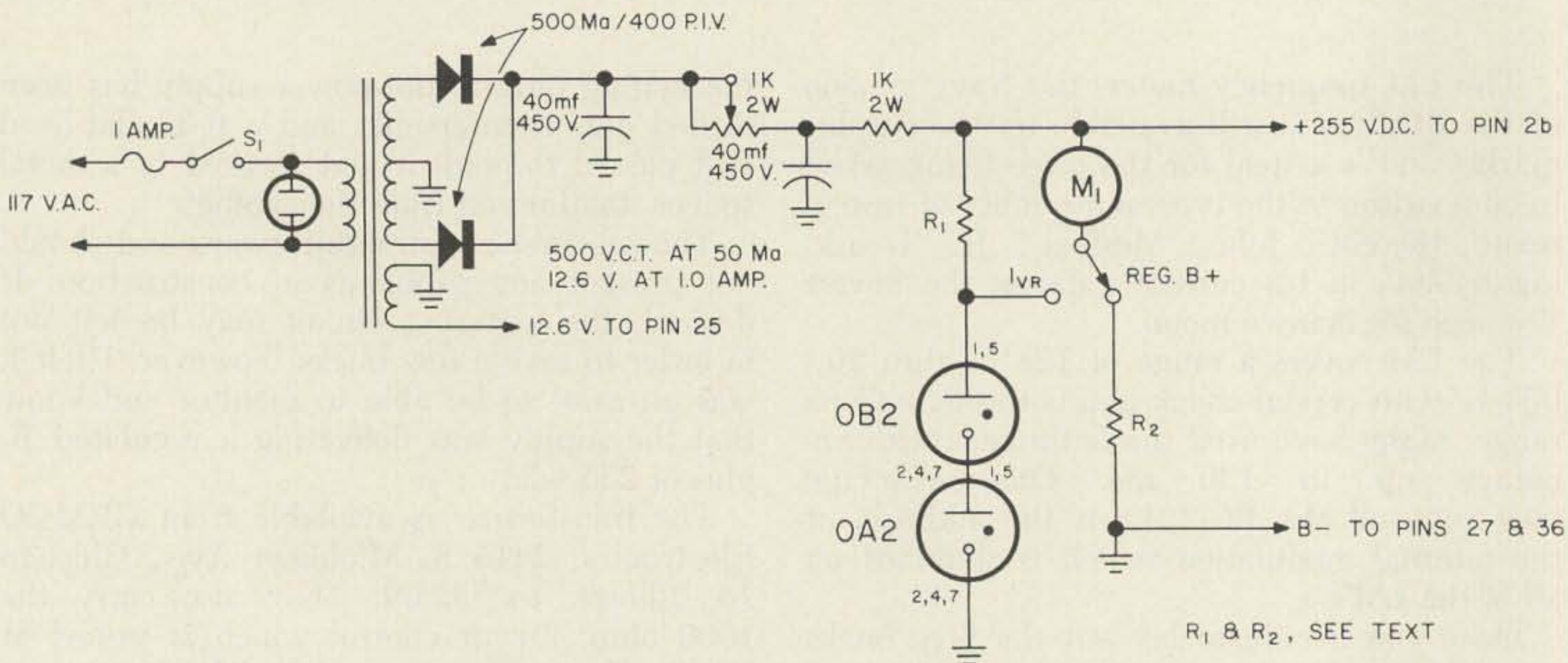Various articles have been written up on the operation and uses of Surplus Frequency Meters so I need not bother going into it at this time. All in all you will find the LM with the regulated supply to be a useful asset around the shack or bench, and a worthwhile investment.



Correction

Dear Wayne,

But like ouch! did I goof one up. I'm referring, of course, to "The Case of the Naughty Pi-Net." About all I can say in my defense is that to date not one of the guys who have written to point out specific mistakes have caught them all, but by now I'm getting a pretty good idea how mixed up it was.

Before I go into any detail, though, I have to re-emphasize that the major conclusion of that article is still correct. It's especially true in the 3.5 to 4 mc region, and on VHF, where it's the usual thing for a pi-net not to have quite enough range to take care of everything. Naturally, an antenna tuner is still the best answer, but some careful line pruning can work wonders.

Now to the biggest of the mistakes. I don't know

which was the worst—getting it into my head that a full trip around a Smith Chart is a full wavelength (of course it's only a half wavelength, which in itself made all the column headings twice as large as they should have been), or trying to add and subtract impedances in parallel. To do this kind of cancellation, the impedances have to be converted to admittances for the calculations, then converted back to impedances for use.

The "circumference" error's major contribution to inaccuracy was, as I said, the change in line lengths involved. The other one, however, makes many of the numerical examples incorrect.

Still and all, even when worked out properly we find that at a point 13 electrical degrees either side of the starting point (minimum resistive impedance), the output capacitor of our pi-net operating on 7 mc must be about 1200 pf,

SURPLUS TUBES

All are brand new, satisfaction guaranteed

0A2wa .75	6AQ5 .50	6J7 1.50	12H6 .50	832a 3.50	5781 1.00
0B2wa .75	6AQ6 .50	6L6 meta. 2.00	12SA7 1.00	843 .75	5814 .50
0C3w 1.00	6AS5 .50	6L6g 1.00	12SC7 .50	884 1.00	5840 1.00
1B3 .75	6AS7g 2.00	6L6wgb 1.50	12SJ7 .75	927 2.50	5841 5.00
1Z2 2.00	6AU6 .50	6SJ7wgt 1.00	12SK7 .75	955 1.00	5842 3.00
5R4wgb 6.00	6AU6wa 1.00	6SL7gt .50	12SQ7 1.00	1274 .75	5847 3.00
5U4gb .75	6BA6 .50	6SN7wgt 1.00	80 1.00	1625 .50	5881 1.50
5X4 .75	6BD6 .70	6V6gty .75	83 1.00	2050 .75	5896 .75
5Y3gt .60	6BE6 .50	6X4 .50	117Z6 1.00	5636 2.00	5933 3.00
5Y3wgtb 2.00	6BK7 1.00	6X5wgt 1.00	2E22 2.00	5647 3.00	5963 .75
6AD4 1.00	6BQ6 1.00	6Y6 .75	304TH 20.00	5651 .50	6005 .50
6AG5 .50	6B4g 3.00	12A6 .50	3B29 3.00	5670 .50	6080 3.00
6AC7 .50	6C4wa .75	12AS7 2.00	3B24 .75	5676 1.00	6111 1.50
6AG7y 1.00	6CL6 1.00	12AT7 .50	4-65 5.00	5681 .50	6112 1.50
6AH6 1.00	6D4 .50	12AU7 .50	807 1.50	5687 1.00	6146 3.00
6AL5 .50	6E5 1.00	12AX7 .50	812 3.00	5722 6.00	6384 10.00
6AK5 1.00	6J5 .50	12AY7 .75	814 4.50	5751 1.00	6336 7.00
6AK6 .75	6J6 .50	12BH7 .50	829b 6.00	5763 1.50	6476 8.00
					7363 \$20.00

many of the small receiving types listed are also available as factory seconds, pulls from new surplus, or guaranteed used tubes—these are 1/2 of prices listed above, tubes shipped will depend on what's in stock when your order arrives.

RESISTORS—we have all standard RETMA values in stock, carbon composition type, all color coded, long leads, new stock, 10% tol. 1/2 watt 10c ea, 1 watt 15c ea, 2 watt 22c ea, for 5% tolerance double the prices of these listed for 10% tolerance.

TG-34a tapes, inked ready to use, perfect code practice—\$2.00 each

7120Kc crystal, CR/1a holder 30c ea, **SO-239**—removed from new equipment 25c

Parachute—will handle 30 lb load easily, ideal for air dropping supplies—originally used for CRT-3 (gibson girl)—used, appear in perfect shape, packed ready for use—\$15.00

UG-274—BNC T Connector—used, perfect 75c **MC-359** "N" type right angle 40c

All items offered limited in supply, subject to stock close out or prior sale. Minimum order \$2.00 or add 25c handling charge. Include sufficient estimated funds for postage, we'll refund the excess in stamps.

PROPAGATION PRODUCTS COMPANY

P.O. BOX 242

Jacksonville 1, Florida, 32201

which while within range of most rigs is distinctly an abnormal situation. This is for a 2-to-1 SWR. Under the same conditions on 80 meters, the output capacitor would have to be 2400 pf, and it's seldom indeed that one this large is found in a rig. So I'll stand by my conclusions even if I did mis-chart my Smiths!

Thanks to the many fellows across the country who pointed out the circumference error, and to WB6HGC in particular who pointed out the error of adding parallel impedances. You can stop writing nasty notes now, gang. I know when I'm wrong!

And since, as I said, not one of the gang so far has caught *all* the mistakes in my use of the Smith chart, maybe I ought to write you a piece on "How to Use the Smith Chart." Believe me, I know how now—and we could invite all the fellows who caught the Pi-Net mistakes to check it over first, as well. What say?

Jim Kyle K5JKX

Hams in the News

LOS ANGELES: Lt. General Francis Griswold sent the following message from a military plane over the Pacific enroute from Washington to Honolulu: "I'd like to convey to all the amateurs the Government's sincere appreciation for the yoeman service in communications they have done in the Alaskan earthquake disaster. It has been terrific."

DETROIT: Nearly one hundred Michigan mobile hams assisted in a mass polio vaccine drive. With over 900 vaccine stations and an estimated 3 1/2 milion persons getting the vaccine, communications was of extreme importance to see that supplies of vaccine were rushed to depleted stations.

INDIANAPOLIS. Pentagon radio operators said all contact with their Alaskan military bases had been cut off for over an hour after the quake. They asked any operators who gained contact to notify the Pentagon at once.

50 - 144 - 220 CONVERTERS & PREAMPS

I.F.'s at 7, 10, 14, 20, 22, 24, 26, 27, 28, 30.5 & 50 Mc. All with built-in power supply. 6 Meter (6CW4-6U8) \$34.50 ppd. 2 meter (4-6CW4) \$54.95 ppd. Best appearance and workmanship of any VHF converters. Weak-signal performance equal to or better than any other nuvistor or 417A manufactured converters. Best value by far. Write for descriptive literature.

Parks Electronics

Rt. 2, Box 35

Beaverton, Ore.

Want High Efficiency and Small Size?

6 10 15 20 METERS

MINIATURIZED-4-BANDS

- ★ 500 Watts AM.
- ★ Turning Radius - 7'
- ★ Total Weight - 11 lbs.
- ★ Size - 5' x 11'



Model B-24

Mini-Product's time-proved B-24 4-band antenna combines maximum efficiency and miniaturization to provide hams with an excellent antenna where space must be considered.

Like all Mini-Products antennas, the B-24 employs "Multiple Hat" loading for maximum efficiency. TV rotor adequate; Feed line, 50 ohm coax; SWR 1.5:1.

Amateur Net

\$59.95

Write for data on the B-24 and other compact antennas:

- Model B-4010—40 and 10 M. two 18' elements, 10' boom Net \$79.50
- Model C-4—Coax Vertical (no radials) 6, 10, 15, 20 M. Net \$34.95
- Model M-4 Mobile 6, 10, 15, 20 M. Net \$16.95


Patents pending

Mini-Products, Inc.

1001 WEST 18th STREET • ERIE, PENNSYLVANIA

See your local distributor or order direct from factory

New Products

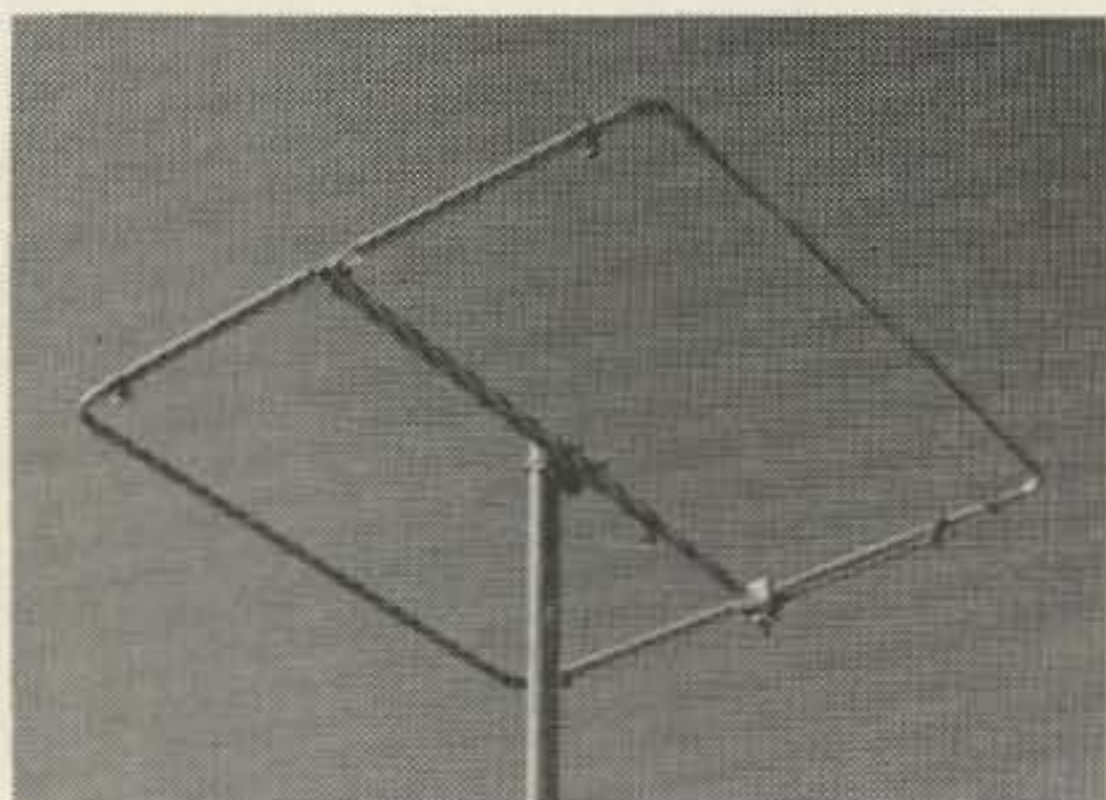


Squalo?

Yep, Cushcraft has invented a square halo. Models are available all the way from six meters right on up to 40 meters! The six and ten meter models are small enough to mount on top of a car and come with rubber suction cups for mounting. The Squalo has a 360° pattern with no deep nulls and is extremely compact. The 20 meter model, for instance, is only 100" square. This is about eight feet square instead of 32 feet long. The prices are very reasonable, the six meter model being only \$12.50 and the 20 meter job \$29.50. Cushcraft, 621 Hayward, Manchester, N. H.

B & W

Send a card right away for the new B & W catalog. They make a whole raft of things . . . miniductors, phase shift networks, pi-net inductors, coax switches, knobs, transmitter, linear, power supply, etc. B & W, Bristol, Penna.

Revealed at Dayton

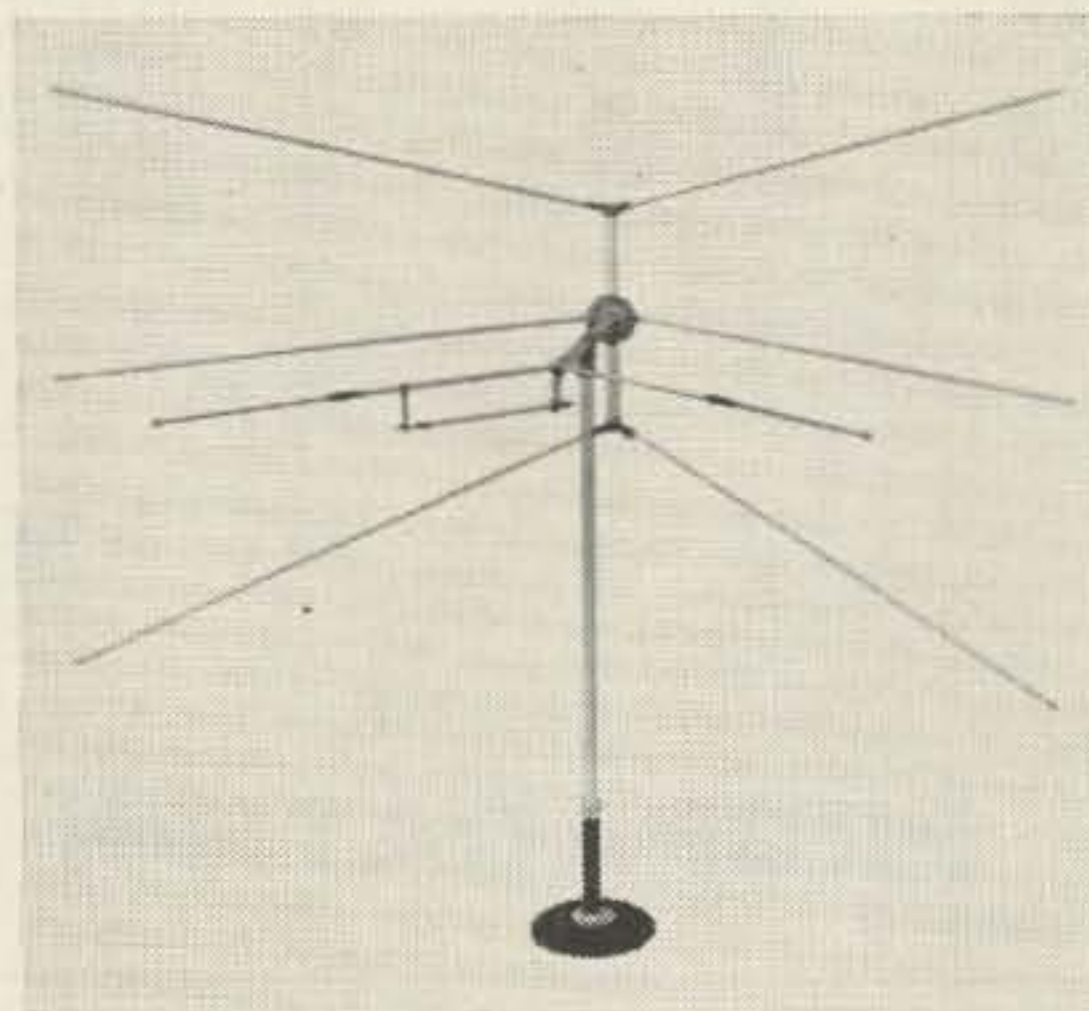

One of the booths that was particularly hard to get into at the Dayton Hamvention was Newtronics'. The commotion had a lot to do with their first showing of their Coveya 6 beam. The Coveya is a combination of colinear, vee and yagi. Their specs say it has a 10 db gain over a dipole and 25 db front-to-back. It is gamma matched to 52 ohms and presents a VSWR of less than 2:1 over a full megacycle, which megacycle can be adjusted from 50-54 mc. The price is \$39.90. You'd better take a look at this one, or send for a data sheet from New-Tronics, 3455 Vega Ave., Cleveland 9, Ohio.

Using the TS-118A/ AP Wattmeter

Gordon Hopper W1MEG
75 Kendall Ave.
Framingham, Mass.

RF wattmeter TS-118A/AP is a portable load-resistor-type absorption wattmeter used for the measurement of rf power within the frequency range of 20 to 1400 mc. It is used with a selected thermocouple for power measurements, or is used without a thermocouple as a dummy load on these and lower frequencies.

The entire unit is housed in a metal case with a detachable cover and consists of the rf wattmeter, a tuning shunt, four thermocouples, three adapters, and an rf cable. There are four calibration curve charts, one for use with each thermocouple, attached to a cover which protects the meter face when the unit is not in use.

There are no operating controls on the wattmeter nor does it require any external source of power. Its meter is calibrated from 0 to 1 and indicates the output of the thermocouple. The meter reading is used to determine the power being measured and the four thermocouples cover a power range of 2 to 500 watts. The calibration charts are used to enable the operator to select the proper thermocouple.

Each calibration chart contains a K factor which are used in power calculations when used with the particular thermocouple indicated on its individual chart. This K factor is actually a representation of the maximum amount of power that each individual thermocouple is capable of handling. Each thermocouple has a C factor etched into it which is incorporated into the power measurement calculations. To measure a transmitter's output power, a simple formula is used. This formula is:

$$\text{Power (watts)} = \text{K times C factor times meter reading.}$$

An example of a power measurement is as follows:

1. Determine the transmitter's approximate power and frequency.
2. Determine from the charts the K factor for the approximate frequency.
3. Select the thermocouple whose K factor is closest to, but greater than, the approximate power. (The K factor can be equal to the approximate power.)
4. Assume that the transmitter frequency is 144 mc and that the approximate power output is 200 watts. Refer to the calibration charts and select the thermocouple whose K factor at 144 mc is greater than 200. If the approximate power is not known, use thermocouple MX-1783/U first.
5. If the transmitter output is terminated with a UHF or N type receptacle, connect the wattmeter as shown in Fig. 1.

ADAPTER UG-83/U FOR UHF
ADAPTER UG-213A/U FOR TYPE N

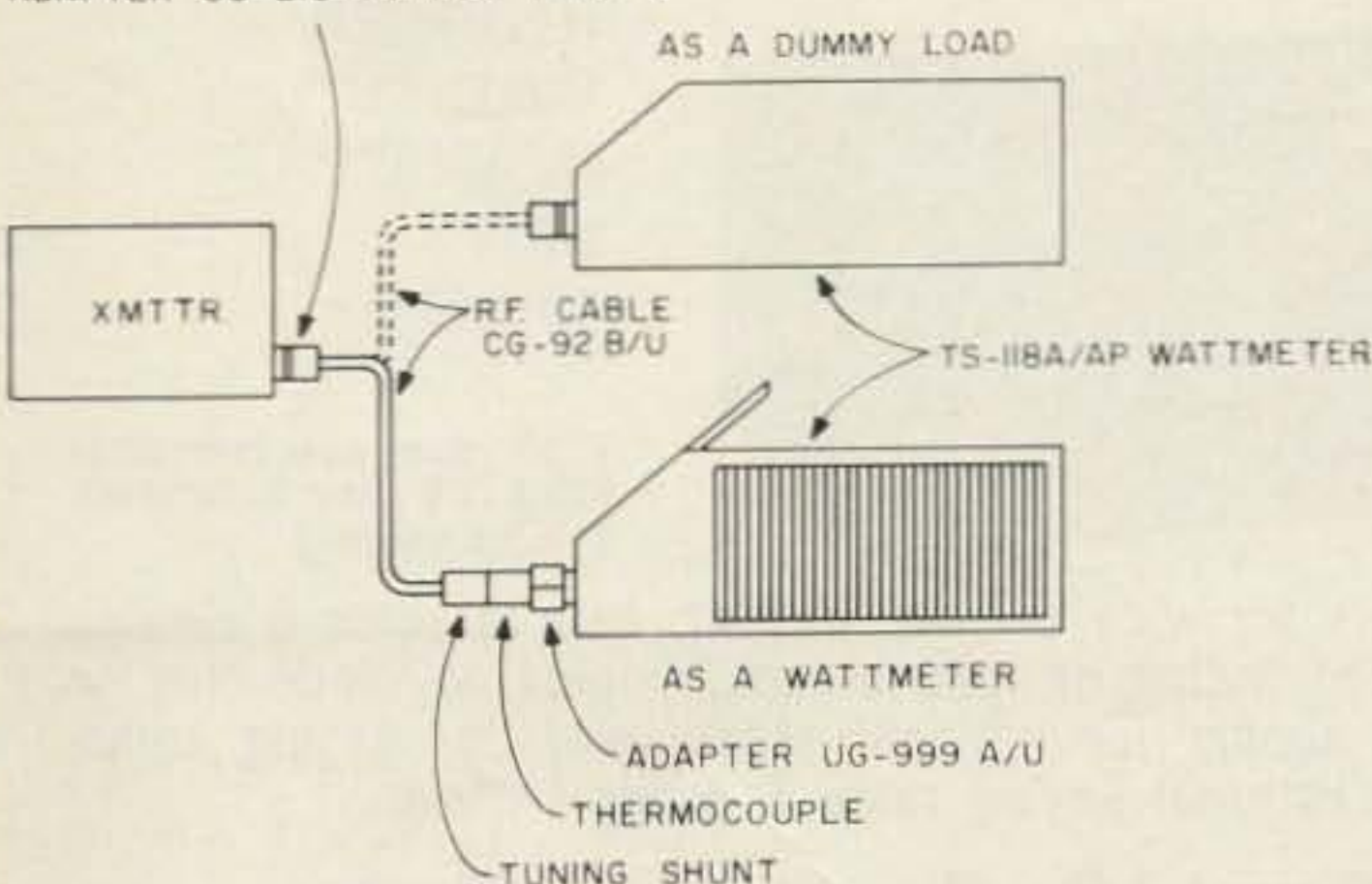


FIGURE 1

Tone Converter: dual freq. shift radio teletype, Radio Northern type 152, model 2, 110-220 V. 50-60 cy. 1 ph. O/A dimensions 17" x 3½" x 19" complete with tubes used excellent \$50.00 ea.

Reperforator-Trans-Dist. (Combo) complete in sound proof cabinet & slide out table \$130.00 each

ATLANTIC SURPLUS SALES

181 SACKETT STREET

BROOKLYN 31, N. Y.



DOW RADIO & Electronics

1759 E. Colorado Blvd. ---PASADENA---Mu 1-6683
222 West Main St. ---SANTA MARIA---WA 2-1765
5857 Hollister Ave. ---GOLETA---WO 7-3401
1505 S. Oxnard Blvd. ---OXNARD---HU 6-6353

GAIN Inc.

YOUR
VHF—UHF
HEADQUARTERS

NORTH AMERICAN IMPORTER
OF THE FAMOUS J BEAM

WE HAVE EXPANDED OUR FACILITIES AND NOW OFFER:

- ANTENNAS** Telrex - Mosley - Andrews and Communications Products to supplement our Famous J Beams.
- TOWERS** Rohn - Triex - EZ Way - We will install to 150 miles from Chicago.
- CONVERTERS AND FILTERS** Parks and Ameco Converters - Comaire re entrant filters and tuners.

Whether you want PL259 or S0239 Co-ax connectors at \$.45 each—3 for \$1.25 or a 27 DB, 432 MC antenna on a 200 ft. tower, we can furnish it.

Extremely fine prices on combination deals.

NOW! One stop shopping.

WRITE and ASK
Bill Roberts W9HOV
how he can help you.

1209 West 74th Street
Chicago 36, Illinois

GUARANTEED RECONDITIONED
HAM GEAR



Phone: (415)
DI 2-5757

ELECTRONICS

WRITE NOW
FOR MONTHLY
FLYER.

999 HOWARD AVE-BURLINGAME, CAL.

Semi-Conductor Speed Control

For Universal AC-DC Type Motors

Portable Drills, Saws, Grinders, Sanders Etc

Full Power at All Speeds.

5 AMP.—12.95 W & T. 7 AMP.—15.95 10 AMP.—18.95

BELL ELECTRONICS

1 No. Academy Ave.

Danville, Pa.

Reyco Multiband Antenna Coils

Traps for dipoles . . . high strength . . . moisture proof guaranteed to handle a full KW.

Model KW-40 coils will, with a 108 foot antenna, provide operation on 10-15-20-40-80. \$12.50 set.

For information on other models write:

FRED L. REYNOLDS W2VS, 492 Ravenswood Ave., Rochester 19, New York

6. Note the correction, or C factor, that is marked on the thermocouple.

7. Turn the transmitter on and tune it using its own indicators, allowing one minute for the transmitter and the wattmeter to stabilize before taking a reading. (The wattmeter will lag slightly behind any power level changes.)

8. Take the wattmeter reading which will be 1.0 or some even hundredth part of 1.0 such as 0.84.

9. Calculate the power using the formula given previously:

$$W = 238 \text{ times } 0.960 \text{ times } 0.84$$

(K for MX-1782/U (C factor for (meter
at 144 mc) MX-1782/U reading)

$$W = 191.92$$

Be sure to turn the transmitter off before opening any rf connections to the wattmeter. The power reading obtained indicates the power that the transmitter will deliver to a 50-ohm resistive load. Retuning of the transmitter will be necessary when it is reconnected to its antenna system.

If the TS-118A/AP is to be used only as a dummy load, connect it to the transmitter as shown in Fig. 1. It can be used as a dummy load in a 50-ohm coaxial line in the 20 to 1400 mc frequency range. However, it can also serve as a dummy load on frequencies below 20 mc by disconnecting meter M201 at jack J202. This will prevent the high vswr from damaging the meter.

... WIMEG

Modifying the BC-348

Harold Mohr K8ZHZ
5670 Taylor Road
Gahanna, Ohio


The 348 is a good stable receiver but is very hard to tune side band satisfactorily due to the tuning ratio of the dial.

First, obtain a small midget variable capacitor that has a shaft for a tuning knob. Then a 2 preferably, or not over a 3 mmfd ceramic capacitor. Remove the 2¼-inch by 6 inch metal panel that covers the rf tune sockets on the right front of the 348 panel. Remove all but one rotor and one stator plate from the small variable and mount it on the left of this panel cover. Make sure it does not interfere with anything in the tube socket compartment. You can place a small indication mark on the panel above the knob and place the knob in a straight upright position with the rotor plate of the variable condenser half in and half out of the stationary plate. This way you will be able to go plus or minus capacity.

You will find a wire running from the oscillator condenser (this is the gang nearest the

center of the 348). You can solder one end of the 2 mmfd capacitor where this wire enters the oscillator coil, after you have clipped the capacitor lead wire rather short; then route a wire from the remaining capacitor lead to the stator of the midget variable. This is all there is to it.

You may notice that this will throw the dial calibration off about the width of the marker, especially on the higher bands, and if you are a perfectionist you can touch up the oscillator padders on WWV or some known standard, but be sure you leave the small capacitor with the knob in straight up position when doing this. Always leave it here and tune in the SSB or CW station the best you can on main dial with the bfo adjusted for best reception. Then you can go to the vernier knob of the small variable and tune in as easy as falling off a log. Leave the bfo set after you have found where it works best, and reduce the gain of the 348

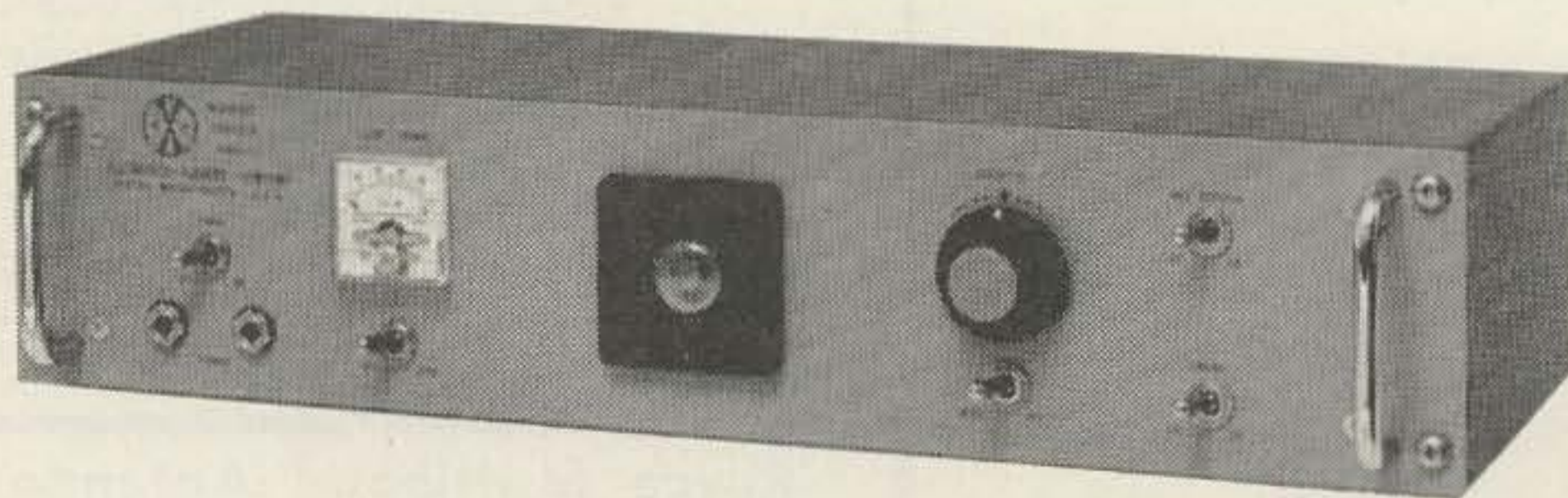

TELEWRITER
MODEL "L"
FREQUENCY
SHIFT
CONVERTER

\$199 (dual eye indicator)
\$279 (CR tube indicator)
\$14.50 cabinet

Audio input. Scope or dual eye indicator. Plug-in inductors for wide or narrow shift. Axis restorer & Limiter can be switched in or out of circuit, to suit conditions of fading or interference. Copies on Mark only or Space only automatically Mark hold circuit. Loop & Bias supply for optional polar relay for keying transmitter. Keying tube keys magnet. Terminals on chassis for external keying relay & scope indicator.

ALLTRONICS-HOWARD CO., Box 19, Boston 1, Mass.

if you have the gain and volume controls separated. If not, use as little gain as needed.

You will be able to listen to both sides of an SSB QSO, often by just adjusting the small capacitor. Then there is not any danger of losing the other station, as you will find you can tune most SSB signals in with AM quality by careful adjustment of this small capacitor.

Although especially designed for the BC 348, it should work as well with many other receivers.

...K8ZHZ

THE BIG WHEELS* ARE ROLLING!

Cush-Craft offers "New Dimension" to Mobile and Fixed Station Communication in Amateur and Commercial Services.

*... the brain child of Dr. Robert Mellen and Carl Milner plus the production know-how of Cush Craft now presents this new VHF-UHF antenna. This new clover leaf antenna gives fantastic performance: omnidirectional, it has horizontal polarization and extremely low Q. This results in improved band width, ease of matching and large "capture area." Dual stacked, Big Wheel gain figures (in all directions) compare favorably with the 7 element Yagi in its favored direction.

Pattern: 360 horizontal, variations of \pm 2DB or less
 Band Width: SWR 1 : 1.2 or less over 4 Mc
 Gain: Single bay — approx. 10 DB over Halo

PRICES


3/4 meter Model No. ABW — 420 — \$ 8.95
 1 1/4 meter Model No. ABW — 220 — \$10.95
 2 meter Model No. ABW — 144 — \$12.95

For Further Information & Illustrations Refer to:
 Page 42 September QST and Page 60 October QST

Cush 621 Hayward Street
 Manchester, N. H. **Craft**

VHF OPERATORS!!

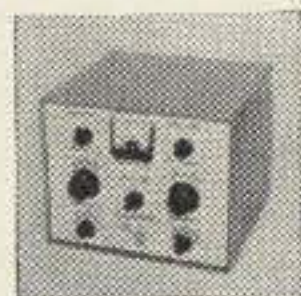- Greater Signal
- Reduced TVI
- Max. Pwr. to Any Antenna
- Match Coax to Balanced Line
- Match Coax to Coax Lines
- Built in SWR Bridge
- 6 and 2 meter switching



ANTENNA MATCHBOX
 LM-6N2-C \$64.50
 Gray w/white panel

TVI ON 6 AND 2 ???

- Superior to Low Pass type filters.
- Hi-Q Resonant Cavity Filtering
- Removes both Harmonic and Sub-Harmonic energy.
- 50 DB or greater attenuation of energy outside 6 or 2.
 CF-2 \$15.75 CF-6 \$19.75

WRITE for specs on these and other top quality COMAIRE VHF products. Also, subscribe to the VHFER, the VHF builders monthly journal. Sample copy on request.

COMAIRE ELECTRONIC, Box 126, Ellsworth, Michigan

TWO METER antennas. Something new in antenna design—guaranteed (money back). Will outperform any factory job on the market—a front-to-back ratio that is out of this world. Forward gain that will "push" a signal into the DX horizon. Seven element with a special reflector . . . AND a method of coupling the 52 ohm lead in to the antenna that is just about perfect. They sell for **\$19.50 ea**; or two with matching harness and hardware at **\$45.00**

Two Meter xmitters that use xtal mikes and carry a good punch in the audio system! Two watts (it's enough!) into the antenna with modulator and tubes, **\$25.00**

Power supply for above **\$12.50**—Mikes are xtal and can be had for **\$7.50 ea**. Units only—less all other accessories, only **\$18.00**

Can supply six meter xmitters also, same as above—except over three watts. WILL put out four watts with higher plate voltage. Same prices as the two meter rigs.

EVERYTHING SHIPT PREPAID IN THE CONTINENTAL U.S.A.

A very good little receiver (we make one for six meters also) designed for two meters. Consist of the following:—An RF stage ahead, super/regen detector, and two audio stages. Very sensitive little receivers—for average users, beginners etc.

ALL ABOVE UNITS ARE SOLD LESS CABINETS. Just the finished unit in chassis form.

Save your money—they work fine as they are—but you CAN get cabinets if desired.

We also have a fine transmitter/receiver with AC power and mike ready to go at **\$78.00**. These units are on two meters. Also can supply them for six meters. Same price. THEY MAKE EXCELLENT DRIVER UNITS FOR A HIGH POWER FINAL, LINEAR, ETC.

FULTON ELECTRONICS

MANTECA, CALIF.

If in the central part of the state, drop over any time and see the results.



WANTED Transistors, Tubes all types, Test Equip., Ground Equip., PRC, GRC. TS, URM, UPM, Aircraft Communications & Navigation Equip. **ELECTRONIC TUBES** — Industrial, Special Purpose, Receiving-TV, Transistors-Diodes, **LAB. TEST EQUIPMENT, AIR-CRAFT & GROUND, COMM. EQUIPMENT, INTERNATIONAL SERVICE.** Write or Phone

V & H RADIO

2053 VENICE, L. A. 6, CALIF.

RE 5-0215

RT82/APX6 Get on 1215-1296 mc the EASY way . . . NEW 24.75
 TS726/UPM8 Tests APX6.W/27 Tubes, 10 Diodes GOOD 12.50
 RT18/ARC! 100-156 mc X'ceivr. 832A final . . . GOOD 22.75
 MT230/ARC Mounting for ARC1 and ARC4 . . . EX 2.35
 RT58/ARC12 225-350 mc W/42 Tubes, 2-2C39A's . . . EX 29.75
 C45 Control Box for ARC1 and ARC12 . . . GOOD 1.25
 ARN6 X'ceivr 100-1750 kc. Four band Superhet . . . EX 19.25
 MT274/ARN6 Mounting, single control type . . . EX 2.35
 MT273/ARN6 Mounting, dual control type w/relay. . . EX 2.85
 AS313B/ARN6 Antenna. Station seeking loop . . . GOOD 8.90
 C403A/ARN6 Control Box, Bind. post connections . . . EX 6.75
 C4/ARN7 Converts to control for ARN6 . . . NEW 2.25
 T465/ALT7 168-352mc continuous. 100W min o'put . . . EX 22.50
 SCHEMATIC for T465/ALT7 with parts values . . . 1.00
 SWR Bridge 200W 10-100mc W/diodes and meter . . . EX 8.25
 Axivane Blower 60 c.f.m. 12-24 VAC-DC . . . EX 8.75
 6161 Tube Full power to 900 mc Good to 2000 mc . . . EX 4.75
 Weston Meter 500 microamp 240 deg 0-60 scale . . . NEW 2.25
 HV Probe 50kv Insulation 500 Meg series res . . . NEW 2.45
 RE2/ARC5 Ant. Relay W/Meter & Vacuum Capacitor . . . EX 1.85
 TS12 SWR Meter 9305-9445 mc W/60 cycle supply . . . EX 19.75
 IP223/APS38 Sweep Amplifier 4 Tubes, 2-807W's . . . NEW 6.75
 ID59/APA11 W/3BP1 & 16 tubes Ex for Panadapt. . . EX 17.50
 APX1 less tubes. A Warehouse of Parts, 30 lbs. . . GD 2.75
 TN8 or TN90 Tuning Unit for APX1 w/3 tubes . . . GD 1.00
 TS155C Sig Gen 2700-3400 mc W/Book and Case . . . NEW 75.00
 AT141 Antenna 225-440 mc W/VSWR Chart . . . NEW 4.75
 APN1 420 mc W/Tubes, Wobulator, Dynamotor . . . GOOD 3.85
 FT243 XTAL SET 5675 thm 8650 kc CH270-CH389 120/17.75
 M92U Dynamic Mic W/Cord & PL68 Plug. Ex for CB. . . EX 1.85
 WILCOX AM43B/FRC 2 channel Amp W/60 cy supply. . . GD 12.75
 WILCOX 90A2 lkc Gen & Keying Osc. 60 cy supply. . . GD 11.50
 WILCOX 63A1 Volume limiting Amp 60 cy supply. . . GD 14.75
 PRS3 '53 Model. Locates Pipe & Sunken Metal . . . NEW 37.50

E. C. HAYDEN

BOX 294 Bay Saint Louis
 Mississippi

Shipment: FOB Bay Saint Louis. . . Terms: Net, Cash.

(High Gain from page 33)

Like the previous circuit, this one makes use of an extremely high-valued plate load resistor. However, no shunt is necessary to keep transconductance up since pentodes maintain reasonable values of gm down to almost zero plate voltage.

TONS OF AMATEUR EQUIPMENT IN STOCK

WESTERN RADIO

SAN DIEGO

1413 India Street BE 9-0361
MON - FRI 8:30 to 8:00 SAT 8:30 to 5:00

ALL BAND TRAP ANTENNA!



Reduces interference and Noise on All Makes Short Wave Receivers. Makes World Wide Reception Stronger. Clearer on All Bands!

For ALL Amateur Transmitters. Guaranteed for 600 Watts AM 1200 SSB Pi-Net or Link Direct Feed. Light, Neat, Weatherproof.

Complete as shown total length 102 ft. use Coax RG59U or balanced twinline. Hi-impact molded resonant traps. (Wt. 3 oz. 1" x 5" long). You just tune to desired band for beamlike results. Excellent for ALL world-wide short-wave receivers and amateur transmitters. For NOVICE AND ALL CLASS AMATEURS! NO EXTRA TUNERS OR GADGETS NEEDED! Eliminates 5 separate antennas with excellent performance guaranteed. Inconspicuous for snooty neighborhoods! NO HAYWIRE HOUSE APPEARANCE! EASY INSTALLATION! 80-40-20-15-10 meter bands. Less F.L. \$13.95
40-20-15-10 meter bands. 54-ft. ant. (best for swl's) less F.L. \$12.95

Feedlines: (specify) for Pi-Net output 90 ft. RG59U. \$5.00 extra
For Link coupling — 96 ft. balanced twinline \$2.00 extra
SEND ONLY \$3.00 (cash, ck., mo) and pay postman balance
COD plus postage on arrival or send full price for postpaid delivery. Complete installation & technical instructions furnished. Free information on many other 160-6 meter antennas.
Available only from:

WESTERN RADIO — Dept. A7-6 — Kearney, Nebraska

The cathode resistor and bypass capacitor are eliminated by going to "contact-potential" bias for the grid, via a 2.2 meg resistor, while screen supply problems are bypassed by using a tap on the output stage's cathode resistor to supply the 10 volt screen potential necessary. Because of the high value of load resistor, which tends to limit current, and because cathode bias is used in the output stage, the grid of the 6AK6 can be direct-coupled to the plate of the amplifier.

This circuit has slightly lower gain than the super-gain cascode, but is still plenty hot. Its gain ranges from about 900 to 1500 depending on screen voltage and plate-supply potential. If more power is desired, you can substitute a 6AQ5 or a 6BQ5 for the 6AK6 shown. However, if 2 watts will suffice, the 6AK6 has a big advantage in its extremely low heater current requirement. As shown, the circuit requires only 35 ma at 6.3 volts on the heaters, and around 40 ma at 300 volts from the power supply.

Like the super-gain cascode, high-frequency response of the starved pentode is limited. However, it is plenty adequate up past 3 kc. To use the pentode with a dynamic mike, add a series capacitor between the mike and grid to prevent shorting out the bias voltage.

... K5JKX

Subscriptions

If you like 73 we'd appreciate your help in getting more fellows to subscribe. The big difficulty is to overcome inertia and actually get them to sit down to get it done. We try to make it as simple as possible on our end. The price is a simple (and low) \$4. Our address is simple: 73, Peterborough, N. H.

MASTER ORDER BLANK

73 Subscriptions	Name _____	Call _____
1 yr \$ 4.00 _____	Address _____	
2 yr \$ 7.00 _____	City _____	Zone _____ State _____ Zip _____
3 yr \$10.00 _____	One year subscriptions	
LIFE \$50.00 _____	6up \$2 _____	ATV \$2 _____
New sub. _____		
Renewal sub. _____	IoAR Membership 1 yr \$10 _____	
Start with _____		
Back issues (50c each) _____		

some sort of award can be made to Phil Spencer W5LDH of the Delta Division for chirping off key just for one instant at a board meeting. It has been a long time since that has happened. It's something.

Eight of the directors come up for re-election or replacement this year. How about it, shall we see if we can't get something in there besides a set of puppets?

OK, now let's see what the directors accomplished with those 47 unanimous votes. Hunty has been looking a bit peaked lately . . . I'll bet that handsome raise the board gave him will make up for a lot of the harassing he has been getting. The board gave the Executive Committee carte blanche to increase Budlong's "retirement" pay too. Hmm, I understood that Bud was already getting 100% pay in "retirement," am I wrong?

Another big appropriation was \$100,000 for the defense of amateur frequencies in the coming years. This is quite an appropriation . . . it is the dues of 40,000 members of the League, about one half of the members.

The hundred grand won't go very far if Hunty spends up a storm like he did back in 1959. He and Budlong represented the ARRL at the Geneva Conference that year and turned in a bill for \$15,701.68, if I read the fine print on the League financial reports right. I don't like to bite the hand that has fed me (yes I do), but the dinner Bud and Hunty bought me in Geneva took care of my own ARRL membership dues for a number of years. I figure that I'm just making time payments on that dinner each year as I send in my check. Their hotel was palacial . . . the sitting room of their suit was larger than the lobby of my hotel. Nothing but the best . . . right?

Seems to me I remember their flying president Dosland over for a couple of weeks vacation. . . and didn't they pay his salary while he was taking time off his regular employment?

Shucks, there I go getting sarcastic again and I wanted to be straight forward this time. You'll have to admit that I passed up the opportunity to say something about the directors grabbing a ribbon for a dance around the May-pole. Well, I almost passed it up. I'll also not say anything about their dance around my February poll.

Seriously, is there any way that us members of ARRL can find out where this 100G goes to? If some good can be done with it, all the better for us all . . . but we don't want it to turn into a big "fact finding" vacation fund.

. . . Wayne

"RW" MAY BARGAINS

- RA-42B POWER SUPPLY UNIT. Input 115/220v 60 cy; output 210vDC, 60ma & 6.3v 3.5A. 5V4 Rectifier choke input & dual oil capacitor. Used, Good \$ 6.75
- Same with Volt & MA meters. Used, Good \$10.45
- MOBILE TRANSMITTER 8-193B/VRC-2 30-40 mc FM with 7 tubes (807 final), 6vDC dynamotor & schematic. Used, Good \$12.95
- LAZY MAN'S "Q-5er" Navy Radio Beam Filter for CW. Single signal selectivity. The easy way. New \$ 2.49
- MN-26C Bendix Receiver— 150-1500kc. 3 bands. 2 RF Amp, AVC & BFO. W/12 tubes, 24vdc dynamotor & schematic. Used, Good \$14.95
- 3AP1 CRT Xint for Modulation Monitor & etc. Brand New in original cartons \$ 1.95
- ARC-3 TRANSMITTER— 100-156mc AM. Uses 2-832A's, 2-6L6's, 3-6V6's, 12SH7 & 6J5. Used, Good with schematic—Less Tubes \$ 9.95

SEND MONEY ORDER OR CHECK WITH ORDER
MINIMUM C.O.D. ORDER \$10.00 with 25% DEPOSIT

Write for Latest Bulletin #39—Loads of Bargains.

R. W. ELECTRONICS, INC.

2430 So. Michigan Ave.
Chicago, Ill. 60616

Dept. 735
Phone CALumet-5-1281

LOOKING? SHOPPING? TRADING? TRYING TO SAVE MONEY?

Write Bob Graham for Special Deals on New and Re-conditioned used gear. Cash or Budget.

Graham Radio

Dept. C., Reading, Mass.

Tel: 944-4000.

Only QUAKER can give you Price and Quality. So why buy crystals elsewhere.

Crystals in FT-243 holders. .05% tolerance. Fully guaranteed.
Only 55c ea. postpaid USA.

Frequency in Kcs.				
6000	6425	8014.29	8164.28	8350
6006.6	6440	8018.82	8173.3	8375
6025	6450	8021.42	8175	8380
6050	6473.3	8022.22	8178.75	8389.29
6075	6475	8023.64	8183.3	8418.75
6100	6500	8030	8186.66	8423.08
6106.6	6506.6	8032	8192.86	8423.53
6125	6525	8035.71	8188	8435.71
6140	6540	8036.25	8188.24	8436.92
6150	6550	8045	8200	8453.85
6173.3	6573.3	8050	8225	8463.75
6175	6575	8070	8240	8469.23
6200	6600	8078.57	8250	8466.7
6206.6	6606.6	8080	8273.3	8475
6225	6625	8081.25	8275	8480
6240	6640	8090.77	8315	8483.3
6250	6650	8092.50	8315.38	8491.7
6273.3	6673	8100	8317.5	8541.7
6275	6675	8103.53	8318.18	8550
6300	6700	8104.62	8325.98	8575
6306.6	6706.6	8105.46	8326.15	8583.3
6325	6740	8118.46	8328.75	8600
6340	6750	8121.43	8330.76	8625
6350	8000	8121.81	8332	8650
6373.3	8007.14	8135.71	8335.71	8700
6375	8007.69	8140	8338	8716.7
6400	8008	8145.88	8340	
6406.6	8010	8161.53	8341.7	

Sub miniatance xtals type CR55/U in HC18/U holders.
Tolerance .005% Fully guaranteed. . . . \$1.05

Frequency. mc.		
50.383	51.050	52.050
50.716	51.383	52.383
50.050	51.716	52.716

Give 2nd choice selections
Watch 6Up & 73 for further lists

QUAKER ELECTRONICS

PO Box 215

Hunlock Creek, Pa.

What is the Institute?

1. Members
2. Directors
3. Coordinators
4. 73 Staff
5. Temporary secretary: Wayne Green

WHAT IS THE INSTITUTES' PROGRAM?

1. See that our legislators and government get publicity about amateur radio via the publication of a weekly newsletter.
2. A representative in Washington, Harry Longerich W2GQY/4.
3. Support amateurs in legal battles.
4. Establish club stations in new countries.
5. Sell ham radio world wide.
6. Get information on current events to all interested amateurs and IoAR members and encourage members to make their views known to ARRL directors and ARRL HQ.

Why is there a need for the IoAR?

1. Amateur radio has no representation in Washington.

a. Other users of radio frequencies have organizations in Washington to help protect their frequencies and privileges. See 73 April 64 page 18 for details. We, who have been the constant losers, more than any other group, should be strongly represented. We've tried doing without, can we learn?

b. Other hobbies have organizations in Washington to keep in touch with the government, and protect the privileges of the members against restrictive legislation and promote positive legislation. Good examples of this are the Aircraft Owners and Pilots Association and the National Rifle Association. AOPA, being on the spot, was able to get legislation through Congress quickly when they wanted alien pilots to be able to use their plane radios while in the U. S. Look how many years we've been trying to get reciprocal licensing.

c. The ARRL HQ group has been fighting a Washington office for years. There was considerable discussion of this in 1958 at the National Convention in Washington and the main

reason against a Washington Office for the ARRL at that time was that HQ was convinced that such an office would grow quickly and would eventually overshadow the Connecticut HQ, forcing everyone to move to Washington. They didn't want to move.

d. The Institute of Amateur Radio will be centered in Washington DC. Four of the nine interim directors of the Institute are in the Washington area and they are proceeding with the bulk of the organizational work from there.

e. One of the IoAR interim directors is an official representative and is in touch with the Senate, Representatives of the administration, etc. The voice of amateur radio is being heard where it counts.

2. Nothing is being done to keep our own government behind us.

a. We had very little support at the 1959 Geneva Conference. U. S. delegates representing the various users of radio frequencies admitted that amateur radio was at the bottom of the list.

b. The ARRL has proposed no program whatever.

c. The Institute started in April sending a weekly newsletter to every U. S. Senator, every U. S. Representative, every state Governor and all Government officials involved with radio. This newsletter stresses the public service of amateur radio and the benefits to the country of our having a strong amateur service.

d. Government officials and Congressmen have an office to call when any problems come up regarding amateur radio. The Institute Washington representative has personal contact for all of us.

3. Little is being done to prepare for Geneva.

a. The outlook for the next frequency conference is indeed black for amateur radio at present. Educated estimates are that we will lose 40 meters plus parts of 80 and 20.

b. The ARRL has proposed no plan. It is depending on the IARU.

c. The IARU is in bad shape. It was flatly turned down in region 2 (North and South America) in April when president Hoover had no program to offer for saving our bands. Instead a separate organization was formed with separate officers. IARU region 3 (Australasia) is virtually unorganized. Region 1 (Europe & Africa) is partially organized, but may soon fall apart over lack of any program.

d. The Institute proposes to make club stations available to locals in DX countries who are trained in amateur radio by visiting DX-peditioners. This should help introduce radio

IoAR News

to newer countries. Several manufacturers have volunteered to supply equipment for this program.

e. The Institute plans to send out an international newsletter to government officials concerned with amateur radio to point out the advantages of having a strong amateur service. All probable delegates to the Geneva Conference will also get this newsletter.

4. Amateurs fighting legal battles get little support.

a. Whenever an amateur loses a legal case involving amateur radio this sets a precedent which can then be pointed to in the future wherever a similar case is in contest. It is therefore of great importance for all precedent setting cases to be won.

b. The ARRL provides legal advice, but not money. Legal cases can be very expensive. WØJRQ has spent well over \$1500 fighting a suit against his tower. People that moved into his neighborhood well after he had his tower up have sued him for \$8000 damages to the value of their property because of the unsightliness of his tower. If he loses this case every amateur in the country with a tower would live in fear of a law suit for thousands of dollars and with a precedent for the suers to point to.

c. The Institute position is that cases like this are a responsibility of all of us and that funds should be provided to help amateurs who, through no fault of their own, have to fight a suit which could hurt all of us if lost. The Institute has sent \$500 to help WØJRQ with his case. We understand that this has resulted in quite a change in the ARRL position and that there is a good possibility that the League's council may now be available to help fight the case. This is an additional benefit which wasn't planned for. With this array of support there is a good chance that the complainants may give up the case.

d. In Santa Barbara three hams have been prosecuted by the city as public nuisances to put them off the air. The entrance of the Institute into this case, we are informed, has again seen an offer of ARRL council Booth to fly out and help fight. We understand that the city, informed of this turn of events, has thought better of the suit.

e. The Institute is investigating the possibilities of providing all members with an insurance policy to protect them from suits connected with amateur radio. The Institute intends to help as much as possible amateurs with legal battles involving amateur radio.

5. There are at present no checks and bal-

ances for immense power of ARRL HQ.

a. ARRL admits that they do not represent the amateur (July 63 QST page 9, paragraph 4).

b. ARRL HQ suffers from frailties. 1) Irresponsible submission of RM-499. 2) Coca-Cola deal. 3) Santa Barbara legal battle 4) WØJRQ legal battle

c. It is much more difficult to succumb to frailties when you know that some group is watching your every move. Much more.

6. Little is being done to improve the technical standards of amateurs.

a. ARRL recognizes and decries the situation, yet has not furnished leadership.


b. The Institute proposes to establish a program of technical achievement with certificates and awards. 1) Exams to be given at hamfests and conventions under close supervision of clubs. 2) Awards for outstanding developments, break-throughs, unusual construction projects, patents, etc.

7. There is no organization program to keep commercials out of our bands.

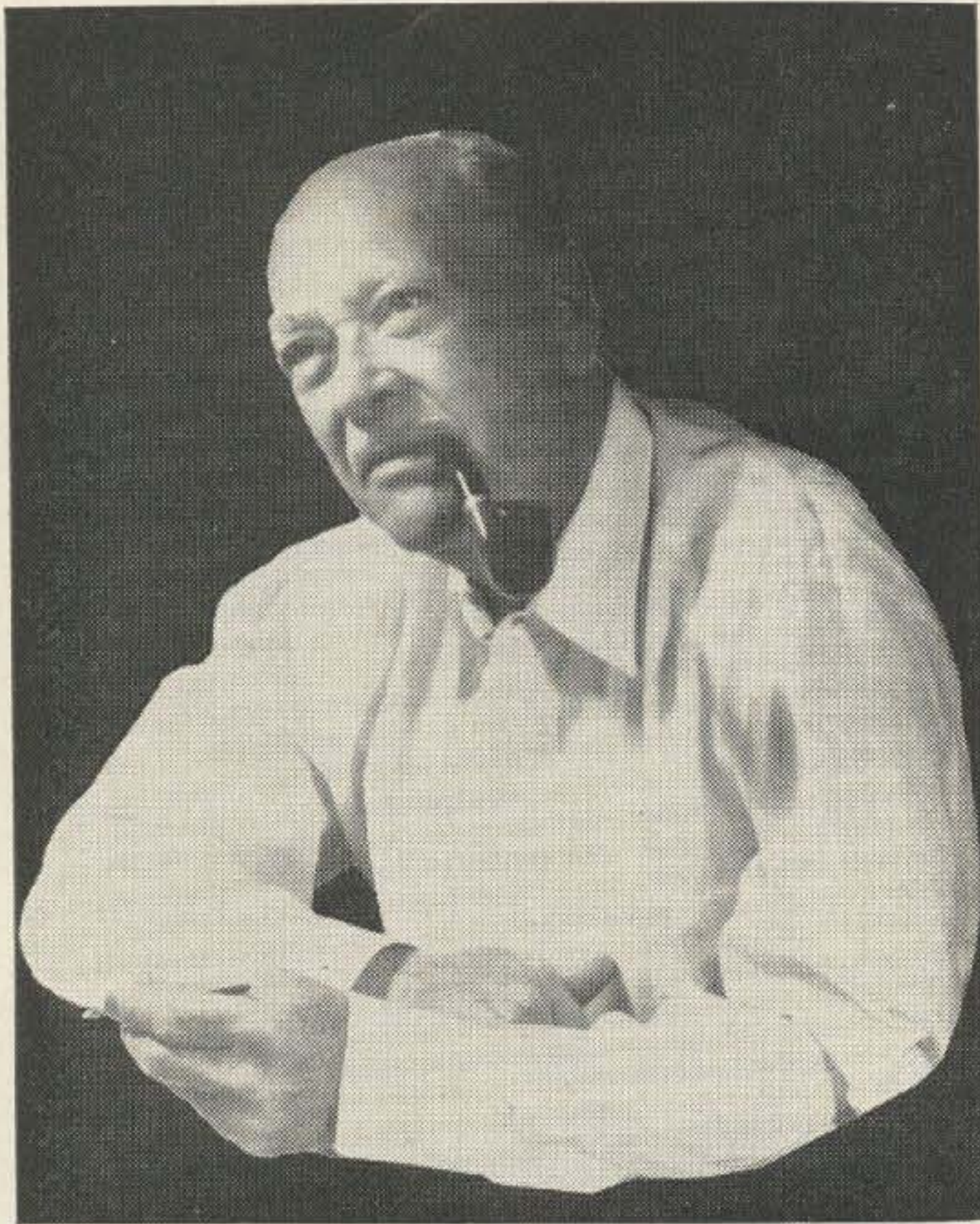a. Mount a full scale attack on illicit use of our bands by other services. Co-ordinate a serious effort to identify all transgressors. Lodge official complaints against them with our government, the ITU, the government of the country involved through their representatives in the U. S. and directly. Should this not get results we can muster the full strength of IoAR membership to put pressure on their government, their representatives in the U. S., their travel bureaus, etc. We will also let all the members of our own Congress know that the country is operating or condoning operation of transmitters contrary to international agreement through the ITU.

Interim Director W70E

Howard Pyle W70E. Age 66, licensed 1912, now Extra Class. Past calls: HP, MA, 7HP, 7NG, 7FT, 7OE, 7ASL, 8FT, 8RI, 8DAG. ARRL member since inception. Also member of SM, IAE; VWOA; OOTC; OTC; DeForest Pioneers; A-1 op; Morse Telegraph Club. Has had hundreds of articles published over the past 50 years plus six books, four of which are current. Retired Electronics Engineer with U. S. Gov't. Has worked as a sea-going merchant marine operator, marine coastal station operator and manager, 5 years Chief Radioman (permanent appt.) U. S. Navy, Chief Engineer several radio manufacturing com-



panies, manager RCA marine dept. Chicago, wholesale radio salesman, radio and later electronics engineer, U. S. Gov't. (2 depts.), Asst. U. S. Radio Inspector, Bureau of Navigation, etc. Charter and Founding member of IoAR.

Biography and Comments de K2TKN

It seems like a long time ago, and I guess it was . . .

A cousin came to spend the summer vacation. He was the same age as my brother and life became somewhat strained for me, being five years younger. This cousin was an electronics wizard, for altho only aged 12 or so, he had constructed a crystal set that actually worked.

After weeks of untold favors, cajolery, and outright bribery these two hooligans condescended to show little brother how to construct a set. A tightly wound coil of wire on a cardboard tube of well-known but unmentionable origin, manufacture of a sulphur and lead crystal, and trading him out of his spare headphone (as I recall, my soul was only a small concession in the deal) and I was the proud possessor of the finest crystal set in Kansas City that stoutly refused to utter even a faint squeal. Long weeks were spent that summer, winding and rewinding that coil, carefully scraping a path for the slide tuner to contact, all under the close supervision of this radio whiz kid. Noth'in . . . Not the faintest sound. He went

back to Des Moines and school and after several months more of fruitless effort my brother let slip that that tightly wound coil of mine was bare wire while the working model had enamel insulation. After 30 years I do occasionally speak to my brother again. In spite of his perversity, the cousin went on to become W9TGL (three gorgeous ladies) of pre-WW2 fame and today is a slightly tarnished BRASS HAT in the AIR FORCE who has been known to get on the air as W4WGO. After what seemed eons at the time, I recall learning the code at government expense. This consisted of religiously taking the amateur tests every time the FCC inspector came to town with his tape machine, always flunking but each time by a little less, meanwhile frantically bootlegging on 160 meter fone far into every night. To this day, I am sure that kindly inspector (MacDonald) overlooked an uncrossed T or misplaced punctuation mark to get me 65 in a row and out of his hair, or off 160, I am not sure which.

What a thrill to legally call CQ and hear an answer—Ollie W9EKJ who was clear across town was in there loud and clear. He promptly, with some knowledge of prior operation, demanded that I get off the air and quit using his call—refusing to listen to my attempts at phonetics to explain my call was plainly W9ETJ on my license and he went clear ape when my buddy George Horner, who had received his ticket that day also, called in with W9EDJ. Half the whole 160 meter was in that ruckus before the air cleared that night. Shortly after, I was initiated into the business side of this game, chasing parts at Van Sickle Radio, St. Louis for Griff W9OWD, God rest his soul. I am sure he and Walter Ashe gave more young squirts their start in this business than all the DeForrests, Sarnoff's, etc., put together. And Walter is still doing it.

Wells Chapin W9DUD was building some of the biggest and prettiest KW rigs ever known by the late '30's. I know, for he used to come into the store and buy a \$1.19 17 x 13 x 4 steel chassis, they didn't come any bigger and my job was to punch out the holes he drew on the brown paper cover. Try going into the parts house today, buy a chassis and ask them to punch the holes for you (HA) and all we had in those days were Greenlee hammer punches. That's what the part-time after school amateur kids working there were for. After working there several years, the Naval Reserve was called out and I got out of High School concurrently in early 1941. That free crystal cost me 5 years in the Navy. As I recall, I owed Griff about \$3000 for parts purchased

IoAR News

at employee discount above my wages, which he had tallied every week then written off as a dead loss. I had DXCC before I found out boys were supposed to go out with girls and had collected several Grand Island FCC QSL's for shorting out the only choke in the PWR supply on my push-pull parallel TW-150's after a W6 let slip how to get that sure fire bat of 120 cycle gargle that no DX on the low end of twenty could resist. If there hadn't been plenty of science courses and a ham as principal of the school, it couldn't have been done. In those days, OM, DX was pure work. They hadn't been Gus'ized, Danny'ized or Collins'ized and neither had we.

By 1946, an old grizzled hash-marked Chief Radio Technician was let out to pasture, after all he had been thru every radio and radar tech school they had and then several years of too many TBM-TBK, SA, SC, SQ, SG, over two hundred SJ's each with cronic problems someone had to suffer with. I was 22, but felt everyday of 100. One bright spot stands out in my memory of those days. One Christmas eve when I had the duty at the RMO 15th Naval District Panama and after finishing straightening out the bumps in the linoleum of the radio shack floor or some other highly secret technical detail transit ships demanded the base experts attend to while the crew bellied up in RioBahoo, some other dis-franchised ham and I were sitting there sloppin up coffee and discussing the hell of being in DX country at such a time. This was in the radio shack of a tin-can, I believe, and there was a TBK transmitter with the filaments lit, tuned up at a full gallon on 8120 kc or such. Deciding they could only shoot you once, I let out a long slow CQ DX and signed W9ETJ. This was 1944 when we were not exactly winning the war in the Pacific and there hadn't been a legal Amateur contact since 1941. The band opened up for 20 kc either side with the \$\$\$""&# pile-up of DX ever packed in at one time in the history of radio. For the next two hours we worked'em by the gross. There were Japs, Germans, Iti's, Russians and Allies by the numbers. On the frequency, that night before Xmas, there were just Amateurs, doing what they like best—there just wasn't any war for us for abt two hours. Half the GI's were too chicken to sign their own calls and used initials, etc.—it sounded like 75 meters the night before we got the band back after the war. Finally, someone decided this amateur bit was not the way to fight a war, and NSS cranked up on frequency and demanded identifiers which rather squelched the whole thing. At noon the next day, there were still a

couple of PY's working J's for WAC on the frequency. The fact that Boyd Phelps W9BP was RMO may have helped keep in out of the brig.

By 1950, after deciding there had to be better ways of making a living than AM soap-radio engineering including owning a peanut-whistle, KXGI, and going thru the BOOM TV shop periods, I ended up a field engineer with Raytheon Mfg., Chicago. Six hundred and fifty service meetings later moved over to the Magnecord and sales. By this time, WØETJ out of Elsberry Mo. had done fairly well on six and two. That five or six miles west of the Mississippi river sure made that an ideal location. Being the first WØ going west when six and two were new was some pumpkins, I'll tell you. There were more than numerous occasions when Dallas W9AAG, Red W9EHX, W9MUD and many other W9's in western Illinois sat there and heard W1, 2, 3, 4's calling and at times working that ### Ø just over the line. Before leaving, a 25 ft. cylindrical parabola 70 feet in the air had effectively removed about two states from the distance to the East Coast. W2AZL and W2CXY still claim I must have been using that xtal set with the bare wire coil but the 4-125's at 4 KV and 1 amp put out a fair signal after little taming, and care not to make long dashes. Don't get out your slide rule to figure out the input—that was the most legal KW ever generated to snag DX on two. If you held the key down long enough for the meters to slow down long enough to read, those 4-125's would have been walking around the ceiling of the shack.

Ten years ago, Ed WØLFE, inherited the favored WØ position and has done very well for himself, while I am in the middle of the gibbest pile of locals on VHF in the world. The band could be wide open to W6 on two from New Jersey and the call K2TKN and 10 cents would get me a bad cup of coffee under the pile-ups. There was nothing else to do but go on 1296 mc to find some elbow-room. I find there is plenty.

An old man from up the road, after looking at the 20 ft parabola and other contraptions cluttering up the QTH and learning I point these at the moon on occasion, asked "But what does the Moon say" and you know he may be right. There sure isn't much of a QRM problem.

Being a gadgeteer by nature, VHF and UHF have always fascinated me for here are vast areas of uncluttered space where an untutored amateur, by the expedient of extreme specialization and simply wanting to do something of value badly enough, can make monkeys out of

IoAR News

the communication "experts." We've got receivers now that make their Kilobuck specials about equal to xtal sets and we have always been willing to try anything. They can't get a contract from the Gov. unless their theory looks right. We can't lose, all we have to do is play the cards. They may have been stacked in our favor up in this range of frequencies.

Below 100 mc, I am afraid it is another story. The majority of my actual operating time in the DC bands recently has been on Air Force MARS channels. If you would like to fully understand what the HF amateur bands are going to sound like shortly at the present descent levels, try copying SSB traffic on 3295 kc at 0200 Z or 7460 kc. These are military channels with the full authority of the US backing them up and this makes them open season for every raw ac crud generator in this hemisphere. Reread W4LCY article in May 73—then read it again and see that every meeting of your local beer-chowder club is devoted to actually what can be done. Let someone else win field day, for at the present rate of descent there aren't going to be many more anyway.

I am a lousy commercial—I make a living selling Cornell Dubilier products to the parts distributors that sell to amateurs. Loss of the HF amateurs bands or incentive louse-up would mean reduced HAM-M and TR-44 rotor sales. (It already has in truth.) That would only leave less than 28,000 other items for CD to sell to the distributor whose amateur sales dollars are a small part of his total. You don't seriously believe the amateur sales of Collins, Hallicrafters, etc., keep these companies in business, do you—this isn't 1938—it is pretty late in 1964. And if you don't think I know this market and how to peddle merchandise, reread the sub-liminal (free) ad built into the second sentence of this paragraph. Bill Orr and his group of old pro's couldn't have done better in QST. Which reminds me, you couldn't buy my ARRL membership for kilobucks during this hassel. I've found as a mem—I am entitled to vote now and then. It isn't for much, but few bothered in the past so who cared? I've had go-rounds with Headquarters before about raw commercialism in QST and their lack of interest in 432 mcs when we needed it most, and found them subject to the same human frailties as most. Pressure on a Director who in turn does a little desk-pounding has it's effect. I like to remember copying code practice on a one-tube blooper and the thrill of W1AW's big signal in the middle-west a long time ago, but as I have gotten older and a bit more experienced in worldly ways, I'm

afraid the ARRL doesn't have the same image it once did for me. As a commercial corp. they would bumble along making large noises of extremely conservative gooble-de-gook til the first highly specialized, market and cost conscious—sales oriented competitor took them to the cleaners by the chapter and verse. The crime in this case is that *you* are going to lose forty meters and large chunks of the other HF bands while *we* try to straighten out our internal organization. Everything is new at Headquarters except the direction and point of view. The outpourings and apparent objectives seem about ten years old.

Our first preliminary organizational meeting of IoAR directors was, by necessity, in regard to immediate and extremely necessary actions and short range objectives. A great deal was said about the average amateur and what they could do, given the opportunity, to keep what they own. I didn't say much, for I was in complete agreement with what was being said. But, after the meeting, when driving home, I had a chance to sort out the multitude of thoughts proposed by this keenly and currently aware group. It suddenly struck me. . . I have never met an *average amateur*. I'm not average, and you're not either. If I was, I wouldn't admit it, and anyone that says I am is in for a very hard time. As sure as I am sitting here looking for the erase key on this mill, my ARRL director has me lumped up with all the other K2's and he tries his best to represent this image. No wonder things are in such a mess. And if this is true, the HdQtrs people must think of the average director and his views as representative when making daily decisions that affect everyone of us . . . My God—I'd rather eat a can of worms than picture that, but it is true, and it has been going on for years.

But that is democratic government, you state. Not by a long shot, not in professional politics in modern times. We live in the best country in the world today because a finely balanced set of check and counter checks have developed at all levels, individual, ward, city, county, state, and national, keeping everyone aware of current situations and on their toes. The very intricate system of lobbying at all levels of government, from your local school board to congress, is an extremely important part of this system of government that we are justly proud of. I'll guarantee you are not first in line waiting to vote in some local or even national election, but even a hint of increased property tax will put you firmly up front pounding the desk of your alderman or town council member, etc. I've never heard of a lob-

IoAR News

by in Washington actually representing me as a US citizen, but there are hundreds of them representing in fine detail every facet of my every day action, each highly specialized in a certain field. This I can understand and now it is apparent to me how IoAR can provide an aggressive and healthy additional service to every amateur. Just keep in mind that each of us is an individual with divergent views, pet-peeves, and care-less's. If you don't think so just ask your wife—I wouldn't dare ask mine!

Let me illustrate my point. You are a paid-up member of IoAR and without your individual approval, I am a temporary director of IoAR. I am professionally employed in electronic industry, an advertizer and paid-up member of ARRL-QST and am going to stay that way. That lost about 25% of you. I think we are too little and too late and am sure we are going to lose much of our HF bands in the next few years, and think we are getting just what we deserve for lack of effort. That alienated another 50% right there. DUD just flipped. My opinions on how to clean up the HF bands are well known by some, but in particular by the FCC. My petition to them, countering the ARRL foolishness, makes operation on any mode on any HF band a privilege that must be earned by each individual amateur by personal effort to expand our knowledge of VHF-UHF, by extended occupancy thereof with state-of-the art equipment, homebrew, kit or appliance. Try to DX-country hop and keep your HF privileges under these conditions. If you think I'm kidding just forward SAS plus for duplicating cost and you can read a copy of this bomb. That eliminated most of the rest, but just to make sure, many individuals and clubs have heard me expound on why Technicians should be re-newed after the 1st five year period by formal office exam, only and that the conditional situation stinks to high heaven. Wow!

I do believe that VHF-UHF expansion is our only hope, that a few thousand experienced adult-oriented (no grandfather clause crutches) HF stations can handle 10 times the true emergency possible in the trivia current today, and would present an image to the rest of the world that would help us expand amateur radio, rather than destroy what we all love and wish to preserve, *as is now happening*. I think that the most important single quality of Amateur radio is that you transmit only if you desire, say only what you want about your views, circumstance, convictions or color and can shut off the rcvr and hit the sack at *your*

convenience. There has never been a social precedent similar in history and any personal effort on our part is well spent to preserve it.

I am sure you do not want me standing up representing your personal interest in amateur radio, for these aren't your likes and desires.

This is precisely my point.

IoAR is composed of individual members and there is no reason each cannot actively but even several thousand individual cries in promote and lobby for his particular specialty, the wilderness have no effect without some form of co-ordination. Whether by design or fate, each of the temporary directors in IoAR is fairly specialized in sphere of influence and personal interest.

I propose that IoAR become the most vocal stridently-insistant lobby in the amateur world. Guided by direction and suggestion of the directors, each in his own special interests, thru our own channels and the pages for IoAR in 73 each month, each member should direct one personal message per month to his ARRL Director, a personal message to the home address of John Huntoon or other salaried employee of the League, and one to the most appropriate Washington address indicated by current information. Not by mail, after all we have a fantastic communication system in amateur radio. Can you imagine the result in these comic strip nets on 80 CW when 10,000 30 to 50 group messages hit the NCS. After they give up, we will handle them on IoAR relay. For the first time, RTTY and plenty of it is a necessity. Here is an opportunity for a traffic organization that people will wait in line to join. If you think the Military won't suddenly be interested in this type of operation, think again. The possibilities and complexities could only be handled by amateur radio. Each individual IoAR member can represent himself, or abstain from any issue. Each Director represents special amateur interests, not geography or mass, acting as a focal point and director of attention.

For some reason I have an idea that thought of mail or phone calls around Hdqtrs isn't going to be popular discussion, for the next few years. Just to keep those lovely secretaries busy, every member should write and ask one detailed technical question in regard to any current QST tinker-toy project every month. I have never known a group that talks as much and says so little as the US Amateurs, but if each reserved just 150 well chosen words a month and directed them in certain directions, mountains wouldn't move they would run.

1964 Special Surplus

Our special surplus issue last year brought so many compliments that we thought we'd bring it up to date. We've been using the catalog section quite a bit here at 73, but then I'm a surplus nut, as anyone can verify that has seen our barn.

There was a time when I darned near swore off surplus. It was right after the war when the War Assets Administration was giving large lumps of surplus to schools that would accept them. Well, imagine my delight when an SCR-547 turned up in the vacant lot next to my school. As president of the radio club I could see where we had some fun ahead of us trying to convert that into something useful. We tried to get some official action from the school on the thing, but couldn't find anyone to accept the responsibility. We got more and more frantic about it as the local kids played war with it, using the tubes for grenades and smashing everything breakable. Finally, in desperation, four of us rescued the remains for the club. This brought officialdom to life. The school decided that everything would be alright if we paid for the parts destroyed by the local kids. It was a bitter pill for us, but we paid. Somehow I've never encouraged anyone to go to that school since then.

I've been buying surplus again so I guess the wound has healed. We're busy converting APX-6's, AXT's and ART's for 432 and RDP's for watching the UHF bands for activity. We've got a surplus TV camera chain and some wide band FM gear. We hope to have all of this working from 73 mountain this summer.

Surplus has done a lot for ham radio. Where would two meters have been if the SCR-522 hadn't been available in huge inexpensive quantities? Thousands of them were put on the air. I wonder if the original Gonset Communicator would have made it if there hadn't been all those 522's around? I'm still using a 522 as a driver for my high power rig on two meters . . . the final is a piece of surplus too (Herbach and Rademan \$29.50). How many of you have *not* converted an SCR-274? Not many.


I buy surplus because I am a cheapskate and I want to get the most hamming with the least dollar investment. The following pages represent a pretty fair catalog of the surplus that is available today in all parts of the country. It is a lot easier to read it here than to try to visit Boston, New York, Ohio, Chicago and Los Angeles . . . and most of these fellows don't have time to put out a catalog.

Catalog Section

SPECIALY SELECTED "GOODIES", the CREAM of MILITARY and INDUSTRIAL SURPLUS at SKIM MILK PRICES.

All items guaranteed as described, new except (*) removed from equipment, usually new, in good operable condition. Prices are NET, FOB our store, Chicago. Mail orders, please include enough for postage & insurance, excess returned with order. Illinois orders, add 4%.

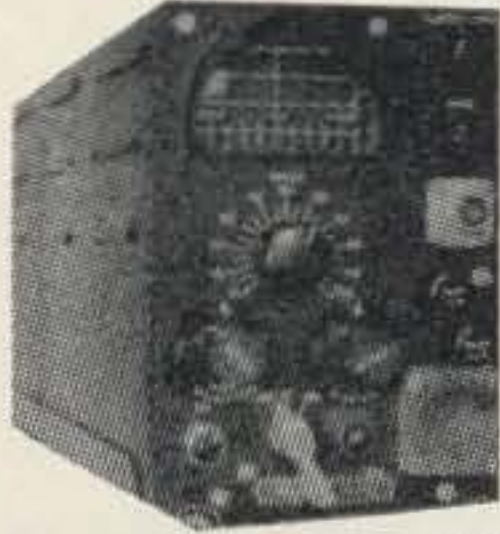IP-274/ALA-10, PANARAMIC ADAPTER, for 2 meter. 30 MC



in, 10 MC width; 110v 400 cycle power supply. Quick, easy conversion, to 60 cycle, solid states power supply; also conversion to 14 MC input, if desired. With conversion schematic and instructions. Ex. used, complete with 3BP-1 and 17 other tubes. 7 3/4" w, 5" h, 19" d. Shipping weight 25 pounds. \$40.00



RT18/ARC-1, 100 to 156 MC Transceiver
10 channel, crystal controlled, with separate guard (monitoring channel). 9.1 MC IF. Complete with 2 832A, and all other tubes. 7 1/2" h, 10 1/2" w, 19 1/2" d. Very excel. used, less 24v dynamotor with conversion instructions and schematic. \$25.00




RT82/APX-6, 1296 MC Transponder (transceiver)
Tunes the 1296 MC ham, or "moonbounce" band. Complete with all tubes. Very excellent used. \$17.00

R11, 190 to 550 KC RECEIVER




"Q-5er REBORN" With 85 KC IFs. See Sept. 1963 issue of 73, for conversion. Complete with all tubes, Ex. used \$20.00; NEW \$30.00

COMMAND SETS, back to 1947 prices!

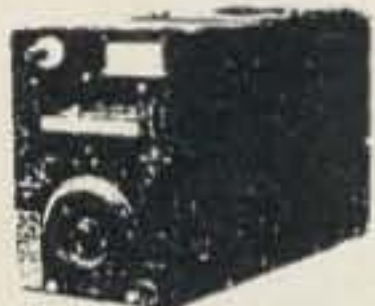


T-18/ARC5, 2.1-3 MC, for 160 meter. Ex used \$5.25; BRAND NEW \$6.50
T-20/ARC5, 4-5.3 MC, for 80, 6, or SSB VFO. excel. used clean \$5.00
BC-458, 5.3-7 MC, for 40 meter, or CENTRAL ELEC. SSB. like new \$6.50

CENTRAL ELECTRONICS' "Q" MULTIPLIER

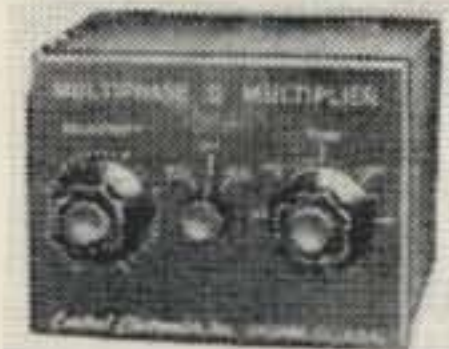

The important parts for this unit—380 mmf & du-30 and 60 mmf variable; 455 KC IF; 20k pot; "Q" coil, wiring diagram & schematic. NEW \$5.00
W/cabinet, no panel \$5.75

VARIABLE CAPACITORS-PI NET, APC

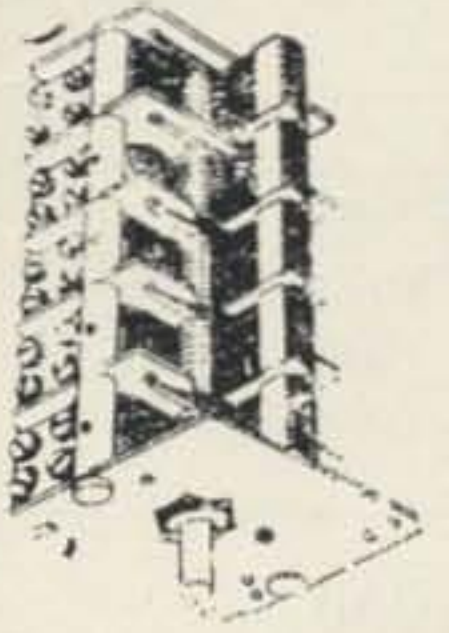


- A) 5 gang, 402 mmf/sec. total 2010 to load 160 meter, no inducance. 3/8" shaft. 60:1 worm drive.* good \$2.50
A) AS above, less drive \$2.00
B) 3 gang, 440 mmf/sec. 3/8" shaft \$2.50
C) dual 150 mmf/sec. 1 KV, 1/4" shaft \$2.50
D) dual 250 mmf/sec 1 KV, 1/4" shaft \$2.50
E) dual 140 & 365 mmf, for BC rec. 39c
G) 143 mmf, 600v APC. 1/4" shaft. 69c: 3/1.95



Vacuum capacitor. 50 mmfd 5 KV.
* clean, good. \$2.00: 3/\$5.50

CO-AX CONNECTORS, LOWEST PRICES

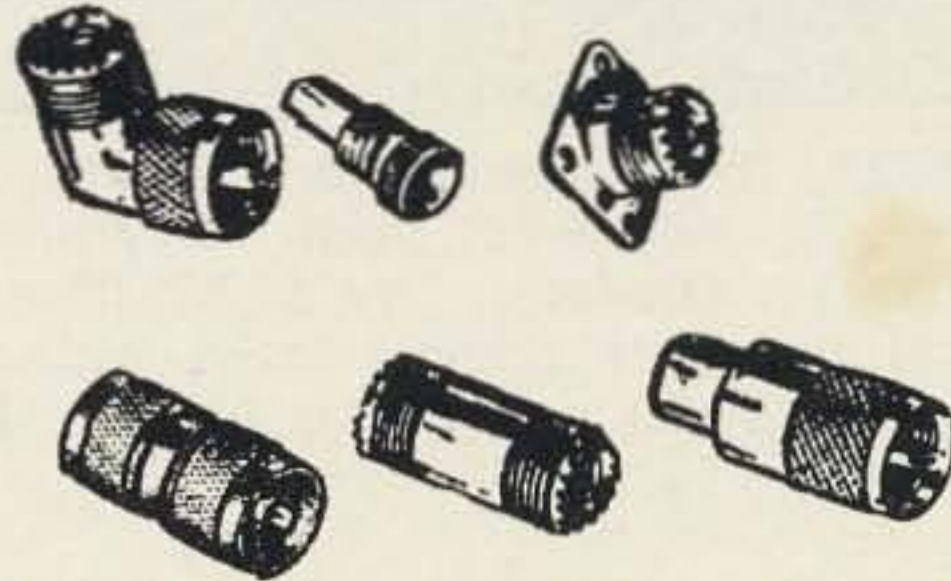

- A) CH-259, chassis male, for SWR bridges, T-R relays, VFOs, etc. 95c ea; 5/\$4.50
B) DOUBLE MALE, DO NOT BIND, 89c; 5/\$4.25
C) S-239, one hole chassis female 50c ea
D) PL-259, E) SO-239, F) UG-21/U, choice 35c each; 12 for \$3.75; 100 for \$30.00
E) UG-175, or UG-176/U, 11c; 10/\$1.00
G) PL-258, double female, 65c ea; 5/\$3.00

CO-ax CABLE

RG8/U, poly-foam, non-contaminable cover. BRAND NEW 50 feet \$6.50; 100 feet \$12.00
RG58A/U poly-foam, stranded center conductor, low loss; 50 ft \$2.50; 100 ft \$4.75

NUVISTORS-NEW, RCA, Bulk Packed

7587, tetrode, 5 watts on 2 meter, \$4.50 ea
6CW4, sharp cut-off triode, \$1.85; 3/\$5.25
SOCKETS, for above, 15c ea; w/3 above, 3/35c

1625 TUBES-OUR VERY BEST BARGAIN

NEW, bulk packed KEN-RAD, 19c each. Min mail order 12/\$2.00; 50 for \$7.50

CATHODE RAY TUBES—Mu Metal Shields

3EP1 \$1.95; 3GP1 \$1.95; 3AP1 \$2.95; 3JP1 \$4.00
5CP-1 \$5.50; 5LP-1A \$7.50; 5RP-1A \$10.00



Mu Metal Shields for
5BP-1 \$2.50; 5CP-1 \$2.50; 3BP-1 or 3JP-1* clean \$1.75

TUBES—TRANSMIT, RECEIVE, SPECIAL PURPOSE

3B28* \$3.25; 6DQ5 \$1.75; 815 \$2.50; 5892 \$1.50
\$1.00 each, 4 for \$3.75
807*; 6DQ6B; 1616; 3B24; 6J4*; 2D21; 6AN4*; 5687* 89c each; 3 for \$2.50
6AS7G, or GA*; 6Y6G*; 5R4GY*; 6L6GA*; 6AG7*; 5T4 79c each; 3 for \$2.25
VR-105; VR-150; 0A2*; 0B2*; 12AT7*; 12AX7*; 5651 69c each, 3 for \$1.95
6AC7; 6SG7GT; 12SG7; 12K8; 12A6; 6SN7GT*; 6SL7GT 6AG5*; 6AK5*; 6AL5*; 6AQ5*; 6AU6*; 12AU7*; 12SF7 49c each, 3 for \$1.35
5Y3GT*; 6X5GT*; 6K7; 12C8*; 12SR7*; 6C4*; 12J5* 29c each, 4 for \$1.10
6SH7*; 955; 957; 1626; 6H6*; 76; 7193; 14B7; 7E7

HEAT DISSIPATING TUBE SHIELDS



See page 24 to 27, Feb. 1964 Issue of 73. For miniature tubes. Made by CINCH.
1 1/2" high, for 7 pin 2" high, for 7 pin

EIMAC HR-8

Heat dissipating plate caps, .578", for 811, 813, 866, etc. NEW \$1.79 each 4 for \$3.00

9 Pin tube Straighteners. BRAND NEW, by STAR. All metal. 35c each, 3 for \$1.00

I'll be at: Starved Rock, June 7, (Ottawa, Ill.); Lancaster, Ohio, June 21.

BC Electronics 2333 S. Michigan Ave., Chicago 16, Ill., CALumet 5-2235



M-359	25c
UG-175	15c
UG-176	15c
S0-239	35c
PL-259	35c
PL-259D	90c
S0-239SH	40c
UG-260	35c
UG-604	35c
PL-258	75c

MAT HI FREQ TRANSISTORS

Micro-Alloy Transistors.
Hi frequency.
5 for \$1.00

UHF TV TUNER

\$4.50

Complete with tube, used to convert Dumont TV for UHF channels. Seem to be useful with other types TV or use as converter. All unused.

BC-221-AH UNUSED	\$ 80.00
BC-221-AK UNUSED	100.00

IBM WIRED MEMORY FRAMES.

Removed from high priced computers. ExInt condition.

4,000 core	\$12.50
8,000 core	15.00
16,384 core	35.00


MEMORY DRUM w/drive motor, 40 read-write heads \$75.00

SPECIAL ★ SPECIAL ★ 2 AMP SILICON RECTIFIER, 1,000 PIV \$1.00 SPECIAL

UNBELIEVABLE COMPUTER GRADE CAPACITOR

80,000 mfd 12 volt	\$4.00
35,000 mfd 12 volt	3.50

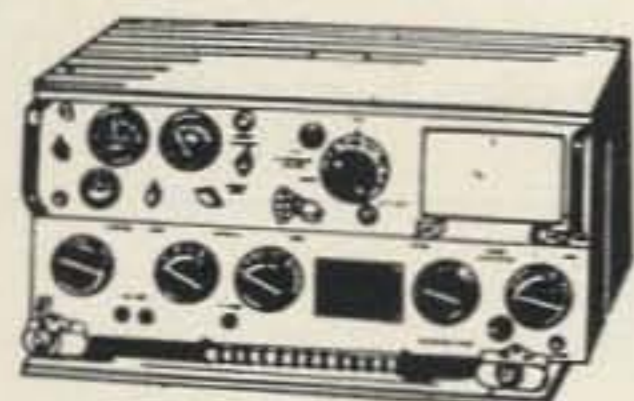AN/ART-13 100-WATT XMTR
11 CHANNELS
200-1500 Kc
2 to 18.1 Mc



Collins Autotune Transmitter, extremely stable and suited for side band. Written up in QST Oct. issue 1963. Used, with tubes. \$50.00

We have parts, what do you need?

NAVY RBA LOW FREQUENCY RECEIVER

RCA mfg, tunes in four bands from 15-600 kc. Direct reading dial, used by the Navy up to recent date and just being released. Outboard 115 AC 60 cycle power supply with each. Just the thing for you old shipboard sparkies. Also picks up the new long wave Navy stations on 60 kc. \$95.00

2N389 NPN SILICON POWER TRANSISTOR

TO-53 case, 85 WATT 60 volt Silicon \$1.00 each

SILICON MESA TRANSISTORS

2 for \$1.00

2N696	NPN	2 Watt	80 MC	TO-5
2N697	NPN	2 Watt	100 MC	TO-5
2N711	PNP	150 MW	150 MC	TO-18
2N705	PNP	300 MW	300 MC	TO-18
2N784	NPN	1 Watt	200 MC	TO-18

LAMBDA POWER SUPPLIES

Used, good shape.

Model #28	\$30.00
#32	50.00
#32M	50.00
#C-280	60.00
#C-280M	70.00
#C-281M	60.00

SILICON CONTROL RECTIFIERS

PIV	2 amp	20 amp
50	1.00	2.50
100	1.60	3.00
200	2.00	3.45
300	2.50	3.75
400	3.00	4.35

28 VOLT DC 40 AMP POWER SUPPLY

In put of 115 or 220 volts AC 60 cycle. A husky power supply useable in a multitude of ways. A suitable variac will permit variable voltage from 0-32 volts DC out. Shipping wgt. 150 lbs. \$50.00

MESA TRANSISTOR 500 mc

TO-18 case, sub min. Germanium PNP, Vce 8 volt, Ic 50 mil, 150 mw power #TRANS-5 80 ea. 3/\$2.00

ALL MATERIAL FOB LYNN, MASS.
JOHN MESHNA, Jr.
Surplus Electronic Material

19 ALLERTON ST.

LY 5-2275

LYNN, MASS.

NAVY BEAM FILTERS

1020 cycles, same as FL-8 but more elaborate, with cord and PL-55 plug. Switching control on slant panel for easy viewing. New\$1.95 ea.

Patch Cord Kit

Consisting of 2 ea. 24 inch cords, 2 ea. 14 inch cords and 2 ea. 6 inch cords. These come complete with plugs that fit standard meters and test equipment. Used for quick connect, all for97c

TCS REMOTE SPEAKER

5" high quality, Jensen PM speaker. A built in transformer is a match for any low impedance headset output jack on any receiver.\$4.95 ea.

GEIGER COUNTER

Uses famous Geiger Mueller Tubes, which detects gamma radiation. Comes complete with earphone and battery. New only\$4.95 ea.

WIRE RECORDER

Compact wire recorder. Used for recording conversation in flight. Can be used in autos or boats since it operates on battery power.\$7.94 ea.

SELSYN MOTORS

such as 5G, 5F, etc. 110 volt 60 cycle \$4.95 per pair

60 MM MOVIE CAMERA

Magazine load type, complete with F3.5 lens. Battery operated. In excellent condition.\$14.95 ea.

CHOPPER

6 volt 400 cycle. Uses: DC amplifier, tone generator or interrupter, etc.\$.97 ea.

KEYER

Designed to provide automatic identification and to send automatic signal. Can be used to key transmitters, etc.\$3.95 ea.

REMOTE AZIMUTH INDICATOR ASSYM.

Consisting of I-81 indicator, with built in autosyn and a model 2J1f1 selsyn generator with 60 cycle transformer all for\$4.95 ea.

RDZ CRYSTAL OVEN

Will hold 10 crystals and works on 12 Volts AC or DC95c ea.

TEST EQUIPMENT

TS-13 A/P signal generator, with self contained wave meter and power monitor. Frequency range from 9300 to 10,000 MC.\$75.00 ea.

ART 22 noise and gate generator. Random noise generated by a magnetized 6D4 gas tube, is amplified and the output may be gated at a rate determined by external trigger source.\$22.50 ea.

TS-239 U/P Oscilloscope. 110 Volts operations. 10 cycle to 5 MC duration of impulse. This equipment consists of a calibrating voltage generator, a timing marker generator and a trigger generator. In good condition\$89.50 ea.

TS-102 AP range calibrator. Produces a square topped. 50 volt synchronizing pulse.\$7.95 ea.

WHEATSTONE BRIDGE

Simply modified into a self contained wheatstone bridge by merely changing a few connections, and will accurately measure the value of unknown resistors, chokes and capacitors. New\$7.95 ea.
Used4.95

UPM 8 Signal Generator

Features, range 980 MC to 1230 MC. Can be used as signal generator, pulse generator, power meter and receiver\$49.50 ea.

TRANSMITTERS AND RECEIVERS

ARC-4 transceiver, 4 channel crystal controlled. Makes an excellent 2 meter mobile.\$29.50 ea.
12 VOLT DYNAMOTOR for above\$14.95 ea.

ARC-5 Receivers

3-6 MC automatic selector type\$7.95 ea.
6-9 MC6.95

ARC-5 Transmitters

2-3 MC\$4.95
3-4 MC6.95
4-5.3 MC4.95
5.3-7 MC4.95
BC 456 Modulator for command transmitter3.95
ARC-5 VHF transmitter 100-156 MC14.95
APX-614.95
50 CHANNEL ARC-1 transceiver 100-156 MC for 2 meters or even 6 meters49.50

MOBILE POWER SUPPLY

12 volt transceiver power supply consists of dual dynamotors. Mounted on filtered base with starting solenoid 420 volts at 200 MA and 200 volts at 100 MA. Can be used for ARC-5, ARC-3, 522, etc.

SPECIAL

RA-62 POWER SUPPLY, 110 volt AC rectifier Power Supply for 522, ARC 3, ARC-4, ARC-5, etc.\$39.95

PE-98

12 volt SCR 522 dynamotor. New\$6.95 ea.

MOBILE WONDER

12 volts in, 24 volts out at 4 amps. For operating 24 volt equipment on your 12 volt car battery. 10x4x6 inches, water and moisture proof.\$9.95 ea.

TELETYPE

88 MH mounted in a protective casing in new condition. 5 for \$1.25

Teletype Power Supply

150 volts AC input, output 120 volt/75 at 35 watts\$4.95 ea.

Teletype Power Supply

115 volts input, output 120 volts/130 at 130 watts \$9.95

Teletype Power Supply

110 volt input, output 120/130 volts at 200 watts \$14.95

for Model #15

Teletype Base

In new condition, less hardware\$4.95 ea.

Teletype Keyboard

Brand new\$19.95 ea.
TD COVER\$2.49 ea.

MISC. TUBES

6114 ruggedized 12AU75 for \$1.00
16254 for 1.00
1P28 Photo Multiplier4.95 ea.
931 A Photo Multiplier2.95 ea.
Sub miniature assortment removed from late equip. 6 for 1.00
3EP1 scope tube97 ea
3DP1 scope tube2 for 1.00
2C46 lighthouse1.75 ea.
2C42 lighthouse1.49 ea.

Germanium Rectifier

Mounted in heat sink plate, 200 volts 5 amp per plate, 4 plates in stack can be assembled to higher current lower voltage\$1.49 per plate

2 VOLT STORAGE BATTERY

Rechargeable type, 20 amp hour\$2.49

6 Volt DYNAMOTOR ASSYM.

Mounted on a 19" panel, completely filtered, output 225V at 60 MA. New\$2.96

HOFFMAN SPECIAL

Hoffman TV remote control, consisting of 8 push button channel selector, motor drive and remote speaker, 25' of cable, new\$6.95

Hoffman Stereo Remote Balance

For remote control balancing of 2 speakers complete with 25' of 3 wire cable. New\$1.95

MODULATION TRANSFORMER

Collins 20W, 200 to 5000 primary Z 6000 secondary Z 600097c ea.
2 for \$1.75

NAVY WEATHERPROOF OUTDOOR SPEAKER

12" diameter, heavy duty housing was used on shipboard for speaking to navy personnel, mfg. by Jensen. Brand new \$17.50 ea.

CRADLE TELEPHONES

WITH DIAL\$3.95
Without Dial2.95

WALKIE TALKIE SPARE PARTS KIT

Consists of 24 crystals, 5 antenna coils and 5 tank coils, all in wooden carrying case\$3.95 per kit

VHF FIELD STRENGTH METER

With 200 microamp meter and collapsible antenna, vernier dial tunes from 90 to 160 MC\$9.95

SOUND POWERED TELEPHONE HANDSETS

consists of 2 sound powered handsets, 200 feet of wire, light compact and new all for \$14.95 per pair

24 VOLT GENERATOR

10" long by 6" in diameter. Produces 28V DC at 25 amps\$7.95 ea.

VARIACS

3 Amp variac 125 volts 60 cycles, in good condition \$6.95 ea.
115 volts primary, 240 volts 10 amps secondary \$29.50
115 volts primary, 0-135 volts secondary at 15 amps \$29.50
110 volts, 10 amps, 400 cycle\$3.95

ONE OF KIND

TS-147D Test set. X band signal generator, like new cond. \$350.00 ea.
TS-323/UR Frequency meter 20 to 450 MC \$195.00 ea.
OS/8 pocket scope 3" portable\$97.50
TS 186/UP Frequency meter. 100 to 10,000 MC \$195.00 ea.

TS 175/U Frequency meter 85 to 1000 MC \$149.50

TS 174/U frequency meter 20 to 250 MC \$149.50

USM-32 precision compact scope 6"x8"x14" \$149.50

TS-148/UP Spectrum Analyzer\$195.00

GONSET COMMUNICATOR 111. With crystals Excellent condition\$135.00

ARMY SNOOPERSCOPIES in carrying case good condition\$35.00

AN/USM-24 Oscilloscope\$225.00

SPECIAL

ARC/T11 VHF Transmitter, covers 116 to 132 MC. Can be used on 2 meters with slight modification. 2 watt output. 4 1/2" x 6" x 4 1/2". Weighs 3 1/2 lbs. With tube\$19.95

SPECIAL

Sextants Late style, features automatic averaging readings. All you do is sight it. Automatic features gives you average reading of about 60 sights in 2 min. with carrying case\$8.95

Telephone Dial


Standard Phone dials ideal for use in any remote control relay circuits.\$1.25

Antenna Relay


BC-442 consists of switching relay, 0-10 RF indicator & 50 MMF vacuum capacitor new\$2.25

CRYSTALS

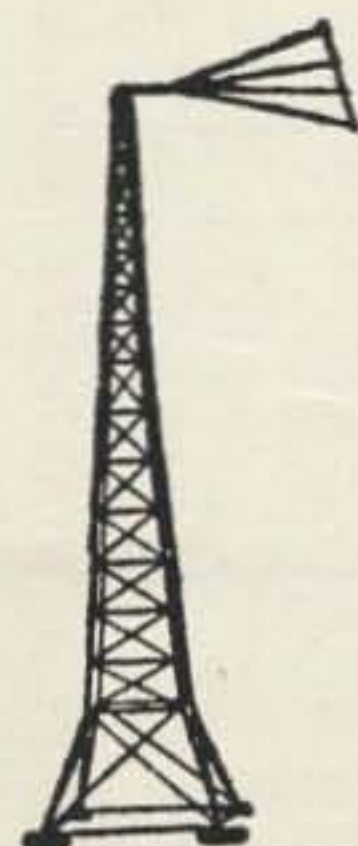100 KC mounted in metal sealed holder 1/2" spacing. New not surplus\$4.95 ea.
1000 KC metal sealed holder 1/2" space4.95
10,000 KC metal sealed holder 1/2" space2.95
200 KC metal sealed holder 1/2" space1.95
Ceramic crystal sockets for 1/2" spacing25c for above crystals




J. J. GLASS ELECTRONICS

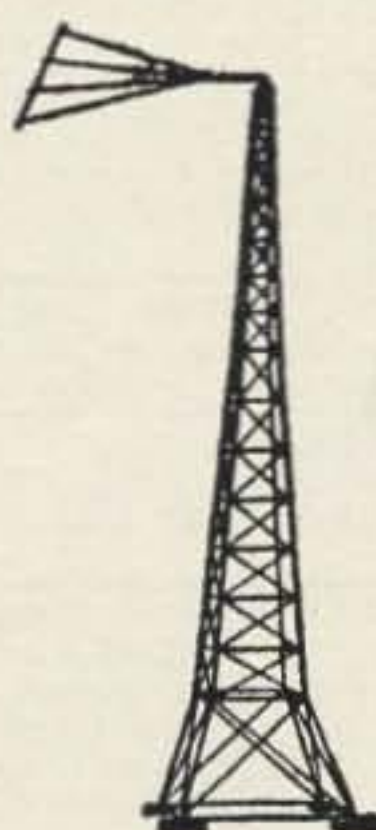

Terms:
FOB our warehouse, L.A.
Cal. 25% deposit with COD
order, Calif. buyers add
4% tax. Minimum order
\$5.00.

1624 SOUTH MAIN STREET
LOS ANGELES 15,
CALIFORNIA
Telephone: RI-91179

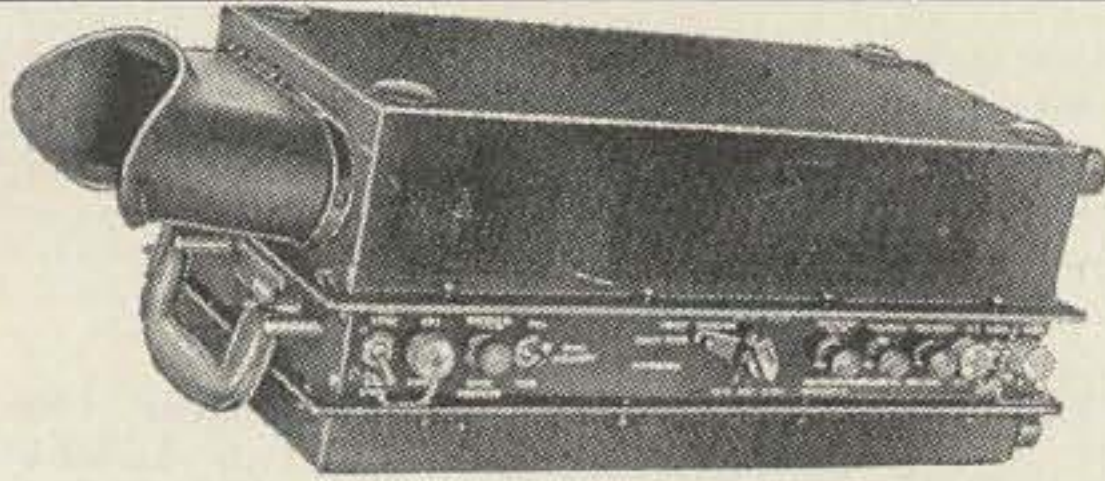GENERAL RADIO #1217A UNIT PULSER with #1203A pwr sply. Rise time .05 usec, fall .15 usec. 0.2 to 60,000 usec duration, calibrated. Top flat to 5%, overshoot 1/3rd; 2 1/2% of max. amplitude. **99.50**



\$850 TEST OSCILLOSCOPE FOR ONLY \$39.50

TEST SCOPE TS-34()/AP: Ready to use! Internal hard-tube sweeps 10-50,000/sec., plus triggered sweeps for pulses. Video 11 cy to 3 1/2 mc. Magnif. lens simulates appearance of a 5" picture. W/reprint of 17 Handbook pages. Checked OK.

DuMONT #304A most-popular DC-150 kc Test Scope. 5" flat-face CR tube. Vert. Defl. calibrated. **149.50**
W/book

DuMONT #264B Calibrator for vert. defl., any scope **14.95**

DuMONT #401A & 401AR (Rack Mt) is "the most advanced low-freq. scope ever made." DC-150 kc. Sensit. 10 mv/cm. Hard-tube sweep. Identical X, Y amplifiers **199.50**

DuMONT #321 Scope Camera, still or variable-speed 16 mm. W/fl. 5 lens, stand, 4 magazines, book, regular \$1395 **395.00**

TEKTRONIX #511A Test Scope 10 cy-10 mc video pass. Sweep calibr. in usec/cm. W/brand-new 5ABP1 flat-face tube installed, sens. 130 mv/cm. W/book **230.00**

TEKTRONIX #511AD is same plus Video Delay Line **275.00**

RCA WO-79A is 3" scope with meter in front panel for use at VTVM **79.50**

RCA WO-56A TEST SCOPE has 7" CR TUBE! DC to 500 kc, sweeps 3-30,000. With book **79.50**

SPENCER-KENNEDY LABS #202 Wide-Band Chain Amplifier, fixed gain 20 db. 1 kc to 210 mc; rise time .0026 usec. Z_i & Z_o both 200 ohms. V_o max. 4 v rms. W/regulated power supply **125.00**

POWER SUPPLY FOR ART-13 and other similar Transmitters. You make the 24 v dc 10 amps you need with your xfrmr & silicon rectifiers; plenty of room in the cabinet. This unit furnishes both HV's you need filtered. 1300 V at .35 A and 500 V at .425 A. Metered, in handsome cabinet 37" h, 21" wd, 15" dp., net wt 229 lbs, shpg wt 350 lbs. NEW! Gen. Elect., cost Navy \$1000.00! FOB Tacoma, Wn. with data, no plugs **79.50**

HANDY-DANDY ROTARY INVERTER puts out 115 v 3 ph 400 cy 250 VA. Input 28 v dc 22A. W/Mating plug, checked **9.95**

NAVY EAO POWER SUPPLY FOR TBX RECEIVER brand new with spares, easily modified to standard receiver-type (unregulated) supply **9.95**

MALLORY POWER SUPPLY NA-1500: V_i 230 v 3 ph 60 cy. V_o DC 12 v 100 A or 24 V 50 A. FOB Mobile, Ala. **79.50**

MAG-AMP REGULATED DC POWER SUPPLY. Perkins #28-30 WXM. V_i 95-130 v 1 ph 60 cy, V_o adjustable 24-32 V, 0-30 Amps. Max. ripple 1%. Static & Dynamic regulation 1/2%. 2 large 2% meters. Perkins price \$723.00. From us fob Los Angeles only **195.00**

SORENSEN #Q-28-0.5 Regulated DC Power Supply in cabinet, unregulated, all solid state. V_i 105-125 v. Output adjustable 18-36 v dc, 0-500 ma. holds to 1/4% for combined line & load changes. Regular \$200.00. From us FOB Los Angeles only **39.50**

SORENSEN B-NOBATRON #300B RANGER in cabinet w/2, meters for E & I. 0-300 VDC, 0-150 ma. Reg. 0.15% max. ripple 5 mv. Also two 6.3 vac 5A outputs. Regular \$310.00 but from us only **69.50**

DRESSEN-BARNES #3-150B in rack cabinet w/meter, 0-300 V dc regulated 0.15% line & load, 0-150 ma. plus negative 150 v dc bias, plus 6.3 v ac CT 6A **69.50**

DRESSEN-BARNES #3-1.5MB: Regul. Pwr sply, rack mtg, w/2 large meters for E & I. 0-300 vdc at 0-1500 ma plus 0 to -150 vdc plus 6.3vac ct, 10 amps **129.50**

DRESSEN-BARNES D3-300E. Regulated DC outputs 0-300 v at 0-150 ma plus 0-300 v at 0-300 ma plus 0 to -145 v at 5 ma plus unregulated Powerstat-controlled and metered 10 v ac up to 10 A. Small meter for AC, two large meters for DC E & I **99.50**

ELECTRONICS MEAS. CORP. #200B: Reg. DC supply in cabinet w/2 large meters, 0-300 vdc, 0-125 ma, 1% regul. line & load, 5 mv max. ripple **69.50**

ERA #TR300-1 ALL SOLID-STATE regulated DC supply in cabinet w/2 meters, adjustable V_o 165-300 vdc at 0-1000 ma. Line regul. .05% 105-125 v, load reg. 0.1% Regular \$595.00 **129.50**

UNIV. ELECTRONICS TWIN Regulated Supply. Switch puts two 0-400 V DC in series, in parallel, or either or both separately. Approx. 65 W from each output, self protecting. If load increases to max. on meters of 250 ma, tops at 250 v, won't rise above. At 100 ma, each supply tops at 410 v. 2 large meters. Also 2 separate 6.3 v ac 8 A **129.50**

POWER DESIGNS INC. #304M2 rack mtg regul. pwr sply 250-300 vdc, 0-500 ma plus two 6.3 vac 5A. Two Weston #741 1% meters for E & I **89.50**

HEWLETT-PACKARD "High Stability" #710B in cabinet, unregulated, adjustable V_o 100-360 v dc, 0-100 ma, also 6.3 vac 5A **37.50**

HEWLETT-PACKARD #715A Klystron Power Supply, Details on request **99.50**

HEWLETT-PACKARD #717A Klystron Power Supply, Details on request **129.50**

IMPEDANCE BRIDGE ZM-30/U (AN/URM-90) similar to ESI's #250DA (\$495). 3-unit concentric dial. Galvo for dc null, magic eye for ac null, int. osc. 1 kc. ext. to 10 kc. .0001 ohm to 11 meg ±15%; 0.1 uuf to 1100 uf ±5%; 0.1 uh to 1100 H ±1%. Q, .02-1000; D, .001 to 1.05; both ±5%. W/Handbook **250.00**

HEWLETT-PACKARD #803A VHF BRIDGE **295.00**

SHALLCROSS #617B %-LIMIT BRIDGE OHC by Shallcross **188.00**

L&N #5365 Power Cable Fault Bridge plus 6 amp Rheostat **275.00**

SIGNAL CORP I-49 (ZM-4()/U) Wheatstone Bridge approx. 0.1% accur., 0-10K X.001 to X100 w/Instructions **125.00**

Gen. Radio #783A AF POWER METER, regular \$410 **175.00**

WESTINGHOUSE PX-5 PRECISION DC VOLT-METER 1/2% FS 0-750 v **99.50**

L&N Students Pot. #7651 w/book, 0-1.5 v, steps of 1/2 mv, ±.04% **59.50**


L&N Kelvin-Varley Voltage Divider 0-350v, dc to 400 cy, use same as potent., ±.01%, reads 4 digits. W/instruct. to measure E & I **69.50**

METER TEST SET TS-682/GSM-1, you fix one meter **395.00**

Biddle-Evershed Bridge Megger 0-1000 megohms **150.00**

RCA #69-C (MI-7512-H) Noise & Distortion Meter **99.50**

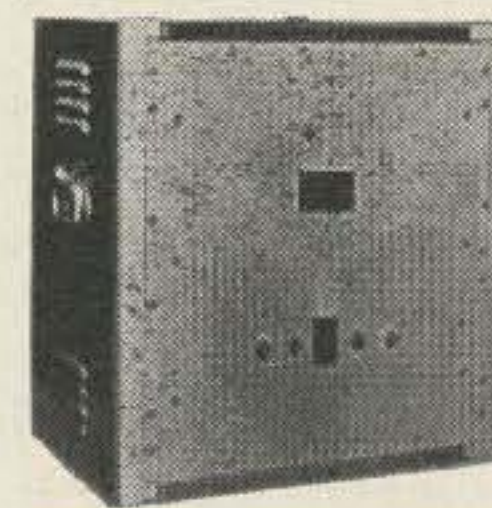Gen. Radio #1303-A Two-Signal Audio Generator for use as osc. 20-40,000 cy or measure IM by SMPTE or by CCIF methods or measure Harmonics. With Gen. Radio #736A Wave Analyzer (4 cy width) for use as Detector 20-16,000 cy. Total catalog value \$2,825. In grtd-OK condition both for **595.00**



STABILINE IE-20060: 3kva Line Volt. Regul. Adjust V_o 110-120 v 1 ph 50/60 cy. holds ±0.1% for line changes 95-130 v and/or load changes 0-26 A. Electronic, almost instant correct., no mvq parts, max. harm. 5%. On 19" rack panel 21" h, 14 1/2" dp, no cabinet. Mil Spec HS xfrms & chokes. Regular \$960, but from us, brand new, w/dwgs. & data 330# fob Utica, N. Y. only **279.50**
(If cabinet needed, add \$30.00.)

STABILINE S429 is Mil EM4106 6 kva electromech. line regul. 95-130 v 1 ph 45-65 cy. ZERO harmon. 0-52 A. Metered in cabinet, exc. used. OK grtd, fob Utica, N. Y. **279.50**

STABILINE EM type S345 2 kva made special for Litton Ind. as CN-203/MRN, same ckt. in slide-out drawer, brand new fob Utica, N. Y. W/dwg. **149.50**

SORENSEN 3000SH is Mil-Spec HS xfrmr/choke electronic regulator, 95-125 v in to 110-120 V_o ±0.1%. Max harm. 3%. In cabinet, factory overhauled & grtd, w/book, fob So. Norwalk, Conn. **279.50**

SORENSEN #1500 SPECIAL Line Voltage Regulator, all electronic, V_i 105-125 v 60 cy, V_o adjustable 110-120 v. holds to 0.3% for rated line input variations and for load variations 150-1500 VA. Max. harmonics 5%. FOB Los Ang. (factory overhauled) w/book **179.50**

SORENSEN #10,000S: Same specs as the #3000SH except 0-10 kva. Factory overhauled & grtd, w/book; fob So. Norwalk, Conn. **595.00**

Sorensen #500S: Same specs as above except 0-1/2 kva. Checked, grtd, fob Los Angeles **99.50**

SOLAVOLT #5106: Harmonic-corrected Sola Constant-Voltage Transformer 500 W in case w/contin.-adjust. auto-transformer for regul. 0-135 v ±1%. Unmetered model **49.50**

SOLA 190-25C V_i to 230 V_o ±1% fob Los Ang. **89.50**


G.E. Isolatin STEP-DOWN/STEP-UP xfrmr 120/240 v 1 ph 50/60 cy 7 1/2 kva fob Oakland **49.50**

PLENTY MORE: For example, on way in to us now is Hewlett-Packard 0-10 mc digital counter; not mentioned here is our large stock of Brush graphic recorders, Varian mv recorder, transistor tester, tube testers, tuning fork oscillators, VTVM's etc. Always BUYING! SO IF YOU HAVE SOMETHING TO SELL US, tell us about it and PUT A PRICE ON IT same as we did in this ad... we didn't ask YOU for offers! AND WRITE US ON YOUR SPECIFIC NEEDS!

R. E. GOODHEART CO., INC.

Box 1220-GC BEVERLY HILLS, CALIF. 90213
Phones: Area 213, office 272-5707, messages 275-5342.

**ALL-BAND SSB RECEIV-
ER BARGAIN:** R-45/
ARR-7 has 2 stages RF,
2 stages 455 kc IF,
separate Local Osc. w/VR
AF, S-Meter, Noise-Lim-
iter, Crystal & non-
crystal IF Pass in 6 pass
selections . . . and now
we add **PRODUCT DE-
TECTOR** in the empty
socket left by removal of
the reradiation suppressor
preceding the 1st RF. Goes on
when BFO is flipped on, works like a charm! **CONTINUOUS
TUNING 550 KC to 43 MC!** Voice, CW, MCW. With 120/
230 v. 50/60 cy power supply, ready to plug in and use.
HOT and SHARP! With book 90 lbs fob LA **199.50**

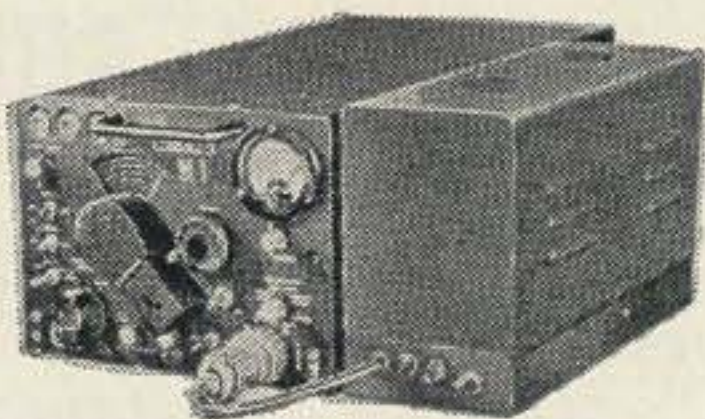

Same but without the SBB addition fob San Antonio **179.50**

TIME PAY PLAN: Any purchase totalling \$160.00 or more
send us only 10% for Down Payment!

NEW LOW PRICES ON TELETYPE! Model 14 Transmitter-
Distributor, with cover, synm motor, **37.50**
only

Mod. 15 w/keyboard, plus Mod. 14 Typing Reperforator,
plus Mod. 14 Transmitter-Distr., all in handy
operating console cabinet fob Los Ang. only **175.00**

Mod. 19 plus same additions in same Console **195.00**

TM11-352 on Mod. 15, \$5.00. TM 11-2222 on #14TD, \$5.00.
TM 11-2216 on Mod. 19, \$8.00. TM 11-2223 on #14 Typ-
ing Reperforator, \$8.00.

NEW LOW PRICE on latest-type **MINE DETECTOR:** AN/
PRS-3 has waterproof Search head, coils embedded in plastic,
drag under water or use above ground, find **PIRATE'S GOLD**
or **PLUMBER'S PIPES!** Exc. cond., with all parts & Hand-
book in Fiberglass Suitcase, 40 lbs, fob
Tacoma, Wn., only **19.95**

NEW LOW PRICE on ungraded **SILICON DIODES**, various
PIV's & Currents, some good, some bad, you grade them
with Instruction included. **2.95**
100 for only

LOW FREQUENCY LONG WAVES RCVRs: Superhet DZ-2,
15-70 and 100-1750 kc. You make power supply same as
in a Command Receiver (250 v & htr for 6 v tubes) **79.50**

RCA Shipboard VLF Superhet, 70-1500 kc cont. Exc. cond.
and works hot as a firecracker. Ready to go on
115 v 60 cy. No other information available. Only **69.50**

R-44/ARR-5 AM/FM superhet 27-140 mc. reradiation suppres-
sor removed & bypassed, 6AK5 substituted for acorn to
make it **HOT**, and 5.25 mc IF brought out to pin jack
on front panel case in double converting Look
same as picture at top of page. **179.50**

HALLICRAFTERS S-37 Receiver AM/FM w/6AK5
substitutions as above, 130-210 mc AM/FM **179.50**

455 KC PANADAPTOR BC-1031-C like new, with
book, fob Los Angeles only **99.50**

RBS RECEIVER 14-TUBE superhet 2-20 mc,
aligned, w/pwr sply, instructions, only **69.50**

BC-348-F Revr, checked OK operating, no power
supply. 1.5-18 mc. W/Schematic **69.50**

RT-18/ARC-1, 100-156 mc Revr-Transmitter in shock-mt
connection-making rack, 10-channel Autotune, w/schem. &
setup instructions which show all power voltages,
currents needed **39.50**

Add DIRECTION FINDER To Your Receiver



Navy DU-1 gives **TRUE BEARING** in
3 seconds! No 180 deg. ambiguity! Goes
ahead of your receiver; takes 200-250
v., 16 ma and heater voltage from your
receiver. 2 12SKY7's in tuned preamp
and phasing circuit, 200 to 1600 KC in
3 bands. Instructions tell how to modify
to get Marine Band if desired. Only 7
lbs. net wt. 11" loop, 4 1/2" azimuth
scale. **BRAND NEW**, with plugs,
mount, diagram, instruc-
tions **29.95**

NOISE & FIELD STRENGTH METER, STODDART
NMA-5A with I.F. and plug-in Tuner for
88-400 mc with book **199.50**

FM XMTR-RCVR base station, Farnsworth AN/FRC-6A, puts
50 W into antenna, 30-40 mc, Voice, 120 v 60
cy pwr sply, speaker, meters, etc. in rack cabinet **99.50**

AN/APR-4 RECEIVER SET w/Tuning Units TN-16 & 17,
38-300 mc, checked 100% OK, w/plug &
Handbook **149.50**

(Write for prices on AM/FM type and on other tuning
units, up to 4 kmc.)

R-111/APR-5 RCVR 1-3. kmc AM has 115 v 60 cy
pwr sply built in, exc. for SPECTRUM ANAL-
YSIS **79.50**

A Model goes to 6 kmc **99.50**

A Model in rack w/30 mc Panadapter RDP, also 115 v
60 cy, displays ± 5 mc, plus other material, useful also
for APR-4 Set above which also has 30 mc.
I.F. **199.50**

LM FREQUENCY METERS 125 kc-20 mc, with
Cal. bk, plug, xtl, instruct., gorgeous **57.50**

LM FREQUENCY METER same as above except with some-
what dog-eared calibration book, guaranteed
100% readable! Only **42.50**

TS-175/U FREQUENCY METER 85-1000 mc, crystal cali-
brated, wit serial-matched Cal. Bk. & Handbook,
exc. condition! **150.00**

MAKE POWER SUPPLY for LM's and/or TS-175 by modify-
ing brand new EAO 60 cy portable power supplies with
Instructions and Silicon Diodes we supply. **9.95**
47 lbs fob San Diego

GENERAL RADIO Type 620A **FREQUENCY ME-
TER**, 300 kc to 300 mc, .01%, crystal cali-
brated **99.50**

TS-186(*)/UP FREQUENCY METER, 0.1%, crystal calibrated,
100 mc to 10,000 mc! With calibration book,
crystal, waveguide-to-Coax Adapter, Handbook **199.50**

TS-69/AP WAVEMETER 350-1000 mc, w/Calib.
Charts, tune for max. reading on large Microameter **69.50**

TS-311A/AP Echo Box COMBINED WITH Crystal
Tester! 8730-8910 mc **49.50**

TS-501/UP Echo Box 6250-3900 mc **49.50**

TS-488/UP Echo Box w/Horn, 8990-9160 mc
 ± 0.5 mc **79.50**

**GENERAL RADIO WIDE-BAND BEAT-FREQUENCY OS-
CILLATOR** generates 50 cy to 5 mc in 2 accurately-calibrated
bands, put 10 v into open ckt constant $\pm 1\frac{1}{2}$ db.
Not Gen. Radio's \$750.00 but only **129.50**

BOONTON UNIVERTER 203B beats your VHF signal gen-
erator a 70 mc to provide 100 kc to 25 mc at
same Vc as you set at the VHF generator,
 ± 1 db **99.50**

NAVY VERSION OF GENERAL RADIO #605-B

LP Microvolter, 9 1/2 kc -30 mc
dial-calibrated $\pm 1\%$, 7 bands
& 30-50 mc graph-calibrated.
CW or mod. 1000 cy, 0-50%,
read on VTVM. Output cali-
brated 1/2 uV to 0.1 V at
lower plug & 1.0 V at upper
plug. Logging scale w/300
divisions & vernier knob w/
135 divisions provide super-
accurate resetability. Stabili-
ty is phenomenal. Holds a
zero beat with WWV for 12
hours with less than 100 cy
drift. Aligned, quart'd, ready
to use on 120 V, 60 cy, only **199.50**



TS-413/U SIGNAL GEN. 0.75-40 mc, 1%, xtl
calib., Vo calib. to 1.0 v. Certif. w/book. **279.50**

GEN. RADIO'S SUPER-DE-LUXE LOW-FREQUENCY
Standard Signal Generator #805-C. In the current Cat. R
it is almost identical, called D Model, at \$2250. In Cat. Q
it is C Model, \$1975. 16 kc-50 mc. Puts 2 v into 37 1/2
ohms; 1/2 reading into 50 ohms with simple
2-resistor pad. W/book, 100% grtd. **795.00**

BORG-WARNER (ROLLINS) Model 30-A 40.7-400 mc High-
Pwr Standard Signal Generator AM, PM, CW, puts up
to 10 volts into 50 ohms w/accurate attenuator; in High
position (CW only) puts out 10 watts at most frequencies.
With book. Current price is \$18,000! **EXCELLENT** for
RFI measurements, Antenna Pattern work, etc. **1295.00**
100% Grtd OK

PRECISION APP. CO. Series E-200-C Serviceman's
Signal Gen. 90 kc to 120 mc, apparently OK **39.50**

NAVY LX-2 is Wash. Inst. of Tech. version of Gen. Radio
Mod. 804B Standard Signal Generator, 7 1/2 to
330 mc. 100% grtd, w/schematic. **149.50**

MEASUREMENTS CORP. Mod. 80 Standard Signal Gen-
erator: 2 to 400 mc $\pm 1/2\%$, Vo calib., .1 uV
to .1 V. 100% grtd, w/book. **375.00**

NAVY LAE-2 BRAND NEW with serialized charts, graphs,
Handbook, puts out same uV as above but 520-1300 mc
 $\pm 1\%$, CW & PM w/provisions for external sine mod. AM
PM has variable pulse width and delay. With
all cor's **129.50**

50% DISCOUNT on Gen. Radio Standard Signal Generator
#1021A. 1/2 uv to 1 v into 50 ohms, ± 2 db, also direct read-
ing 0 to -126 dbm. AM 0-50%, 1 kc. Extremely low leakage.
Cabinet w/Pwr Unit 1021P1 & Osc. 1021P3,
40-250 mc. 100% grtd OK. W/book **397.50**

Same except w/Osc. 1021P2, 250-940 mc **397.50**

Cabinet w/pl & P3 PLUS EXTRA plug-in osc.
P2, covers 40-940 mc. 1/2 Cat. price is **635.00**

C-BAND: POLARAD MSG-3 Signal Gen. 4.5-8 kmc. -10 to
-125 dbm into 50 ohms. Similar to Hewlett-
Packard's \$2250 #618B **695.00**

WRITE FOR PRICES on TS-419/U, 900-2100 mc, and on
POLARAD MSG-34, 4-11 kmc.

KAY MEGASWEEP #111A checked 100% OK only **175.00**

X-BAND SPECTRUM ANALYZER TS-148/UP
w/Handbook and flexible Waveguide attachment **195.00**


Same in Shpg Case is AN/UPM-33A **245.00**

R. E. GOODHEART CO., INC.

Box 1220-GC BEVERLY HILLS, CALIF. 90213
Phones: Area 213, office 272-5707, messages 275-5342.

TELEMARINE FOR THE BEST IN SURPLUS!

WALKIE-TALKIE

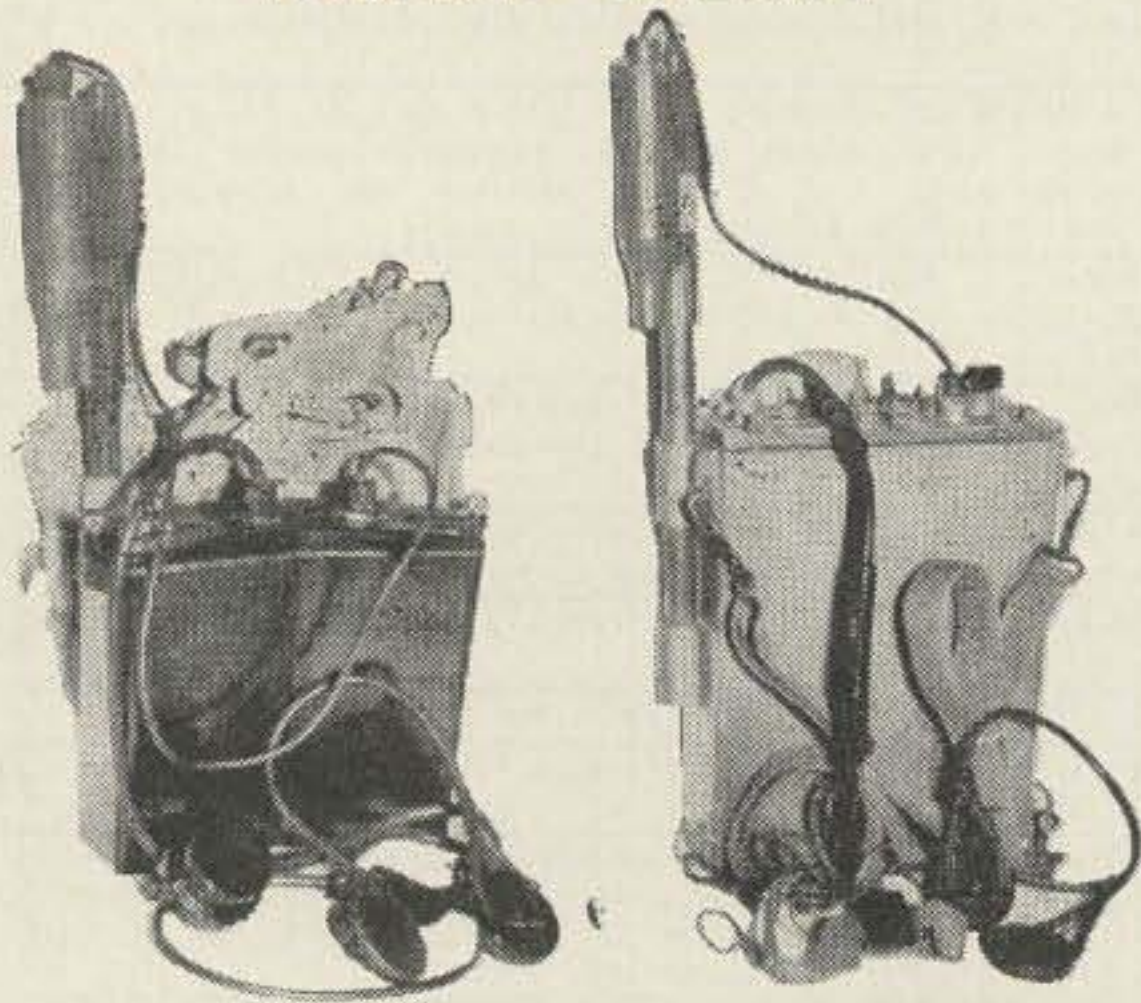

MODEL "MAB" is a Navy Walkie-Talkie which provides single-channel, crystal-controlled reception and transmission (AM) between 2.0 and 4.5 MC. Receiver uses miniature tubes in a superheterodyne circuit for maximum sensitivity and selectivity. Transmitter employs miniature tubes in a crystal-controlled oscillator (1T4), a 3S4 RF Power Amplifier which will deliver from 200 to 250 milliwatts RF power to the antenna (can be souped up), and a 3S4 Heising (plate) Modulator stage. 7 tubes total in trans-receiver. Unit is housed in a water-tight bakelite case, 7½"H. x 10"W. x 3-9/16"D. **RANGE 1 MILE OR BETTER**, depending on location and conditions. Requires 135 volts "B" and 1½ volts "A" batteries. Excellent for 75 meter Ham. CD, Fire Dep't, emergency marine, or conversion to other uses. Supplied Complete with all tubes, r'c'ing & x'mitting crystals (sorry, we cannot accept orders for a specified frequency. Crystals are FT-243 type, and can be easily changed), telescopic antenna with adjustable loading coil, headphones, microphone, and canvas carrying case with straps. In Almost-New condition, but not-tested at this price. Shpg. wt. per set 15 lbs. **EACH** as described, only \$12.95 **PER PAIR** 2 Complete Sets, as above \$24.50

MODEL DAV is a Navy Walkie-Talkie, same as above, but with Direction Finding Loop within so that receiver section may be used for D.F. or Homing on the crystal-controlled receiving frequency. Same transmitter as outlined above for Walkie-Talkie use with supplied adjustable telescopic antenna. Encased in watertight, sturdy plywood case, slightly larger than above. Shpg. wt. Complete with accessories as for MAB. 20 lbs. **EACH, AS NEW**—but not tested at this low price \$16.95

INSTRUCTION BOOK FOR MAB OR DAV only with purchase of units \$ 1.00
MINIATURE VIBRATOR PACK FOR MAB OR DAV, eliminates nuisance and expense of dry batteries. Operates from miniature 6 volt storage battery, not supplied, available from many surplus dealers. With Instruction Book. Shpg. wt. 5 lbs. **UNUSED. EACH** \$7.95

NEW, WALKY-TALKY (BC-611) CHASSIS




Here's the chance to build your own real compact, lightweight hand-held Walky-Talky! Designed to transmit and receive on one (crystal-controlled) frequency between 3.0 and 6.0 mc., any real Ham could revamp the coils for operation on higher frequency amateur phone bands. This will result in increased antenna power output and longer distance transmission. By building your own case for this chassis, with space for larger batteries and increased B voltage, further increased power and longer service from batteries will result. These chassis are NEW, unused, complete with telescoping antenna but less tubes, coils, or crystals. Tubes required: 1-1R5, 1-1S5, 1-1T4, and 2-3S4. 2 miniature plug-in coils required (sold separately), 1-Antenna, and 1-RF Tank. Battery voltages required (original) 1-1.5 volt "A" and 103.5 volts "B" battery, the latter may be increased to 135 or 167.5 volts to produce higher transmitter output. Supplied as specified with Schematic diagram. Shpg. wt. 6 lbs. **\$8.95**
EACH—Chassis only
PAIR OF COILS, for above, Ant. & RF Tank \$1.25

ACCESSORIES FOR ABOVE

CAST ALUMINUM HOUSING, case for Above Walky-Talky. Includes battery compartment. Push-to-Talk Switch with rubber weatherproof cover, top and bottom covers. All items separate for home assembly. **PRICE, as outlined \$17.75**
ALUMINUM HOUSING ONLY. Less Top & Bottom Covers or push-to-talk switch \$9.95
MICROPHONE OR RECEIVER ELEMENTS, with matching transformer and bakelite covering caps.
EITHER ELEMENT (New) \$5.50
TEST UNIT 1-135. Contains Microphone and Receiver elements. Volt-Milliammeter, and RF Pierce Oscillator circuit to thoroughly test above Walky-Talky. Parts can be used to help complete unit. Used-Excellent. Shpg. wt. 35 lbs. **PRICE. EACH** \$17.95

PUSH-TO-TALK SWITCH, and Fulcrum assembly for actuating trans-receive slide-switch on chassis. Also includes separate rubber cover for inclosing and weatherproofing switch. Shipped Postpaid (add 10c if insurance desired). **PER SET** \$1.95

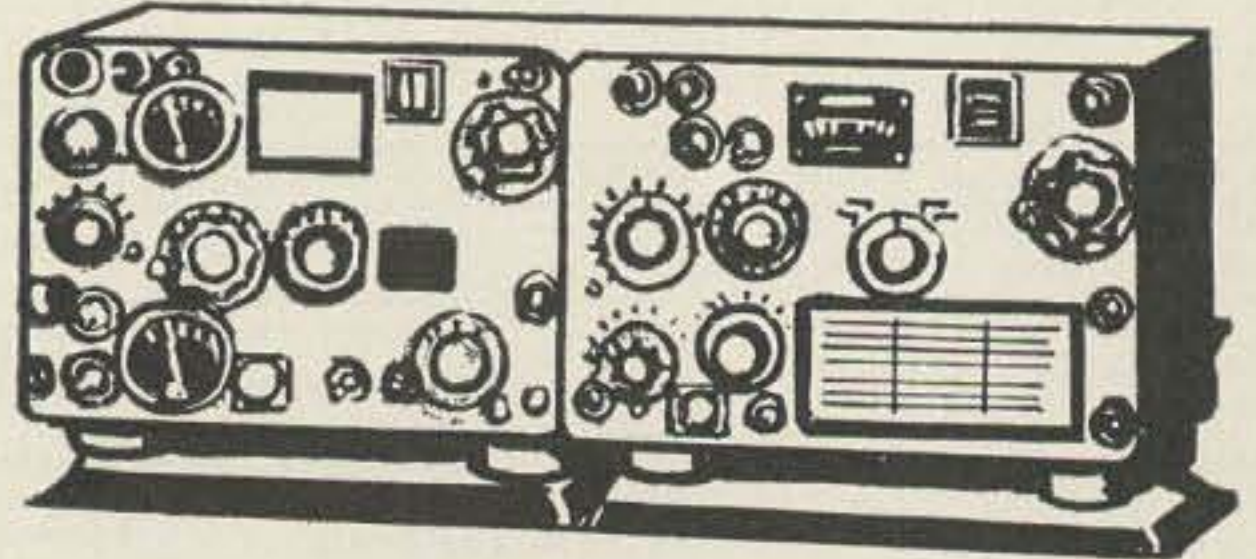SENSATIONAL BARGAIN!! TCS TRANSMITTERS, RECEIVERS, AND ACCESSORIES



TCS TRANSMITTER. Famous work-horse of the Navy, rugged, efficient reliable. Delivers 20 watts phone, 40 watts CW in 1500KC to 12.0 MC range. Incorporates VFO or 4-crystal controlled channels. Excellent for mobile or fixed station use. Complete with tubes, Used-Very Clean condition. Shpg. wt. 60 lbs. All Accessories extra.

EACH, not tested at this low price \$39.95
TCS RECEIVER, companion to above 1.5 to 12.0 MC in 3-bands. Continuous tuning of 4 fixed crystal controlled frequencies selection. Employs a stage of RF amplification and 2 stages of IF to provide good sensitivity and selectivity. Requires separate Power Supply. Excellent for Hams, CD, MARS, etc. Shpg. wt. 50 lbs. **USED—EXCELLENT** Condition.
PRICE EACH, not tested at this low price, with tubes \$49.95
TCS 12 VOLT DC POWER SUPPLY, to operate above units from 12 V. DC. Contains 2 Dynamotors, one for transmitter and one for receiver supply, complete filtering, starting relay, etc. **NEW UNITS**. Shpg. wt. 40 lbs. **PRICE EACH** \$17.95
TCS REMOTE CONTROL UNIT with built-in loudspeaker, volume control, microphone and phone jacks. Shpg. wt. 10 lbs. **NEW UNITS, EACH** \$9.95


As Above, but "Used—Very Good" \$6.95
Plug Connector for Remote Control \$1.50

TCS CONNECTOR CABLE. Transmitter or Receiver to Power Supply. Shielded. (Specify which). 3 foot length \$5.95; 11 foot length wt. 5 lbs. \$9.95.
TCS ANTENNA LOADING COIL, permits use of short, whip type antennas on lower frequencies. Shpg. wt. 8 lbs. "Used—Good." **EACH** \$6.95

30-40 MC DE-LUXE FM RECEIVER. Model R-237/VRC—2 Single-Channel, Double-Conversion Superhet, with features such as double limiter, squelch circuit, crystal-control of both 1st and 2nd Converter Oscillators, built-in 6 V DC Power Supply, etc. Dimensions 11½" x 10" x 15". Used—Excellent condition units, with tubes, 2nd conv. crystal; no control unit or loudspeaker, with schematic diagrams. **\$29.95**
Shpg. wt. 65 lbs. EACH

TRANSMITTER COMPANION TO ABOVE. Model T-193/VRC—2. Power Output 25 watts, Crystal-controlled single-channel unit with built-in 6 V DC Power Supply. Can be used for NB FM amateur transmissions, or may be applicable to Fire, Police, or other applications. Used—Excellent conditions units. With schematic. Shipping **\$19.95**
weight 65 lbs. EACH

25-30 W. SPEAKER UNIT

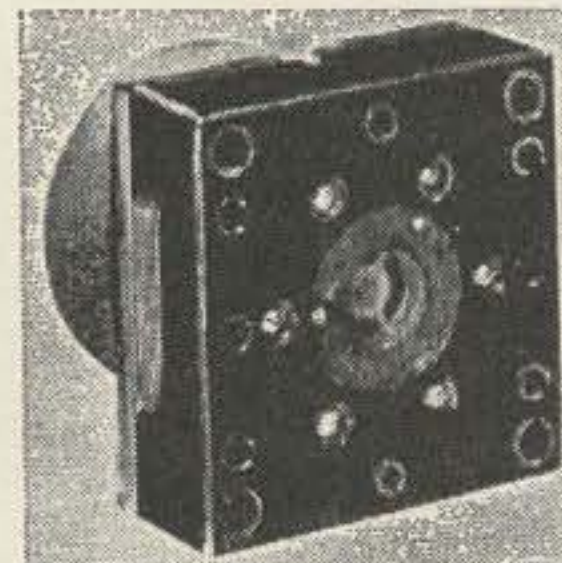


Western Electric Speaker units, D173246, for horn or baffleboard mtg. Shock and blast proof diaphragm, will handle up to 30 watts. Response to 12,000 cps, favoring high freq. Impedance 5.5 ohms. Dim: 4 3/16" x 4 3/16" x 2 9/16" deep. Throat opening—1½" dia. Alnico 5 slug. wt. approx. 3 lbs. Shpg. wt. 8 lbs. **SLASHED TO . EACH \$8.95**

MINIATURE STORAGE "A" & "B" BATTERIES. For Walkie-Talkies, Radio Portables, Radio-Controlled devices, Radio-Sondes, or equivalent meteorological devices. Supplied as a set of 3—"B" batteries of 36 volts each, and 1—"A" battery of 6 volts. Batteries dry-charged, less electrolyte and packed in a hermetically sealed vacuum metal container which prevents possibility of deterioration or loss of efficiency until opened and ready for use. Both "A" battery (BB-51) and "B" battery (BB-52) are ¾" deep x 1½" high x 3½" long, with 2 connection pins of ½" length protruding from each battery. Hypodermic needle required for acid—water filling 1280-1350 specific gravity. Full instructions supplied with each set of batteries for filling and charging. **NEW-UNUSED**, shipping weight 4 lbs. **PER SET** of 4 batteries as described. \$3.35

PLEASE!! DO NOT REQUEST CATALOGUES! MATERIAL LISTED IS "HERE TODAY, GONE TOMORROW," AND CATALOGUES WOULD BE USELESS.

— SUMMER CLEARANCE BARGAINS —

HAM OR CB VERTICAL BEAM BARGAIN!

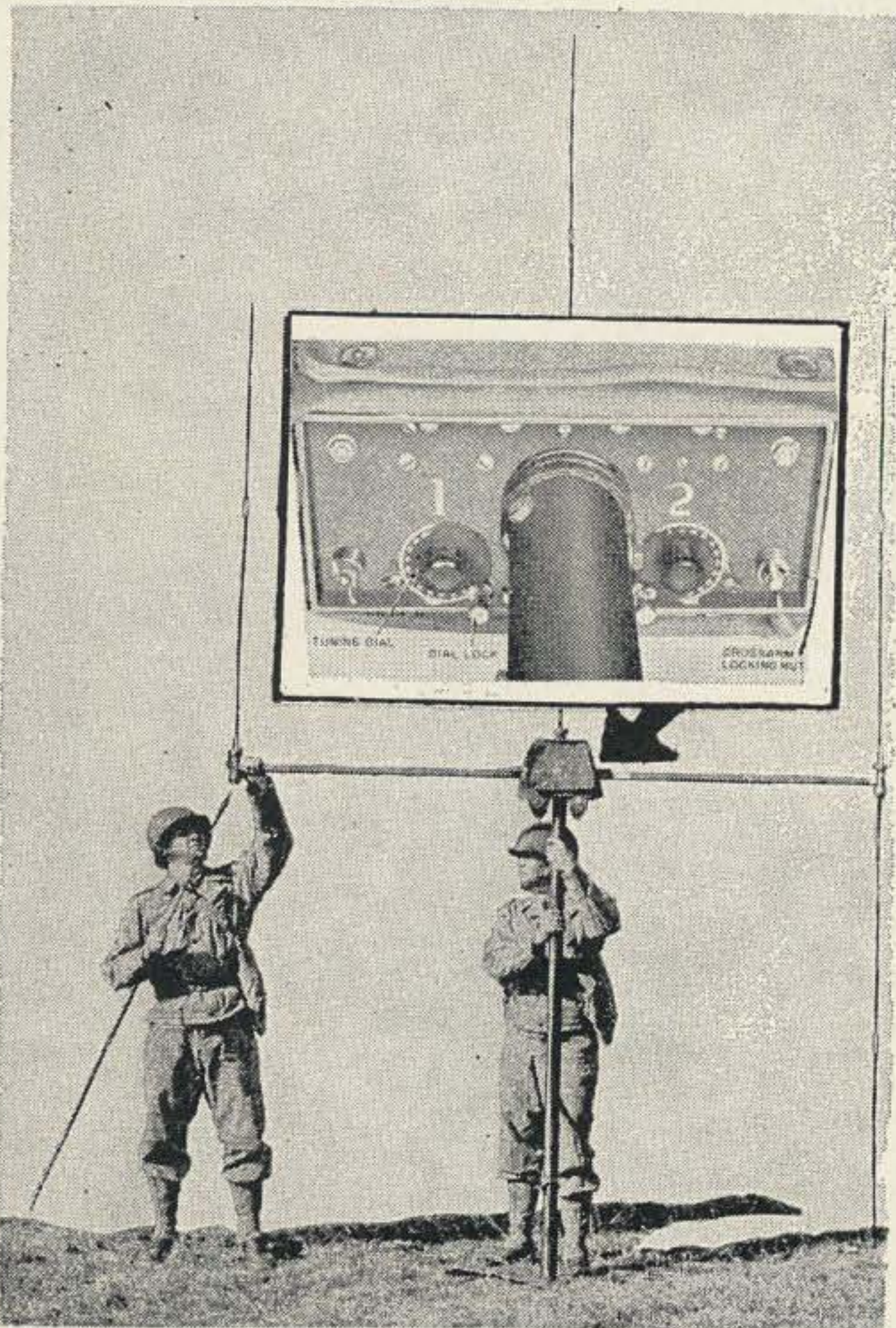

PRICE \$17.95

TELEMARINE discovered this outstanding 3-Element Adcock Type Beam Antenna in Army Surplus. It includes a vertical dipole and phase-load tuning box, which permits tuning and phasing in the radiator and director elements, and phasing out the reflector element so that an unusually high front-to-back ratio results along with exceptionally high forward gain. Plug-in inductors permits use of this antenna over a frequency range of 20 to 40.0 MC. Operates with 52 or 72 ohm transmission line. Sturdy, weather-resistant construction! Operates satisfactorily with CDR-AR-22 Beam Rotator, or equivalent. New-Unused, with Instruction Book which covers complete equipment for which antenna was intended, but provides full installation and tuning-up data. Net wt. of beam 39.5 lbs. Shpg. wt. 102 lbs. Supplied with 2 plug-in inductors to cover 25-30 MC, installed in phase-load box. **COILS, PER PAIR (2 required) for 20-22.5 MC; 22.5 to 25.0 MC; or 30-40 MC., specify freq. \$4.95**


MALLORY UIBRACK, TYPE 6369, 12.0V. DC INPUT, output 275 at 85ma., or 250V, at 100 ma. Uses Synchronous Vibrator, no tubes necessary. Vibrator plug polarized for positive or negative ground. Dim. 5½" deep, 2¾" wide, 6" high. "Used-good" tested condition. Shpg. wt. 8 lbs. **PRICE, EACH \$6.95**

COMMUNICATION ANTENNA BARGAINS!!

PREMAX TELESCOPIC VERTICAL ANTENNA, Chromed Monel Metal, 3 telescoping sections with watertight collet-type chucks to lock each section at desired length. Extends from 6 ft. 9 inches to a maximum of 19 ft. Excellent for Marine, Ham, CB, or Base short-wave operation. NEW-UNUSED units. Shpg. wt. 12 lbs. Originally price at over \$90.00. Our **PRICE, ONLY \$14.45**

30 MC MOTOROLA COAXIAL ANTENNA. Heavy duty, high-power construction. Easily modified by reducing length of upper whip section for higher frequencies, or increasing length by a few inches for CB application. Present length of top radiator 102". Equipped with female receptacle for PL-259 coax connector and 50 ohm line. Important mounting hardware included. UNUSED Units. Shpg. wt. 130 lbs. **PRICE, EACH \$14.95**

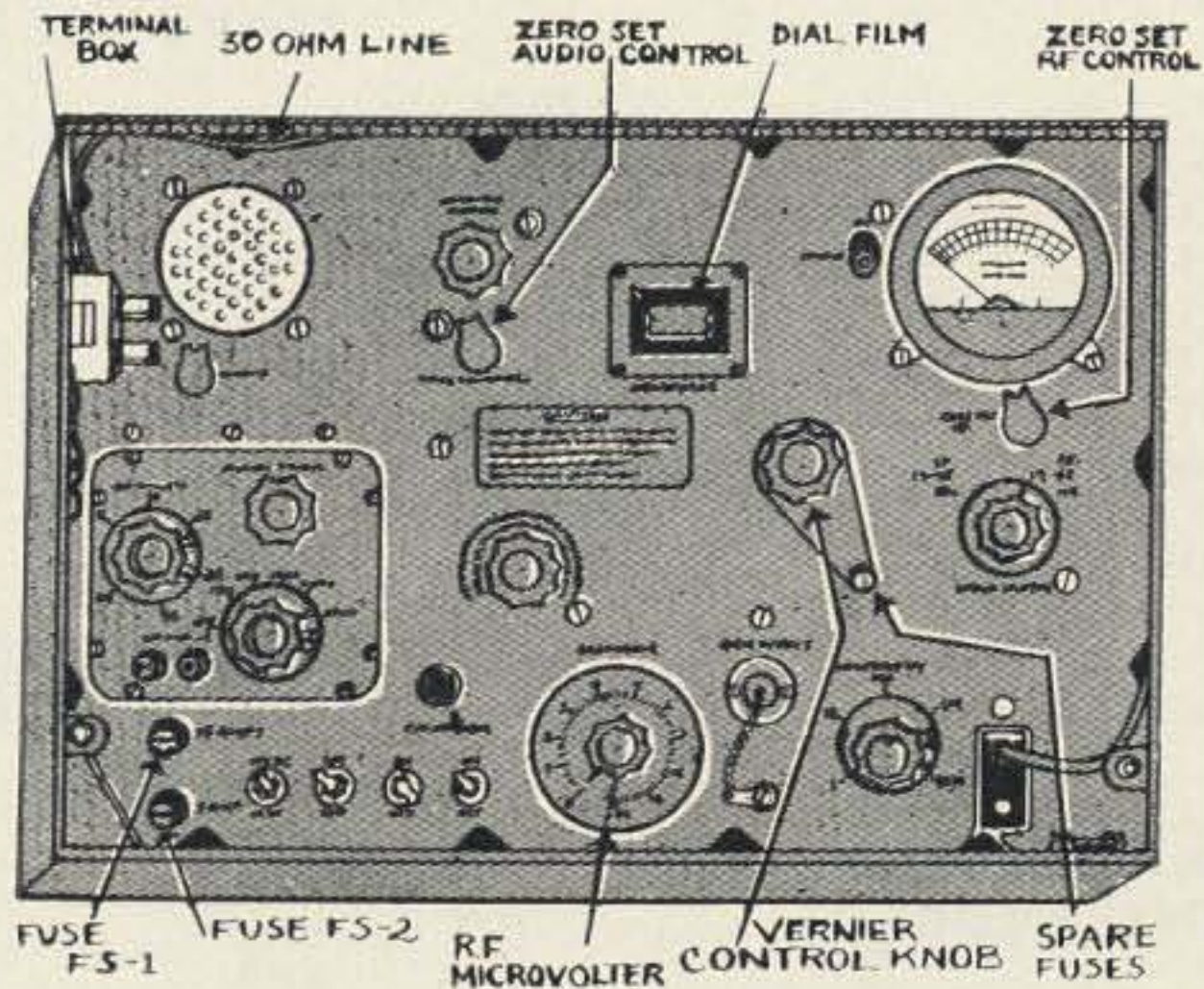HI-PRECISION FM SIGNAL Generator—Mobile Band



Model I-208, is a precision instrument worthy of the finest lab, mobile service and installation shop, or for production testing of mobile FM equipment. Previously, it was a scarce and expensive instrument, until we made a fortunate "buy" in a limited quantity. Freq. Range in 2 bands, 1.9 to 4.5 mc (for IF alignment and tests) and 19 to 45 mc. Freq. of output of signal is maintained with .03% of dial calibration over a temperature range from 0 to 60 degrees. Other outstanding features are: *Variable Frequency Deviation, 0-5 KC on 1.9 to 4.5 mc band, 0-50 KC each side of resting frequency on 19 to 45 mc band. *Calibrated Microvolter-Attenuator, adjustable up to 100,000 microvolts, developed at the termination of a 30-ohm line. Up to .84 volt available at high output terminals. *RF Vacuum Tube Voltmeter incorporated, 5 modulation frequencies provided by internal audio oscillator, 150, 400, 1,000, 2,500, and 5,000 cps. External modulation also provided for. *Operates from either 110 volts, 60 cycles AC, or 12 volts DC which is ideal for in the field work. *Crystal Calibrator, whose output is 1 mc and harmonics for checking and maintaining accuracy of signal generator. Each I-208 is supplied complete with tubes, calibrator crystal, 12V, DC Dynamotor and 110V. AC power supply are self-contained. Instruction Sheets and Schematic Diagram. Shpg. wt. is 145 lbs. (in wooden case). Available in NEW-Unused (tested) or Used-Excellent (not tested) condition. Act fast, our limited supply won't last long!
USED. EXCELLENT EACH \$69.95

FM MOBILE BARGAINS, FOR SPECIALISTS

GE MOBILE FM, 152-172 MC, Model ES-12A, 25 Watts Output. Combination Transmitter Receiver, with built-in rugged 12.0 Volt DC Power Supply. Double conversion Superhet Receiver circuit, ideal for FM monitoring of hi-band FM transmissions. Used-Excellent condition, with all tubes, but less accessories. Shpg. wt. 50 lbs. **PRICE, ONLY \$49.50**

COMCO FM, 152-172 MC MOBILE UNIT. Transmitter-Receiver and 6.0 Volt Power Supply in one housing. Single channel, crystal-controlled. Excellent for conversion to 110V. AC operation, for monitor application. Used-Very Good condition, with all tubes, but less accessories. Shpg. wt. 50 lbs. **PRICE, ONLY \$37.50**

PHILCO 30-40 MC FM MOBILE TRANSMITTER, Model PRT-336T. Single-channel, crystal-controlled, with built-in 6.0 Volt Dynamotor Power Supply output of which is 600 volts at 175 ma. Excellent for conversion for Ham, CB, Emergency application and others. Used-Good condition, with tubes, but less accessories. **BARGAIN PRICE, ONLY \$19.50**

PHILCO 30-40 MC FM RECEIVER, Model PRT-336. Single-channel crystal-controlled. Easily changed to 110V. AC operation, and will make an excellent, inexpensive monitor of Low-Band FM transmissions. Used-Good condition units, with tubes but less accessories. Shpg. wt. 35 lbs. **PRICE, ONLY \$22.50**

RCA MODEL CTR-1A, FM TRANSMITTER-RECEIVER, 152-174MC. Ideal Base Station FM Monitor on "high-band." Has self contained loudspeaker, 110V AC Power Supply, Squelch & Volume Controls. Transmitter has 15kc deviation which can be modified to meet new FCC requirements. Power Output 15 watts. Receiver is double-conversion superhet. Single-Channel operation, "Used-Clean" Condition, with tubes and schematic diagram. Shpg. wt. 60 lbs. Not tested at the low price of **EACH \$49.95**

All Above Material Subject to Prior Sale. 25%
 Minimum Deposit with all C.O.D.'s. Min. Order—\$5.00.

All Prices F.O.B. Our Address.
 WE BUY PRC, GRC, R-390 OR 391, SP-600, ETC. WE
 WILL PAY TOP DOLLARS FOR GOOD CONDITION EQPT.

— TELEMARINE — COMMUNICATIONS

142 West B'WAY, NEW YORK 13, N. Y.
 PHONE: COrtland 7-5444

SALE - NEW & RECONDITIONED

FREQUENCY METERS

BC-221	70.00
With modulation	95.00
TS-174/U	150.00
TS-173/U	135.00
TS-175/U	150.00
TS-323/UR	210.00
TS-186/U	250.00
AN/URM79	P.U.R.
FR-5/U	P.U.R.
AN/URM-81	P.U.R.
FR-6/U	

SIGNAL SOURCES & GENERATORS

TS-382/U	295.00
TS-47/APR	100.00
AN/URM-25	350.00
AN/URM-26	325.00
TS-497/URR	350.00
TS-419/U	700.00
TS-418/U	350.00
TS-155/U	175.00
TS-403A/U	900.00
SG-12/URM-48	P.U.R.

METERS

Ballentine 300	\$99.00
TS-375A/U	65.00
TS-297/U	P.U.R.
TS505D/U	195.00
TS-352/U	P.U.R.
AN/PRM-15	125.00

HEWLETT-PACKARD WAVE GUIDES

H-530A	\$140.00
X-880A	110.00
X-914A	52.00
X-421A	38.00
X-281A	14.00
X-920A	50.00
X-750C	35.00

HEWLETT-PACKARD TEST EQUIPMENT

200C	\$80.00
200D	115.00
200CD	150.00
202B	240.00
202D	165.00
205AG	325.00
330B	340.00
400C	135.00
400CR	135.00
410A	125.00
410R	175.00
415AR	125.00
415B	150.00
420A	30.00
430B	145.00
455A	24.00
458A	18.00
475B	120.00
500A	150.00
500A	75.00
520A	365.00
525A	130.00
526A	135.00
526B	110.00
526C	125.00
608B, C, D	P.U.R.
614	P.U.R.
616	P.U.R.
616A	900.00
623	P.U.R.
624	P.U.R.
624B	1350.00

SCOPES

Dumont 324	\$245.00
Dumont 304AR	195.00
Dumont 256D	95.00
TEKTRONIX	
535, 545 and 585	P.U.R.

TUBES

Klystrons	
2K25	\$ 6.00
2K28	18.00
2K29	P.U.R.
2K33	P.U.R.
2K33A	P.U.R.
2K41	P.U.R.
2K43	P.U.R.
2K50	P.U.R.
BL-800	42.50
X-12	P.U.R.
X-13	95.00
VA214	95.00
6043	40.00
Magnetrons	
725A	15.00
2J42	P.U.R.
2J42H	75.00
2J70	P.U.R.
QK-456	P.U.R.
Transmitting Tube	
2C39A	7.50
3CX100A5	10.00
4-65A	9.50
4-125A	20.00
4-250A	25.00
4-400A	P.U.R.
4-1000A	65.00
6360	3.25
5894	17.50
7212	4.95
4X150A	9.50
4X150G	21.00
4X250B	P.U.R.
4X250F	25.00
4CX300A	29.00
7580	34.00
100TH	P.U.R.
250TH	P.U.R.
807	1.00
807W	1.50

Many others in Stock—Call or Write for Quotation.

Just a sample listing. We have or we can get anything fast . . . and at low cost. Call collect for your needs. All equipment first class; new or reconditioned. Export shipping and documents. Every shipment fully tested and guaranteed.

WANTED TO BUY, TRADE


TURN YOUR SURPLUS GEAR INTO READY CASH. WE ARE READY TO BUY NOW ANY OF THE ITEMS LISTED BELOW. CALL COLLECT NOW CY-9-0300 AND GET OUR BID. WE PAY CASH-ON-THE-BARREL, AND PAY THE SHIPPING CHARGES ALSO. NAVY: TDH-4, or 231D Transmitters; "TED" Transmitters; AN/URR-35 Receivers; AN/URT-14 (complete); AN/SPS-10 Radar; AN/SPN-5, 7, 11, 18

Radar; Raytheon Pathfinder #1400, 1500 AN/GRC: 3, 4, 5, 6, 7, 8, 10, 19, 26, 46; RT-66, 67, 68, 70; AM-65/GR; PP-109/GR; PP-112/GR; R-108/GRC; R-109/GRC; R-110/GRC; SB-22/PT; AN/GRR-5; T-368/URT; BC-610E, F, G, H, I; RT-196/PRC-6; RT-174A/PRC-8; RT-175A/PRC-9; RT-176A/PRC-10; AN/GRC-27; AN/TRC-24
Commercial Aircraft Communications:
Collins 17L-4, 51X2, 51Y3, 17L7,

618T-2, 618T3, 618S1, 618-S3; Bendix RDR-1B Radar

Also looking for special purpose Tubes. TRANSMITTING, KLYSTRON, AND MAGNETRONS.

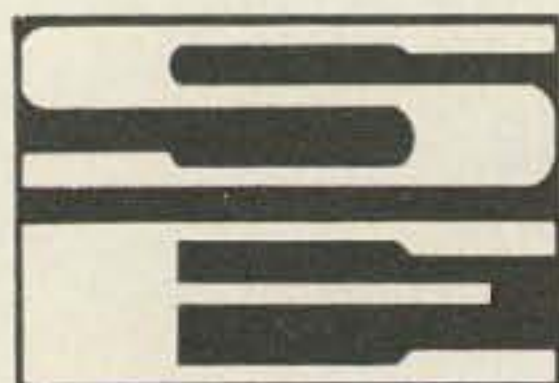AIRCRAFT: AN/ARC-44, AN/ARN-14, AN/ARN-59, AN/ARN-67, AN/APN-70, AN/APS-81, AN/ARC-34, AN/ARN-21, AN/ARC-52, AN/ARC-38, AN/ARC-58, AN/APN-22, AN/APR-4



SPACE ELECTRONICS

4178 PARK AVE., BX, N. Y.

CY-9-0300



ELI HEFFRON & SONS, INC.

Air Force & Navy Surplus Materials

Electronic Equipment & Parts

10 lbs. of Scotch Cast Epoxy Resin with
Catalyst, Type XR-5034 \$6.00

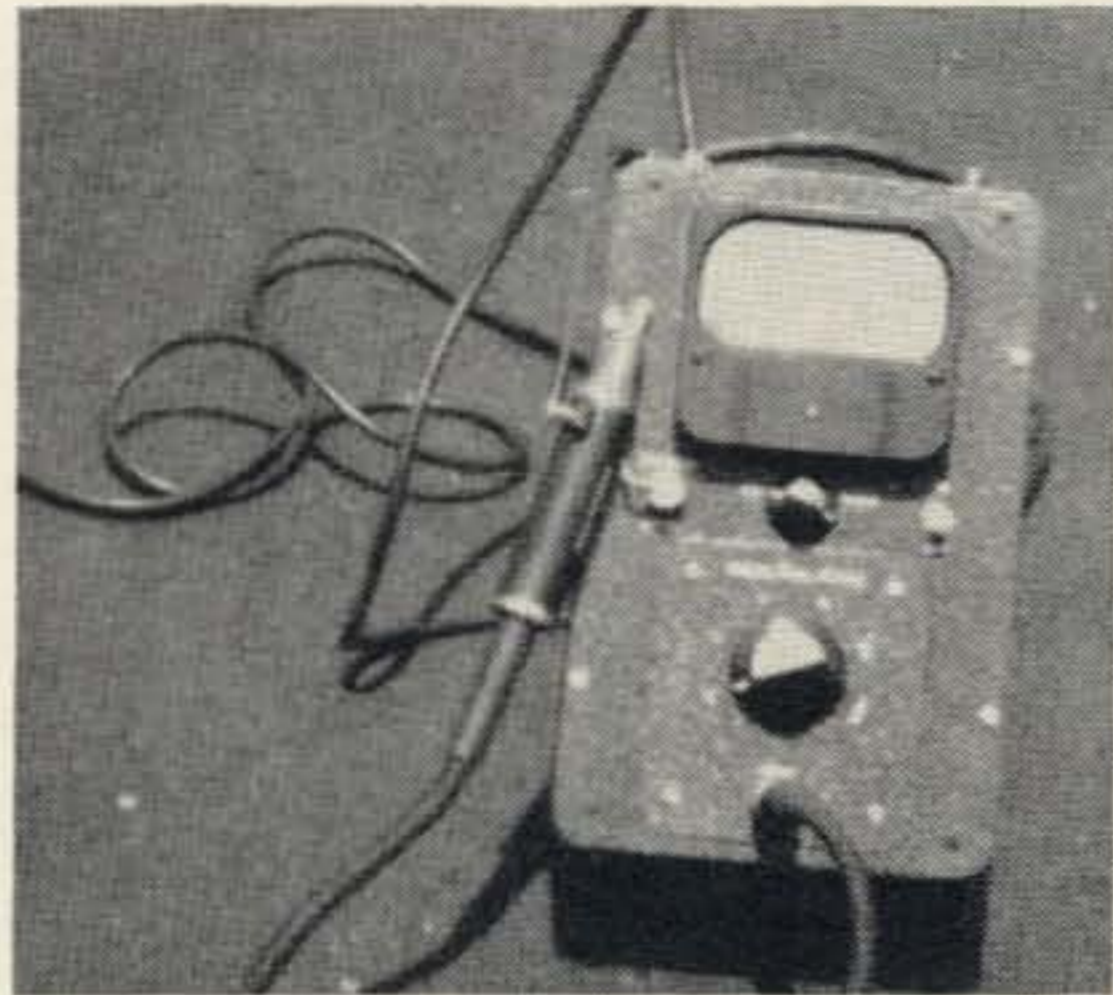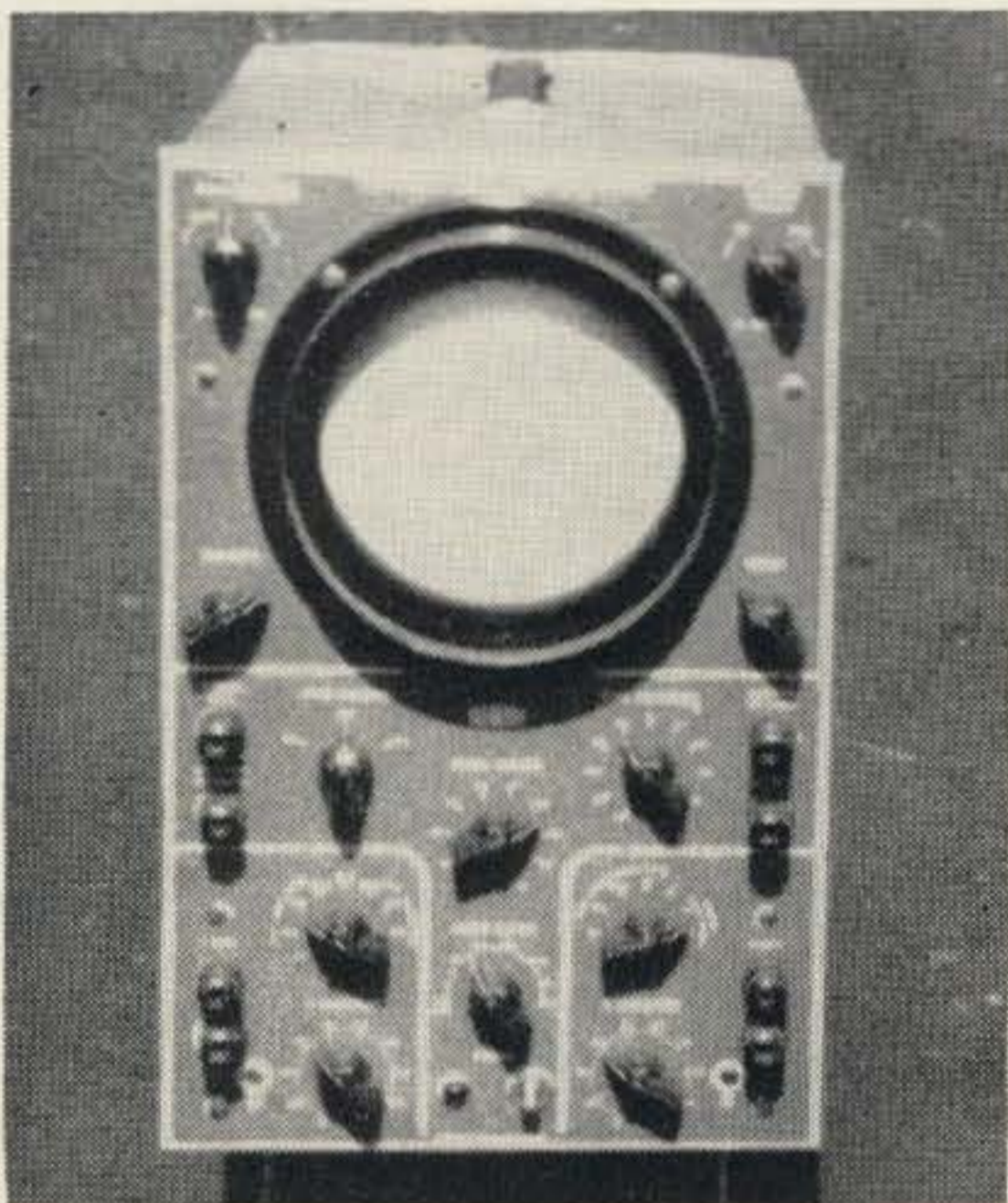Approximately 17,000 Ferrite memory
cores \$12.00



314 Ballantine Voltmeters \$125.00

1500 watt Sorensen militarized elec-
tronic regulators \$150.00

410B or 410BR Hewlett Packard volt-
meters \$125.00

Dumont 304H Scopes \$75.00

KM75 Opad 0-32 volts, 5 Amp supplies \$40.00

D6 Oregon 0-600 volt, 500mil
regulated supplies \$75.00



We have in stock a number of power supplies
to a 100 volts up to 15 Amps, these supplies
being regulated and/or transistorized.

NFB Electro power supply, 0-32 volts, 15 amps .. \$60.00

Sorry we do not issue catalogs or lists.

**321-329 ELM STREET
CAMBRIDGE 39, MASS**

EL 4-8572

LA 7-3406

Coaxial Cable & Connectors

RG8A with 2 PL259	
35 Feet	3.95
15 Feet	1.49
18 Inches	.98
Bulk (Foot)	.10



RG-54A/U. COAXIAL CABLE. 58 Ohms impedance. 1/4" diameter. 385 foot rolls. Shpg wt 25 lbs. **\$9.95**
Cat. No. 1006CC21

PL259	.39
SO239	.25
M359	.39
M258	.59
Double M	.98
"T"	1.75
UG175	.10
UG88	.39
UG290	.39

Tubes

2C39	6.00	5Y3	.40	715B	3.00
2C40	4.00	6AU6	.50	807	1.25
2C42	4.00	6CG8	.40	808	.75
2C43	4.00	6J4	1.25	813	8.75
2C44	.50	6J6	.40	815	1.95
2C46	3.00	6L6G	.98	832A	3.95
2E26	1.95	12AT7	.50	902PI	3.95
2K25	7.00	12AU7	.50	1625	.20
3AP1	1.75	12AX7	.50	5763	1.00
3C24	2.50	VR105	.50	5894	12.00
3C45	3.00	VR150	.50	6146	1.95
4X150A	8.75	371	2.00	6360	2.00
5C22	12.00	304TH	27.50	8012	1.00
5FP7	1.75	304TL	27.50	8020	2.50
5R4GY	1.00	416B	5.00	8025	1.00

Converter, Signal Data—This unit, just arrived, contains 25 tubes (12AU7, 12AT7, etc) 16 relays, (Plate plug in type) resistors, condensers, band pass filter, 5 unitized chassis etc

New equipment **\$19.95**

IP243/ALA Scope—contains 3 WPI, 5-5814, 2-5670, 2-6AQ5, 2-5654, 1-5725—400 cycles power supply with plenty space for conversion. **\$17.50**

BC221 Frequency Meter—Tip Top condition with original manual etc **\$69.50**

R28/ARC5 Receiver—100 to 150 mc **\$14.95**

Top Hat Rectifiers—600 PIV 200 ma **\$3.39**

Selenium Rectifiers 28v 1 amp. F.W. **\$7.79**

MN26C Receiver 150 to 1500 kc Some damage—mostly External **\$4.95**

H58U—Head set—Navy Hi. Imp. **\$3.95**

Panel Meters

0-9	"S" Hammarlund Super Pro.	Spec.	\$2.95
0-20	Microamps DC	3 1/2" Rd.	5.95
0-500	"	2 1/2" Rd. Triplet	3.95
0-1	MA DC	3 1/2" Rd. Multiscale	3.95
0-1.2	"	2 1/2" Rd. G.E.	1.95
0-3	"	2 1/2" Rd. Marion	1.95
0-5	"	3 1/2" Rd. "	4.95
0-100	"	2 1/2" Rd. Triplet	2.95
0-1	Amp. DC	2 1/2" Rd. Weston	2.95
0-100	R.F. M.A.	2 1/2" Rd. G.E.	1.95
0-5	R.F. Amp.	2 1/2" Rd. G.E.	1.95

This is a partial Listing—many others in stock. Send Addressed Envelope for Complete Listing.


Crystals

100 KC—Holder	1 3/16 x 1 5/8 x 2 1/8	2.95
100 KC—	" " " " 1" Diam. x 2"	3.95
200 KC—	" " " " Octal	2.50
400 KC—	" " " " FT 241.	1.50
500 KC—	" " " " FT 241.	2.50
1000 KC—	" " " " Octal (for Freq. Meters)	3.95
1000 KC—	" " " " HC6 (Midgets).	2.95
10000 KC—	" " " " CR1.	2.95
50 Assorted Miscl. Crystals.	FT 243, FT 241, CR1. Etc.	7.50

Send Addressed Envelope for Complete

TEST-SCOPE FOUNDATION with Conversion

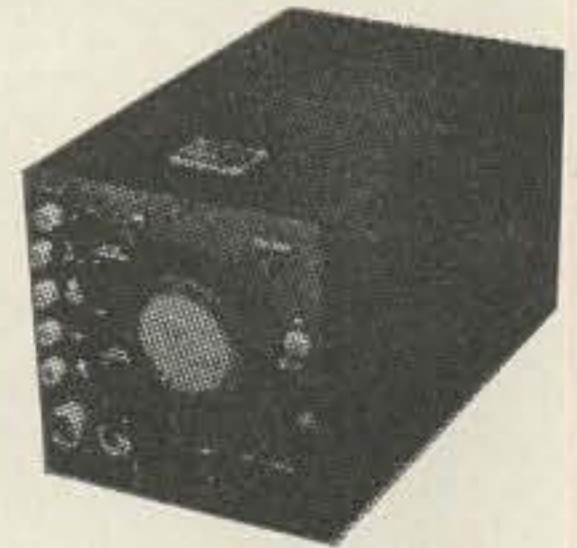BC-929 is a compact radar display unit with 3BP1, 2-6SN7GT, 6C8G, 6X5GT, 2X2, 2-6H6GT; high-voltage divider from -1600 V; intensity, focus, and positioning controls; plus a DPDT motor-driven switch you can use for many automatic-switching functions outside of an oscilloscope.



BC-929 has been the TTY enthusiast's favorite foundation for a converter with cross-line scope presentation, and also the Amateur's favorite Modulation-Monitor foundation.

It is small (only 8.75" X 9" X 16") and light (only 22.5 lbs.). Ask for and get with your order the **original** schematic with parts values and Circuit explanations, **plus** a conversion instruction and **converted** schematic with parts values. Excel. Cond. With all tubes. Shpg wt 30 lbs. **\$12.95**
Cat. 2306SC3. Only

Command Receiver

BC453 (R23ARC5) 190 to 550 KC	\$12.95
BC458 (T21) Transmitter 5.3 to 7 MC	4.95
R4ARR2 Receiver 234 to 258 MC Easily	
Converted to many frequencies	4.95
TN-1 —Receiver Tuning head 38 to 90 MC	12.95
RTTY—SSB—Phone Patch Transformer by Lionel	.95
RTTY —#255 Polar Relay	2.95
TN174 —Antenna Tuner contains 244mmfd Jenings Variable etc.	1.95
Power Supply —vibrator—6VDC to 300V @ 90MA Complete with Battery Cables, Switch etc.	2.95
Beam Filter —with cord, PL55 plug, jacks, Sw. etc.	1.95
85KC IF Transformer	1.25
RF-Ant—etc. Receiver Sub assembly 190-550KC	.75

 **Arrow SALES, CHICAGO, INC.**
ELECTRONIC DISTRIBUTORS

2534 SOUTH MICHIGAN AVENUE

CHICAGO 16, ILLINOIS

CALUMET 5-4750

METERS

Westinghouse, 2 1/2" rd*	Westinghouse, 3 1/2" rd*
0-1 ma dc \$4.50	0-20 ma dc \$5.50
0-30 ma dc 4.00	0-50 ma dc 5.50
0-50 ma dc 4.00	0-100 ma dc 5.50
0-200 ma dc 4.00	0-150 ma dc 5.50
0-300 ma dc 4.00	0-250 ma dc 5.50
0-100 mma dc 6.50	0-500 ma dc 5.50
100-0-100 mma dc 4.50	0-500 v dc 5.50
0-50 a dc w/shunt 6.50	0-2.5 kv dc 5.50
0-1000 a dc w/shunt 9.50	0-10 mil. v dc 7.50
0-30 a ac 5.50	Westinghouse, 4 1/2" rd*
0-100 vac rect type 5.50	3-6 kv dc 8.50
Westinghouse, 4" sq.sw.bd.	* square cases 50c extra
0-10 adc, 270° scale 22.50	Westinghouse, 5 1/2" rd
Weston	0-300 aac sw.bd. 24.50
3" sq 0-200 mma dc 9.50	0-4000 amps dc 24.50
2" rd* 30-0-30 adc 3.50	Roller-Smith
Aircraft, 0-30 vdc 7.50	Type sa switchboard
Aircraft, 0-150 vdc 7.50	200 aac f.s. 7.50

Meter Multiplier Resistors

IRC high-voltage, ferrule type, MFB255 2.5 meg 5.00
Weston, type 2, 20 meg 45.00
Wire wound, 1 meg, 2 1/2 meg, etc.75

Relays

6vdc dpdt; 24 ohm coil 5a sil. cont., P&B type SP11D 3.50
12vdc dpst no; 30a 110vac, Leach 6104 4.50
12vdc spdt; 96 ohm coil 8A sil. cont., P&B type MR5D 1.25
12vdc dpdt; 65 ohm coil 10A sil. cont. Advance 964B 2.00
24vdc 3pdt; 160 ohm coil 10A cont. Allied POX-12 3.75
24vdc 4 pst no; 250 ohm coil 12A sil. cont. Leach 1274 3.00
24vdc 3pdt; 10a contacts, Leach 9031-SS. hs. wrap term. 1.50
24vdc 40dt; 3a contacts Allied SKHX-12a. hs. hook term. 1.25
115vdc dpdt; 10k ohm coil 12a sil. cont., Leach type 1257 3.00
Pl. dpst nc; 5k ohm coil, 15 ma., Leach 1073BF 1.75
Pl. dpdt; 5k ohm coil, adj. cont., Leach 1037 2.50
115vac spst nc; dbl brk, 30a sil. cont., S-D type 84XXH 2.95

Relays

115 vac spdt; 10a cont. Allied BNAX-1 5.50
Overcurrent; Adj. .04 - .16 adc, reset coil 115 vac
Westinghouse type MN 6.50
Time delay pneumatic; Agastat NF-15; 24vdc coil
adjust 0.5 sec. to 9 min., delayed make, inst. brk.
two circuit contacts 5.50
Power, Arrow-Hart type RA 115 v 60cyc coil, 3pst
no 25a, dbl brk contacts 15.50
Cramer motor driven time delay, operates on 115 v
60 cyc. 10 a contacts. Set at 120 sec. adj 0-120
seconds 7.50
Edison type 501 thermal delay. 115v heater, 45 sec
delay n.o. contacts, plugs into octal socket 1.35

Capacitors

Sangamo
Type A mica transmitting, 250 w.v.d.c., 5000 v.d.c.
test. CM60B103J, 0.01 mfd. 5% 1.00
Type F1 mica transmitting, .0002mfd. 3000wv. 2.4
amps at 3mc. 1.2a. at 1 mc. CM65B201J 1.00
Type G3, transmitting mica, .004mfd. 15kv 32.50
Silver mica, 1500 mmf., CM30E152J20

Cernell-Dullier

Medium power mica, .001 mfd. 6000v 10 amps at 3mc. 5.00
Transm. mica, CM95F242J, .0024mfd, 30kv, 20a at
3000kc 99.50
Vertical mtg clamps for 1 3/8" d. cylinder caps05
Oil, screw base, both term. insulated from case, 10%
tol. CP41B1FF205K, 2mfd. 600v75
Electrolytic threaded neck, 50 mfd, 400 vdc,
CE41C5000Q, 50 mfd 400 v60

General Electric

Oil filled, 2 mfd. 10,000 v., CP70D1FS205K 32.50
--

Capacitors

Westinghouse type FP; 1 mfd. 10kv oil 17.50
Oil, 120mfd, 3000vdc, 5 1/4x13 1/2x15 1/2 over. term. 38.50
Micas, transmitting, 1200 wvdc - \$.35, 2500 wvdc85
Jennings type "U" vacuum var. 15kv. 50-250 mmfd 44.50
Johnson, type "M", miniature variable
Single section, 160-102/5M11-1.5 to 5 mmfd50
Single section, 20M11, 21-2.7 mmf95
Single section, 160-104.9M11-1.8 to 8.7 mmfd55
Butterfly, 160-205/5MB11-1.8 to 8.7 mmfd 1.10
Butterfly, 160-208/9MB11-2.2 to 8.0 mmfd 1.20
Butterfly, 11M11, 10.8-2.7 mmf 1.30
Differential; 160-303/5MA11-1.5 to 5mmfd 1.10
Hammerlund, variable
Screwdriver adj. MAPC-50, 50-3.2 mmf60
Screwdriver adj. MAPC-100, 100-4.5 mmf75
Screwdriver adj. with lock, APC-50-C, 50-3.9 mmf75
1000v. rms test, rotor stops, MC-20-S, 20-5.5 mmf 1.00
1750v. rms test, rotor stops, MC-50-MX-5d-10.5 mmf 1.50

Sprague, electrolytic

Threaded neck, 30mfd, 450vdc, CE41E200B, 30mfd 450v.50
Plug-in type, 4% H, 2000mfd, 15vdc, CE51A202E50

Centralab

Ceramic Trimmer, N650 temp. coeff, 822-BN, 45-7mmf45
JV-900 series switch sec. sp, 2-17 pos. non-shorting 2.00
Erie CV11 series ceramicon trimmer, N650 temp. coeff.
CV11D450 45-7 mmf55

Mallory, electrolytic

TS-13815 4000mfd 50v 1.85
TS-12984 2500mfd 100v 1.75
TS-13985 1300mfd 150v 1.60


10-71864 2200mfd 150v 1.95
TS-13812 150mfd 400v 2.00
Ohmite power tap switches
SP11pos. 10a contacts, 111-11 2.50
Contacts 50a, 412-3, SP3pos 6.50
Contacts 50a, 412-9 SP9pos. 7.00
Johnson tube sockets
Super jumbo 4 pin wafer for 8008, 122-244-200 1.10
Vhp septar for 826, 832, etc. 122-101-200 1.30
Giant 7 pin wafer, for 813, 4e27, 122-237-20070
Cinch Shield-base 7 & 9 pin miniature tube sockets
TS102C01 ceramic, 7 pin20
TS103C01 ceramic, 9 pin20
Transformers
Isolation, type R-76, 115-115v, 1200vs, cord recept. UTC 24.50
S-46 plate, 1000-750-750-1000v at 300 ma UTC 14.50
S-14, output, pri 2.5k/4k/7k/10k, sec 500/15/8/2.10w 2.50
Type CG filament. pri 105, 115, 210, 220, 230v, UTC
sec. 5vct at 25a. ins. for 5kv working, 11kv test UTC. 8.50
Choke: filter; 2 hys. at 2 amps. 12.5kv test UTC 22.50
Herm. sealed, power, 650vct, 6.3 & 5v. 2a; 6.3v 4a,
3-9/16x1-1/16x3-7/8 h. PMS-70A Chi-Tran 7.30
Herm. sealed filter choke, 8hy, 300made, 60 ohm dc res.
3500vrms test. 4.57x4.12x5.32h. rh8300 hCi-Tran 7.47
Plate*, 115-230/60/1 pri. 1100vac. ct. 212ma. sec.
Chi-Tran 3.85
Filament*, 115-230/60/1 pri. 5 vac. ct. 6a sec. Chi-Tran 2.25
Filament*, 115-230/60/1 pri 16.6 v. 1.25a; & 12.6 vac.
3.5 Chi-Tran 2.50
Choke*, filter, 4hy. 300ma 2500tv. 30-ohm res. 3.85
*above units basic power supply for TCS equipment and
any other low power transmitter and receiver.
Low voltage, 31/21/35/36.7v 6 amp sec. 117/60/1, pri
4 1/4x4 1/4x5 h. 6D3706 Thermador 8.50
Filament, pri. 117v-60cyc. sec. 2.5v ct at 10a sec.
insul. for 5000 v rms test. 6D-2515 Thermador 2.75
Plate, 1460-0-1460 vac 500 ma, 115v/60/1 pri.
6 1/2x7x7", 45 lbs. shipping weight Kenyon 21.50
150w step up/step down/isolation. 115/230v or
115/115v. herm. sealed. 3.75x4.25x6"h. Freed 7.95
SCR-522 modulation, 22000 ohms ct to 5500 ohms. 5w.
mil. rating. should be good for 10-15w. 7-54426 2.25
Triad, hs-23 audio int st. pri 15k, 1:2.7 turn ratio. 4.50
20-20,000 cps. HS-23
General Electric 200 amp. choke. .00025hy., dc res.
0.0032 ohms. 87G715 22.75
Choke: filter; 2 hys. at 2 amps., 12.5kv test 22.50
Moloney. Line transf. TF-5B: 1.5 kva; 480, 240, 120 to
264, 240, 216, 132, 120, or 108, in weatherproof case,
suitable for outdoor mounting 35.00
Superior Electric type 20 three phase variable. wve con-
ected for 230v 60 cyc. 0-230 or 0-270v. 3 amps out.
20L3Y 39.50
Deluxe metal cabinet std. 19" width, 12 1/4" panel space,
gray crackle finish, Bud No. Cr-1742-G 11.50
Dynamotors, 12vdc output 500 vdc at 250 ma 8.75
Dynamotors, 6vdc, output 600vdc at 175ma 6.75
Contactor, 12vdc for 12v dynamotor 1.35
Carter Genemotor, 11v. in at 13a 500vdc out at 200
ma. 7000 rpm. 520 BSM 11.50
Leland rotary inverter, input 27.5 at 60a. output 115vac
at 750va 3ph. 400 cyc pf or 0.9, and 26v at 50va 1ph
400 cyc pf of 0.4 continuous duty. Operating speed of
6000 rpm. 94-32270-A 29.50
General Electric silicon rectifier assembly. 3ph full-wave.
max. working ratings for resistive or inductive load.
Line to line ac input; 210vrms. dc output: 283v at 106
amps. 4JA6211CF1AB1 50.00
E. F. Johnson steatite cone 3" insulator s/hardware50
Broadband conical antenna for 300-3300mc. type N con-
ductor, AT49A/APR-4 5.50
Variable capacity type wave trap. Tunes 80-300mc. type
n input and output connectors. F-19/UPR 2.50
Airtron waveguide clamps, for use with "x" band guide.
Provides quick connect-disconnect; ideal for test equip-
ment, 42470 1.50
Airtron 1 foot flexible x band waveguide, cover flanges,
CG-179A/U 1'-0" 3.50
BNC type coax connectors, teflon insul. UG-88c/U plug.
UG-1094/U receptacle60
BNC type coaxial connector for RG-59, 62, etc.
Teflon insul. mfg'd by Aviel. UG-260B/U plug75
BNC type coaxial bulkhead feed-thru connector by IPC,
UG-492A/U 1.25
Cannon coax adapter. Type N female to type BNC male.
UG-260B/U plug75
N Type coaxial straight adaptor, Amphenol. UG-29/U. 2.00
Coaxial cable assembly: 50 ohm; RG-9b/U cable with
type N UG21b/U connectors. 6' long. CG-92/U 2.00
PL-259 coax connectors, made by Gold-Line 5 for \$2.00
Coax connectors, PL-258, connects 2 PL-259 plugs
together 3 for \$1.50
Heineman 15A 120vac 60 cyc circuit breaker
spst; curve 3. AM1510M6 2.25 ea.
Waldon planetary drive. Two speed with 5:1 and
1:1 ratios. 599 1.25 ea.
Waldom 4" dia. direct drive dial. Calibrated 0-100 on
180 deg. 292 w/vernier 1.60 ea.
Harry Davies skirted instrument knob, brass insert,
3" dia. 410930 ea.
General radio 1 15/16" dia knob. KNSP-850 ea.
TCS cable, trans. \$3.50, rec. \$3.00, remote \$4.50,
or set \$10.00
Mounting FT-154 for BC-348 revr 2.59 ea.

HIWAY CO. 1147 VENICE BLVD. LOS ANGELES, CALIF. 90015


All items F.O.B. Los Angeles. Orders over \$30.00 deduct 20% excess shipping. Money will be refunded.

Satisfaction guaranteed.

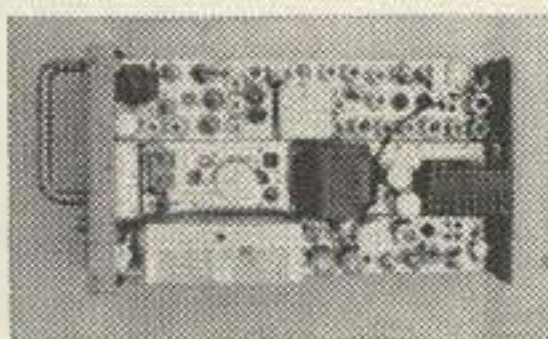Our extensive stock of Motorola Wide Band F. M. equipment includes the models illustrated, plus many other F.M. items. Representative prices are as follows:




FMTR-41V
10W RF

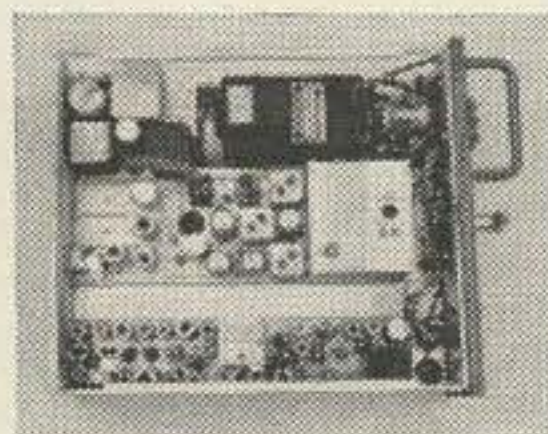


FMTR-80D
30W RF

FMTR-140D
60W RF

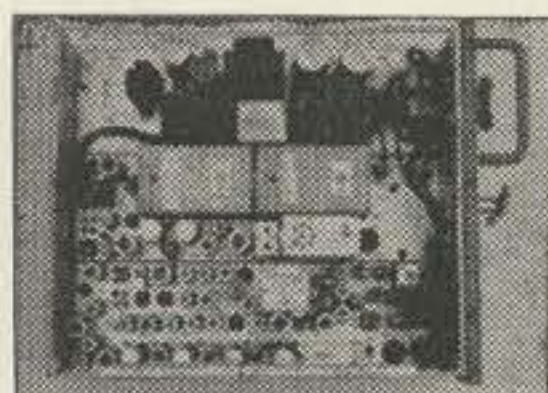

MOTOROLA T44A
18WRF 450MC

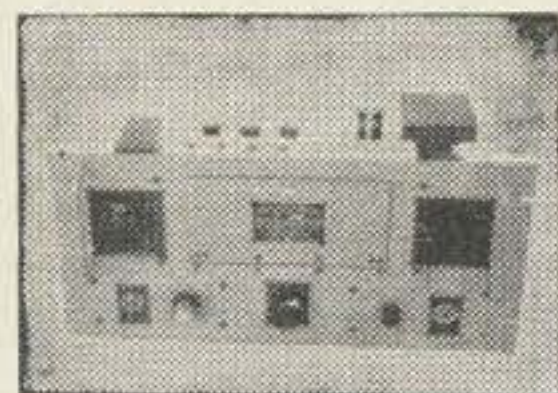

TT-63/FGC

MODEL	VOLTS	WATTS	FREQUENCY RANGE	CONDITION	PRICE
FMTRU-41V (1C)	6V	10W	150MC	Dirty but complete	\$29.95
FMTR-80D	12V	30W	30-40MC	Sensicon Receiver & Transmitter, clean with Dynamotor	39.95
FMTR-80D	12V	30W	40-50MC	Clean with Dynamotor	44.95
FMTR-80D	6V	30W	30-40MC	"	34.95
FMTR-80D	6V	30W	40-50MC	"	39.95
FMTRU-80D	6V	30W	150MC	Clean, With Sensicon or unchannel receiver	44.95
FMTRU-80D	12V	30W	150MC	Clean, With Sensicon or unchannel receiver	52.95
FMTR-140D	6V	60W	30-40MC	Clean with Dynamotor	32.95
FMTR-140D	6V	60W	40-50MC	"	39.95
FMTRU-5V	6V	10W	150MC	Clean with case	25.95
FMTRU-5V	12V	10W	150MC	"	29.95
FMTRU-40V	6V	10W	150MC	These units are dispatcher transmitters with Sensicon A receivers. The units are exceptionally clean.	35.95

No accessories or cables available.

Cases for above with order; 15" case \$2.50, 10" case \$4.00

Above units are complete drawers less case, including receiver, power supply, and transmitter.

ODDS & ENDS

MOTOROLA 10W	30-50 MC	Transmitter strip with tpbes	2.95
MOTOROLA 30W	30-50 MC	Transmitter strip with tubes	5.95
MOTOROLA 10W	150 MC	Transmitter strip with tubes	3.95

General Radio Primary Frequency Standard Model 1100A, Syncrometer 1103A, Crystal 1101A, and Multivibrator—P.S.1102A. In operating condition (1 x 10⁰—stability) **690.00**

TT-/63A/FGC Regenerator, Repeater Set, capable of receiving teletype writer signals in audio or direct current form having up to 45% distortion and regenerating the signal to have less than 5% distortion. With Diagram. **34.95**

WRITE FOR OUR LATEST FLYER WHICH LISTS OUR CURRENT STOCK SPECIALS

F M SURPLUS SALES CO.

100 Tremont Street, Roxbury 20, Massachusetts

CRAZY


INCREDIBLE

IMPOSSIBLE

FANTASTIC

Hit The BULLS EYE

**with our warehouse
CLEARANCE SALE**

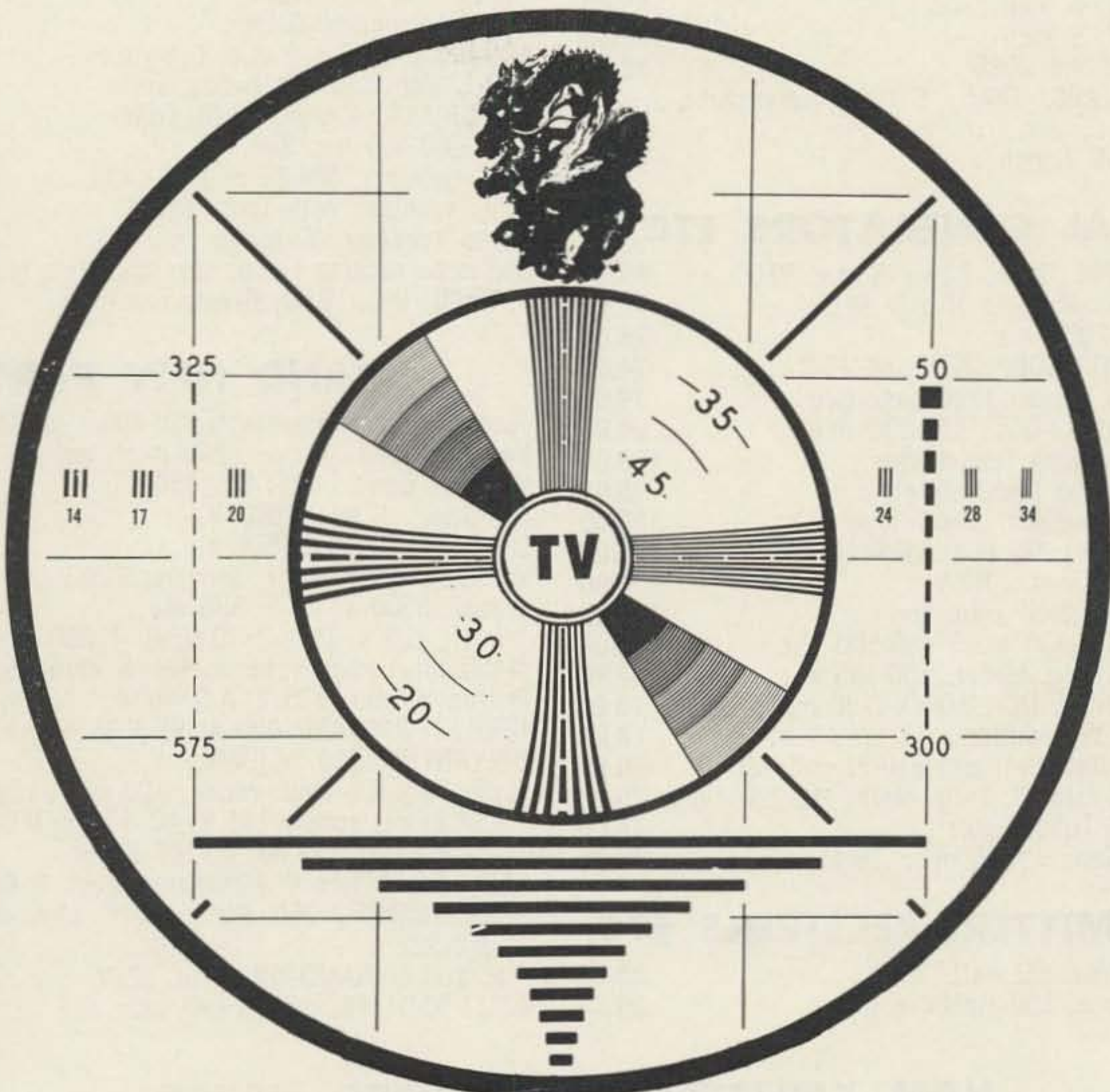

F 1.9-48 mm
LENS
7 Element-
color
Leica/
Cannon
Leica/Cannon
Thread
\$19.95
Adaptor to
Adaptor
to
"C"
Mount
\$3.50

NEW
GRADE "A"
1" VIDICON
TUBES
Type 7038 H
\$99.50

**WE MUST HAVE ROOM TO WORK !!!
∴ THOUSANDS OF GOODIES MUST GO-GO-GO
CAMERA KIT BUILDERS**

COMPLETE TV Camera Cabinet, Punched Chassis and Lens Mount—Only \$17.95 WITH INSTRUCTIONS

Type 1698 TEST MONOTRON TUBE—ONLY \$7.95
With FREE Instructions

(Special Price on these items ends Sept. 1, 1964)

FREE New Warehouse Clearance
Flyer 964 M2—available May 1

DENSON ELECTRONICS
"Your One COMPLETE source of CCTV-ATV Equipment"
Rockville, Conn.

Surplus Clearance Sale

TEST EQUIP.

FREQ. METER, B.C. 221, with Orig. Calib. Book	\$55.00
FREQ. METER, Navy LM, with Orig. Calib. Book	50.00
FREQ. METER, B.C. 221, with Book & 115 V. Supply	59.00
FREQ. METER, Navy LM, with Orig. Calib. book, NEW	65.00

SCOPES

TEKTRONIX 511A with Delay line	175.00
USM-38, 5 inch	95.00
OS-8E/U, 3 inch, NEW	95.00
DUMONT 304-H, 5 inch	95.00
DUMONT 241, 5 inch	65.00
DUMONT 303, 5 inch	125.00
DUMONT 208 and 208B	50.00
BROWNING LABS, ON-5, 5" Oscillasynchroscope	75.00
PRECISE 300-C 7 inch	95.00

SIGNAL GENERATORS ETC.

GENERAL RADIO 700-A, 50 cy.-5 m.c. BFO.	95.00
General Radio P522-A, 50-100 M.C.	95.00
L A D, 2700-2900 m.c.	29.00
MEASUREMENTS CORP. 78-B and 79-B	24.00
DUMONT 215, Linear time base Gen.	49.00
OAP Wavemeter—Osc., 150-230 m.c.	24.00
G. R. 740, Capacity test bridge	125.00
G. R. 759, Sound Level Meter	75.00
G. R. 561-D, Vacuum tube bridge	95.00
URM-25D, 10 k.c.-50 m.c. NEW	295.00
URM-26B, 5-405 m.c. NEW	250.00
URM-26, used, good condition	150.00
RCA 710A, 370-445 m.c., 450-500 m.c.	29.00
B. C. 338-A, Freq. Meter, 100-155 m.c.	24.00
CLOUGH-BREngle OCA, 100 k.c.-30 m.c.	19.00
B. C. 906-D, Wavemeter	14.00
G. R. 619-E, Het. Det. and 619-PI coil set	50.00
Bendix S-29B/FMQ-1, Freq. Meter, 10-220 c.p.s.	75.00
PRECISE 116, Tube Tester	49.00
1-208, Sig. Gen., 1.9-45 m.c., 19-45 m.c.	49.00

TRANSMITTERS-RECEIVERS ETC.

ATD, 2-15.8 m.c. 50 watt	35.00
TBS, 60-80 m.c. 100 watts, 6 mtr.	24.00

ARC-4, 2 mtr, T. R.	19.00
B29-Mark II, with 12 v. supply	29.00
MAW-1, 2 Mtr T. R.	29.00
B. C. 611 or B. C. 721, Handy-Talky	29.00
TBY, 2840 m.c. T. R.	18.00
Teletype receiver, 12 tubes, 115 v.a.c.	9.00
NATIONAL HRO, Military, with 3 coil sets	65.00
B. C. 620-A, FM., T. R. 20-27.9 m.c.	15.00
APT-5, Hi Freq. Xmitter	18.00
TCS, T. R. and 12 V. P.S.	49.00
RAL, 300 kc-23 m.c.	29.00
RAK, 15-600 k.c.	35.00
RBS or RBM, 2-20 m.c.	39.00
B.C. 348 or B.C. 342 Receivers	49.00
WICOX F-3, Receiver	24.00
TBS, Receiver 60-80 m.c.	19.00
ARB-Rec., 195 k.c.-9 m.c. 115 v.a.c.	24.00
APR-1, Rec. and one tuning unit	49.00
RCA-CRU-1A, 450 m.c. F.M. NEW	39.00
RDZ, 200-400 k.c. Rec.	29.00
D. F. receiver, MN-26 or B. C. 433	9.00
D. F. receiver with loop, DAE-1	24.00
RU-16 receiver, 6 tubes	6.00
QJB echo ranging Equip. new in crates, receiver	19.00, Osc.-19.00, Driver amplifier 24.00

BRAND NEW PARTS

Jennings Vacuum variable, 10-400 mmf 10 k.v.	\$39.00
Variable Cond., 4 Sec., 240 mmf/sec	3.95
Variable Cond., 425/425/850	12.00
Oil Cond. 4 MFD-4000 V.	8.00
Oil Cond. 10 MFD-1500 V.	2.95
Var. Tuning Inductor, Johnson 226-1	24.00
Transf. 6300 V. C. T. 500 ma	18.00
Transf. 220 V. Pri., 2770 V. C. T.-680 ma	9.00
4-400 air cooled tube socket & chimney, NEW	9.00
Rotron Blower, 115 V. A.C. NEW	7.50
HEWLETT-PACKARD 400 A, V.T.V.M.	49.00
BALLANTINE 300, V.T.V.M.	59.00
G. R. #60, 7.5 amp. variac, 400 cy., 115v. NEW	8.00
RA-87 Power supply 115 V. AC.-115 V. D.C.	10.00
TG-34-A Keyer \$24.00, TG-10F Keyer	24.00
LEECE-NEVILLE, 6 V. Alternator, Rest. & REG.	20.00
MOD. TRANSF., 250 Watt audio, Multi-match, UTC-S22	18.00
P.E. 103 DYNAMOTOR, 6 or 12 V.	12.00
GF-11 XMITTER, with 3 coil sets	9.00

HAM XMITTERS & RECEIVERS

Guaranteed
good condition

NATIONAL 303	\$275.00	VIKING RANGER	125.00
NATIONAL N.C.-190	129.00	VIKING II	135.00
NATIONAL-NC-125	75.00	VIKING CHALLENGER	75.00
HALLICRAFTERS-SX-99	75.00	VIKING MOBILE	59.00
HALLICRAFTERS-S-107	59.00	ELMAC AF-67	85.00
HALLICRAFTERS-S-108	95.00	GLOBE CHIEF DELUXE	45.00
HAMMARLUND H.Q. 129	120.00	EICO 720	65.00
HEATH HR-10	69.00	LETTINE 240	45.00
LAFAYETTE HE-10	59.00	GLOBE CHIEF 90	45.00

All Prices F.O.B. Hempstead, 25% with C.O.D. orders. Avoid delay send sufficient postage—excess will be returned.

ALGERADIO ELECTRONICS CO.

PHONE IV-9-0808
37 GREENWICH ST.
HEMPSTEAD, N.Y.

ELECTRONIC SURPLUS BARGAINS

SAVE UP TO 90%

RCA 6032 IMAGE-CONVERTER TUBE

Combined with suitable optical systems, this 3-electrode tube permits viewing of scene with infrared radiation. Scene to be viewed is imaged by optical objective upon semi-transparent photocathode. Spectral resp., S-1; good response up to about 1200A. Max. rating, absolute, grid #2, 20,000VDC or peak AC, grid #1, 2700VDC. **\$9.95 ppd.**



NT-6 WILLARD 6-VOLT STORAGE BATTERY
Rated 2.4 amp. hr. Approx. dimensions: 3 1/2" l. x 1 3/4" w. x 2 1/8" h. Weight: 1 lb. 3 oz. (plastic case) Dry-charged. **\$2.50**


POTTER & BRUMFIELD RELAY
#SM5LS SPDT
8000 ohm 11/16" dia. x 1 11/16" long. Approx. weight 1 oz. Hermetically sealed. Standard 7-pin miniature base. **\$2.00**



MINOR SWITCH
10-position, 3-pole with stopper coil and reset coil 6-12 volts D.C. off-normal non-bridging wiper approx. dimensions: 4" long x 4 1/2" high x 1 3/8" wide. weight: 1 lb. **\$9.95**



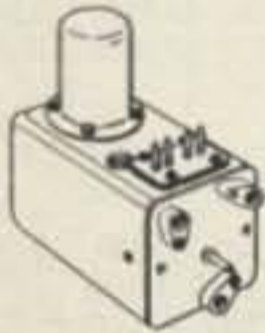
COLLINS PERMABILITY TUNER-OSCILLATOR
2 to 3 mc, 250 volt plate, 12.6 volt filament. Model 70E-2. New packaged. **PRICE\$12.50 each**



RT-82/APX6 TRANSPONDER
Good used condition less tubes. **\$9.95**


OIL CAPACITORS
1 mfd. 25,000 V. DC Westinghouse Interteen Type FP Style 1313854. **\$39.95 each**
10 or more. **\$35.00 each.**

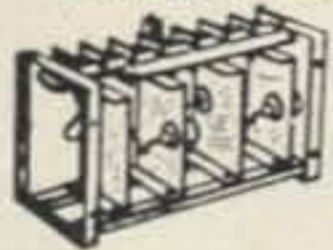GENERAL ELECTRIC FULL WAVE BRIDGE GERMANIUM RECTIFIER
input 117 volt AC, output 115 volt DC at 10 amperes approximate dimensions: 4 3/4" x 4 3/4" x 7 1/2" long weight: 3 1/2 lbs. **PRICE\$9.95 each**



TEST SCOPE—SYNCHROSCOPE—PULSE ANALYZER

ID-59/APA-11. Late production. Modular subassembly construction. Video amplifier is flat to 4 mc. 3BP1 presentation. Test-scope sawtooth 25-20,000 cy. Has all normal test-scope controls. As synchroscope and pulse analyzer, accepts positive or negative pulses. Video delay circuit permits leading edge of pulse to be seen. Calibrated-dial horizontal shift measures pulse durations from 0.5 to 100 microseconds. Sinewave-oscillator calibrator measures recurrence rates from 200 to 6000 pps accurate within 0.4%. Built-in power supply requires 115v, 400 cy, 196 watts. External 60 cy power supply may be made to furnish plus 350 and -1300 vdc and 6.3 vac. In excellent condition, with all 19 tubes, schematic with parts values, parts-location pictures, operating instructions, theory explanation, and maintenance charts. Shipping weight 60 lbs. Used, good. **Price each \$19.50**

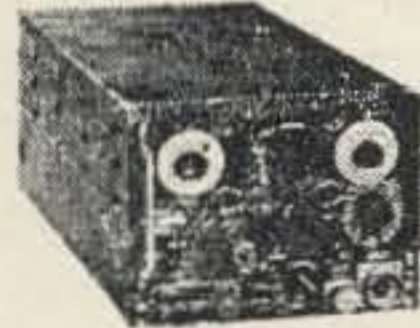

RG 58A COAX CABLE
52 OHM, 100 ft. lengths**\$3.95**

NICKEL CADMIUM BATTERY 1.2 VOLTS



Rechargeable thousands of times. Alkaline storage battery sintered-plate. Flat voltage curve during discharge. Will hold charge for long period of time. High discharge rate up to 50 amps. Spill-proof, may be used in any position. Approx. 6-ampere-hour capacity. Dimensions: 6" high; 2" wide; 1/2" thick. Approx. wt.: 6 oz. Uses potassium hydroxide (30% Electrolyte).**\$1.95**

SIGMA EXTRA-SENSITIVE PRECISION RELAY—SERIES 5F
Extremely precise, rugged DC general purpose sensitive relay. Balanced armature, single-pole, double-throw. Suitable for wide range of adjustments. Dimensions: 1 3/4" x 1 5/16" x 1 11/16" high. Weight: 4 1/4 oz. 5F-10,000S: 10,000 coil ohms. Operates 1.0 ma DC**\$3.95**



POWER TRANSFORMER
Output: 12, 24, 36 volt. Input: 100 volts, 60 cycles, single-phase. Will handle 2 1/2 amps. Steel case is hermetically sealed, 3 1/2" x 2 3/4" x 4 1/8". Wt. 3 1/4 pounds. **\$2.95**



DIRECT-READING MAGNETIC COMPASS
Full-floating card, compensating magnets, and dial light avail. in 6- or 12-v. bulb. Luminous dial. Mfgd. by Bendix-Pioneer. 3 1/4" x 3 1/4" x 3 1/2". 1 1/4 lbs. **\$8.50 postpaid.**



TCS DYNAMOTORS
12 volt D.C. input, 9.9 amps; output 440 volt D.C. at 200 ma new.**\$7.95**

12 volt D.C. input, 3.6 amps; output 225 volt D.C. at 100 ma new.**\$2.95 each**

RADIO COMPASS RECEIVER
B5/ARN7 Frequency 100 to 1750 KC Price**\$17.50**
R5A/ARN7 Price**\$27.50**
Loop LP21 LM Price**\$12.50**
Control Box C4/ARN7 Price**\$ 7.50**
Indicator 181A Price.....**\$ 4.95**

VARIAC TYPE V20
input 120 volt AC 50/60 cycles output range 0-140 volts, 20 amperes. **PRICE\$37.50 each**



TYPE AN/ARN-6 RADIO COMPASS
Receiver R/101/ARNN-6, 100-1750 kc. in 4 bands. Excellent condition. **Price\$34.50**
Loop AS313-B. Excellent Condition. Price**\$27.50**
Indicator ID91B/ARN-6 Price**\$ 9.95**
Mounts MT-273 or MT-274 Excellent Condition. Price Ea.**\$ 9.95**
Control Box C-149A. Price**\$15.00**



MANUAL
Handbook of operating instructions, general installation adjustment plus 5 pages of diagrams and Schematics. Price **\$ 3.50**

ANTENNA WIRE
150 ft. stranded copper on windup reel complete. **PRICE\$2.95 ea.**



12 FT. TELEPHONE STRETCH CORD
3 conductor wire with JK-53 and a U31/GT plug. **PRICE\$1.49 ea.**



SILICON RECTIFIERS

All rectifiers listed at maximum peak inverse voltage ratings; approximate forward voltage drop, 1.5 volts.



1N1446	.075 amp.	100 volts	.50
1N1477	.075 amp.	200 volts	.60
1N1448	.075 amp.	300 volts	.75
1N1449	.075 amp.	400 volts	.85
1N1450	5 amp.	100 volts	1.00
1N1451	5 amp.	200 volts	1.25
1N1452	5 amp.	200 volts	1.50
1N1453	5 amp.	400 volts	2.00
1N1454	25 amp.	100 volts	3.00
1N1455	25 amp.	200 volts	3.50
1N1456	25 amp.	300 volts	4.50
1N1458	35 amp.	100 volt	3.50
1N1459	35 amp.	200 volts	4.00
1N051P7	50 amp.	50 volts	6.00
1N1462	50 amp.	100 volts	7.00
1N1466	75 amp.	100 volts	10.00
1N1467	75 amp.	300 volts	11.00
1N1468	75 amp.	300 volts	12.50
1N05V7	150 amp.	50 volts	16.50
1N1474	150 amp.	100 volts	17.00

X-BAND POWER LEVEL TEST SET, TS-36/AP
Brand new, in original packing, was accessories. Measures 10 to 30 dbm, 8700-9500 mc. **\$14.95**

RT-82/APX-6 TRANSCEIVER
Easy to convert to 1215 Mc Ham Station. Good Condition, Less Tubes.....**\$9.95**

TS-34A/AP OSCILLOSCOPE
This is ready to plug into 120 v, 60 cy. Used but checked out and OK'd, in carrying case, less cords which are easy to make. You look into light-shielding hood, thru a magnifying lens, and the small-tube picture is same as on a 5" screen. 0-40 db attenuators in 2 db steps are so accurate that you use as a VTVM. Video flat 40 cy-2 1/2 mc. Contin. variable sweep 10 cy-50 kc. BEST OF ALL, there is a "Start-Stop" sw. position in which pulses to be viewed each trigger their own sweep; sweeps can be varied 4 1/2-8, 20-50, and 120-280 microseconds so accurate and linear that you use to measure pulse width. INVALUABLE TO VIEW TV PULSES! Pulses may be periodic or random, pos. or neg., as low as 0.1 v, and from a pip to 200 u-sec wd. Built-in delay lets sweep start before pulse appears. AT THIS LOW PRICE NO ONE NEED DO WITHOUT THIS WONDERFUL SCOPE!
USED, GOOD CONDITION.....**\$29.95**

BC1335 2-CHANNEL FM TRANSCEIVER
30-39 mc. This unit is complete with 18 tubes operating from either 6 or 16 volts D.C. (Self-contained power supply). Crystal control, sensitive supreme circuit. Approx. dimensions 11" x 10" x 6". Approx. 24 lbs. Unit complete with tubes, schematic diagram and presetting instructions. Like new. **\$25.00**



POWERSTAT TYPE 20
input 120 volt AC, 50/60 cycle output range 0-140 volts AC, 2 amperes. **PRICE\$8.95 each**



POWERSTAT TYPE 116
input 120 volts, 50/60 cycle output range 0-140 volts AC, 7.5 amperes. **PRICE\$16.95 each**

COAX CABLE RG59A/U
50 ft. roll complete with coax fittings. **PRICE\$2.49 ea.**



All prices FOB Pasadena unless otherwise noted. No COD's.

C & H SALES CO.
2176 E. Colorado St., Pasadena, Calif.
Murray 1-7393

"TAB" FOR THE BEST KITS!

Each "TAB" Kit Contains The Finest Selection!!!

- Kit 35 Precision Resistors
- Kit 75 Resistors 1/2/1&2W
- Kit 12 Electrolyte Cond's
- Kit 65 Tubular Condensers
- Kit 500 Lugs & Eyelets
- Kit 10 Bathtub Oil Cond's
- Kit 5 lbs Surprise Package
- Kit 10 Transmit Mica Cond's
- Kit 3 Phone/Patch Xfmr's
- Kit 6 Insld Tuning Tools
- Kit 4 "Suncells" Asstd.
- Kit 5 Sub-Min Tubes
- Kit 75 Mica Condensers
- Kit 8 Crystal Diodes
- Kit 200ft Hook Up Wire
- 4 Rolls, 50ft/ea. Assorted. Color
- Kit 5 FT243 Xtal Holders
- Kit 8 Xtal Osc-Blanks
- Kit 4 Asstd Rectifiers
- Kit 100 Self/Tap Screws
- Kit Adj Wire Stripper & Cut
- Kit Hi Gain Xtal Mike
- Kit 2 pair S0239 & PL59
- Kit 12 Binding Posts Asstd

99c
Order Ten Kits—We Ship Eleven!!!
ONE EACH ABOVE KIT ONLY

SELENIUM F.W. BRIDGE RECTIFIERS

One Year Grid	DC AMP	18VAC 14VDC	36VAC 28VDC	72VAC 54VDC	130VAC 100VDC
1/2	1	\$1.00	\$1.90	\$3.85	\$5.00
2	2	1.30	2.00	4.90	8.15
3	3	2.15	3.00	6.25	11.10
6	6	2.90	4.00	8.60	13.45
10	10	4.15	8.00	18.75	31.90
12	12	6.10	12.15	26.30	41.60
20	20	7.75	14.90	30.95	43.45
24	24	12.85	24.60		

Write For Rectifier Catalog

Leece Neville Charger Systems
Sealed Silicon Stud Rectifier
Finned Stack, Direct Replacement
FOR 6 or 12VDC @ 100A,
Type YJ9 \$18

SILICON TUBE REPLACEMENTS

TYPE	VRMS/PIV	AMPS	PRICE
T866	5000/10400	0.3	\$16
T5R4	1900/2800	0.5	\$7
5U4	1120/1600		\$3.90
OZ4	UNIVERSAL		\$1.50



GTD! POWER-DIAMOND-TRANSISTOR
Factory Tested
***MFGD in U.S.A.
Replaces Medium & HiWattage Types
2N155, 2N156, 2N234,
2N256, 2N307, 2N554
35c each, 4 for \$1

Two 866A's and FILAMENT
XFMR 10 Kv Insld SPECIAL! **\$6**

- DIAMOND BASE MICA MTG KIT \$.30**
ROUND BASE MICA MTG KIT \$.30
DELCO PWR HEAT SINK 80 SQ" \$1.75
KIT TRSTB NPN or PNP. 36c ea.; 8, \$2
1N34A DIODES .19c ea.; 6 for \$1

- "TAB" BARGAINS**
- New Variacs/or equiv 0-135V/7.5A \$15.30
 - New Variacs/or equiv 0-135V/3 Amp \$10.65
 - DC-METER Dejur 800 Ma/2 1/2" \$3@
 - DC-MTR 100Ma/2 1/2" \$3@
 - RF-MTG GE/475 Ma & 5 Amp \$4@, 2/\$7
 - DC-METER One Ma/4" Rd. \$5@, 2/\$8
 - SNOOPERSCOPE TUBE 2" \$5@, 2/\$9
 - MINI-FAN 6 or 12VAC/60 Cys \$2@, 3/\$5
 - Xmitting Mica's .006 @ 2500V, 5 for \$1.00
 - 4x150 Ceramic/LOKTA \$2 for \$1.00
 - 866A Xfmr. 2.5V/10A/10KV Insl. \$3.95
 - Microswitch B1/SPNC/30 Amp 49c@
 - Tube Clamps Bircher 5 for \$1.00
 - .012 at 25Kv CD Condenser 4@
 - WE Choke 4Hy/450Ma/27 Ohms \$4@
 - Line Filter 50Amp/250VAC . . . \$10@
 - Line Filter 200Amp/130VAC . . \$18@
 - Bruning Parallel 6" Rule 69c@
 - KS15138 Linear Sawtooth Pot. . . 2 for \$1.00
 - "CTC" Delay Line 1 Microsec'd \$1@, 3/\$2
 - Vacuum Cond's 50Mmf/7.5Kv \$3@
 - .01 at 7500v oil \$2@
 - BALLENTINE #300AC/LAB MTR \$54

"TAB" THAT'S A BUY

"TAB" Tubes Factory Tested, Insptd,
Six Months Guaranteed! No Rejects! Boxed!
GOVT & MFGRS Surplus! new & Used

Buy & Sell	Buy & Sell	Buy & Sell
0A2 .89	6BZ7 1.25	43 .75
0A3 .80	6C4 .45	45 .49
0B2 .65	6C5 .69	50L6 .69
0C3 .70	6C6 1.08	RK59 1.39
0D3 .50	6C8 1.08	RK60 1.17
0Z4 .79	We Trade!	HY69 2.20
1A7 .90	6CB6 .89	75 .81
1B3 .99	6CD6 1.49	HY75 5.00
1L4 .82	6CF6 .85	83V .95
1R4 5/\$1	6CL6 1.40	

We Swap Tubes! What Do/You Have?

IR5 .78	6CB6 .89	IPR60A 37.50
IS4 .78	6CG8 1.12	4-125A 27.50
IS5 .68	6CM6 .79	4X150G 15.00
IT4 .85	6CS6 .70	4X250B 41.00
IT5 .95	6CU6 1.29	4-400A 41.75
IU4 6/\$1	6D6 .99	4E27A 39.00
IU5 .75	6E5 .79	250TL 19.45
IX2 .99	6F4 2.49	307A 2/\$1
2C39A Q	6F5 .63	316A 5/\$1
2C40 5.50	6F6 .99	VR92 5/\$1

Send 25c for Catalog!

2C43 6.50	6F7 .99	388A 3/\$1
2C51 2.00	6F8 1.39	350A 2.45
2D21 .65	6H6 .59	350B 1.75
2E22 Q	6J4 1.72	371B .95
2E24 Q	6J5 .59	6146 3.90
2E25 2.50	6J6 .59	416B 16.00
2E26 Q	6J7 .99	450TH 43.00
2E30 Q	6J8 1.39	450TL 43.00
2E35 1.60	6K6 .59	460 11.50
2K25 9.75	6K7 .79	

All Tubes Stocked at Low Prices!

2K26 34.00	6K8 .99	703A Q
2K28 30.00	6L6 1.19	707B 3.50
2V3 2/\$1	6SN7 .72	715C 10.90
2X2 .48	6T8 .98	717A 5/\$1
3A4 .70	6V6GT .90	723AB 5.00
3A5 1.00	6X5 .49	725A 2.75
3AP1 5.95	12AT6 .59	803 3.50
3BP1 3.99	12AT7 .89	804 8.85
3C24 3.50	12AU6 .63	805 6.00
3D23 3.95	12AU7 .69	

We Buy! We Sell!

3E29 6.00	12AX7 .79	807 1.10
3Q4 .68	12AY7 1.29	5/\$5
3Q5 .86	12B4 .95	10/\$12
4-65A 13.50	12BA6 .65	
4-125A 27.50	12BA7 .99	811 Q
4-250A 34.00	12BD6 .59	811A Q
4X150A Q	12BE6 .59	812 Q
4X250 36.00	12BH6 .79	813 9.95
4X500 Q	12BH7 .99	815 1.75
5AP1 2.95	12BY7 1.00	826 .99

Wanted Test Sets and Equipment

5BP1 Q	12BZ7 .99	828 9.00
5BP4 7.95	12H6 .75	829B 8.00
5CP1 4.99	12J5 .69	832A 6.00
5CP7 9.00	12J7 .69	833A 36.00
5R4 1.00	12J8 1.35	837 Q
5T4 .90	12K8 .89	866A 2.25
5U4 .99	12SA7 .69	954 Q
5V4 .89	12SC7 .89	955 3/\$1
5Y3 .60	12SF5 .69	957 3/\$1
5Z3 .89	12SG7 .89	958A 2/\$1

Send 25c for Catalog!

15GP22 89.00	12SH7 .89	991 5/\$1
6A7 1.00	12SJ7 .75	1614 2.75
6A8 .99	12SK7 .75	1619 5/\$1
6AB4 .59	12SL7 .79	1620 2.00
6AC7 .72	12SN7 .69	1625 3/\$1
6AG5 .65	12SQ7 .69	1626 5/\$1
6AG7 .75	12SR7 .69	1629 4/\$1
6AK5 .69	15E 1.19	1050 1.25
6AL5 .59	15R 4/\$1	5517 1.25
6AQ5 .66	FG17 Q	5608 3.95

Top \$\$\$ Paid for 304TL, 813, 811A, 812A Tubes

6AR6 1.95	19T8 1.16	5618 3.25
6AS7 3.49	24G Q	5651 1.35
6AT6 2/\$1	25A6 1.19	5654 1.20
6AU6 .79	25A7 2.19	5656 4.25
6B8 1.35	25C5 .81	5663 1.15
6BA6 .59	25L6 .72	5670 .90
6BE6 .59	25T 4.00	5686 1.75
6BG6 1.49	25Z5 .72	5687 1.15
6BH6 .79	25Z6 .75	5691 4.70
6BJ6 .72	26A7 3.69	5725 1.95

Top \$\$\$ Paid for XMTR Tubes!

6BK7 .99	FG27 8.28	5732 2.00
6BL7 1.35	HV27 19.39	5736 85.00
6BN4 .69	28D7 .89	5749 1.95
6BN6 1.08	FG33 15.00	5750 2.75
6BN7 1.99	EL34 3.49	5751 1.25
6BQ6 1.19	35A5 .69	5814 1.20
6BQ7 .99	35L6 .59	5879 1.20
6BX7 1.11	35T 4.49	5894 12.00
6BY5 1.19	35Z5 1.25	
6BZ6 .91	RK39 2.99	

No See—Write!

"TAB" SCR's * TRANSISTORS * DIODES!!!
Full Leads Factory Tested & Gtd!
U.S.A. Mfg

PNP 50Watt/15Amp HiPower
TO36 Pckg! 2N441, 442, 277,
278, D5501 up to 50 volts/
VCBO \$1.25 @, 5 for \$5.
2N278, 443, 174 up to 80v
@ 2 for \$5.



PNP/10Watt/3A-2N155, 156, 235, 242,
254, 255, 256, 257, 301, 351 35c @ 4 for \$1
PNP/Signal up to 350MW TO5. 25c @,
6 for \$1
NPN/Signal IF, RF, OSC. TO5, 0V5, 25c
@, 6 for \$1
PNP 2N670/300MW . . . 35c @, 4 for \$1
PNP 2N671/1Watt . . . 50c @, 3 for \$1
Silicon PNP TO5 & TO18, Pckg 25c @,
5 for \$1

TO36, TO3, Pckg Mica Mtg Kit 5 for \$1
Power Heat Sink Finned 80 Sq \$1.25 @,
5 for \$5
3 Amp/TO3/Pwr Transistors Untested!
10 for \$1
Pwr Transistors TO3/3A Untested 10 for \$1
Stabistor Diodes up to one watt 5 for \$1
Silicon Diodes 35 Amp Studs Untested
3 for \$1
Silicon Diodes epoxy/750Ma Untested
25 for \$1

2N1038/3A Int Sink	40v	4 for \$1
2N1039/3A Int Sink	60v	3 for \$1
2N1040/3A Int Sink	80v	2 for \$1
2N1041/3A Int Sink	100v	1 for \$1
2N538-39-40/3A small		2 for \$1

"TAB," SILICON 750MA* DIODES
Factory Tested Gtd!

***NEWEST TYPE! LOW LEAKAGE**

Piv/Rms	Piv/Rms	Piv/Rms	Piv/Rms
50/35	100/70	200/140	300/210
.05	.09	.12	.16
400/280	500/350	600/420	700/490
.22	.26	.34	.43
800/560	900/630	1000/700	100/770
.50	.60	.72	.88

ALL TESTS AC & DC & FWD & LOAD!
400 PIV @ 750MA Quantities 1000 \$200
600 PIV @ 750MA Quantities 1000 \$300
1100 PIV @ 750MA Quantities 15 for \$10

D.C. Power Supply 115V/60 to 800 Cys. Output 330 & 165 VDC up to 150 MA. Cased SPECIAL \$5.

Silicon Power Diodes Studs & P.F.*

D.C. Amps	50Piv 35Rms	100PIV 70Rms	150Piv 105Rms	200Piv 140Rms
3	.15	.20	.25	.35
12	.50	.70	.80	.95
*18	.30	.45	.60	.90
35	1.15	1.40	1.60	1.80
100	1.90	2.50	3.00	3.50
240	6.50	7.70	8.90	10.40
D.C. Amps	300Piv 210Rms	400Piv 280Rms	500Piv 350Rms	600Piv 420Rms
3	.45	.55	.65	.70
12	1.15	1.40	1.60	1.80
*18	1.10	1.35	Query	Query
35	2.50	2.75	3.25	3.90
100	4.00	4.75	5.75	8.50
240	19.50	27.50		

Sil. Pressfit 18A up to 100 Piv
4 for \$1
Micro or MuSwitch CSD 35 Amp/AC-DC
3 for \$1

"SCR" Silicon Controlled Rectifiers!

PRV	7A	16A	PRV	7A	16A
25	.60	1.00	260	2.70	3.00
50	1.00	1.35	300	3.00	3.45
100	1.60	2.15	400	3.75	3.90
150	1.95	2.45	500	4.75	4.80
200	2.20	2.80	600	5.45	5.65

SCR KIT UNITS UP TO 25-AMPS UNTESTED
4 for \$2

Silicon Diodes 3&6 Amp Studs
Untested .12 for \$1
Glass Diodes 1N34/48/60/64
Untested .20 for \$1

TERMS: Min Order \$3—25% with order F.O.B. New York. Ten day guarantee, price of mdse. only. Our 17th year.
Prices shown are subject to change.
"TAB" 111MJ Liberty St., N.Y. 6, N.Y. • RE 2-6246

JEFF-TRONICS

Now in our fifth year, and still growing

Selenium Rectifiers, 3-phase, 14 volts, 60 Amps. Leece-Neville #30605, for use with Leece-Neville Alternators. Shpg. Wt. 6 lbs. **\$7.73**

Selenium Rectifiers, single-phase, full-wave bridge 55 volts, 3 amps. 3 1/2" x 4 1/2" x 8 1/2". Useful for powering surplus relays, motors, etc. 3 lbs. **Only \$1.00**

APX-6 IFF Set. Transceiver for 1296 MC. With 31 tubes. Used, good. Shipping Wt. 50 pounds. **\$16.50**

Collins ART-13 Transmitter, complete with tubes, less calibration book. Excellent used condition. Shpg. wt. 90 pounds. Limited quantity at **\$40.00**.

BC-221 Freq. meter, with xtal & original calibration book. No modulation. Excellent used condition. Limited quantity **\$75.00**

3BP1 Cathode Ray Tubes **\$2.49**

2E25 tubes. Special **75c each. 4 for \$2.50**

Plate Transformer 390-0-390 v. 450ma. Use in bridge circuit for 750 volts, 300 ma. 4 1/2" x 6 x 6 1/2". 20 lbs. **\$4.00 each. 3 for \$10.00**


Power Transformer, 350-0-350 v. 130 ma., 5v, 3 A., 6.3v. 3.6A. 3" x 3 3/4" x 3 1/2". Uncased. 7 lbs. **\$1.95**

Output Trans. 8000r P-P to 4, 8, 16, 500r. 15 watts. 3 x 3 1/2 x 3 1/2". Upright mounting with end bells. 4 lbs. **\$2.00**

Modulation Transformer. 1.75 to 1 ratio. For 807, 1625, 6146, etc. 100 watts. Fully enclosed use, 4 x 5 x 5", 13 lbs. **\$3.95**

Scope Transformer, 2750v. @ 6ma., 220-0-220v. @ 224ma. 135v. @ 8ma. Oil-filled. 3 1/2" x 4 1/4 x 5". 12 lbs. **\$2.00. 3 for \$5.00**

2-METER STATION in one neat package

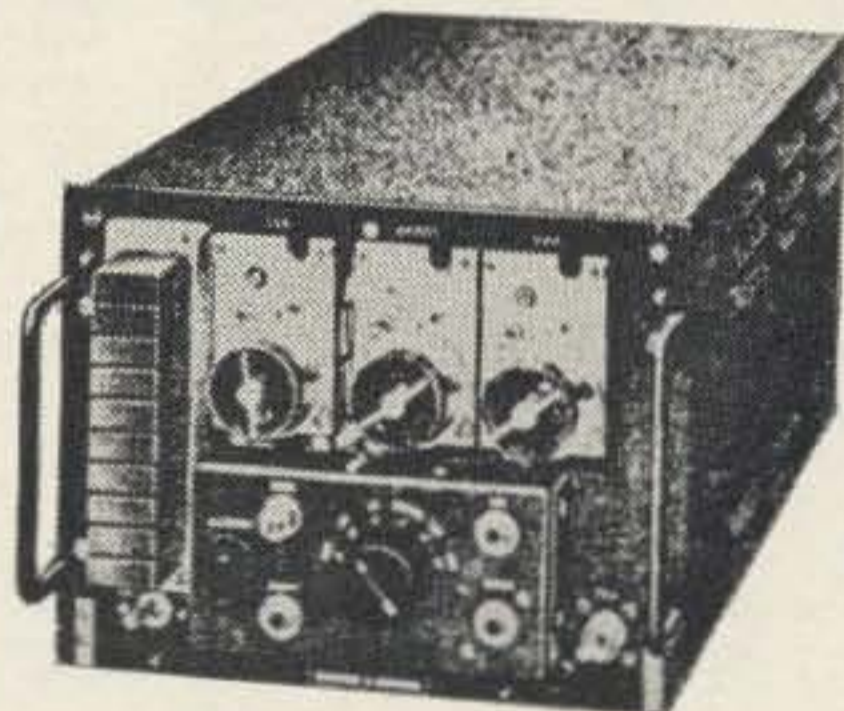

ARC-1 Navy Surplus Transmitter Receiver Xmtr, uses 832A in final, 20 watts input, with AM push-pull plate modulation. Ten crystal controlled channels. Freq range 100-156 Mc. Receiver has extra, separate guard channel which can be tuned for your net frequency. Complete with tubes, schematic diagram, and conversion instructions for AC power supply and tunable oscillator. Shipping wt. 60 pounds. Used good. **\$24.95**

POWER SUPPLY Kit for ARC-1

Complete with isolating power transformer, 115v 60 cycles, silicon rectifiers, punched chassis, and all necessary parts. Fits inside ARC-1 case. Shipping wt. 20 pounds. **\$19.95**

Write for info & prices on completely converted ARC-1. A ready-to-use 2-meter station for under \$100.00.

BC-221 Technical Manuals. 3 different books available. Specify (Models N, AA); (Models P, T, AF, AH); (Model AK). **\$1.50 each book.**

Filter choke. Stancor C-1003 16 Hy. 50ma. 580 ohms. 1500v. insulation. 1 1/2 x 2 1/2 x 3. 2 lbs. **75c.**

10uf-600v. oil-filled capacitors. 1 1/4 x 3 3/4 x 5 1/2." 2 lbs. **95c ea. 10 for \$7.50**
1uf-3kv. GE Pyranol. 1 3/4 x 3 3/4 x 4 1/2". 2 lbs. **\$1.50 ea. 5 for \$5.00.**

Coaxial Cables. 10 feet RG8/U with UG-21 type N connectors on each end. **\$1.00 each. \$10.00 dozen.**

Send for our flyer of good, clean surplus. Please include sufficient money with your order to cover shipping charges & insurance.

JEFF-TRONICS

4791 Memphis Ave .

Cleveland, Ohio 44109

T E C H N I C I A N M A N U A L S

AM-609 \$7.50
 APA-6 7.50
 APA-10 6.50
 APA-11 7.50
 APA-16 7.50
 APA-17 8.50
 APA-24 7.50
 APA-38 7.50
 APA-56 4.50
 APA-81 7.50
 APG-30 15.00
 APG-30a 15.00
 APN-1 5.00
 APN-11 8.50
 APN-4 10.00
 APN-9 10.00
 APN-41 7.50
 APN-59 12.00
 APN-67 12.00
 APN-122 9.00
 APQ-2a,b 7.50
 APR-1 7.50
 APR-2 7.50
 APR-4 7.50
 APR-12 12.00
 APS-2 15.00
 APS-3a 15.00
 APS-4 15.00
 APS-15a, b 20.00
 APS-19a 20.00
 APS-20b, c 20.00
 APS-20e, f 35.00
 APS-31, a+ 30.00
 APS-33, a+ 30.00
 APS-38, a+ 35.00
 APS-42b 30.00
 APS-44, a 35.00
 APS-80 25.00
 APT-5, 5a 7.50
 APX-6 8.50
 APX-6b 8.50
 APX-7 8.50
 ARB 7.50
 ARC-1 8.50
 ARC-1a 8.50
 ARC-2 10.00
 ARC-3 10.00
 ARC-5 LF 8.50
 ARC-5 VHF 9.00
 ARC-12 for
 RT-58 8.50
 ARC-12 for
 R-11, T-11 9.00
 ARC-19 9.00
 ARC-27 8.50
 ARC-28 6.50
 ARC-30 5.00
 ARC-39 8.50
 ARC-44 8.50
 ARC-48 8.50
 ARC-51 8.50
 ARC-52 8.50
 ARM-5 8.00
 ARM-10 6.50
 ARM-19 7.50
 ARM-22 6.00
 ARM-25 9.00
 ARM-32 6.50
 ARM-35 6.50
 ARM-53 6.50
 ARN-5 7.50
 ARN-6 8.50
 ARN-7 9.00
 ARN-8 5.00
 ARN-12 5.00
 ARN-14 10.00
 ARN-14a 10.00
 ARN-14b 10.00
 ARN-14c 10.00
 ARN-14d 10.00
 ARN-21 10.00
 ARN-21b 10.00
 ARN-18 4.00
 ARN-30 8.00
 ARN-52 12.00
 ARQ-8 8.00
 ARR-2 8.50
 ARR-5 7.50
 ARR-7 7.50
 ARR-7ax 7.50
 ARR-15 10.00
 ARR-16b 6.50
 ARR-26 10.00
 ARR-31 7.50
 ARR-41 10.00
 ART-13
 maintenance \$10.
 operation \$4.
 Calibration \$5.
 ART-26 8.00
 ART-28 8.00
 ATD 7.00
 ATB 7.50
 ATK-ARK 12.00
 TS-7 \$5.00
 TS-10 5.00
 TS-12 5.50
 TS-19 5.00
 TS-23 6.50
 TS-23a 6.50
 TS-24 8.50
 TS-34 7.50
 TS-34a 7.50
 TS-47 6.50
 TS-62 6.00

TS-67 5.00
 TS-70 5.00
 TS-74 4.00
 TS-85 4.00
 TS-89 5.00
 TS-92 6.50
 TS-100 7.50
 TS-101 6.50
 TS-102 7.50
 TS-118 5.00
 TS-125 5.50
 TS-146 6.50
 TS-147 6.50
 TS-147a 6.50
 TS-147d 6.50
 TS-170 6.50
 TS-174 6.50
 TS-174a 6.50
 TS-175 6.50
 TS-175a 6.50
 TS-186 6.50
 TS-189 6.50
 TS-202a 6.00
 TS-218 6.00
 TS-250 6.50
 TS-251 6.50
 TS-268 5.00
 TS-270 6.50
 TS-299 6.50
 TS-297 5.00
 TS-306/07 7.50
 TS-311 6.50
 TS-320 5.00
 TS-322 5.00
 TS-323 6.50
 TS-388 4.00
 TS-345a 4.00
 TS-352a 5.00
 TS-352b 5.00
 TS-355 6.50
 TS-375, a 7.50
 TS-382a, c 5.00
 TS-382d, f 5.00
 TS-382b 4.00
 TS-387 6.50
 TS-403 8.50
 TS-406 6.50
 TS-413, a 7.00
 TS-418a, b 10.00
 TS-419, a 10.00
 TS-452 6.50
 TS-452a 7.50
 TS-453 3.50
 TS-487 5.00
 TS-488a 4.00
 TS-508 5.00
 TS-509 5.00
 TS-505 6.50
 TS-505a, c 6.50
 TS-522 5.00
 TS-535a 7.00
 TS-621 8.50
 TS-622 7.50
 TS-689 7.50
 TS-690 7.00
 TS-691 6.50
 TS-730 5.00
 TS-738 6.50
 TS-757 7.50
 TS-768 7.50
 TS-768b, c 7.50
 TS-872 6.50
 TS-1178 6.50
 TS-1235 7.50
 TS-1320 7.50
 TS-1506 8.50
 UPM-4a 8.50
 UPM-6a, b 8.50
 UPM-8b 7.50
 UPM-9 6.50
 UPM-11a 6.50
 UPM-14 7.50
 UPM-26 6.50
 UPM-42 7.50
 UPM-44, a 7.50
 UPM-44b, c 7.50
 UPM-46 5.00
 UPM-55, a 6.00
 UPM-109 7.50
 UPM-116a 6.50
 UQM-3 5.50
 URA-35 12.00
 URM-1 5.00
 URM-23 \$5.00
 URM-25f 7.50
 URM-26a 7.50
 URM-26b 7.50
 URM-44 7.50
 URM-49 10.00
 URM-52, a 8.50
 URM-58 3.00
 URM-64, a 8.50
 URM-72 7.50
 URM-129 6.50
 URW-14a 12.00
 URW-16 12.00
 USM-24 9.00
 USM-24c 9.00
 USM-32 8.50
 ZM-3 6.50

LM-14 7.50
 LM-18 7.50
 RA-18C-1, 2, 3 9.00
 RA-21a 10.00
 51R3 12.00
 51V 9.00
 51V-2 9.00
 51X2b 7.00
 AVR-104 5.00
 17L7a 7.50
 TA-18bb 5.00
 TA-20a 8.00
 18-S-4, 4a 10.00
 51Y3 12.00
 DF-202 12.00
 MN-26c 7.50
 TA-12 7.50

BC-348 maintenance manuals, specify series letter, we have them for the E, J, M, N, O, P, Q, S, letters — \$7.50 each

SCR-274N maintenance manual—covers BC-457, 458, 459, BC-696 —\$7.50 per copy

These are RARE—all are maintenance books—
 URA-6, 7—CV-57 \$12.00
 URA-8 CV-60 \$10.00
 URA-8b—CV-89a \$10.00
 SCR-522a, covers BC-624a, and BC-625a —\$7.50
 SCR-624a, b, covers BC-624, BC-625, RA-62—\$7.50
 BC-640a, b maintenance \$8.50
 BC-640d maintenance \$8.50
 BC-639a maintenance \$8.50
 BC-638 maintenance \$7.50

the manuals listed in the two columns at left are all either maintenance manuals or instruction books, all contain schematics, all manuals offered by our firm are complete originals, not copies, or abridged editions. 90% are new, a few of the really scarce manuals may be used but are still complete and in good condition. This we cannot help as many manuals are collectors items and unobtainable in any other than used condition. All prices include postage prepaid to any U. S. address, for export orders add 10% to listed prices to cover export packing and necessary export documentation. Many manuals listed may be one of a kind, so avoid disappointment and order soon. All manuals are offered subject to prior sale, and are subject to price changes without notice. We buy manuals too, currently in need of Navy NAVSHIP & BUSHIP Manuals for receivers and Transmitters

with prefixes of R. & T, such as RAK, RAL, TCS, TDQ etc.

AM-65 \$6.50
 BC-191 7.50
 BC-221 7.50
 BC-224 7.50
 BC-312 5.00
 BC-314 5.00
 BC-342 5.00
 BC-344 5.00
 BC-348 7.50
 BC-375 7.50
 BC-474a 4.00
 BC-603 5.00
 BC-604 5.00
 BC-610 10.00
 BC-611 4.00
 BC-614 5.00
 BC-620 4.00
 BC-624 7.50
 BC-625 7.50
 BC-638 7.50
 BC-639a 8.50
 BC-640a, b 8.50
 BC-640d 10.00
 BC-653a 4.00
 BC-655a 5.00
 BC-659 5.00
 BC-666 4.00
 BC-669 4.00
 BC-745 5.00
 BC-779 7.50
 BC-792 7.50
 BC-794 7.50
 BC-906 4.00
 BC-923a 6.50
 BC-918b 4.00
 BC-973a, b 4.00
 BC-1000 6.50
 BC-1004 7.50
 BC-1005 4.00
 BC-1006 5.00
 BC-1032a 6.50
 BC-1147a 7.00
 BC-1159a 7.00
 BC-1306 6.50
 BC-1338 7.00
 BC-339 6.50
 BC-447 6.50
 BC-684 6.50
 BC-652 6.50
 BC-683 6.50
 BC-728 6.50
 BC-733F 6.50

Navy Manuals — for the most part these are all one of a kind, quite scarce, high in demand, used, but perfect condition:
 ABK \$8.50
 ARA 7.50
 ATA 7.50
 ASB-3 7.50
 ASB-7 7.50
 CPN-6 12.00
 DAB 10.00
 DAB-1 10.00
 DAE 8.00
 DU-1 7.00
 DZ-1 7.50
 DZ-2 7.50
 FRT-5 12.00
 FRT-15a 10.00
 FRT-39 8.60
 FRR-27 8.50
 FRR-49V 7.50
 GF-12 7.50
 GO-9 7.00
 I-177 4.00
 LAF-2 7.50
 LN 7.00
 LP-5 7.50
 LR-1 7.50
 MAB 3.00
 MAW-1 8.00
 MBF 9.00
 NGB 10.00
 RA-10CA 6.50
 RAK 8.00
 RAK-1 8.00
 RAK-6 9.00
 RAK-8 9.00
 RAL-6 9.00
 RAS-4 9.00
 RAX-1 7.50
 RBA 8.50
 RBA-1 7.50
 RBB-1 8.50
 RBB-3, 4 8.50
 RBC-1 8.50
 RBC-3, 4 8.50
 RBK 7.50
 RBK-9 7.50
 RBK-12 7.50
 VRC-2 \$7.00
 VRC-3 6.00
 VRC-4 6.00
 VRC-5 6.50
 VRC-6, 6x, y 6.50

VRC-7 6.50
 VRC-8, 9, 10 6.50
 VRC-13, 14, 15 6.50
 VRC-19, 19x, y 6.50
 VRC-20, 21 6.50
 VRC-22 6.50
 VRQ-1, 2, 3 6.50
 VRR-7 6.50
 RT-66, 70 6.50
 RT-67, 68 6.50
 RT-70a 6.50
 RT-77 6.50
 RT-196 4.00
 RT-306a 6.00
 TG-34a 2.00

Equipment in the three columns on this side of ad are covered in their own manual or in a manual with another piece of equipment, therefore FM-11 numbers and other manual identification is not given. When ordering, be sure to give all identification possible on your equip-

High demand teletype manuals
 TM-11-352 TG-7a, TG-7b, TG-37b \$6.50
 TM-11-356 AN/FGC-1, 1c, 1x 6.50
 TM-11-854 Radio receiver R-388/URR 10.00
 TM-11-855 Radio receiver R-389/URR 10.00
 TM-11-856 Radio receiver R-390/URR 10.00
 TM-11-856a Radio receiver R-390a/URR 10.00
 TM-11-2205 Exciter units 0-5/FR, 0-5a/FR, 0-86 6.00
 TM-11-2208 Test set TS-2/TG, TS-2a, TS-2b 6.00
 TM-11-2214 Teletype set AN/TGC-3 9.00
 TM-11-2215 Teletype set TT-5, TT-6 9.00
 TM-11-2216 Teletype set TT-7, TT-8, mod. 19 9.00
 TM-11-2217 TS-383 distortion test set 8.00
 TM-11-2222 TT-26, TT-52, TT-12, 13, 21, 24 etc 8.00
 TM-11-2223 Teletype model 14 9.00
 TM-11-2229 Teletype model TT-47, 48, 69 9.00
 TM-11-2234 Teletype TGC-7, TT-4, TT-4a etc 9.00
 TM-11-257—O-39, 0-39a, b, c 6.50
 TM-11-261—CV-31, CV-31a, b, c, d 6.50
 TM-11-266—CV-157/URR 6.50

ment and we will supply the best manual in stock to cover your needs. The listings here do not always give suffix numbers for the equipment such as BC-603, BC-603a, etc—but if such minor letters are on the name plate of your equipment, let us know about it as it is all important in making sure you receive the proper manual. Manuals for the different variations of equipment are the same price as for the basic models shown—example—manual for the BC-603a is the same price as for the BC-603 —\$5.00 — These manuals all have schematics and service or repair instructions.

Technical literature is our business, not a sideline. We stock thousands of different manuals, not just a few various volumes, and we feel we have one of the largest and most diversified libraries in the country. We have tried to list here only the manuals most called for, so if your need is not listed—please write. New manuals arrive daily, and stock is constantly changing so it is impossible to keep accurate lists in print of what we have to offer, however we do keep accurate files of whats on the shelf and will do our best to turn up a manual to fill your needs. Sometimes we fall—lots of manuals are really rare and have virtually disappeared, some are so low in demand that its impractical to stock and catalog them. Still we send out more availability quotes and fill more orders than we return. Give us a chance at that next need for tech literature. Often times the proper manual will enable you to convert that boat anchor to an operating piece of equipment, and return many times its price in time and labor saved.

PROPAGATION PRODUCTS COMPANY
 P. O. BOX 242, Jacksonville 1, Fla.

GOING TO THE FAIR?

VISIT OUR NEW STORE

Ham Industrial Export

TEST EQUIPMENT

TS-173/UR Freq mtr	\$145
TS-174/U Freq mtr	\$135
TS-175/U Freq mtr	\$135
TS-186/UP Freq mtr 100 mc-10 kmc	\$165
TS-230/UP Freq mtr X-band	\$200
TS-251/UP Loran test	\$100
TS-263/UP Sig Gen X-band	\$ 75
TS-268/UP Diode test	\$ 50
TS-323/UR Sig Gen	\$175
TS-330/TSM Xtal test	\$750
TS-382D/UP Audio osc	\$300
TS-403/U Sig gen	\$475
TS-413/UP Sig Gen	\$150
TS-414/U Dyn Test	\$225
TS-419/U Sig Gen	\$475
TS-488A Echo Box X-band	\$ 75
TS-452/UP Sweep Gen	\$300

Many Other TS Types

TEKTRONIX SCOPES

511	\$145
512	\$175
513	\$325
514	\$350
517A	\$850

Many Other TEK Items

DUMONT SCOPES

304H	\$150	324	
322		256D	\$130

HEWLETT PACKARD

200C Audio osc	\$ 80
200CD Audio osc	\$125
202A Function gen	\$350
233A Osc	\$375
205AG Audio osc	\$225
212A Pulse gen	\$400
330B Distortion anal.	\$350
400C VTMR	\$125
410B VTMR	\$150
521A Counter	\$350
523 Counter	\$825
524C Nixi counter	\$2,350
608B Sig gen	\$525
608C Sig gen	\$850
610A Sig gen	\$425
715A	\$150
430B Pwr mtr	\$150
415B Vswr mtr	\$135

H.P. Waveguide in Stock

AN/URM-25 Sig gen	\$300
AN/URM-26 Sig gen	\$300
AN/URM-48 Sig gen	\$1250
AN/URM-49 Sig gen	\$550
AN/UPM-4A I.F.F. test	\$550
AN/UPM-6B I.F.F. Test	\$425
AN/UPM-8 I.F.F. Test	\$ 75
AN/UPM-11A Range calib. X-band	\$500
AN/UPM-25 Sig gen	\$135
AN/UPM-33 Spec anal.	\$375
AN/UPM-44B Sig gen	\$425
AN/UPM-98 & 99 I.F.F. test write	

Many Other UPM, URM, USM etc

MISC TYPES

Meas Corp 84 300-1000 mc	\$300
LA-592A	\$250
PH angle volt mtr	\$250
Panoramic AP-1 sonic spectrum analyzer	\$375
WE X75444A radar echo (10 mi range) type telephone line Break finder	\$950
BC-221	\$ 60
AN/USM-29 Digit freq mtr and sig gen 15kc-300 mc	\$1000
ASQ-1 Magnetometers	\$300
ASQ-8 Magnetometers	\$4,000
APN-84 and CPN-2A Shoran/Hiran write	
PPS-4 Battlefield portable radar X-band	\$750
TDQ Xmtrs 100-156 mc	\$135

RADIO "RADAR"

TRC-2 2-6 mc 15w	\$200
TRC-7 100-156 mc walkie talkie	\$125
ARC-21 350w 2-22mc	\$1,300
ARC-48 200-400 mc	\$135
ARC-65 350w 2-22mc S.S.B. transceiver mobile 28,000 channel automatic tuning	\$2,000
ARN-7 Adf	\$125
ARN-21-B Tacan	\$2,000
ARN-21-C Tacan	\$2,400
APR-4 30-4000 mc	\$300
APR-5 1-4 kmc	\$100
APR-6 3-10 kmc	\$175
APR-9 i-10 kmc	\$3,000
APR-14 30-1000 mc AM, FM, built in panadaptor	\$2,500
R-390 .54kc-40mc	\$650
R-390A .54kc-40mc	\$900
R-388	\$550
SP-600	\$450
APX-6 RT-82	\$ 40
TT-IB page printing fascimile Transceiver	\$ 85
Rem dual. indic. panadaptor 5.25 mc & 455 kc 1 only	\$300
63 mc I.F. strips	\$25

GENERAL RADIO

GR-650A Imp Bridge	\$135
GR-1604-B Compar. Bridge	\$175
GR-916 R.F. Bridge	\$300
GR-561 Vac. Tube Bridge	\$375
GR-8746BA Slot Line	\$150
GR-720A Freq. Mtr.	\$150
GR-1001A Sig. Gen	\$575
GR-805-C Sig. Gen	\$800
G.R. Unit OSC: Write	
GR-783 Output Meter	\$200
GR Sound & Vib, Mtrs. Write	
GR-631 Strobotron	\$ 85
GR-648A Strobotron	\$125

Many other types

FERRIS

16-C Sig. Gen.	\$1,250
40-A Sig. Gen.	\$2,000
48A Sig. Gen.	\$2,000
22A Sig. Gen.	\$200
20B Sig. Gen.	\$85
32-B N.F.M. Noise Field Mtr	\$275

MARINE ELECTRONICS

Raytheon RD-132 A.D.F. 200-400 kc and 2.3-mc	\$450
AN/ARN-44 A.D.F. 200 kc to 3.5 mc	\$750
RCA CR-101, 103, 104 radars	
Bendix MR-2-3 radars	
Emergency hand, generator operated radios 2-6 mc 6-10 watts output. Phone & c.w.	\$350
U.H.F. VHF 243 & 121.5 mc Handi Talkie aBtt operated waterproof radios on emerg freq.	\$175
VHF 121.5 emerg radios	\$135
Hi-power navy echo sounders and scanning sonars.	

Many other items
Parts or above items

Loads of Tubes, Microwave Plumbing, Parts

WANTED WANTED

AN/GRC-3 thru 8, AN/GRC-9, RT-77, AN/GRC-10, PRC, GRR, TRC, TS, UPM, URM, USM, USM, TEK, H.P., Meas Equipment R-390, R-388, SP-600 Broadcast A.M. FM TV Equipment
You name it

ALL EQUIPMENT GUARANTEED. PRICES ARE
P O S T P A I D
To You in U.S.A. If Returned You Pay Shipping.
TERMS PAYMENT WITH ORDER

TECHNICAL SYSTEMS CORP.

42 W 15th. ST.

N. Y. 11, N. Y. call Ed Charol

CH 2-1949



HUNDREDS and HUNDREDS OF TOP QUALITY SURPLUS ITEMS TO SELECT FROM:

ANTENNAS
AMPLIFIERS
RECEIVERS
TRANSMITTERS
GENERATORS

CONVERTERS
TRANSFORMERS
POWER SUPPLIES
TEST EQUIPMENT
CONTROL BOXES

DYNAMOTORS
INDICATORS
MICROPHONES
TELEPHONES
CONDENSERS

RECEIVERS:

R-394 FM-152 to 172 MC	Used:	\$49.50	
BC-617 FM Tone-30 to 40 MC	New:	24.50	
R-4/ARR-2 234 to 258 MC	Re-Cond:	6.95	
RAX-1 200 to 1500 KC	Re-New:	29.95	
BC-348 200 to 500 KC—1.5 to 18 MC	Used:	89.50	
R-48/TRC-8 230 to 250 MC FM (No meter)	Used:	19.95	
R-23/ARC-5 190 to 550 KC	Used:	12.95	
R-25/ARC-5 1.5 to 3 MC	New:	19.95	
BC-454 3 to 6 MC	New:	19.95	
BC-455 6 to 9 MC	Used:	11.95	
R-77/ARC-3 100 to 156 MC	Used:	22.50	
BC-1206 200 to 400 KC	Used:	9.95	
BC-733 108 to 110 MC	Used:	5.95	
BC-229 200 to 400 KC—2500-7700 KC	Used:	8.95	
R-5/ARN-7 100 to 1750 KC	Used:	18.95	
BC-433G 100 to 1750 KC	Used:	12.95	
MN-26C 150 to 1500 KC	Used:	9.95	
MN-26 LB 200-410, 500-1200 KC—2.9-6 MC	Used:	9.95	
R-156/ARR-16 62.8 to 72.1 MC FM	Used:	16.95	
R-89/ARN-5	Used: \$5.95	R-443/ARN-5	Used: 7.95

TRANSMITTERS:

T-14 FM 40 Watt, 70 to 100 MC	Used:	\$24.95
Wilcox #96 2500 Watt, 2 to 18 MC	Used:	75.00
ART-13 2 to 18 MC	Used:	59.50
BC-604 21 to 27 MC FM	New:	7.95
BC-684 27 to 38 MC FM	Used:	6.95
BC-924 27 to 38 MC FM	New:	12.95
T-14/TRC-1 70 to 100 MC FM	Used:	24.95
BC-1158 53.3 to 95 MC AM	New:	29.95
BC-191 1.5 to 12.5 MC	New:	34.95
BC-230 3000 to 7000 KC	Used:	8.95
T-17/ARC-5 1.3 to 2.1 MC	New:	14.95
T-18/ARC-5 2.1 to 3.0 MC	Unused:	8.95
T-21/ARC-5 5.3 to 7 MC	New:	8.95
T-20/ARC-5 4.0 to 5.3 MC	New:	9.95
BC-459 7.0 to 9 MC	New:	14.95
T-23/ARC-5 100 to 156 MC	Used:	18.95
T-67/ARC-3 100 to 156 MC	Used:	22.95
GP-7 350 to 9050 KC	New:	34.95

RECEIVER-TRANSMITTERS:

RT-58/ARC-12 230 to 250 MC	Used:	\$29.50
BC-745 AM 2 to 6 MC	New:	19.95
LINK 1905-1906 152 to 172 MC FM	Used:	59.50
AN/VRC-4 1.7 to 8.7 MC	Unused:	59.95
RT-19/ARC-4 140 to 144 MC AM	Used:	22.95
BC-1335 27 to 38.9 MC FM	As is Used:	6.95
SCR-522 100 to 156 MC AM	Used:	29.95
BC-645 (Converts to: 435 to 500 MC)	New:	14.95
RU-18 Complete Set, 12 Volts	New:	19.95
RU-19 Complete Set, 24 Volts	New:	19.95

TELEPHONE-TELETYPE-TELEGRAPH:

Model 14 AT Teletype	Used:	\$89.50
Paper Tape 3/8" 900 Ft. Roll 25c—30 for \$3.00—60 for \$5.00		
Telegraph Repeater WE-61824A	New:	39.50
TP-7 Portable Repeater	New:	12.95
TG-30 Telegraph Repeater—Used: \$14.95 or	New:	19.95
TG-31 Telegraph Repeater	New:	16.95
PE-250 Telephone Ringer	Re-New:	7.95
EE-8 Field Telephone	Used:	12.95
BD-71 Switchboard—6 line	Used:	9.95
BD-72 Switchboard—12 line	Used:	18.95
BD-89 Switchboard—20 Mag. & 40 CB lines	Used:	59.50
BD-95 Switchboard—Cordless	New:	24.95

MICROPHONES:

T-30 Throat Microphone: Used 3/1.00	New:	\$.75
T-45 Lip Microphone: Used @ 65c ea.	New:	1.00
RS-38 Microphone Button only	New:	1.50
T-17 Microphone Carbon: Re-Cond: \$5.95	New:	7.95
T-26 Microphone Carbon: Used: \$1.00	New:	1.75
T-24/M Microphone Carbon	New:	4.95

RECTIFIERS-POWER SUPPLIES:

RA-87 Rectifier for Teletype	New:	\$ 8.95
RA-62 AC Power Supply for SCR-522	Used:	59.50
PP-855/PRC-14 6 Volt DC Pow. Sup.	New:	4.95
PP-18/AR 12 VDC to 28 VDC 1.5 Amp.	New:	7.95
BC-603/683 AC Power Supply: Kit \$10.00—Wired:		14.95
R-77/ARC-3 AC Power Supply: Kit \$15.00—Wired:		19.95
BC-923 AC Power Supply: Kit \$16.00—Wired:		20.95
BC-652 AC Power Supply: Kit \$15.00—Wired:		19.95
AC Power Supply with Speaker—Command Receivers BC-348, 342, 344, 429, & RAX: Kit \$15.00—Wired:		18.95

DC SUPPLIES:

All operate from 115 Volts 60 cycles:

DUAL OUTPUT—12/14 or 24/28 VDC @ 6 Amps—Parts Kit: \$20.00—Wired Complete:	\$24.95
OUTPUT—12/14 VDC @ 6 Amps. Size: 5 1/2 x 9 1/2 x 5"—Parts Kit: \$14.00—Wired Complete:	\$18.95
OUTPUT—24/28 VDC @ 4 Amps. Size: 5 1/2 x 9 1/2 x 5"—Parts Kit: \$13.00—Wired Complete:	\$17.95
OUTPUT—12/14 VDC @ 4 Amps. Size: 5 1/2 x 9 1/2 x 5"—Parts Kit: \$10.00—Wired Complete:	\$14.95

AMPLIFIERS:

AM-26/AIC—4 Tubes	Used:	\$3.9
AM-203/ARA-19—3 Tubes	New:	3.9
AM-142/AIC—1 Tube	Used:	1.2
TCS-CMX50L28 2/12A6 Tubes	New:	2.9

INDICATORS:

T-9 TRACKER RADAR—5" CR	Used:	\$27.9
ID-169/APN-12 Radar Range 3"	Used:	9.9
ID-80/APA-17 Radar Range 5"	New:	16.9
R-61/ARQ-5 Panoramic Rec. 5" 18 to 80 MC.	New:	49.5
GPA-23 Monitor Scope 3"	Used:	12.9
24360 Foundation—5" Scope	Used:	5.9

CODE EQUIPMENT:

TG-34 Keyer—Code Practice	Used:	\$24.9
TG-10 Keyer—Code Practice	Used:	14.9
VO-3 Code Oscillator	Used:	12.9
MX-333/GG Code Tape Puller	New:	12.9
Blank Paper Tape 3/8" 900 Ft. Rolls 25c ea. 30/\$3 60/\$6		

HANDSETS:

TS-9 Butterfly switch	Used: \$2.95—Re-Cond:	\$ 3.9
TS-13 Butterfly switch w/PL-55/PL-68	Used:	4.9
	New:	6.9
H-22/U Butterfly switch w/PL-55/PL-68	Used:	4.9
D170312 Sound Powered	New:	7.9

HEADSETS:

HS-33 Headset: with chamois cushions	New:	\$ 7.9
	with rubber cushions	New: 6.9
HS-23 Headset: with chamois cushions	New:	6.9
	with rubber cushions	New: 5.9
Chamois Cushions only		1.5
Rubber Cushions only		1.0
HB-7 Headband only for HS-33/23	New:	3.0
ANBH—1 Element only for HS-33	New:	3.0
H-63 Headset with Boom Microphone	Used:	3.9
HS-30 Headset—Hearing Aid Type: Used 75c	New:	1.0

SEND FOR BIG FREE CATALOG TODAY!

Address Dept. 73 • All Prices F.O.B., Lima, O. • Minimum Order \$5.00 • 25% Deposit on C.O.D.

FAIR RADIO SALES • P.O. Box 1105 • LIMA, OHIO

TESTED 10 WATT



ZENERS

\$1.49 EA.

- 5V
- 6V
- 12V
- 20V
- 24V
- 42V
- 45V
- 60V
- 70V
- 80V
- 90V
- 100V
- 110V
- 124V

2 FOR 2.75

15 Amp Cartwheel DIODES

SILICON	PIV	Sale	<input type="checkbox"/> 250	79c
AXIAL	<input type="checkbox"/> 50	39c	<input type="checkbox"/> 250	39c
LEADS	<input type="checkbox"/> 150	55c	<input type="checkbox"/> 400	\$1.15
	<input type="checkbox"/> 200	69c	<input type="checkbox"/> 600	\$1.59

150 WATT IGNITION TRANSISTORS

2N1907 ONLY \$1.47

By "Texas"
20 Amps
Freq. 15MC
PNP - TO3

Base Voltage 100

\$1

ANNIVERSARY DOUBLE BONUS

FREE \$25.00 GIFT PAK Check Here

Radio, TV Parts. Add 25c for handling

PLUS

CHOOSE ANY \$1 ITEM FREE

BOTH "GIFTS" FREE WITH \$10.00 ORDERS

SILICON NPN



MESA

85 WATTS

2N424

\$1.00

WORTH \$42.00

TESTED TRANSITRON SCRs

	PRV	7 AMP	15 AMP	25 AMP
<input type="checkbox"/>	50	1.00	1.25	1.75
<input type="checkbox"/>	100	1.50	1.95	2.95
<input type="checkbox"/>	150	—	2.25	3.15
<input type="checkbox"/>	200	—	2.75	3.45
<input type="checkbox"/>	250	—	2.95	3.62
<input type="checkbox"/>	300	2.69	3.19	3.75
<input type="checkbox"/>	350	—	3.50	4.25
<input type="checkbox"/>	400	—	3.95	4.95



Sale - "TEXAS"

Imagine 20 WATTS in TO5 case. Like 2N1039, 2N1040, etc. with built-in heat sink.

NOW 4 for \$1*

*Sale till July 15th

FACTORY TESTED SEMI-KON-DUCTORS

- 1—SILICON NPN "PLANAR" 2N718, TO18 case. \$1
- 6 TOP HAT RECTIFIERS, 750 mil, 400 volts. \$1
- 2—500 MC PNP MESA TRANSISTORS, TO18 case \$1
- 20 WATT NPN SILICON MESA 2N1648 tr'sistors \$1
- 1—2N705 MESA 300 mc, 300 mw, pnp, TO18. \$1
- 2—25-AMP SILICON STUD RECTIFIERS. \$1
- 6 TRANSISTOR RADIO SET, osc-ifs-driver, p-p. \$1
- 4 2N35 NPN TRANSISTORS, TO22 case. \$1
- 2 'MESA' 4-WATT TRANSSTRS, npn, silicon, TO5. \$1
- 15 UPRIGHT SILICON DIODES, worth \$40. \$1
- HOFFMAN SATELITE SILICON SUN CELL, 3/8x1" \$1
- 4 GENERAL ELECTRIC 2N170 RF NPN transistors \$1
- 5 GENERAL ELECTRIC 2N107 PNP transistors. \$1
- 3 ONE WATT ZENERS, 6V, gold, axial. \$1
- 2 40-WATT TRANSISTORS, 2N174 style, TO36. \$1
- 25 SEMI-KON-DUCTORS: transistors, diodes, rect. \$1
- 3 2N255 PWR TRANSISTORS, or equal, TO3 case \$1
- 5 SUN BATTERIES TO 1 1/2" sizes, lite sensitive. \$1
- 1 3N35 TETRODE 150mc transistor, silicon. \$1
- 3 CBS 20-WATT TRANSSTRS, pnp, stud, 2N1320. \$1
- 2—2N341 NPN SILICON TRANSISTORS, 1 watt \$1

3-TRANSISTOR SUBMINIATURE

AMPLIFIER 1.95

* Only 3" x 2" x 3/4" * Wired * Printed Circuit * Complete with Transistors

- 15 CBS GERMANIUM DIODES, 1N34 equals. \$1
- 15 NPN TRANSISTORS, asst types and cases. \$1
- 15 PNP TRANSISTORS, asst types and cases. \$1
- 10 FAMOUS CK722 TRANSISTORS, pnp. \$1
- 2 CBS 35W PWR TRANSSTRS, 2N1434, pnp, stud. \$1
- 10 NPN SWITCHING transistors, 2N440 equals. \$1
- 4 SUBMINIATURE 2N131 TRANSTRS, rf-if, pnp. \$1
- 4 CK721 TRANSTRS in new aluminum case, pnp. \$1
- 20 TOP HAT RECTIFIERS, 750 mil, silicon untest'd \$1
- SILICON PLANARS: 2N497, 2N498, each. \$1
- 2 TRANSITRON 1N429 ZENER REFERENCES. \$1
- 10 2-AMP SILICON POWER RECTIFIERS, stud. \$1
- 1 85W SILICON PWR TRANSTR, npn, like 2N1212. \$1
- 3 2N243 750 MW NPN SILICON trans'tors, TO22. \$1
- 6 ZENER DIODES, upright styles, assorted. \$1
- 4 2N43 OUTPUT TRANSISTOR EQUALS, pnp, TO5. \$1
- 6 "TEXAS" 750 MA 400V EPOXY DIODES. \$1
- TEXAS 20-WATT, TO5, heat sink stud, 2N1042. \$1
- 6—2N408 RCA OUTPUT TRANSISTORS, pnp, TO1. \$1
- 10 PNP SWITCHING TRANSISTORS, 2N1303, etc. \$1
- 4 2N117 TRANSISTORS, npn silicon, TO22. \$1
- 2—2N1264 UHF TRANSISTORS, 300 mc. \$1

10c FOR OUR "SUMMER" BARGAIN CATALOG ON:

- Semiconductors
- Poly Paks
- Parts

WORLD'S MOST POPULAR \$1 PARTS PAKS

- 10 PHONO PLUG-n-JACK SETS, tuners-amps. \$1
- 30 MOLDED COND., black beauty, mylar, vit-Q. \$1
- 10 TANTALUM ELECTROLYTICS, worth \$15. \$1
- 60 HI-Q RESISTORS, 1/2, 1, 2W to 1 meg, 5% too. \$1
- 100 ASST. HALF WATT RESISTORS, 5% too. \$1
- 35 ALLEN BRADLEY & IRC TWO WATERS. \$1
- 50 COILS & CHOKES, rf-if, osc-peaking-etc. \$1
- \$25 RADIO-n-TV SURPRISE, wide variety. \$1
- 10 TRANSISTOR ELECTROLYTICS, 10 to 100mf. \$1
- 50 RADIO & TV KNOBS, asstd. colors, styles. \$1
- 10 VOLUME CONTROLS to 1 meg, switch too. \$1
- 50 MICA CAPACITORS, to .01mf, silvers too. \$1
- 30 POWER RESISTORS, to 50W, to 24 Kohms. \$1
- 10 PANEL SWITCHES, rotary-micro-slide-power. \$1
- 60 TUBE SOCKETS, receptacles, audio, etc. \$1
- 40 DISC CONDENSERS, 27mmf to .05mf to 1KV. \$1
- 60 TUBULAR CONDENSERS, to .5mf to 1KV. \$1
- 50 ONE WATERS, resistors, asstd values, 5% too. \$1
- 30 PRECISION RESISTORS, 1/2, 1, 2W, 1%. \$1
- 1—INFRA-RED PARABOLIC REFLECTOR & FILTER. \$1
- 1—INFRA-RED PHOTO DETECTOR TRANSDUCER. \$1
- 4 TRANSISTOR TRANSFORMERS, asst, worth \$25. \$1
- 3 'TINY' V. CONTROLS, w/sw. 2K, .5meg, 1meg. \$1
- 40 SUBMINIATURE COND., to .05mf, cerafil too. \$1
- 40 WORLD'S SMALLEST RESIST., 5% too, 1/10W. \$1
- 4 TRANSISTOR TRANSFORMERS, worth \$25. \$1
- 60 CERAMIC CONDENSERS, discs, npo's to .05mf. \$1
- 30 "TEXAS" PRECISION RESISTORS, to 2W, 1%. \$1
- 10 ELECTROLYTICS, FP & tubulars, to 500 mf. \$1
- 3 SUBOUNCER TR'STOR tr'sformer, input, output. \$1
- 2 SENSITIVE RELAYS, 6500 OHM, 2-mil, SPST. \$1
- 3 MERCURY SWITCHES, 115 VAC SPST. \$1



ANNIVERSARY SPECIAL SILICON POWER DIODE STUDS

Amps	Volts	Sale	Amps	Volts	Sale
<input type="checkbox"/> 6	50	15c	<input type="checkbox"/> 35	200	1.85
<input type="checkbox"/> 6	100	29c	<input type="checkbox"/> 50	25	1.50
<input type="checkbox"/> 6	200	37c	<input type="checkbox"/> 50	50	1.95
<input type="checkbox"/> 6	400	59c	<input type="checkbox"/> 50	100	2.95
<input type="checkbox"/> 6	600	69c	<input type="checkbox"/> 25	100	3.75
<input type="checkbox"/> 6	800	89c	<input type="checkbox"/> 25	200	2.15
<input type="checkbox"/> 6	1000	95c	<input type="checkbox"/> 25	300	2.59
<input type="checkbox"/> 12	50	49c	<input type="checkbox"/> 25	400	1.95
<input type="checkbox"/> 12	100	69c	<input type="checkbox"/> 25	600	2.50
			<input type="checkbox"/> 35	50	1.25
			<input type="checkbox"/> 35	100	1.49
			<input type="checkbox"/> 200	100	4.95

POLY PAKS

TERMS: send check, money order, include postage—avg. wt. per pak 1 lb. Rated, net 30 days. CODs 25%

P.O. BOX 942A
SO. LYNFIELD, MASS.
"PAK-KING" OF THE WORLD



HEWLETT PACKARD

540A Transfer Oscillator	325.00	400A VTVM	69.00
211A Square Wave Gen. Like New	225.00	712B Power Supply	195.00
212A Pulse Gen. Like New	300.00	417A New	250.00
400H VTVM New	195.00	AC-4 Plug-in Decade Counters	20.00
400C VTVM	100.00	805 Slotted Line	200.00

GENERAL RADIO



620A Frequency Mtr 300kc-300mc	275.00	760A Sound Analyzer	125.00
544B Meg Ohm Bridge	175.00	761A Vibration Analyzer	175.00
1450 TBR Decade Attenuator	250.00	1602 Admittance Mtr	95.00
1604B Comparison Bridge	200.00	1231B Amplifier & Null Dector	150.00
561D Vacuum Tube Bridge	200.00		



TEKTRONIX

511AD Scope	225.00	121 Wide Band Pre Amp.	95.00
511AD Rack Mount	225.00	161 Pulse Gen	75.00
512 Scope	250.00	190A Sig Gen	175.00
513D Scope	425.00	190A Sig Gen Rack Mount	175.00
514AD Scope	395.00	180S1 Time Mark Gen.	300.00
517 Scope	750.00		

DUMONT



304A Scope	125.00	336 Scope	325.00
304H Scope	125.00	279 Dual Beam Scope	195.00
350R Scope	225.00	322 Dual Beam Scope	275.00
303A Scope	125.00	404R Pulse Gen	225.00
324R Scope	195.00	330 Switch	75.00



MILITARY TEST EQUIPMENT

TS375A VTVM	65.00	OS8E/U Scope New	125.00
PSM4C VOM New	69.00	CM 21 Frequency Mtr New	75.00
PSM4A VOM	50.00	TS107A/TPM1 Wave & Power Mtr	150.00
URM 25 D Sig Gen 10kc-20mc	325.00	UPM-19c SG76A Pulse Gen	P.U.R.
URM 26 A Sig Gen 4-408mc	275.00	TS155c/up Sig Gen 80-2600mc	150.00
URM 26 B Sig Gen 4-408mc	325.00	TV-10 Tube Tester New	150.00
ME11/U RF Watt Mtr	95.00		

MISC TEST EQUIPMENT

Stoddart Noise & Field Strength Mfr's		Sanborn Recorder Mod 150 (#152-100A)	
OCA 100-420mc	195.00	with 2 DC Pre Ampl #150-1800 & #287-1800	
NMA-5A 15-125mc	250.00	1 Coupling/DC Pre Ampl #150-1300	
Brush Recorders BL 201	75.00	1 AC/DC Pre Ampl #150-1000	
BL 202	125.00	1 Servo Monitor Pre Ampl #150-1200	
Amplifiers BC 913	100.00	1 Multi Marker #E-1848-600	
BL 923	125.00	3 Power Supplies #284-400	
Ballantine 300 VTN	79.00	2 Power Supplies #150-400	
220A Decade Amp	50.00	in original cabinet in New to	
Boonton "Q" Mtr 160A	275.00	Excellent Cond	\$1500.00
"QX" Checker 110A	125.00	Berkey Digital Printer Mod 1450	250.00
Ferris Microvolter 18-C	95.00	Hughes Memo Scope Mod 103	750.00
Measurements Square Wave Gen Mod 71	95.00	Hughes Memo Scope Mod 104	850.00
Phazor Phase Mtr Mod 200 AB	150.00	Potter Frequency-Time Counter Mod 840	250.00
P.R.D. Broad Band Oscillator 705	75.00	Shallcross Percent Limit Bridge 621H	125.00
Broad Band Oscillator 706	75.00	Sierra Frequency Selective Voltmeter Model 125B	550.00
Sweep Freq Osc. 907	125.00	Gas Engine Generator (Miniature 12 Powers)	
Universal Klytrow P/S 801A	275.00	115 VAC-300 watts	NEW
Standing Wave Amp. 275	125.00	and 12 VDC-Battery Charger	65.00
Universal Power Bridge 650B	125.00		

RECEIVERS - TRANSMITTERS

NC-300	179.00	Transmitter T-401/FR 1.5 to 26mc 2500 watts	
SP-600 JX	350.00 to 750.00	5D22 Drives 5762 Final	1500.00
R390A 500kc to 32mc	975.00	ARC-5 2.1-3mc	
URR-13 200 to 400mc	250.00	Transmitters 3-4mc New	
URC-4 New with Cables	49.00	4-5.3mc Your	
		5.3-7mc choice	9.95

COMPONENTS - ACCESSORIES

High Voltage (Sylvania) New Probe G-30kv	\$1.95	Tubes 807	1.10
Tektronic Scope Probes New	4.95	811A	3.89
Mallory Miniture Power Supply Input 1.5v (Pen Lite		813	8.95
Cell) Output 1650v @ 350ma	1.49	866	1.50
Meter 3" 0-300 VDC	2.89	5R4GY	.90
GE Scope Transformer (Compact)			
Pri 115v-60r	1.49		
Sec 1350 5 mils			

We Buy and Sell Military & Commercial Test Equipment, Communication Equipmt., Components, Tubes, Transistors. Large or Small Lots, FAIR PRICES.

Satisfaction or Money Back Guarantee
All Prices FOB Hempstead, N. Y.

COMMUNITY ELECTRONICS INC.

372 FULTON AVE.


HEMPSTEAD, LONG ISLAND, N. Y.

IVanhoe 5-0055

COLUMBIA GEMS!

RBB & RBC COMMUNICATIONS RECEIVERS

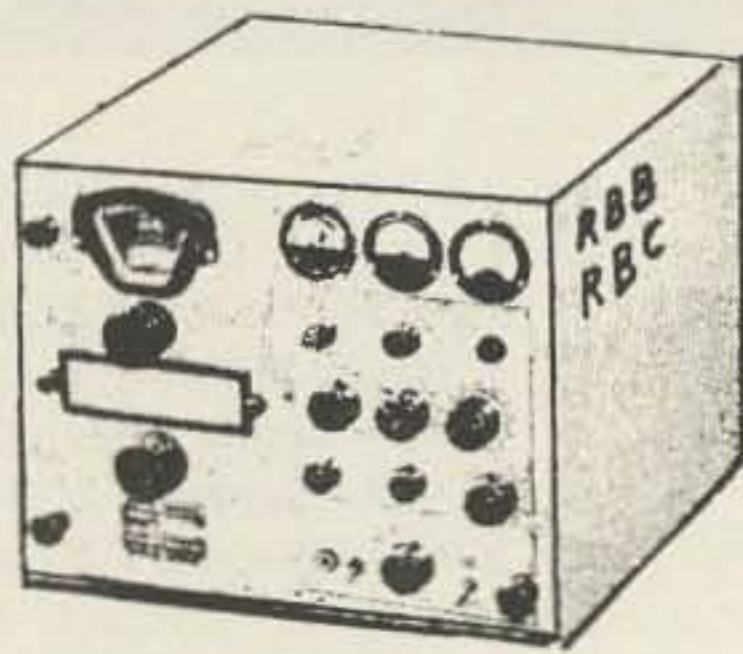RCA for Navy use. Sensitive and stable freq. range RBB 500 kc to 4mc RBC 4-27 mc in 4 bands. Tube line up 6SK7 1st RF. 6SK7 2nd RF. 6AB7 Oscillator.



6AB7 1st Det., 3-6SK7 IF amps. 6AB7 BFO. 6H6 AVC. 6H6. Noise Limiter, 6SK7 1st AF. 6SK7 Squelch, 6AB7 2nd AF. 6K6 Output. 5U4 Rectifier, VR-105 Regulator IF Freq. 400kc power input 110v. AC. 60cps. has following controls: Tuning, RF Input. AF Output, Selectivity 3 Positions, Squelch, MVC, CW, AVC, Ant. Trimmer Direct Reading Freq. Dial and Logging Scale. Input & Output DB Meter & V Meter

Receivers Below Checked Out
RBB Receivers with pwr supply Ex. Cond. \$75.00
RBC Receiver with pwr supply 95.00

Model RBA

Almost same as above but tunes 15-600kc in 4 bands. Direct reading. Uses sensitive TRF circuit: Ideal for labs wishing to receive the new NBS station on 60kc. Same size as RBC. With pwr supply, checked out Ex. Cond. \$95.00

COMMAND RECEIVERS

R-23/ARC-5 Rec. 190-550 kc \$14.95 Ex. Con.
R-25/ARC-5 Rec. 1.5-3 MC 19.95 New
R-26/ARC-5 Rec. 3-6 MC 12.95 Ex. Cond.
R-27/ARC-5 Rec. 6-9.1 MC 12.95 Ex. Cond.
R-28/ARC-5 100-156 MC 22.50 Ex. Cond.
Spinned Knobs 95c ea. Ex. Cond.
12V. Dynamotor for ARC-5 MC 4.95 New

COMMAND TRANSMITTERS

T-18/ARC-5 2.1-3MC \$6.95 New
T-19/ARC-5 3-4MC 8.95 Ex. Cond.
T-20/ARC-5 4-5.3 6.95 New
BC-457 4-5.3 6.95 New
BC-458 5.3-7 4.95 Ex. Cond.
MD-7/ARC-5 Plate Mod. 5.95 Ex. Cond.
BC-456 Screen Mod. 3.95 Ex. Cond.




A. R. C.
190-550KC
Q-"5 ER"
MODEL R-11A
(28V)

\$14.95

Late Model
Excellent Condition

**ARC-MODEL R-22 (28 V)
BROADCAST COMMAND RECEIVER**
550-1500 KC LATE MODEL
LIKE NEW **\$24.95**

THERMADOR POWER XFMR

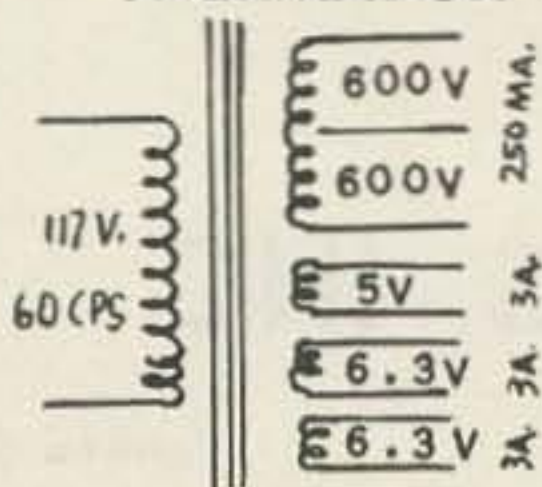

Fully
Enclosed
Upright
Mounting

\$8.95

BRAND NEW!

Send us a list of what you have we will make you the best deal in the country.

Columbia Electronics

4365 W. PICO BLVD.
LOS ANGELES 19, CALIF.

TRANSMITTING TUBES




NEW	Fully Guaranteed	NEW
2C39A/7289 \$9.95	4CX300A 18.50	
4-65A 9.95	810 14.95	
4-125A 19.95	811-A 5.95	
4-400A 24.95	813 12.95	
4X150A 7.95	866-A 2.25	
4CX250B 19.95	872A 5.95	
	304-TL 29.50	

O-16/ART-13

COLLINS P.T.O. LOW FREQUENCY OSCILLATOR

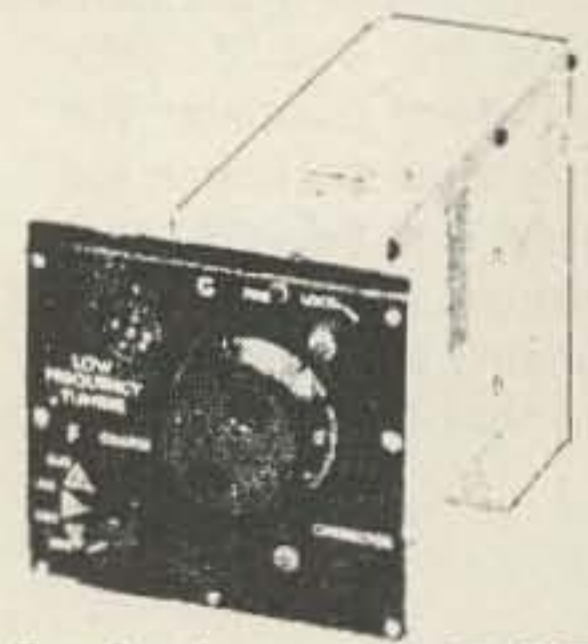A high stability permability tuned oscillator using a 1625 tube. Covers 200 to 1500KC in 6 bands with a 20 turn dial (100 increments per turn) and turn counting dial.



Ex. Cond **7.95**




TELETYPE RECEIVING AUDIO CONVERTER

Northern Radio
Frequency Shift
Converter Type 152.

Sold less frequency determining network. You can use standard 88 MC toroids. Complete with tubes & power supply for Loop. Input 110/1/60cps. Size: 3 1/2 x 8 1/2. With conversion info.
Ex. Cond. **\$49.50**

NORTHERN RADIO TYPE 153 TELETYPE TONE KEYS

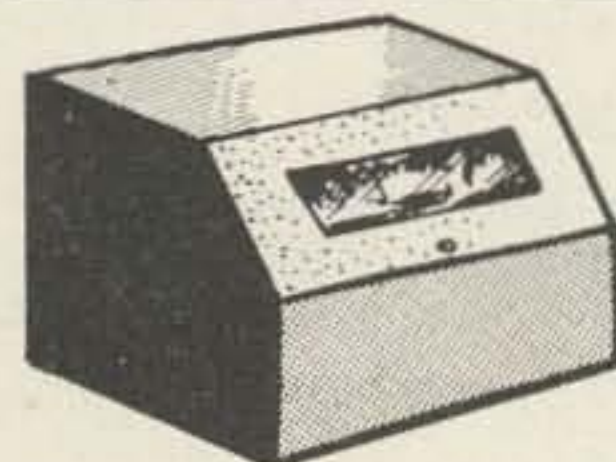Less frequency determining network. Use your own toroids. Same photo as type 152. Ex. cond. **\$39.95**
With conversion info



Late Model
TELETYPE
14FRXD T.D. &
Reperferator
Combo

Features Sync.-Motor, creep head T.D. See Feb. 1964 CQ for more details. This unit replaces the older type T.D. and model 14 Reperferator and it saves space. Ex. Cond. Non Typing. Not Tested \$65.50
Ex. Cond. Typing Not Tested 75.00
Add \$25 for overhauled and guaranteed units.

NAVY QRM FILTER

1020 cycles. Same as the FL-8 but more elaborate. With cord and PL55 and switching control on slant panel for easy viewing. **\$1.95**



WE WANT TO BUY YOUR SURPLUS EQUIP. WE NEED

BC-610, E, H & I, ARC-27, 34, R-388, 390, SP-600, High quality Test Equipment Commercial and Military.

Radar Principles - Simplified

Gordon Hopper W1MEG

Although radar is not one of the forms of communication generally used by radio amateurs, the author feels that amateurs should have a "speaking acquaintance" with this very important and fascinating phase of electronics. Possibly reading this article may capture your interest enough to cause you to investigate in detail what makes a radar "tick." In any case, we hope that this article will clear up some of the questions you may have had about radar.

Introduction

The word RADAR is made up by extractions from the phrase "RADIO Detection and Ranging." Basically, radar is the application of radio principles to detect unseen objects and to determine their direction and range. In special types of radar, elevation and speed may be indicated also.

Radar is one of the greatest scientific developments to come out of World War 2. Its basic principles are relatively simple, and the seemingly complicated circuits can be resolved into a series of functions that, when taken individually, will afford identification and understanding.

Basic Principles

The basic principle of radar operation is dependent on creating (transmitting) and picking up (receiving) an echo. A radar transmitter emits powerful, short bursts of rf energy. Some of this energy will strike objects within the range of the transmitted signal and be reflected back to the radar receiver. It is possible to determine the distance of the object causing the reflected signal to return by carefully measuring the time required for the energy to go to the object and to return, and then translating this information into a measure of distance.

Sound echoes or wave reflection is the principle used in radar operation. If a person shouts in the direction of a sound-reflecting surface 2200 feet away, he will hear his shout return in about 4 seconds. If a directional de-

vice was built to transmit and receive sound, the principles of echo and a knowledge of sound velocity could be used to determine the distance, the height, and the direction of an unseen object.

All radar sets work on principles much like these in the preceding paragraph except that a radio wave of extremely high frequency is used instead of a sound wave. The radar set transmits a short pulse of rf energy and receives its own echo signal, then transmits another pulse and receives these echoes. Depending on the design of the radar set, this cycle is repeated 60 to 4000 times each second. If the energy is sent into clear space, there will naturally be no returning echoes and the energy is lost. If the energy strikes an object such as a building, ship, airplane, or hill, some of the energy will be reflected back to the radar's antenna and receiver. If the object is large, a strong echo (but only a fraction of the radiated energy) is returned to the antenna. If the object is small, the echo will be weak. Radar waves travel at the speed of light, approximately 186,000 land miles per second or approximately 162,000 nautical miles per second. Radar signals have been directed to the moon and their echoes have been received approximately $2\frac{1}{2}$ seconds later.

Because radar utilizes the uhf and the shf bands, the energy will travel in a straight line with very little effect from the earth's atmosphere. Consequently, there is a very short time interval between the transmission of a radar pulse and the reception of its echo. It is possible to measure the amount of elapsed time to an accuracy of one ten-millionth of one second (1×10^{-7} seconds). The forming, timing, and presentation of these pulses are accomplished by special circuitry and devices.

The antennas used by a radar set are designed with a sharply defined beam. When a signal is being received, the antenna will be rotated until the received signal is maximum. The direction of the target (object) is then determined by the position of the antenna.

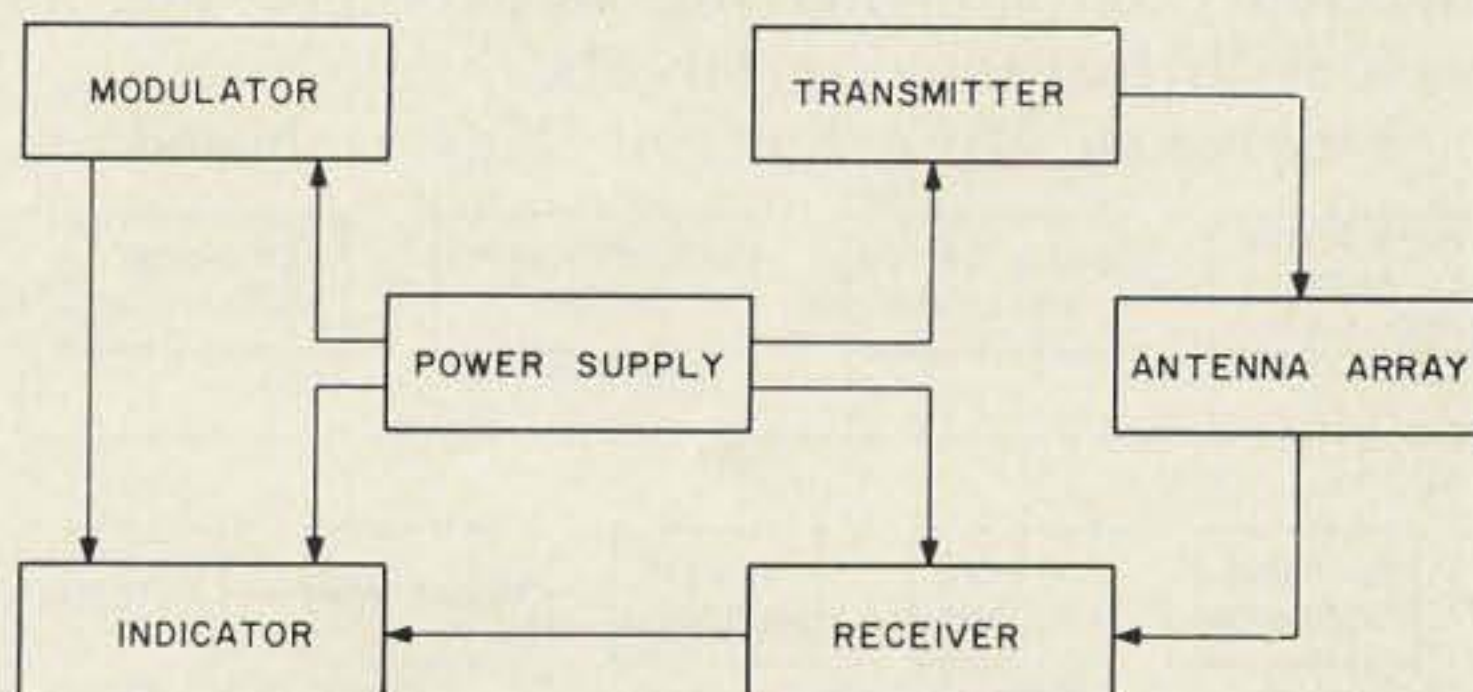


FIGURE 1

Fundamental elements of a radar system

The echoes received by the radar receiver are observed on an oscilloscope (built as part of the radar) as marks of light. This scope may be calibrated in miles, yards, or degrees. A radar operator can tell the bearing and range of a target by the position of the echo on the scope indicator.

Azimuth is the relative horizontal direction of a target with respect to some particular direction reference expressed in degrees. Elevation expresses the angular degrees that the target is above or below the radar set. Both azimuth and elevation must be considered in determining the direction of a target. The determination of both azimuth and elevation depend upon the directional characteristics of the radar antenna.

Types of Radar Systems

There are several radar systems in current use, each with major differences between them. They are the frequency modulation system, the frequency shift system, and the pulse modulation system (most commonly used today.)

Frequency Modulation System. Because each cycle of a frequency-modulated wave differs by a small increase in frequency from the others of that wave, a frequency-modulation system makes it possible to identify each cycle of the transmitted wave and to recognize it from all others when it returns to the receiver. If a transmitter is designed to produce a signal which regularly changes over a known range of frequencies, it is possible to identify any particular reflected signal cycle. Two separate signals are fed to the receiver and, when mixed, produce a beat note. The frequency of the beat note varies directly with the distance to the object, increasing as the distance increases. A device that measures frequency can be calibrated to indicate range (distance to object). A measurement of the difference in frequency between the transmitted and reflected energy determines the presence and speed of a moving target. The frequency-modulation system works well with stationary or slow-moving targets but not as well with fast-moving targets.

Frequency Shift System. This is based on

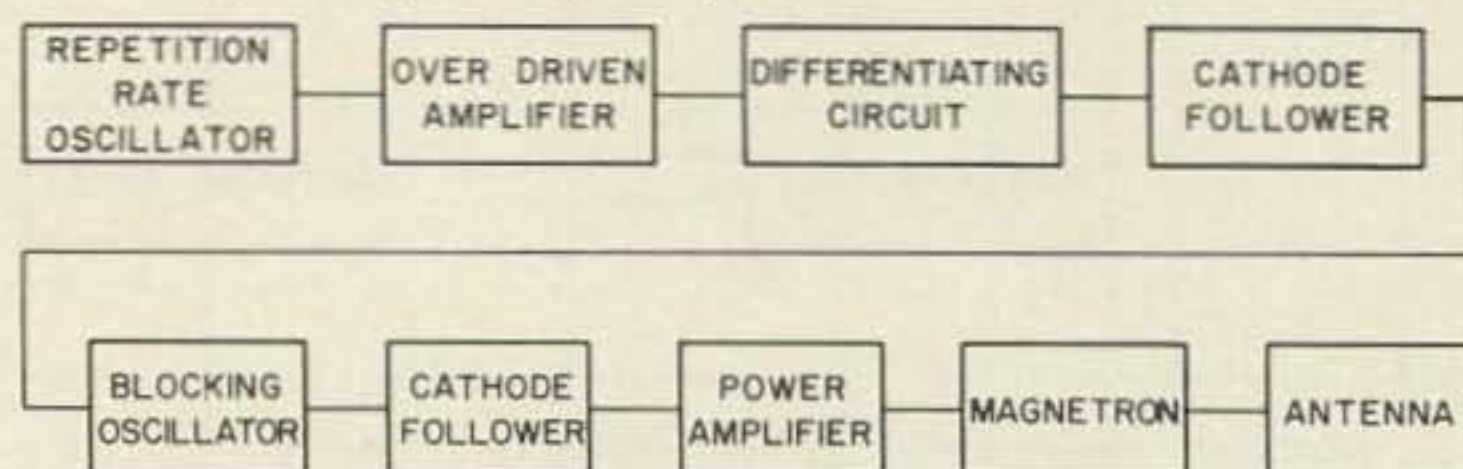


FIGURE 2

Simplified block diagram of a modulator and Transmitter

the Doppler effect. If the source of radio energy (an aircraft from which radio waves are reflected) is moving rapidly, the frequency of the echo return signal will change provided that the object is moving toward or away from the receiving antenna. The circling of an aircraft (or cross-wise movement) will not change the frequency. The amount of frequency change is proportional to the speed at which the object is moving toward or away from the receiving point. The detector in the receiver responds to the difference in frequency. If the object is not moving, or if it is moving crosswise, the detector response is zero. In a mountainous area where the echo return signals are stronger than the echo return signals from an aircraft, the frequency shift principle is sometimes combined with a pulsed radar system. The moving objects are differentiated from the stationary ones, the stationary objects are eliminated, and the operator sees only the moving objects. In this type of system, the frequency shift detector device is supplementary equipment attached to the radar set and is called a moving target indicator.

Pulse Modulation System. Most radar sets employ the pulse system of deflection. In this system, the transmitter is turned on for short periods and off for long periods. When the transmitter is on, it radiates a short burst of energy called a pulse. This pulse will strike an object, part of the reflected energy is returned to the receiver, and is displayed on a cathode-ray tube. As the transmitter is turned off after every pulse, it does not interfere with the receiver. Complete location of an object in space depends on the range or distance of the target from the antenna and the direction including both the azimuth and elevation directions. The primary purpose of a radar set is its ability to measure distance in terms of time. In useful terms for radar, radio waves travel one nautical mile in 6.2 microseconds, or one radar mile (out and back) in 12.4 microseconds. If a pulse of energy was transmitted toward a target and the echo returned 620 microseconds later, the distance of the target would be 50 miles.

$$\frac{620}{12.4} = 50 \text{ miles}$$

In the pulse system, the time duration of the pulses may vary from 0.1 to 50 microseconds. If the transmitter is turned off before the reflected energy returns from the target, the receiver can distinguish between the transmitted pulse and the reflected pulse. After the reflections have returned, the transmitter can

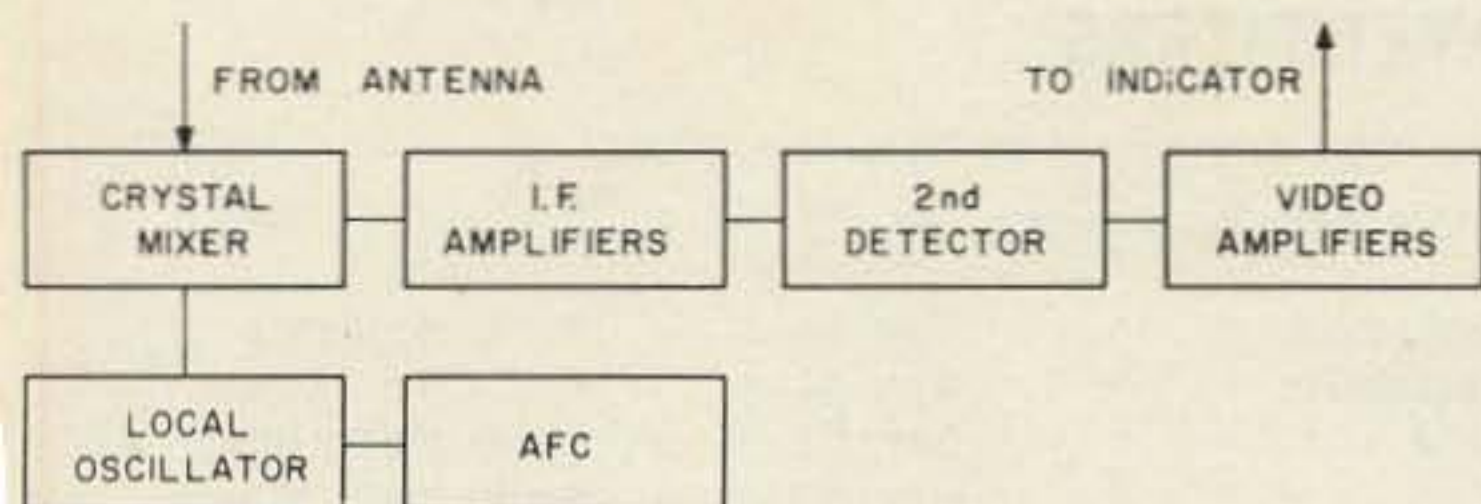


FIGURE 3

Simplified block diagram of a radar receiver

be turned on again and the process repeated. The receiver output is applied to an indicator that measures the time interval between the transmission of the energy and its return as a reflection.

Fundamental Radio Concepts

The fundamental elements of a radar system consist of the transmitter, modulator, antenna, receiver, indicator, and power supply. A functional diagram of a simple radar system is shown in Figure 1. Figure 2 shows a simplified block diagram of a transmitter and modulator and Figure 3 shows a simplified block diagram of a receiver.

The transmitter provides extremely high-power pulses of rf energy for a very short time. The frequency must be very high to allow many cycles to get into the short pulse.

The modulator produces the synchronizing signals that trigger the transmitter the required number of times each second. It triggers the indicator sweep and coordinates the other associated circuits.

The antenna is very directional and usually is a dipole used in conjunction with parabolic reflectors. Ordinarily, one antenna is used for both the transmitter and the receiver and a switching device is used to connect it to the transmitter when a pulse is radiated, and to the receiver during the interval between pulses. The antenna is a rotatable array and continually searches for targets within its range.

The receiver is usually a superheterodyne type, is very sensitive, and is capable of accepting signals within a 1 to 10 megacycle bandwidth. It presents video pulses to the indicator.

The indicator presents necessary information to locate a target on the indicator screen. The method of presentation is called "scan." There are about 15 types of scan used in radar receivers but the most common ones are: type A, B, PPI, and E.

The power supply furnishes all ac and dc voltages to the radar system.

Certain parameters are associated with all radar systems. These parameters consist of

carrier frequency, pulse-repetition frequency (PRF) (the number of pulses sent out each second), pulse width (in microseconds), and power relation (relationship of peak and average power).

The carrier frequency is the frequency at which the rf energy is generated.

The range of a radar set depends upon the pulse-repetition rate provided the power is sufficient. For example, if the repetition rate is 250 pulses per second, the period of time is $\frac{10^6}{250} = 4000$ microseconds. At 12.4 microseconds per mile, the range will be $\frac{4000}{12.4} =$ approx. 322 miles.

The minimum range at which a target can be detected is determined largely by the width of the transmitted pulse. For example, a pulse width of one microsecond will have a minimum range of 164 yards. A target within this range will be blocked out on the indicator. For radar navigation work, the pulse width is normally in the order of 0.1 microsecond. For long range work, the pulse width is normally from 1 to 5 microseconds.

The transmitter's useful power contained in the radiated pulses is called peak power. The transmitter's average power is low compared with the peak power. The greater the pulse width, the higher will be the average power. The longer the pulse-repetition time, the lower will be the average power. Duty cycle is the fraction of the total time that rf energy is radiated. This is represented as

$$\text{duty cycle} = \frac{\text{pulse width}}{\text{pulse-repetition time}}$$

High peak power is desirable to produce a strong echo return and low average power is desirable to keep the equipment compact.

Summary

Throughout the years that radar has been in use, it was pioneered and developed primarily by the various military services. In addition to being used by the military, it is used by civilian organizations for:

1. Determination of vehicle speeds on highways,
2. Radar weather prediction,
3. Commercial air navigation, and
4. Safeguarding aircraft and merchant ships from collision hazards.

Radar equipments are grouped into many classes, but in general it can be said that some of the classes are air search, surface search, fire control, identification, ground and carrier-controlled aircraft approach, range rate or speed, and height finding. . . . WIMEG

INDEX TO ADVERTISERS

To aid you in finding ads which are not running in this issue we have listed the last ad run by each company in 73.

Oct. 63	Aaron	Mar. 64	Gavin Instruments	May 64	Radio Bookshop
51	Adcom	Mar. 64	Gem Electronics	Apr. 64	Radio Ham Shack
Jan. 64	Adirondack	102	Glass, J. J.	Apr. 63	Radio Industries
Oct. 63	A & F Electromart	45	Gonset	Nov. 63	Radio Publications
Sept. 63	Alco	104	Goodheart	May 64	Rand
Mar. 64	Alcom	91	Graham Radio	May 64	Ready Radials
Oct. 63	Alden	Jan. 64	Groth	60, 72	Redline
114	Algeradio	Nov. 63	Grove	Sept. 63	Reed
Sept. 63	Allied	Aug. 63	Ham Trader	June 63	Rex
88	Alltronics-Howard	May 64	Hallicrafters	87	Reyco
79	Amateur Elect. Supply	5	Hammarlund	Apr. 63	Ritco
Feb. 63	Amateur Radio Exchange	Nov. 63	Harrington	Apr. 64	Roberts
Nov. 63	Amber	Mar. 63	Harrison, Ivan	43	Fohn
July 63	American Crystal	89	Hayden	Nov. 63	Rowe
May 63	Amperex	May 64	HCJ	Dec. 63	R & S
Apr. 64	Amplidyne	36	Heath	91	RW Electronics
87	Amrad	109	Hefron	Sept. 63	Sams
Nov. 63	Antenna Specialists	47	Henry	35	Saxton
Apr. 63	Arrow Electronics	Apr. 64	Hi-Par	Feb. 63	Schober
June 63	Arrow Sales, Cal.	111	Hi-Way	81	Scientific Assoc.
110	Arrow Sales, Chi.	Oct. 63	Holstrom	Apr. 64	Seatronics
87	Atlantic	Aug. 63	Howard	25	Sideband Engineers
Oct. 63	Badges	Nov. 63	Hunter	Apr. 63	S. J. Electronics
Sept. 63	Bald Eagle	Mar. 64	Hy Gain	Mar. 64	Skylane
99	BC Electronics	Jan. 64	Identoplate	Mar. 64	Slep
87	Bell	May 63	Instructograph	108	Space
Apr. 64	Best	3	International Crystal	Feb. 64	Spitz
Oct. 63	BF	Feb. 64	Irving Electronics	Nov. 63	Sprague
Oct. 61	British Radio	Oct. 63	Jays	May 64	Squire-Sanders
57	Burghardt	117	Jeffronics	June 63	Star
71	B & W	Nov. 63	Johnson	90	Subscriptions
Apr. 64	Byron Airpack	Jan. 63	Kar-Tenna	Apr. 64	Super-Q
23	Callbook	Nov. 63	Kniper	May 64	Surplus Spec
Aug. 63	Candee	Mar. 64	Knox	Cover II	Swan
115	C & H	Sept. 63	KTV Towers	116	T A B
July 63	Charter Oak	June 63	Ladd	Feb. 63	Technical Manuals
21	Clegg	63	Lafayette Radio	17	Technical Materiel
Apr. 64	Cleveland Institute	Apr. 64	Lawrence Eng	119	Technical Syst.
July 63	Collins	51	Linear Systems	106	Telemarine
124	Columbia	Apr. 64	L R Electronics	Feb. 64	Telemethods
May 63	Columbia Products	Apr. 64	Mach	49	Telrex
May 64	Comaire	67	Madison	Apr. 63	Tepabco
11	Cornell-Dubilier	July 63	Maps	27	Texas Crystal
Jan. 64	Coral Cliffs	41	Master Mobile	Feb. 64	Thermoelectric D.
Jan. 64	Cubex	Apr. 64	McCoy	May 64	Topaz
13	Cushcraft	100	Meshna	May 64	Transistors Ult.
Jan. 64	Dames	May 64	Metro	Jan. 64	Trans Pro
Apr. 64	Dayton Hamvention	May 63	Metrodynamics	Nov. 63	Trice
Apr. 63	Delta	May 64	Midwest	Nov. 63	Tri-Ex
May 64	Denver Crystals	June 63	Miller	June 63	Tri-State
113	Denson	85	Mini-Products	48, 77	Tucker
Apr. 64	Dow Key	61	Mission	Aug. 63	United
87	Dow Radio	49	M & M	Feb. 63	US Crystals
9	Drake	Jan. 63	Mor-Gain	May 64	U. T. C.
Mar. 63	Ebco	Nov. 63	Mosley	Apr. 63	Valley
Apr. 64	Editors & Engineers	Cover IV	National	48, 49, 77	Vanguard
Feb. 63	Ed-U-Cord	Apr. 64	Newark	Oct. 63	Verns
Mar. 63	Electro-com	May 63	New Products	July 63	Versatronics
June 63	Electronic Servicecenter	Aug. 63	Newtronics	Feb. 63	Vesto
May 64	Electronic Specialists	July 63	North American	89	V & H
Oct. 63	Emrad	Feb. 64	Northwest	77	VHF Associates
May 64	Epsilon Records	Dec. 62	Nortronics	Jan. 63	Vibroplex
71	Evans	Aug. 63	Ole's	77	Viking
Feb. 64	E-Z Etch	May 63	Out-O-Door	Oct. 63	WA6DUW
4	E-Z Way	Jan. 64	Ontario	25	Waters
120	Fair	June 63	Palmer	Sept. 63	Webster
July 63	Fairbrother	85	Parks	∞0	Western (Calif.)
49	Fichter	Jan. 64	Pauls Surplus	∞0	Western (Neb.)
29	Finney	Mar. 64	Pausan	Jan. 64	Wildcat Press
112	F-M	Apr. 64	P & H	49	Woodruff
Apr. 64	FM Ham Sales	Apr. 64	Petrilak	Cover III	World Radio Labs
Aug. 63	Foreign Projects	121	Poly-Paks	Apr. 62	Zalytron
81	Foreign Subs	Mar. 63	Polytronics	90	73 Subscriptions
89	Fulton	81, 85, 118	Propagation Products	May 64	73 Products
87	Gain, Inc.	July 63	QTH MAPS	May 64	73 Parts Kits
64	Galaxy	91	Quaker	May 64	6 Up
Feb. 63	Gam	59	Quement		

~~\$1585~~

Up to now you've had to pay at least \$1585 for a commercial grade 2 KW amplifier. No longer. The brand-new National NCL-2000 maximum kilowatt is only \$585, including its built-in power supply. Up to now most amplifiers in the price range of the NCL-2000 have been 500 watt jobs, usually using a whole string of low power tubes straining to deliver a peak kilowatt. Not now. The new NCL-2000 is a real brute of a desk-top amplifier for the 80 through 10 meter bands that was designed from power supply to output tubes to loaf along at a "D.C." kilowatt . . . 2000 watts PEP input and 1300 watts of peak output into your antenna on any band. Operate CW? AM? RTTY? The National NCL-2000 is rated for full kilowatt operation in these services.


The output tubes in the NCL-2000 are a pair of RCA 8122 ceramic tetrodes designed specifically for high power SSB service, and 800 watts of available plate dissipation assure low distortion, linear operation at full output. The NCL-2000 utilizes a passive, untuned grid circuit, so that it may be adjusted to allow excitation to full output from any transmitter or transceiver providing from 20 watts to 200 watts of peak drive. The passive grid circuit in the NCL-2000

allows its use as a dummy load for easy exciter tune-up with amplifier plate voltage removed!

The National NCL-2000 is a particularly handsome unit . . . styled to complement any ham shack or equipment (of course we think it looks best next to our own NCX-3)! Compare these features with any unit on the market at any price

- one kilowatt average input, 2000 watts PEP on all bands
- may be driven to full output with 20 to 200 watts from the exciter
- ALC output for use with exciters incorporating such provision
- separate plate and multi-meters
- tune-up at 1 KW level to comply with F.C.C.
- built-in dummy load with multi-meter relative power indication for optimum exciter tune-up with amplifier plate voltage removed
- all changeover relays incorporated for use with either transceiver or transmitter-receiver combinations
- automatic switchover to exciter-only when plate voltage is removed
- most complete safety and overload protection, including interlock, automatic shorting bar, time delay and current overload relays
- National's exclusive one-year warranty.

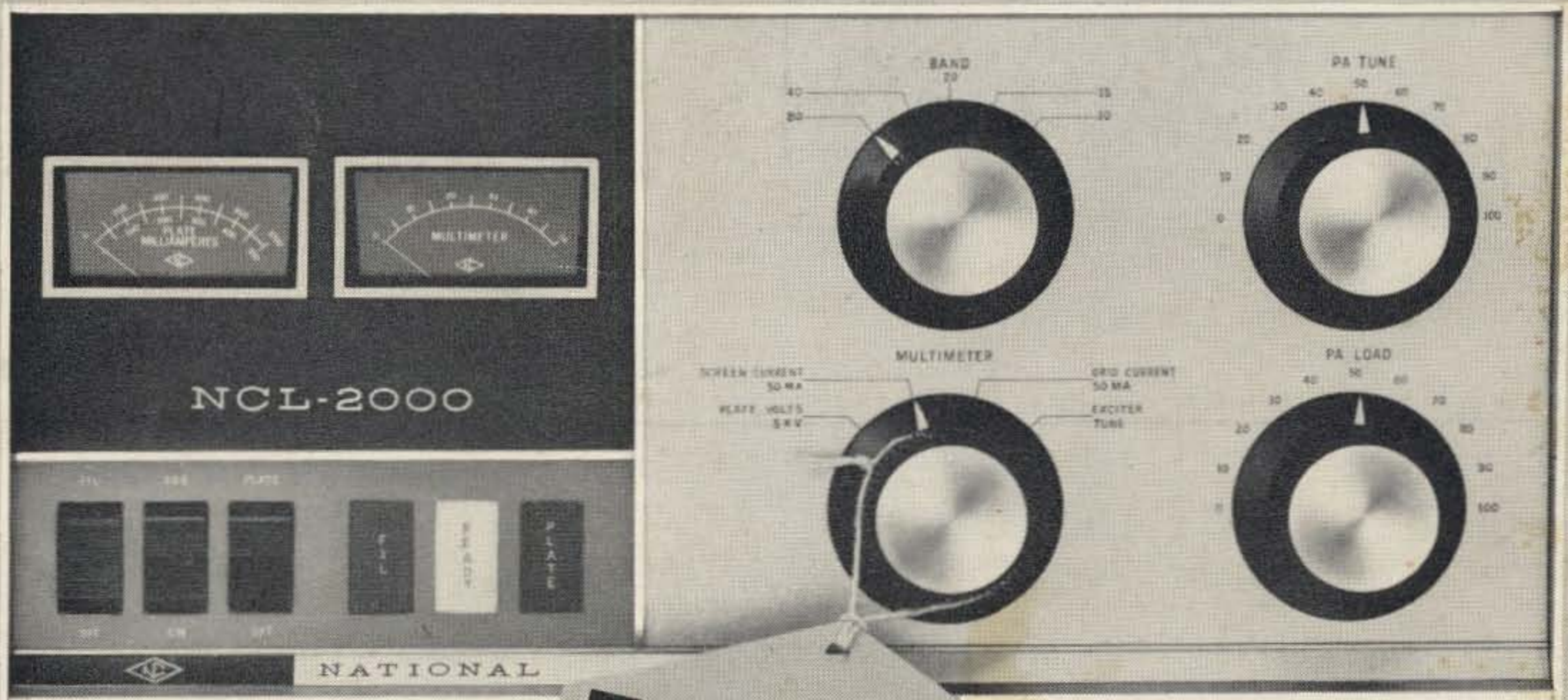Your National Dealer will have the NCL-2000 in June . . . why not call him today to reserve yours for immediate delivery.



**NEW
NATIONAL
2000 WATT
LINEAR
AMPLIFIER**

ONLY \$585

ADDITIONAL NCL-2000 SPECIFICATIONS
Frequency Range: 80 through 10 meter bands plus overlap at band edges. Output Impedance Matching Range: 40-60 ohms. Input Impedance: 50 ohms nominal, unbalanced. Distortion Products: 30-45 db signal to distortion ratio at full rated output. Noise: NLT 40 db down. Ambient Temperature Range: to +45°C. Ambient Humidity Range: to 90%. Altitude: To 8,000 ft. Primary Power: 115/230 V. A. C. 60 cycle single phase, 3 wire, neutral ground, current 15 amperes max. at 230 V. Tube and semi-conductor complement: 2 RCA 8122 output tubes, 13 semi-conductors for rectification and regulation. Size: 7⁵/₈" H, 16¹/₄" W, 12³/₄" D. Weight: 62 lbs.



NATIONAL RADIO COMPANY, INC.

Export: Ad Auriema Inc., 85 Broad St., N. Y. C.; Canada: Tri-Tel Associates, 81 Sheppard Ave., W. Willowdale, Ontario


37 WASHINGTON STREET, MELROSE, MASS. 02176



LEO MEYERSON WØGFQ

IT'S HERE WE'VE GOT IT

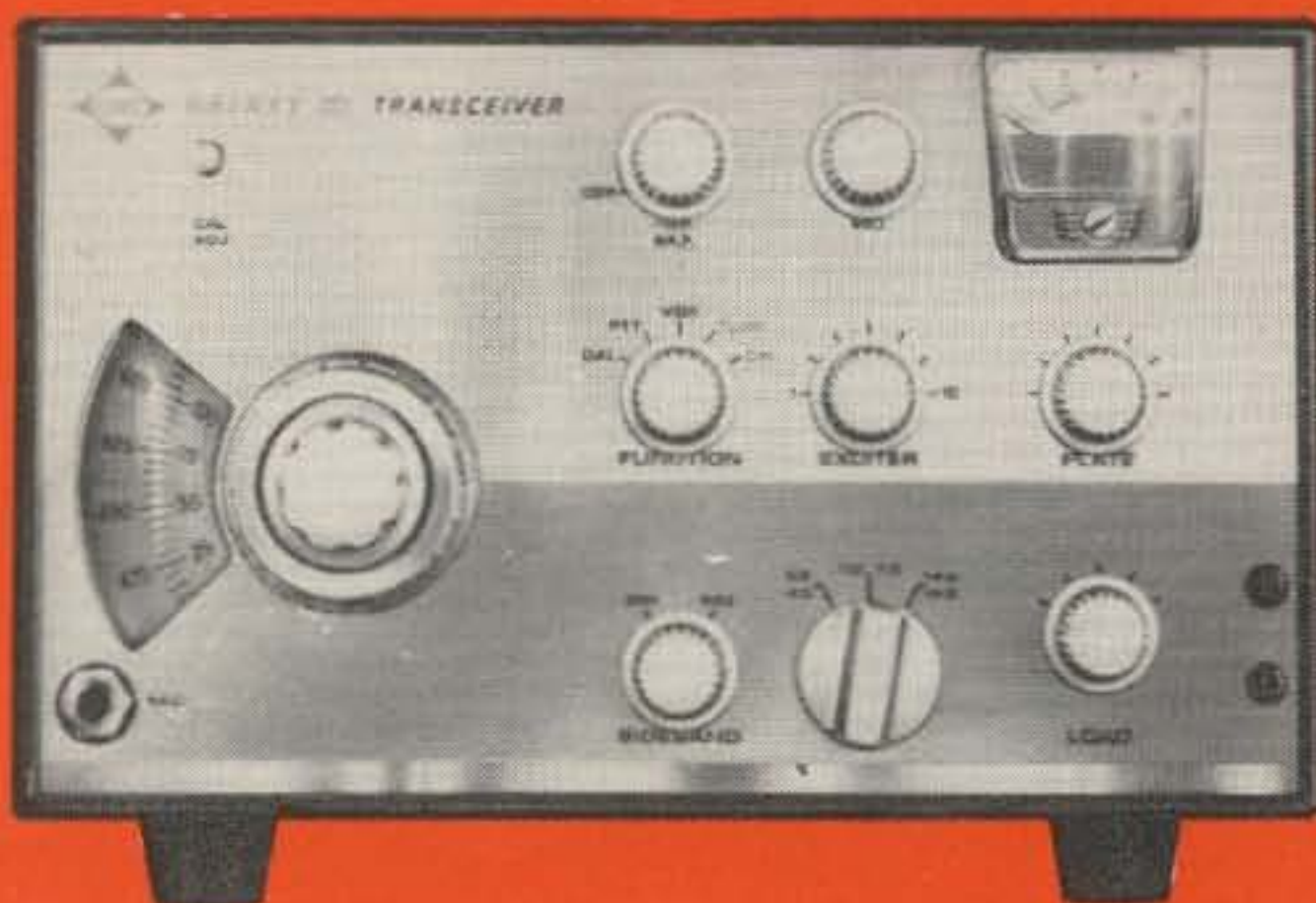THE **NEWEST** MOST POWERFUL— **MOST COMPACT**— FULL
COVERAGE 80-40-20 METER 300 WATT-SSB/CW ANYWHERE!!!
GALAXY III SSB/CW TRANSCEIVER



**NO DOWN
PAYMENT**
ONLY \$17.00 MONTHLY
ON WRL
CHARG-A-PLAN
\$349⁹⁵

THE AMAZING **GALAXY III** IS SO GREAT WE'LL BUY IT
BACK IF YOU'RE NOT COMPLETELY SATISFIED! AND THE
GALAXY III IN ITS ACTUAL SIZE (6x10¹/₄x11¹/₄) IS
SMALLER THAN THIS OPEN MAGAZINE.
TWO-WEEK FREE TRIAL*

*Write for Trial Terms

The Startling Features of the **GALAXY III** prove that it was designed to meet all the require-
ments (including the price) for both the fixed and mobile operators.

Most power-output of any three-band transceiver today; smallest 300 Watt SSB/CW transceiver; full coverage on 80-40-20 meters; SSB upper and lower sidebands; newest and best 6-section crystal filter; highest receiver sensitivity. Shifted carrier CW

eliminates "leap frogging"; hybrid circuitry—transistorized AVC/AUDIO/VOX; dual vernier tuning; handsome styling; modern 4-color brushed aluminum panel. Perforated steel cabinet, hinged top; meter & VFO beautifully illuminated, plus many other features.

**WRITE FOR COMPLETE
DETAILED BROCHURE**

WORLD RADIO LABORATORIES
3415 West Broadway
Council Bluffs, Iowa
Zip Code 51504

WRL WORLD RADIO LABORATORIES
3415 WEST BROADWAY
COUNCIL BLUFFS, IOWA

- Enter order on attached sheet. Send Galaxy III brochure.
- Send trial terms.
- Quote trade allowance on attached sheet.

Name _____ Call _____

Address _____

City _____ State _____