

73

50c
(Not 75c, not even 60c)

Amateur Radio

Amateur Radio Report Card

Public Service **A**

International Good Will **B**

Inventiveness **B**

Activity **A**

DXing **B**

Moonbouncing **A**

FCC **F**



Cush Craft
**VHF AMATEUR
COMMUNICATION
ANTENNAS**

MULTI-POLARIZED TWIST

For tracking, back scatter, Moonbounce
Priced from \$29.50 to \$186.00

PERFORMANCE PROVEN 6 METER BEAMS

3-5-6-10 elements
Priced from \$14.95 to \$49.50

THE BIG WHEEL

Omnidirectional gain antennas
Priced from \$8.95 to \$55.55

COLINEAR ARRAYS

16-32-64 elements
Priced from \$9.85 to \$133.50

MULTI-ELEMENT YAGIS

Single, dual, quad stack arrays
Priced from \$9.75 to \$84.50

SQUALO MOBILE & FIXED ANTENNAS

Omni-directional, horizontally polarized, square
antenna. For car top or base station mounting.
Priced from \$9.45 to \$66.50

MAKE YOURS A REAL SIGNAL . . . use a CUSH CRAFT ANTENNA!

Whether you are Tracking Satellites, Moon Bouncing, DX-ing, Rag Chewing or Winning Contests — you will do it better, more efficiently, and at a lower cost with a Cush Craft Antenna. You will have a signal that really radiates when you buy Cush Craft . . . the antennas with a "PATTERN OF FIRSTS" in Amateur Communications.

Cush Craft

BUY FROM YOUR DISTRIBUTOR
OR WRITE FOR FREE CATALOG

621 HAYWARD ST., MANCHESTER, N. H.

73

Magazine

Wayne Green W2NSD/1

Editor & Publisher

Paul Franson WA1CCH

Assistant Editor

August, 1965

Vol. XXXIV, No. 1

This One Sounds Good— Like a Transmitter Should	W2BHT	6
A fancy name for an article about a 20 watt six meter AM transmitter.		
Going RTTY: Part III	W4RWM	12
The scope monitor.		
Imagineering with Meters	W8BPY	14
Put those miscellaneous meters to good use.		
The EHS Portable Dipole	W9FQN	16
Works from 80 to 6.		
Some notes on Grounded-Grid Linear Amplifiers	K4ZZV	18
And some interesting ideas in a 8072 linear.		
Simplified Solid State	WA2INM/1	24
Simple, easy-to-use, practical ham transistor circuits.		
All Band Tuning for the Drake 2B?	K9LTD	26
Easier and harder than you think.		
When Standard Switches Won't Fit	Ives	28
Making and using odd-ball switching arrangements.		
A CHU Time Receiver	W2LYH	30
In case you don't have a watch.		
Switching with Diodes	K1SDX	34
It's easy—and very useful.		
Improving the Paco GDO	K1AMN	41
And other tube-type grid dip meters.		
Another Way to Measure Noise Figure	K5JKX	44
Hmm. What's the other way.		
The Big Sail	K6MIO	50
The neighborscaring-ist 432 mc antenna you'll ever see.		
Gus: Part IV	W4BPD	62
Now what's he up to?		
The SB-34	W8QUR	68
Sideband Engineers improves their already excellent SB-33.		
A DC Dummy Load	Lyman	70
Here's a use for those tubes you were going to use for lamp bases.		
Quick and Easy Add-on Neutralization	K1CLL	72
In case, unlike most hams, you don't plan ahead.		
Polar versus Solar Beam Orientation	W6TAQ	74
Personally, I use my Boy Scout compass.		
Parallel Resistance Nomogram	WA2BWQ	76
Now all you have to do is find this article when you need it.		
An RF Amplifier for 432	K1CLL	78
Not exactly a 3 db noise figure, but . . .		
The National HRO-500	W2NSD	80
Sigh.		

ADVERTISING RATES

	1X	6X	12X
1 p	\$268	\$252	\$236
1/2 p	138	130	122
1/4 p	71	67	63
2"	37	35	33
1"	20	19	18

Roughly, these are our rates. You would do very well, if you are interested in advertising, to get our official rates and all of the details. You'll never get rich selling to hams, but you won't be quite as poor if you advertise in 73.

73 Magazine is published monthly (thank heavens it's not weekly) by 73, Inc., Peterborough, N. H. Telephone 603-924-3873. Subscription rates \$4.00 per year, \$7.00 two years, \$10.00 three years world wide. Second class postage is paid at Peterborough, New Hampshire and at additional mailing offices. Printed in New Hampshire, U.S.A. Entire contents copyright 1965 by 73, Inc. Postmasters, please send form 3579 to Wood Old 73 Magazine, Peterborough, New Hampshire. Don't forget your zip code when you renew or change your address.

Idiotorial	2	Letters	82, 93
The Eico 720-730	22	Columns	84
Improving RTTY Patterns	43	Caveat Emptor	90
Teletype Tester	60	Propagation	94



The Docket

There is, I am relieved to report, growing pressure to have the FCC put 15928 aside until some sort of study can be made of the whole situation. You can help this movement by sending a letter to the FCC requesting that 15928 be killed outright or that the time for filing comments on 15928 be extended for six more months. It will not hurt one bit if you send this letter via your own personal Senator or Congressman so that he can include a little note of his own when forwarding it to the FCC. The deadline for such a note is July 30th, so you'd better get going.

We've got major troubles fellows, and we're going to have to pull a strain to get out of them. We've got the FCC against us for one thing . . . and that's bad. Even worse, we've got the ARRL against us. That doesn't leave us much, does it?

I can hear you now . . . there goes Wayne Green running down the ARRL again. Who the heck does he think he is? OK, let me tell you who Wayne Green is and what he knows. My ham career started out in Brooklyn almost 30 years ago. I was a teenager on roller skates and I visited every active ham that I could find in Brooklyn . . . I still run into those old

Updating the R-S-T reports.

R means readability.	
R-1 to R-4	Unreadable
R5	Readable with difficulty to armchair copy
S means signal strength.	
S-0 to S8	Too weak to copy or too much QRM to copy
S9	Readable with difficulty
S9-plus	Reasonably readable signal to thunderous signal
T means tone.	
T-0 to T8	Pulses or raw ac note
T9	Rough note or bad chirp
T9X	Anything from absolutely perfect signal to one complete with chirps, thumps, clicks, a bit of hum, buzz, parasitics, etc.

de W2NSD/1

never say diet

timers on the air who remember my visits. I got my ticket in 1940 . . . was active on 160-40-10-2½ meters . . . won the SS contest for my section in 1941 and was extremely active right up to and including December 7th. No one can buffalo me about the old days . . . I was there . . . I know what the hams then knew . . . how little they knew . . . how they built rigs from the Handbook and Radio, but had to call in one of the local "experts" when a 6C5 crystal oscillator wouldn't perk. Sure there were a few complex rigs, but most of the gang were struggling with their 6L6 oscillator modulated by a 6L6. Don't hand me any guff about the technical level of the old timers . . . I was one . . . and I knew the rest of them.

The ARRL in RM-499 claimed that they had detected that we have been going down hill and apparently they have convinced the FCC of this too. My response to 499 was a letter asking the ARRL to give any facts they had to support their claim that something was wrong with amateur radio. They did not answer my request . . . they *can't* answer it for there are no facts to prove this fallacy. On the contrary, all the facts indicate that ham radio is better and more valuable than it has ever been.

Let me get down to brass tacks. One of the biggest complaints we've been hearing is about "appliance operators." OK, I'm an appliance operator . . . my rig is a transceiver, commercially made, even my antenna and tower are commercial products. I don't see any reason to spend the time and effort needed to build a transmitter today any more than the hams of 30 years ago saw any need for building their receivers. But I do build my RTTY converters and whip up anything else special that I need. Between the VHF gang . . . take a look at the July VHF issue of 73 again and see for yourself, the surplus users . . . see our June issue, the RTTY gang, the TV gang, and a dozen or so other gangs . . . plus the fellow


NEW FROM INTERNATIONAL

VHF/UHF UNITIZED TRANSMITTERS 50 mc - 420 mc


International's new unitized VHF/UHF transmitters make it extremely easy to get on the air in the 50-420 mc range with a solid signal. Start with the basic 50 or 70 mc driver. For higher frequencies add a multiplier-amplifier. All units are completely wired. Plug-in cables are used to interconnect the driver and amplifier.



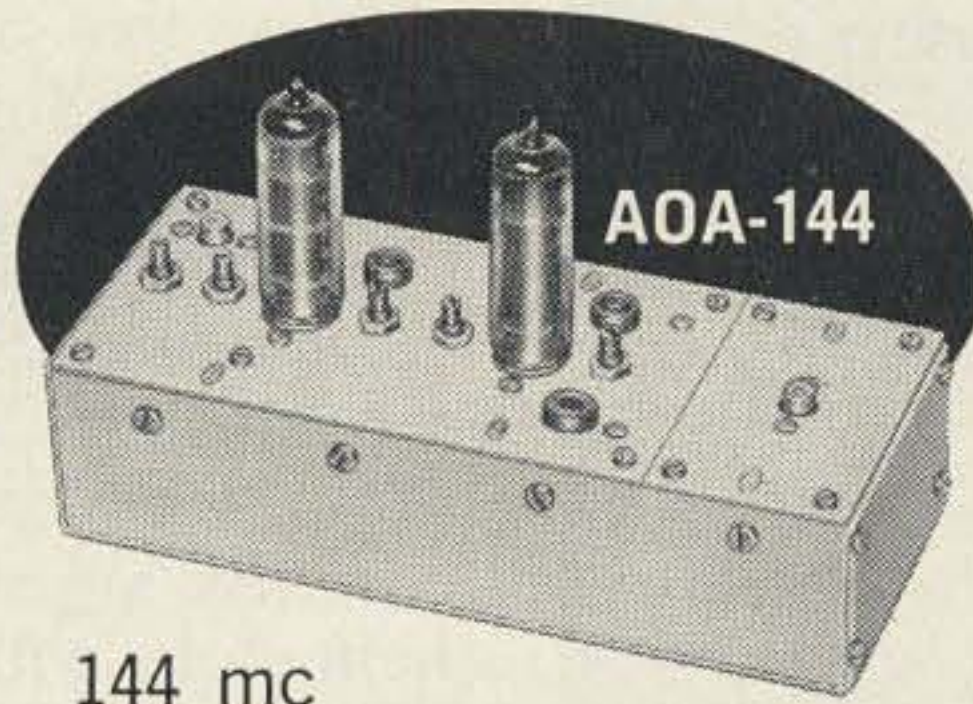
AOD-57
50 or 70 mc
DRIVER/TRANSMITTER
The AOD-57 completely wired with one 6360 tube, two 12BY7 tubes and crystal (specify frequency). Heater power: 6.3 volts @ 1.2 amps. Plate power: 250 vdc @ 50 ma.
AOD-57 complete.....\$69.50



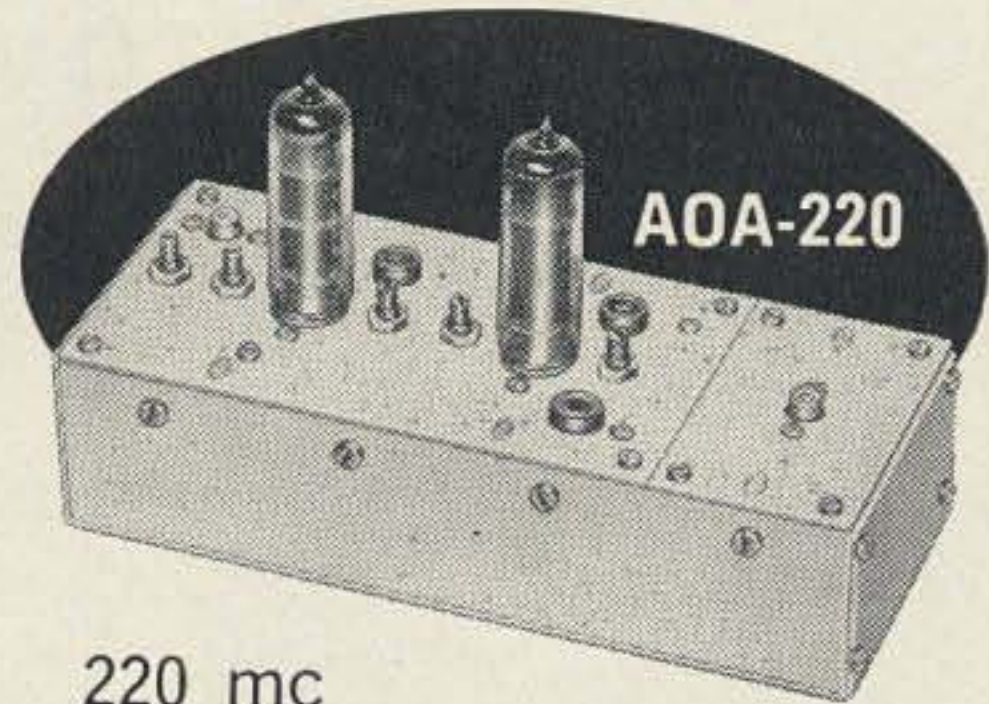AOA-144
144 mc
MULTIPLIER/AMPLIFIER
The AOA-144 uses two 6360 tubes providing 6 to 10 watts output. Requires AOD-57 for driver. Heater power: 6.3 volts @ 1.64 amps. Plate power: 250 vdc @ 180 ma.
AOA-144 complete.....\$39.50



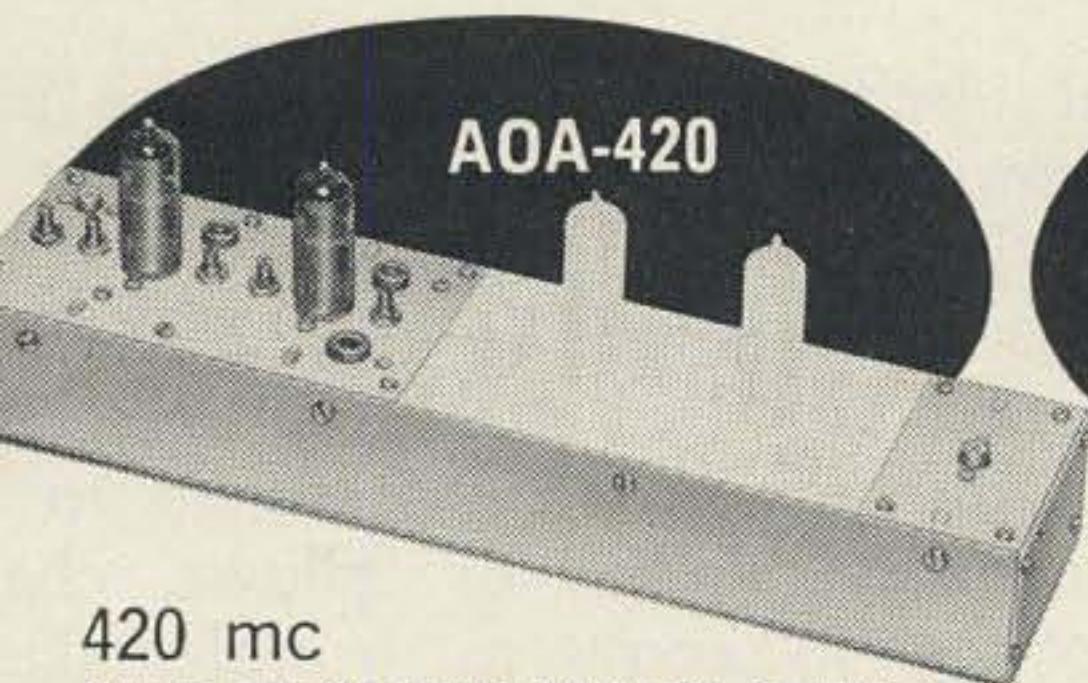
AOA-220
220 mc
MULTIPLIER/AMPLIFIER
The AOA-220 uses two 6360 tubes providing 6 to 8 watts output on 220 mc. Requires AOD-57 for driver. Heater power: 6.3 volts @ 1.64 amps. Plate: 250 vdc @ 150 ma.
AOA-220 complete.....\$39.50




AOA-420
420 mc
MULTIPLIER/AMPLIFIER
The AOA-420 uses two 6939 tubes providing 4 to 8 watts output on 420 mc. Requires AOA-57 plus AOA-144 for drive. Heater: 6.3 volts @ 1.2 amps. Plate: 220 vdc @ 130 ma.
AOA-420 complete.....\$69.50



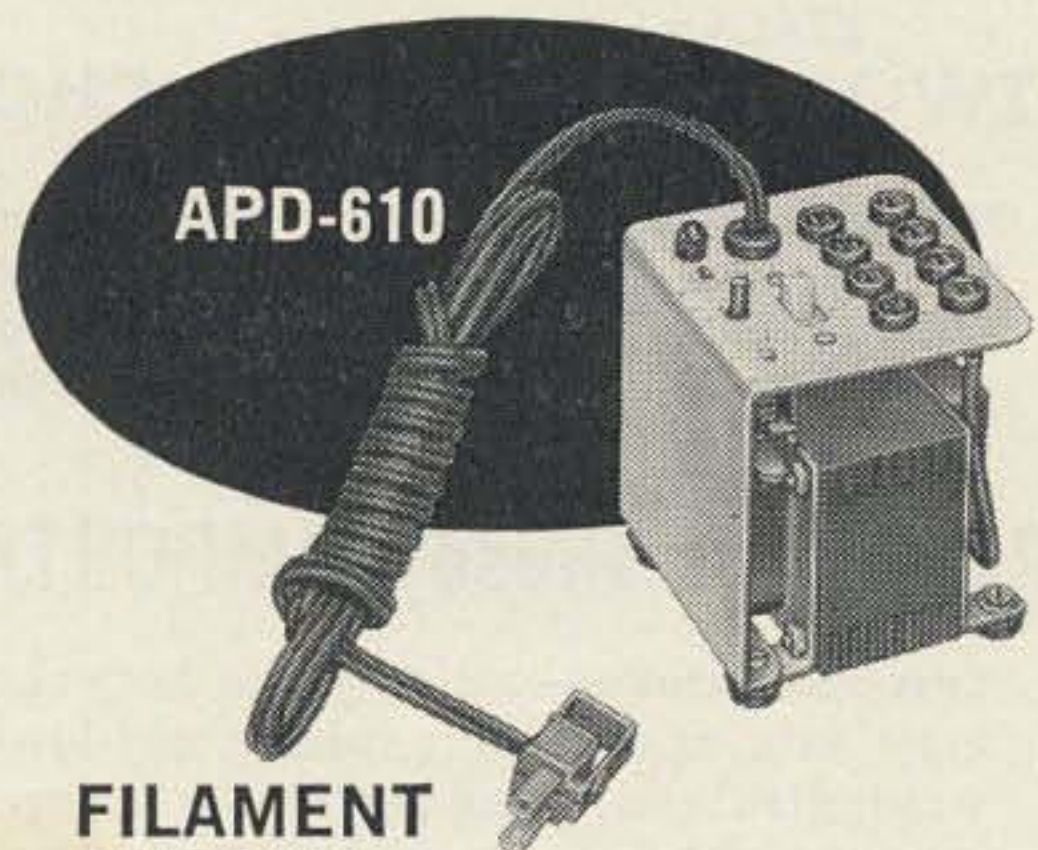ARY-4
RELAY BOX
Four circuit double throw. Includes coil rectifier for 6.3 vac operation.
ARY-4 Relay Box complete\$12.50



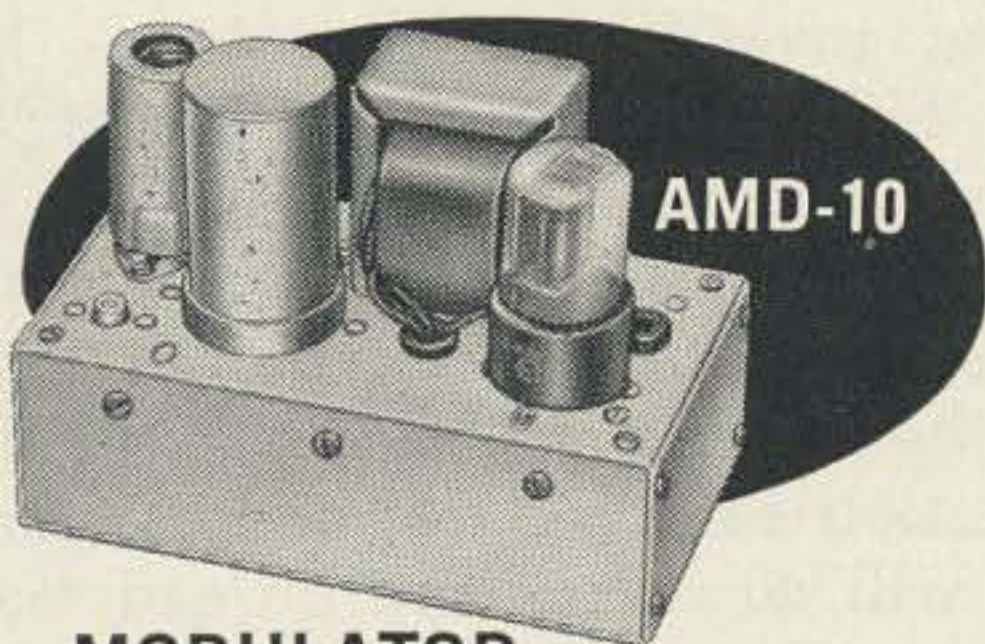APD-610
FILAMENT SUPPLY
The APD-610 provides 6.3 vac @ 10 amperes.
APD-610 complete.....\$9.50



AMD-10
MODULATOR
The AMD-10 is designed as a companion unit to the AOA series of transmitters. Uses 6AN8 speech amplifier and driver, 1635 modulator. Output: 10 watts. Input: crystal mic. (High Imped.) Requires 300 vdc 20 ma, no signal, 70 ma peak: 6.3 vac @ 1.05 amps.
AMD-10 complete\$24.50

COMPLETE TRANSMITTER		
6 METERS	50 mc	AOD-57
2 METERS	144 mc	AOD-57 PLUS AOA-144
	220 mc	AOD-57 PLUS AOA-220
	420 mc	AOD-57 PLUS AOA-144 PLUS AOA-420

**INTERNATIONAL
CRYSTAL MFG. CO. INC.**
18 NORTH LEE — OKLA. CITY, OKLA.

Order Direct
from International

ROHN sets the standard

for
**CRANK-UP
TOWERS**

Why settle
for less
than the best?



K7ASK

TWO CATEGORIES TO CHOOSE FROM

Standard Duty Guyed in
Heights of 37 - 54 - 88 - 105
and 122 feet

Heavy Duty Self Supporting
and Guyed in Heights of
37 - 54 feet (SS)
71 - 88 feet (guyed)

ROHN has these 6 IMPORTANT POINTS:

Ease of Operation—roller guides between sections assure easy, safe, friction-free raising and lowering. **Strength**—welded tubular steel sections overlap 3 feet at maximum height for extra sturdiness and strength. Unique ROHN raising procedure **raises all sections together**—uniformly with an equal section overlap at all heights! **Versatility**—designed to support the largest antennae with complete safety and assurance at any height desired! **Simple Installation**—install it yourself—use either flat base or special tilting base (illustrated above) depending on your needs. **Rated and Tested**—entire line engineered so you can get exactly the right size and properly rated tower for your antenna. The ROHN line of towers is complete. **Zinc Galvanized**—hot dipped galvanizing a standard—not an extra—with all ROHN towers! Prices start at less than \$100.

SEND FOR ROHN TOWER HANDBOOK

—\$1.25 Value

—**ONLY \$100** postpaid (special to readers of this magazine). Nearest source of supply sent on request. Representatives world-wide to serve you. Write today to:



ROHN Manufacturing Co.

P. O. Box 2000

Peoria, Illinois

"World's Largest EXCLUSIVE Manufacturer of Towers; designers, engineers, and installers of complete communication tower systems."

all over the country like Bill Hoisington K1CLL who love to build and design things we are doing just fine. A look at the 1940 ham magazines in comparison to the 1965 will tell you the same story . . . even the average ham today is way way ahead of the average ham of 25 years ago. Way ahead.

I'm not trying to sell you a bill of goods . . . these are facts. Check for yourself. Would you like an experience? Build up something from an issue of 73 and then take it around to a club or two and show what you've done. I'll bet you will find that a number of the club members will ask you questions that will amaze you about your unit. I've had this happen to me too many times . . . and the worst of all are the high school radio clubs . . . some of those kids are incredible. Don't believe me . . . ask anyone that has made the rounds of ham clubs with any kind of technical talk.

If we're all appliance operators then who is that is buying all that surplus gear? I've been trying to get Meshna to run bigger ads and he won't because he is selling all he can handle right now. 85% of our readers say they buy surplus gear and our surplus advertisers back this up with some amazing stories of sales.

OK, what else? Bad manners on the air. Sure . . . I run into 'em now and then. But in all the years I've been operating . . . and at the thousands of stations I've contacted, I've run into darned few bad manners. Somehow every time I do have troubles it seems to be from just a small handful of fellows, chap that I've gotten to know as troublemaker. Unfortunately, we have virtually no way to get these jokers off the air. Bad manners is an exaggerated problem. I've operated from several rare DX spots and almost without exception I've found that everyone was as cooperative as I could ask. When I operated well I got good results, when I goofed it things got messed up . . . and I could take the easy way out and blame myself, but experience has taught me how to handle pileups so that everyone gets worked and everyone is happy . . . when it doesn't work this way for me it is my own fault. I can sympathize with the DX chum who is sitting there dying a slow death waiting for the DX station to stand by and is afraid that the band will go out before he can make the QSO. This can be very nervewracking and lead to chaos if the DX station tries to ignore it . . . bad manners? Baloney.

Hams don't invent things anymore. Yeah. Listen chum, before you start telling anyone

Turn to p. 86.

**from 2
to 160
meters**



relax...
for the **BEST**
in HF and VHF
listening


HAMMARLUND'S NEW HQ-170A-VHF
the only receiver capturing all popular Ham Bands.*

The exciting HQ-170A-VHF is the first and only Ham Band receiver that gives you **everything** you want. Separate NuVistor front ends ($0.3\mu\text{V}$ for 10 db S/N) for both 6 and 2 meters completely eliminates the need for add-on converters or jury-rigged adaptations. Built-in 6 and 2 meter operation employs **matched circuitry** for outstanding performance.

Here is an SSB receiver that combines basic operating excellence with all of the extra features you want to make it a versatile, "fun-to-work-with" unit. Full coverage from 2 to 160 meters, excellent electrical and mechanical stability, expanded vernier tuning and a host of truly incomparable HQ-170A features makes this receiver the new **First Choice** for the amateur fraternity.

The HQ-170A-VHF is the most versatile, and most **complete** amateur band receiver now available on the market—one neat package contains all the flexibility you need—superlative AM, CW and SSB reception on **All** popular amateur bands.

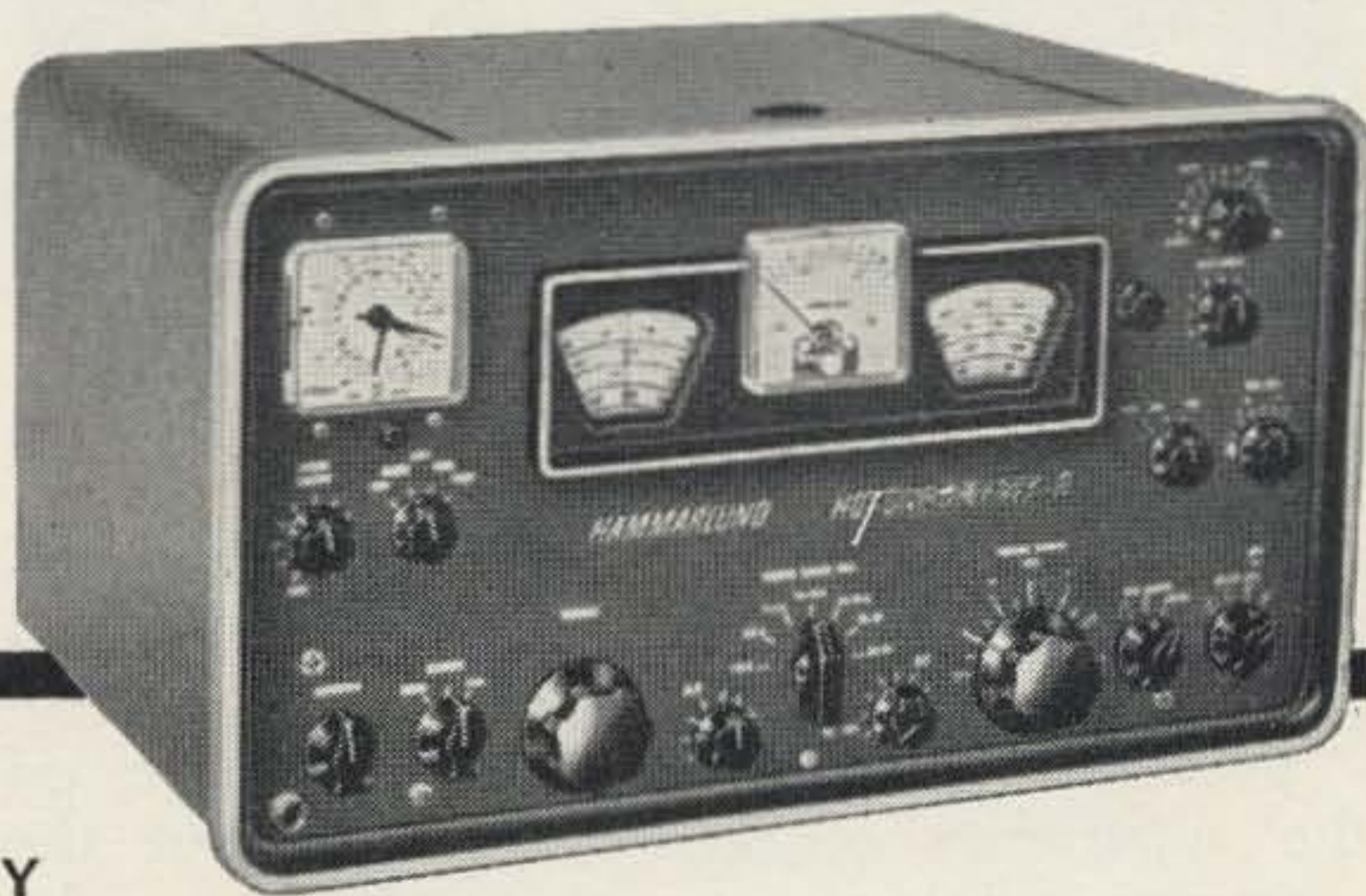Coming soon—Matching transmit accessories
for the Fabulous HX-50.



*Except for the Hammarlund HQ-110A-VHF



HAMMARLUND
MANUFACTURING COMPANY
A GIANNINI SCIENTIFIC COMPANY

73-88 Hammarlund Drive • Mars Hill, North Carolina 28754

I'm interested. Please send HQ-170A-VHF info to:

Name _____
Address _____
City _____ Zone _____ State _____

This One Sounds Good – Like a Transmitter Should

For some reason or other, going mobile has meant spending a good sum of money for a rig that most likely offered three times the features that the average mobile ham needed. Or, if the ham was a build-it-yourselfer, it usually meant sacrificing audio quality or transmitter power or operating convenience. This may have been because of cost, space limitation, or just because no one, aside from a few commercial units, had taken the time to design a quality prototype, field test it for months to remove and bugs, and then re-build the final proven design.

Well, all you potential mobile hams, here is an article on just such a design: a mobile (or fixed-station) transmitter complete with all the features you'd like, the size you need (only 3 inches high), and even where to put each component and wire to assure identical

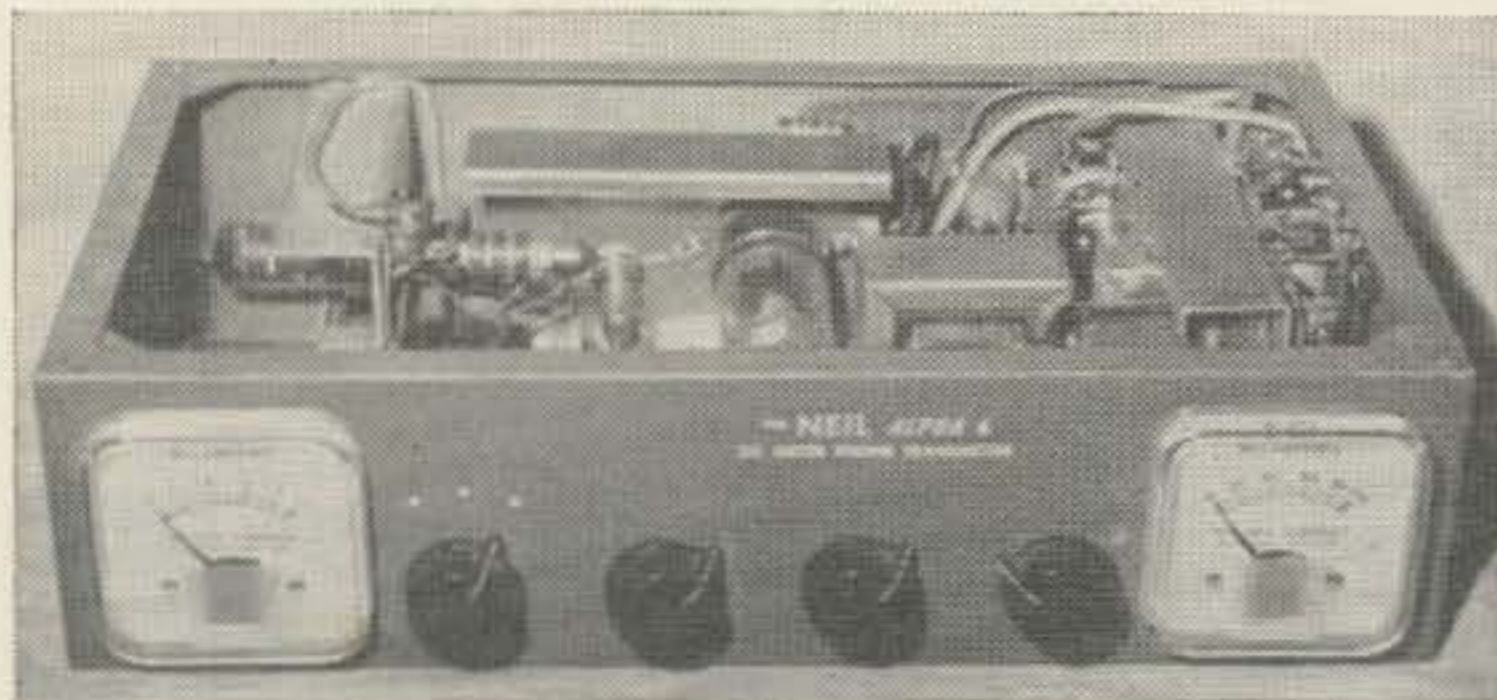


Fig. 2A—Front View: This is the original prototype, and does not have a crystal socket on the front panel.

results with the final prototype, which by the way was field-tested for three years with no breakdowns or operating problems.

It would be easy to write several pages on the superiority of this transmitter, but the outstanding features are that it tunes easily, and it "sounds better." This has been attested to by every signal report we've received. "It's the finest sounding rig we've ever heard," and, "I can't believe you're running only 20 watts—sounds better than any hundred watt rig I've heard." This is characteristic of the glowing reports we've had with this transmitter. And

it happens every time we make a new QSO!

What makes this so? There are no gimmicks, no special components. The answer is that the rf section is *stable*, and a great deal of time was spent in designing and testing the audio section. The audio passband and power were carefully designed to provide superior audio, and were not merely "something" that would modulate the final stage. The speech amplifier is highly filtered, and

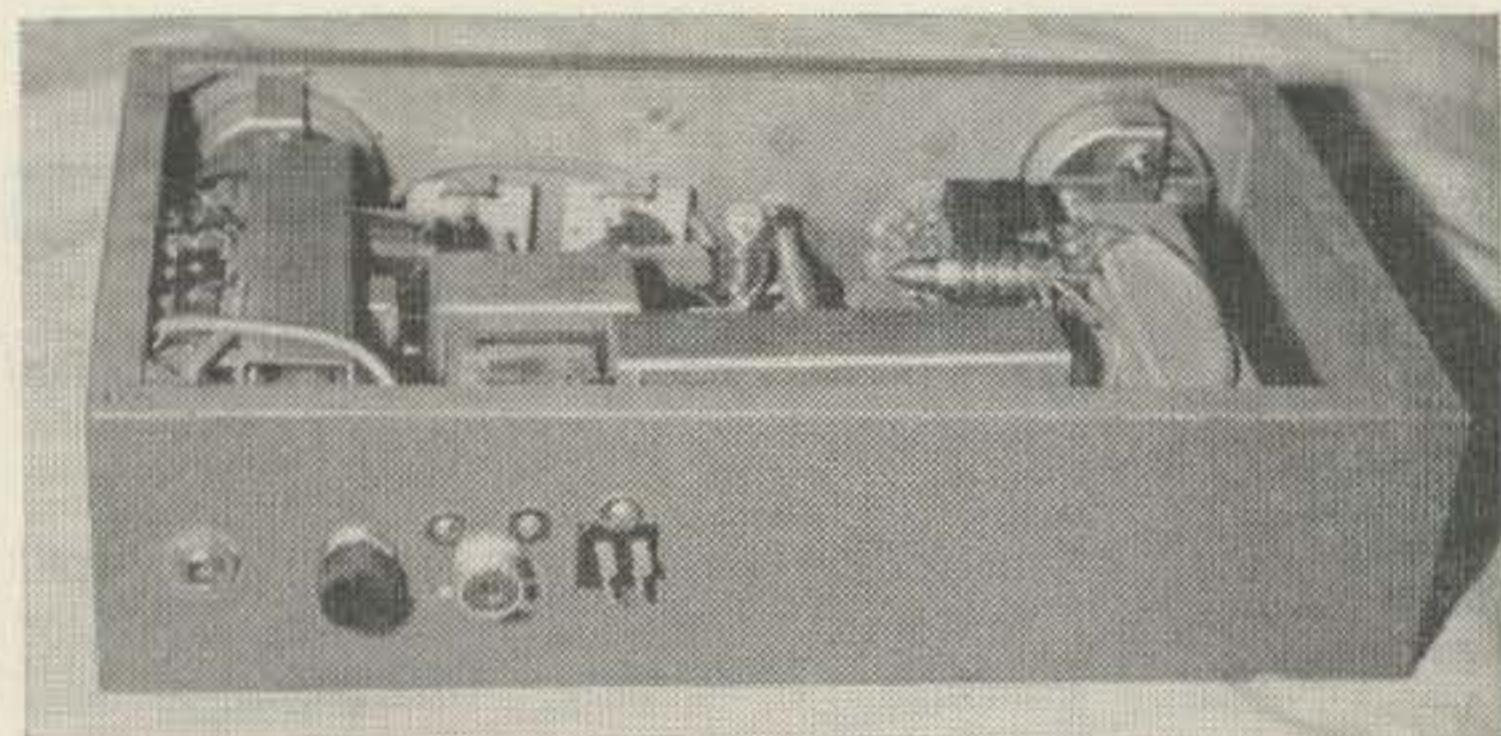


Fig. 2B—Back View: Note components mounted on back panel. From left, mike input, gain control, antenna output, 4-pin power input plug.

stable. Yet it contains no tricks, is easy to build, and is not over-designed. In fact, the modulator by itself will improve the signal quality of most 20 watt AM transmitters in use today.

Design Philosophy

The transmitter was originally intended for mobile operation, but the finished unit performed so well that one is currently being used as the main 6 meter transmitter at W2BHT. Since the greatest local mobile activity is on 6 meters, the transmitter was designed to cover this band, though it may easily be converted to 10 meters by the proper choice of coils.

Single-band operation was selected mainly for simplicity, and because it was found that most of the local mobile hams on 6 meter rarely used any other band for mobile activity. Twenty watts input was chosen not because of size limitation, but because of intelligent

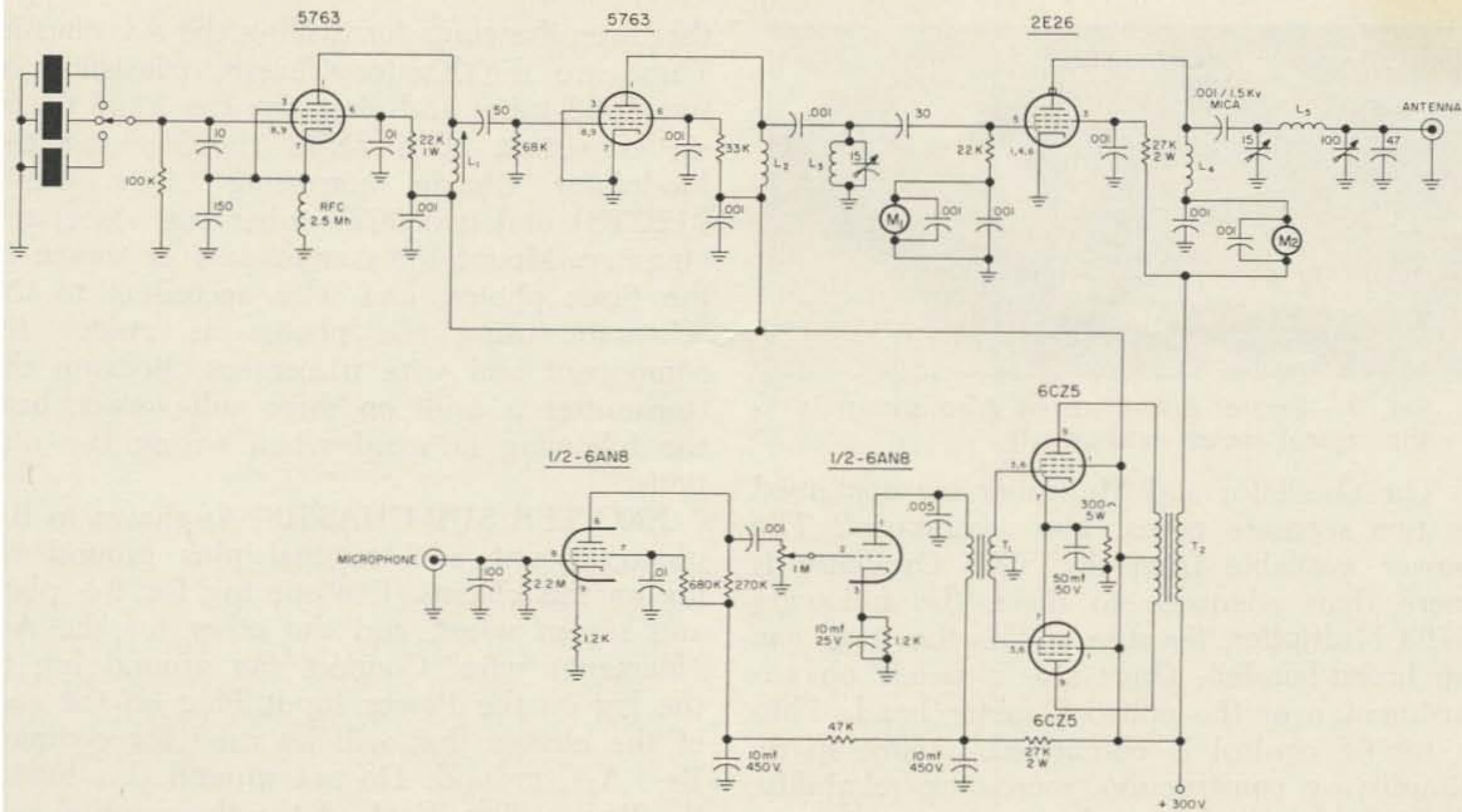


FIGURE 1

Parts List

- L1 Approx. 2 microhenry slug-tuned coil, North Hills Electric 1300F or equivalent
 - L2 7 microhenry RF choke, Ohmite Z-50
 - L3 5 3/4 turns of B&W 3002 miniductor
 - L4 2 1/2 mh rf choke
 - L5 5 turns of B&W 3010 miniductor
 - M1 0-5 ma meter
 - M2 0-100 ma meter
 - T1 1 to 3 ratio interstage transformer, single plate to push-pull grids
 - T2 10 watt modulation transformer, 8000 ohm primary to 5000 ohm secondary
- The parts values are not critical, and any reasonable substitution can be made.

battery drain and power supply requirements. And, as has been borne out by all who have built this transmitter, it will out-perform home-brew and commercial units with 2 or 3 times the power. The unit we built contains a 3-position crystal switch and socket in addition to a crystal socket mounted on the front panel. In this way we could seal in two net frequency crystals with the third position giving us an additional crystal frequency from the front panel, or, as in our home station, providing us with an easy vfo input.

The first reaction we received upon showing the transmitter was, as we anticipated, "why two panel meters?" Simple. We're operating

mobile. How nice to be able to read plate and grid current to the final stage constantly, without meter switching. A real boon when we want to either QSY quickly or make sure the drive is adequate when we crystal-switch without taking our hands from the steering wheel or microphone. Besides, a good rotary switch costs about a buck, plus resistors and wiring. The extra meter can be had for just over a buck. So why not put in this desirable feature, which by the way is also a good conversation piece.

When tuning the transmitter, there are no screwdriver adjustments to make, and no coil adjustments which were so prevalent in other 6 meter transmitters when this one was designed. All tuning is done from the front panel, and instead of requiring minutes of tedious tuning, this little doll can be put on the air in less than five seconds, anywhere in the 6 meter band. And furthermore, no overtone circuits with their tricky adjustments are employed. Inexpensive 8 mc crystals can be used.

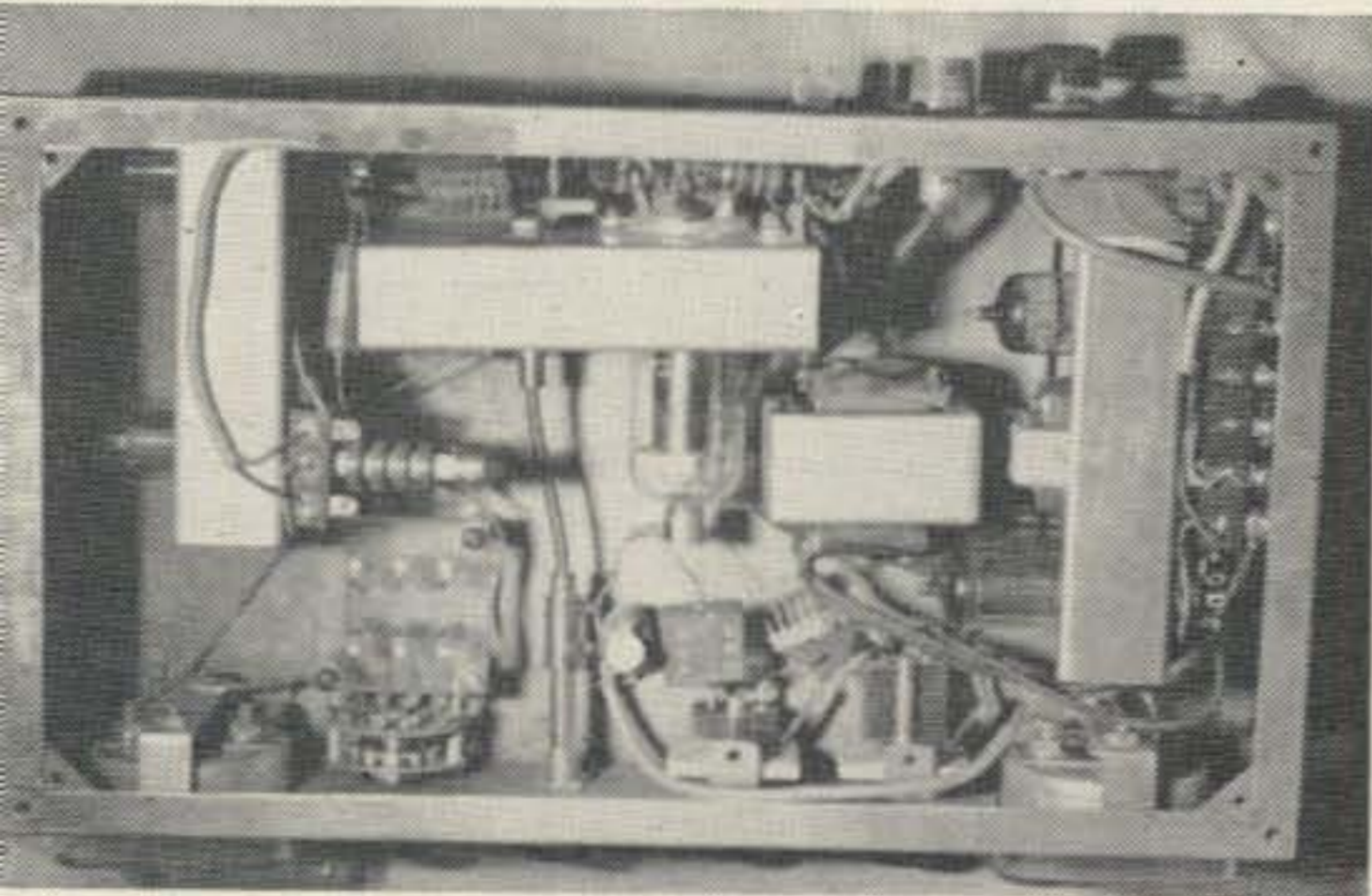


Fig. 2C—Looking into the Transmitter: The Exciter Sub-Chassis is the vertical chassis at the left. The Modulator Sub-Chassis is the vertical chassis at the right. The Final Chassis is shown near the back. Note placement of components on front panel and location of Modulation Transformer between the 2E26 tube and the Interstage Transformer mounted on the Modulator Sub-Chassis.

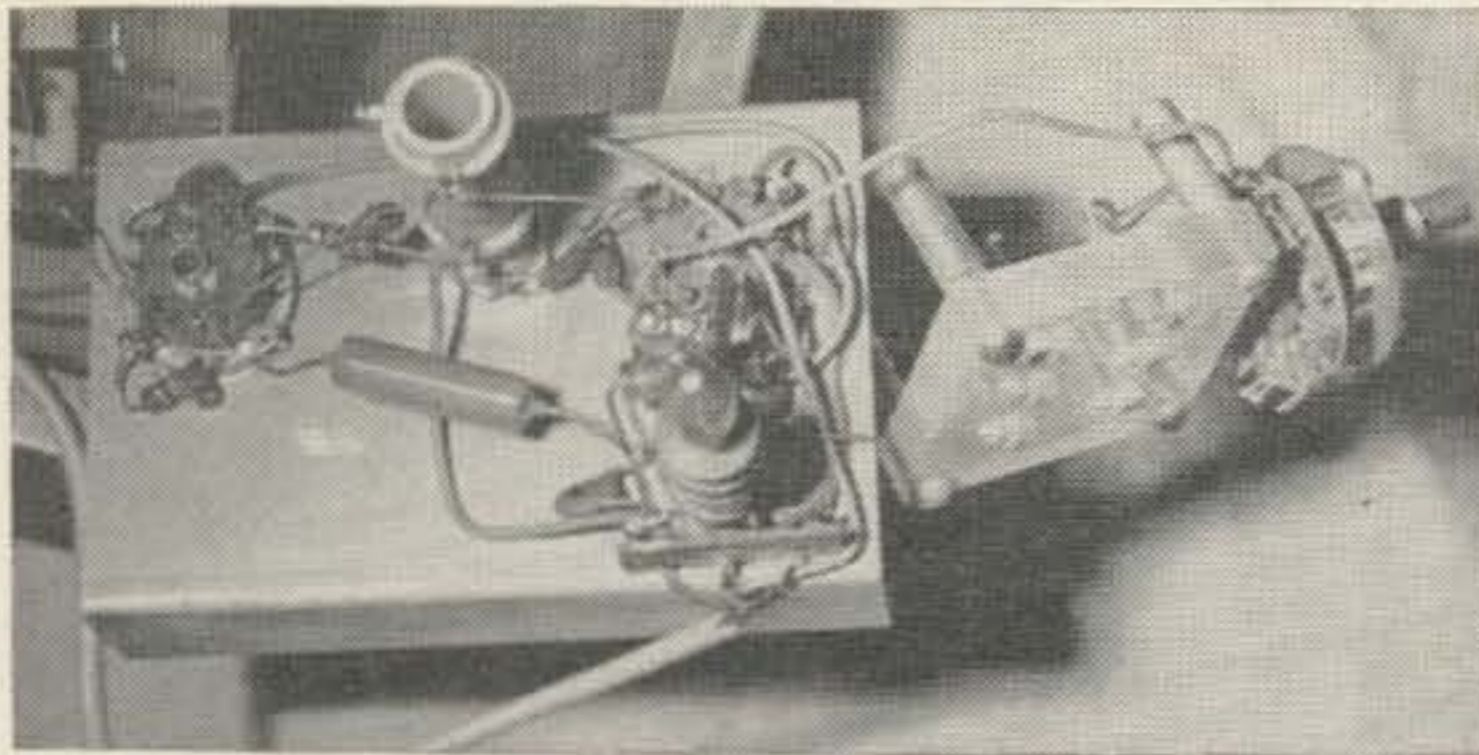


Fig. 3—Exciter Sub-Chassis: Also shown is the crystal socket and switch.

The Oscillator and Multiplier are contained in two separate tubes. The advantages? The power available from the 5763 Oscillator is more than adequate to drive the following 5763 Multiplier. Because of this the stage can be broad-banded. Once set, it needs no adjustment over the entire 6 meter band. Thus a tuning control is eliminated, saving space, simplifying construction, increasing reliability, and greatly decreasing the time spent in tuning or frequency changing. The two tubes are so operated that the total cathode current is no more than a suitable dual-tube would require.

All that need be said about the Speech Amplifier and Modulator is—wait until you receive your first signal report. You'll glow! There is plenty of audio to 100% modulate the transmitter, and the modulator automatically limits overmodulation by uniquely turning to square wave.

If by now you aren't eager to build and operate this amazing transmitter, either mobile or fixed station, it's probably because you're operating 400 watts right now. For once you get the pleasure of tuning up this rig, and hear the same high quality signal report every time, you'll never want to operate any other low power 6 meter rig again. And if you've just built or bought a 6 meter transmitter—well, you'd better build this one right away, while you can still sell the other one.


Simplified Construction

For a cabinet we used a chassis 3" x 7" x 12" upside down. It could be made a little smaller, but this chassis is readily available commercially.

The schematic is shown in Fig. 1, but we've made it really easy for you. Fig. 2 shows a photo of the front and back panels and bottom section, along with a dimensional drawing so that you can easily mark out the holes to be drilled. The entire unit consists of three sections or sub-chassis, plus the larger chassis cabinet. Each of the three sub-chassis is an open-end aluminum chassis 2 3/4" x 4 1/8" x 1", available at any radio supply house. Follow

the three drawings for drilling the sub-chassis. These are the Exciter Chassis, consisting of two 5763 tubes and circuitry; the Final Chassis, consisting of a 2E26 (6893); and the Modulator Chassis consisting of a 6AN8 (12CT8) and two 6CZ5 tubes and associated circuitry. Mount the components as shown in the three photos, and wire according to the schematic—using the photos as guides for component and wire placement. Because the transmitter is built on three sub-chassis, bear the following in mind when wiring the sections.

EXCITER SUB-CHASSIS—As shown in the photo, mount a 2-terminal plus ground tie lug on this chassis. Use one lug for B+ plate and screen wires, and the other for the A+ (filament) wire. Connect the ground lug to the lug on the Power Input Plug on the rear of the chassis that will be used for common B-, A-, ground. Do not ground this lug at the Power Plug. Each of the three sub-chassis must have its own ground wire connecting to the ground lug on the Power Input Plug even though each sub-chassis is used as common ground for its own circuitry. This will give each sub-chassis its own negative lead to the Power Plug. But more about this later.

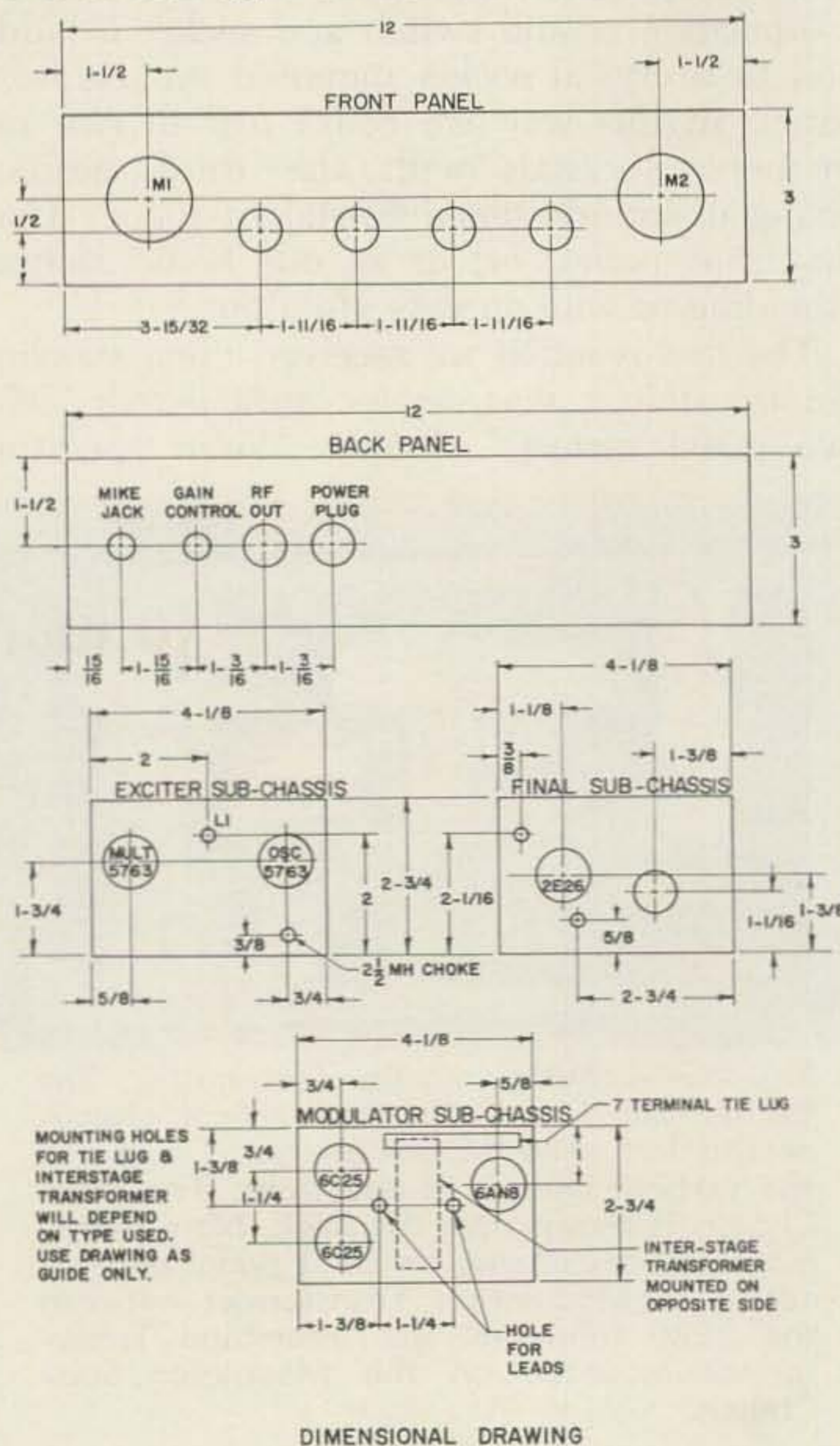

Stronger Signals! Stronger Construction!


NEW *Waters* AUTO-MATCH

the Stronger Mobile Antenna

With Waters new AUTO-MATCH, you'll get the signal strength out that's engineered into your modern, compact transceiver. Every precious DB of it! And AUTO-MATCH is built to endure with its stainless steel tapered radiator tip and tough aircraft aluminum mast. It operates on any band with a simple change of top-center loading coils. (Coils are sealed in protective, low-loss Epoxy.) AUTO-MATCH—the permanent solution to your mobile antenna problems!

PRICES


Mast 370-1	\$12.95	Coil 370-20	\$13.45
Radiator Tip 370-2	\$ 9.95	Coil 370-15	\$12.75
Coil 370-75	\$15.95	Coil 370-11	\$11.95
Coil 370-40	\$14.95	Coil 370-10	\$11.95

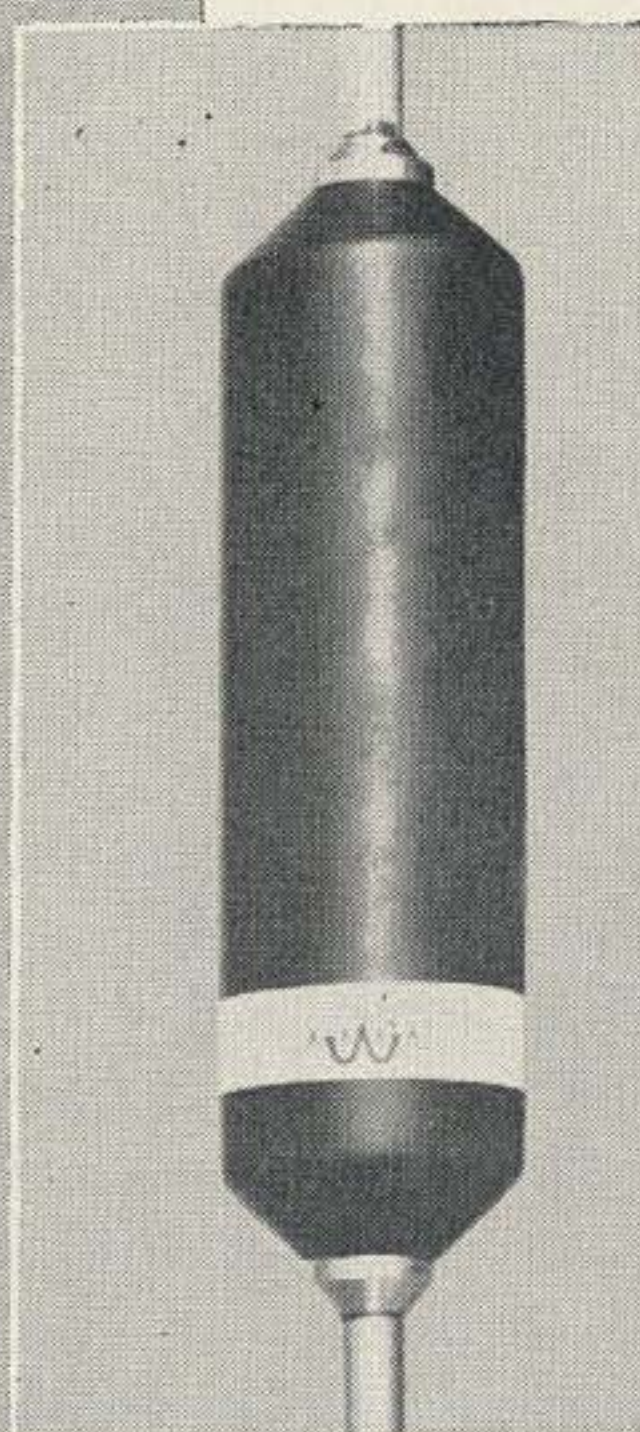

Waters

CODAX — new rhythm-smooth automatic keyer by Waters — never anything like it! Feather-touch double paddle is factory-adjusted for precise gap and tension. Spacing and timing from 5 to 50 WPM is fully automatic. Battery powered all-solid state digital circuitry with sealed Reed Relay output for block grid keying. Also operates into mike jack to work VOX CW on upper or lower sideband. Unique audio circuit provides for monitoring and mixing incoming signals.

NEW CODAX™ Automatic Keyer

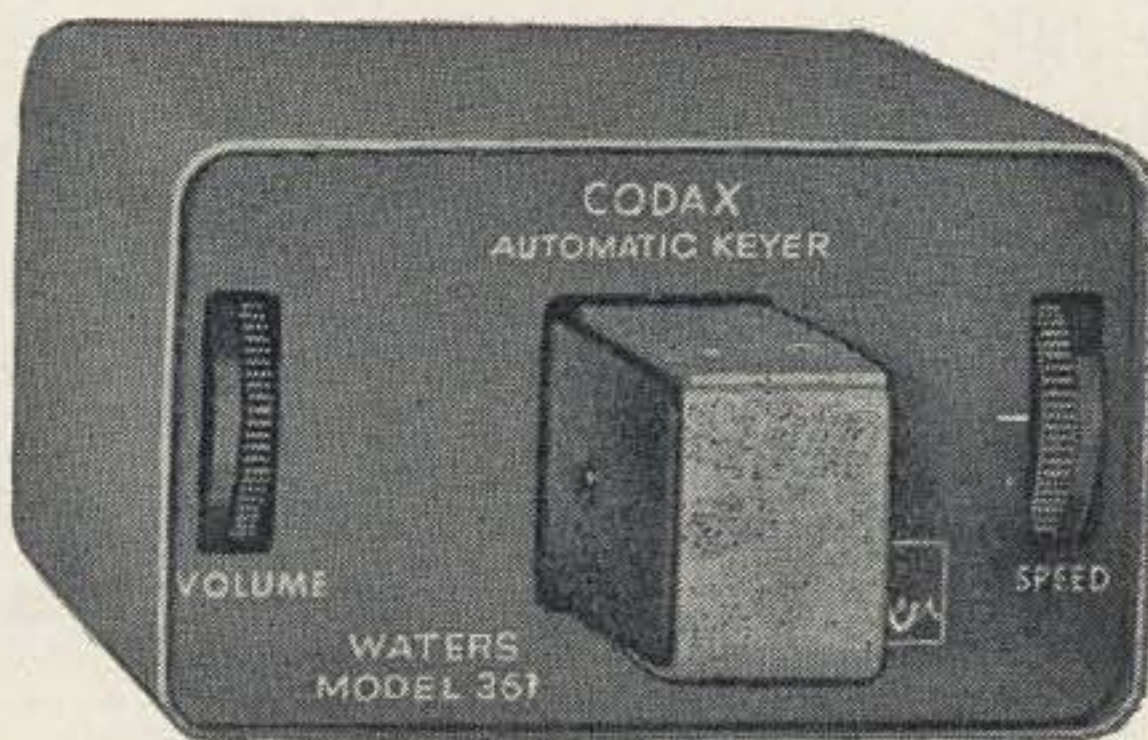

Model 361 \$92.50 (Less batteries)

Introducing . . . *Waters* CLIPREAMP™ to increase your "talk power"

A solid state clipper-preamplifier, the brand new Waters CLIPREAMP will increase your intelligibility and talk-power up to 4 times when band conditions are tough! Self-powered and weighing but 6½ ounces, CLIPREAMP installs externally between microphone and transmitter in a matter of minutes. Front panel controls switch CLIPREAMP IN or OUT, OFF or ON, and permit Compression-Level adjustment to individual requirements. Input: 100K ohms; Output: 50K ohms; Voltage Gain: 10 DB nominal; Power: 9-volt battery.

Model 372 \$21.95
(Less battery)



WATERS
MANUFACTURING INC.
WAYLAND, MASSACHUSETTS

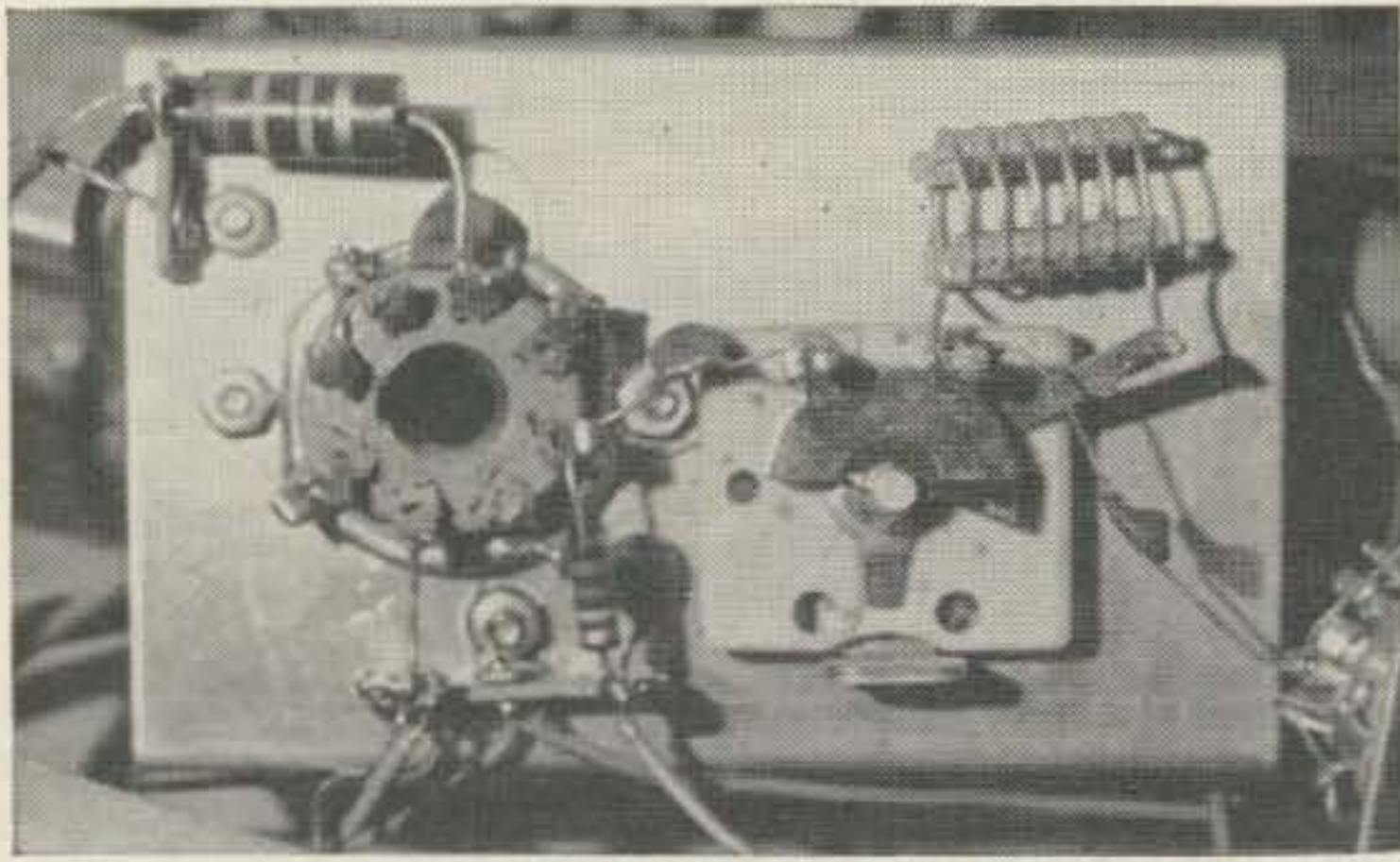


Fig. 4—Final Sub-Chassis: Screen resistor is shown at upper left. Coupling capacitor, .001 mfd mentioned in text, is shown at lower right.

When you connect the .001 mfd capacitor to the 5763 Multiplier plate, leave the other end hanging with a one inch lead. This will later be connected to the variable capacitor on the Final Chassis.

FINAL SUB-CHASSIS—Mount a 2-terminal plus ground tie lug as shown in the photo. The 22K ohm grid resistor will connect to one terminal along with a 15 inch length of wire which will later be connected to the Grid Meter on the front panel. Connect the filament wire to the other terminal. Also mount a 1-terminal tie lug, as shown, to which you will connect the screen resistor, and later on, the modulation transformer and Plate Meter wire.

MODULATOR SUB-CHASSIS — Connect the microphone jack to the 6AN8 socket on this chassis with a short length of wire. The jack will be mounted on the back panel at the same time the Modulator Sub-Chassis is mounted. The Gain Control on the back panel is connected to the Modulator Sub-Chassis by two 3 inch lengths of shielded wire. Do not cut the primary leads of the modulation transformer, but connect them full length to the 6CZ5 tubes. This transformer also will be mounted the same time as the Modulator Sub-Chassis.

Mounting

After wiring the sub-chassis, take the main chassis-cabinet. Mount on the front panel, from left to right as shown: Grid Meter; leave next hole open for crystal switch; panel bearing to which will be connected the variable capacitor mounted on the Final Sub-Chassis by a 3 inch flexible shaft; 15 mmfd variable capacitor; 100 mmfd variable capacitor; Plate Meter. On the back panel mount the Gain Control, Power Plug, and antenna coax connector as shown.

Mount the Exciter Sub-Chassis on the left as shown, mounting at the same time the crystal socket and crystal switch. Now back to the

ground connections we were talking about. Using 3 separate wires or a 3-conductor cable, connect the 2-terminal plus ground tie lug to the B+, A+, and ground terminals on the Power Input Plug.

Mount the Final Sub-Chassis in the center rear as shown. Connect the .001 mfd capacitor from the Exciter Sub-Chassis to the variable capacitor on the Final Sub-Chassis. Connect the A+ filament terminal on the tie lug to the A+ lug on the Power Input Plug. Connect the ground terminal on the tie lug to the ground lug on the Power Plug. Connect the 15 inch lead to the Grid Meter. Ground the other terminal on the Grid Meter. The B+ will be connected later.

Attach a 3 inch flexible shaft from the variable capacitor on the Final Sub-Chassis to the panel bearing on the front panel. Connect a plate cap, output coupling capacitor, output coil, and 52 ohm coax to the front panel variable capacitors, antenna connector, and rf choke. The photo of the top view will aid you here, using the schematic for exact connections. The rf choke connects from the plate cap to the Plate Meter. The other meter terminal connects to the 1-terminal tie lug on the Final Sub-Chassis through a shielded lead.

Mount the Modulator Sub-Chassis on the right. At the same time mount the microphone jack and modulation transformer. Connect the 2 shielded leads to the Gain Control. Select the wires on the secondary of the modulation transformer corresponding to 5000 ohms, and connect one to the 1-terminal tie lug on the Final Sub-Chassis. Connect the other to the B+ terminal on the Power Input Plug. Do not solder the lead to the 1-terminal tie lug until after the testing section.

Special Filament Consideration

If fixed operation is intended with a 6 volt filament supply, wire the filaments as shown. If mobile operation is considered with a 12



Fig. 5—Modulator Sub-Chassis: The two 6CZ5 sockets are at the left. The choke in the photo was wired in the filament lead of the 6AN8. It was later found not to be necessary, but was left in.

volt filament supply, make the following changes.

Wire the two 5763 tube filaments in series. Replace the 2E26 tube with its 12-volt equivalent, 6893. Wire the two 6CZ5 tube filaments in series. Replace the 6AN8 tube with a 12CT8 tube (direct replacement).

Testing


Install the Exciter tubes and the 2E26 (6893). Do not yet install the Modulator tubes. Plug in a crystal. Temporarily disconnect the modulation transformer wire connected to the 1-terminal lug on the Final Sub-Chassis. Connect a 300 volt, 200 ma, 6 volt, 3.6 amp (12 volt, 1.8 amp) power supply to the Power Input Plug and adjust the slug coil on the Exciter Sub-Chassis for maximum reading on the Grid Meter. If the recommended coil is used, the slug will be about $\frac{1}{2}$ inch out of the coil. Disconnect the 300 volts. Re-connect and solder the modulation transformer wire. Install the tubes on the Modulation Sub-Chassis.

Tuning

The transmitter is extremely easy to tune. The general procedures are as follows: Close all 3 variable capacitors (full capacitance). With power applied, crystal or vfo connected, and antenna connected, turn the knob connected to the variable capacitor on the Final Sub-Chassis to get about $2\frac{1}{2}$ ma reading on the Grid Meter. Then turn the 15 mmfd variable capacitor mounted on the front panel for minimum reading on the Plate Meter. If this reading is about 60 ma, tuning is finished. This will depend upon antenna being used. If this reading, however, is much below 60 ma (45-55ma) turn the 100 mmfd variable capacitor mounted on the front panel until the Plate Meter reads slightly over 60 ma, and again turn the panel-mounted 15 mmfd variable in the same direction as before for minimum reading on the Plate Meter. That's all here is to it. Easy? You bet!

Use a high impedance crystal or dynamic microphone, and do not ruin the superior audio ability of the modulator by rewiring for a carbon mike. About a $\frac{3}{4}$ turn of the Gain Control should provide the correct gain with the average crystal microphone.

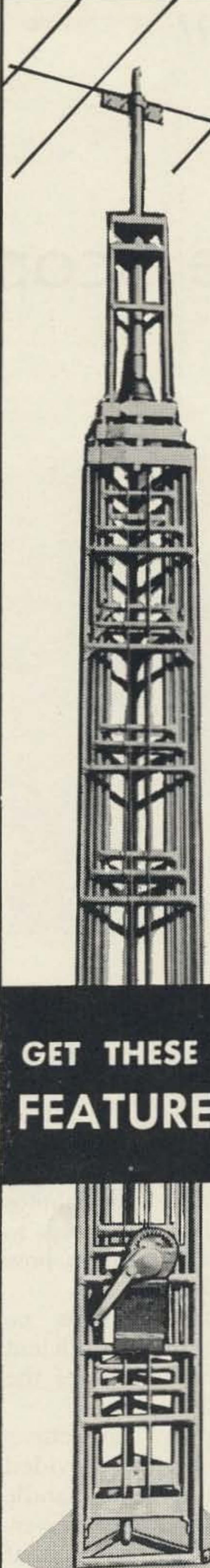You now have a compact transmitter that will literally give you years of trouble-free, high-performance operation. And when your first QSO tells you you've got the finest sounding rig he's heard—and what? You're only running 20 watts?—Sounds like 60! Just sit back comfortably and smile. After all, it's not your fault he didn't build one of these units too. . . . W2BHT



TRI-EX'S
NEW
IMPROVED
THD-471
GUYED TOWER

shown with internal rotator, 2" mast, Tri-Band Beam

Choose from 8 models, 4 with 20 ft. sections, 4 with 10 ft. sections — all hot-dipped galvanized, inside and out, *after* fabrication.

GET THESE FEATURES


- Tower Heights to 88 ft.
- Easy to Erect
- Cranks up & down
- Geared winch
- Aircraft raising cable
- Ball-bearing pulleys
- Precision formed guides
- Hinged base plate

PRICES START AT
\$127⁹⁰

FREE BROCHURE

**Tri-Ex TOWER CORPORATION**
7182 RASMUSSEN AVE., VISALIA, CALIF.

The Scope Monitor

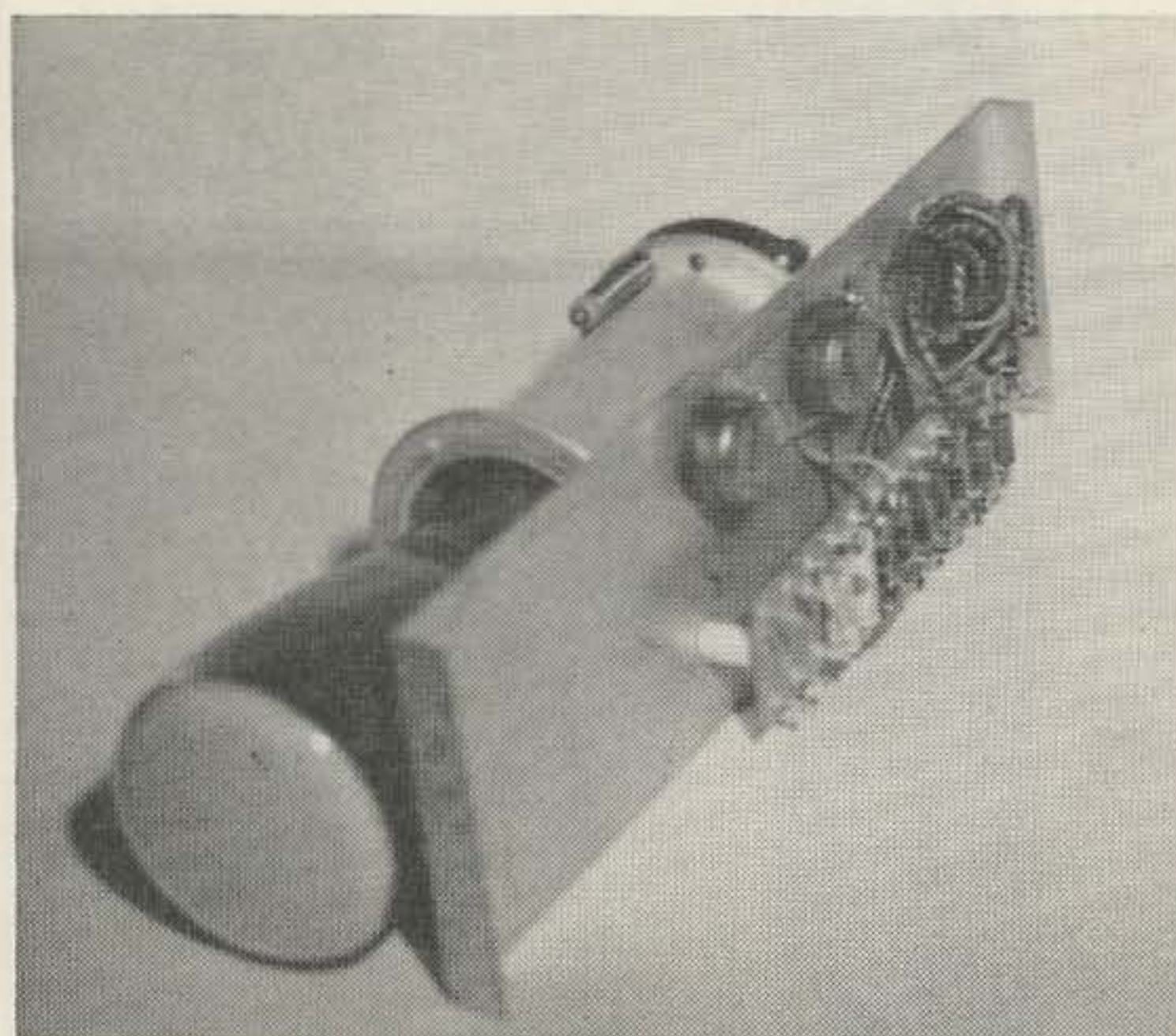

Scope subchassis.

Tuning RTTY signals without the use of a scope monitor will be found to be a difficult job to say the least. In fact it is almost next to impossible, so every good RTTY set-up should include such a device.

In designing the complete converter we included a scope monitor and the photos shown with this article which appeared in 73 for December 1964, clearly indicate how it was fitted into the completed unit.

In order to make the circuit simple, no amplifiers are used since there is sufficient signal delivered to the deflection plates of the 3BP1 for good scope presentation.


In Fig. 1, the power supply connections are shown, since the power supply provided for the converter circuit is ample to handle the scope monitor. See Fig. 2 in the converter article. Simply make the connections at the right point on the original circuit and you are in business. Construction details can be seen in the accompanying photo. All wiring is done on one side of the sub-chassis to a terminal board. The two pots shown are the horizontal and vertical controls. The focus and

intensity controls are mounted on the front panel.

The sub-chassis is three and three-quarters inches wide by 12 $\frac{3}{4}$ inches long, with a one half inch flange at each end.

After completing the wiring as shown in Fig. 1, fit the sub-chassis into the overall chassis and fix into position with self-tapping screws. This part of the converter is dressed up by using a Millen bezel No. 80073.

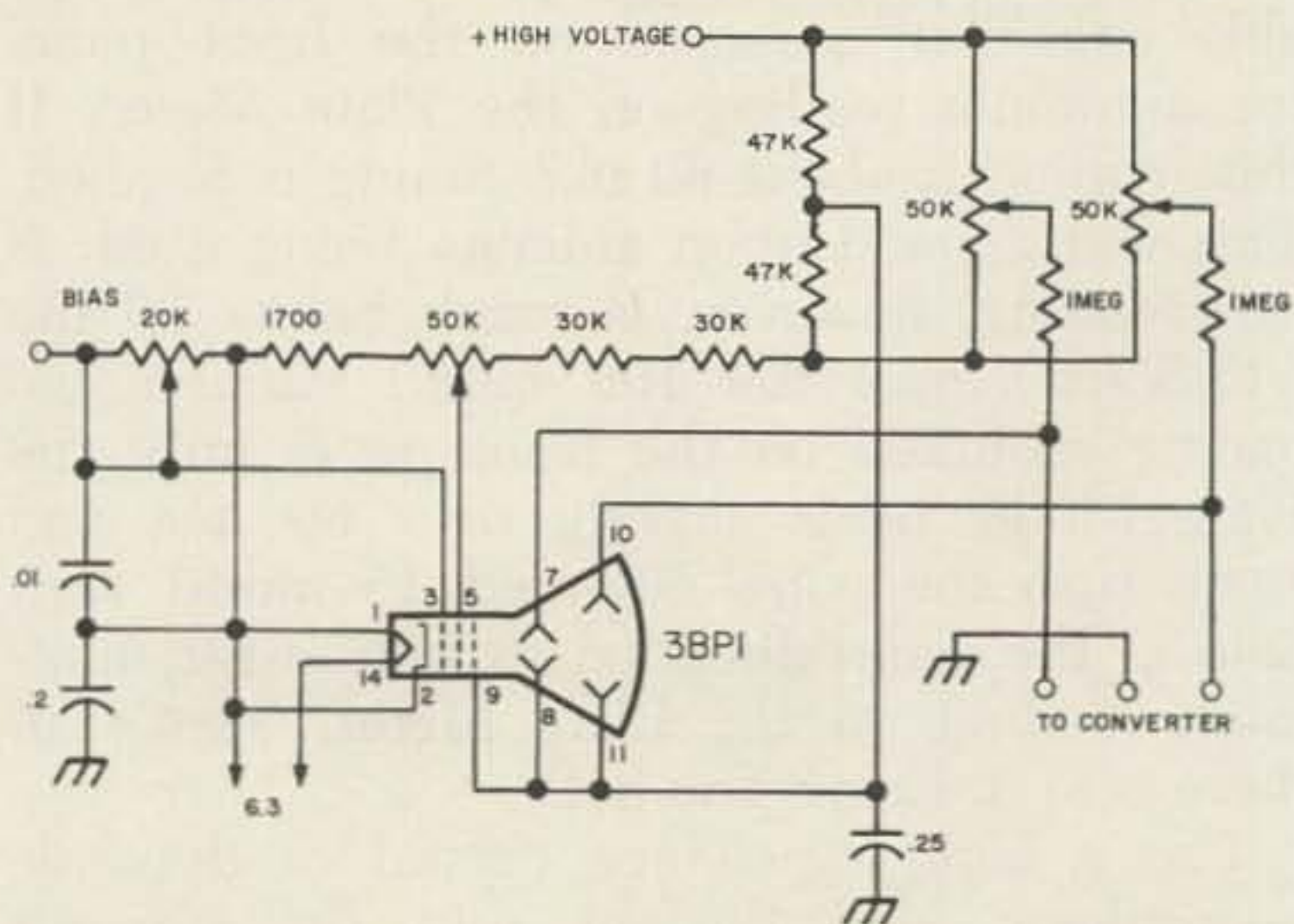After wiring is completed, turn the converter power supply on and adjust the vertical and horizontal controls and then with an incoming signal applied, adjust the focus and intensity controls.



Schematic of scope.


The pattern which should appear when the signal is properly tuned is a cross.

Tuning by the scope monitor is easy, as you have a visible indication of when proper tuning is achieved since the scope presentation will be a perfect cross, if the shift of the transmitting station is correct. Here again a little practice will soon give you the necessary skill to quickly recognize the proper pattern when it appears on the scope.

going mobile?


GET MORE POWER... BETTER
AUDIO QUALITY... GREATER VERSATILITY
WITH SWAN
5 BANDS 400 WATTS

MODEL 350

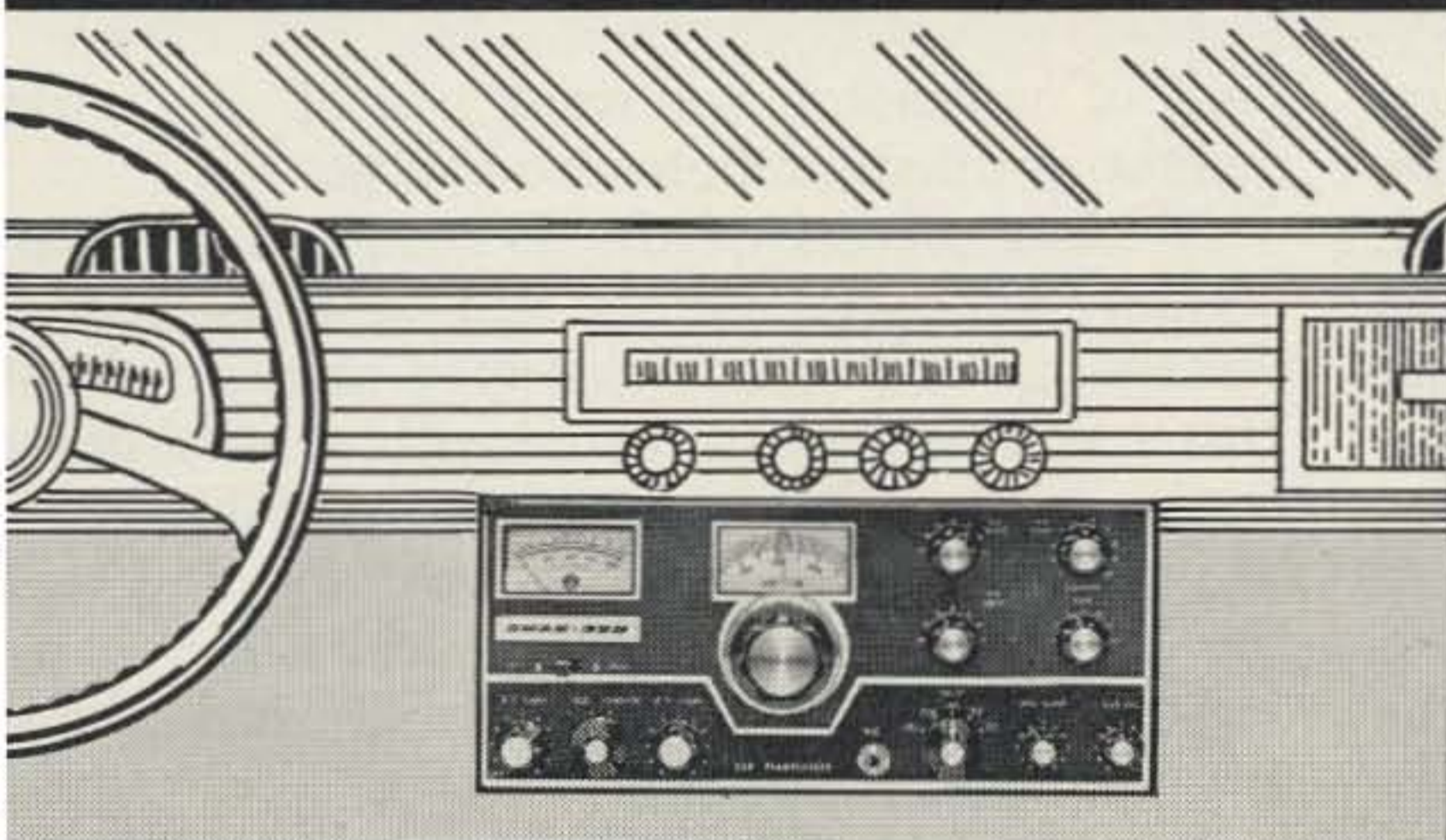

Mounts under dash or on
tunnel, or with a Model 22
Adapter and Model 405
mobile VFO can be mounted
in the trunk. **\$395**

MODEL 400

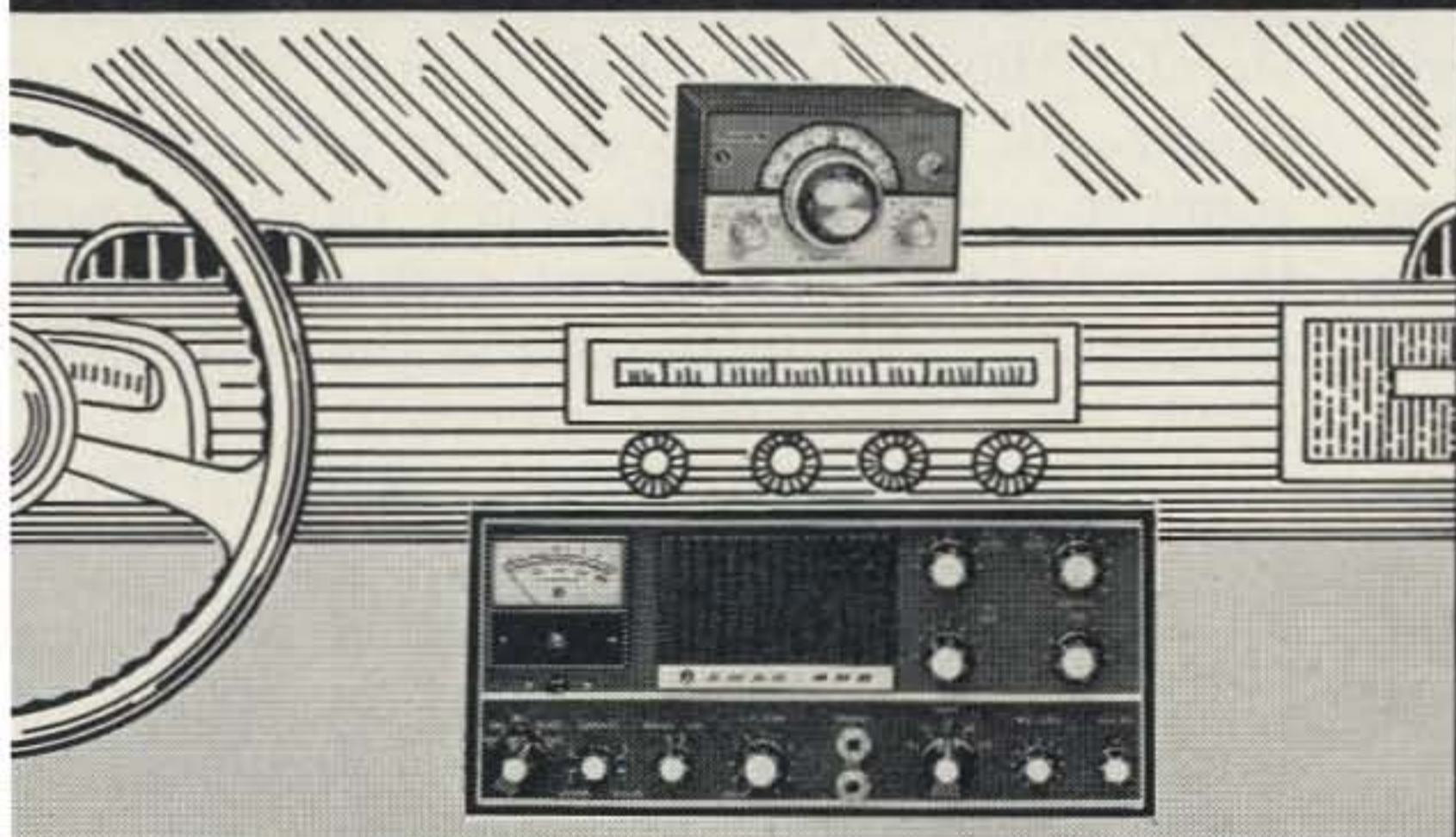

Particularly adaptable to sports
cars with consoles and bucket
seats. New Model 400 deluxe with
outboard VFO can be mounted in
trunk, under dash or on tunnel
with Model 406 VFO mounted on
dash or steering column for maxi-
mum ease of operation.


Model 400 **\$395**
Model 406 **\$ 75**

MODEL 55 SWANTENNA

Developed specifically for use with Model 350 and Model 400 transceivers. Remote controlled band switching, mobile antenna covers all phone bands 75 through 10 meters. Built-in output indicator for tune up to maximum efficiency. Rated 500 watts PEP input to transceiver. Complete with control unit.

\$95

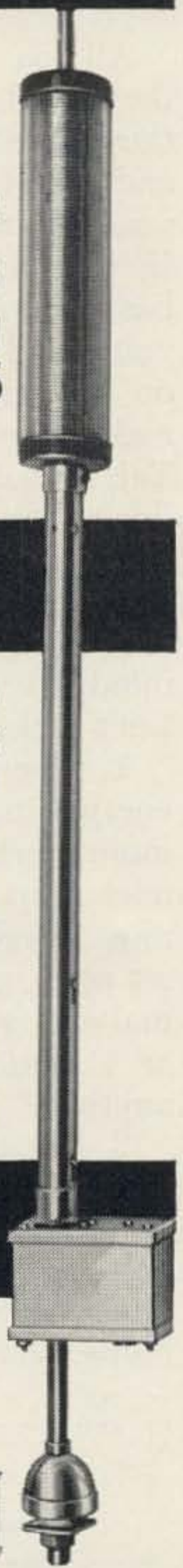MODEL 412 DC SUPPLY for either Model
350 or 400 **\$130**



SWAN

ELECTRONICS CORP.
Oceanside, California

Imagineering with Meters

All too many hams seem to feel that when they need a meter to do a certain specific job, they have to have exactly the meter required, and don't realize that within certain limits you can make almost any meter do any job. If we had a buck for every meter someone has blown out trying to make it read kilovolts, and every meter someone has given up on, for being too slow when they tried to make it read heavier currents, I could buy the Taj Mahal. This doesn't happen because we don't have the knowledge, it's because we lack imagination, and refuse to apply the knowledge properly.

Bearing a few good basic principles in mind, we can do wonders with surplus meters. Let's look at the basics.

1. The more sensitive a meter is, the less energy it takes to go to full scale, and the more versatility we have. Don't sell a 100 microamp meter short. It can be made to read most anything. In general, we can make a meter read what we want it to, except we cannot make it more sensitive unless it has a shunt or a multiplier in it, then we can do most anything.

2. Use the fact that a one milliamper basic meter is rated at *1000 ohms per volt*. Thus a 100 microampere meter is 10,000 ohms per volt, and a 50 microampere meter is 20,000 ohms per volt. Remember the one mil is 1000 ohms per volt. This will allow us to make any

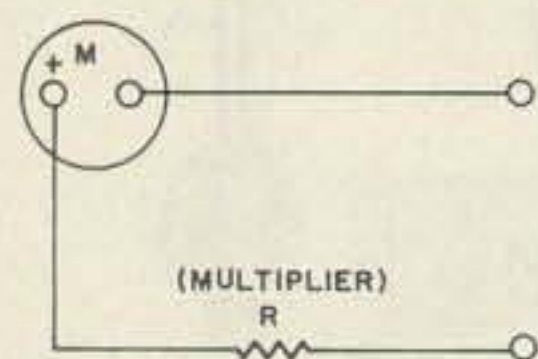


FIG. 1

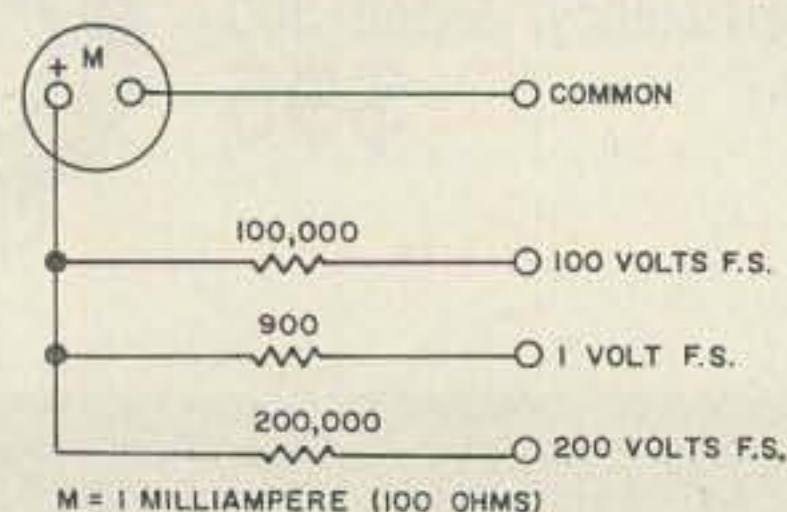


FIG. 2

kind of voltmeter we want out of any milliammeter or microammeter we can get.

3. Most meters of the D'Arsonval type are actually millivolt meters and actually read a voltage, in millivolts, developed across a shunt. Often you will see a meter with a little designation in the lower left of the dial FS-50mv. This means that no matter what the dial says, the basic movement is 50 millivolts. By changing the shunt, you can make it read almost any range.

4. We have two ways, and herein lies a trick, or *combinations* of these ways, to alter a meter's range. We can use a multiplier; (this is a series resistor), or we can use a shunt; (this is a parallel resistor.) The multiplier will be used to make a voltmeter; the shunt to extend current ranges. Oddly enough the most common current meters for higher ranges use a millivolt meter as the basic movement, while voltmeters use current meters.

Now let's apply some basics. Look at Fig. 1. Let us first assume that the meter is a one milliamper unit. Remember that 1000 ohms per volt rating. (Incidentally the meter will usually have a resistance of 100 ohms, and unless you want to make a meter under 10 volts full range, forget it. Under 10 volts subtract this 100 ohms from the multiplier resistor value.) If we want to make this meter read 200 volts at full scale, we need merely to make R a resistor of 200,000 ohms. To make it read 500 volts, R must equal 500,000

Meter Multiplier Chart—Voltmeters Meter Sensitivity

0-100 ma.—	10 Ω per volt *
0-10 ma.—	100 Ω per volt *
0-1 ma.—	1000 Ω per volt
0-100 μ A.—	10,000 Ω per volt
0-10 μ A.—	100,000 Ω per volt

* Watch multiplier resistor wattages.

ohms. One caution to be observed is that it is a good practice not to allow over 300 volts to appear across one physical resistor; so, to make 500,000 use two 250,000 ohm units. Now if the meter were a 100 microampere unit, we would use 2,000,000 ohms to make it read 200 volts. Remember it is rated at 10,000 ohms per volt.

Simple application of the above principles will allow you to make an accurate voltmeter out of any reasonably sensitive meter you may have. When you get up above 10 milliamperes full scale, or if you will, 100 ohms per volt, watch out for power ratings of resistors. Think in terms of ohms per volt for voltmeters and you have the problem licked. You may apply the same principles to extend the range of a voltmeter. Usually you will find the basic movement listed on the dial. You may also, if the basic range is adequate, go inside a meter rated at a much higher voltage rating and pull out the present multiplier and make it read what you want it to by calculating a new multiplier, and installing same.

Naturally, by installing the multipliers externally and switching them in, you can make a multiple range meter readily. See Fig. 2. (Note the 900 ohm resistor for the one volt range; in lower ranges, you must include the meter coil's resistance in calculating; in the higher ranges, this gets negligible so is forgotten.)

The above principles are very simple and a little imagineering on your part should take care of most voltmeter problems. Remember, keep the voltage drop across a resistor less than 300 volts, and put the resistor in the plus lead of the meter. (Viewed from the back, this is conventionally the left hand terminal.)

Extending the range of current meters, or making millivolt meters or microameters read currents of magnitude can be simple, or complex. It all depends what basic meter you start to work with. The easiest thing in the world is to take an existing meter, which reads relatively high currents, and extend its range. Measure its resistance, and put the proper shunt across it. This is the simplest kind of ohms law calculation. The meter meas-

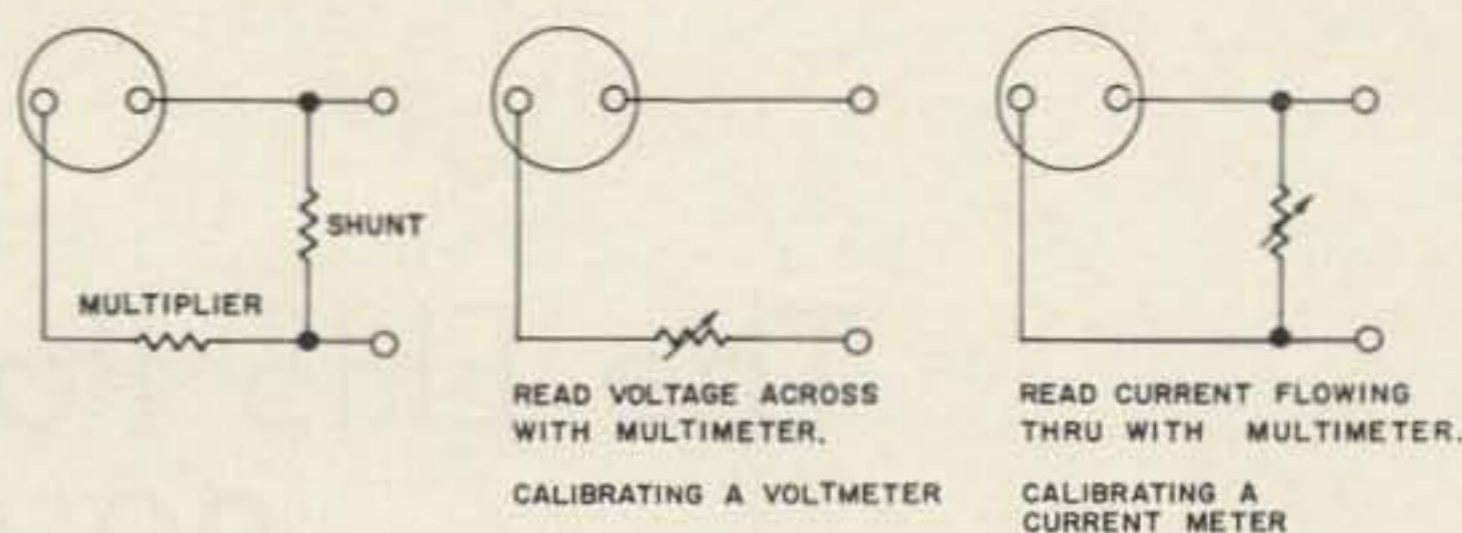


FIG. 3

ures 5 ohms, and reads 200 milliamperes at full scale. Want it to read 400 mils at FS? Put a 5 ohm resistor across it, and presto, half the current through the resistor, half through the meter, 400 mils full scale. This is as simple as calculating the value of two resistors in parallel, and we won't go into it. Apply this basic principle to extending the range of existing current meters, which are in the ball park area. Sometimes the only meter we can get is something which reads 50 microamperes full scale, and we want a meter to read 250 milliamperes. You can use the simple shunt technique, but you may have to stay around until your hair gets gray waiting for the meter to make a reading, since shunting meters with low resistance always slows down their response time, or the time they take to read . . . The trick here is to use a combination of shunt and series or multiplier resistances. You can almost always find a value of series, which can be used with a shunt as shown in Fig. 3, which will allow the meter to read the range you want, and with reasonable response time.

Calibrating these home converted meters is easy if you have a good multimeter. Just use it in series for current calibration, and in parallel for voltage measurements. For playing around with series parallel units to get response time, as well as desired ranges, pots, or decade boxes will do the job. Don't try to get the meters super-accurate, ball park figures are usually good enough for ham purposes. For some ranges you will have to wind your own shunts; these should generally not be of copper wire. Beg, borrow or ? some resistance wire.

Pots may be used for test purposes, then measured, and replaced with fixed resistances.


. . . W8BPY

telrex "BALUN" FED INVERTED "V" ANTENNA KITS

SIMPLE-TO-INSTALL, HI-PERFORMANCE ANTENNA SYSTEMS:

- 1 KW P.E.P. Mono-Band Kit... 1KMB1V/81K... \$19.95*
- 2 KW P.E.P. Mono-Band Kit... 2KMB1V/81K... \$24.95*

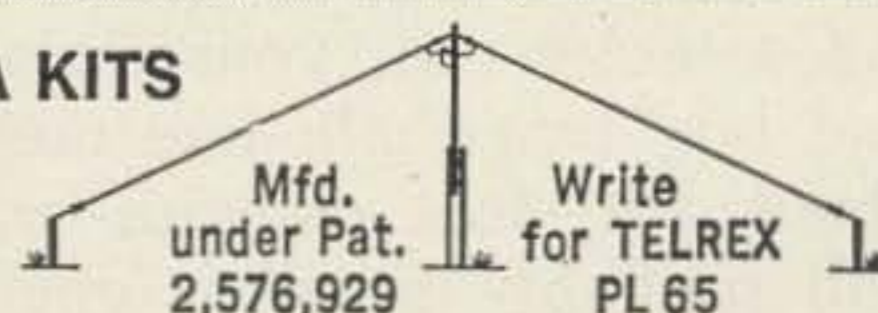*Kit comprises, encapsulated, "Balun," copperweld, insulators, plus installation and adjustment instructions for any Mono-band 80 thru 10 Meters. Also available 2, 3, 4, 5 Band Models.



TELREX LABORATORIES
ASBURY PARK, NEW JERSEY



The EHS Portable Dipole 80 thru 6

Several years ago the Elkhart High School Amateur Radio Club became interested in a portable dipole which could be used during emergencies and Field Day. It was decided that the antenna must meet the following specifications:

1. The antennas must be fed with either 72 ohm or 52 ohm coax.
2. It must be capable of operation on all bands from 80 meters through 6 meters.
3. It must be adjustable for an SWR of at least 1.2 to one at any desired frequency on any of the bands 80 thru 6.
4. The antenna system must be simple and most important the cost should be low.
5. The entire antenna system must be small enough to be easily carried in a pocket or the glove compartment of a car.

After many hours of searching through past issues of CQ, QST, and several ARRL publications (73 magazine was only several months old then) it was decided that we would have to come up with something new since none of the antennas would measure up to our five specifications. Traps are hard to adjust. Multi-wires are a mess to work with and commercial antennas are too expensive and too large for most of our pockets.

While looking through one of the local hardware stores we were able to locate a metal chalk line dispenser which is used by carpenters to make chalk lines on floors. We removed the chalk line and noted that we could replace the chalk line with small diameter wire. We bought two of the chalk line units and loaded each of them up with 100 feet of wire (say you want to broadcast on 2.34 Mc).

A quick check of the system on 21 Mc with the antenna ten feet off of the ground indicated an SWR of less than 1.3 to one with a hank of 72 ohm coax.

Construction

Go down to your local hardware store and buy two chalk line units which will hold about 100 feet of wire on each spool. You will probably have to open up the units to see what capacity the spools have since several of the units were found to have large dia-

meter spools and would not have been able to store the proper amount of wire. We were able to find a chalk line unit which stored the proper amount of wire and had the added bonus of having a built in lock which will keep the wire on the spool when the antenna is erected. (Evans Chalk Line, CL-50, Elizabeth, N.J.)

Remove the chalk line and attach 100 feet of number 18 solid wire to the spool. There is some reason to believe that stranded wire might go on the spool easier but we have experienced practically no difficulty with the solid wire.

The other ends of the wire are connected to an SO-239 coax connector or insulator.

A hole is drilled through the end of each of the chalk line units and a loop of insulated wire is attached. This loop serves as the end insulator for the dipole.

It should be noted that insulated wire *must not* be used with these units since proper operation of the antenna can only be obtained when the wire automatically shorts out on the spool. Otherwise you will end up with a loading coil at the ends of the dipole. The loaded spools in the chalk line units contribute to the "end effect" and we found that our antennas had to be shorter than the calculated value

$$L = \frac{468}{Fmc} . \text{ We found this to vary}$$

from two to eight percent with the greatest variation coming at the higher frequencies.

It is a rather simple matter to adjust the portable antenna to any desired frequency with an SWR meter. Different colors of paint can be put on the wire for each selected frequency so that further measuring need not be made in case of emergency operation.

This antenna works 80 through 6 meters and easily fits in two pockets. It is readily adjusted to any spot frequency with a low SWR. As an emergency antenna it is very hard to beat. If the antenna is used in damp weather it would probably be wise to wrap the chalk line units in Saran Wrap to prevent rust damage.

. . . W9FQN



**a KW ssb
station**

**only 64½
cents per watt**

The brilliant new **SB-34**, SSB 4-band transceiver serves as your receiver and exciter... the new matching **SB2-LA** Linear furnishes the big bang! This advanced design power combo costs you only 644.50, unquestionably the lowest cost per watt obtainable! But this is only part of the value story. **SB-34** has a **built-in power supply, 117V AC and 12V DC**... needs no separate inverter... connects directly to the 12V car battery when you want the added pleasure of 4-band mobile transceiver operation. **There's just no comparable value!**

SB2-LA LINEAR AMPLIFIER . . 249.50

Husky, heavy-duty, with 1KW P.E.P. input capability on 80-40-20-meters, 750 watts on 15 meters, this exceptionally compact amplifier matches SB-34 in general size and appearance. Operates perfectly with SB-34 but can boost the output of any SSB exciter to a full KW. AC power supply is built-in.

4-bands, 80, 40, 20, 15 meters • Full band switching • Passive grid input for resistive load to exciter. Drive: 60W or more depending upon the linear amplifier power output • Low plate voltage (800 volts) and high plate current • Easier on capacitors, rectifiers, power transformers • Safer under environmental extremes • High filter capacity for dynamic regulation • Built-in antenna relays (2), internal blocking bias • HI/LO power and TUNE/OPERATE switches • Panel meters for output and plate current • Six parallel-connected 6JE6's are used in amplifier • 115V AC power supply (built-in) is all-solid-state. Size: 5¼"H, 11¾"W, 11⅝"D. Wgt, 35 lbs. (apprx).


SB-34 TRANSCEIVER 395.00

New... advanced... with important plus performance features! Transistors and diodes replace vacuum tubes (except for the 2-6GB5's in PA and 12DQ7 in RF driver) — equipment size is reduced greatly — current drain lowered substantially. Example: **SB-34** draws only 500 ma on receive standby.

Built-in supply for 12V DC and 117V AC • Power input: 135 watts P.E.P. (Slightly lower on 15 meters) • Frequency range: 3775-4025 kc, 7050-7300 kc, 14.1-14.35 mc, 21.2-21.45 mc • 23-transistors, 18-diodes, 1-zener, 1-varactor, 2-6GB5's PA, 1-12DQ7 driver • No relays — solid state switching — breakthrough! USB or LSB selectable by panel switch • Collins mechanical filter — transmit/receive • Delta receiver tuning • Solid-state dial corrector • prewired for VOX/100kc calibrator accessories — both units are optionally available. Single-knob dual-speed tuning. Size: 5"H, 11¼"W, 10"D. Weight 20 lbs. (Approx).

SIDEBAND **SBE** ENGINEERS

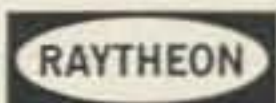317 ROEBLING ROAD, SOUTH SAN FRANCISCO, CALIF.




Export sales: Raytheon Company, International Sales & Services, Lexington 73, Mass, U.S.A.

A 8072 linear with many interesting ideas for the SSB ham who wants to step up to higher power.

Some Notes on Grounded-Grid Linear Amplifiers

I have been doodling on a scratch pad over the design of a miniaturized 2 KW pep linear amplifier for quite some time. Miniaturization seems to be the order of the day and 2 KW is a practical limit for an amateur band linear amplifier. A voice average KW can be run with a little ALC or audio compression. About 600 w on the average voice is the best that can be done without it and hold within these peak limits.

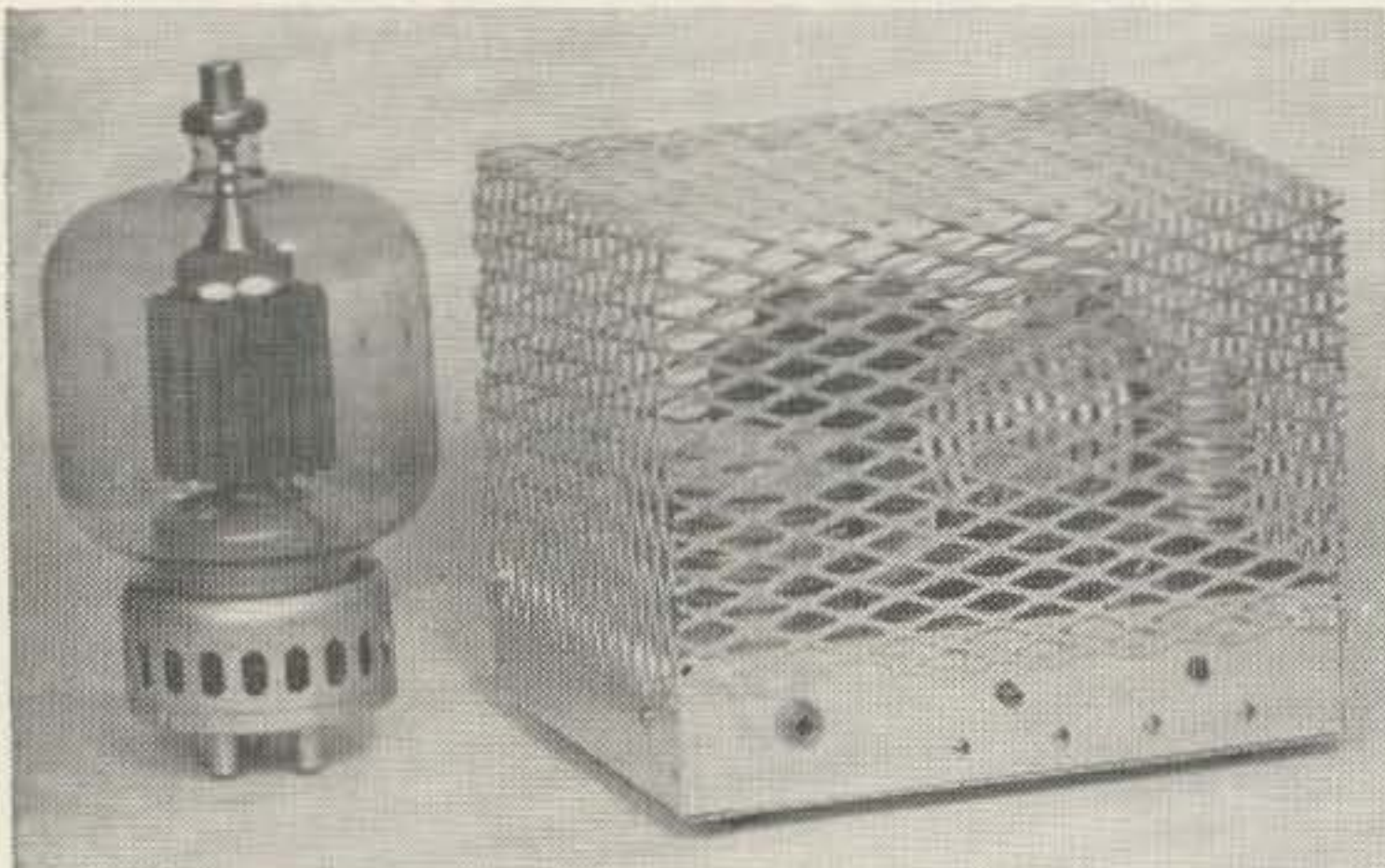This is not intended as a construction article. The amateur with reasonable experience could duplicate the linear amplifier down to the last nut and bolt by looking at the accompanying photos. A self-addressed stamped envelope along with any queries to me might even bring some help. This article is intended to bring out a tube application and some circuit ideas for grounded-grid linear amplifiers




The 8072 Amplifier compared to a 4-1000A.

that the technical minded amateur might like to include in his own amplifier. The amplifier as shown is experimental to try out the tubes. It is used only for single band unattended operation. No adjustment is necessary over the top 100 kc of the 14 mc band so there are no dials to twiddle, no meters to watch and no on the air "helloooooo test" necessary once it is set up.

The tubes were the big miniaturization problem. Jo Jennings W6EI has long since taken care of the tank condenser problem with his small vacuum capacitors. The tank coil, well it has not progressed any since I wound them up for my first "TNT" in the early thirties. The ultimate of simplification is a hi-mu "zero bias" cathode type triode used in a grounded-grid circuit. According to my research, there seemed to be no tube to fit this requirement. The RCA type 8072, 812 and 8122 series came along that could be turned into "simulated hi-mu triodes". Other more common types have no cathode or cannot be hi-mu triode operated due to the low grid current ratings. The RCA tubes mentioned have a CCS rating of 100 ma of grid current which qualifies them for the application. All of the three tubes have the same electrical characteristics. The difference in the plate dissipation ratings is due to the cooling and the maximum rating is 400 w CCS, not the "ICAS" rating that the amateur is used to. I chose the type 8072 as it fit the miniaturization

Fig. 1. Grounded-grid Linear Amplifier using 2 8072's.

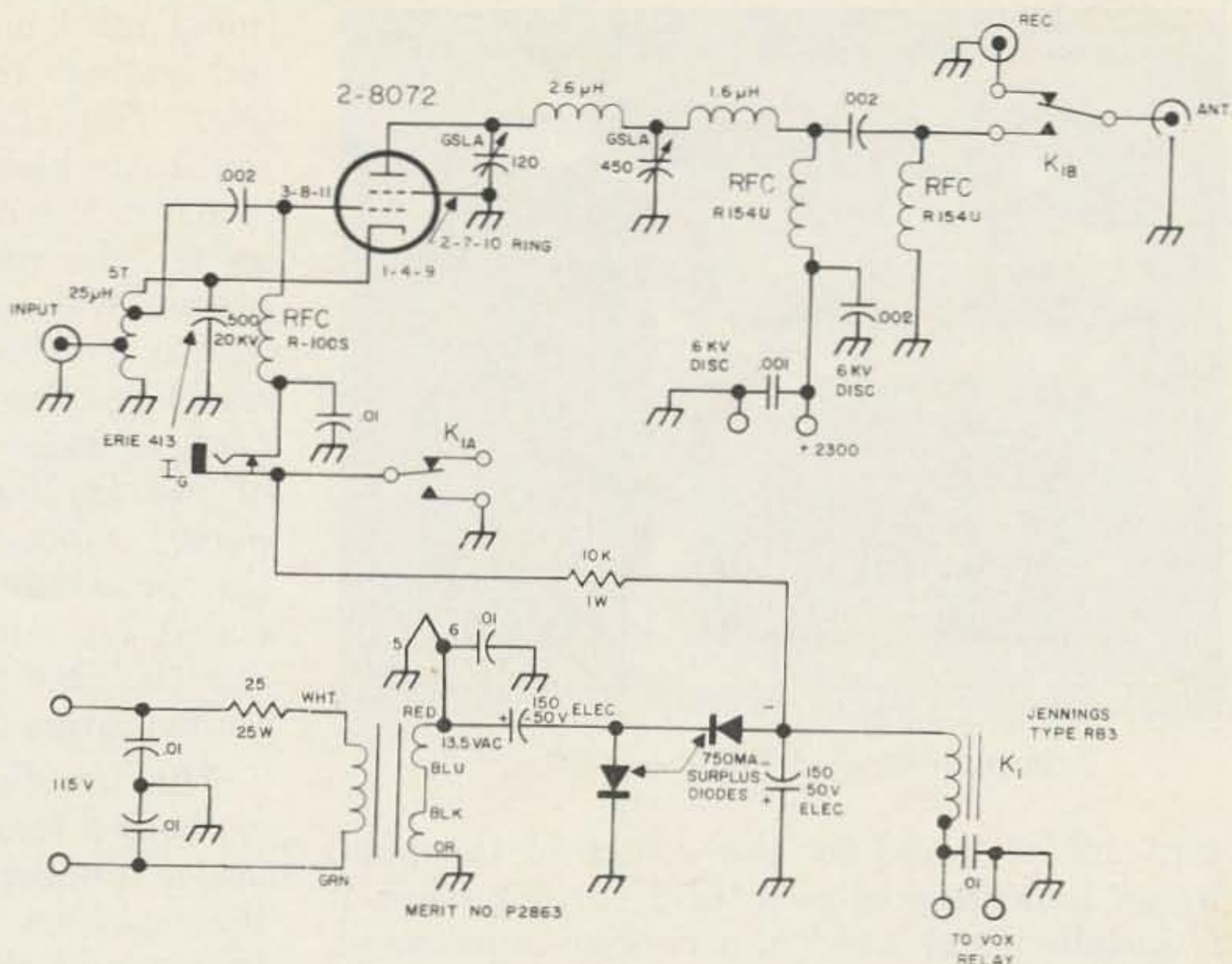


zation application better though the nominal rating is only 100 w and it is the least expensive of the series!

It is possible to reduce the size of the amplifier down to a 7" x 9" chassis. The heat dissipation requirement could not be reduced. A study of the photos will show the over-sized heat sinks that were turned out and installed to handle the plate dissipation by circulation cooling. It will also be noted that the base socket is recessed so that the screen ring seats firmly on the chassis. This turns the chassis into a heat sink for the base of the tube. Adequate circulation cooling for the duty cycle involved with a SSB linear in amateur service is obtained from a 4" fan placed next to the tubes just outside the wide mesh protective screen.


The type 8122 was not considered as required blower and air chimneys would have doubled the size of the amplifier. Some people also object to blower noise. Having a remov-

able heat sink, one does not have to buy new ones when the tubes are replaced, not a small item in tube costs. 72% in this case.


The input circuit shown is not particularly new but it does not seem to be too widely used either by the commercial or home-brew amateur band linear amplifier builders. The hi-C circuit from the cathode to ground gives a short direct path for the circulating rf current. If this is not provided, the current path is projected back to the driver tank load circuit. This can cause instability in the amplifier as well as making the driver hard to load. If the driver and final are together on the same chassis, one properly designed tank circuit will do very well. The usual set-up is for a separate exciter and amplifier where it takes a low impedance path from the cathode (or filament as the case may be) to ground to tie things down. The same LC ratio as shown for the input tank circuit has been used on all bands with good results. The in-

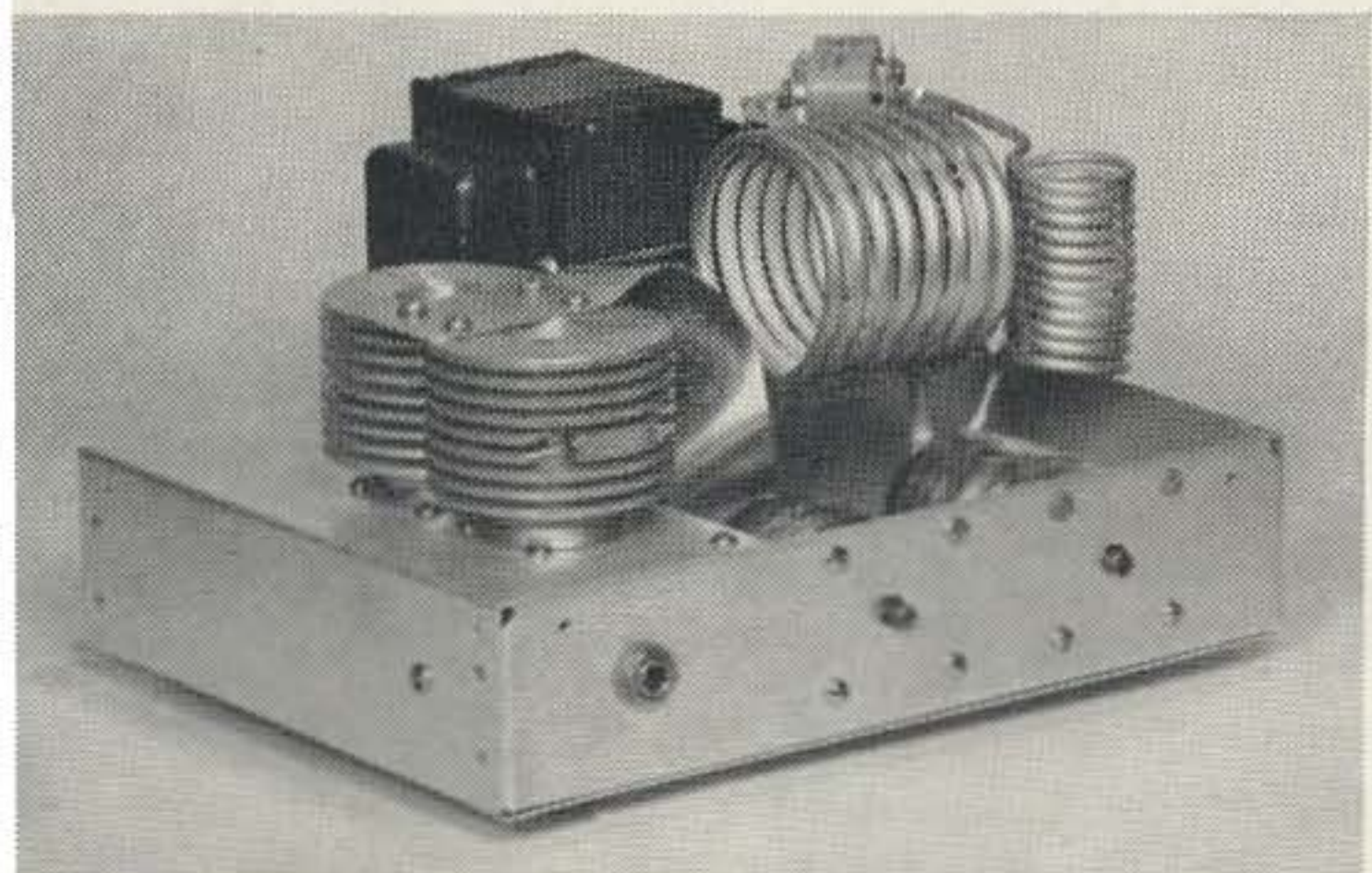

Front view of amplifier.

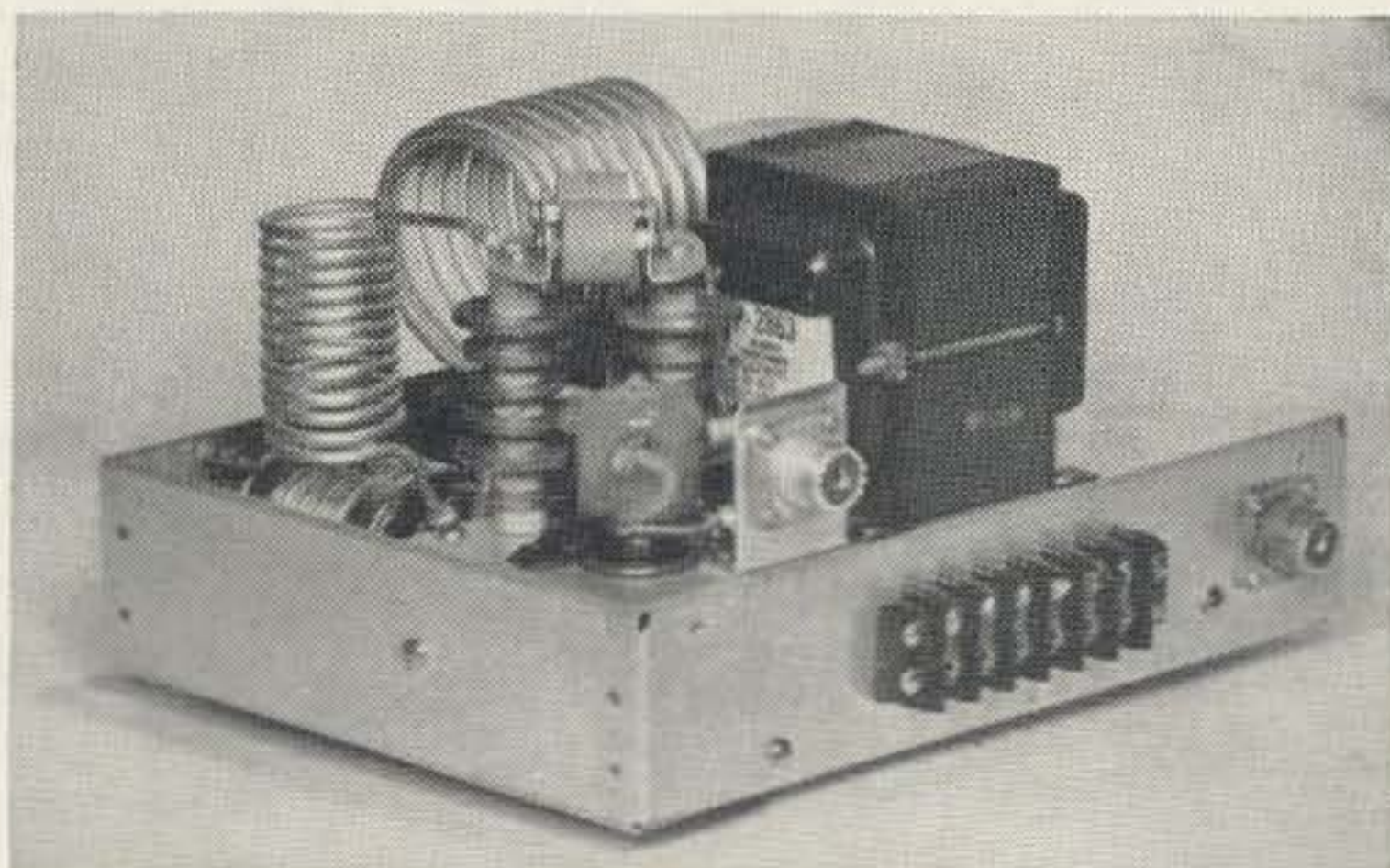

Back view of amplifier.

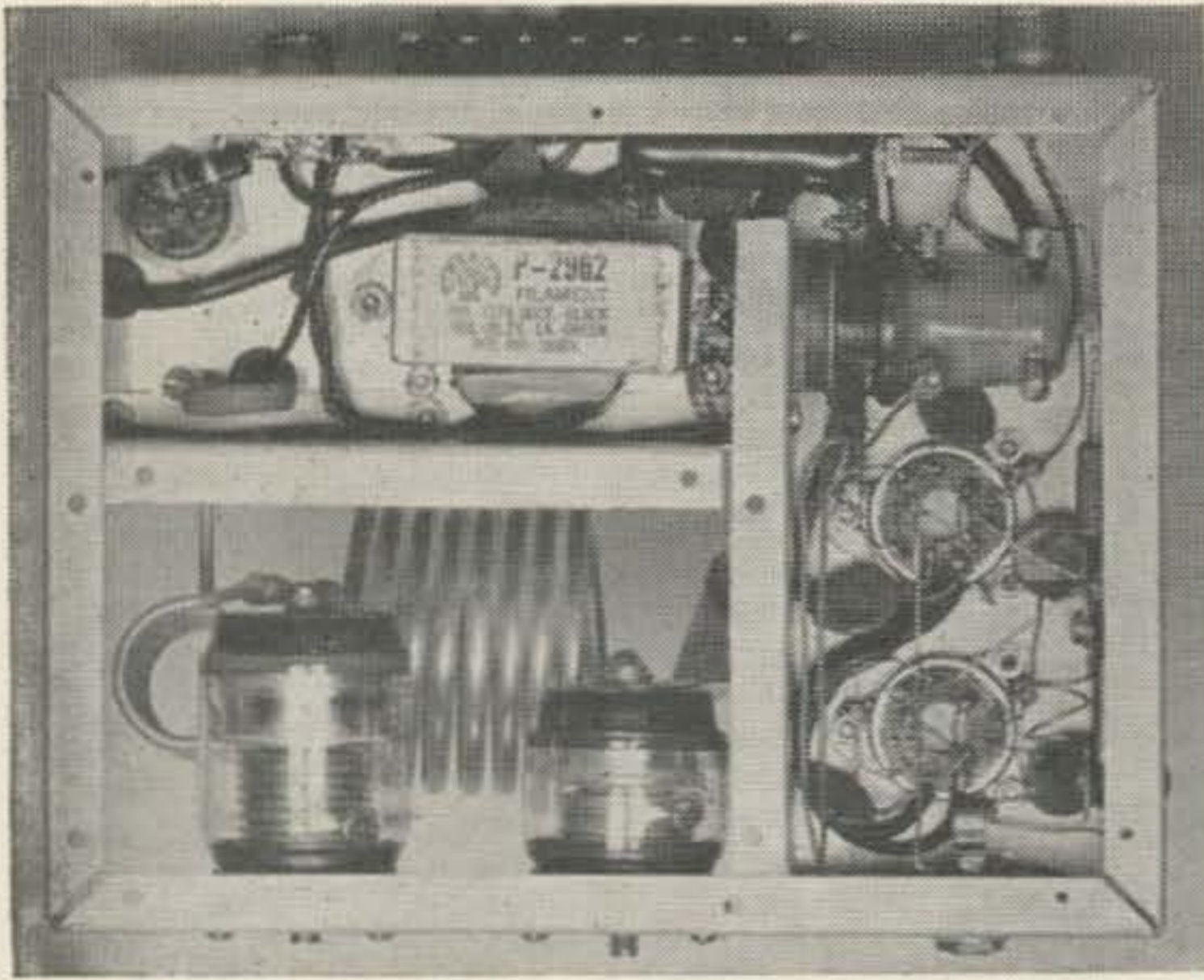

Bottom view of 8072 amplifier.

put tank is tuned for the center of the band by an indication of peak grid current when it is installed and needs no further adjustment.

Varying the spacing of the coil turns simplified things in the amplifier shown. A variable condenser can also be used. Preliminary calculations showed that the amplifier input impedance would not match the usual 52 ohm exciter output impedance. Experimentally the excitation was tapped up from ground to a point where the SWR approached 1:1, which worked out to be a center-tap on the coil. The grid tap on the input coil can also be calculated to equalize the grid and screen currents, but it provided only a starting point. The grid is closer to the cathode and when tied to ground with the screen, the grid current is much higher than the screen current and may exceed the plate current! The calculated point for the grid tap where the grid and screen currents would be equal is about 8.3% of the way down the coil from the cathode. The grid current at this point was well below the 200 ma rating of the two tubes and the amplifier was hard to drive. The tap was placed at one turn from the cathode end which raised the single-tone grid current to a little over 200 ma and brought the drive down to the range of the 100 w exciter. I have heard that distortion checks have been made on grounded-grid amplifiers and no improvement was noted with a tuned input circuit installed, so it was left out. This has never been checked here, but the results would depend on the test set-up. I have always included a low impedance input tank in grounded-grid circuits after having had a pair of 813's "take off" in an amplifier a number of years ago and ending up having to neutralize them.

The plate tank circuit is a little unconven-

tional for ham equipment in that it is series fed rather than the parallel feed usually used. This eliminates the need of a high current plate blocking condenser and the rf choke is across the 52 ohm load, reducing the strain on it. The usual resistor-choke parasitic suppressor was not needed and the plate-to-tank lead is a 1½" wide flexible copper strap which really ties the two together. A pi-L tank circuit configuration was used as it reduced the size of the loading capacitor to an available capacity. Since a lead had to be connected to the pi section anyway it might as well be coiled up into enough inductance to attenuate the 2nd harmonic the 15 db that this configuration is supposed to give.

The transfer relays need not be the rather expensive Jennings vacuum relays used. There are a number of small relays on the market that can be built into the linear amplifiers that would eliminate the expensive (count all the fittings too), bulky and clacking coaxial relays on the wall or on the back of the amplifier. I never could quite understand why this was not done but then maybe everybody but me owns stock in a coaxial relay company! There is nothing coaxial inside of the amplifier so no discontinuities will occur. In this particular application the extra contacts came in handy to apply a blocking bias. The static I_p is about 120 ma with 2300 v on the plates. The -40 v (no load) bias in standby drops the I_p to about 40 ma which lowers the static dissipation and helps with the cooling.

The filament transformer used is the only one that could be found available. It is rated at a higher current than required which made the filament voltage a volt too high. This required the series 25 ohm resistor in the primary which would not be needed if a 13.5 v under load filament transformer can be found.

The adjustment of this linear amplifier or any linear amplifier is quite simple with a 'scope and envelop detector to produce a trapezoid pattern when a two-tone test signal is used. There are probably other methods of tuning up linears, judging from the carrier and "hello test" one hears on the air, but I do not know of any good ones. A dummy load is connected to the output and the load condenser is set near the high capacity end. Feed in enough two-tone signal to produce 200-250 ma of plate current. Tune the tank input condenser for resonance or maximum rf output as indicated on the 'scope or a meter on the dummy load. Now turn up the gain momentarily to 550 ma and see if there are nice clean peaks on the 'scope pattern.

Here's the SPECTACULAR NEW ALL TRANSISTOR SBT-3 SSB TRANSCEIVER

PRICED AT ONLY \$299⁵⁰

SPECIFICATIONS

Freq. Range: 3780-4010 KC, 7180-7320 KC, 14130-14360 KC
Semiconductors: 2—8042 instant heating tubes, 18 transistors,
2—varicaps, 1—zener, 9 diodes


Size: 4 3/8" H x 11 3/8" W x 8 3/4" D. Weight 10 lbs.

TRANSMITTER

Power Input: 165W pep
Carrier Suppression: —45 DB
S.B. Selection: 80-40M lower
20M upper
Unwanted SB: —40 DB
Ant. Imped.: 30-100 ohm adj.
Power Consumption: .5 amps
Receive, 12-15 amps
SSB XMIT.
Operation: P. T. T. No tube
filament on in rec.

RECEIVER

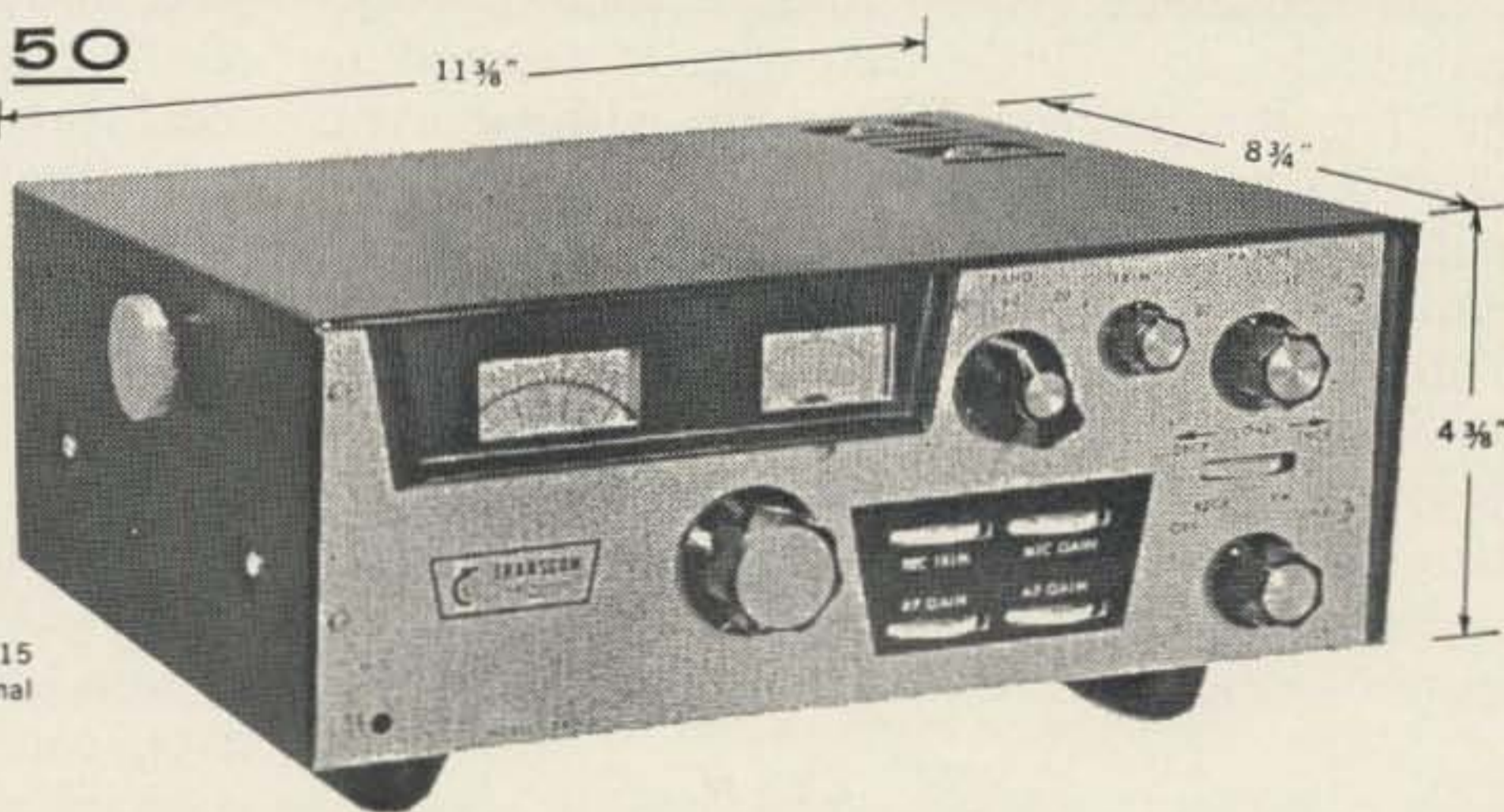Sensitivity: .5 μ v for 10 DB
S + N/N
Selectivity: 3 KC @ 6 DB
Spurious: Image better than
60 DB
Stability: Less 100 cps in any 15
min. period under normal
ambient conditions
Audio Output: 2 watts



TRANSCOM ELECTRONICS, INC.

375 HALE AVENUE

ESCONDIDO, CALIFORNIA

Keep decreasing the output or load capacitor and re-peaking the input or tuning capacitor until the peaks start to flatten at the 550 ma point then back off until they just do not. The point is rather sharp. A few per cent change in the load capacitor will make the difference whether there is flat-topping or not. When later checking with the antenna it would be best to rotate the beam 360° and set the loading at a point where there is no flat-topping at any point in the rotation in case there is any load variation. Now remove the tone generator, plug in the mike and set the gain to talk-up to about 400 ma or a voice average 2KW. The peaks on the 'scope will still be of the same amplitude so there is still "2 KW pep output". Do not worry if the 'micro-match' only averages a couple of hundred watts or so as it won't follow the peaks up to 1200 w or so, but they are there. In case somebody checks my math, they will find 1800 w pep and 900 w voice average input was used. This allows for the driver power input which adds to the amplifier input in series and the total must be no more than 1000 w. Most of the drive power is fed through the amplifier and adds to the output power. I once worked a chap that said since he bought a KW transmitter he wanted to see it indicated on the

output meter. I am glad that I did not live next door!

The above tuning procedure can be applied to any amplifier at any power level. There was no curvature on the 'scope pattern so it was concluded the tubes have good linear characteristics connected as hi-mu triodes. The exciter that was used to drive the amplifier under test had 3rd harmonic distortion down 30 db. It was still 30 db on the spectrum analyzer, out of the amplifier. That is a usable figure so the tests were concluded.


Prior to the final modification there was an input cut out relay in the circuit as shown in the underside photo. A switch turned ON in series with the VOX relay line at the control position allows a 10 db boost of the signal over the 100 w exciter. Leaving it OFF if it is not needed complies with good operating practice as well as the letter of the law. As shown in the final form any desired power reduction can be obtained by turning down the microphone gain control which can be calibrated in db.

Thanks for the helpful suggestions that guided the application of the RCA 8072 tubes goes to Mr. H. C. Vance, K2FF, Manager, Sales Engineering of the RCA Tube Division.

... K4ZZV

Eico 720-730

The article in the March, 1963, issue of 73 on the mode switch for the Eico 720-730 led me to do a little thinking. It seemed to me that the job could be done without extra wires leading between the units. The resulting modification is shown here. It has several advantages over the WØDSU scheme. First, the plate supply switch, S-2, may be left intact. Second, one switch is used to turn on the ac to the 730 and select AM or CW. Last, no external wires are needed. The existing wiring between J-5 on the modulator and the transmitter do the job.

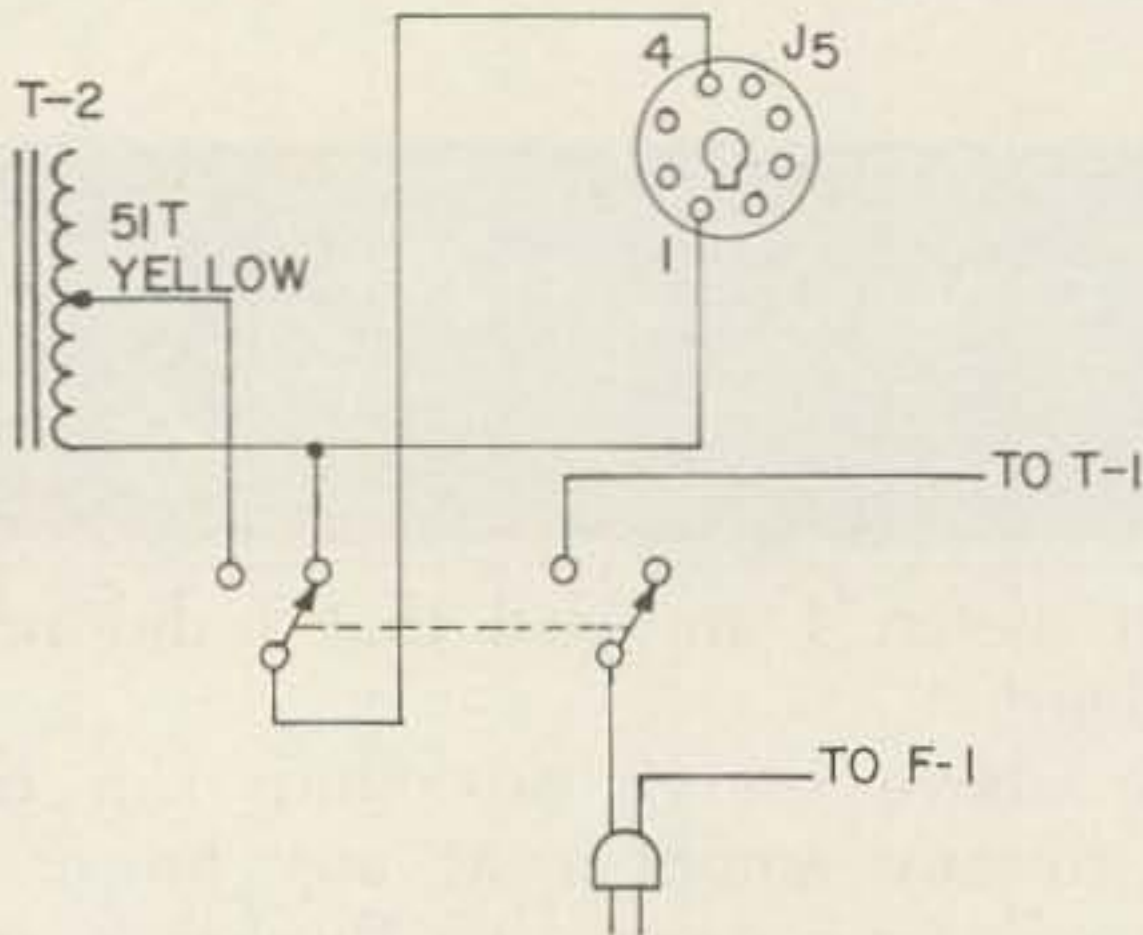


Modifications to 720 and 730.

The only part needed for this modification is a dpdt switch to replace S-1 in the original 730. A two lug terminal strip is nice, but not necessary. First remove the original ac switch S-1. Replace it with a dpdt switch and reconnect the wires removed from S-1 so that when the new switch is in the on position, ac is provided to the modulator. Next disconnect the yellow modulation transformer lead from pin 4 of octal socket J-5. At this time I replaced the single lug terminal strip TB-5 with a two lug strip, using one lug as before and connecting the yellow lead to the other. This step can be eliminated, however, and a wire spliced directly to the yellow lead. In any event the yellow modulation transformer lead is wired to the dpdt switch on the *on* side of the switch. Wire pin 1 of J-5 to the *off* side and pin 4 of J-5 to the common lug of the switch and the modification is complete.

Now when the switch is off, the secondary of the modulation transformer T-2 is bypassed for transmitter B+. When the switch is on, ac is provided to the modulator and the secondary of the modulation transformer is placed in the transmitter B+ circuit.

... WA4DQS

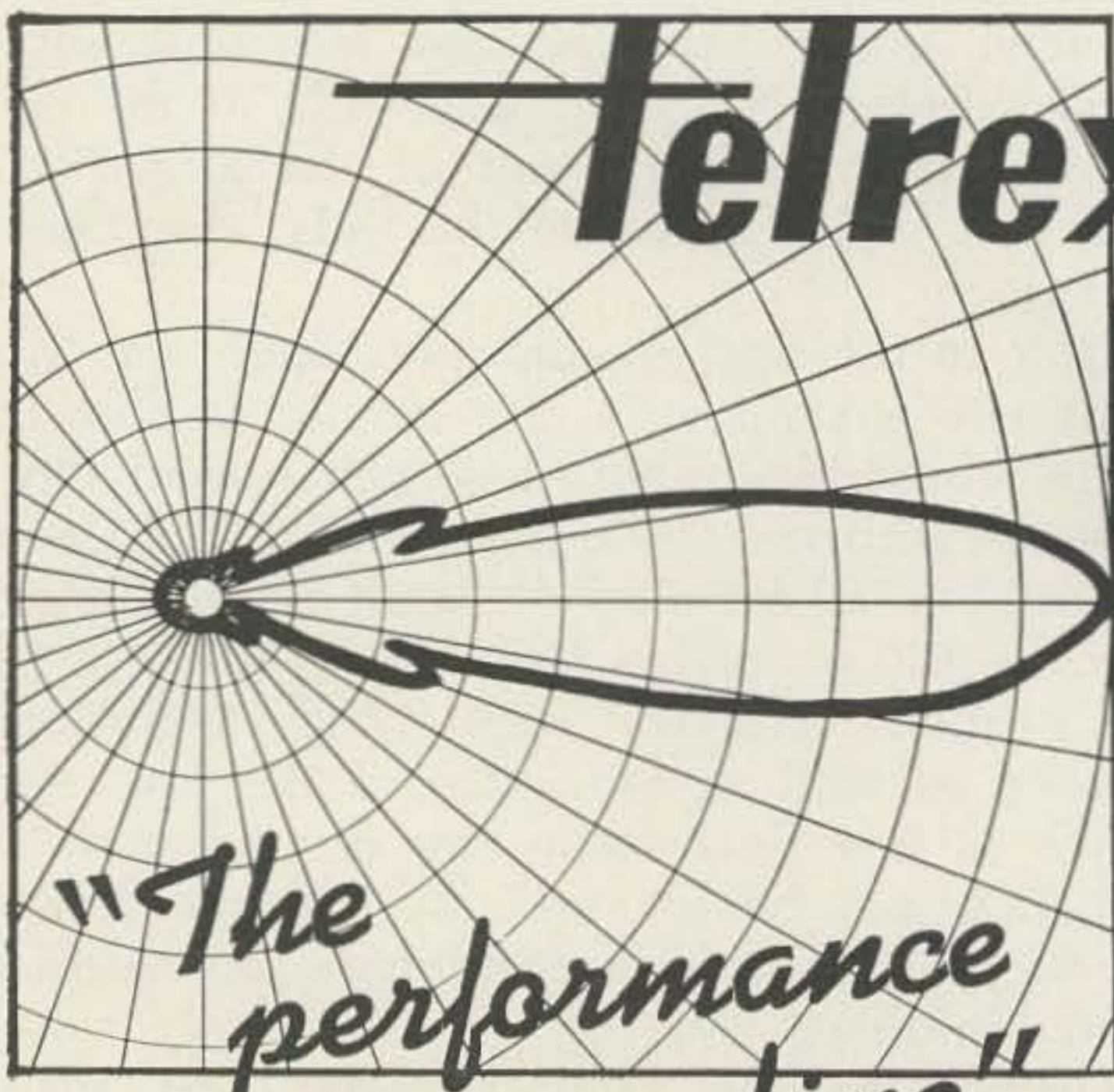

"The performance with a line"

MATERIAL DIFFERENCE
—IN USE IN 135 LANDS!

"BEAMED-POWER" ANTENNAS and ANTENNA SYSTEMS

The Choice of the Discriminating Communication Engineer . . . the Man who Never Settles for Anything Less than THE-VERY-BEST!

You too—can enjoy world renowned TELREX performance and value! Send for PL65 condensed data and pricing catalog, describing the lowest priced antennas on the market, in relation to materials and performance! Expanded data sheets—including your favorite band, are also available.

ANTENNAS
SINCE
1921

COMMUNICATION SYSTEM
telrex LABORATORIE

ASBURY PARK 25, NEW JERSEY, U.S.A.

Now!

for discriminating amateurs
who are satisfied
with nothing less than *THE VERY BEST*

McCoy SINGLE SIDE BAND FILTERS

The GOLDEN GUARDIAN (48B1)

TECHNICAL DATA

Impedance: 640 Ohms in and out (unbalanced to ground)

Unwanted Side Band Rejection: Greater than 55db


Passband Ripple: $\pm .5$ db

Shape factor: 6 to 20db
1.15 to 1

Shape factor: 6 to 50db
1.44 to 1

Package Size: $2\frac{7}{16}$ " x $1\frac{19}{32}$ " x 1"

Price: \$42.95 Each

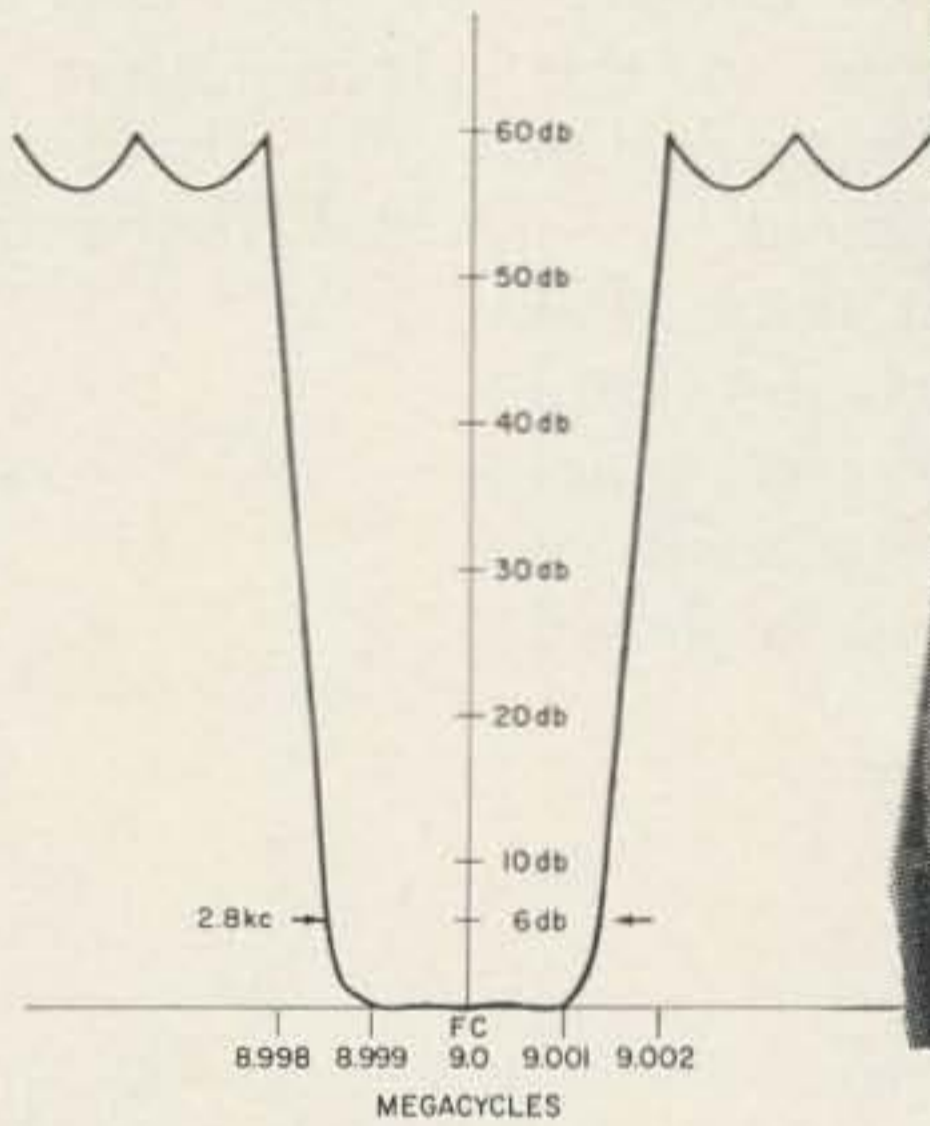

The SILVER SENTINEL (32B1)

TECHNICAL DATA

Impedance: 560 Ohms in and out

Unwanted Side Band Rejection: Greater than 40db



Passband Ripple: $\pm .5$ db

Shape factor: 6 to 20db
1.21 to 1

Shape factor: 6 to 50db
1.56 to 1

Package Size: $1\frac{3}{4}$ " x $1\frac{1}{4}$ " x 1"

Price: \$32.95 Each

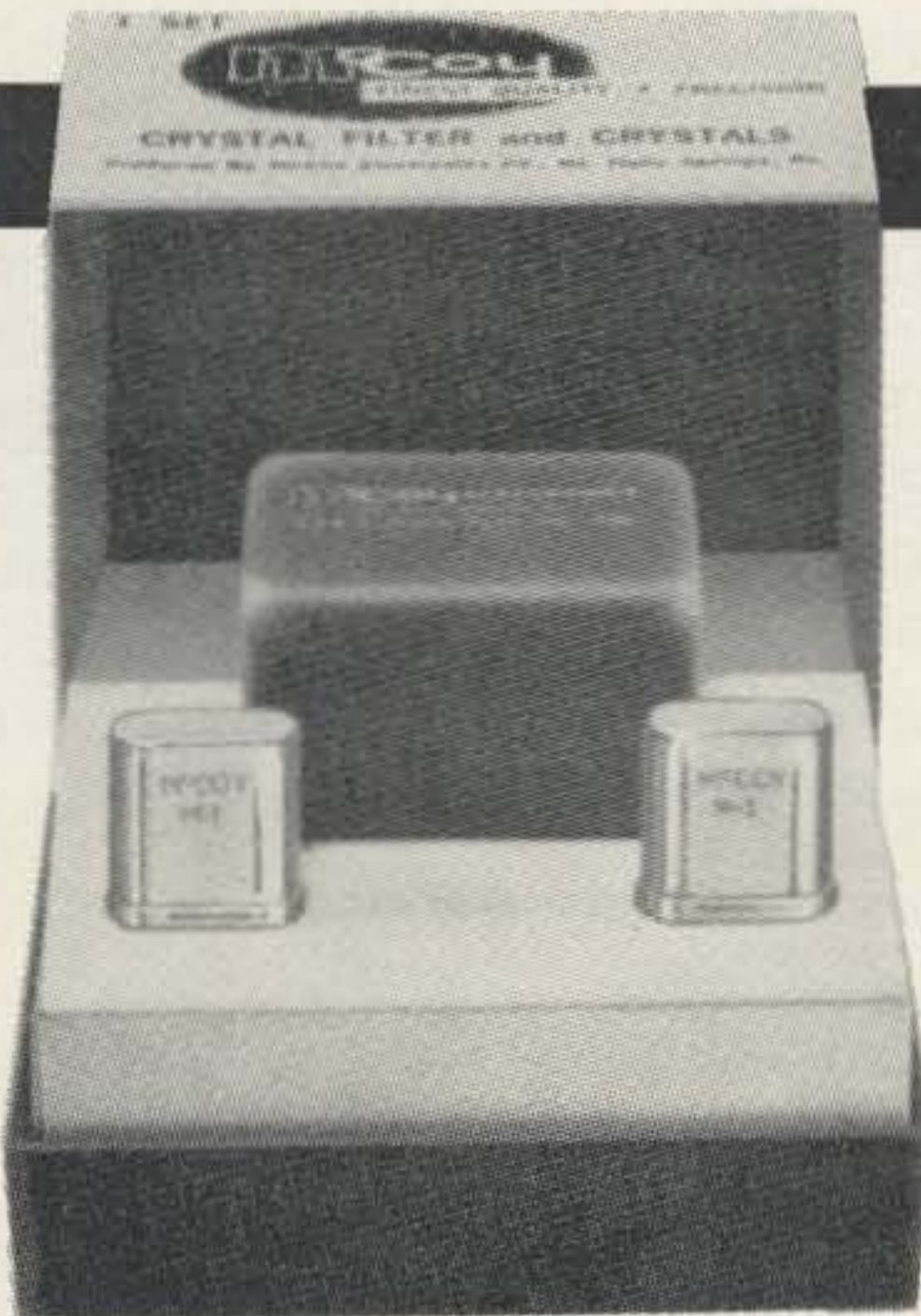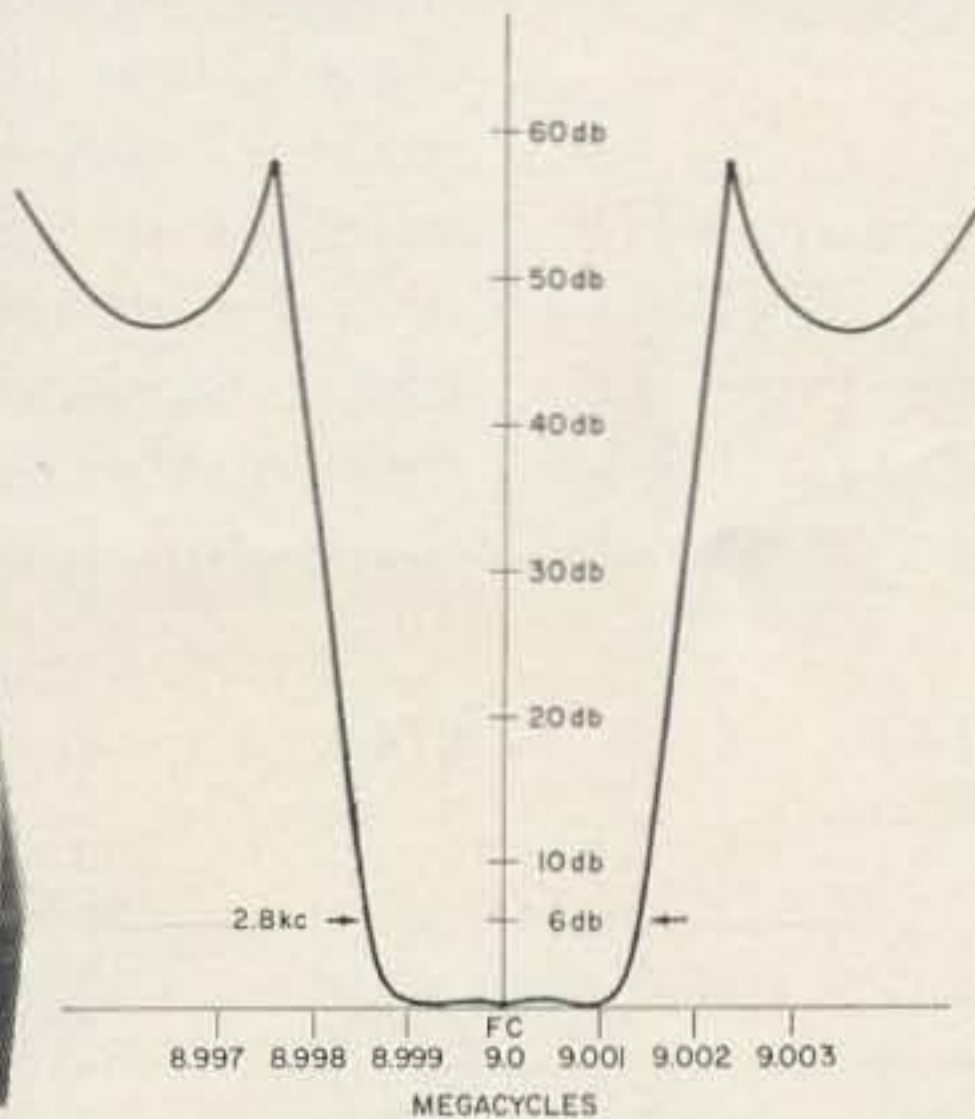

Both the Golden Guardian and the Silver Sentinel contain a precision McCoy filter and two of the famous M-1 McCoy Oscillator crystals. By switching crystals

either upper or lower side band operation may be selected. Balanced modulator circuit will be supplied upon request.

Both sets are available through leading distributors. To obtain the name of the distributor nearest you, or for additional specific information, write: Dept. E-11



MCCOY ELECTRONICS COMPANY

Mt. Holly Springs, Pa.

Tel. 717-486-3411 TWX: 717-486-3400

A SUBSIDIARY OF OAK ELECTRO/NETICS CORP

Simplified Solid State

Transistor circuitry is really simple. It is not as complicated as vacuum tube circuitry for most applications. The purpose of this article is to show just how easy it is to design and build transistorized ham equipment.

For most rf equipment, the first thing that is needed is an oscillator. The overtone crystal oscillator is the easiest, cheapest and most practical way of generating stable rf signals in the VHF spectrum. The basic circuit is shown

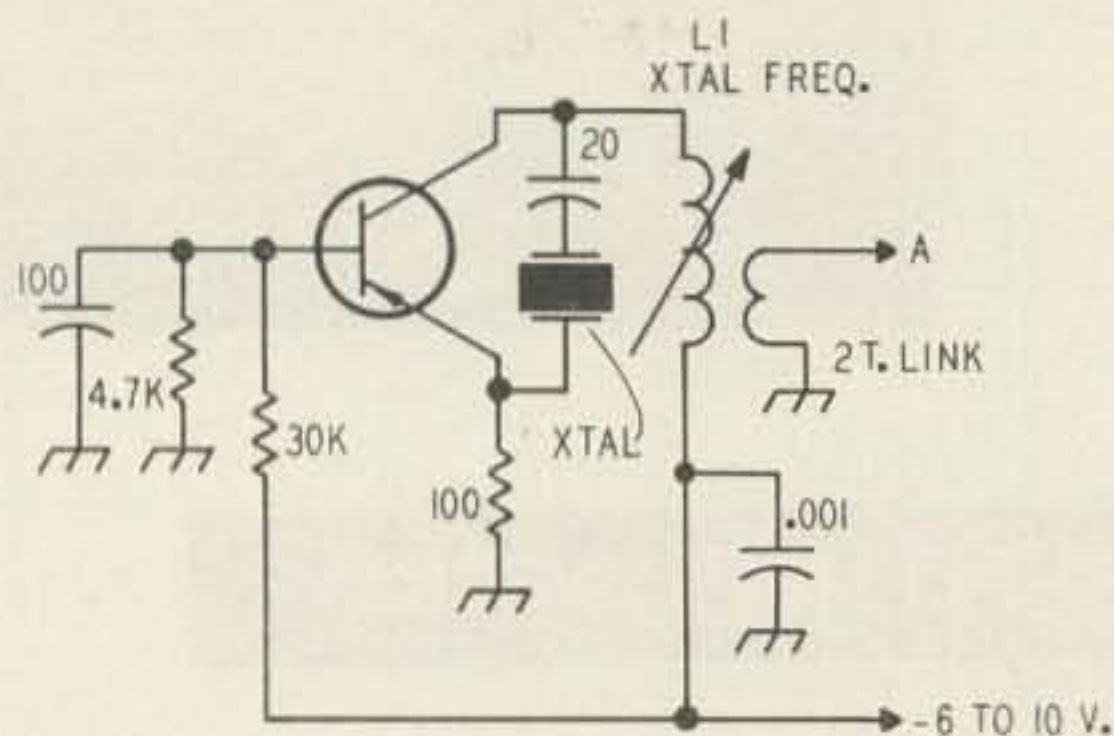


Fig. 1. Overtone oscillator.

in Fig. 1. The transistor can be any VHF oscillator type, such as the RT82, 2N1744, etc. The crystal is a third overtone type. L1 is a slug tuned coil tuned to the crystal frequency. A link of two or three turns of wire is

wound over the coil for coupling to the next stage. This is the basic oscillator for VHF transmitters and converters. It is stable and just about idiot-proof. L1 is tuned to the xtal frequency to make it oscillate.

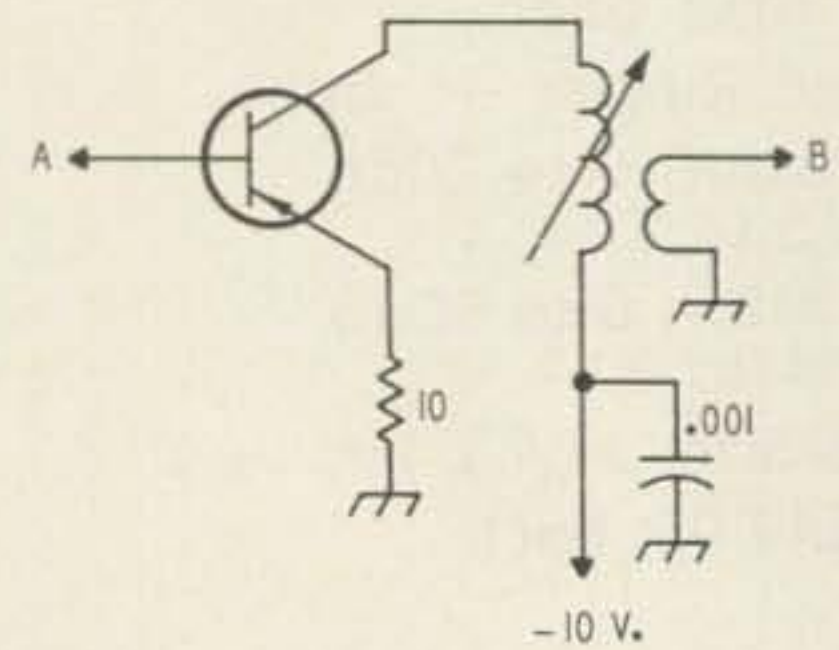


Fig. 2. Class C amplifier or buffer.

For a transmitter, the next thing needed is a final, buffer, or frequency multiplier, depending upon the application. Just about the simplest transistor circuit that exists is the class C amplifier shown in Fig. 2. The emitter resistor can be omitted. Depending upon whether it will be used for a buffer, a final, or a frequency multiplier, the tuned circuit is tuned to either the input frequency or a multiple of the input frequency. It is hard to get drive for future stages if the frequency is

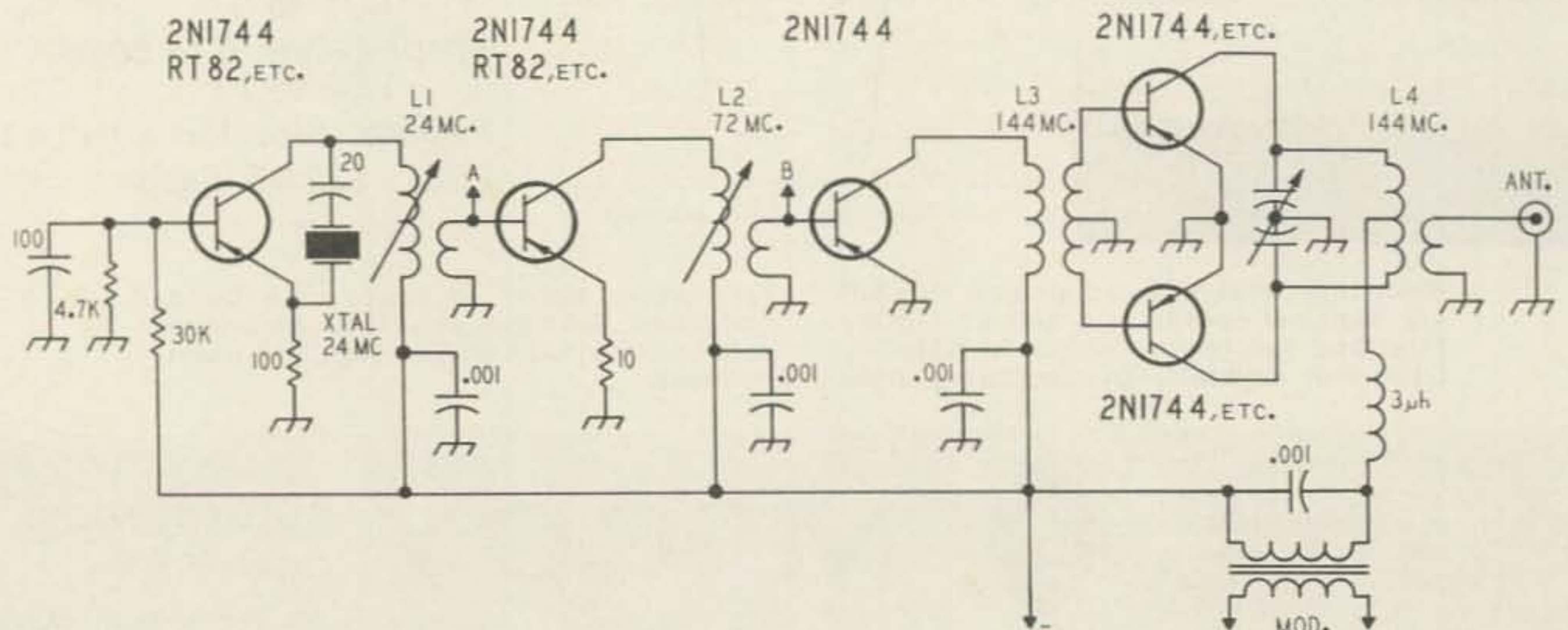


Fig. 3. Two meter transmitter.

being multiplied more than three times, so limit the frequency multipliers to triplers. The stage is biased beyond cutoff with no drive, so no additional protective bias is needed. Excitation is measured by collector current.

Fig. 3 shows a possible application of the previous circuits combined to form a two meter transmitter. It is a perfect example of solid state simplicity.

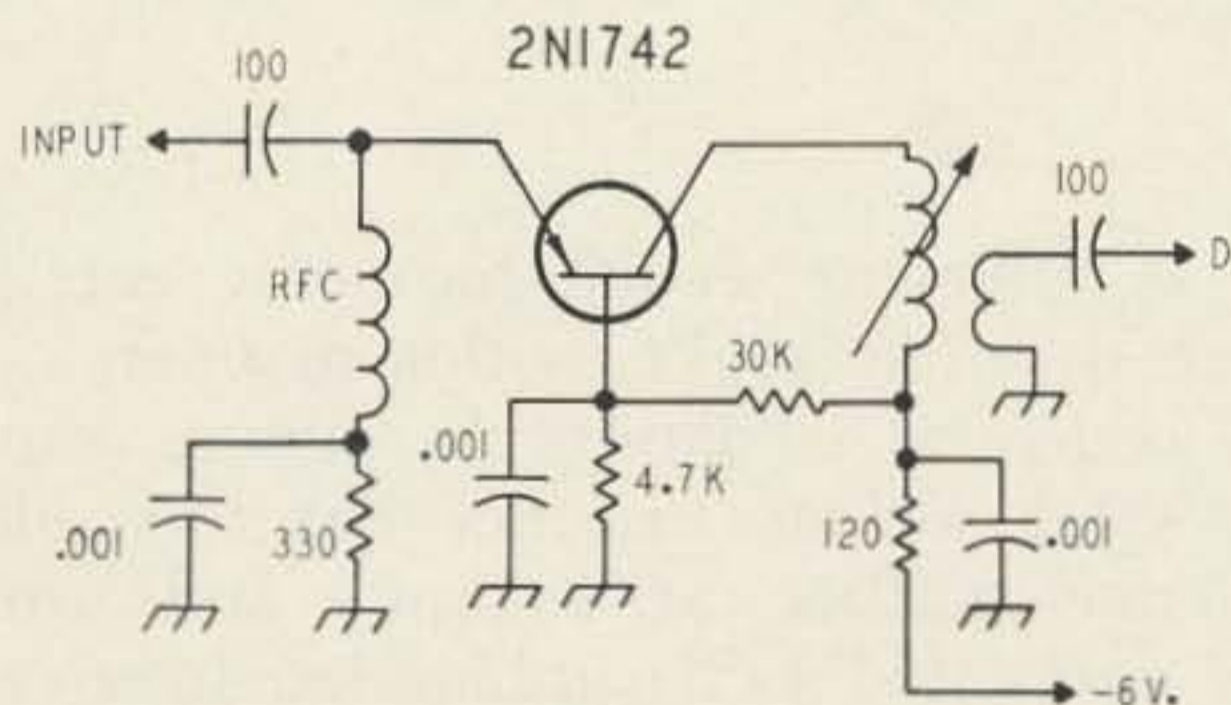


Fig. 4. Grounded base rf amplifier.

Converters are also simple. Fig. 4 shows a grounded base rf amplifier. The rf choke and coil are chosen for the frequency being amplified. One or more of these rf stages may be used before the mixer.

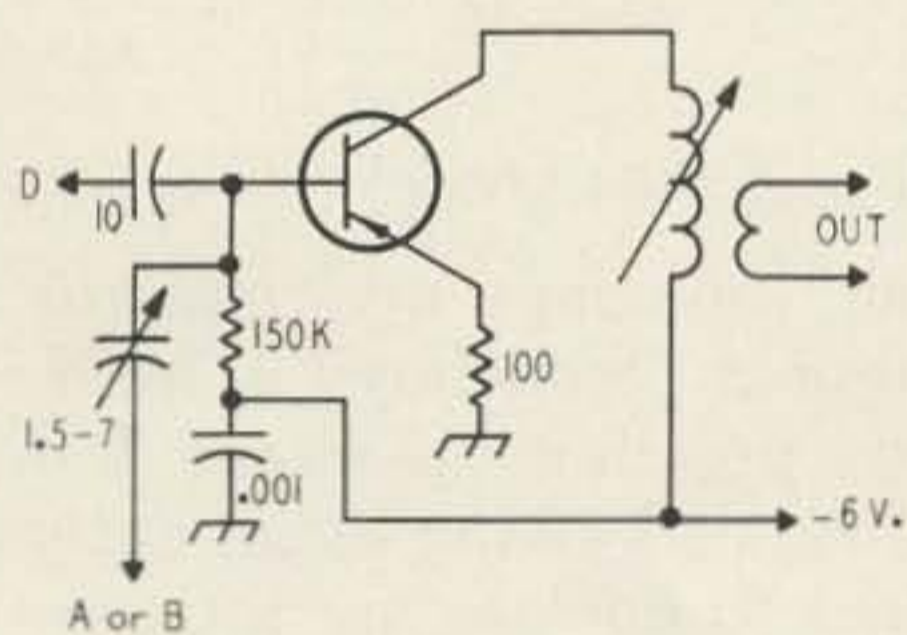


Fig. 5. Mixer.

The mixer is shown in Fig. 5. Point D is connected to the preceding rf stage. Point A or B goes to either an oscillator or a frequency multiplier chain as shown in Fig. 1, 2 and 3. The output can either go to a receiver or to another mixer for multiple conversion. These circuits are good up to about 250 or 300 mc. The values shown are typical values, although they may have to be changed slightly to get optimum performance from particular transistors.

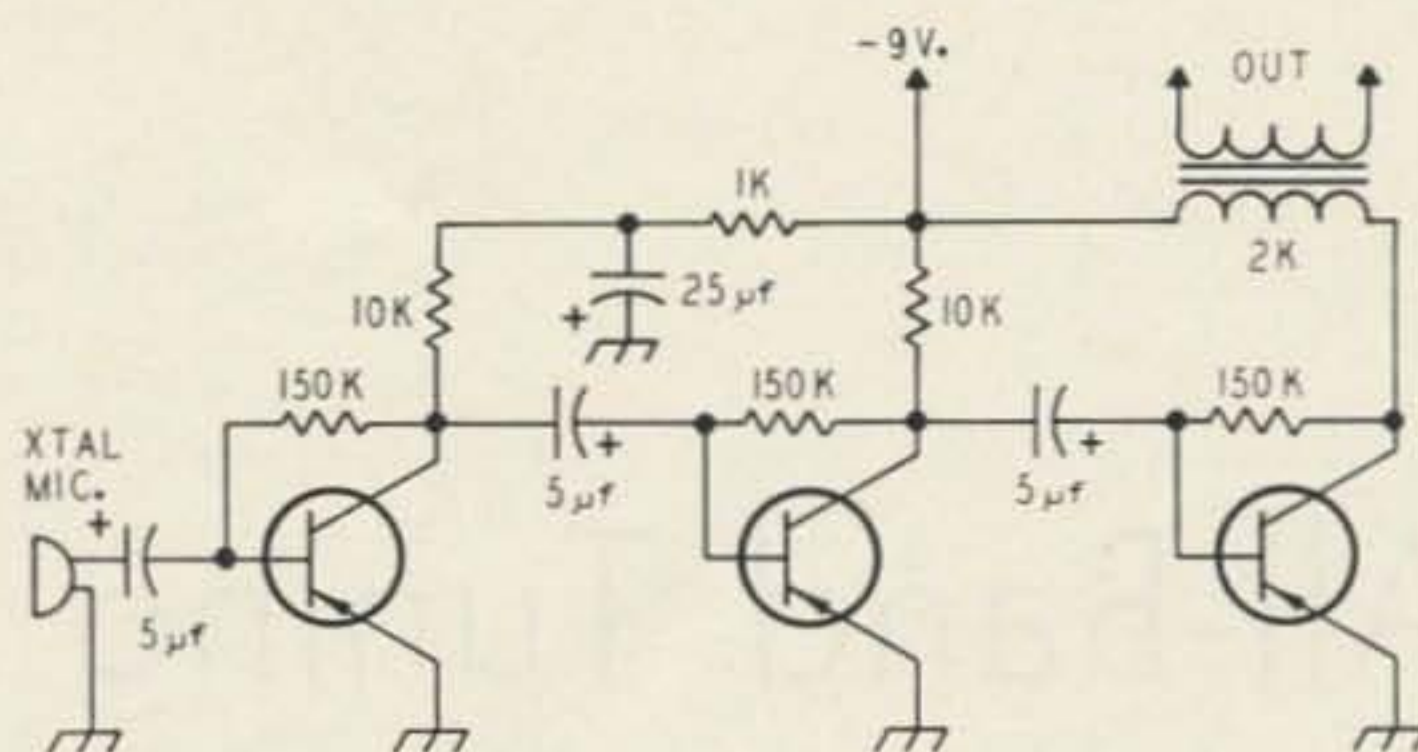


Fig. 6. Audio amplifier and modulator.

Fig. 6 shows a general purpose audio amplifier that can be used as a speech amp, a low power modulator, or an audio monitor amp for a receiver. The transistors are general purpose PNP audio types, available for a few cents. The secondary impedance of the transformer is chosen for the application.

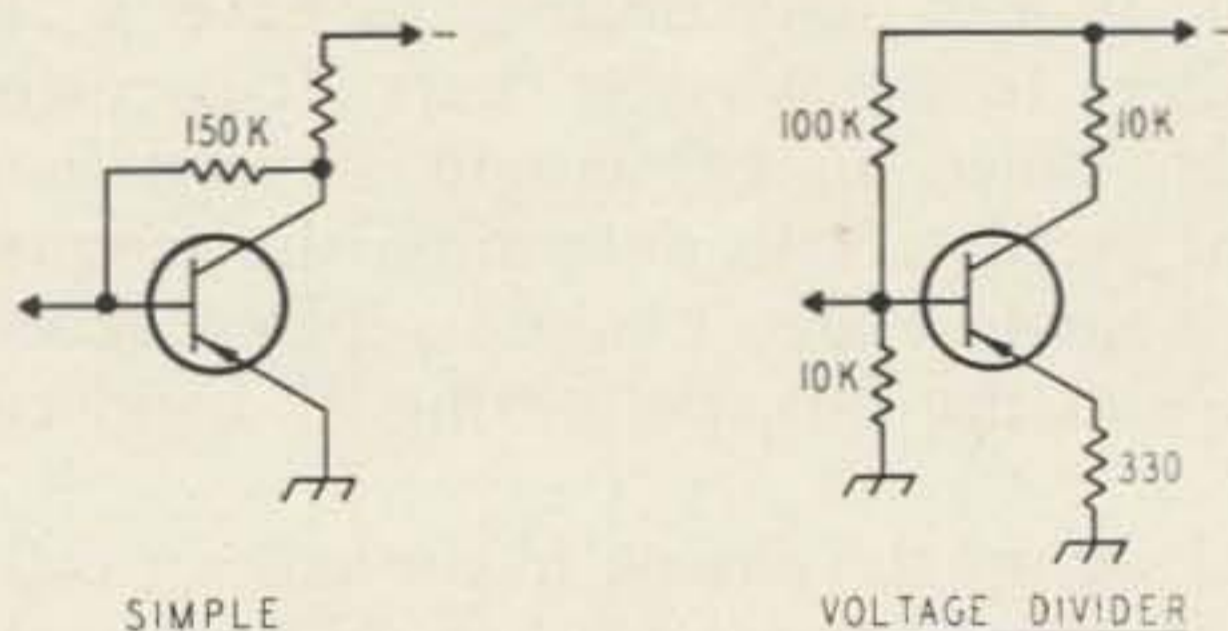


Fig. 7. Biasing methods.

Fig. 7 shows two possible methods of biasing a class A amplifier. The first is the simple bias resistor method, which is cheap and easy, although it does not have the dc and thermal stability of the second method. For audio amplifiers, etc., the first is adequate. For rf amplifiers, the second is preferable.

The above should be a useful outline for designing transistorized equipment. While it does not go into all the possible circuits or applications, or go into any great detail, it should provide a starting point for design work. When values are given, they are only typical values, to be used as a starting point in trying to optimize any design. I hope that this will be of value or at least give you a few ideas when you decide to design some solid state gear.

... WA2INM/1



TELREX ROTATOR-INDICATOR SYSTEM MODEL TS250-RIS

Mast Feeds Thru Rotator For Safe, Easier, Installation

- 1300 IN./LBS ROTATION TORQUE
- SELF LOCKING BY STURDY WORM GEARS
- SELSYN AZIMUTH INDICATION
- ACCOMMODATES 2" O.D. MASTING
- MALLEABLE CAST MASTING CLAMP SUPPLIED
- OUTPUT SPEED APPROX. 1 RPM
- WILL FIT INTO OR ONTO A 6" SIDED TOWER

A Really Sturdy
ROTATOR-INDICATOR
SYSTEM
NOT a Modified
TV Rotator!
Designed To
Out-Perform, Outlast!

\$25000
F.O.B.

ALSO:

- TS325-RIS \$325.00
- TS435-RIS \$435.00
- TS535-RIS \$535.00
- TS585-RIS \$585.00

TELREX LABS.
ASBURY PARK, N.J.



Write for FREE PL65 Describing Rotators and Antennas

All-Band Tuning for the Drake 2B?

When I read WN4QGQ's item in November 73 about the use of the crystals supplied with the Drake 2-B to obtain band segments not originally intended, I was reminded of a similar article that appeared in the July '62 issue of QST. The crystal switching approach strikes me as a lot of monkeyshines for so little benefit if it is only desired to have a "look" elsewhere to see what is there. It occurred to me that since an LC circuit is used in non-crystal oscillators to determine the frequency, a variable LC circuit might replace accessory crystals in the 2-B, permitting all-band coverage.

Picking up the closest likely looking coil and capacitor from the junk box (19 turns B&W 3004 and a National 100 pf transmitting variable), I was pleasantly surprised to find that the combination would tune from about 8 to 27 mc. Adding about 18" of RG-58/U loused that up until I inserted a 33 pf disc ceramic in series with the center conductor. I still could not get above about 21 mc. I attached the other end of the coax to a piece of surplus circuit board, cut down to about $\frac{3}{4}$ " \times 1", as shown in Fig. 1. Of course the copper conductors were peeled off first, and then the holes drilled to support the wires. I used resistor trimmings (tinned #18) for the pins.

With the circuit tuned to 12 mc, I was able to copy both sides of a CB ragchew between a local and one about 30 miles from here. The preselector was at about $9\frac{1}{4}$, and it was the E position, I believe. This indicated to me that

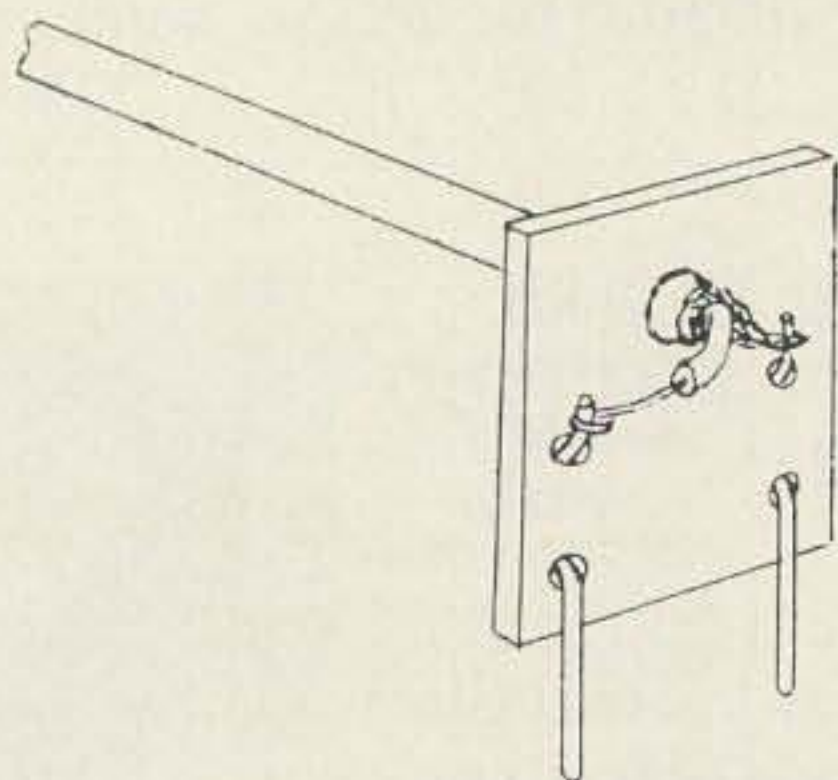


Fig 1. Single dummy crystal.

there is sufficient second harmonic energy to replace overtone rocks in this manner.

Of course it is natural to picture ganging the crystal sockets together (as the selector picks one position at a time) and using a single calibrated LC combination to give the full coverage desired. Just add (or subtract) the 3.5 to 4.1 mc *if* (I find 3.8 mc to band center easier) to the LC frequency. This could even be taken into account when calibrating.

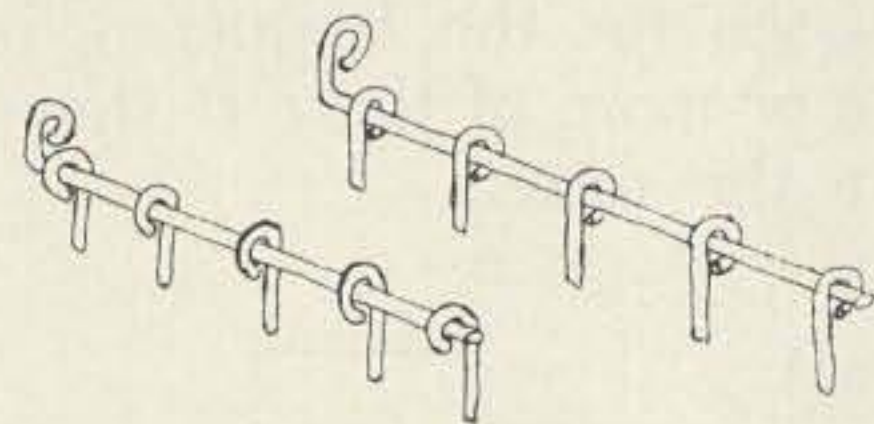


Fig. 2. Buss crystal connections.



You can imagine my chagrin when I couldn't repeat. Somehow a local 80 meter station kept popping up where I didn't want him. Was the coil acting as an antenna? I dug up a cabinet to enclose my little jewel. It still didn't work. In checking the Drake schematic, I learned that the "E" position is not connected as are the other 4, so I cut off the pins to the "E" socket. And it still wouldn't seem to work again. I removed my bus conductors from the crystal sockets, and tried the single dummy again. No better. That local on 80 was still in there pitching. So I switched to 80 and yakked a while.

While playing with this thing, I found that I could inject the grid-dipper oscillator frequency into the receiver through this combination, and come up with new band segments. Then in trying to rig up a transistor oscillator (on the same LC combination) I couldn't get it to take off.

But rather than let this project suffer the fate that seems to have befallen about 20 other projects that are in various stages of progress(?) in my shop, I felt that maybe someone who knows more about what he is doing would like to take it from here. Be my guest.

... K9LTD

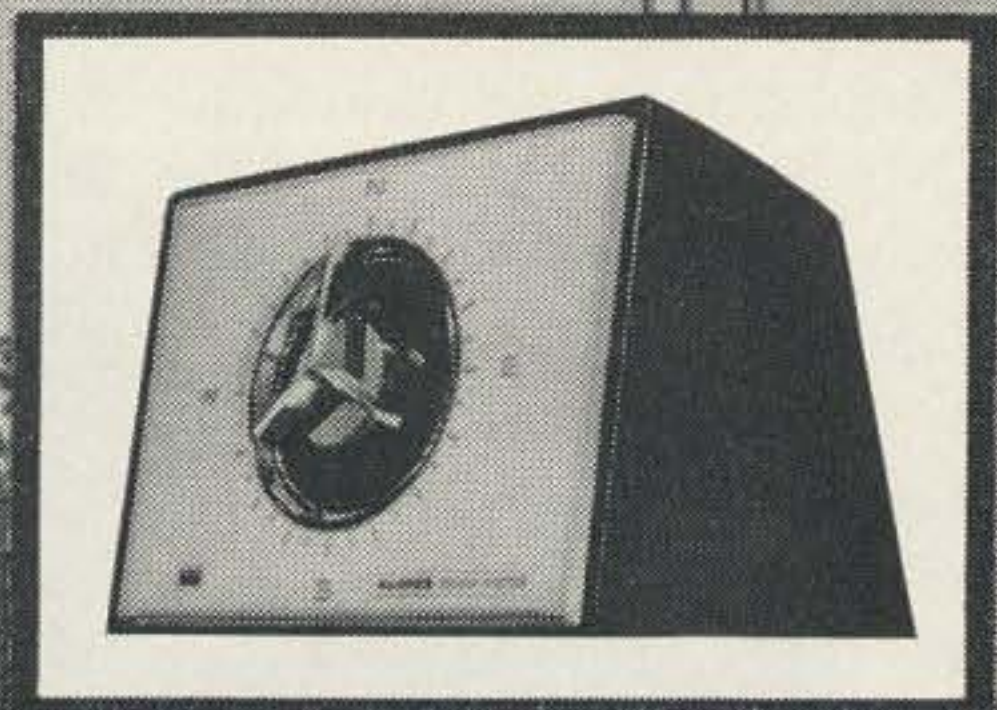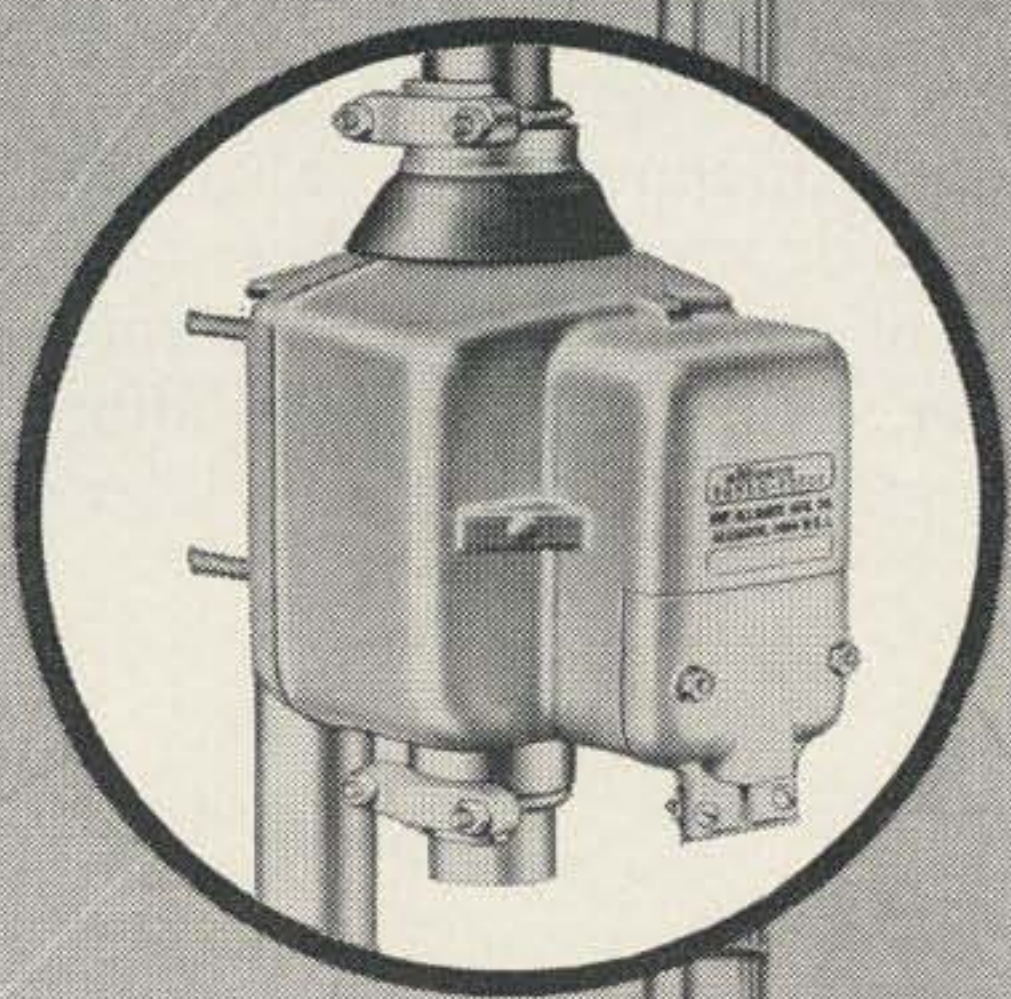ALLIANCE Tenna-Rotor[®] for 10-15-20 Tri-Bander Ham Installations



Tenna-Rotor stands up under severe conditions. Tests prove it is the strongest, most durable antenna rotator available for amateur use on all antennas up to 25 sq. feet in cross section, including six element 10-15-20 Tri-bander antennas.

This latest Alliance Tenna-Rotor will turn heavy antennas and is designed to withstand wind velocities to 90 m.p.h. in accordance with E. I. A. wind loading standards. The patented rigid offset design distributes the load resulting in superior strength to weight ratio for greater ease of installation. Features anti-windmilling, gearing and brake system to maintain positive positioning and eliminate overtravel. Unit, enclosed in a sturdy, ribbed die-cast zinc housing, is lightweight and simple to set up. If you can lift your antenna and put it on the Tenna-Rotor... it will support it, hold it and turn it.

- New Precision Machined Steel Drive Gear
- Greatest Positioning Accuracy Possible

The new Alliance transistorized automatic C-225 features a patented phase-sensing bridge similar to laboratory test equipment and is now available exclusively from Alliance for HAM users. Affords automatic, stepless, synchronous pinpoint positioning accuracy throughout 360° of rotation that reduces or eliminates interference.

All this with noiseless control.



The **ALLIANCE**
Manufacturing Company, Inc.

(Subsidiary of Consolidated Electronics Industries Corp.)

ALLIANCE, OHIO

CSA approved

When Standard Switches Won't Fit

Modification and updating of equipment almost invariably calls for addition of functions, which need more controls than were originally supplied with the equipment. In most instances, the panel does not have enough room for the added controls, and space inside the chassis is not too plentiful.

Back in the days when one Shicklgruber was still a struggling artist about one third of this problem was solved by the manufacturers of potentiometers, who attached a switch to their product, so that when the audio volume was turned full off (CCW), the switch opened. Combined potentiometers and switches are used on a wide variety of electronic devices, from your wife's "kitchen radio" to the GPR-90 you wish you could afford.

With the coming of the TV boom dual controls with concentric shafts were introduced. These range in quality from the mechanical abortions used on cheap TV sets to the beautifully-built and smoothly-working dual controls used on Tektronix oscilloscopes, and other items of premium equipment. In many


instances, already-made dual concentric controls will solve your specific problem, with a minimum of labor and a minimum of cost. Check a good controls catalog before deciding to build a special control.


In some instances, however, no available commercially-made control will do the job, and something must be made to fit the special need. Even here, use of standard components will save a great deal of time and work, and will facilitate eventual repair and replacement.

Experience with a wide variety of special switching devices shows that most of them can be constructed from available standard components, without any very complex machine work, and that most of them can be made to work very well indeed. A little patience and ingenuity are a great help in designing such special switches; and a few minutes spent in lining up the components, after assembly, and before installation, will save many hours of "diddling" at a later date.

. . . Ives

1 When additional switching is needed with a potentiometer, beyond that obtainable with an available "attachable" switch, a switch-actuating cam can usually be mounted on the front shaft extension (which is commonly about 2" long), and this can be made to operate one or more Microswitches. Such a special switched control is shown in Fig. 1. Here, the Ohmite pot (type CU) with its attached switch (type CS-1) is mounted on a small bakelite sub-panel. The cam actuator, a gear with its teeth turned off, and an operating notch filed in, is then placed on the shaft. In front of this, and separated from the rear sub panel by brass spacers is a second sub-panel large enough to support a Microswitch with a roller actuator. Bearing for the outer end of the pot shaft, and ferrule for mounting the assembly on the main panel, is provided by a conventional panel bearing (Johnson 115-255).

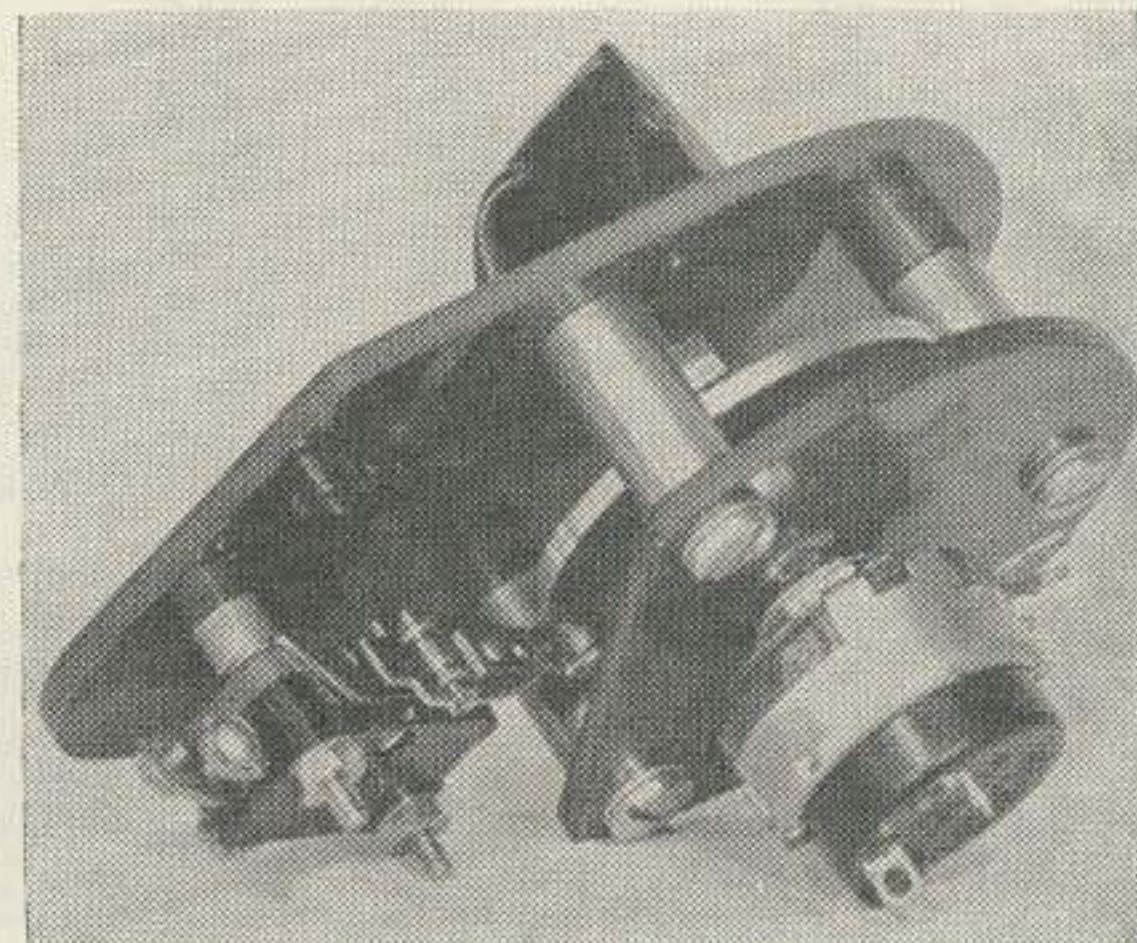

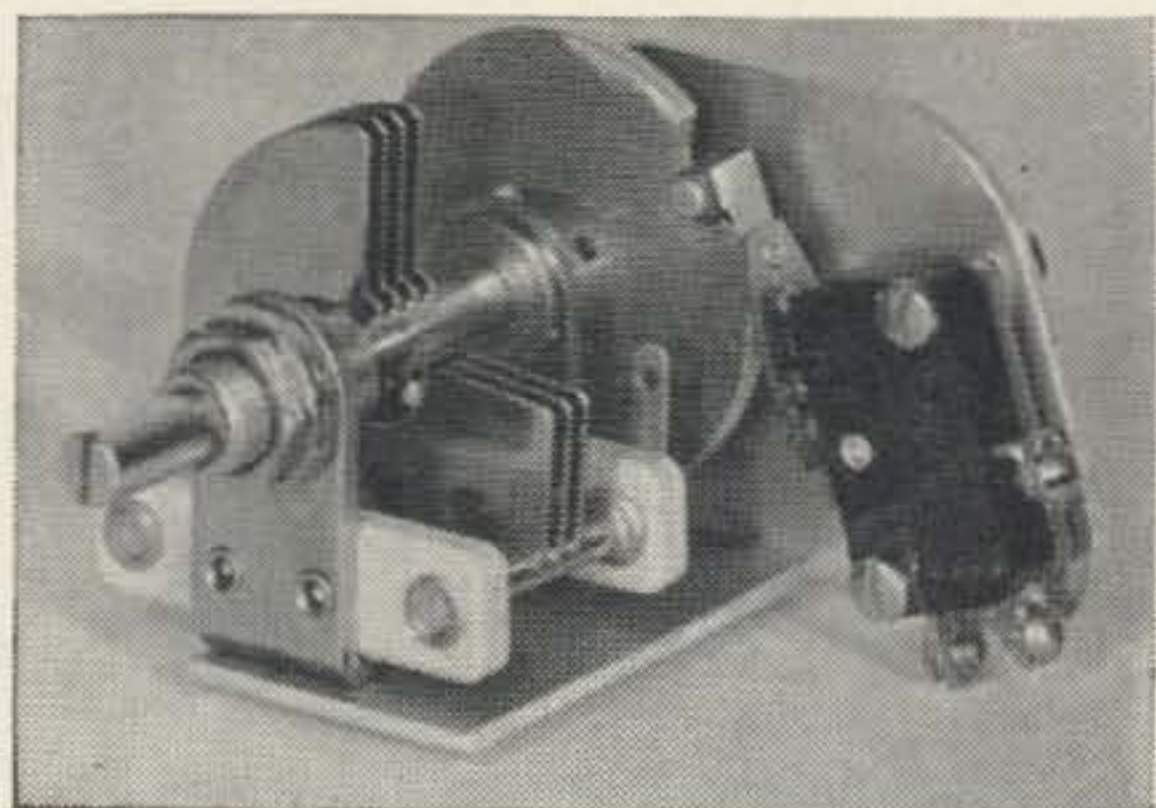


When a switch must be actuated by a capacitor shaft, the same technique can be used when the shaft length is adequate. In most instances, a capacitor with sufficient front shaft extension will not be available, and a capacitor with a rear shaft extension should be chosen. Actuating cam is attached to the rear shaft extension, and the microswitch is supported by a small aluminum or brass bracket as in Fig. 2.

2


3

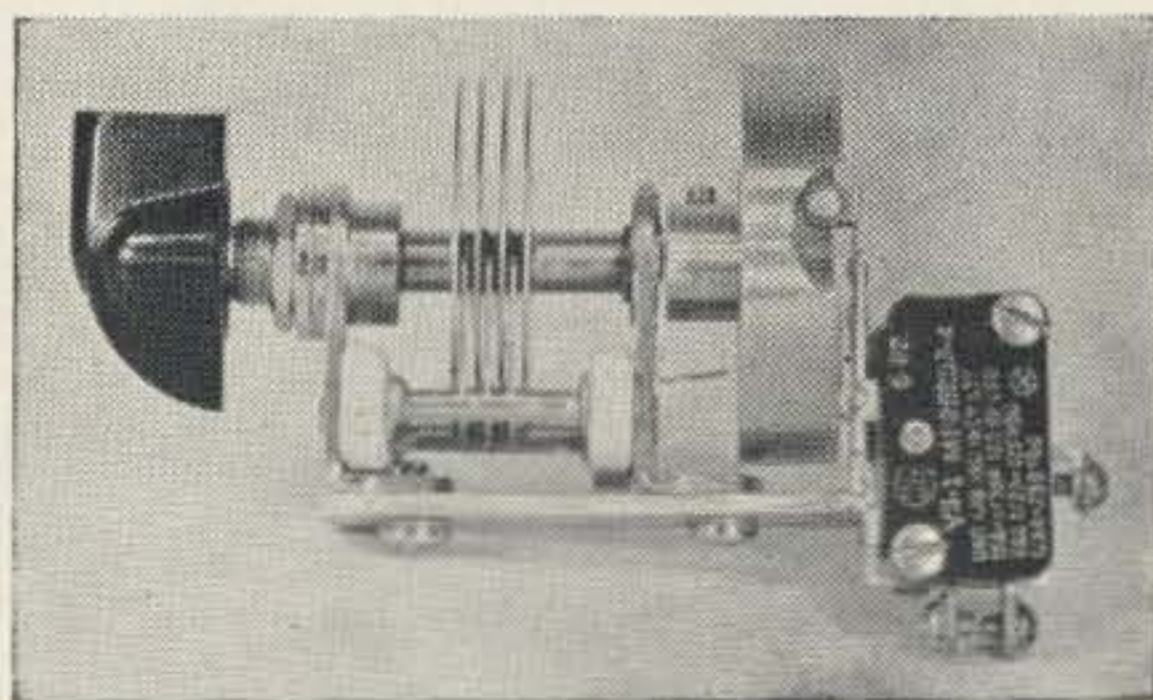Where side clearance is inadequate, the flat cam can be replaced by a cup cam (turned on a lathe), and the microswitch mounted in back of the capacitor, as in Fig. 3. As with the pot, more than one Microswitch can be operated by a single cam; and multiple cams can be used if necessary, although the capacitor bearings are not usually suited for large external mechanical loads.




With very small capacitors, such as the familiar APC types, neither front nor rear shaft is suitable for mounting a cam. With these, however, if the rotor is grounded (usual case), a stud can be soldered to the rear rotor plate, and this can actuate the extension wire of a type V-4 Microswitch, originally made for use in coin-operated equipment. Ordinary paper clips make good extension wires. An example of switch operation with an APC capacitor is shown in Fig. 4. Here, one switch turns on the BFO, which is tunable through 180 degrees of the capacitor shaft rotation. Further rotation of the shaft, beyond 180 degrees, actuates the second switch, which turns off the tunable BFO and turns on a crystal BFO. Returning the shaft to zero position (counterclockwise) turns everything off. Although the V-4 Microswitch, with its wire actuation, appears quite fragile, the illustrated assembly lasted for nine years of service with no maintenance whatsoever. It was taken out of service only because the related equipment became obsolete.

4

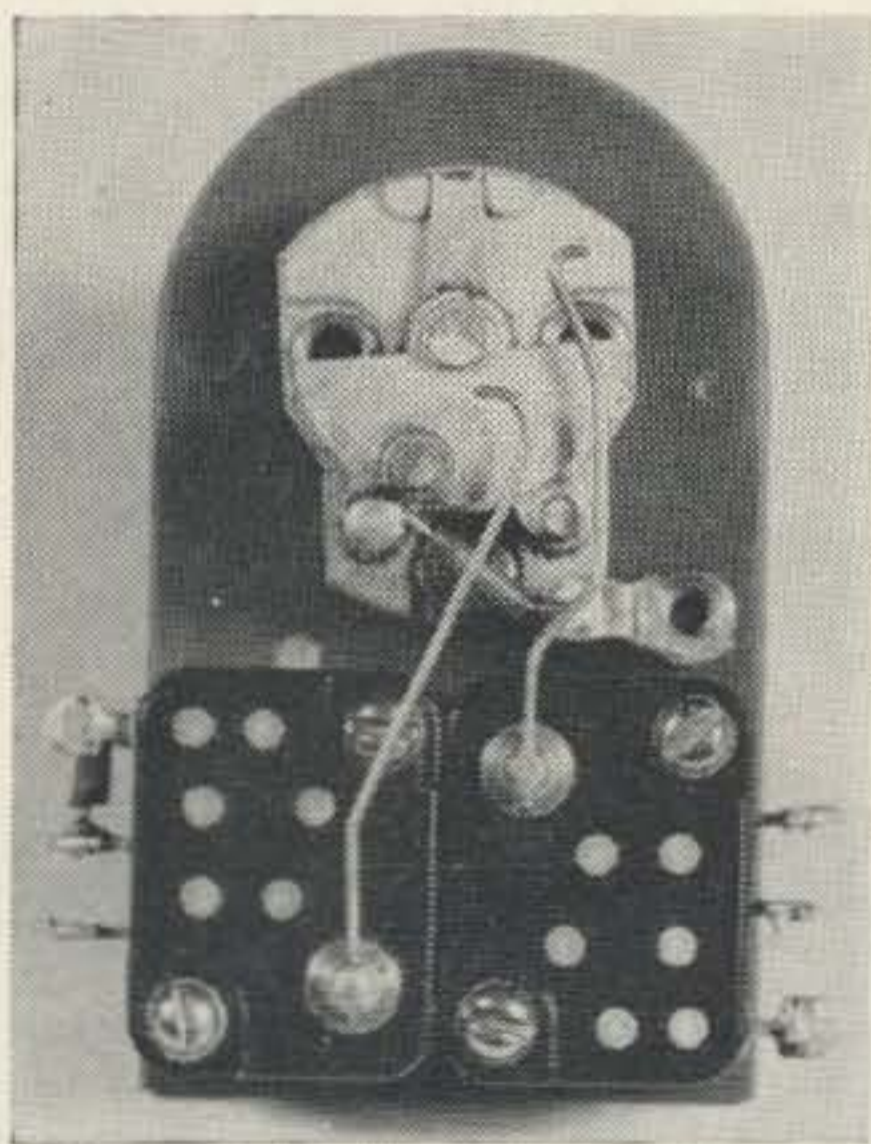

5

Another special switched control, this time using a dual concentric shaft, is shown in Fig. 5. This combination includes a switch, a capacitor, and a potentiometer. The switch is actuated by a stud on the rear rotor plate of the capacitor, and is controlled by the inner shaft (BFO tuning and off-on). The potentiometer is controlled by the outer (hollow) shaft (BFO injection). No special problems are encountered here, but care must be taken to align all the components exactly, so that the controls work smoothly, and have a correct "feel".

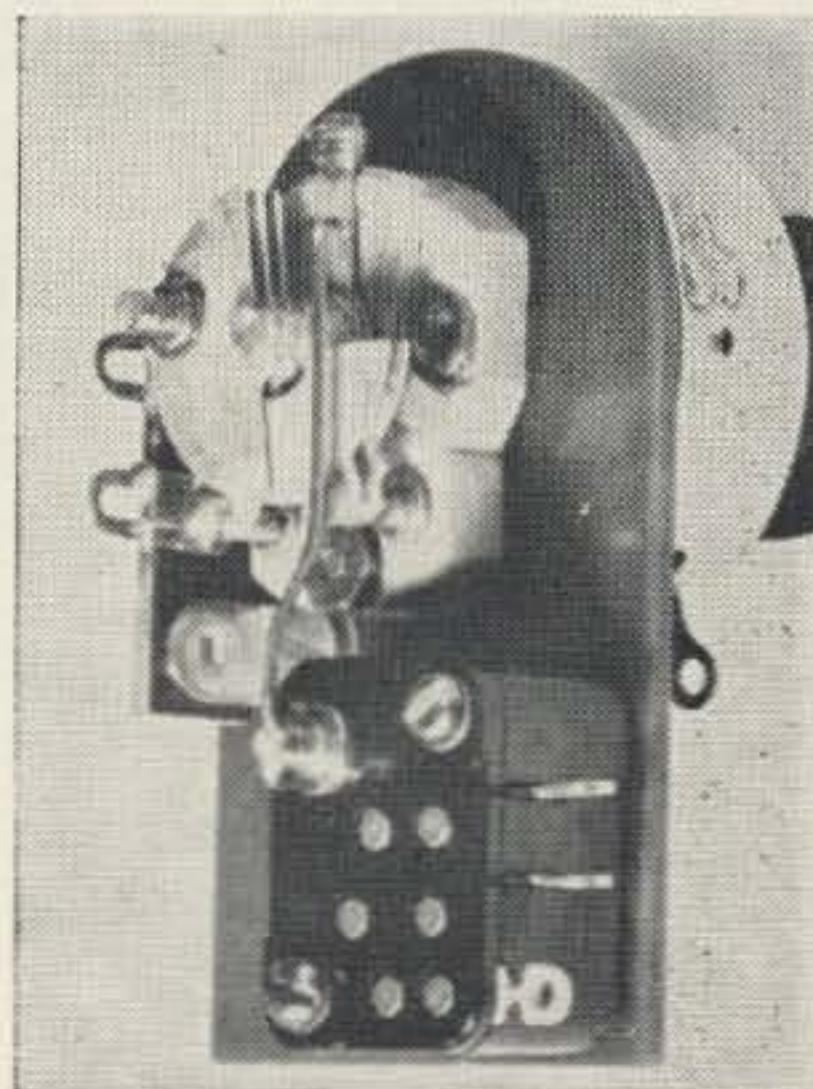



A CHU Time Receiver

Bob McGraw W2LYH
9 Peg's Lane
Riverhead, L. I., N. Y.

Radio station CHU, of the Dominion Observatory, Canada, broadcasts some very useful time signals on 3330, 7335, and 14670 kc. While anybody can use these signals for setting his watch, all of you hams who also have

amateur astronomy for a hobby can do more with them if you have a receiver like the one described here. The set is crystal-controlled, to receive CHU on 3330 and 7335 kc, which happen to be the best frequencies at this QTH.



Side view of the CHU Receiver.



FREE

send today for
your 508-page

ALLIED
1966 CATALOG



the catalog every ham uses biggest selection, biggest savings

It's your one dependable source for everything in station gear, for everything in electronics. You know, too, you can rely on our staff of over 100 licensed hams to give you the kind of ham-to-ham help you want—in *every* way. Get the 1966 Allied Catalog now—it's invaluable for your shack.



FREE send for it!

get every Ham buying
advantage—plus
top dollar for trade-ins



EASY TERMS, TOO
Use the Allied Credit Fund
Plan—over 24 months to pay.

ALLIED RADIO
serving the Amateur for 45 years


ALLIED RADIO, Dept. 14-H
100 N. Western Ave., Chicago, Ill. 60680

Send FREE 1966 Allied Catalog.


Name _____
PLEASE PRINT

Address _____


City _____ State _____ Zip _____

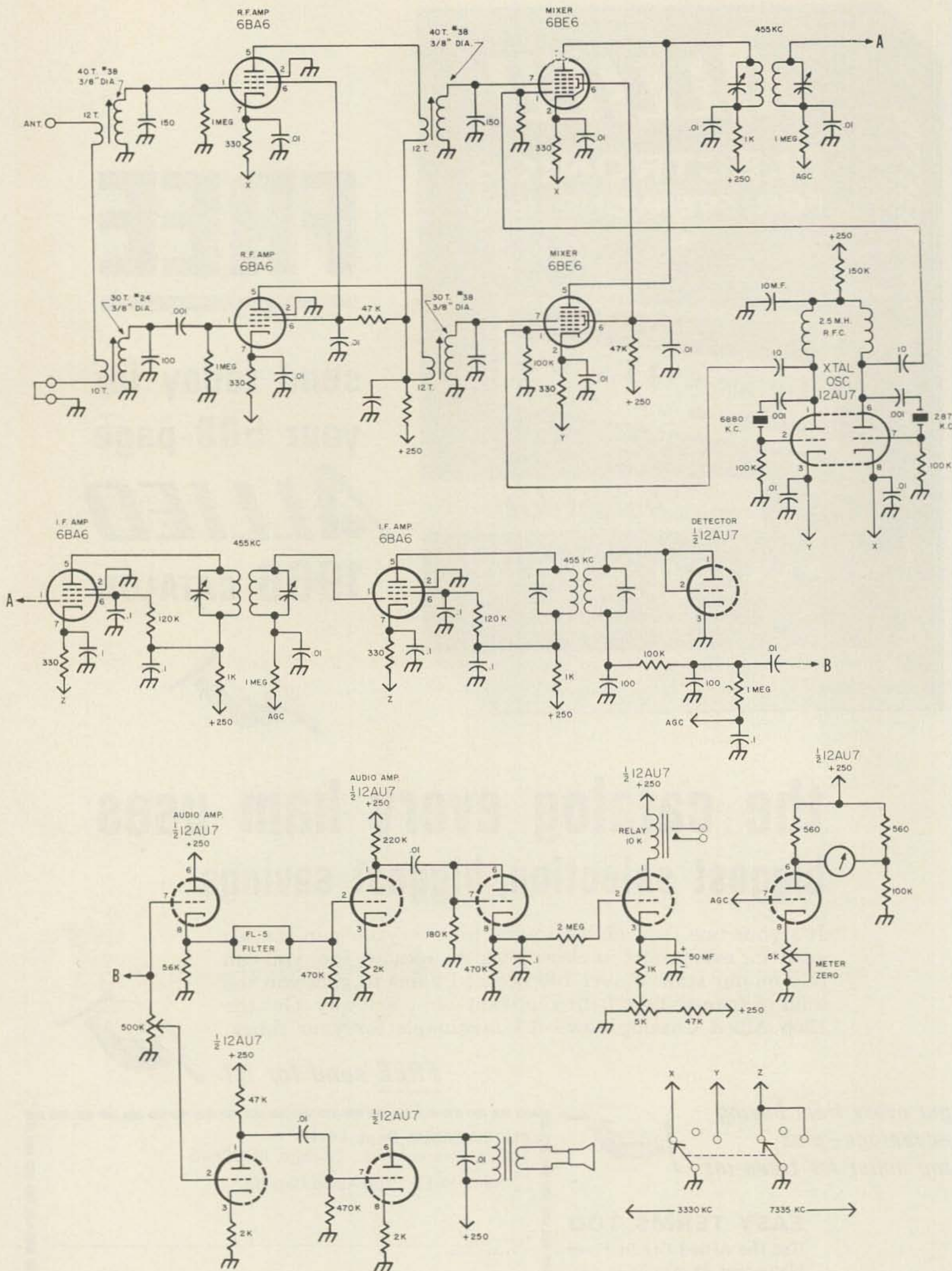

Schematic of CHU Receiver.

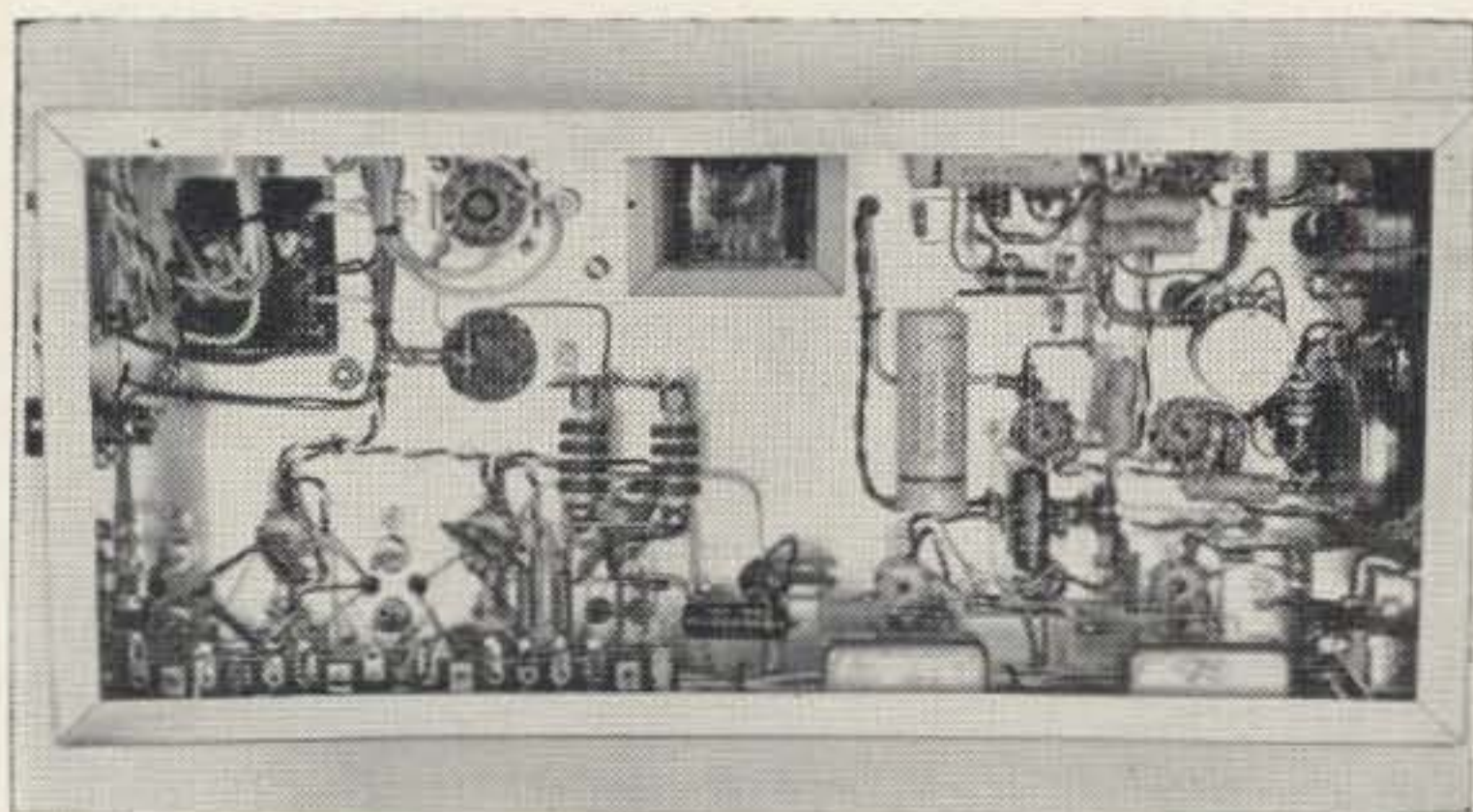

Bottom view.

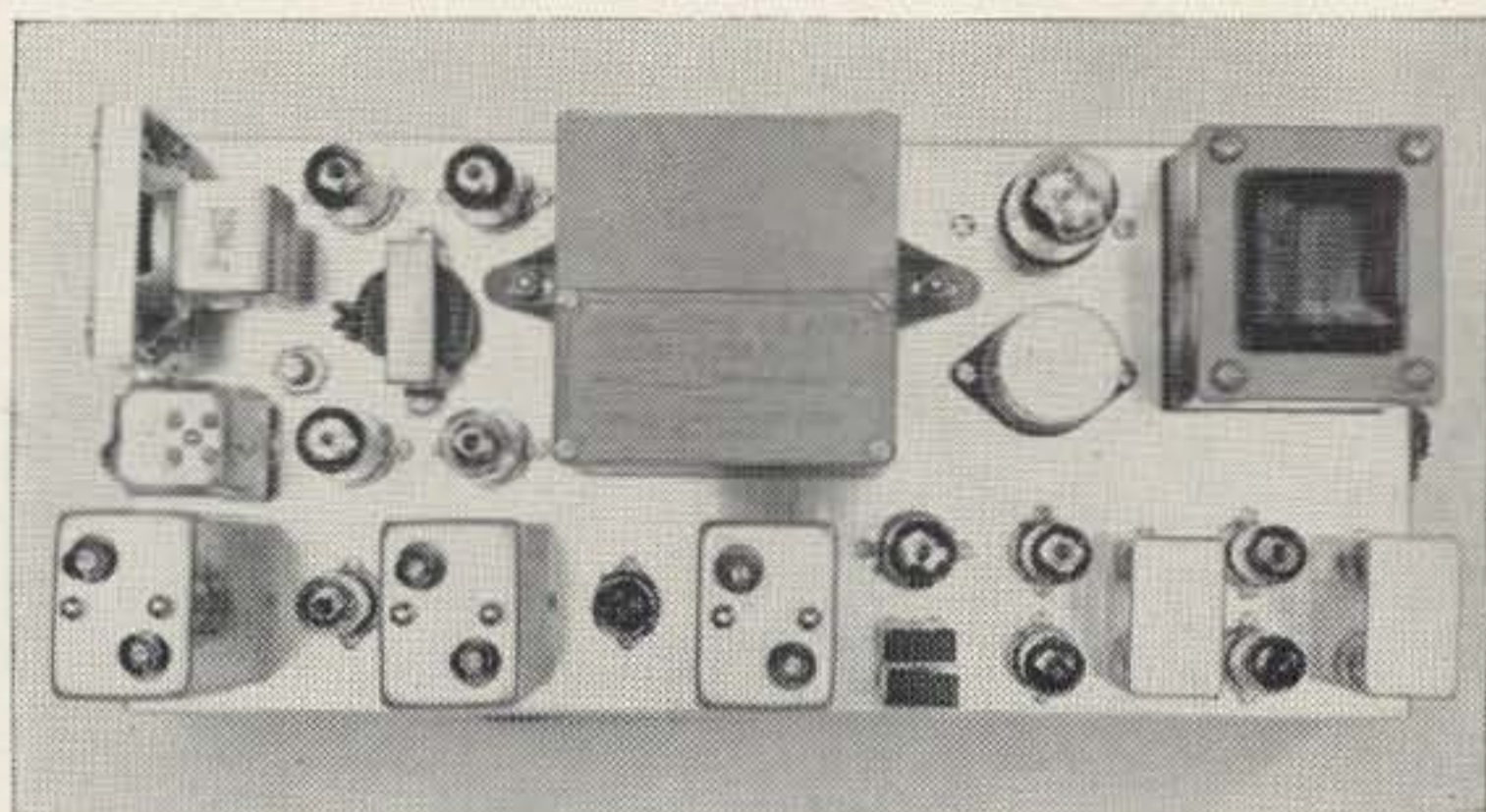

Top view.

The time signals operate a relay in the receiver, which keys one pen of a two-pen recorder. The other pen is keyed by the local clock, through a photo-cell system which looks at the pendulum. This allows precise measurement of the clock rate, and either pen can be switched to a remote location for recording transit sightings against either the clock or CHU.

A separate rf amplifier, mixer, and crystal oscillator is used for each of the two frequencies, as this is simpler than switching the rf circuits, and allows the use of a regular toggle switch in the cathodes for selecting either frequency. The mixers feed a two-stage 455 kc *if* amplifier. A diode detector furnishes *agc* voltage, which controls the gain of the rf and *if* stages. A two-stage audio amplifier drives the small built-in speaker. The time signals consist of voice announcements every minute, and 1000-cycle tone beeps at one second intervals. These tone signals are filtered through a FL-5 range filter, which does an excellent job, even though it is centered on 1020 cycles. The filter output is amplified, rectified, and the resulting dc voltage used to control the relay tube. A meter circuit is included to indicate relative signal strength, and for peaking the rf and *if* circuits.

I will be glad to answer any letters from anyone who desires further information on the receiver.

. . . W2LYH



ANTENNA GROUNDING SWITCH

Protective equipment for all receivers within 10-miles of stations equipped with SBE, SB2-LA one KW linears.

TELCO

SIX METER 2 KW PEP LINEAR



MODEL TLA-2050

- * Only 6 watts of drive required
- * Uses four 4X150's (1 KW on CW)
- * Built-in solid state power supply
- * Desk or rack mount
- * Covers 50-54 mc with no tuning

ONLY \$495.00

TELCO
575 Technology Square
Cambridge, Mass. 02139
Phone 617-491-4050

TELCO

Switching with Diodes

Many hams tend to think of the semiconductor diode only in terms of its use as a rectifier. This is understandable because the use of semiconductor diodes in much of the commercially manufactured ham gear is restricted to rectifying applications in power supplies, detector circuits, balanced modulators and clippers. In properly designed circuits, however, the diode may also function as a highly efficient and reliable non-rectifying switch. Diode switches may frequently be used to replace the conventional mechanical switch in ham communications equipment while offering a significant advantage in reduced size and cost and increased design flexibility and dependability. Before discussing practical switching circuits and associated design considerations, it might be helpful to briefly review the basic principles of solid state physics necessary for an understanding of the theory of semiconductor diode operation.

The basic materials currently being used in semiconductor manufacture are elements from Group IV on the chemical periodic chart, usually either silicon (Si) or germanium (Ge). The Group IV elements each have four bonding electrons (valence electrons) and in their pure, solid state are characterized by the formation of the tetrahedral crystal lattice. In the tetrahedral crystal lattice each atom is pictured as being at the center of a tetrahedron surrounded by four like atoms at the vertices of the tetrahedron. (See Fig. 1).

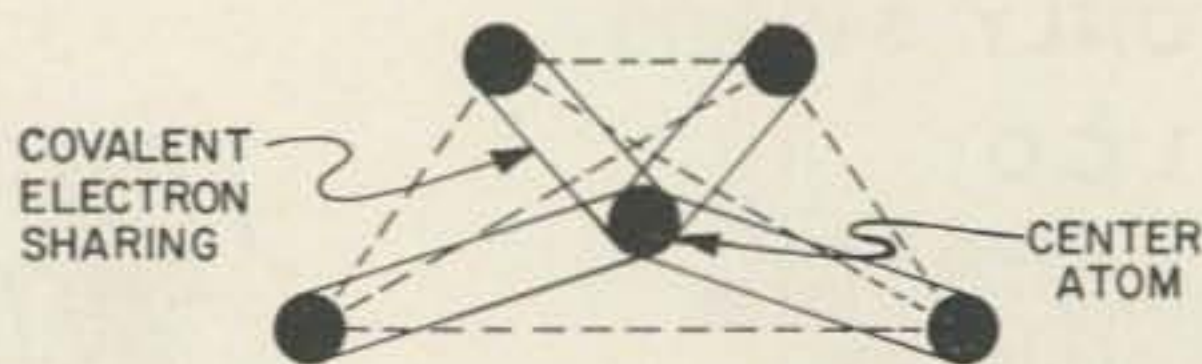


Fig. 1

Each atom in the lattice except those on the outside surfaces forms four covalent bonds by sharing one electron with each of the four adjacent atoms. This effectively results in giving each atom the highly stable octet arrangement of electrons in its outer shell. Thus all available electrons in the crystal lattice of the pure element are used in forming rigid covalent bonds and under normal conditions cannot be excited into the higher energy "conductive bands" for the conduction of electric currents. As a result, pure silicon and germanium are notably poor conductors.

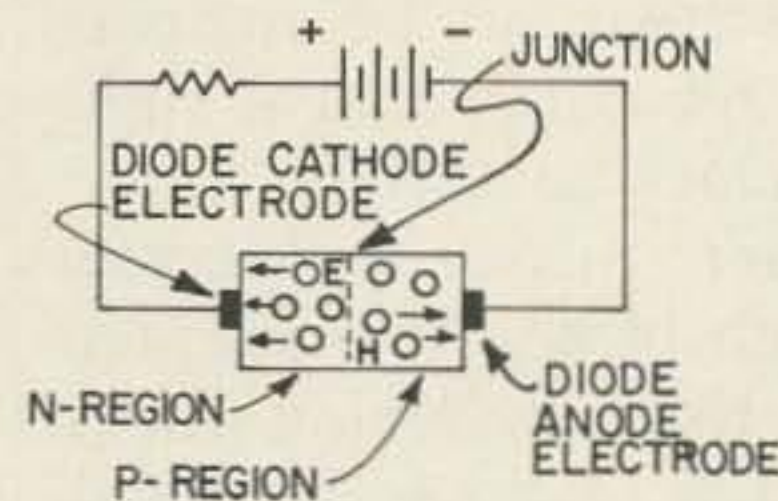


Fig. 2


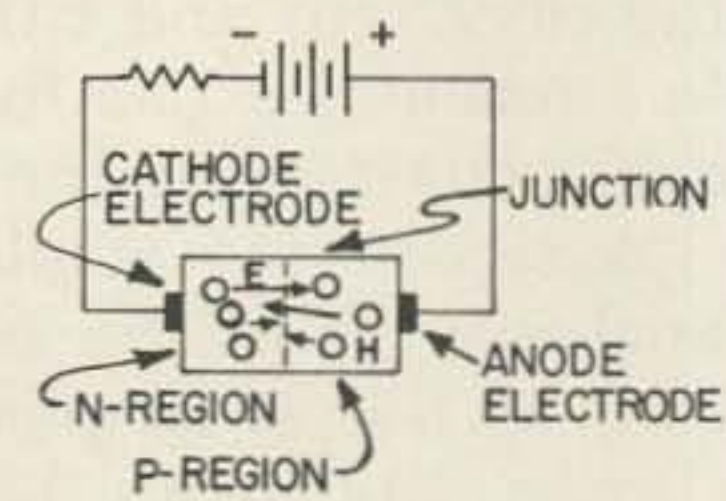


Fig. 3

The "trick" in the manufacture of semiconductors is to introduce either tri- or penta-valent "impurity atoms" into the silicon or germanium crystal lattice. In practice, certain chemical elements from Group III with only three bonding electrons or from Group V with five valence electrons are used as impurities. When a proper Group V impurity is placed into a tetrahedral silicon lattice, for instance, it is found that the impurity atom forms covalent bonds with its four adjacent atoms. However, the impurity atom has five valence electrons and only four of them are required for chemical bonding. As a result there is one electron which is "left over." Although the one unused electron for each Group V atom is electrostatically balanced out by the additional proton in the nucleus of the impurity atom, it can easily be excited into

From any angle...inside or out...

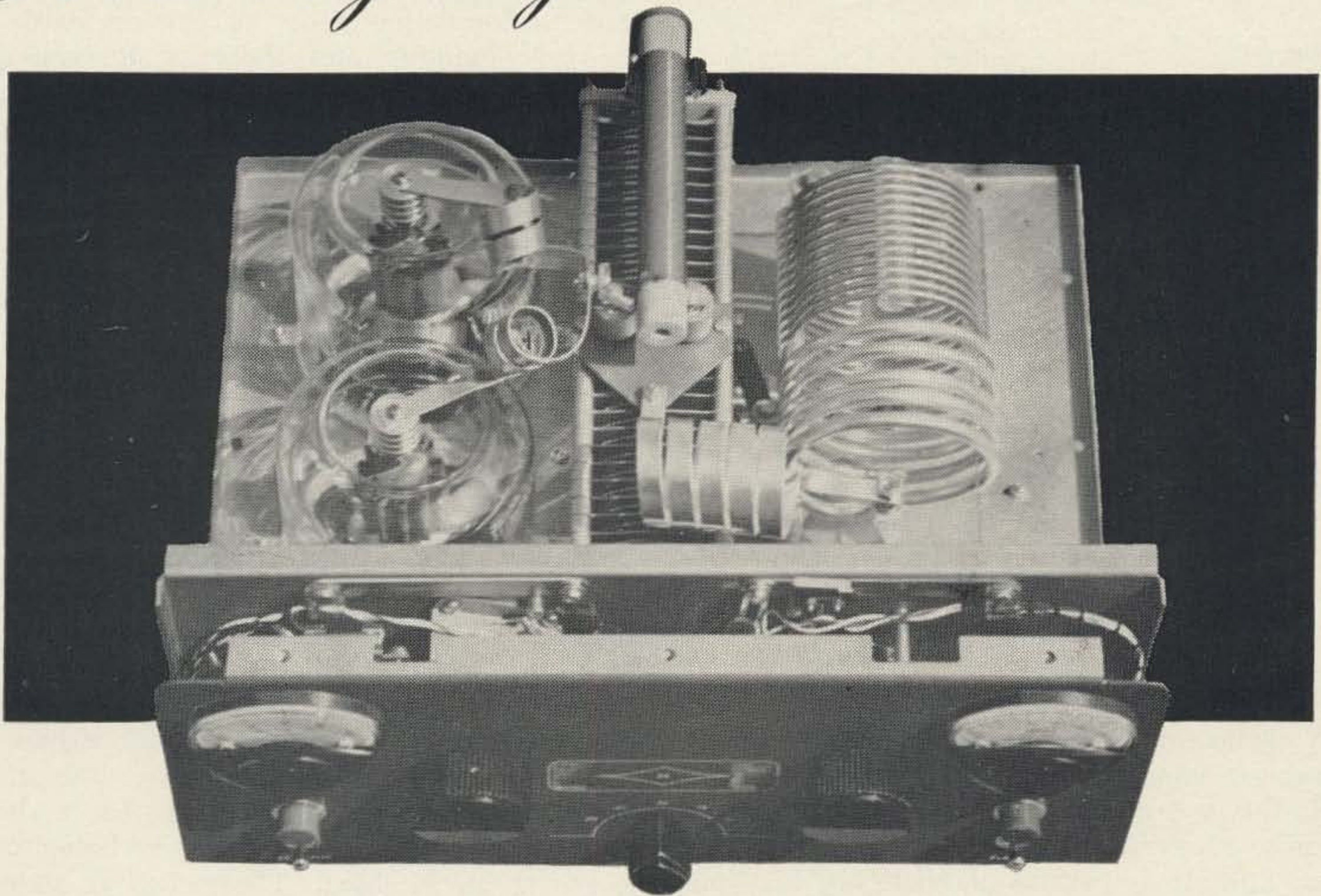

IT'S A CLASSIC!

With the **2-K LINEAR AMPLIFIER** beauty is obviously more than skin deep. The true functional beauty of the RF module is evident when removed from its cabinet. Designed to be the Rolls-Royce of linear amplifiers, the enthusiastic response to the 2-K proves again that the amateur wants the finest. And make no mistake, it is the finest. You cannot buy a better linear.

The 2-K is loaded with engineering plus values which guarantee the highest quality possible at any price.

- Pi-L output circuit
- Cathode-Pi input
- Double rugged band change switch
- Step-start relay system
- Ultra heavy duty power supply with resonant input filler choke and 5000 volt oil-filter condenser
- Two superbly linear 3-400 Z zero bias triodes
- High efficiency silver plated tank coil
- All aluminum cabinet

The 2-K is rugged, reliable and "rarin' to go." Ten years from now you'll be saying what we tell you today . . . "The 2-K is a Classic!"


The 2-K console or desk model \$675.00 RF unit only \$425.00

Henry Radio Stores

CALL DIRECT . . . USE AREA CODE
Butler 1, Missouri 816 679-3127
11240 W. Olympic, Los Angeles, Calif. 213 477-6701
931 N. Euclid, Anaheim, Calif. 714 772-9200
431 E. Green St., Pasadena, Calif. 213 684-0861
6116 N. 27th Ave., Phoenix, Ariz. 602 AM 4-3895

"Worlds Largest Distributors of Short Wave Receivers"

Fig. 4

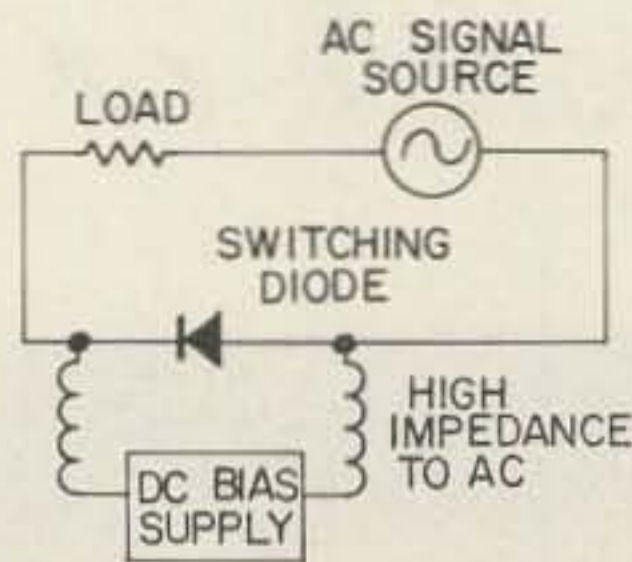

the "conductive bands" where it can migrate as an electric current when only a small voltage is applied across the semiconductor crystal. Group V impurities produce a region of "freeable" electrons which is commonly called an "N" region. On the other hand, Group III impurities in a tetrahedral lattice produce a region of "electron deficiency" known as a "P" region. It is possible for a P-region as well as an N-region to conduct electric current because both freeable electrons and electron deficiencies (called "holes") can migrate through a semiconductor crystal lattice if the proper impurity density has been established.

A semiconductor diode is manufactured by forming a junction between a piece of N-type and P-type semiconductor crystal material. Because diode switch circuits, as we will see later, operate by virtue of changing bias polarity and voltage across the switching diode, it might be helpful to quickly examine the electronic operation of reverse and forward biased diodes.

Fig. 2 shows a reversed biased diode. The "holes" in the P-region are attracted by electrostatic forces toward the negative terminal of the applied voltage, a direction away from the P-N junction. At the same time the "free electrons" in the N-region migrate away from junction towards the diode electrode which is connected to the positive battery terminal. Remembering that the basic units for voltage ("volts") are joules per elementary charge, it follows that as the reverse bias voltage is raised, the electrostatic forces acting on the carriers (ie. freeable electrons and holes) increase. Thus as the bias increases, the concentration of carriers further decreases in the

regions of the N and P crystals near the P-N junction. Under normal conditions current cannot flow through the reverse biased diode because a "depletion zone" of carriers exists at the P-N junction and there is no available mechanism for a transfer of charge. Under abnormal conditions (for most purposes), the reversed biased diode may be made to conduct by raising the bias voltage to the point where "break down" occurs in the crystal with chemical decomposition and the formation of movable ions.

In a forward biased diode, the situation is reversed. See Fig. 3. Due to the bias voltage polarity difference in the forward biased diode, the carriers migrate across the P-N junction instead of away from it. This permits current to flow through the diode.

So far, we have looked at forward and reverse biased diode circuits where the bias voltage or current has remained constant with time. In practical diode switching circuits where ac voltages and currents are being switched, however, the effective values of "bias" current and voltage vary with time. Fig. 4 shows a general diagram for a diode switch circuit where the diode is being used to switch an ac signal. The switching state of the diode depends upon both the value of its steady dc bias and the instantaneous values of ac current and voltage. If the value of dc bias is zero, we recognize the circuit to be identical to that of a half-wave rectifier. In this case, rectified ac in the form of pulsating dc appears across the load. We are interested, however, in switching the ac signal without clipping or rectifying it. With proper adjustment of the value of dc bias and polarity, it is possible to make the diode function as a switch without rectifying. The graphs in Fig. 5 show how this is accomplished. In graph A, the value of fixed dc bias is periodically exceeded by peaks in the waveform of the signal which is being switched. As a result clipping takes place whenever the instantaneous bias amplitude changes polarity. The ordinate axis,

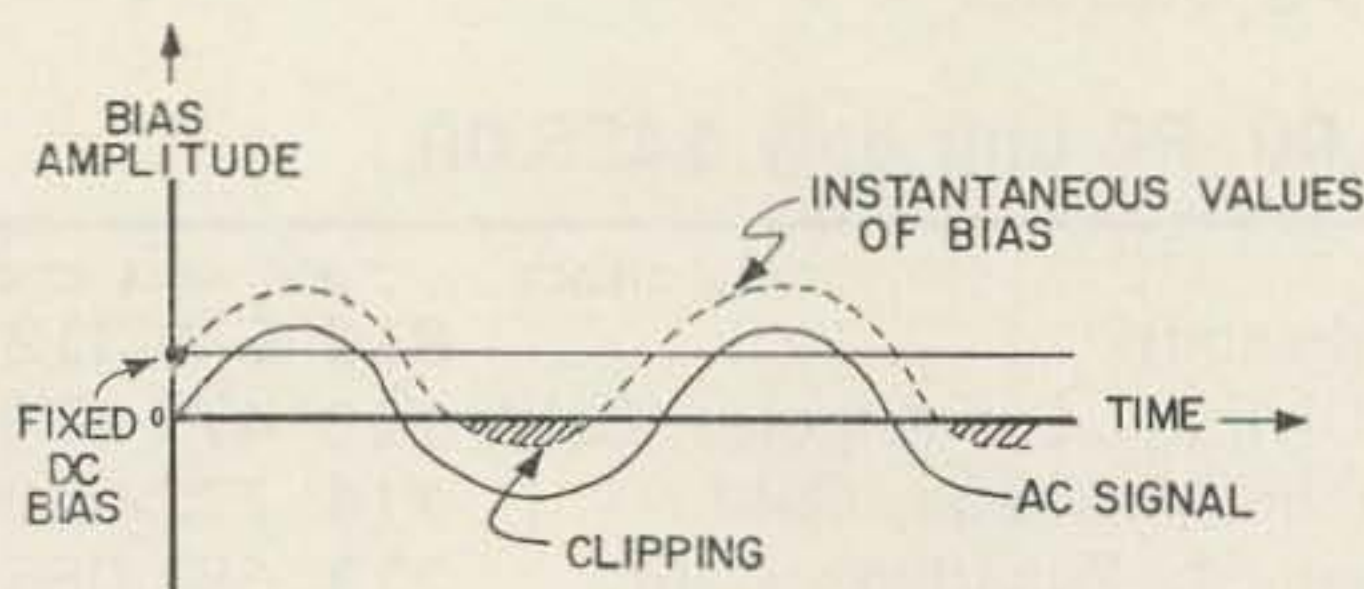


Fig. 5A

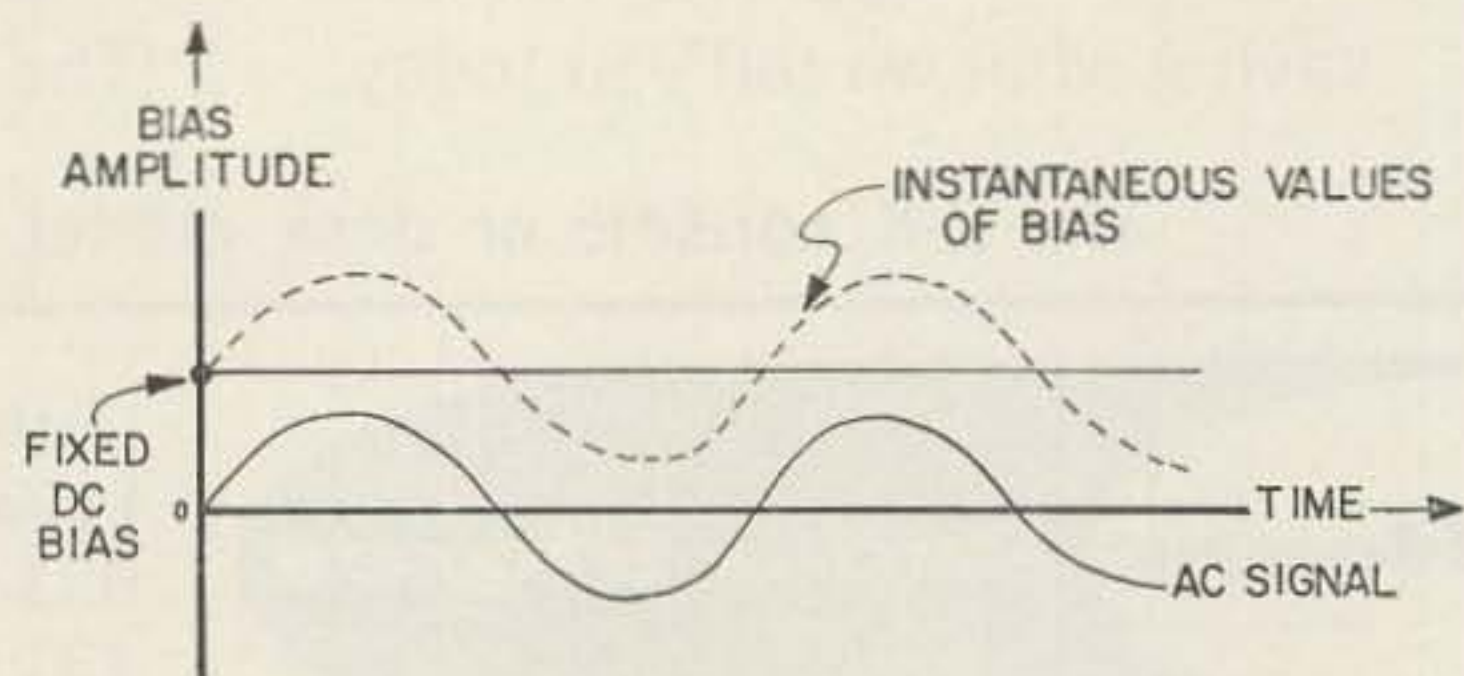


Fig. 5B


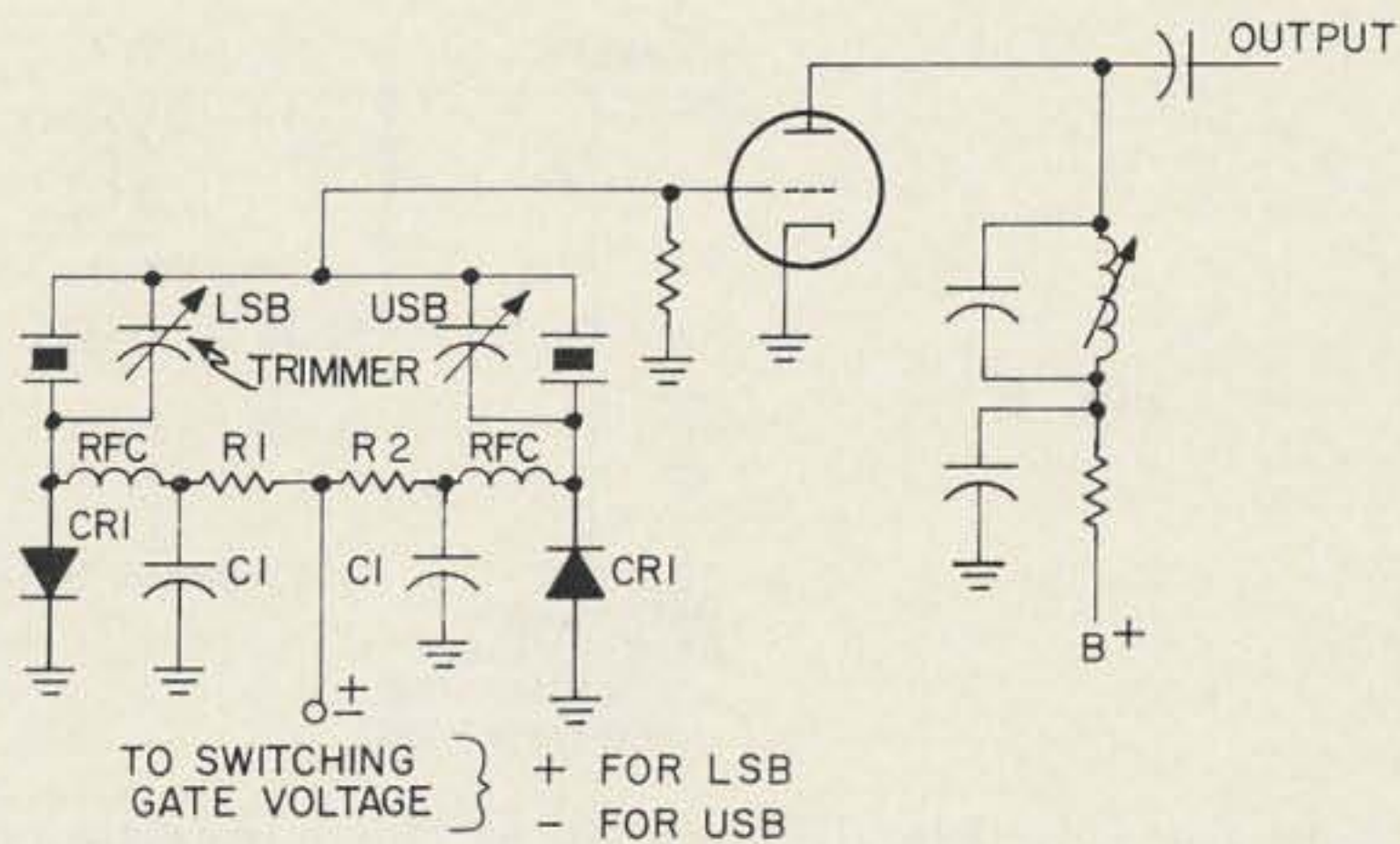


Fig. 6

“bias amplitude,” can represent “current” in the case of the conducting (“ON”) forward biased diode or “voltage” in the case of the non-conducting (“OFF”) reverse biased diode. In graph B the fixed dc bias exceeds the peak values of the ac signal and as a result, the bias polarity never changes. Thus when the diode switch is on, the ac signal is passed without being rectified; when the switch is off, no ac signal appears across the load.

By now the reader has hopefully studied Fig. 4 and Fig. 5 and understands the theory of how diodes can be used as non-rectifying switches for ac signals. Therefore we will now go on and look at several practical working circuits employing semiconductor diode switching elements. Fig. 6 shows a method of using a diode switch to switch crystals in a crystal oscillator. The basic oscillator circuit shown here is similar to one used as the carrier oscillator for LSB and USB with a popular commercial sideband crystal filter. However, by using diode switches instead of a mechanical switch to switch LSB and USB crystals, an advantage is gained because it is no longer necessary to locate the carrier oscillator circuitry physically close to a front panel LSB-USB switch so that the wire leads from the crystals to the switch can be kept short. Furthermore, an rf quality LSB-USB switch is no longer required since it is only necessary to switch the diodes’ bias voltage to select different crystals. Resistors R1 and R2 are selected to provide proper biasing for each diode. The rfc choke and by-pass capacitor (C1) are chosen to minimize rf voltages on the switching bias lead. Almost any diode with a high reverse-forward resistance ratio can be used for CR1. The positive and negative voltages needed for the diode switching gate lead can be selected with a single pole double throw switch from voltage dividers across the transmitter bias supply and across the transmitter B+.

Fig. 7 shows a method of using a diode

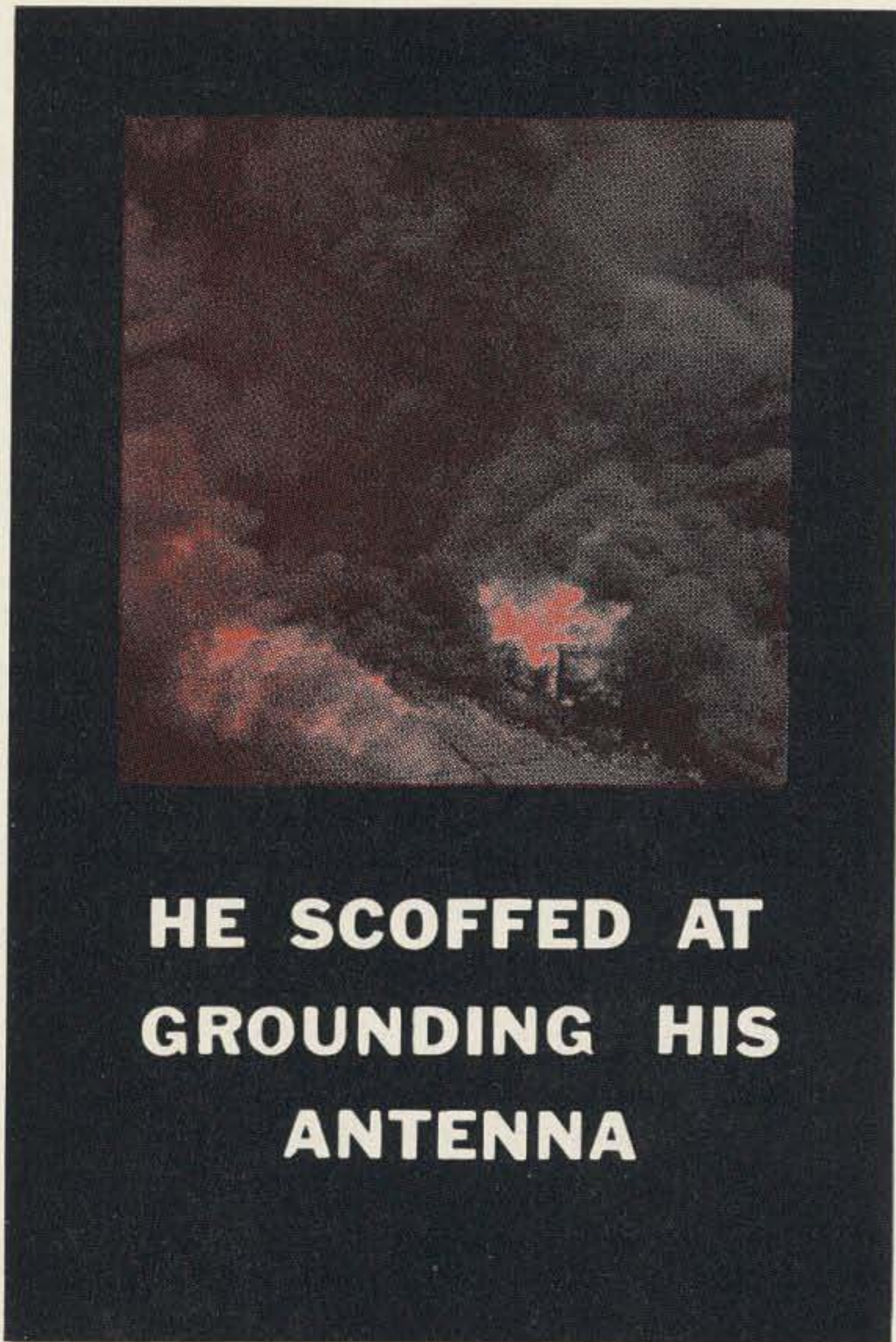

HE SCOFFED AT GROUNDING HIS ANTENNA

FREE ALL NEW

1966 HAM/CB CATALOG

SEE WRL'S EX-
CLUSIVE HAM/CB
GEAR!

TUBES, PARTS
ETC., AT LOW-
LOW PRICES.

SELECTED GOOD
BUYS ON RADIOS,
RECORDERS, ETC.

SPECIAL PUR-
CHASES FOR
ELECTRONIC
BUILDERS

MOST COMPLETE
AMATEUR EQUIP-
MENT LISTINGS
EVER COMPILED

BUY ANYTHING
ON OUR EASY-
PURCHASE CRED-
IT PLAN

GET
YOURS
TODAY

WORLD RADIO LABORATORIES

3415 WEST BROADWAY, COUNCIL BLUFFS, IOWA 51504

Rush me your Free 1966 Catalog

Name _____

Address _____

City _____

State _____

Zip _____

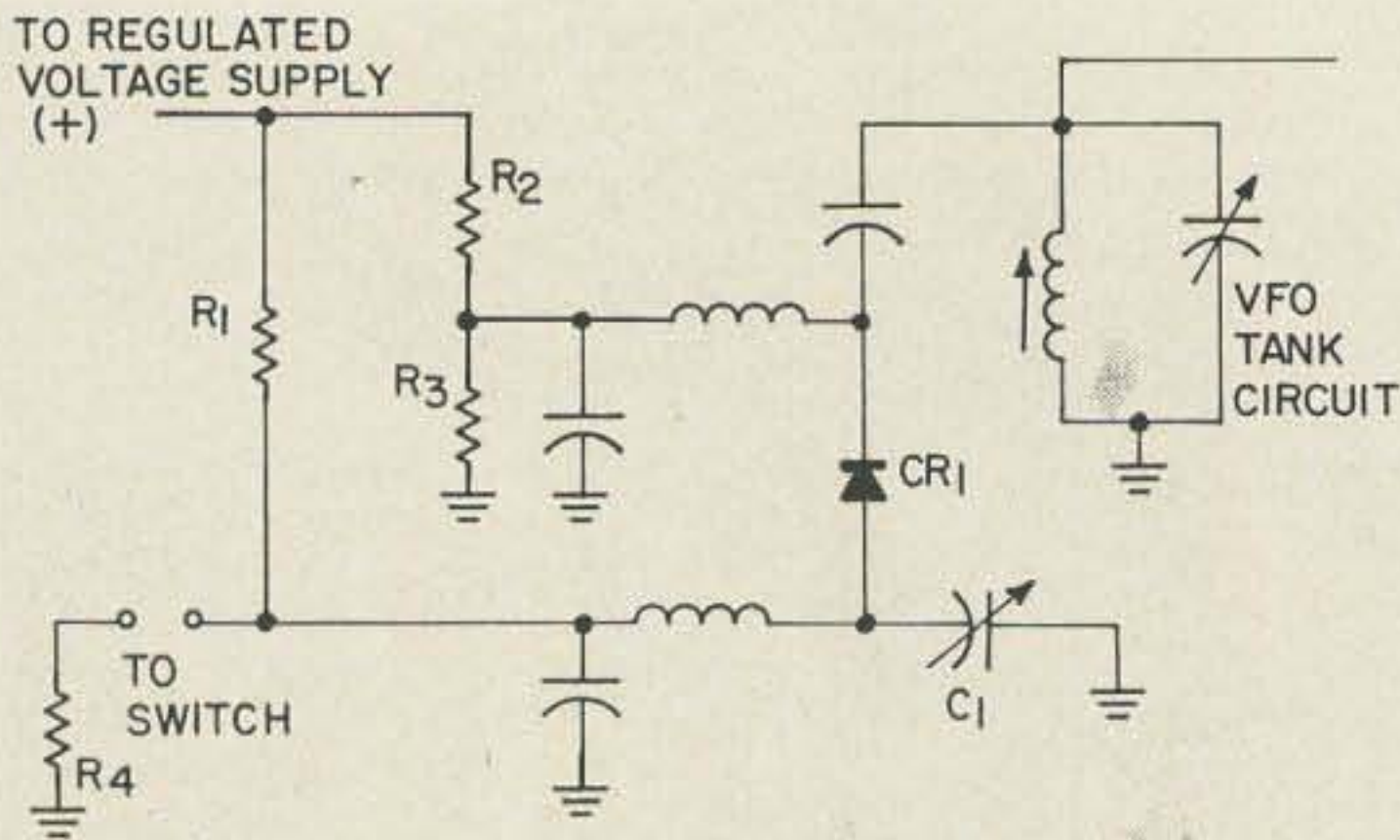


Fig. 7

switch to switch a capacitor across a vfo tank circuit to produce a frequency shift. Circuits similar to this one can be used to advantage for LSB-USB vfo dial correction in SSB transmitters or for FSKing for synchronous detection or RTTY. A regulated bias voltage which can easily be obtained with a zener regulator should be used in this instance because all diodes show a change in capacitance as their reverse bias changes. The values of R1, R2, R3, and R4 should be chosen for proper diode biasing and bias polarity reversal. It might be helpful to note that the biasing arrangement used here is identical to placing the switching diode across a Wheatstone Bridge composed of R1-R4. Capacitor C1 can be used to control the amount of frequency shift. Again, almost any good quality junk box diode may be used for CR1.

Fig. 8 is the diagram of a method for using diode switches to switch a transformer primary between two inputs. This circuit may readily be used for switching low level audio stages, for switching a receiver between various antennas or VHF converters, or for switching an *if* stage or a crystal filter. If transformer T1 happens to be a tuned transformer, it is recommended that trimmer capacitors be placed across both CR1 and CR2 to compen-

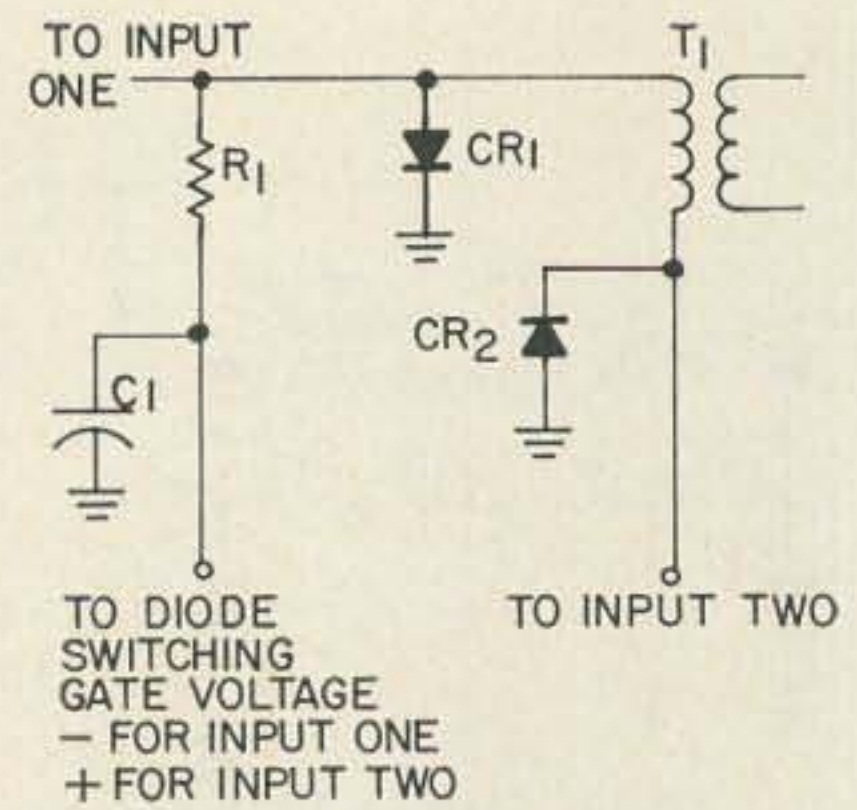



Fig. 8

sate for possible differences in the capacitance of each diode. If audio is being switched, R1 and C1 should be chosen to provide adequate decoupling without loading down "input #1" more than necessary. For rf or *if* stages, an rfc can be used in place of R1.

Diode switching circuits are truly "cheap and easy." In practice it is possible to use just about any diode which is in reasonably good condition. This includes everything between crystal-set detectors and high power silicon rectifiers. The only requirement on the switching diode is that it be capable of conducting "forward" currents of two or three times the signal current and capable of withstanding an inverse voltage of two or three times the signal voltage. Other than this, the main thing to remember is that the diode bias resistors should be adjusted so that the bias current through the "ON" diode is not exceeded by the signal current and that the bias voltage across the "OFF" diode is not exceeded by the signal voltage. Switching gate lead filtering is not at all critical and bias supply regulation must be used only in special instances. Diode switches are readily adaptable to hundreds of different circuits in ham equipment. Next time you need something to switch low level ac, why not use one?

. . . K1SDX

PARAMETRIC AMPLIFIERS

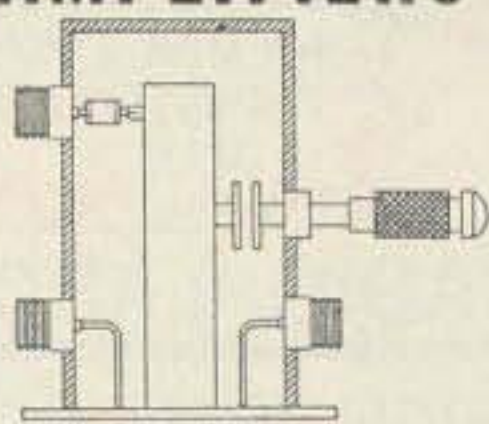

Jim Fisk WA6BS0

COPYRIGHT 1961 BY 73 INC., PETERBOROUGH, N.H. \$2

A New Book Published by 73

This book, the first on parametric amplifiers for the ham, is written for the average amateur and explains in simple language how they work, how to build your own for the various UHF bands, and how to tune them up. Parametrics have helped UHF move into the space age, but don't forget that the first working parametric amplifier was built by W1FZJ and worked on six meters.

Order this book direct, \$2.00 postpaid, or from your local parts distributor.

73 Magazine

Peterborough, N. H.

THINK SMALL...



PERFORM BIG



GO GONSET Sidewinder 2 Mtr.

Here's coverage of the entire 2 meter band in four, one megacycle segments, operation on SSB, AM, or CW, and all packaged in a sharp little chassis only 9" wide, 5" high and 7 $\frac{3}{16}$ " deep.

The Gonset Sidewinder 2 meter transceiver is so compact that it's ideal for mobile as well as fixed station application. Separate 117 VAC and 12 V DC solid state power supplies snap on to the rear of chassis, or may be remotely positioned to simplify installation.

And look at some of the features Gonset builds in to provide top performance: complete push-to-talk operation, full 20 watts P.E.P. input, crystal lattice filtering, vernier tuning, transistors at primary stages, stabilized VFO and high-sensitivity reception.

SPECIFICATIONS*

Frequency Range	143.975 to 148.025 MC
Modes of Operation	AM, SSB, CW
Carrier Suppression	50 db
Sensitivity	0.5 μ v for 10 db $\frac{S+N}{N}$
Selectivity	3.1 KC crystal bandpass filter
Output impedance	50 ohms
Audio Output	2.5 watts into 3.2 ohms
Antenna Input Impedance	50 ohms unbalanced

NEW* - from GONSET

- Two new power amplifiers—model 903A for 2-meter, model 913A for 6-meter
- The GSB-201 Linear Amplifier—provides 2000 watts PEP(SSB) for 10 to 80 meter operation
- Gonset Sidewinder 6-meter SSB-AM-CW Transceiver with all the features of the 2-meter.

* Complete descriptions and specifications on all Gonset equipment is yours for the asking. Write to Dept. 73-7.

© 1965 GONSET, INC.



GONSET, INC.

A Subsidiary of *QST* Ling Altec, Inc.

1515 South Manchester Avenue, Anaheim, California

**AMATEUR TELEVISION is the EXCITING NEW FRONTIER
GO ON THE AIR NOW WITH A VANGUARD TV CAMERA**



\$149.95

Model 400 for TV channels 2-6 (closed circuit) } Only \$149.95
Model 440 for ATV 436-450 mcs. } less vidicon
and lens.

25 mm. F1.9 normal angle lens in focusing "C" mount \$18.95

Other lens available from \$15 to \$250 for our fantastic F1.4 ZOOM lens.

Complete description in our catalog for 10c.

Vidicon tubes:	7038	7735A
Grade A	\$85.00	\$100.00
Grade B+	\$75.00	\$ 90.00
Grade B	\$60.00	\$ 75.00

Grade C Our choice of any type 1" vidicon, new or used—guaranteed to give satisfactory service for amateur use. \$35.00

The VANGUARD Models 400 and 440 are factory assembled with the same precision as our industrial cameras now in continuous duty throughout the U.S. Complete with self-contained synchronizing generators, 4 mc. video amplifiers, power supply, tripod base plate and low power TV transmitter which can easily be increased with simple linear amplifiers. Illumination can be as low as 1 foot-candle when using our vidicon and lens. Picture sharpness is guaranteed to be equal to the best capabilities of any standard 525 line TV receiver. Modular construction and printed circuits permit quick replacement and servicing of major circuits. Weighs 11 lbs.—measures approx. 8" x 6" x 6".

Crystal controlled horizontal scan available on either model for only \$20.00 more. Add the suffix X to model number.

Building your own TV camera? Our complete line of tested circuit modules and deflection yokes will save you much time and money. Fully described in our catalog for 10c coin or stamps.



\$11.95 up

**VANGUARD
TRANSISTORIZED CONVERTERS**

New series 300 with 3 VHF-UHF transistors, crystal-controlled oscillator, tuned R.F. stage and low noise mixer. One microvolt sensitivity. More than 30 high quality parts carefully assembled and tested. Measure only 3" x 2½" x 2". Operate at 12 volts DC 4-5 ma.

Nuvistor converters available from \$10. Circuit modules and government surplus equipment also available. Send 10c coin or stamps for complete catalog. For prompt shipment please include postal money order

Available in the following models:

	Model	Input mc.	Output mc.	Price
2M	{ 300-D	144-148	50-54	\$12.95 ppd.
	{ 300-E	144-145	.6-1.6	\$12.95 ppd.
	{ 300-F	144-146	28-30	\$12.95 ppd.
	{ 300-Q	144-148	14-18	\$12.95 ppd.
6M	{ 300-B	50-51	.6-1.6	\$12.95 ppd.
	{ 300-C	50-54	14-18	\$12.95 ppd.
	{ 300-J	50-52	28-30	\$12.95 ppd.
20M	300-G	14.0-14.35	1.0-1.35	\$11.95 ppd.
CB	300-A	26.965-27.255	1.0-1.29	\$11.95 ppd.
WWV	300-H	5.0	1.0	\$11.95 ppd.
Int'l.	300-I	9.0-10.0	.6-1.6	\$11.95 ppd.
CHU	300-K	7.3	1.0	\$11.95 ppd.
CHU	300-L	3.35	1.0	\$11.95 ppd.
Marine	300-M	2-3	.6-1.6	\$11.95 ppd.
Aircraft	{ 300-N4	121-122	.6-1.6	\$13.95 ppd.
	{ 300-N5	122-123	.6-1.6	\$13.95 ppd.
Fire, Police etc.	300-P	155-156	.6-1.6	\$13.95 ppd.

All above converters are supplied with Motorola type connectors. For two SO-239 connectors instead, add 75c. N.Y.C. residents add 4% sales tax.

or cashier's check. COD's must include 20% deposit. N.Y.C. residents add 4% sales tax. Include sufficient postage for all items except converters and circuit modules which are postpaid.

VANGUARD LABS

Dept. H-8
190-48 99th Avenue
Hollis, N. Y. 11423

Improving the Paco GDO

I purchased the Paco G-14 grid dip meter in kit form about four months ago. I assembled it and found that it worked quite well on all but the highest frequency range (110-250 mc). There was very little indication of grid current over much of the tuning range. This was traced to a defective sensitivity control which left a small bias on the meter. When I shorted out the control I was able to get a usable reading, but now, I found so many spurious responses that the instrument was still of little use over this frequency range.

At this point it was back to the drawing board for a long look at the circuit diagram where a new problem became apparent. Even with the sensitivity control working properly the meter would be shunted with the 270 ohm resistor, R4, which would lower its sensitivity anyway. The problem was a twofold one. I had to kill the residual bias from the sensitivity control and also block the shunting action of the resistor, R4. I decided to insert a small silicon diode between the sensitivity control and R4 with its cathode towards R4. In this application I hoped to use the forward voltage drop of the diode to solve both my problems. The result far exceeded my hopes. I now obtained grid current indication varying from a low of 70 μA . to a high of 250 μA . and the sensitivity control functioned nicely. To make sure that the diode wouldn't misbehave I bypassed both sides of it to ground with .02 ceramic discs (probably unnecessary) and established a di-

rect ground to the cover of the sensitivity control.


Now there were excellent meter readings but the many spurious dips throughout the tuning range left much to be desired. I examined the meter for possible clues. The most promising lay in the fact that the front end of the tuning capacitor rotor was grounded only by the ball bearings. The shaft extended through the chassis and connected to the large aluminum tuning dial. The top edge of the dial in turn was exposed to the plug in coil. I made a small wiping contact from spring brass and fastened one end under one of the condenser mounting screws. The other end was arranged to rub against the back side of the tuning dial. This proved to be the answer. There remained only a small dip at 190 mc and another small one at 250 mc. Both dips are smooth and so slight that they don't interfere with operation. Although one spring worked nicely, I placed two springs against the back of the dial and one against the capacitor shaft where it extends through the chassis.

With the electrical details corrected, I found that there remained a mechanical one. The plastic hairline indicator was threatening to wear away the graduations printed on the tuning dial. I solved this by cutting out a circular piece of thin, transparent plastic slightly smaller in diameter than the tuning dial. I clamped it between the hub and the tuning dial so that it rotates with the dial and takes the wear from the indicator.

I would also like to offer a suggestion to the manufacturer. The various coils supplied with the G-15 are very nicely color coded so that it would be much more logical and convenient to designate the corresponding bands numerically rather than alphabetically.

After making the changes outlined here, I have been very pleased with the performance of my G-15 and I hope others may do likewise.

. . . K1AMN

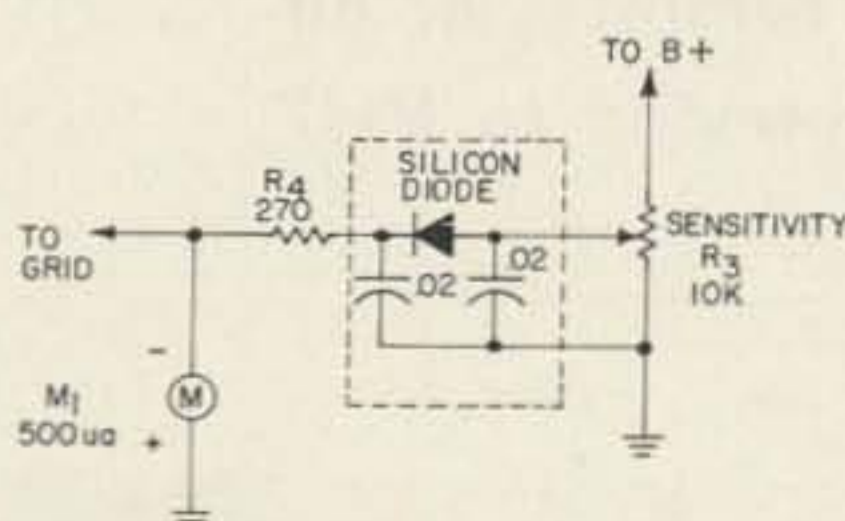


Partial Schematic of Paco G-15 grid dip meter. Added parts are enclosed by dotted line.

It's Here!

Topics Covered

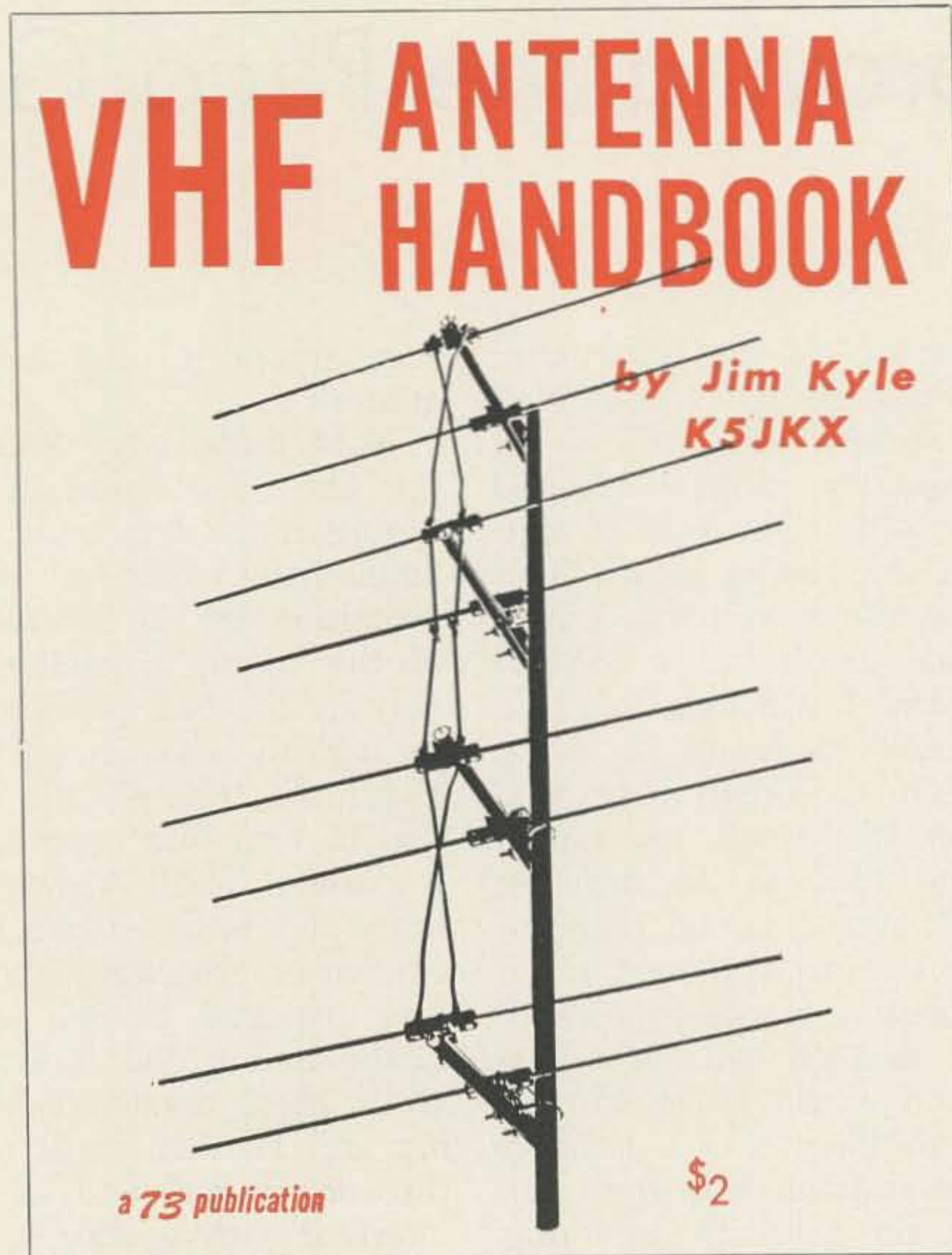Basic Concepts:
Dipoles:
Folded Dipole
Slot
Conical
Coaxial
Halo
Abe Lincoln
Turnstile
Ground Plane
Phased Arrays:
Broadside
Endfire
Mattress
Sterba Curtain
ZL Special
Parasitic Arrays:
Long and Short Yagis
Weeping Willow
Quads
2 Band Quad
Circularly Polarized
Antennas:
Helix
Cross Beam
Circular Quad
Non-Resonant
Antennas:



Topics Covered

Transmission-line
Antennas
Long Wires
V Antennas
Rhombic
Log Periodic
Log Periodic for
6 through 70 cm
Horn
Discone
Reflective Antennas:
Corner Reflector
Trough
Paraboloid
Plane Reflector
Backfire
Cylindrical Parabola
Practical Antenna
Techniques:
Construction
Mounts
Phasing Lines
Q-Sections
Baluns
Commercial
Equipment
Amateur and
Commercial Photos

The VHF Antenna Handbook

The VHF Antenna Handbook is your complete guide to VHF and UHF antennas. This outstanding book is by Jim Kyle K5JKX, one of the outstanding technical authors in the electronics field. The VHF Antenna Handbook covers complete theory and all practical details for every type of VHF and UHF antennas. A special feature is the commercial antenna catalog section. If you're interested in VHF, you should have this book.

Price is \$2 from

73 Magazine
Peterborough, N. H.

Curing Distorted RTTY Patterns

The simplest means of tuning in a RTTY signal is with a scope. Most homebuilt converters obtain the mark and space signals directly from the toroid filters feeding the discriminator, similar to the circuit of Fig. 1. However, the main drawback in using this method is that the scope pattern is sometimes distorted as in Fig. 2-A and tuning is difficult.


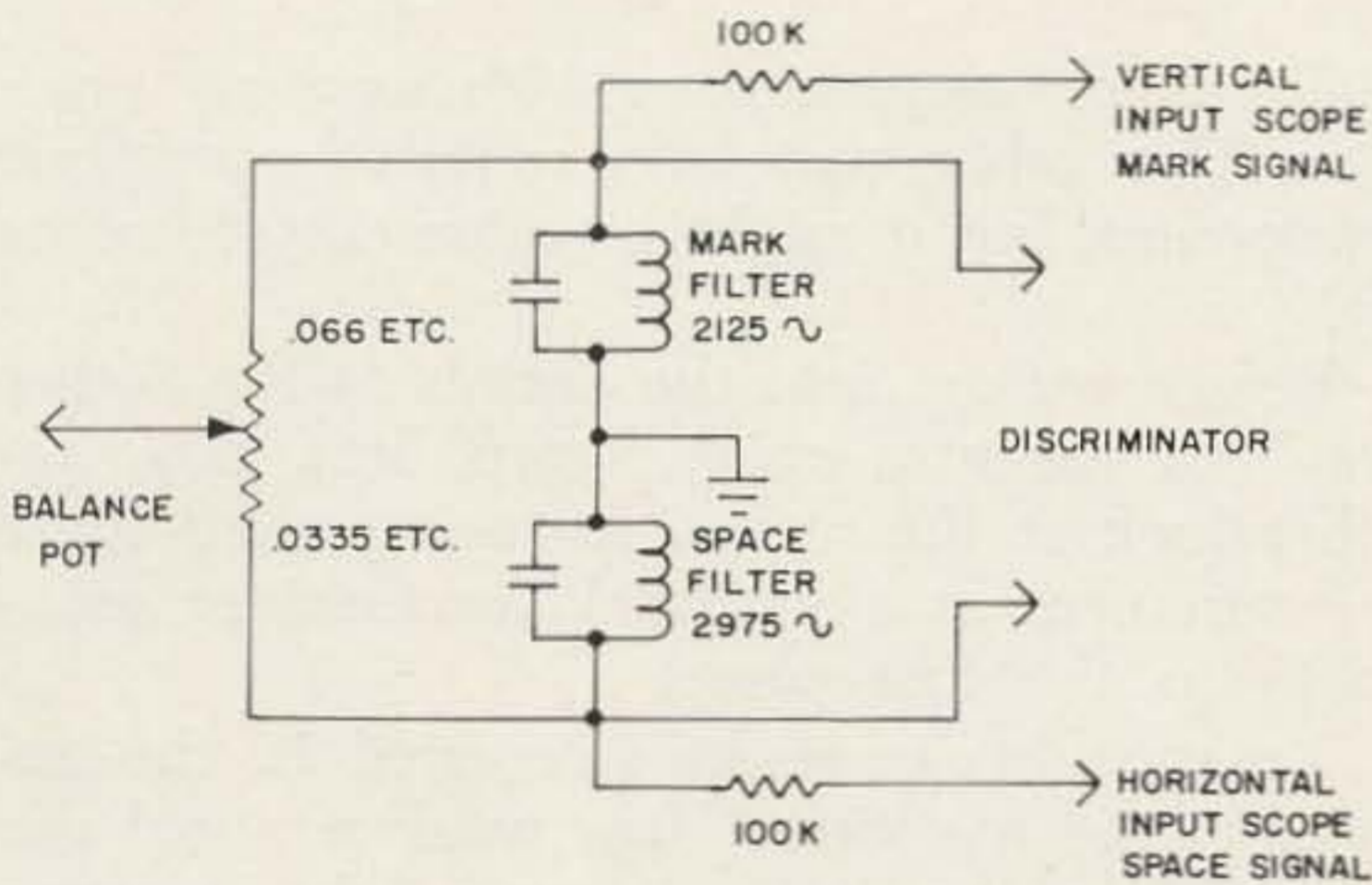


FIG. 1

If the converter is working properly an FSK signal will be only slightly elliptical, as in Fig. 2-B. In tuning in a mark or space signal the patterns should be similar to Fig. 3-A and 3-B.

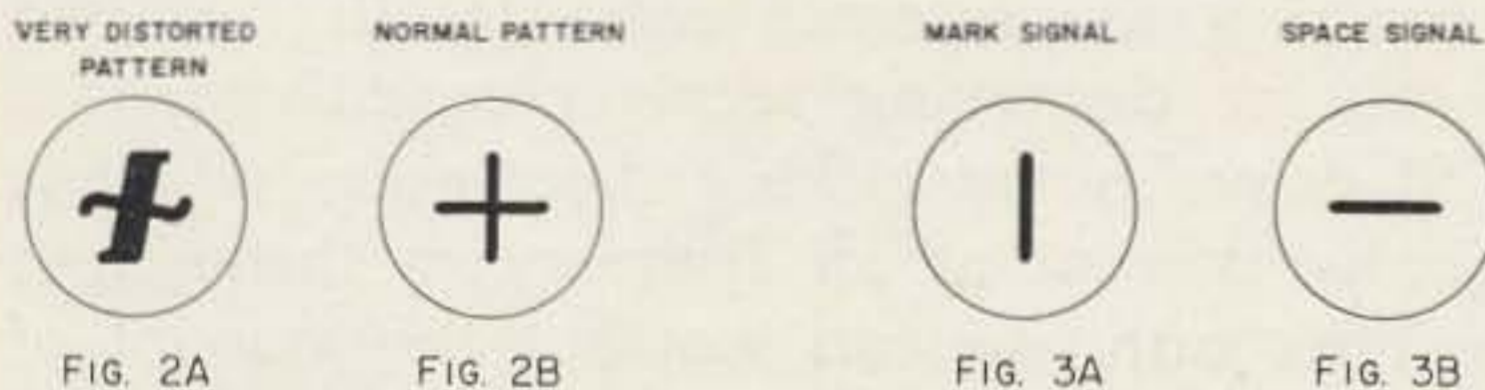The distortion can often be cured by putting two 100-K resistors in series with the toroid filters feeding the vertical and horizontal input of the scope.



Another cause can be ringing taking place somewhere in the unit as a result of poor layout of the converter. All circuits should be run in a straight line and under no condition should an input circuit be located close to its output circuit. Also—remember that aluminum is a poor shield where wiring is done close to power transformers, chokes, input transformers, and mark and space filters, so keep the low level circuits away from such hazards.


With care we can obtain the kind of performance stated in TU designs and our tuning becomes a pleasure with a clean scope pattern. BCNU on RTTY.

. . . K4GRY



**HE
GROUNDED**
(but not quite in time)

DOW-KEY DK60 SERIES COAXIAL RELAYS

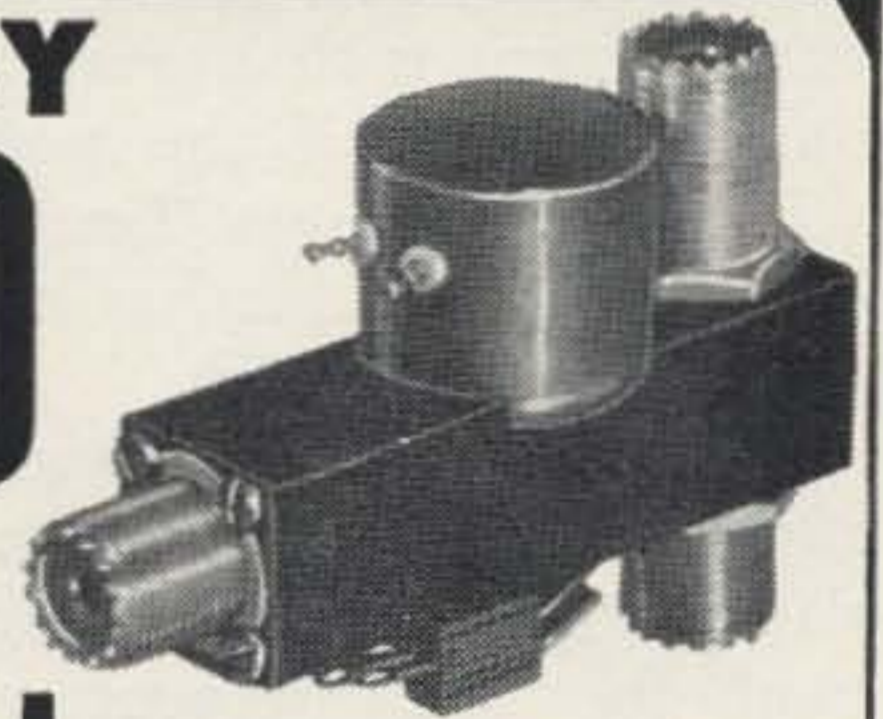

Size
2 3/4 x 3 3/4 x 1 1/8
Less than 9 oz.

DK60-G2C

4 Standard Models, AC or DC,
UHF, N, BNC, TNC or C Conn.

Outstanding favorite for amateurs . . . Versatile combinations for industrials! Low VSWR less than 1.15:1 from 0 to 500 mc. LOW LOSSES . . . High Contact Pressures. LOW CROSS-TALK through use of patented "isolated connector" arrangement. HIGH POWER RATING. All coils encapsulated in epoxy resin for quieter operation and resistance to moisture.

★ UNCONDITIONAL GUARANTEE for one year. (We will repair if faulty within 1 year.)

★ All Relays available in weatherproof boxes for exterior installation.
★ Ganged, multiple position switch arrangement available for remote control selection of antennas.

★ For a catalog of complete line of coaxial relays, write:

STANDARD RELAYS: DK60, DK60-G, DK60-2C and DK60-G2C —

PRICED FROM . . . \$12.45

DOW-KEY CO., Thief River Falls, Minn.

Another Way to Measure Noise Figure

Many times it's been said, but it can always bear repeating. Noise figure is probably the least-well-known measurement in any amateur station.

At least a part of the difficulty with noise figure lies in the means usually employed to measure it. While it's not too difficult to figure out the power input to your final, or even the power *output* (often a surprisingly different figure), measurement of receiver noise figure tends to be a complicated and somewhat inaccurate process at best. It requires special equipment, and even then may be no more accurate than plus-or-minus 100 percent.

The classic means of measuring noise figure is to use a noise generator and crank in additional noise until receiver output is doubled. This means, of course, that the noise generator output is then exactly equal to the original noise, and if the noise-generator output is accurately known then the original noise is also known. All this has been gone into in detail in another article.

However, a noise generator with accurate calibration isn't so easy to come by, and an inaccurate noise generator doesn't do much good for measurement purposes (although it's fine for tune-up).

There is another way to do it, which is ac-

tually much more in line with amateur practice. This other way also requires some test equipment, but it might be more easy to come by.

Before we get into the details of the "other way" to measure noise figure, let's take another look at the reason for using noise-figure measurement as a yardstick for receiver sensitivity in the first place.


To start, we're really interested in the answer to the question "How weak a signal can I hear?" In the 3-30 mc range, the question can be answered directly—how many microvolts must the receiver have to give readable output?

As the vhf region is entered, though, the fractional microvolts become alarmingly small. Somebody figured out that most of the problem lay in the receiver's own internal noise, and came up with the idea of a "perfect" receiver which would have no noise at all. This is a noise figure of 0 db. Now by comparing existing receivers to this perfect ideal, and comparing the internal noise in db, we had a way of discussing receiver sensitivity.

Since we're now talking about noise, which is equally present at all frequencies throughout the spectrum, we can see that the amount of noise present in a receiver's output is at least partially determined by how much of the spectrum we are looking at. A broad receiver has more noise output than a narrow one, all other things being equal. If you don't believe it, fiddle with the selectivity switch on your own rig and listen to the change of noise output.

This dependence of noise on bandwidth is another reason for using noise figure as a comparison. The *actual* amount of noise is cancelled out in the comparison, leaving only the relative amounts of noise in the "perfect" receiver and the receiver under test to be measured.

When all this became established, nobody

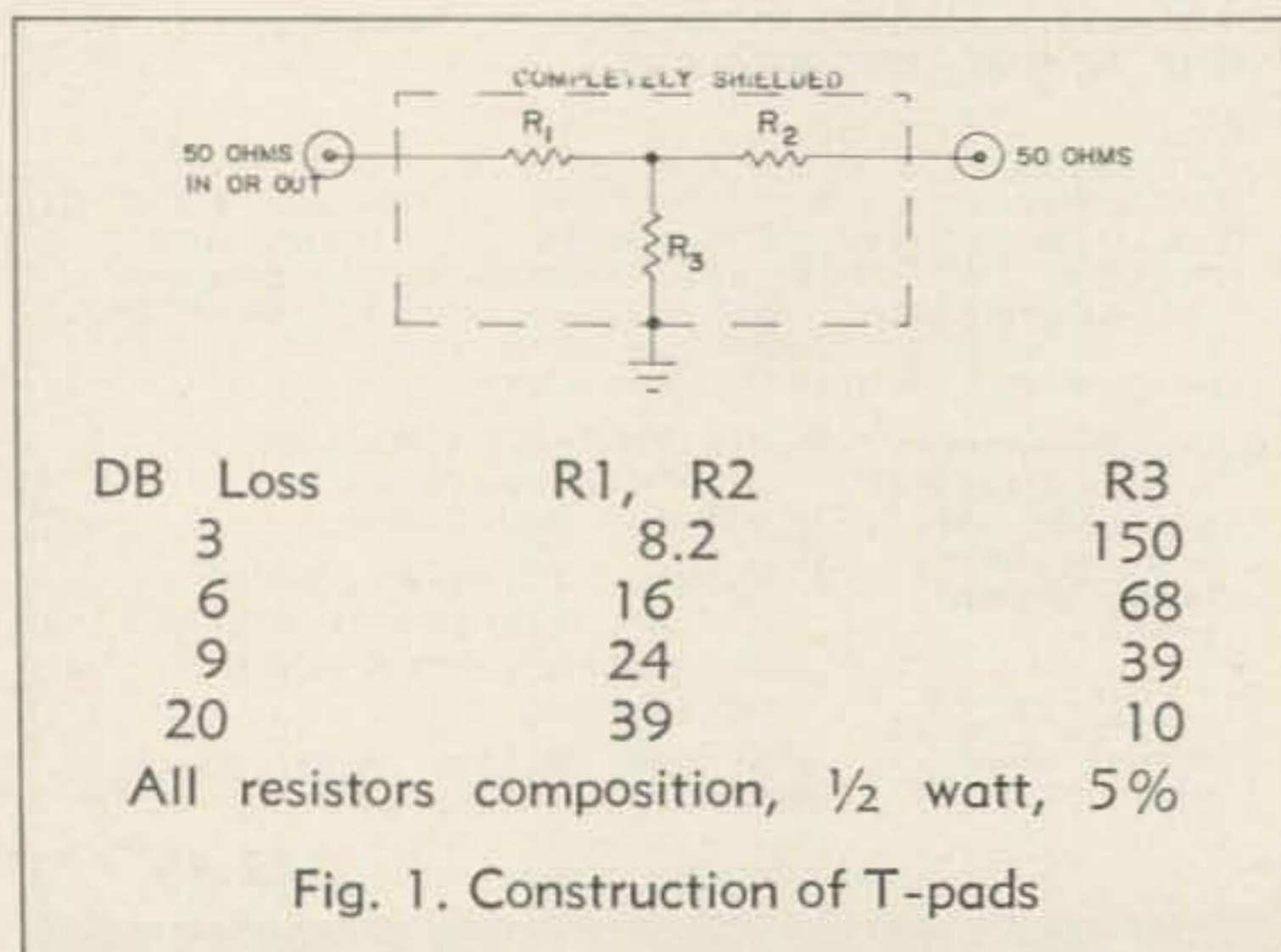

was paying much attention to receiver bandwidth and it was felt that a true determination of the effective noise bandwidth of a receiver was much more complicated than the comparison measurement. However, in these days of SSB and special filters, that's not so true any more.

As you may have guessed by now, the "other method" of determining noise figure depends on a microvolt measurement and knowledge of the receiver's effective noise bandwidth. The only reason for converting the results back to noise figure is to allow comparison with measurements made in the more conventional manner.

With typical ham measurement techniques, the results won't be of National-Bureau-of-Standards accuracy. However, if you're reasonably careful, results using this method will be at least comparable in accuracy to those made with a homebrew noise generator. Ready? Let's go:

You'll need two items of test equipment (only one if you're really lucky). These are an rf signal generator covering the desired frequency range on fundamental output, and an rf VTVM reasonably accurate at the desired frequency. If you have access to a "microvolter" or similar laboratory signal generator, you won't need the VTVM.

In addition, you'll need a whole handful of 50 ohm T-pads; these can easily be put together in a hurry by following the schematic in Fig. 1. You'll probably need about 8 20-db pads, as well as one each in 3-db, 6-db, and 12-db values.

Turn on both the receiver and the signal generator and let them warm up. For protection against any leakage from signal-generator to receiver through the power lines, it's best to supply them from separate circuits and to use a power-line filter such as that used to eliminate rf interference between the power line and the unit.

Connect a string of six 20-db pads to the signal-generator output as shown in Fig. 2, and adjust output of the signal generator to 0.1 volt. If you have a microvolter or equiv-

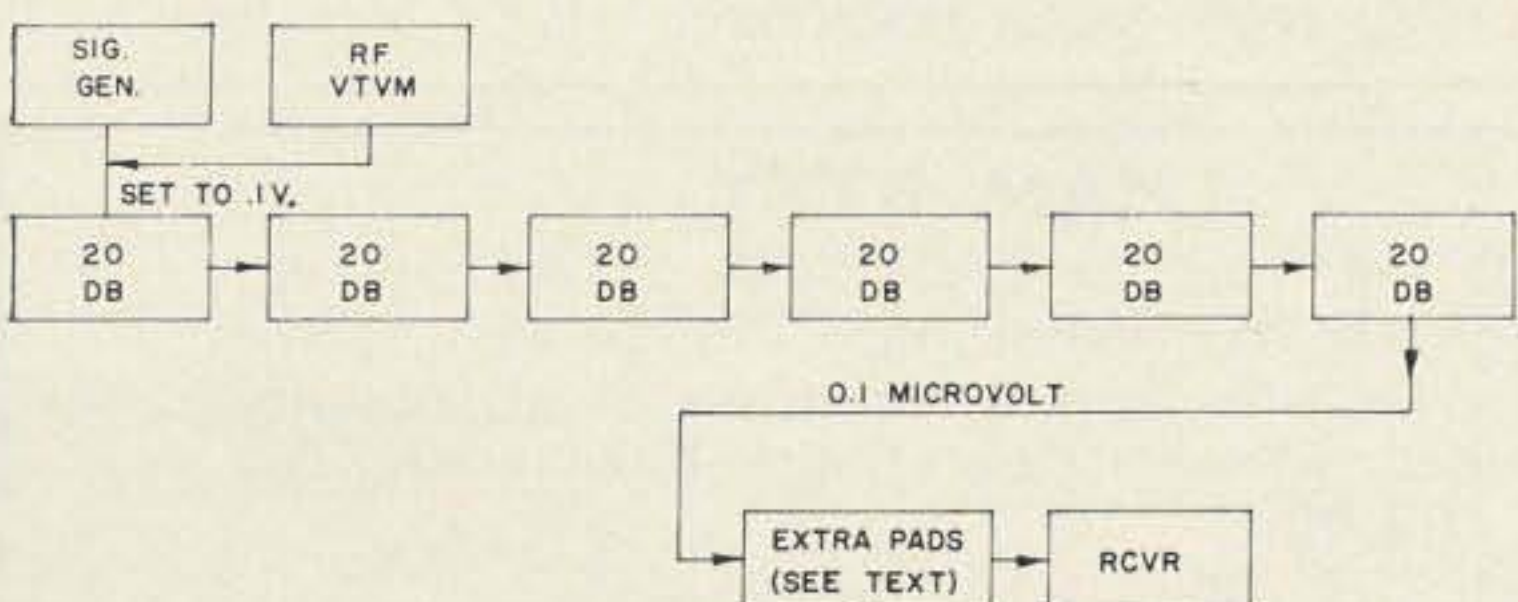


Fig. 2. Test set up.

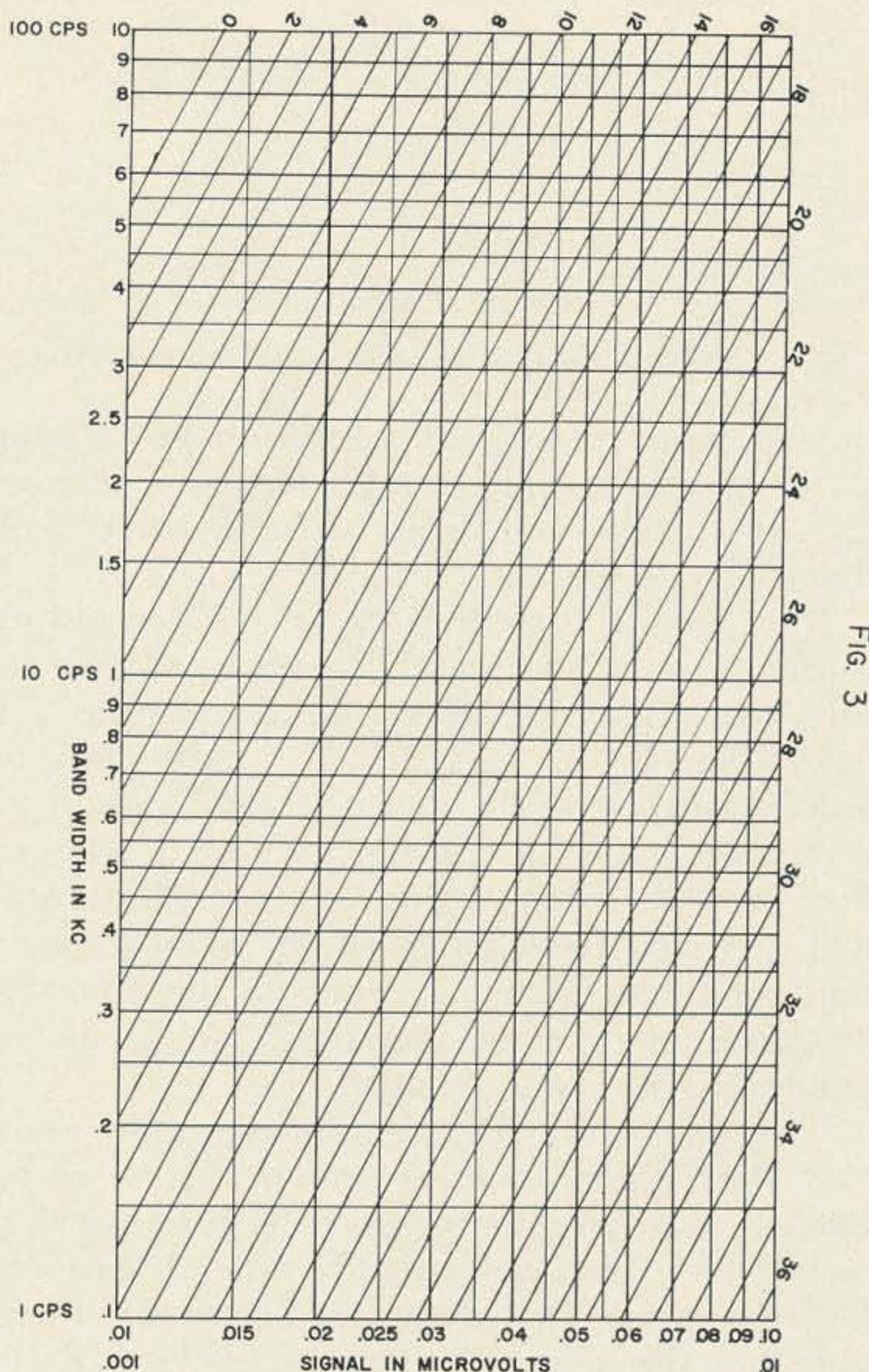


Fig. 3. Noise figure vs. microvolts.

alent, use only one 20-db pad and set generator output to 1 microvolt.

In either event, the output of the final T-pad will be a 0.1 microvolt CW signal. This should be more than adequate for any reasonably-sensitive receiver to allow spotting of the signal.

Switch the receiver's avc off and the bfo on, and place the selectivity switch in any position for which the selectivity is accurately known. The selectivity marked on the front panel will not be the effective noise bandwidth, but you can use it as a starting point to guesstimate the noise bandwidth. If your receiver uses a mechanical filter or other device with approximately the same skirt selectivity, effective noise bandwidth will be about 1½ times the bandwidth marked on the front panel. If it is one of the older types with reasonably broad skirts, noise bandwidth will be about 3 times the marked value. Both these correction factors are approximate, of course; if you have any means of measuring effective noise bandwidth, use it instead.

For a start, use a fairly broad selectivity position; this requires more signal and makes things a bit easier.

Now tune in the signal from the generator,

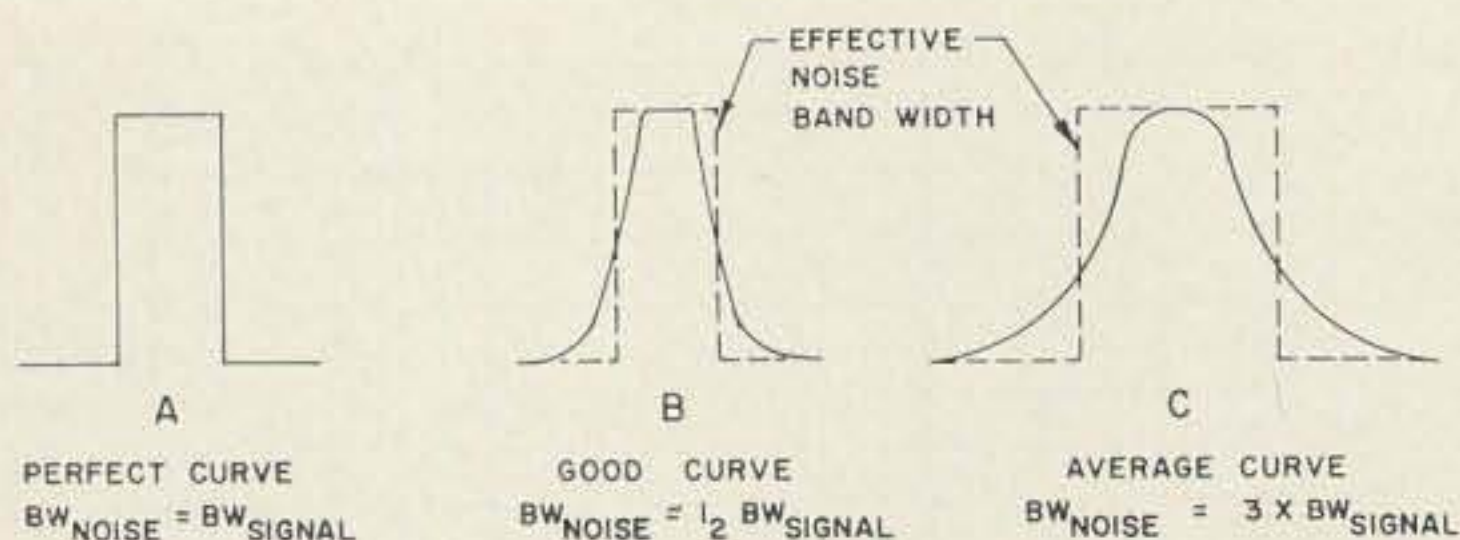


Fig. 4. Relation of noise and signal bandwidths.

leaving gain controls at maximum but tuning for maximum signal strength just as if it were the new state you need. The 0.1-microvolt signal should be easy to find.

Next step is to reduce the generator output by hooking in additional T-pads until you locate the point of "minimum discernible signal." The 3, 6, and 12 db pads may be hooked up in series in any combination to give you from 3 to 24 db additional attenuation in 3-db steps. Using another 20-db pad will give you from 20 to 44 db more attenuation, and the signal is sure to become too weak to copy before you reach 44 db below one-tenth of a microvolt!

The point of MDS is approximately equal to a 0-db signal-to-noise ratio for most of us, and is considerably easier to determine than would be a true output S/N ratio. When you find this point, record the db below 0.1 microvolt and the selectivity (in kilocycles) used.

Now switch to a different bandwidth on the receiver and repeat the test. Record its results also. For maximum accuracy, repeat each of the tests 10 to 12 times and average the result.

The signal level in microvolts corresponding to db below 0.1 microvolt is given in Table I. Locate it there and move to Fig. 3, the graph of signal versus bandwidth by noise figure.

Enter the graph from the side with effective noise bandwidth, and move across until you intersect the line corresponding to signal level in microvolts. The diagonal lines are noise figure; if one passes through the intersection point, read noise figure in db from it. If not, interpolate between the lines.

In reading Fig. 3, use the 10 kc-100 cps scale with the .01-.1 microvolt scale, and the 100 cps-1 cps scale with the .001-.01 microvolt scale. If your bandwidth-signal level combination falls off the graph to the left, use the

lower signal-level scale with the higher bandwidth scale and subtract 20 db from the resulting noise figure.

In the happy event that all your errors (and our approximations) cancel out, you'll find the noise figure to be the same at both the narrow and the broad bandwidth positions. However, it's more likely that you'll measure different noise figures at different positions of the selectivity control. It's safest to take the highest noise figure measured as being closest to correct, but you can average them if you prefer. Either way, you will probably be within 1 db of the real figure—and this is as accurate as most noise-generator techniques can be, also.

That completes the measurement, but before we wind this up let's take a more detailed look at the idea of "effective noise bandwidth" which is such a key part of this measurement technique.

Most of us are familiar with the idea of a "perfect" curve for receiver selectivity such as that shown at A in Fig. 4. Here the receiver has equal response over the desired band, and response drops to zero at the band edge. Such a curve is said to have a shape factor of 1, and is of course impossible to achieve in practice.

Now back to noise; it's spread out equally over the spectrum. A noise bandwidth of 1000 cycles per second contains 10 times as much noise as one of 100 cps. Thus "noise bandwidth" inherently has a shape factor of 1.

Since such a shape factor is impossible to achieve, it follows that "noise bandwidth" and actual receiver bandwidth must differ. If receiver bandwidth is measured at the -60 db points, the noise bandwidth will always be smaller than this receiver bandwidth. If receiver bandwidth is measured at the points where response drops 1 db below peak, the noise bandwidth will always be greater.

The mathematical expression for noise bandwidth is an integral equation involving differential gain, which is a cumbersome thing to solve. In general, the noise bandwidth of a receiver is said to be approximately equal to the bandwidth between points which are 3 db down from peak response.

HAM-RTTY



HAM RTTY

This is the most complete book on the subject. Written for the beginning TT'er as well as the expert. Pictures and descriptions of all popular machines, where to get them, how much, etc.

\$2.00

73 Magazine
Peterborough, N. H.

db BELOW 0.1 MICROVOLT	MICROVOLTS
3	.07
6	.05
9	.035
12	.025
15	.018
18	.013
20	.01
21	.009
23	.007
24	.0063
26	.005
29	.0035
32	.0025
35	.0018
38	.0013
41	.0009

Table 1.

In practice, if the shape factor (6 to 60 db) of the receiver is 2, the effective noise bandwidth will be approximately 1.3 times the 6-db bandwidth. If shape factor is between 2 and 10, noise bandwidth will be approximately equal to the square root of the shape factor (6 to 60 db) times the 6-db bandwidth. Few receivers have shape factors greater than 10.

The approximations quoted earlier (1.5 times marked bandwidth for SSB-selectivity receivers, 3 times marked bandwidth for others) are based on these relations. If you're really interested in calibrating your receiver's noise bandwidth for using this measurement technique, however, you might take a converter and have it measured for noise figure by the generator technique, then run this technique backwards to determine the effective noise bandwidth of your receiver in each position of the selectivity control.

The technique described here, incidentally, assumes that no audio filters are used following the detector. If they are, all results are off, since the effective noise bandwidth will have been changed in an unpredictable manner by the audio filters.

However, you can remove the audio filters from the hookup for measurement purposes, determine noise figure, then return the audio filters to the circuit and run the measurement backward to find out your effective noise bandwidth with filters present. Don't be surprised if it comes out in the region from 1 to 10 cycles per second; a good audio filter can work wonders with weak-signal reception.

For additional details on this technique of measuring noise figure, you can consult Reference Data for Radio Engineers, 4th edition, published by IT&T and available from Radio Bookshop, or any good radar text.

... K5JKX



HE DIDN'T HAVE TO GROUND AT ALL

(He owned the linear)

He's well pleased of course, and proud of that highly potent KW signal, as who wouldn't be? Yes, and perhaps he's just a bit self-satisfied in the knowledge that he had the foresight to take advantage of a really exceptional bargain. This linear operates on 80-40-20-15, has built-in, heavy-duty 117V AC power supply, costs only **249.50**.

YOUR **SBE** DISTRIBUTOR IS THE MAN TO SEE

"Your Friendly Supplier"

THE **SBE**
SIDE BAND ENGINEERS
SB-34
SSB Transceiver

OFFERS



The SBE SB-34 packs plenty of punch on 80, 40, 20, and 15 meters sideband with 135 watts PEP. (Slightly lower on 15). Also covers MARS and out-of-band DX frequencies. Built-in Supply for 12 Volt and 117V AC. Solid-state switching . . . no relays. Solid-state dial calibration. Delta Receiver tuning. Low frequency drift. Dual-speed tuning.

Feature-wise . . . Dollar-wise . . .
The Biggest Transceiver Value ever!

Model SB-34 . . . Only \$395.00 Net
Matching Mike No. SB2-MIC . . . \$14.50 Net

Also in stock: SBE Model SB2-LA 4-band
Linear Amplifier . . . \$249.50 Net

We maintain the largest stock of used equipment in the Northeast — Engineering Department — Time Payment Plan available.

WRITE FOR LATEST COMPLETE LIST

Evans RADIO

P.O. BOX 312

FONE
603-225-3358

CONCORD, N. H.

The improved full coverage SIDEBAND TRANSCEIVER



\$585.00
Amateur Net



DRAKE TR-4

All features of Drake TR-3
PLUS ...

- ★ Solid State VFO with linear permeability tuning for maximum stability
- ★ Automatic Transmit/Receive Switching on CW (semi break-in)
- ★ CW Sidetone Oscillator built-in
- ★ VOX or PTT on AM
- ★ Connections for External Receiver
- ★ Diode Detector on AM
- ★ Relative RF Output Indication

Features of TR-4 and TR-3

- Full Frequency Coverage on all amateur bands 10 through 80 meters. No additional crystals required.
- Upper and Lower Sideband on all bands.
- VOX or PTT built-in.
- Output Impedance Adjustable with pi-network.
- Separate Receiver S-Meter and Transmitter Plate Ammeter.
- 300 Watts PEP input on SSB.
- Controlled-Carrier Screen Modulator for AM built-in.
- Shifted-Carrier CW 260 watts input.
- Two Special 9 Mc Crystal Filters for sideband selection.
- Separate RF and AF Gain Controls.
- 1 Kc Dial Accuracy.
- 100 Kc Crystal Calibrator built-in.

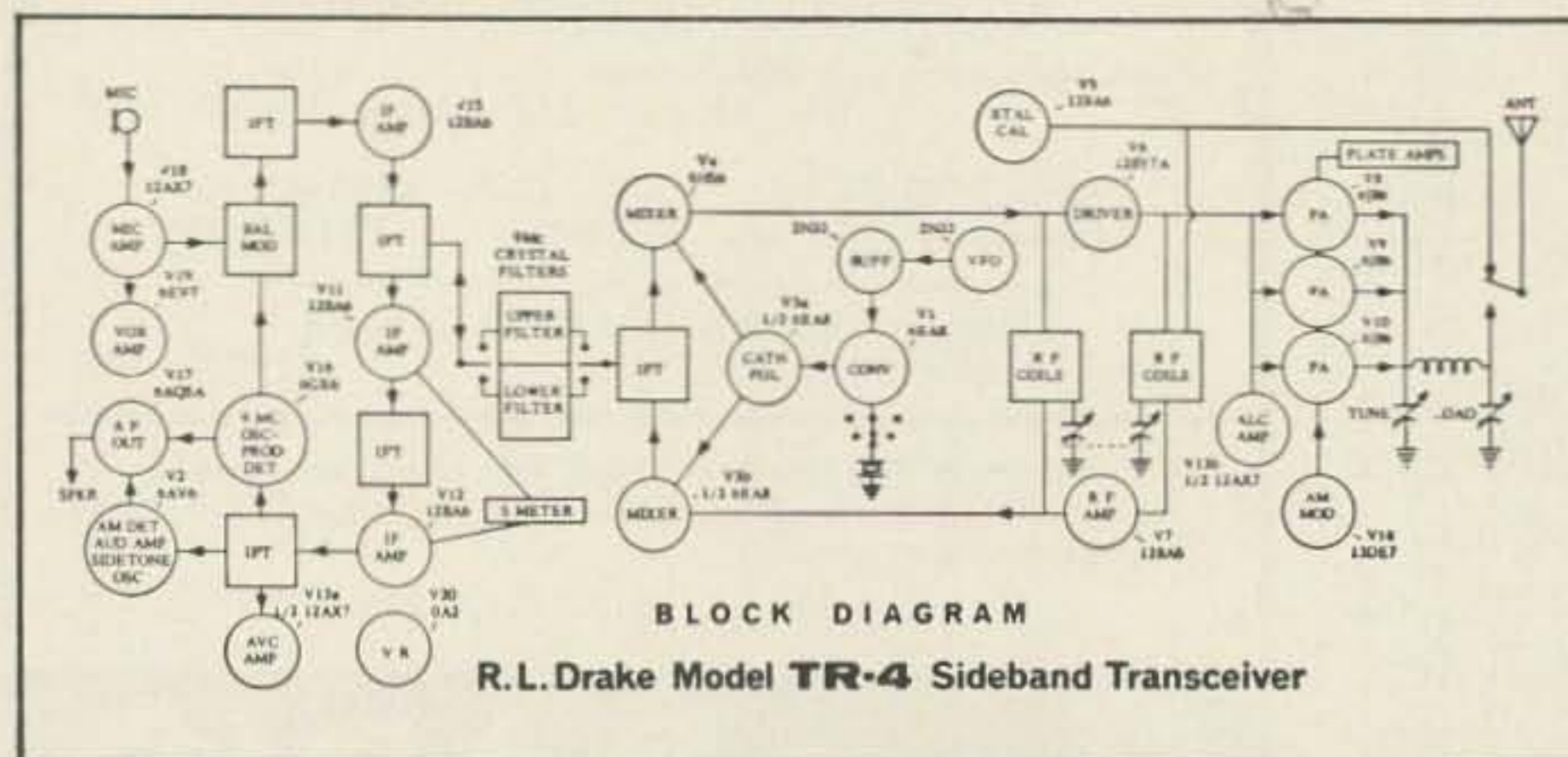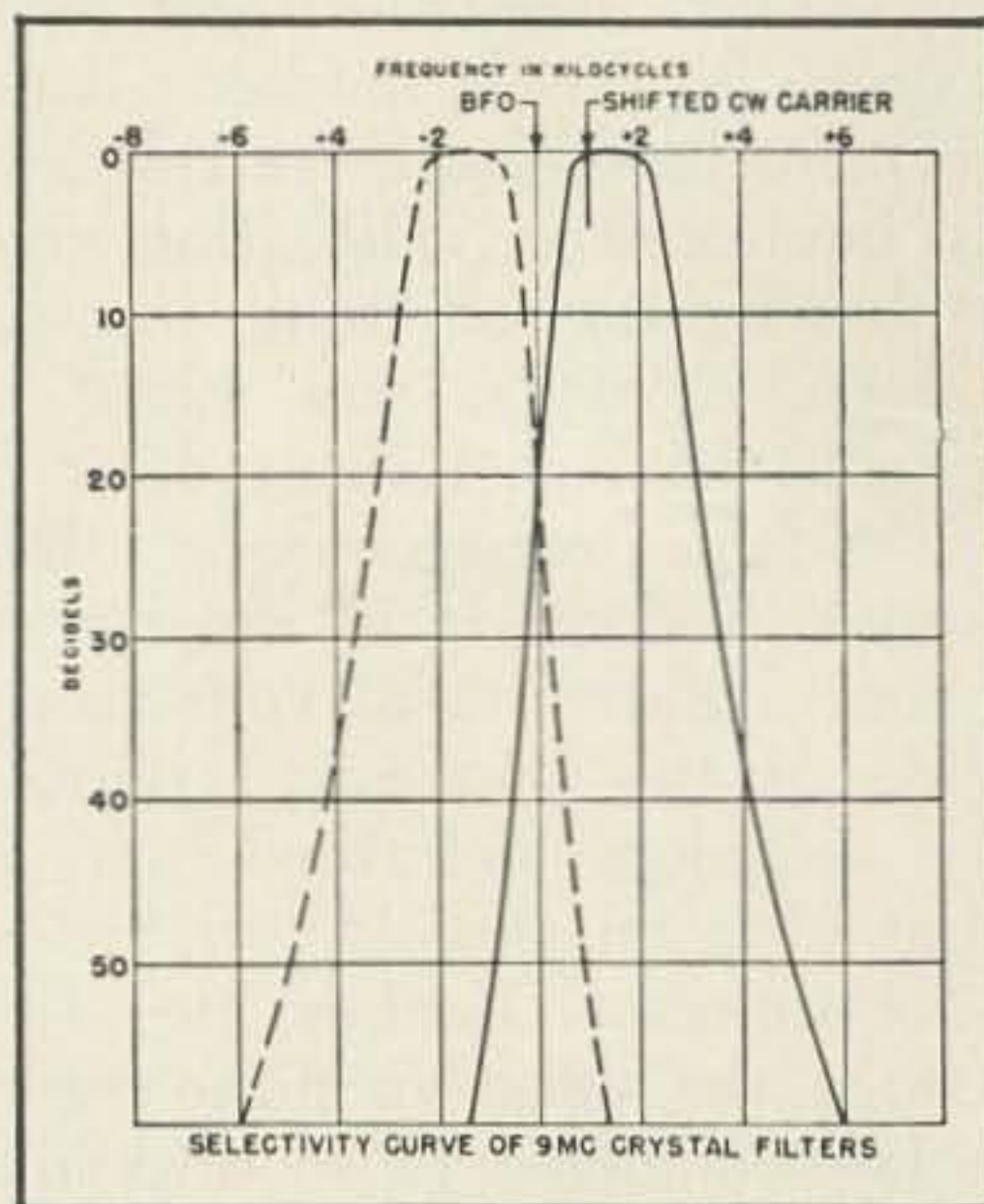

ACCESSORIES

for either TR-4 or TR-3

REMOTE VFO

Model RV-3 . . . \$79.95

MATCHING SPEAKER

Model MS-4 . . . \$19.95

MOBILE MOUNTING KIT

Model MMK-3 . . . \$6.95

POWER SUPPLIES

AC Power Supply Model AC-3 \$79.95

DC Power Supply Model DC-3 \$129.95

For more information, see your distributor or write:

R. L. DRAKE COMPANY MIAMISBURG, OHIO, 45342

Super-combination for transceiving...

The new Receiver-controlled Exciter...

DRAKE
T-4
EXCITER

+

DRAKE
R-4
RECEIVER

=

The ultimate in transceiving



Model T-4 **\$269⁹⁵** Amateur Net

T-4 Features

- Covers all Ham Bands 160 thru 10 meters.
- Covers MARS and Other Frequencies between ham bands.
- Upper and Lower Sideband on all frequencies.
- Automatic Transmit Receive Switching on CW (semi break-in).
- Controlled Carrier Modulation for AM is completely compatible with SSB linear amplifiers.
- VOX or PTT on SSB and AM built-in.
- Adjustable Pi-Network Output.
- Two Crystal Lattice Filters for sideband selection, 2.4 Kc bandwidth.
- Transmitting AGC prevents flat topping.
- Shaped Grid Block Keying with side tone output.
- 200 Watts PEP Input on SSB—180 watts input CW.
- Meter indicates plate current and relative output.
- Compact size; rugged construction.

Complete Transmitter (LESS POWER SUPPLY)



Model T-4X, Amateur Net:

DRAKE
T-4X

- All T-4 features plus
- Solid State VFO and
 - XTAL Oscillators...

Give:


- Separate control of receive and transmit frequencies
- Transceiver operation with frequency control by either Rcvr or Xmtr
- Coverage on 80, 40, 20, 15 meters completely and 28.5 to 29.0 Mc of 10 meters with crystals furnished
- Four extra 500 Kc ranges can be covered with accessory crystals (160 meters, other 10 meter ranges, MARS, etc.)

\$379⁹⁵

AC-3 Power Supply for T-4 and T-4X: \$79.95

R. L. DRAKE COMPANY MIAMISBURG, OHIO 45342

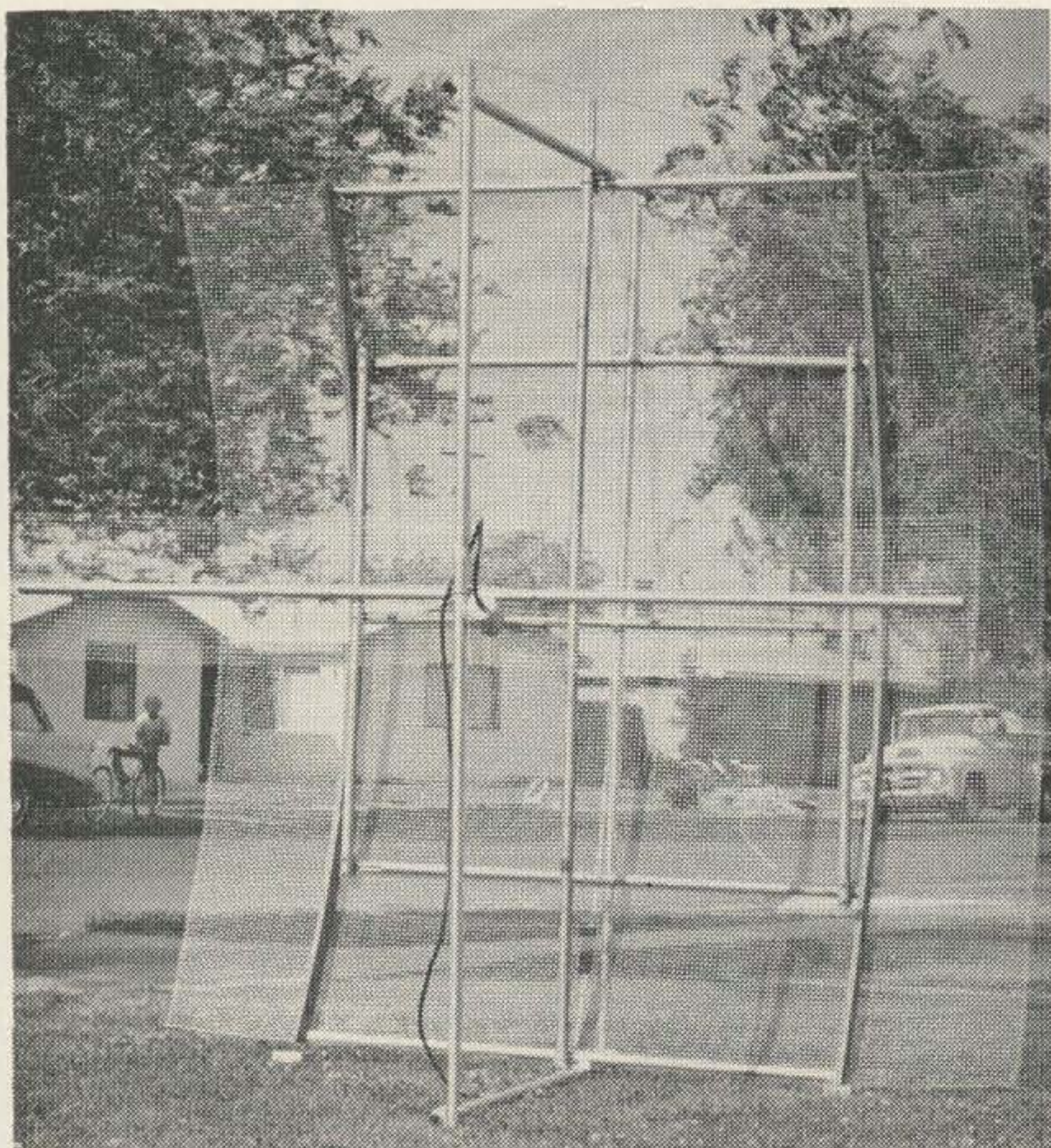Jim Kennedy K6MIO
2816 E. Norwich
Fresno 26, Calif.



Photos by Joe De Young WA6CQL

The Big Sail

The Ultimate for 70 Cm.

The 432 Mc band has over the years, offered a fertile proving ground for antenna designs. However, building antennas for 432 involves some considerations and problems that are not evident at lower frequencies.

The close tolerances required by parasitic arrays such as the yagi become difficult to handle. Designs that work well at 144 Mc give very disappointing performance when scaled down to 432.

In many cases, the failure of such yagi layouts is the fact that the antennas are built "according to the book" and not on a test stand where the various parameters can be varied to compensate for factors the "book" failed to take into account.

However, even with yagis which have apparently been tuned properly, there are stories in circulation about antennas which showed good patterns but poor gain, though why this would be I don't know.

In any case, the yagi, even if working properly, is a delicate beast and suffers from rather severe bandwidth limitations.

True, if operation on 432.000 ± 3 Mc is

all that is desired, then the 6 to 7 Mc bandwidth of the yagi would be acceptable—assuming you could get your antenna to peak on the *right* six megacycles. If TV or some other broadband operation is desired, even a working yagi leaves something to be desired.

Various types of colinear—broadside arrays can be made to perform quite well. The extended, expanded H arrays can and do deliver about 15 db of gain while 32 element

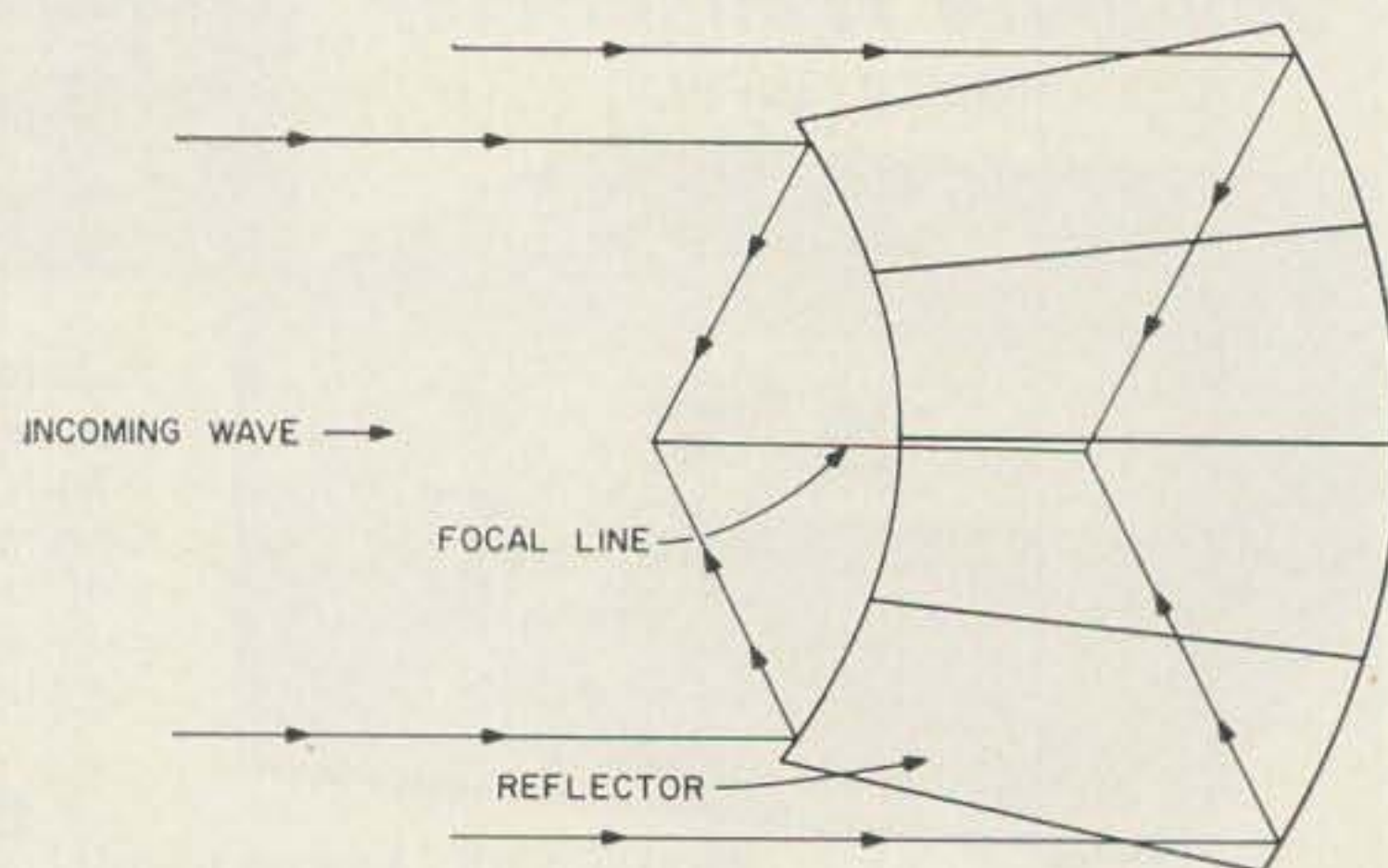


Fig. 1. Focus action of the cylindrical parabola.

SUPPRESS RFI IN YOUR MOBILE RADIO GEAR!



NEW!
SPRAGUE SUPPRESSIKITS
FOR VEHICLES WITH
ALTERNATOR SYSTEMS

Easily installed on cars or trucks with citizens' band, amateur, industrial, or public service mobile radio equipment

- ★ Three different Suppressikits to choose from—Type SK-10 for Chrysler Corp. cars and trucks, Type SK-20 for Ford Motor Co. vehicles, and Type SK-30 for General Motors Corp. equipment.
- ★ Designed to fit most newer vehicles through the 1965 model year. (for older vehicles, see the SK-1 Suppressikit, below.)
- ★ Well-engineered L-C Networks and/or heavy-duty Thru-pass Capacitors handle the hash and eliminate the siren-like whine caused by the alternator output.

- ★ Extremely easy to install—no cutting, no soldering, no wiring harnesses. All components are neatly marked and packaged, and come complete with comprehensive step-by-step installation instructions.
- ★ Provide really *effective* interference suppression through 400 mc, at moderate cost.
- ★ Will stand up under continuous operation in hot engine compartments.
- ★ Permit faster, more readable, less tiring communication at greater ranges.


TYPE SK-1 SUPPRESSIKIT FOR VEHICLES WITH D-C GENERATORS



Designed for simple but effective installation. The generator capacitor is built for continuous heavy duty 257°F (125°C) operation. A full 60 ampere current rating plus the high rated operating temperature provide an extra factor of safety against expensive generator burnouts, unlike many suppression assemblies containing general-purpose capacitors. Effectively suppresses RFI through 400 mc. Includes easy-to-follow installation instructions.



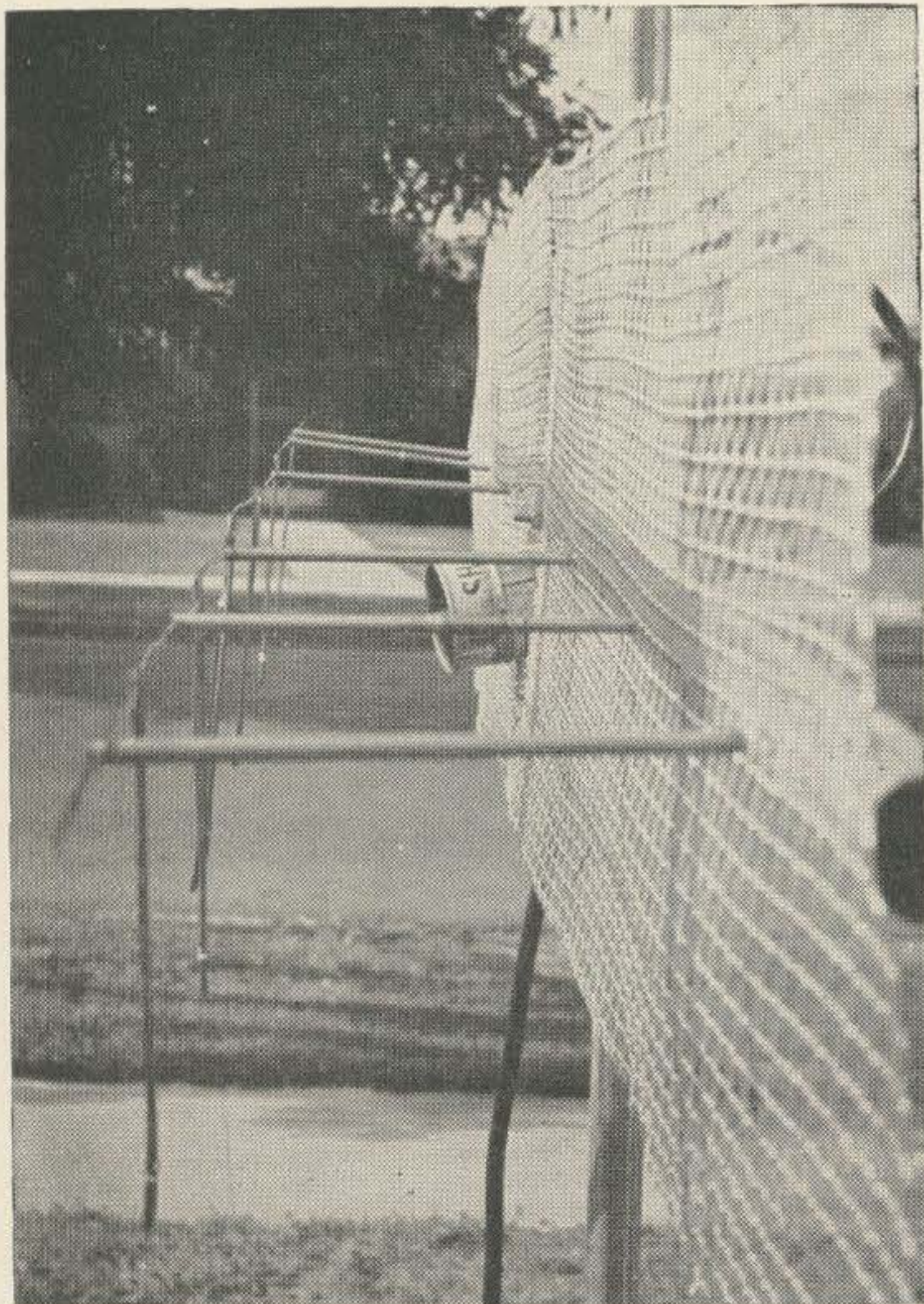GET YOUR SUPPRESSIKIT FROM A SPRAGUE DISTRIBUTOR TODAY !



Side view of collinear feed.

units have been measured at over 17 db.

Though they are much easier to make work than the yagi, the large colinears have one drawback in common with the yagi and any other multi-element array—the more elements, the higher the Q and the narrower the bandwidth. Unlike the yagi, you can reliably increase the gain of the collinear by adding elements. However, the bandwidth will be reduced, though it is difficult to say to what precise figure.

When it was decided to build some sort of “ultimate” antenna for 432, several basic requirements were established. It was concluded that the antenna should have a minimum honest gain of 18 db referenced to a dipole, the widest bandwidth possible up to the limit of the band edges; and electrical and mechanical simplicity that would guarantee ease of tune up and reliability of operation.

The yagis were immediately discounted on the basis of a number of previously unsatisfactory experiments.

The collinear broadside was given considerable thought but the idea was set aside on the basis of the feed harness nightmare involved in feeding what would have to be a minimum of 64 elements.

The high gain, broad bandwidth require-

ment suggested a parabolic dish. Certainly nothing could be much simpler to feed than a single dipole and the reliability of the antenna should be considerably higher than any of the other types considered.

However, the conventional dish (paraboloid of revolution) is mechanically difficult to construct. The curve in two planes makes it difficult to get a smooth surface on the dish without considerable trouble.

Another, less familiar, form of the paraboloid reflector—the parabolic sheet or cylindrical parabola—was then studied. This is merely a sheet of reflecting material bent into a parabolic shape in one plane only. Mechanically, such a device is very easy to construct with simple tools and a minimum of expense.

As has probably occurred to many readers, the sheet parabola has a distinct electrical difference from the dish parabola, that is, its focus is not a point, but, rather, a line, as diagramed in Fig. 1. In order to extract the maximum amount of energy incident on the reflector, it is necessary to place an energy extractor (antenna) all the way along this focus line. Some sort of simple colinear or broadside configuration would seem ideal depending on whatever other considerations might arise.

The original gain requirement put forth was 18 db. A quick investigation of some antenna charts shows that a 9 foot circular dish would provide just about 18 db computed by radar formula. The area of a 9 foot circular dish is 63.6 square feet. A square parabolic sheet 8 feet on a side has an area of 64 square feet and should, if properly fed, produce about the same gain. The approach seemed to hold considerable promise and it was decided to build such an antenna and give it a try.

One of the first problems was the choosing of the focal length of the dish. In order to minimize electrical coupling between the reflector and the driven element, it is desirable to use a focal length of several wave lengths with all parabolic reflectors. Though a little short, a focal length of 4 feet—2 wave lengths—was settled upon. In order to operate properly at 432 Mc it is necessary that the “peak to peak” deviation of the dish surface from the true paraboloid shape not exceed 1/8 wave length or about 1½ inches. This is necessary, if the performance is not to be degraded by phase cancellation. This tolerance is very easy to maintain. In fact, the tolerance achieved on the sheet was better than ½ inch by a fair amount and no extraordinary care was necessary. The reflector itself would be quite satisfactory for 1296 Mc

(and have about 28 db gain, but that's another story).

Reflector

Table 1 shows the measurements of the parabola at 6 inch intervals each side of the center. Fig. 2 shows how these were laid out and marked on a sheet of 5/8 inch plywood eight feet long and 24 inches wide.

Several 10 foot lengths of inexpensive TV mast were obtained and four of them were cut in half, yielding eight pieces 5 feet long. Five of these pieces will, with the plywood slats, be used as the basic framework for the reflector surface. The mast should be of some material other than aluminum.

The mast tubing pieces are attached to the plywood at equal intervals by placing a 10 - 32 screw through the tubing about one inch from each end. The eye of a two inch eye bolt is threaded onto the 10 - 32 screw inside the tubing as the screw is placed through the tubing. The threaded portion of the eye bolt should then extend about one inch from the end of the tubing.

The eye bolts are then inserted into holes drilled into the plywood slats and held in place with a nut and large flat washer on the other side.

The mast pieces are attached so that their back edges are just flush with the back edges of plywood slats. This is necessary because the reflecting surface, when attached, will be applied to the back side of the framework and both the slats and the masts will be used to anchor the surface.

In order to minimize any twisting or skewing of the antenna two 5 foot masts are attached across the second and fourth masts in the framework next to the slats with TV antenna U clamps. This adds considerably to the rigidity of the antenna.

The next requirement will be about a 19 ft. length of 4 foot wide 1/2 inch mesh hardware cloth. This length is cut in half and the two 9 1/2 foot pieces are laid side by side and tied together with tinned copper wire. The lacings should be soldered to the mesh to assure good electrical connection and mechanical stability, though this can be done later, if desired.

The framework should be laid on the ground, face down, and the mesh should be laid across it so that the seam in the mesh runs along the long dimension of the framework. Place the mesh so that one end comes flush with the tubing at the top (or bottom) of the framework. Tinned copper wire is then used to attach the mesh to the framework.

The mesh should be pulled tight and it should be attached starting at one end (top or bottom) and proceeding to the other end.

When the mesh is attached there should be something more than a foot of hardware cloth left over at one end. This should be cut off and saved; it will be used later. The mesh can now be spot soldered to the tubing with a propane torch to insure that it is firmly in place.

The mesh will overlap the narrow dimension of framework by 1 1/2 feet on each side. The corners of the mesh have a tendency to curl because of the lack of support. This can be corrected in a number of ways. One way which works quite well is to reinforce the top and bottom edges of the mesh by running 2 foot lengths of brazing rod along each side of the top and bottom masts in the frameworks. They are extended 1 1/2 feet past the ends of the masts and soldered to both the mesh and the masts.

This procedure will add considerably to the rigidity of the corners of the mesh.

Several coats of lacquer applied to the plywood slats will help protect the wood from the elements.

Driven Array

The reflector now being essentially finished the next problem is to feed it properly. Some sort of an array must be constructed to extract energy from the focus line of the reflector.

At this point it might be well to digress from the construction discussion and consider some of the theoretical aspects of feeding a parabolic reflector.

The basic problem in feeding the dish is


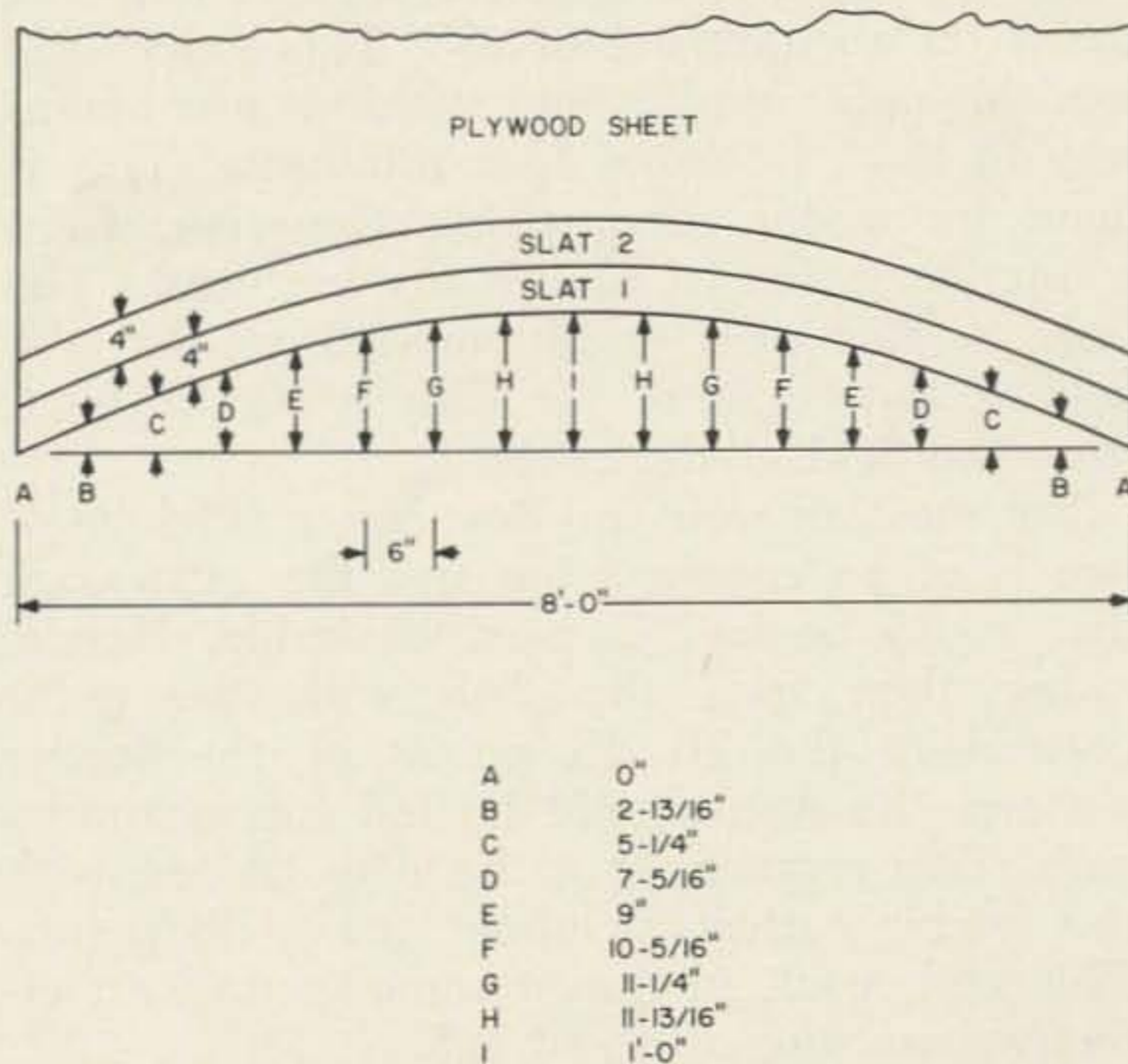


Fig. 2. Plywood layout. Table 1. Values for parabolic curve.

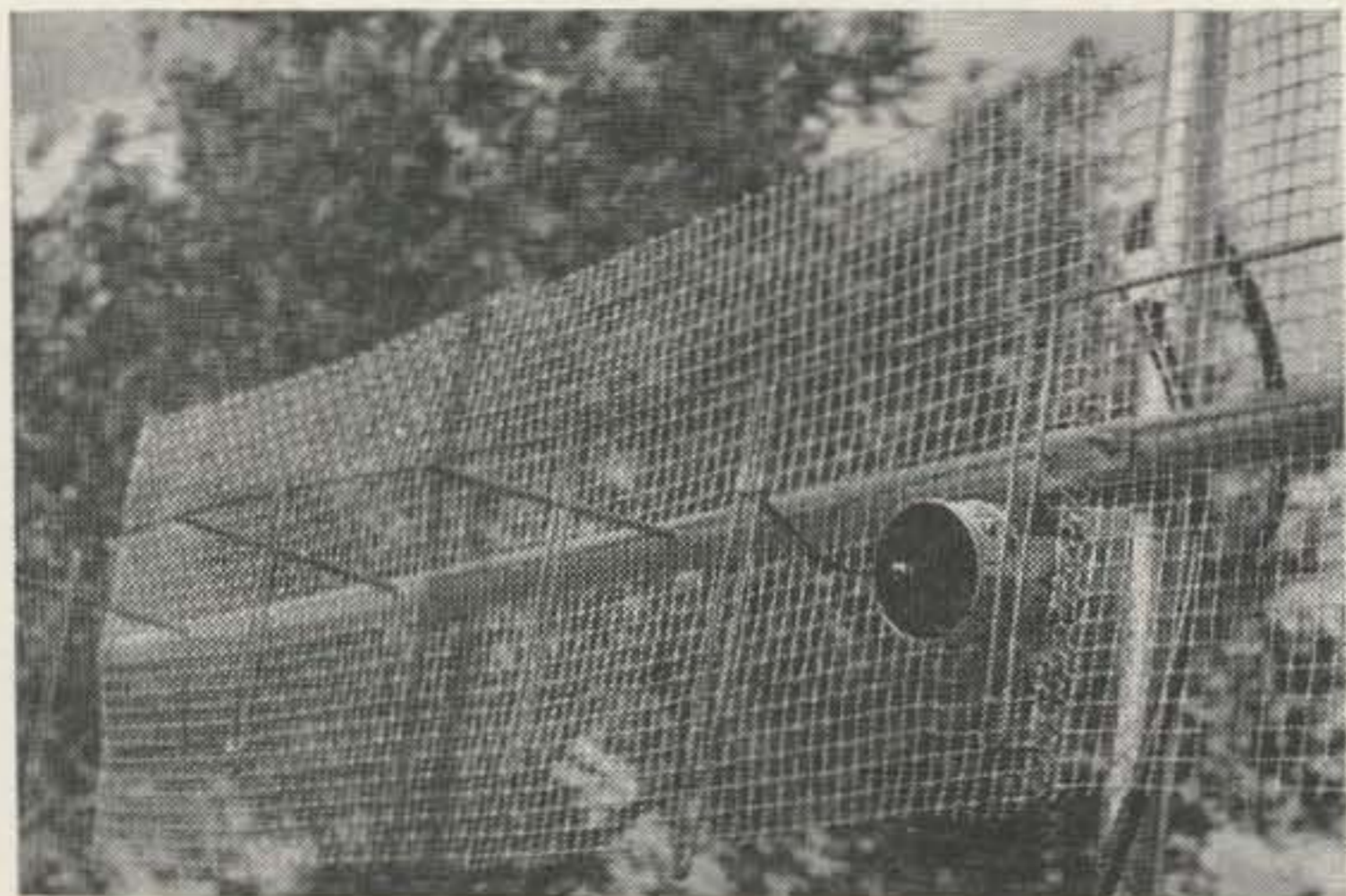

Detail of balun.

one of illumination. That is, placing the energy on the dish surface in the most efficient fashion. The field pattern of the driven element (or array, as the case may be) should be such that a maximum amount of energy is directed at the largest possible amount of reflector surface. If the pattern of the driven element is too broad, then excessive amounts of energy will miss the dish entirely and be wasted. If, on the other hand, the pattern is too narrow, the full width of the reflector is not used and gain is therefore lost; the effect is the same as using a smaller dish to start with.

It is because of the necessity of a compromise between these two somewhat conflicting factors that the effective aperture or capture area of dish is always smaller than the physical area of the dish. Values of 0.5 to 0.7 are typical.

Several of the handbooks consulted indicated that the gain of a 9 ft dish was about 18 db. Some neglected to mention that this was based on an aperture of .55. This value was used for radar applications where it was necessary to limit sidelobes to a minimum. This is done by under illuminating the dish. Gain is sacrificed but sidelobes are reduced. The dish, in this case, is illuminated so that the field at the edges of the dish is 10 db down from the field at the center.

For most amateur applications, a sidelobe or two is of no consequence and the extra gain that could be had is most desirable. Hence, rather than feed the dish with the radar pattern—to the 10 db points of the feeder pattern—the dish should be fed for maximum gain. This requires that the dish be fed with the feeder pattern to about the 3 db points. This will result in maximum gain and an effective aperture of about 0.7.

The final result is a gain of not 18 db but closer to 19.3 db with reference to a dipole

or about 21.5 db with reference to an isotropic radiator.

This discussion of illumination has been primarily concerned with the paraboloid of revolution. It is, however, likewise true of the parabolic plane of the parabolic sheet.

A little geometry will reveal that the 3 db beam width of the feeder in the parabolic plane should be in the neighborhood of 110 degrees.

This pattern will be compressed considerably by the parabolic shape of the reflector and the reflector will, by this compression, produce the final beam width of the sheet in the parabolic plane.

In the other plane, the "flat" or non parabolic plane, the feed should simply exist all along the focus, whatever beamwidth the feed itself has will simply be reflected by the sheet and will become the final beam width of the sheet in the flat plane.


The feed array which seemed most likely to satisfy these requirements was a seven element series fed collinear. This is, in essence, a string of dipoles laid end to end and end fed, in phase, by a series of half wave delay lines (quarter wave shorted stubs).

This type of array has several good points. The series feeding system eliminates the necessity of the usual feed harness, it allows very simple adjustment of the dipole phasing for optimum gain and it virtually eliminates the necessity of insulators and allows rigid all metal construction.

Fig. 3 shows the various dimensions of the array. The array is bent from a single piece of #10 soft drawn solid copper wire.

The dipoles are supported at their centers on the ends of $\frac{1}{4}$ inch brass tubes. The tubes are mounted in quarter inch holes through an 8 foot long piece of TV mast. The lengths of the brass tubes should be such that the dipoles are supported $\frac{1}{4}$ wave—6 $\frac{3}{8}$ inches—from the front edge of the mast.

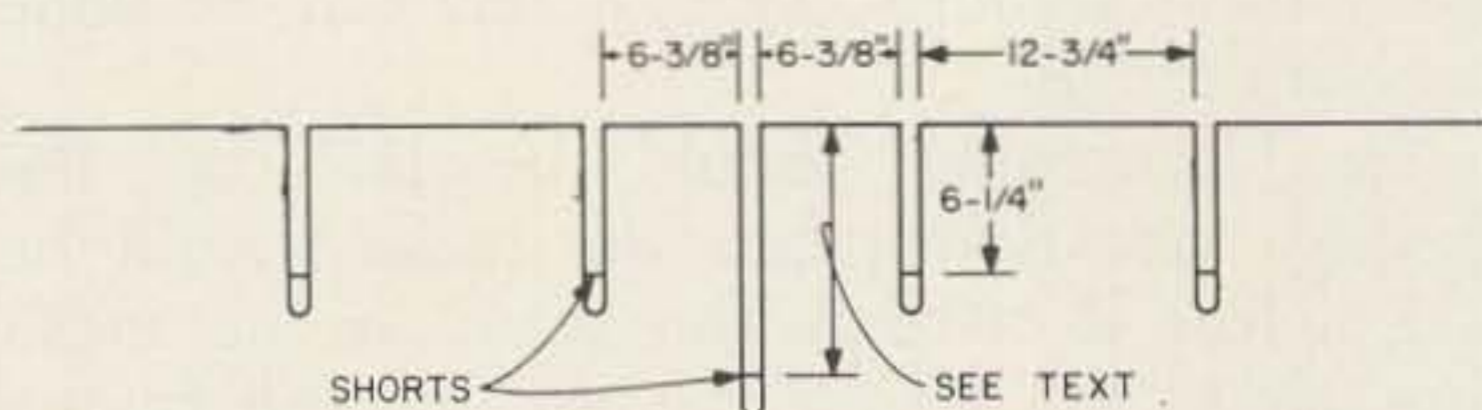
After the tubes have been attached to the mast but before the dipoles are added, a piece of the left over hardware cloth 8 feet



ONLY 5 OF THE 7 DIPOLES ARE SHOWN. ALL DIPOLES AND STUBS ARE SAME LENGTHS EXCEPT FOR CENTER DIPOLE AND STUB.

Fig. 3. 432 Mc collinear dimensions.

TRANSCEIVER HIT PARADE

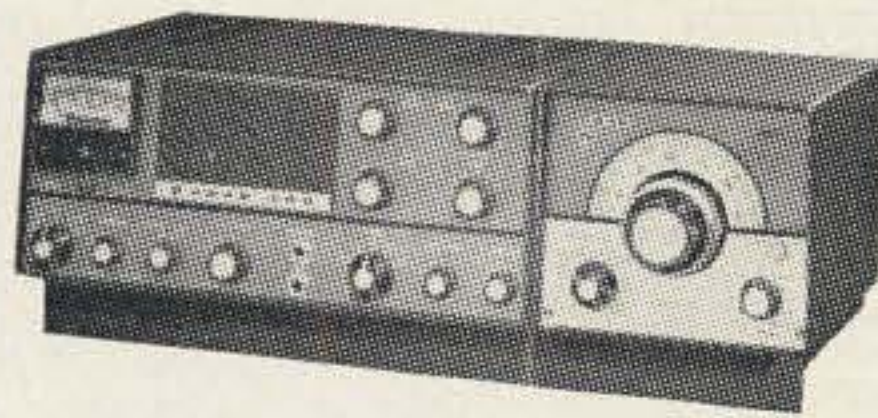

Use our tailor-made
time payment plan.

COLLINS

KWM 2 Transceiver	1150.00
516 F2 AC Supply	115.00
MP 1 DC Supply	198.00
351 D2 Mobile Mount	120.00

DRAKE

TR 4 Transceiver	585.00
AC 3 AC Supply	79.85
MS 3 Speaker	19.95
DC 3 DC Supply	129.95
Mk III	6.95

HALLICRAFTERS

SR500 Tornado	395.00
P500 AC Supp'y/speaker	109.95
P500 DC Supply	149.95

NATIONAL

NCX-5 Transceiver	685.00
NCX 3 Transceiver	369.00
NCX-A AC Supply/speaker	110.00
NCX-D DC Supply	119.50

SBE

SB 34	395.00
SB 2LA	249.50
SB 2MB	12.50
SB 2VOX	34.50
SB 2XC	24.50
SBE Mike	14.50

SWAN

Swan 350	395.00
Swan 117C AC Supply	85.00
Swan 512 DC Supply	145.00

Write for our Special
Transceiver Packet

Hi OM:

Ham business is real good. We need your top quality trade ins. Now is an excellent time to trade for new equipment and receive top value for your trade.

73—Stan Burghardt WØBJV

	PRICE *
CENTRAL Electronics Model B Slicer	\$25.00
CLEGG 99'er 6 mtr Transceiver	99.00
COLLINS 30L-1 Linear	399.00
COLLINS 32V3 Transmitter	229.00
COLLINS 75S-3 Receiver	459.00
COLLINS 312-B4	139.00
COLLINS KWM-2 Transceiver	825.00
COLLINS SM-1 Mike	20.00
GLOBE Champ 300	164.00
GLOBE Chief Deluxe Transmitter	39.00
GLOBE Scout 680A Transmitter	44.00
GONSET GC-105, 2 mtr Transceiver	139.00
HALLICRAFTERS S-40 Receiver	49.00
HALLICRAFTERS SR-150 Transceiver	349.00
HALLICRAFTERS SX-62A	199.00
HAMMARLUND HQ-170	199.00
HEATH DX-100	99.00
HEATH DX-100B Transmitter	129.00
HEATH HW-32 Transceiver	109.00
HEATH VF-1	15.00
HEATH APACHE & SB-10	219.00
HEATH Cheyenne, Comanche and UT-1	100.00
HUNTER Bandit 2000A	369.00
HY-GAIN 215 15el, 2mtr used (Wtn Pickup)	15.00
HY-GAIN TH-2 (discontinued model)	49.00
JOHNSON 250-23 Matchbox	39.00
JOHNSON Adventurer	29.00
JOHNSON Courier Linear	139.00
JOHNSON Invader 200	249.00
JOHNSON Pacemaker	149.00
JOHNSON Ranger	109.00
JOHNSON Valiant	169.00
JOHNSON Directional Coupler & Indicator	19.00
LINCOLN 6 mtr Transceiver & 12v supply	39.00
MILLEN 92101 Preamplifier 20, 10 & 6 mtr coils	15.00
MORROW MB-560 Transmitter	49.00
NATIONAL 2 mtr Converter for NC-300	25.00
NATIONAL NC-88 Receiver	65.00
NATIONAL NC-98 Receiver & Speaker	85.00
NATIONAL NCL-2000 Demo	585.00
NATIONAL HRO-50 Speaker & Calib.	189.00
NATIONAL HRO-60, A, AC, B, D, E, F	279.00
RME 4300 Receiver	85.00
RME DB-23 Pre-Selector	29.00
SHURE 444 Ham Mike	19.00
WRL SS-3 "Q" Multiplier	9.00

* These prices are subject to 10% for cash and no trade in!

WRITE FOR LATEST REVISED BULLETIN
ISSUED MONTHLY

Box 37A Watertown, So. Dak. Phone 605 886-5749

Burghardt
RADIO SUPPLY, Inc.

America's Most Reliable Amateur Dealer.

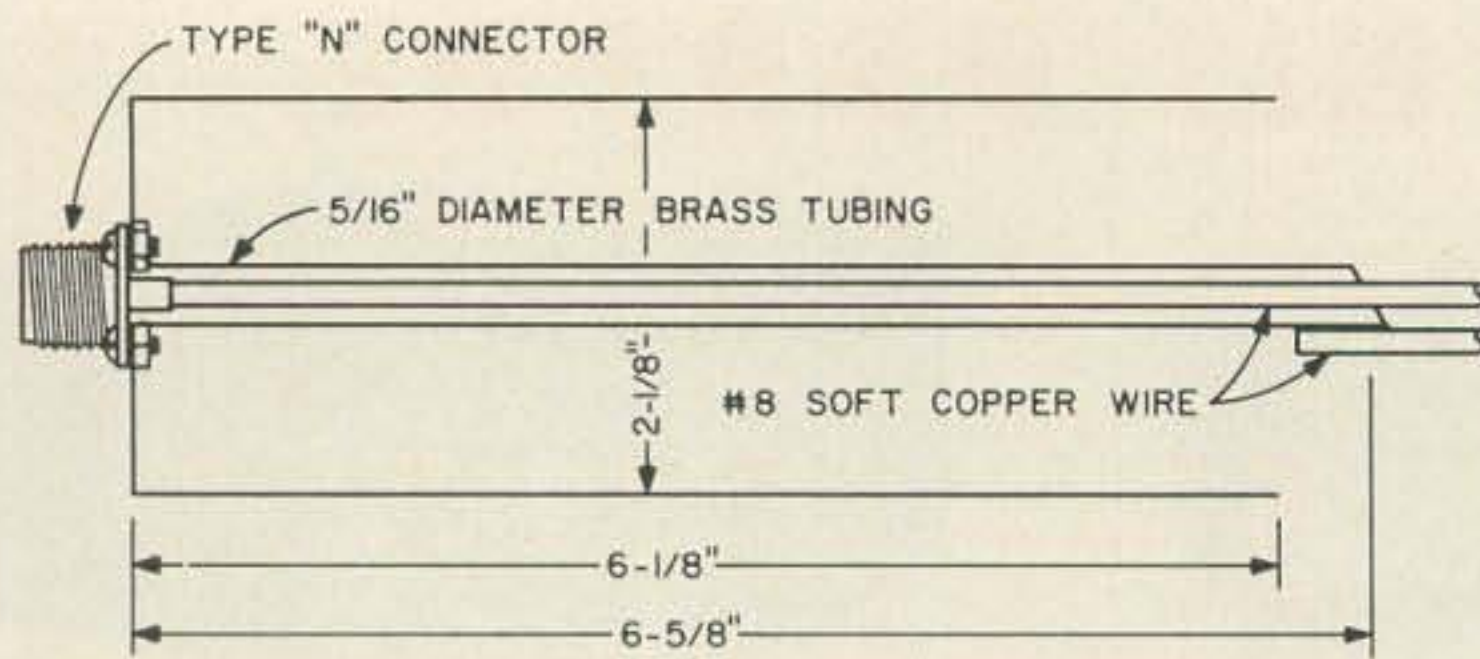


Fig. 4. Balun dimensions.

long and 14 inches high should be attached to the dipole side of the mast.

The mesh can be held in place with wire and then spot soldered to the mast with a heavy iron or propane torch.

The dipoles should then be soldered in place.

It will be noted from Fig. 3 that the $\frac{1}{4}$ wave phasings stubs are actually longer than the length required and that shorting bars are used to set the final adjustment. In all probability, this array will perform properly if the shorts are set to the measurements given, however, if the time can be spared, a simple diode test stand step up with a signal source of some sort will allow the array to be tweaked just to be sure.

If the test stand method is used, it should be found that, when the shorts are tweaked for maximum gain, the horizontal beam width of the antenna is at a minimum which should be about 16 degrees.

As with many antennas, the beam direction can be changed by altering the phasing balance among the dipoles. Be sure to set all the shorts the same distance. It is possible to achieve the proper beam width and then squirt the beam out sideways, if the shorts are not pretty close to the same length.

To illustrate the necessity of proper phasing, Fig. 5 shows the E plane pattern of the first trial collinear which was built "by the book." The screen reflector was not used in this test. The unidirectionality of the pattern was apparently due to the reflecting action of the length of tubing used to support the dipole string.

In contrast, Fig. 6 shows the pattern obtained in the E plane with the second trial collinear, which was also without screen reflector. In this case, the phasing stubs were made longer and the movable shorting stubs added and adjusted for maximum gain.

It can be seen that the second antenna has a much cleaner pattern, lower sidelobes and narrower beamwidth.

Though not shown, the H plane beamwidth of this antenna is much too broad to satisfy the feed requirements of the parabolic sheet.

Fig. 7 shows E plane plot the final array. This was built like the second trial except that the reflector screen was added and the stubs retuned as required.

The sidelobes are further reduced and the back lobe is almost completely suppressed. The H plane beamwidth is reduced to about 100 degrees which is a quite satisfactory value for the feeding sheet. In fact, the array is, in itself, a fairly decent antenna, which, if used without the parabolic reflector, will have about 10 db gain.

The collinear is mounted at the focus of the sheet by using four additional lengths of TV mast. Two 5 foot lengths and two 8 foot 4 inch lengths are used to form the collinear support which is held together and to the sheet by antenna U clamps.

Reference to the photographs will provide the details of this construction. The U clamp which ties the mast behind the sheet to the center tubing in the framework is particularly important if the collinear support is to remain rigid.

The collinear is then clamped at the focus of the sheet.

Two lengths of nylon rope were tied between the edges of the framework and the ends of the collinear to insure against the collinear twisting on its mount. If this were to happen the pattern would be upset and, if carried to an extreme, the effectiveness of the antenna would be destroyed altogether.

To this point, nothing has been said about the matching scheme used. It will be noted that the middle dipole in the array is split at the center and a shorted stub has been inserted.

The center impedance of the array is rather low and requires a balanced feed. The simplest matching arrangement seemed to be the "beer can balun," in this case, a soft drink can balun" and shorted stub match.

The balun is used to transform the 50 ohm unbalanced transmission line to a 50 ohms balanced shorted line. The 50 ohms balanced line is tapped onto the shorted stub. The tap point and the short are positioned for minimum VSWR.

The details of the balun are shown in Fig. 4. These details vary slightly from the balun shown in the photographs, however, they are essentially the same. It is also well to note that the short 50 ohm balanced line is not actually 50 ohms but somewhat higher,

RED HOT LOW, LOW PRICES ON USED EQUIPMENT

YOU CAN'T BEAT OUR PRICES

CENTRAL ELECTRONICS

20-A	\$ 99
100-V	395
200-V	495

CLEGG

99'er	\$ 89
Thor w/AC P/S	249

COLLINS

75A-4	\$399
755-1	319
755-1 w/500 cycle	349
755-3	479
32V-1	119
32S-1	429
32S-3	539
KWM-2-New demo	1035
R-388 (51J-3)	439
516F-2	85
312B-4	129
516E-1 DC P/S	85
516E-2	99

DRAKE

2-A	\$179
2-B	199
2-BQ	25
2-AC	12
TR-3	439

ELMAC

AF-67	\$ 39
-------	-------

GALAXY

III Transceiver	\$279
V Transceiver	369

GLOBE

King 400A	\$119
PSA-63	29

GONSET

G-66	\$ 49
G-77	69

G-76	149
G-76 AC	49
G-76 DC (New)	59
GSB-100	199
GSB-201	269
2 Meter linear	99
Com II 2 meters	109
Com III 6 meters	159
Com IV 2 meters	169

HALLICRAFTERS

HT-32	\$279
HT-37	269
HT-41	219
SR-150	429
SR-160	269
PS-150-AC	79
PS-150-DC	79
SX-42	89
SX-43	69
SX-71	69
S-76	69
S-85	49
SX-140	49

HEATH

DX-35	\$ 24
DX-40	29
HA-10	189
HX-10	269
HW-12	119
HW-22	119
HW-32	119
DX-60	49
VHF-1	139
HX-30	149
SB-300	269
HP-10	19
HP-13	49
HP-20	19
HP-23	29

HAMMARLUND

SP-600	\$199
HQ-100	89
HQ-100A	139
HQ-140	99
HQ-145	119
HQ-150	109
HQ-160	119
HQ-170	179
HQ-105TR	119

JOHNSON

Challenger	\$ 49
Pacemaker	149
Ranger	99
Valiant	149
Valiant SSB Aadpter	179
Viking I	39
Invader 200	269
KW Matchbox	65

NATIONAL

NC-109	\$ 69
NC-190	149
NC-240D	69
NC-300	139
NCX-3	269
NCX-5	499
NCL-2000	499

SBE

SB-33	\$249
SB1-LA	189
SBE DC P/S	39

SWAN

SW-140	\$129
SW-120	129
SW-240	239
SW-350	339
SW-400	319
AC P/S	69
DC P/S	89

All Equipment Completely Reconditioned

ACT NOW!

USE OUR
TIME PAYMENT
PLAN

**Edwards
Electronics**

TELEPHONE PO rter 2-8759
1320 19TH ST. / LUBBOCK, TEXAS 79401

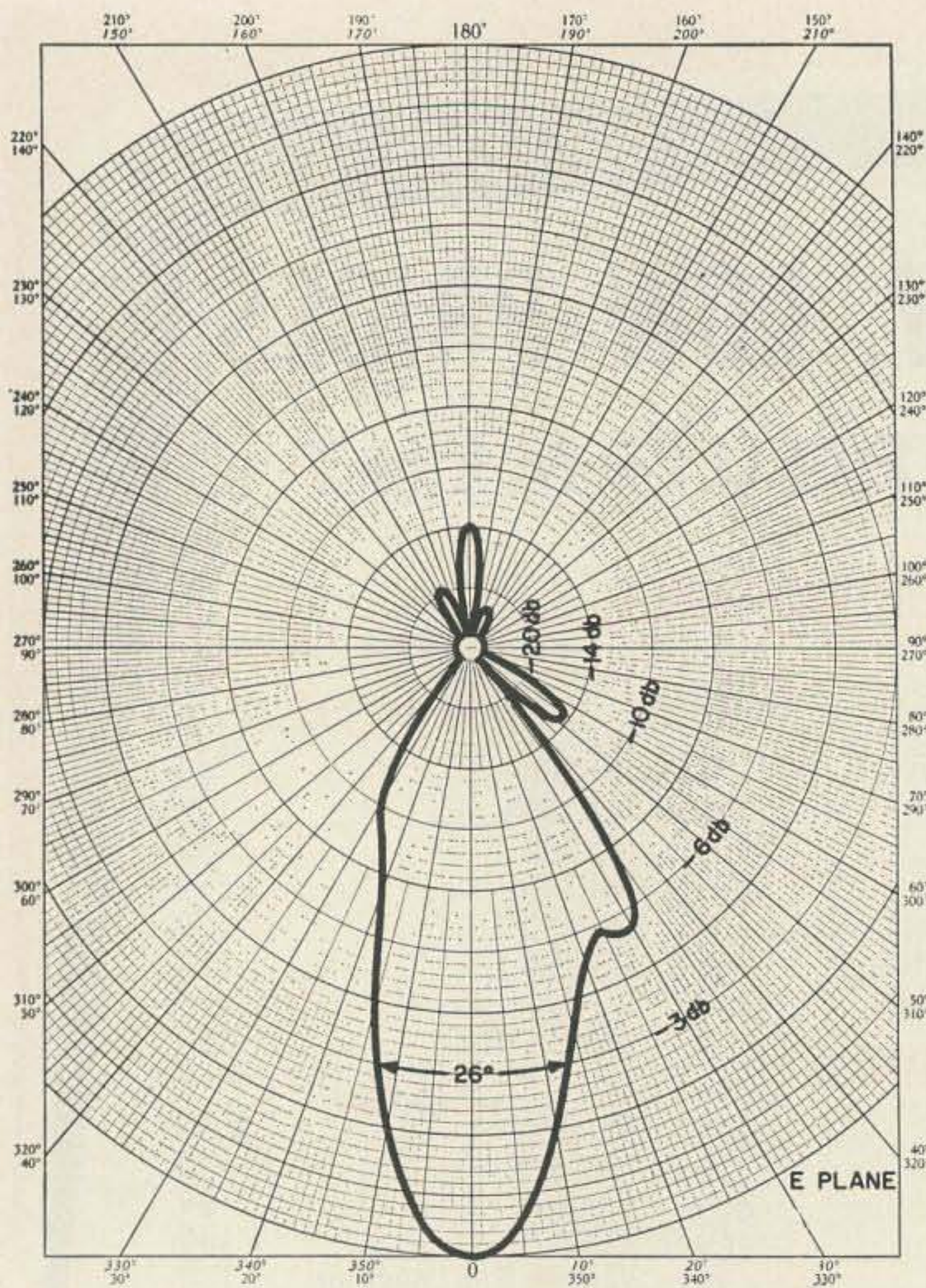


Fig. 5. First trial array.

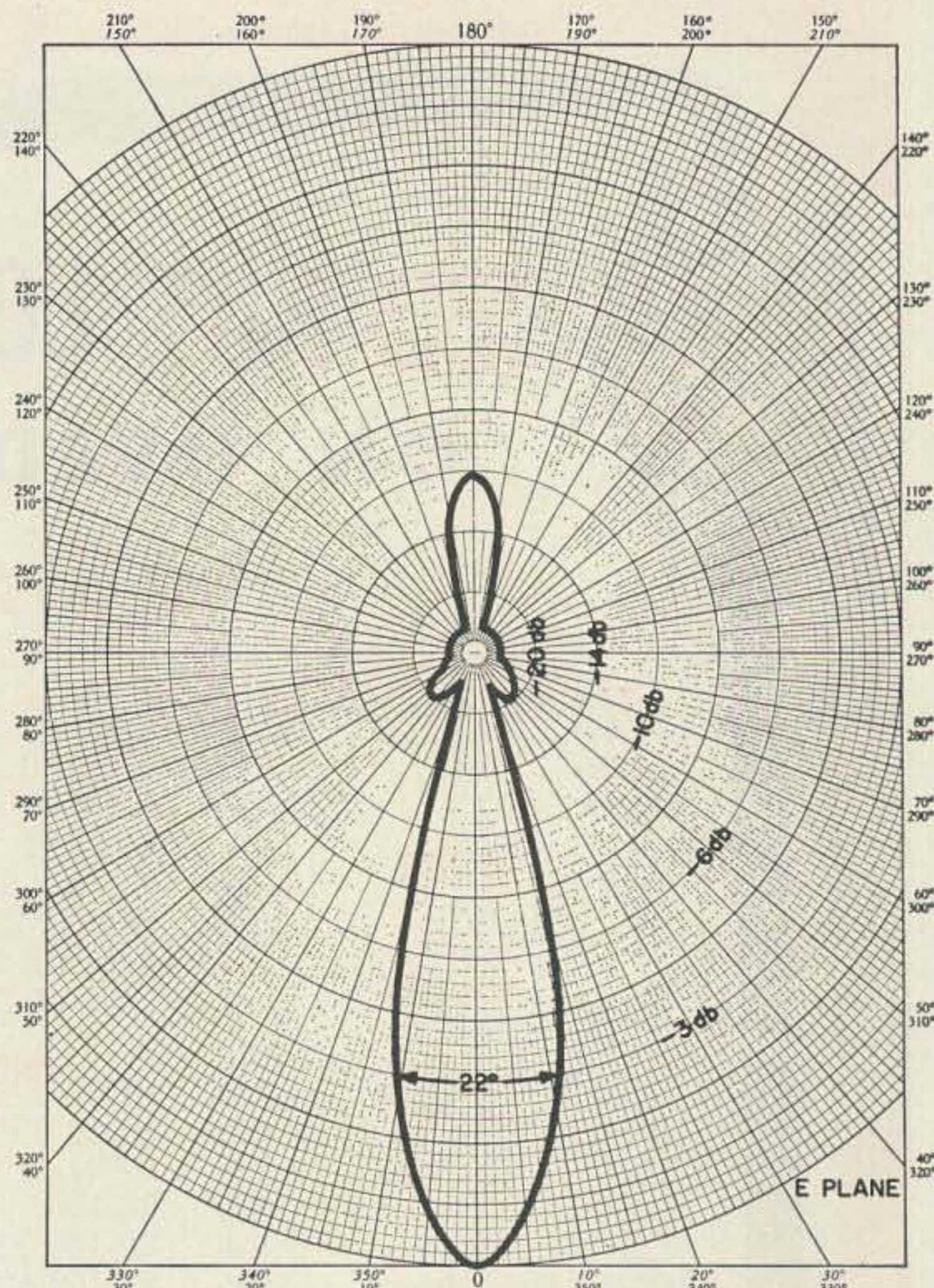


Fig. 6. Properly phased array without screen reflector.

but the discontinuity is short and can be tuned out in the normal stub matching procedure.

Once the stub is tuned for minimum VSWR, it is well to check the match with several different lengths of transmission line to be sure that the line itself is not acting as a part of the matching network—it can happen. If the VSWR remains low with varying lengths of line, then the match can be assumed to be proper.

When the line is matched the balun can be bolted to the dipole mast.

Quick checks showed that with the antenna tuned for 436 Mc, the VSWR was below 1.5/1 across the entire band and below 1.2/1 from 425 Mc to 445 Mc.

Though less thoroughly checked, indications are that the gain was acceptable over the band. Very little difference was noted between the gain at 436 Mc and 432 Mc.

Transmission line losses at 432 Mc can present a formidable problem, however, if the shortest possible length of RG-8 foam line is used losses can be kept to a minimum. Needless to say, if RG-17 is available, a substantial decrease in losses can be wrought, if the line is lengthy. It is sometimes possible to obtain lengths of used RG-17 quite reasonably from commercial two-way radio communication companies.

The weight of the antenna poses a problem in mounting the antenna atop your tower or mast. The fully assembled antenna weighs about 60 pounds.

Conventional TV mast, even the heavy duty variety, will result in disaster. Instead, a length of one inch heavy wall rigid pipe was used. This has a one inch inner diameter and a 1/8 inch wall.

The photographs show the temporary main support mast across the face of the sheet which was used in the test stand checks.

The antenna should be mounted very close to the rotator to allow a minimum amount of sway. The wind resistance of the antenna is fairly high and every practical precaution should be made to insure it doesn't end up a pile of junk in your backyard, or, worse yet, a neighbor's yard.

A rotator with an external thrust bearing should be used. If possible, the bearing should be mounted three feet or more below the rotor to minimize sway strain on the rotor and the top of the tower.

It was found that, if the thrust bearing was true with the rotator, my seven year old Alliance Tenna Rotor would turn the sheet and the 6 element six meter beam mounted directly beneath it, without seeming unreliable.

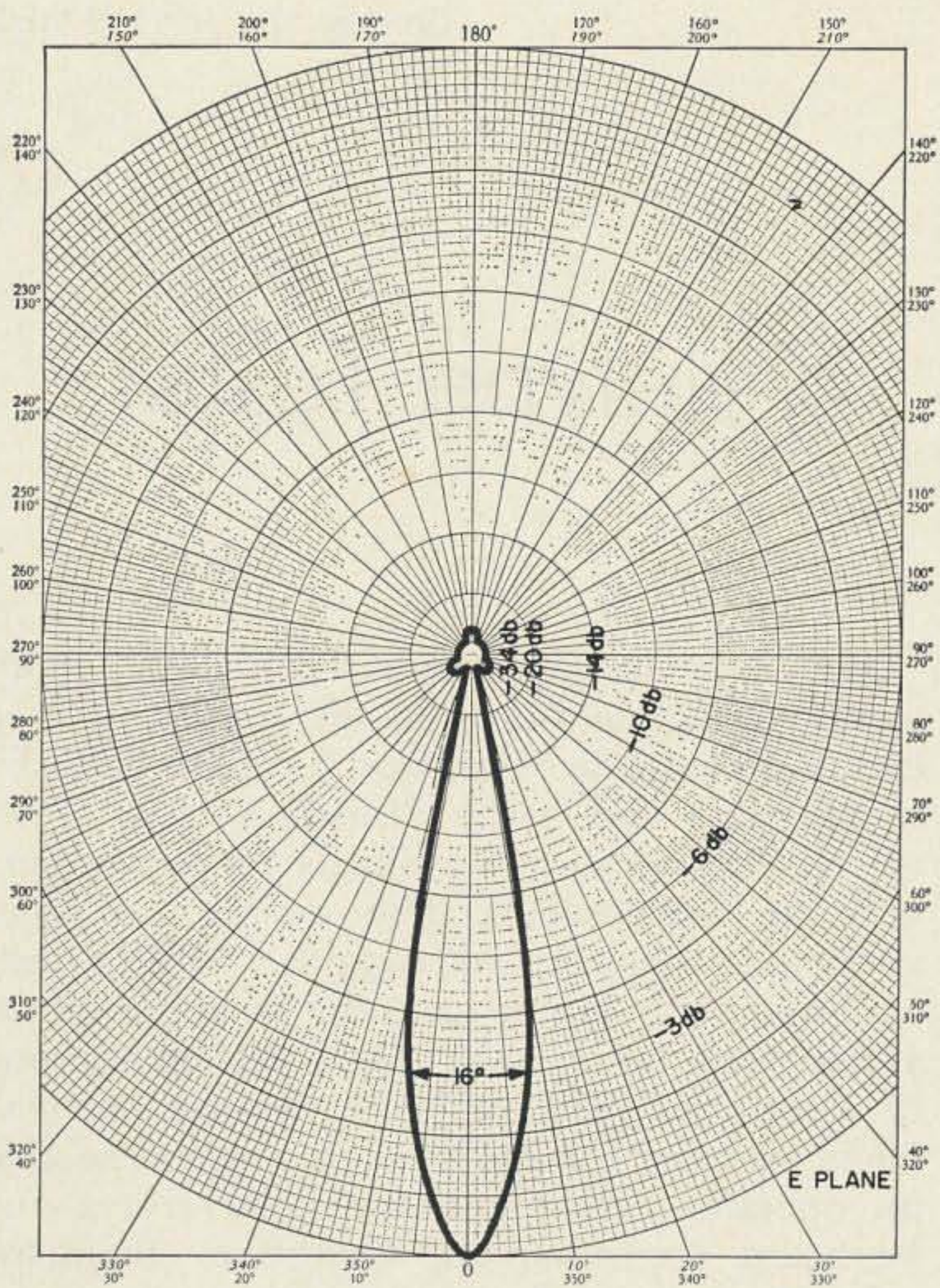


Fig. 7. Array with $\lambda/2$ screen reflector.

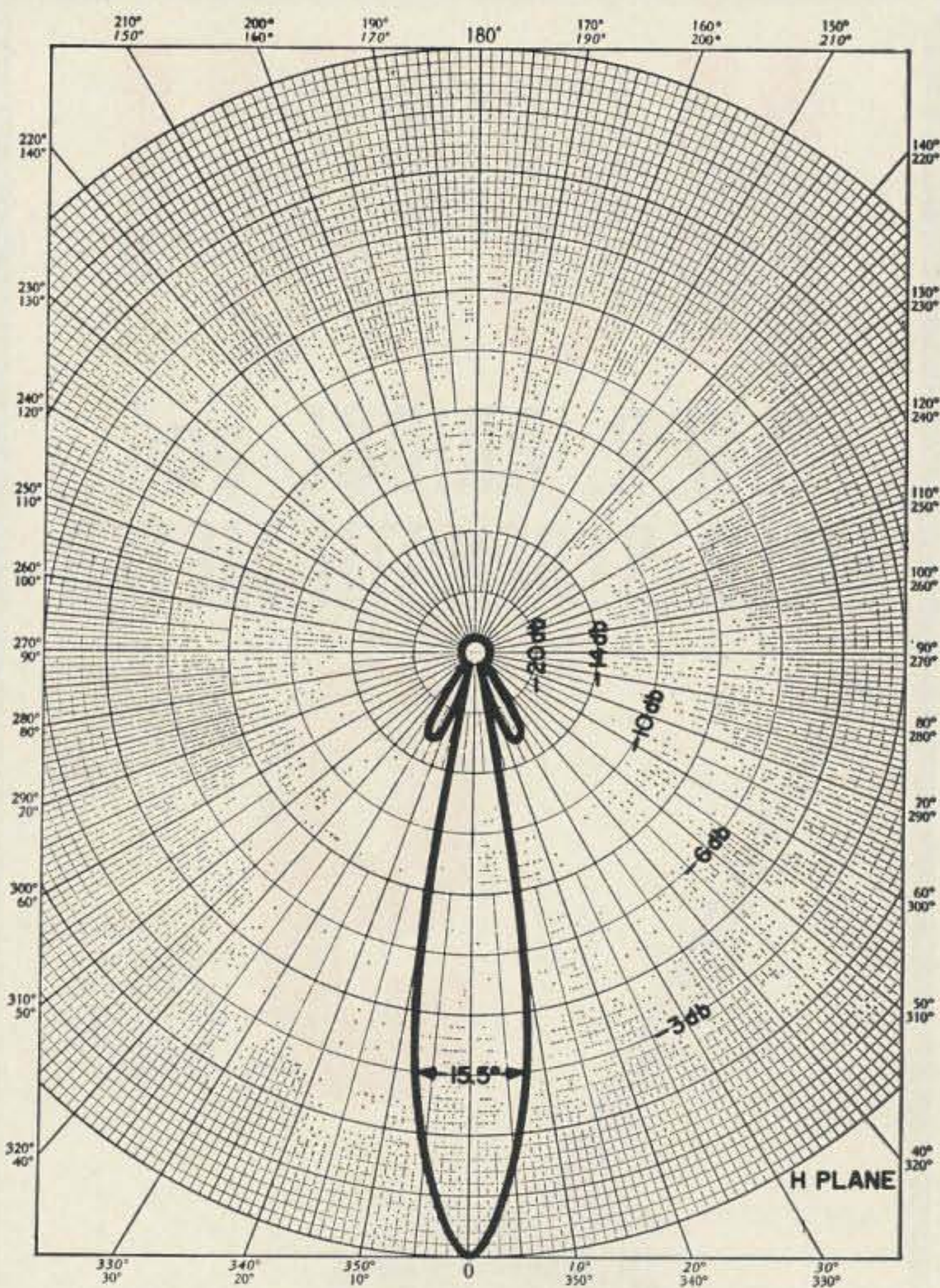


Fig. 8. H plane plot of the parabolic reflector.

Fig. 8 shows the plot of the H plane pattern of the sheet reflector. The E plane plot was observed to be almost identical to the E plane plot of the driven array (Fig. 6) except that the F/B was better and sidelobes were slightly stronger.

Using conventional gain, beamwidth formula the forward gain, based on the measured beamwidths, is 19.3 db. This is almost exactly the predicted value and is a happy place to stop.

To be scientifically correct, a statement of measurement tolerances would be appropriate at this point. The instruments used in these measurements were not laboratory calibrated, but rather were homebrewed and not at all fool proof. However, I believe that the measurements were accurate within a degree or so. If both beamwidths were off by as much as 3 degrees (20%) the gain would still be over 18 db. Though, regardless of "paper gain," on the air results are the most important criterion for a judgment of performance.

The front to back ratio seems to be in excess of 40 db on the test stand. When the antenna was actually put into service, the front to back ratio seemed to be less than this value, in some cases, by a considerable amount. Later tests seemed to indicate that the f/b was actually quite high but the strong

forward lobe was picking up signals reflected by ground objects in the general vicinity of the antenna. By observing television sync pulse phase comparisons, indications are that objects at least as far away as 5 miles from the receiving antenna could and did cause fairly strong reflections.

The antenna has withstood the rf of the KW transmitter for long periods of time with no apparent ill effects. There were no thermal hot spots on the antenna. The high current points on the dipoles were warmed perceptibly above the ambient but the effect was just noticeable. The small wire used in the shorts in the phasing stubs seemed to be no problem at all.

At this writing the antenna has produced among others an R5 CW QSO over a 180 mile path obstructed by a 7000 ft mountain chain and an R5 S2 CW reception report over 270 mile path obstructed by two mountain chains, one about 8,000 feet high. In both cases, these results were obtained in spite of cross polarization.

Why call the article the Big Sail? Well, that's a local joke, but, it does look more like something that belongs on a boat than on a radio tower, or so some of the neighbors say.

... K6MIO

NOW!

S.W.R. BRIDGE and FIELD STRENGTH METER



9⁹⁵

Allow 50¢ for
packing and
shipping.
California residents include
4% sales tax.

**THE BEST
VALUE WE
HAVE
EVER
OFFERED!**

An excellent combination unit for either home station or mobile use . . . as an accurate Standing Wave Bridge and a sensitive Field Strength Meter. 52 ohm impedance. Will take a full kilowatt and can remain in the line all of the time.

Grey metal case, 5¼" H x 1¼" W x 2¼" D, with standard fittings, 1⅝" Bright-vue meter, and detachable, telescoping antenna which extends to 10¾". With instructions and schematic.

QUEMENT ELECTRONICS

1000 SOUTH BASCOM SAN JOSE, CALIFORNIA


"Northern California's Most Complete Ham Store"

SINCE 1933

Teletype Tester

Here is a useful piece of RTTY test equipment which can be built very easily. It is a transistorized tone oscillator for testing RTTY signal mark and space distortion of both received and transmitted signals in conjunction with an oscilloscope. The majority of conventional scopes are not capable of RTTY tests as they either do not have the dc input or the sweep time is too slow for receiving a string of dc pulses. This piece of equipment will allow viewing the dc loop on a scope so that an operator can adjust the polar relays and keyboard for minimum distortion. Bouncing relay contacts can be easily seen on the scope.

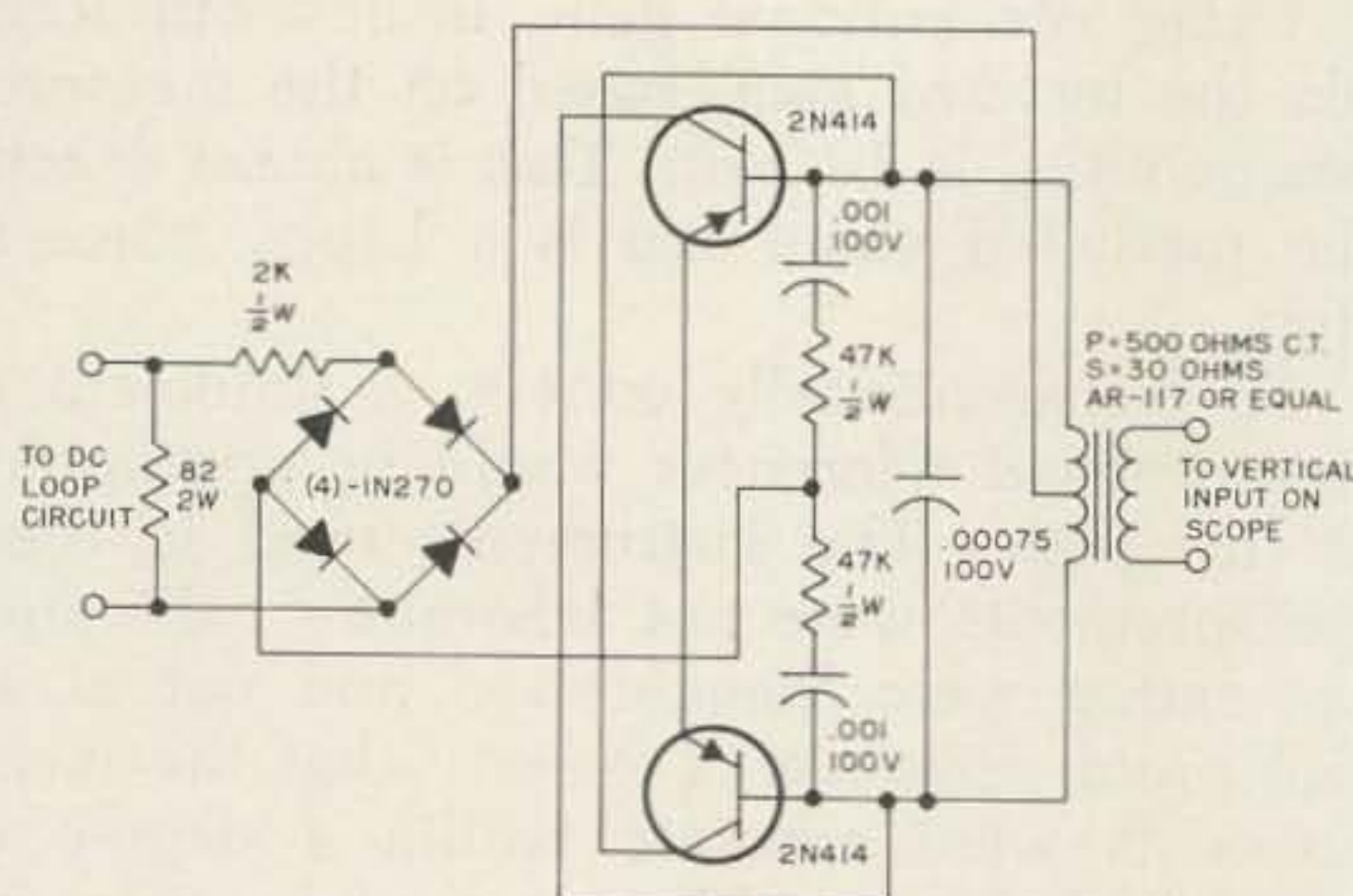The tone oscillator obtains its operating power from a small voltage developed across an 82 ohm resistor connected in series with the dc loop. This voltage is fed to a bridge circuit of four type 1N270 diodes so you can ignore polarity when inserting the unit into the loop circuit.



A pair of 2N414 transistors oscillate around 20 kc and their output is coupled to the input of the scope through a small output transformer.

Pulses containing no distortion will appear on the scope as evenly spaced rectangles. Pulses containing mark distortion will appear as evenly spaced square boxes. Pulses containing relay contact bounce will appear as pairs of rectangles on the oscilloscope.

. . . W1MEG

INVENTORY CLEARANCE SALE!

Service Tested Equipment

ORDERS PREPAID WITH
CASH REMITTANCE
IN CONTINENTAL U. S.



TRANSCEIVERS

Galaxy III	\$199.00
Gonset G-76 w/DC Supply	199.00
Hallicrafters SR-150	399.00
Heath HW-32	110.00
National NCX-3	225.00
SBE SB-33 demo	225.00
Swan SW-120	149.00
Swan SW-140	149.00
Swan SW-175	149.00
Swan SW-240	199.00
Swan 400	349.00

RECEIVERS

Collins 51J4	\$695.00
Collins 75A2	179.00
Collins 75A3	225.00
Collins 75S3	499.00
Drake 2A	169.00
Drake 2B	199.00
Elmac PMR-6A	29.00
Elmac PMR-8	59.00
Gonset G66	49.00
Gonset G66B	59.00
Hallicrafters SX-100	149.00
Hallicrafters SX-101 III	169.00
Hallicrafters SX-111 (like new)	159.00
Hammarlund HQ105TR	125.00
Hammarlund HQ145	175.00
Hammarlund HQ170C	195.00
Hammarlund HQ170AC	249.00
Hammarlund HQ180AC (like new)	350.00
Hammarlund SP600JX	325.00
Heath Mohawk w/spkr.	125.00
National HRO-60 5 coils	199.00
National NC98	69.00
National NC-300 w/calib.	169.00
National NC-303 w/calib.	225.00
RME 4350A	99.00

VHF EQUIPMENT

Clegg Zeus	\$349.00
Clegg Interceptor	299.00
Clegg Interceptor B	349.00
Gonset Comm II 6 mtr	79.00
Gonset Comm III 6 mtr	129.00
Gonset Comm IV 2 mtr	249.00
Gonset Comm IV 6 mtr	199.00
Gonset Sidewinder 2 mtr	329.00
Gonset 901A AC Sup	39.00
Gonset 902A DC Sup	49.00
Gonset Model 3112 220 Mc	199.00
Lincoln 6 mtr Xcvr	49.00
Poly Com PC62 Xcvr	199.00
Poly Com PC2 2 mtr Xcvr	249.00
Poly Com PC6 6 mtr Xcvr	229.00
Checker Rangemaster 2 mtr FM transceiver	99.00
Neil Beta 6 mtr Xmtr	59.00

TRANSMITTERS

B & W LPA-1	\$225.00
B & W 5100	125.00
Collins 30L-1 (like new)	375.00
Collins 302C-3 wattmeter	99.00
Elmac A-54H	19.00
Elmac AF67	39.00
Globe Champion	99.00
Globe Scout 680	29.00
Globe Scout Deluxe	49.00
Globe Sidebander	39.00
Hallicrafters HT-31 linear	99.00
Hallicrafters HT-32A (like new)	299.00
Hallicrafters HT-33 linear	249.00
Heath Apache	129.00
Heath DX-20	19.00
Heath DX-35	25.00
Heath DX-100	89.00
Heath HA-10 Warrior linear	199.00
Heath Marauder	299.00

NEW EQUIPMENT SPECIALS

Demonstrators & Display Samples

	Reg.	Special
Clegg 99'er 6M Transceiver	\$179.95	\$139.00
Drake TR-3 Transceiver	550.00	449.00
Galaxy III Transceiver	299.95	199.00
Gonset Super 12 (Conv)	94.50	29.00
Gonset GPP-1 Phone Patch	49.95	29.00
Hallicrafters HT40K Trans. (Kit)	99.95	69.00
Hallicrafters HT-44 Transmitter	395.00	249.00
Hallicrafters HT-45 Linear	365.00	289.00
Hallicrafters S-108 Receiver	149.95	99.00
Hallicrafters S-119 Receiver	59.95	39.00
Hallicrafters SR-150 Transceiver	650.00	399.00
National NC-105 Receiver	139.95	79.00
National NC-121 Receiver	139.95	99.00
National NC-155 Receiver	199.95	149.00
National NC-303 Receiver	449.00	299.00
National NCL2000 Linear	685.00	449.00
National NCX-3 Transceiver	369.00	249.00
National NCX-5 Transceiver	685.00	449.00
Swan TCU (VFO for SW-240)	115.00	49.00

MISSION HAM SUPPLIES

3316 Main Street
Riverside, California 92501

Phone 683-0523 (area code 714)

(Calif. orders add 4% tax)

Gus: Part IV

In planning my first DXpedition one of the first problems I faced was getting equipment to use. I had been told by lots of fellows that getting equipment for a DXpedition was very easy. Well, maybe it's easy for some fellows but in my case it was not. I wrote a nice letter to every manufacturer I knew of telling them my plans. Only one bothered to answer my letter! That was the equipment I took with me and it must have been good gear because I had no trouble with it at all.

I began to write letters about then to the fellows who said they had spare bedrooms for visiting hams. I mean to tell you I really wrote letters, getting telephone numbers, street addresses, and directions as to how to find their homes. I also wrote many letters to the licensing people in many countries too. Let me add right here I have found that this (in my case) is *not* the best thing to do—it gives them too much time to read the fine print in their regulations. To this day I think the “out of a clear sky” approach is the best—don't even give them any warning that you are on the way. In fact, it's best to not tell anyone where you are going, because then someone will try to beat you there, or foul you up!

I was in a lucky position that I had a good partner with me at our broadcasting station. Things were going smoothly (as smoothly as they usually go at a BC station) and it was OK for me to stay away from my station any reasonable length of time. It would operate all OK whether I was there or not. My wife had her own radio and TV shop with a good technician working for her. All the children were out of school and one or two of them were about to get married. My wife had given me the Official Nod. (I told you I had one

out of a thousand wives—didn't I?)

The news of my DXpedition was really getting around by this time. The “LW” gang helped lots (14050 KC—Sundays at 1300 GMT) Oh yes, let me tell you how W5UX and I organized this “LW” net. I had always heard about these big city 2 meter and 6 meter DX nets—I think most of them have one by now. I once made a trip to Philly to visit my in laws and found out about that big club meeting there.

I sneaked into their meeting and sat down in the back row where it was dark. I heard the trial of one of their members. Up on the platform were the club's secretary, president, vice president, and a few of the club's officials. After reading the minutes of the last meeting, calling the roll, and discussing other run-of-the-mill business, they called one certain ham up to the platform to be tried. They first asked him if he were at home the past Tuesday night. He answered yes. Then they asked him if he worked a VR3 that night at about 3 am. He said yes, he had. Then they asked him if his 2 meter DX net station was in working order—he said no. Then they asked him if he had a telephone. He answered yes. They asked if he had his list of the club members who needed VR3 and he said yes. Then they asked him why he did not telephone the boys who needed VR3, and he said his telephone was in his bedroom and he did not want to wake their baby. They asked him if he had ever read the by-laws of the club about having the telephone placed where it could be used anytime day or night without disturbing anyone. I think his answer to that was that he was planning on having it moved to a better location in the house soon. Well, I think it was a \$50.00 fine given to him. Right then I said

SUBSCRIBE TO 73

Don't take a chance on missing the more than 250 excellent articles, the infuriating editorials and the fascinating ads in the next twelve months of 73. Our circulation and advertising are increasing at a fantastic rate, so 73 is getting better and better each month. Subscribe now!

Name _____ Call _____ 1 year \$4 _____ 2 years \$7 _____
 Address _____ 3 years \$10 _____ New subscription _____
 City _____ Renewal _____ Extension of sub _____
 State _____ Zip Code _____ loAR for one year \$5 _____
 Please include your zip code and save us money. loAR for one year and 73 for one year \$7 _____

Send your money to:

73 Magazine, Peterborough, N. H. 03458


to myself, boy, us fellows in small cities just don't have a chance to work lots of good DX with clubs like this being organized like they are.

When I got back down to South Carolina I gave lots of thought to how to overcome our disadvantages of not having a big club and all their members to act as our ears for alerting us fellows in small towns across the USA. I had a QSO with Bob and told him that we fellows in towns with no DX 2 meter nets should get organized. I suggested that we start a "Lone Wolf" (LW) DX club and for us to meet every Sunday. So the LW got going—this was a number of years ago—and it still is going strong.

For a DXpedition to understand the problems the USA gang faces in working DX, I think it's the best training in the world to chase DX from the USA for a number of years. Then you see how things go with them and hear the problems that they face when working DX. Anyone not living in the USA just can't picture the sounds of kilowatts QRMing each other, or understand how eager most of the gang is to work DX. They can never understand the strength of those KW's when we have short skip; they can't picture the competition between the fellows. They just don't know how badly a DX station can get

MOBILIERS! ~~~~~ FREE OFFER!

WHY GUESSAVERT IF U CAN TUNAVERT?

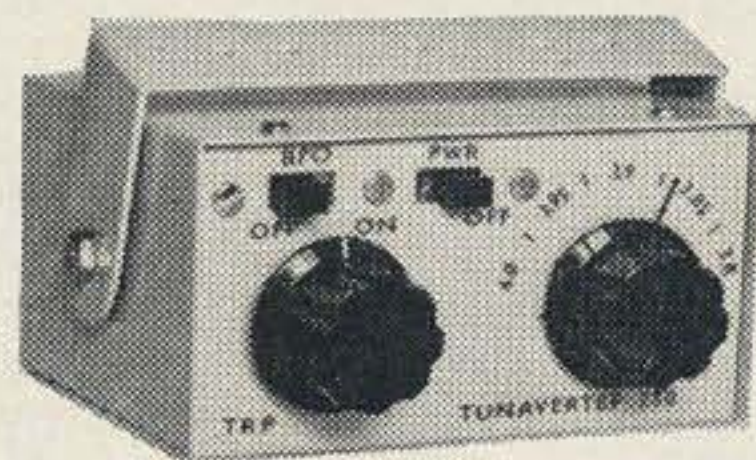

TUNAVERT AM SSB & CW

All transistor single band converter for car and home radios. A model for MARINE, 160,80,75, 40,20,15 M & International B.C.I Vernier 6-1 planetary tuning Int. 9 V batt power. Perfect for Broadcast radios and Q5'er.

TUNAVERT with BFO, excellent stability ... \$24.95
 Conn, coax \$.85 without BFO \$19.95

LIMITED OFFER! with this ad.
 1 gov't surplus coax 12 v. coax relay FREE
 with ea. TUNAVERTER!


ORDER TODAY FROM:

MARKETING DIVISION **HERBERT SALCH & CO.** DEALERS INVITED

Woodsboro, Texas

2 METER NON-DIRECTIONAL ANTENNA

2M Con-ex

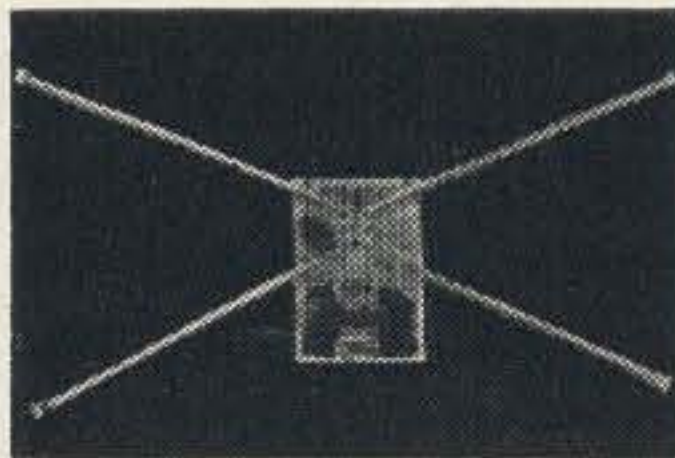

A rugged antenna for 2 meters that will give more gain and better coverage than a dipole. The Con-ex will withstand gales in excess of 100 mph. Perfect for local nets. An antenna every VHF ham can afford and should have for local contacts. Mounts for either vertical or horizontal polarizations. Can be used with 52 ohm coax or parallel feed line.


\$8.95ppd in continental USA

ELL-CONN PRODUCTS

Box 83, Ellington, Conn. 06029

INTRODUCING

OUR NEW

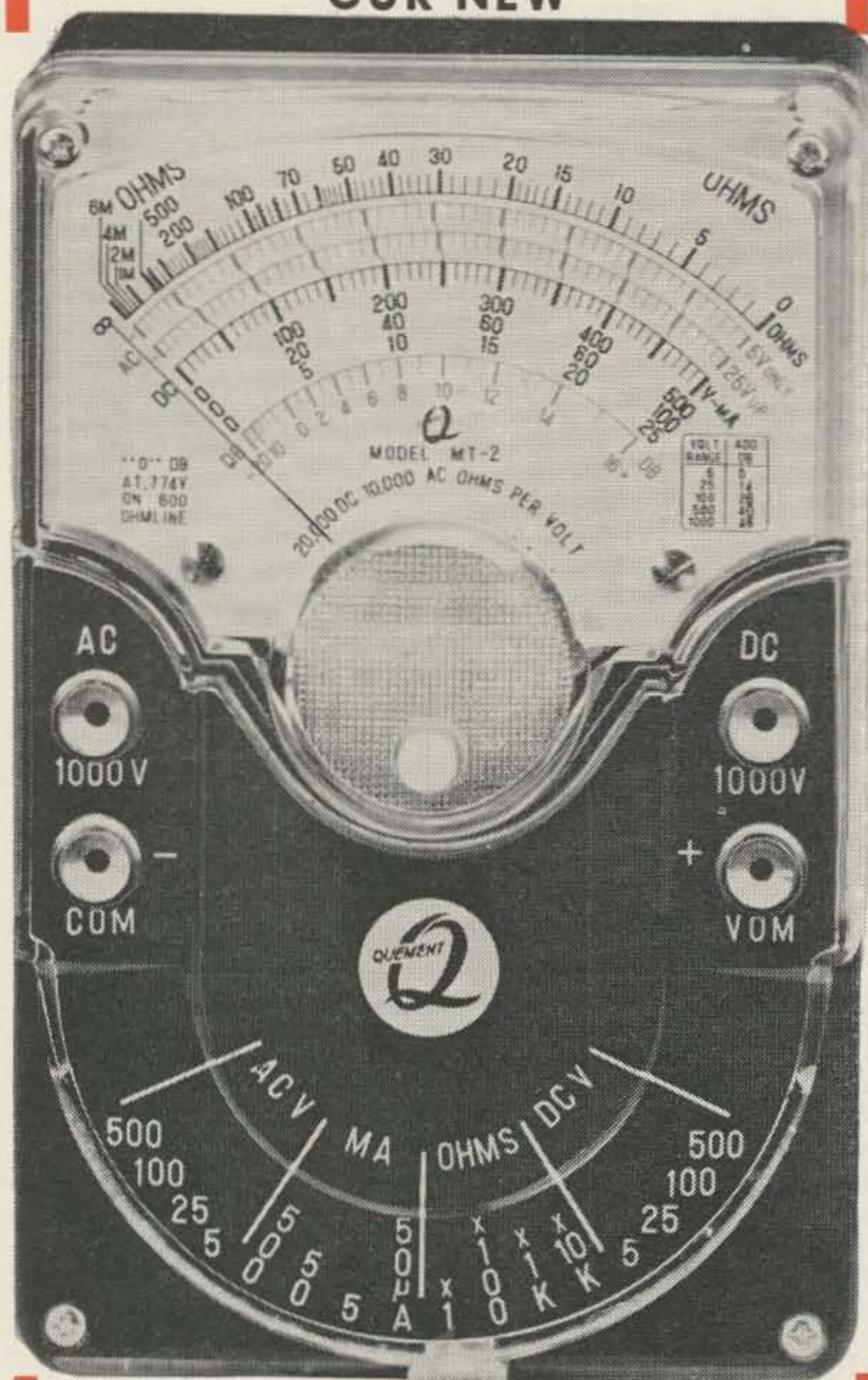

ACTUAL SIZE MODEL MT-2

MULTI-METER

- \$12.95 -

POST-PAID USA & CANADA

**QUEMENT
ELECTRONICS**

1000 SOUTH BASCOM SAN JOSE, CALIFORNIA

"Northern California's Most Complete Ham Store"

SINCE 1933

covered up with QRM especially if the DX station is in the USA portion of our phone bands. All of this knowledge has helped me to see how a DXpedition should be run, especially when the W/K's are coming through. It's even good to know of the 2 meter net boys alerting each other when something good is coming through. The odd part is that many of the DX stations don't realize that they have the situation in their control—if they will control things right! Danny Weil (VP2VD) taught me lots about handling the pile-ups and I think old Dick (KV4AA) taught Danny! I have heard so many DX fellows trying to handle things the wrong way that I made up my mind that I most certainly did not want to make their mistakes.

I will admit some of them don't show "good bringing up" and they do get downright dirty at times, but I figure it's all in the game. You know the old saying, "all's fair in love and war and chasing DX." With me it's no holds barred, do what you want, you can't make me mad and I won't Black List you either. Course I just might not "hear you"! hi hi. And if I work you, your call might not get into the log, and then no QSL and that's bad! You will be surprised how fine 99.99999% of the fellows are though.

When the news really gets around that you are going on a DXpedition, you begin to get lots of mail. Everyone tells you where to go, how to operate, what frequency to use, to listen for them. Some fellows offer you things to take along with you, some fellows suggest what medicines to take with you.

You can make all the plans you want when you are sitting down in your office or at home, but when you get to the rare spots, all of your plans seem to change. Things just don't work out like you thought they would. A lot of the time you just have to go along with the wind. Lots of fellows asked me if I had ever traveled much and I told them I once drove to Mexico and had also driven to Niagra Falls on my honeymoon. Then they asked me if I had ever been out at sea in a boat. My answer to that was a flat no—but I was sure I would not get sea sick. They usually answered "Brother, you have a lot to learn," or something like that. I was pretty sure that I could control things OK at sea because I had too much at stake to do otherwise—and to this day I still believe what I said! I even believe that I can control myself with mild sickness too. You have just gotta say to yourself—"Look here, you cannot afford to get sick." And if you really mean what you say, you just won't get sick—or at least you can pull yourself out

Look... **BUILT-IN 12V DC AND 117V AC POWER SUPPLY
IN A TRANSCEIVER SELLING FOR ONLY \$395.00**



THE **SB-34**

THE FACT THAT THE SB-34 DOESN'T NEED AN INVERTER IS ONLY ONE OF DOZENS OF REASONS WHY YOU SHOULD CHECK THIS ONE OUT BEFORE BUYING ANY TRANSCEIVER.

AND THE BEST PLACE TO CHECK ONE OUT . . . HENRY RADIO, OF COURSE. NO ONE ELSE HAS THE KNOWLEDGE, INVENTORY AND DESIRE TO PLEASE THAT WE HAVE. FOR COMPLETE INFORMATION ON THIS OR ANY OTHER SHORT WAVE EQUIPMENT PLEASE PHONE, WRITE OR COME IN TO YOUR NEAREST HENRY RADIO STORE.

TED HENRY
W6UOU

BOB HENRY
W0ARA

WALT HENRY
W6NRV

**6% FINANCE CHARGE • 10% DOWN OR TRADE-IN DOWN
• NO FINANCE CHARGE IF PAID IN 90 DAYS GOOD
RECONDITIONED APPARATUS.** Nearly all makes and models.
Big savings! 15 day trial — 90 day warranty. 90 day full
trade back on new apparatus. Write for bulletin.

Henry Radio Stores

CALL DIRECT . . . USE AREA CODE

Butler 1, Missouri	813 679-3127
11240 W. Olympic, Los Angeles, Calif.	213 477-6701
931 N. Euclid, Anaheim, Calif.	714 772-9200
431 E. Green St., Pasadena, Calif.	213 684-0861
6116 N. 27th Ave., Phoenix, Ariz.	602 AM 4-3895

"Worlds Largest Distributors of Short Wave Receivers"

of it before it gets you down.

Things were coming along nicely on my DXpedition plans. Buck W4TO over in Atlanta, told me he would be glad to handle the QSL cards and would assist with funds. In fact, we both put money in the bank. Buck matched what I had and said he would see if he could get some contributors lined up in case their help was needed. Buck did a very splendid job in keeping me going too. It's very rough to get over-seas and have to worry about your funds running out on you. Before you do anything in the line of a DXpedition, get rid of your money troubles and worries. Stay home if that problem is not solved, unless you are filthy rich!

After a number of meetings with Buck I was ready to depart—I wanted to get going! But there were a number of things I had to do yet. For instance, I had to get my passport, and visas for the countries I wanted to visit. Don't ever mention the word radio or radio amateur to those Consulates in Washington, because they will tell you they will have to write to their home government to get your visa approved. Just tell them you will be a tourist. Tell them you want to buy—*BUY*—lots of pretty things in their country (they like that word *BUY*) and you will be surprised how fast you get your visa. Act like you have no money worries at all (that was hard for me to do).

At last I was all fixed with visas, all my clothes were packed (much too many too), my little address book was in my pocket, my little money was changed to Travelers Checks and my health card was OK. I had the little electronic keyer W3KVQ had built for me and that fine paddle Sandy W5AZB had made. The equipment was to be shipped to me in Amsterdam. Even a getting-together date was arranged, to meet Lee WØAIW, Mike WØMAF, and Mac WØUQV in Nairobi. We four were going to VQ9 land together. I could see a lot of interesting developments in the wind.

The BIG ADVENTURE was about to commence. I was going to be on the other end of the DX pile ups, and I was going to see some of the world and meet some of the DX fellows I had been talking to all these years.

When the plane left New York at 4:30 pm I decided I would let my wrist watch just stay on E.S.T. I found that Cokes were free on the plane, so I more than drank my share. I saw other people on the plane sleeping, but there was none for me. I guess I was excited too much and had too much on my mind to think about sleep. I just kept drinking Cokes and watching my watch and at 1:30 (by my

watch) the sun came up., I said to myself, boy, that sure was a short night. The plane came in and landed—I was in PAØ land! Immediately I took another plane for Hamburg, Germany and then I was in DL land. Things were going just fine with me, no trouble with Customs at all (Boy I had a lot to learn)!

I was met at the Hamburg Airport by DL6ZZ—good old Brother Gus, whom I had QSO'ed many, many times and his nice XYL-Helene. Just like I had told him I would do, I ran up and planted a big kiss on Helene. I think they were both surprised when this happened, because people over there just don't run around kissing people at airports. Over the air Gus had used almost perfect English, but when we met in person I found that I really had to talk very, very slowly for him to even almost understand me. Gus and Helene went all out to treat me very, very good. They wanted my stay in Hamburg to be a memorable occasion. It seemed like we were always eating and drinking at their house. The best darn sauerkrout I had ever had, and boy, those German weiners were out of this world. (Here in Bhutan where I am now, I do good to even get yak meat. Oh yes, we do have yak butter tea a few times each day—I guess just to keep the taste in your mouth—and let me tell you, that taste sure sticks with you a long time after you have had a cup of that stuff—hi hi).

Gus evidently had taken a few days off from his work just to show me around. We went everywhere in Hamburg, which is a very nice city. I met many of Gus's and Helene's friends and many of his relatives. All of them were real down to earth kind of people and very friendly. Of course, at each house we had to be served coffee and cakes, and even at times a Coke would appear. Gus had two sons, one away in the army and one at home. The one at home had a very pretty girl friend who I got to sit on my lap and we took a picture of that. This picture was discussed at length with my ZYL when I got back home—I mean it was discussed and discussed, and a little hard to explain I must say. (Boys, be very careful of those pictures you take!)

After staying with Gus and his family about 5 or 6 days my allotted time finally ran out, and it was time for me to depart. The time was much too short and I would have liked to have stayed much longer, because I was having such a nice time. They asked me where I was going when I left, and I said East Berlin—that did it! Helene cried and Gus tried his best to discourage me going there. He told me all kinds of things that might happen to me and said it might even be a one way trip! But I told


them I had promised some of the boys in East Berlin that I was going to visit them and that was what I was going to do regardless of the consequences. I told them I was not afraid of anything that anyone would do to me. I had not done anything to anyone and I was no spy. Against their better wishes they finally more or less gave in. Then they asked me how was I going to get to East Berlin and I said by train, since it was the cheapest way and the cheapest way was all I could afford. This brought tears in the eyes of Helene again. They told me that I should not go by train because the train has to run nearly all the way from Hamburg to Berlin through East Germany with police all over the place and everybody suspecting almost everyone of being a spy.

All this time, I was telephoning Amsterdam Airport daily asking them if my equipment had arrived there from New York. Up to the day I departed for Berlin it had not arrived, which probably was best or I might have had it with me when I arrived in Berlin, and then the fun would have started sure enough.

Gus, Helene, and their son came down to the train to see me off. They were not happy seeing me leaving for East Germany.

After the train left the Hamburg station it was not long before it stopped and the West German conductors and train crew along with got off the train, and the East German officials the immigration officials got off the train, and of course their Police and special officers took over the train and it was under their jurisdiction from then on, until the train arrived to the border of West Berlin and East Germany. They gave me the eye any number of times. I was asked why I was going to West Berlin and what business I had there. My answer was always "I am a tourist, and I want to see as much of Europe as possible." They really went through my little suitcase, even looking in the pockets of every garment. At every stop along the way they made every passenger getting off the train show their identification pass and a few questions were asked of each person with a nod or two from the official asking the question. Police were everywhere at each stop along the way. I was at last seeing a police state in operation. Sometimes two or three of their Police would look at me and say something to each other. I was a little concerned about this and I wondered what would happen before I got to West Berlin. Here was old Gus in the middle of Communism—these fellows did not smile at all. What was in store for me?—Next month, boys—
 . . . Gus

73 Books

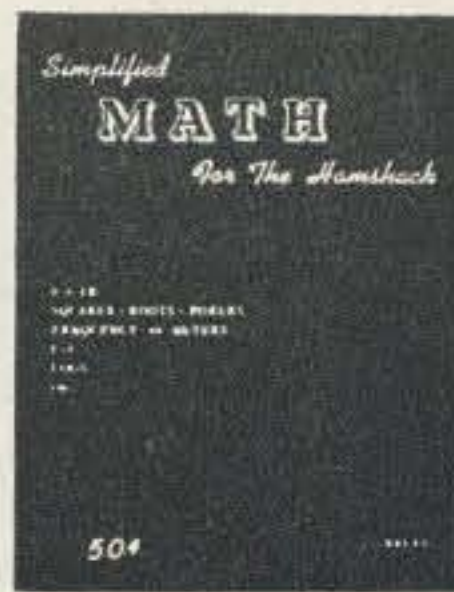

2—SIMPLIFIED MATH FOR THE HAMSHACK—K8LFI.—This is the simplest and easiest to fathom explanation of Ohm's Law, squares, roots, powers, frequency/meters, logs, slide rules, etc. If our schools ever got wind of this amazing method of understanding basic math our kids would have a lot less trouble. **50c**


12—CW—W6SFM.—Anyone can learn the code. This book, by an expert, lays in a good foundation for later high speed CW ability. **50c**

15—FREQUENCY MEASURING—WØHKF—Ever want to set yourself up to measure frequency right down to the gnat's eyebrow? An expert lets you in on all of the secrets. Join Bob high up on the list of Frequency Measuring Test winners. **\$1.00**

1—CARE AND FEEDING OF HAM CLUBS—K9AMD.—Carole did a thorough research job on over a hundred ham clubs to find out what aspects went to make them successful and what seemed to lead to their demise. This book tells all and will be invaluable to all club officers or anyone interested in forming a successful ham club. **\$1.00**



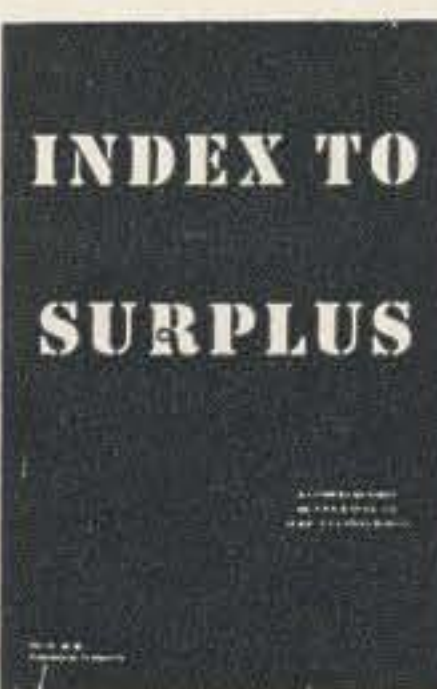ATV ANTHOLOGY. WØKYQ and WA4HWH.—A collection of the construction and technical articles from the ATV Experimenter. Includes a complete, easy to build vidicon camera and 50 other projects. The only book available about ham TV. **\$3.00**



3—REVISED INDEX TO SURPLUS—W4WKM.—This is a complete list of every article ever published on the conversion of surplus equipment. Gives a brief rundown on the article and source. Complete to date. **\$1.50**

RECEIVERS. K5JKX.—If you want to build a receiver or to really understand your receiver, this is the book for you. It covers every aspect of receiving in author Kyles usual thorough manner. **\$2.00**

TEST EQUIPMENT HANDBOOK. W6VAT.—Every ham needs to have and know how to use test equipment. This book tells you how to make valuable ham test gear easily and cheaply. It also covers the use of test equipment. **50c**

Ralph Hanna W8QUR
3023 Emmick Drive
Toledo, Ohio 43606



The SB-34

When the SBE 33 came out, I knew that it was the ideal transceiver for me. I was looking for a rig that would be convenient for use on a cabin cruiser. Boat mobile is a bit different than car mobile. The boat is not usually kept at home. Once you get on it you stay at least for the weekend. This means that you have to lug most transceivers out to the car with the speaker and two power supplies and then everything from the car to the boat. Two power supplies are usually necessary because commercial power is used dockside and batteries are used when underway. But a 250 watt inverter was already installed on my boat, so with the SB-33 all that had to be carried was the one little 18-pound package and the microphone, as the speaker and AC power supply are built in.

The SBE 33 is a fine transceiver and has some real clever design features. It was covered quite well by W1CUT¹ some time back. But as with any piece of ham gear, the user will wish for improvements. Several had been thought out and were considered for a winter project when SBE came along and announced the SB-34. Here were all the improvements you could ask for: slower tuning rate, incremental tuning, provisions for a calibrator, a dial corrector and best of all, a built-in 12 volt DC power supply, and all this at no increase in size or weight and no sacrifice in any of the plus features of the SBE 33. The new dial is marked in 5 kc division and the set covers 50 kc more of each band.

The dial corrector is a much needed improvement. It uses a varactor diode (voltage variable capacitor) in parallel with the VFO



coil and tuning capacitor. Varying the voltage on it with a conveniently located pot varies its capacitance enough to shift the frequency as much as 10 kc. The delta tuning is effective only in the receive position. The same varactor diode is used by changing the voltage a bit more for about 1 kc change in the receiver tuning. Properly biased diodes cut out the effect in the transmit position so that the transmitter is always on the same frequency as originally set. This is an ideal feature for round tables and when working other transceivers that are not as stable as they might be.

The most unique feature of the SB-34 is the method of switching from receive to transmit without the use of a relay. This is real tricky. Two transistors perform this function. The base of one is coupled through a resistor to the cathode of the driver tube. In the receive condition, because of the high negative bias on the grid of the driver tube, no current is drawn and therefore the base of the first transistor is at ground potential and it too is cut off so that its collector is at +12 volts. This voltage is applied to the receive control line. This same 12 volts is supplied to the second transistor which causes it to conduct to saturation so that its collector is at ground potential. This ground potential is applied to all the controls requiring ground potential.

When the push-to-talk button is depressed, the high negative bias on the driver is grounded so that the tube begins to conduct and build up to about 6 volts at its cathode. This voltage will now cause the first transistor to conduct and thus reduce the 12 volts to zero to cut off the receiver. With zero volts on the second transistor, it will be cut off so that its collector is now at 12 volts for the transmit

1. The SBE 33, E. L. Campbell W1CUT, QST, April 1964, p. 52.

CRYSTALS are not all the same!

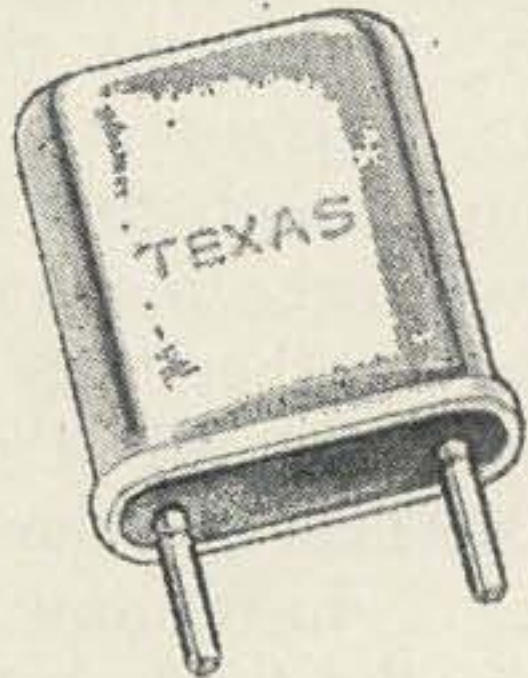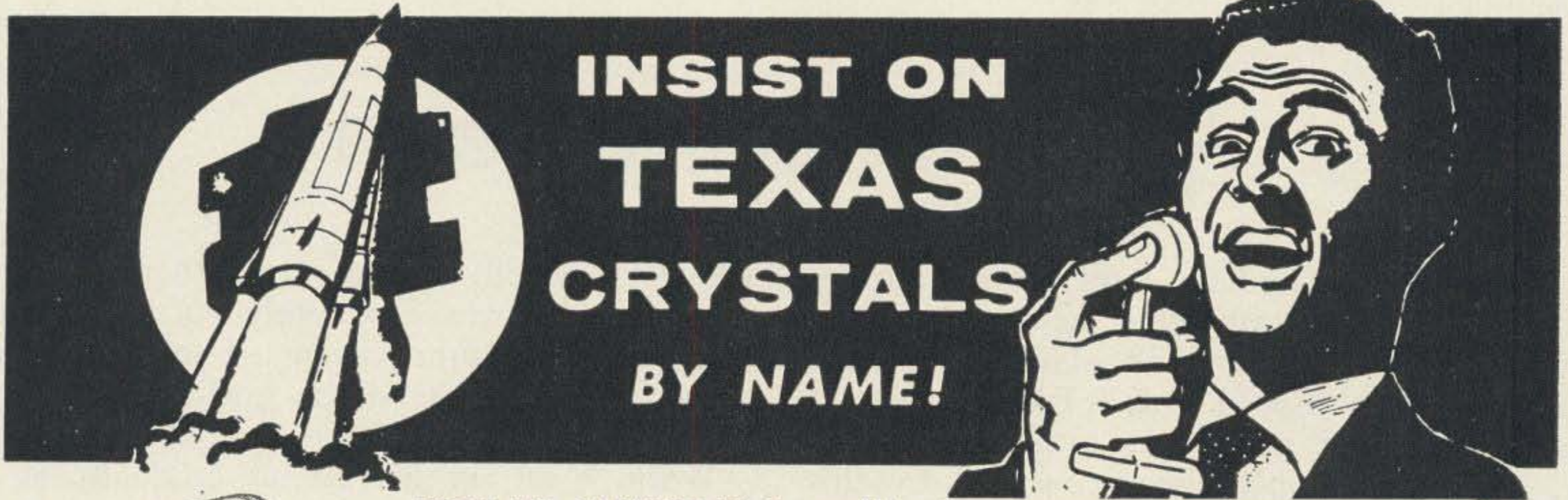


TEXAS CRYSTALS quality is outstanding as evidenced by use in numerous government space projects where there's no compromise with quality, reliability or accuracy. For commercial two-way, ham operation or special frequency control crystals, Texas Crystals are your best buy.

If your dealer is temporarily out of stock or does not carry Texas Crystals, send us his name along with your order. Minimum order, check or C.O.D. is \$5.00. Add 5¢ per crystal for postage, 10¢ for air mail.

TEXAS

1000 Crystal Drive
Fort Myers, Florida 33901
Phone 813 — WE 6-2109



A Division of Whitehall Electronics Corp.

Send for Free Catalog with Circuits

CRYSTALS

4117 W. Jefferson Blvd.
Los Angeles, California 90016
Phone 213 — 731-2258

function. A third transistor will energize an external relay to control a linear amplifier. Clever, huh?

The main feature of the power supply is that it will function on either 115 volt 60 cycle or 12 volt DC. Changing power cords does the switching. This feature makes the SBE 34 a truly universal transceiver that can easily be used mobile or fixed. And it will eliminate the fuss I had with Virginia, out in the middle of Lake Erie, as to who got to use the inverter on the boat—she to watch the noon time soap operas on TV or me to keep a 1200 sked. Incidentally, there was no TVI even on the small boat.

Just to see how really good the SBE 34 is, Ray Abain K8NBQ and I took it over to Rowe Industries and put it through its paces on the Panaramic Corp. Panalyzer, the Bird wattmeter, the distortion meter and all the other good things. Here is what we found using a single cycle tone:

Power Output—80 meters	62 watts
40 meters	77 watts
20 meters	78 watts
15 meters	57 watts

Carrier Suppression—56 db down from output signal

Unwanted Sideband Suppression—58 db

down from output signal

Distortion Products—28 db down from output signal

Spurious Responses—42 db down from output signal

Sensitivity—0.9 mv for 10 db signal plus noise ratio

Selectivity—2.1 kc at 6 db down 4.6 kc at 60 db down

The SBE 34 has a dual speed Jackson Brothers tuning drive that moves the dial at a high rate of speed in one direction, then goes into a fine tuning speed when backed up. The high speed is 90 kc per turn and the low speed is 20 kc per turn. The slow speed moves the dial 17 kc then goes back into high speed. For someone who likes to scan the bands as I do, I think the Jackson Brother continuous 6-to-1 dial drive would be better.

The usual accessory items are available, the most important of which is the 100 kc calibrator. This is a small two transistor unit that plugs in the back and only sticks out about $\frac{3}{4}$ of an inch. A switch on the front panel turns it on and off.

Dollar for dollar you will have to look a long way to find such a small package with so many features as the SBE 34 for under \$400.

... W8QUR

Brooks Lyman
7 Healey Street
Cambridge 38, Mass.

A DC Dummy Load

How many of us have built power supplies and tested them by plugging them in and turning them on—if they don't blow up or start smoking, then they're O.K.? Probably all of us have done this at one time or another. Usually, when the supply checks out OK by this method, then all is truly well, and one can plug in the rig or whatever and get on the air.

But there are always the exceptions to the rule, such as the time recently when I built a power supply for an ultrasonic cleaner. The cleaner was to use a pair of 811-A's in class B, drawing about 350 watts dc from the power supply. The only plate transformer that I had anywhere near that rating was one of the standard 2400 volts center-tapped at about 220 ma types. This meant that the dc output from the power supply after filtering would be about 1100 volts at 220 ma—very definitely *not* 350 watts. Therefore I wanted to test the supply at a rather large overload without running the cleaner (which was not built yet anyway). This meant a large load resistor—about 3K at 300 or so watts. I had no resistors which could possibly be combined to make such a value, and a swift look at the box containing the light bulb collection told me that a lamp bank was not the answer either. A look at the local distributor's catalog decided me against buying the necessary resistors.

Just as I was about to give up, it occurred to me that a vacuum tube was really nothing more than a variable resistor. With this thought in mind, I grabbed an old 304TH off the shelf and set up the circuit in Fig. 1.

From the tube curves, I found that with about 1000 volts on the plate, I needed about

100 volts negative on the grid to make *sure* that the tube was completely cut off. When I had the load tube connected to the power supply, I then lowered the grid voltage until the tube was drawing the desired current.

While I set up the circuit originally as a breadboard-haywire affair, I thought that it was sufficiently useful to warrant its being built in a small (well, big enough to get the 304TH in) metal cabinet with the meters built in and a built-in bias supply, rather than using the laboratory power supply. Not all of us are lucky enough to have 304TH's in our junk box, and often one doesn't have any other power tube than the one in the final. Actually, any tube can be used as a load, so long as the ratings are not exceeded too much (note that I was dissipating 350 watts in the 304TH, which is rated at 300 watts dissipation). I would recommend the use of triodes, both because they are often cheaply obtained and because there are fewer problems involved in using them in the circuit. The following tubes are suggested, since they are common: 304TH, 304TL, 6C21, 450TH, 450TL, 250TH, 250TL, 810, 805, 811 or 811-A (note that the last two tubes mentioned are zero bias triodes, and that they will probably draw grid current. Design the bias supply accordingly). Naturally, any tube can be used, and if you are really desperate, you can use the one in your final but be careful not to blow the grids out of it or melt the plate. . .

Fig. 2 is the circuit of the final version as mounted in the cabinet. I grounded the center of the filament transformer to the chassis, as the transformer was only rated for 2500 volts

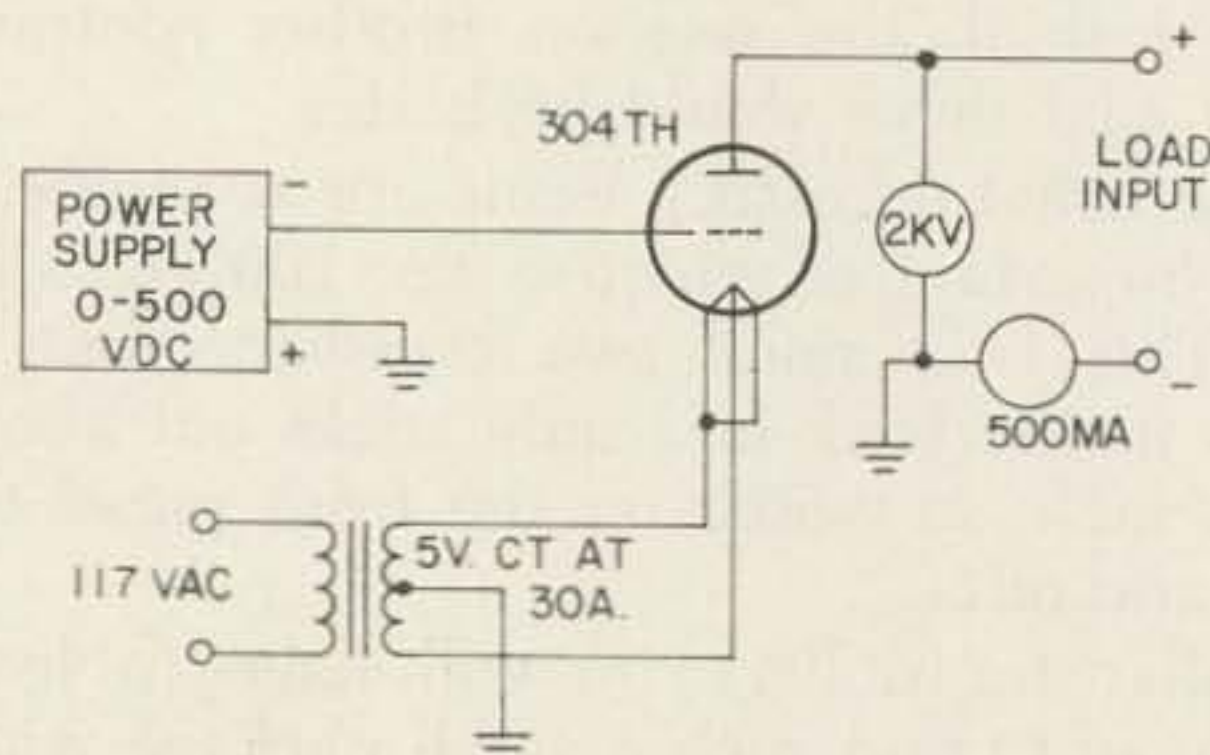


Fig. 1.

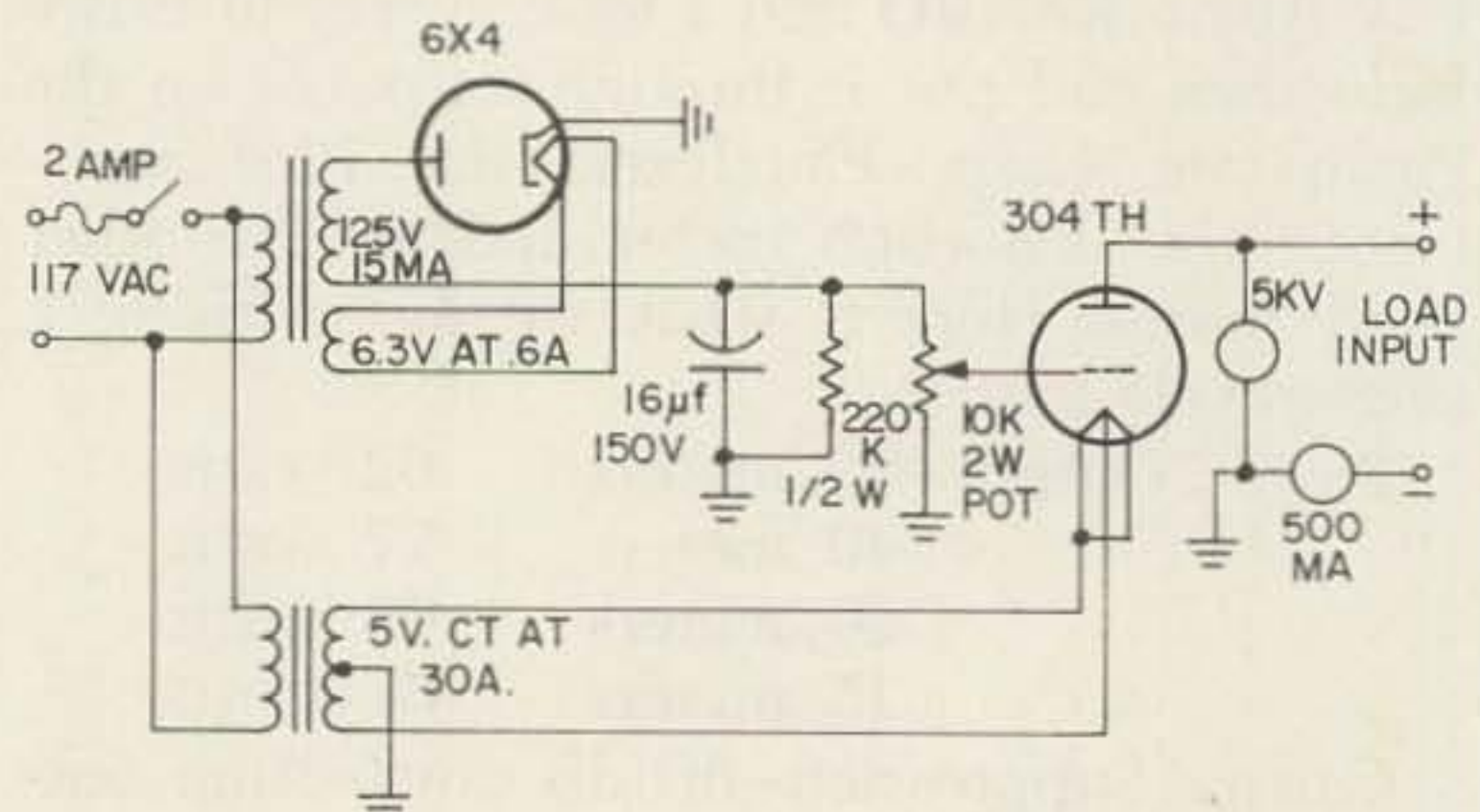


Fig. 2.

insulation to ground, and I was not in a mood to play around with that kind of fire. If you have a better transformer, it might be advantageous to isolate the entire circuit (including the bias supply) from the chassis. The bias supply is standard, and delivers from 0 to -120 volts. None of the values are critical. Note the 220K resistor across the filter capacitor. This is a safety bleeder and is there for the following reason: when I started to build this thing, it was about one in the morning, and as a result I chose a chassis which was too small to simply build sides around in order to make a cabinet—the meters wouldn't fit. So I had to make the cabinet larger and put the meters and controls (including the bias control pot) in the front panel with some space between the panel and the chassis. The controls were attached to the chassis by means of a cable with a plug on the end, and to make sure that the filter capacitor discharged if the plug should be pulled out, the resistor was added. A more wide-awake constructor will probably avoid most of the pitfalls into which I fell that morning. Note that since one should start to test a supply with no load (to make sure that you haven't got too much load), the counter-clockwise position of the bias control should give maximum bias voltage to the tube, and the control should be adjusted for the desired current on the meter *after* the supply is hooked up to the load.


Since this circuit will probably be used close to hand, on the bench, rather than across the room in the rack cabinet, it is worthwhile bringing up a few of the well worn but true sayings regarding safety: don't adjust the meter zero set screw when there is voltage applied to the circuit—there isn't much between you and the HV—just a little piece of plastic (and some meters use metal adjusting screws). Keep one hand in your pocket when playing around with live wires, etc. The tube is HOT—don't touch it or spill water or other liquid on it.

The circuit mentioned above is not new, but it is seldom used due to the need for more components than a simple resistor bank contains. For the experimenter, however, it has the advantage of being variable, and the parts used are such that most hams and experimenters can readily obtain them. The circuit could also be used as a bleeder resistor and could be built into a power supply if desired. Also, while the tubes mentioned have been in the 100 to 600 watt range, there is no reason why larger or smaller tubes could not be used.

. . . Lyman

NEW callbook

HOT OFF THE PRESS!

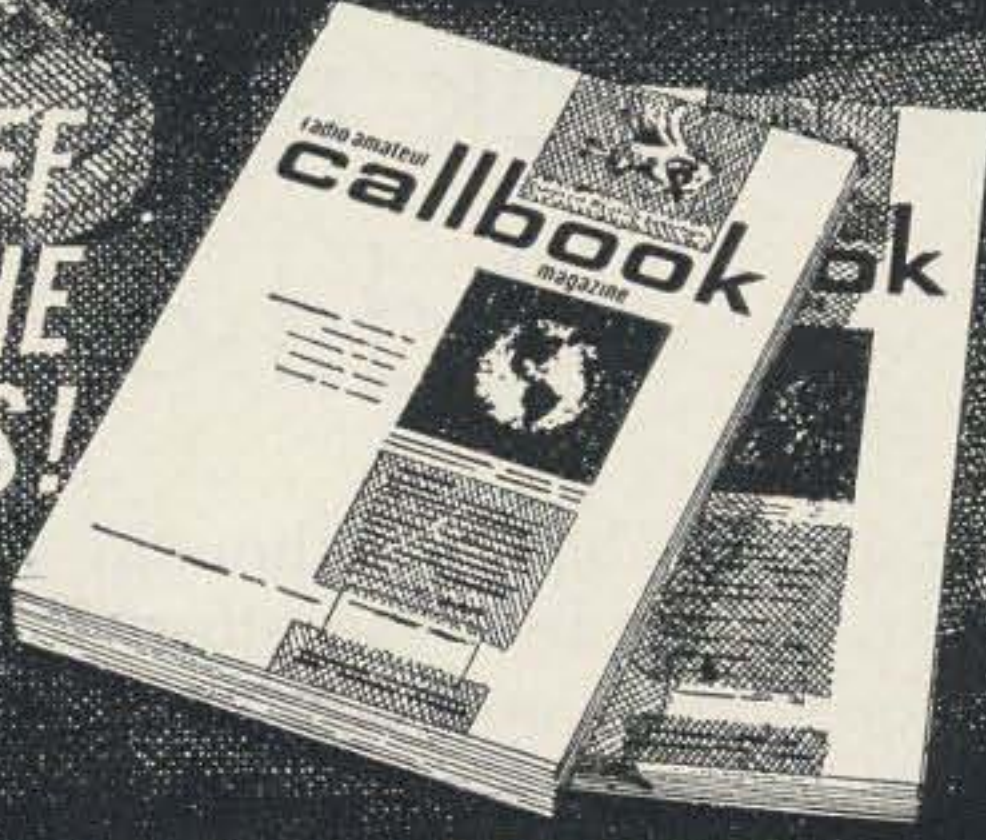

Over 60% of listings changed in only a year!

- Great Circle Bearings
 - Great Circle Charts
 - Prefixes by Countries
 - "Q" and "Z" Signals
 - World Time Chart
 - Int'l. Postal Rates
- United States Listings... \$5.00**
DX Listings..... 3.25

See your favorite dealer or order direct (add 25¢ for mailing)

RADIO AMATEURS REFERENCE LIBRARY OF MAPS — ORDER YOUR SET TODAY!



WORLD PREFIX MAP—Full color, 42" x 29", shows prefixes on each country . . . DX zones, time zones, cities, cross referenced tables.....postpaid \$1.00

RADIO AMATEURS GREAT CIRCLE CHART OF THE WORLD—from the center of the United States! Full color, 29" x 25", listing Great Circle bearings in degrees for six major U.S. cities; Boston, Washington, D.C., Miami, Seattle, San Francisco & Los Angeles. postpaid \$1.00

UNITED STATES MAP—All 50 States with call areas, prefixes, DX and time zones, FCC frequency allocation chart. Plus interesting information on all 50 States. full color, 29" x 17".....postpaid 50¢

WORLD ATLAS—Only Atlas compiled for amateurs. Polar projection, six continents, prefixes on each country . . . full color, 16 pages.....postpaid \$1.50

Complete reference library of maps—set of 4 as listed above.....postpaid \$2.50

See your favorite dealer or order direct.

WRITE FOR FREE BROCHURE!

RADIO AMATEUR

callbook INC.

Dept. B, 4844 W. Fullerton Ave.
Chicago, Ill. 60639



Quick and Easy Add-on Neutralization

Ever build what you thought was going to be "just a simple straightforward amplifier" when you found you needed a little more gain, a little more isolation, a little more power, or all three and then find you can't eliminate self-oscillation? I just did. And it oscillated. Bad. Lit a bulb with no rf input, just from it's own nasty little internal grid-plate capacity.

This was a 5763 amplifier on 50 megacycles driven by half of a 12AT7 crystal oscillator. Nothing to it. Done every day. But, after it was built with great care to make a nice input circuit, which tuned well out on both sides of 50 mc, very complete shielding, and an equally nice tuning plate circuit, it had self-oscillation.

Now I've fought this sort of thing since 1938, and that's about 26 years, but I find there's still a lot to learn. So young lads starting out today probably need a little assistance. I sure did. Now what do the books say? Some of the "best" are worse than useless! Listen to this one. "Any amplifier will oscillate if sufficient energy having the same frequency and the same phase as the grid voltage is fed back from the plate circuit to the grid circuit."

If you think a little about the energy fed from a plate to a grid by the internal C_{gp} of the tube, you will see that this is in *phase* or nearly so. And this is not the proper phase for a vacuum tube oscillator, which as I'm sure you know, should be *out of phase*. Grid going

positive, plate going negative, etc. Actually a tube which is self-oscillating does so in spite of the phase effect. There is some phase shift in the small C_{gp} and the frequency of the plate and grid circuits are *not* exactly in tune either. Remember how a crystal oscillator tunes "up one side" and then jumps out of oscillation?

Now the funny thing is that proper neutralizing energy which is fed back by the neutralizing circuit is in the correct phase for oscillation! That is, 180 degrees out of phase. Of course, if you will look back at the previous paragraph you will see that the nuisance feedback from plate to grid through the GP capacity is in phase, so that neutralizing energy would have to be out of phase to cancel it.

Let's take the tube I used above, the 5763. Here's a good tube. Used in loads of circuits. Does anyone tell you whether or not it has to be neutralized? No Sir. I haven't found a word on that yet. You look up the C_{gp} and find that it is listed as only .3 (three tenths) of one micro-micro-farad. That's pretty small isn't it? Or is it? Will it self oscillate? Should you first build a split tank with a neutralizing capacitor over to the grid? You'd think the handbooks suddenly ran out of ink! Let's look at a tube which we know is generally not neutralized. The 6BA6, for example. Ah hah! The C_{gp} is only .0035 max. Thirty-five ten thousandths of a micro-micro-farad. That's real small!

The 807 has a C_{gp} of .2 mmf which is where a lot of that tube's instability comes from. In the 2C39, a triode, but generally used in grounded grid circuits, with the cathode the active element that could generate trouble, we find that the C_{kp} (note, plate to cathode) is .035 max. Not quite as good as the 6BA6 but a good deal better than a lot of other transmitting tubes.

So, how do you know when to build a neutralizing circuit in or not? You don't really. The books don't tell you. I generally figure that when the C_{gp} is in two decimal places or less, like .05, you *may* not need to neutralize. If it's in the tenths, like .2 or more, you probably will. You can also see that due


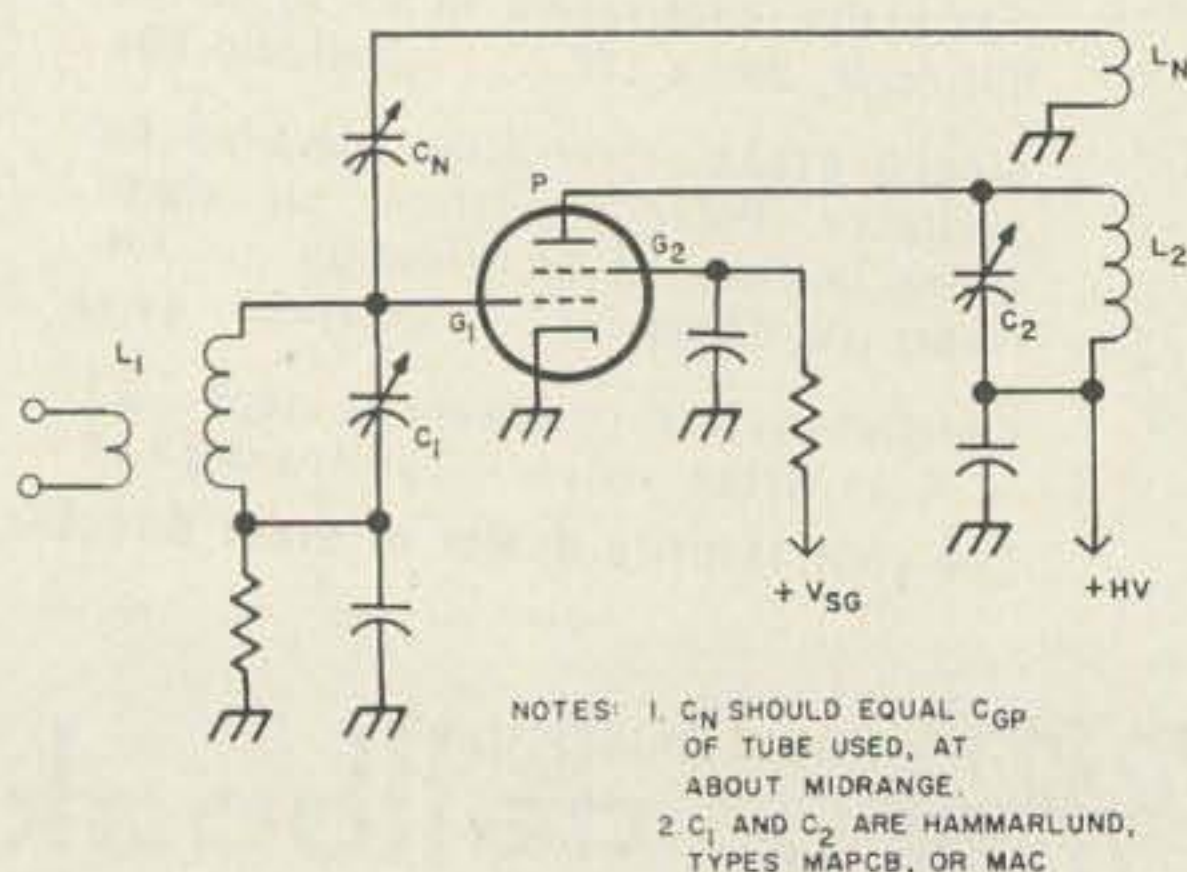


Fig. 1. "Outboard" neutralizing circuit.

Fig. 2

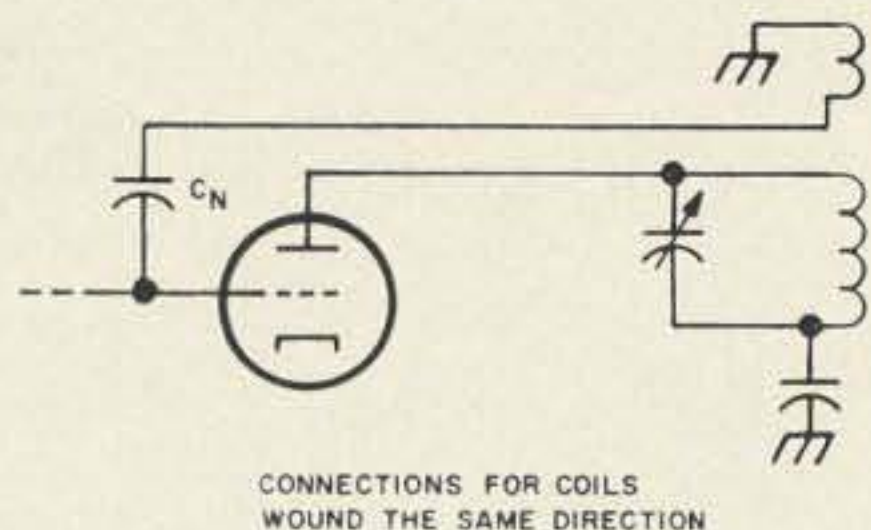

CONNECTIONS FOR COILS WOUND THE SAME DIRECTION

to the natural-born increase in power through a small capacitor with increasing frequency where this will lead you to on VHF or UHF. Note that the 6AK5 has a C_{gp} of .02, quite a bit more than the 6BA6. The 6AK5 was found in lots of places where perhaps it should not have been, but all's fair in love and war, and that was a war tube.

One of my favorite transmitting tubes is the quick-heating 7 watter, the 5618. However, its C_{gp} is .24 so I have always had to neutralize it.

So by now you get the general idea, and if you did build that amplifier without the usual neutralizing tank circuit, or can't make up your mind, or just plain don't want to, never mind. We are about to show you how to add it on later as an after thought. Easy like. You know, "No time like the future for things that don't stuit yer." Of course, you *may* belong to the "No time like the present for things that aren't pleasant" school.

Actually, this neutralizing circuit works even with a high-gain grounded cathode triode on two meters, so I'm going to try it every time from now on myself. Even on 432 I hope.

So far it has worked every time. Just build up a good grid circuit, use good shielding, a good plate circuit, fire it up, watch your grid drive go as you tune through resonance with the plate circuit, and then go to work and neutralize it. Of course you can build it in first, if you insist.

Just put a few turns of reverse phase winding (L_n) in or around L_2 and couple it over to the grid, through the shield, with C_n for amplitude adjustment. Remember that this reverse phase is just what the doctor ordered


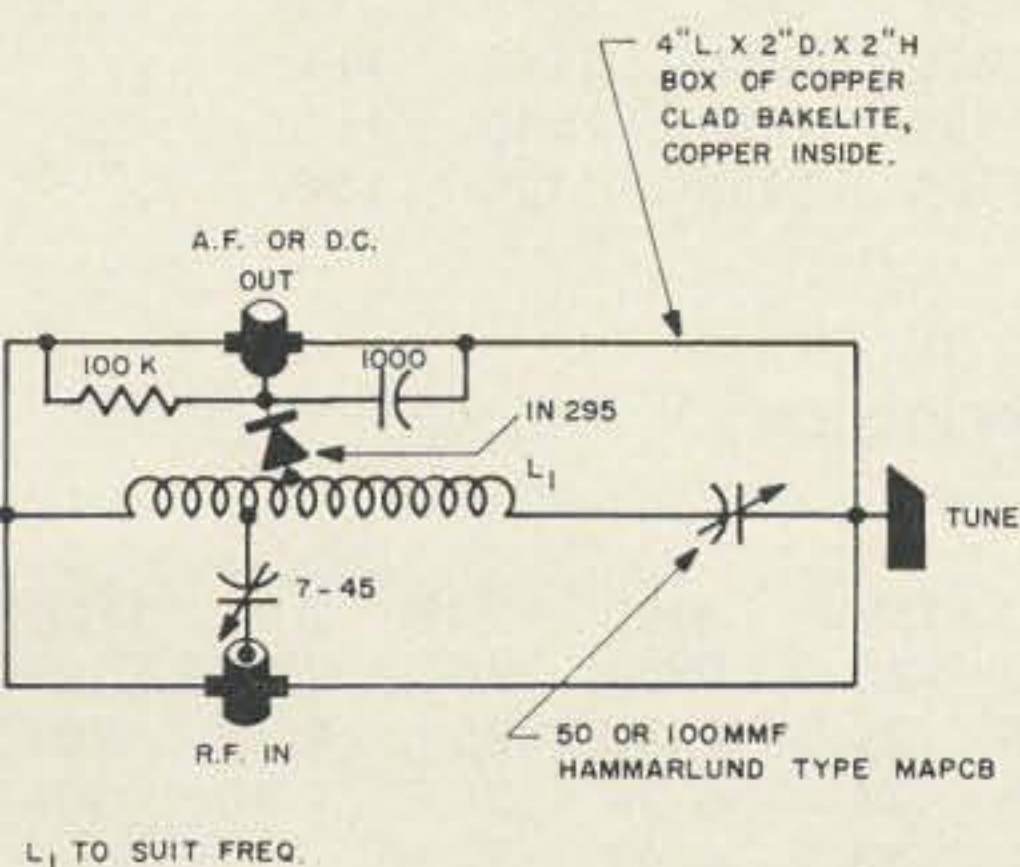


Fig. 4. Tuned detector.

Fig. 3

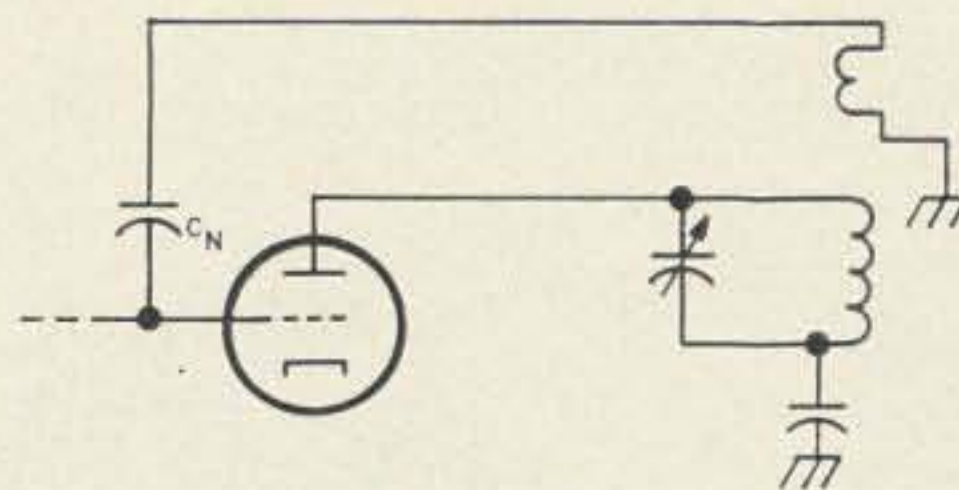

CONNECTIONS FOR COIL L_n WOUND OPPOSITE DIRECTION

to make an oscillator and can be done in more ways than one. If you wind L_n in the same direction, that is clock-wise, or counter-clock-wise, as L_2 is wound, use the opposite end from the plate to get the out of phase energy. See Fig. 2.

If you wind it in the opposite direction from the plate coil L_2 , use the same end to get the out of phase energy. See Fig. 3.

There's a real fancy deal going on here in fundamental magnetic coupling like left and right hand snail shells, but we'll leave *that* to the *Scientific American*. Some smart transformer people can wiggle three fingers so as to point in three different directions at once, and call this the magnetic rule of thumb. Never mind, just remember "with a tube oscillator coil, put the plate on one end and the grid on the other."

Also, you can put L_n almost anywhere and it will work. On the end of L_2 , interleaved, inside L_2 , or outside. I've tried it.


To adjust C_n , do like the books say. I use a tuned circuit detector. It helps to be sure just what frequency you *are* neutralizing. Plug the detector right into the output jack, but, unless you have lots of spare diodes, don't turn on the amplifier plate and screen supply!

It is really helpful to watch that meter (the diode meter) go down to, or near, zero, in the neutralizing null. It kind of restores your confidence in the fact that, if the theory you're using is correct and if your circuit is built right, it is a law of nature that it must work! And, I almost forgot, you can use that same detector, with a little transistor amplifier and a pair of "Hi-Fi" padded earphones, the kind with the real big large pads on them, to listen to your own modulation. But don't plug it into the rf output with the power on! Just have it nearby! And be sure it's the *diode* you're listening to. The af amplifier can pick up rf and rectify it plenty loud, but you won't like that modulation. Another reason for the tuned detector. It works FB for almost any purpose. It also goes to 432, with a strap for L_1 . Also ditto for a 1215-1296 megacycles detector.

I hope this helps you to make better rigs easier, especially on VHF and UHF.

. . . K1CLL

DIAGRAM A

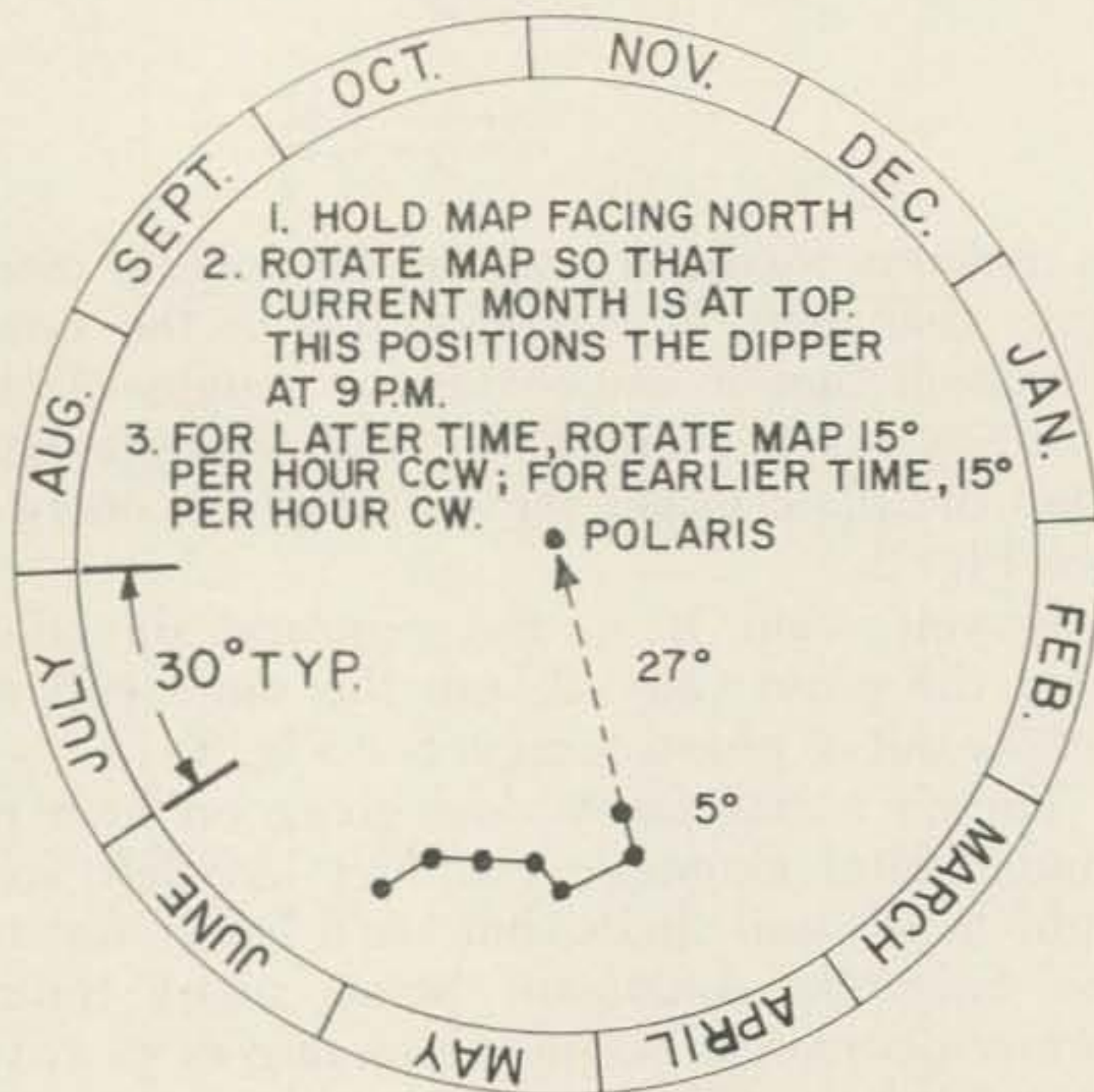

Polar vs. Solar Beam Orientation

One of the common methods of orienting a beam antenna is to align the boom in the direction of the Pole Star. Since Polaris rotates daily counterclockwise around the north celestial pole in a circle whose radius is approximately 1° , the error in true north indication need not exceed 1° .

To assist in locating the Pole Star, the "Pointers" of the Big Dipper are often used as a guide. Instructions are given in Diagram A for proper identification of the Pole Star.

Using the angular distance of 5° between the Pointers as a yardstick, one easily identifies

Polaris as a fairly bright star (second magnitude) 27° from the top Pointer at an altitude above the north point of the horizon corresponding to the observer's latitude.

The Polaris method of beam orientation is not available to observers in the southern hemisphere because there is no accommodating star of comparable brightness close to the south celestial pole. One shaft of the Southern Cross (Gacrux to Acrux) points roughly to the south celestial pole and could be used in a pinch. On the other hand, the solar method is good anywhere in the world

TABLE I LMT OF SUN'S MERIDIAN PASSAGE

	Jan	Feb	Mar	Apr	May	June	July	Aug	Sept	Oct	Nov	Dec
1	1203	1214	1212	1204	1157	1158	1204	1206	1200	1150	1144	1149
10	1207	1214	1210	1201	1156	1159	1205	1205	1157	1147	1144	1153
20	1211	1214	1208	1159	1156	1201	1206	1203	1154	1145	1146	1157

TABLE II DIFFERENCE OF LONGITUDE CONVERSION
 (time in minutes)

ARC	TIME	ARC	TIME	ARC	TIME	ARC	TIME	ARC	TIME	ARC	TIME	ARC	TIME	ARC	TIME
0 ⁰⁰ '	0	1 ⁰⁰ '	4	2 ⁰⁰ '	8	3 ⁰⁰ '	12	4 ⁰⁰ '	16	5 ⁰⁰ '	20	6 ⁰⁰ '	24	7 ⁰⁰ '	28
0 15	1	1 15	5	2 15	9	3 15	13	4 15	17	5 15	21	6 15	25	7 15	29
0 30	2	1 30	6	2 30	10	3 30	14	4 30	18	5 30	22	6 30	26	7 30	30
0 45	3	1 45	7	2 45	11	3 45	15	4 45	19	5 45	23	6 45	27		

at any latitude and longitude.

All one need know is his approximate longitude and the local mean time (LMT) of the sun's meridian passage. Table I lists this LMT on the first, tenth, and twentieth of each month. These values do not vary by more than about one minute from year to year. Even if the time is in error by four minutes, the angular error of the sun's direction is only 1° .

Since our clocks are based on standard or zone time, it is necessary to apply a longitude correction, converted to time units by mean of Table II, to the nearest standard meridian. The standard meridians are theoretically spaced 15° apart to the east or west of the Greenwich prime meridian. If the station longitude is east of the standard meridian, subtract the difference in longitude in time units between your station and the nearest standard meridian from the LMT; if the station longitude is west of the standard meridian, add the longitude difference in time units to the LMT. Thus, Standard Time or Zone Time = LMT \pm Long, Dif. to Stand. Mer.

To demonstrate the simplicity of the solar method, two examples are chosen.

1) What is the standard time of meridian passage of the sun at Longitude $118^\circ 20' W$ on June 15?

From Table I we interpolate a value of LMT = 1200. The nearest standard meridian is $120^\circ W$. The difference in longitude between the station and the nearest standard meridian is $1^\circ 40'$. From Table II this amounts to 7 minutes. Since the station is east of the standard meridian, Pacific Standard Time of the sun's meridian passage is PST = 1200 - 0007 = 1153.

2) What is the standard time of meridian passage of the sun at Longitude $40^\circ 19' E$ on December 8?

From Table I, LMT = 1152. The difference in longitude between the station and the nearest standard meridian of $45^\circ E$ is $4^\circ 41'$ which by Table II is equivalent to 19 minutes. Since the station is west of the standard meridian, Standard Time of sun's meridian passage is 1152 + 0019 = 1211.

About one minute before the sun is due south or north depending on your latitude, put on your dark glasses, stand back, point your antenna boom toward the sun as it crosses the meridian, and set your direction indicator. It's so simple; why bother to orient your beam at night with a fumbling flashlight?

... W6TAQ

CLF-401

SLF-401

THE HEAVILY OVERCROWDED BANDS with which today's amateur is confronted has brought about the development of two highly specialized audio filters by the Selectronix Company. The characteristics of these filters have set new industrial standards in several respects:

* Skirt of transition band cut off from 6 to 60 db is literally five times sharper than the BEST mechanical or crystal filters in the amateur radio field today!

* Insertion loss is only 3 db.

* The simple "speaker or phone line hook-up has never before been part of a previous high performance filter system.

ONE OF THESE FILTERS has been designed strictly for CW purposes—model CLF-401. The other is for SSB—model SLF-401. Both have bandwidths chosen to be optimum UNDER QRM CONDITIONS: 200 cps and 1500 cps respectively.* An "In-Out" switch on the panel enables by-pass of the Selectronix filter when desired.

WITHIN TEN DAYS after the purchase of any Selectronix product, you may return it via parcel post and receive full refund of the purchase price. This offer enables you to try our filters with complete confidence.

WE HOPE you will enjoy the absolute ultimate in selectivity devices the next time QRM annoys you.

CLF-401 ... \$39.50 plus \$2.00 postage and handling

SLF-401 ... \$39.00 plus \$2.00 postage and handling

Write for more information or order direct.


SELECTRONIX

COMPANY

1951 Selby Avenue

Los Angeles, California 90025

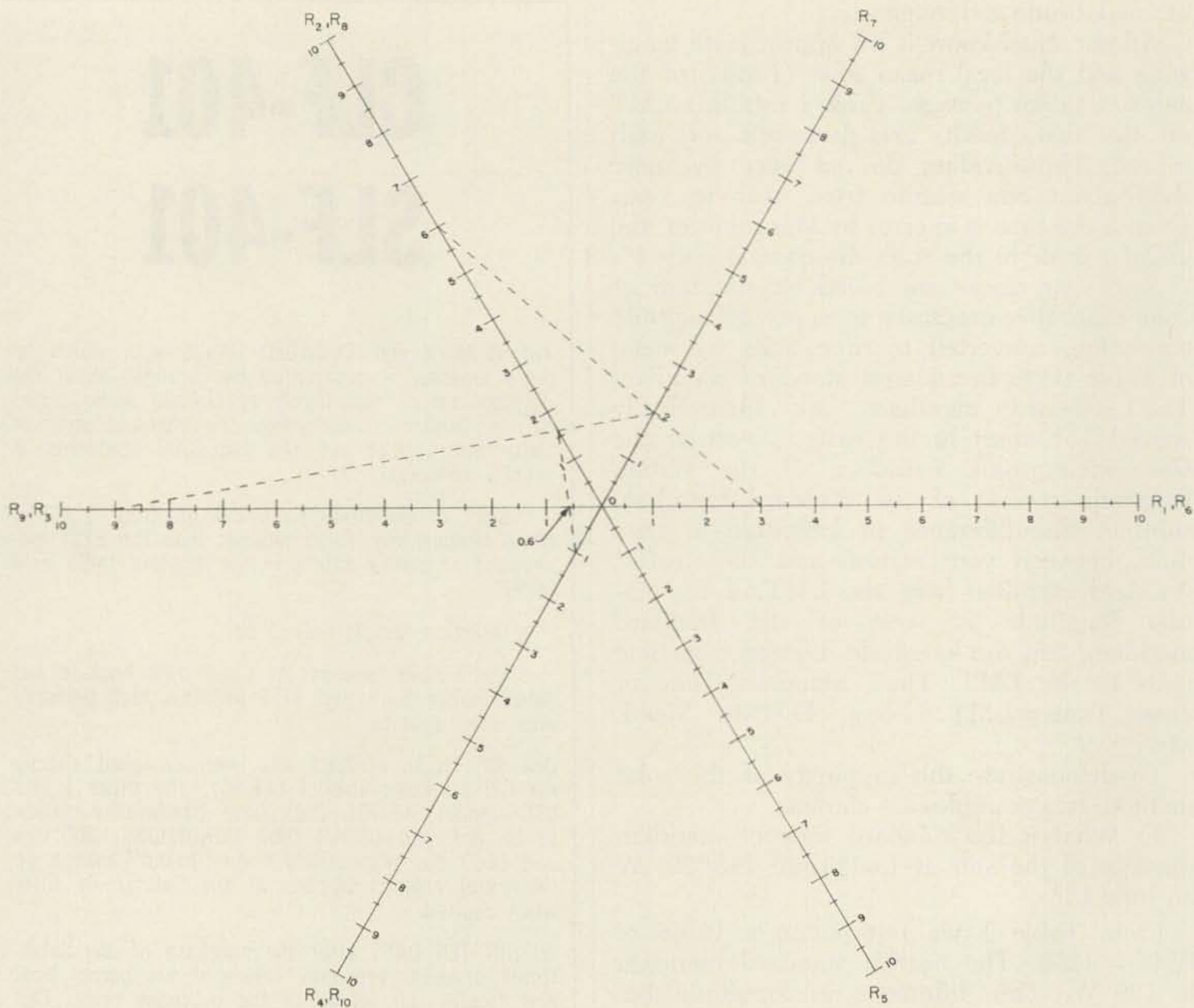* Measured from audio roll off of most receivers of 200 cycles.



Parallel Resistance Nomogram

Harvey B. Rock WA2BWQ
1865 77th Street
Brooklyn, New York 11214

Solving for the resistance of a parallel resistance combination can be a tedious job, especially if there are more than two resistances in the combination. Series capacitors present exactly the same problem. The equation

$$R = \frac{R_1 R_2}{R_1 + R_2}$$

is fine for two resistances, but even this requires computation. The above nomogram allows solution of this type of problem in seconds, with an accuracy of 3% (most resistors have tolerances of 5% or 10%). In addition, this nomogram can be used for any number of parallel resistors or series capacitors.

A glance at the nomogram will reveal that the scales are calibrated from 0 to 10. It is very important to use resistors whose multipliers are the same (same number of places after the first number). Cases where the multipliers are different will be explained later. The operation of this nomogram will be best explained by the following example.

Suppose we have a parallel combination of resistors with characteristic numbers of 3, 6, 9, and 1. These could be, for example, 3,000 ohms, 6000 ohms, 9000 ohms and 1000 ohms, or, 30000 ohms, 60000 ohms, 90000 ohms and 10000 ohms. Let us take for our example the parallel combination of $R_1 = 3000$ ohms, $R_2 = 6000$ ohms, $R_3 = 9000$ ohms

PATENT PENDING

E·Z

MOBILE ANTENNA MOUNT

FOR ANY C.B. OR HAM ANTENNA

\$8.95

POSTPAID

MODEL C103
STANDARD
BALL MOUNT

MODEL C750
3/4" HOLE

MODEL C375
3/8" HOLE

- ✓ NO BODY HOLES ARE NECESSARY
- ✓ FASTENS TO DECK LID IN MINUTES
- ✓ SUPERIOR GROUND PLANE EFFECT
- ✓ RADIATION EFFICIENCY INCREASED 100% OVER BUMPER TYPE MOUNTS
- ✓ CHROMED RIGID TEMPERED STEEL

SPECIFY MODEL AND/OR ANTENNA STYLE DESIRED WITH CHECK OR MONEY ORDER FOR \$8.95 (MICHIGAN RESIDENTS ADD 4% SALES TAX) SHIPPED PREPAID WITH MONEY BACK GUARANTEE. DEALER INQUIRIES INVITED.



E·Z

MOBILE ANTENNA MOUNT INC.

P. O. BOX 277 ALGONAC, MICHIGAN

and $R_4 = 1000$ ohms. To solve for the equivalent resistance of the circuit: connect "3" on the R_1 scale with "6" on the R_2 scale. From the point where this line crosses the scale between these two, draw a line to "9" on the R_3 scale. Again, from the point where this line crosses the intermediate scale (R_2 scale) draw a line to "1" on the R_4 scale. The point where this crosses the intermediate scale is the equivalent resistance, which in this case is 0.6. Since each resistance was one thousand times the characteristic number, the equivalent resistance is 600 ohms. If there were more resistors in parallel, we would continue in this manner, always in a counterclockwise direction.

If we were working with series capacitors of values, for example, 3 pf, 6 pf, 9 pf, and 1 pf the result would be 0.6 pf.

Going back to our resistor problem, suppose in addition to the four resistors above, we also had in parallel a 200 ohm resistor. Since this is just like having a 200 ohm resistor in parallel with a 600 ohm equivalent resistor, we simply connect the "6" point on R_1 with the "2" point on R_2 and read off 1.5 or 150 ohms. Doing it takes less time than explaining it.

. . . WA2BWQ

The Amateur Radio Handbook

This fabulous hardbound 540 page handbook completely and thoroughly covers every aspect of amateur radio: tubes, transistors, receivers, transmitters, VHF gear, antennas, sideband, FM, mobile gear, noise, power supplies and much, much more. This handbook is a necessity of the building ham. Published by the RSGB. \$5.50

Radio Data Reference Book

Have you noticed a basic lack in your ARRL handbook? The RSGB Radio Data Reference Book supplies everything left out and far more. It contains all of the formulae you'll ever need in one hardbound book. Also contains complete design information on RF power amplifiers, pi nets, tanks, filters, antenna design charts, coil data, math, and a tremendous amount more. You need this one. \$2.25

Order 73 Magazine Peterborough, N. H.

ATTENTION VHF'ERS

Send for a sample of the VHF'ER, the magazine for serious VHF-UHF hams. Ideal for anyone interested in improving his knowledge of the most interesting field in ham radio.


Subscriptions: \$2 per year
\$3 foreign

THE VHF'ER

Parks Laboratories
Route 2
Beaverton, Oregon

Another RF amplifier
for the 432'er in July '64.

RF Amplifier for 432

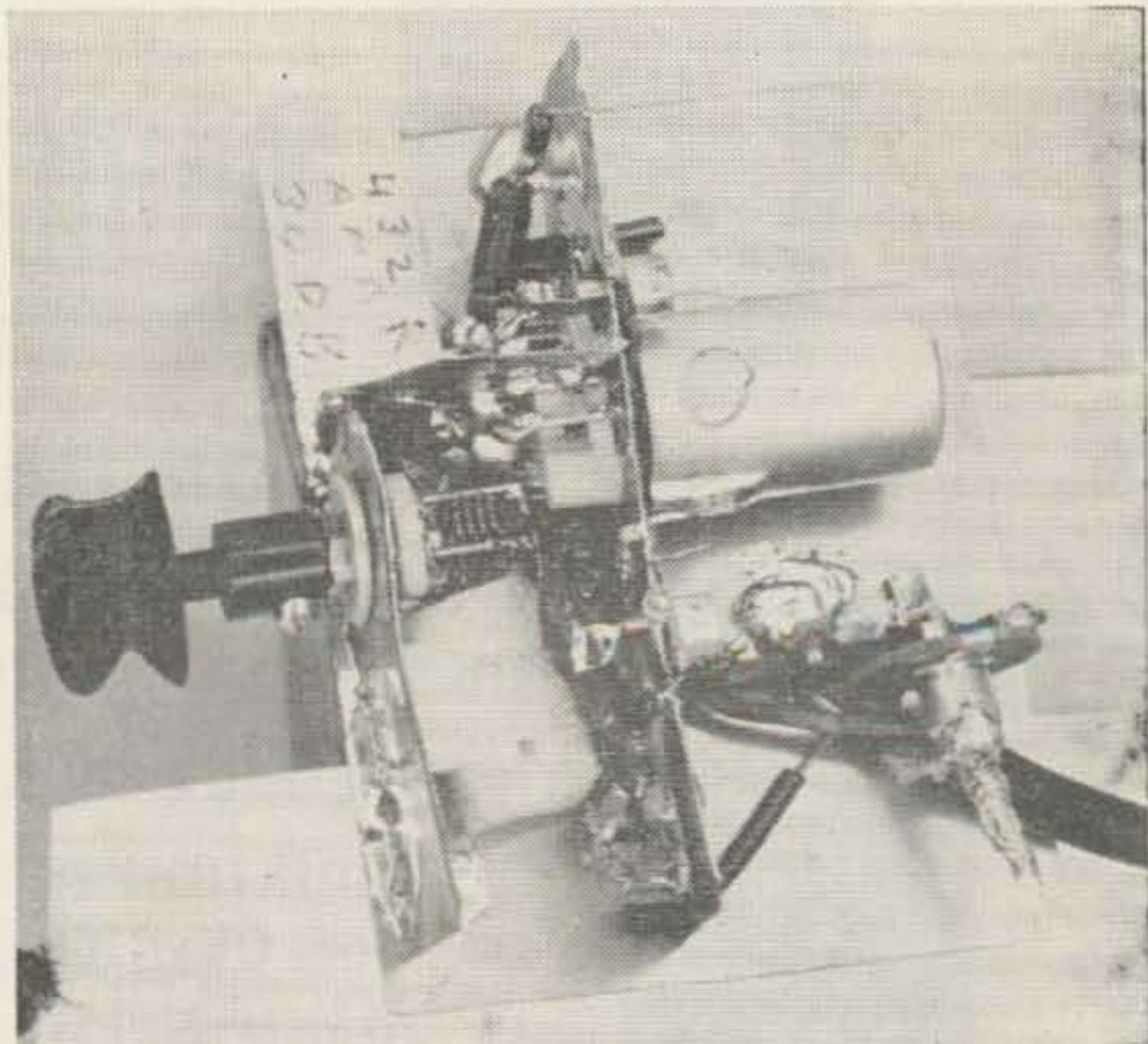

Bill Hoisington K1CLL
Peterborough, N. H.

Digging hard into the practical possibilities of low-cost amplifier tubes for 432 megacycles, we found (after building an odd ½ dozen or so amplifiers) that well over 20 db gain is possible with a 6AM4 tube at this frequency, with a stable circuit. Including this high gain unit, we are thus describing three 432 megacycle amplifiers using tubes, which should be enough to choose from.

This one, (see Figs. 1 & 2) using a straight ¼ wave line beginning with the grounded end of the plate strap line, through the socket pins, on through the plate structure itself, and ending up with the top of the plate as the hottest to rf (or open end portion of the line), seems to have more gain than the previous one described in which the plate was tapped on to the plate line. You have to be more careful with unwanted grid inductance though, due to the gain. This is the inductance you *don't* want, and that you thought you elim-

inated by grounding all those five grid pins!

Also, just as a confirmation of the old warning about bakelite on high frequencies, I built one of these units with a bakelite 9 pin socket. Gain of about 9 db! Ugh! Nuff sed.

It really pays off at 432 to look up and get the thin version of the porcelain sockets. This thin version allows the socket pins to grab the tube pins way up close to the glass.

Note that the plate structure of the tube (to a certain extent) along with the shield of the tube, forms a partial cylindrical cavity for the plate circuit.

Fig. 1 shows a view of the back wall of the unit. In a sense, everything except the tuning capacitor is referred to the back wall as ground. It is hard enough to find a "ground" at 432 megacycles, so I'm mentioning this one. It is quite efficient also. Items needing such rf reference to ground are: the input jack outer conductor, the five grids, the two heater connections, the rf output jack outer connections, the plate line cold end bypass capacitors, and the tuning capacitor. This last is actually referred to the *front* wall, but that is still OK, if used as shown.

Still talking about grounding, I also used on one of the units a socket which was definitely *not* UHF. It was of good porcelain, but the pins were quite *long*. With everything buttoned down tight I still got feedback oscillation at one spot on the dial (without plate load). With all the five grids grounded, one of them made a loop about an inch long—starting from the wall, up to the pin, and down through the tube base to the actual grid structure. This was enough to cause the feedback. Note (as mentioned before) this is a high gain, high Q job. Operating



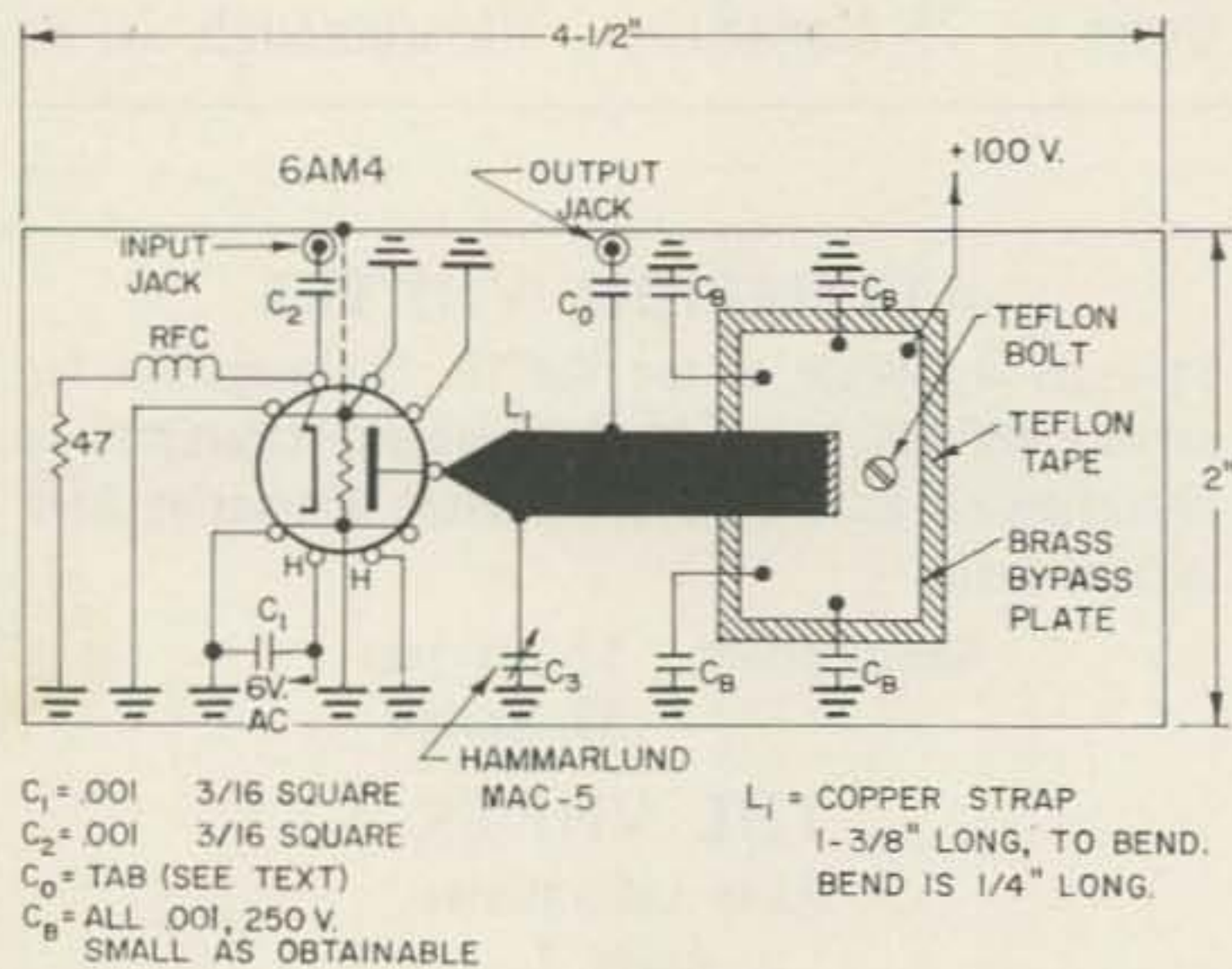


Fig. 1—Front "inside" view of rear wall—
high gain 432 mc Amplifier

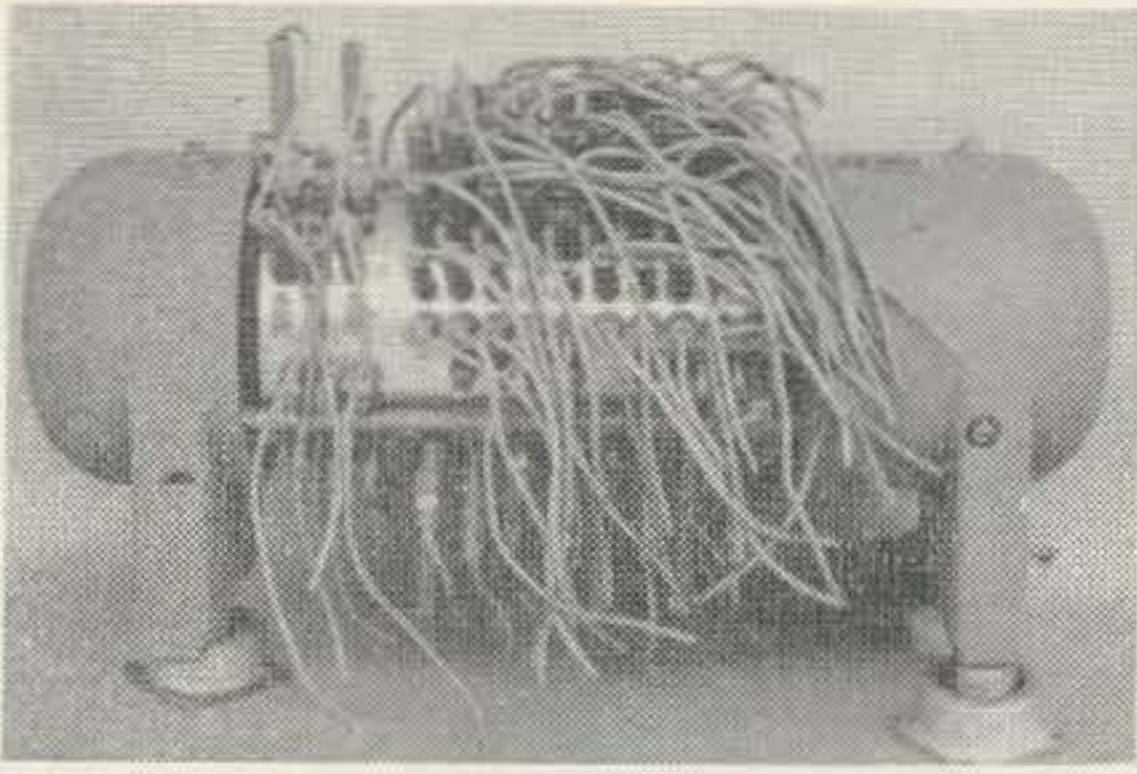

UNIVAC MAGNETIC STORAGE DRUM

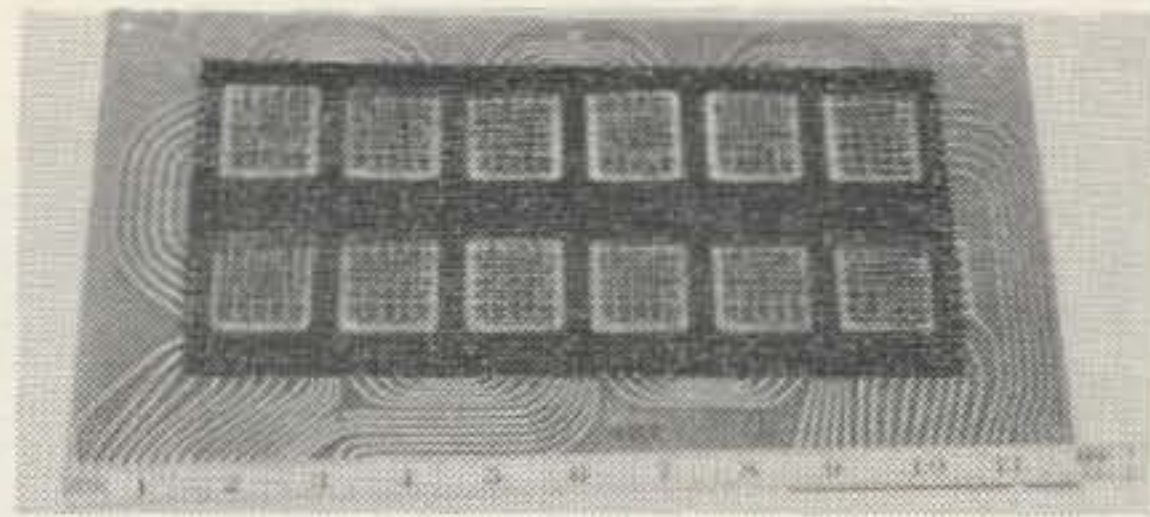Removed from equipment, approx. 100 heads, most have mating plugs attached. Motor drive 12,000 RPM, 3 phase AC 115 volt 420 cycle. Overall approx. 19 inches. Only a few available. **\$100.00**



UNIVAC WIRED MEMORY PLANES

As shown, each section on plane 10x12 cores with 12 sections to the plane for a total of 1,440 cores. All wiring to the cores terminated by printed circuitry to two sets of printed circuit contacts. Excellent condition, fully guaranteed. 12 inches wide.

\$12.00 frame, 10 for \$100.00

nuArc ARC LAMP for negative making, offset plate making, or printed circuit work. Model N-110 original cost \$550.00. Slightly used, good shape. Light intensity 7,200 foot candles at 3 feet. Color temp. 7,000° K. Spec sheet available fully detailed with picture. Ideal for photographic printed circuit work. **\$150.00**

TRANSISTRON TRANSISTOR BONANZA

An exceptional assortment of Transistron factory marked material. Most of these sell for over \$6.00 each. Your choice of the following at only **75c** each or **\$7.50** the dozen. Fully marked with 2N numbers, long leads. All listed are 2N numbers, we left off the 2N to save space.

339 - 340 - 341 - 342 - 343 - 497 - 498 - 547 - 549 - 550 - 551 - 552 - 706 - 728 - 729 - 735 - 736 - 740 - 754 - 755 - 839 - 840 - 841 - 842 - 843 - 844 - 845 - 1055 - 1116 - 1140 - 1206 - 1207 - 2040 - 2041 - 2427

MESHNA

19 ALLERTON ST., LYNN, MASS.

Meshna's new Spring catalog now ready. Send 20c for yours before they are all gone.

All Material F.O.B. Lynn, Mass.

without the plate load is, of course, done intentionally in order to *find* the feedback. With the over 20 db gain, this means that one microvolt coming back to the grid circuit (supposedly grounded) can produce over 100 microvolts in the plate, etc., etc. The remedy was to strap over all the grids. Better, of course, is a thin UHF socket.

The results with this amplifier were worth the effort. A good tuning range is obtained with (for this frequency) a large "store-bought" parallel tuning capacitor, running

from under 400 megacycles to over 475. This can be trimmed later if you wish. No oscillation occurs, even with the over 20 db gain. The nice thing about this much gain is that you can throw away some by overcoupling the output circuit if you want to, for greater bandwidth. Co does this. Co is a small copper tab about 1/2 inch long soldered directly to the output jack center conductor. It lies flat against L1, which has Teflon tape over it at this point, and can be bent closer or further from L1 as needed. This adjustment depends on mixer loading, cable, etc.

The high Q of this circuit should keep out lots of unwanted signals. Don't forget 70 more Tee Vee channels are coming up! And all of them *above* 432!

The plate return or B plus bypassing, has now become a "science" here. A thin brass plate about 3/4 inch by one inch is bolted onto the wall, with Teflon between. Then four 1000 mmfd discs are soldered on. These must be the smallest you can get that will take 250 volts, and the leads must be about 1/16 of an inch long. No more!

Just a reminder here of another tube choice, the 6AN4 job, also in 73 Mag. So now you have a choice of three amplifiers for 432. Solid state ones being written up also. More coming. . . . KICLL

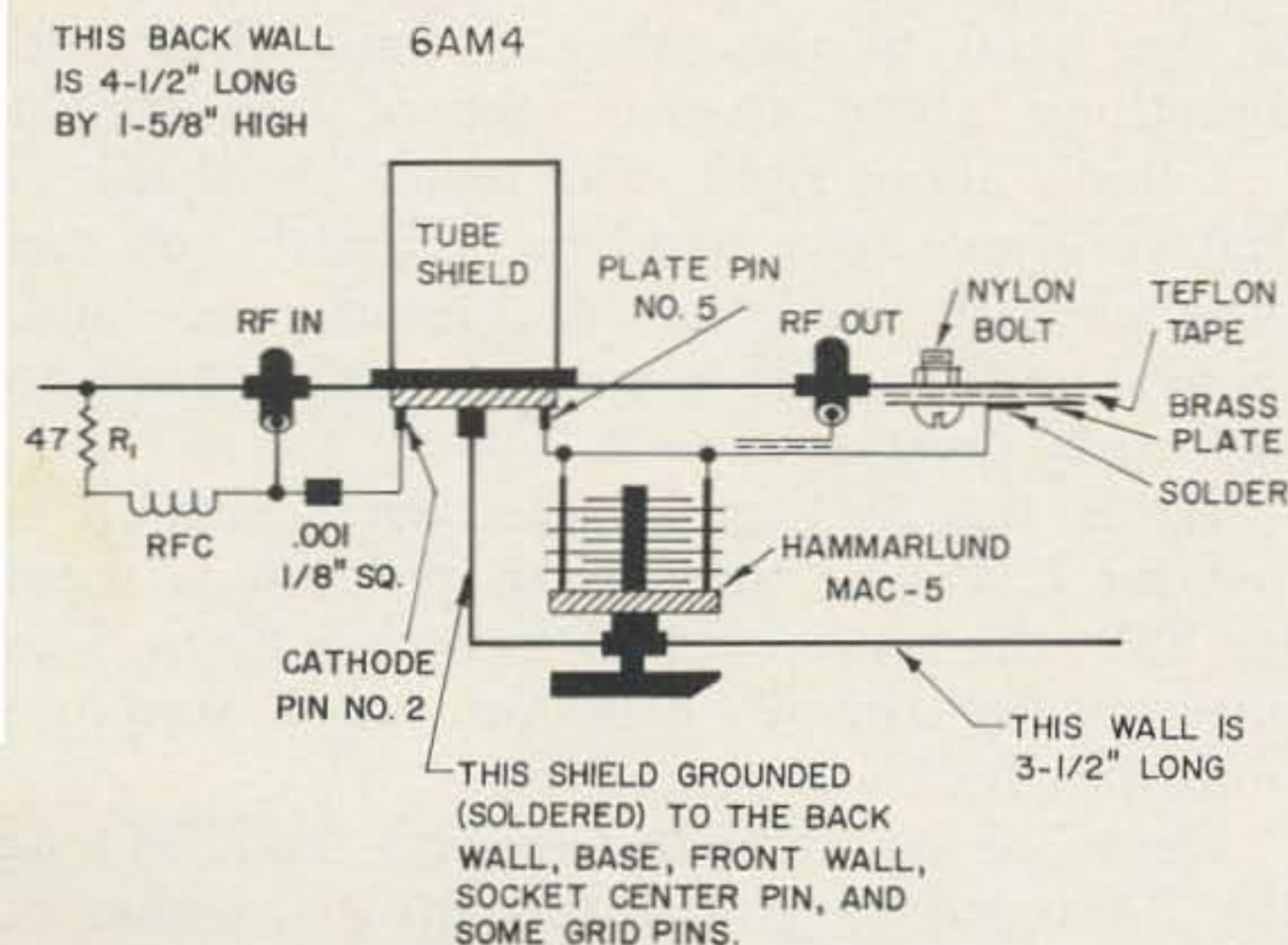


Fig. 2—Top view, 6AM4 high gain wide range 432 mc Amplifier



The National HRO-500

Wayne Green W2NSD/1

Perhaps I'm not the best person in the world to test something as expensive as this. When the original HRO came out some thirty-odd years ago I looked at it with awe and longing. By the time I finally could afford one they were just a little out of date . . . about two years ago.

But here I sit, through the kindness of National, with an HRO-500. True, it has to go back, but in the interim I will be able to mention to a few hundred fellows quite casually that, yes, I'm using the 500 here.

The more I use the 500 the more convinced I am that all ham receivers will eventually have to adopt the one kc per division type of tuning. The old HRO had that on some bands . . . as did the NC-101, and it is awfully easy to get used to. Collins cottoned on to this idea too.

The 500, being transistorized, snaps on immediately when you flick the switch. I like that. It gets me on the air a lot more than when I have to turn on my receiver and wait for it to warm up so I can hear what is happening. Perhaps I am more impatient than most people. Of course not only is the warm up period almost instantaneous, so is the warm up drift period. Brings to mind my old SX-28, which used to drift about 50 kc on 20 meters as it warmed up to its task. When I remember that, I guess I'm not quite as furious over the garbage eating W2 that borrowed it one day and proceeded to sell it and pocket the money.

The general coverage receivers that I've used

in the past were never quite adequate for optimum ham band usage . . . the 500, which tunes continuously from 5 kc to 30 mc, seems to sacrifice nothing for this flexibility.

The most unusual aspect of the 500 is the frequency synthesizer which permits you to tune any 500 kc segment of the five band-switching bands. The basic bands are:
0-1.5 mc; 1.5-4.0 mc; 4.0-10 mc; 10-20 mc;
20-30 mc.

As you tune the synthesizer the first numbers of the frequency you are tuning light up over the dial. The PW dial is calibrated to one kc and the 10 kc readings are indicated in the PW windows. By the way, one turn of the outside PW knob equals 10 kc, which makes tuning in QRM a snap, though it gives you a bit of a workout when you swing from one end of the band to the other. I think they said something about twelve feet of bandspread . . . that's about right. The result of all this is that you have sixty bandspread bands you can tune, all with one kc per dial division . . . and, thanks to the synthesizer, you don't have to have sixty crystals to do it.

While the 500 cycle selectivity position is fine for CW and the 2.5 kc position is great for SSB, the receiver does have a 5 kc to 8 kc position for "hi fi" listening or, I suppose, multiplex RTTY or something.

Those of you who have used the 75A4 or the 2A receivers will appreciate the value of the passband tuning on the 500. This is wonderful for SSB and CW work where QRM is a

problem . . . something not altogether foreign to our amateur bands. Another handy gadget when the interference piles up is the "Rejection Tune" control which swings a deep notch (50 db) across the passband for you, removing heterodynes.

The Automatic Gain Control system keeps the output steady within less than 10 db with a variation in input of from 5 to 50,000 microvolts: There is also an adjustment for matching the action of this circuit to various levels of background noise.


The S-meter is calibrated accurately. Who knows what will happen to us when we can believe S-meters. Imagine the impact on DX stations when you tell them what their signal strength really is! I've been doing this and for some strange reason many of them have taken a second look at their S-meters and lowered my signal reports. Hmmm. Honesty is the best policy and the 500 is honest.

Another nice feature of this receiver is that it will operate directly from a 12 volt source if you want to use it in the car or on a trip. The 100 ma that it draws doesn't even strain a small lantern battery . . . imagine, you can get far away from all line noise and hear what a radio should really sound like.

Oh, there are a lot more interesting features on the 500, but if you go out and spend \$1300 on a receiver you certainly want to have a few surprises waiting for you.

I dunno who is responsible for making the PRO-500 look so good, but they should get a raise.

. . . W2NSD/1

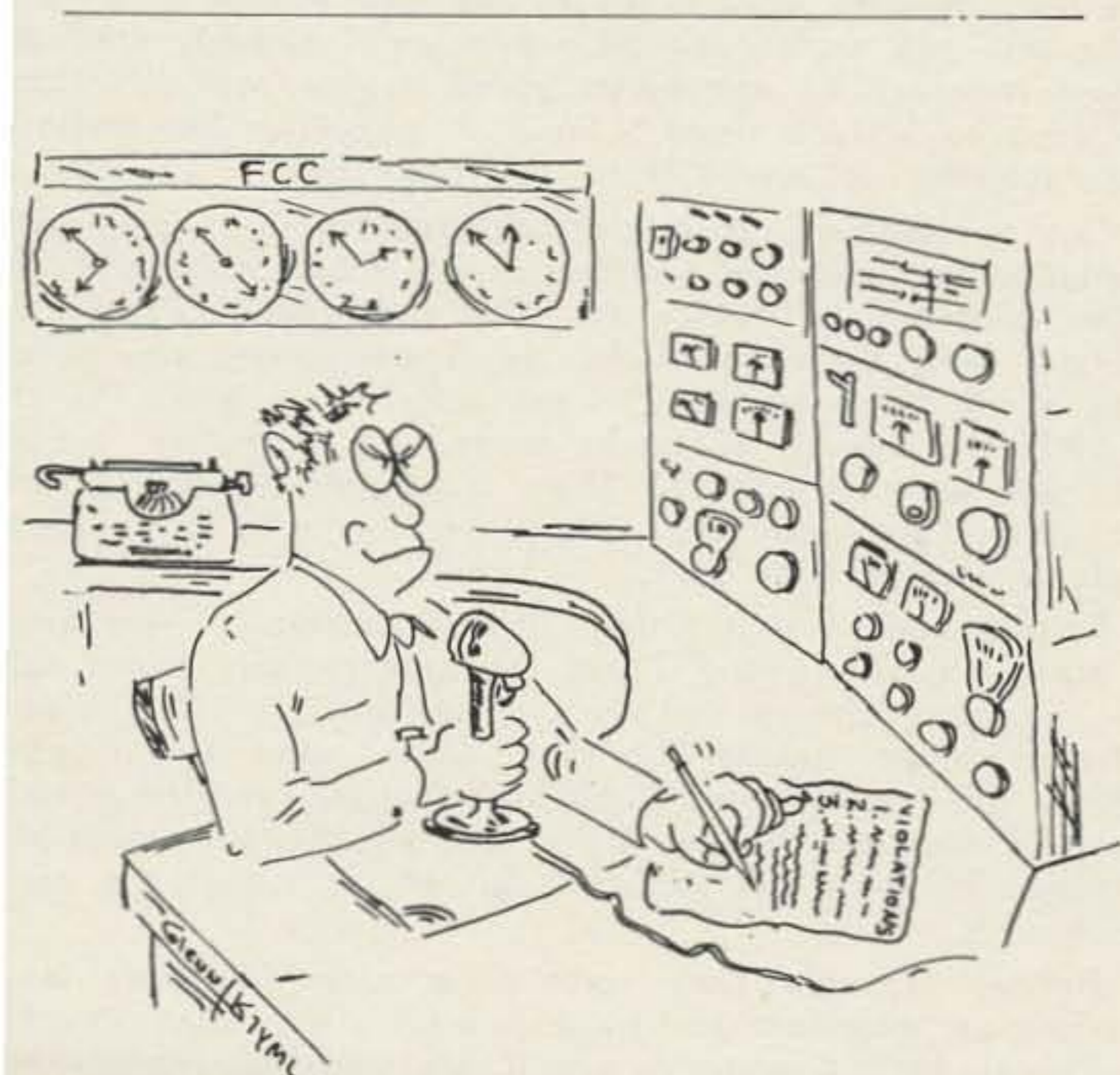


"OK on this being your 496th skip contact on CB, OM. We do QSL . . . as a matter of fact, I'm making out a card for you right now"

BUDDY NUVISTOR PRE-AMP

2M - \$9.95 6M - \$8.95

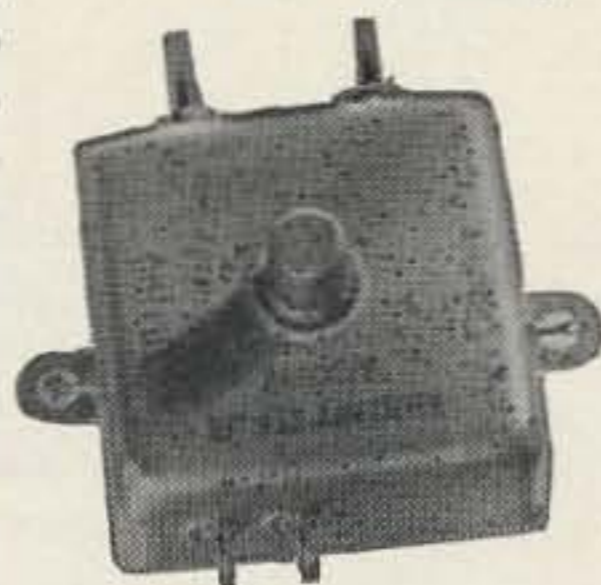
- ★ Increases sensitivity up to 20 db.
- ★ Small size 2 x 2 7/8" fits anywhere
- ★ Completely wired and assembled



- ★ Reduces images
- ★ Improves selectivity
- ★ Simply installed
- ★ CB model \$7.95

Autronics Corporation
180 North Vinedo Avenue
Pasadena, California

HYE-QUE ANTENNA-FEEDLINE CONNECTOR

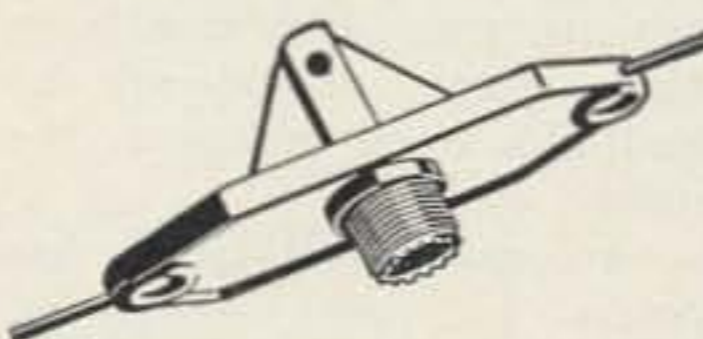

New 3-in-1 molded plastic-and-metal fitting provides: coax feeder connection, heavy copper leads to elements, antenna center support. Hye-Que I Connector fits standard PL259. Reinforced, weather protected, ultra-efficient. At your ham store, or \$2.95 ppd. Companion insulators, 2 for 99¢ ppd. Includes complete instructions.

BUDWIG MFG. CO., P.O. Box 97, Ramona, Calif. 92065

TWO-WAY COMMUNICATION CRYSTALS

AMERICAN CRYSTAL CO.
PO BOX 2366 KANSAS CITY, MO.

ARROW SPECIALS

Panadapter—IP69C/ALA2. See June 1964 issue of 73.

New with tubes \$22.50
Used with tubes \$17.50

Collins—Single Side Band multiplex generator using mechanical filter F84Z-2 or similar. With schematic and data. \$22.50

APX6—Transponder for 1215 mc. Excellent less tubes. 40#. \$7.95

2C39A—Tripler cavity—less tube. \$3.95
2500—Cavity tuner for IB40, IB43 and IB37. New, less tubes. \$3.95
416B—Cavity complete with 416B tube. \$12.95

Nicad Batteries

1.2 v-4 amp hour capacity. \$1.49 per cell.
Battery of 24 per above in metal container \$31.00
1.25 v-20 amp hour capacity. \$3.75 per cell.

Silicon Controlled rectifier GEC40B. 25 amp. \$3.95
Silicon top hat. 600 piv-200 ma. \$.39
Selenium rectifier. 30 v-1 amp. \$.49
Selenium rectifier. 52 v-2 amp. \$1.79
Diodes—assorted—all new. 10 for \$1.50

LM—Frequency Meter 125 to 20000 Kc—Complete with original Calibration Book in excellent condition. \$47.50

ARROW SALES-CHICAGO, INC.

2534 S. MICHIGAN AVENUE
CHICAGO 16, ILLINOIS
Send for Catalog #131—FREE—

advised by my lawyers that
don't you ever proofread y
are a bunch of crooks and
Letters
this is the last straw for
have no other recourse but
should be tarred and feath

Dear Wayne:

In reference to the June issue of the 73 magazine, Letters, portion, many of us of the Yakima Amateur Radio Club, have read the letter from the person who calls himself the Yakima Ham, and wish to state the following:

First, a person who uses such words as hell, you nut, and etc., apparently does not have any other way to express himself.

Second, we feel sure that the said letter would never have been approved by the club, while we may or may not agree with statements you have made in the past.

Third, we strongly feel that anyone who does not have the decency to sign his name to a letter, should not be allowed to have the letter published. As, even in court, the one has the right to face his accuser.

Fourth, to our knowledge, no so called CHECK has been made on your so called charges.

Garrett Derrey W7ZMS, Pres.
Yakima Amateur Radio Club

P.S. This letter has been read and approved by the Board of Directors of the Yakima Amateur Radio Club.

1. Hell nut, etc., are expressive. 2. Thank you. 3. Signed or unsigned the chap who sent the letter has a view which should be considered. 4. Check the "charges" and see if I'm lying. Many others have verified every statement that I have made.

Dear Wayne:

I just don't understand how a person that can put out such a wonderful technical magazine can be so far off base in the field of amateur radio politics! Referring to your June editorial I can agree with only a very few of the points you are trying to make. I do not feel out of line in making these statements because in all my conversations with other hams the majority of them feel the same—i.e., that you are some kind of nut!!

At a recent club meeting there were over 85 members present and Docket 15928 was discussed. There was no hostility to it at all. With two exceptions most people appeared to accept it. The Call Letter changes and Advance Class Downgrading were the only exceptions. They didn't feel like the ARRL had pulled any kind of swindle. From monitoring many QSO's here on the West Coast I get the impression that the greatest majority of the people feel the same way.

Now the question is—are we out here on the West Coast getting an incorrect picture of the overall opinion—or are you indeed "some kind of nut"?

I certainly don't like you to be the spokesman for the group if you are not reflecting the true picture.

Please take stock of this thing again, are you just trying to sell magazines or are you truly doing the best thing for amateur radio?

Ed Munsell W6PCP
Los Angeles, California

Dear Wayne:

I would like to see you champion some CW privileges on one or more of the low bands for Technicians. It seems to me this goes along with increasing the Novice to two years and incentive licensing. Despite the FCC's intent, the Technician license has become an intermediate step to the General. Now it is extremely difficult to improve one's CW (on the air) on the VHF frequencies alone.

John Ott K9AHX
Lafayette, Indiana

John, when someone comes up with a good reason why we should continue the CW test, I might go along with you.

Dear Wayne,

Got to looking at ARRL/QST leadoff idiotorial in April QST. This is probably their April fool item. It does not flatter those that read it. Like "In fact, by the power of his ballot, the member can require that his representative take the time and make the effort to become adequately informed as to membership needs and desires."

Like Mort Kahn didn't do for the last few years of his directorship, maybe?

Wonder what you can make out of this:—I wrote Dick Baldwin some time ago and getting a reply was startled to note that he was now "Assistant General Manager." This got me to thinking . . . went thru QST's back to mid year of 63 (I think) and he was still listed in QST as Editor, but not A.G.M. for June QST of said year (June mag going to press sometime in mid-May I reckon) . . . but looking thru later issues found that the switcheroo took place in 2nd half of said year . . . got to looking up the minutes of ARRL Bored of Directors, also Executive Committee minutes (as reported in Q-ST) but no information. Looked up all notes about changes in staff (Parenthetical thought: did you ever notice that they tell of upward changes in their staff, but seldom if ever tell that Joe Blough left to go to work elsewhere?)

Anyway, I looked all around in those "Happenings of the month" and while they reported about some office-clerk going up by half-a-notch, no news about Dick Baldwin and his elevation to AGM. I responded to DB's letter by the way & offered up congrats upon his elevation to heir-apparent status & asked "when did it happen?" but he was mum about this 110%. Hmmm . . . I wonder . . .

Wrote to League a month ago. Said please send annual report (copy or summary) so I can see how we're doing. Got reply as follows: "Dear OM: Enclosed is our statement for 1963. The 1964 one is now in the works, but won't be available until after the annual meeting of the ARRL Board of Directors in May, 73, Gary L. Foskett, W1ECH Assistant Secretary" I responded last week, but I felt that maybe you could put the thought to greater function. I commented, in effect: Thanks, but I still would appreciate a copy of the 1964 annual report. . . . I own stocks in a couple small corporations, belong to a couple of fraternal & charitable organizations, etc. and they all depend upon my interest and confidence in their operations for my continued support. With annual reports coming out in June (After B o D annual meeting & approval, plus trip to printers) when everybody's thinking of vacation, how can the typical Joe Blow League member think intelligently with 6 month old information (even if bona-fide)?? In short, how can the guys in the League tell the Directors what to do in the year ahead, if the HQ gang says you can't have 64 report until mid-65, after the Board meeting? In newspaper game, saying sez: "Nothing so dead as YDA's news." So . . . get your hot rreports here fellows, get em 150 to 180 days old!!

Got to thinking, it might be advisable for some righteous-looking member to inquire of ARRL, "Kin I see your contribution books for the new Bldg Fund?" I wonder who these wonderful gentlemen were who promised to pony-up on the 2-for-1 offer. You know, if the ARRL put up 10 K bucks more, the "mystery donor" will put up another 10K. Who could the mystery donors (mystery sponsors) be?? They say he who pays piper calls honorable tune . . .


Firmly believe that your editorial balance is very good I sense (maybe wrong) that the average guy won't take too heavy a diet of criticism, even tho it's 100% right. That's human nature for you. Look what the English people did for Winston Churchill. He did everything right most of the time during WW2, but the British voters still "turned him out" at the polls in '46, or rather the party he headed. Hi.

Believe strongly that your main rock-of-support is in having an excellent technical journal . . . keep the FE technical stuff flowing & you'll see that the readers will not object to your continual fault-pointing!


I apprehend—from reading between the lines—that this must have been your decision already. . . .

Neil Johnson W20LU
Tappan, New York

TS 418A 400-1000 meg signal generators, AM, PM or CW emission	\$325.00
Baird Atomic 162 Glow transfer counters	\$100.00
Ballantine 300 Voltmeter	\$60.00
Millivac MV-17C Voltmeter 1mv-1000V	\$75.00
Dumont 304A scope with 264B voltage calibrator	\$100.00
Lambda C-281M 125-325 v, 200 ma	\$60.00
Lambda C-481M 125-325 v, 400 ma	95.00
Lambda C-881M 125-325 v, 800 ma	125.00
Electronic Measurements 235AM 0-600 v, 0-500 ma	225.00
Electronic Measurements 234AM 0-300 v, 0-500 ma	125.00
Electronic Measurements 204AB 0-500 v, 0-300 ma	100.00
DuMont 404 Pulse Generator 0.05-105 microsec	175.00
RCA WV 84A DC Microammeter without batteries	\$30.00

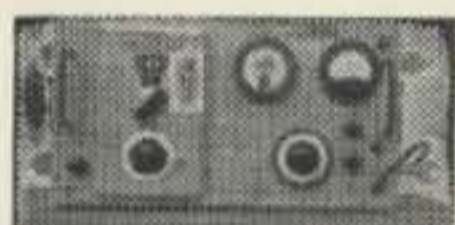

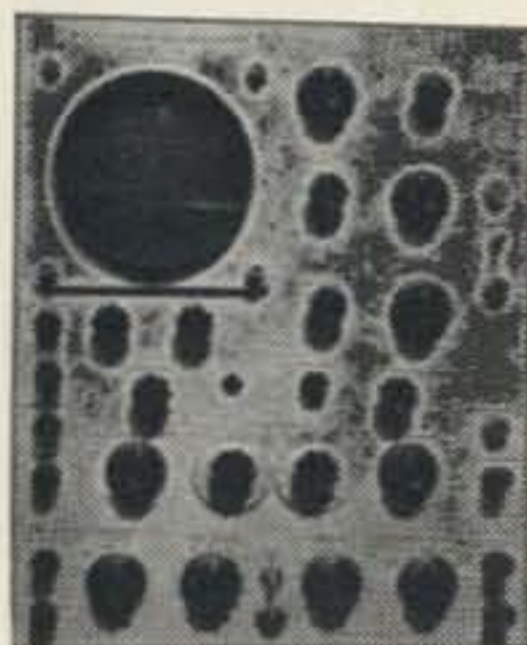TS-497B 2-400 Meg Signal Generator with manual \$225.00



Tektronix 514D Scopes \$275.00

All equipment used and surplus, in good condition.

Orders FOB Cambridge, Mass.

Sorry we do not issue catalogs or lists

ELI HEFFRON & SONS, INC.

321-329 ELM STREET

CAMBRIDGE 39, MASS.

EL 4-8572

ARRL VHF Manual

I just received a long awaited copy of the ARRL *Radio Amateur's V.H.F. Manual* by Ed Tilton W1HDQ. It's quite a bargain—over 325 pages for only \$2. The book is written particularly for beginners, so it's perfectly understandable, but contains plenty of interest to the most advanced VHF ham as well. The first part of the book gives a brief history of VHF hamming and a discussion of the capabilities of the VHF bands. Then chapters are devoted to theory and practical construction of receivers, converters, preamps, transmitters, antennas, test equipment, etc. Most of the projects and information in the book are adapted from *QST* articles (In fact, the extensive bibliography doesn't even hint that other electronics magazines exist), but many of the projects are new and interesting. I have a few small criticisms, such as the scarcity of transistor projects and the great amount of space devoted to condensation of the recent *QST* articles on UHF pulse systems in contrast to nothing practical on the simple duplex system that is more likely to appeal to beginners. Antennas seems to be shortchanged, but the *73 VHF Antenna Handbook* will take care of that for you.

But these are minor criticisms. All in all, it's an excellent book and one that every VHF'er

and prospective VHF'er will want to have. The newcomer will find that it contains a tremendous amount of practical information. The old-time will find some new projects, valuable reference and lots of opinions to argue about in time-honored ham fashion.

... WA1CCH



"... and dear, Rodney's been the best little boy. He went into your hamshack three hours ago to play and I haven't heard a peep from him since."

Letter from Gus

Bhutan, June 13, 1965

This is being written on my last day in Bhutan. During the past 5 months I have been into ALL the AC areas. I have had (without counting them exactly) over 30,000 QSO's on this trip, over 5,000 from AC3 and about that same number from AC4. Over 2,500 QSO's from each AC spot. If anyone needed AC spots for a new one I surely hope that they have worked me by now. With the total of something like 20,000 or so QSO on my first stop here a few years ago, the total is now something like 50,000 QSO's from AC lands. I believe I have had more QSO's from AC land than I have had from W4BPD!

I want to tell you of operating here. This is certainly the hardest spot in the world to work the USA. W4 this time was the hardest place to QSO, W8 was second hardest, then the rest (starting with the easiest): W6, W7, VE8, VE7, W2, W1, W3, VE2 and 3, W5, W9, W0. It was not due to the fact that I was not on the air, you can bet your last buck I was there trying my very best to open up the band. Every day I was on starting at 2300 until 0330, then again at 1100 until 1830 GMT or until the band folded up completely. Boys, it was not ME, it was conditions. I tried my very best to dodge what QRM I could. Those commercial RTTY stations on 14035 and 14065 caused me lots of trouble but I would try and sneak as close to them as possible, usually just below them a kc or two. On this portion of my trip I was stuck with transceive. I altered a transceiver here by adding a small trimmer condenser to it so I could tune about 12 kc below my operating frequency. It worked fairly well, but was NG to work the boys in the USA ssb portion. I did have an old beat-up BC-348 that I had pepped up somewhat and this was used when I worked the ssb boys. The best frequency seemed to be around 14101 or another fair frequency towards the end of my stay was around 14135 to 14140 kc. During the past week or so I have had to stop trying to work the USA boys on ssb because the power transformer went up in smoke in the BC-348. I have found that this 50 cycles gives a regular power transformer a fit. I suppose if the rig I were using was operated as a regular ham would operate it, maybe 3 or 4 hours each day, it would be all OK for a long time. But when you operate each day 4 to 5 hours in the morning and then again 9 to 10 hours every night, and 50 cycles (maybe even 40 cycles—they do this to conserve petrol) then you can expect things really to heat up—and brother they DO. After the first 2 hours you can't hold your hand on the power transformer—I don't see how it takes it. Of course, I turn the rig off everytime I get a chance, even when I say QWC one boys, or gas in putt-putt, or chow time. If turning it off these few minutes cooled it down I certainly could not feel the difference BUT theoretically it should—so I did it every chance. Maybe the one in this rig is fire proof! You should see this poor old Hy Gain model 14AVQ antenna I have. The boys out in Lincoln, Nebraska made this one up specially for me, the maximum length of any portion of it is about 3 feet, with every section slipping into the next section. The spot to stop at on each section was marked with a Markall. This one now has gone up and down I suppose 20 or more times. It's been mounted many different ways, on many different supports: it's had a real beating, let me tell you. Usually the support is a big bamboo pole about 60 or more feet high. These bamboos when they are green are quite heavy. The people who help me put it up usually cannot speak English, they have had no experience at all in putting up or taking down poles, so about 25% of the time they will let the pole get out of control, especially while taking it down, and then it's slam-bang and the whole works flat on the ground. It's murder to the antenna: it's been bent (a few that will never come out), the traps are pushed in: in other words, it's a MESS, the darn thing still works FB and the SWR is still very, very low. It works a lot better than it looks.

Something I just cannot understand is why at almost every place I operated that it's very easy to work the W2 boys. If you take a map of the world and look at it and place a circle around W2 area and another around the AC area all you have is two small dots on a map. Can anyone explain to me why it was possible to have QSO's

with just this W2 area without any difficulty at all, practically every day? Do you think maybe that the W2 boys have a better organized group to hunt the DX and a better system to alert them to the fact that DX is on and coming through on such and such a frequency?

On this trip into the AC lands I got to know the people a lot better and really saw the country. They have lots of strange customs up there. What do you think of trying to chase evil spirits or devils out of a power plant by burning yak butter lamps in each corner of the room: burning all kinds of very bad smelling things all around the power plant and then pounding on the plant itself, then praying to it, sprawling out flat on the floor? Well I have seen this done and many many more such things are done in AC lands. This applies to transmitters and receivers also. After seeing and hearing of such things they begin to get you down and it looks like a lost battle when you are doing your very best to assist them in getting things repaired and in good working condition.

I found a few very fine spots to operate from up there. Take AC8 area. You come into a big wide valley that's about 5 miles wide. Right in its middle there is a hill about 2,500 ft. high with no trees on top at all. You climb up there and then pull out your compass and BOY oh BOY the valley runs exactly NORTH and SOUTH, which is in the exact direction for the USA, either by Short Path or Long Path. There are any number of spots here and there you come across. Well, it's 9N1MM land next fellows, and after that, plans are not definite yet. Sure hope to work you all from every spot even if you don't need it for a NEW ONE! I like lots of QSO's!

. . . Gus

VHF

Bill Smith K CER
1301 Churchill Ave
Sioux Falls, S. D.

Last month I said that we would look at circular polarized antennas this month. Unfortunately, a heavy work load and never-ending weekend rains have prevented raising the antennas. Will try again next month.

From my participation in the ARRL June VHF contest, it seems that six meters was open for all areas of the country, far different from last year. There should be some excellent scores.

Tropospheric conditions are finally starting to come around in the midwest. The large stationary front which brought rain and devastation by flood waters in Colorado during the third week of June led to the first tropo opening in the midwest since January sixth. Stations in South Dakota and Minnesota worked south to Texas, east to Arkansas and all points in between. K5WXZ, W5AJG and W5JWL put good two meter signals into the upper midwest boosting states-worked totals. The signal levels were not especially strong but they were in for parts of three days. Better start watching the stationary fronts from now until late September.

Sam and Helen Harris (W1BU, W1FZJ, W1HOY) have moved to Arecibo, Puerto Rico, where Sam will be working with the 1000 foot reflector. KP4BPZ was to have been active on 432 mc moonbounce July 3. Another test is scheduled for July 24 beginning at 1110 GMT with a two minute CW CQ on 432.000 mc. The test will last for just over two hours with calls being accepted between 432.010 and 432.1000. SSB may also be tried. No two meter operation is planned. Sam said here in Sioux Falls during the April meeting that he doubted that KP4BPZ would operate on two because of the inconvenience in moving equipment, etc.

On the west coast W6DNG is continuing his 144 mc EME (Earth-Moon-Earth) skeds with OH1NL and UA1DZ. Several of the west coast gang have reported hearing the UA1 calling Bill.

More reports on Oscar III have been received. Oscar is still sending back HI's erratically as the beacon goes on and off depending on the charge of the solar cells. The Oscar Association still would like your report if you haven't sent it in.

W1QKA and W1DUB in Nashua, N. H., have been running some interesting tests on 2415 mc. They are three miles apart, but have been bouncing CW pulses signals

off Pack Monadnock Mountain (2310 feet) for a 48 mile total path. W1QKA says that the signals were about 30 db above the noise using modified APG-5's (2C43 oscillator) into four foot dishes at both ends. Both also used superhets with 1N21F mixers, 6CW4 cascode if preamps, modified APG-5 local oscillators, four stage 6AK5 if amplifiers and threshold detectors a la K1 JIX.

Don't forget to send in your reports on interesting activities.

... KØCER



SEMICONDUCTORS

Paul Franson WA1CCH
Peterborough, N. H.

As promised last month, here is a quick look at the most common parameters that transistor manufacturers use in rating their transistors:

The maximum voltage that can be applied between elements of a transistor without risk of damage (breakdown voltage):

BV_{CE} Collector to emitter with the base open (not connected to anything). Sometimes called BV_{CEO}.

BV_{CES} Collector to emitter with base shorted to the emitter.

BV_{CER} Collector to emitter with a resistor connected from base to emitter.

BV_{CB} Collector to base. Sometimes called BV_{CBO}.

BV_{EB} Maximum reverse voltage from emitter to base. The *B* standing for breakdown is often omitted if there is no possibility for confusion in specifications.

I_C Collector current.

P_T Total transistor power dissipation.

I_{CBO} Current leakage between collector and base with the emitter open.

f_{ab} Frequency at which gain in common base configuration drops to 70.7% of that at a low frequency (usually 1 c.)

f_T Gain-bandwidth product. Frequency at which the current gain drops to one, i.e. no longer amplifies.

f_{MAX} Maximum frequency at which the transistor oscillates.

Some of these can be a bit tricky unless you know how to interpret them. Your best bet is to use the specification sheets that you can get from the manufacturer or distributor. These spec sheets give typical circuits, noise figure, possible gain, power outputs, etc., depending on the use the transistor is tended for.

A new RCA transistor of considerable interest is the 2N3866. It's a silicon NPN triple-diffused planar transistor which provides considerable power output at VHF and UHF with a reasonable price. It will put out as much as two watts on two, and one on 432. Even more important, one watt is possible on two with 18 db of gain. On 432, gain is about 9 db for one watt out. V_{CE} is 55 volts, and the 2N3866 is ok for automobile AM service, though it's cutting it close. P_T is five watts. Price is only \$4.95 apiece, considerably less than previous transistors with these specs. Write RCA Electronic Components and Devices, Commercial Engineering, Section 738, Harrison, N. J., for spec sheets on the 2N3866. May as well get them on the 2N3478 while you're at it.

... WA1CCH

INCENTIVATE!

Subscribe to 73 — \$4 a year from 73, Peterborough, N. H.

Model 14 Transmitter Distributor with synchronous motor, slide base and two instruction books. Brand new in original case. \$70
Also model 14 typing reperforators synchronous motors or model 28, power supplies, etc. Send for free catalog.

ATLANTIC SURPLUS SALES

250 COLUMBIA STREET
BROOKLYN, N. Y. 11231
PHONE 212-855-7607

AMERICAN
MADE

TRANSISTORS


WHILE LIMITED
QUANTITY LASTS



4¢

SPECIAL LOW PRICE ONLY

Each

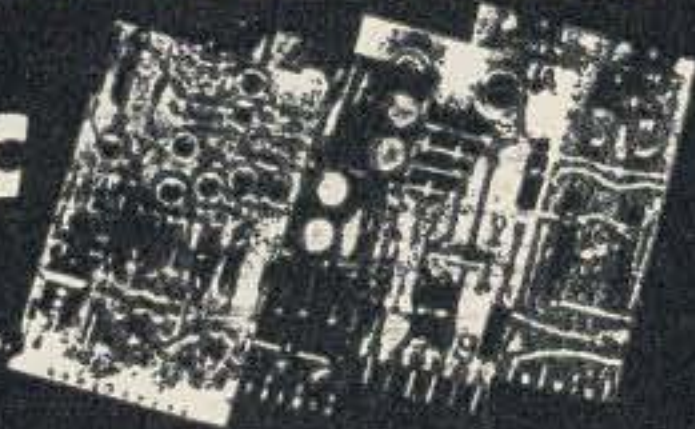

A fortunate purchase allows us to offer these high priced computer grade transistors at such ridiculously low prices. All are mounted on printed circuit boards, along with assorted components such as resistors, capacitors and a host of other surprises. You pay only for the transistors, other parts are FREE!

BUY 100 FOR \$4.00 or 1000 FOR \$35.00 PREPAID

... NOW TAKE ADVANTAGE OF THIS SPECIAL PRICE

SEND YOUR ORDERS TO **ALCO** LAWRENCE, MASS.

VHF-UHF

Converters and Preamps for 50 thru 432 Mc.
Write for literature.

Send for a sample copy of the VHF'er, the only magazine for VHF and UHF hams.
Parks Electronics, Rt. 2, Beaverton, Oregon

OUR GOAL: TO HELP YOU BUILD A TV CAMERA!!
(For less than \$40)

Enjoy the fun of building your own LIVE TV camera. Most of the components can be found right in your own junkbox. We furnish only the hard-to-locate parts and easy-to-follow construction plans. INTERESTED?? Send 10¢ for more info.

Box 396 ATV RESEARCH So. Sioux City, Nebr.



CALL-LETTER SIGNS

Order your call in neat 2-inch die cut letters with base. Just right for the shack. You assemble — Letters: 3/32" silver showcard stock. Base: Satin finish black plastic.

Price \$1.50 postpaid

GIFT SHOP

Box 73

Northfield, Ohio 44067

R.W. AUGUST BARGAINS

LM-21 FREQUENCY METER—Late type, Reconditioned & Recalibrated. With crystal, New Calibration book & power plug. \$95.00

OIL CAPACITOR—For KW Power Supply 25MFD; Westinghouse, Inerteen filled; Rated 2500vDC, Will handle 4000vDC at lamp safely & up to 5000vDC at lamp or less in an emergency. Ship wt. 32 lbs. BRAND NEW \$12.95

BC-1366 CONTROL BOX—Die cast case 5 3/8" x 3" x 27" with phone & mike jacks, vol. control & rotary switch. New 59c each 4/\$2.00

BC-454 VARIABLE CAPACITOR—Three Gang, 25-147mmf. per section with geared drive. BRAND NEW \$1.95

902A CRT 2"—Takes octal socket, 6.3v Fil & up to 500vDC Max. Only 7 1/4" long. Xint for Rtty or modulation monitor. BRAND NEW \$3.95

MOTOROLA CRYSTAL OVEN—Takes one crystal in HC-6/U holder. Operates on 12vDC. Used good. \$1.50

MOTOROLA 2M WB FM MOBILE TRANSCEIVER—144-174MC 10-15 Watts. FMTRU-40V. 12vDC Used good less vibrators. \$39.95

WRITE FOR BULLETIN #42—LOADS OF BARGAINS

Send check or money order—Minimum order \$2.50
PLEASE INCLUDE AMPLE POSTAGE—Excess refunded
Minimum C.O.D. order \$10.00 with 25% Deposit

R. W. ELECTRONICS, INC.

2244 South Michigan Ave.
Chicago, Illinois 60616

Dept. 738
Phone CALumet 5-1281

Continued from p. 4.

that jazz you should ask around a little bit. Perhaps I am more in touch with this than many of you, being an editor, but surely you know that the first working parametric amplifier in the world was built by W1FZJ on six meters. Read Scientific American . . . or read the article I ran in CQ by Sam at the time. Everyone thought it was a humor article . . . imagine, a receiver using a UHF pump oscillator . . . how ridiculous. Another even more recent first was the K2TKN Flying Noise Lock receiver which was a breakthrough in under-the-noise detection. This was in 73 first. Many of K1CLL's UHF techniques are finding their way into commercial applications. The RTTY gang have advanced the design of converters considerably during the last few years and many of the current commercial designs are right out of 73.

When the ITU wanted to conduct a propagation study of the world who did they turn to for facts and reports? The hams, of course. By the way, if you'd like to help with this project just drop a letter to OK1WI, Propagation Study, ITU, Geneva 20, Switzerland.

Have I covered all of our so-called bad points? Isn't it about time that the League stopped poor-mouthing ham radio and spent some time and maybe even a little of our money in promoting us with the FCC? The FCC has no way to get a broad picture of ham radio . . . they get the TVI complaints . . . the petitions . . . the bickering letters . . . the grumbles. Sure, they read about our great work in Alaska. But they don't read about the hundreds of other public services that we accomplish. The FCC doesn't have a news clipping service to let them know all the things we are doing to help all over the country . . . they don't see the hundreds of reports that come into League HQ on our successes. Isn't it about time they got a truer picture of ham radio? Isn't it way past time?

Before we let the FCC make major changes in ham radio we should take the time to see just what is really necessary. Write to the FCC and ask them to extend the filing time on Docket 15928 until January 31, 1966. Let's have some time to work out our own future instead of plunging into massive call changes, new exams for everyone, 20 words per minute, wholesale changes in most of our bands, etc.

I make a motion that Herb Hoover find out what ham radio is like in this day and age and then that he go to Washington and visit the FCC Commissioners and staff and tell them what he has found so we can get out of the trouble we are in. Herb will get to know ham

radio by spending about a month on twenty and eighty meters, several hours a day, plus some time on six and two, and don't forget a little 160 and 40. Ten and fifteen probably won't be open much this summer. Now, about 1000 QSO's later, he should zip down to Serrana Bank with WA6WTD who has a license and is looking for company and taste DXing from the DX viewpoint for a few days. Next he should bone up on some technical topic and visit about ten ham clubs giving a technical talk . . . and not the usual apologies for 499 and viva ARRL speeches. Then he should try to grapple with the appliance operators as they pop technical questions at him. A one month subscription to a newspaper clipping service will round out his portfolio and he will be ready to answer every critical question the FCC can ask. By the time he is through 15928 will be in the wastebasket where it belongs.

Things Are Good

Lest we get too wrapped up in our little problems with the FCC that the League has visited upon us, a look at the prospects before us is in order. I think we will get our license problems straightened out all OK . . . so what's cooking elsewhere?

432 More and more activity on this band. The advent of low cost front end transistors will, I think, revolutionize this band. Converters that used to cost hundreds of dollars can now be surpassed with inexpensive simple units. I wouldn't be surprised to see some come commercially available for around \$20 soon. Add to this the removal of Mr. Moonbounce W1FZJ to Arecibo, which is like giving a kid a job in a candy factory, and I think 432 will be blossoming. The first skeds are for July 3rd and 24th . . . and there will probably be a lot more in the future. The day is here when anyone who wants to work Puerto Rico on 432 can make it using a simple transistor converter, a reasonably sized beam (say 100 elements) and a medium powered transmitter. Now if we could just get a few more ham with 1000 foot dishes around we could have a few more moon contacts.

144 Activity is quite high on this band and sideband activity is growing rapidly. The increasing sunspots will probably bring us a lot more aurora activity this year, which is a real ball on both CW and SSB. It does take a fair antenna for consistent results . . . sixteen elements or more, and 200 watts or better.

50 Tropo is going strong on six meter these days with openings almost every day. From up here in New Hampshire we can see


3-TRANSISTOR

AMPLIFIER

- Only 3"x2"x3/4"
- Printed circuit
- Wired, subminiature

\$1.00 EA.

PARTS by POUND

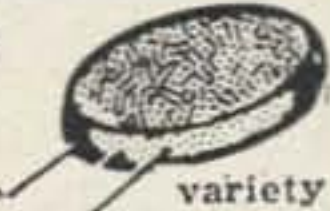

500-1000 pcs. **\$4.95** per pound

Worth \$85, NOW **\$4.95** per pound

ONE POUND Disc Condensers

DOUBLE BONUS

\$25

- WORTH OF
- Transistors
- Rectifiers
- Condensers
- Knobs, Coils
- Resistors
- Diodes, etc.

Add 25¢ for handling.

PLUS FREE

CHOOSE ANY **\$1.00** ITEM FREE



BOTH GIFT PAKS FREE WITH \$10 ORDERS

SUBMINIATURE RELAYS

Worth 22.45 **3**



for \$1

Actual Size

5 WATT SILICON MESA POWER TRANSISTOR

2N656 **4 \$1** For **1** TO-5



WORLD FAMOUS DOLLAR POLY PAKS

- 3 TRANSISTOR AUDIO AMP, tiny, wired\$1
- MAGNETIC REED SWITCH, glass sealed\$1
- 40 WORLD'S SMALLEST COND., to .05mf\$1
- 4 TRANSISTOR TRANSFORMERS, asst. worth \$25 \$1
- 1 FILAMENT TRANSFORMER, 117 to 6.3vct, 3A \$1
- \$25 RELAY SURPRISE, sealed, tiny types\$1
- 3 INFRA-RED DETECTORS, with leads\$1
- \$25 SURPRISE PAK: transistors, rect, diodes, etc.\$1
- 30 CORNING "LOW NOISE" resistors, asst. . . \$1
- 60 TUBULAR CONDENSERS, to .5mf, to 1Kv, asst \$1



WORLD FAMOUS DOLLAR POLY PAKS

- "MICRO-T" TRANSISTOR, like TMT-1613. \$1
- 4 2N35 TRANSISTORS, npn, by Sylvania, TO22 . \$1
- 4 "MICRO" TRANSISTORS, 2N131's, 1/16", rf \$1
- 4 CK721 TRANSISTORS, pnp, aluminum case . \$1
- 85 WATT 2N424 PLANAR, silicon, TO-53 npn, \$1
- 85 WATT 2N1212 PLANAR, drift, 10mc, npn\$1
- 1 CONTROLLED SCR SWITCH, Transiron, TO18. \$1
- 2/ 1AMP 1000 volt, RECTIFIERS, axial, leads. \$1
- 2 2N721 PNP PLANAR, 2W. 75MC, TO-18 . . . \$1
- 3 2N735 NPN MESA, 500MW, 135MC, TO-18 . \$1
- 2- CLAIREX PHOTO ELECTRIC CELL, CL607 . . \$1
- 2 500MC TRANS'TRS, 2N964, mesas, pnp, TO18 \$1
- 10 "PIN HEAD" TRANSISTORS, rf, if, no test. \$1
- 4 2N43 OUTPUT TRANSISTORS, by GE, pnp, TO5 \$1
- 4 2N333 NPN SILICON transistors, by GE, TO5 \$1
- 8, 2-6Amp RECT's, studs, silicon, 50 to 400V . \$1
- 10 1000 MC-1N251 GERMANIUM DIODES . . . \$1
- 5 30MC TRANSISTORS, like 2N247, Sylvania . \$1
- 4 -2N155 TRANSISTORS, or equals, TO3 cases \$1
- 2-800 MC, 2N709 NPN Silicon planar TO46 . . \$1
- 3 2N711 300MW. 300 MC, PNP MESA, TO18 . \$1
- 15 1AMP 200V epoxy rectifiers, made by Sylvania \$1

100's SOLD AT 4:95

TRANSISTORS

100 for **2⁹⁸**

POWER, RF, IF, AUDIO, SWITCHING no test

GERMANIUM AND SILICON GLASS

DIODES

100 \$1.49

FOR

- 60 TUBE SOCKETS, receptacles, plugs, audio, etc. \$1
- 30 POWER RESISTORS, 5 to 50W. to 24 Kohms. \$1
- 50 MICA CONDENSERS, to .1mf, silvers too! . \$1
- 10 VOLUME CONTROLS, to 1 meg, switch too! . \$1
- 10° ELECTROLYTICS, to 500mf, asst FP & tubulars \$1
- 50 RADIO & TV KNOBS, asstd. colors & styles . \$1
- 10 TRANSISTOR ELECTROLYTICS: 10mf to 500mf \$1
- 50 COILS & CHOKES, if, rf, ant, osc, & more . \$1
- 35 TWO WATTERS, asst incl: A.B., 5 % too! . . \$1
- 75 HALF WATTERS, asst incl: A.B., 5 % too! . . \$1
- 60 HI-Q RESISTORS, 1/2, 1, 2W, 1 % & 5 % values \$1
- 10 PHONO PLUG & JACK SETS, tuners, amps . \$1
- 50 TERMINALSTRIPS, 1 to 8 solder lug types . \$1
- 30 "YELLOW" MYLAR CONDENSERS, asstd val \$1
- 60 CERAMIC CONDENSERS. discs. nbo's: to .05 \$1
- 3 GEIGER COUNTER DETECTOR, tubes, assorted \$1

1000 MC Worth 10.29 similar to
Silicon Epitaxial **Fairchild 2N918**
Planar **NPN \$1.49**
TO-18, 4-lead

- 4 ZENER REFERENCES, 1N429, 6-volt, silicon . \$1
- 6 "TEXAS" 750 MA 400V RECTIFIERS, leads \$1
- 6 2N408 TRANSISTORS, TO1, pnp, driver . . . \$1
- 2 2N718 NPN SILICON PLANARS, by Fairchild . \$1
- 4 2N219 TRANSISTORS, mixer-conv, TO22 . . . \$1
- 10 MICRODIODE STABISTORS, epoxy, silicon . \$1
- 2 2N706 500MW, 300MC NPN PLANAR, TO46 . \$1
- 10 POPULAR CK722, TRANSISTORS, pnp, no test \$1
- 5 2N107 TRANS'TRS, by GE, pnp, pop. audio pak \$1
- 10 PNP SWITCHING TRANSISTORS, 2N1305, TO5 \$1
- 10 NPN SWITCHING TRANSISTORS, 2N338, 440 \$1
- 15 PNP TRANSISTORS, CK722, 2N35, 107 no test \$1
- 15 NPN TRANSISTORS, 2N35, 170, 440, no test \$1

TRANSITRON
40-WATT Frequency (Mc) **1.00** EA
SILICON NPN MESA TRANSISTORS 10
2N1647-50

1¢ SALE!

- DISC CONDENSERS, . . . 30 for \$1 60 for 1.01
- PRECISION RESISTORS, . . . 30 for \$1 60 for 1.01
- PLANAR TRANSISTORS, . . . 4 for \$1 8 for 1.01
- POWER TRANSISTORS, . . . 3 for \$1 6 for 1.01
- SWITCHING TRANS'TRS, . . . 15 for \$1 30 for 1.01
- ZENER REFERENCES, . . . 6 for \$1 12 for 1.01
- GERMANIUM DIODES . . . 25 for \$1 50 for 1.01
- TOP HAT RECTIFIERS . . . 25 for \$1 50 for 1.01
- TRANSISTORS . . . 30 for \$1 60 for 1.01
- 25-AMP RECTIFIERS . . . 2 for \$1 4 for 1.01
- 2N1613 100MC TRANS. . . 1 for \$1 2 for 1.01
- 4W PLANARS 2N497-98 . . 2 for \$1 4 for 1.01
- "LOW NOISE" RESISTORS 25 for \$1 50 for 1.01

500 Mc SILICON PLANAR POWER TRANSISTORS
(ACTUAL SIZE) PANCAKE
similar to Fairchild

DISS Watts @25C <1w	V Vce	GAIN	
		β@C'B*	hFE ma
<input type="checkbox"/> PNP	3 12	30-120	1000
<input type="checkbox"/> NPN	3 12	30-120	1000

ONLY \$1.49 Each

6 AMP 1000V RECTIFIER STUD 2 for 1.49

Full Leads Factory Tested & Gtd! U.S.A. Mfg.
POLY PAKS
TERMS: send check, money order. Include postage—avg. wt. per pak 1 lb. Rated net 30 days. CODs 25%. CATALOG 10¢
P.O. BOX 942A, SO. LYNNFIELD, MASS.

and talk with the Bahamas, Cuba, every state east of the Mississippi and plenty west of it several days a week. I think we're up close to 45 states already this year. California comes popping through every now and then. And you don't need a lot of power or antenna on six to get through . . . we work too many Sixers to believe that. Not that high power and a good beam don't get you in there first every time. It's nice not to miss anything coming through and a five or ten element beam with 200 or so watts will rarely miss.

28 Sunspots are perking things up on ten and some good DX has been popping up. This band will be hot quite a bit this fall so you would be prudent to be set for it with at least three elements and sideband.

21 Activity is high on fifteen already, with several rare DX stations coming through only on this band. If you don't like to fight the QRM you can often have nice DX contacts on this band.

14 More and more twenty is staying open all night. Despite all the gripes about QRM and everything, this isn't that much of a problem if you don't insist on operating during the peak activity hours. Anyone with a three element beam and a sturdy sideband signal can work his 100 countries during a two week vacation. Conditions are going to nothing but improve on this band for the next few years.

Thanks Vote

If we are able to fight off 15928 all of you who sat by and let this happen to you without a whimper owe a lot to the few hundred hams who took the time and trouble to file their comments with the FCC and to complain to Senator Magnuson and Chairman Henry of the FCC. It should have been thousands. Fellows, stop waiting for someone to come to your door with a petition you can sign and write at least one lousy letter telling the FCC, Washington 25, D.C. that you personally think their proposals are preposterous.

Field Day

Luckily for me I didn't get into the Field Day contest until quite late, otherwise I might have gotten hooked into seeing it through. As it was I made 301 contacts in 300 minutes, including one new country (FP8CK) and a VK. Judging from the activity I found on 20 meterphone . . . the only band I tried . . . interest was high this year in this contest. Good show. Activity was widespread too . . . outside of the states too close in for 20 during the day I worked everything except Idaho. Hmm, maybe I'll go in the Sweepstakes Contest this fall.

Maryland VHF Society

This is a swinging outfit down Baltimore way. They were kind enough to invite me down for their annual Dinner in May and even gave me an opportunity to air my views on VHF as well as our current crisis. I tried to talk more of them into big arrays and kilowatts so I could get to talk with them from up in New Hampshire. VHF'ers around that area would do well to drop a line to Box 8554 in Baltimore and join up.

Good Idea

XE1NNN has been sending QSL cards to ham manufacturers that are not advertising in 73 telling them that his subscriptions to the other magazines have run out and if they want to reach him it has to be through 73. Olé!

Fame and Fortune Available

Fame, anyway. 73 still needs someone to take over as Advertising Manager. Salary details are classified, but the take should run around \$8-10G as a starter and maybe double that eventually. Advantages? Well, you get to live where it is so wonderful that people come as a vacation both summer and winter (as well as spring and fall). Prices are reasonable, taxes as low as they come, and the people are wonderful. Hamming is great up here too.

We need someone who is a good talker, presentable, educated, intelligent, has a good background in ham radio and sales, has initiative and who is looking for a job that will allow him to grow. He should be making around \$10G right now, at least.

Write, if you think we need you.

Lobby Group Formed

The National Association of Business and Educational Radio (Naber) just recently formed. They want more frequencies. From offices in Chicago and Washington, D. C., this association of two-way radio users will seek representation in FCC rule-making procedures and attempt to provide representation on Government/Industry committees relating to two way communication. Where, in a spectrum already crowded, will they get them? They already got our 11-meter band. Will they take more?

Only one amateur radio groups exists that can deal with Congress and lobby for amateur radio: the Institute of Amateur Radio. The ARRL can't do it, the law prevents; should they try, they face heavy fines. (They would first need proper certification which they surely can't get with their present organization). Re

member, organized pressure brings results. Join the IoAR. Don't let a recently formed Citizen group beat our sixty-five-year-old amateur radio hobby out of more frequencies.

The Institute takes your problems right to Congress. You need the Institute's *voice*; the Institute needs your *support*. A mere membership fee of \$5 a year satisfies both. Naber charges \$15 per first base station plus \$10 for each additional base station per member per year. But even at the price, 4000 joined before planned promotion started just from word-of-mouth and phone calls. When promotion starts, they expect the total to swell to 30,000. Unless the members of the Institute campaign harder to recruit more members, Naber will get the new frequencies. Get the population up! *Our frequencies need protection*. Naber predicts over a million transmitters by the end of '69.

Moonbounce

Now that Sam W1FZJ is in residence down at Arecibo Puerto Rico it was only natural that he would tune up that 1000 foot 56 db dish on 432 now and then. The first test came on July 3rd and was remarkably successful. Sam started out on CW, went to SSB, and stayed on SSB for about an hour and then finished up on CW again. The following contacts were reported for the first hour or so of the marathon: W1BU, W1HIV, W3SDZ, HB9RG, W9GAB, DL3YBA, K1IGY/1, G3LTF, WA4BYR, W7ORG, W9HGE, W8TTY, W2ZEME, W2CCY, W4HHK, W1OUN/1, W7AUB, DJ4AUD, W1HGT, W2ROP, K2CBA, K3GYF, K6MIO, K2MBA, K1SDX/1, LX1SI, W1OOP . . . etc. Worked on two way sideband were HB9RG, W1BU, G3LTF, WA4BYR.

There were an awful lot of fellows that didn't make the hop . . . fellows that were hearing Sam fine. The problem is the same as it was with Oscar . . . signals fading up and down by 20 db or so, and terrific QRM. Sam suggests that those without dishes get out of the low end QRM bin and spread out a bit. Drop him a line and tell him what frequency you are using so he can look for you and will know from even a fragment of your call who he is hearing. This will speed things up tremendously. The next test is July 24th, so get right at it. W1OOP worked through with a 4 element colinear and 200 watts, but this is a minimum. The signals from the dishes stood out like sore thumbs on the band and everyone else was in there, fading in and out, with weak signals.

I'm planning on being on the Arecibo end for the 24th test . . . say hello.

That Building Fund

Many amateurs felt that the League had sort of given them a kick in the . . . er . . . teeth with RM-499 and its resultant Docket 15928 and quite a few have expressed to me their regret over having contributed to the ARRL Building Fund. A letter from John Huntoon says, "As participation in the Building Fund Drive is purely a voluntary matter, under no circumstances would we want any contributor to be dissatisfied with his action. Accordingly, I am enclosing our check for \$2.00 in refund of your donation." In another letter John writes, "I repeat I would not want to have any part of our Building Fund made up of contributions from people who have regretted their actions." These letters were forwarded to me along with the refund checks endorsed over to the Institute.

This certainly is a very commendable thing, though the refunds may get out of hand.

73 Hamfest

How many do you expect, they kept asking me. I have no way to guess, I'd reply. Probably be over a hundred and it might run to a thousand. Well, we counted a little over 1200! Pretty good for a little hamfest way up in the mountains of New Hampshire, eh?

Scattered showers on the third cooled us off and gave us a bright shining clean New Hampshire on the 4th of July with magnificent visibility from the mountains.

Among the events to keep people busy during the day we had a two meter transmitter hunt, an antenna measuring contest for both 144 and 432 mc, a home brew contest, exhibits of manufacturers, twelve tables of bargains spread out to browse over, and an auction that lasted a good part of the day and sold over \$30,000 worth of equipment! All sorts of home brew and commercial gear went, from an NCX-3 on down to 25c grab bags. We had about an hour discussion of Docket 15928. A great many took out an hour or so and visited the 73 headquarters building and the 73 mountain ham shack.

Bill Hoisington K1CLL was on hand to show off his home brew UHF gear and mc the antenna measuring contest. Bill did a splendid job and the winner of the contest was Jud K2CBA with a 432 mc colinear.

There was a considerable clamor for us to have another hamfest next year. I wouldn't be surprised if we did. If anyone didn't have a good time, I didn't hear about it.

. . . Wayne

SURPLUS BARGAINS

We have moved to new quarters to start the new year with. Lucky finds and scarce items.

TCS DYNAMOTOR MOBILE POWER SUPPLY
NEW 12 v dc input, 400 v dc @ 200 ma output.
\$3.95 postpaid west of Denver. \$4.95 postpaid east

Dow Trading Company
N. Dowdell W6LR 2057 E. Huntington
Elliott 7-3981 Duarte, California

Signal Lack "Punch"?

Try our model CPR Speech Compressor!
Miniature, transistorized, mounts on button panel connector.
TRIPLES your SSB output power or AM modulation!
NEW low noise circuits; with compression switch; for low and high impedance microphones. only \$14.95
Fully warranted and guaranteed

COMMUNICATION COMPONENTS COMPANY
P. O. Box 8721 Orlando, Florida

BIG CATALOG

World's "BEST BUYS"
in GOV'T. SURPLUS
Electronic Equipment

FULL OF TOP QUALITY ITEMS — Transmitters, Receivers, Power Supplies, Inverters, Microphones, Filters, Meters, Cable, Keyers, Phones, Antennas, Chokes, Dynamotors, Blowers, Switches, Test Equipment, Headsets, Amplifiers, Indicators, Handsets, Converters, Control Boxes, etc., etc. **SEND 25¢** (stamps or coin) for CATALOG and receive 50¢ CREDIT on your order. Address Dept. 73

FAIR RADIO SALES
P. O. Box 1105 • LIMA, OHIO • 45802

ALL BAND TRAP ANTENNA!



Reduces Interference and Noise on All Makes Short Wave Receivers. Makes World Wide Reception Stronger. Clearer on All Bands!

For ALL Amateur Transmitters. Guaranteed for 600 Watts AM 1200 SSB Pi-Net or Link Direct Feed. Light, Neat, Weatherproof.

Complete as shown total length 102 ft. with 96 ft. of 72 ohm balanced twinline. Hi-impact molded resonant traps. (Wt. 3 oz. 1" x 5" long). You just tune to desired band for beamlike results. Excellent for ALL world-wide short-wave receivers and amateur transmitters. For NOVICE AND ALL CLASS AMATEURS! NO EXTRA TUNERS OR GADGETS NEEDED! Eliminates 5 separate antennas with excellent performance guaranteed. Inconspicuous for Fussy Neighborhoods! NO HAY-WIRE HOUSE APPEARANCE! EASY INSTALLATION! Complete Instructions.

75-40-20-15-10 meter bands. Complete \$15.95
40-20-15-10 meter. 54-ft. (best for swl's) Complete \$14.95

SEND ONLY \$3.00 (cash, ck., mo) and pay postman balance COD plus postage on arrival or send full price for postpaid delivery. Complete installation & technical instructions furnished. Free information on many other 160-6 meter antennas.

Available only from:

WESTERN RADIO • Dept. A7-8 • Kearney, Nebraska

DUMONT SCOPES

304	115.00	322A	325.00
304R	100.00	333	350.00
340	150.00	401A	250.00
340R	135.00	401AR	225.00

SEND YOUR ORDERS TO **ALCO LAWRENCE, MASS**

CAVEAT EMPTOR?

- ★ Price—\$2 per 25 words for non-commercial ads; \$5 per 25 words for business ventures. No display ads or agency discount. Include your check with order.
- ★ Type copy on standard size paper. Phrase and punctuate exactly as you wish it to appear. No all-capital ads. Include your signature with order.
- ★ We can only accept ads related to ham radio. We will be the judge of suitability of ads. Our responsibility for errors extends only to printing a correct ad in a later issue.
- ★ For \$1 extra and an SASE, we can maintain a reply box for you.
- ★ We cannot check into each advertiser, so Caveat Emptor . . .

CONVERTERS \$10 and up. World's largest selection of frequencies. Ham TV vidicon cameras and parts at low factory-direct prices. See them all now in our full page ad in this issue. Vanguard Labs, 190-48 99th Ave., Hollis, N. Y. 11423.

YOUR CALL LETTERS and name in gold, on your very own coffee mug. \$2.00 (helps me through college). Latterman K7ZOV, 2511 N. 68th Street, Scottsdale, Arizona.

TOOOOBBES, TRANSMITTING-SPECIAL PURPOSE, New, Boxed, Guaranteed...6CW4 — \$1.40, 6146B — \$4.75, 417A — \$3.95, 826 — \$6.90...Free Catalog...Vanbar Dist. Box 444, Stirling, N. J. 07980.

DUMMY LOAD, 50 ohms. All bands up to legal limit. Size, 3 x 4 x 7. Coax connector. Kit \$7.75, wired \$9.75 pp. Ham Kits. Bx 175, Cranford, N. J.

NORTH ALABAMA HAMFEST sponsored by the Huntsville ARC, Community Center in Big Spring Park on Sunday August 15. Contact William Probus WA4DBQ, 2607 Woodview Drive, SE, Huntsville for more information.

SCARA HAMFEST Sunday August 29th at Lake Lenape Park, Mays Landing, New Jersey. Get more dope from Charles Bengal W2TUR, 815 Seaside Avenue Absecon, N. J.

SIX METER MOBILEER HAMFEST. Sunday August 8, Weymouth Fairgrounds, Weymouth, Mass. More info from P. O. Box 94, Wollaton, Mass.

HENDERSON ARC HAMFEST: Sunday August 8 at the Audubon Raceway Park, Henderson, Kentucky. You can find out more from Larry Yates WA4PMA, P. O. Box 83, Henderson.

DELAWARE HAMFEST. August 15, Harrington, Delaware. Write Pete Robinson K30CI, 304 Kesselring Ave., Dover, Del.

WARREN ARA HAMFEST. Sunday August 29th, Newton Falls Community Center, Newton Falls, Ohio. Get more information from K8BXT.

DRAKE 2B RECEIVER, 2BQ Q Multiplier, 2AC calibrator, Knight V-66 VFO. All excellent, all for \$200. Brian Kassel K3LSB, 976 South Hills Blvd., Pottstown Pa.

LPA1 KW LINEAR AND LPS1 power supply. Brand new, never used. \$450. L. J. Maggora, 575 Pierce St. San Francisco, Calif.

GONSET G-50: 10 hours use. \$210 postpaid anywhere in U. S. Check or money order. Dick Sullivan, Box 156, Boone, Iowa.

PH565 HAM-TV camera converted and airtested UHF converter included \$65.00 prepaid. Al Johnson, K7VQI 1018 E. Cooper Street, Tucson, Ariz. 85711

TOROID BALUN KITS—2" core & #14 Formvar. 4:1 or 1:1 Z ratio. Handles Kilowatt. \$5 plus 25c postage. Ami-Tron, 12033 Otsego St., North Hollywood, Calif.

SCHEMATICS of surplus electronics, hand gear, and test equipment. Send dime or stamps for list to Hill Enterprises, RD #1, Box 241, Kingstown, Pa. 17967

RT14 SYNTHESIZER MODULES UNIT 11C now available . . . Also Units 6, 8, 9, 10, 11A, 11B. All New, Less tubes, With Schematic . . . \$8.00 each or any three \$6.50 each. Also schematics any unit, one thru twelve, Fifty cents, or full set of Fourteen \$3.00 . . . RITCO Box 156, Annandale, Virginia.

WANTED: All types, Military, Commercial, Airborne, Ground, Electronic items—Testsets, GRC, PRC, Collins, Bendix, Others . . . We Pay Freight . . . RITCO Box 156, Annandale, Virginia.

WANTED Hy-Gain 18-HT Vertical. Have 14-AVS Vertical and TH-3 10-15-20 beam for sale. WAØEJF. Box 41, Cedar Rapids, Iowa.

COLLINS 75-A-4 OWNERS: Don't trade up! Investigate our conversion that makes the 75-A-4 a real dream. V2VCZ—30 Pitcairn Ave., Ho-Ho-Kus, N. J. 201-652-494.

NAVY TCS transmitter, receiver, 115 volt power supply, VTT microphone, loading coil, and extra tubes \$85.00 FOB. Model 15 teletype very good condx \$70.00 FOB. Robert N. Hogaboam WB6KNN, 374 Elder Ave., Imperial Beach, Calif.

OX-60 Perfect unused. Estate of W1QJ. FB 2nd rig, ask for new ham. \$60 plus shipping. W1KSB Cushing, Bickford Rd., Malden, Mass. 02148

LANGING 'EM UP. Complete Collins Station for sale. 35S-3, 32S-3, 30L-1, 312B-4, 516F-2 all Rack Mounted in Collins rack mounts, on 61 inch Bud Deluxe Relay Rack with Trans-Aire Blower Mounted in top. Complete KW station will roll right in closet. Not just good, but the best. A \$2400 value. Best offer over \$1800. F.O.B. Also WMM-2, MP-1, PM-2, CC-2, 351D-2, \$1050. J. B. Holmes, Jr., P. O. Box 36146, Houston, Texas 77036.

DIGGEST, Nope. BEST? Heck yes! Warren ARA Hamfest, Aug. 29. Newton Falls. Arrows from Rt. 534, Turnpike Warren Exit 14. Details: WARA Hamfest, Box 09, Warren, Ohio.

20 MC. EQUIPMENT, ERCO AM Xmitter/Mod. 6252 \$70.00, R-48/TRC-8 receiver AC, converted to 220 VAC \$30.00. W1HMT, 25 W. Union St., Goffstown, N. H.

DEATH 1 watt CB handy-talkies, model GW-52, professionally wired, rechargeable batteries, channel 3, excellent, \$125.00/pair. I. Gray, 25 W. Union St., Goffstown, N. H.

PEORIA HAMFEST September 19, Exposition Gardens, Peoria Area Amateur Radio Club, advance registration \$1.00 until Sept. 11. Ferrel Lytle, W9DHE, 419 Stonegate Rd., Peoria, Illinois

BE-33 very little use, guaranteed to look and operate like new, with manual and cables, \$200. Stan Flegler W8RPA, 1400 Poxson, Lansing, Mich., 48910.

COLLINS 75A2 \$160, National NC-183D \$100, Johnson Ranger I \$60. This gear requires minor repairs but is clean. We box, you pay shipping. WØEBE Memorial, Southwest Missouri Amateur Radio Club Inc., P. O. Box 11, Springfield, Missouri 65801

NE TS-47/APR, see June "73", VG \$40. Two T23/AR- 5 Xmttr (2-832A's) new \$14. ea., both \$24.00 FOB, G. Wick, 26 Ridge Rd., Smithtown, N. Y.

OLD Mine. See 73, June 1965 page 78. R105/ARR15— 5. Brand new M19 RTTY. \$225. I-193 Polar Relay Test set, see CQ May 1965 p. 66, \$14. Loop supply for M15 \$1.50. All FOB Maywood. Send SASE for list of other stuff. J. Cooper, W2BVE, 834 Palmer Ave., Maywood, N. J.



BROAD BAND BALUN \$10 net ppd. in U.S.A.

● Flat in the amateur bands from 3 to 30 Mcs. ● Full legal power ● Fully weather sealed ● Matches coax to antenna or balanced line. ● Improves efficiency and radiation pattern.

Two models, 1 to 1 or 4 to 1 impedance ratio
Size 1 1/4" OD x 4" long. Wt. 4 oz.

FUGLE LABS 1835 Watchung Ave., Plainfield, N.J.

MOTOROLA FM EQUIPMENT SCHEMATIC DIGEST

Contains a comprehensive collection of Motorola transmitters, receivers, power supplies, and interconnecting diagrams for Motorola FM equipment manufactured between 1949 and 1954. Covered are crystal formulas, crystal correlation data and basic alignment instructions.

92 pages

Price \$3.95 pp

TWO WAY RADIO ENGINEERS

1100 TREMONT STREET
BOSTON 20, MASSACHUSETTS

NEW ARRIVALS—TERRIFIC SAVINGS

Tubes are BRAND NEW except * pulls from new equipment. All are fully guaranteed.

4-125A Brand new	\$12.50
2C39A Brand new	7.50
3B28* Xenon filled 866, direct replacement, no warmup time; no flash-over; no hash.	\$3.00 each 4/\$11.50
EFJ #123-210 4 pin ceramic, bayonet base 25W socket for 811, 866, 3B28. Take-outs, wired in parallel.	69c pair, 3 pr for 1.95
7C7 For MOTOROLA VHF gear. Choice	\$1.00 each
7H7	4/\$3.75
ACORNS, 954, 955, 956, 957, 958A. Choice, any 12	\$3.30
Sockets for acorn, ceramic wafer	6 for \$1.10
EFJ #123-211 4 pin jumbo, ceramic, bayonet base, 50 watt socket for 872A	\$1.25 each 4/\$4.50
UTC #S-35 8 hry, 60 ohm, 400 ma, 5 KV, potted choke	\$5.50
THORDARSON 21F18 Filament transformer, 117v 60 cyc. to 10v CT, 5A, 3 KV. wire leads	\$3.50
APC 4 to 25 mmf, brass plates, 1/4 x 1 1/2" shaft	59c 3/\$1.95
Dual 5 to 15 mmf/sec. with tapped coil, tunes 140 to 260 mc. 1/4 x 1/2" shaft.	\$1.25 each 4/\$4.50
6 meter, slug (brass insert), tuned coil needs 50 to 60 mmf variable. 1/4 x 1 1/2". Less mounting nut.	39 each 3/\$1.10
Sprague Hy-Pass #48P18, .5 mfd, 50 vdc, 40A. Generator noise suppressor.	59c each, 3/1.65
Toroids 25 microhenry. 3/4" OD, 1/2" ID x 3/16". * Like new, cheap core source.	39c each, 3/\$1

Save your loot * * * Hamfesters, Sante Fe Park, Chicago, Aug. 8; 6 meter, Frankfort, Ill., Aug. 1; WARA, Warren, Ohio, Aug. 29.

All orders, except in emergency or I'm at a hamfest, shipped same day received. For free "GOODIE" sheet, send self addressed stamped envelope—PLEASE, PLEASE—include sufficient for postage & insurance. Any excess returned with order.

B C Electronics

Telephone 312 CALumet 5-2235

2333 S. Michigan Ave.

Chicago, Illinois 60616

URGENT, NEED IMMEDIATELY

Very high prices paid. Freight prepaid. AN/GRC; PRC; APR; APN; ARC; ALT; URM; UPM; TS. We also buy all military and commercial test, radar, and communication equipment.
CALL COLLECT. IT COSTS YOU NOTHING TO HEAR OUR HIGH OFFER.

SPACE ELECTRONICS
4178 Park Ave., Bronx, N. Y. • (212) CY 9-0300

RADIO TELETYPE EQUIPMENT

Teletype Models 14, 15, 19, 20, FRXD, 28, Klein-schmidt printers. Boehme CW keyers. Radio Receivers Collins 51J-3, 51J-4, R-390, R-390A, R-391, Hammarlund SP-600JX. Frequency Shift Converters.

ALLTRONICS HOWARD CO.

Box 19, Boston, Mass. 02101 Tel. 617-742-0048

GUARANTEED RECONDITIONED



HAM GEAR

Phone: (415)
DI 2-5757

ELECTRONICS

WRITE NOW
FOR MONTHLY
FLYER.

999 HOWARD AVE-BURLINGAME, CAL.

- New E. F. Johnson Tube Sockets 122-101-100**, Aluminum Shell with 3/8 vent. holes submounts tube 1" below Chassis, takes 5894, 829B, '32A, etc. \$1.80 value **\$75c ea.**
Type 122-247-100 top mount 7 pin steatite, same tubes **50c ea.**
- Transmitting Caps CRL #851**, 25 mmf, 15 KV New **2/\$1.25**
- Clear Plexiglass Strips 9" x 2 1/2" x 1/16"** **5/\$1.00**
- 2" speakers**, large magnet, used as microphone and speaker in Hallicrafters CB-4 **2/\$1.75**
- New Plate Current Meter 0-200** used in Hallicrafters HA-2. Keep a spare **\$3.50**
- New "S" Meter** used in Hallicrafters SX-115 **\$3.50**
- Sarkes Tarzian Diodes F-6** (1N2484), 600PIV, 750Ma. **10/\$3.75**
- All items subject to prior Sale, minimum order \$3.50**

Government Warehouse, Inc.

264 Shrewsbury Ave., Red Bank, N. J.

- SG93/URM75 4-220mc Signal & Sweep Generator. Crystal Calibrator & Modulation. Manuals. For 60 cy. EX 67.75
- GR 667-A Induct. Bridge .1 Microhenry-1 Henry EX 130
- HP 200 I Interpolation Audio Osc 6cy-6Kc 6 Bands EX 95
- Ferris 32-B RF Noise and Field Strength Meter EX 195
- Tektronix 121 Wide Band Preamp for 511 Scope EX 47.75
- Ballantine 300 AC VTVM in 19" Rack Panel EX 38.50
- Ballantine 316 AC VTVM .05cy-30Kc .02-200V P-P. EX 135
- 315SP Similar except 2cy-20Kc .02-200V P-P & RMS. EX 85
- Lambda 28 200-325VDC @ 100ma 1% Reg. 6. 3VAC EX 19.50
- Lambda 32 200-325VDC @ 300 ma 1% Reg. 2X6.3VAC EX 29.75
- TS147B Sperry 38A Sig Gen & Freq Mtr. 8.5-9.6 Kmc EX 95
- TS155E Signal Generator 2700-3400mc EX 80
- T61/AXT2 TV Xmtr W/Video & Sync Modulators NEW 17.50
- RT82/APX6 Converts to 1215-1296 mc Xceiver NEW 21.75
- UPM8 Tests APX6. 27 Tubes, 10 Diodes. For 60 cy. GD 14.50
- Same Reconditioned by US Government LIKE NEW 19.75
- Complete Manual for TS726/UPM8 above. Postpaid NEW 2.90
- R105/ARR15 COL'INS 1.5-18mc Recvr W/Schematic EX 44.50
- Reflectometer SWR Sridge w/Meter, 30-1000mc EX 8.25
- R23/ARC5 The Q-5er tunable IF. 190-550kc EX 11.25
- Scope Xformr 1950@3ma, 6 Fil Windings, 60 cycle NEW 2.75
- RT18/ARC1 100-156mc Xceivr. W/Tubes & DY9 EX 19.75
- Same less tubes and Dynamotor DY9 GOOD 9.75
- T465/ALT7 Xmtrtr 168-352mc W/2-6161s, 100W out. EX 22.50
- Schematic for T465/ALT7 with parts values 1.00
- Tube type 6161 w/connectors.. 65W to 2000mc EX 7.50
- SA325/U Coaxial Relay SP4T. With 28 VDC Motor EX 3.25
- Set of 120 Xtals Type FT243 5675 thru 8650kc. 120/17.50
- CU119A Coupler 13 one-tube amplifiers w/tubes EX 6.25
- R122A/ARN12 75 mc Superhet w/9 Tubes & Xtal. EX 2/7.00
- Rt. Angle Drive w/Gears & Universal. 1/4" Shaft. EX 3/5.00
- UPM11A AFC Unit w/8 Tubes & Wiring Diagram NEW 3.75

E. C. HAYDEN

BOX 294 Bay Saint Louis
Mississippi

Shipment: FOB Bay Saint Louis. Terms: Net, Cash.

HQ-170C with speaker, unblemished, \$200. NC-100 receiver general coverage. \$30. Benson Gyro Glider, \$250. 4X250B new, unused. Will trade all but HQ-170. Want Band Spanner, Heath HP13 or similar mobilepower supply. Art Linehan, 124 A. Street, Manchester, N. H.

SELLING OUT: Tremendous bargains in equipment, tubes, parts. TBS50D xmtr with PS, \$35. Knight VFO, \$15. Stamp for list. W3CNS, Box 1, Rheems, Pa.

NCX-3 AND NCX-A, \$325. K1AJE Jesse Bryant, Box 829, Trafton Lane, Kittery, Maine.

GONSET COMMUNICATOR IIB. 6 Meters, 12 v mike, xtals, halo. Mint, never used mobile. Selling for widow of ham. \$135. E. Christie W1GGI, 72 Martin St., W. Roxbury, Mass. 02132.

STAMP COLLECTORS: Will swap stamps (your choice) for amateur and military radio equipment, supplies, tech manuals, etc. J. J. Reilly, 3519 167 Street, Flushing, New York 11358.

WANTED: W3DZZ Tri-Band Beam. Jean LeBorgne W6LZV, 12022 Celine St., El Monte, Calif. 443-8500. Long distance collect calls not accepted.

FREE! Blue book list. Leo has over 1000 bargains in used gear. KWM2 \$675; Galaxy 300 \$215.10; Viking 500 \$350.10; NCL 2000 \$485.00; SX101A \$229.50; Collins 62S1 \$625.00; King 500A \$259.00; SB400 \$299.95; SX117 \$260.10; Drake 2A \$189.00; and many more. Free 1965 catalog-WRL, WøGFQ, Box 919, Council Bluffs, Iowa.

NEW MOTOROLA miniature seven tube, 455 KC II amplifier and discriminator with circuit diagram. Complete postpaid, \$2.75 each. R and R Electronics, 1953 South Yellow Springs, Springfield, Ohio.

WE WILL PAY CASH OR TRADE . . . On popular clean unmodified amateur gear. World Radio Laboratories Box 919, Council Bluffs, Iowa.

NATIONAL NCX-5 TRANSCEIVER. Brand new. Never opened factory sealed box. \$555. Joe Duffin W2)RA, 24 Kings Highway, West, Haddonfield, N. J.

4CX250B TWO METER FINAL, Johnson 6N2, Eico modulator and all power supplies including HV. \$250 for all or sell separately. Hy Gain 15 element 2 meter yagi, Hy Gain 10 element 2 meter yagi, Gain Skybeam 10 element yagi, W2AZL 417A 2 meter converter. Want J and H model 2-150. Bill Smith KØCER, 1301 Church Ave., Sioux Falls, S. D.

ANNUAL NETTERS PICNIC Frantz Grove, New Ringgold, Pa. Sunday July 25. K3YVG can give you more information.

WABASH VALLEY VHF PICNIC. Sunday July 25 at Turkey Run State Park near Terre Haute, Ind. K9WH is the chairman.

SX101 III in very good condition only \$200. Will deliver within 50 miles. A. E. Frisbie WB6AYV, 161 N. Thompson, Hemet, California 92343.

GOOD NOVICE STATION—HQ 110C, matching speaker, \$125; Globe Scout 680A, \$45; both, \$160. Prefer local buyer. Ken WA2FPV, 75-46 190 St., Flushing, N. Y. HO 8-3234.

TELCO WILL PAY FOR HELP . . . we want to get the names of people who buy equipment for military and commercial applications. Our new 1 kw linear with bandwidth of 2-30 mc is a natural for commercial use. We'll buy you a one year subscription to 73 if you'll send us the names and addresses of six commercial buyers. **TELCO, Inc.**, 575 Technology Square, Cambridge, Mass. Current Events—

TELETYPE MODEL 30A PRINTER. Tiny light weight unit (19 lbs). Has 28 type keyboard, 115 vac motor, end-of-line indicator, aluminum case. Excellent condition. Just the thing for portable operation and demonstration. \$90. Box 152, 73 Magazine, Peterborough, N. H.

WIDE SCREEN TV CAMERA AND 18" MONITOR Made by Crimson Color, Inc. Model 700. Sells for over \$1000 new. Complete in excellent working condition. Like new with all cables, power supplies and manual. \$649. Box 153, 73 Magazine, Peterborough, N. H.

More Letters

Dear Wayne:

I have been an avid reader of your magazine for the past two years. Technically, it cannot be surpassed. However, it has just occurred to me that seldom is any mention made of the important role that our hobby may play in our everyday family relationships. I would assume that there are just as many "rig widows" as "golf widows."

With the above thought in mind, I thought your readers might be interested in the program our local mobile radio group initiated. Each month, of course, we had our usual business meeting. However, the following weekend was our "family" meeting; in other words, a road trip with our families.

Scenic Arizona has many educational and historical landmarks, and we had no difficulty deciding where to go. We have many one-day trips to places such as Miami, where there is open pit mining for copper, to Globe to "dig" for "Apache Tears" (Obsidian), to Colossal Cave, the only cave in the U. S. where the temperature always remains at 73°. Also, there were several overnight camping trips to such places as Grand Canyon, Tombstone, etc. When mobile to and from these sites, we were in direct communication with one another by our rigs.

We found these trips not only valuable from a technical standpoint, but also, it acquainted the XYL with what we were doing and why we enjoyed doing it. It brought families closer together because we shared a hobby; we enjoyed being out in the woods, the mountains, the desert, wherever the road led us.

Our Club feels that our mobile cavalcades have brought the family more closely together, and that our hobby now is better accepted by our XYL.

Alex J. Kenwright K7JNY
Mesa, Arizona

Dear Wayne:

Please advise if an IoAR cut is available for imprinting on my QSL cards. My present card which bears the insignia of another amateur organization has suddenly become obsolete!

George Firmin WA4FSK
Atlanta, Georgia

Yes indeed George. The IoAR cut is available for only \$1.

Dear Wayne,

Just read your April 1965 editorial. I want to add my name to that long list of people who never received payment for articles printed in ham magazines. My case was an article published in CQ in October 1957, the title was All Band Mobile (Almost). It was a very poor article, but CQ printed it and I never received any payment. I really enjoy your 73 magazine and I would really enjoy visiting you this summer and seeing 73 Mountain, etc. Hope I can.

L. L. Chilton W5THI
Fort Worth, Texas

Doc, I checked my records. Your article was in October 1958 and I had you down for \$16.00 in payment for it. I'm sorry you never received your money, but that was up to the bookkeeper and the publisher.

Wayne:

June was a very good issue. In this day of commercial rigs it is about time that a magazine has the foresight to encourage the use of surplus equipment. The FCC proposal might not have been if more ham magazines published information on home-brew and surplus conversions. More power to you and your convictions, there are lots of hams behind you. A check will soon follow from the Institute. I have one thing to say about the FCC proposal: one cannot legislate incentive!

Jack Swords WA6WTH
Fresno, California


THE BEST WAY TO BUY SURPLUS:

Ask for what you need. We will then send you **COMPREHENSIVE DATA** on what we have to meet your needs. **DON'T** ask for a catalog . . . it would take a fat book . . .

We **DON'T** sell mdse the way we get it in just to be able to advertise at a price lower than someone else's. We work it over . . . test it . . . overhaul and calibrate it . . . and **GUARANTEE SATISFACTION OR MONEY REFUNDED!**

WE ALSO BUY so if you have anything to sell, tell us about it and how much you want for it. When we answer your inquiries and describe material we are offering, we also price it. . . . You wouldn't think very much of us if we asked you to make us an offer!

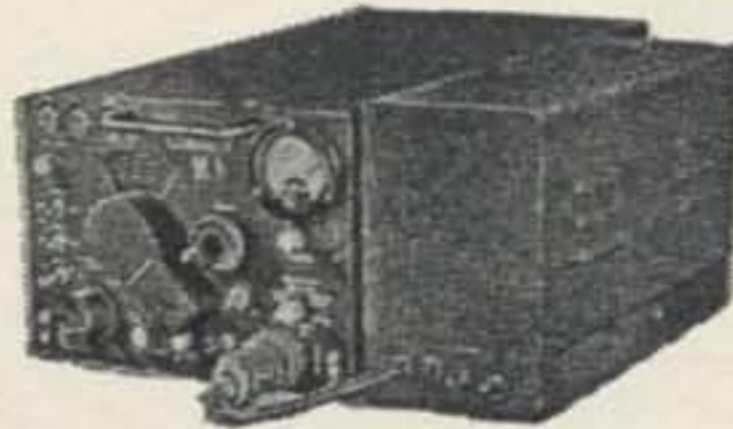BROADCAST-BAND COMMAND RECEIVER: ARC Type 12, No. R-22. Late type! 540-1600 kc, 6 tubes: RF, converter, 2 IF's & AVC, det. & Noise Limiter, & AF. 2 uv sensit. Needs external pwr sply & control ekts & has no tuning dial. With spline tuning knob, chart to tune exact freq. by turns count, lots of tech data, OK **17.95**
grtd. 9 lbs. FOB Los Angeles
(Add \$3 for extra-clean selected unit.)



ALL-BAND SSB RCVR BARGAIN: Hallicrafters R-45/ARR-7. 550 kc to 43 mc continuous: Voice, CW. MCW: 2 RF's. 2 IF's: S-meter: 455 kc Xtl. 6 select. choices. Ready to use. w/60 cy pwr sply & book. aligned. fob Los Angeles **199.50**

Deduct \$30 if you make your own pwr sply from schematic we furnish. Deduct \$20 if SSB not required, or deduct \$15 if you will wire in your own SSB with kit & diagram we furnish.

TIME PAY PLAN: Any purchase totaling \$160.00 or more, down payment only **10%**

ARC-5 Q-5'er Rcvr 190-550 kc w/85 kc IF's. Use as 2nd converter for above or other rcvrs. Checked electrically, w/lots of tech. data. w/spline knob. 9 lbs. fob Los Angeles **14.95**
(Add \$3 for extra-clean selected unit.)

AC PWR for SCR-522: RA-62-B made by Signal Corps for the specific job! 115/230v, 40 60 cy in. Regul. & flt. outputs 300v, .26A; 18v, 4A; -150v. 10 ma. OK **17.95**
grtd, w/data, 90 lbs. fob Sacramento

AN/APR-4 RECEIVING UNIT w/tuning units to tune 38-1000 mc plug & handbook. all checked & grtd 100% OK, ready to use on 60 cy fob Los Angeles **179.50**

Add \$30 for am/fm version modified for 60 cy pwr input: add \$60 for TN-19, 975-2200 mc; add \$125 for TN-54, 2175-4000 mc. All uncond. grtd. OK.

LM FREQ METER 125 kc to 20 mc is combin. heter. freq. meter & signal source. CW or AM, accuracy .01%. xtl calib. Clean, checked 100% grtd. w/plug. data. 16 lbs fob Los Angeles **57.50**

Add \$10 for EAO, converts for LM Power Supply w/parts, data, included 47 lbs fob San Diego

TS-323/UR, 20-480 mc. Crystal. 001%. W/handbook supplement giving supplementary xtl check points & instrus. to closely approach crystal accuracy. W/schematic, instruct., pwr sply data, clean, checked. 100% grtd. fob Los Angeles **199.50**

TELETYPE BARGAINS

U: Unchecked, as is, fair condition, some minor parts may be missing. C: Checked & repaired as needed, ready to use, grtd OK.

#14 Trans-Dist, sync., C \$49.50, U	35.00
Handbook TM 11-2222 for above	8.50
#14 Typ. Reperf, no keybd, C \$74.50, U	49.50
Same with keyboard, C \$89.50, U	69.50
Handbook TM 11-2223 for above two	9.00
TG-26B, like #19 but tape, C \$139.50, U	99.50
40 rolls oiled tape 11/16" wide	11.95
#15 w/keybd, sync. C \$149.50, U	95.00
Handbook TM 11-352 for Mod. 15	7.50
#19 w/keybd, syn. C 249.50, U	149.50

BEST OSCILLOSCOPE AT MODEST COST: Tektronix 514AD: DC-10 mc. Calib. defl. 30 mv-100 v/cm. Calib. sweep 0.1 usec-10 msec/cm. Sq. wave w/variable duty cycle, .05-50 v, available to test amplifiers. Other outputs: Sweep sawtooth, pos. & neg. gate pulses. Signal delay network, ¼ usec, permits viewing the signal which triggers the sweep. Locked-in triggering provides stable-as-a-rock picture. Completely overhauled, 100% grtd OK, with Book, **395.00**
clean and pretty, only

R. E. GOODHEART CO., INC.

Box 1220-GC BEVERLY HILLS, CALIF. 90213
Phones: Area 213, office 272-5707, messages 275-5342.

BACK ISSUES AND OTHER JUNK

73 Magazine Back Issue Grab Bag

An assortment of 20 different back issues of 73 from 1961 to 1963. No choice at this low price. We send what's available. \$5

Cheapskate's Assortment

Eight back issues of 73 for a puny \$2.

Single Back Copies

Individual copies of back issues from March 1961 to present are available for 50c each. Earlier ones (except the unavailable January 1961) are \$1.

ATV Experimenter

Five or more back issues for 50c. No choice. They're running out fast.

6 Up

We don't have any more 6 Up. Write Parks Labs, Beaverton, Oregon.

Binders and Bound Volumes

Beautiful red binders for each year of 73 are available for only \$3 apiece. Years are 60-61, 62, 63, 64, 65. A few 62, 63 and 64 bound volumes are occasionally available for the incredible price of only \$15.

73 Magazine Peterborough, N. H. 03458

PRICE INCREASE

Due to the rising cost of printing, postage, salaries, rent, heat, electricity, water, food, property taxes, etc., the cost of individual copies of 73 has been increased effective with this issue to 50c. Notice that that is \$6 per year if you buy 73 at the newsstand or parts distributor (not including sales tax). Subscriptions are still only \$4 per year (no sales tax). Why pay 50% more for each copy? Subscribe.

73, Peterborough, N. H. 03458

INDEX TO ADVERTISERS

Alco, 85, 90
Alliance, 27
Allied, 31
Alltronics-Howard, 92
American Crystal, 81
Amrad, 92
Arrow Sales, 81
ATV Research, 85
Autronics, 81
BC Electronics, 91
Budwig, 81
Burghardt, 55
Callbook, 71
Communication Comp., 90
Cushcraft, Cover II
Dow Key, 43
Dow Trading, 90
Drake, 48, 49
Edwards, 57
Ell-Conn, 63
Evans, 47
EZ Antenna Mount, 77
Fair, 90
Fugle, 91
Gift Shop, 85
Gonset, 39
Goodheart, 93
Government Whse, 92
Ham RTTY, 46
Hammarlund, 5
Hayden, 92
Heffron, 83
Henry, 35, 65
Int. Crystal, 3
McCoy, 23
Meshna, 79
Mission, 61
National, Cover IV
Parametric Amplifiers, 38
Parks, 85
Poly-Paks, 87
Quement, 60, 64
Rohn, 4
RSGB Books, 77
RW Electronics, 85
Salch, 63
SBE, 17, 33, 37, 43, 47
Selectronix, 75
Space, 92
Sprague, 51
Swan, 13
T A B, 95
Telco, 33
Telrex, 15, 22, 25
Texas Crystal, 69
Transcom, 21
Tri-Ex, 11
Two Way, 91
Vanguard, 40
VHF Antenna Book, 42
VHF'er, 77
Waters, 9
Western (Neb.), 90
World Radio Labs, 96, Cover III
73 Books, 67
73 Subscriptions, 63

Propagation Chart

August 1965

J. H. Nelson

EASTERN UNITED STATES TO:

	GMT: 00	02	04	06	08	10	12	14	16	18	20	22
ALASKA	14	14	7	7	7	7	7	7*	14	14	14	14
ARGENTINA	21	14	14	7*	7	7#	14#	14	14	14*	21	21*
AUSTRALIA	14	14	14	7#	7	7	7*	7	7#	7#	14#	14
CANAL ZONE	14	14	7	7	7	7	14	14	14	14	14	21
ENGLAND	14	7	7	7	7	7*	14	14	14	14	14	14
HAWAII	14	14	7*	7	7	7	7	7#	14#	14	14	14
INDIA	14	7#	7#	7#	7#	7#	14#	14	14	14	14	14
JAPAN	14	14#	7#	7	7	7	7*	7*	7#	7#	14#	14
MEXICO	14	14	7	7	7	7	7#	14	14	14	14	14
PHILIPPINES	14	14#	14#	7#	7#	7#	7#	7*	14	14	14#	14
PUERTO RICO	14	7	7	7	7	7	14	14	14	14	14	14
SOUTH AFRICA	7	7	7	7#	7#	14	14	14	14	14	14	14#
U. S. S. R.	7	7	7	7	7	7#	14#	14	14	14	14	14
WEST COAST	14	14	14	7	7	7	7	14	14	14	14	14

CENTRAL UNITED STATES TO:

ALASKA	14	14	14	7	7	7	7	7	7*	14	14	14
ARGENTINA	21	14	14	7*	7	7#	14#	14	14	14	21	21*
AUSTRALIA	14	14	14	7#	7	7	7	7*	7#	7#	14#	14
CANAL ZONE	21	14	7*	7	7	7	14	14	14	14	14	21
ENGLAND	14	7	7	7	7	7	7*	14	14	14	14	14
HAWAII	14	14	14	7	7	7	7	7#	14	14	14	14
INDIA	14	14#	7#	7#	7#	7#	7#	14#	14	14	14	14
JAPAN	14	14#	7#	7	7	7	7	7*	7	7#	14#	14
MEXICO	14	14	7	7	7	7	7	7*	14	14	14	14
PHILIPPINES	14	14	14#	7#	7#	7#	7#	7*	14	14	14#	14
PUERTO RICO	14	14	7	7	7	7	14	14	14	14	14	14
SOUTH AFRICA	7	7	7	7#	7#	7#	14	14	14	14	14	14#
U. S. S. R.	7	7	7	7	7	7#	14#	14	14	14	14	7*

WESTERN UNITED STATES TO:

ALASKA	14	14	14	7*	7	7	7	7	7*	14	14	14
ARGENTINA	21	14	14	7*	7	7	7#	14#	14	14	21	21*
AUSTRALIA	21*	21	21	14	14	7*	7	7	7	7*	14*	14
CANAL ZONE	21	14	14	14	7*	7	7	14	14	14	14	21
ENGLAND	7*	7	7	7	7	7	7#	14#	14	14	14	14
HAWAII	14	21	21	14	7*	7	7	7	14	14	14	14
INDIA	14	14	14	7#	7#	7#	7#	7#	14#	14	14	14
JAPAN	14	14	14	14	7	7	7	7	7#	14#	14	14
MEXICO	14	14	7	7	7	7	7	7*	14	14	14	14
PHILIPPINES	14	14	14	14	14#	7#	7	7	14	14	14#	14
PUERTO RICO	14	14	7*	7	7	7	7	14	14	14	14	14
SOUTH AFRICA	7	7	7*	7#	7#	7#	7#	14	14	14	14	14#
U. S. S. R.	7	7	7	7#	7#	7#	7#	7*	14	14	14	7#
EAST COAST	14	14	14	7	7	7	7	14	14	14	14	14

Very difficult circuit this hour.

* Next higher frequency may be useful this hour.

Good: 1-6, 25-27, 29-31

Fair: 9-14, 16-19, 23, 24, 28


Poor: 7, 8, 15, 20-22

VHF DX: 4-7, 13-15, 22-26

BREAK

THROUGH

\$450⁰⁰
 Includes Separate
POWER SUPPLY

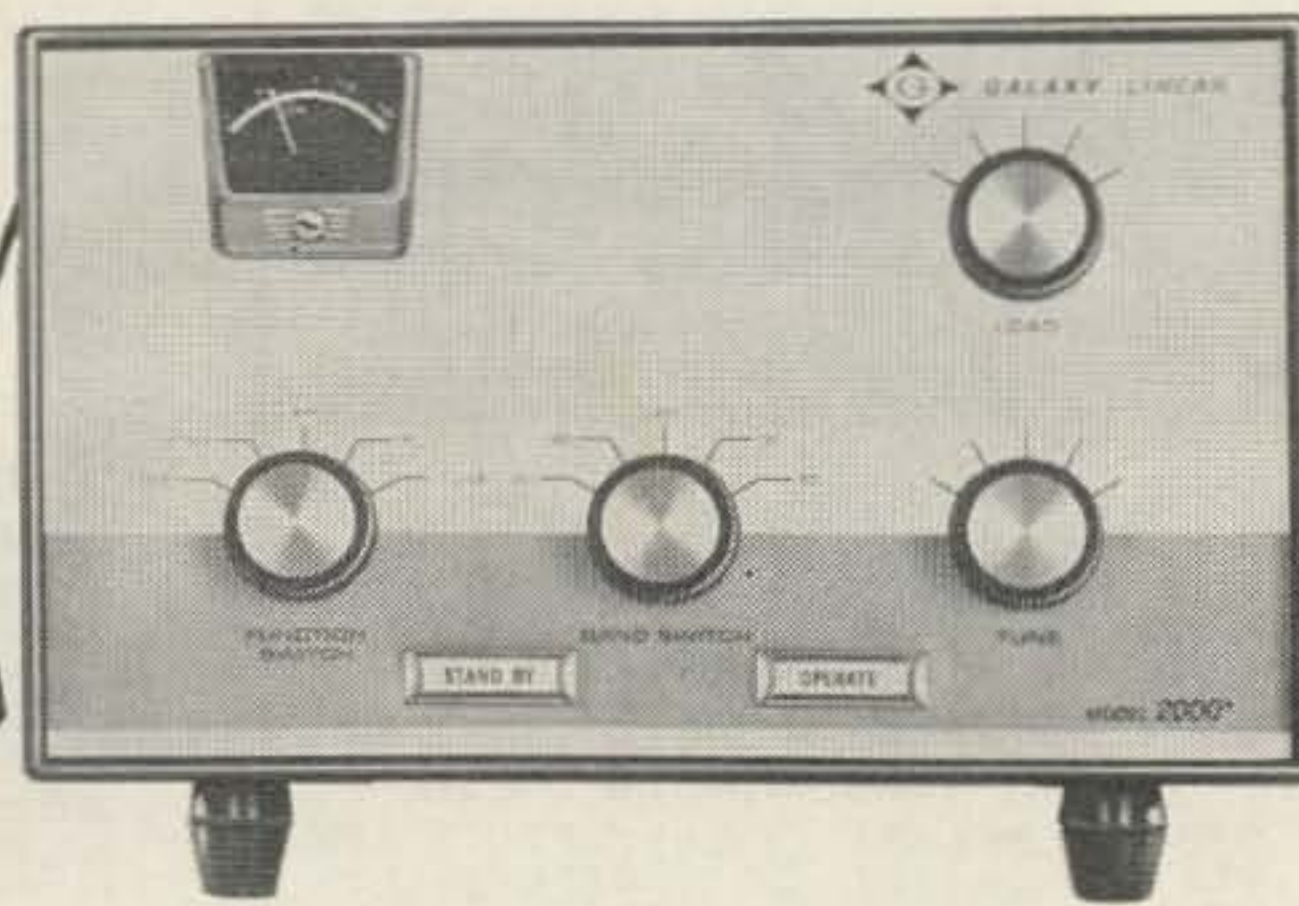

**MORE
 "TALK POWER"
 PER DOLLAR
 Than Ever Before!!**

**WRITE US NOW
 FOR KING SIZE TRADE-INS ON
 YOUR PRESENT GEAR!**

**NOW FOR THE FIRST TIME
 2KW+ TABLE TOP LINEAR FOR UNDER \$500.00
 GUARANTEED! 2KW+ PEP SSB INPUT and 1200
 WATTS PEP OUTPUT, ALL BANDS 80
 THROUGH 10 METERS.**

EXCLUSIVE GALAXY LINEAR FEATURES

- * *Revolutionary new circuit.* Sustains Hi-Efficiency 10-80 Meters.
- * *Most compact 2KW Linear ever made.* R.F. unit just 6" x 10¹/₄" x 11¹/₄". Same as Galaxy III and V.
- * *NEW ALS!* (Automatic Linearity System) An improvement over conventional ALC.
- * *MOST TALK-POWER EVER* in this small size.
- * *Operates AB₁* at all times.
- * *Built-in antenna switching relays.*

MORE OUTSTANDING FEATURES

- * *INPUT: 2,000 Watts PEP-SSB, 1,000 Watts-CW, 1,000 Watts-RTTY.*
- * Complete tube replacement cost under \$30.00.
- * Uses ten 6HF5's in new, efficient design.
- * Full Power from any 100-200 watt output exciter.
- * Tubes fan cooled for longer life.
- * SIMPLIFIED, reduced power tune-up.
- * One knob bandswitching, 80 through 10 meters.
- * High efficiency PI-NET, matches 40/90 Ohms impedance.
- * Built-in, adjustable low-pass filter.
- * 3rd order distortion - 30DB.
- * 115/230 VAC power supply.
- * Shipping weight (Linear and Supply) Approx. 55 lbs.

POWER SUPPLY

Heavy duty power supply has 115/230 VAC primary, conservative 2KW CCS rating with grain-oriented silicon steel core, solid state rectifiers. All cables supplied. Power supply can be placed under desk for operating convenience. Protected by attractive cover.



**GET
 YOUR
 FREE
 '65 CATALOG**

WRL

**WORLD RADIO
 LABORATORIES**

3415 West Broadway
 Council Bluffs, Iowa 51504

- Send information on Linear Amplifier.
- Send quote on separate sheet.
- Send new catalog.


Name _____ Call _____

Address _____

City _____ State _____ Zip _____

NOBODY CAN BEAT OUR ANNIVERSARY

SPECTACULAR TRANSCEIVER SPECIAL

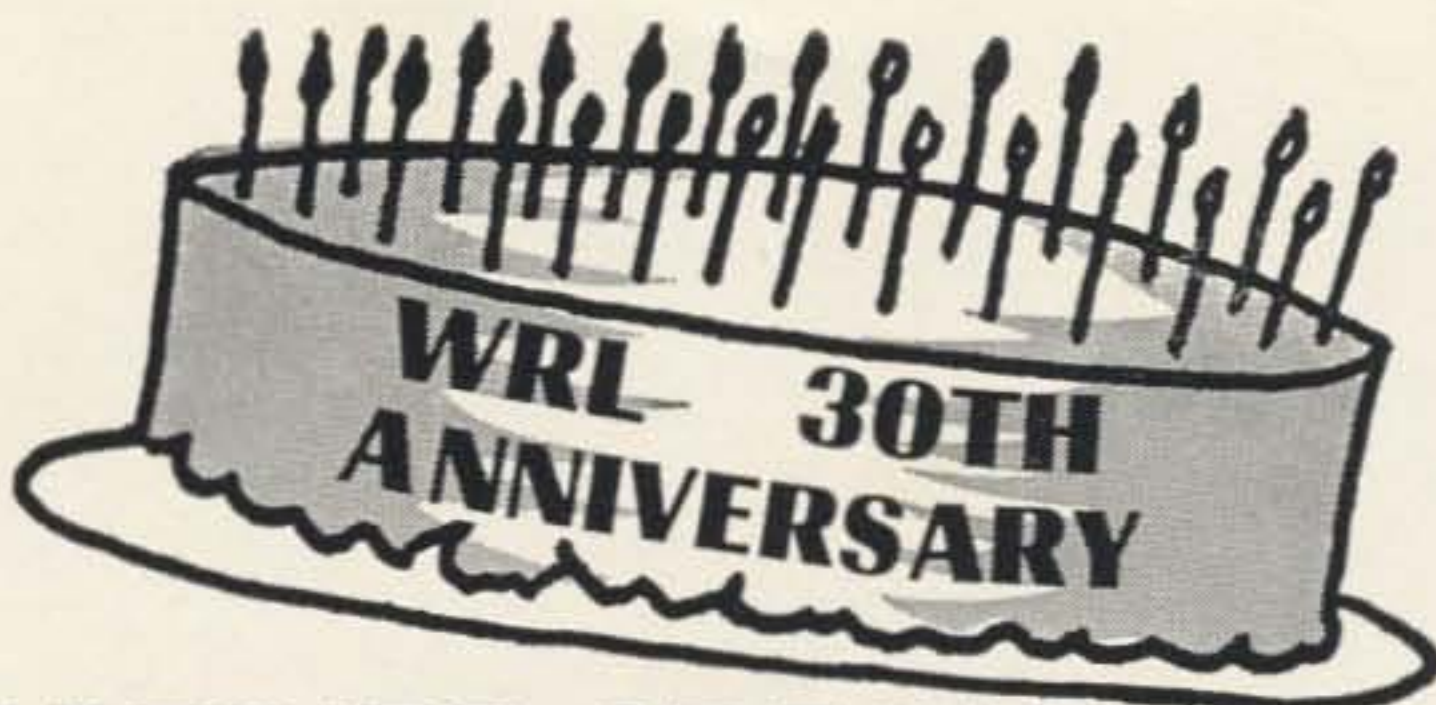

MOBILE GALAXY V

POSITIVELY THE BEST TRANSCEIVER BUY EVER OFFERED THE AMATEUR . . .



REGULARLY PRICED AT \$469.95

NOW JUST \$399.95 SAVE \$70.00

USE WRL'S CHARG-A-PLAN — JUST \$20 MONTHLY


SAVE \$70.00 . . . If you buy now . . . A NEW GALAXY V TRANSCEIVER . . . featuring 300 WATTS PEP SSB/CW; FULL BAND COVERAGE on 80-40-20-15-10 meters . . . and it boasts the BEST — SELECTIVE RECEIVER (because of its 6 Xtal filter); and UPPER and LOWER selectable SIDEBAND!

Don't Forget . . . We're still offering you a 2 WEEK FREE TRIAL* plus you can use our NO DOWN PAYMENT CHARG-A-PLAN.

We'll also allow you WRL'S TOP TRADE-INS on your present gear.

YOU JUST CAN'T GO WRONG! TAKE ADVANTAGE OF THIS SPECIAL OFFER TODAY!

*Write for free trial terms.

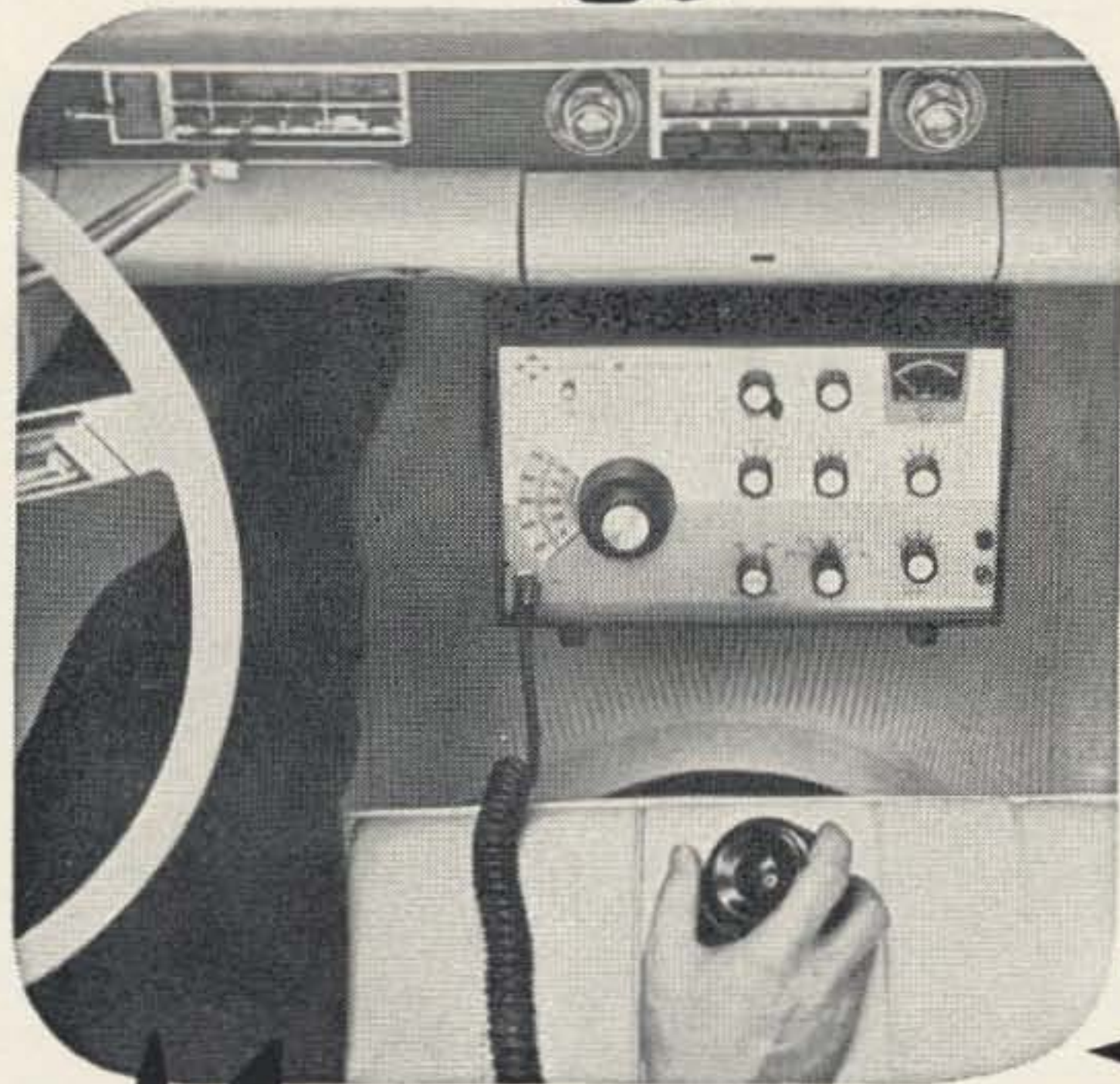

**SPECIAL PURPOSE
VFO covers MARS,
CAP etc. . . \$89.95
write for details**



DC SUPPLY

REGULAR \$119.95

NOW \$89.95

SAVE \$30.00

**GALAXY V & DC P.S.
MOBILE STATION**

\$489.90

SAVE \$100.00

HURRY! OFFER LIMITED TO SUPPLY ON HAND

WRL

WORLD RADIO LABORATORIES
3415 West Broadway
Council Bluffs, Iowa 51504



LEO I. MEYERSON
WØGFQ
PRESIDENT

WORLD RADIO LABORATORIES

3415 West Broadway Council Bluffs, Iowa 51504


- | | |
|--|--|
| <input type="checkbox"/> Send details on Free Trial Offer. | <input type="checkbox"/> Send quote on gear on attached sheet. |
| <input type="checkbox"/> Ship Galaxy V — \$399.95 | <input type="checkbox"/> Send catalog and Reconditioned Listing. |
| <input type="checkbox"/> Ship "Mobile Pkg. V" — \$489.90. | |

Name _____ Call _____

Address _____

City _____ State _____ Zip _____

Live a little

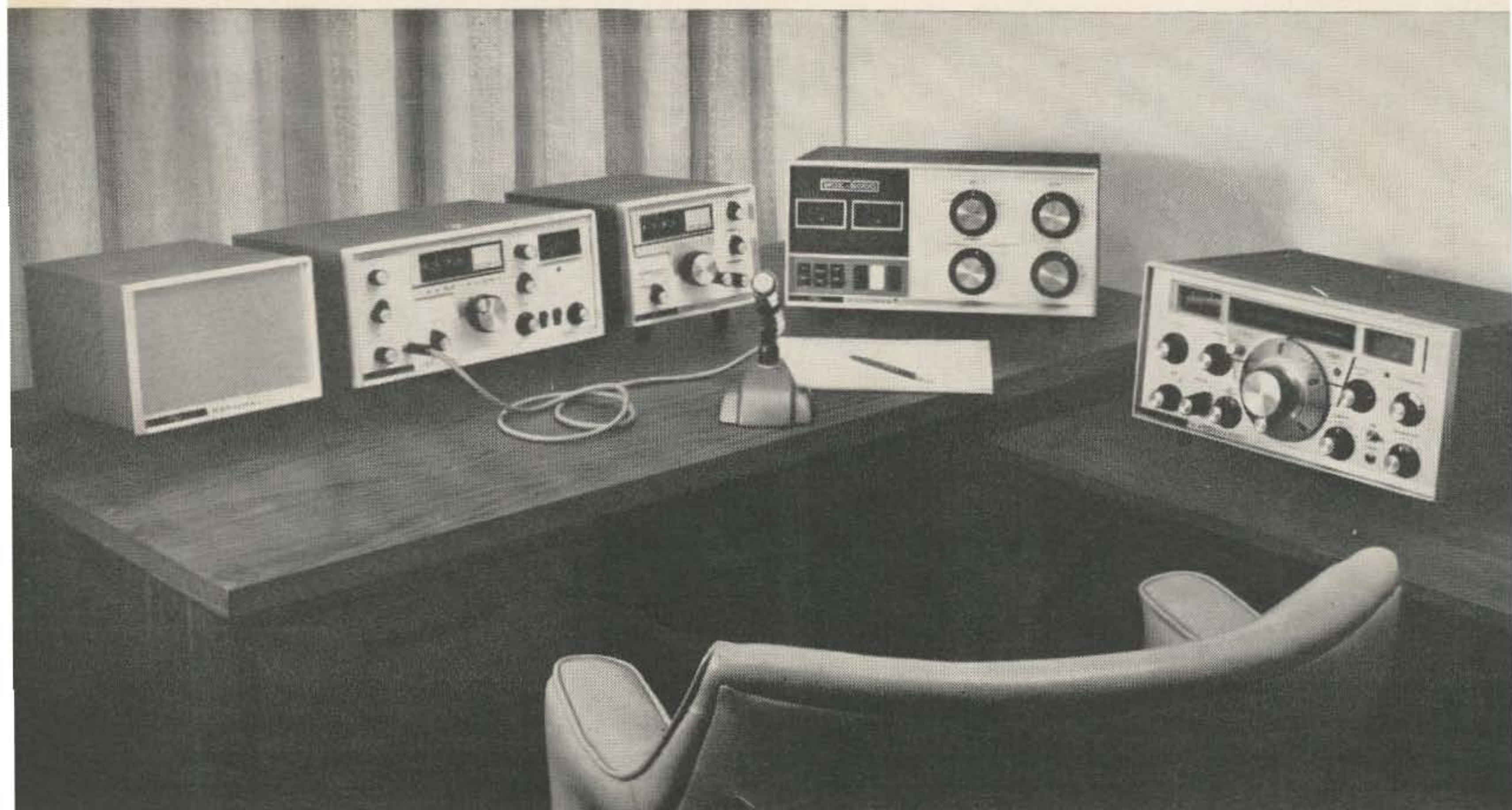

This desk-top amateur station by National includes the NCX-5 all-band transceiver, with digital counter read-out accurate to 1 Kc on each band and **Transceive Vernier** control to provide up to ± 5 Kc separation of receive and transmit frequencies. Transmit-receive selectivity is provided by National's 8-pole crystal filter with greater skirt selectivity than any filter ever manufactured for amateur equipment. The NCX-5 provides operation on upper or lower sideband, compatible AM, or break-in CW. \$685 ■ The NCX-A power supply/speaker console operates from either 115/230 V.A.C. and provides all operating voltages for the NCX-5. \$110 ■ The VX-501 VFO console provides choice of completely independent transmit-receive frequency control of the NCX-5, as well as transceive operation from either VX-501 or NCX-5, and also offers five crystal

channel positions for net or novice use. \$249.95 ■ The NCL-2000 is a completely self-contained 2 Kw SSB PEP linear amplifier for the 80 through 10 meter bands, with minimum peak output of 1300 watts. It may also be operated for CW, AM, or RTTY at 1000 watts DC input. \$685 ■ The HRO-500 is a frequency synthesized and phase-locked solid state receiver covering the five kilocycle through 30 Mc frequency range with identical 1 Kc calibration, high stability from turn-on, and 10 Kc per turn tuning rate throughout. **Passband Tuning** is offered for SSB and CW operation, and IF bandwidths up to 8 Kc are included. Operates from either 115/230 V.A.C. or 12 V.D.C. sources. Power drain from a 12 V. battery (with pilot lamps switched off) is 200 Ma. \$1295 ■ Not pictured is the popular NCX-3 tri-band transceiver, at \$369.