

By the Publishers of
**MECHANIX
ILLUSTRATED**

Extra — 16 PAGES MORE

ELECTRONICS ILLUSTRATED

FEBRUARY • 35¢



Exclusive!

**Radio Powered
Sky Station**

**HOW TO BUILD
POWER SUPPLIES FOR—**

Battery Chargers • Auto Radios
Transistor Radios • Etc.

How To:

Flash Your Photofloods
Wire Radio Control Models



New Tiny Tape Recorders

FAWCETT HOW-TO BOOKS

HANDY MAN'S HOME MANUAL



HANDY MAN'S HOME MANUAL • Block flooring, insulation, built-ins, fences, swimming pool, etc. (No. 426)

Peter Basch Photographs GLAMOROUS WOMEN • Fashion, theater, foreign pin-ups, 200 photos. (No. 425)

Electronics Illustrated HI-FI HANDBOOK • Preamps, cartridges, changers, tuners, AM, FM, stereo. (No. 424)

HOME IMPROVEMENTS You Can Do • Build kitchens, basement playroom, garage, closet, built-ins. (No. 423)

GOOD PHOTOGRAPHY • Beauty portraits, animals, closeups, nudes, fog photos, jazz impressions. (No. 422)

STOCK BUYING GUIDE • Investment clubs, mutual funds, retirement, penny stocks, debentures. (No. 421)
Also available in hard cover edition at \$2.50 per copy.

ATTIC AND BASEMENT IDEAS • Proper planning, stairways, panel walls, ceilings, flooring, etc. (No. 420)

FRED RUSSELL'S CAR CARE • Power steering, carburetors, radiators, tires, batteries, brakes. (No. 419)

LUCIAN CARY ON GUNS • Streamlined firepower, preserve shooting, air guns, rifles, equipment. (No. 418)

RUSSIA and THE BIG RED LIE • Exposes hoax of Soviet supremacy; missiles, air power, space. (No. 417)

Electronics Illustrated HAM RADIO HANDBOOK • Mobile rigs, transmitters, receivers, codes, etc. (No. 416)
Also available in hard cover edition at \$2.50 per copy.

To order direct, send 75c per copy for regular edition or \$2.50 per copy for De Luxe edition to: **FAWCETT BOOKS, Dept. E1, Greenwich, Conn.** Add 10c per copy mailing charge for all books. Specify title and number. Canadian orders cannot be accepted.



PRIZE WINNING PHOTOGRAPHY • Nudes, portraits, children, news, glamour, sport, animals, action. (No. 415)

PLYWOOD PROJECTS You Can Build • Headboards, desk, cabinets, tables, racks, bookcase, divider. (No. 414)

How To Build and Race HOT RODS • Go Karts, dragsters, sports rods, souped T-Bird & Chev V-8, etc. (No. 413)
Also available in hard cover edition at \$2.50 per copy.

PHOTOGRAPHING GLAMOUR • Gowland, Ornitz, Meyer, Yulsman, Jerger and many others. (No. 412)

WATER SKIING HANDBOOK • Fundamentals, equipment, driving boats, motors, jumping, shows. (No. 411)

PHOTOGRAPHY HANDBOOK • Underwater nudes, camera tricks, offbeat glamour, montages. (No. 410)

TV REPAIR AND MAINTENANCE • Receivers, tubes, sockets, sound, antennas, trouble shooting. (No. 409)

NEW GOLF SECRETS OF THE PROS • Hogan, Venturi, Snead, Middlecoff, Casper, Ford, etc. (No. 408)

HOW TO BUILD • Outdoor barbecues, patios, terraces, swimming pools, walls, fences, paths, steps. (No. 407)

BOATING HANDBOOK • Piloting, sail racing, hull and engine care, build a dock, outboards. (No. 406)

CANDID PHOTOGRAPHY • Nudes, glamour, children, humor, animals, camera news, salon section. (No. 405)

A FAWCETT HOW-TO BOOK 75c

AT YOUR LOCAL NEWSSTAND, LEADING DRUG STORE, SUPER MARKET, HARDWARE STORE AND BUILDING SUPPLY DEALER



**A HIGHLY
RESPECTED TRADE—
START SOON TO
EARN EXTRA MONEY
IN SPARE TIME**

Learn at Home IN YOUR SPARE TIME to Fix Electrical Appliances

To build a better future, get into a field where there's much important work and the security that comes from knowing a good trade. Servicing electrical appliances offers that OPPORTUNITY. Every wired home has many electrical appliances and millions and millions of new appliances are sold every year. Owners pay well to keep them in repair. That's making a fast-growing need for trained men.

Add To Your Income Starting Soon Need For Service Technicians Increasing

Make extra money in your spare time. Start soon to fix electric toasters, fans, clocks, vacuum cleaners, and other electric appliances for your neighbors and friends. Work in your basement, garage or spare room. It's easy to increase your earning power—to pay for your training many times over—to have extra money to buy things you need.

Learn and Earn with Multi-Use Tester Built with Parts We Send

This course includes the parts to build a portable, sturdy Appliance Tester that helps you locate electrical defects quickly and easily. You use it to learn and do actual electrical appliance repair jobs. If you want better pay learn this good trade. No need to give up your present

job. You can train at home in your spare time for only \$3.00 down and \$6.00 a month. A small price to pay for increased earnings, a more secure future. Paste coupon below on a postal or mail in envelope for free book and sample lesson. Address **National Radio Institute, Dept. KBO, Washington 16, D. C.**

**MAILING THIS
COUPON MAY START
YOU TO SUCCESS**

**LESSON AND BOOK
FREE**



NATIONAL RADIO INSTITUTE, Dept. KBO, Washington 16, D. C.


Please send me Electric Appliance Training lesson and book (free. (No salesman will call.)

Name Age

Address

City Zone State

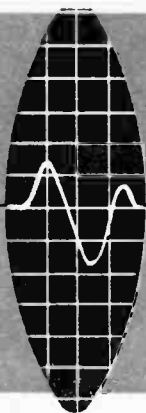ACCREDITED MEMBER NATIONAL HOME STUDY COUNCIL



ELECTRONICS ILLUSTRATED

February, 1960

Vol. 3, No. 2


A Fawcett Publication

CONTENTS



A Message From The Editor	4
Electronics In The News	8
Radio-Powered Sky Station	27
Tweeter Globe	31
New Tiny Tape Recorders	34
Spotlight On 40 Meters	38
SWL Antenna Tuner	42
Flash Your Photofloods	44
Loran Lights The Way	47
CB Beam Antenna	50
Milt Kiver On Probes	52
Make Your Own Probes	56
RCA Voltohmyst Kit	58

All About Ham Nets	60
Try These	64
Design And Build Power Supplies	65
The Fuel Cell	81
Build-It Course — 6	84
TV Around The World	88
Knight-Kit Clock Radio	92
Electronic Brain	94
El Picturescope	96
Radio Aids Driver Trainees	98
Universal Cable Adapter	100
Brainy Man Builds Better Brain	102
Hi-Fi Doctor and Clinic	104

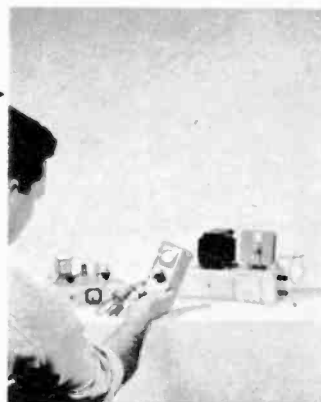

CHARLES TEPPER Editor
 Leonard Buckwalter..... Associate Editor
 Edward Nanas Feature Editor
 David Kipnes..... Assistant Editor
 Murray Cooper..... Art Editor
 Lou Rubsamen..... Art Associate
 Elaine Sapoff..... Editorial Assistant

Larry Eisinger Editor-in-Chief
 Phyllis Bendremer..... Production Editor
 Benita Mills..... Assistant Production Editor
 John F. Webster..... Advertising Manager

Ralph Daigh..... Editorial Director
 James Boynton..... Advertising Director
 Al Allard..... Art Director
 Ralph Maltison..... Associate Art Director
 George N. Carl..... Production Director

ELECTRONICS ILLUSTRATED is published monthly by Fawcett Publications, Inc., Fawcett Place, Greenwich, Conn. W. H. Fawcett, Jr., President; Gordon Fawcett, Secretary and Treasurer; Roger Fawcett, General Manager; Roscoe K. Fawcett, Circulation Director; Donald P. Hanson, Assistant General Manager.

EDITORIAL AND ADVERTISING OFFICES: 67 West 44th Street, New York 36, N. Y.
 ADDRESS ALL MAIL: Subscriptions, change of address, Form 3579 to Circulation Dept., Fawcett Bldg., Greenwich, Conn.; and all editorial and advertising to Fawcett Publications, Inc., 67 W. 44th St., New York 36, N. Y.

Second-class postage paid at Greenwich, Conn., and at additional mailing offices.
 Subscription price \$4.00 per year in the U. S. and possessions and Canada. All other countries \$6.00 per year. Foreign subscriptions and sales should be remitted by International Money Order in U. S. funds payable at Greenwich, Conn.
 Printed in U.S.A. Copyright 1960 by Fawcett Publications, Inc.
 Permission hereby granted to quote from this issue of this magazine on radio or television provided a total of not more than 1,000 words is quoted and credit is given to the title of the magazine and issue, as well as the statement, copyright 1960, by Fawcett Publications, Inc.

These men are getting practical training in...

ELECTRICITY ELECTRONICS



On Real:

- A.C. and D.C. Motors
- Generators
- Switchboards
- Controllers
- Modern Appliances
- Automatic Electronic Control Units


(Shown at left—Instructor explaining operation and testing of a large Motor Generator in our A.C. Department.)

TELEVISION RADIO ELECTRONICS

On Real:

- Television Receivers
- Black & White and Color
- AM-FM and Auto Radios
- Transistors—Printed Circuits—Test Equipment

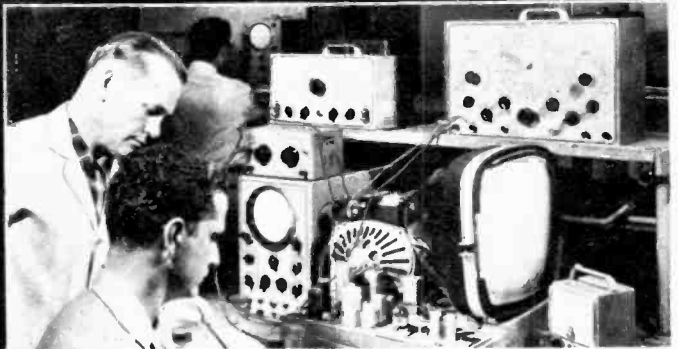(Right — Instructor helping students check the wiring and trace circuits of television receivers.)



Train in the NEW SHOP-LABS of COYNE

Largest, Oldest, Best Equipped School of its Kind in the U.S.

Prepare for your future now in today's top opportunity field. Don't be satisfied with a "No Future" job. Train the Coyne way for a better job in a field that offers a world of opportunities in the years ahead.

You train in Chicago—the Electrical and Electronic Center of the World—on real equipment. Professional and experienced instructors show you how, then you do practical jobs yourself. No previous experience or advanced education is needed.

FINANCE PLAN: Enroll now, pay most of tuition after graduation. Part-time employment help for students.

Mail coupon or write to address below for free book—"Guide to Careers". Whether you prefer Electricity, Television-Radio or Combined Electronics Training, which includes both fields, this book describes all training and gives facts to Vets and Non-Vets.



Mail Coupon or Write for FREE Book

Book comes by mail. No obligation and no salesman will call.

Mail coupon below in an Envelope or paste on a Postal Card or write Address given and Free book, "Guide to Careers", with information will be sent to you by return mail.

COYNE ELECTRICAL SCHOOL
Dept. 20-8C, New Coyne Building
1501 W. Congress Pkwy., Chicago 7, Illinois

Send **BIG FREE** book and details of all the training you offer. However, I am especially interested in:

- Electricity Television Both Fields

Name _____

Address _____

City _____ State _____

(I understand no Salesman will call)

B. W. Cook, Jr., Pres. **COYNE** Founded 1899
ELECTRICAL SCHOOL

CHARTERED AS AN EDUCATIONAL INSTITUTION NOT FOR PROFIT
1501 W. CONGRESS PARKWAY, CHICAGO 7 Dept. 20-8C
ELECTRICITY ★ RADIO ★ TELEVISION ★ REFRIGERATION ★ ELECTRONICS

A Message From the Editor

IT seems we have underestimated the technical knowhow of our readers. Believing that our magazine would be most popular with electronic kit builders and those who have never built any electronic device before, we intentionally de-emphasized the schematic diagrams in our construction articles and developed the unique wiring guides which have become our trademark. These guides are so easy to follow that we assumed our schematic-reading constructors would use them also. Well, we have done many of our construction fans a great injustice. We have received many letters from you asking us to make our schematics bigger and easier to read, and this we are doing promptly. As you will notice in this issue, our schematics are now larger and clearer. As some of the letters indicate, many of the complainers were those who could not read the schematics to begin with, but have learned by reading *EI* regularly. Good, this is a step in the right direction.

Not so long ago in this column I promised to bring you an article on amateur radio informational networks and I am pleased to say that it appears on page 60 in this issue. It took some doing to find the man who we think knows as much or more about this subject as anyone in hamming today, but we think we found him. If you are looking for one more good reason for becoming a ham, read this story. Two other exciting stories

in this issue are: "Radio Powered Sky Station," (page 27), and "New Tiny Tape Recorders," (page 34). Our article on the sky station is the first detailed story on this epic making advance to appear in any of the electronic publications. Although the one on our cover actually appears to be flying, I must admit that it was a rigged shot since the device we photographed was a static display model. However, I can tell you that the Raytheon Company has actually demonstrated a flying model to the government, but turn to page 27 to get the full story.

We had no idea as to how many tiny battery-operated tape recorders there were available at a modest price until we started to investigate the field for our story. Most of the units in our story are imported from Japan or Europe, and if you have not seen them it is because their



Coming next month! *EI*'s all transistor organ

In Spare Time at Home—Prepare for a Better Job—or
Your Own Business in One of the Many Branches of

ELECTRONICS

You build and keep this valuable
Vacuum Tube
VOLTMETER

You build and keep this 5-
inch COLOR OSCILLOSCOPE
—almost a "mu" for TV
servicing.

COLOR TV

DeVry Tech's
program also
includes training
in Color Television

HOME MOVIES . . .

. . . make important points crystal
clear. Speeds your learning. It's
almost like having an instructor
at your side!

MILITARY SERVICE

If you are subject to military
service, the information we
have should prove very
helpful. Mail coupon to-
day.

RADIO - TELEVISION - RADAR

If you are seeking a better job or a business of your own,
the appealing field of Television-Radio-Electronics offers
REAL PROMISE!

In this fast-growing field, trained Electronic technicians find
many good-paying, interesting jobs in manufacturing, in-
stalling, operating, servicing. Equally important is the fact
that these are **GOOD JOBS**—offering the kind of a future
that an untrained man often dreams about.

No previous technical experi-
ence or advanced education
needed. Prepare for this profit-
able field in your spare time
at home, or in our modern
Chicago or Toronto Labora-
tories. Nothing else like it!
Send for **FREE** details.

EARN WHILE YOU LEARN

After you get part of DeVry Tech's
training with equipment at home,
you may then in your spare time,
begin to earn real money serv-
icing Radio and Television sets.

21 INCH

Build and keep this BIG
DeVry Engineered TV set—
easily converted to U.H.F.
(DeVry offers another home
training, but without
the TV set.)

Your GUIDE

to Profitable Job Opportunities

TV-Radio Broadcast Technician
Color Television Specialist
Radar Operator • Laboratory Technician
Airline Radio Man • Computer Specialist
Quality Control Manager
Your Own Sales & Service Shop
PLUS MANY OTHERS

YOU GET THE SAME EMPLOYMENT SERVICE

that has helped thousands of our graduates
toward fine careers in Electronics.



Build over 300 practical projects from many shipments of
Radio-Electronic parts. You build and operate TV-Radio
circuits . . . wireless microphone . . . and many other major
projects—all designed to provide outstanding practical
experience at home.

Send for **FREE BOOKLET TODAY!**

Accredited Member of National Home Study Council

"One of North America's
Foremost Electronics
Training Centers"



DeVRY TECHNICAL INSTITUTE

CHICAGO 41, ILLINOIS

ACT NOW! Get information-packed publica-
tion **FREE!** Mail coupon today.

DeVRY TECHNICAL INSTITUTE

4141 Belmont Ave., Chicago 41, Ill., Dept. EI-2-Q

Please give me your **FREE** booklet, "Electronics and YOU," and
tell me how I may prepare to enter one or more branches of
Electronics.

Name _____ Age _____

PLEASE PRINT

Street _____ Apt. _____

City _____ Zone _____ State _____

2044 Canadian residents address DeVry Tech of Canada, Ltd.
626 Roselawn Ave., Toronto 12, Ontario

Complete Training

FOR BETTER RADIO-TV SERVICE JOBS



Let these two great Ghirardi training books teach you to handle all types of AM, FM and TV service jobs by approved professional methods—and watch your efficiency and earnings soar!

Each book is a complete service training guide. Each contains complete data on modern methods and equipment—NOT a re-hash of old, out-of-date material. Each is co-authored by A. A. Ghirardi whose famous RADIO PHYSICS COURSE and MODERN RADIO SERVICING were, for 20 years, more widely used for military, school and home study training than any other books of their type!

THE NEW Ghirardi RADIO-TV SERVICE LIBRARY

Almost 1500 pages and over 800 clear illustrations show step-by-step how to handle every phase of troubleshooting and servicing.

1—Radio and Television Receiver TROUBLESHOOTING AND REPAIR

A complete guide to profitable professional methods. For the beginner, it is a comprehensive training course. For the experienced serviceman, it is a quick way to "brush up" on specific jobs, to develop improved techniques or to find fast answers to puzzling service problems. Includes invaluable "step-by-step" service charts. 820 pages, 417 illus., price \$7.50 separately.

2—Radio and Television Receiver CIRCUITRY AND OPERATION

This 669-page volume is the ideal guide for servicemen who realize it pays to know what really makes modern radio-TV receivers "tick" and why. Gives a complete understanding of basic circuits and circuit variations; how to recognize them at a glance; how to eliminate guesswork and useless testing in servicing them. 417 illus. Price separately \$6.75.

Special low price . . . you save \$1.25

If broken into lesson form and sent to you as a "course," you'd regard these two great books as a bargain at \$50 or more!

Under this new offer, you save \$1.25 on the price of the two books—and have the privilege of paying in easy installments while you use them! No lessons to wait for. You learn fast—and right!

(Order from: Dept. PR-20, Rinehart & Co., Inc., 232 Madison Ave., New York 16, N. Y. (Price only \$13.00 plus postage for both books.)

STUDY 10 DAYS FREE.

Dept. PR-20, RINEHART & CO., Inc.

232 Madison Ave., New York 16, N. Y.

Send books below for 10-day FREE EXAMINATION. In 10 days I will either remit price indicated (plus postage) or return books postpaid and owe you nothing.

Radio & TV Receiver TROUBLESHOOTING & REPAIR (Price \$7.50 separately)

Radio & TV CIRCUITRY & OPERATION (Price \$6.75)

Check here for MONEY-SAVING COMBINATION OFFER . . . Save \$1.25. Send both of above big books at special price of only \$13.00 for the two. (Regular price \$14.25 . . . you save \$1.25) Payable at rate of \$4 plus postage after 10 days if you decide to keep books and \$3 a month for 3 months until the total of \$13.00 has been paid.

Name _____

Address _____

City, Zone, State _____

Outside U.S.A.—\$8.00 for TROUBLESHOOTING & REPAIR; \$7.25 for CIRCUITRY & OPERATION; \$14.00 for both. Cash only, but money refunded if you return books in 10 days.

importers didn't feel that a mass market existed for them. Our story may change all this.

Not long ago *EI* regular Harry Kursh did a story for us on how to patent an electronic invention. The facts he dug up proved so fascinating that he followed them up and the result is his new book called, "Inside the U.S. Patent Office," published by W. W. Norton & Co., Inc., New York City. I recommend this book very highly to anyone interested in how our patent system works, and how to obtain a patent on new ideas.

Although commercial television is not a startling new innovation to our readers, it is still a subject of great interest. You may be interested, therefore, in some recently acquired statistics relative to TV in various countries of the world. It is presently estimated that there are about 85,000,000 TV sets in use in the world today. The United States alone has about 57,000,000. U. S. viewers have available to them 550 TV broadcast stations. The rest of the world at large has 965 stations. This should give you some idea of the tremendous interference problem that would be involved if some satellite could reflect all signals from earth back down again to all sets within view.

Our March issue will be jammed with many exciting construction and feature articles. Our special 16-page bonus section will show you, in clear diagrams, photos and text, how to build an *all-transistor electronic organ*. Among electronic constructors, this type of item has consistently been one of the most popular. We have tested the *EI* organ using local editorial talent and we can authoritatively say that whereas we may not have struck the right keys at all times, at least the organ knew what it was doing. We will also bring you a construction article on how to build a 2-way Citizens Band radio as well as a feature article describing the newest items for stereo hi-fi.

Be sure to be with us next month.

Charles Tupper

This story actually happened. The man's name has been changed and this is not his photograph, but the facts are true.

"Your name is on the list"



Doug Mott was not surprised. The recession was on and the assembly line where he worked was almost at a standstill.

And then, strangely, the boss began to smile. "You know how the Engineering Department sends us blueprints and then we have to send them back for revision because they just aren't practical to produce?" Doug nodded . . . wondering. "That's waste . . . and we can't allow it to continue. That's why we thought that if we had a man who knew assembly and production — and drafting, too — he could act as liaison man between engineering and production. You know production, Doug . . . and you're studying drafting with I.C.S. You've got a *new* job. Congratulations!"

Doug Mott now heads a drafting room. But he will never forget the day his name was on the list to be laid off.

Good times or bad, I. C. S. training sets a man off from his fellows, puts him on the road to promotion. You can start on that road by filling out the coupon *now!*

For Real Job Security—Get an I. C. S. Diploma!

I. C. S., Scranton 15, Penna.

Accredited Member,
National Home Study Council

INTERNATIONAL CORRESPONDENCE SCHOOLS



BOX 58574A, SCRANTON 15, PENNA.

(Partial list of 258 courses)

Without cost or obligation, send me "HOW TO SUCCEED" and the opportunity booklet about the field BEFORE which I have marked X (plus sample lesson):


- | | | | | |
|--|--|--|---|---|
| <p>ARCHITECTURE and BUILDING CONSTRUCTION</p> <ul style="list-style-type: none"> <input type="checkbox"/> Air Conditioning <input type="checkbox"/> Architecture <input type="checkbox"/> Arch. Drawing and Designing <input type="checkbox"/> Building Contractor <input type="checkbox"/> Building Estimator <input type="checkbox"/> Carpenter Builder <input type="checkbox"/> Carpentry and Millwork <input type="checkbox"/> Carpenter Foreman <input type="checkbox"/> Heating <input type="checkbox"/> Painting Contractor <input type="checkbox"/> Plumbing <input type="checkbox"/> Reading Arch. Blueprints <p>ART</p> <ul style="list-style-type: none"> <input type="checkbox"/> Commercial Art <input type="checkbox"/> Magazine Illus. <input type="checkbox"/> Show Card and Sign Lettering <input type="checkbox"/> Sketching and Painting <p>AUTOMOTIVE</p> <ul style="list-style-type: none"> <input type="checkbox"/> Automobile <input type="checkbox"/> Auto Body Rebuilding and Refinishing <input type="checkbox"/> Auto Engine Tuneup <input type="checkbox"/> Auto Technician | <p>AVIATION</p> <ul style="list-style-type: none"> <input type="checkbox"/> Aero-Engineering Technology <input type="checkbox"/> Aircraft & Engine Mechanic <p>BUSINESS</p> <ul style="list-style-type: none"> <input type="checkbox"/> Accounting <input type="checkbox"/> Advertising <input type="checkbox"/> Business Administration <input type="checkbox"/> Business Management <input type="checkbox"/> Cost Accounting <input type="checkbox"/> Creative Salesmanship <input type="checkbox"/> Managing a Small Business <input type="checkbox"/> Professional Secretary <input type="checkbox"/> Public Accounting <input type="checkbox"/> Purchasing Agent <input type="checkbox"/> Salesmanship <input type="checkbox"/> Salesmanship and Management <input type="checkbox"/> Traffic Management <p>CHEMICAL</p> <ul style="list-style-type: none"> <input type="checkbox"/> Analytical Chemistry <input type="checkbox"/> Chemical Engineering <input type="checkbox"/> Chem. Lab. Technician <input type="checkbox"/> Elements of Nuclear Energy <input type="checkbox"/> General Chemistry <input type="checkbox"/> Natural Gas Prod. and Trans. <input type="checkbox"/> Petroleum Prod. and Engr. <input type="checkbox"/> Professional Engineer (Chem) <input type="checkbox"/> Pulp and Paper Making | <p>CIVIL ENGINEERING</p> <ul style="list-style-type: none"> <input type="checkbox"/> Civil Engineering <input type="checkbox"/> Construction Engineering <input type="checkbox"/> Highway Engineering <input type="checkbox"/> Professional Engineer (Civil) <input type="checkbox"/> Reading Struc. Blueprints <input type="checkbox"/> Sanitary Engineer <input type="checkbox"/> Structural Engineering <input type="checkbox"/> Surveying and Mapping <p>DRAFTING</p> <ul style="list-style-type: none"> <input type="checkbox"/> Aircraft Drafting <input type="checkbox"/> Architectural Drafting <input type="checkbox"/> Drafting & Machine Design <input type="checkbox"/> Electrical Drafting <input type="checkbox"/> Mechanical Drafting <input type="checkbox"/> Sheet Metal Drafting <input type="checkbox"/> Structural Drafting <p>ELECTRICAL</p> <ul style="list-style-type: none"> <input type="checkbox"/> Electrical Engineering <input type="checkbox"/> Elec. Engr. Technician <input type="checkbox"/> Elec. Light and Power <input type="checkbox"/> Practical Electrician <input type="checkbox"/> Practical Lineman <input type="checkbox"/> Professional Engineer (Elec) <p>HIGH SCHOOL</p> <ul style="list-style-type: none"> <input type="checkbox"/> High School Diploma | <ul style="list-style-type: none"> <input type="checkbox"/> Good English <input type="checkbox"/> High School Mathematics <input type="checkbox"/> High School Science <input type="checkbox"/> Short Story Writing <p>LEADERSHIP</p> <ul style="list-style-type: none"> <input type="checkbox"/> Industrial Foremanship <input type="checkbox"/> Industrial Supervision <input type="checkbox"/> Personnel-Labor Relations <input type="checkbox"/> Supervision <p>MECHANICAL and SHOP</p> <ul style="list-style-type: none"> <input type="checkbox"/> Diesel Engines <input type="checkbox"/> Gas-Elec. Welding <input type="checkbox"/> Industrial Engineering <input type="checkbox"/> Industrial Instrumentation <input type="checkbox"/> Industrial Metallurgy <input type="checkbox"/> Industrial Safety <input type="checkbox"/> Machine Shop Practice <input type="checkbox"/> Mechanical Engineering <input type="checkbox"/> Professional Engineer (Mech) <input type="checkbox"/> Quality Control <input type="checkbox"/> Reading Shop Blueprints <input type="checkbox"/> Refrigeration and Air Conditioning <input type="checkbox"/> Tool Design <input type="checkbox"/> Tool Making <p>RADIO, TELEVISION</p> <ul style="list-style-type: none"> <input type="checkbox"/> General Electronics Tech. | <ul style="list-style-type: none"> <input type="checkbox"/> Industrial Electronics <input type="checkbox"/> Practical Radio-TV Engr'g <input type="checkbox"/> Practical Telephony <input type="checkbox"/> Radio-TV Servicing <p>RAILROAD</p> <ul style="list-style-type: none"> <input type="checkbox"/> Car Inspector and Air Brake <input type="checkbox"/> Diesel Electrician <input type="checkbox"/> Diesel Engr. and Fireman <input type="checkbox"/> Diesel Locomotive <p>STEAM and DIESEL POWER</p> <ul style="list-style-type: none"> <input type="checkbox"/> Combustion Engineering <input type="checkbox"/> Power Plant Engineer <input type="checkbox"/> Stationary Diesel Engr. <input type="checkbox"/> Stationary Fireman <p>TEXTILE</p> <ul style="list-style-type: none"> <input type="checkbox"/> Carding and Spinning <input type="checkbox"/> Cotton Manufacture <input type="checkbox"/> Cotton Waring and Weaving <input type="checkbox"/> Loom Flxing Technician <input type="checkbox"/> Textile Designing <input type="checkbox"/> Textile Finishing & Dyeing <input type="checkbox"/> Throwing <input type="checkbox"/> Warping and Weaving <input type="checkbox"/> Worsted Manufacturing |
|--|--|--|---|---|

Name _____ Age _____ Home Address _____
 City _____ Zone _____ State _____ Working Hours _____ A. M. to P. M. _____
 Occupation _____



Canadian residents send coupon to International Correspondence Schools, Canadian, Ltd., Montreal, Canada. . . . Special low monthly tuition rates to members of the U. S. Armed Forces.



Electronics
in the news

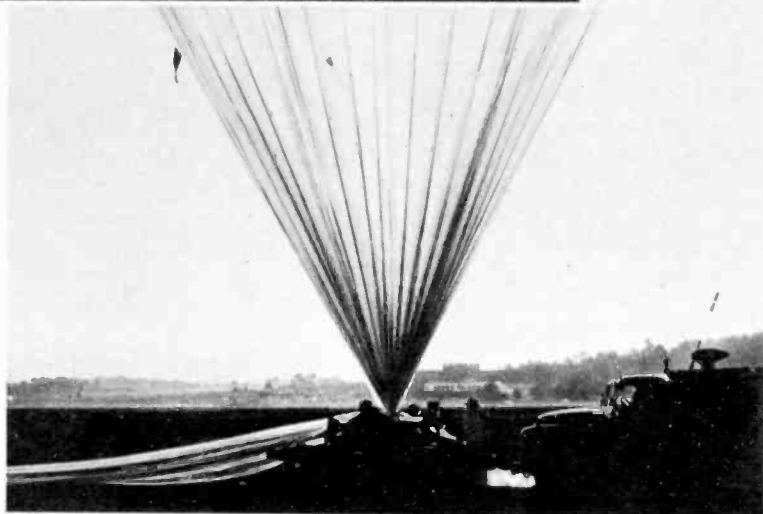

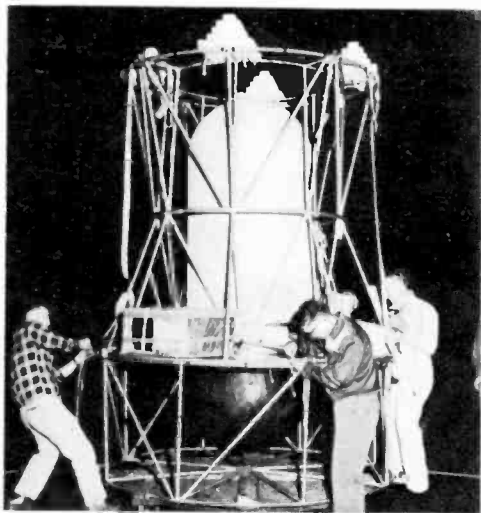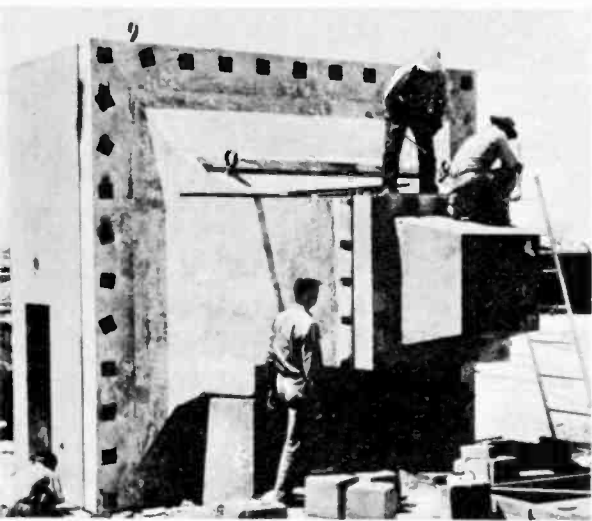In an attempt to learn more about radar characteristics at stratospheric altitudes, scientists at Goodyear have developed the radar unit at right to take aerial radar photos of the earth. Carried aloft by the unmanned balloon above, the radar does its job and is returned to earth by a radio controlled signal.



Audiophiles! Dig this crazy 53-ton loudspeaker horn at left. As part of an eventual 100-ton acoustical test chamber at Goodyear Aircraft Corporation, this device will be used to direct sound to plane-wave and reverberant type chambers. The chamber is to be used to study sound waves and their effect on electronic components used in supersonic aircraft.

NOW!
at a price
you can afford!

MAKE MORE MONEY in TELEVISION RADIO-ELECTRONICS

BETTER...MORE COMPLETE...LOWER COST..
WITH NATIONAL SCHOOLS SHOP-METHOD
HOME TRAINING!

BETTER... Training that is proved and tested
in Resident School shops and
laboratories, by a School that is
the **OLDEST** and **LARGEST** of
its kind in the world.

MORE COMPLETE... You learn **ALL PHASES** of
Television-Radio-Electronics.

LOWER COST... Other schools make several courses
out of the material in our **ONE**
MASTER COURSE... and you
pay more for less training than
you get in *our course* at **CHEAP**
LOW TUITION!



These
two FREE books will
show you how!

You get all information
by mail... You make
your own decision... at
home! **NO SALESMAN**
WILL CALL!

TOP PAY... UNLIMITED OPPORTUNITIES LIFETIME SECURITY CAN BE YOURS!

You are needed in the Television, Radio, and Electronics industry! Trained technicians are in growing demand at excellent pay—in **ALL PHASES**, including Servicing, Manufacturing, Broadcasting and Communications, Automation, Radar, Government Missile Projects.

NATIONAL SCHOOLS SHOP-METHOD HOME TRAINING, with newly added lessons and equipment, trains you in your spare time at home, for these unlimited opportunities, including many technical jobs leading to supervisory positions.

YOU LEARN BY BUILDING EQUIPMENT WITH KITS AND PARTS WE SEND YOU. Your National Schools course includes thorough *Practical* training—**YOU LEARN BY DOING!** We send you complete standard equipment of professional quality for building various experimental and test units. You advance step by step, perform more than 100 experiments, and you build a complete TV set from the ground up, that is yours to keep! A big, new TV picture tube is included at no extra charge.

EARN AS YOU LEARN. We'll show you how to earn extra money right from the start. Many of our students pay for their course—and more—while studying. So can you!

RESIDENT TRAINING AT LOS ANGELES

If you wish to take your training in our Resident School at Los Angeles, the world's TV capital, start **NOW** in our big, modern Shops, Labs and Radio-TV Studios. Here you work with latest Electronic equipment—professionally installed—finest, most complete facilities offered by any school. Expert, friendly instructors. Personal attention. Graduate Employment Service. Help in finding home near school—part time job while you learn. Check box in coupon for full information.

LESSONS AND INSTRUCTION MATERIAL ARE UP-TO-DATE, PRACTICAL, INTERESTING. Every National Schools Shop-Method lesson is made easy to understand by numerous illustrations and diagrams. All instruction material has been developed and tested in our own Resident School Shops, Laboratories and Studios.

SEND FOR INFORMATION TODAY... it can mean the difference between **SUCCESS** and failure for you! Send for your **FREE BOOK** "Your Future in Television-Radio-Electronics" and **FREE Sample Lesson**. Do it **TODAY**, while you are thinking about your future. It doesn't cost you anything to investigate!

GET THE BENEFITS OF OUR OVER 50 YEARS EXPERIENCE

Approved for
GI Training



NATIONAL SCHOOLS

Los Angeles 37, Calif.

YOU GET...

- 19 Big Kits—**YOURS TO KEEP!**
- Friendly Instruction and Guidance
- Job Placement Service
- Unlimited Consultation
- Diploma—Recognized by Industry
- **EVERYTHING YOU NEED FOR SUCCESS!**

**SHOP-METHOD HOME TRAINING
COVERS ALL PHASES OF INDUSTRY**

1. Television, including Color TV
2. Radio AM & FM
3. Electronics for Guided Missiles
4. Sound Recording and Hi-Fidelity
5. FCC License
6. Automation and Computers
7. Radar & Micro-Waves
8. Broadcasting and Communications

NATIONAL TECHNICAL SCHOOLS

WORLD-WIDE TRAINING SINCE 1905

MAIL NOW TO

NATIONAL SCHOOLS, Dept R4Y-10
4000 S. FIGUEROA ST. LOS ANGELES 37, CALIF.

Rush free TV-Radio "Opportunity" Book and sample lesson. No salesman will call.

NAME _____ AGE _____

ADDRESS _____

CITY _____ ZONE _____ STATE _____

Check if interested **ONLY** in Resident School training at Los Angeles
 VETERANS Give date of Discharge _____

Learn **ELECTRIC** **APPLIANCE REPAIR** IN YOUR *Spare Time at Home*



START YOUR OWN BUSINESS

With a Potential Market of 100,000 Customers

New shop-method, home training system gives you electrical know-how that used to take years to learn. Learn at home by building valuable testing kits, repairing your own and neighbor's appliances. It is not unusual for appliance repairmen to charge on the basis of \$5.00-\$6.00 an hour. **FREE ILLUSTRATED BOOK** Shows you how to learn every phase of electrical appliance repair. How to make money while you learn. Write today for your **FREE** copy.

CHRISTY TRADES SCHOOL, Dept. A-213

3214 W. Lawrence Ave., Chicago 25, Illinois

NOW!

Step ahead faster as an **INDUSTRIAL ELECTRONICS TECHNICIAN**

Turn your experience into a big, new better-paying career!

Day by day industrial plants are adding more electronic devices—for sorting, counting, checking almost any control job you can name. Cash in on industry's great need for men who can keep these devices in top working order. Make more money, feel more secure, doing work that is second nature to you. With what you already know about electronics you have a long head start in a field just beginning to boom. GET INTO IT RIGHT NOW with the help of

PRACTICAL INDUSTRIAL ELECTRONICS LIBRARY

No long sessions on math or theory! These 4 practical volumes show you how to keep the plant's electronic equipment working . . . how to locate and correct tube and circuit troubles . . . how to install, service, and maintain even brand new equipment without being stumped by new circuits.



EASY TERMS FREE TRIAL—

4 volumes (1369 pp., 1102 illus.); Chuce's Electronics in Industry

Miller's Maintenance Manual of Electronic Control.

Markus & Zeffiff's Handbook of Industrial Electronics Circuits.

Henney & Fahnestock's Electron Tubes in Industry.

McGraw-Hill Book Co., 327 W. 41st St., NYC 36, Dept. E1-2

Send me the Practical Industrial Electronics Library for 10 days' examination on approval. In 10 days I will send \$3.50, then \$5.00 a month until \$23.50 is paid. (A saving of \$5.00 under the regular price of \$28.50.) Otherwise I will return books postpaid.

(Print) Name _____

Address _____

City _____ Zone _____ State _____

Company _____

Position _____ E1-2


This offer applies in U.S. only.

...News



National Sonics Corp. has introduced a build-it-yourself electronic organ featuring two keyboards, built-in speakers, etc. A brochure giving full details is available from the manufacturer, 680 E. Taylor Ave., Sunnyvale, California.

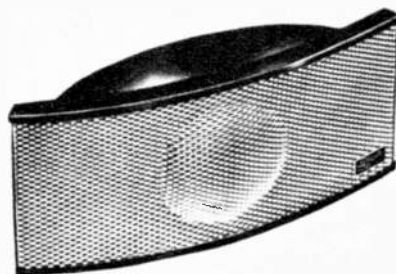RCA is now producing a ceramic-metal superpower tube especially designed for use in long-range search-radar and particle-accelerator service. This water-cooled tube can provide a useful peak power output of 1.5 million watts at 200 mc for a pulse duration of 2500 microseconds.



Lafayette Radio has placed the new SK-131 "Sphericon" tweeter on the hi-fi market. Priced at \$19.50, it is equipped with a built-in 3000 cycle crossover network. Complete specifications available from Lafayette at 165-08 Liberty Avenue, Jamaica, N. Y.

**AT
LAST!**

RADIO-TV and ELECTRONICS TRAINING

**... AT A PRICE
YOU CAN AFFORD!**



***21 INCH**
Receiver Kit included

Yes, this great course costs far less than any training of its kind given by other major schools! Radio-Television Training School will train you for a good job in Television or Industrial Electronics — **AT HOME IN YOUR SPARE TIME.**

Think of it — a complete training program including over 120 lessons. Fourteen Big Radio-Television Kits, Complete Color-TV Instruction, Unlimited Consultation Service... **ALL at a really big saving to you.** How can we do this? Write to us today... and find out!

And what's more — you can (if you wish)
**OPEN YOUR OWN RTS-APPROVED AND
FINANCED RADIO-TV SERVICE SHOP**

We Want Many More Shops This Year

This 38 year old training organization — called RTS, that's Radio-Television Training School — wants to establish a string of Radio-TV Repair Shops in principal cities throughout the U. S. So far, a great many such shops are **NOW IN BUSINESS AND PROSPERING.** We are helping and training ambitious men to become future owners and operators of these shops in all areas.

**FOR UNSKILLED
INEXPERIENCED MEN ONLY —
WE TRAIN YOU OUR WAY!**

We must insist that the men we sign up be trained in Radio-TV Repair, Merchandising and Sales by our training methods—because **WE KNOW** the requirements of the industry. Therefore, we will **TRAIN YOU**... we will show you how to earn **EXTRA CASH**, during the first month or two of your training period. **YOU KEEP YOUR PRESENT JOB. TRAINING TAKES PLACE IN YOUR OWN HOME. IN YOUR SPARE TIME!**



Get your free book on the
FAMOUS RTS BUSINESS PLAN
find out how you can open
A REPAIR SHOP OF YOUR OWN


We supply and finance your equipment

When you are ready and qualified to operate one of our RTS-Approved TV Repair Shops **WE WILL SUPPLY AND FINANCE EVERY BIT OF EQUIPMENT YOU NEED TO GET STARTED** plus an inventory of parts and supplies. In other words we will stake you **AN OFFER NEVER MADE BEFORE BY ANY TRAINING ORGANIZATION.** Under the RTS Business Plan you receive:

1. An electric sign for the shop front.
2. Complete laboratory of test equipment.
3. Letterheads, calling cards, repair tickets, etc.
4. Basic inventory of tubes, parts, supplies.
5. Complete advertising and promotional material.
6. Plans for shop arrangement.
7. Instructions on how to go into business.
8. Continuous consultation and help.
9. The right to use RTS Seal of Approval, and the RTS Crest.
10. The right to use the Famous Trade Mark.

**COMPLETE
COLOR
INSTRUCTION
INCLUDED**

you build these
and other units

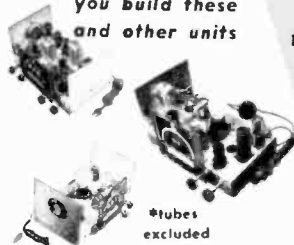


*tubes
excluded

RADIO-TELEVISION TRAINING SCHOOL

5100 S. VERMONT AVENUE
LOS ANGELES 37, CALIFORNIA

Est. 1922

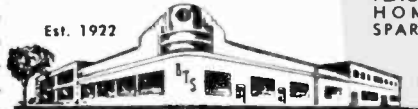

**ACT
NOW!**

CUT OUT AND MAIL — TODAY!

RADIO-TELEVISION TRAINING SCHOOL

5100 S. Vermont Avenue, Dept E1-260
Los Angeles 37, California

SEND ME FREE — all of these big opportunity books — "Good Jobs in TV-Electronics," "A Repair Shop of Your Own" and "Sample Lesson." I am interested in:

- Radio-Television Industrial Electronics
(Automation)

Name _____ please print _____ Age _____

Address _____

City & State _____
300




RTS' Membership in The Association of Home Study Schools is your assurance of Reliability, Integrity, and Quality of Training.

**ALL
THESE
FREE!**



RESIDENT SCHOOL COURSES

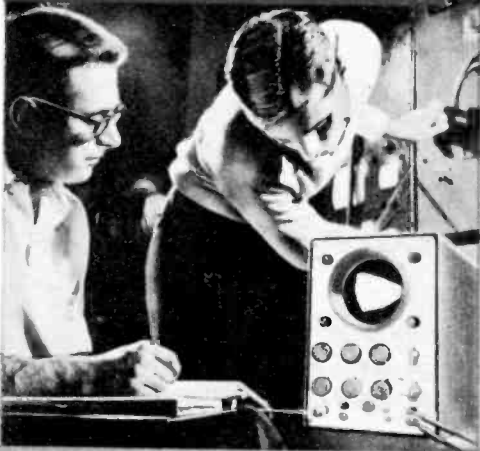

Industry needs Electronic Technicians!

Let RCA train you in Advanced Electronics

This is the college-level training you need to work with professional engineers on research, development or production projects in such fields as: automation, guided missiles, radar, television, computers and other advanced electronic applications.

RCA Institutes Resident School in New York City offers this comprehensive course that prepares you for any field of electronics you may choose. Other courses in TV & General Electronics, Radio & TV Servicing, and Radio Telegraph Operating.

Classes start four times each year. Applications now being accepted. Approved for Veterans.



RCA INSTITUTES, INC.

SCHOOLS OF TELEVISION
AND ELECTRONIC TECHNOLOGY

A Service of Radio Corporation of America
ANOTHER WAY RCA SERVES EDUCATION THROUGH ELECTRONICS

RCA INSTITUTES, DEPT. EIR-20
350 W. Fourth St., N.Y. 14, N.Y.

Please send me your FREE catalog of
Resident School courses in New York.


NAME
please print

ADDRESS


CITY ZONE STATE

For Home Study Courses see ad on opposite page


... News

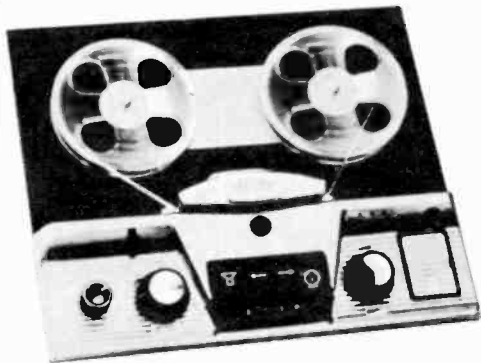

A stereo tape deck, the Arkay/Harting MS-5, has been introduced to the component market. Priced at \$129.95, it has a dual-track magnetic tape head, for record and playback, and separate erase head coupled with an automatic interlock to prevent accidental tape wipes. Metal tape guards control vertical tape alignment. The MS-5 features 7½ and 3¾ ips speeds, recording level indicator, digital tape counter, drop-in loading, and push-button operating controls. More information is available from Arkay International, Inc., 88-06 Van Wyck Exp., Richmond Hill, N. Y.

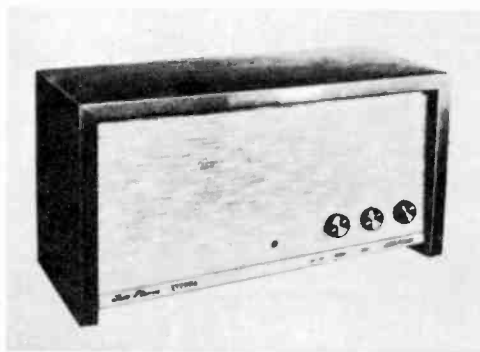

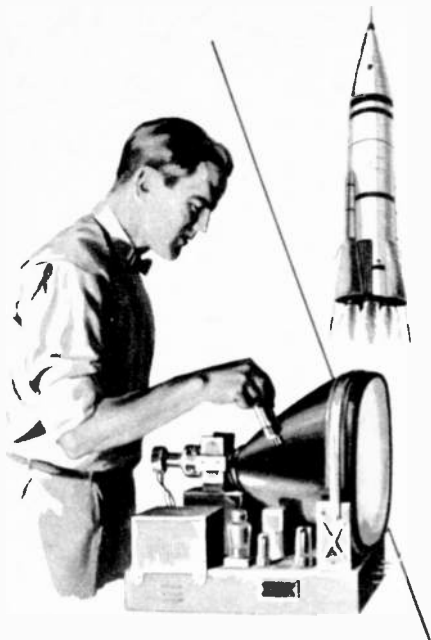Affiliated Television Laboratories has introduced a "plug-in" stereo converter complete with stereo cartridge. It consists of an amplifier with built-in pre-amp, 8" bass and mid-range and 3½" tweeter speakers and crossover. The converter, SC-7, is priced at \$59.95 from the manufacturer at 39 Rosell St., Minneola, N. Y.



ANOTHER WAY RCA
SERVES EDUCATION
THROUGH
ELECTRONICS



6 REASONS WHY RCA TRAINING IN ELECTRONICS

can be the smartest investment
you'll make in your *entire lifetime!*

1. You get the finest training-at-home under the supervision of the RCA INSTITUTES, experts in technical training for over 50 years. The very name "RCA" means dependability, integrity, and scientific advance.

2. You get comprehensive training in your choice of four complete, up-to-date Courses . . . from basic electronics theory to Color TV and Automation.

3. You get an evaluation of your aptitude for advanced training. RCA determines, for your benefit, whether you have the requirements for a career in the electronics field.

4. You get prime quality equipment as a regular part of your Course . . . equipment that you keep and use on the job. You never have to take apart one piece to build another.

5. You get each study group on a pay-as-you-go basis. Should you wish to interrupt your training at any time, you will not owe RCA Institutes a penny more, unless and until you decide to resume the Course.

6. You get top recognition — worldwide. Graduates of RCA Institutes now work for leaders in the electronics field; many have their own businesses. This record is true tribute to the high quality of RCA Institutes training.

Send for this
64-page Home
Study Catalog
FREE!



FOR RESIDENT
SCHOOL COURSES SEE
AD ON OPPOSITE PAGE

RCA INSTITUTES, Inc. Home Study School E.I.-20

A Service of Radio Corporation of America
350 West Fourth Street, New York 14, N. Y.
Without obligation, send me FREE 64-page CATALOG on Home Study Courses. No salesman will call.

Name Age

(Please Print)

Address

City Zone State

Korean Vets! Enter discharge date

CANADIANS — Take advantage of these same RCA courses at no additional cost. No postage, no customs, no delay. Send coupon to: RCA Victor Company, Ltd., 5001 Cote de Liesse Rd., Montreal 9, Quebec

To save time, paste coupon on postcard.

**MORE
PICTURE
POWER**
new
**BLONDER-TONGUE
B-24
POW-R
BOOSTER**



\$24⁹⁵
list

*it's a powerful booster
...or an amplified coupler!*

**provides sharp, clear TV pictures on
1, 2 or more TV sets with only 1 antenna**

'straight-thru' circuit provides up to 10 db gain as a powerful one-set booster

'couple-two' circuit provides up to 5 db gain (per set) as an amplified two-set coupler

'straight-thru' circuit and B-T 4-set coupler provide no-loss 4-set distribution system

Employs new frame-grid tube 6DJ8, new circuitry to achieve highest signal gain and "lower-than-cascade" noise factor. Provides full broadband amplification covering low and high VHF channels. Features "NO-STRIP" 300 ohm terminals for positive, electrical connections in seconds. Has "on/off" switch.

Improve TV reception today on 1, 2 or more TV sets with a single antenna.



Available at parts distributors. For details write:
BLONDER-TONGUE LABORATORIES, INC.
9 Alling Street • Newark 2, N. J. • Dept. EI-2

In Canada: Tequipment Mfg. Co., Ltd., London, Ont. Export: Morhan Export Corp., N. Y. 13. N. Y. • hi-fi components • UHF converters • master TV systems • industrial TV cameras • FM-AM radios

... News



Twin AM and FM tuners, that can combine to form one stereo tuner unit, have been announced by Stromberg-Carlson. The AM-441 does not have its own power supply, but derives its power from the FM-443 when they are operated together. It is available with a power supply as the AM-442, \$59.95. Separately, the FM-443 is priced at \$79.95 and the AM-441 at \$49.95. Combined as the SR-445 it is \$129.95. They are available in gold and white, or black and chrome with covers in white, black, tan or red from Stromberg-Carlson, Rochester 3, New York.



Small enough to fit in a tube shorter than the size of a pin, a thermometer developed by scientists at Bell Telephone Laboratories can measure temperatures close to absolute zero ($-459.7^{\circ}\text{F}.$) The thermometer employs a germanium crystal whose resistance increases rapidly as temperature falls. To find the temperature an electric current is sent through the thermometer and the resistance afforded by the germanium is measured and thus tells the temperature.



An ultra sensitive television camera that will truly see in the dark is being built by Dage Television. This transistorized TV camera will contain a sensitive "intensifier image orthicon" tube which combines the features of an image orthicon, to date the most sensitive television camera tube, with an "image intensifier" or "light amplifier." This camera is to be used by the Air Force.

knight-kits® are years ahead...

A PRODUCT OF ALLIED RADIO

so much easier to build...so much more value



see them all in
ALLIED'S 1960 CATALOG
FREE send for it

K *BEST...by Design!*

exciting to build...satisfying to own!
quality electronic equipment at

SAVINGS UP TO 50%



Y-731 Deluxe FM-AM Stereo Hi-Fi Tuner (Multiplex add-in) \$67.50
only \$5 down



Y-774 Deluxe 40-Watt Stereo Amplifier (with Center Channel) \$79.50
only \$5 down



Y-773 Super-Value 20-Watt Stereo Hi-Fi Amplifier...\$44.50
only \$2 down



Y-787 FM-AM Hi-Fi Tuner (with Multiplex jack)...\$49.95
only \$2 down



Y-737 "Ranger" Clock-Radio with "sleep" switch...\$24.95
only \$2 down



Y-258 4-Band "Span Master" Receiver (with cabinet) \$25.95
only \$2 down



R-100 Amateur Communications Receiver (HI-gain, with built-in Q-Multiplier)...\$104.50
only \$5 down



Y-708 1000 Ohm Volt Pocket Volt-Ohm-Milliammeter \$9.95



Y-713 Citizen's Band, 27 mc Transceiver...\$39.95
only \$2 down



Y-771 5-Transistor Superhet Portable Radio (less battery) \$25.95
only \$2 down



Y-125 Electronic VTVM (11 meg. input resistance) \$25.75
only \$2 down



Y-143 Model "600" Tube Checker (checks over 700 types)...\$32.95
only \$2 down

see scores of other **knight-kits**

HI-FI KITS

- Stereo Preamp
- 60-W Stereo Amplifier
- 25-W Amplifier
- 18-W Amplifier
- 12-W Amplifier
- Hi-Fi Tuners
- Speaker Systems
- and others

HOBBYIST KITS

- "Space-Spanner" Radio
- "Ranger" Radios
- "Ocean Hopper" Radio
- Transistor Radios
- 2-Way Intercom
- Electronic Lab Kits
- and many others

INSTRUMENT KITS

- Lab AC VTVM
- VOM's
- 5" Scopes
- Tube Checkers
- Signal Tracer
- Audio Generator
- Sweep Generator
- plus many others

AMATEUR KITS

- 400-Watt Transmitter
- 50-Watt Transmitter
- Self-Powered VFO
- 100 kc Crystal Callibrator
- Code Practice Oscillator
- Grid Dip Oscillator

ONLY \$2 DOWN
on orders up to \$50;
\$5 down on orders
up to \$200.

There's a money-saving **knight-kit** for every need...see them all in **ALLIED'S 1960 CATALOG**

Describes the complete **KNIGHT-KIT** line in detail—the leading Buying Guide to everything in Electronics. Send for your **FREE** copy today!

FREE



ALLIED RADIO

ALLIED RADIO, Dept. 75-B
100 N. Western Ave., Chicago 80, Ill.

SEND FREE 1960 ALLIED CATALOG

Name _____
Address _____
City _____ Zone _____ State _____



Ercona has announced the new Connoisseur, a British pickup arm equipped with a .0006 diamond stereo ceramic pickup. A knob is fitted on the 10 1/4" arm above the pivot point. When the knob is rotated clockwise the arm is lifted from the record. The arm is lowered by turning the knob in a counter-clockwise direction. The pickup arm may be raised and lowered at any position on the record. A pivot base column allows the arm to be adjusted to fit any turntable height. Complete specs available from Ercona Corp., 16 West 46th Street, New York 36, N. Y. \$59.50.

Scientists have discovered still another device to "bounce" messages off. Radio signals are now being reflected off the ionized air that is left in the wake of meteors. A message is first recorded, then a suitable meteor trail is located within a few thousandths of a second, and the message is sent at the rate of 2,400 words per minute. Tests show this 49 mc transmission is as effective as other long-range systems. Developed by the National Bureau of Standards.

New developments in solid-state electronic circuitry now make it possible to make an automatic pilot with no moving parts. Dr. A. S. Robinson, head of Bendix Aviation's Advanced Research and Development Laboratory, said "the new developments will mean the elimination of such devices as rotating shafts, gear trains, motors, etc." He predicted that the effect of these developments would be to cut in half the size, weight, power consumption, and cost of tomorrow's comparable automatic flight control systems.


PLACES THE WONDERFUL WORLD OF ELECTRONICS AT YOUR FINGERTIPS
1960 RADIO-ELECTRONIC MASTER
NOW AVAILABLE AT YOUR DISTRIBUTOR

WORLD'S LARGEST BUYING GUIDE OF TV-RADIO-ELECTRONIC-AUDIO PRODUCTS

1551 pages of complete descriptions, specs, illustrations, prices for 175,000 items including all latest products of 350 manufacturers systematically arranged in 28 product sections for easy reference

KEY TO A PROFITABLE CAREER IN ELECTRONICS

The MASTER is an electronic education in itself. It fully describes and illustrates every radio-tv-audio-electronic product used in assembling, repairing and designing. When you rely on the MASTER, you are sure to get the right products to do the job because you are shopping in the electronic supermarket. Shows complete details and prices of latest ham gear, TV items, transistors, printed circuits, stereo components, sub-miniature parts plus thousands of hard-to-locate items not usually found in smaller, incomplete catalogs. No matter what electronic item you require. You'll find it faster in the '60 MASTER. At your local parts distributor, or write for list.

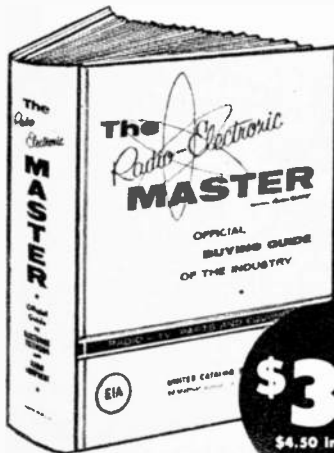

\$3.50
at parts distributors
\$4.50 in Canada

1551 Pages

FREE... FROM YOUR DISTRIBUTOR

24-page Foreign Tube Interchangeability Guide
or write direct enclosing 25¢ for handling

RADIO-ELECTRONIC MASTER, 58E Madison Ave., Hempstead, N.Y.

BUILD 16 RADIO

CIRCUITS AT HOME

with the New Deluxe
PROGRESSIVE RADIO "EDU-KIT"®

only
\$22.95



Reg. U.S.
Pat. Off.

A Practical Home Radio Course

Now Includes

- ★ 12 RECEIVERS
- ★ TRANSMITTER
- ★ SIGNAL TRACER
- ★ SIGNAL INJECTOR
- ★ CODE OSCILLATOR

- ★ No Knowledge of Radio Necessary
- ★ No Additional Parts or Tools Needed
- ★ EXCELLENT BACKGROUND FOR TV
- ★ School Inquiries Invited
- ★ Sold in 79 Countries

**YOU DON'T HAVE TO SPEND
HUNDREDS OF DOLLARS FOR A RADIO COURSE**

The "Edu-Kit" offers you an outstanding PRACTICAL HOME RADIO COURSE at a rock-bottom price. Our Kit is designed to train Radio & Electronics Technicians, making use of the most modern methods of home training. You will learn radio theory, construction practice and servicing. THIS IS A COMPLETE RADIO COURSE IN EVERY DETAIL.

You will learn how to build radios, using regular schematics; how to wire and solder in a professional manner, how to service radios. You will work with the standard type of punched metal chassis as well as the latest development of Printed Circuit chassis.

You will learn the basic principles of radio. You will construct, study and work with RF and AF amplifiers and oscillators, detectors, rectifiers, test equipment. You will learn and practice the Progressive Code Oscillator. You will learn and practice trouble-shooting, using the Progressive Signal Tracer, Progressive Signal Injector, Progressive Dynamic Radio & Electronics Tester and the accompanying instructional material.

You will receive training for the Novice, Technician and General classes of F.C.C. Radio Amateur Licenses. You will build 16 Receiver, Transmitter, Code Oscillator, Signal Tracer and Signal Injector circuits, and learn how to operate them. You will receive an excellent background for Television and Electronics.

Absolutely no previous knowledge of radio or science is required. The "Edu-Kit" is the product of many years of teaching and engineering experience. The "Edu-Kit" will provide you with the most complete and up-to-date radio training available at the rock-bottom price of \$22.95. The Signal Tracer alone is worth more than the price of the entire Kit.

THE KIT FOR EVERYONE

You do not need the slightest background in radio or science. Whether you are interested in Radio & Electronics because you want an interesting hobby, a well paying business or a job with a future, you will find the "Edu-Kit" a worth-while investment. Many thousands

ages and backgrounds have successfully used the "Edu-Kit" in more than 79 countries of the world. The "Edu-Kit" has been carefully designed, step by step, so that you cannot make a mistake. The "Edu-Kit" allows you to teach yourself at your own rate. No instructor is necessary.

PROGRESSIVE TEACHING METHOD

The Progressive Radio "Edu-Kit" is the foremost educational radio kit in the world, and is universally accepted as the standard in the field of electronics training. The "Edu-Kit" uses the modern educational principle of "Learn by Doing." Therefore you construct, learn schematics, study theory, practice trouble-shooting—all in a closely integrated program designed to provide an easily-learned, thorough and interesting background in radio.

You begin by examining the various radio parts of the "Edu-Kit." You then learn the function, theory and wiring of these parts. Then you build a simple radio. With this first set you will enjoy listening to regular broadcast stations, learn theory, practice testing and trouble-shooting. Then you build a more advanced radio, learn more advanced theory and techniques. Gradually, in a progressive manner, and at your own rate, you will find yourself constructing more advanced multi-tube radio circuits, and doing work like a professional Radio Technician.

Included in the "Edu-Kit" course are sixteen Receiver, Transmitter, Code Oscillator, Signal Tracer, and Signal Injector circuits. These are not unprofessional "breadboard" experiments, but genuine radio circuits, constructed by means of professional wiring and soldering on metal chassis, plus the new method of radio construction known as "Printed Circuitry." These circuits operate on your regular AC or DC house current.

THE "EDU-KIT" IS COMPLETE

You will receive all parts and instructions necessary to build 16 different radio and electronics circuits, each guaranteed to operate. Our Kits contain tubes, tube sockets, variable, electrolytic, mica, ceramic and paper dielectric condensers, resistors, tin strips, coils, hardware, tubing, punched metal chassis, Instruction Manuals, hook-up wire, solder, etc.

In addition, you receive Printed Circuit Materials, including Printed Circuit chassis, special tube sockets, hardware and instructions. You also receive a useful set of tools, a professional electric soldering iron, and a self-powered Dynamic Radio & Electronics Tester. The "Edu-Kit" also includes Code instructions and the Progressive Code Oscillator, in addition to F.C.C.-type Questions and Answers for Radio Amateur License training. You will also receive lessons for servicing with the Progressive Signal Tracer and the Progressive Signal Injector, a High Fidelity Guide and a Quiz Book to receive Membership in Radio-TV Club, Free Consultation Service, Certificate of Merit and Discount Privileges. You receive all parts, tools, instructions, etc. Everything is yours to keep.

PRINTED CIRCUITRY

At no increase in price, the "Edu-Kit" now includes Printed Circuitry. You build a Printed Circuit Signal Injector, a unique servicing instrument that can detect many Radio and TV troubles. This revolutionary new technique of radio construction is now becoming popular in commercial radio and TV sets.

A Printed Circuit is a special insulated chassis on which has been deposited a conducting material which takes the place of wiring. The various parts are merely plugged in and soldered to terminals.

Printed Circuitry is the basis of modern Automation Electronics. A knowledge of this subject is a necessity today for anyone interested in Electronics.

FREE EXTRAS

- SET OF TOOLS
- SOLDERING IRON
- ELECTRONICS TESTER
- PLIERS-CUTTERS • ALIGNMENT TOOL
- WRENCH SET
- VALUABLE DISCOUNT CARD
- CERTIFICATE OF MERIT
- TESTER INSTRUCTION MANUAL
- HIGH FIDELITY GUIDE • QUIZZES
- TELEVISION BOOK • RADIO TROUBLE-SHOOTING BOOK
- MEMBERSHIP IN RADIO-TV CLUB: CONSULTATION SERVICE • FCC AMATEUR LICENSE TRAINING
- PRINTED CIRCUITRY

SERVICING LESSONS

You will learn trouble-shooting and servicing in a progressive manner. You will practice repairs on the sets that you construct. You will learn symptoms and causes of troubles in home, portable and car radios. You will learn how to use the professional Signal Tracer, the unique Signal Injector and the Dynamic Radio & Electronics Tester. While you are learning in this practical way, you will be able to do many a repair job for your friends and neighbors, and charge fees which will far exceed the price of the "Edu-Kit." Our Consultation Service will help you with any technical problems you may have.

J. Stalitis, of 25 Poplar Pl., Waterbury, Conn., writes: "I have repaired several sets for my friends, and made money. The "Edu-Kit" paid for itself, I was ready to spend \$240 for a Course, but I found your ad and sent for your Kit."

FROM OUR MAIL BAG

Ben Valerio, P. O. Box 21, Magna, Utah: "The Edu-Kits are wonderful. Here I am sending you the questions and also the answers for them that have been in Radio for the last seven years, but like to work with Radio Kits, and like to build Radio Testers. I enjoyed every minute I worked with the different kits; the Signal Tracer works fine. Also like to let you know that I feel proud of becoming a member of your Radio-TV Club."

Robert L. Snuff, 1534 Monroe Ave., Huntington, W. Va.: "Thought I would drop you a few lines to say that I received my Edu-Kit, and was really amazed that such a bargain can be had at such a low price. I have already started repairing radios and phonographs. My friends were really surprised to see me get into the swing of it so quickly. The trouble-shooting Tester that comes with the Kit is really swell, and finds the trouble, if there is any to be found."

UNCONDITIONAL MONEY-BACK GUARANTEE

**ORDER DIRECT FROM AD—RECEIVE FREE BONUS
RESISTOR AND CONDENSER KITS WORTH \$7**

- Send "Edu-Kit" Postpaid. I enclose full payment of \$22.95.
- Send "Edu-Kit" C.O.D. I will pay \$22.95 plus postage.
- Rush me FREE descriptive literature concerning "Edu-Kit."

Name

Address

PROGRESSIVE "EDU-KITS" INC.

1186 Broadway, Dept. 520AE, Hewlett, N. Y.

FREE ALLIED'S
MONEY-SAVING 1960
ELECTRONIC SUPPLY CATALOG



value-packed
SEND FOR IT!

SAVE
ON EVERYTHING
IN ELECTRONICS

EASIEST TERMS
only \$2 down on
orders up to \$50

WORLD'S LARGEST STOCKS

Send for the most widely used buying guide to everything in Electronics for Experimenters, Builders, Amateurs, Servicemen, Engineers and Hi-Fi enthusiasts. Save on:

- KNIGHT-KITS®—Best in Build-Your-Own
- Everything in STEREO Hi-Fi
- Hi-Fi Music Systems and Components
- Tape Recorders & Phono Equipment
- Public Address & Paging Systems
- TV Tubes, Antennas, Accessories
- Amateur Station Equipment
- Latest Test & Lab Instruments
- Parts, Tubes, Transistors
- Everything in Tools & Technical Books

SAVE on everything in Electronics at ALLIED—get fastest service, expert personal help, guaranteed satisfaction. Send today for your FREE 1960 ALLIED Catalog.

Everything in Electronics from One Reliable Source

our 39th year



• ALLIED RADIO CORP., Dept. 84-8
100 N. Western Ave., Chicago 80, Ill.

Rush FREE 1960 ALLIED Catalog.


Name _____

Address _____

City _____ Zone _____ State _____



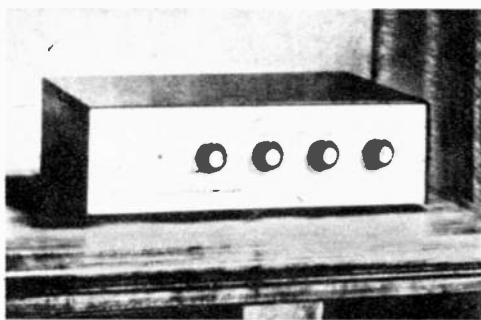Audio Empire, the new hi-fi product division of Dyna-Empire, Inc., is entering the market with the Empire 88 "Stereo/Balance" cartridge. The Empire 88 with a .0007 diamond stylus is priced at \$24.50 and the Empire 88S with .0007 sapphire stylus is \$18.50. Replacement styli are available. Audio Empire, 1075 Stewart Ave., Garden City, N. Y.



A 20-watt stereo amplifier, featuring dual 10-watt amp-preamp sections has been announced by Knight. The KN-520 contains four 7408 output tubes and features DC on preamp filaments. Priced at \$62.50 from Allied Radio, 100 N. Western Avenue, Chicago 80, Illinois.

Learn Electronics

PREPARE FOR YOUR F. C. C. LICENSE—YOUR TICKET TO A BETTER JOB AND HIGHER PAY!

F. C. C. LICENSE—THE KEY TO BETTER JOBS

An F. C. C. *commercial* (not amateur) license is your ticket to higher pay and more interesting employment. This license is Federal Government evidence of your qualifications in electronics. Employers are eager to hire *licensed* technicians.

WHICH LICENSE FOR WHICH JOB?

The **THIRD CLASS** radiotelephone license is of value primarily in that it qualifies you to take the second class examination. The scope of authority covered by a third class license is extremely limited.

The **SECOND CLASS** radiotelephone license qualifies you to install, maintain and operate most all radiotelephone equipment except commercial broadcast station equipment.

The **FIRST CLASS** radiotelephone license qualifies you to install, maintain and operate every type of radiotelephone equipment (except amateur) including all radio and television stations in the United States, its territories and possessions. This is the highest class of radiotelephone license available.

GRANTHAM TRAINING PREPARES YOU

The Grantham Communications Electronics Course prepares you for a **FIRST CLASS F. C. C.** license, and it does this by **TEACHING** you electronics. Each point is covered simply and in detail, with emphasis on making the subject easy to understand. The organization of the subject matter is such that you progress, step-by-step, to your specific objective—a first class F. C. C. license.

CORRESPONDENCE OR RESIDENCE CLASSES

Grantham training is available by correspondence or in resident classes. Either way (residence or correspondence), we train you quickly and well—no previous training required. Even a beginner may qualify for his first class license in a relatively short time.

FOUR COMPLETE SCHOOLS: To better serve our many students throughout the entire country, Grantham School of Electronics maintains four complete Divisions—located in Hollywood, Calif., Seattle, Wash., Kansas City, Mo., and Washington, D. C. All Divisions of Grantham School of Electronics offer the same rapid courses in F. C. C. license preparation, either by home study or in resident classes.

This booklet

FREE!



This free booklet gives details of our training and explains what an F. C. C. license can do for your future.

Upgrade Your Income with a First Class F. C. C. LICENSE

HERE'S PROOF...

that Grantham students prepare for F. C. C. examinations in a minimum of time. Here is a list of a few of our recent graduates, the class of license they got, and how long it took them:

	License	Weeks
Donald E. Mason, 2659 Centinella, Santa Monica, Calif.	1st	12
Everett T. Bozard, 411 N. Wash. St., Alexandria, Va.	1st	12
Henry M. Best, 1003 Vermont St., Fremont, N. C.	1st	11
Harold V. Jones, P. O. Box 705, Alamogordo, N. M.	1st	13
Michael F. Aperio, 916 Townsend St., Chester, Pa.	1st	12
Earl A. Stewart, 3918 Modesto Dr., San Bernardino, Calif.	1st	14
Donald L. Leeburg, Box 1075, Anchorage, Alaska	1st	12
J. Milton Condit, 1312 N. 78th Street, Seattle, Wash.	1st	8
John R. Bahrs, 72 Hazelton St., Ridgefield Park, N. J.	1st	12
Richard Baden, 4226 - 37th St., N.W., Washington, D.C.	1st	12
James F. Stewart, 2618 1/2 Prospect Ave., La Graciosa, Calif.	1st	12
Norman R. Cook, 130 Olive Street, Neodesha, Kans.	1st	12

GRANTHAM SCHOOL OF ELECTRONICS

HOLLYWOOD CALIF.

1505 N. Western Ave. (HO 3-7727)
Hollywood, Calif.

SEATTLE WASH.

408 Marion Street (MA 3-7287)
Seattle, Wash.

KANSAS CITY MO.

3123 Gillham Road (JE 1-4370)
Kansas City, Mo.

WASHINGTON D. C.

821 - 19th Street, N. W. (ST 3-3614)
Washington, D. C.

MAIL COUPON TO SCHOOL NEAREST YOU

(Mail in envelope or paste on postal card)

To: GRANTHAM SCHOOL OF ELECTRONICS

1505 N. Western • 408 Marion • 3123 Gillham Rd. • 821-19th, NW
Hollywood • Seattle • Kansas City • Washington



Gentlemen:

Please send me your free booklet telling how I can get my commercial F. C. C. license quickly. I understand there is no obligation and no sclesman will call.

Name _____ Age _____

Address _____

City _____ State _____

I am interested in: Home Study, Resident Classes **OR-B**

That!

Greatest Savings
and Precision Features
all inclusive in this
"QUALITY LINE"!



EMC TEST EQUIPMENT

Compare all our features and you'll
AGREE the name to buy is EMC



Model 102 Voltmeter

Features a 3½", 2% accurate—800 microamperes O'arsonval-type plastic front meter with 3 AC current ranges; and the same zero adjustment for both resistance ranges. Specifications . . . AC Voltage—5 Ranges: 0 to 12-120-600-1200-3000 volts. DC Voltage—5 Ranges: 0 to 6-60-300-600-3000 volts. AC Current—3 Ranges: 0 to 30-150-600ma. DC Current—4 Ranges: 0 to 6-30-130ma: 0 to 1.2 amps. Two Resistance Ranges: 0 to 1000 ohms, 0 to 1 megohms. Model 102, Wt. 1 lb. 5 oz. Size: 3¼" x 6¼" x 2". \$14.90; Kit, \$12.50.

Model 205 Tube Tester

Uses standard emission test. Tests all tubes including Noval and subminiatures. Completely flexible switching arrangement. Checks for shorts, leakages and opens.

Model 205P, Hand rubbed oak carrying case, \$47.50 (illustrated); Kit, \$36.20. Model CRA, Cathode ray tube adaptor, \$4.50.



Model 700 RF-AF-Crystal Marker TV Bar-Generator

Complete coverage from 18 cycles to 108 megacycles on fundamentals. Bar generator for TV adjustment with a variable number of bars available for horizontal or vertical alignment.

Square wave generator to 20 kilocycles. Wien Bridge AF oscillator with sine wave output from 18 cycles to 300 kilocycles. Crystal marker and amplitude control. Individually tuned coils. Constant RF output impedance. Stepped RF attenuator. Variable percentage of modulation.

Model 700 \$55.00



Yes, tell me more, send me FREE—a detailed catalog of the complete EMC line. EL-2

NAME _____

ADDRESS _____

CITY _____

STATE _____

EMC Electronic Measurements Corp.
625 B'way, New York 12, N. Y.
Ex. Dept., 432 Greenwich St., New York 13, N. Y.

...News



Superex Electronics Corp. has announced a new transistor radio kit, model DYN. This two transistor kit features matched transistor and diode, selective variable capacitive tuning, a loopstick, earphone, headband and comes with a black and gold case. It operates on flashlight batteries. The manufacturer says the kit can be assembled in an evening with only a screwdriver. A free catalog is offered to the readers of *EI* just by writing to Superex Electronics Corp., 4-6 Radford Place, Yonkers, New York. The price of the kit is \$7.49.



Chelmsford, England sends the news that a new shortwave radio transmitter that can simultaneously broadcast two or more independent transmissions on different wavelengths was developed.

The Marconi Wireless Telegraph Company's transmitter (1 kw) enables service on one frequency to be put on a second frequency before being discontinued on the first frequency. This is possible by the use of a distributed amplifier which provides wide-band amplification over the entire high frequency band. This dispenses with the need to retune the amplifier whenever a change of frequency is desired. This amplifier also permits simultaneous radiation of two or more independent transmissions. The idea of the distributed amplifier used as a low-level voltage amplifying device is not new, however, this transmission is believed to be the first successful use in this type of service.


**WE'RE MAKING IT EASIER THAN EVER TO BECOME A WELL PAID
RADIO-TELEVISION SERVICE TECHNICIAN**

**NOW - Just \$6 Starts You Training in
RADIO-TELEVISION**


the SPRAYBERRY "Learn-by-Doing" Way . . .

**25 BIG, COMPLETE KITS
of PARTS & EQUIPMENT**

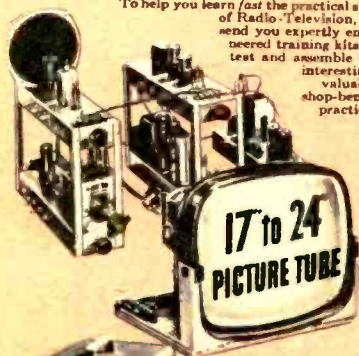To help you learn fast the practical side of Radio-Television, we send you expertly engineered training kits to test and assemble for interesting, valuable shop-bench practice!



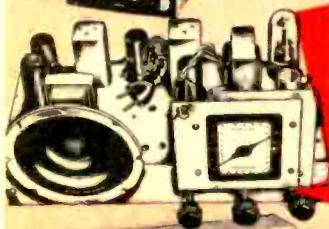- The new Sprayberry Training Television Receiver, built and tested in 5 sections.
- Now offered . . . this fine modern oscilloscope.
- You build this powerful two-band superheterodyne radio receiver.



**Big New
CATALOG
AND
Sample Lesson
FREE!**



You build the new Sprayberry tester — a complete 18-range Volt-Ohm-Milliammeter test meter.

*** This great industry is begging for trained men . . . to step into good paying jobs or a profitable business of their own! Our new plan opens the doors of Radio-Television wide to every ambitious man who is ready to act at once!

Men by the thousands . . . trained Radio-Television Service Technicians . . . are needed at once! Perhaps you've thought about entering this interesting, top paying field, but lack of ready money held you back. Now — just \$6 enrolls you for America's finest, most up to date home study training in Radio-Television! Unbelievable? No, the explanation is simple! We believe Radio-Television *must* have the additional men it needs as quickly as possible. We are willing to do our part by making Sprayberry Training available for less money down and on easier terms than ever before. This is your big opportunity to get the training you need . . . to step into a fine job or your own Radio-Television Service Business.

Complete Facts Free — Act Now; Offer Limited

Only a limited number of students may be accepted on this liberal and unusual basis. We urge you to act at once . . . mail the coupon below and get complete details plus our big new catalog and an actual sample lesson — *all free*. No obligation . . . no salesman will bother you.

HOME STUDY TRAINING IN SPARE TIME

Under world-famous 27-year old Sprayberry Plan, you learn entirely at home in spare time. You keep on with your present job and income. You train as fast or as slowly as you wish. You get valuable kits of parts and equipment for priceless shop-bench practice. And everything you receive, lessons and equipment alike, is all yours to keep.

LET US PROVE HOW EASILY YOU CAN LEARN!

Radio-Television needs YOU! And Sprayberry is ready to train you on better, easier terms, that any ambitious man can afford. *Just \$6 starts you!* Mail coupon today . . . let the facts speak for themselves. You have everything to gain. Let us prove the kind of opportunity in store for you!

SPRAYBERRY Academy of Radio-Television
1512 Jarvis Avenue, Dept. 120-G, Chicago 26, Illinois

Mail This Coupon Now — No Salesman Will Call

Sprayberry Academy of Radio-Television
Dept. 120-G 1512 W. Jarvis Ave., Chicago 26, Ill.

Please rush all information on your ALL-NEW Radio-Television Training Plan. I understand this does not obligate me and that no salesman will call upon me. Include New Catalog and Sample Lesson FREE.

NAME..... Age.....

ADDRESS.....

CITY..... ZONE..... STATE.....



prepare for your career in


ELECTRONICS ELECTRICAL ENGINEERING RADIO-TV COMPUTERS

At MSOE, you can equip yourself for a career in many exciting, growing fields: MISSILES • RADAR • AVIONICS AUTOMATION • RESEARCH DEVELOPMENT • ELECTRICAL POWER • ROCKETRY

When you graduate from the Milwaukee School of Engineering, you are prepared for a dynamic career as an Electrical Engineer or Engineering Technician. Under a faculty of specialists, you gain a sound technical education in modern, completely equipped laboratories and classrooms. As a result, MSOE graduates are in great demand and highly accepted by industries nationally.

At MSOE, you will meet men from all walks of life and all parts of the country — some fresh out of high school or prep school, others in their twenties — veterans and non-veterans.

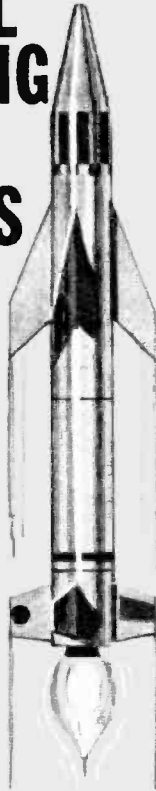You can start school in any one of four quarters and begin specializing immediately. Engineering technicians graduate in 2 years with an Associate in Applied Science degree. For a Bachelor of Science degree in Engineering, you attend 4 years. A 3-month preparatory course also is available.



FREE CAREER BOOKLET!

If you're interested in any phase of electronics, radio or television, be sure to look into the programs of study offered by the Milwaukee School of Engineering. Just mail the coupon.

MILWAUKEE SCHOOL OF ENGINEERING

Dept. EI-260, 1025 N. Milwaukee St.
Milwaukee, Wisconsin

Please send FREE Career Booklet. I'm interested in

- Electronics Electrical Power Television
- Mechanical Engineering Radio Computers
- Electrical Engineering Industrial Electronics

PLEASE PRINT

Name _____ Age _____

Address _____

City _____ Zone _____ State _____

I'm eligible for veterans education benefits MS-125

... News

New Bulletins and Catalogs ...

A handbook entitled "Understanding Transistors" written by *EI*'s test equipment expert, Milt Kiver, is available from Allied Radio Corp., for 50¢.

The 1960 Hi-Fi Buying Guide, a catalog on hi-fi components, has been published by Harvey Radio. Available for the asking from Harvey at 103 West 43rd St., N. Y. 36, N. Y.

Bulletin SR-257 from International Rectifier Corp. describes their line of silicon zener diodes. El Segundo, Calif.

A Semi-Conductor directory listing the latest in transistors, diodes, etc. has been announced by Lafayette Radio. Manufacturers and types are listed with descriptions and applications. Free from Lafayette at 165-08 Liberty Avenue, Jamaica 88, New York.

Pentron Corporation has published a new catalog sheet giving general information on their 1960 Tape Recorders. Dept. NR-101, 777 S. Tripp Ave., Chicago 24, Ill.

R-Columbia Products Co., Inc. of 305 Waukegan Avenue, Highwood, Ill. has announced a catalog (No. 59) of professional hints for the inventor.

A bulletin, R-14, describing enclosures and cabinets for hi-fi mono and stereo has been issued by Rockford Special Furniture Co. Copy available from Rockford at 2024 23rd Avenue, Rockford, Illinois.

Full details of Seco Manufacturing Company's line of test equipment appear in that company's new brochure. Free copies of Folder M-C099 are available from Seco at 5015 Penn Avenue, South Minneapolis, Minnesota.

"The Microphone in Public Address Systems" which contains rules of microphone techniques and common microphone usage problems and solutions is available from Shure Brothers, Inc., 222 Hartrey Avenue, Evanston, Ill.

A 32-page booklet called "Entertainment Transistors for Every Design Approach" is being offered by Sylvania. It contains ratings and characteristics for transistors for use in hi-fi, toys, etc. Free from 1100 Main St., Buffalo 9, N. Y.



Look what \$29⁹⁵ buys in high fidelity equipment!

A complete 14-watt hi-fi rated amplifier-preamplifier combination in one attractively styled unit . . . and at less than half the price you would expect to pay!


Learn how you can "build-it-yourself" and save 50% or more on the world's finest high fidelity equipment. Send today for your FREE Heathkit catalog—or see your nearest authorized Heathkit dealer!

14-WATT HI-FI RATED AMPLIFIER KIT (EA-3)

From HEATHKIT audio labs comes an exciting new amplifier . . . New Styling, New Features. Brilliant Performance! Designed to function as the "heart" of your hi-fi system, the EA-3 combines the pre-amplifier and amplifier functions into one compact package with an

honest 14 watts of high-fidelity-rated power, capable of driving the most demanding systems, and all the necessary controls for precise blending of sound reproduction to your individual taste. Clearly marked controls give you finger-tip command of bass and treble "boost" and "cut" action, switch selection of three separate inputs, "on-off" and volume control. A hum balance control is also provided. **ORDER YOUR EA-3 TODAY!** . . . a few hours of easy kit building fun will earn you a lifetime of hi-fi pleasure! Shpg. Wt. 15 lbs.

NOTE THESE OUTSTANDING SPECIFICATIONS: Power output: 14 watts, Hi-Fi; 12 watts, Professional; 16 watts, Utility. Power response: ± 1 db from 20 cps to 20 kc at 14 watts output. Total harmonic distortion: less than 2%, 30 cps to 15 kc at 14 watts output. Intermodulation distortion: less than 1% at 16 watts output using 60 cps and 6 kc signal mixed 4:1. Hum and noise: mag. phono input, 47 db below 14 watts; tuner and crystal phono, 63 db below 14 watts.

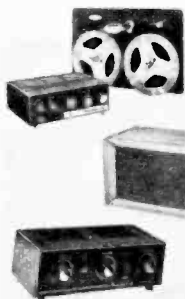

Complete line of monophonic stereo-tape recorders . . . from \$99.95

Finest quality hi-fi speaker systems . . . from \$34.95

Everything for stereo Amplifiers . . . from \$29.95

World's finest monophonic amplifiers . . . from \$15.95

HEATH COMPANY
 a subsidiary of Daystrom, Inc.
 Benton Harbor 39, Michigan

Please send the latest Free Heathkit Catalog.

NAME _____
 ADDRESS _____
 CITY _____ STATE _____

All prices F.O.B. Benton Harbor, Mich. Prices and specifications subject to change without notice.



A kit of 15 electrolytic capacitors in five values has been made available by Pyramid Electric Co. Transistor Maintenance Assortment, Kit #515, is available for \$7.70 from local radio parts distributors.



For audiophiles who like to feel the deep bass in recorded music, Electro-Voice has perfected its 30-inch loudspeaker, the model 30W. Write to manufacturer in Buchanan, Michigan for more information.



Build the Best Portable... **EICO**

6-TRANSISTOR RADIO RA-6

Kit \$29.95

Wired \$49.95

INCLUDES F.E.T., LESS 9V BATTERY

Easy creative fun to build... a lifetime of big-set entertainment wherever you go... designed so that even the novice can build it & obtain a handsome professional assembly & outstanding performance. American-made modern super-heterodyne all-transistor circuitry, plus finest quality parts throughout, assure you of highest durability & stability.

- high sensitivity & selectivity • big-set volume & tone quality with 4" x 6" PM speaker & 250 mw push-pull audio output stage • built-in Ferrite rod antenna for good reception in any location • pre-aligned RF & IF transformers • planetary vernier tuning (7:1 reduction) for easy station selection & tuning • high-impedance earphone jack for private listening; eliminates drain of output stage when using earphone • attractive tan leatherette case, retractable handle • compact: 8½" w, 4½" h, 2½" d. Only 3 lbs.

Build the BEST BUYS in "HAM" gear...



• U.S. Pat. No. D-184,776

90-WATT CW TRANSMITTER #720
 Kit \$79.95 Wired \$119.95
 "Ideal for veteran or novice" — **ELECTRONIC KITS GUIDE**. "Top quality" — **POPULAR ELECTRONICS**. "Well designed" — **ELECTRONICS WORLD**. 80 thru 10 meters with one-knob band-switching. Full "clean" 90W input, 65W external plate mod. Matches loads 50 to 1000 ohms. May be used as basic exciter unit. TVI shielded. Tubes: 6146, 6CL6, 2-6AQ5, G234. Attractive "living room" low-silhouette design. 15" w, 5" h, 9" d.



UNIVERSAL MODULATOR-DRIVER #730
 Kit \$49.95 Wired \$79.95
 Cover E-5 \$4.50
 Delivers 50W undistorted audio. Modulates transmitters having r.f. inputs up to 100W. Unique over-modulation indicator. Output transformer matches 500-10,000 ohms. Low-level speech clipping & filtering. Inputs for xtal or dynamic mikes, phone patch, etc. 7 tubes. 6" h, 14" w, 6" d.



GRID DIP METER #710
 Kit \$29.95 Wired \$49.95
 Includes complete set of coils for full band coverage. 400 kc-230 mc in 8 overlapping ranges. 500 ua meter. Plug-in coils are pre-wound, pre-calibrated to 0.5% accuracy. Transformer-operated power supply. 2¼" h, 2¾" w, 6¾" l.

Compare — Judge for yourself — at your neighborhood EICO distributor. For free catalog on 65 models of EICO test instruments, hi-fi & "ham" gear, fill out coupon on Page 26. Add 5% in the West.

ELECTRONIC INSTRUMENT CO., Inc., 33-00 N. Blvd., L. I. C. 1, N. Y.



Prepare now
IN SPARE TIME
AT HOME
for great opportunity
field of...

TELEVISION

The future is YOURS in TELEVISION—RADIO—COLOR-TV!

A fabulous field—good pay—fascinating work—a prosperous future! Good jobs or independence in your own business!

Modern Training by Coyne RIGHT IN YOUR OWN HOME

Coyne brings you the first truly lower cost, MODERN—QUALITY Television Home Training; training designed to meet Coyne standards. Not an old Radio Course with Television "tacked on." Here is MODERN TELEVISION TRAINING including RADIO, UHF and COLOR TV. No previous experience needed. Personal guidance by Coyne Staff.

The Institution Behind this Training

Famous for over a half century, COYNE occupies this entire building which is the new home of COYNE. COYNE'S modern resident training of men for Television, Radio, Electronics and Electricity has produced thousands of successful graduates.



D. W. COYNE, Jr., President

FOUNDED 1899

COYNE ELECTRICAL SCHOOL

CHARTERED AS AN EDUCATIONAL INSTITUTION NOT FOR PROFIT

1501 W. Congress Parkway, Chicago 7, Dept. 20-H8

MAIL COUPON NOW FOR DETAILS FREE

LEARN TO

EARN IN SPARE TIME AT HOME

COYNE offers a most practical, Home Television Training. Easy to follow step-by-step instructions, fully illustrated with 2150 photos and diagrams. Practical Job Guides to show you how to do actual servicing jobs—make money early in course. Keep your present job while training.


Low Cost—Easy Terms

We save you money because we don't send you—AND CHARGE FOR—a long list of parts or "put together kits," which you may not want or do not need. With Coyne Television Home Training you pay only for your training, no costly extras.

Let us show you that this is not only the newest, most up-to-the-minute Training in Television—but also it costs you much less than other leading home training courses. Send coupon today for details including Easy Payment Plan.

SEND COUPON OR WRITE TO ADDRESS BELOW FOR FREE BOOK

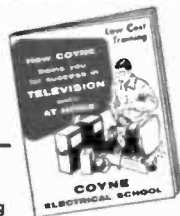and full details, including Easy Payment Plan. No obligation, no salesman will call.



COYNE Television Home Training Division
 Dept. 20-H8—New Coyne Building
 1501 W. Congress Parkway, Chicago 7, Illinois

Send Free Book and details on Television Home Training. This does not obligate me in any way.

Name _____

Address _____

City _____ State _____

(It is understood no salesman will call.)

the experts say
your BEST BUY
 is **EICO**...

EICO, 33-00 Northern Blvd., L. I. C. 1, N. Y. E-I-2
 Show me HOW TO SAVE 50% on 65 models of
 top-quality:

HI-FI TEST INSTRUMENTS "HAM" GEAR
 Send FREE catalog & name of neighborhood EICO
 dealer. Send free STEREO HI-FI Guide.

NAME.....
 ADDRESS.....
 CITY..... ZONE..... STATE.....

ADD 5% IN THE WEST

...in
STEREO and MONO HI-FI



STEREO Dual Amplifier-Preamplifier HF81
 Kit \$69.95. Wired \$109.95.
 "Excellent" — SATURDAY REVIEW; HI-FI MUSIC AT HOME.



Mono Preamplifier HF65A:
 Kit \$29.95. Wired \$44.95.
 With Power Supply HF65: Kit \$33.95. Wired \$49.95.



FM Tuner HFT90
 Kit \$39.95*. Wired \$63.95*.
 Cover \$3.95.
 "One of the best buys" **AUDIOCRAFT.**
AM Tuner HFT94
 Kit \$39.95. Wired \$65.95, incl. Cover & F.E.T.
FM/AM Tuner HFT92
 Kit \$59.95. Wired \$94.95. Includes Cover & F.E.T.

*Less Cover, F.E.T. incl.



STEREO Dual Preamplifier HF85
 Kit \$39.95. Wired \$64.95.
 "Extreme flexibility a bargain" — HI-FI REVIEW



Mono Power Amplifiers (60, 50, 35, 30, 22, 14-Watt; use 2 for Stereo)
 from Kit \$23.50. Wired \$41.50.



2-Way Bookshelf Speaker System HFS1
 complete with factory-built cabinet: \$39.95.



STEREO Dual Power Amplifier HF86
 Kit \$43.95. Wired \$74.95.



Mono Integrated Amplifiers (50, 30, 20, 12-Watt; use 2 for Stereo)
 from Kit \$34.95. Wired \$57.95.



NEW! COMPLETE STEREO DUAL AMPLIFIER AF-4
 Kit \$38.95. Wired \$64.95

TRUE Hi-Fi quality to drive hi efficiency speakers to concert volume.

70W STEREO Dual Power Amplifier HF87
 Kit \$74.95. Wired \$114.95

...and in
TEST INSTRUMENTS



New Power & Bias Supply for Transistorized Eqpt. #1820*
 Kit \$19.95. Wired \$27.95
 * Patent Pending



Miniaturized Multi-Signal Tracer #145A
 Kit \$19.95. Wired \$28.95.



Vacuum Tube Voltmeter #221
 Kit \$25.95. Wired \$39.95.



Peak-to-Peak VTVM #232 & Uni-Probe (pat. pend.)
 Kit \$29.95. Wired \$49.95.



New TUBE & CRT FIL. Tester #612
 Kit \$3.95. Wired \$5.95.
 Fast-checks radio/TV tubes, pilot lamps, etc.



1000 Ohms/Volt V-O-M. #536
 Kit \$12.90. Wired \$14.90.



5" Push-Pull Scope #425
 Kit \$44.95. Wired \$79.95



DC-5 MC 5" Scope #460
 Kit \$79.95. Wired \$129.50.

Tube Tester #625
 Kit \$34.95. Wired \$49.95.



RF Signal Generator #324
 Kit \$26.95. Wired \$39.95.



Series/Parallel R-C Combination Box #1140
 Kit \$13.95. Wired \$19.95
 1350 Combinations!



6V & 12V Battery Eliminator & Charger #1050
 Kit \$29.95. Wired \$38.95.
 Extra-filtered for transistor equip. #1060
 Kit \$38.95. Wired \$47.95



R-C Bridge & R-C-L Comparator #950B
 Kit \$19.95. Wired \$29.95.

IN STOCK! Compare, take them home — right "off the shelf" — from 2000 neighborhood dealers. Over 1 MILLION EICO instruments in use throughout the world.

© 1960, ELECTRONIC INSTRUMENT CO., INC., 33-00 N. BLVD., L. I. C. 1, N. Y.


See Page 24 for EICO'S BEST BUYS in "HAM" GEAR and TRANSISTOR RADIOS.

Radio-Powered Sky Station

Aloft on microwave power, sky station will provide better communications, better missile-age defense.

THE controlled transmission of energy through space is no longer a dream of scientists or the exclusive tool of fiction writers—it is reality.

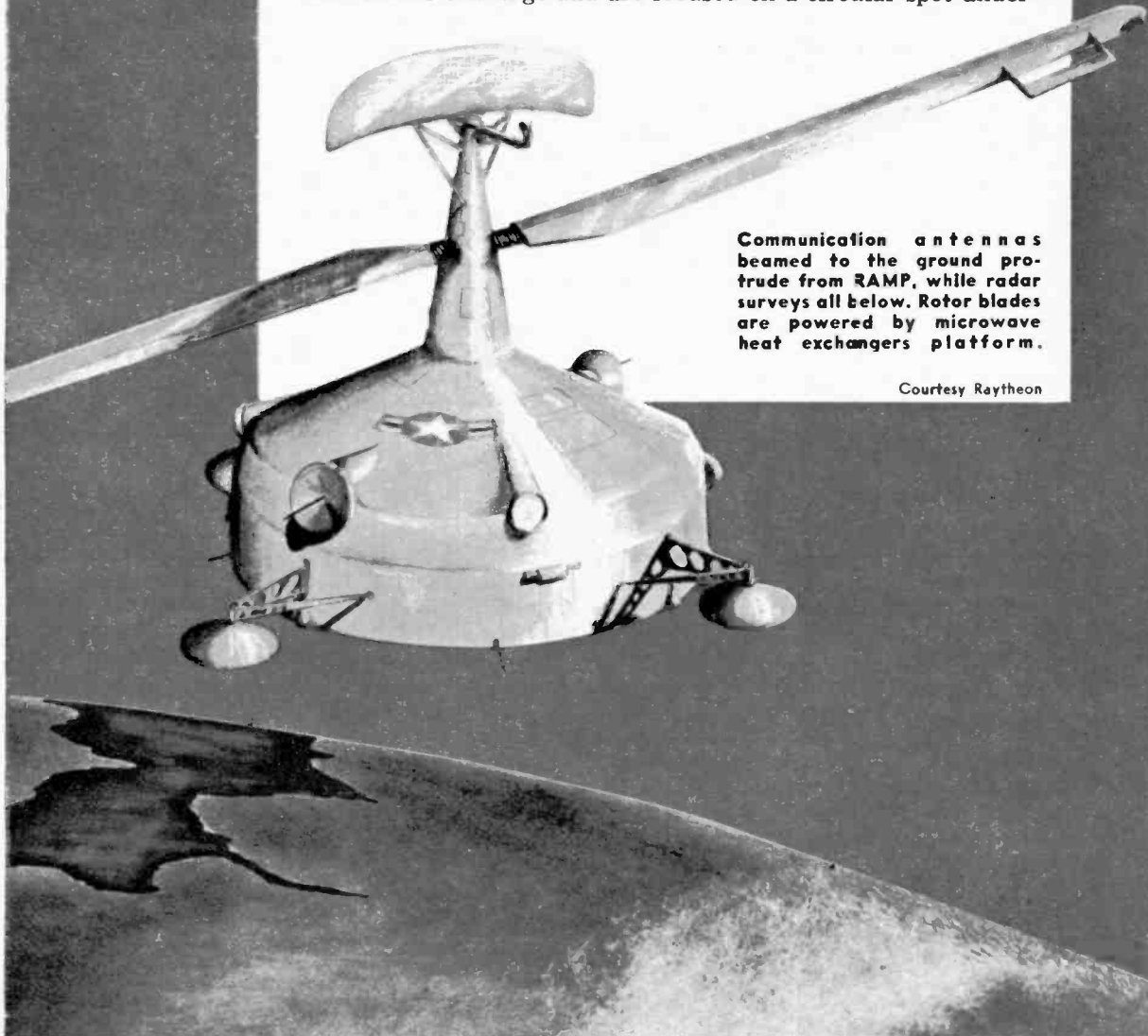Raytheon's Airborne Microwave Platform (RAMP) is a sky station, not an orbiting satellite, that is powered and supported aloft by microwave energy generated at a ground station and beamed to the platform by antennas grouped in a 400-foot-square antenna array. Like a battery of searchlights all operating as one, these beams converge and are focused on a circular spot under-



Communication antennas beamed to the ground protrude from RAMP, while radar surveys all below. Rotor blades are powered by microwave heat exchangers platform.

Courtesy Raytheon



New Amplitrons are designed for 50 times more power than early (hand-held) unit.

neath the sky station, which is about 50 feet in diameter.

Why a sky station? The projected military and commercial capabilities are tremendous. RAMP is designed to raise itself 65,000 feet above the earth and become a highly stable "stationary" platform far above the weather. The curvature of the earth will not matter at that height.


To the average man, this would mean that he could watch the Folies Bergere from Paris, the Olympics from Europe, and other world events on his TV set as they happen. It would also mean that business and personal telephone calls and telegrams to distant points could be made at a fraction of the present rate.

A system of such platforms would act as a long-range missile alarm, guide defense vehicles (such as Bomarc anti-missile missiles), and reliably relay broadband communications and weather surveillance data to stations on the ground. The entire North Atlantic can be covered with only four such platforms. This amounts to an extension of

the DEW Line all the way to Europe.

Until recently, tubes with high enough power to keep a sky station aloft were available only at relatively low microwave frequencies. Low frequencies meant antenna arrays covering many acres would be needed to focus the microwaves on a high altitude sky station. The new Amplitron tubes now can provide power at much higher frequencies and they have the stability required to ensure an efficient, highly directional antenna pattern. This means that antennas can be brought down to reasonable size.


The Amplitron is the key to the entire project. A high-efficiency microwave amplifier tube developed by Raytheon, it can increase the microwave energy generated by the older magnetron many times. Under security wraps for many months the Amplitron's effectiveness has been proved in the "Flight-Tracker" air traffic control system and other long-range radar systems. The heat dissipation problem has always placed severe limitations on the design of high-power

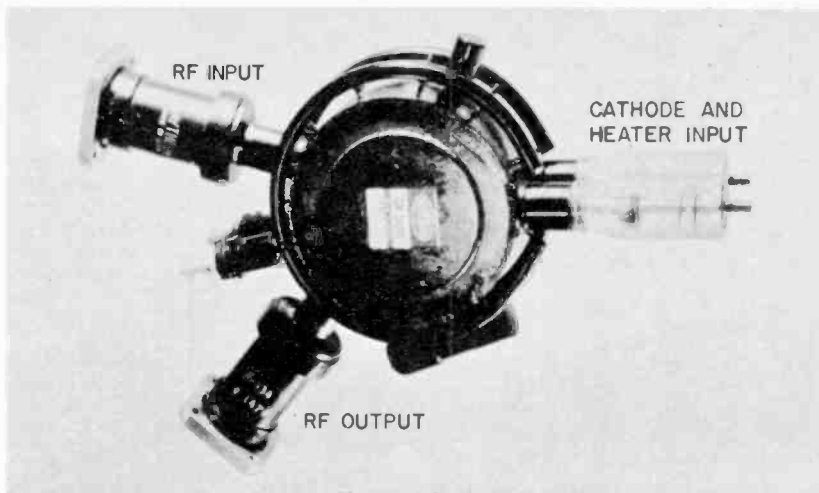


Amplitron tubes are able to efficiently amplify RF energy to a degree never before achieved. It is capable of operating in the higher microwave frequencies.

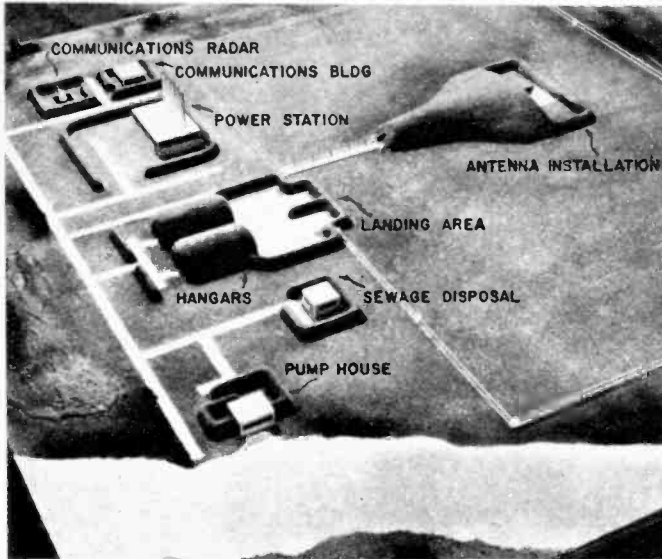High military brass engaged in directing advanced research and development, get the low-down on model of sky station from Raytheon vice president.





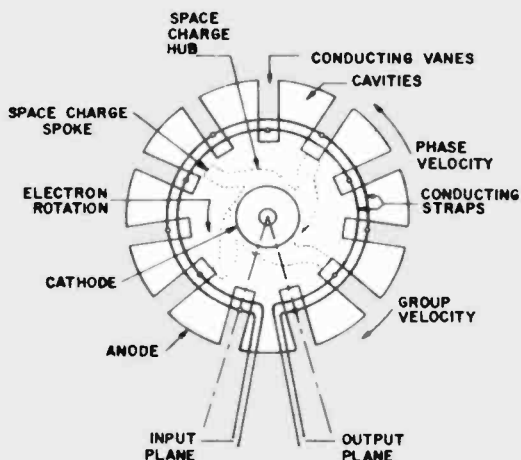
Typical power-beaming ground installation has been constructed in model form. Higher frequency capabilities of new Amplitrons permit smaller antenna arrays, good efficiency.



Here is a diagram of the Amplitron's internal structure. It uses a continuous, cylindrical cathode to produce a rotating space charge in interaction space between cathode, vane tips.

tubes, but the improved Amplitron can now handle many kilowatts thanks to new forced water cooling technology. Three-thousand megacycle tubes of 20 horsepower output are in production and units of 100 horsepower will be available shortly. Five hundred horsepower tubes are expected to be available in the foreseeable future.

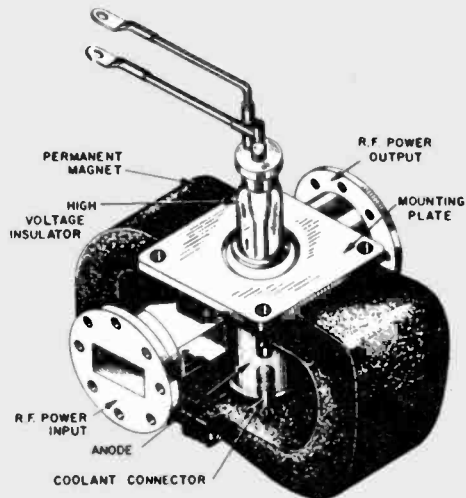The RAMP sky station has a projected 50-foot diameter (dictated by the antenna size on the underside), with a rotary wing 170 feet from tip to tip.



External construction of typical Amplitron bears striking resemblance to that of a conventional magnetron oscillator. Size and weight are also comparable to magnetrons.

The circular collection antenna array on the underside is designed to pick up the microwave energy beamed from the ground and conduct it through waveguides to "lossy" elements, which convert microwaves to heat in much the same manner that a stove element converts electricity to heat. Compressed air or gas heated by the lossy elements will drive a heat engine while turbines operate the rotor blades keeping the platform aloft and supplying the power

[Continued on page 127]




Unit is shown atop woofer cabinet. Pair of wires go to the speaker terminals on amplifier.

Tweeter Globe

By Steven Hahn

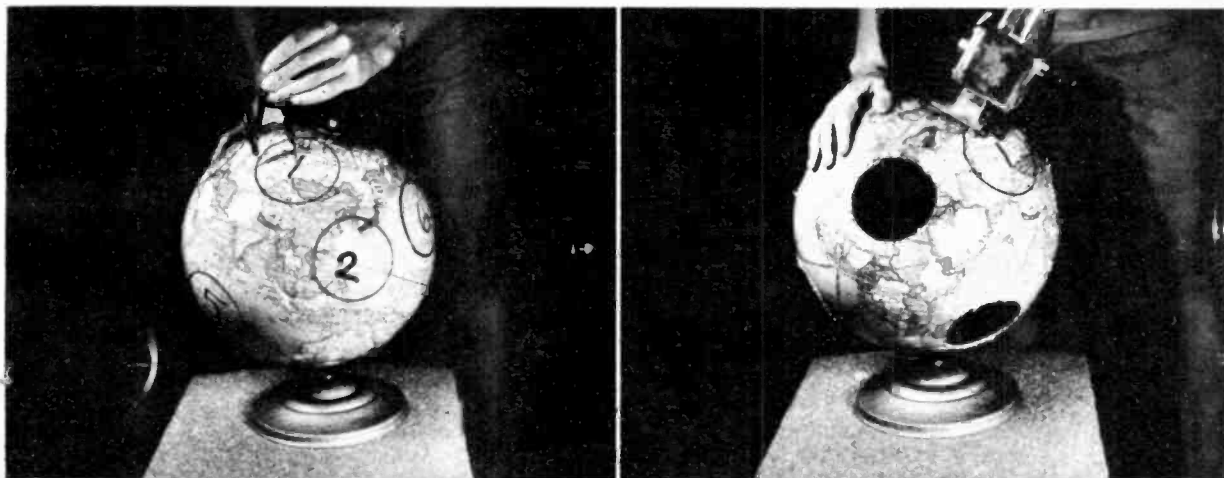This novel addition to your hi-fi system will overcome the problem of high frequency distribution.




Once the number of speakers is decided upon, a compass is used to mark off holes. These holes should be random, not evenly spaced, for minimum interaction between cones. Right photo shows holes being cut with sabre saw.

ONE problem in high fidelity reproduction is the distribution of high frequency sounds. In the low frequency range, this is a minor problem because of the comparatively large size of the speaker radiating element and the distribution patterns of the sound waves. However, as one increases the frequency, the waves begin to take on more and more the characteristics of light beams; that is, they are comparatively narrow and have a tendency to

Globe is cut along its equator line with saw after all the speakers holes have been cut.



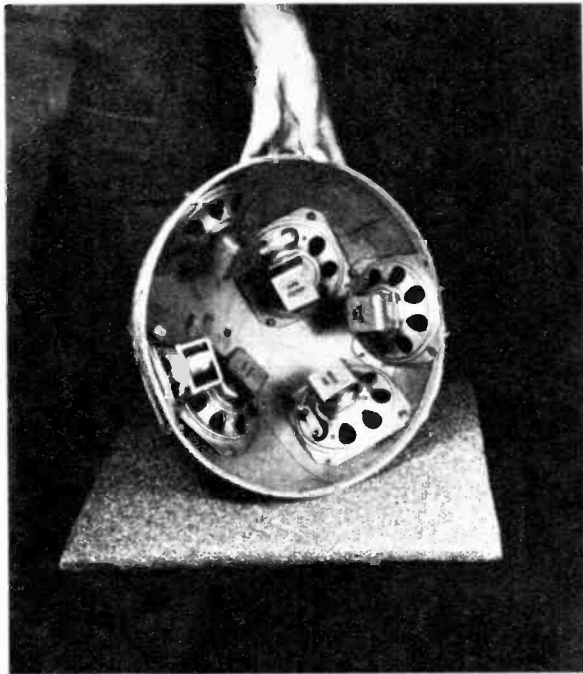Speakers are mounted after their flanges are bent to conform to curvature of the globe.



reflect from various surfaces. The problem is increased by the fact that most high frequency radiators, whether they be horns or tweeters, have a comparatively small radiating surface. If only one of these devices is used to reproduce the high frequencies, a virtual high frequency beam results and if one moves out of this beam, a severe drop in the high frequency response is noted.

The unit which we have built here can be considered a point source of high frequency sound with even high frequency distribution patterns over the entire listening area. It consists of nine 4" hard cone tweeters mounted in random positions in a 12" cardboard ball. An L-pad is added for volume control and a 5 mfd oil capacitor serves as a dividing network. The entire unit, tweeters and all, costs about \$35 to build.

Construction



The ball in this radiator is actually a cheap 12" cardboard globe, available from many department stores. The first

step is to lay out the tweeter openings on the surface of the cardboard globe. This is done with a compass. After marking the opening, a $\frac{3}{8}$ " drill is used to drill a hole in the center of each speaker opening. An electric sabre saw with a fine tooth metal cutting blade is then used to cut out the openings. All this work is done with the globe fully assembled on its stand. The tweeter openings can also be cut out with a very sharp razor or modelling knife. In addition to the nine cutouts, a $\frac{3}{8}$ " hole is drilled near the bottom of the globe to accommodate the L-pad and a smaller hole to take the speaker cable. After this work has been done, the globe is cut in half along the equator.


The flange mounting holes for the tweeters are then laid out by placing the tweeters on the inside of the two globe halves and using a pencil to mark the mounting holes. Generally speaking, speakers of this size require four mounting holes; however, two will more than suffice in this instance. An important

[Continued on page 121]

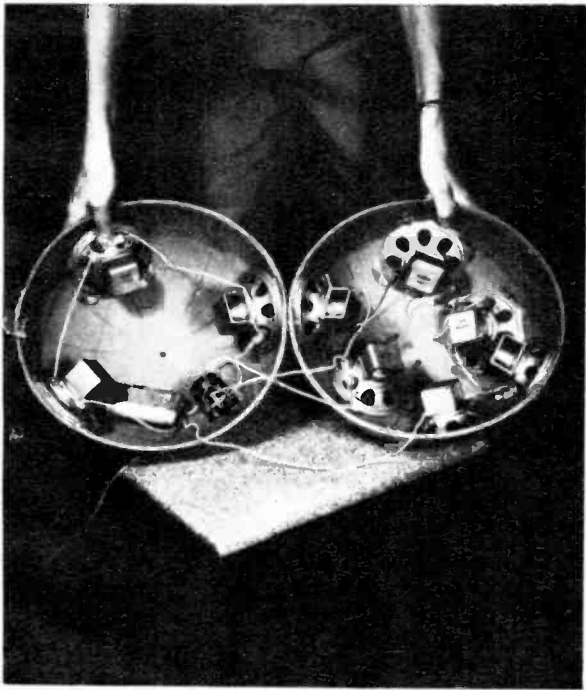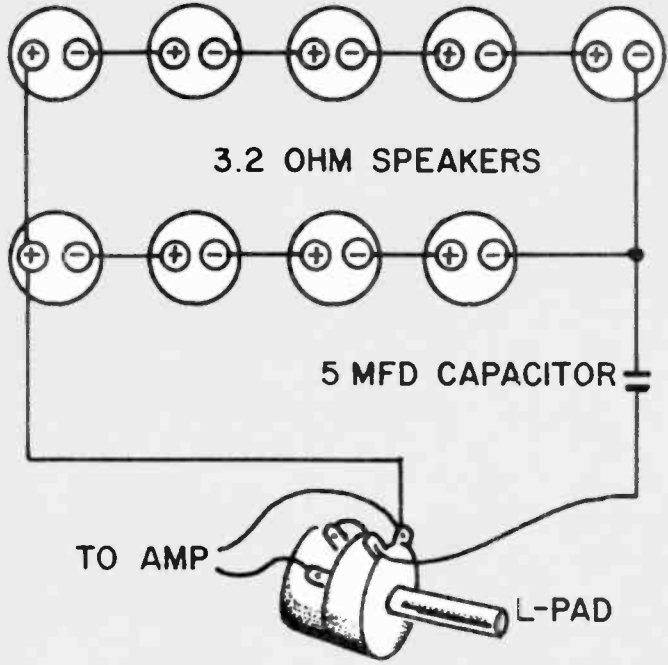Speakers are connected in series-parallel and controlled by 8-ohm L-pad, as shown.



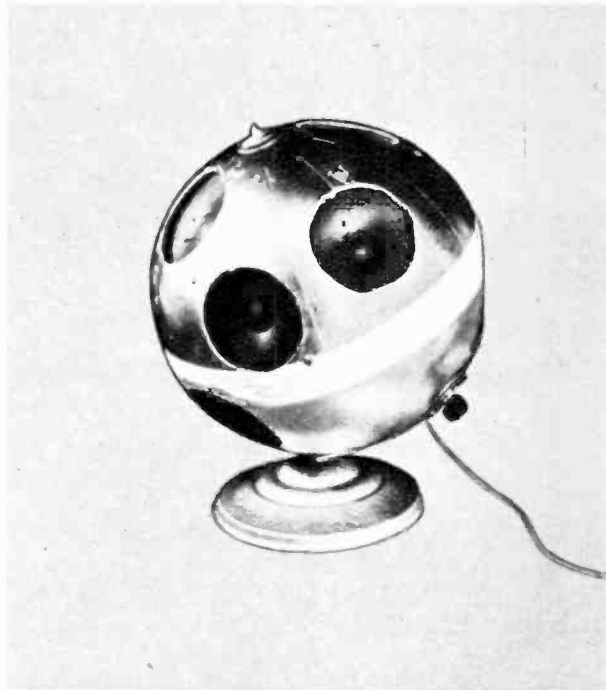Wiring complete. 5 mfd capacitor is at bottom of globe's left half. L-pad is next to it.



Two halves are held together by tape. Globe may now be finished with a coat of paint.




British-made "Fi-Cord," with rechargeable batteries, records at 7½ ips and has a more expensive Swiss "near-twin" in "Stellavox."

New Tiny Tape Recorders

Once there were none, now there are many battery-powered tape recorders at a variety of prices.

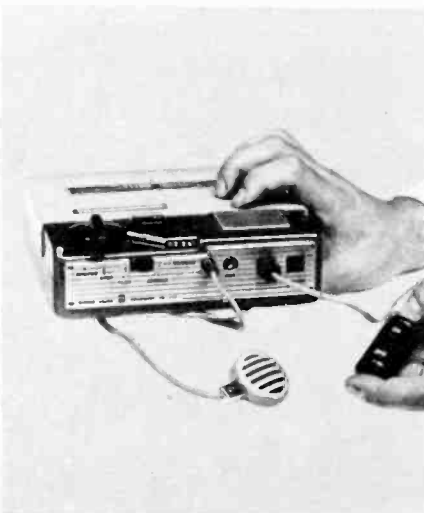So new it doesn't yet have a price tag—that's this Nippon Sound "Transi-corder." It operates on AC or battery, has meter, 2 speeds, remote switch.





Four conventional flashlight batteries run the Mark III Phonotrix tape recorder with speaker.



Not yet available in this country is the Japanese Kowa, which is a 9-volt unit, 3 3/4 ips only.



Stuzzi comes from Austria and records on two speeds. Push-button controls are on the top.





Here's the "Hi-Delity" 401B machine from Japan at \$159.50. Single lever controls all.

ABOUT five years ago you would have had to look mighty hard to find a small, battery-operated tape recorder. Chances are that if you had wanted one badly enough, you would have had it especially made for you at a fancy figure. Today, however, all that is changed. Whether you be in America, Europe, or Asia, you can take your pick of many transistorized recorders—and there are more coming all the time!

The battery-operated tape recorders we've seen range from "gimmick" machines that sell for under \$30, to professional broadcast quality three-speed instruments that carry price tags close to \$1000. While some of these small machines operate only at the 1 7/8 ips speed, other more sophisticated units zip the tape along as fast as 15 ips. Many have a myriad of specially designed accessories that include such items as magnetic telephone pickup coils, extension speakers and remote control switches, while still others don't even have an electrical fast rewind.

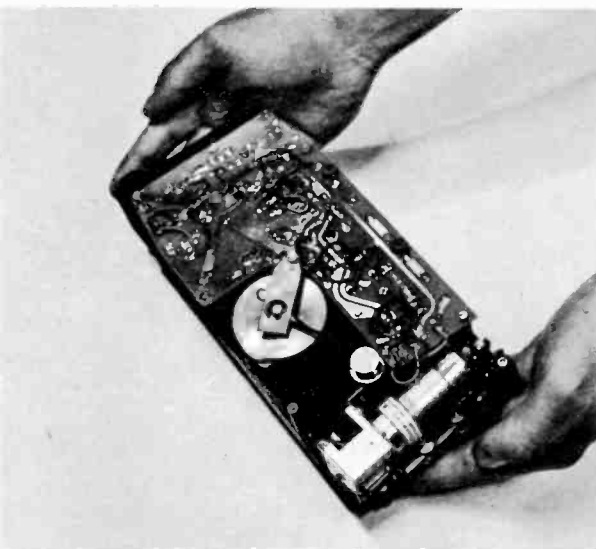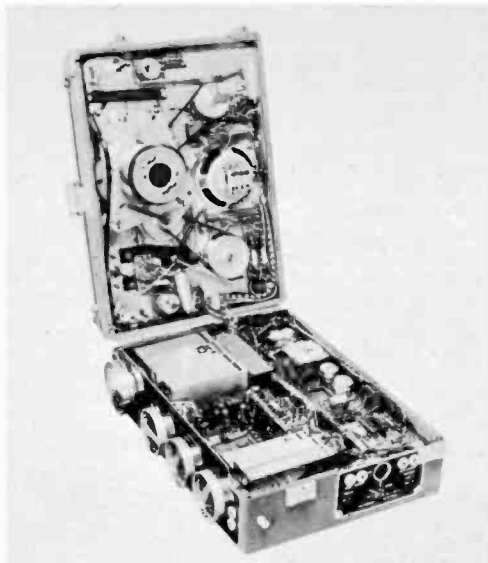Electronics Illustrated's survey of this new and exciting field



Upper left: The circuitry of the deluxe Nagra III, a Swiss-made instrument with thirty transistors, three speeds to 15 ips.

Above is the same unit put back together. There are several input and output sockets and a meter located on panel.

Photo at left shows how the bottom of the 5330 "Fi-Cord" looks. All battery-operated machines use printed circuits.

has turned up some very interesting tape recorders, along with the dismaying fact that American companies seem to be avoiding the manufacture of general purpose units, leaving this field almost exclusively (but not quite) in the hands of makers in Japan, West Germany, Switzerland and Austria.

What have the American manufacturers been doing? Twiddling their thumbs? Well, evidently some have, but not all. A few have been working out miniature models for inclusion in guided missile and space rocket systems. Perhaps we'll hear more about them when present-day military electronic developments finally filter down

to you and me on the consumer level.

Other U. S. companies have concentrated on making miniature tape recorders primarily designed for dictation. Among them are units by Dictaphone, Comptometer, Peirce, etc. Of course, these may be used for on-the-spot recording other than dictation, however they usually feature elaborate (hence more expensive) start-stop mechanisms and generally record only at the slowest speed, $1\frac{1}{8}$ ips.

Let's take a look at some of the battery-operated general purpose tape recorders that can be used anywhere.

The Grundig "Niki" lists for only \$79.95 and is made by one of West Ger-

many's leading electronics manufacturers. It is one of the few portables we've seen that has a plastic case, which tends to cut down on its weight (4½ pounds). It operates on ordinary "D" flashlight batteries and its fidelity is more than adequate for voice reproduction. Just like most small tape recorders, this one records in the half-track fashion and only at 3¾ ips. The tape, on standard three-inch reels, does not have to be threaded through any intricate capstan system, but is simply dropped "into the slot." The machine we tested had very good positive action controls. A single knob handles the start, stop, record-playback and fast rewind functions. The built-in four-transistor amplifier draws little current from the batteries, which can last as long as 50 hours. Batteries,

printed circuit, motor, etc., are all easily accessible for servicing. Distributor: North American Industries, 101 W. 31st Street, New York 1, N. Y.

There are a couple of miniature tape recorders on the way that are shrouded in all the legendary "mystery of the Orient." How come mysterious? Well, we have seen and tested them, but for the life of us we cannot get anyone to quote prices at this writing. Both units are from Japan and one is the recorder pictured on this month's cover. It is the Yashica YTR-330, which will be marketed here by the famous camera company. Also using three-inch reels and half-track recording head, this portable is designed to operate at 6 volts and the convenient 3¾ ips. Besides a built-in
[Continued on page 114]



The low-priced (\$79.95) Grundig Niki has its innards exposed in picture top left. Circuit is accessible for servicing.

Above right is the same tape recorder. To thread tape from three inch reels you just drop it into slot above stop button.

Mohawk Business Machines makes this tiny pocket tape recorder which actually has twins under other trade names.



spotlight on:

40-Meters

By C. M. Stanbury II


This article, second in a series, covers 7 to 7.3 megacycles—what's on the band and how hams and SWL's can help free the band from Red propaganda.

THOSE frequencies between 7000 and 7300 kc comprise the most complex band anywhere in the radio spectrum. Its uses are myriad. Historically, 40 meter channels are used by both broadcaster and amateur; have started an international donnybrook; and have been open territory in the Cold War.

The experienced ham uses the 40 meter band for rag chewing, for regional and national message networks, and also has found plenty of DX in these midlands. Almost more important, it's one of the best bands for the Novice. Does this sound like an active band to you? . . . Well, you're right! Why?

In the first article of this series we mentioned that 75 and 80 meters were just above the dividing line between short and medium wave. Forty meters is also near a dividing line—the one between regional and international shortwave. It lies at about 7 mc, depending upon sunspot activity, season of the year and even day-to-day variations of ionospheric density. Ionospheric absorption of the 40 meter signals can be very high or close to nil. Skip distances during daylight hours can be so short as to almost permit semi-local QSO's via skywave. But at night, under ideal DX conditions, they can be so long as to allow only transcontinental contacts.



In other words, the day-night pattern of 75 and 80 meters is repeated here, but in much more generous proportions. While the sun is high, maximum range is somewhere around 500 miles, but this increases perceptibly toward sunset and even more rapidly during the hours of darkness. With a decreased noise level and the longer period of darkness, a winter night is obviously the peak period for 40 meters. And with all of these variations, it is obvious that not only is anything possible, but

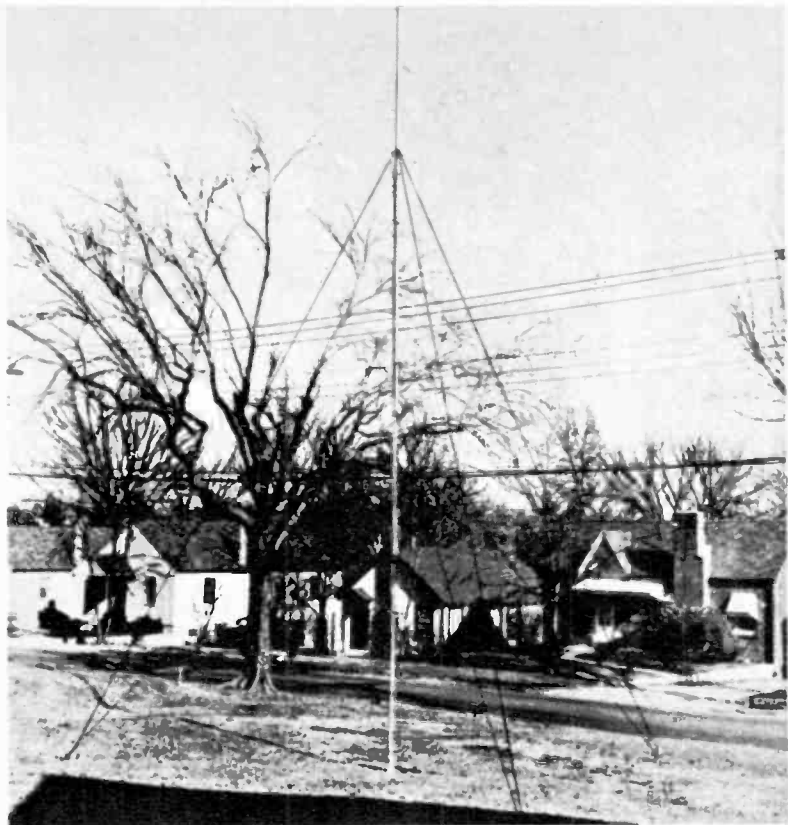

Here's a commercial vertical antenna (Mosely V-5) designed to work on 10-80 meter bands. For homemade 40 meter antennas, turn page.

Reds love to QSL propaganda broadcasts. Note frequency—smack in middle of U.S. ham band.

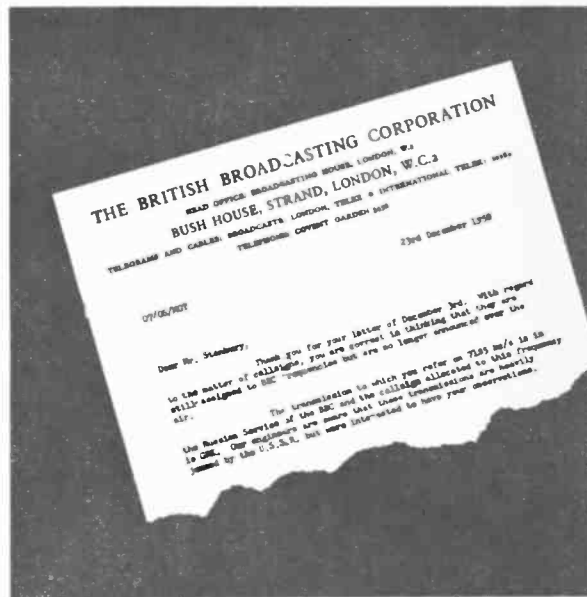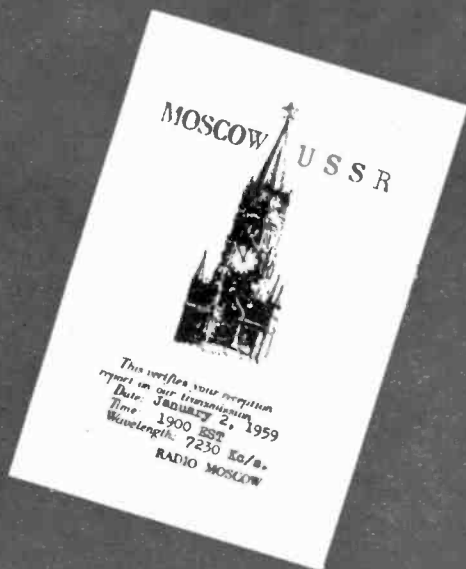This letter from the BBC confirms two types of interference experienced on the 40 meter baad.



also, everything should be expected.

The 40 meter band is 200 kc smaller than the 75-80 meter allocation, and the 'phone portion of the band is only half the size of 75 meters. (Here both the CW and 'phone portions of the band go by the same name.) While increased skipping tends to reduce QRM (man-made interference), reduction in space cancels this out. There are very few clear channels available for 'phone.

Forty meters is traditionally a CW (radio-telegraph) band. It has only been within the last ten years that the FCC has permitted any voice transmissions on the band at all, and because of these crowded conditions for voice between 7200-7300 kc, CW still remains the most effective means of communication, especially for DX.

Many hams overseas are permitted to use only the lowest 100 kc of the band and 75 percent of these are limited entirely to CW. Hams in the United States wishing to work them generally have to use CW also.



With half the wavelength of 80 meters, it is possible, but not likely that some antenna directionality can be achieved. Sixty-five feet of wire is still a heck of a lot to "rotate." Obviously, with a better antenna, the less powerful and less expensive transmitter becomes more effective. (See diagrams.)

We said 40 meters was a good band for the Novice, and so it is. Limited to

75 watts transmitter input, he can use the great variation in skip and range of 40 meters to his advantage. During the course of most days, a Novice is able, propagation-wise, to work contacts in every part of the United States. And unlike higher frequency bands, 40 meters is almost never completely dead. Even at 0300 EST an East Coast amateur would be able to QSO with operators on the Pacific Coast, where it is only midnight. Should a Far Western Novice wish a QSO at 0300 PST, he would find that it was 0600 along the Atlantic Seaboard and a number of early bird amateurs will have returned to the band.

In 1947 the International Telecommunications Union (ITU) divided the 40 meter band between amateur and broadcast stations. Seven to 7.1 mc is allocated to hams throughout the world. In Europe and Asia, 7.1 to 7.3 mc was proclaimed broadcast territory, while in the Americas the remainder of 40 meters was turned over to the amateur. As you can see, this was a regional solution and as 40 meters is frequently *not* a regional band, such a compromise was far from perfect. For example, many broadcast stations, although beamed into broadcast territory, are received in this hemisphere. Further, when such a station is jammed, the interference is still worse.

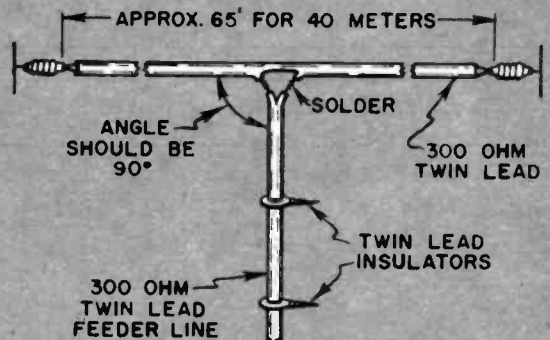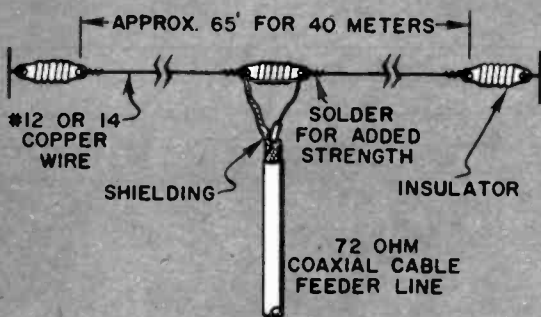Undoubtedly the ITU took all this into account when it set up the dividing




lines and almost all concerned thought they had made the best of a difficult situation. But they did *not* figure on Radio Moscow taking advantage of the situation.

What Moscow has done is to beam 40 meter transmitters toward the United States. At certain winter hours they use no less than five outlets with a total power of approximately half a million watts! Each puts out in the neighborhood of 100,000 watts (a hundred times the maximum power permitted for amateur use). With this system the Kremlin holds down at least one channel, often two or three. If this does not violate the letter of the agreement, it is certainly contrary to its spirit.

With a dropping sunspot count and the resultant increase of low frequency range, this situation is going to get worse. Radio Prague (in Red Czechoslovakia) has added another 100 kw to the assault and there may be more.

There is little that can be done about such stations as GRK. The operating agency, in this case the BBC, is sticking to the ITU agreement and any interference caused by them is accidental.

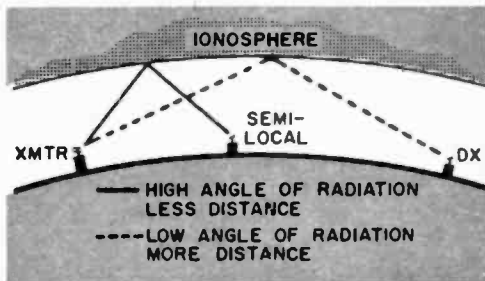The propaganda broadcasts are in a different category. First, you must understand that Moscow has no special desire to give the ham a hard time. There would be no point in it, and the Kremlin never does anything without a reason. The use of 40 meters simply




An antenna on 40 meters should be at least a half wavelength above the ground so that the low angle of radiation will not be attenuated.

increases their propaganda coverage. If it didn't, they would stay off the band.

Okay, why not fix things so it *doesn't* increase their coverage!

EI's plan consists of two parts. First and most important, amateurs when making semi-local (short skip) or other cinch contacts on 40 meters should use the propaganda channels, 7130, 7150, 7180, 7230, 7240 and 7255 kc. His QSO will be unaffected, but the Red broadcasts will certainly be wrecked.

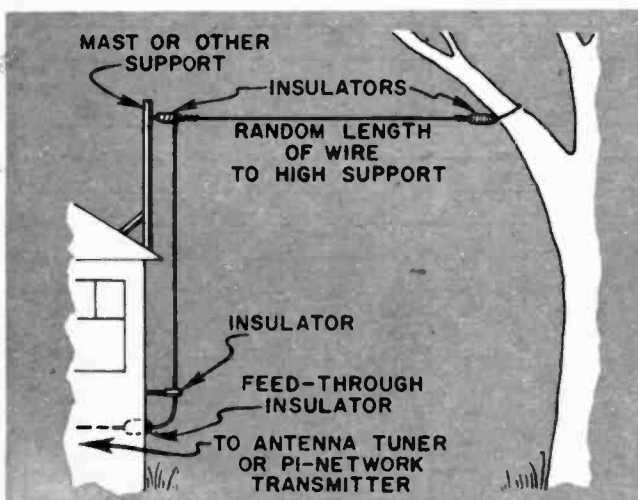The second step is in the hands of the SWL's, particularly those who listen in on the amateur bands. They should send a reception report to Radio Moscow stressing the interference on 40 meters. This way the Kremlin will be sure to know their transmissions are not getting through. 📻



A simple, efficient 40 meter antenna is the half-wave dipole, far left. If you can't run it 65', up to 13' from each end may droop down.

In center panel we have the popular folded dipole, similar to the plain dipole, but using 300 ohm twin lead feeder instead of 72 ohm co-ax.

Most basic antenna is the long wire, right. It is tuned electrically to compensate for random wire, which must be matched to half wave.

SWL Antenna Tuner

By Don A. Smith

Improve the reception of your short-wave receiver with this unit. It will peak up those weak stations.


MANY short-wave listeners are forced, through lack of space, to use short antennas. Undesirably short lengths of ten to twenty feet seem to be common. To make matters worse, many receivers do not come equipped with an antenna trimmer adjustment to peak up the signals.

The unit described here goes a long way toward correcting this condition and requires no internal connection to the set. The circuit is a simple pi-network, used quite often in the output stage of ham transmitters. Its ability to *electrically* change the length of a physically short wire makes it an excellent adjunct to a receiver.


Construction begins by winding the coil. Follow the specifications given in the parts list. The total length of the winding will take up approximately 1 5/8" on the form. Drill two small holes near the beginning of the coil and two more at the end. The wire can then be threaded through these holes [Continued on page 119]

PARTS LIST

C1, C2—140 mmfd variable air capacitor	turns. 1 1/4" diameter coil form of plastic, Bakelite, etc., approx. 3/2" long
SW—5-position rotary switch, non-shorting (Centralab PA 1002 or equiv.)	Misc.—Chassis box (LMB #136), 2-lug Cinch-Jones Barrier strip, banana plug and jack
L—Close-wound coil, 100 turns of #26 enamel wire tapped at 5, 12, 35 and 60	

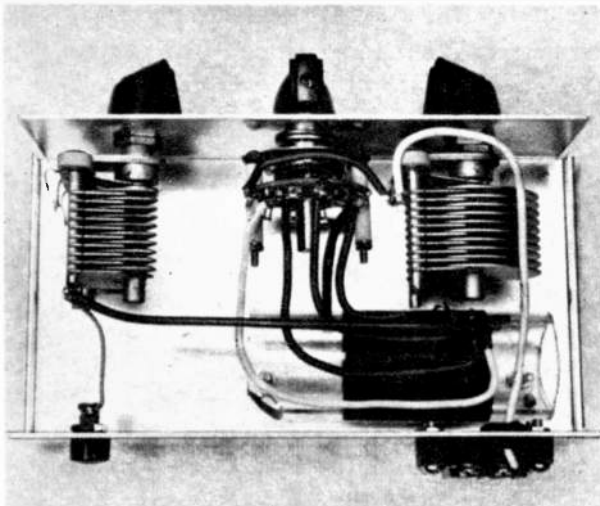


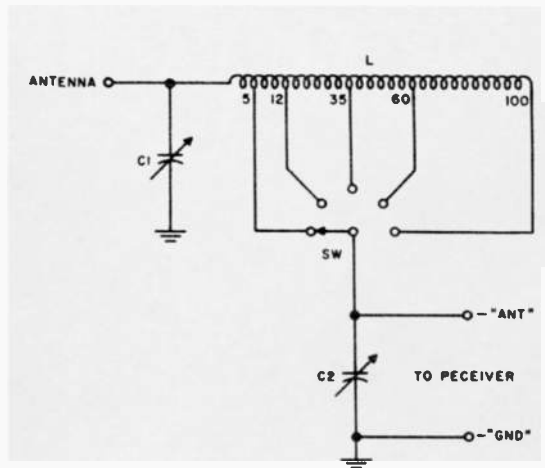Inside view of the tuner with cover removed. Two tuning capacitors are along top edge with switch between them. Coil is at lower right.




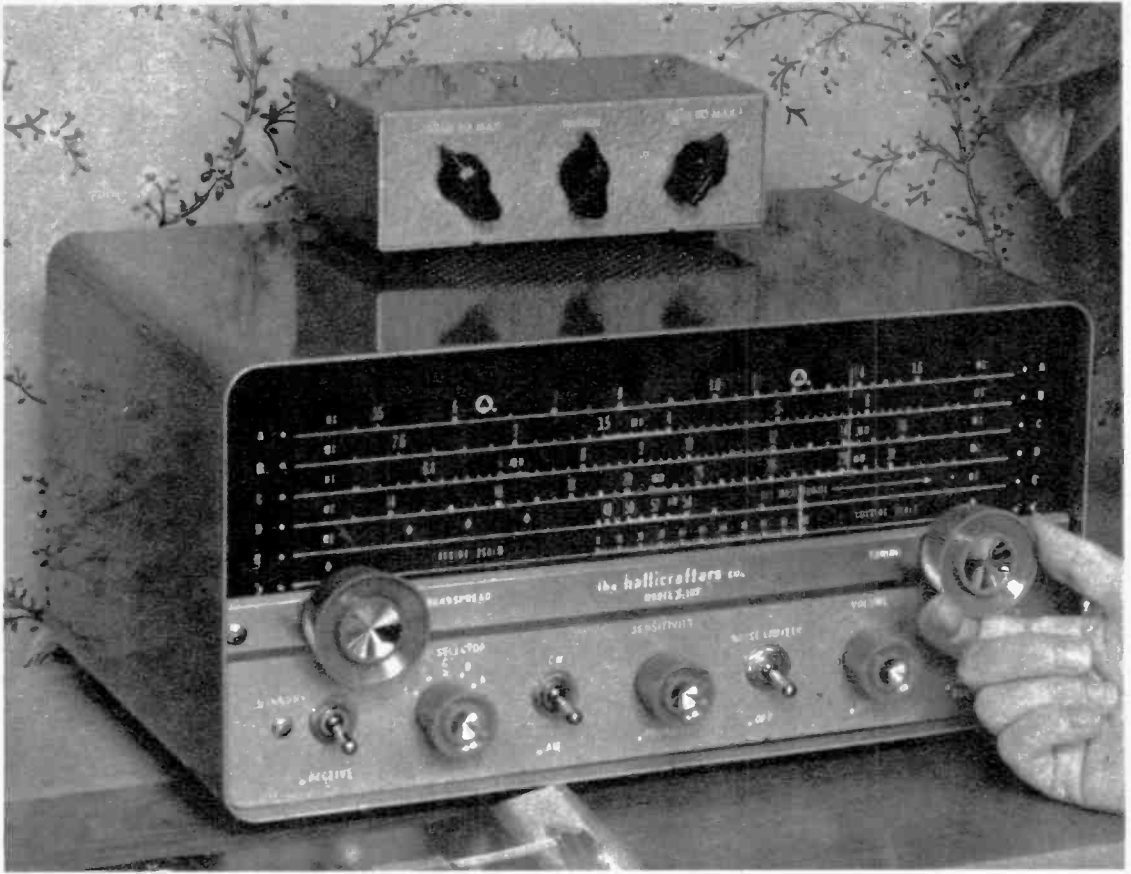
Schematic indicates the location in turns of each tap on the coil. "Ant" and "Gnd" go to a 2-terminal barrier strip at rear of unit.





To use model, connect a banana jack to the antenna wire and plug into tuner. Run a short shielded wire from tuner's output terminals to the receiver. Vary switch and tuning capacitors for best signal strength.

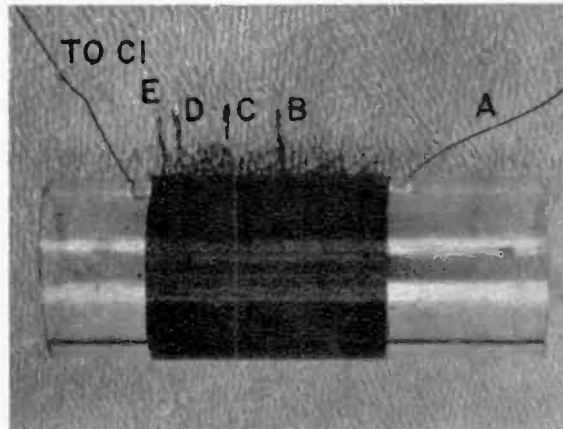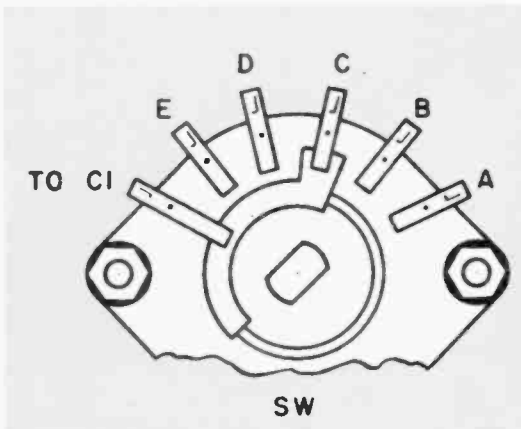Switch layout is below left. Letters indicate the coil lead connections in photo at right. Letter "E" corresponds to 5th turn on coil, the first tap.





Unit is between tripod legs with two photofloods plugged into it. Photographer presses solenoid button which will turn up floods and release shutter.

Flash your Photofloods

By W. F. Gephart

Pose a subject in dim light for natural expression.

This unit eliminates the glare of photofloods.



PHOTOFLOODS offer a number of advantages over flash in many cases, but have a definite disadvantage in portrait work because the bright light prevents a natural expression. This is particularly true when several lamps are used for balancing.


It would be highly desirable if the bulbs could be synchronized with the shutter like flash bulbs, and the exposure made before the subject could react to the brightness.

The unit shown here handles the high currents and is designed to be used with both solenoids (operated by a battery in this unit), and synchronizing shutters, such as an "M" type, set for a 20 millisecond delay. It can also be used with a zero delay ("X") synchronized shutter if exposure compensation is made.

While it takes substantial time for a flood bulb to reach maximum brilliance from the cold or "off" condition, this time is drastically reduced if the filament is well-heated, as it is when oper-

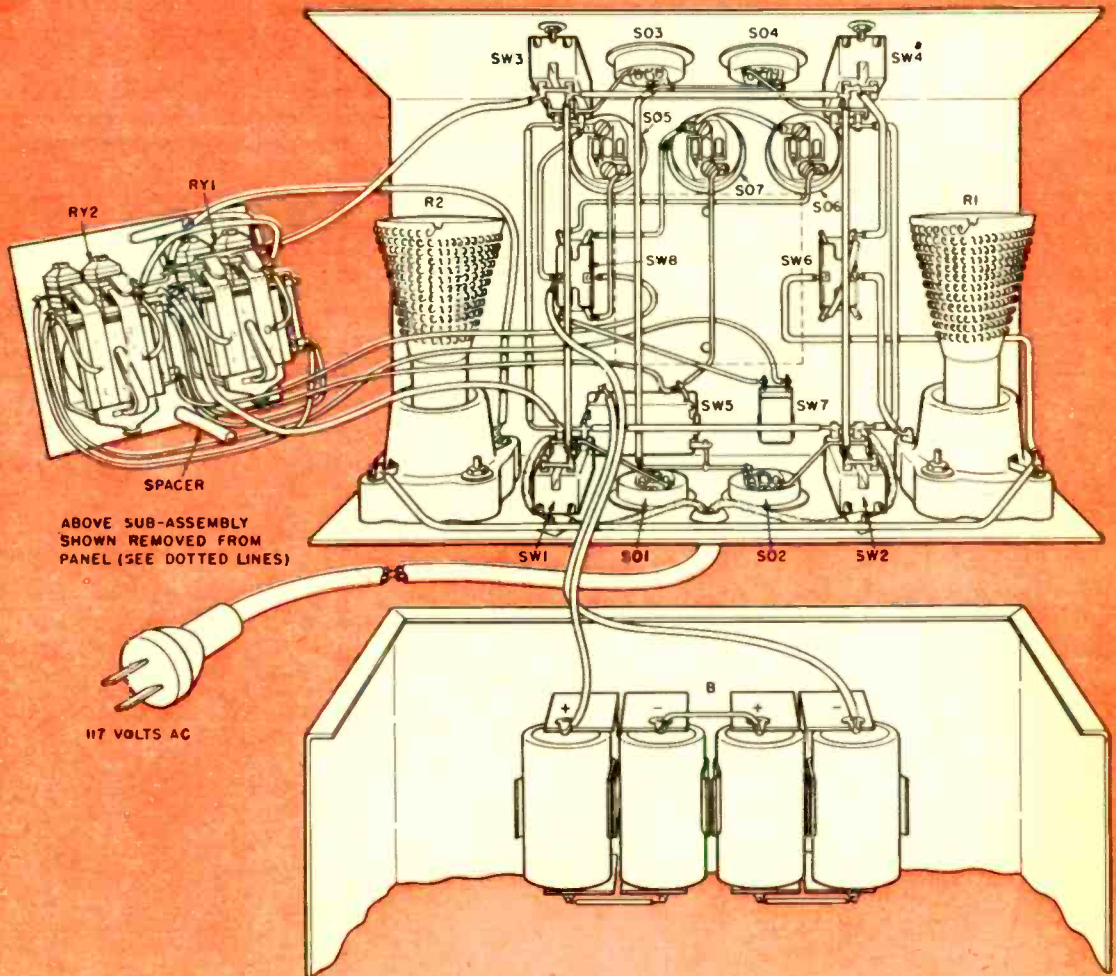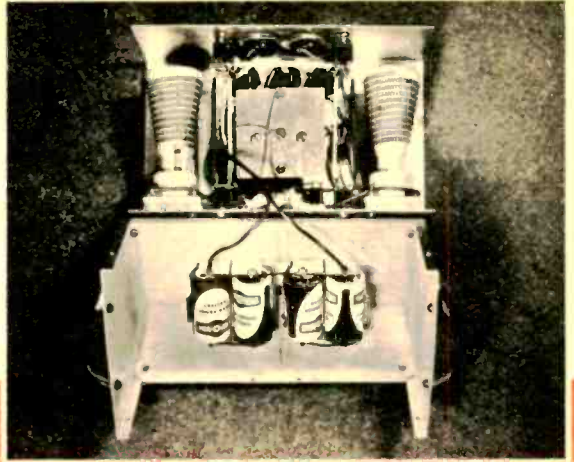
Note square panel located in upper half of case (between two heater elements). It is shown removed in guide below.



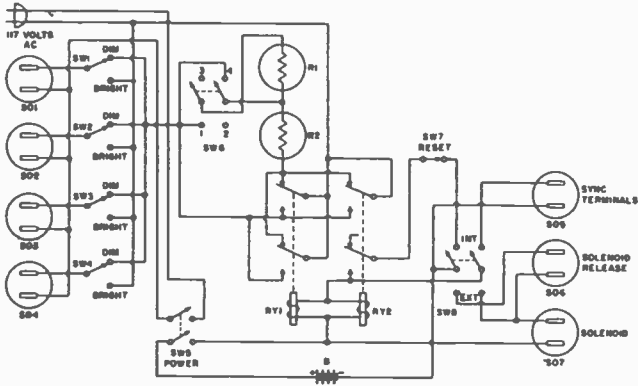

In right of schematic; sync terminals receive cable from camera shutter, solenoid release from pushbutton on cable.

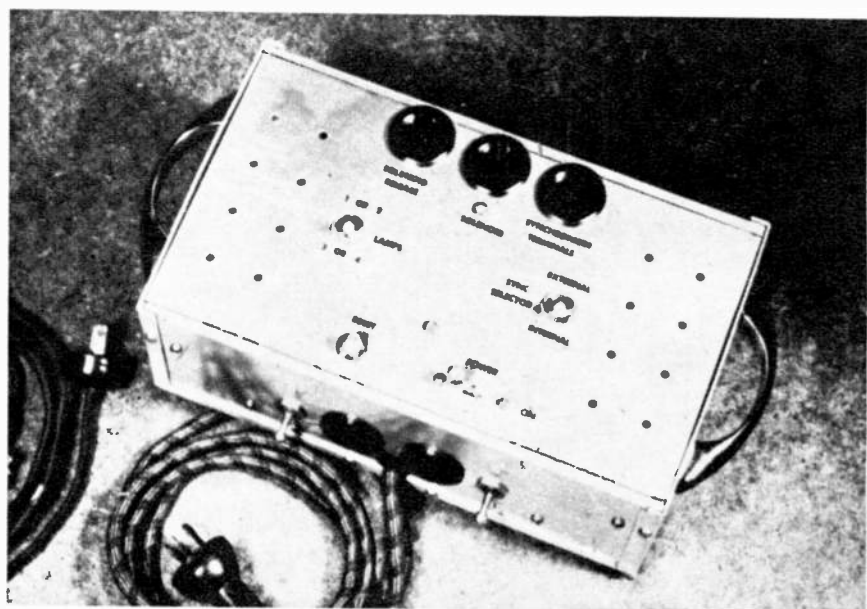Holes on both ends of front panel provide ventilation for heater elements inside case.



ating under lowered voltage. When a Number 1 photoflood is glowing to an extent equal to about a 25 watt bulb, it will reach full brilliance in about 5 milliseconds after full voltage goes on.

Since the shutter contacts cannot handle the high current used by photofloods, the actual switching is done by relays, which also involves a delay. It takes about 5 milliseconds for the relay to close after the voltage is applied. In this unit therefore, the photofloods will reach full brilliance about 10 milliseconds after the synchronizer contacts

[Continued on page 116]


PARTS LIST

- SO1 through SO7—Chassis-mount female socket (Amphenol 61-F)
- SW1 through SW4—DPDT toggle switch 15 amp, contacts in parallel
- SW5—DPST toggle switch 20 amp
- SW6—DPDT toggle switch 6 amp
- SW7—SPST pushbutton switch normally closed (Carling 170)
- SW8—DPDT toggle switch 3 amp (Carling 316-73)
- RY1, RY2—DPDT relay, 6 volt DC coil, 12 amp contacts. (Guardian Series 200 coil with Type 200-4 contacts)
- R1, R2—600 watt Edison base heater elements
- B—6 volt battery (four "D" cells in series)
- Misc.—Metal case 10"x6"x3 1/2" (Bud CU-3010), two porcelain Edison sockets, asbestos line cord, two dual battery clips, 3"x3" metal plate for mounting RY1, RY2 (used with two 1/4" screws and two 1 1/2" spacers), Solenoid push-button release switch mounted on cable (Switchcraft E-913)

Loran Lights the Way

By Rafe Gibbs

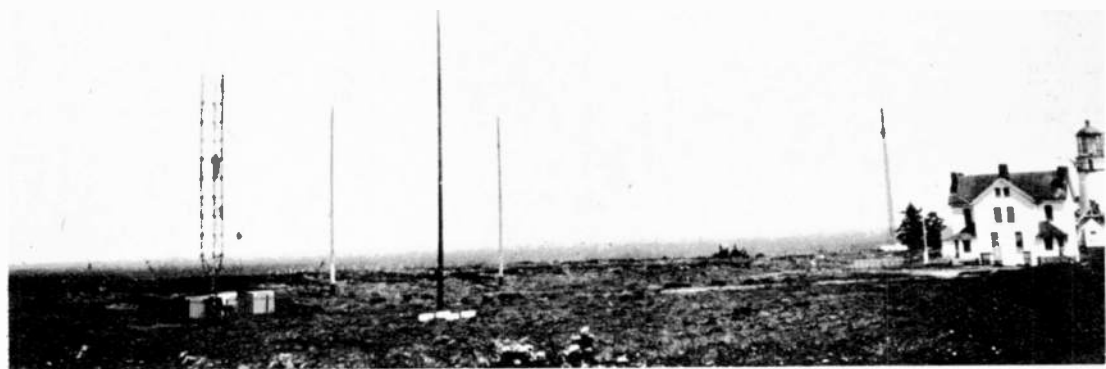What happens when bad weather blots out the sun and stars? Navigator lost? Not if he has LORAN!




A 300-foot LORAN antenna (left) is flanked by communications antennas. Cape Blanco lighthouse. Below, technicians check transmitter pulse width.



LIGHTNING zipped down the guy wire of the 300-foot steel tower and danced along a wire fence. It was a rugged night at the isolated U. S. Coast Guard Station on Oregon's Cape Blanco. The historic lighthouse shone little farther than a

sailor could throw his hat. But in an adjacent building, electronic signals continued to reach out across the rough North Pacific helping to guide ships and planes as far as 1400 nautical miles away. These signals, part of the world-wide LORAN system, are of vital importance to safe navigation.

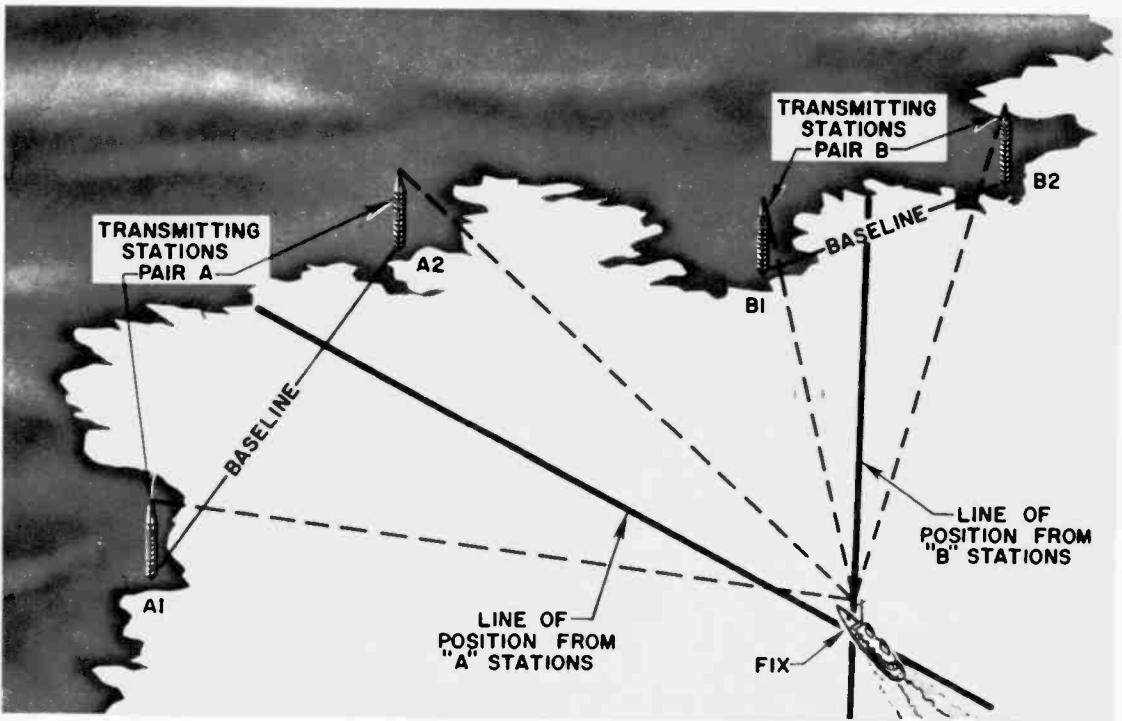The Cape Blanco station is one of 60 LORAN installations strategically placed on the globe. Fifty are operated by the United States; 6 by Canada; Denmark 2; Iceland 1; and the United Kingdom 1. The world's principal sea and air lanes are covered by LORAN 24 hours a day, providing navigators on or over the



Lines of position are found by measuring time difference between signals from paired LORAN stations. Navigator's fix is established at point where two lines of position meet. Latitude and longitude are then obtained from LORAN charts.

ocean with accurate positions day or night and under practically any condition of weather or sea.

The term "LORAN" is derived from the initial letters of the words "LONG RANGE Navigation." Ordinarily, over water, ranges may be expected from 500 to 900 nautical miles during the daytime and up to 1,400 nautical miles at night.

The principle of operation is based on the difference in travel time (in millionths of a second) between radio signals from two transmitting stations spaced several hundred miles apart. Pulses from one station are delayed ever so slightly so as to arrive last.

On the ship or aircraft, a LORAN receiver-indicator electronically determines the difference in times of arrival between pulses from the "master" and from the "slave" (or second) station. This measurement yields a line of position, as indicated on a specially prepared area chart. The intersection of two or more lines of position fixes the location of the ship or plane.

LORAN utilizes radio because radio waves have a constant speed and hence a direct relationship exists between time of travel and distance traveled. Thus, measurement of time is, in effect, a measurement of distance itself.

The radio signals which are transmitted by LORAN stations are not continuous transmissions, such as those of commercial broadcasting stations, but are "pulse" signals, short bursts of radio energy transmitted at regular intervals. The use of specially timed "pulse" signals permits the signals to be properly identified by the receiving ship or plane.

The Cape Blanco LORAN station, for example, is a double slave station paired with Cape Arena, Calif., on one chart line, and with Point Grenville, Wash., on another LORAN line. Pulses having a peak power of almost a million watts are transmitted on 1950 kc. The repetition rate is $33\frac{2}{3}$ cycles per second.

The receiver-indicator equipment
[Continued on page 115]

Complex radio and teletype systems connect the Cape Blanco LORAN station with other Coast Guard units so that up-to-the minute weather data can be transmitted to ships and planes thus permitting the station to serve more than a single purpose.




Wreck of the small fishing boat *Suzy Ann*, blown off course by a bad storm, rests amid driftwood at the very doorstep of the Cape Blanco lighthouse. Almost all large ships and fishing trawlers carry LORAN gear to safeguard against a similar fate.



An off-the-air station serves no one. Here a technician repairs electronic timer used to obtain precisely synchronized LORAN signals.



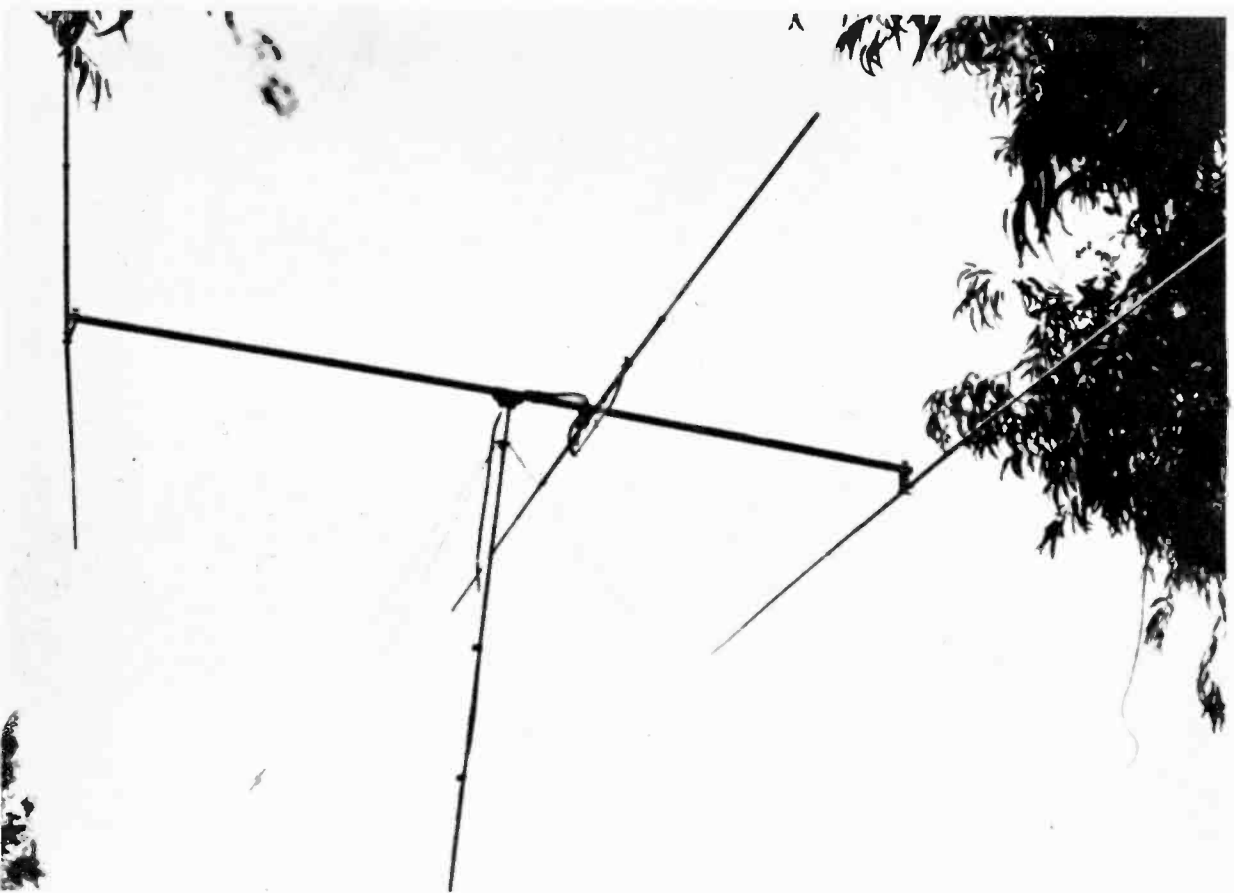Each LORAN station automatically keeps its own log, providing a continuous record of synchronizer. It must be checked regularly.



Three-element beam sits atop mast supported by guy wires. Directivity of this antenna would be to the left, a rotator will make it omnidirectional.

build a


CB Beam Antenna

By Donald L. Stoner


Triple your signal strength with a beam—and pick up less interference on the crowded Citizens band.

EVEN though the government limits your power to five watts input, you can increase your range if you construct a *beam antenna*, which should just about triple your signal strength. This device is a variation of the simple dipole antenna, however, *parasitic elements* are added to focus or concentrate the radio energy. Thus you can squirt your signals in any desired direction just like a water hose. This, of course, reduces interference to and from other stations.

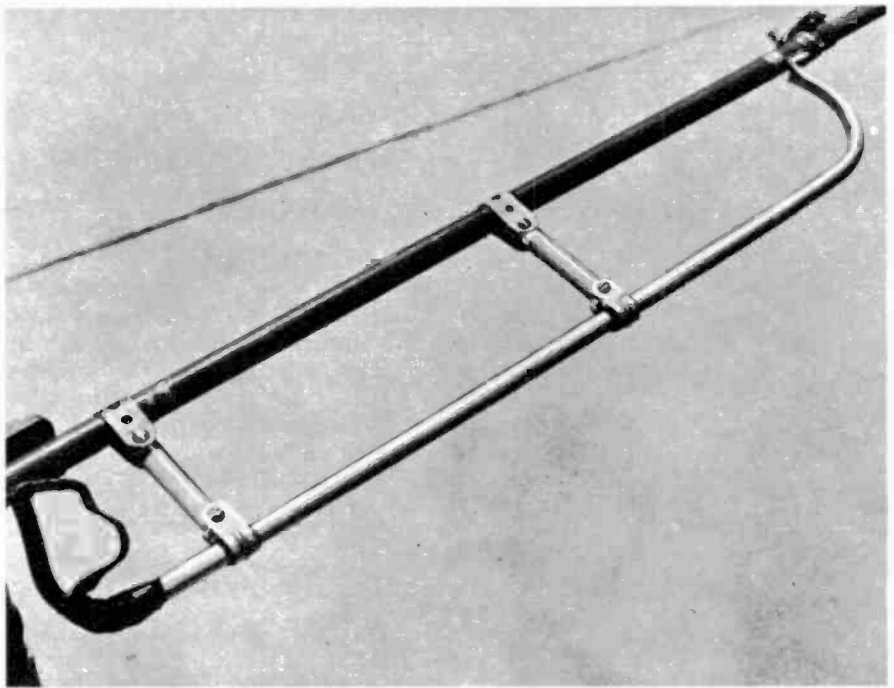
The three elements are supported by a 10 foot length of 1½ inch thin-wall conduit. This part of the antenna is called the boom. Automobile muffler clamps are used to secure each element to the boom. An additional [Continued on page 106]



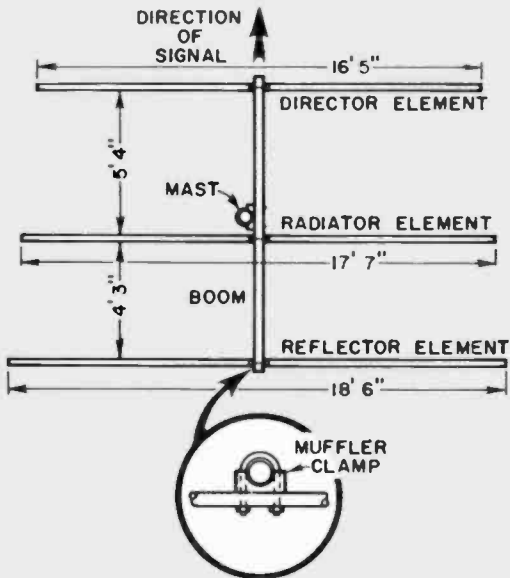Close-up of gamma tube, held to radiator by two insulators, and clamp at right end. Note that left end of tube is taped to prevent moisture from affecting performance.



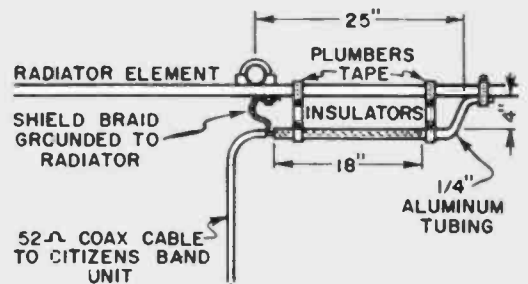Follow these dimensions and mechanical details for construction of boom and 3 elements.



Detail for gamma tube construction. This matching device hangs below the radiator.

Milt Kiver on

Probes


These valuable accessories extend the range of measurements you can make with a meter or 'scope.

PROBES are auxiliary devices used primarily with VOM's, VTVM's and oscilloscopes. They are designed to enable these instruments to perform measurements that could not be made without them. For example, a vacuum-tube voltmeter can ordinarily measure up to 1,000 volts DC without any special probes. However, by substituting a high voltage probe in place of the conventional probe, voltages up to 50,000 volts can be measured. This is one illustration; there are others as we shall see presently.

High-Voltage Probes

A high-voltage probe is a probe that contains an exceedingly high resistor within its housing. All of the applied high voltage,

Fig. 1. Kit of probes for use with 'scope includes Direct, Isolating, Crystal, Low Capacitance and Vacuum Tube type in large pocket at left. At extreme left is a high voltage probe. Note its large insulating fins.

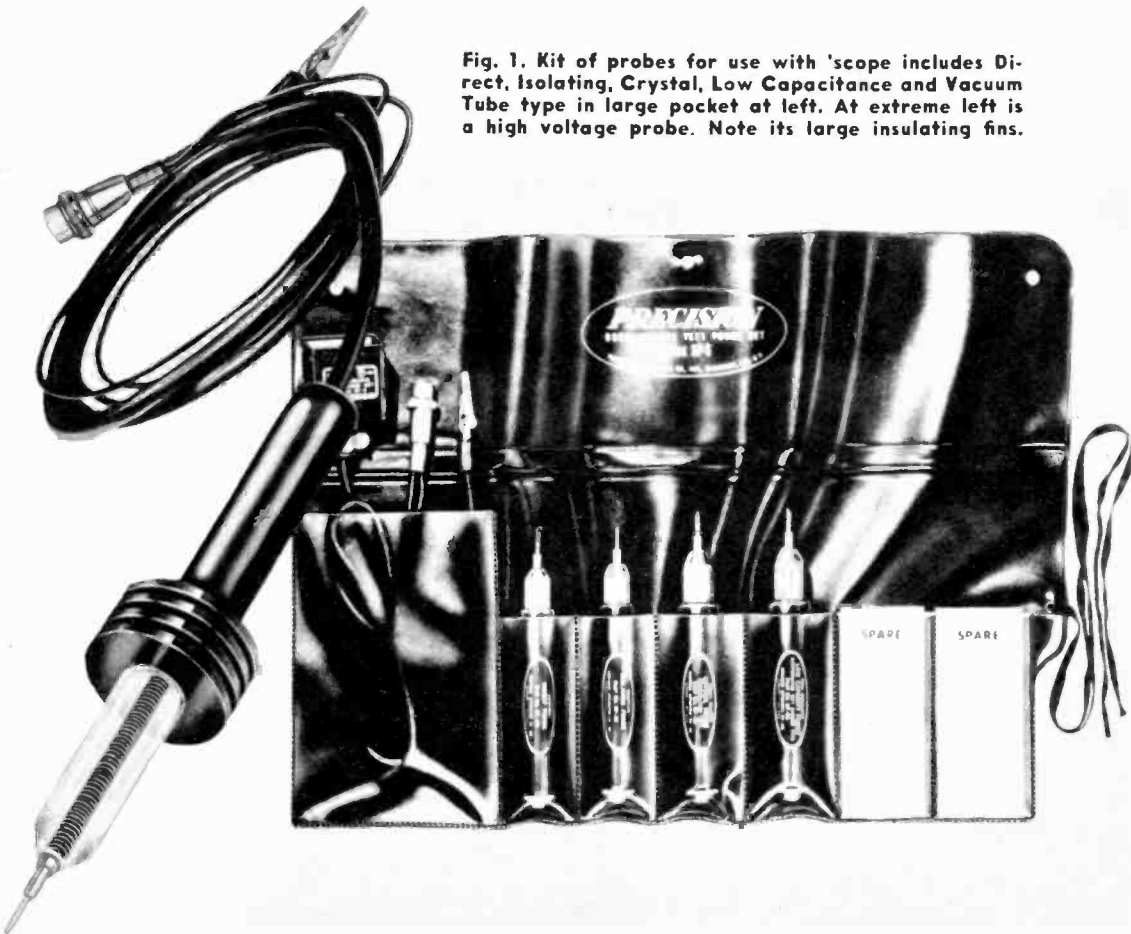


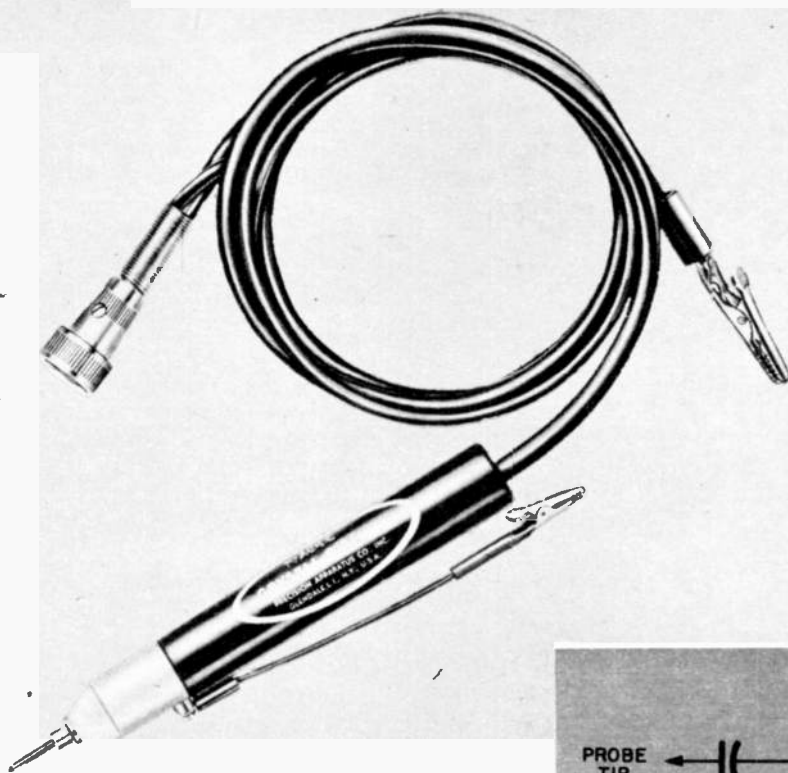


Fig. 2. RF probe enables a meter to measure high frequency voltage. It is useful in signal tracing RF and IF stages. The 1N48 rectifier in the schematic changes input to DC.

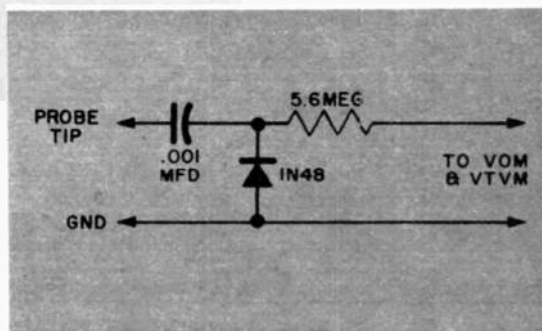

except a small part of it, is absorbed by this probe resistor. Thus, if 30,000 volts is being measured and the voltmeter is set to its 1,000 volts scale, then 29,000 volts might be dropped across the probe internal resistor and only 1,000 volts appears across the voltmeter input.

Physically, the high voltage probe appears as illustrated in Fig. 1. It is constructed of bakelite, lucite, polystyrene, or some other suitable plastic material. The overall length, from probe tip to handle end, is considerably greater than the conventional VOM or VTVM probe. This is done purposely to prevent any possibility of arc-over between the tip and the person grasping the handle.

High voltage probes must be specifically fashioned to the voltmeter (VOM

or VTVM) with which they are being used. This stems from the fact that any applied voltage divides between the probe resistor and the input resistance of the voltmeter and the latter value is different for each instrument. In VTVM's the input resistance for DC voltage measurements remains fixed for every setting of the range control. In VOM's this resistance will change with each range setting and is arrived at by multiplying the ohms-per-volt value of the instrument and the highest value of the range in question. For example, if a 20,000 ohms/volt VOM is set to its 5,000-volt range, the input resistance of the VOM is $5,000 \times 20,000$ or 100 meg.

Some probe manufacturers have available a variety of different probe

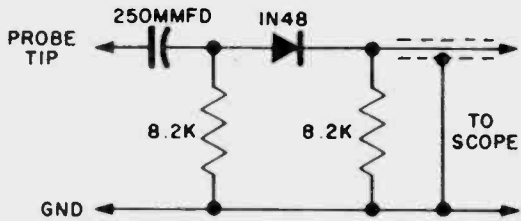


Fig. 3. RF detector probe enables scope to display signal modulation.

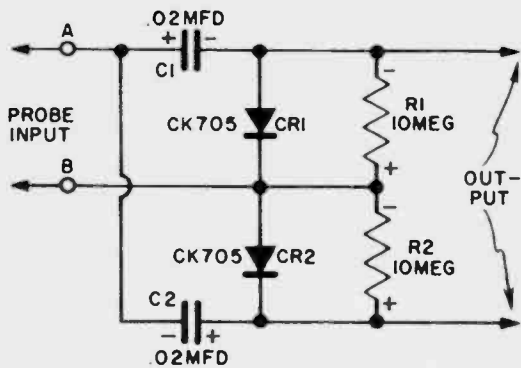


Fig. 4. Peak-to-peak RF probe uses 2 diodes to double its output voltage.

Probe with tiny vacuum tube rectifier permits high accuracy measurement.





Fig. 5. Use of 'scope without low-capacity probe produces distortion of square waves.

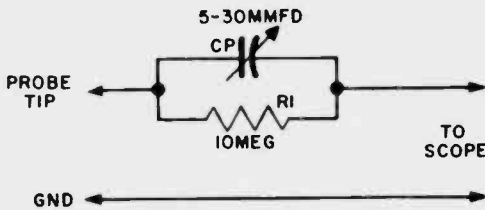


Fig. 6. Capacitor CP in low-capacity probe trims probe for best square wave response.

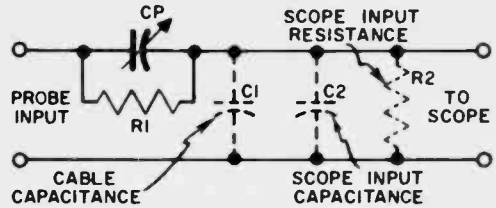


Fig. 7. Equivalent circuit (described in text) of low capacity probe, cable and 'scope input.

resistors, so that a number of VOM's and VTVM's can be matched. In the case of a VOM, only those with movements of 20,000 ohms/volt or higher are suitable for such probes. Movements with lower ohms/volt values require too much current which, if drawn from most high-voltage sources, would cause the voltage to drop.

It is quite simple to determine what value the probe resistor should be for any given VOM or VTVM. In the case of a VOM, it is necessary to know what scale will be used during the high-voltage measurements. Let us assume that the 5,000-volt scale is to be employed on a 20,000 ohms/volt VOM. We desire to be able to measure a maximum of 50,000 volts; this requires a scale factor of 10.

Formula to compute probe resistor is:

$$R_{\text{probe}} = M (R_{\text{input}}) - (R_{\text{input}})$$

where:

R_{probe} = resistance of probe

M = scale factor

R_{input} = input resistance of VOM on scale designated.

For example given,

$$\begin{aligned} R_{\text{probe}} &= 10 (20,000 \times 5,000) - \\ &\quad (20,000 \times 5,000) \\ &= 900 \text{ megohms.} \end{aligned}$$


To find the probe resistor for a VTVM, the formula is modified slightly because VTVM's use a probe for normal DC voltages which contain a 1-meg resistor in it. This resistor is taken into account when the scales are calibrated and it *must* be considered when the resistance of the high-voltage probe is being computed.

To illustrate, assume a VTVM has an input impedance of 10 megohms and its regular DC probe has a resistor of 1 megohm. A scale factor of 100 is desired so that the probe may be used to measure up to 50,000 volts on the 500-volt scale. The equation now becomes:

$$\begin{aligned} R_{\text{probe}} &= M (R_{\text{input}}) - (R_{\text{input}} - R_{\text{cable}}) \\ &= 100 (10,000,000) - \\ &\quad (10,000,000 - 1,000,000) \\ &= 991 \text{ megohms.} \end{aligned}$$

[Continued on page 110]

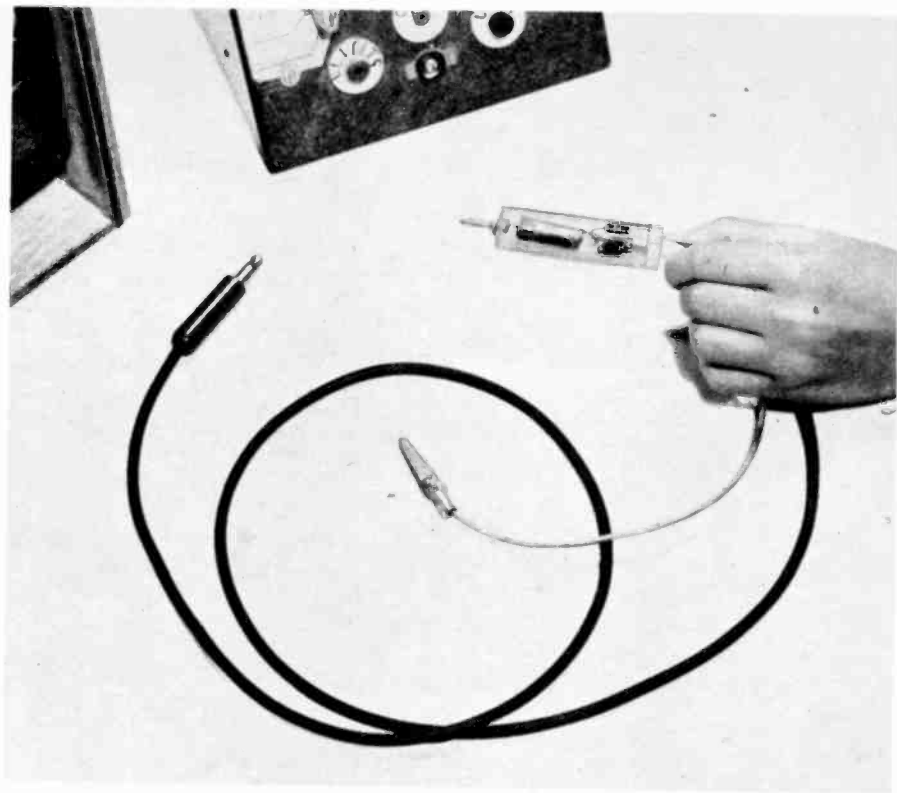Probe built into a small plastic bottle. Phone plug goes to meter, alligator clip to equipment ground.



Make Your Own Probes

By Joe W. Rocke

For use with meter or 'scope, these three probes feature inexpensive parts and simple circuits.

CRYSTAL probes are to test instruments as solder is to a soldering iron; the two just naturally go together. The versatility of the probe makes it an indispensable tool for both circuit design and troubleshooting.

The spare parts box will usually yield the materials necessary to construct a probe. Aside from the germanium crystal the balance of the parts is not critical. Resistors and capacitors rated within 20% of the values shown are acceptable.


The crystal in the probe serves primarily as a rectifier. The 1N34 crystal, or its equivalent, will do for most probes. However, if the probe is to be used where high AC or RF voltages are likely to be encountered it is advisable to use a crystal having a higher voltage rating.

A container for the probe is where you find it. If you have a rich uncle who smokes El Ropo cigars packaged in capped aluminum tubes you have a made-to-order container. I used plastic.



Shielded cable must be used for the probe lead to shield against effects of body capacity and hum pickup. The crystal end of the probe does not ordinarily require close shielding unless the probe is to be used for VHF work.

Construction of the probe is



[Continued on page 106]

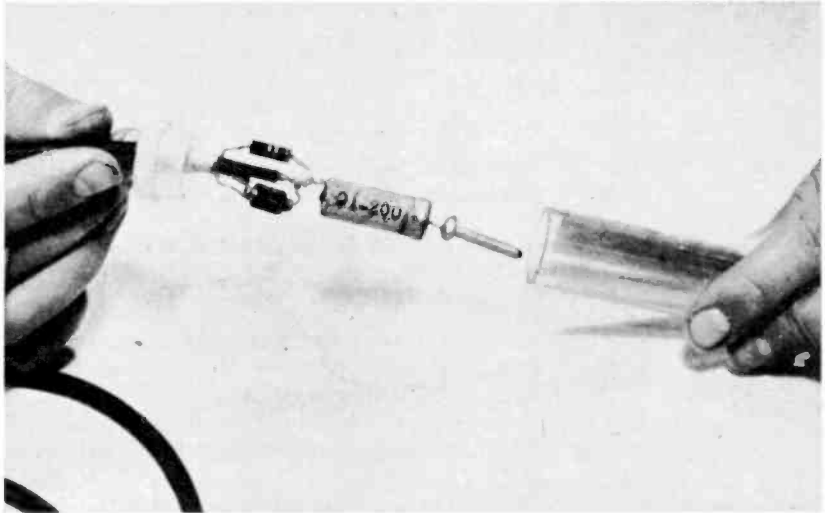

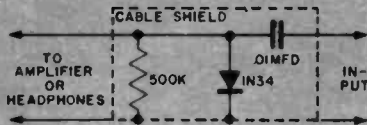
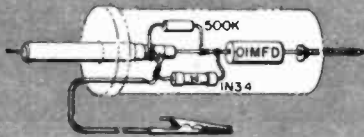
Wire probe as compactly as possible since parts are supported by their pig-tails. Pointed screw is test prod which also serves to fasten assembly to case.



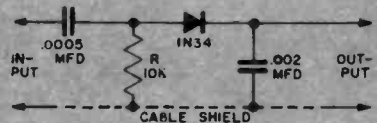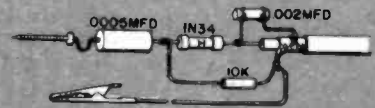Signal tracing probe, used on an amplifier, will deliver audio to headphones. Demodulates RF, too.



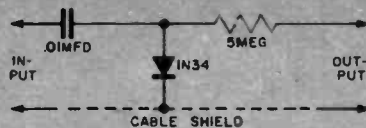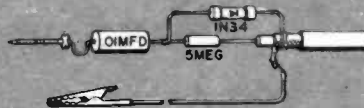Probe for use with VOM of at least 5000 ohms-per-volt. Will indicate RF on a 50 or 100 microammeter.



VTVM probe measures RF voltage in circuits that are easily disturbed by lower input resistance of VOM.

E I reports on the

C


Long available in a factory-wired version, this sensitive VTVM is now being offered in kit form.

THE Voltohmyst, in kit form, marked the entry of RCA into the kit field. It closely resembles the "Junior" model of RCA's series of meters that include the Senior and Master Voltohmyst.

Thus, another VTVM, a most valuable piece of basic test equipment is available to the hobbyist or serviceman—at considerable saving. Wired at the factory the cost is \$49.95, while kit price is \$29.95.

The WV-77E(K) employs vacuum-tube voltmeter circuitry. On its DC ranges the input sensitivity is 11 megohms. This simply means that most circuits under test will be little affected by the voltmeter. Very high resistances, too, are measurable (up to 1000 megohms).


[Continued on page 124]

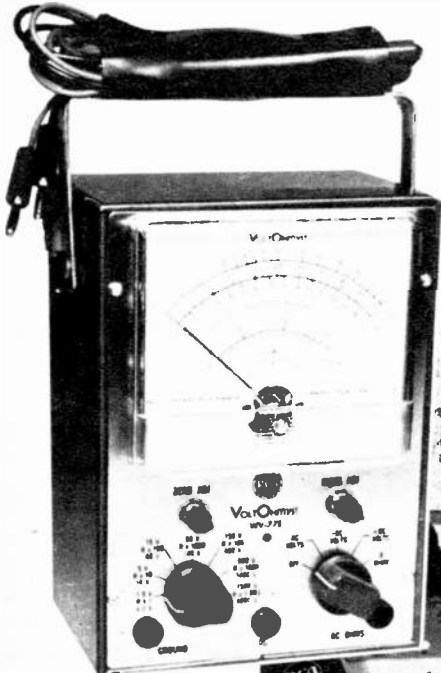


Front view of the completed WV-77E(K) is at left. A leatherette pouch, snapped onto the carrying handle, is a convenient place for probes.

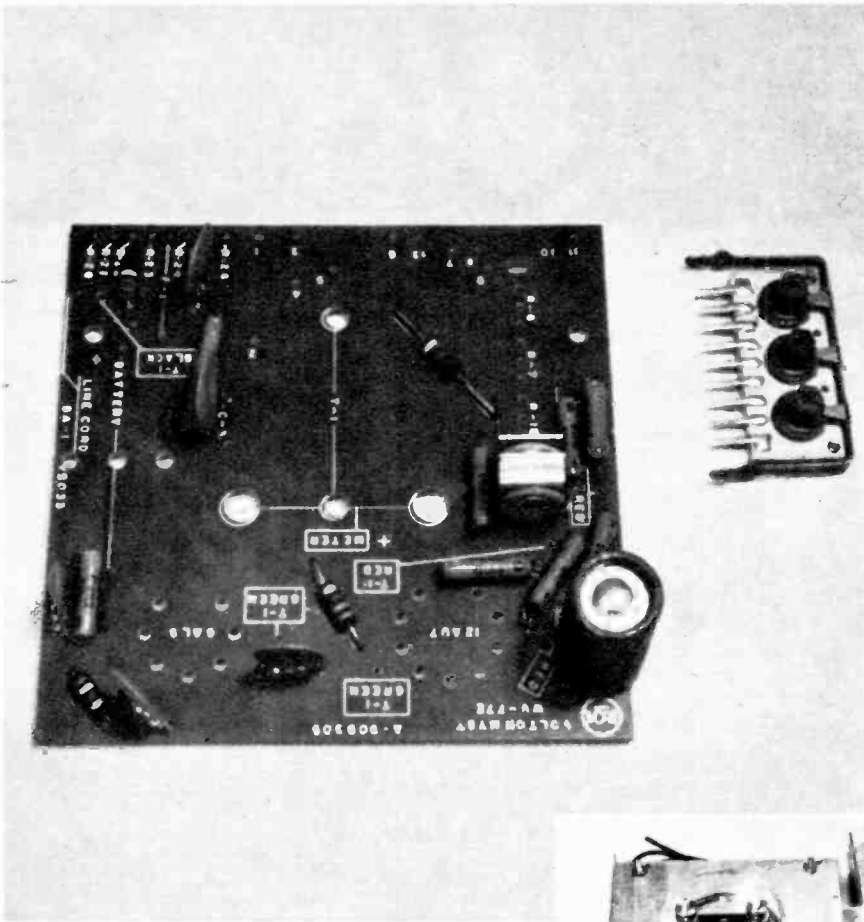Layout of parts included in the kit. Assembly instructions near the top are on a single sheet. Additional information is in booklets below.






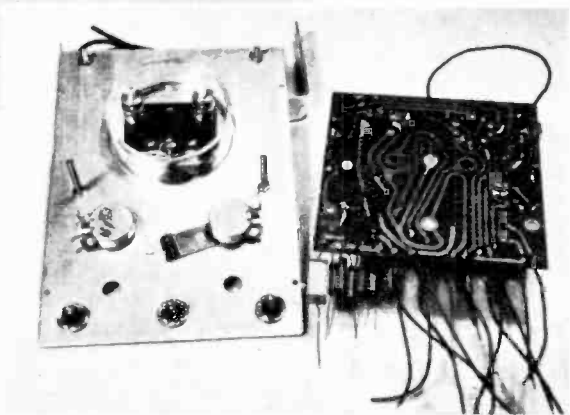Note the three calibrating pots to right of board. They are plugged into board and soldered to it as a single unit.



Underside of printed board ready to be joined to rear of front panel. Wires protruding from it will go to switches.

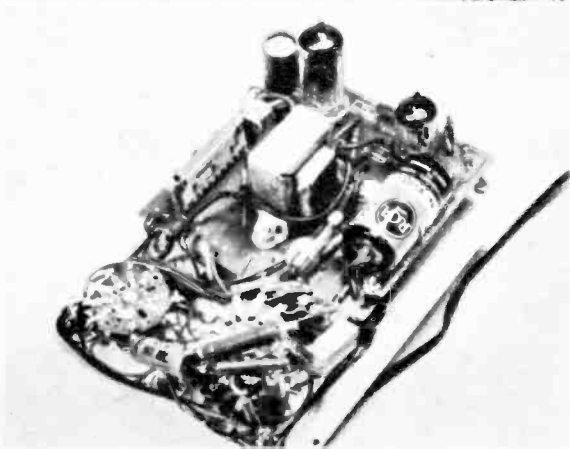View of component side of printed board, after attachment to front panel. Two selector switches are along the bottom.





A self-contained net control station on wheels is operated by the Winston-Salem (N.C.) Amateur Radio Club in cooperation with the county's Civil Defense organization. Beam antennas are easily collapsed.

All About Ham Nets

By George Hart, WINJM

Yes, there's a place for organized "rag chewing," but the byword of most ham nets is "service."

ALL over the amateur radio bands you can hear them—between 500 and 1,000 groups of operators calling themselves "nets." You might hear, for example, one station say: "Old man, you're interfering with the Podunk Net. Wonder if you'd mind standing by or moving to another frequency so we can clear our traffic."

The offending station may or may not move. He doesn't have to. A ham can operate anywhere in any amateur band (providing he has a Conditional Class license or better), and he has as much right to a particular frequency as the Podunk Net. Usually he will move since amateurs are courteous.

Young Julius Madey, K2KGJ, typifies unselfish ham radio operators all over the country. He has won an award for handling thousands of messages from servicemen in Antarctica.




L. A. Peek, W7BA, of Seattle, devotes much of his spare time and radio skill to the handling of traffic from military men stationed overseas. These messages are delivered gratis.



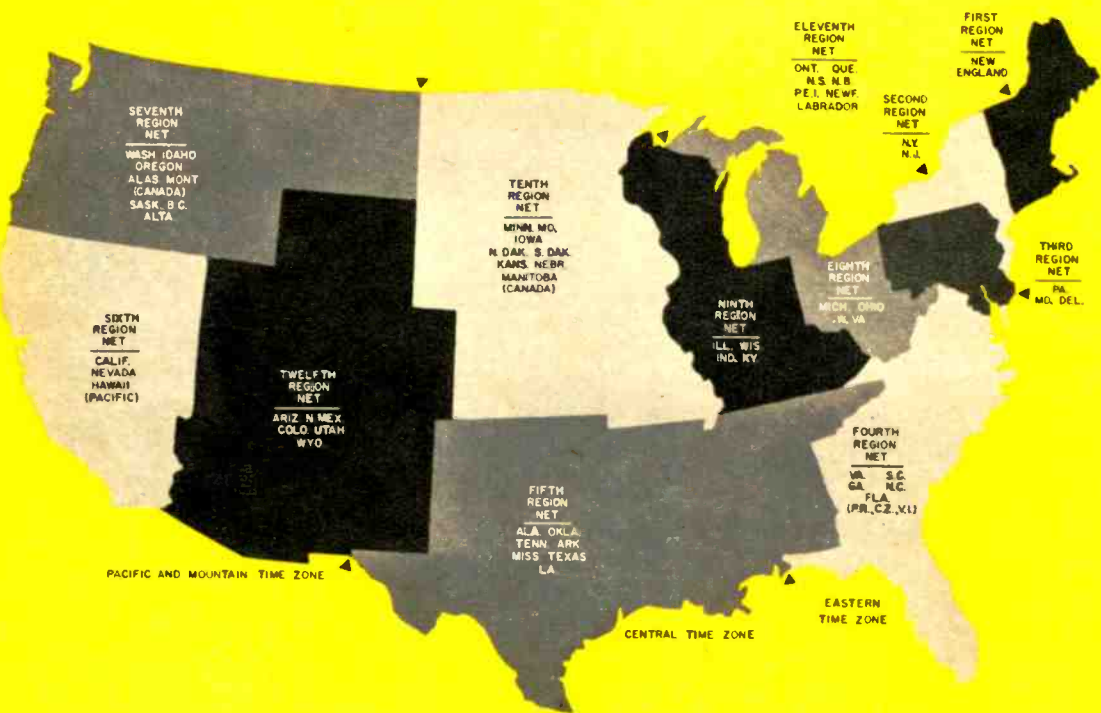At the other end of the line, personnel on Operation Deep Freeze get the chance to talk with families back in the United States via ham phone patches. Beards keep out severe cold.





The National Traffic System is composed of over 100 amateur nets arranged so that messages can be handled in a minimum of time. State nets feed regional nets which feed area nets that are divided roughly into time zones.

Training of emergency network operators is a big job. Here volunteers check out for field stations with Civil Defense handie-talkies over their shoulders. This drill, being held in New York City, is one of several held each year.

Photo courtesy N. Y. City Civil Defense



What Are Nets?

When a group of amateurs all get on the same frequency and one station at a time transmits while the rest listen, we have a "round table." Usually they just take turns and each, in turn, talks about anything or about nothing. When one of the stations assumes charge and tells the others *when* to transmit and to whom, this station is called the "net control station" and the whole group operating in this fashion becomes a "net," or network. Sound regimented? It is, to a certain extent, although no one has to be in the net if he doesn't want to be.

Nets operate for a number of reasons such as preparing to provide emergency communications, or handling traffic (third party messages). There are training nets, such as those attempting to build up code speed. Some nets involve special interest groups within or outside the field of radio, such as doctors, dentists, teenagers, YLs (young ladies), or fraternal organizations. And some of them operate just for the good old fun of yakking together.

General Electric photos

Both men and women are coached in Morse code proficiency and network procedure on a voluntary basis. This group is from California.

Some nets include only amateurs in a particular city or radio club, some extend through county or state, and some even spread from coast to coast and beyond!


Depending on what it does, what it is for and who is in it, a net might operate by voice ('phone), Morse code (CW) or radioteletype (RTTY). Amateur TV nets are also on the horizon. CW nets may be slow, medium or high speed, depending upon the proficiency level of the net members.

How can you identify a net when you hear one? Almost without exception they begin with a "call up." The net control station comes on at a prearranged time with a general call to all net members, something like this:


"Calling the Podunk Net, calling the Podunk Net, this is K2ABC, net control station. The Podunk Net operates daily on this frequency starting at 7:30 P.M., Central Standard Time, for the purpose of emergency communication in the Podunk area. Amateur stations operating on or near this frequency are re-

[Continued on page 122]

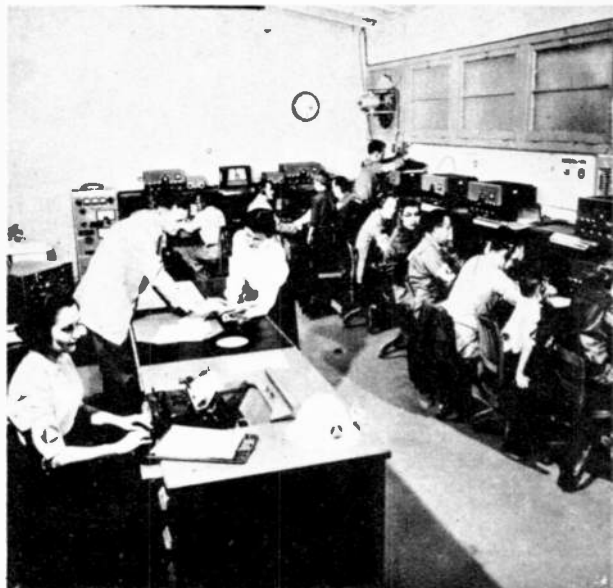Net control center on West Coast holds drill. Your life may one day depend on these hams. Boy, right, is licensed General class operator.




Try These

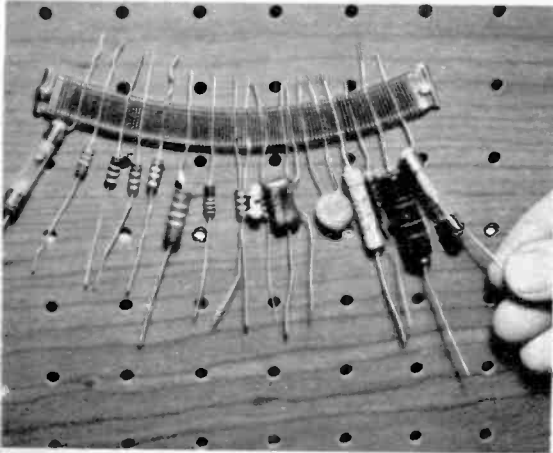

Watchband Parts Rack

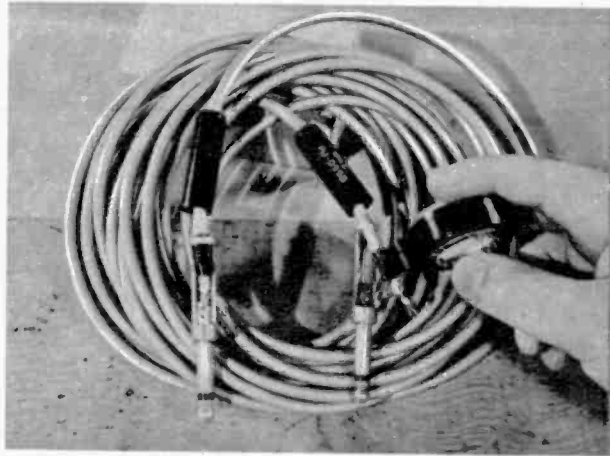An old spring-type expansion watchband can serve as a parts rack. Screw its two ends to your workbench or board.




Tape Cushion

Repeated movement of center wire in phone jack causes break. Wrap with plastic electrical tape for tight fit.

Wire Stripper

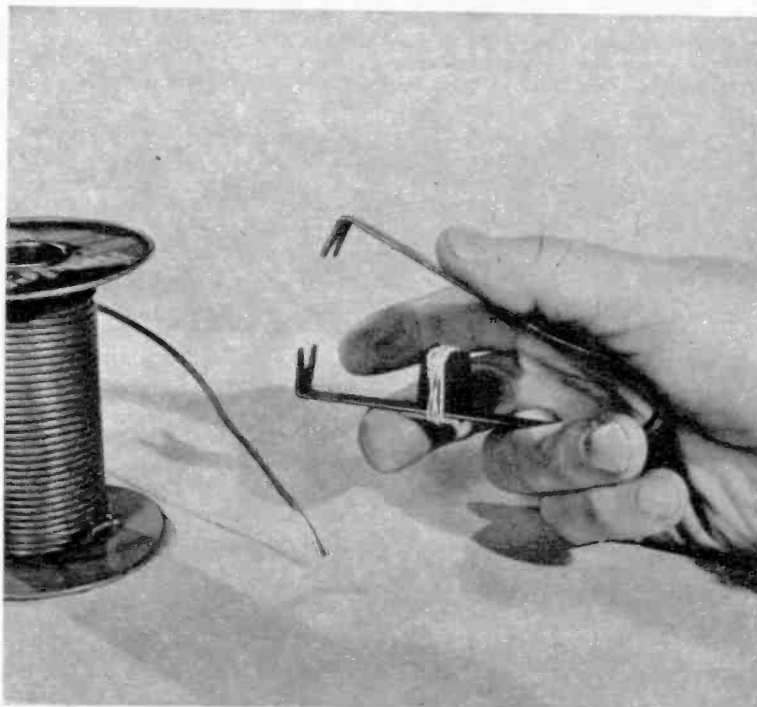To prevent stripper from cutting wire, mount block (from a rubber heel), between jaws. Square of cardboard under rubber band permits sliding adjustment for jaws.




how to design and build **Power Supplies**

By Harvey Pollack

Three of the most-often requested supplies are detailed here: for transistor sets, tube portables and auto radios—you can use them all on the AC line.


IN its broadest sense, a power supply is a device that converts one form of available electric power into another form needed to operate a given device. For example, when the batteries in your portable radio wear out and you want to use it directly from the AC lines in your home, you need a power supply of a very special kind. It must be able to convert the 117 volt, 60 cycle AC into two kinds of pure DC: (a) 1.5 volts for the filaments of the portable radio tubes and (b) 45 to 90 volts for the plates and screens of the same tubes. Or suppose you have just bought a new car that came equipped with a 12-volt radio. What do you do with the perfectly fine 6-volt receiver from your old car? If you would like it as a spare radio at home, you need a power supply that will provide 6.3 volts at 4 to 8 amperes—again direct current—from the 60 cycle lines. Perhaps you now own a transistor radio that you want to use as bedside receiver without wasting its batteries. For this you would have to construct a power supply that can provide anything from 6 to 12 volts of ripple-free DC at currents that may range from 10 ma up to 50 ma or more depending upon the radio. There are literally dozens of other special applications that require power supplies of more or less unique conception. Since relatively few fundamental principles are involved, there is no reason why you cannot build any type you want once you have developed little more than a passing acquaintance with these principles.

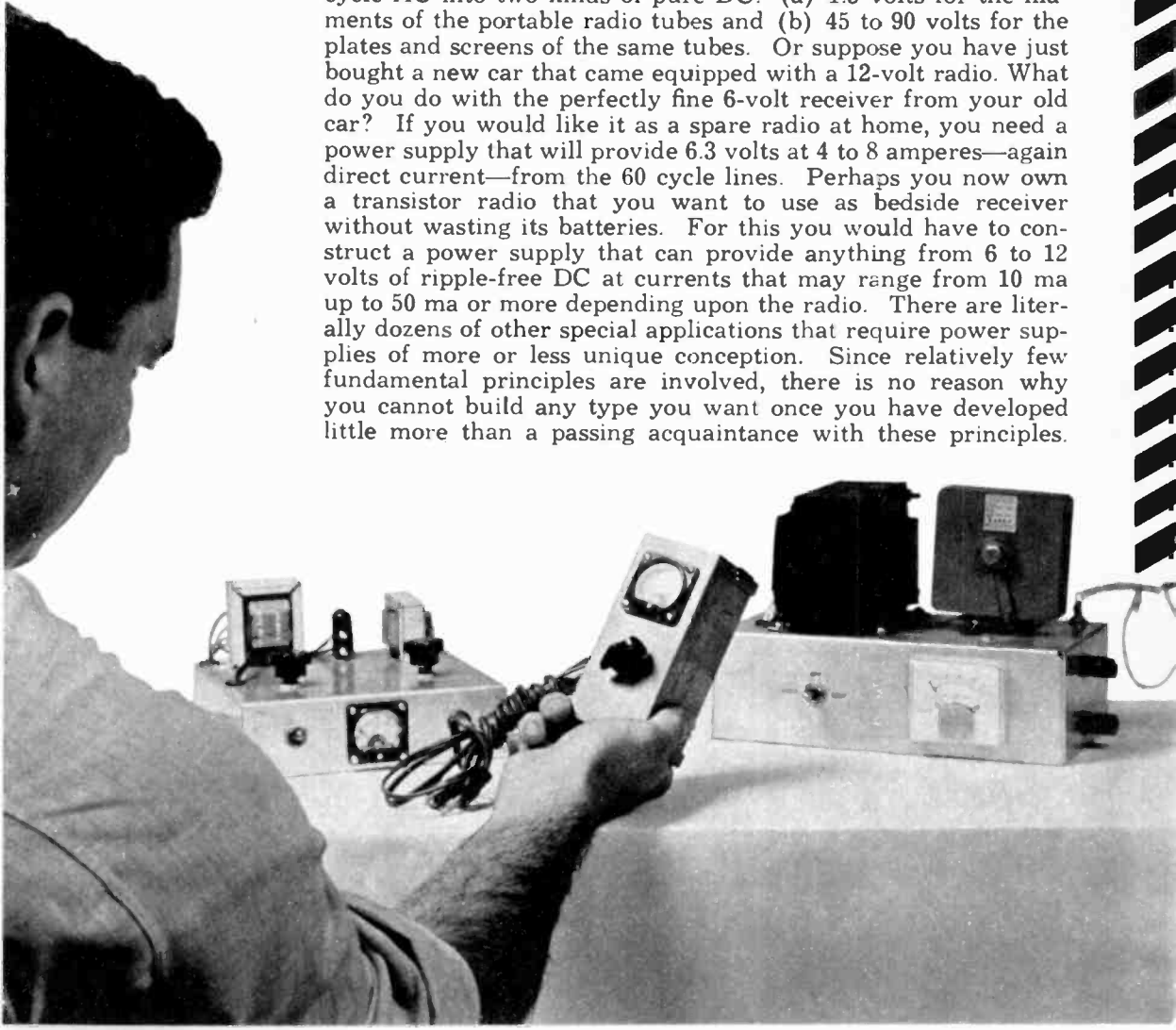

Classification of Power Supplies

Power supplies may be classified in terms of (a) type of coupling to the AC line, (b) the kind of circuit employed, (c) the nature of the filter or smoothing network, and (d) the kind of rectifier used.

Fig. 1

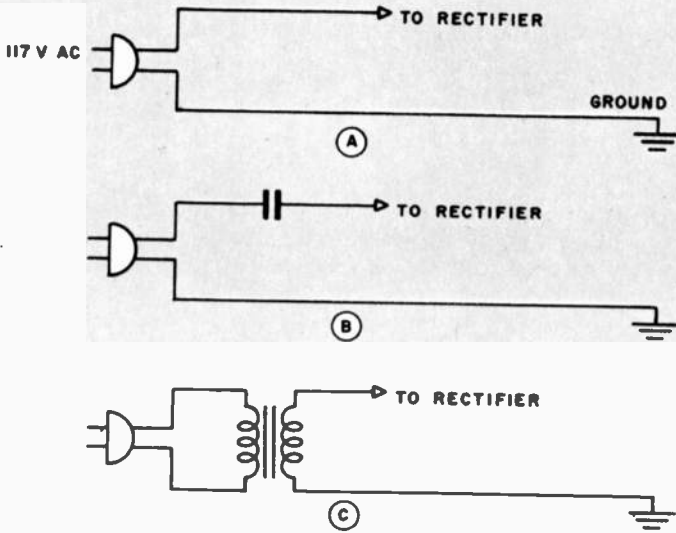


Line coupling: Three types of line coupling methods are in common use: (1) direct connection to the AC lines without any form of isolation (Figure 1A); (2) capacitor isolation in the "hot" leg of the AC line connection (Figure 1B); and (3) transformer isolation (Figure 1C).

Of the three methods, transformer coupling offers several important advantages. Voltages may be stepped up or down by selecting a transformer with the proper turns ratio; in

addition, a transformer completely isolates the power supply from the AC line thus reducing the hazard of electrical shock to the user. Although a transformer supply is the safest and most versatile of all, it does increase the cost, bulk and weight of the completed assembly.

Fig. 2

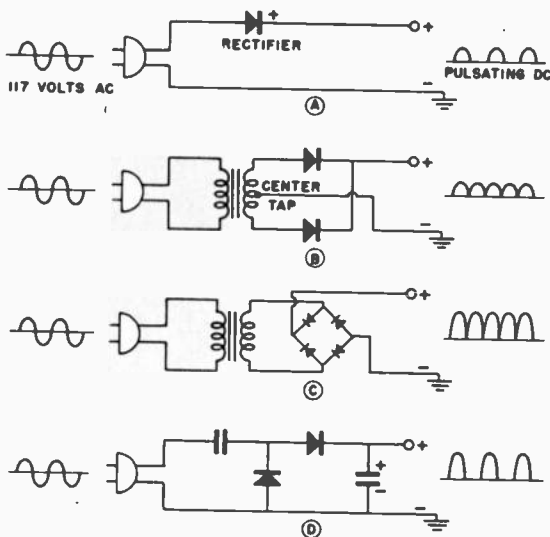

Circuit: Power supply circuits may be simple half-wave, full-wave, bridge or multiplier arrangements. In the half-wave circuit, only one-half of the available AC cycle is used (Figure 2A). This kind of power supply may be made inexpensive and compact, but does require larger filter components to reduce the residual ripple to an acceptable value.


By utilizing a center-tapped transformer and an additional rectifier sec-

tion, the entire AC cycle is put to use. It is much easier to minimize hum voltages (ripple) in a full-wave system than in a half-wave type, but the cost and bulk are generally greater. (Figure 2B).

The bridge circuit (Figure 2C) eliminates the need for center-tapping of the transformer and makes the output voltage *twice* that of a full-wave circuit using the same transformer. A bridge requires 4 rectifier sections, however, in contrast to the 2 sections needed with full-wave center-tapped rectification.

Multiplier circuits are generally voltage-doublers but may be arranged to triple or quadruple the line voltage. This is an inexpensive way to obtain high voltages without recourse to step-up transformers but is satisfactory only when the current demanded by the load is relatively small. (Figure 2D). This particular voltage doubler circuit is one of the most common in modern equipment; it is a half-wave type with one leg of the input line forming a "common ground."

Fig. 3

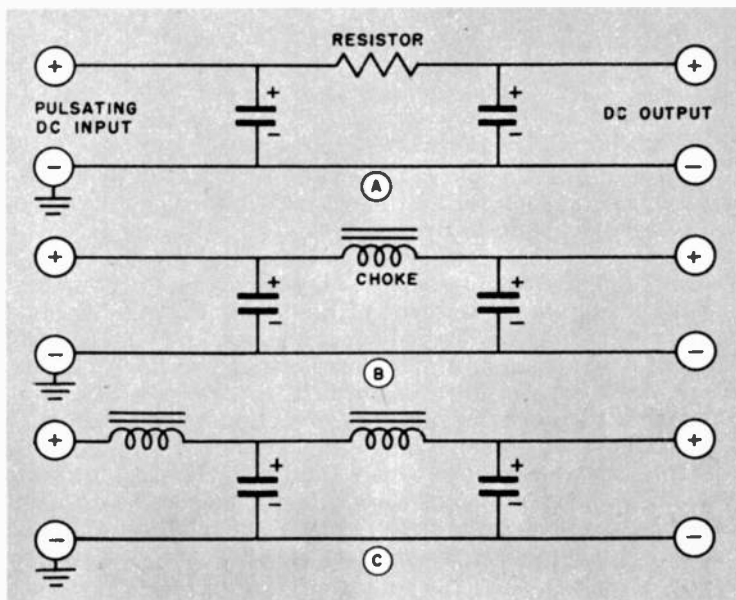

Filter Network: Smoothing components take the form of capacitors, resistors and chokes in various combinations. For our purposes, we may limit the filter networks to three types.

An R-C (resistor-capacitor) filter usually consists of two capacitors separated by a resistor as shown in Figure 3A. Since the first component that is encountered after the rectifier is a capacitor, this arrangement is called *capacitor-input*. Capacitor-input filters are utilized when the

highest possible DC voltage is desired from a given AC input voltage.

A superior arrangement of capacitor-input is illustrated in Figure 3B. In this case, an inductor or *choke* replaces the filter resistor. Such a circuit is capable of better smoothing action, more constant output voltage under varying loads, and higher over-all voltage than that of Figure 3A. Its disadvantages include higher cost and greater bulk and weight.

When very constant voltage output and extremely low ripple is specified, a choke is generally used ahead of the first capacitor to make up what is called a *choke-input* filter network (Figure 3C). Obviously, a supply of this kind would be used only in costly equipment where weight and volume are not important.

Rectifier: Rectifiers are grouped as vacuum tubes, gas-filled tubes, or semi-conductors.

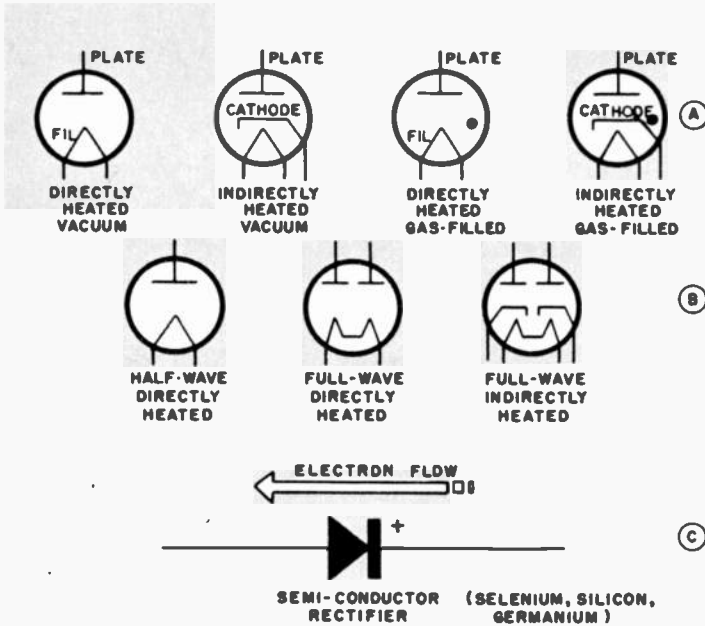


Fig. 4

Small power supplies equipped with rectifier tubes employ the vacuum type for the most part. Gas-filled tubes are found in supplies where the voltage and current requirements are higher than those normally anticipated in receiving and low-power transmitting equipment. In schematic form, the gas-filled rectifier is distinguished from the vacuum type by a black dot within the circle representing the tube's glass envelope (Figure 4A).

A rectifier tube containing a single

plate (or anode) is used for half-wave rectification; one containing two plates is applied in full-wave circuits. (Figure 4B).

The semi-conductor rectifier—such as selenium and silicon units—has gained substantial popularity in the past few years. These have the great advantages of not requiring any filament power nor warm-up time. The only disadvantage they have is that they permit a small amount of reverse current to flow whereas tubes are virtually perfect insulators in the reverse direction. Improvements in recent rectifier construction techniques have made this disadvantage insignificant, however. The semi-conductor rectifier is shown schematically in Figure 4C. It is important to correlate the diagram with the direction of electron flow as illustrated. Note that electrons flow from the "flat" section of the schematic symbol toward the "point," leaving the flat portion positive.

Voltage and Current Considerations

In planning to design and build a power supply, you must take into account four fundamental electrical considerations, aside from the size, shape and cost of the finished product. You must first know the *final output voltage* required for the device you want to operate; whether or not you will get this depends not only upon the internal construction and selection of parts for the power supply, but also upon the *current your load will need at the specified voltage*. In addition, you should know beforehand what the *maximum allowable ripple voltage* can be without causing objectionable hum. Finally, you must consider a factor called *voltage regulation*, or ability of the power supply to maintain a constant output voltage despite fluctuations in the load current. We are particularly interested in the first two considerations and only incidentally concerned with the last two for reasons that will

resistor R1 in Figure 5. An input capacitor (C1) charges up to the *peak* line voltage from the transformer secondary. Since this transformer has an effective rating of 240 volts, the potential across C1 at no load is approximately 240×1.4 or about 340 volts. Since we want 240 volts output, there will be a voltage drop of 100 volts in R1. At the rated current of 55 ma, we find the value of R1 by substituting in Ohm's Law as follows:

$$R = \frac{E}{I} = \frac{100}{.055} = 1800 \text{ ohms (approximately)}$$

and to find the power rating required for this resistor, we use the equation:


$$P = I^2R = (.055)^2 \times 1800 = 5.4 \text{ watts}$$


so that for a nice large safety factor, we could use a 10 watt resistor. The nearest commercial resistor available is a 2000 ohms @ 10 watt type such as the IRC PW-10-2000.

Note resistor R2 shown in broken lines in Figure 5. This resistor is unnecessary if the load is always connected to the power supply and if the current is always 55 ma, a hi-fi amplifier, for example. For situations in which the power supply may be operated without load, or if the drain is less than the rated current, R2 should be inserted. A 25,000 ohm 5 watt resistor in this position will take about 10 ma and serve to improve the voltage regulation as well as to discharge the capacitors should the load be absent.

Using design procedures similar to those just described, three special purpose power supplies are detailed in this article. The first is a tiny unit that will provide from 6 to 15 volts @ 5 to 60 ma for operating virtually any transistor radio; the second is a supply for any portable radio; the third will run a 6 or 12 volt auto radio or mobile citizen's band transceiver and serve as a battery charger.

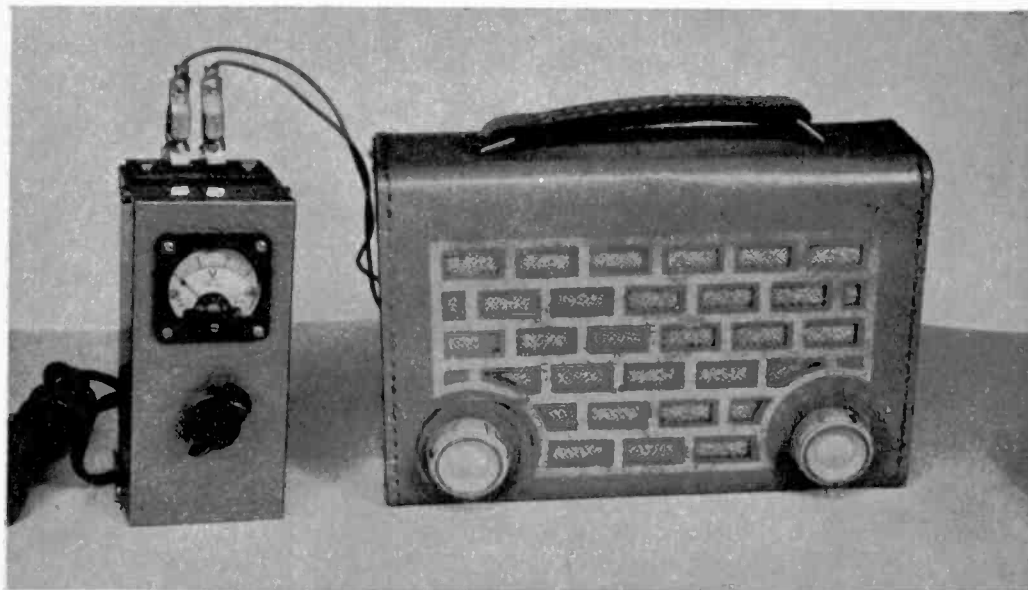Transistor power supply shown in use with a transistor receiver. Pair of leads from the supply connect to the battery clips at rear of the radio.



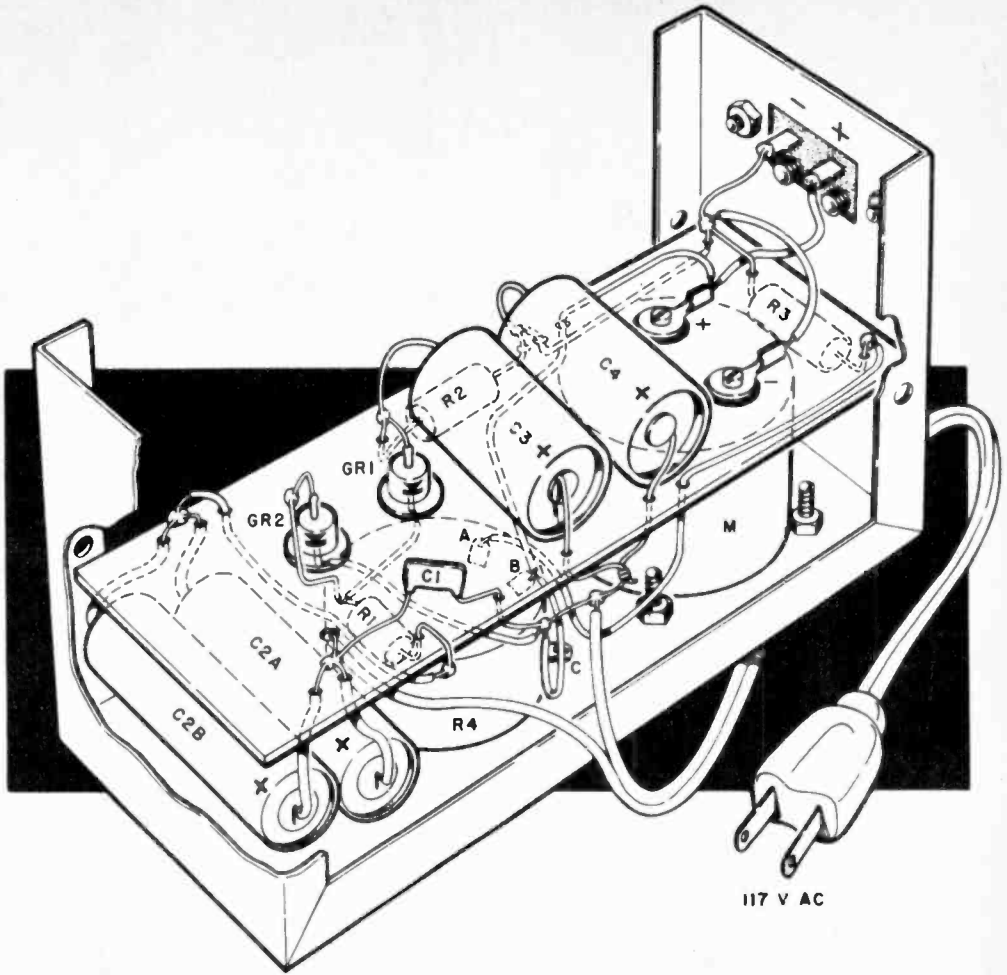

Wiring guide for transistor supply. Be sure that no bare wires touch the metal case. Output terminals at upper right are also insulated from case.


Transistor Radio Power Supply

Classification: (a) Capacitor isolated, (b) half-wave voltage doubler, (c) R-C filter, capacitor-input, (d) two 1N91 rectifiers.


Specifications: Adjustable voltage output, from 6 to 15 volts @ any current from 5 ma to 60 ma. Ripple, approximately 1%.

Construction: This power supply is housed in a miniature cabinet, a 5"x2¼"x2¼" Minibox, equipped with a 0-15 volt voltmeter for precise adjustment of the voltage fed to the transistor radio it operates. If the power supply is to be used for one particular receiver, the meter is unnecessary.

The voltage doubler circuit operates as follows: on one half of the AC input cycle, GR2 passes current so that C2 becomes charged almost to the peak voltage of the AC line. On the next half-cycle, C2 discharges in series with the line voltage through GR1 into the input capacitor C3, charging this capacitor to the sum of the two voltages. Thus, if there were no load drawing current steadily through C2, capacitor C3 could charge up to 300

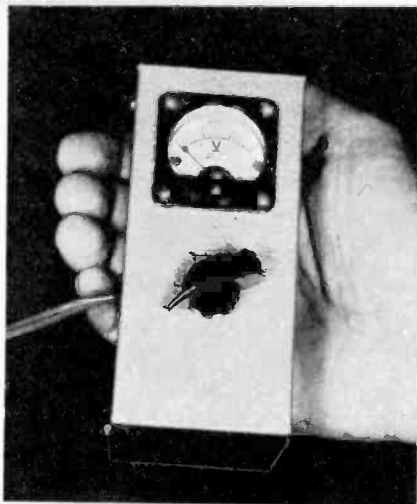


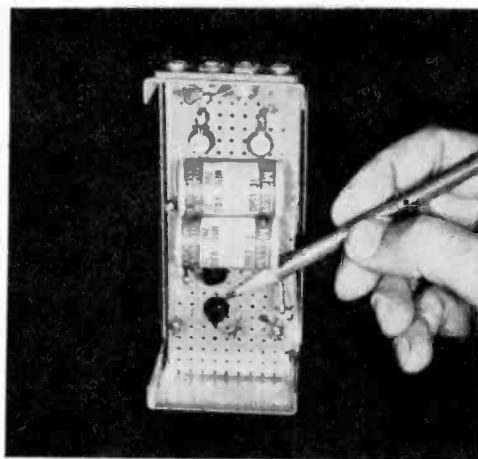Above, voltmeter and voltage control knob are on front panel of supply. AC line cord emerges from left side.



Internal view of the supply is at top right. Pencil points to one of the 1N91 rectifiers mounted on board.

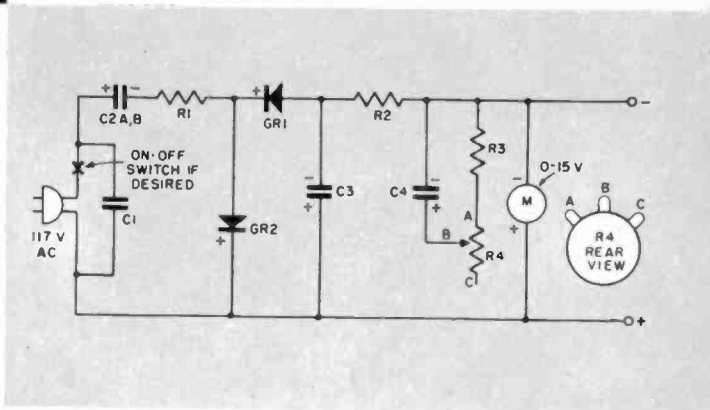Note "X" in left of schematic. It indicates optional use of a SPST switch, not in the author's model.



volts or more! This, of course, would play havoc with a capacitor rated at 15 working volts.

R3 and R4 serve as a variable load, producing a voltage drop across C2 which limits the voltage applied to C3 to a maximum of 15 volts. It is very important that the wiper of R4 be kept at point A while the power supply is not connected to an external load. Should you then turn it on inadvertently without a load, C3 and C4 will be protected against overvoltage. R1 is a surge-protective resistor. Without it, either GR1 or GR2 may burn out if you happen to plug in the power supply at the instant that the AC cycle has reached its peak. C1 is a line filter capacitor whose function it is to by-pass line noises out of the power supply.

A small piece of perforated board supports the small components, the board itself being held in place by the meter terminal screws. Since there is no transformer isolation, *the metal case must not be made the common ground* since this would be inviting a dangerous, if not lethal, shock from the lines.

PARTS LIST

- | | |
|---|---|
| C1—.01 mfd capacitor 300 volt | R4—1000 ohm potentiometer 3 watt wire-wound (IRC WPK-1000 or equiv.) |
| C2A,B—4 mfd electrolytic capacitor 200 volt (use two 2 mfd in parallel) | GR1,GR2—Germanium rectifier (GE type 1N91) |
| C3,C4—200 mfd electrolytic capacitor 15 volt | M—0-15 volt DC meter (Lafayette TM-100) |
| R1—2.7 ohm resistor 1 watt | Misc.—case 5"x2¼"x2¼" (Bud CU-2104), perforated board 4½"x2"x2", one 2-screw terminal strip, line cord. |
| R2,R3—100 ohm resistor 2 watt | |

Portable Radio Power Supply

Classification: (a) Transformer isolated, (b) full-wave circuit, (c) L-C filter, capacitor-input, (d) rectifiers—two selenium rectifiers.


Specifications: "B" voltage supply adjustable from zero to 135 volts at any current from zero to 25 ma; ripple approximately 1%. "A" voltage supply adjustable from zero to 3 volts @ any current from zero to 250 ma; ripple less than 0.5%.

Construction: This should prove to be an extremely popular power supply for our experimentally-minded readers. It is ideally suited for powering any one of the tens of thousands of portable tube-type radios for which the owners no longer care to buy expensive "A" and "B" batteries. As the photos show, a meter is included to make the power supply more versatile but may be omitted once the proper voltage has been established for a given application. Furthermore, with the help of the accompanying graph, the "B" voltage need not be made variable since a small fixed resistor may be substituted for the potentiometer in the high voltage circuit.

The "A" supply section utilizes a magnesium-copper oxide bridge rectifier of inexpensive type to provide full-wave output filtered by a capacitor-input R-C network. A 20 ohm wirewound potentiometer controls the DC output voltage, permitting adjust-

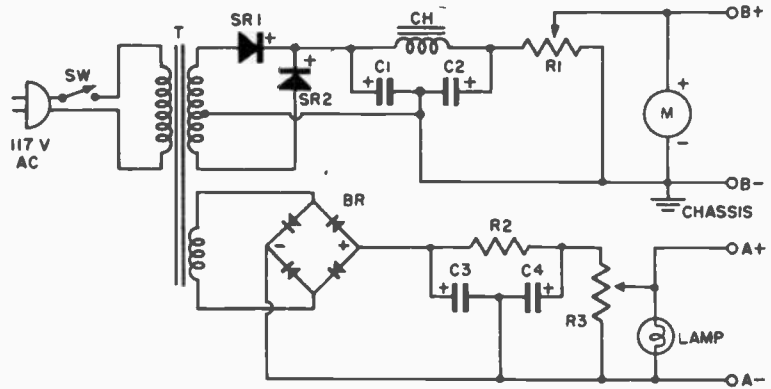
Portable radio power supply shown in use with an old battery radio. The supply replaces both "A" and "B" batteries displayed on top of the radio.





Schematic of portable radio power supply. Lamp at lower right is used in place of a meter in the "A," or filament voltage section.

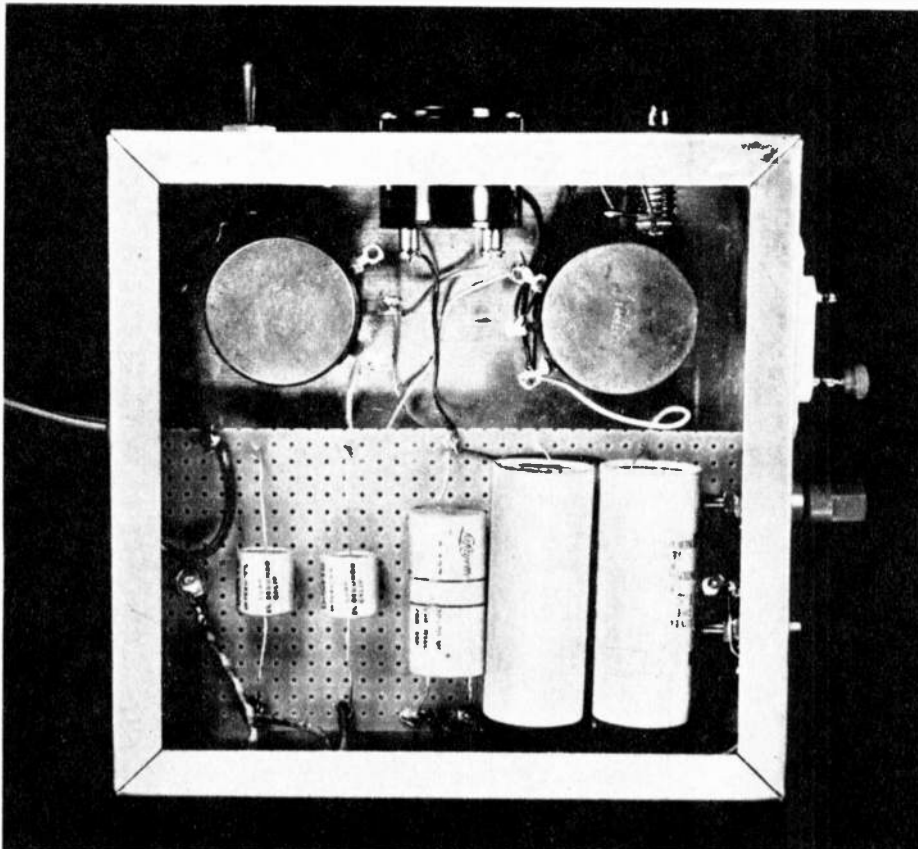Chassis underside. Perforated board, convenient for mounting parts, is supported at both ends by two long nuts and bolts with 1/2" spacers.






ment from zero to 3 volts at currents up to 250 ma. The "A" voltage is metered by a 2 volt pilot lamp (really a low-cost metering device!).

The use of a 6"x3½" piece of G pattern epoxy paper Vectorbord with .093 Vectorbord holes makes this a well-insulated and practical design. (Vectorbord in all sizes, push-in terminals for the .093 holes, and various other fittings are available from Vector Electronic Company, 1100 Flower Street, Glendale 1, California or from their distributors.) The Vectorbord assembly is mounted and pre-wired before securing it to the chassis. It is supported by machine screws passed through a ⅜" brass spacer at each end.

The wiring guide shows the construction of the power supply. Should you want to build the unit for operating one particular

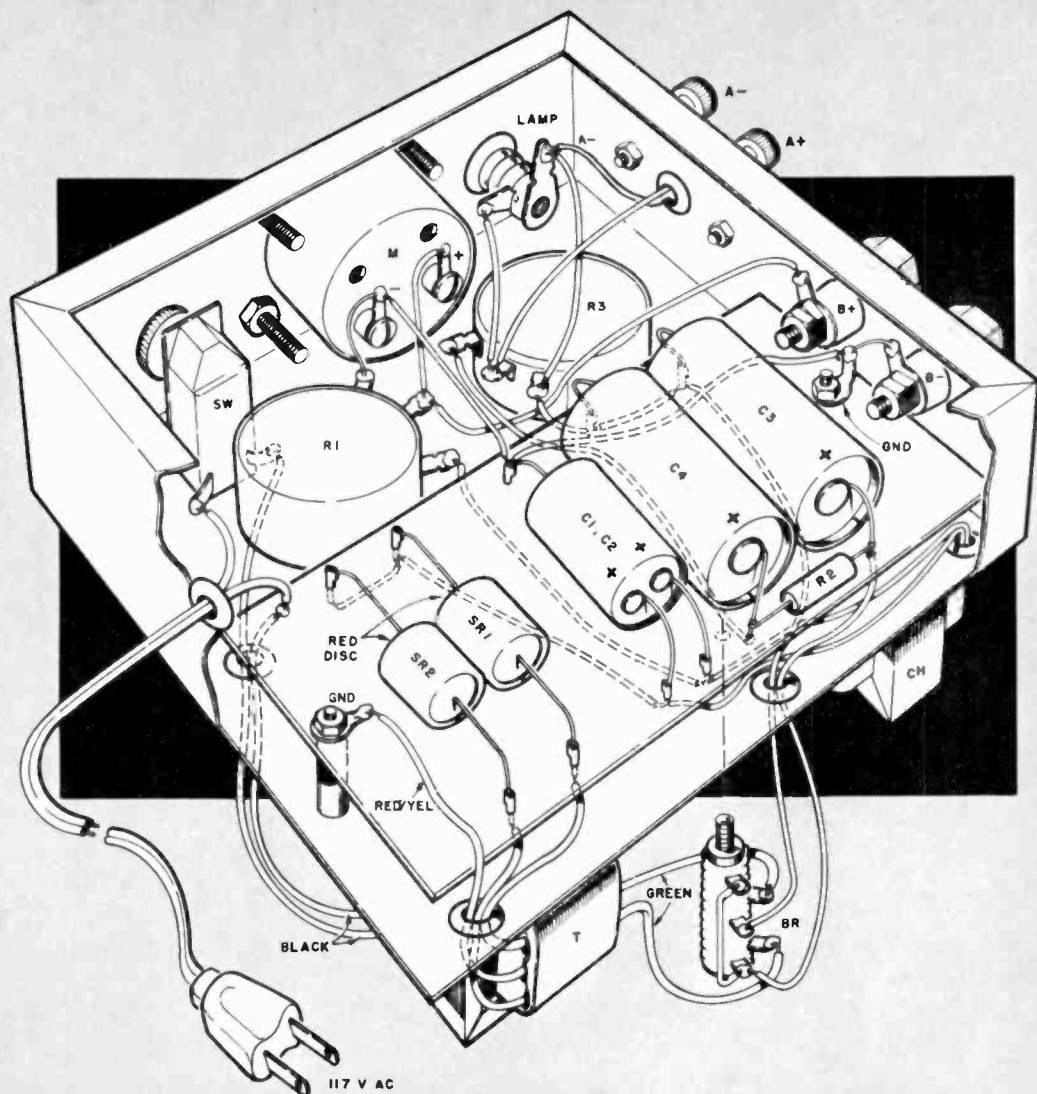Wiring guide for portable radio supply. Follow the pin layout on bridge rectifier BR, removed from main chassis at bottom, for reasons of clarity.



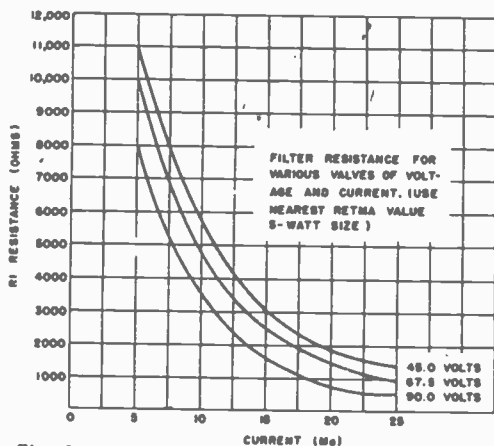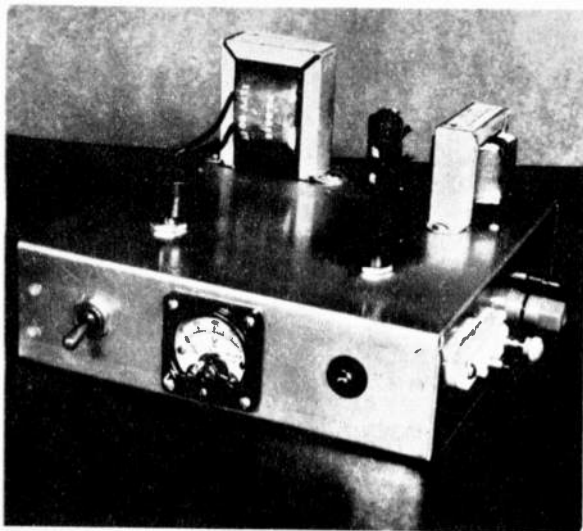

Relative brightness of lamp, to right of meter, indicates filament voltage. See text for explanation of Fig. 6, used for selecting filter resistor.

radio, first determine the voltage required for the "B" circuit and the current that the "B" battery had to deliver in the original application. Then, by using the proper voltage curve in Figure 6, you can determine the correct value of resistor to use for replacing R1, the control potentiometer. This will eliminate two costly items: the meter and the wirewound potentiometer.

Since this power supply is transformer-isolated, the chassis may be used as common ground for the "B" supply. Neither "A" terminal should be grounded to the chassis, however.

If you build the power supply just as shown, the portable radio should be connected as a load to both "A" and "B" sections before applying power. Both potentiometers should be rotated to their zero-voltage positions when the switch is turned on. Now, gradually turn up the "A" control (R3) while you watch the indicator lamp. Since this is 2.0 volt type, it will indicate 1.4 volts when lit almost to full brilliance. With filament voltage adjusted properly, bring up the "B" voltage in accordance with the requirements of the receiver. Some portables were made for 45 volts, others for 67.5 volts, still others for higher voltages. Use the recommended voltage at all times to avoid blowing capacitors and overheating resistors. When used correctly, this power supply will make a portable radio perform as well or better than it did when battery-operated.

PARTS LIST

- | | |
|--|---|
| C1, C2—20-20 mfd electrolytic capacitor (dual-section) 150 volt | S1, S2—Selenium rectifier (Int'l Rectifier type D-5416) |
| C3, C4—2000 mfd electrolytic capacitor 6 volt | SW—SPST toggle switch |
| CH—Filter choke 9 henry @ 50 ma (Stancor C-1215) | T—Power transformer, primary 117 volt, secondaries 6.3 volts @ 1 amp, 250 volt CT @ 25 ma (Stancor P58416) |
| BR—Bridge rectifier Mg-CuS type for low voltage (Mallory 1B12R) | Meter—0-200 volt DC (Lafayette TM-101) |
| R1—10,000 ohm 3 watt wirewound potentiometer. See Fig. 6 (Clarostat Type 58) | Misc.—2-volt pilot lamp (Mazda #49); chassis 7"x7"x2" (Bud AC-405); "B" terminals 5-way Bakelite type (Lafayette "Jumbos"); "A" terminals twin binding posts red and black (Philmore #121); 1/2-inch spacers, perforated board. |
| R2—2.7 ohm resistor 1 watt | |
| R3—20 ohm potentiometer 3 watt wirewound (Clarostat Series 10) | |

Auto-Radio Power Supply and Battery Charger

Classification: (a) Transformer isolated, (b) full-wave bridge circuit, (c) capacitive filter, (d) rectifier—selenium bridge.

Specifications: 6 or 12 volts DC selected by switch; output voltages adjustable for currents ranging from 2 to 4 amperes for continuous use; up to 8 amperes at 6 or 12 volts available for intermittent use.


Construction: This power supply has several unique features. A switch with a neutral center position is used to turn the equipment off by breaking the transformer primary circuit, or to switch to 6 or 12 volt output on either side. A heavy capacitive filter reduces the ripple to approximately 2% to provide hum-free




Auto radio supply in use as a car battery charger. It will supply either 6 or 12 volts.

operation of any auto radio or transceiver designed for mobile use. The use of a costly power potentiometer for fine control of output voltage under various current demands is avoided by means of a very simple expedient: a heating element from an old parabolic electric heater (such elements are available in hardware stores, but you may have an old heater around) is taken apart and sections of the nichrome coil used as a current-limiting resistor in series with the common transformer leg (see R in diagrams). Sections of different lengths ranging from 5 or 6 turns to 15 turns or more may be mounted on banana plugs as in the model, and a shorting clip employed to include as many turns as desired in the circuit. Exact specifications for heater element lengths cannot be given since various elements have different nichrome wire thicknesses. This is very easily determined by

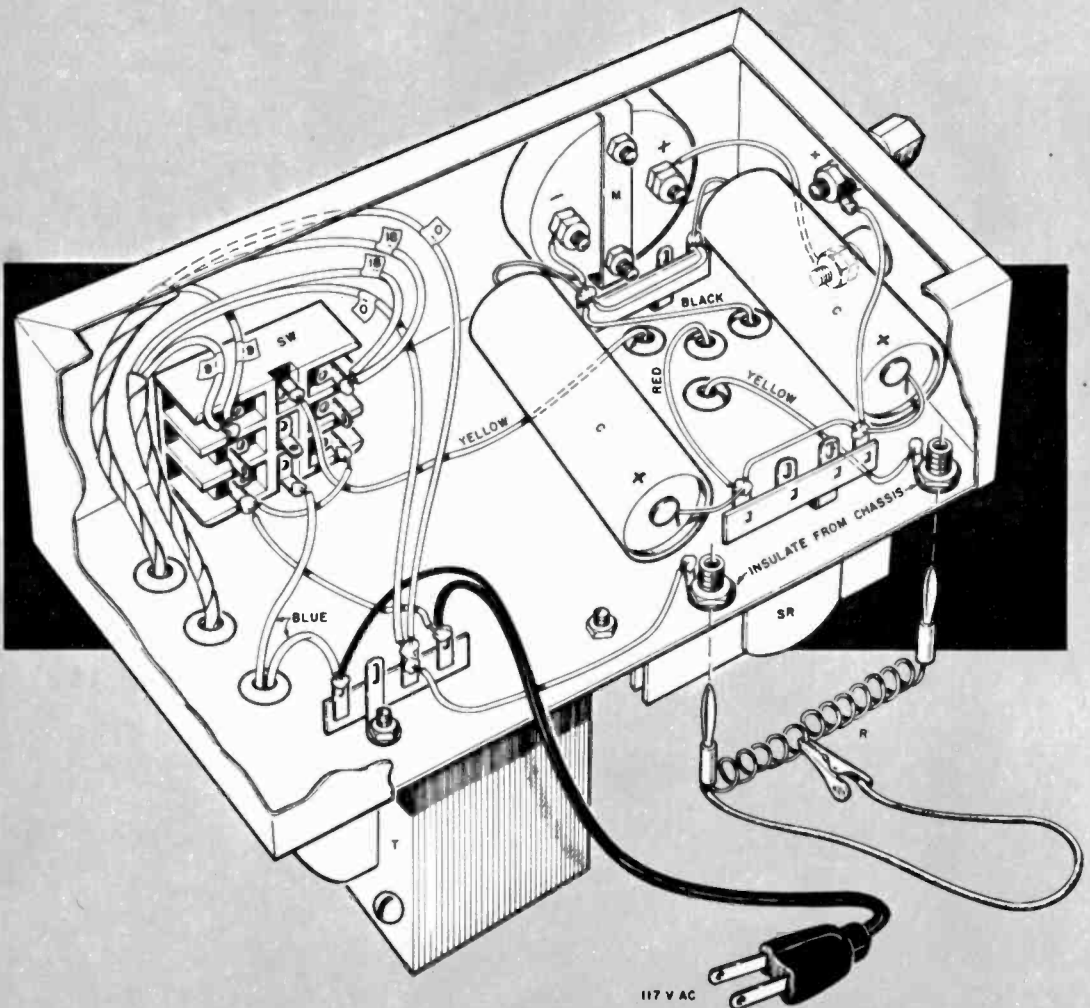Auto supply wiring guide. Resistor R, at lower right, is a length of nichrome wire, used in place of a more expensive rheostat. It adjusts output voltage.



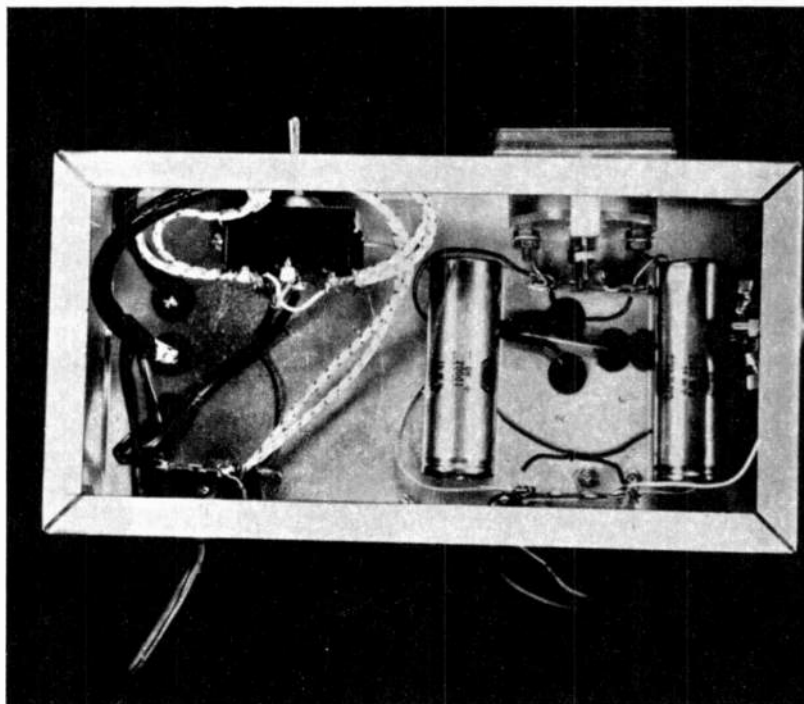


Underside view of auto supply. The two large filter capacitors at right are actually connected in parallel to total the required 4000 mfd (part C).

experiment, however. Of course, if you don't mind spending about \$5.00, you can use a 50 watt power rheostat in place of a plug-in resistance. (For example, an Ohmite Industrial Rheostat, Model 0311, 4 ohms, selling for \$4.53 would serve admirably here.)

A word about the transformer would not be out of place. This transformer has two identical center-tapped secondaries rated at 0-9-18 volts AC each @ 4 amperes per winding. By connecting them in parallel, properly phased, the current output then rises to 8 amperes. The wire leads of this transformer (see parts list) are coded with tape markers showing which is the "0," "9," and "18" volt terminals of the windings, so that phasing is no problem. The selenium rectifier is rated at 4 amperes continuous (or 8 amperes intermittent). Should you want a rectifier of higher current rating for continuous operation of 8 ampere equipment, these are also available at the same distributor given in the parts list.

In this case again, it is suggested that the chassis *not* be made the common ground. Should you want to charge a battery right in your car, it is best if the chassis is neither positive nor negative just in case your car has a positive ground. In charging a battery, the positive terminal of the power supply goes to the + terminal of the battery and, of course, negative to negative. A 4-ampere charging rate is more than enough for an overnight charge.

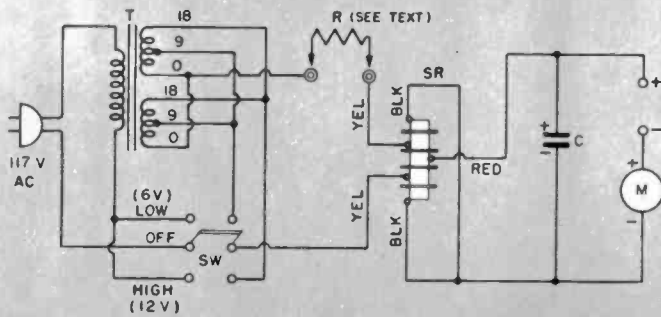A few precautions relative to construction and use of this power supply: (1) mount the selenium rectifier above the chassis in a vertical position as shown in the photos. This permits convection of air needed for maintaining proper operating tempera-





R in the schematic at left is the nichrome wire. Note windings on secondary of T are in parallel.

Below left, supply is used to power a Citizens Radio set that's originally designed for mobile use.

Top view of supply. Output is adjusted by alligator clip which shorts out turns of nichrome wire.

Fig. 7

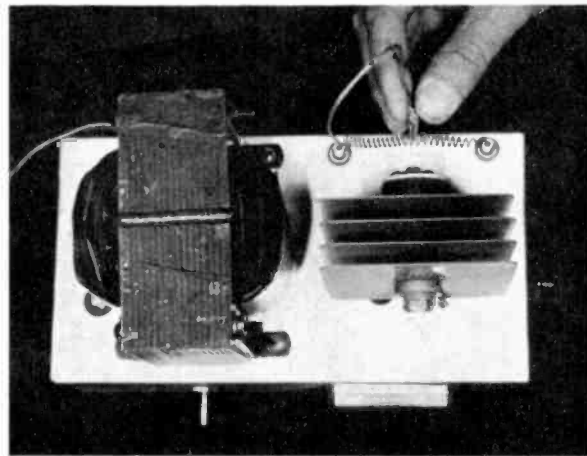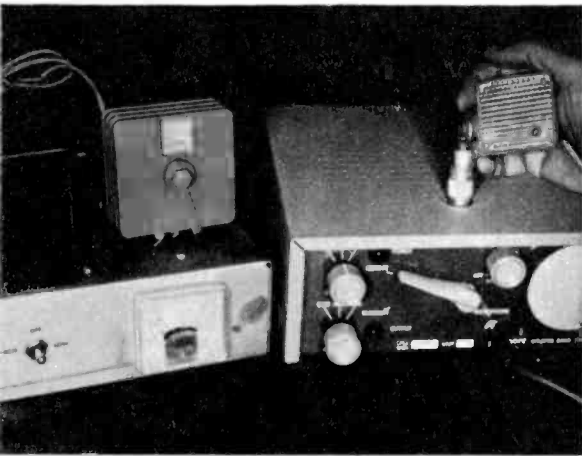

ture; (2) always connect the load before applying power; (3) never run the supply in excess of the rated continuous current for more than 10 or 15 minutes at a time; (4) if your funds permit, include a meter in the construction. Inexpensive meters such as the one shown are very helpful in keeping the equipment within rating. Going even further, a very useful addition would be a 0-10 volt DC meter connected right across C to meter the output voltage.

The filter capacitor C consists of two 2000 mfd capacitors in parallel; for further reduction of hum (there should be none noticeable), a third capacitor might be added in parallel.

PARTS LIST

- C—Two 2000 mfd electrolytic capacitors 15 volt in parallel
- R—Section of nichrome heater element wire (See text)
- SR—Selenium rectifier 18 volt input, 14 volt output, rated at 4 amps continuous. (Available from Barry Electronics, 512 Broadway, New York, N. Y.)
- SW—DPDT switch, neutral center position, rated at 6 amps 125 volts. (Philmore Mfg. Co., 130-01 Jamaica Ave., Richmond Hill 19, N. Y., type 226A)
- T—Transformer, 117 volt primary with two center-tapped secondaries, 9 volts each side of center tap, connected in parallel as shown. (Available from Barry Electronics Corp., address above.)
- M—0-10 ampere DC meter
- Misc.—5"x9"x3" chassis (Bud AC-421), alligator clip, line cord, two binding posts.



Hydrogen in balloon reacts with air's oxygen to produce enough electricity in plastic cell to spin miniature propeller. GE research staffers look on.

electricity from air...

The Fuel Cell

The life blood of electronics—electricity—is now being concocted directly from gaseous fuels.



Fuel cells, 1008 of them, power new Allis-Chalmers tractor. Propane and oxygen yield 15 kw.


THERE'S a fuel cell in your future. Dozens of scientists and engineers all over the world are racing to perfect this new way—that is also one of the oldest ways—of making electricity.

Within two years, highly efficient fuel cells should be generating the electricity needed in satellites and space probes to

run communication and other electronic equipment.

In five years, electric vehicles such as fork-lift trucks will be powered by fuel cells. About the same time, fuel cells will be

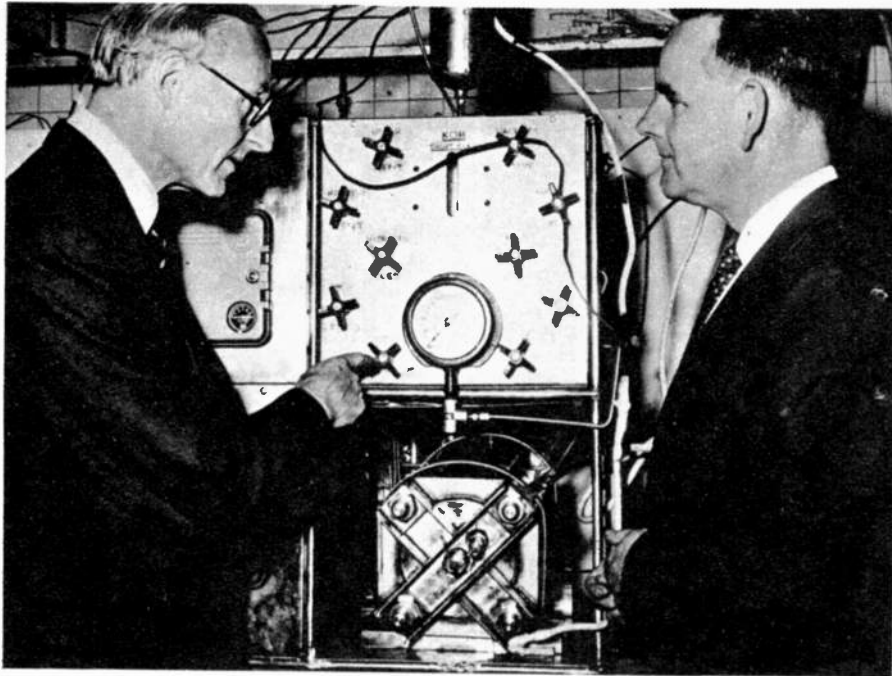English scientist F. T. Bacon, left, and colleague, examine a Hydrox fuel cell. It uses only hydrogen and oxygen to produce electricity without conventional engines or generators. The volatile hydrogen requires a control set-up larger than the fuel cell itself.



available to power remote ranches and unattended radio relay stations.

Will they be used to power autos? The experts believe there is a very strong possibility of this after 1970.

These predictions are substantiated by the following accomplishments:

- Recently, a British engineer, Francis T. Bacon demonstrated a fuel cell that operated a fork-lift truck.

- The Allis-Chalmers Co. showed an experimental tractor powered by a battery of 1008 small fuel cells. Without so much as a whisper from the power source, the 5270-pound tractor dragged a gang plow through a large field.

- Throughout the entire run of the Brussels World Fair, an American-made fuel cell kept a bank of lights glowing.

Many big corporations and the government are anxiously pushing fuel cell projects because these cells have several great advantages over other ways of making electricity. Let's look at them:

- *High efficiency:* Some fuel cells convert up to 70 percent of the energy pumped into them into electrical energy. This compares with 41 percent efficiency

for the newest and largest power plant turbo-generators, and 35 percent for large diesel generator combinations.

- *Silence:* There are no moving parts.

- *No fumes:* The only waste products of most fuel cells is water.

- *Long life:* Some fuel cells have operated continuously for more than a year.

- *No heat necessary:* Some fuel cells operate at room temperature.

What is a fuel cell? Just mix two gases in a chemical solution called an "electrolyte." The energy they give off when they combine is immediately converted into electricity at special collection plates. There is no intermediate and wasteful heat stage, so the cell doesn't heat up of its own accord. The byproduct, usually water, is simply drawn off.


Since the fuel cell is so simple, it's reasonable to ask why it hasn't been perfected up till now. Scientists have certainly been plugging away at the fuel cell long enough. Sir Humphrey Davy talked about the fuel cell 150 years ago. Way back in 1839, Sir William Grove built a fuel cell powered by hydrogen and oxygen.

Most of the early researchers found

that their cells were quickly contaminated and soon stopped working. Extremely pure gases are needed, and purity means high cost. In addition, the favorite fuel, pure hydrogen, is dangerous to handle.

New knowledge of materials has spurred recent progress in fuel cells. Researchers at Lockheed laboratories in Sunnyvale, Calif., have developed ceramic-like electrodes made out of the rarer "transition metals," more familiarly known as the "rare earth metals." National Carbon Company researchers are using carbon for the electrodes and a potassium hydroxide solution for the electrolyte. General Electric scientists have developed a solid, plastic-like electrolyte in place of the liquids that most other researchers use. They claim that this will enable them to pack cells more densely into a given volume. The plas-

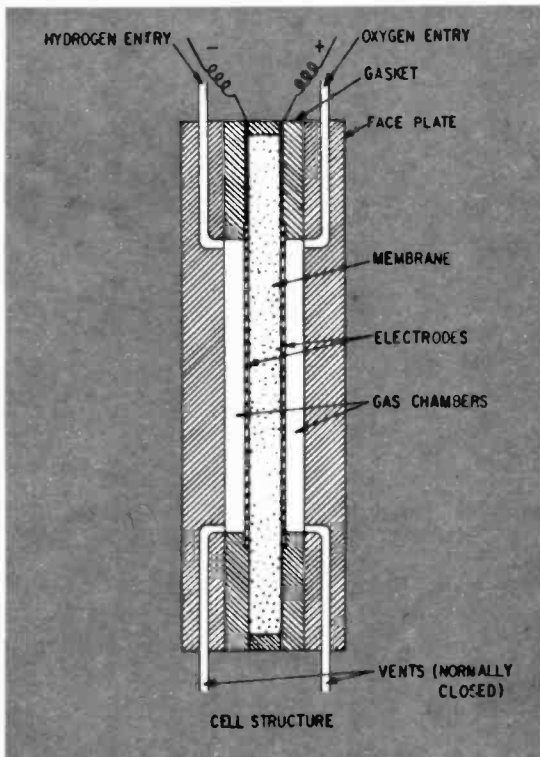Speed and direction controls on tractor vary polarity and amount of current to 20-hp motor.



Here's a diagram of GE's fuel cell which uses plasticized electrodes instead of metal. Water is waste product. Unit is encased in plastic.

tized material is said to pass electrons between the electrodes in much the same manner as the solid electrolyte in a dry cell.

All this talk of "electrodes" and "electrolytes" brings to mind the familiar dry cell and storage battery. After all, they also convert chemical energy into electricity. What's the big difference between the fuel cell and conventional batteries?

The big difference is in the *location* of the chemical energy. The energy in dry cells is stored in the electrodes, which are eventually consumed. In storage batteries, the energy is also stored in the electrodes. However, the chemical reaction that produces electricity is reversed when the storage battery is recharged, restoring the electrodes to approximately their original condition.


In the fuel cell the chemical energy is stored *outside* the cell in gas tanks. The electrodes *promote* the reaction, but are not eaten up by it. Therefore, they should last indefinitely.

The inventors of the various fuel cells each see their devices in different applications. [Continued on page 120]

the E I

Build-It Course-6

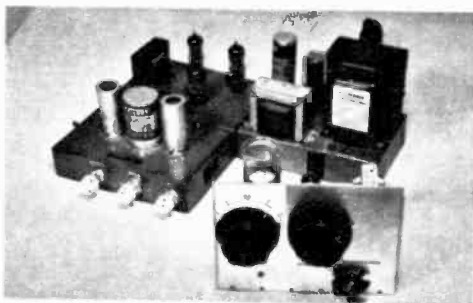This month's project, combining theory with practice, is a regenerative detector for the SWL.



Unit may be built to plug into the previous projects in this series; in place of FM tuner.


THE AM and FM tuners recently described in this series use the superheterodyne circuit, notable for its ease of tuning, sensitivity and selectivity. This combination of features has virtually eclipsed the *regenerative detector*, which previously enjoyed wide popularity. We are going to revive it here; it still has much to offer the electronic hobbyist.

It can't be surpassed for performance versus amount of parts required (and low cost, too). Several manufacturers of Citizens Radio transceivers are using regenerative circuitry for this reason. Speak to old-timers in ham radio and there's a good chance that they've "worked the world with a regen."

The regenerative set shown here employs a single tube to

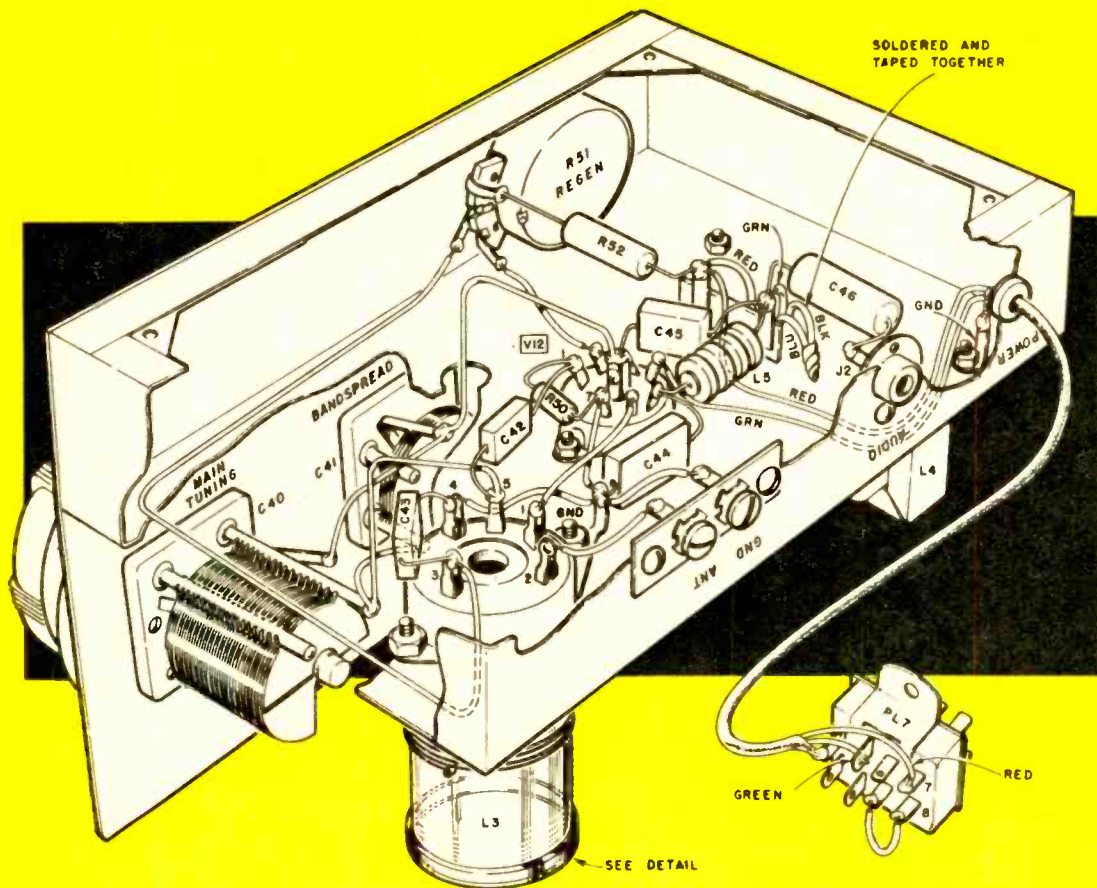Frequencies are pencilled on white paper pasted behind main tuning knob (only lowest band shown). Use Bandspread for tuning individual stations.








Above, left side of chassis is shown broken away to reveal detail of tuning capacitor wiring above chassis.

Underside view of model. Arrow near center points to $\frac{1}{2}$ " hole where ground wire from C40, C41 emerges.

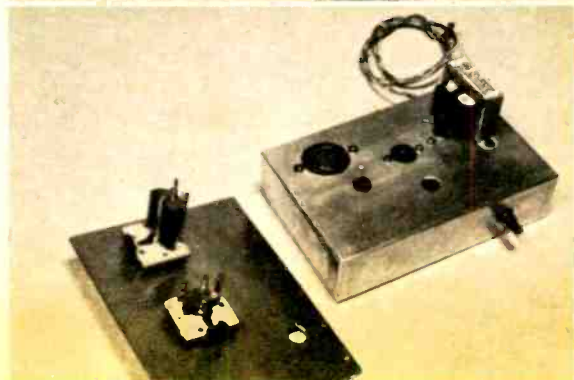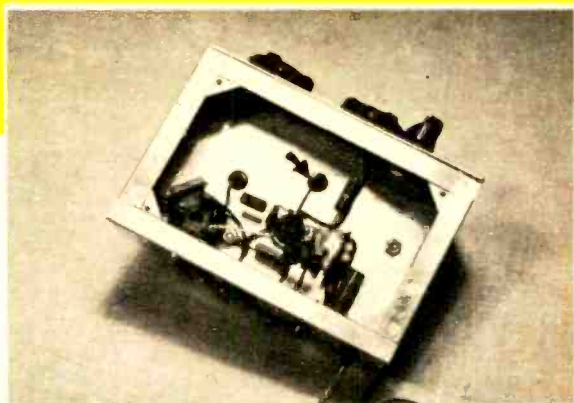C40 and C41 mount to front panel, which is fastened to chassis by R51 on one side, nut and bolt on the other.



HOW THE REGENERATIVE DETECTOR WORKS


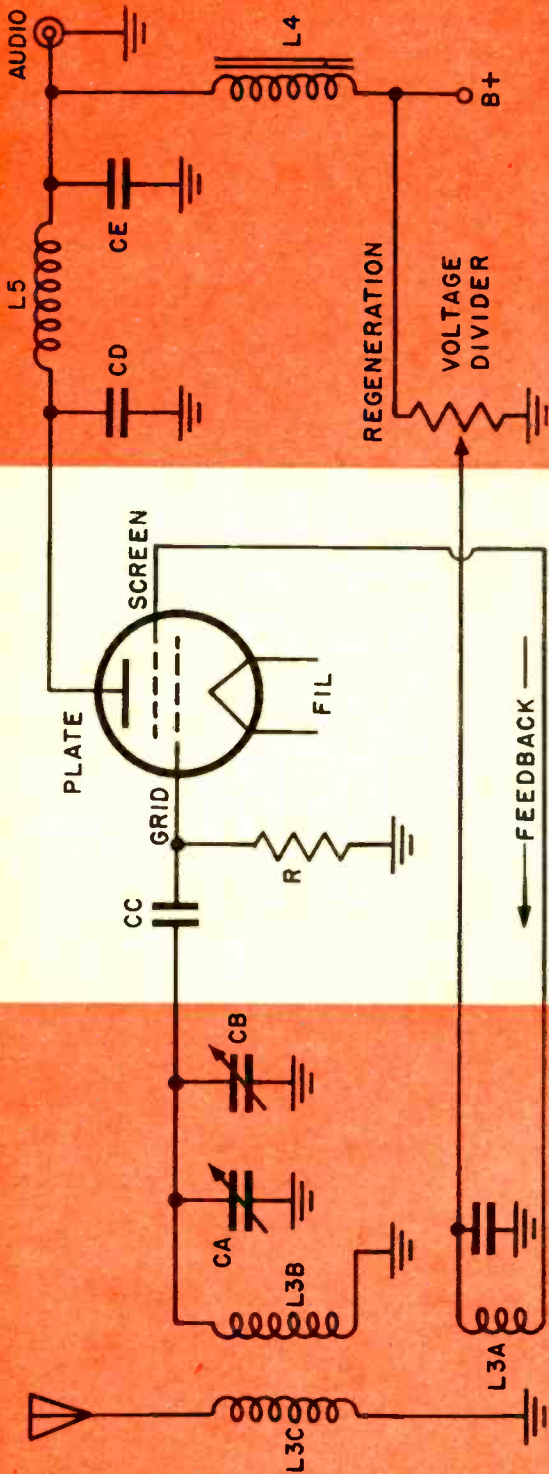


Signals are intercepted by the antenna and appear in the antenna winding (L3C) of the plug-in coil. They couple to tuning coil L3B. Variable capacitors CA and CB are across the tuning coil to resonate it and select the desired station. The slow tuning rate of CB serves to bandspread the stations. L3A is the tickler winding of the coil. It couples energy from the output of the tube back into tuning coil L3B to provide the regenerative action which greatly reinforces the original signal. Note that the feedback signal in the tickler is identical to the signal that has been selected by the variable capacitors and tuning coil except for one important difference: it is an amplified version of it since it has passed through the tube. All coils are wound on the same form.

Selected signal enters capacitor CC and the resistor R. They form a grid leak for detection purposes. Detection removes the negative half of the input signal, the first step toward converting it from a radio to an audio waveform. It works in the following manner: the signal drives the grid positive causing it to conduct electrons from the filament. They flow through resistor R and produce a voltage drop that makes the grid negative. CC blocks the passage of electrons back through the tuning coil; they can only "leak" through the resistor. The negative grid voltage is the operating point (or bias) that determines the portion of the waveform that will be amplified in the tube. Thus, only the positive pulses drive the grid sufficiently positive to permit electrons to flow in the screen and plate circuits.

Regeneration control is across the B+, its movable arm selecting out the desired voltage. This voltage is applied to the screen, through coil L3A thereby determining the amount of electrons attracted to the screen. If the arm is moved toward ground, the screen is made less positive and the amount of feedback is reduced. L5 with its associated capacitor CD and CE form a radio frequency filter. Here, the spaces between the RF pulses are "filled in," much in the same manner as the power supply filter described earlier in this series. The net result is an audio waveform, fed to the audio jack into which the earphones are plugged. L4 is an iron-core choke whose large inductance opposes low audio frequency passage.


PLUG-IN COIL L3

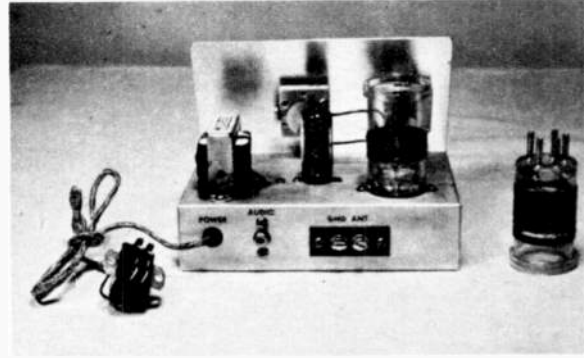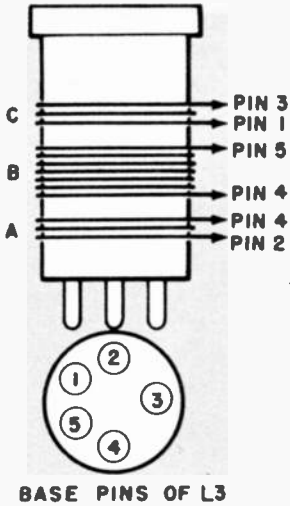

Rear of unit reveals input and output. Two of the three coils are shown; one in its socket.

At left is coil winding guide. Pin numbers along side correspond to base pins of L3.

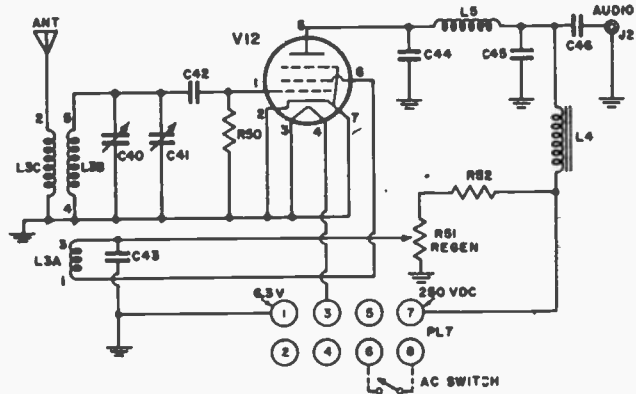Schematic of detector. Pins 1 and 7 on PL7 show required voltages if an external power supply is used.



accomplish each function of receiving. It tunes radio signals in the antenna and supplies audio; sufficient to drive ear-phones at the output. Code reception is easily possible, too.

Consider this tube (for a moment) as a basic radio frequency amplifier. Im-

press a signal voltage on its control grid and amplification occurs in the plate circuit. This is because the large plate current flow varies with control grid fluctuations. But our aim is *maximum* amplification. This could be done by

[Continued on page 117]

PARTS LIST

(Part numbers continue from last month's project)

R50—220,000 ohm resistor 1/2 watt
R51—50,000 ohm potentiometer
R52—18,000 ohm resistor 2 watt
C40—140 mmfd variable air capacitor
C41—15 mmfd variable air capacitor
C42—100 mmfd mica capacitor 500 volt
C43, C44, C45—.001 mfd mica capacitor 500 volt
C46—.01 mfd paper capacitor 400 volt
V12—6B5 tube
L3—Plug-in coil, #24 enamel wire closewound. Space windings approx. 1/16" apart. Wind three forms for following frequency coverage:

L1, L3	1.8 mc-5 mc	5 mc-12 mc	12 mc-20 mc
L2	5 turns	3 turns	2 turns
	25 turns	12 turns	5 turns

L4—Audio choke. Use Stancor A-53 and wire as shown in wiring guide
L5—2.5 mh choke
PL7—8-pin chassis mount plug (Cinch-Jones P308A8)


J2—chassis-mount phono jack

Misc.—Aluminum chassis 4"x6"x1 1/2" (Premier ACH-436), one 7-pin tube socket with centerpost, rubber grommets, #14 enamel wire, #24 enamel wire, three coil forms (Amphenol 24-5P), one standard 5-pin tube socket, one 2-lug terminal strip, 2-screw terminal strip for antenna-ground, 2-conductor shielded cable, scrap aluminum for front panel, knobs

TV Around the World: A Confused Picture

By John K. Friebohn

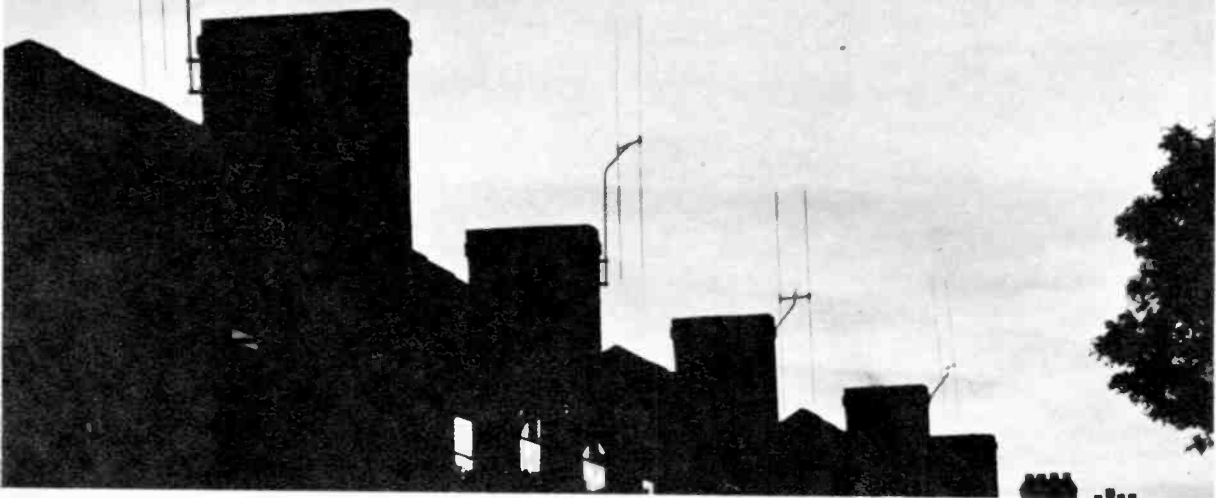How is American TV different from British, French, and Russian TV? Why do they use different antennas?



Rooftops in England: Notice that even the antennas are different. In U. S. we have horizontal polarization while English prefer vertical. No reasons given.

CAN you watch foreign programs on your television set? Could you use your set in another country? If visitors to the United States take home American sets, will they be able to use them?

Standard U. S. equipment may be used almost anywhere in the Americas. But elsewhere the owner of an American set would run into trouble. Even in Europe, a set made for one country may be just this side of worthless in another.

A variation in power line voltage is perhaps the first difficulty. In some Latin American and European countries the voltage is around 117, as in the United States. But many other countries use 220 volts. This problem is not confined to television and can easily be solved with a step-up transformer.

But the real problem, whether you take your TV set to another country or stay home and try to pick up foreign stations, is in the TV signals themselves. Channels may be on entirely different frequencies. Even if your set could be made to bring in the video signal of an overseas channel, the sound may not be along for the ride.

Chances are that video and sound carrier frequencies are not separated in the same degree as in standard U. S. TV.


And the detail of the picture may be spoiled because your set does not have the kind of frequency response required by the




Number of horizontal scanning lines per frame varies in several systems. Number can make a difference in picture definition. Example: (L. to r.) 60, 400, 800 lines respectively.

Radiodiffusion-Television Francaise photos

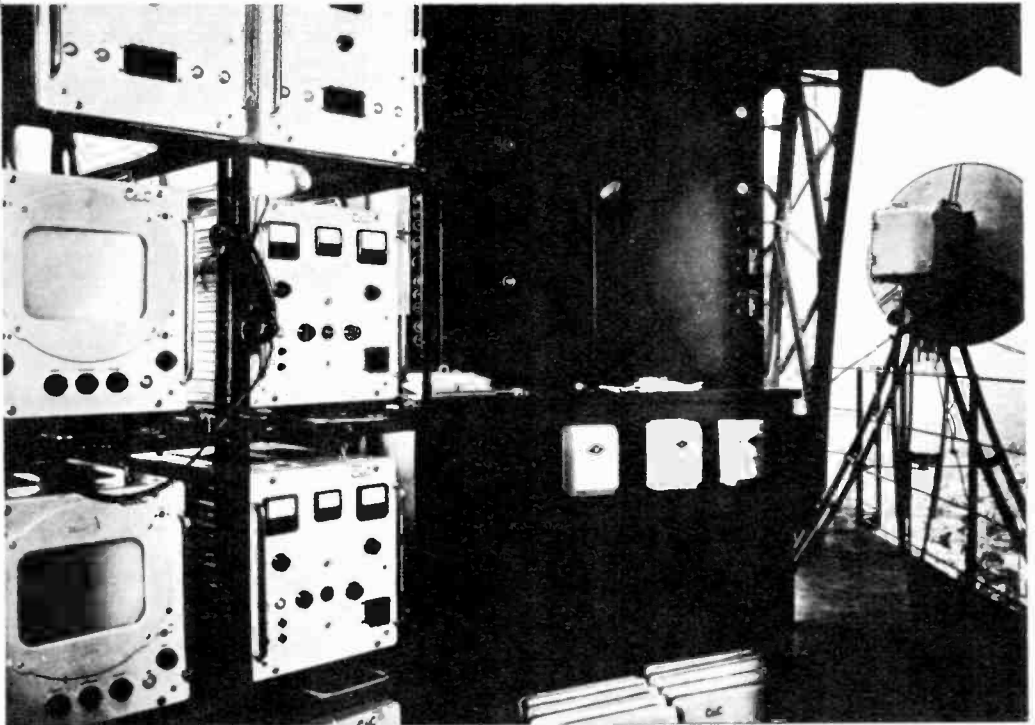Paris TV gets into provinces thanks to facilities atop Eiffel Tower. But American set couldn't get good signal even if it was within a mile because of 819 line scan, etc.



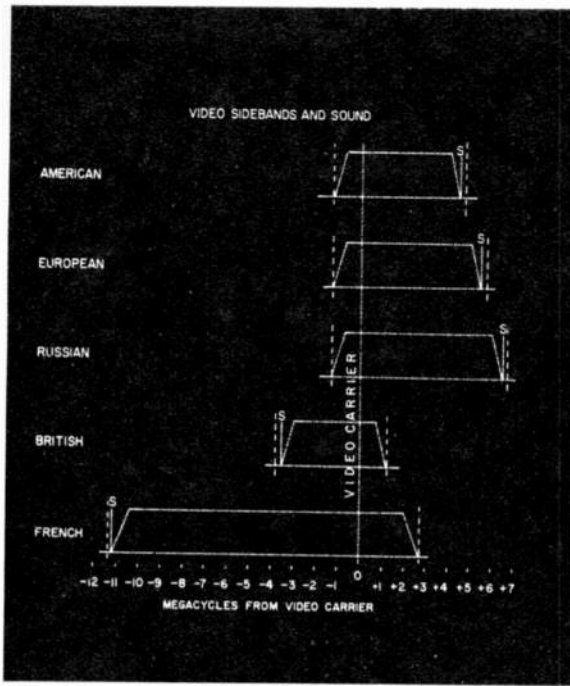

Amount of detail in a television picture is a function of bandwidth, but the wider the bandwidth, the fewer the number of channels available to the viewer. The trapezoidal sections represent bandwidths of the video signals. All video carriers are shown along the same vertical axis. The short, solid vertical line marked "S" represents the sound carrier. Broken lines are nominal edges of the channels. French have widest bands.

transmitted signal. Then too, it may not be possible to get a synchronized picture.

If you modify your set to take care of all these differences, you may get a picture which is fine except for one thing: It is like a photographic negative, dark where the original scene was bright and vice versa.

The parts of the radio spectrum available for television and FM broadcasting are fixed by international agreement. One set of bands is used in the Americas, slightly different bands in Europe and Africa, and a third variation in Asia and Australia. The USSR and its satellites use bands slightly different from those used by other countries.

Tuning to a channel would not necessarily be the same as tuning all of the channel in properly. U. S. television

channels are 6 mc wide; others are 5, 7, 8, 9, or 14 mc.

U. S. TV channels have the sound carrier 4.5 mc higher in frequency than the video. Elsewhere in the world the difference is 5.5 or 6.5 mc. The British and French have depressed their sound below the video.




All of these differences in frequency arrangement within a channel require differences in video and sound circuits.

The vertical sweep frequency in a television set usually is the same as the local power line frequency, 60 cps in the U. S., 50 in some other countries. Two vertical sweeps are required to make one picture or frame, so there are either 30 or 25 frames per second. A TV set's vertical hold control usually has



[Continued on page 123]

TV SCANNING STANDARDS				
System	Frames Per Second	Vertical Sweep Frequency	Lines Per Frame	Horizontal Sweep Frequency
American	30	60	525	15,750
European	25	50	625	15,625
Russian	25	50	625	15,625
British	25	50	405	10,125
French	25	50	441	11,025
French	25	50	819	20,475



Henry and Me Electronic Handymen

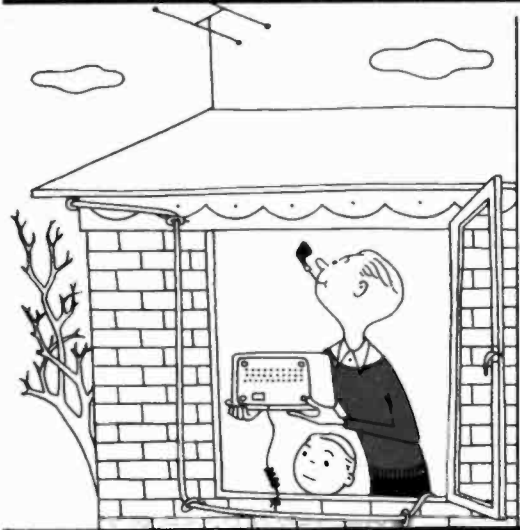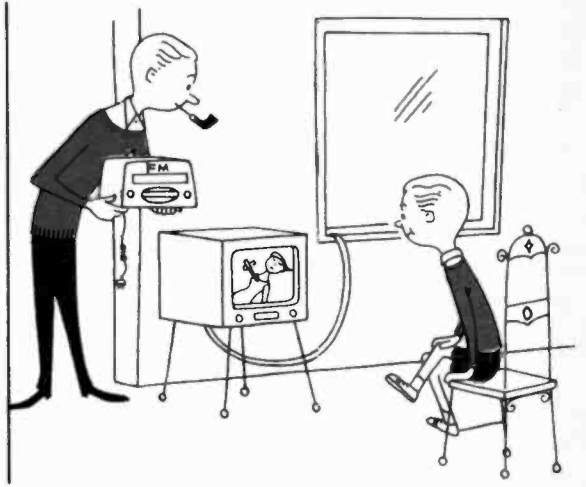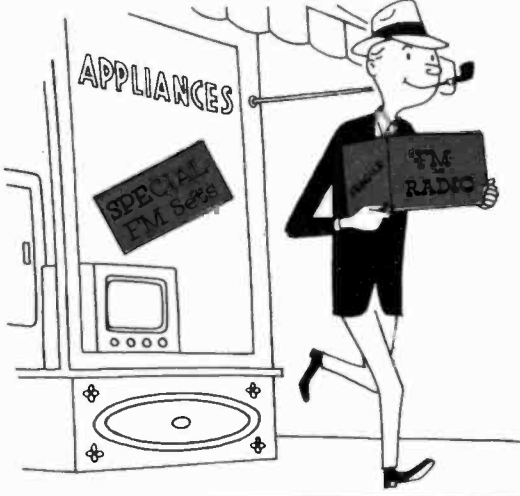

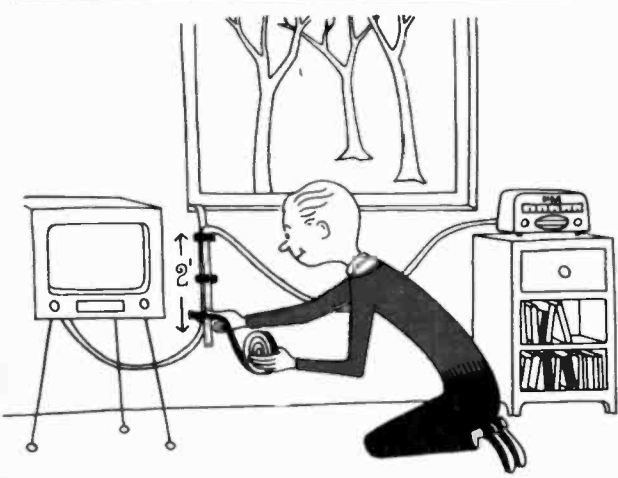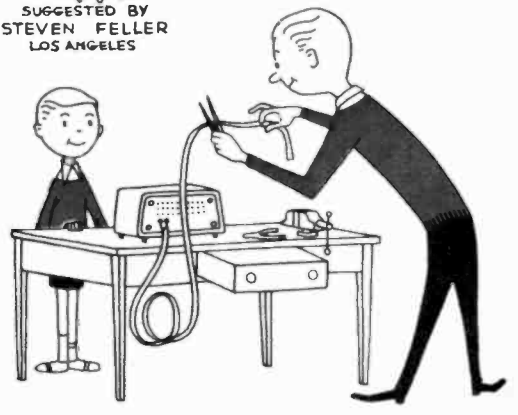
harry goff
SUGGESTED BY
STEVEN FELLER
LOS ANGELES



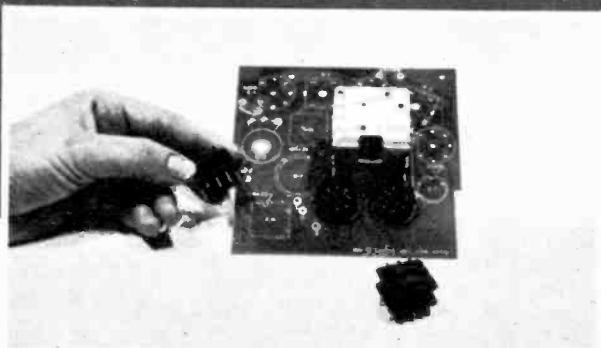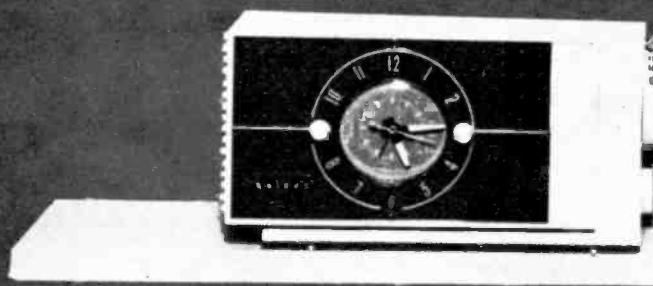
E I reports on the
**Knight - Kit
Clock Radio**



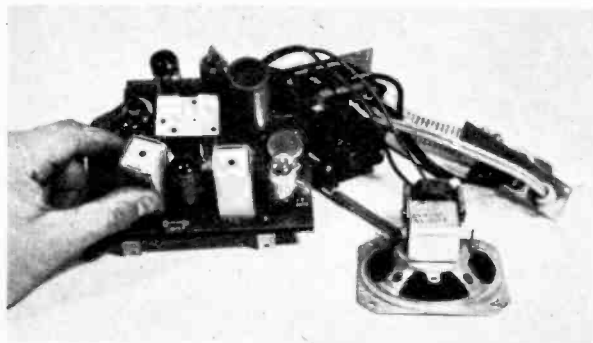Tuning and volume controls are at right side of the cabinet. Clock and its timer controls are on the front panel.



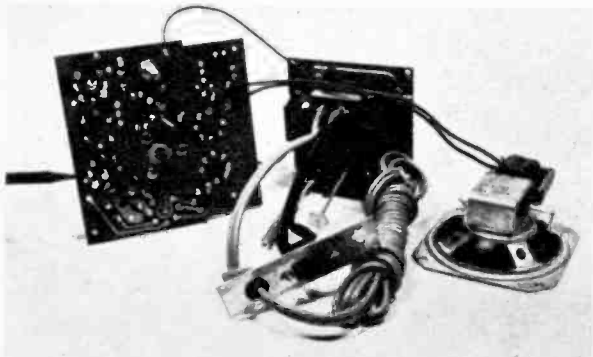Hand holds one of two plug-in modules containing resistors and capacitors. External wires are soldered to board.



Component leads are soldered to the board's underside, left. Clock, line cord and speaker are visible next to it.

Plug-in modules, used in a kit for the first time, reduce this unit's construction time to two hours.


ALLIED Radio of Chicago is marketing a unique clock-radio kit. A conventional five tube superheterodyne circuit is assembled on a printed circuit board which utilizes two plug-in modules that contain most of the small parts—resistors and capacitors.

A soldering iron, cutting pliers and a screwdriver are all that are needed to assemble the set. Five tube sockets snap into place on the board, as well as the IF cans, oscillator coil and filter capacitor. Three screws secure the tuning capacitor to the board. The output transformer is mounted on the speaker frame and slides into place between two brackets moulded into the plastic cabinet.


A Telechron clock and alarm is attached to the cabinet by four self-tapping screws. Any appliance that draws up to fifteen amperes can be turned on automatically at a predetermined time.

The instruction booklet is well written and the easy-to-follow drawings make errors almost impossible. Parts fit into just one designated spot, the entire kit requiring about two hours of construction time. The set operated perfectly without any adjustment to its oscillator or IF circuits. Slight trimming and peaking of the transformers can be done with a signal generator, but alignment by ear and a plastic adjusting tool is quite sufficient. Soldering the modules into the circuit is simple once the first "riser" is solidly in place.

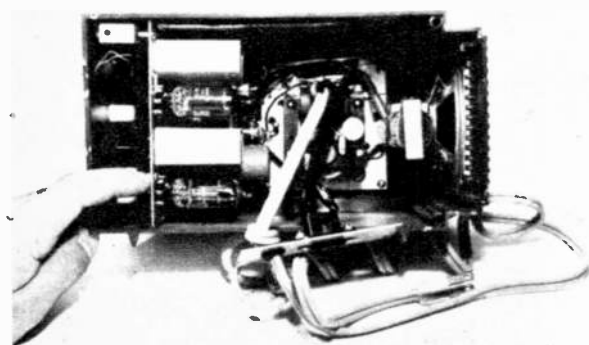The clock movement is rugged and the printed circuit should give many years of reliable service if the radio is not manhandled unreasonably. The kit sells for \$24.95. —



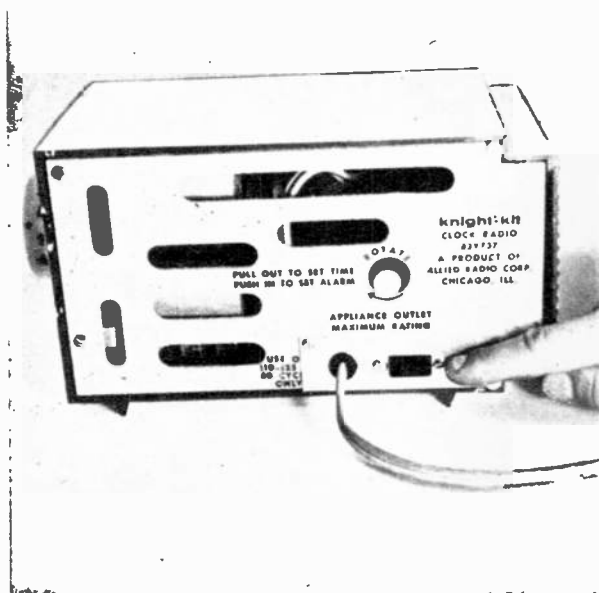Rear view of open cabinet. Note vertical mounting of the printed circuit board at left.



Rear cover in place. Finger points to AC accessory socket for controlling appliances.


Electronic Brain

Have you any question on electronics? Send it in and the Electronic Brain will provide the answer.

Amplifier for Crystal Set

I have a crystal radio to which I would like to add a transistor amplifier. Can you give me the circuit for this?

Charles Miller, Tonawanda, N. Y.

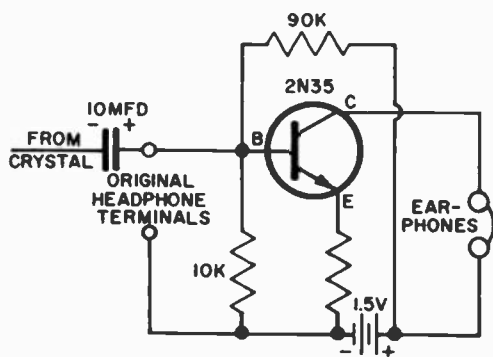

The circuit for the additional transistor amplifier stage is given in the accompanying diagram. To make the connections, remove your headphones from the position indicated in your diagram and add the transistor stage as shown. This circuit has been thoroughly tested and can provide good amplification.

You will note that the .002 mfd coupling capacitor originally present in the crystal set has been replaced by a 10 mfd type. This is very important if you are to realize the gain this circuit can provide. We might also mention that it is much better to mount transistors in special sockets intended for them than to try to solder them directly into the circuit. They are easily damaged by heat. In addition, be sure to observe the battery polarity shown, otherwise the transistor can be ruined.

Hydrophones

Can you provide me with details concerning hydrophone systems including information on microphones, connecting cables, amplifiers, etc.? Can hydrophones be purchased commercially?

R. W. Szulewski, West Seneca, N. Y.

A hydrophone is an underwater listening device. Its principal application is that of an echo depth sounder in ultrasonic sonar systems; in wartime, of course, hydrophones have been used to locate submarines by the transmission of noise from their propellers through the water. Sound travels great distances through water due to the density of this medium.

Microphones for hydrophonic application must be thoroughly waterproofed. The waterproof housing requires careful design in that it must admit sonic or ultrasonic pulses without excessive loss due to boundary reflections. Any type of microphone may be used, provided that these specifications are fulfilled. A PM speaker with output transformer should make an excellent transducer, but such a unit would be extremely difficult to waterproof. Due to the fact that the transmission line from such a microphone is low impedance, any waterproof cable would be satisfactory to connect it through the water to the equipment above the surface. On the other hand, a crystal microphone would call for a shielded and waterproofed transmission line to the surface.

Either transistor or vacuum tube amplifiers may be used with hydrophones. The requirement is that the amplifier, regardless of type, have sufficient gain for the microphone being used. Generally, an input transformer is required to match a crystal microphone to the input of transistor amplifiers due to the differences in impedance, although some circuits showing direct connections have been published.

The only hydrophones now being sold commercially are the ultrasonic type used for echo depth sounding. Manufacturers of such equipment may be located by referring to the advertiser's index in publications such as Electronics, Electronic Industries, Electronic Design, etc.

Tape Recorder Interference

When my tape recorder is placed on record or erase, it produces a high-pitched whine at 930 kc on my radio. What causes this and how can it be corrected?

Stacey Jarvin, Alberta, Canada

Erasure of recorded material on magnetic tapes is accomplished by passing the tape through a high-frequency alternating magnetic field. To produce this field, the tape recorder contains a built-in oscillator that generally operates continuously at about 80 kc. When switched to "erase," the field produced by the oscillator's AC appears in the head and is applied to the tape.

When this signal causes interference with a radio, the trouble may be due to one of two causes:

(a) Harmonics may be feeding back into the radio via the AC power lines. If this is taking place, the effect can be spotted by connecting a 0.5 mfd capacitor across the AC input terminals of the recorder as close to the recorder as possible. Line feedback will be greatly reduced or entirely eliminated by this method.

(b) The signal may be radiating through the air directly to the radio. The remedy for this is thorough shielding (metallic) of the entire unit, grounding of the shield, and by-passing the power lines at the recorder as in (a).

TV Inputs

Can a microphone and phono input be installed on a television receiver?

Thomas Stanley, Renns, N. Y.

First you must identify the first audio voltage amplifier in the sound section of the receiver. This tube may be either a triode or a pentode and is usually located close to the power output tube that feeds the loudspeaker. For the easiest possible circuit connections, secure an open circuit jack or a standard phono jack with its shell grounded to the chassis. Run a shielded wire from the center terminal of the jack to the control grid (grid #1) of the previously located audio voltage amplifier. Either a crystal cartridge or a high-output crystal microphone should be used.

Your next step depends upon your


location and the type of receiver you have. With the microphone plugged in, try the noise level by rotating your channel selector to an unused frequency. If the noise level is too high, remove the last i-f sound tube from its socket. This procedure cannot be followed with series-type tubes, however, since it will extinguish a whole string. In this case, a closed circuit jack that disconnects the audio discriminator or ratio detector from the voltage amplifier would have to be used. As the microphone or phono plug is inserted in this type of jack, it automatically disconnects the audio amplifier from the preceding circuit while it simultaneously connects the microphone to the control grid of the audio stage. Unless you are experienced at electronic wiring, this procedure is not recommended since it may disturb receiver operation.

400 Cycle Power Supply

Can I use surplus equipment designed for 115 volts at 400 cycles on 115 volts, 60 cycle line? If not, what changes must be made in the equipment?

*Richard Lagerstrom,
Marine-on-St.-Croix, Minn.*

No, you cannot. Power transformers designed for 400 cycles have entirely different primary windings than those used on 60 cycles. The 400 cycle transformer would overheat badly soon after being connected to a 60 cycle line and its windings would probably burn out.


It is necessary to replace the 400 cycle transformer with a 60 cycle type having the same voltage and power ratings. This data is usually obtainable from the specification plate on the equipment. In addition to this, the filter capacitor(s) and filter choke (or filter resistor) would have to be replaced since a 400 cycle ripple is much easier to remove than a 60 cycle ripple. If the original power supply was not "overdesigned," its filter components will be too small to do an acceptable job on 60 cycles. Increase capacitor size to at least 16 mfd and be sure that the choke is 10 henries or more. In the event that a filter resistor rather than a filter choke is used, its value for 60 cycles should be 10% larger than for 400 cycle operation. 

E I Picturescope



Back in 1929, a pretty girl who wanted to listen to a portable radio had to have a weightlifter for a boy friend. Nowadays, a pert lass, such as West German starlet Maria Perschy, can "lug" her own portable, in this case a Telefunken. Sports attire also seems to have dwindled over the years.

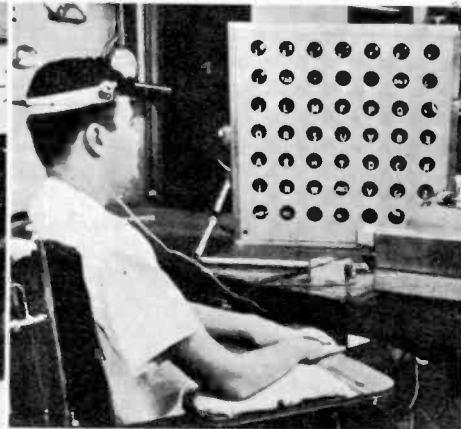So you want a bank loan, eh? At lower left, unbeknownst to the applicant across the desk, London bank executive views his account and ledger records via Marconi closed circuit TV to determine how much credit to extend.





A transistorized radio which tunes the standard AM broadcast band is shown looped over the ear of lovely Karin Krause in Frankfurt, West Germany. In her hand is a second receiver with a wire antenna that can pull in stations within a 15 mile radius. A tiny battery supplies enough power for 150 hours of operation. Tuning this lilliputian unit is done by changing inductance of a tuning coil. They can be converted to receive other frequencies.

Typewriting, which normally requires considerable finger dexterity, may now be accomplished by handicapped persons who do not have the use of their hands. An electric typewriter has been hooked up with an "upright keyboard." Behind each letter or character on the board is a photo cell. In order to activate any given key, the patient simply aims a light strapped to his head at the appropriate "hole" in the board. Yes, it takes much practice.



Hy-Com receiver is installed in trunk of driver training cars, feeds speaker on dash. Antenna is pipe-like affair.

Radio Aids Driver Trainees

High school students learning to drive hear about their "road manners" through in-car radio setup.

Before the anxious Flint teenagers take to the road they must attend classroom lectures on driving safety, technique. Before heading for cars, left, they get some last minute instructions. Once on the course, right, they may hear teacher in tower say: "Slow down, 3!" "Turn left, 1."






Instructor in tower has a clear view of the entire range. The small Hy-Com panel allows him to talk to one, two or all three areas of the course at once.

BEFORE Flint, Mich., began its driver training program four years ago it had hit rock bottom in traffic safety for cities its size. Now Flint is number two. According to the latest fiscal figures available, driver training graduates were not involved in a single serious accident, and 95.5 percent had absolutely no traffic violations.

Delco Radio Division of GM has now joined the program with Hy-Com, their novel very low frequency radio communications system in which a single transmitter broadcasts messages to an all-transistorized in-car receiver. Hy-Com was designed primarily to allow authorities to inform drivers about speed limits, traffic conditions, exits—even historical points of interest. When the driver left the controlled road, he would return the receiver.

On the Flint driver training course, a permanent buried wire installation carries comments from a single instructor in an elevated tower to the would-be driver at the wheel. The instructor can communicate with any one of 20 drivers on the range and his messages are not heard beyond the immediate area. 

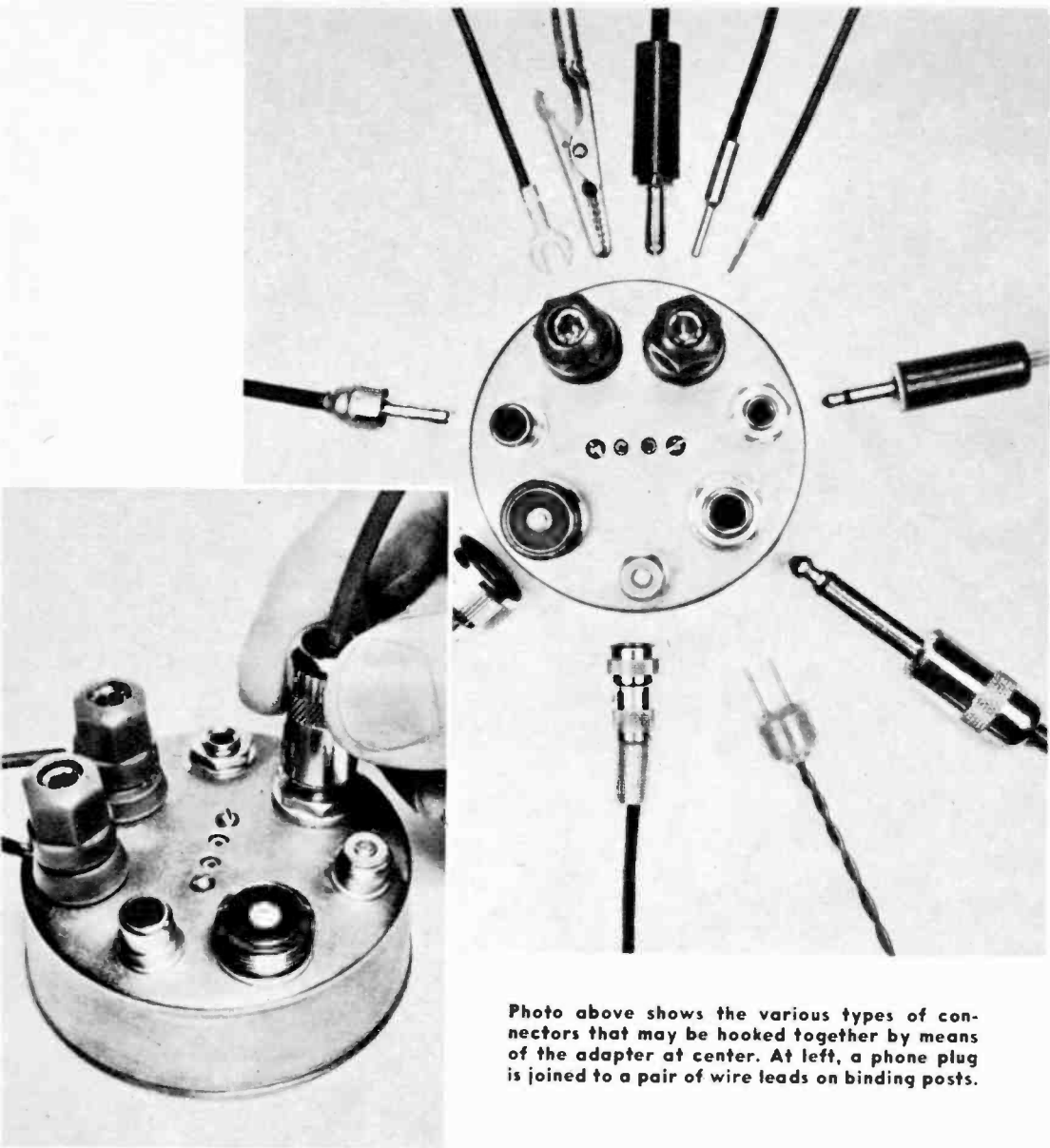


Photo above shows the various types of connectors that may be hooked together by means of the adapter at center. At left, a phone plug is joined to a pair of wire leads on binding posts.

Universal Cable Adapter

By Art Trauffer

Built into a typewriter ribbon case, this adapter permits over 50 combinations of cable connections.

WHEN the writer finished making this adapter he started to count the different combinations of connections that can be made with it, but when he reached 50 he gave up. Certainly, 50 is not the limit for this versatile and easily-made adapter. If you build one of these you will save much time and trouble when

joining together various types of connectors in radio and electronics experimental and test work.

To provide a degree of shielding, the adapter is built in a 2½" by 1" metal container for a typewriter ribbon, but any similar metal container with a friction lid will do. The enamel coating on the outside of the container was removed with sandpaper and scouring powder.

The illustrations show how the two 5-way binding posts, and five of the jacks, are mounted in a circle on the friction lid. The "Tiny Jack" is screw-fastened in the center. The exact placement of the parts is not critical—just arrange them for convenience and good looks. Instead of drilling the mounting holes the required size, the writer found he could do a neater job by drilling small holes and enlarging them to the required size with rat-tail files. However, the four small holes for the "Tiny Jack" are easily drilled as required—use a No. 44 drill for the two mounting screws, and a No. 31 drill to clear the two pin holes in the jack.



All of the parts are wired in parallel, and the wiring is simple because the "ground side" of most of the parts are automatically connected together when the parts are mounted onto the metal lid of the can. If the inside of the metal container is coated, be sure to scrape the metal clean at the places where the parts are supposed to contact the metal lid.

If your metal container isn't quite deep enough when the container is closed, simply raise the friction lid a little and then solder both parts of the can together with some solder spots.

PARTS LIST

- 2 5-way binding posts
- 1 single-hole mount phono pin jack
- 1 standard microphone chassis connector
- 1 miniature microphone chassis connector (Switchcraft)
- 1 standard open circuit phone jack
- 1 miniature phone jack
- 1 "Tiny Jack" (Lafayette MS-284)
- 1 round metal container with friction lid about 2½" wide and 1" deep. (Carter typewriter ribbon case or equiv.)
- 2 2-56 or 2-64 round head machine screws ¼" long with hex nuts for "Tiny Jack"
- Misc.—Few assorted lockwashers, few inches #22 hookup wire

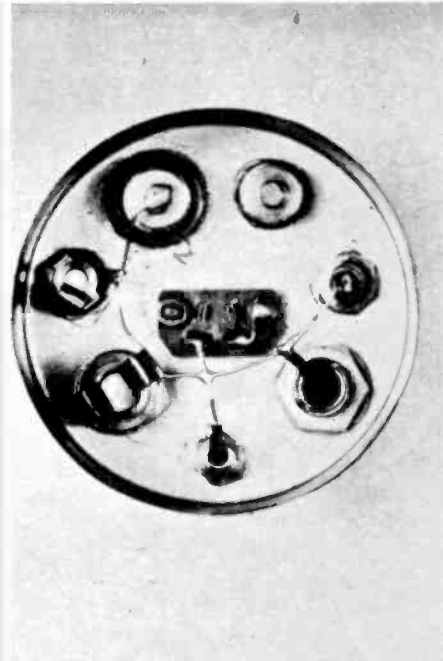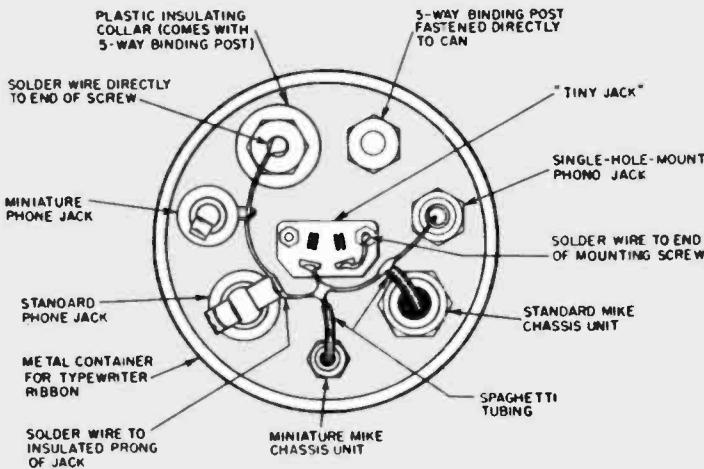Drawing and photo show how parts are mounted and wired inside the case. Use #22 hookup wire. Note that one 5-way binding post has no wire connected to it since it grounds directly to case.



Brainy Man Builds Better Brains


What does it take to be an electronics genius?
Here is a profile of a young British candidate.


THE electronic genius of 27-year-old Gordon Pask hasn't exactly stood the world on its ear. For example, his first invention, a musical typewriter, was simply too expensive to run. Then came "Musicolor," a 70-tube, 100-relay brain designed to listen to music and automatically adjust the lighting of a stage or dance hall. A London theatre gave it a try and the critics were unanimous: "The show was a shambles!"

Undaunted Pask—his hair falling over his ears, his sad blue eyes rimmed with red—set about building an electronic brain so nearly human that it even has neurotic complexes. He has completed his masterpiece and has dubbed it "Eucrates I."

Exactly what is Eucrates I? Well, besides its many knobs, relays and vacuum tubes, it is a home- [Continued on page 125]

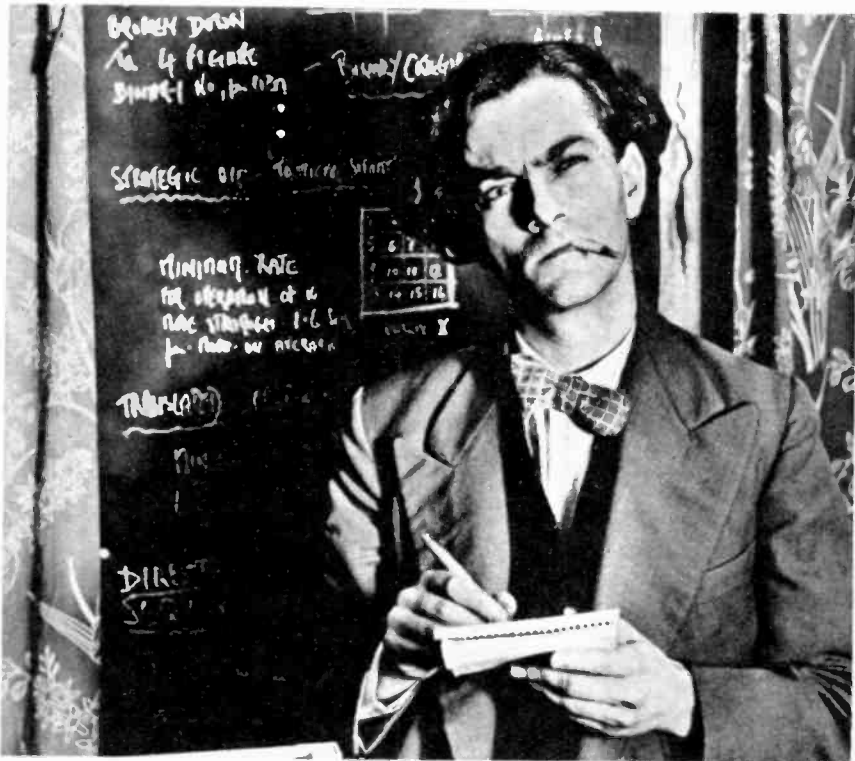Deep concentration furrows the brow of Gordon Pask as his "mind's eye" works on some complex counting. On blackboard is matrix for his theories.



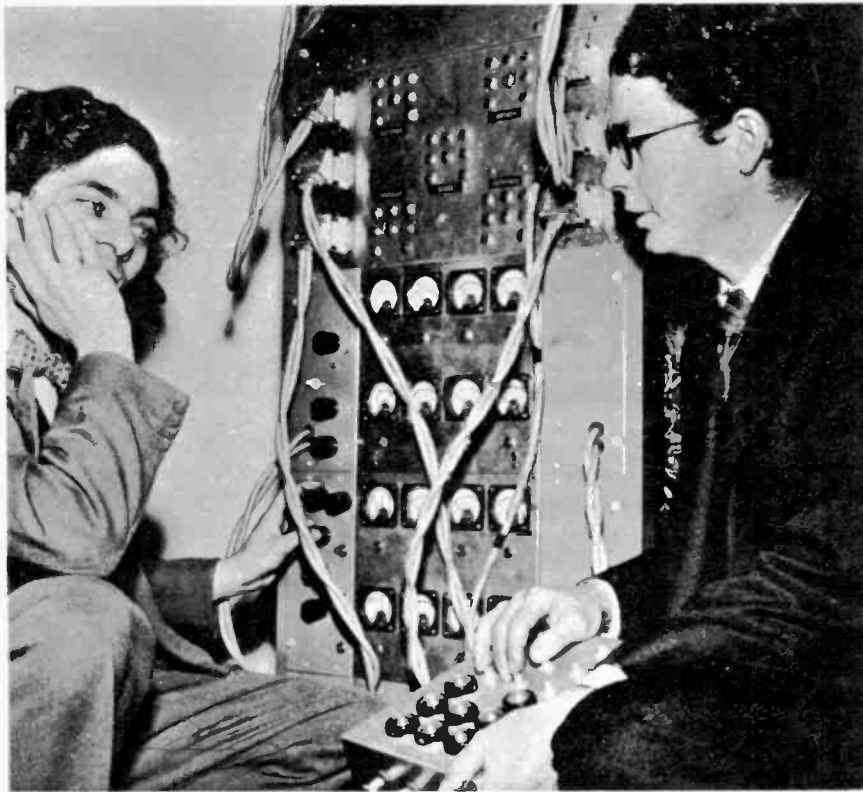

Pask and pal Wood, right, give Eucrates I a workout. Callouts under sets of bulbs read: Question, Answer, Stimulus, Clues, and finally Response.

Photos by BIPS



Eucrates I project, more successful than Pask's previous ventures into invention, is under the sponsorship of Solartron, a British industrial concern which is billing it as teaching aid.

Some sixty cigarettes a day seem to sustain Pask as he ponders the problems of electronic circuitry in his modest kitchen. Friends call him the "man who never sleeps," 6 hours in 3 days.

In the true do-it-yourself tradition, Pask makes his own chassis in the workshop of Systems Research Limited, an organization devoted to improving automation. He is co-proprietor.


EI'S Hi-Fi Doctor . . .

How Hi the Fi?

Hi-fi fans have been worrying for years about the frequency response of their outfits. They sink dough into woofers and cabinets for 30 cps output and for tweeters that go up to 16 kc. They buy special pickups and preamps for clean response above 10 kc and massive turntables to assure low (or no) rumble below 50 cps. They buy special test records, and then listen tensely, biting their lips and worrying about the response to harmonics in the 12 to 18 kc range.

Let's get back to fundamentals a bit: are we fixing up these hi-fi rigs so we can listen to matches being lit and keys being jingled? Or are we after music? Old-fashioned music with notes appeals to me and I don't have to have response from 20 cps to 20 kc within 1 db. Let's look at the notes of a musical scale in terms of frequency:

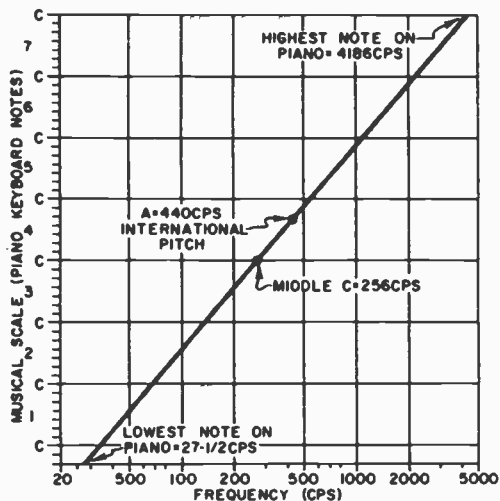The lowest and the highest notes on the piano scale are $27\frac{1}{2}$ and 4186 cps




respectively. Did you ever see a piece of piano music calling for either the top or bottom note? Or even a note in the

top or bottom octaves? I haven't and I've looked. The notes actually played on the piano range from 50 to 2000 cps.

What about other instruments? The bottom note on a string bass is 40 cps, and man alive, that is awful low. You hear it when the boys are tuning up. Maybe it's played sometimes but not often. At the top end, there are violin harmonics up to 5500, and the triangle, cymbals, and a few exotic noisemakers that go up to 6500 or so. Pretty rare, too.

Where do we get the notion that we need response from 10 to 20 kc? There is sound up there but it isn't music. It is key clicks, air hissing through mouthpieces, and fingernails hitting the music stands when pages are turned.

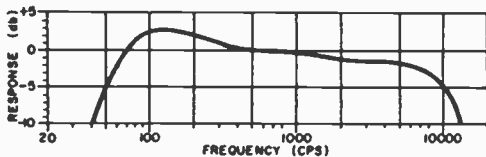A hi-fi bug friend told me my outfit sounded wonderful—much better than his. He asked for my curve and was incredulous when I said I'd never run one. We ran one then and there with his own test record. Here is the curve we got:



The frequency response of my amplifier at the common advertising specifications of ± 1 db was 70 to 2000 cps! The response was only 50 to 10,000 cps at -5 db! And there was an obvious peak at 100 cps.

My friend was appalled and wanted to help me fix up my rig. I reminded him that he thought mine sounded better than his own. "Yes," he said, "but that was before I saw your curve. Mine is much better than this."

Hi-Fi questions are all answered by mail. If of general interest, they will appear in this column.

Adjustable Crossover Net for Guitar

I need a dividing network that has a crossover of close to 175 cycles for use with two 8-ohm speakers. I want to use it with a guitar so that sound from 3 strings comes from one speaker and the sound from the other 3 from the other speaker. I want to be able to vary the crossover frequency. Also how can I convert the values for use with speakers of different impedances?

Robert John Damis, Elmont, N. Y.


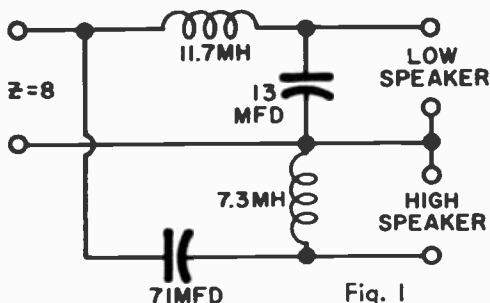


Fig. 1 is a conventional m-derived dividing network for 175 cps and 8 ohm speakers. Because power is involved, we must use coils, and because impedance is low, the reactances must be small—hence balanced pretty carefully. This runs the cost up. I recommend you don't build this until you are sure of the frequency and the impedances.

I recommend instead that you build a breadboard high-impedance circuit (see Fig. 2) that has cheap parts which can be changed easily. Borrow or rent an extra amplifier and speaker, run your pickup signal into this net and feed the outputs into your own and a borrowed mike input. Try it out for pitch. This crossover is about 160 cps here. To increase the frequency, decrease either R's or C's, to make the pitch lower, increase either one. Play your guitar and try it out.

When your plans are firm, then you

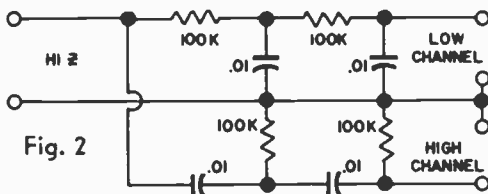
can go for the m-derived unit. The formulas are in many textbooks—*MO-TION PICTURE SOUND ENGINEERING** is one. Computing the values is easier than building it.



Volume Indicator

Is there any way I can use a 0-200 DC microamp meter as a volume indicator on the output of an amplifier?

M. E. Harmon, Sandston, Va.

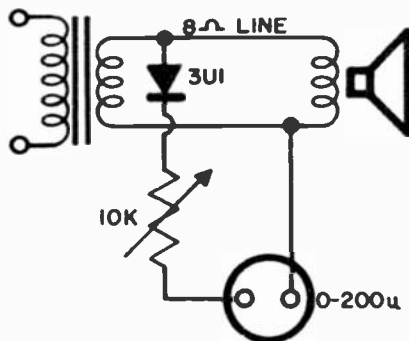

A 200-microamp meter is a voltmeter with a sensitivity of 5000 ohms per volt. You can hitch it across a speaker line with a diode to make the AC into DC and enough series resistance to make the total come to 5000 times the level you want to show full scale. For example, 5 watts in an 8 ohm line is 6.4 volts and total R should be 33K. Crystal impedances vary a lot. You could use a 3U1 here which has about 30K. I'd recommend a 10K pot in series so that you can adjust your indication to full scale on the loudest of your peaks.

*D. Van Nostrand, Inc., N. Y. 1938

Build a CB Beam Antenna

Continued from page 50

muffler clamp mounts the beam on mast.

Although not shown in the photographs, wooden dowels are inserted in each element and positioned below the muffler clamps. This prevents the clamp pressure from crushing the aluminum tubing. Also it will reinforce the splice if you are unable to locate 20 foot lengths for the elements.

A system of matching the coaxial cable transmission line to the antenna is necessary. This is accomplished with a device called a *gamma tube*. It is constructed from a 30-inch length of $\frac{1}{4}$ inch aluminum tubing, similar to the type used in television antennas.

Start construction by cutting the three 20 foot lengths of one inch aluminum tubing to the dimensions shown. Mark the centers, slide the 12 inch wood dowel in each element, position and drill a hole each side of center for the muffler clamp studs. If you use two 10 foot lengths of tubing for each element, pin the element to the dowel for mechanical rigidity.

Next, prepare the gamma tube. The only point in this assembly that must be a good electrical connection is the junction of the gamma and the radiator element. Shine both points with steel wool before assembly. Mount the gamma tube to the element with the plumbers tape (or strap), and insulators, using 6/32 hardware. Join gamma tube to radiator with a $1\frac{1}{4}$ inch auto hose clamp.

The electrical connections are made by stripping back 20 inches of outer insulation and braid from the coaxial cable transmission line. Exactly 18 inches of the center conductor *with its insulation* is inserted inside the gamma tube. The copper shield braid is grounded to the center of the radiator with a sheet metal screw. Tape the opening in the gamma tube with Scotch #33 electrical tape, to keep the wire from moving and prevent moisture from entering the tube.

The elements can now be fastened to the boom. Once the antenna is assembled, you can determine the center of

gravity and install the mast clamp at this point. Use 3 guy wires containing insulators, to support the mast. ⚙

BILL OF MATERIALS

3—20' lengths of one inch aluminum tubing
1—10' length of $1\frac{1}{2}$ inch thin-wall conduit
1—30 inch length of $\frac{1}{4}$ inch tubing
4— $1\frac{1}{2}$ inch muffler clamps
3—20"x $1\frac{1}{8}$ " wood dowels
2—4"x $\frac{1}{2}$ " piece of polystyrene rod
4—1"x6/32 bolts, nuts, and washers
Mast as required (2 10' lengths of "Swedge-Tube" recommended)
10' plumbers tape
 $1\frac{1}{4}$ " hose clamp
Sheet metal screw and ground lug
Coax cable as required

Make Your Own Probe

Continued from page 56

non-critical. Strip back the cable insulation at the probe end as illustrated in the drawing. Couple the components together as compactly as possible and solder all joints securely. Support the leads of the crystal diode with a pair of pliers when soldering it in position.

A machine screw filed to a point makes an easily attached test prod as it can be secured to the probe housing with a nut. A deluxe test prod can be made by cementing an insulated plug tip into the probe housing.

Make all internal ground connections to the cable shield. Attach a short length of insulated wire to the shield for an external ground. This lead runs outside the probe housing and is terminated with an alligator clip. It must be clipped to the chassis of the item being checked for it completes the probe circuit.

Terminate the output end of the probe's lead with fittings that match your test equipment. Make sure the cable braid is attached to common or grounded terminal if phone jack is used.

Chances are that sooner or later you will use your probe to trace a signal through a piece of AC-DC equipment. Assure your electrical safety when doing so by checking the polarity of the radio chassis. Reverse the line cord plug as necessary to put the chassis at ground potential.

Each type of probe has a specific purpose but may be used interchangeably for the more routine jobs. ⚙



The data that Launched Thousands of Careers is yours *FREE* Tells how you can be successful in **ELECTRONICS** Send for your Free Copy today!

This is a brand new edition of the book that has launched thousands of men on good-paying careers in electronics.

It brings you completely up to date—answers important questions on newest career developments in electronics, including Automation, Instrumentation, Industrial Electronics, Aeronautical Electronics, Guided Missiles, Radar, Servo-Mechanisms, Computers, Astronautics, Telemetering, Communications, Manufacturing.

Since its founding in 1927, CREI has provided thousands of professional electronics men with technical education. During World War II, CREI trained thousands for the Armed Services. Leading firms recommend CREI home study courses for their own personnel. Among them: All America Cables and Radio, Inc.; Canadian Broadcasting Corporation; Columbia Broadcasting System; Gates Radio Company; Federal Electric Corp.; The Martin Company; Douglas Aircraft Co.; U. S. Information Agency (Voice of America); Canadair Limited; Trans-Canada Air Lines; United Air Lines. Their choice of education for their own personnel is a good cue for your choice of a school.

You don't have to be a college graduate. You do have to be willing to study—at home. You can do it while holding down a full-time job. Thousands have. Since 1927 CREI has provided alert young men with the technical

knowledge that leads to more responsibility, more job security, more money. And CREI has constantly kept pace with the rapid expansion and progress in electronic achievement. Remember this: CREI starts with a review of the fundamentals and takes you along at your own speed. You are not held back by a class, not pushed to keep up with others. You set your own pace. CREI instructors guide you through the lesson material and grade your written work personally. You master the fundamentals, then get into more advanced phases of electronics engineering principles and practice.

Brand-New Course Added: Automation and Industrial Electronics Engineering Technology: Complete course, covers all electronic phases of automation. Special emphasis on theory, functioning and applications of servo-mechanisms and computers. Also note-worthy: Lessons on machine control, instrumentation, data processing and telemetry.

CREI ALSO OFFERS residence training in Washington, D. C. ... at the same high technical level. Day and evening classes start at regular intervals. Qualified residence school graduates earn degree as "Associate in Applied Science." You can qualify for CREI home study education if you have had electronic training, or experience in electronics—and realize the need of a high level technical knowledge to make good in the better electronic jobs. (Electronics experience is not required for admission to CREI Residence School.)
What's the next step? Certainly to get more information than we can cram into one page. Fill out and mail coupon today, or write Capitol Radio Engineering Institute, Dept. 1702-G, 3224 - 16th St., N.W., Wash. 10, D. C.

MAIL THIS COUPON . . . TODAY!

CAPITOL RADIO ENGINEERING INSTITUTE

ECPD Accredited Technical Institute Curricula—Founded 1927
Dept. 1702-G, 3224 Sixteenth St., N.W., Washington 10, D. C.

Please send me your course outline and FREE illustrated Booklet "Insurance for Your Future in the New World of Electronics" describing opportunities and CREI Home Study courses in Practical Electronic Engineering Technology.

- CHECK FIELD OF GREATEST INTEREST
- Radar, Servo and Computer Engineering Technology
 - Electronic Engineering Technology
 - Communications, Engineering Technology
 - Television Engineering Technology
 - Aeronautical Electronic Engineering Technology
 - Automation and Industrial Electronics Engineering Technology

B³

Name _____ Age _____
 Street _____
 City _____ Zone _____ State _____
 CHECK: Home Study Residence School Korean Veteran



To obtain fast, immediate service, and to avoid delay it is necessary that the following information be filled in:

Employed By _____
 Type of Present Work _____
 Education: Years High School _____
 Other _____
 Electronics Experience _____

SHIPPED ON APPROVAL

NEW

CRT TESTER-REACTIVATOR Model CRT-2

NOW . . . a TESTER-REACTIVATOR really designed to test, repair and reactivate EVERY PICTURE TUBE MADE — whether black and white or color . . . with exclusive features never before found in picture tube testers.



Housed in hand-rubbed oak carrying case—complete with MULTI-HEAD*

Model CRT-2
\$57.50
Net

TERMS: \$13.50 within 10 days. Balance \$11 monthly for 4 months.

The CRT-2 steps in and solves the limitations and shortcomings of present day CRT Testers. Unlike ordinary CRT testers that keep entering the field with a limited range of operation, the CRT-2 employs a new brilliantly engineered circuit designed to test, repair and reactivate every black and white or color picture tube made. The CRT-2 eliminates the guesswork and risk that until now, has always been present when a picture tube is "reactivated." It accomplishes this by providing perfect control of either the "Boost" or "Shot" method of reactivation.

THE CRT-2 DOES ALL THIS RIGHT IN THE CARTON, OUT OF THE CARTON OR IN THE SET

TEST

- ✓ for quality of every black and white and color picture tube
- ✓ for all inter-element shorts and leakage up to one megohm for life expectancy

REPAIR

- ✓ Will clear inter-element shorts and leakage
- ✓ Will weld opens between any two elements in the tube gun

REACTIVATE

- ✓ The unique controlled "SHOT" (high voltage pulse) method of reactivation provided by the CRT-2 will restore picture tubes to new life in those instances where it was not possible before. Furthermore the high voltage is applied without danger of stripping the cathode as you always have perfect control of the high voltage pulse.
- ✓ The "BOOST" method of reactivation also provided by the CRT-2 is used effectively on tubes with a superficially good picture but with poor emission and short life expectancy. It will improve definition, contrast and focus greatly and add longer life to the picture tube.

1. **THE MULTI-HEAD** (patent pending) . . . A SINGLE PLUG IN CABLE AND UNIQUE TEST HEAD — A tremendous advance over the maize of cable and adapters generally found with other testers. Enables you to test, repair and reactivate every type of picture tube with greater convenience than ever before . . . 50 degree to 110 degree types from 8" to 30", whether 12 pin base, 9 pin base, 14 pin base . . . even the very latest 7 pin base. A special color switch on the MULTI-HEAD enables you to test, repair and reactivate each of the red, green and blue color guns separately.
2. **WATCH IT REACTIVATE THE PICTURE TUBE** — You actually see and control the reactivation directly on the meter as it takes place, allowing you for the first time to properly control the oxidation coating. It enables you to see the danger of stripping the cathode and whether the build-up is lasting. You will see if the cathode contamination is too great and if the picture tube is too far gone to be reactivated.
3. **CONTROLLED "SHOT" WITH HIGHER VOLTAGE FOR BETTER REACTIVATION** — Stronger than any found in other testers . . . high enough to really do the job — yet controlled to avoid damage to the picture tube.
4. **UNIQUE HIGH VOLTAGE PULSE CIRCUIT** — Will burn out inter-element shorts and weld open circuits with complete safety to the picture tube.
5. **VISUAL LIFE TEST** — Enables both you and your customer to see the life expectancy of any picture tube right on the meter. The fact that your customer can see the results of your tests as you make them virtually eliminates resistance to picture tube replacement when necessary.
6. **TESTS, REPAIRS AND REACTIVATES SPECIAL LOW SCREEN VOLTAGE TUBES** — Many new type picture tubes use special low voltage of approximately 50 volts. The CRT-2 will test, repair and reactivate these types with the same thoroughness as the regular types with complete safety.
7. **SEPARATE FILAMENT VOLTAGES** — including the very latest 2.35 volt and 8.4 volt types as well as the older 6.3 volt types.
8. **TESTS, REPAIRS AND REACTIVATES "SF" PICTURE TUBES** — found in the newest Sylvania and Philco TV sets. These picture tubes have different base pin connections than standard picture tubes and there is always an element of risk that the tube may be burned out when tested with ordinary picture tube testers. The CRT-2 is designed to accommodate this new base pin arrangement and will test the tube with no danger of damage.

ADDITIONAL FEATURES

- Employs the time proven dynamic cathode emission test principle • Large 4½" meter with heavily damped movement for smooth action, accuracy and long life
- Provides separate shorts test for each element in the picture tube • Filament continuity is shown on a separate glow indicator • An easy to read instruction manual contains all the latest testing information on old and new type picture tubes • Housed in handsome hand-rubbed oak carrying case with special compartment for MULTI-HEAD and line cord. * patent pending

IN-CIRCUIT CONDENSER TESTER Model CT-1

Here is an IN-CIRCUIT CONDENSER that DOES THE WHOLE JOB! The CT-1 actually steps in and takes over where all other in-circuit condensers fail. The ingenious application of a dual bridge principle gives the CT-1 a tremendous range of operation . . . and makes it an absolute "must" for every serviceman.

in-circuit checks:

- ✓ Quality of condensers even with circuit shunt resistance . . . (This includes leakage, shorts, opens, intermittents)
- ✓ Value of all condensers, from 200 mmd. to .5 mfd.
- ✓ Quality of all electrolytic condensers (the ability to hold a charge)
- ✓ Transformer, socket and wiring leakage capacity

out-of-circuit checks:

- ✓ Quality of condensers . . . (This includes leakage, shorts, opens and intermittents)
- ✓ Value of all condensers from 50 mmd. to .5 mfd.
- ✓ Quality of all electrolytic condensers (the ability to hold a charge)
- ✓ High resistance leakage up to 300 megohms
- ✓ New or unknown condensers . . . transformer, socket, component and wiring leakage capacity

OUTSTANDING FEATURES

- Ultra-sensitive 2 tube drift-free circuitry
- Multi-color direct scale readings for both quality and value . . . in-circuit or out-of-circuit
- Simultaneous readings of circuit capacity and circuit resistance
- Built-in hi-leakage indicator sensitive to over 300 megohms
- Cannot damage circuit components
- Electronic eye balance indicator for ever greater accuracy
- Isolated power line
- Housed in sturdy hammertone finish steel case . . . comes complete with test leads



Model CT-1
\$34.50
Net

TERMS: \$9.50 within 10 days. Balance \$5 monthly for 5 months.

EASY TO BUY IF SATISFIED — see order form on facing page

FOR 10 DAY FREE TRIAL

Convince yourself at no risk that CENTURY instruments are indispensable in your every day work. Send for instruments of your choice without obligation... try them for 10 days before your buy... only then, when satisfied, pay in easy-to-buy monthly installments — without any financing or carrying charges added.

NOW a Battery Operated Peak-to-Peak **VACUUM TUBE VOLT METER** Model VT-1

WITH LARGE EASY-TO-READ 6" METER —

featuring the sensational new **MULTI-PROBE** Patent Pending

- 1 DC Probe 2 AC-Ohms Probe 3 Lo-Cap Probe 4 RF Probe

No extra probes to buy! The versatile MULTI-PROBE does the work of 4 probes. The VT-1 is a tremendous achievement in test equipment. With its unique MULTI-PROBE it will do all the jobs a V.T.V.M. should do without the expense of buying additional probes. No longer do you have to cart around a maze of entangled cables, lose time alternating cables or hunting for a misplaced probe. With just a twist of the MULTI-PROBE tip you can set it to do any one of many time-saving jobs. A special holder on side of case keeps MULTI-PROBE firmly in place ready for use.

FUNCTIONS

DC VOLTMETER — Will measure D.C. down to 1.5 volts full scale with minimum circuit loading and give accurate readings of scale divisions as low as 0.25 volts. Will measure low A.C. and oscillator bias voltages from .1 volts or less up to 1500 volts with consistent laboratory accuracy on all ranges. Zero center provided for all balancing measurements such as discriminator, ratio detector alignment and hi-fi amplifier balancing.

AC VOLTMETER — True Peak-to-Peak measurements as low as 3 volts of any wave form including TV sync, deflection voltages, video pulses, distortion in hi-fi amplifiers, A.C. and color TV gating pulses. Scale divisions are easily read down to .1 volts. Measures RMS at 1/20th the circuit loading of a V.O.M. Unlike most other V.T.V.M.'s there is no loss in accuracy on the lowest AC range.

ELECTRONIC OHMMETER — Measures from 0 to 1000 megohms. Scale divisions are easily read down to .2 ohms. Will measure resistance values high resistance leakage in electrolytic and by-pass condensers.

RF and LO-CAP MEASUREMENTS — With these extra VT-1 functions you can measure voltages in extremely high-impedance circuits such as sync and A.C. pulses, driving saw tooth voltages, color TV gating pulses, mixer output levels, i.f. stage-by-stage gain and detector inputs.

OUTSTANDING FEATURES

- Completely portable — self powered with long life batteries — permits use everywhere
- New advanced pentode amplifier circuit assures amazingly low battery drain
- Large 6" 100-microampere meter, many times more sensitive than meters used in most V.T.V.M.'s
- Laboratory accuracy performance — 2% of full scale on DC, 5% of full scale on AC
- Simplified multi-color easy-to-read 4-scale meter
- No heat operation assures rigid stability and accuracy
- Immune to power line compensated alternator — a feature found only in costly laboratory instruments
- Meter completely isolated — practically burn-out proof
- Hand-crafted circuitry eliminates the service headaches of printed circuitry
- 1% resistors used for permanent accuracy
- Separate RF ground return for low-loss RF measurement
- Micro-ohm type coaxial connector
- Matching cover protects instrument face — snaps on and off instantly.

SPECIFICATIONS

- DC Volts — 0 to 1.5/6/30/150/300/600/1500 volts
- AC Volts (RMS and Peak-to-Peak) — 0 to 3/12/30/300/1200 volts
- Ohms — 0 to a billion ohms, 10 ohms center scale — R1, 10/100/1K/10K/100K/1M
- RF — Peak reading demodulator supplied for use on all DC ranges
- Zero Center — available on all DC volt ranges with zero at mid-scale
- Decibels — from -10 Db to +10, 22, 36, 50, 62 based on the Dbm unit: 0Db 1mW in 600 ohms
- Impedance — 1 megohms DC, 1 megohm AC, 10 megohms Lo-Cap
- Input Capacity — 130 mmdf, RMS, 250 mmdf, Peak-to-Peak, 25 mmdf, Lo-Cap



Housed in hammer-tone steel-case — complete with MULTI-PROBE

Model VT-1
\$58.50
Net

TERMS: \$14.50 within 10 days. Balance \$11 monthly for 4 months.



Housed in hand-rubbed oak carrying case complete with CRT adapter

Model FC-2
\$69.50
Net

TERMS: \$14.50 within 10 days. Balance \$11 monthly for 5 months.

FAST-CHECK TUBE TESTER Model FC-2

Simply set two controls... insert tube... and press quality button to test any of over 700 tube types completely, accurately... IN JUST SECONDS!

Over 20,000 servicemen are now using the FAST-CHECK in their every day work and are cutting servicing time way down, eliminating unprofitable call-backs and increasing their dollar earnings by selling more tubes with very little effort. See for yourself at no risk why so many servicemen choose the FAST-CHECK above all other tube testers.

PICTURE TUBE TEST ADAPTER INCLUDED WITH FAST-CHECK
Enables you to check all picture tubes (including the new short-neck 110 degree type) for cathode emission, shorts and life expectancy... also to rejuvenate weak picture tubes.

RANGE OF OPERATION

- Checks quality of over 700 tube types, employing the time proven dynamic cathode emission test.
- Covers more than 90% of all tubes in use today including the newest series-string TV tubes, auto 12 plate-volt tubes, 024s, magic eye tubes, gas regulators, special purpose hi-fi tubes and even foreign tubes.
- Checks for inter-element shorts and leakage.
- Checks for gas content.
- Checks for life-expectancy.

SPECIFICATIONS

- No time consuming multiple switching... only two settings are required instead of banks of switches located inside cover.
- No annoying roll chart checking... tube chart listing over 700 tube types is on multi-section tubes and if only one section is defective the tube will read "Bad" on the meter scale
- 41 phosphor bronze beryllium tube sockets never need replacement
- Checks each section protected against accidental burn-out
- Dissonant type meter is the most sensitive available, yet rugged — fully no shock hazards
- Long filament positions on meter for low current tubes
- Compensation for the Fast-Check positively cannot become obsolete... circuitry is engineered to accommodate all future tube types as they come out.
- New tube listings are furnished periodically at no cost.

CONVENIENT TIME PAYMENT PLAN — NO FINANCING CHARGES

ALL CENTURY INSTRUMENTS ARE GUARANTEED FOR ONE FULL YEAR. The extremely low prices are made possible because you are buying direct from the manufacturer.

CENTURY ELECTRONICS CO., INC.

CHECK INSTRUMENTS DESIRED

- Model CRT-2 CRT TESTER REACTIVATOR \$57.50 \$13.50 within 10 days. Balance \$11 monthly for 4 months.
- Model CT-1 In-Circuit Condenser Tester \$34.50 \$9.50 within 10 days. Balance \$5 monthly for 5 months.
- Model VT-1 Battery Vacuum Tube Volt Meter \$58.50 \$14.50 within 10 days. Balance \$11 monthly for 4 months.
- Model FC-2 Fast-Check Tube Tester \$69.50 \$14.50 within 10 days. Balance \$11 monthly for 5 months.

Prices Net F.O.B. Mineola, N. Y.

111 Roosevelt Avenue, Dept. 4E2, Mineola, New York

Please rush the instruments checked for a 10 day free trial. If satisfied I agree to pay the down payment within 10 days and the monthly installments as shown. If not completely satisfied I will return the instruments within 10 days and there is no further obligation. It is understood there will be NO INTEREST or FINANCING charges added.

Name _____ Please print clearly

Address _____

City _____ State _____

Milt Kiver on Probes

Continued from page 55

RF Probes

RF or high-frequency probes enable VOM's, VTVM's, and oscilloscopes to be employed in higher frequency circuits than they could ordinarily without such probes. Basically, the RF probe is a detector which rectifies the high-frequency signal. When such a probe is designed for a VOM or VTVM, a rectified output voltage proportional to the RF input voltage is desired. Since most RF voltages for which this type of probe is to be employed possess essentially a sine-wave form, the rectifying circuit in the probe is of the half-wave variety. See Fig. 2. The voltage developed by this rectifier is then passed through a long time constant filter and applied to the input circuit of the VOM or VTVM.

In using this probe for signal tracing, the probe is touched to the grid or plate of each tube and the resulting DC voltage noted on the VOM or VTVM. If you start at the grid of a stage and then go to the plate, there should be a noticeable increase if any amplification is occurring. By dividing the indication obtained at the plate by the voltage obtained with the probe at the grid, the stage gain can be quickly computed.

When an RF detector probe is designed to be used with an oscilloscope, it employs a slightly modified rectifier circuit. See Fig. 3. The basic difference is the much shorter time constant of the filter network. Thus, this probe will not only make available the rectified DC, but also any modulation that the signal may contain.

Peak-To-Peak Probes

The output of an RF probe can be increased by employing a voltage doubler arrangement. See Fig. 4. Two crystal diodes are employed, one conducting during the positive half cycle of the applied wave while the other conducts during the negative half cycle. The input is applied in like measure to each diode; the outputs are in series aiding.

Operation of the circuit is relatively

simple to follow. During the half cycle when terminal A is positive with respect to terminal B, crystal CR1 will conduct and charge capacitor C1 to the polarity indicated. C1 will attain the peak value of this positive half cycle. A DC voltage equal to this peak value will appear across resistor R1, with the top end of R1 negative with respect to the bottom end. During the next half cycle, crystal CR 2 will conduct, charging capacitor C2 to the polarity indicated. This voltage across C2, equal to the peak value of the negative half cycle of the applied voltage, will appear across R2. Polarity of this voltage will make the top end of R2 negative with respect to the bottom end. Since the voltages across R1 and R2 are in series aiding, the output voltage will be equal to the peak-to-peak value of the applied signal.

Low-Capacitance Probes

Low-capacitance probes are employed with an oscilloscope when it is desired to view high-frequency waveforms in high-impedance circuits. For example, TV sync signal tracing. These sync waveforms possess a steep-sided, square-wave form with a good many high-frequency components. If the input of the probe contains a fairly high capacitance, it will load the circuit down and alter the shape of the sync pulses. Thus, instead of seeing the desired pulse, what you will see on the oscilloscope is a distorted version of it, Fig. 5.

The basic circuit of a low-capacity probe is shown in Fig. 6. It contains two components, a small trimmer capacitor with a high-valued resistor shunted across it. If we consider the capacitor first, we see that it is in series with the capacitance of the cable and the input capacitance of the oscilloscope. See Fig. 7. When we place the probe end (and the associated ground lead) across a point in a circuit, C_p and $(C_1 + C_2)$ are in series with each other. The total value of two capacitors in series is less than the smallest one. Equation-wise, this can be expressed as:

$$C_t = \frac{C_p \times (C_1 + C_2)}{C_p + (C_1 + C_2)}$$

[Continued on page 117]



Accredited by the National Home Study Council

good training
doesn't cost . . .
it pays!

How To Get an



FCC License (Commercial)

Get Your FCC License
Quickly

We Guarantee to train you until you receive Your FCC License

Get all 3 FREE

We guarantee
to train you until you receive
Your FCC License
—or your money back

The master Course in Electronics will provide you with the mental tools of the electronics technician and prepare you for a First Class FCC License (Commercial) with a radar endorsement. When you successfully complete the Master Course, if you fail to pass the FCC examination, you will receive a full refund of all tuition payments.


Our Trainees Get Good Jobs

"Investment in training really pays off!"

"I am now employed by the Western Electric Company as an electronic tester. My status as a student of Cleveland Institute was an important factor in my being employed. Knowledge gained through the course has proved amazingly helpful and affords me a feeling of complete confidence."

T. E. Spence, Greensboro, N. C.

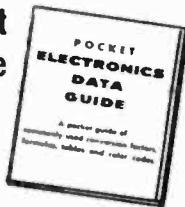Get this handy Pocket
Electronics Data Guide
Free



Puts all the commonly used conversion factors, formulas, tables, and color codes at your fingertips. Yours absolutely free if you mail the coupon in 30 days. No further obligation!

TO GET THIS FREE GIFT, MAIL COUPON Within 30 Days!

Cleveland Institute of Electronics

4900 Euclid Ave., Desk EI-17

Cleveland 3, Ohio



Cleveland Institute of Electronics

4900 Euclid Ave., Desk EI-17, Cleveland 3, Ohio

Please send Free Booklets prepared to help me get ahead in Electronics and a free copy of your "Pocket Electronics Data Guide." I have had training or experience in Electronics as indicated below:

- | | |
|---|---|
| <input type="checkbox"/> Military | <input type="checkbox"/> Broadcasting |
| <input type="checkbox"/> Radio-TV Servicing | <input type="checkbox"/> Home Experimenting |
| <input type="checkbox"/> Manufacturing | <input type="checkbox"/> Telephone Company |
| <input type="checkbox"/> Amateur Radio | <input type="checkbox"/> Other _____ |

In what kind of work are you now engaged?

In what branch of Electronics are you interested?

Name _____ Age _____

Address _____

City _____ Zone _____ State _____

EI-17

Superior's New Model 77

VACUUM TUBE VOLTMETER WITH NEW 6" FULL-VIEW METER

Compare it to any peak-to-peak V. T. V. M.
made by any other manufacturer at any price!

- ✓ Model 77 completely wired and calibrated with accessories (including probe, test leads and portable carrying case) sells for only \$42.50.
- ✓ Model 77 employs a sensitive six inch meter. Extra large meter scale enables us to print all calibrations in large easy-to-read type.
- ✓ Model 77 uses new improved SICO printed circuitry.
- ✓ Model 77 employs a 12AU7 as D.C. amplifier and two 9006's as peak-to-peak voltage rectifiers to assure maximum stability.
- ✓ Model 77 uses a selenium-rectified power supply resulting in less heat and thus reducing possibility of damage or value changes of delicate components.
- ✓ Model 77 meter is virtually burn-out proof. The sensitive 400 microampere meter is isolated from the measuring circuit by a balanced push-pull amplifier.
- ✓ Model 77 uses selected 1% zero temperature coefficient resistors as multipliers. This assures unchanging accurate readings on all ranges.

Specifications

• DC VOLTS — 0 to 3/15/75/150/300/750/1,500 volts at 11 megohms input resistance.
• AC VOLTS (RMS) — 0 to 3/15/75/150/300/750/1,500 volts. • AC VOLTS (Peak to Peak) — 0 to 8/40/200/400/800/2,000 volts. • ELECTRONIC OHMMETER — 0 to 1,000 ohms/10,000 ohms/100,000 ohms/1 megohm/10 megohms/100 megohms/1,000 megohms. • DECIBELS: — 10 db to + 18 db + 10 db to + 38 db. + 30 db to + 58 db. All based on 0 db = .006 watts (6 mw) into a 500 ohm line (1.73v). • ZERO CENTER METER — For discriminator alignment with full scale range of 0 to 1.5/7.5/37.5/75/150/375/750 volts at 11 megohms input resistance.

Model 77—VACUUM TUBE VOLTMETER. . . Total Price . . . \$42.50
Terms: \$12.50 after 10 day trial, then \$6.00 monthly for 5 months if satisfactory. Otherwise return, no explanation necessary.

AS A DC VOLTMETER:

The Model 77 is indispensable in Hi-Fi Amplifier servicing and a must for Black and White and color TV Receiver servicing where circuit loading cannot be tolerated.

AS AN ELECTRONIC OHMMETER:

Because of its wide range of measurement leaky capacitors show up glaringly. Because of its sensitivity and low loading, intermittents are easily found, isolated and repaired.

AS AN AC VOLTMETER:

Measures RMS values if sine wave, and peak-to-peak value if complex wave. Pedestal voltages that determine the "black" level in TV receivers are easily read.

Comes complete with operating instructions, probe leads, and streamlined carrying case. Operates on 110-120 volt 60 cycle. Only..

\$42⁵⁰

RCA RADIATION COUNTER

MADE TO SELL FOR \$150 — OFFERED FOR ONLY \$47⁵⁰
(Much less than cost of Manufacture.)

**INDICATES
RADIOACTIVITY
IN 3 WAYS!**

- 1—BY NEON
- 2—BY PHONE
- 3—BY METER



Endless experiments and discoveries in the new exciting field of nuclear energy are made possible when you acquire this finely built and engineered device. In the past, a rugged counter which was suitable for the prospecting of radioactive ores such as uranium, thorium and radium, was unsuitable for laboratory work due to the inability of combining accuracy with ruggedness. Conversely, a laboratory counter, while being extremely sensitive, could not withstand use in the field where it would be subjected to abuse and abnormally hard knocks. The Model WF-10AWB combines the laboratory and field counter in one rugged instrument. The use of phones and a visible lamp permits the operator greater freedom of operation as he no longer has to keep his eyes on a relatively small indicator.

In the laboratory where determinations of intensity (counts) of a reading are necessary, the WF-10AWB provides sensitivity far surpassing many laboratory counters.

- Employs the extra sensitive 1B85 Bismuth Type Geiger Counter tube. Sensitivity is .05 Roentgens per hour (1 MR/HR=2000 counts per minute).
- Three counting ranges: 0-100/1,000/10,000 counts per minute.
- Handy reset button.
- Ideal for survey work as the complete unit weighs only 5 1/2 lbs.
- Sight and sound indications by neon

- flashes and headphone. Then when an indication is obtained you switch to meter reading for exact measurements.
- Decontamination easy with damp cloth applied to the weatherproofed aluminum case.
- A radioactive specimen is included for instrument checking and experiments.
- Included at no extra charge—U.S. Atomic Energy Commission booklet titled "Prospecting with a Counter."

SPECIFICATIONS

Three counting ranges are available 0-100 counts per minute—used in cosmic ray and extremely low activity determinations. 0-1,000 counts per minute—used for average activity and normal work. 0-10,000 counts per minute—used for tracer and high activity determinations. High accuracy is assured by the handy reset button, located on the front panel, which permits compensation for variations of battery voltages and background count.


A rugged weather-proof aluminum case houses this light economical unit. The batteries will provide over 200 hours of intermittent operation from the two 67 1/2 volt batteries and 50 hours from the three flash light batteries. Comes with complete set of batteries, carrying strap, headphone, radio-active specimen and A.E.C. booklet Only

\$47⁵⁰

RCA Radiation Counter
Total Price . . . \$47.50
Terms: \$11.50 after 10 day trial, then \$6.00 monthly for 6 months if satisfactory. Otherwise return, no explanation necessary.

EXAMINE BEFORE YOU BUY!
USE APPROVAL FORM ON NEXT PAGE

Superior's New Model 70 UTILITY TESTER® FOR REPAIRING ALL ELECTRICAL APPLIANCES and AUTOMOBILE CIRCUITS

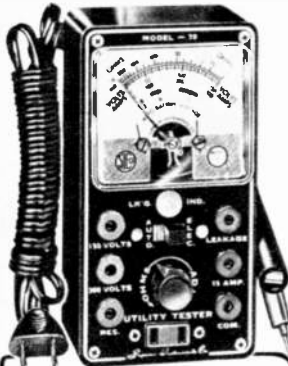

Model 70—UTILITY TESTER
Total Price...\$15.85—
Terms: \$3.85 after 10 day
trial, then \$4.00 monthly for
3 months, if satisfactory.
Otherwise return, no ex-
planation necessary.

As an electrical trouble shooter the Model 70:

- Will test Toasters, Irons, Broilers, Heating Pads, Clocks, Fans, Vacuum Cleaners, Refrigerators, Lamps, Fluorescents, Switches, Thermostats, etc.
- Measures A.C. and D.C. Voltages, A.C. and D.C. Current, Resistances, Leakages, etc.
- Will measure current consumption while the appliance under test is in operation.
- Incorporates a sensitive direct-reading resistance range which will measure all resistances commonly used in electrical appliances, motors, etc.
- Leakage detecting circuit will indicate continuity from zero ohms to 5 megohms (5,000,000 ohms).

As an Automotive Tester the Model 70 will test:

- Both 6 Volt and 12 Volt Storage Batteries • Generators • Starters • Distributors
- Ignition Coils • Regulators • Relays • Circuit Breakers • Cigarette Lighters • Stop Lights
- Condensers • Directional Signal Systems • All Lamps and Bulbs • Fuses
- Heating Systems • Horns • Also will locate poor grounds, breaks in wiring, poor connections, etc.



INCLUDED FREE This 64-page book—practically a condensed course in electricity. Learn by doing.

Just read the following partial list of contents: What is electricity? • Simplified version of Ohms Law • What is wattage? • Simplified wattage charts • How to measure voltage, current, resistance and leakage • How to test all electrical appliances and motors using a simplified trouble-shooting technique.

Model 70 comes complete with 64 page book and test leads

\$15.85
Only

Superior's New Model 82A A truly do-it-yourself type



Model 82A—Tube Tester
Total Price \$36.50
Terms: \$6.50 after 10 day trial, then \$6.00 monthly for 5 months if satisfactory. Otherwise return, no explanation necessary.

TUBE TESTER

TEST ANY TUBE IN 10 SECONDS FLAT!

- 1 Turn the filament selector switch to position specified.
- 2 Insert it into a numbered socket as designated on our chart (over 600 types included).
- 3 Press down the quality button—

THAT'S ALL! Read emission quality direct on bad-good meter scale.

FEATURES:

- Tests over 600 tube types. • Tests OZ4 and other gas-filled tubes. • Employs new 4" meter with sealed air-damping chamber resulting in accurate vibrationless readings. • Use of 22 sockets permits testing all popular tube types and prevents possible obsolescence. • Dual Scale meter permits testing of low current tubes. • 7 and 9 pin straighteners mounted on panel. • All sections of multi-element tubes tested simultaneously. • Ultra-sensitive leakage test circuit will indicate leakage up to 5 megohms.

Production of this Model was delayed a full year pending careful study by Superior's engineering staff of this new method of testing tubes. Don't let the low price mislead you! We claim Model 82A will outperform similar looking units which sell for much more—and as proof, we offer to ship it on our examine before you buy policy.

Model 82A comes housed in handsome, portable Saddle-Stitched Texon case (Picture Tube Adapter available for \$5.50 additional)

Only **\$36.50**

SHIPPED ON APPROVAL NO MONEY WITH ORDER—NO C. O. D.

Try any of the instruments on this or the facing page for 10 days before you buy. If completely satisfied then send down payment and pay balance as indicated on coupon. **No Interest or Finance Charges Added!** If not completely satisfied return unit to us, no explanation necessary.

MOSS ELECTRONIC, INC.

Dept. D-703, 3849 Tenth Ave., New York 34, N. Y.

Please send me the units checked on approval. If completely satisfied I will pay on the terms specified with no interest or finance charges added. Otherwise, I will return after a 10 day trial positively cancelling all further obligation.

Name

Address

City Zone State.....

All prices net, F.O.B., N. Y. C.

- Model 77..... Total Price \$42.50
\$12.50 within 10 days. Balance \$4.00
monthly for 5 months
- RCA RADIATION COUNTER
Total Price \$47.50
\$11.50 within 10 days. Balance \$6.00
monthly for 6 months.
- Model 70..... Total Price \$15.85
\$3.85 within 10 days. Balance \$4.00
monthly for 3 months.
- Model 82A..... Total Price \$36.50
\$6.50 within 10 days. Balance \$6.00
monthly for 5 months.
- Include Model 82A Picture Tube
Adapter at \$5.50

New Tiny Tape Recorder

Continued from page 37

2¼-inch speaker, there is an output socket for attaching an external speaker. The amplifier has six transistors and the unit has a midget-sized ammeter which indicates recording level and also serves as a check on the condition of the battery. Yashica, Inc. is at 234 Fifth Avenue, New York 1, N. Y.

The Japanese Transi-corder TR 100 also has six transistors, but in addition to being battery-operated (9 volts), it has an AC switch so that it can be used with ordinary house current. There is a remote control switch for AC use. Changing the speed from 1⅞ ips to 3¾ ips is accomplished mechanically by simply sliding off an external capstan sheath, thereby reducing the size of the drive capstan (increasing the speed). A tiny but very sensitive meter monitors the recording level and also can be used to read battery voltage. Accessories to the Transi-corder include a small induction coil designed to be hung over the cradle prongs of your telephone. There is no beeper, as required by law, so we tried it out by recording telephone weather reports. The playback was extraordinarily good. Nippon Sound Equipment Co. makes it; it is distributed by Toyo Menka Company, 2 Broadway, New York, New York.

The American manufacturer, Mohawk Business Machines, makes a tiny tape recorder called the Midgetape 300. Similar machines appear under other names, such as Lafayette's "Transi-corder" and the "Vanguard Midget." Depending upon who you buy it from, the price varies from \$189.50 to \$249.50. The main feature of the Midgetape is its weight: Three pounds. It records only at the 1⅞ ips speed and uses special cartridge-enclosed reels. It doesn't have a power rewind nor recording level indicator. There are four transistors in the circuit.

The British-made "Fi-Cord" and the Swiss-made "Stellavox" are very similar. In fact, they were both designed by the same person—Swiss engineer Georges Quellet. The half-track tape-

head was engineered to NARTB specifications. While the Stellavox operates only at 7½ ips, the Fi-Cord also provides the 1⅞ ips speed. Frequency response up to 14,000 cps are claimed for these units. You can record approximately 10 minutes in each direction at 7½ ips. The four 2-volt batteries that power these recorders can be recharged with a small accessory charger. The Fi-Cord is \$330 from Kingdom Products, 514 Broadway, New York, N. Y. The Stellavox sells for \$399 from Electronics Applications, Inc., 194 Richmond Hill Avenue, Stamford, Conn.

Also available from Electronic Applications is the Nagra III, another Swiss instrument that is the superduper granddaddy of all small tape recorders. The price is a clue: \$945. And they're not kidding! It has no less than thirty transistors and operates off several types of batteries, or AC.

The "Hi-Delity" trade name appears on two small tape recorders, the model TR401B and the TR-403. The 401B, which lists for \$159.50, has a single-lever operation for "play," "record" and "rewind." Without a speaker, tapes can be monitored through earphones. An extension speaker costs \$24.95. You get 34 minutes of half-track recording time at 3¾ ips from this four-transistor job. Ten penlight cells (four for the amplifier and six for the motor) make up the power supply.

The model TR-403 (\$199.50) has a built-in speaker, an AC adapter, remote control switch, two speeds (3¾ and 1⅞ ips), and weighs five pounds without leather case. An extension speaker can be plugged in. There are six transistors in the circuit, and all power comes from the same 10 penlight cells as are in the lower priced unit. Both Hi-Delity models are available from Petely Enterprises, Inc., 300 Park Avenue South, New York 10, New York.

The two-speed (1⅞ and 3¾ ips) Steelman "Transitape" weighs eight pounds and handles the standard three-inch tape reels. Equipped with power rewind, it draws its power from 13 Mallory batteries. There are a total of seven transistors in the circuit. List price: \$199.50 from Steelman Phonograph &

Radio Co., Mount Vernon, N. Y. A telephone pickup is included.

Phono-Trix Mark II and Mark III tape recorders are from West Germany. The Mark II (\$79.95) has a sliding switch which controls tape speed from 1-8 ips, while the Mark III (\$99.95) is available in either the 3¼ ips or 1⅞ ips speeds. There is a built-in speaker on both models and both operate from four "D" cell flashlight batteries. A variety of accessories, including an AC adapter, can be had for the Mark III. Matthew Stuart & Company, 353 West 54th Street, New York 19, N. Y., handles these units.

The Austrian-made Stuzzi Magnette is a seven-transistor push-button unit that sells for \$269.50. Featuring two speeds (3¼ and 1⅞ ips), the power source is four Burgess 532 batteries. It is distributed by Ercona Corporation, 16 West 46th Street, New York 36, N. Y.

Reeves Equipment Company makes the "Pocketape," weighing exactly two pounds and small enough to be slipped into a shirt pocket. It is also supplied in three speeds to 7½ ips. Price: \$349.50 from Reeves, 8 Third Avenue, Pelham, N. Y.

Loran Lights the Way

Continued from page 48

used by navigators on shipboard or aircraft performs like an ordinary radio receiver, but delivers the output to a visual indicator rather than to a loud-speaker. It is also designed to receive pulsed signals. The indicator is essentially an "electronic stop-watch" capable of measuring, in microseconds, the difference in times of arrival of the signals from the paired stations. Horizontal traces, or "lines" of light on the screen of a cathode ray oscilloscope form the equivalent of the dial of a watch. A vibrating quartz crystal is the balance wheel, and circuits known as "dividers" or "counters" take the place of gears.

LORAN has proven so accurate and reliable as a navigation aid that it is also being used for speed trials of new ships.

In one of its trial runs, the *SS United*


FIRST TIME . . . a soldering kit with

DUAL HEAT GUN

FOR ONLY

\$795

LIST
Model 8200K

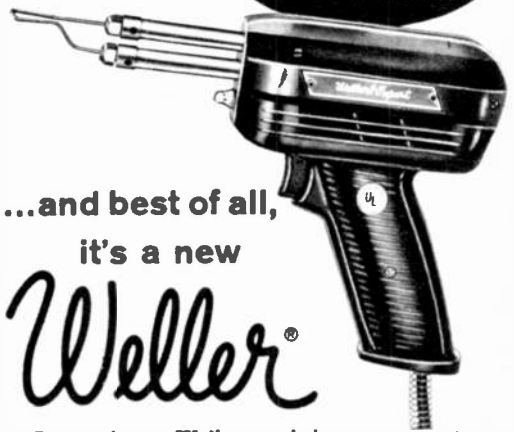

...and best of all,
it's a new

Weller®

Leave it to Weller to bring you greater soldering advances and values! Here's the newest and finest gun made . . . with the versatility of *Dual Heat*. Just touch the trigger for high (125 watt) or low (90 watt) heat as your job requires. Saves time, gives extra convenience for precision soldering. Tip life is also increased because you use high heat only when necessary. New *high efficiency tip*. Instant heat. Spotlight.

Model 8200K is supplied in a kit which includes: New Dual Heat Soldering Gun, cleaning brush, soldering aid and all-purpose solder.

New Single Heat Weller Gun!

New design and superior tip performance at a low price. Single heat—100 watts. Instant heat. Spotlight.

Model 8100B **\$644**
list

These new Weller Guns are on sale now at your Electronic Parts Distributor.



WELLER ELECTRIC CORP. 601 Stone's Crossing Rd., Easton, Pa.

States traveled a 53-mile course in the Atlantic established along the baseline of the LORAN pair of Nantucket and Cape Hatteras. The maximum error for the speed determination in the run was figured to be less than one fourth of one percent!

Go aboard almost any sizeable fishing boat today and you will find a LORAN receiver. Trawler nets are towed for approximately an hour and a half, then pulled onto the deck and emptied. If it is a good haul the skipper will want to travel exactly the same path again. And, with LORAN, he can. By taking a fix at the beginning of the tow, and another fix when the nets are hauled in, the exact run can be plotted on a chart and the boat can follow the same course.

Air-France, after several years of experimenting, reports the successful use of multi-reflection signals from Nantucket and Cape Hatteras on its regular flights between Dakar and Recife in Africa. That means that transmission distances of more than 3,500 nautical miles are involved. ⚙

Flash Your Photofloods

Continued from page 46

close (or the external switch is pressed). Since there are "holding" contacts on the relays, the lights will stay on full brilliance until released by the "Reset" button, and if the shutter opens 20 milliseconds after contact is made, the lights will be up. This unit cannot be used with "zero" delay shutters at high speeds of 1/100 second (10 milliseconds) or above, but can be used at slower speeds, such as 1/10 or 1/25 second, if compensation is made on the exposure meter.

The unit provides for up to four lights (either No. 1 or No. 2 photofloods), and has individual switches (SW1, SW2, SW3 & SW4), for each light.

When the unit is turned on, and the four individual switches are in the "Dim" position, voltage for the bulbs is fed through the upper side of the relay contacts and through a high wattage resistance. The cheapest form of such resistance is the ordinary screw-in type

of heating element, one of which is used for 1 or 2 bulbs, and two in series for 3 or 4 bulbs. The switching of these resistances is done with the SW6.

Then the two shutter synchronizer contacts (or the solenoid release button) close, the relay is energized by the battery voltage and the resistance is bypassed allowing full voltage to reach the bulbs. One set of relay contacts continues to supply battery voltage to the relay coils, holding the relays closed until the voltage is disconnected by pressing the "Reset" button (SW7). In the case of using a solenoid, this feature is eliminated since the relay control is manual and can be held closed as long as desired.

The switching of this latter function and the selection on control sockets is done by the "Sync Selector" switch (SW8). The "Power" switch (SW5) closes the circuit of both the battery voltage and line voltage.

All wiring in the lamp circuits is done with heavy-gauge wire, not less than No. 12, and the switches used should be heavy duty.

If it is ever contemplated that more than two No. 2 photoflood bulbs (or three No. 1 bulbs) are to be used, it might be well to provide for separate line cords; you'll be drawing over 20 amps! Keep in mind that household fuses are usually 15 amperes and a 20 ampere circuit is needed.

When using the unit, plug all lamps into place (with the individual bulb switches on "Dim"), set the "Lamp" switch, and plug the unit into an outlet before turning the "Power" switch on. Any or all lamps can then be turned to "Bright" by individual switches to adjust the lights, check exposure, focus, etc. Then turn the lamps back to "Dim" and let the subject relax. As soon as the exposure is made, reduce the glare by pressing the "Reset" button (if using a synchronized shutter) or releasing the "Solenoid Release" button, if using a solenoid.

If substantial use of the unit is contemplated, a larger size battery should be used, as the relay and solenoid drain is fairly heavy, and the relay action slows down as the battery ages. ⚙

Milt Kiver on Probes

Continued from page 110

(We are considering C1 and C2 as a single capacitor equal to the sum of their values.) If the probe capacitance is 10 mmfd and (C1 + C2) is 100 mmfd, the total capacitance becomes:

$$C_t = \frac{10 \times 100}{10 + 100} = \frac{1000}{110}$$

$$= 9.1 \text{ mmfd}$$

Thus, the input capacity of the oscilloscope and the low-capacity probe is reduced by a factor somewhat greater than 10. If, now, we also shunt Cp by a resistance which raises the total series input resistance to a value 10 times its former value, then we have increased this item by a factor of 10, as well. This is done by R1, in Fig. 6.

The lowered input capacitance and increased resistance is not obtained without a penalty, however. In this case, the signal reaching the oscilloscope input is reduced in the same proportion. Generally, however, the circuits where these probes are employed are high signal level circuits.

Low-capacity probes frequently employ a variable trimmer capacitor to enable the user to adjust the frequency characteristics of the probe to match the frequency compensating network at the scope input.

To obtain maximum usage from the low-capacity probe, the input attenuator of the oscilloscope must be frequency-compensated in each position of this switch. Most modern oscilloscopes have a satisfactorily constant input impedance on the X1, X10, X100, and X1000 positions. ☺

EI Build-It Course-6

Continued from page 87

adding RF amplifier stages, but up go the cost and complexity. A radical increase in signal voltage on the control grid, with no sacrifice to the circuit's simplicity can be obtained.



The Beautiful Schober CONSOLETTTE

—only small organ with two full 61-note keyboards and 22 stops. Requires only 2x3 1/2" floor space! Commercial value approximately \$1600 or more.

BUILD THIS SUPERB Schober ORGAN FROM SIMPLE KITS and save over 50%!

Give Your Family A Lifetime of Musical Joy With A Magnificent Schober Electronic Organ!

Now you can build the brilliant, full-range Schober CONSOLETTTE or the larger CONCERT MODEL with simple hand tools! No skills are needed; no woodworking necessary. Just assemble clearly marked electronic parts guided by step-by-step instructions. You build from kits, as fast or as slowly as you please... at home, in your spare time — with a small table serving as your entire work shop.

THE GREAT CONCERT MODEL meets specifications of American Guild of Organists

ment you assemble is as fine, and technically perfect, as a commercial organ... yet you save over 50% on quality electronic parts, high-priced labor, usual store mark-up!

Free Booklet

Send for 16-page booklet in full color describing Schober organs you may build for home, church or school, plus articles on how easy it is to build your own organ and how pleasant it is to learn to play. Also available is 10" LP demonstration record (price \$2.00 — refundable on first order). Send for literature. No obligation and no salesman will call.

Pay As You Build!

Start building your organ at once, investing just \$18.94! The superb instru-

Mail This Coupon For FREE Schober Literature And Hi-Fi Demonstration Record TODAY!



The Schober Organ Corp., Dept. EI-1
2248 Broadway, New York 24, N. Y.

- Please send me FREE full-color booklet and other literature on the Schober organs.
- Please send me the 10" hi-fi Schober demonstration record. I enclose \$2.00 (refundable on receipt of my first kit order).

Name.....

Address.....

City..... Zone... State.....

Regeneration provides the answer. Recall that the plate circuit contains an amplified version (though still not strong enough) of the weak grid signal. If some of this voltage could be "stolen" and returned back to the grid, the original signal would be greatly reinforced.

The route of the feedback signal is shown in the full-page theory diagram. Trace it through and the derivation of the word "regenerative" should become apparent. The original signal is "generated over again."

Note that the screen grid of the tube is used as the feedback source, not the plate circuit as previously explained. The reason is mainly one of control. The screen grid attracts electrons by virtue of its high positive voltage. It's true that most electrons will fly through spaces in the screen on their way to the plate, but sufficient numbers flow through its wires to supply feedback. It is a simple matter to regulate the screen's positive charge by a potentiometer. An important advantage is that the screen current is small compared to plate current.

For the "tickler" (in the theory diagram) to feed back signals properly, its turns must be *phased*. This consists of winding its coil in the same direction on the coil form as the tuning coil. Otherwise its magnetic field will oppose—and *reduce* the voltage in the tuning coil. This is opposite to the desired effect of boosting the input signals (negative, rather than positive feedback).

Varying the voltage on the tube's screen grid controls the amount of feedback and, consequently, the gain of the tube. But—once the regeneration control is advanced beyond a critical point, the tube goes into oscillation. A sustained circulation of current travels from tuning coil to screen, feedback coil and back to the tuning coil. This adheres to a fundamental prerequisite for oscillators; when positive feedback is great enough to overcome resistances in the circuit, the stage self-oscillates. The frequency of the oscillation is determined by the coil and variable tuning capacitor.

Oscillation easily occurs with no external signals being received. Random

electrons flowing in the tube can trigger it off.

With the tube in this condition, what happens when a received signal finds its way down the antenna and on to the control grid? It encounters the oscillation frequency and the two signals mix. It is the difference between the two that is heard in the earphones. This is the basis for code reception in the regenerative detector.

Construction of the regenerative detector may be done in one of two ways. It can be designed to be compatible with the other plug-in projects already described in this series, or operated solely in conjunction with a source of power. Voltages needed: 6.3 volts AC and 250 volts DC. The unit shown in the illustrations, as it is set up, will not physically fit into the space formerly occupied by the AM or FM tuner; a cable running to the power supply was used instead. However, with some modification it could be made to fit into place and not be an "outboard" unit. Use an 8-pin plug (same as PL7 in the Parts List) on the side of the chassis that goes to the receptacle on the preamplifier, and mount PL7 so it matches the receptacle on the power supply. Run a pair of leads between pins 6 and 8 on the two plugs to complete the AC primary switch connection. This is the reason pins 6 and 8 are jumped together on the outboard model. It serves to complete the power supply circuit.

Another change must be made for the full plug-in feature. The input and output terminals must be mounted on the top surface of the chassis.

While winding the coil, remember that the turns must be in the same direction, or the feedback will not be positive. One expedient is to hold the coil form in the left hand, with its prongs always pointing to the left as the turns are wound. As each winding is completed, make a hole in the plastic with a sharp instrument (at the end of the last turn), poke the wire through, and route it to its associated pin. Note that two of the coil leads will go to pin 4, and thus may run through the same hole in the coil form.

Keep the antenna fairly long, starting out with a length of wire about thirty feet long.

If dead spots occur as the tuning capacitor is rotated, the antenna coupling is probably not adjusted correctly. This may be changed in two ways. First, alter the spacing between the antenna winding (L3C) and the tuning coil (L3B). The amount of turns may be changed also.

Don't solder the coil wires to the pins in the coil form until the set is operating properly. As each winding is completed, scrape the enamel insulation on the wire, push it through its coil form pin, and bend it back. The coil may then be inserted into its socket with its wires making proper contact. If changes are necessary, they can be made rapidly, without the need for repeated soldering. Coil dope may be applied to the turns of wire to hold them in place.

The secret of obtaining good operation with this receiver is proper use of the regeneration control. For 'phone reception, the most sensitive point is just before oscillation occurs. Oscillation starts with a characteristic "click" which becomes a hissing sound as the control is advanced. When code stations are tuned in, the control should be set to the point where oscillation just begins.

SWL Antenna Tuner

Continued from page 42

for holding it in place securely. By turning the form counter-clockwise with your left hand you can guide the wire with your right. When the first five turns have been wound, stop and put a twist in the wire, forming an "eyelet." The second tap is 12 turns from the beginning, etc.

Coat the finished coil with dope and with razor blade, carefully scrape the enamel insulation off each coil tap. It is helpful to tin each one with a coating of solder. Drill two small 6-32 holes in each end of the form for mounting the form to the case. Wire the unit as shown in the drawings and photos.

BIG MONEY IN THE 4 CORNERS OF THE WORLD!

in TELEVISION, RADIO,
ELECTRONICS, RADAR, SONAR

**CHRISTY OFFERS
COMPLETE TRAINING!**

Investigate the Christy Complete Course. Why be satisfied with less? CTS Shop Method Home Training makes learning easy. You learn by working with actual equipment. You receive Comprehensive training from the start. Can EARN AS YOU LEARN. You become qualified to open your own Electronics Repair business or to gain high pay as a TV, Radio, Electronics, etc. Technician.

19 TRAINING KITS INCLUDED!

You receive a Multi-Tester, Oscillator, Signal Tracer, Oscilloscope, Signal Generator, Electronic Timer, Regenerative Radio, 24" TV set (optional) and other valuable testing equipment. FREE BOOKS and TWO FREE LESSONS yours for the asking! No obligation.

CHRISTY TRADES SCHOOL

Dept. T-813, 3214 W. Lawrence Ave.,
Chicago 25, Ill.



CHRISTY TRADES SCHOOL, Dept. T-813
3214 W. Lawrence Ave., Chicago 25, Ill.

Please send me the 3 FREE BOOKS and Special Form for
PAYING LATER from EARNINGS MADE WHILE LEARNING.

NAME _____ AGE _____

ADDRESS _____

CITY _____ ZONE _____ STATE _____



FREE!
350 BIG PAGES
OF BARGAINS
LIKE THIS



24 36 JUMBO PAGES
MONTH AFTER MONTH

- Hi-Fi Records
- LP Records
- Power Tools
- Optical Goods
- Test Equipment
- Hi-Fi Components

STEREO AMPLIFIER \$10.95
LOWEST PRICE EVER

For converting mono phones to stereo, for "basic" stereo systems. Use with crystal or ceramic cartridges, 5 1/2" x 5" x 4 1/2" deep — fits anywhere! 5 lbs.

Because Radio Shack has millions of mail order customers, Radio Shack gets first offerings from manufacturers needing cash, first refusal on closeouts, first choice on new items! All these opportunities are passed along to Radio Shack customers in our Bargain Bulletins and Record Flyers. To be "in the know", just fill in and mail the coupon!

RADIO SHACK Corporation
730 Commonwealth Ave., Boston 17, Mass.

Please send me

- FREE Bargain Bulletins for 12 Months DEPT 2 P
- FREE Record Flyers for 12 Months
- 1960 Electronic Buying Guide @ 35c Check
- Stereo-3 amplifier, #90L021, of \$10.95 M.O.
- C.O.D.

Name _____

Street _____

City _____ Zone _____ State _____



35c
NOW AVAILABLE!
1960 GUIDE
TO ELECTRONIC
PARTS BUYING
300 pages, 8 1/2 x 11, illustrated handbook. Articles, engineering data plus buying guide. Over 40,000 items. Use coupon to order today!

The Fuel Cell

Continued from page 83

cations. "Peaking" is the major application for Bacon's "Hydrox" cell. The cells would help provide that "extra" electricity demanded of central power stations during peak periods. In off hours, the central stations would manufacture hydrogen and oxygen to fuel the cells.

The General Electric fuel cell requires only simple, compact controls and would be suitable for something as small as a portable television set. Since all fuel cells produce direct current, the TV set could be made without a rectifier circuit—just as though it were powered by conventional batteries.

The Allis-Chalmers fuel cell runs on air and propane. Any cell that can use air instead of expensive bottled oxygen has obvious advantages. An English competitor to the Hydrox cell known as the "carbox" cell also runs on air instead of oxygen. The other fuel component can be natural gas, manufactured gas, or vaporized kerosene.

The fuel cell does very well at steady, long-time jobs. Engineers with a leading American oil company have calculated that a 36-horsepower fuel cell could equal the performance of a 300-hp conventional engine in a car weighing as much as an Oldsmobile. DeSoto engineers have already made a model of a car powered by fuel cells. The electricity would feed an electric motor in each wheel. A four-wheel drive like this would offer very smooth acceleration.

Not only would no transmission be required, but the electric motors could be switched to act as generators, feeding the electricity generated by the braking action into a bank of resistors (which could heat the car)! Electric trains work on the same "dynamic braking" system.


One factor that would affect the rate of commercialization of the fuel cell is its competition. The strongest competition in the "no moving parts" category is thermoelectric generation (see "Thermoelectricity: A Look Into the Future," *Electronics Illustrated*, Sept. 1959).

Thermoelectric devices require heat to generate electricity. This means that

Don't Miss this Fabulous Contest!

1st Grand Prize: a Mercedes-Benz

300SL
Sports Roadster
worth
\$10,950

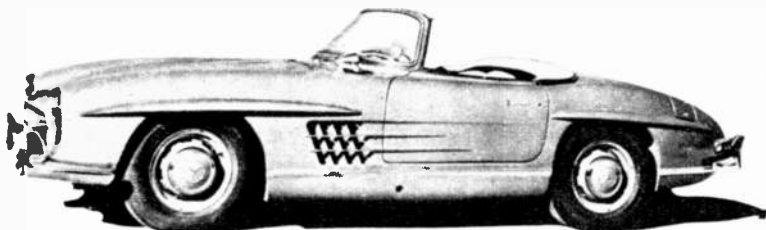

40 other exciting automobiles also being given away in

TRUE'S \$100,000 GLAMOR CAR CONTEST

ENTER NOW!

Get TRUE, the Man's Magazine, at your newsdealer today

thermoelectric generators could go into all sorts of waste-heat situations where the fuel cell does not apply.

Fuel cells are much more efficient than thermoelectric generators, running as high as 70 percent conversion of energy compared to a high of 10 percent for thermoelectricity.

In view of all the new ways of making electricity (don't forget the solar cell), it would be rash to predict that the fuel cell will be the star of the younger generation of power sources. With each new method finding its own best applications, there is little doubt that the fuel cell will gain an important place. *By E. M. Delman*

Tweeter Globe

Continued from page 32

trick here is to bend back the mounting flange lip of the speaker in order that the speaker can better accommodate the internal curvature of the globe. After the mounting holes have been laid out and drilled, the globe's rough paper edges of the cutouts and holes should be sanded smooth.

Sofar as impedance match is concerned, standard formulas for figuring impedance are employed. In this case, some surplus tweeters were used having a voice coil impedance of 3.2 ohms. A set of five and four were connected in series, giving an impedance string of 16 ohms and 12.8 ohms. These two strings were then connected in parallel, resulting in an approximate impedance figure of about 7 ohms. Any set of small cone tweeters will do. A reasonably priced unit is the Jensen P 35 VH (\$4.00) or Lafayette SK100 (2 for \$5.95—bracket must be removed). Consult the Olson Radio Warehouse or Allied Radio catalogs for others.

After the unit has been assembled and wired, the two halves are put together and the globe is mounted back on its stand. A 1/2" to 1" masking tape is used to bind the two halves together. If you desire to paint a new color, save tweeter cutouts to use as masks while painting with one of the popular aerosol spray cans.

SHOOT TV TROUBLE FAST

With H. G. Cisin's Copyrighted RAPID "TV TROUBLE SHOOTING METHOD"

Without experience or knowledge, this guaranteed new method of servicing TV sets enables you to DIAGNOSE TV troubles as rapidly as an expert. NO THEORY—NO MATH—you can locate all faults in record-breaking time regardless of make or model. "TV TROUBLE SHOOTING METHOD" is the most valuable aid to TV servicing ever written. Be a TV Trouble Diagnostician. Increase your present earnings. Open your own Profitable Business or get a high-paying skilled job.

It's all in this book . . .

Nothing more to Pay—nothing else to Buy

Alphabetically listed are 85 picture troubles, over 58 raster and 17 sound troubles. By this unique copyrighted method you know EXACTLY WHERE the trouble is; plus step-by-step instructions, including 69 RAPID CHECKS, help to find faulty part.

IS IMPORTANT PRELIMINARY CHECKS NEED NO INSTRUMENTS! (Of the 69 Rapid Checks, OVER 45 ALSO REQUIRE NO INSTRUMENTS!) Rapid checks include emergency checks for distorted pictures, defective tubes including PIX tube, plus 57 others. ALL EXPLAINED IN SIMPLE LANGUAGE, PERFORMED WITHOUT INSTRUMENTS. MANY CHECKS USE THE PICTURE TUBE AS A GUIDE.

H. G. Cisin, the author, is the inventor of the AC/DC midjet radio. He licenses RCA, AT&T, etc. He has also trained thousands of technicians now owning their own prosperous TV service organizations or holding highly paid TV positions. His years of experience are embodied in this remarkable new book.

Guaranteed Money Back in 5 Days if Not Satisfied!

ABSOLUTELY FREE with each order: Your choice of Cisin's newest books: BASIC ELECTRICITY—Vol. 1 or TV-RADIO TUBE SUBSTITUTION GUIDE. These sell for 50c ea. ACT NOW—get 2 books postpaid at cost of only one!

\$1 Post-paid

RUSH COUPON NOW!

H. G. Cisin, Consulting Engineer—Dept. EL-11
Amagansett, N. Y.
Enclosed find \$1. Rush Trouble Shooting Method and free book marked above (if not marked Basic Elec. will be sent).
(1) Send all 2 books. Enclosed find \$1.50

Name _____
Address _____
City _____ Zone _____ State _____



Olson



FREE

Fill in coupon for a FREE One Year Subscription to OLSON RADIO'S Fantastic Bargain Packed Catalog — Unheard of LOW, LOW, WHOLESALE PRICES on Brand Name Speakers, Changers, Tubes, Tools, Hi-Fi's, Stereo Amps, Tuners, and other Bargains.

NAME _____
ADDRESS _____
CITY _____ ZONE _____ STATE _____

If you have a friend interested in electronics send his name and address for a FREE subscription also.

OLSON RADIO CORPORATION

404 Forge Street
Akron 8, Ohio

All About Ham Nets

Continued from page 63

quested to stand by or move to another frequency while the net is in session."

He then invites net members to "report in," stating their location, any messages they have to send (or "traffic on the hook"). This "reporting in" may be at random, by alphabetical or pre-arranged order, or by roll call.

On CW nets the procedure is similar, except that abbreviations are used because it takes longer to say things via CW than by voice. The CW net control might send, for example: "PN (Podunk Net) PN PN DE (from) K2ABC K2ABC K2ABC QNN (net control station) QNZ (adjust your frequency to mine) QND (the net is directed) QNI (stations report into the net) QNA (by prearranged order) K (go ahead).

Long ago amateurs discovered that they could be useful in providing emergency communications during floods, fires, storms, and explosions which would wipe out telephone and telegraph lines, isolating communities. A ham or two in the stricken area would crank up their rigs from batteries or gasoline generators and establish a communication with the outside world. As this kind of thing became more frequent, the amateurs decided that it could be done more effectively if they were prepared and trained for it.

So about 25 years ago the ARRL organized the Amateur Radio Emergency Corps and encouraged amateurs to form local groups, prepare equipment, lay plans and conduct operator training for this specific purpose. Today there are about 1800 amateur Emergency Coordinators and over 40,000 amateurs "signed up" in the Emergency Corps.

Radio amateurs in this country can do something that amateurs in most countries are forbidden to do: handle messages for third parties. What kind of messages? Why, any kind at all, just so they don't get paid for it. They are usually written and handled in a standard amateur message form, not unlike the Western Union form. These messages are called "traffic," hence the nets

that handle them are called "traffic nets." The idea is to get the message from its point of origin to its destination in the least possible time by passing it from one amateur to another.

Traffic nets are generally well organized and some of them are set up in "systems." One such system, sponsored by ARRL, is called the National Traffic System and consists of about 100 nets working together in chains covering the entire U.S., its possessions and Canada. In emergencies, these traffic nets and systems are often the means for handling important point-to-point traffic.

In a sense, the above nets are training nets. Whatever their primary purpose, a great part of it is in getting trained to do a job.

Newcomers to the amateur ranks via the Novice license need training, especially in Morse code. The Novice speed requirement is only five words per minute. You can't handle much communication at that speed, hence the purposes of many Novice nets are to increase code speed and teach net procedure.

Sometimes a group of amateurs with something in common will get together in a net. Doctors, dentists, religious groups, engineers, pilots, etc., have been known to form nets. A year or so ago a group of doctors formed a net to discuss latest medical developments. Teenagers discuss rock 'n roll, scouting, sports, television shows (real crazy, dad!). The YLs have their own nationwide fraternal organization, the Young Ladies Radio League (YLRL) and have a number of nets consisting strictly of members of their own sex (no men allowed), such as the Ironing Board Net, the Nylon Net and the Tangle Net.

A few groups operate just for the sheer pleasure of getting to know each other. Usually started quite spontaneously, they might call themselves the Gum-Beaters Net, the Idiots Net, or the Hot Air Net. No telling what you might hear them talking about.

Most nets are deliberately set up by responsible amateurs for a specific purpose, usually emergency preparedness or traffic handling. These hams are bent on doing something useful with their hobby. ♀

ONE CENT SALE

BUY ONE AT OUR REGULAR LOW PRICE AND GET THE SECOND FOR ONLY 1¢ MORE

CITIZENS BAND TRANSMITTER (27 MC) chassis complete with crystal. \$12.49 each, two for \$12.50.

TRANSMITTER similar to above but with 5 watt RF stage instead of 1 watt. \$14.99 each, two for \$15.00.

CITIZENS BAND RECEIVER chassis tunable through all 22 channels. Complete with audio amplifier. \$9.99 each, two for \$10.00.

AMATEUR BAND RECEIVER (144-148 MC) chassis with dual VHF triodes for walkie-talkie radiophone. \$9.99 each, two for \$10.00.

RECEIVER TRANSFORMER: Mike to grid input and plate to low impedance headphone output. Good for telephone handsets. \$1.99 pair, two for \$2.00.

TELEPHONE HANDBSET with push-to-talk switch. \$5.99 each, two for \$6.00.

MICROPHONE High output 200 ohm carbon with terminal lugs. \$1.49 each, two for \$1.50.

COILED CORD 4 conductor 11" telephone cord. Extends to over 4 ft. .99 each, two for \$1.00.

KIT OF PARTS for AM-FM VHF radio receiver. Tunable from 80-200 mc. which includes U. S. satellite frequencies. \$6.99 each, two for \$7.00.

TRANSISTOR AUDIO AMPLIFIER gives 50X voltage gain on low level signals. Operates on 1½ volts. \$3.99 each, two for \$4.00.

CONVERTER (crystal controlled) for 27 MC Citizens Band. Adapts any standard broadcast radio to 27 MC band. Tunes all 22 channels. Complete with tubes and crystal. \$14.99 each, 2 for \$15.00.

TRANSMITTER CRYSTALS in holders. Assorted frequencies for experimenters. Bag of 10 only \$1.49. two bags for \$1.50.

ALL MERCHANDISE GUARANTEED

Limited Quantity—No Literature or Catalog

Remit in full, include sufficient postage. No C.O.D.'s.

VANGUARD ELECTRONIC LABS. Box 12-EL2
Hollis 23, N. Y.



Fires both .22 short & long ammo. This sensational NEW 6-shot Rosco Vest Pocket .22 revolver is a tremendous value at 3 times its price. Made in W. Germany, it is a tight, well-made, exceedingly accurate handgun. Fires easy-to-get Win., Rem. Western & Peters .22 Long & Short ammo. Features side gate loading, triaquer adjustment, screw-in ejector rod. Has STEEL RIFLED BARREL with blade front sights. Easy and fun to shoot. Terrific for target shooting, varmint hunting or as a home defense weapon. Only \$12.95. Leather holster \$2.25. 100 rds. of .22 short ball ammo only \$1. Shipped F.O.B., Los Angeles express charges collect. Send cash, check or M.O. COD's require \$7.50 deposit. Satisfaction guaranteed. **Purchasers must be 18 years old.** Res. of L. A. & vicinity, please purchase at our store.

SEAPORT TRADERS, INC., Dept. EI-2
1221 S. Grand Ave. Los Angeles 15, Calif.

RCA Voltohmyst Kit

Continued from page 58

This model differs somewhat from other kit-packaged VTVM's. More components specifically designed for insertion into a printed circuit board are included; the filter capacitor, selenium rectifier and of most interest, the three calibrating potentiometers. Note in the photo how this item plugs into a series of holes in the printed board, thereby eliminating the usual wiring between nine lugs and the rest of the board.

The format of the step-by-step instructions yields another difference between this model and other kits. Instead of the customary booklet, one large sheet contains the construction data.

All steps in construction went smoothly, totaling about eight hours. A supplementary booklet urges the beginner to solder properly and suggests the use of fine sandpaper for cleaning the copper foil on the printed circuit board. Solder will flow much more readily on a shiny surface uncontaminated by oxides. Steel wool will serve as admirably as sandpaper.

Excessive heat applied to the precision resistors can radically change their value and upset the accuracy of the meter. Use a heat sink; pliers that grasp the lead between the resistor and the soldering iron. Hold them there several seconds while the joint cools.

The wired kit is calibrated with the assistance of the small battery used in the ohmmeter section of the instrument. It's a simple procedure if no error in assembly has occurred. Rough calibration is done as soon as the unit has been completed, while more accurate settings are possible after the tubes have aged for two days. Have no qualm about leaving the unit on for that period of time. In a well-designed piece of equipment, the tubes last longer if left glowing than when periodically turned on and off.

Long a popular test instrument in its factory-wired version, the Voltohmyst should prove equally as durable in kit form. In our laboratory tests it proved simple to use and accurate. We rate it as a Good Buy. —

Brainy Man Builds Better Brains

Continued from page 103

built computer that can remember what it is taught and will try to make human-like decisions on a practical level. Pask is of the opinion that our complex industrial society requires semi-human machines capable of teaching humans intricacies of other semi-human machines.

Eucrates I and a special companion device called "The Teacher," can be set up to interview a job applicant or to teach skills such as operating radar equipment, typewriting, piloting aircraft, driving cars or playing a musical instrument. By asking a series of questions and outlining situations that may arise, the device, in effect, forces the interviewee or the student to make a decision. If the student makes a wrong decision, signs of electronic emotion—equivalent to bursting into tears—are displayed. The computer-teacher then eases up on the student.

Pask, whose talents range from painting in oils (a bedroom wall mural), to geology, medicine, psychology, music, logic and writing poetry, first became interested in electronics while studying the rusty, grotesque slag heaps and old machinery scattered around the deserted lead mines of Wales.

In 1950, Pask teamed with physicist Bobbie McKinnon Wood and set up their own business, Systems Research Ltd., which aims at bringing British and world automation up to the highest possible standards. Pask lives at Number 5, Jordan's Yard, just behind St. John's College, Cambridge, England.

Save 1/2 on New ACCORDIONS



IMPORTER-TO-YOU PRICES!
over 40 new models from Italy!
5 DAY FREE TRIAL

Buy on EASY TERMS!

Small Down Payment!
Low as \$9.90 Monthly!

All Famous Makes!

Get in on these sensational values in world's finest Italian-made accordions! Play most popular instrument of all—for fun, leadership and profit! 40 newest models of glorious tone and breath-taking beauty offered at the **Net price!** Buy direct from world's largest dealer. Small down payment; easiest terms on balance. Extra bonus gifts **FREE!** if you buy during sale. Trade-ins accepted. Try before you buy on **FREE, 5-day No-Risk Plan.** Satisfaction guaranteed or money back. Double guarantee!

RUSH COUPON TODAY!
See how easily you can now own and play a fine accordion. Rush coupon now for big new **COLOR Catalogs** and **Low Discount Prices... ALL FREE!** No obligation. Write to:

Accordion Manufacturers & Wholesalers Outlet, Dept. EL-20
2003 W. Chicago Ave., Chicago 22, Ill.

FREE BONUS GIFTS

for promptness
• E-Z Lessons
• Music Stand
• Deluxe Case
• other gifts, too!

MONEY BACK GUARANTEE

FREE
COLOR CATALOGS
and low discount prices

Send **FREE Color Catalogs** and low discount prices.

NAME.....

ADDRESS.....

CITY..... ZONE..... STATE.....

Check here if you have accordion.

Accordion Manufacturers & Wholesalers Outlet, Dept. EL-20
2003 W. Chicago Ave., Chicago 22, Ill.



HELP yourself to better service from your postal service by including postal zone numbers on all correspondence.

Don't forget to include your own postal zone number in your own return address.


Postal zoning helps your post office give you better service.


.22 CAL. NEW 7 SHOT REPEATER AUTOMATIC

The skilled hand of the German gunsmith is responsible for this .22 caliber 7 shot repeater automatic with self-ejecting empty shells. Just 4 inches long, fits easily into pocket or purse. Ideal for sporting events, stage use (not available to Calif. residents). Not a lethal weapon. Comes for \$6.95 from

BEST VALUES CO.

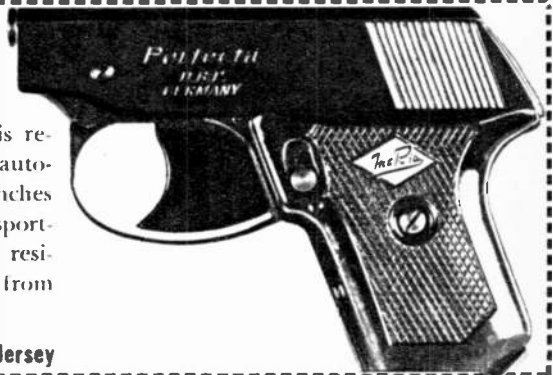Dept. F-84, 403 Market St., Newark, New Jersey



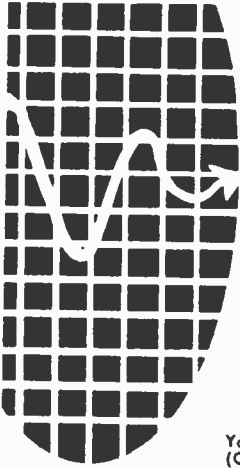

ELECTRONICS ILLUSTRATED

Classified Ads

Your advertisement can reach this mail-buying audience for only 35¢ per word . . . payable in advance (Check or M.O. please) . . . minimum 10 words. Closing dates are the 20th of 3rd preceding month i.e. copy for the May issue must be in our office by February 20th. Mail to **ELECTRONICS ILLUSTRATED**, 67 West 44th St., New York 36, N. Y. Word count: Zone number free. Figure one word: Name of state (New Jersey), name of city (New York); sets of characters as in key (14-D); also abbreviations as 35MM, 8x10, D.C., A.C.

SAVE MONEY • ORDER BY MAIL

• • • FOR SALE

MONEY SAVING Prices on tubes, TV, Radio, Transmitting and Industrial Types. New, 1st quality, guaranteed. Top name brands only. Government surplus and commercial test, lab and communications equipment in stock. Sell us your excess tubes and equipment. Unused, clean tubes of all types wanted. Send specific details in first letter. Write for "Green Sheet" catalog 25¢. Barry Electronics Corp., 512 Broadway, (Dept. E1.), WA 5-7000, New York 12, N. Y.

GOVERNMENT SELLS: Surplus Electronics; Test Equipment; Oscilloscopes; Transceivers; Jeeps; Boats; Aircrafts; Misc.—Send for U. S. Depot Directory & Procedure \$1.00. "Government Surplus Sales," Box 425-EL, Nanuet, N. Y.

78 R.P.M. RECORDINGS. Many types. Free lists. Collections bought, P.O.B. 155(EL), Verona, N. J.

• • • PRINTING, MULTIGRAPHING, MIMEOGRAPHING

DIGNIFIED BUSINESS Cards yet inexpensive—Samples. Woerndel, 441AK West 24th, Houston, Texas.

• • • BUSINESS OPPORTUNITIES

MAKE \$5,000-\$10,000 YEARLY at home, in respectable field. Future growth unlimited! No experience necessary, no public contact, nothing to grow or make. Free expert guidance helps you achieve financial success. Rush name for Free, Complete Plan! Columbia Enterprises, 9268-EL Piney Branch Road, Silver Spring, Maryland.

GROW MUSHROOMS. Cellar, shed and outdoors. Spare, full time, year round. We pay \$4.50 lb. dried. We have 29,000 customers. Free Book. Mushrooms, Dept. 315, 2954 Admiral Way, Seattle, Wash.

VENDING MACHINES—No selling. Operate a route of coin machines and earn high profits. 32-page catalog free! Parkway Machine Corp., Dept. 33, 715 Ensor St., Baltimore 2, Md.

• • • EMPLOYMENT OPPORTUNITIES

PRINTING - ADVERTISING SALESMEN. Excellent moneymaking sideline selling Decalcomania Name Plates. Advertising Specialties. Sign letters, Automobile initials. Free Samples. "Ralco"-E1, Box L, Boston 19, Mass.

• • • HI-FI

UNUSUAL BUDGET Values. Tape recorders, tapes and Hi-Fi components. Send for package quotations and free catalogue. Budget Hi-Fi Distributors, 83-06 Victor Ave., Elmhurst, N. Y.

PHONOGRAPH RECORDS cheap, post-paid. Catalogue. Paramount, Box 2026-K, Pine Castle, Fla.

• • • TAPE RECORDERS

TAPE RECORDERS, recording tape, Bell tape decks, Hi-Fi equipment, Norelco speakers. We Will Not Be Undersold! Send for our discount catalog and see why! Commissioned Electronics, 1776 Columbia Road, Washington, D. C.

TAPE RECORDERS, Hi-Fi components, Sleep Learning Equipment, tapes. Unusual values. Free catalog. Dressner 69-02 Z 174 St., Flushing 65, N. Y.

RENT STEREO Tapes—over 900 different — all major labels — free catalog. Stereo-Parti, 1608-J Centinela Ave., Inglewood 3, California.

HI-FI, RECORDERS. Free Wholesale Catalogue. Carston, 125-G East 88, N. Y. C. 28.

• • • RADIO & TV

DIAGRAMS FOR repairing radios, amplifiers, \$1.00; television \$2.00. Give make, model. Diagram Service, Box 672-EL, Hartford 1, Conn.

15 DISTANCE ONE-TUBE plans—25¢, with Transistor experiments, catalog. Laboratories, 1131-K Valota, Redwood City, California.

NEW BOOK (Mobile Hi-Fi) Tape Recorders, Stereo, F-M, etc. \$5.00. Ekeradio, 650 N. Fair Oaks, Pasadena, California.

• • • EDUCATION & INSTRUCTION

COMPLETE YOUR High School at home in spare time with 63-year-old school. Texts furnished. No classes. Diploma. Information booklet free. American School, Dept. X237, Drexel at 58th, Chicago 37, Illinois.

• • • ELECTRICAL SUPPLIES & EQUIPMENT

DYNAMIC CONTINUITY Circuit Tester with Leads, Clips, Spotlight. Electrically, Mechanically, shock-proof. Fits pocket. Home, Industrial, Military. Money back Guarantee. \$4.50. Dynamic, 4011 N.W. 37th Ave., Miami 42, Fla.

• • • MISCELLANEOUS

CHEMICALS and Apparatus Catalog 25¢. Nu-Age Laboratories, Box 232, Bellmore, N. Y.

• • • STAMPS & COINS

THREE BRILLIANT Guaranteed Uncirculated Mexican Silver Dollars \$1.00. Universal Services, Box 675, San Antonio 6-P2, Texas.

• • • DETECTIVES

DETECTIVES—WORK Home—Travel. Experience unnecessary. Detective Particulars free. Write, Wagner, 8-125 West 86th, New York 24.

• • • MUSIC

ACCORDIONS—SAVINGS to 50%. Free trial. Trades accepted. Free catalog. Accordion Manufacturers, Dept. 20-EL, 2003 Chicago, Chicago 22.

SONGPOEMS and Lyrics Wanted! Mail to: Tin Pan Alley, Inc., 1650 Broadway, New York 19, N. Y.

Radio-Powered Sky Station

Continued from page 30

for the electronic detection and transmitting units on board.

The received microwave energy can be efficiently converted to heat by any one of several high temperature heat exchange metals that are placed in a pipe-like waveguide, which is fed from the antenna. This is a key element of the propulsion system. When the platform is operating on microwave power, this heat exchanger performs the same function as the combustor section of a conventional gas turbine engine, which increases the work potential of the engine fluid by raising its temperature. In the combustor this is done by mixing fuel with air and burning the mixture. In the microwave heat exchanger, the same result is achieved by attenuating microwave energy, changing its form from electrical energy to thermal energy, and dissipating this heat directly to the working fluid which ultimately spins the turbine. A new Raytheon government-funded study (details still classified) is said to have conclusively licked the heat exchange problem.

The logical means to get take-off and climb power for the platform's rotor blades is to install a chemical engine in the propulsion system. The supplementary chemical engine would amount only to a fuel tank, burner and heat exchanger in parallel with the microwave heat exchanger.

Even in high winds capped by gusts up to 20 to 30 knots the chemical system could lift the platform. At low altitudes the greater air density provides a power advantage despite the fact that the rotors are geared to work best at high altitudes. The RAMP would climb to altitude in a spiral path.

The science fiction writers are hard-pressed to keep ahead of present-day scientists. Perhaps in the not too distant future we will have high efficiency Amplitron-type tubes mounted in sky stations all the while beaming power through space at the earth, providing electricity for cars, houses and factories without local wiring. ☐

 **YOU NEED THIS**

FREE GIANT 1960 B-A CATALOG



204 KING-SIZED PAGES

EVERYTHING IN RADIO TV AND ELECTRONICS

100'S OF NEW ITEMS LISTED HERE FOR THE TIME

21 PAGES OF BARGAINS NOT IN ANY OTHER CATALOG

BURSTEIN-APPLEBEE CO.
 Dept. E1, 1012 McGee St., Kansas City 6, Mo.
 Send Free 1960 B-A Catalog No. 601.

Name

Address

City State

SEND FOR IT TODAY

FREE!

H. H. Scott Helps You PLAN FOR STEREO

With New Hi Fi Guide and Catalog



H.H. Scott Inc., 111 Powdermill Road, Dept. E1-2, Maynard, Mass.
 Rush me your FREE Hi Fi Guide and catalog to help me plan my stereo system.

Name

Address

City State

NEW! *Lafayette* 50 Watt Complete Stereo Phono System




LAFAYETTE LA-250



GARRARD RC121/11
WOOD BASE



LAFAYETTE
SK-58

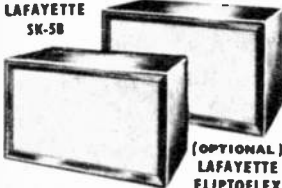

(OPTIONAL)
LAFAYETTE
ELIPTOFLEX

COMPLETE
STEREO SYSTEM
174.50

NEW GE
VR-22

This superb system will add a new dimension in living to your home with all the excitement and realism of a live concert. The new Lafayette LA-250, 50-watt stereo amplifier (25 watts each channel) forms the heart of this outstanding stereo hi-fi phonograph music system—the features, versatility and advanced circuitry of this unit are second to none. Also included is the famous Garrard RC121/11 intermix 4-speed automatic record changer with full manual or automatic operation supplied with your choice of stereo cartridges—the new GE VR-22 (.7 Mil) diamond stereo cartridge, Pickering 371-7D (.7 Mil) diamond stereo cartridge, Shure M7D (.7 Mil) diamond stereo cartridge or the new Electro-Voice 31 MD7 (.7 Mil) diamond stereo cartridge. Supplied with the Lafayette wood base cut for the RC121 in your choice of finishes. These outstanding components are coupled

COMPONENTS

LAFAYETTE LA-250 50-WATT AMPLIFIER	89.50
NEW GE VR-22 (.7 MIL) DIAMOND STEREO CARTRIDGE ...	24.45
GARRARD RC 121/11 STEREO CHANGER	41.65
LAFAYETTE WOOD CHANGER BASE	3.95
2- LAFAYETTE SK-58 FAMOUS FREE EDGE	
12" COAXIAL SPEAKERS @ 29.50	59.00

REGULAR CATALOG PRICE ~~219.99~~

YOUR GUARANTEED BEST STEREO SYSTEM BUY!
You Save 44.05

with the 2 famous free edge Lafayette SK-58 12" Coaxial speakers with built-in crossover network and brilliance level control. System supplied with plugs, cables and simple instructions. Shpg. wt., 67 lbs.

MF-681 HI-FI STEREO PHONO SYSTEM with choice of cartridge and mahogany, walnut or blond changer base (please specify) 17.45 down 12.00 MonthlyNet 174.50

MF-683 Same as MF-681, but with 2 Lafayette Eliploflex Series Bookshelf Enclosures (please specify finish). Shpg. wt., 143 lbs. 22.99 Down, 15.00 MonthlyNet 229.95

MF-682. Stereo AM-FM-Phone System. Same as MF-681 but including the new Lafayette LT-50 stereo tuner. Shpg. wt., 85 lbs. 28.75 Down, 17.00 MonthlyNet 287.50

LAFAYETTE'S FREE CATALOG!

308 GIANT SIZED PAGES

The Complete Catalog Featuring
"The Best Buys In The Business"



FOR THE NEWEST AND FINEST IN
STEREOPHONIC HI-FI EQUIPMENT AND SYSTEMS

- TAPE RECORDERS ● PUBLIC ADDRESS SYSTEMS
- AMATEUR EQUIPMENT ● INDUSTRIAL SUPPLIES
- MINIATURE COMPONENTS ● RADIO & TV TUBES AND PARTS
- EXCLUSIVE LAFAYETTE TRANSISTOR & HI-FI KITS

Send for Lafayette's FREE Catalog—the most complete, up-to-the-minute electronic supply catalog crammed full of everything in electronics at our customary down-to-earth money-saving prices.

Leaders in Hi-Fi

The most complete selection and largest stocks of hi-fi components and systems—available for immediate delivery at the lowest possible prices. Save even more on Lafayette endorsed "best-buy" complete systems.

NEW YORK
100 SIXTH AVENUE
NEW YORK 13, N. Y.

JAMAICA
165-06 LIBERTY AVE.
JAMAICA 33, N. Y.

BOSTON
110 FEDERAL ST.
BOSTON 10, MASS.

NEWARK
24 CENTRAL AVE.
NEWARK 2, N. J.

PLAINFIELD
139 W. 2nd ST.
PLAINFIELD, N. J.

FREE!
1960
CATALOG

CUT OUT
AND PASTE
ON POST
CARD

LAFAYETTE RADIO
P.O. BOX 222
JAMAICA 31, N. Y.
DEPT. E1B-6

Name.....
Address.....
City..... Zone..... State.....





Mail Postage-Free Card for
SAMPLE LESSON
FREE

Shows how easy it is to
 Train at Home for **RADIO**
TELEVISION ELECTRONICS

Find Out What NRI—
 Oldest, Largest Home
 Study Radio-TV School
 Can Do For You

Since 1914—NRI has been training ambitious men at home. Thousands have found NRI's training the way to higher earnings.

← See Inside

The ABC's of
SERVICING



Jobs Like These Go to the
 Radio-Television Technicians



NRI Trained these Men



"I knew practically nothing about Electronics. After 15 months I started repairing sets. My future looks bright." D. A. KERMANN, Minneapolis, Minn.

"Thanks to NRI, I operated a successful Radio Repair shop. Then got a job with WPAQ; now I am an engineer for WHPB-TV. A WORKMAN, High Point, N. C."



"Have good job in a TV repair shop plus a small business in my home. In one year I went from lowest paid to head benchman." V. BARR, Toronto, Ont.

BUSINESS REPLY CARD
 No Postage Stamp Necessary If Mailed in The United States

POSTAGE WILL BE PAID BY

NATIONAL RADIO INSTITUTE

Washington 16, D. C.

FIRST CLASS
 Permit No. 20-R
 (Sec. 349 P.L.R.)
 Washington, D.C.



Pick the training you want!
choose-it-yourself... before enlistment

The Army's new "Choose-it-Yourself" System lets you do the choosing! Here's how it works: **1. choose** ... before enlistment. Choose your training from fields like Construction Equipment Operation, Electronics, Missiles, Machine Accounting, Radar & TV Repair—and many more. **2. qualify** ... before enlistment. Take aptitude and physical exams to qualify for your chosen training. **3. know** ... before enlistment.

If you qualify, you know you'll get the training you like. Your choice is written right into your future Army record—guaranteed before you enlist.

no obligation! Choose, qualify and know—without the slightest obligation to enlist. This week, ask your Army recruiter to show you his complete list of available training fields.



CHOOSE IT YOURSELF VOCATIONAL TRAINING SYSTEM

US ARMY