

**First Class-E CB Project!**

# Electronics ILLUSTRATED®

CONSISTENTLY THE BEST IN HOBBY ELECTRONICS

SEPTEMBER 1972 **50c**  
By the Publishers of

MECHANIX ILLUSTRATED  
06125



## **Build-It Special!**

### **Six Great Projects:**

**1-Tube Radio (Nostalgia!)**

**1-Tube Amplifier**

**Flea-Power Ham Transmitter**

**CB Converter for Your Car**

**One-IC Intercom**

**One-IC Signal Tracer**

---

## **Basic Transistor Circuits**

**Six More Build-It Projects  
to Give You the Fundamentals!**

---

**We Update Our Famous  
24-HOUR SHORTWAVE SCHEDULE!**

---

**Injections to Cure Color TV Ills**

57 86 7530 HIN724LNM-4 ITG01  
MICHAEL J HINDMAN  
2724 E-LINWOOD  
-SPRINGFIELD  
MO 65804

er Meter

# NOW you can train at home building a NEW 25" Solid State Color TV engineered by NRI for learning and trouble-shooting

*So much better for learning TV servicing than any hobby kit, because NRI designed and created it as an educational tool.*

Unlike hobby kits which are designed for creating a TV set as the end product, NRI built its exclusive 25" Solid State Color TV kit as a real training kit. You can introduce and correct defects . . . for trouble-shooting and hands-on experience in circuitry and servicing. The kits include a wide-band oscilloscope, color bar crosshatch generator, transistorized volt-ohmmeter and other valuable equipment that can soon have you earning \$5 to \$7 an hour servicing color sets in your spare time.

Handsome woodgrain cabinet, at no extra cost. (Offered only by NRI)

New square-cornered Sylvania picture tube

100% solid state chassis

6-position detented UHF channel selector




Modular construction with plug-in circuit boards

Automatic degaussing


Automatic fine tuning

Automatic tint control

Automatic color control

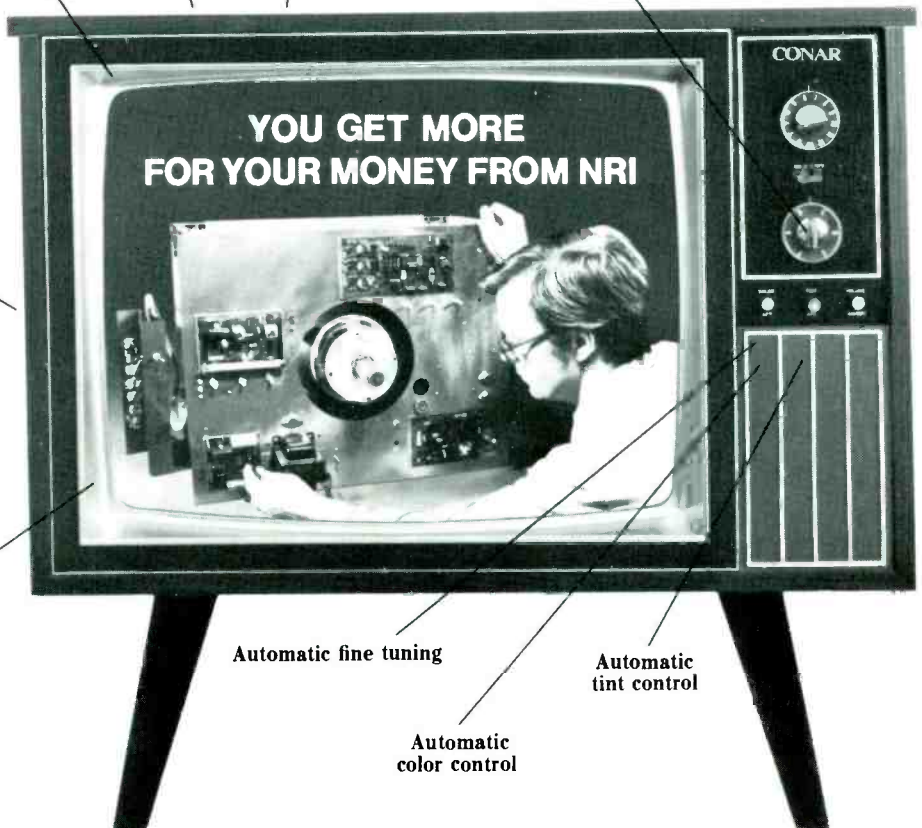
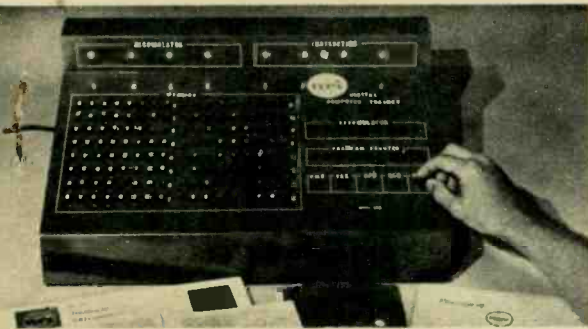
# NRI FIRSTS make learning Electronics fast and fascinating—to give you priceless confidence



**FIRST** to give you a complete programmable digital computer, with memory, you build yourself . . . to learn organization, operation, trouble-shooting and programming. This remarkable computer is one of ten training kits you receive with the new NRI Complete Computer Electronics Course.



**FIRST** to give you true-to-life experiences as a Communications Technician. Every fascinating step you take in NRI Communications training, including circuit analysis of your own 15-watt, phone/cw transmitter, is engineered to help you prove theory and later apply it on the job. Studio equipment operation and trouble shooting become a matter of easily remembered logic.



**FIRST** to give you completely specialized training kits engineered for business, industrial and military Electronics Technology. Shown is your own training center in solid-state motor control and analog computer servo-mechanisms. Telemetering circuits, solid-state multivibrators and the latest types of integrated circuits are included in your course.

The NRI color TV and digital computer kits are the latest in a long line of "firsts" for NRI. For more than fifty years, NRI has been providing unique 3-dimensional home-study training that has helped hundreds of thousands of students reach their goals quickly and easily.

What NRI provides is a combination of kits and bite-size texts that give you hands-on experience while you are learning. The texts average only 40 pages each, and they are fully illustrated. You are taken step-by-step from the first stages into the more advanced theory and techniques . . . with an expert instructor ready at all times to provide valuable guidance and personal attention. (The level of personal attention provided is more than you would receive in many classrooms.) Once you've grasped the fundamentals, you move with confidence and enthusiasm into new discoveries in the fascinating world of electronics.

You start out with NRI's exclusive Achievement Kit, containing everything you need to get moving fast. Lessons have been specifically written so that experiments build upon one another like stepping stones. You can perform a hundred experiments, build hundreds of circuits . . . as you learn to use the professional test equipment provided, building radios and TV sets, transmitter or computer circuits. It's the priceless "third dimension" in NRI training . . . practical experience.

## Train with the leader—NRI

Compare training kits, texts, techniques and overall training . . . and you'll find that you get more for your money from NRI. Whatever your reason for wanting more knowledge of Electronics, NRI has an instruction plan that will meet your needs. Choose from major programs in Advanced Color TV Servicing, Complete Computer Electronics, Industrial Electronics and the other special courses designed to meet specific needs. With NRI home training, you can learn new skills while you're still working at your present job . . . and turn yourself into the man in demand.

### GET FACTS ABOUT GI BILL

If you have served since January 31, 1955, or are in service now, check GI line on postage-free card.

## Send for free NRI catalog

MAIL THE POSTAGE-FREE CARD FOR THE FREE NRI CATALOG IN THE FIELD OF YOUR CHOICE. YOU WILL BE UNDER NO OBLIGATION. NO SALESMAN WILL CALL.

If the card has been used, write direct to:



**NRI TRAINING**  
3939 Wisconsin Ave.  
Washington, D.C. 20016

# Electronics ILLUSTRATED

A Fawcett Publication

September 1972

Vol. 15 No. 5

Member Institute of High Fidelity, Inc.  
COVER: Ektachrome by Henry Ries Studios  
Figures by Robert Laughlin

## COMING NEXT ISSUE

Apartment Dweller's Hi-Fi

Servicing Aids for Hobbyists

Phone Patch for Hams

How to Fix Your Bum Cassettes

### AMATEUR RADIO

Flea-Power Ham Transmitter .....	Herb Cohen	32
E-Dipper for VHF and UHF Hams .....	Herb Cohen	76
The Ham Shack .....	Wayne Green, W2NSD/1	89

### CITIZENS BAND

CB Converter for Your Car .....	Herb Cohen	33
CB Corner .....	Len Buckwalter, KQA5012	71
The E-Dipper: First Class E Project .....	Herb Cohen	76

### AUDIO & HI-FI

One-Tube Phono Amplifier .....	Len Buckwalter	31
Direct-Reading Wow & Flutter Meter, Part II .....	Harry Kolbe	42
Hi-Fi Today .....	Robert Angus	81

### SHORTWAVE LISTENING

One-Tube Radio for SWLs .....	Herb Cohen	30
A Primer For Cuba Watchers .....	Alex Bower	40
The Listener .....	C. M. Stanbury II	62
Updated 24-Hour Shortwave Schedule .....		66

### SERVICE

Service Tips .....	Art Margolis	26
One-IC Signal Tracer .....	Herb Friedman	35
Signal Injecting Pinpoints Color TV Troubles .....	Art Margolis	58
A Lo-Lo-Ohm Ohmmeter .....	C. R. Lewart	63

### ELECTRONICS IN THE HOME

One-IC Home Intercom .....	Leslie Powell	34
TV Antenna System That Lasts & Lasts & Lasts .....		82

### SOLID-STATE ELECTRONICS

Beginner's Guide to Basic Transistor Circuits .....	Len Buckwalter	48
---	----------------	----

### EI'S NEW HI-FI CONTEST

.....		80
-------	--	----

### KIT REPORTS

Home-Protection System .....		53
Triggered-Sweep Oscilloscope .....		86

### NEW PRODUCTS

Electronic Marketplace .....		14
------------------------------	--	----

### YOUR LIBRARY

Good Reading .....	Tim Cartwright	88
--------------------	----------------	----


### HOBBY & BUSINESS OPPORTUNITIES

Classified Ads .....		105
----------------------	--	-----

### REGULAR DEPARTMENTS

Feedback .....		8
Uncle Tom's Corner .....	Tom Kneitel, K2AES/KQD4552	12
The EI Ticker .....		85
Over & Out .....		94
Subscription Offer .....		102

# WHICH WAY FOUR CHANNEL ?

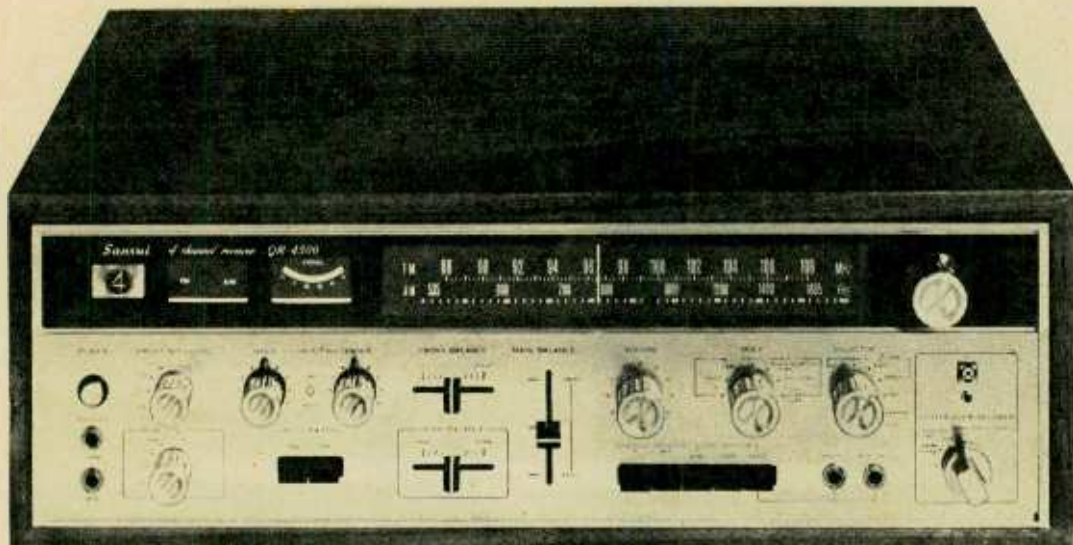

## THIS WAY

If the four-channel merry-go-round has you confused, you have lots of company. Discrete or matrixed. Compatible or non-compatible. This system or that one.

Now Sansui offers you total-capability QR Receivers that will transport you into the four-channel world to day and can handle every variation to the four-channel game that anyone's dreamed up for tomorrow.

Take the QR4500 AM/FM Two-Channel and Four-Channel Stereo Receiver-Synthesizer-Decoder-Amplifier-and-Control-Center. It can decode any compatibly matrixed four-channel recording or FM broadcast, or it can synthesize two rear channels from any two-channel source. Exclusive Sansui phase-shift matrixing prevents the sound dropouts and false dislocations that plague many matrixed systems. And exclusive phase modulators duplicate the live sound field.

It can handle any tape or other discrete source and accepts adaptors, converters or other accessories for any four-channel technique anyone's hinted at.

It boasts 240 watts of total IHF power (continuous power per channel of 38 watts at 4 ohms, 27 watts at 8 ohms) with less than 0.5% TH or IM distortion at rated output and normal response of 20 to 30,000 Hz  $\pm$ 1dB. In a walnut cabinet, \$599.95.

You'll find the same universal four-channel versatility in all Sansui QR Quadphonic Receivers, including the QR1500, with 100 watts of total IHF power (20 watts continuous per channel at 4 ohms). With walnut cabinet, \$299.95.



### SANSUI ELECTRONICS CORP.


Woodside, New York 11377 • Gardena, California 90247

ELECTRONIC DISTRIBUTORS (Canada), Vancouver 9, B.C.

SANSUI ELECTRIC CO., LTD., Tokyo, Japan • Sansui Audio Europe S. A., Antwerp, Belgium

© COPYRIGHT BY SANSUI

how often could  
you have used...

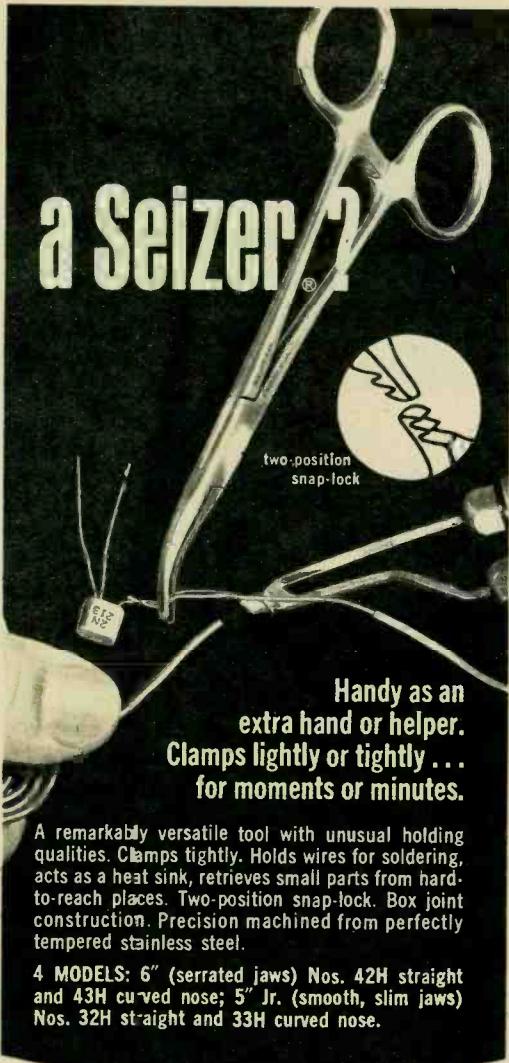

A remarkably versatile tool with unusual holding qualities. Clamps tightly. Holds wires for soldering, acts as a heat sink, retrieves small parts from hard-to-reach places. Two-position snap-lock. Box joint construction. Precision machined from perfectly tempered stainless steel.

4 MODELS: 6" (serrated jaws) Nos. 42H straight and 43H curved nose; 5" Jr. (smooth, slim jaws) Nos. 32H straight and 33H curved nose.

**XCELITE**

XCELITE, INC., 16 Bank St., Orchard Park, N. Y. 14127  
Send Bulletin N564 on Seizers®.

name \_\_\_\_\_  
address \_\_\_\_\_  
city \_\_\_\_\_ state & zip \_\_\_\_\_

In Canada contact Charles W. Pointon, Ltd.

# Electronics ILLUSTRATED

By the Publishers of MECHANIX ILLUSTRATED

editor **ROBERT G. BEASON**  
managing editor **Clifford L. Forbes**  
technical editor **Robert Wollins**  
art editor **Lou Rubsamen**  
associate editor **Jean E. Lee**  
production editor **Priscilla Moody**  
national adv. mgr. **Stanley Tessler**  
vp., adv. director **John F. Webster**  
publisher **George H. Allen**

## CONTRIBUTING EDITORS

amateur radio **Wayne Green, W2NSD/1**  
citizens band **Len Buckwalter, KQA5012**  
swl-dx **C. M. Stanbury II**  
special projects **Herb Friedman**  
**W2ZLF/KB19457**  
service **Art Margolis**  
audio **Harry Kolbe**  
audio **Robert Angus**

## EXECUTIVE STAFF

president **Roger Fawcett**  
secretary-treasurer **Gordon Fawcett**  
circulation director **Roscoe K. Fawcett**  
publisher, exec. vp.,  
magazine div. **George H. Allen**  
exec. vp., book div. **Ralph Daigh**  
vp., asst. to pres. **Frederick A. Klein**  
vp., comptroller **F. Paul Simmering**  
vp., dir. admin. services **Joseph Cunningham**  
vp., circ. mgr., mag. div. **Luther Bugbee**  
vp., circ. mgr., book div. **Edmund Pendergast**  
vp., production dir. **Thomas R. Marvel**  
vp., marketing dir. **Edward W. Reed**  
vp., dir. data processing **Joseph M. Federici**  
subscription mgr. **Ted Sloat**  
production mgr. **Judy Schaefer**  
art dir. **Ralph Mattison**

ELECTRONICS ILLUSTRATED is published bi-monthly by Fawcett Publications, Inc., Fawcett Bldg., Greenwich, Conn. 06830. Second-class postage paid at Greenwich, Conn., and at additional mailing offices.

EDITORIAL OFFICES: 1515 Broadway, New York, N.Y. 10036 (phone 212-869-3000). Contributions must be accompanied by sufficient postage and will be handled with care, though the publishers assume no responsibility for return thereof.

ADVERTISING OFFICES: 1515 Broadway, New York, N.Y. 10036 (phone 212-869-3000); Midwestern Representatives, Kingwill Co., 5526 N. Elston Ave., Chicago, Ill. 60630 (phone 312-774-9660); 211 W. Fort St., Suite 1010, Detroit, Mich. 48226 (phone 313-962-3860); 3807 Wilshire Blvd., Los Angeles, Calif. 90010 (phone 213-287-8258); 681 Market St., San Francisco, Calif. 94105 (phone 415-EX 7-3441); 1422 W. Peachtree St., N.W., Atlanta, Ga. 30309 (phone 404-TR 5-0373).

SUBSCRIPTIONS: \$3 per year (6 issues) in U.S. and possessions and Canada. All other countries \$4 for 6 issues. All subscription correspondence, including changes of address (Form 3579), should be addressed to ELECTRONICS ILLUSTRATED, Subscription Dept., Fawcett Bldg., Greenwich, Conn. 06830. Foreign subscriptions and sales should be remitted by International Money Order in U.S. funds payable at Greenwich, Conn.

COPYRIGHT © 1972 by Fawcett Publications, Inc. The title ELECTRONICS ILLUSTRATED is registered in the U.S. Patent Office. Reproduction in whole or in part is forbidden without written permission of the publishers; however, permission is hereby granted to quote from this issue of this magazine on radio or television, provided a total of not more than 1,000 words is quoted and credit is given to the title of this magazine and issue, as well as the statement, copyright 1972, by Fawcett Publications, Inc. Member ABC, MPA.

PRINTED IN U.S.A. BY FAWCETT PRINTING CORP., LOUISVILLE, KY. 40201. Microfilm copies of current and back issues are available from University Microfilms, 313 N. First St., Ann Arbor, Mich. 48103.

# 20 RADIO

## and Electronics Circuits

# PROGRESSIVE HOME RADIO-TV COURSE

Reg. U.S. Pat. Off.



Training Electronics Technicians Since 1946

### Now Includes

- ★ 12 RECEIVERS
- ★ 3 TRANSMITTERS
- ★ SQ. WAVE GENERATOR
- ★ SIGNAL TRACER
- ★ AMPLIFIER
- ★ SIGNAL INJECTOR
- ★ CODE OSCILLATOR
- ★ TRANSISTOR (Solid State) CIRCUITS
- ★ VACUUM TUBE CIRCUITS
- ★ PRINTED CIRCUITS
- ★ HAND WIRED CIRCUITS

**YOU DON'T HAVE TO SPEND HUNDREDS OF DOLLARS FOR A RADIO COURSE**

The "Edu-Kit" offers you an outstanding PRACTICAL HOME RADIO COURSE at a rock-bottom price. Our Kit is designed to train Radio & Electronics Technicians, making use of the most modern methods of home training. You will learn radio theory, construction practice and servicing. THIS IS A COMPLETE RADIO COURSE IN EVERY DETAIL. You will learn how to build radios, using regular schematics; how to wire and solder in a professional manner; how to service radios. You will work with the standard type of punched metal chassis as well as the latest development of Printed Circuit chassis.

You will learn the basic Principles of radio. You will construct, study and work with RF and AF amplifiers and oscillators, detectors, rectifiers, test equipment. You will learn and practice code, using the Progressive Code Oscillator. You will learn and practice trouble-shooting, using the Progressive Signal Tracer, Progressive Signal Injector, Progressive Dynamic Radio & Electronics Tester, Square Wave Generator and the accompanying instructional material.

You will receive training for the Novice, Technician and General Classes of F.C.C. Radio Amateur Licenses. You will build Receiver, Transmitter, Square Wave Generator, Code Oscillator, Signal Tracer and Signal Injector circuits, and learn how to operate them. You will receive an excellent background for television, Hi-Fi and Electronics.

Absolutely no previous knowledge of radio or science is required. The "Edu-Kit" is the product of many years of teaching and engineering experience. The "Edu-Kit" will provide you with an excellent background in Electronics and Radio, worth many times the low price you pay. The Signal Tracer alone is worth more than the price of the Kit.

### THE KIT FOR EVERYONE

You do not need the slightest background in radio or science. Whether you are interested in Radio & Electronics because you want an interesting hobby, a well paying business or a job with a future, you will find the "Edu-Kit" a worth-while investment. Many thousands of individuals of all

ages and backgrounds have successfully used the "Edu-Kit" in more than 79 countries of the world. The "Edu-Kit" has been carefully designed, step by step, so that you cannot make a mistake. The "Edu-Kit" allows you to teach yourself at your own rate. No instructor is necessary.

### PROGRESSIVE TEACHING METHOD

The Progressive Radio "Edu-Kit" is the foremost educational radio kit in the world, and is universally accepted as the standard in the field of electronics training. The "Edu-Kit" uses the modern educational principle of "Learn by Doing." Therefore you construct, learn schematics, study theory, practice trouble-shooting—all in a closely integrated program designed to provide an easily-learned, thorough and interesting background in radio.

You begin by examining the various radio parts of the "Edu-Kit." You then learn the function, theory and wiring of these parts. Then you build a simple radio. With this first set you will enjoy listening to regular broadcast stations, learn theory, practice testing and trouble-shooting. Then you build a more advanced radio, learn more advanced theory and techniques. Gradually, in a progressive manner, and at your own rate, you will find yourself constructing more advanced multi-tube radio circuits, and doing work like a professional Radio Technician.

Included in the "Edu-Kit" course are Receiver, Transmitter, Code Oscillator, Signal Tracer, Square Wave Generator and Signal Injector Circuits. These are not unprofessional "breadboard" experiments, but genuine radio circuits, constructed by means of professional wiring and soldering on metal chassis, plus the new method of radio construction known as "Printed Circuitry." These circuits operate on your regular AC or DC house current.

### THE "EDU-KIT" IS COMPLETE

You will receive all parts and instructions necessary to build twenty different radio and electronics circuits, each guaranteed to operate. Our Kits contain tubes, tube sockets, variable, electrolytic, mica, ceramic and paper dielectric condensers, resistors, tie strips, hardware, tubing, punched metal chassis, Instruction Manuals, hook-up wire, solder, selenium rectifiers, coils, volume controls and switches, solid state materials.

In addition, you receive Printed Circuit materials, including Printed Circuits chassis, special tube sockets, hardware and instructions. You also receive a useful set of tools; a professional electric soldering iron, and a self-powered Dynamic Radio and Electronics Tester. The "Edu-Kit" also includes Code Instructions and the Progressive Code Oscillator, in addition to F.C.C. Radio Amateur License training. You will also receive lessons for servicing with the Progressive Signal Tracer and the Progressive Signal Injector, a High Fidelity Guide and a Quiz Book. You receive Membership in Radio-TV Club, Free Consultation Service, Certificate of Merit and Discount Privileges. You receive all parts, tools, instructions, etc. Everything is yours to keep.

Progressive "Edu-Kit" Inc., 1189 Broadway, Dept. 628AE, Hewlett, N.Y. 11557

### PRINTED CIRCUITRY

At no increase in price, the "Edu-Kit" now includes Printed Circuitry. You build a Printed Circuit Signal Injector, a unique servicing instrument that can detect many Radio and TV troubles. This revolutionary new technique of radio construction is now becoming popular in commercial radio and TV sets.

A Printed Circuit is a special insulated chassis on which has been deposited a conducting material which takes the place of wiring. The various parts are merely plugged in and soldered to terminals.

Printed Circuitry is the basis of modern Automation Electronics. A knowledge of this subject is a necessity today for anyone interested in Electronics.

### UNCONDITIONAL MONEY-BACK GUARANTEE

Please rush my Expanded Radio-TV Course with "Edu-Kits"® to me.

- Send Course with Edu-Kits postpaid. I enclose full payment of \$34.95
- I enclose \$5.00 deposit. Send Course with Edu-Kits C.O.D. for balance of \$29.95 plus postage.
- Send me FREE additional information describing Course with Edu-Kits.

NAME

ADDRESS

CITY & STATE

ZIP

### PROGRESSIVE "EDU-KITS" INC.

1189 Broadway, Dept. 628AE, Hewlett, N.Y. 11557

### FREE EXTRAS

#### • SET OF TOOLS

- SOLDERING IRON
- ELECTRONICS TESTER
- PLIERS-CUTTERS
- VALUABLE DISCOUNT CARD
- CERTIFICATE OF MERIT
- TESTER INSTRUCTION MANUAL
- HIGH FIDELITY GUIDE & QUIZZES
- TELEVISION BOOK & RADIO TROUBLE SHOOTING BOOK
- MEMBERSHIP IN RADIO-TV CLUB: CONSULTATION SERVICE & F.C.C. AMATEUR LICENSE TRAINING
- PRINTED CIRCUITRY

### SERVICING LESSONS

You will learn trouble-shooting and servicing in a progressive manner. You will practice repairs on the sets that you construct. You will learn symptoms and causes of trouble in home, portable and car radios. You will learn how to use the professional Signal Tracer, the unique Signal Injector, and the Dynamic Radio & Electronics Tester. While you are learning in this practical way, you will be able to do many a repair job for your friends and neighbors, and charge fees which will far exceed the price of the "Edu-Kit." Our Consultation Service will help you with any technical problems you may have.

### FROM OUR MAIL BAG

J. Stataitis, of 25 Poplar Pl., Waterbury, Conn., writes: "I have repaired several sets for my friends, and made money. The "Edu-Kit" paid for itself. I was ready to spend \$240 for a Course, but I found your ad and sent for your Kit."

Ben Valerio, P. O. Box 21, Magna, Utah, writes: "The Edu-Kits are wonderful. Here I am sending you the questions and also the answers for them. I have been in Radio for the last seven years, but like to work with Radio Kits, and like to build Radio Testing Equipment. I enjoyed every minute I worked with the different kits; the Signal Tracer works fine. Also like to let you know that I feel proud of becoming a member of your Radio-TV Club."

Robert L. Shuff, 1534 Monroe Ave., Huntington, W. Va.: "Thought I would drop you a few lines to say that I received my Edu-Kit, and was really amazed that such a bargain can be had at such a low price. I have already started repairing radios, and phonographs. My friends were really surprised to see me get into the swing of it so quickly. The Trouble-shooting Tester that comes with the Kit is real good and finds the trouble, if there is any to be found."

# Feedback from Our Readers


Write to: Letters Editor, Electronics Illustrated, 1515 Broadway, New York, N.Y. 10036

## ● SPREAD THE NEWS

Thanks to you and Art Margolis for your excellent Service Tips and related TV servicing articles. Being the owner of an electronics sales and service business, I look forward to reading Art's little tricks of the trade which are presented so well in your magazine. Living in a small community presents problems of learning most servicing techniques by experience. We limit ourselves by not sharing these techniques with others. Again, thanks for a job well done.

Alan Brown  
West Bend, Wis.

## ● A POX ON YOUR PULSE

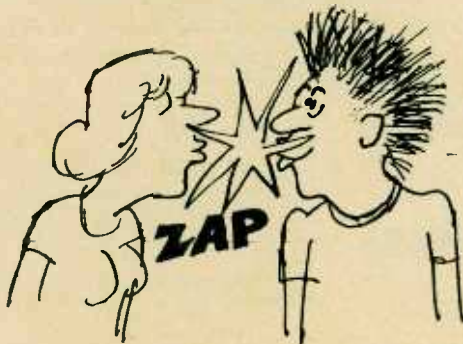

Built your Cardio-Tach (July '72 EI) and was somewhat surprised by the results. After a bit of hand-holding with my favorite gal, both of us thought it would be a cute idea to try out my latest project. You know, see if she turns me on. No luck. The meter showed nothing more than a normal pulse rate. Too little sensitivity?

Ron Brand  
Tupulo, Miss.

*Next time try sexier components.*

## ● TAKING TIME OUT

Enjoyed your May issue. Heathkit appreciates the coverage given its new desk-top calculator and hi-fi components. Some problems, however. The readouts on the calculator aren't RCA's Numitron incandescent lamps. They are Sperry-Rand gas-discharge displays. Also, we feel it's a mistake to compare our AJ-1510 digital tuner with tuners

that have digital readouts but lack the accurate tuning achieved with digital circuits.

Earl Broihier  
Heath Co.  
Benton Harbor, Mich.

## ● LONG-PLAYING FLAPJACK?



Your article on the new thin LP records (July '72 EI) was quite a shocker. I immediately went to a record store and searched for one. I found one with the help of a salesman, took it home and placed it. Sounded fine—very low noise level as you stated. Only problem is, I can't separate it from the standard LP which was underneath on the changer's platter. Is this going to mean one record for the price of two?

Peter Pearlman  
Hempstead, N.Y.

## ● CHIPS FOR EVERYTHING

I read your GOOD READING column in the March '72 EI with interest but was dismayed to find that the information you published about RCA's SK replacement series of transistors, rectifiers, thyristors and ICs is now obsolete. For the record, please note that RCA SK Series Top-of-the-Line devices now replace more than 46,000 domestic and foreign semiconductor types. That's with only 120 SK devices. A new replacement guide (SPG-202M) is now available.

Arnold Durham  
RCA Electronic Components  
Harrison, N.J.






# FREE

## Heathkit Catalog Build and save on over 350 kits

Your free 1972 Heathkit catalog describes more kits than ever... over 350... all designed to give you fine performance and save you money when you buy and when you use. Choose solid state color TV, stereo, marine, automotive, test instruments, amateur radio, short-wave, home appliances, and more! Send for your free copy today.

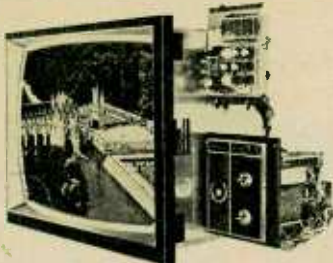
### NEW Solid-State Heathkit Color TV — the best TV kit ever offered



25" diagonal matrix tube, 24-position UHF/VHF detune power tuning, varactor UHF tuner, MOSFET VHF tuner, tint switch. New performance and convenience. Detune tuned UHF & VHF. Preselect any 12 favorite UHF stations, then power pushbutton (or remote) tune all 24 channels in either direction. New angular tint control switch selects normal or wide angle color to reduce tint changes between stations. Exclusive Heath MTX-5 ultra-rectangular black matrix tube has brighter pictures, better contrast. "Instant-On." Automatic fine tuning. Adjustable tone control. Automatic chroma control. Adjustable video peaking. More sensitive tuners. Transformer operated. Built-in dot generator and volt-ohm meter. Choice of cabinet styles from \$81.95\*.

- Kit GR-900, less cabinet ..... \$599.95\*
- Kit GRA-900-6, remote control ..... \$79.95\*

### NEW Heathkit Digital FM Tuner

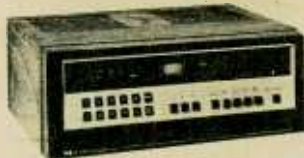

Another Heathkit "first" in consumer electronics. Pure digital computer design including digital frequency synthesizer tuning employing phase-lock-loop techniques, FET varactor FM RF front end, digital discriminator and readout result in performance specs and tuning convenience that already are the talk of the audio world: channel frequency accuracy better than 0.005%; less than 1.8 uV sensitivity; distortion levels of 0.1%; selectivity and IF rejection better than 95 dB; image & spurious rejection better than 90 dB; S/N ratio better than 65 dB; separation better than 40 dB. One of a kind, the AJ-1510 "computer tuner" is the only tuner offering you 3 distinct tuning modes: keyboard, computer-type punch cards (up to 3), plus automatic band scanning with variable speed and stereo-only capability. The 55 ICs, 50 transistors and 50 signal diodes mount on 10 modules with 7 plugging into a master board for optimum computer modularity & ease of assembly. Join the computer generation of audio equipment — order your AJ-1510 today.

- Kit AJ-1510, tuner only ..... \$539.95\*
- Cabinet ..... \$24.95\*

### NEW Heathkit Solid-State Ignition Analyzer

Analyzes standard, transistor, or capacitive discharge systems on 3, 4, 6, or 8 cyl. engines to find bad plugs, points, wiring or distributor parts, incorrect dwell time, coil, condenser, transistor or CD circuitry problems. Built-in tach, 0-1000 & 0-5000 rpm ranges for carb. adjustments. Constant width patterns, primary or secondary, parade or superimposed, plus expanded. Optional 12VDC supply for road checks, \$24.95\*.

- Kit CO-1015 ..... \$129.95\*



### NEW Heathkit 4-Channel Amplifier

Brings you 200 versatile watts for discrete or matrixed 4-channel sound, and stereo or mono. Built-in matrix circuitry decodes matrixed 4-channel recordings or broadcasts, lets you use your existing stereo equipment as well as enhancing your present stereo records and tapes. As discrete 4-channel media grows the AA-2004 is ready... with four amplifiers producing 260 watts into 4 ohms (4x65), 200 watts into 8 ohms (4x50), 120 watts into 16 ohms (4x30), and controls for every source, mode and installation. Amplifier sections are controlled in pairs with one complete stereo system for left and right front speakers and another for left and right rear — so it can be used to power two complete 4-channel systems (up to 8 speakers)... or four separate-source mono systems if desired. Easy circuit board assembly.

- Kit AA-2004, amplifier only ..... \$349.95\*
- Cabinet ..... \$24.95\*



### NEW Heathkit 8-Digit Calculator

Adds, subtracts, multiplies, divides, chain or mixed functions, and constant. Floating or selectable 7 position decimal. Plus, minus, and overflow indicators. Overflow protection of most significant 8 digits. Clear-display key to correct last entry. Standard keyboard. American LSI circuitry. Bright 1/2" red digits. 120 or 240 VAC operation. Desktop black & white cabinet, 3 1/2" h x 6" w x 10 1/4" d.

- Kit IC-2008 ..... \$129.95\*



### NEW Heathkit Solid-State FET VOM

Dual FET portable multimeter with lab grade accuracy, 10 megohm input and the ranges you really need. 9 DCV & ACV ranges, 0.1 to 1000 v, ± 2% accuracy. 6 DC & AC current ranges, 10 microamps. to 1 amp. 7 resistance ranges, X1 (10 ohm center) to X1Meg. 9 dB ranges, -40 to + 62. 1% precision metal-film dividers. 4 1/2", 100 uA, ruggedized taut-band meter, diode & fuse protected. Battery check.

- Kit IM-104, less batteries, \$79.95\*.



See them all at your Heathkit Electronic Center... or fill out the coupon below

HEATHKIT ELECTRONIC CENTERS — ARIZ: Phoenix, 2727 W. Indian School Rd.; CALIF: Anaheim, 330 E. Ball Rd.; El Cerrito, 6000 Potrero Ave.; Los Angeles, 2309 S. Flower St.; Pasadena, 1555 Orange Grove Av. N.; Redwood City, 2001 Middlefield Rd.; San Diego (La Mesa), 8363 Center Dr.; Woodland Hills, 22504 Ventura Blvd.; COLO.: Denver, 5540 W. 38th Ave.; FLA.: Miami (Hialeah), 4705 W. 16th Ave.; GA.: Atlanta, 5285 Roswell Rd.; ILL.: Chicago, 3452-66 W. Devon Ave.; Downers Grove, 224 Ogden Ave.; KANSAS: Kansas City (Mission), 5960 Lamar Ave.; MD.: Rockville, 5542 Nicholson Lane; MASS.: Boston (Wellesley), 165 Worcester St.; MICH.: Detroit, 18645 P. Eight Mile Rd. & 18149 E. Eight Mile Rd.; MINN.: Minneapolis (Hopkins), 101 Shady Oak Rd.; MO.: St. Louis, 9296 Gravois Ave.; N.J.: Fair Lawn, 35-07 Broadway (Rte. 4); N.Y.: Buffalo (Amherst), 3476 Sheridan Ave.; New York, 35 W. 45th St.; Jericho, L.I., 15 Jericho Turnpike; Rochester, Long Ridge Plaza; OHIO: Cincinnati (Wardlaw), 10133 Springfield Pike; Cleveland, 5444 Pearl Rd.; PA.: Philadelphia, 6318 Roosevelt Blvd.; Pittsburgh, 3482 Wm. Penn Hwy.; TEXAS: Dallas, 2715 Ross Ave.; Houston, 3705 Westheimer; WASH.: Seattle, 2221 Third Ave.; WIS.: Milwaukee, 5215 Fond du Lac.

HEATHKIT Schlumberger	
HEATH COMPANY, Dept. 39-9 Benton Harbor, Michigan 49022	
<input type="checkbox"/> Please send FREE Heathkit Catalog.	
<input type="checkbox"/> Enclosed is \$ _____, plus shipping.	
Please send model(s) _____	
Name _____	
Address _____	
City _____ State _____ Zip _____	
Prices & specifications subject to change without notice. *Mail order prices; F.O.B. factory.	
CL-434R	

# FOR INVENTIVE PEOPLE ONLY

If you're the kind of guy who likes to devise his own equipment or the kind who appreciates clever mechanical design, then Mallory do-your-thing products are for you.

They'll let you invent, create, modify, so things work your way. And of course, you'll get famous Mallory quality and performance you can count on too. Get them at your nearby Mallory Distributor.



## AUTOMOBILE REMINDER ALARM

Ever leave your lights on? Never again... with solid-state Sonalert®. Its shrill sound warns you, prevents battery drain. Use on turn signals, reverse gear... or any electrical component on your car, truck, boat, tractor. For 6 and 12 volt.



## CONTROL YOUR TIME

Use "Easy Time" 24-hour timer. Turns anything you plug into it on and off. Appliances, lights, pumps, motors, humidifiers... you name it. Tough enough to handle 12 amps, 1500 watts.



## HIGH INTENSITY NOISE

Compact, purse-size, big-sound Handy Blast... your personal alarm. Use it for anything... boat horn, emergencies, scare muggers, signals, call kids, scouting, bicycling... even cheer your team.

## ON-THE-GO GROOMING

Free yourself from conventional, bulky shaving gear. Handy Shaver... it's about the size of a cigarette pack. Hi-speed, quiet, 3-volt motor for fast, no-pull shaving. Comes with Duracell® batteries, mirror cap and tough carrying case. Also available in new sideburn trimmer model.



## SILENT PROTECTION

Crime Alert®... uses invisible, silent ultrasonic sound-waves. Anything that moves triggers its piercing alarm. Use anywhere... battery or plug in. Accessories to make it total security system.



## SOUND WHERE YOU WANT IT



The most popular, portable recorder/player around. Batteries or plug in. Push-button operation, pop-up ejection, automatic shut off. With sensitive dynamic mike, earphone, Duratape® cassette, Duracell® alkaline batteries. Ask for the MCR 1211.



### FOR GOOD LISTENING

Don't be restricted to one tape for every kind of sound... Duratape® is the answer. It's high performance tape with its own built-in head cleaner. Low noise, moderate price. 30, 60, 90 and 120 minutes.

Professional Duratape® — For discriminating listeners. High density cobalt-energized, extended frequency. For 4-track stereo. 30, 60, 90 minutes.



### VOICETAPE™

Created especially for voice... dictation, lectures, conferences, rehearsals. In 12-cassette file pak or single box. 60 minutes.

### POWER WHEN YOU NEED IT

Alkaline Duracells®... with the extra power. Perfect for high drain uses... photoflash, cameras, radios, instruments, recorders. Up to 10 times longer life than zinc-carbon batteries.



### FLIPTAPE™

The bright, colorful tape. Captures the highs and lows of today's music. For general use too. Economical 3-paks... 60, 90 minutes.

# MALLORY

**MALLORY DISTRIBUTOR PRODUCTS COMPANY**  
a division of P. R. MALLORY & CO. INC.  
Box 1284, Indianapolis, Indiana 46206; Telephone: 317-636-5353



---

# Uncle Tom's Corner

By Tom Kneitel, K2AES/KQD4552

Uncle Tom answers his most interesting letters in this column.  
Write him at Electronics Illustrated, 1515 Broadway, New York, N.Y. 10036.

---

★ *My vote for the Useless Idea Gold Medal goes to the logging scales still found on many shortwave and FM receiver dials. I bet that they're never used. What say?*

Ken Greenberg  
Chicago, Ill.

I agree, especially the shortwave sets which list Rome, Prague, London, Peking, etc., on the dials. I once saw an FM receiver which listed the frequencies by channel numbers—or didn't you know that the FCC once set up FM channel numbers, just like TV? That was another Gold Medal idea.

★ *I'm a mobile CB nut using a Courier 23-Plus rig in my car. When I used the set as my base station there were no problems but now, in the car, it keeps popping the bulbs in the S-meter. Why?*

Arnie Freeman  
McKees Rocks, Pa.

Some of the early production runs of this rig—and it's a common problem for many brands—were noted for this trick. It's due to the fact that most car batteries actually deliver 13 volts or more when the engine's running. Increase the value of the resistor connected to the chassis behind the meter from 15 ohms-1 watt to 33 ohms-2 watts. Instant cure!

★ *There is a station I've heard using voice transmissions on CB channel 5 that identifies in Italian with the callsign ISA232. Is this a gag? Heard it only once with a weak signal. This was at 3 a.m.*

R.S. Brancatto  
Arlington, Va.

Can't say if it's a gag but there are Italian CB stations now and they are using the same

channels as U.S. stations. His callsign prefix would place him in Salerno.

★ *I like to watch TV Channel 3 coming from Santa Barbara to pick up certain locally blacked-out sports events. Problem is, although the video comes in clearly, there is absolutely no audio signal. TV set seems to work fine on all my local channels, it's this one DX channel which still defies me.*

Elliot V. Chang, WA6FRX  
Los Angeles, Calif.

Sounds like your tuner needs some tinkering with. Probably the situation can be cured by adjusting the audio slug. It looks like the set just isn't tuned to the center of the audio portion of the TV channel.

★ *I have a four-band regenerative AM-SW receiver covering 550 kc to 30 mc. When I connect my 100-ft. long-wire antenna to it, no matter where the set is tuned, all I can hear is my local 50-kw AM broadcast station. If I use a whip antenna, I still hear the local station, but not as loud. What can I do so that I no longer hear this station?*

David Kleinschmidt  
Parma, Ohio

Don't use any antenna. Problem is, most shortwave rigs aimed at the novice SWL just don't have the selectivity to prevent this kind of situation. My advice is to trade up as soon as possible.

**Flying Saucer Dept.** Back in 1966, NASA began tracking three satellites which they referred to as unknowns. They're still carried in official NASA records as catalog numbers 2428, 2429 and 2430. The vehicles are still zipping around, but nobody knows where

[Continued on page 22]

**LAFAYETTE Introduces the easy way to convert your present stereo system to 4-channel sound...**



**LAFAYETTE LA-524  
SQ Decoder/60-Watt Amplifier**

**Only  
79<sup>95</sup>**

With Built-in



Decoder Circuitry

\*TM of Columbia Broadcasting System, Inc.

**Just Off the Press!  
468 Pages!**

- 4-Channel Stereo Equipment
- Stereo Hi-Fi Systems
- CB Gear ● PA Equipment
- Tape Recorders and Players
- Auto Accessories ● TV's
- Test Equipment
- plus more . . .

Add universal 4-channel stereo capability to your present stereo system with the Lafayette LA-524 and a pair of rear channel speakers. Enjoy the new . . .

**SQ 4-Channel Records**—the LA-524 has a built-in SQ Decoder. SQ records are fully compatible, and your present cartridge and turntable will probably be just fine. The LA-524 has great specs, too. 60 watts (20-20,000 Hz  $\pm$  1.5 db) of rear channel power for . . .

**Discrete 4-Channel Stereo**, when you connect a discrete 4-channel tape source. Plus, there's our exclusive "Composer" circuit for satisfying . . .

**Derived 4 Dimensional Sound** from your conventional 2-channel stereo sources. Check out the LA-524 at your nearest Lafayette store, and have 4-channel stereo at home tonight.

**FREE!**

**LAFAYETTE 1973 Catalog 730**

Lafayette Radio Electronics  
Dept. 29092, P.O. Box 10, Syosset, L.I., N.Y. 11791


Send my FREE Lafayette Catalog 730 29092

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

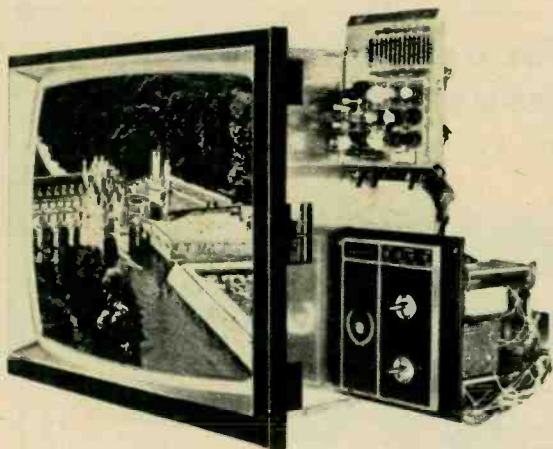

## AUTOMATED COLOR TV.

New top-of-the-line color TV from Heathkit offers 25-in. diagonal screen, detent UHF tuning, pushbutton electronic VHF/UHF scanning, optional wireless remote control, normal or wide-angle color demodulation, solid-state circuit modules. Set includes dot generator and VOM. \$599.95. Heath Co., Benton Harbor, Mich.




**Boost For Broadcasting.** FM wireless condenser mike, Model DM-55, has solid-state FM transmitter tunable from 88 to 108 mc, 9-V battery, is FCC approved. \$21.95. E-V/Game Inc., Freeport, N.Y.



**Noise-Free Deck.** Model KX-700 stereo cassette deck includes Dolby noise reduction system and extra-hard superferrite record-playback head, bias selector switch. Kenwood Electronics, Gardena, Calif.


# Electronic Marketplace

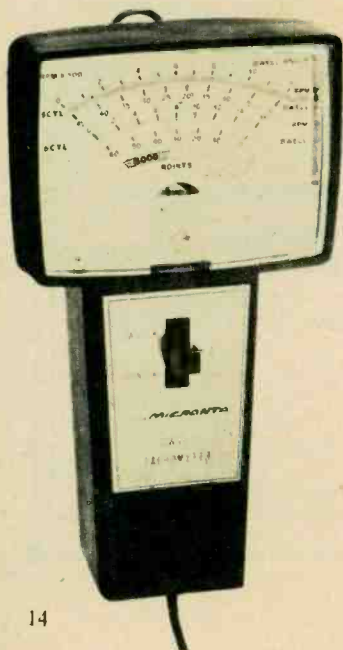

**Three-in-one Value.** Micronta tester for automotive buffs provides accurate readings of dwell angle and engine speed, checks condition of points. \$17.95. Radio Shack, Fort Worth, Tex.



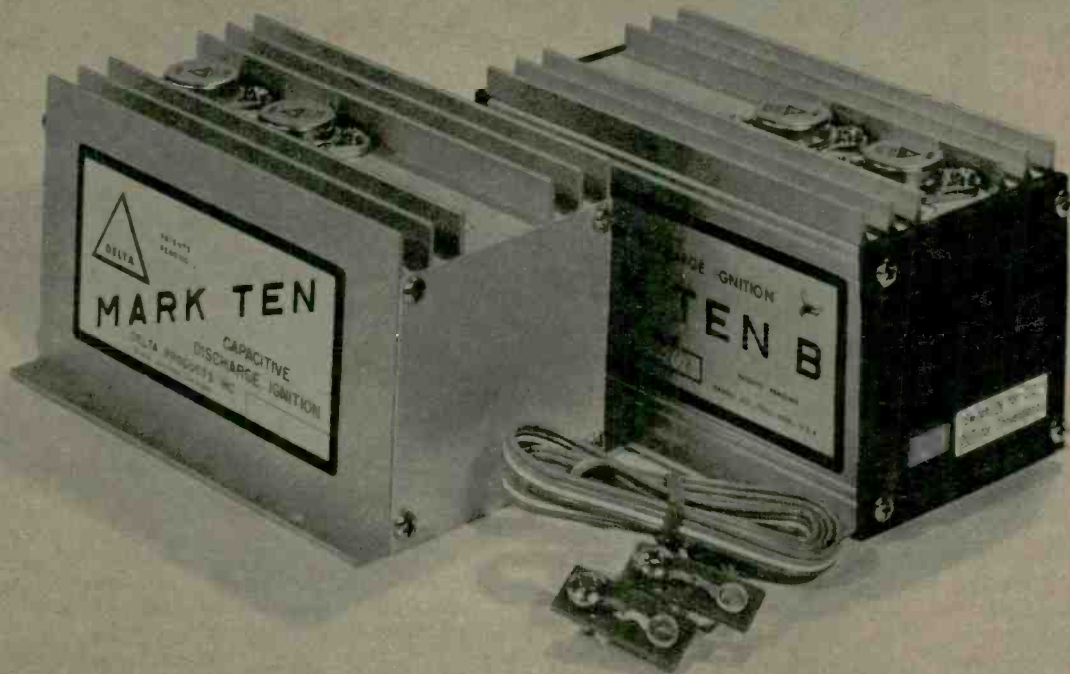**Economical Listening.** Marantz has entered headphone market with its Model SD-1 stereo phones. Impedance is 8 ohms, frequency response, 20 cps to 20 kc. \$29.95. Marantz Co., Sun Valley, Calif.



## Save money and improve car performance at the same time.

Maintenance costs go down and performance increases when you put a Delta Mark Ten Capacitive Discharge Ignition System on your car.

For eight years we've been telling you about the tremendous advantages of CDI systems. We've promised and delivered better performance for cars, boats and trucks. Hundreds of thousands of satisfied customers testify to that fact. However during these eight years, we've been asked over and over again, "If CDI systems are so great, why doesn't Detroit adopt them?" It's taken a long time, but finally Detroit has recognized the value of the CDI system. Chrysler, long noted for excellence in engineering, is now installing electronic ignitions in new cars. Have you seen their ads? Heard their commercials? They're repeating what we've said for eight years. *Electronic ignition systems not only improve performance, but eliminate the need for most tune-ups.* If you're not buying a new car, but want new car performance, put a Mark Ten or Mark Ten B on your present automobile. If you're purchasing a new car with no CDI system, install a Mark Ten or Mark Ten B and enjoy the benefits of low maintenance and increased performance.

### HERE'S WHAT A MARK TEN WILL DO FOR YOU:

Mark Ten and Mark Ten B—up to 20% increase in gasoline mileage  Eliminates 3 out of 4 tune-ups  Installs in only 10 minutes  Spark plugs last 3 to 10 times longer  Dramatic increase in performance  Promotes more complete combustion  Instant starts in all weather.

Mark Ten B—Improves combustion, reducing contaminants  Handy switch with redundant contacts for instant return to standard ignition  Applicable to ANY 12 volt negative ground engine  Eliminates starting and idle problems  Longer spark duration during cranking and idling.

*Superior Products at Sensible Prices*

Mark Ten (Assembled) \$44.95 ppd

Mark Ten (Deltakit) \$29.95 ppd

Kit available in 12 volt only, positive or negative ground

Mark Ten B \$59.95 ppd  
(12 volt negative ground only)

Order today!



Dept. EI  
**DELTA PRODUCTS, INC.**

P.O. Box 1147 / Grand Junction, Colo. 81501  
(303) 242-9000

Please send me literature immediately:

Enclosed is \$\_\_\_\_\_  Ship ppd.  Ship C.O.D.

Please send:

\_\_\_ Mark Ten B @ \$59.95

\_\_\_ Standard Mark Ten (Assembled) @ \$44.95

\_\_\_ 6 Volt: Neg. Ground Only \_\_\_ Positive Ground

\_\_\_ 12 Volt: Specify \_\_\_ Negative Ground


\_\_\_ Standard Mark Ten (Deltakit®) @ \$29.95  
(12 Volt Positive Or Negative Ground Only)

Car Year \_\_\_\_\_ Make \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

City/State \_\_\_\_\_ Zip \_\_\_\_\_

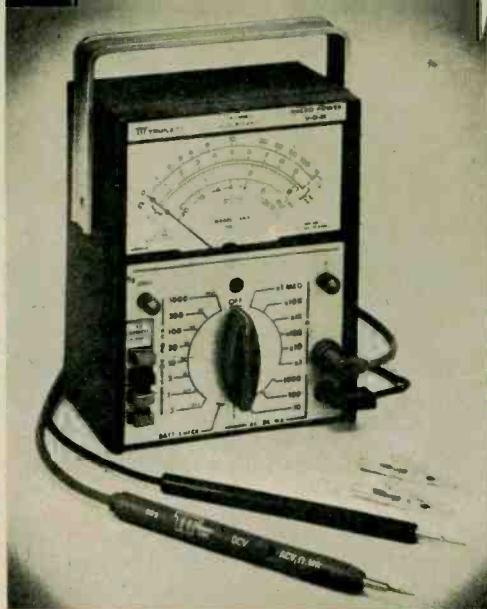


**No Current Down the Drain.** Battery-operated FET-VOM, Model 603, has one probe for all functions (DC, AC, ma, ohms), may be left on continuously. \$150. Triplett, Bluffton, Ohio.



**Listening Pleasure.** Model 4515 cassette recorder has AM/FM radio, built-in condenser mike, ALC, works off rechargeable batteries. \$99.95. Wollensak Div. of 3M Co., St. Paul, Minn.
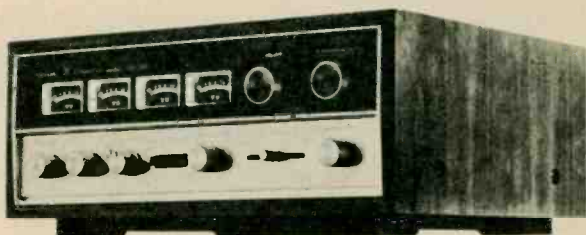
## Electronic Marketplace

**Three Ways to Get Four.** Sansui offers reproduction of discrete, matrix or synthesized four-channel programming via its Model QS500 four-channel converter and control center. User adds pair of rear-channel speakers. Output is 33 watts per channel into 8 ohms. \$289.95. Sansui Electronics Corp., Woodside, N.Y.



**CB Walkie-Talkie.** CBers get five watts of power on three channels at push of a button with the Model CB-505 portable transceiver from Ray Jefferson. Unit is supplied with transmit and receive crystals for channels 9, 11 and 21. Other channels (for 11 or 21) are optional. \$89.95. Ray Jefferson, Philadelphia, Pa.

**Finding Your Way.** Gladding Islander is portable radio direction finder which covers six bands: AM, FM, beacon, 2-4 mc, aircraft, VHF marine including weather. Includes RF gain, AFC. \$139.95. Pearce-Simpson, Miami, Fla.

[Continued on page 24]





# He made it with his own two hands.

There's a name for a place that employs men and women with serious physical and mental handicaps. It's called a "sheltered workshop."

As you might expect, "sheltered workshops" are an unusual kind of business.

But as you might or might not expect, they do an unusual kind of work. Excellent.

In fact, sheltered workshops consistently turn out work every bit as

good as more usual kinds of businesses. And priced just as low.

If your company farms out any of its work, we'd like to invite you to give a sheltered workshop a chance to bid on it—without obligation, of course.

(For more information, write to Workshop, c/o HURRAH, Box 1200, Washington, D.C. 20013.)

If you like their bid, you may decide to give them a chance to do

some of your work.

In which case, you'll be helping a lot more people "make it" with their own two hands.

And, if you like good work, helping yourself in the bargain.

The State-Federal Program of Vocational Rehabilitation.

Help Us Reach & Rehabilitate  
America's Handicapped


**HURRAH**



The U.S. Department of Health,  
Education, and Welfare.

Advertising contributed for the public good.
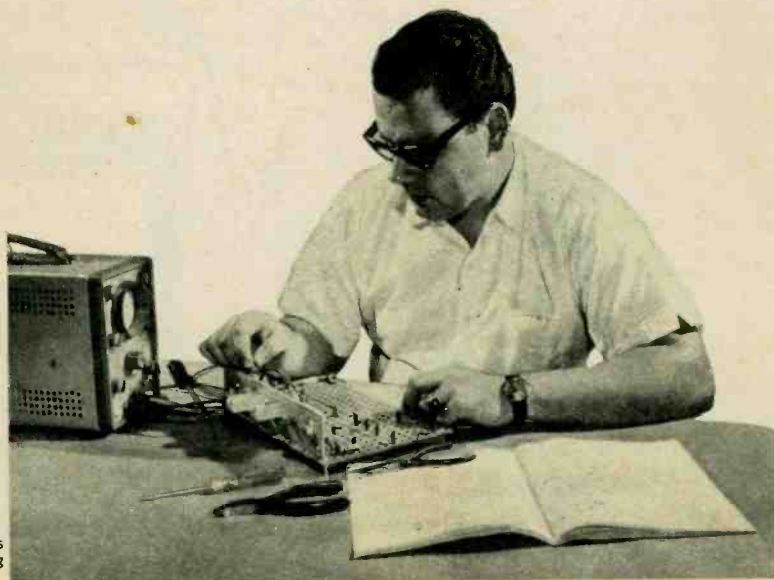
# 10 Reasons why RCA Home Training is your best investment for a rewarding career in electronics:



Performing transistor experiments  
on programmed breadboard – using  
oscilloscope

## 1 LEADER IN ELECTRONICS TRAINING

When you think of electronics, you immediately think of RCA... a name that stands for dependability, integrity, and pioneering scientific advances. For over half a century, RCA Institutes, Inc., a subsidiary of RCA, has been a leader in technical training.

## 2 RCA AUTOTEXT TEACHES ELECTRONICS FASTER, EASIER, ALMOST AUTOMATICALLY

Beginner or refresher, AUTOTEXT, RCA Institutes' own method of programmed Home Training will help you learn electronics more quickly and with less effort, even if you've had trouble with conventional learning methods in the past.

## 3 WELL PAID JOBS ARE OPEN TO MEN SKILLED IN ELECTRONICS

RCA Institutes is doing something positive to help men with an interest in electronics to qualify for rewarding jobs in this fascinating field. There are challenging new fields that need electronics technicians... new careers such as computers, automation, television, space electronics where the work is interesting and earnings are greater.

## 4 WIDE CHOICE OF CAREER PROGRAMS

Start today on the electronics career of your choice. On the attached card is a list of "Career Programs", each of which starts with the amazing AUTOTEXT method of programmed instruction. Look the list over, pick the one best suited to you and check it off on the card.

## 5 SPECIALIZED ADVANCED TRAINING

For those already working in electronics or with previous training, RCA Institutes offers advanced courses. You can start on a higher level without wasting time on work you already know.

## 6 PERSONAL SUPERVISION THROUGHOUT

All during your program of home study, your training is supervised by RCA Institutes experts who become personally involved in your efforts and help you over any "rough spots" that may develop.

## 7 HANDS-ON TRAINING

To give practical application to your studies, a variety of valuable RCA Institutes engineered kits are included in many programs. Each kit is complete in itself. You never have to take apart one piece to build another. They're yours to keep and use on the job.

## 8 FCC LICENSE TRAINING—MONEY BACK AGREEMENT

Take RCA's Communications Career program—or enter with advanced standing and prepare immediately for your 1st, 2nd, or 3rd class FCC Radio Telephone License examinations. RCA Institutes money-back agreement assures you of your money back if you fail to pass the FCC examination taken within 6 months after completing the course.

## 9 CONVENIENT PAYMENT PLANS

You get a selection of low-cost tuition plans. And, we are an eligible insti-

tution under the Federally Insured Student Loan Program.

## 10 RCA INSTITUTES IS FULLY ACCREDITED

RCA Institutes is an accredited member of the National Home Study Council. Licensed by N. Y. State—courses of study and instructional facilities are approved by the State Education Department.

**VETERANS: TRAIN  
UNDER NEW GI BILL**

**SEND ATTACHED POSTAGE PAID CARD TODAY! FREE DESCRIPTIVE BOOK YOURS WITHOUT OBLIGATION!**

If reply card is detached, send this coupon today.

RCA INSTITUTES, INC.  
DEPT. 234-209-0  
320 W. 31 ST.  
NEW YORK, N. Y. 10001

Please send me FREE illustrated career catalog. I understand that I am under no obligation.

Name \_\_\_\_\_

Address \_\_\_\_\_



City \_\_\_\_\_

State \_\_\_\_\_ ZIP \_\_\_\_\_

Age \_\_\_\_\_


Veterans: Check here

Construction of Multimeter.

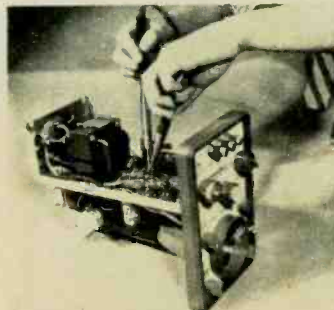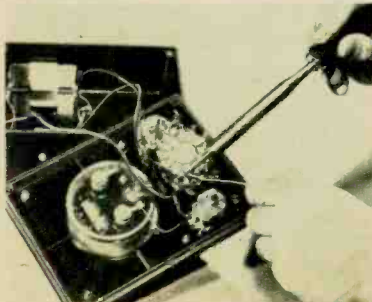

Construction of Oscilloscope.

Temperature experiment with transistors.

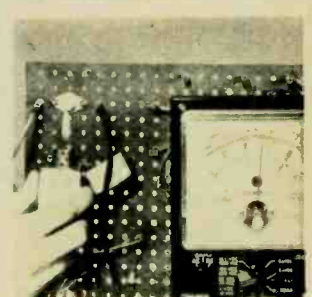

## Uncle Tom's Corner

they came from. Last year NASA quietly added two additional mystery satellites to the list and the agency is currently tracking them with interest. Officially known by NASA catalog numbers 5309 and 5310, NASA frankly admits that they have not been identified with any launch or country of origin. Their orbits cannot be pinned down to any known launch area. Where are they from, why are they there? NASA doesn't know either. Any guesses?

★ *What do you know about a shortwave broadcaster calling himself The Voice of The Purple Pumpkin?*

*George Bennett  
Federsburg, Md.*

It's a bootleg station which appears every few years, I suspect, with a different operator and location. It has been on recently operating from somewhere in the national capital area using a frequency near 7345 kc. Some-

times they ID with the callsign WSWL. Operating times vary but I've heard them on in the early and late afternoons. Strictly a teenage prank. The joke has lived long past any humor which might have once existed.

★ *Someone recently told me that the Illinois State Police have added some new channels for mobile operations. Is this true? How can I find out what these are?*

*Dennis Walbach  
Libertyville, Ill.*

Tune to 42.44 mc and 155.46 mc to hear the increased mobile activity from this agency. Incidentally, a catalog showing extensive directories of police, fire and other emergency radio systems throughout the country is available by sending a stamped, self-addressed No. 10 envelope to CRB Research, Inc., P.O. Box 56-EX, Commack, N.Y. 11725.

★ *Voltage and current seem to be indirectly proportional, so if I take a 250-volt 2-ampere fuse, can it be used at 125 volts, 4 amperes?*

*Charles Brunkhorst  
Paris, Texas*

# unmistakably 2



and error free square roots combined with both constant and independent data memories, exchange operands, and negative sign entry capabilities make the 1440 kit calculator remarkably unparalleled, while the highest quality American parts, comprehensively detailed instructions, built-in interfacing for completely compatible printing and programming modules, and a price of \$199.95 (assembled \$249.95) establish the 1440 as the only kit calculator with high caliber ability and the only unit available anywhere with so much power and such a reasonable price.

**MITS**

Micro Instrumentation & Telemetry Systems, Inc.

2016 San Mateo N.E. Albuquerque, New Mexico 87110 (505) 266-2330

Bank Americard and Master Charge Accepted

## Uncle Tom's Corner

Sorry, Charlie, no dice. The voltage rating relates to the voltage breakdown or the arc created when the fuse blows. A 2-amp 250-volt fuse will still carry only 2 amps on a 120-volt circuit. The carrying capacity depends only on the current which, when excessive, generates sufficient heat to melt the fusing element.

★ *What is the business with the shortwave station which has a lady reading long strings of numbers? The one I heard was on 6730 kc at 0300 GMT. She said, "5 1 9 1 2 3 4 4 7 5 9 8 5." From then on she named a list of numbers too great to be put in this letter.*

*Steve Leary  
Akron, Ohio*

You should have sent along the wild ones because the ones you included in your letter were sort of dull.

★ *Is there any point or satisfaction to be obtained in writing you a serious letter.*

*Ted Boglowski  
Seattle, Wash.*

The glow in knowing that you've accomplished a long cherished dream.

★ *Do you agree with those who feel that plug-in modules are the way of the future? This would seem to imply that all our electronic equipment—including radios, color TVs, CB gear, ham radio stations, test equipment etc.—may arrive at a point in technology where it will be cheaper to buy new rather than replace what's ailing.*

*Michael Rogers  
Muncie, Ind.*

Mike, you're biting off more than I care to chew. It's true, even now, that some items—like pocket transistor radios and battery-operated cassette players—are better thrown away than serviced. Their PC boards are packed so tight with components from Nippon that, next to them, a jeweler's screwdriver looks like a California Redwood. Getting out a bad component and replacing it with a good one (assuming you can get the part) is hardly worth the effort. But plug-in modules can be thrown away, yet you keep all the good stuff. See what I mean?



We know today's CBer is looking for real value. So we redesigned our Messenger 123 where it counts—on the inside. Our engineers gave the model "A" new improved circuitry. With a new acoustically isolated speaker and voice-tailored audio that cuts noise—increases clarity. Plus a new ceramic selectivity filter that rejects adjacent channel chatter. And, of course it has built-in electronic speech compression for famous Johnson "talk power." At \$149.95, the Messenger 123A is a real value. And come to think about it, it's still a great looking CB radio just the way it is.

**Messenger 123A.**  
**New where it counts:**  
**Inside.**



**JOHNSON**

Waseca, Minnesota 56093

Full 1-year parts and labor warranty—  
backed by over 550 authorized service centers nationwide.

LIVE IN THE WORLD OF TOMORROW . . . TODAY!  
**UNUSUAL BARGAINS**  
 NEW PRODUCTS • NEW MATERIALS • NEW IDEAS

**BOXED "LIGHT SHOW"—SAVE \$18!**



Terrific price reduction brings you a fabulous Lumia Light Box under \$12! Creates ever-changing out-of-world colored forms & patterns. Hypnotic & relaxing as a glowing fireplace. They merge, turn, dance in spellbinding, soothing beauty. Dramatic conversation piece for living room, rec-room, den, bedroom, bookshelf, waiting room. Especially effective amid wall picture group. Handsome 11 1/2" sq. x 7" dp. walnut-

finished case, quiet low-rpm motor. 110-120v AC. **—\$11.95 Ppd.**  
 Stock No. 71.180EB

**BLACK-LIGHT MIGHTY MITES**



Relatively small (12") fixtures give surprisingly bright black-light. Mirror-finished reflector makes instant starting. 8-watt, high-intensity bulb look like 40-watter. Up to 5,000 hours of safe, long-wave (3600A) black-light to really turn on parties, light & theatrical shows, psychedelic decors, holiday decorations. Shockproof end-caps remove for safe, easy replacement of bulb and starter. Stands upright or horizontal. Aluminum case.

Stock No. 71.274EB **—\$14.95 Ppd.**  
 DELUXE OUTDOOR/INDOOR MODEL  
 Stock No. 71.299EB **—\$19.95 Ppd.**

**TAPE-SLIDE SYNCHRONIZER**



Coordinate tape recordings with slide series. Hook up stereo recorder to remote control projector and TSS—then record what you wish for each slide. Playback and TSS AUTO-MATICALLY changes slides in synchrony with tape. Your presentation "gives itself." Perfect for sales meetings, lectures, & "talking albums" of child's growth—add new dimension to vacations, parties . . . anywhere.

Stock No. 41.222EB **—\$21.95 Ppd.**  
 6-FT. CONNECTOR CORDS **—\$4.50 Ppd. each**  
 Kodak Proj. (#60,804EB) Airrequisit (#60,805EB)

**\$8.95 ELECTRONIC STROBE!**



Hand-sized solid state electronic strobe light at fantastically low price. Produces bright psychedelic effects like larger, far more expensive Xenon strobes, yet it's just 2 3/4 x 4 x 1 3/4" thick. Adjustable flash rate, approximately 3-10 flashes per second. Make stop motion effects, pointers come alive. Great to take with you to parties, dances, outings, etc. Requires 2 0v transistor batt. (not incl.). Instructions.

Stock No. 41.443EB **—\$8.95 Ppd.**  
 4 REPLACEMENT LAMPS . . . P-41.444EB **—\$1.00 Ppd.**

**TURN BOTTLES INTO TREASURES**



Be ecological and artistic with this low-cost Bottle Cutter Kit. Easiest-to-use one we've found. Make saleable, attractive glasses, lamps, dishes, candleholders, vases from ordinary no-return smooth-surface bottles, jars. Cut any bottle safely, easily in less than 5 minutes for fun, profit, home decorations with just an ice cube and this superior kit. Includes cutter (3 3/4 x 7 3/4 x 2 1/4"), candle, 2-oz. grinding powder, smoothing cloth. Complete instructions.

Stock No. 71.475EB **—\$10.95 Ppd.**

**MAIL COUPON FOR GIANT FREE CATALOG!**

**148 PAGES • MORE THAN 4,000 UNUSUAL BARGAINS**

Completely new 1972 edition. New items, categories, illustrations. Dozens of electrical and electromagnetic parts, accessories. Enormous selection of Astronomical Telescopes, Unique lighting and ecological items, Microscopes, Binoculars, Magnifiers, Magnets, Lenses, Prisms. Many surplus items.

**EDMUND SCIENTIFIC CO., Barrington, N.J. 08007**


Please rush Free Giant Catalog "EB"

Name \_\_\_\_\_  
 Address \_\_\_\_\_  
 City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

**EDMUND SCIENTIFIC CO.** 300 EDSCORP BLDG. BARRINGTON, NEW JERSEY 08007  
 ORDER BY STOCK NUMBER • SEND CHECK OR MONEY ORDER • MONEY-BACK GUARANTEE

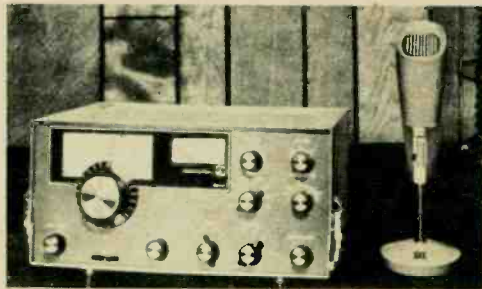**Electronic Marketplace**

**In on the Action.** Model FPM-300 amateur transceiver from Hallicrafters covers 80 through 10 meters. Aside from fixed or mobile amateur communications, unit is said to be useful for networks such as CAP (Civil Air Patrol), MARS (Military Affiliate Radio Stations) and RACES (Radio Amateur Communications Emergency




Service). Rig weighs 25 lb., features solid-state circuitry, speech compressor circuit, is rated at 250 watts PEP for SSB, 180 watts CW. 1M products 30db down. Mounting bracket optional. \$595. Hallicrafters Co., Rolling Meadows, Ill.

**In and Out with Eight-Track.** Model TC-228 stereo eight-track cartridge deck permits both recording and playback of eight-track cartridges. New from Sony, the deck features a three-way ejection system that can be programmed to work after each run of each program, after the total run of all programs, or manually. Recorder shuts off when cartridge is ejected. Convenience AC outlet for amplifier or sound system can be programmed to shut off, too. Features in the record mode include level control, VU meters, fast forward, pause control (with lock). Also included are indicator lights, auxiliary inputs, microphone jacks, stereo headphone monitor jack, record



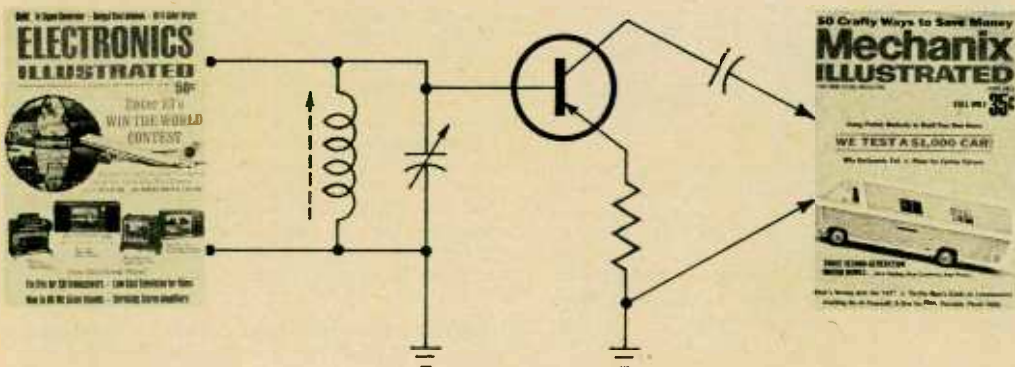interlock and non-magnetizing record head. Walnut cabinet is included. \$169.95 Superscope, Inc., Sun Valley, Calif.



You've got the right hookup if you read **ELECTRONICS ILLUSTRATED**. But let us introduce you also to **MECHANIX ILLUSTRATED**, EI's companion publication. MI, America's favorite how-to-do magazine, tunes in electronics sometimes but also deals with the latest on cars, home improvements, family finances, workshop projects, health, the outdoors, recreation vehicles, boating, snowmobiles, power and hand tools and much, much more.

EI readers are invited to cash in on a special MI offer. Put in for one year—12 big issues—of MI, and it will cost you just \$2.95. We'll bill you later. But if you send in \$2.95 today, we'll throw in one bonus issue. That's 13 information-packed issues in all! Take advantage of this deal pronto!

**MECHANIX ILLUSTRATED, Circulation Dept.,**  
**Fawcett Bldg., Greenwich, Conn. 06830.**

EI

**Please send me MI:**

- Twelve issues—one year.**  
**\$2.95. Bill me later.**
- Thirteen issues—one year**  
**plus one bonus issue. \$2.95.**  
**Payment enclosed.**
- I am now a subscriber, ex-**  
**tend my subscription.**

**NAME** \_\_\_\_\_

**ADDRESS** \_\_\_\_\_

**CITY** \_\_\_\_\_ **STATE** \_\_\_\_\_

**ZIP CODE** \_\_\_\_\_




## Service Tips

By Art Margolis

**WHEN** you change the resistance range on your ohmmeter while checking forward and reverse transistor junction resistance, the readings vary for each range. The readings you get are only relative to each other since an ohmmeter cannot accurately read the true resistance of a semiconductor junction. Readings vary between meter models and from scale-to-scale on the same ohmmeter.

When soldering components to a printed-circuit board, you'll sometimes fill the wrong hole in the board with solder. To open the hole, straighten a paper clip and push it into the blocked hole as far as it will go. Heat up your low-wattage pencil iron, apply the tip to the clip and let it heat up. When the paper clip reaches the solder's melting point, push it through the hole. First try the clip out to make sure solder won't stick to it.

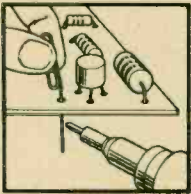

If your pop-up toaster blackens bread on one side but hardly tans it on the other, it's time to examine the elements. Even if they seem to be lighting up properly and nothing seems amiss, the elements probably have aged. The resistance of some elements has increased and they are not delivering as much heat as before, while the rest brown as before. New elements will cure the problem.

Beginning to collect components for an extensive electronic project? Arrange all parts for easy accumulation and later retrieval. The resistors, capacitors and plugs that you had such a hard time scrounging up can easily get lost. Cookie pans and ice cube trays appropriately labelled are handy receptacles for parts.


Service technicians would much rather pull only the color TV chassis when a combination home entertainment/color TV has to be brought to the shop. If you have to service this kind of set and just pull the chassis, keep the limitations of any test jig in mind. Problems traced down to deflection, linearity and brightness are probably caused by the jig itself. When the test jig creates servicing difficulties, the answer is to go back and get the rest of the set, no matter how bulky.

When you are checking the heating element in a partially disassembled hair dryer, do not energize the element for long without blowing air across it. Otherwise, the heater can overheat and melt plastic parts nearby.

*the tape that  
turned the  
cassette into  
a high-fidelity  
medium*




**TDK SUPER DYNAMIC (SD) TAPE**

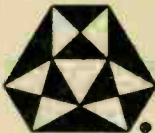
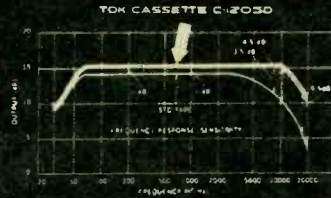
# TDK

Until TDK developed *gamma ferric oxide*, cassette recorders were fine for taping lectures, conferences, verbal memos and family fun—but not for serious high fidelity.

Today you can choose among high-quality stereo cassette decks.



The new magnetic oxide used in TDK Super Dynamic tape distinctively differs from standard formulations in such important properties as coercive force, hysteresis-loop squareness, average particle length (only 0.4 micron!) and particle width/length ratio. These add up to meaningful performance differences—response capability from 30 to 20,000 Hz, drastically reduced background hiss, higher output level, decreased distortion and expanded dynamic range. In response alone, there's about 4 to 10 db more output in the region above 10,000 Hz—and this is immediately evident on any cassette recorder, including older types not designed for high performance. There's a difference in clarity and crispness you can hear.

Available in C30SD, C60SD, C90SD and C120SD length.

**TDK ELECTRONICS CORP.**  
LONG ISLAND CITY, NEW YORK 11103



While they last, yours to use for 2 weeks' trial:

# AMAZING MOTORIZED BELL & HOWELL AUTOMATIC ELECTRIC-EYE CAMERA



Thousands previously sold at \$99<sup>95</sup>! But thanks to our special purchase, you get the complete outfit for

## only \$79<sup>95</sup>

- Spring motor for rapid-fire shooting of 20 pictures
- Around-the-lens electric eye automatic exposure
- Exposure needle in brilliant viewfinder window signals when enough light to shoot
- Superb f/2.8 wide-angle lens captures entire scene in sharp focus
- Split-frame exposure yields twice as many slides or prints from standard 35mm. film

Here's everything you wanted in a camera, yours to try FREE for two whole weeks. It's the amazing BELL & HOWELL DIAL 35.

So slim it slips into a man's coat pocket or woman's handbag. So sensitive it gives you correctly exposed pictures every time, with no complicated adjustments. So quick-shooting, you can get up to 20 PICTURES A MINUTE just by pressing the shutter over and over again.

Spring motor gives you rapid-fire shooting without battery power, a unique feature. Enables you to capture all the changing expressions on faces of family and friends.

Fast, needle-sharp Canon f/2.8 wide-angle lens captures the whole picture. Four shutter speeds up to 1/250th second. Around-the-lens electric eye measures the light, adjusts the lens for correct exposure. Needle in brilliant viewfinder tells you if there's enough light to shoot.

**STRETCHES YOUR PICTURE-TAKING DOLLAR**  
You get twice as many jumbo pictures from the same amount of film! Uses regular 35mm. film, black and white, color transparency, or color prints, but gives you two pictures per frame instead of one. 20-exposure roll yields

up to 40 jumbo prints or slides, 36-exposure roll gives you up to 72 pictures!

### AN EXCITING CONVERSATION PIECE

Because there has never been another camera in the world like this one, so completely different in appearance and operation, your friends will be impressed and fascinated. They'll never dream you were able to buy it for so little through this special offer.

### TRY IT FOR 2 WEEKS—THEN DECIDE

Prove to yourself what a thrill owning this exciting camera can be. Mail coupon with a refundable payment of \$79.95 plus \$1.35 for shipping and handling (total \$81.30). Or use your American Express or Master Charge. We'll send you the complete outfit for two weeks' trial. Use the FREE FILM to make 24 vivid jumbo prints. Then if you're not delighted, return outfit within 2 weeks and your entire deposit will be promptly and cheerfully refunded. That's how certain we are you'll want to keep this great camera outfit for the pictures of a lifetime. But hurry—supplies are limited. Orders filled on a first-come first-served basis. Mail coupon now.

## COMPLETE OUTFIT INCLUDES ALL THIS



**DELUXE CARRYING CASE.** Rich black form-fitting case with chrome trim holds camera safely.



**2 SLIDE GIFT PRESENTATION KITS:** Vinyl cases with folding slide viewer and slide pockets.



**FLASH MOUNT AND FLASH CUBE.** Slips easily onto top of camera. Cube rotates manually for 4 flash shots.



**FREE COLOR FILM.** 35mm. color film gives you up to 24 sparkling jumbo color prints.



**CONVENIENT WRIST STRAP** lets you carry camera safely and conveniently, with or without case.



**BATTERIES.** CdS battery for Electric Eye and 2 batteries for flash cube mount.

.....USE MASTER CHARGE/AMERICAN EXPRESS.....

**HAMILTON HOUSE INC.**  
DEPT. 685-E9,  
COS COB, CONN. 06807

Please send me the complete Bell & Howell Dial 35 Motorized Camera outfit to try for 2 weeks. I am enclosing \$81.30 (\$79.95 plus \$1.35 for shipping and handling) with the understanding that this entire sum will be promptly and cheerfully refunded, with no questions asked, if I decide to return the outfit after trying it. The free film included is mine to keep and use whether I return the outfit or not.  
Conn. residents add appropriate sales tax.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

WANT TO CHARGE IT ON YOUR BANK CHARGE CARD? JUST FILL OUT BELOW

American Express  Master Charge

Card No. \_\_\_\_\_ Exp Date \_\_\_\_\_

Master Charge Bank No. \_\_\_\_\_  
(see lower left of card)

Signature \_\_\_\_\_



## It stopped the traffic in Times Square.

We took our new ST-5130 FM stereo/FM-AM tuner to Times Square, where traffic — and ignition interference noise — are at their peak. Then with a flick of a switch, we stopped the noise dead.

That switch cuts in our new, exclusive, Impulse Noise Suppression circuit. It instantaneously cuts out the man-made impulse noises that can plague FM reception.

With this background interference gone, it's easy to hear and appreciate the rest of the 5130's super-tuner performance. The numbers are unbeatable: 1.5


uV IHF, sensitivity, 1.0 dB capture ratio, 100 dB selectivity, and 100 dB rejection of images, i.f., and spurious response (with equally remarkable AM performance, of course).

And you'll also like such features as the 5130's oscilloscope output jacks for multipath indication, and it's independently-controlled headphone jack.


Impulse Noise Suppression. Hear the difference it makes, at your nearby Sony Dealer. Sony Corporation of America, 47-47 Van Dam Street, Long Island City, N.Y. 11101.
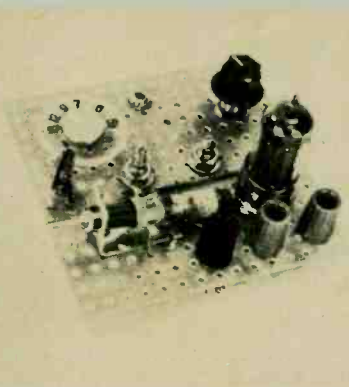
### New **SONY ST-5130 FM Stereo/FM-AM Tuner**


**Tube, transistor and IC projects  
for hobbyists at all levels.**



**1-Tube Radio for SWLs**

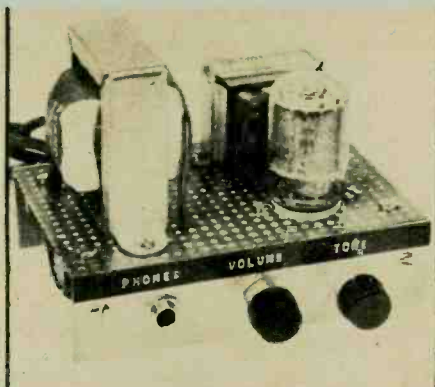


**1-Tube Phono Amplifier**

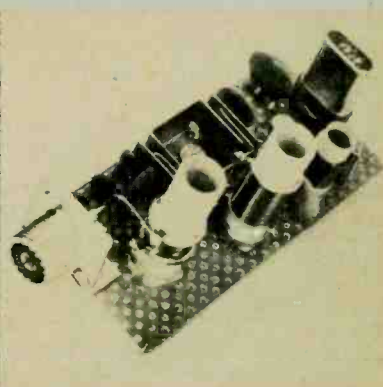

**Flea-Power Ham Transmitter**

*Build-It Special! Six Great Projects*

**CB Converter for Your Car**

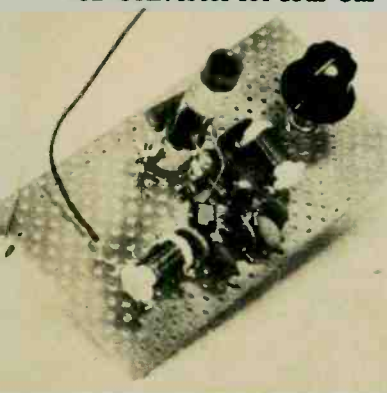

**One-IC Home Intercom**



**One-IC Signal Tracer**



**L**IKE popular songs that become classics, the six Build-It Specials on these pages are representative of the electronic experimenter's all-time favorites. For some of the projects, popularity outweighs technical sophistication. But this doesn't make any one of the Build-It Specials less versatile—or fun to put together. We've updated these old favorites with revamped circuitry to take advantage of up-to-date components. You don't have to follow layouts exactly. As you can see, anything goes.


# 1-Tube Radio for SWLs

**O**UR first project is a regenerative, 3-band receiver which was quite popular back in the early days of radio. The circuit, which tunes the broadcast band, 3 to 8 mc and 8-14 mc, uses a filamentary-type tube just like the original versions. The tube, labelled V1, is a pentode, or five-element device. This particular class of tube does not have a separate cathode. Instead, electrons are supplied directly by the battery-powered filament. After boiling off the filament surface, the electrons are attracted to the plate, as in any other vacuum tube.

Radio frequencies flowing to the antenna terminal are tuned with variable capacitor C1 and the primary coil of L1-L3 (depending on which tuning inductor is selected by band-switch S1). The tuned signal is injected into the control grid of V1 via components C2 and R1. Both components help the tube self-bias on strong incoming signals.

The injected signal is amplified in V1 and appears at the plate terminal. At this point, the signal is fed back to the corresponding RF coil. If coils L1-L3 are wound with primary and secondary windings in-phase, the amplified signal will be added to the incoming signal. The amount of RF fed back to the


[Continued on page 97]

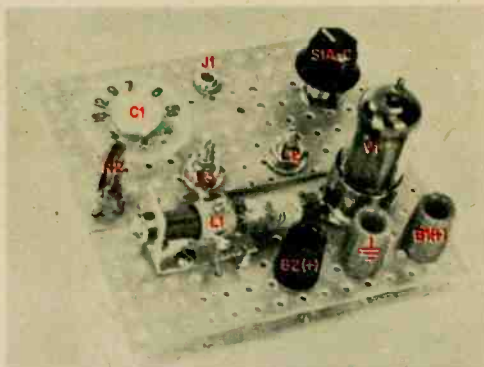

Layout is not critical. You can add vernier dial to C1's shaft for easier, more-accurate tuning.
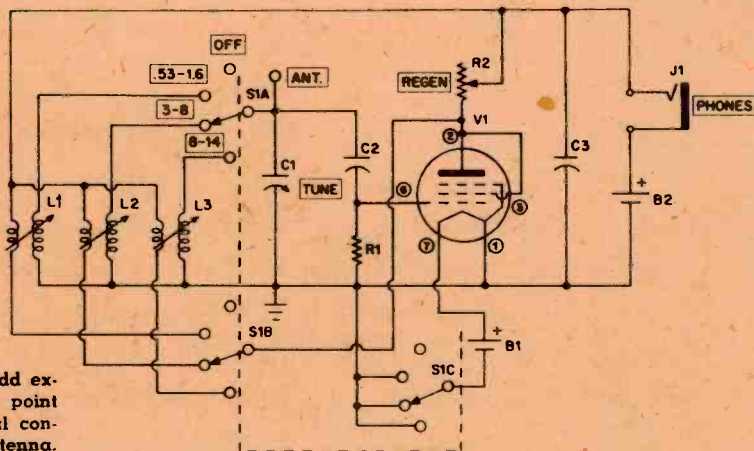
## PARTS LIST

- B1—1.5 V D-cell
- B2—45 V battery
- C1—13-365  $\mu\text{f}$  single-gang, solid-dielectric variable capacitor
- C2—100  $\mu\text{f}$  disc ceramic
- C3—0.0047  $\mu\text{f}$  disc ceramic
- J1—Phone jack
- L1—Ferrite antenna (see text)
- L2—3-8 mc antenna coil (see text)
- L3—8-14 mc antenna coil (see text)
- R1—1,000,000 ohms,  $\frac{1}{2}$  watt
- R2—100,000-ohm, linear-taper miniature pot
- S1—3-pole, 4-position non-shorting rotary switch
- V1—1U4 tube
- Misc.—3 five-way universal binding posts, perfboard, push-in clips, knobs, earphone, tube socket, etc.




For best reception, add external ground to point shown. ANT terminal connects to outdoor antenna.
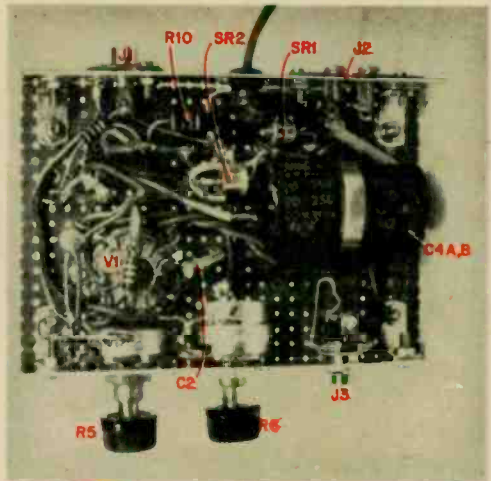
# 1-Tube Phono Amplifier

**O**UR One-Tube Phono Amplifier operates from a ceramic or crystal phono cartridge. It can produce approximately 1 watt of output audio power and will feed either a speaker or headphone. The input circuit, consisting of resistors R1 and R2, limits voltage applied to the triode grid and also helps to equalize audio signals from the cartridge.

After amplification in the triode section, labelled in the schematic  $\frac{1}{2}$ V1(T), audio passes through the tone-control network. As control R5 (Tone) is turned, it brings C2 [Continued on page 97]



Wiring of phono amplifier is point-to-point. Keep input's shielded lead away from output terminals.

## PARTS LIST

Capacitors: 500 VDC disc ceramic unless otherwise noted

C1—0.005  $\mu$ f

C2—25  $\mu$ f, 12 V electrolytic

C3—0.0033  $\mu$ f

C4 A, B—Dual 20-20  $\mu$ f, 250 V electrolytic

C5—0.001  $\mu$ f

J1—phone jack

J2—Two-terminal, screw-type terminal strip

J3— $\frac{1}{4}$ -in. phone jack

Resistors:  $\frac{1}{2}$  watt, 10% unless otherwise noted

R1, R2, R4—470,000 ohms

R3—2,200 ohms

R5—1,000,000-ohm, linear taper pot

R6—1,000,000-ohm, audio-taper pot (with SPST switch)

R7—270,000 ohms

R8—270 ohms

R9—100 ohms

R10—1,500 ohms, 1 watt


S1—SPST switch (part of R6)

SR1, SR2—Silicon rectifier; minimum ratings: 400 PIV @ .75A

T1—Power transformer; secondaries: 250 VCT @ .025A, 6.3 V @ 1A (Stancor PS-8416 or equiv.)


T2—Audio output transformer; primary: 7,000 ohms, secondary: 4 ohms (Stancor A-3878)

V1—6T9 tube

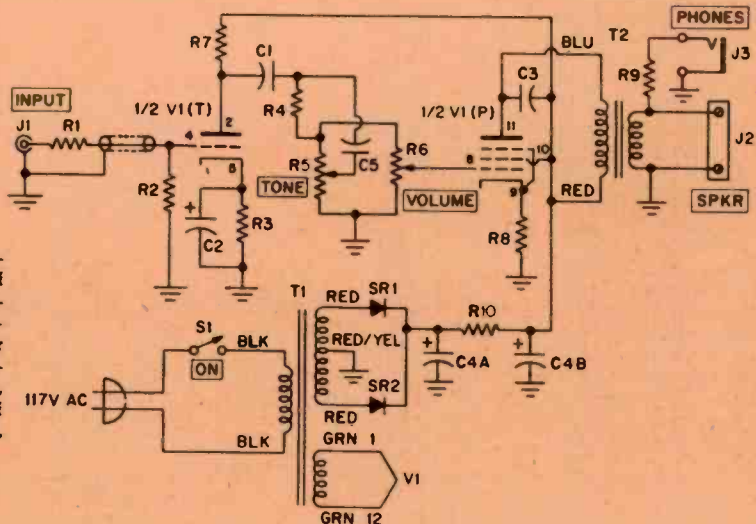

Triode (T) and pentode (P) sections of V1 are housed in 12-pin, Compactron-style tube. To lower distortion of amplifier even further, increase value of bypass capacitor C2.

# Flea-Power Ham Transmitter

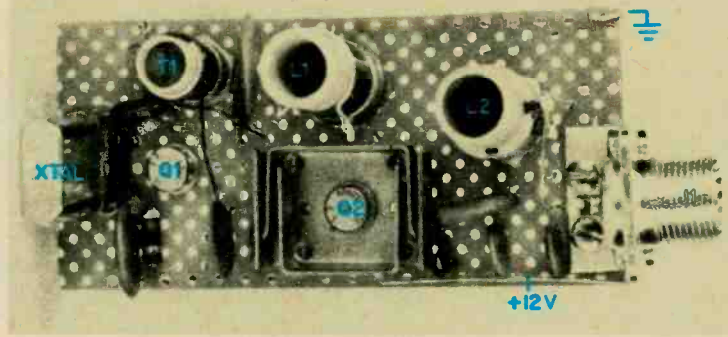

**T**HINK you're up to the challenge of QRP DX? Our Flea-Power Ham Transmitter belts one healthy watt into a 50-ohm antenna system with a 12-volt source supplying power. This transmitter is just the ticket for QRP contests, field trips and any other time you really want to pit your savvy against the vagaries of radio communications.

To key the transmitter, insert a telegraph key in series with the +12-V line. The rig also can be amplitude modulated if a 500-milliwatt audio exciter is connected in series with the B+ line feeding transistor Q2 via a matching transformer.

Our super-low-power rig feeds directly into 50-ohm coax. To tune the transmitter, place a 3730-kc rock in its holder and adjust T1 until you reach resonance. A grid-dip meter is a handy instrument for this adjustment.

Then adjust inductor L2 for maximum output power, meanwhile observing a wattmeter connected across output jack J1, for any unusual fluctuations. After T1 and L2 have been

aligned, go back and rock the slugs in both coil forms for maximum output on the wattmeter. Final transmitter current drain is about 200 ma.—By Herb Cohen

## PARTS LIST

Capacitors: 500 V disc ceramic unless otherwise noted

- C1—0.1  $\mu$ f
- C2, C5—0.01  $\mu$ f
- C3, 8, 9—0.001  $\mu$ f, 1,000 VDC
- C4—470  $\mu$ f, 5% silver mica
- C6—68  $\mu$ f, 5% silver mica
- C7—.05  $\mu$ f

J1—Coax socket (type SO-239)

L1—30 turns No. 24 enamelled wire on 1/2-in. dia. ceramic coil form

L2—12 turns No. 24 enamelled wire on 1/2-in. dia. ceramic coil form

Q1—Npn transistor (40407)

Q2—Npn transistor (40409)

Resistors: 1/2 watt, 10% unless otherwise noted

R1—3,300 ohms

R2—1,000 ohms


R3—47 ohms

R4—2.7 ohms, 5%


T1—RF transformer (see text)

Misc.—perfboard, heatsink for Q2, buswire, etc.

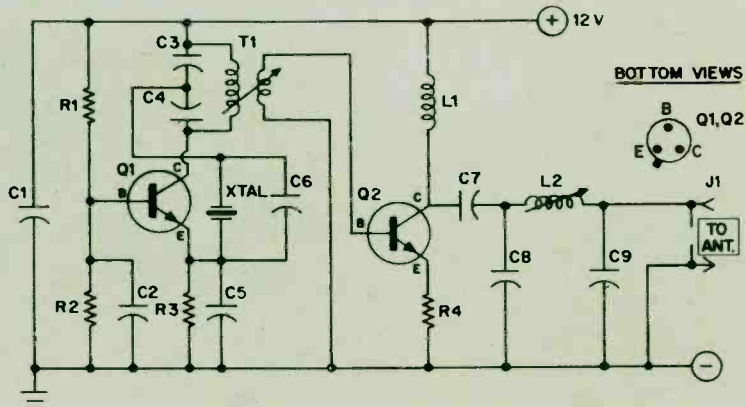Capacitor C6's value may have to be varied for proper excitation of XTAL. When aligning QRP rig, insert VOM in series with +12-V line. Key current after alignment is about 200 milliamperes. See text.



## BOTTOM VIEWS

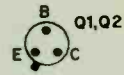


# CB Converter for Your Car

**C**ITIZENS BAND converters can be of use two ways in a car. For once, a CB enthusiast can simply turn on his broadcast radio and, with the converter, listen to what's going on over on the Citizens Band. Alternatively, if there's also a CB rig in the car, the licensee can carry on a two-way while listening to a second channel (such as the local call channel). The converter's input transistor (Q1) protects the receiver from damage even while the CB rig is blasting away right next to it.

Our CB Converter was built especially for the mobile installation. It tunes the entire CB band and has above-average performance, thanks to dual-gate mosfet transistor Q1. CB signals are coupled to Q1 via tank circuit L1/C1 into Q1's input gate G1. This transistor and associated components are connected as a conventional frequency converter. RF signals fed into G1 mix with local oscillator Q2's signal via gate G2. The output frequency is the difference between the two RF signals. It is coupled to output tank circuit components C2 and L2.

The output frequency is in the vicinity of 1500 kc or it can be adjusted to fall at some other point on the BCB dial. Signal pickup is achieved by physically placing L2/C2 next to the antenna coil of the radio. A second method of feeding the output signal into the radio, especially if car-mounted, is to wind a three-turn loop of hookup wire around coil L2. Then loop three turns of the free end around the AM antenna coil inside the car radio. Output frequency can be adjusted

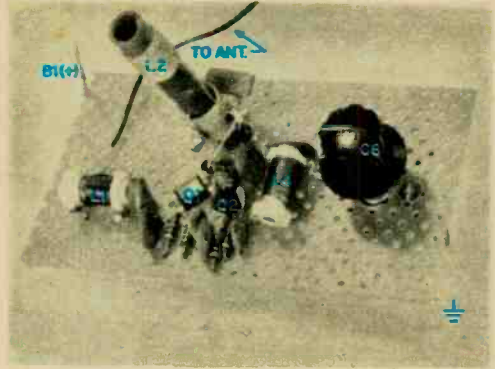

to cover the top end of the broadcast band by turning the ferrite slug in coil L2.

Make RF transformer L1 by winding 11 turns of No. 24 enamelled wire around a 7/32-in.-dia. ceramic coil form. This serves

[Continued on page 98]

## PARTS LIST

Capacitors: 50 V disc ceramic unless otherwise noted

C1—24  $\mu\text{f}$

C2, C9—100  $\mu\text{f}$

C3, C11—0.04  $\mu\text{f}$

C4—0.0015  $\mu\text{f}$

C5—5  $\mu\text{f}$

C6—2.9-30  $\mu\text{f}$  variable capacitor

C7, C8—20  $\mu\text{f}$

C10—0.01  $\mu\text{f}$

L1—Input RF transformer (see text)

L2—BCB Ferrite antenna coil (see text)

L3—RF coupling transformer (see text)

Q1—Dual-gate mosfet (Motorola HEP-F2007)

Q2—Npn transistor (2N4401)

Resistors: 1/4 watt, 10% unless otherwise noted

R1, R2—150,000 ohms

R3—270 ohms


R4—220 ohms

R5—22,000 ohms

R6—4,700 ohms

Misc.—knob, perfboard, No. 24 enamelled wire, etc.

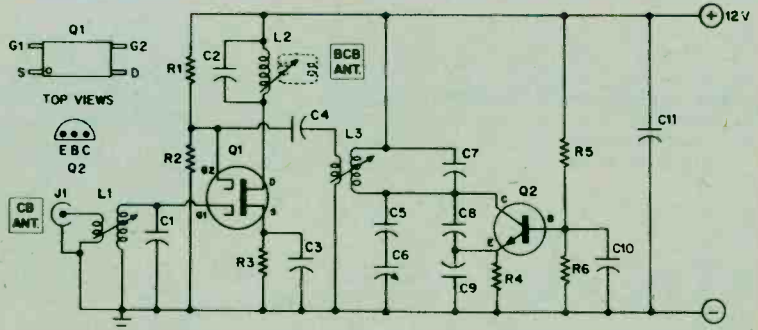Variable capacitor C6 tunes converter across Citizens Band. Coil L2's output link, shown in dotted lines, is three turns of hookup wire wound around coil L2 and BCB antenna coil. See text.




# One-IC Home Intercom

ONE of those handy gadgets you can add to your collection of homebrews is an intercom. With ours, the master always monitors the remote station full-time.

Just two wires are needed to connect the remote to master station. It can be used as an electronic baby-sitter, camper-to-cab communicator or doorbell monitor.

The master station consists of speaker-matching transformer T1, gain control R1 and a master amplifier consisting of transistor Q1 and integrated circuit IC1. Only two components, a speaker and its connecting jack are needed for the remote station.

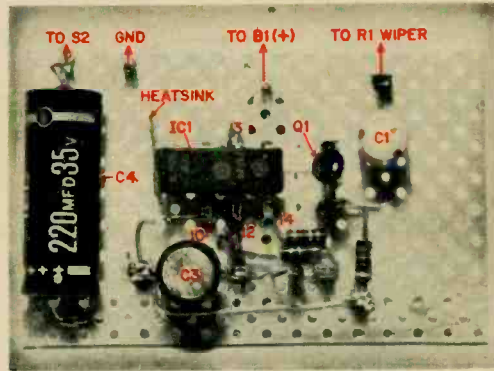Except for T1 and R1, the master amplifier is wired as a small subassembly that fits into the master station call box. Power can be anything from 18 to 22 volts at about 5 ma idling current. In our model, two series-con-



Solder heatsink to tab of IC1 directly. Unused leads of IC1 are cut off before final assembly.

nected 9V transistor radio batteries supply power.


Though the project is simplicity itself, there is a note of caution. Do not eliminate transformer T1. The remote speaker can drive the master amplifier without T1, but direct output from a speaker sounds very bassy and  
[Continued on page 98]

## PARTS LIST

B1—Two 9V transistor radio batteries wired in series  
Capacitors: 20 VDC electrolytic unless otherwise noted  
C1—10  $\mu$ f  
C2—500  $\mu$ f disc ceramic  
C3—50  $\mu$ f  
C4—250  $\mu$ f  
IC1—Integrated circuit (GE PA-234)  
J1, J2—Phono jack  
Q1—Pnp transistor (GE 2N5355 or equiv.)  
Resistors:  $\frac{1}{2}$  watt, 10% unless otherwise noted  
R1—10,000-ohm, audio-taper pot with SPST

switch  
R2—100,000 ohms (see text)  
R3—47,000 ohms  
R4—10,000 ohms  
R5—15 ohms  
R6—1,000 ohms  
S1—SPST switch (part of R1)  
S2—DPDT spring return switch (Lafayette 99R 61830 or equiv.)  
SPK1, SPK2—30- to 45-ohm intercom speaker  
T1—Audio output transformer: primary; 500 ohms, secondary; 3.2 ohms (Lafayette TR-99)  
Misc.—Cabinet, battery holders, heatsink, etc.

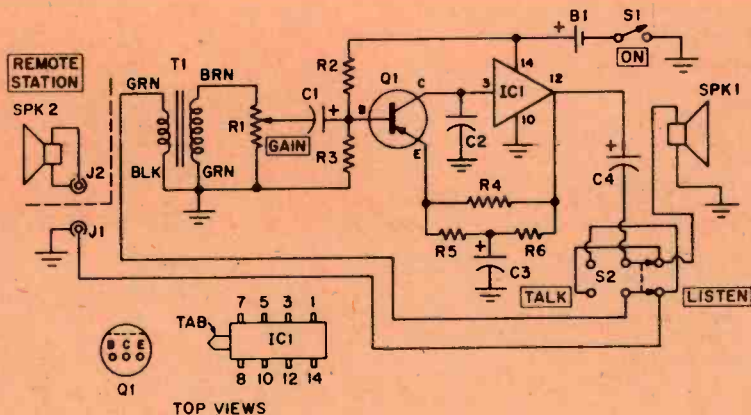Don't omit capacitor C2. Without it, self-oscillation could result. Size of capacitor C4 can be varied to tailor intercom's frequency response.





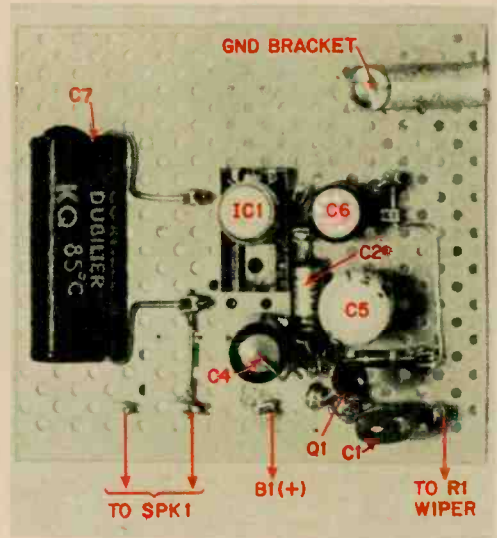
# One-IC Signal Tracer

THE easiest way to troubleshoot a defective amplifier or radio is by tracing a signal fed through the device. A high-gain amplifier and suitable probe pinpoints where the signal gets lost or distorted. Virtually any high-impedance-input, high-gain amplifier can troubleshoot an audio amplifier, while an RF detector probe must be provided to detect the modulation on high-frequency signals. The RF signals can be provided by a radio station or modulated signal generator.

Our one-IC Signal Tracer has everything  
[Continued on page 96]



## PARTS LIST

B1—9V transistor radio battery

Capacitors: 15VDC electrolytic unless otherwise noted

C1—0.05  $\mu\text{f}$ , 500 V disc ceramic

C2—2  $\mu\text{f}$

C3—560  $\mu\text{f}$  disc ceramic

C4—50  $\mu\text{f}$

C5—100  $\mu\text{f}$

C6—30  $\mu\text{f}$

C7—250  $\mu\text{f}$

C8—0.001  $\mu\text{f}$ , 500 V disc ceramic

C9—0.02  $\mu\text{f}$ , 500 V disc ceramic

D1—1N60 diode

IC1—Integrated circuit (Allied Radio Shack

276-016)

J1—Phono jack

Q1—Npn transistor (2N3394 or equiv.)

Resistors:  $\frac{1}{2}$  watt, 10% unless otherwise noted

R1—1,000,000-ohm, audio-taper pot with SPST switch

R2—390,000 ohms

R3—4,700 ohms

R4—27,000 ohms


R5—47 ohms

R6—6,800 ohms

S1—SPST (on rear of R1)

SPK1—8-ohm speaker

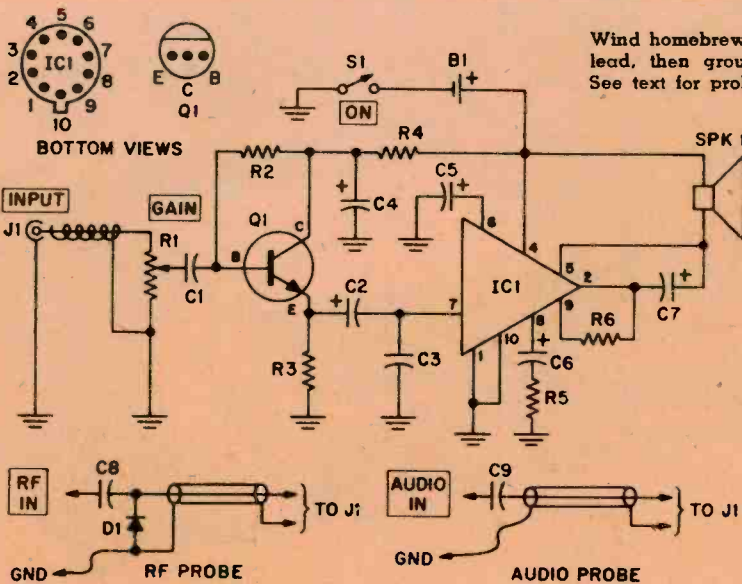Misc.—Cabinet, perfboard, push-in terminals



Wind homebrew shield around input lead, then ground at point shown. See text for probe construction data.

# “At ComSonics we encourage all our technicians and engineers to enroll with CREI. Know why?”

WARREN BRAUN, *President, ComSonics Inc., Virginia Engineer Of The Year, ASE International Award Winner, CREI Graduate*



Photographed at ComSonics, Inc., Harrisonburg, Va.



**"As a CREI graduate myself, I know the advantages of their home-study programs. CREI education has proven an excellent tool of continuing education for our employees and for me. And I strongly believe in CREI's ability to teach a man to learn independently and to use reference materials on his own.**

"As President of ComSonics, I see changes taking place in our Electronics business every day. We're in closed circuit TV and acoustical engineering...and pioneered in Cable TV. CREI gives my men the knowledge they need to work in new areas...CREI's new course in Cable TV is an example. The CATV industry is expected to grow 250% in the next three years. I know the opportunities in Cable TV. I designed one of the first CATV systems in 1950. But technical advances are constantly changing the field. And since CREI's experts know most of what's going on in all areas of Electronics, I know that CREI can give my men some of the important, specialized training they'll need to maintain our position in Cable TV and our reputation in Electronics.

"We've interviewed many technicians and engineers for jobs in the past year and had to reject them because their knowledge is archaic and out-of-date. A man is of no value to us if he doesn't keep up-to-date."

Some of the biggest names in electronics buy CREI courses for their own employees. CREI students and graduates prove themselves on the job. They move ahead of the pack by earning promotions and salary increases.

### The Future Belongs To You

You've been in Electronics long enough to know that the field is changing more rapidly than ever. New industries, like Cable TV, are born almost overnight. But surveys show that three out of four men now working in Electronics aren't technically qualified to work in these new areas. Clearly, the future will belong to the man who gets the right education now.

### Start Learning At Home

But what you learn depends on which school you choose. Here's why CREI is among the best.

With the CREI program you study at home. At your own pace. There are no classes to miss, no work to make up. Each lesson is explained in clear, easy-to-read language. That's why many men do far better in home study than they ever did in school...even if they've been out of school for years. And the study habits they learn from CREI are sustained through life.

As a CREI student, you'll be assigned to an experienced instructor who will grade your assignments and offer constructive comments and criticism. If there's a special problem, the instructor will work with you until you understand it fully. You'll receive personal attention from your instructor because he deals with each student individually—as a class of one.

### What Will I Learn?

You'll be learning the latest in advanced technology, geared to specific industry programs. Both theory and practical material are presented to meet all phases of job-related training needs.

CREI courses are written for the man who knows basic Electronics, but whose advancement depends on keeping his technical know-how current. You choose what you want to learn. You study subjects which help you grow and advance

in your present job and which relate to your career objectives. CREI offers you the opportunity to continue your education throughout your working life.

### Constantly Up-Dated Courses

Because of rapid changes in Electronics, CREI courses are constantly being revised and up-dated by professionals who work in Electronics every day. New developments are included as quickly as they occur. Right now, CREI students are getting the latest up-to-the-minute information on such things as Cable TV, LSI chips, microminiaturization, lasers and masers, telemetry systems, servomechanisms, and data links. If it's new in electronics, CREI—and you—will know about it!

### Developed By Top Scientists And Engineers

CREI maintains a full-time advisory faculty of some of the top names in Electronics. Each is a specialist in his own field, an expert who plans and develops CREI lesson material. After each expert submits his course plan, it is carefully reviewed and written by the CREI educational staff. Then each course is broken down into individual lessons. And they make certain each lesson is clear and self-explanatory. Just the right length for easy understanding and effective study.

### How Can I Qualify?

If you've read this far, your interest in getting ahead in Electronics is evident. Send for our famous book on how to prepare for tomorrow's jobs in Electronics—the book that has helped thousands of men just like you get ahead. For your free copy, simply mail postpaid card today.



Founded 1927

Accredited Member of the National Home Study Council

Free book tells you all about CREI programs. For your copy, mail coupon, postpaid card or write: CREI, Dept. E1709C, 3939 Wisconsin Avenue, Washington, D.C. 20016

**CREI, A Division of the McGraw-Hill Continuing Education Company**  
Dept. E1709C, 3939 Wisconsin Ave.,  
Washington, D.C. 20016

Please mail me free book describing CREI Programs.

I am interested in:  College Credits for CREI Study  
 Space Electronics  Electronic Engineering Technology  
 Computers  Industrial Electronics  Nuclear Engineering  
 Technology  Electronics Systems Engineering  
 Nontechnical Course in Computer Programming  
 CATV Engineering

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip Code \_\_\_\_\_

Employed by \_\_\_\_\_

Type of Present Work \_\_\_\_\_ G. I. Bill \_\_\_\_\_

**APPROVED FOR TRAINING UNDER NEW G. I. BILL**





# A Primer For Cuba Watchers

By ALEX BOWER

**M**ONITORING broadcasts coming from Castro's Cuba has long been a favorite sport with political refugees, the U.S. government and DXers alike. And for a good reason . . . there's plenty to listen to. Even SWLs who own the most inexpensive communications receivers can zero in on at least three different targets: Radio Habana Cuba, the medium-wave broadcast band and aeronautical frequencies which become glamorous whenever an airplane is hijacked and flown to Cuba.

Radio Habana Cuba, one of North America's more powerful SWBC stations, comes in loud and clear most any time, and except for the Voice of America, it's the most easily logged station. The easy tuning is due partly to RHC's being a neighbor; also, Radio Habana Cuba's tropical location insures that her signals do not pass through or near the polar zones so they're not subject to ionospheric disturbances.

Radio Habana Cuba provides English-language broadcasts during evenings on 31 meters (9680 kc) and 25 meters (11840 kc) starting at 2000 EST. These signals are so strong that no matter how roughly your receiver is calibrated you should be able to locate them quickly. (Number one headache for most SWLs is finding stations on rigs priced for the novice pocketbook.) Even if you aren't sure of the frequency, the distinctive accents of RHC's announcers should provide a positive station ID.

When Radio Habana Cuba first became operational, shortly after the Bay of Pigs, RHC seemed to be the most effective Communist shortwave station. Even now it still has more hours of programming per evening (most Communist stations simply repeat programs) than its competitors, and there is no American issue which it will not tackle. When it comes to U.S. domestic affairs, the Cubans seem to have done more research than either Radio Moscow or Radio Peking.

Radio Habana Cuba's broadcasts in Spanish to Latin America are the most extensive of any international shortwave organization and employ the same well-thought-out propaganda techniques. Because censorship is practiced so widely in Central and South America, RHC's broadcasts pack quite a punch and are one of Castro's most deadly weapons.

Fact is, however, that no other nation in Latin America practices as much censorship as Cuba. Taking broadcasting networks as an example, Cuba was the most developed of any Latin American nation before Castro came to power. There were four major networks in private hands: Circuito CMQ (now Radio

Liberacion with a key outlet on 640 kc), Cadena Radio Habana Cuba (now Radio Rebelde with a key Havana outlet on 590 kc), Radio Progreso (with a key outlet on 690 kc) and Union Radio (now Radio Musical Nacional with a key outlet on 910 kc), plus some regional hook-ups and a number of independent outlets. All of these stations were expropriated by Castro and now all non-Marxist broadcasts are jammed by the Cuban government.

Unless you have a local station on 630 or 650 kc, Radio Liberacion can be heard almost any evening east of the Mississippi after sunset (PST). Radio station WHLO in Akron is allowed to operate until that hour. Included in Radio Liberacion's schedule is a series of Spanish-language programs produced by other Communist nations such as Czechoslovakia, North Vietnam and North Korea.

Radio Rebelde (including its relay on 720 and 780 kc) and Radio Progreso can be expected to pop up on shortwave receivers any time an ionospheric disturbance knocks out QRM (interference) from American and Canadian stations. Beginning SWLs shouldn't have trouble making these IDs once they've had some practice.

DXers who are the proud owners of more advanced communications receivers can shoot for many lesser known Cuban medium-wave targets. About once a year, an unlisted Radio Liberacion relay appears near Radio Americas' old frequency, 1163 kc. It seems that no one except the Cuban government (and possibly the CIA) knows where this station is located.

Cuba also operates a network of time and news stations called Radio Reloj Nacional. Key outlets are on 760 and 800 kc. Most other networks sign off at midnight but some of their transmitters are used in a special all-night circuit

Guide to Cuban Aeronautical Frequencies	
Frequency (kc)	General Location
2966	Central Caribbean
5619	Western Caribbean & Mexico
6537	Central Caribbean
8837	Central Caribbean
10017	Western Caribbean

Caribbean aeronautical frequencies are targets for DXers who want to listen in on transmissions from hijacked aircraft. Best bets are 6537 and 8837.


known as La Voz de Cuba. As most adventurous DXers will find out for themselves, Cuba's domestic radio web is one of the most complex to be found anywhere in the world. Latin American countries such as Chile and Peru are starting to copy the regional broadcasting techniques of the Cuban government because of its thoroughness. However, Cuba is still alone when it comes to jamming. These transmitters currently operate around 1140 kc (to combat station WQBA, Radio Cuba, in Miami); a transmitter on 1180 kc interferes with VOA's Marathon station.

The most difficult task for the average SWL will be to monitor transmissions from hijacked aircraft and to listen in on discussions about them. The chart shows a list of aeronautical frequencies used regularly in the Central and Western Caribbean. Signal strength isn't a problem, but finding the more important frequencies (6537 and 8837 kc) on an inexpensive receiver could be a real headache.

One help for the DXer is New York Aeradio which has weather broadcasts 40 minutes after each hour on 8868 kc—just 31 kc above 8837. A more advanced shortwave receiver, however, should be able to sort out these stations quite easily.

Some aeronautical transmissions are in Spanish (especially on 5619 kc) but a majority are in English. The aeradio station at Havana is known as Boyeros, and except when hijack incidents occur, the exchanges between the U.S. and Cuba are normal.

# Build a Direct-Reading

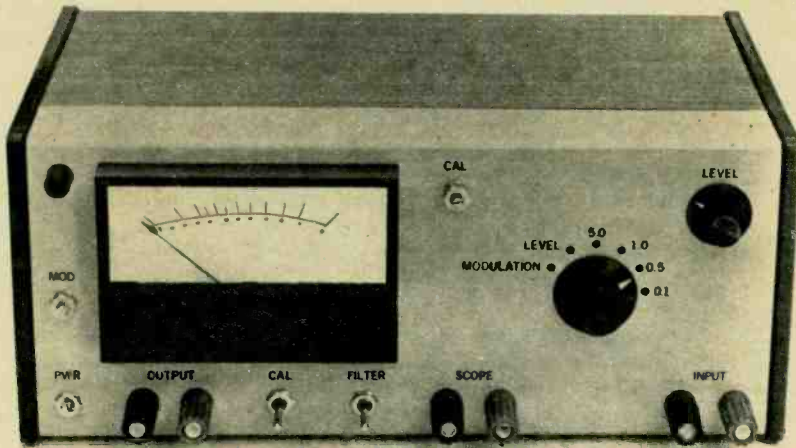

## Wow & Flutter Meter

### Part 2

By **HARRY KOLBE** IN the July issue, we told you what a Wow & Flutter Meter is and how ours works. You also learned the functions of the components and of the various controls. A Parts List was included, too. In this concluding installment, you'll find out how to build the device and calibrate it. Finally, we describe the use of the Wow & Flutter Meter in more detail.

To begin construction, first study the various pictorials indicating parts placement on the printed-circuit boards and front panel. Most of the wiring is single-conductor shielded audio cable. Any kind of shielded cable will work, although we used a miniature variety which was at hand.

It is quite important that you understand the meaning of the diamond-shape callouts on the pc board and front-panel wiring diagrams. These designations key the lugs on both pc boards. Push-in terminals are soldered to lugs designated. Note that the asterisk (\*) is placed by the upper left quadrant of certain designations. This means that the shield wire of a particular cable is connected to it via a push-in terminal.

For example, terminals D and E on the power-supply pc board (labelled PCB1) are connected via shielded cable to R56 (*Modulation*). The cable braid is soldered to ter-


минаl E on PCB1, while the inner lead connects to terminal D. The other end of this cable is run to R56 and is soldered to the pot as shown in the pictorial.

Few of the components used in our Wow & Flutter Meter are critical. But try to obtain new resistors and ICs with known tolerances for best results. Performance of the circuit is, however, strongly affected by capacitor tolerance. For this reason, tantalum capacitors indicated in the Parts List may not be substituted with aluminum electrolytics. Capacitors C12, C13, C14 and C16 must be as close to their ratings as possible. Use the Kemet Type A106M010 for C12, C13 and C16 and Sprague Model 105X9035-A2 tantalum capacitor for C14.

A variety of single-turn miniature potentiometers will fit into the pc board holes where these components are called for. The Bourns 3389P is one model with pins that exactly match these holes.

A less-expensive meter can be substituted for M1, Simpson's Model 543 VU meter. This particular meter was used mostly for legibility and good movement characteristics. Either substitute a less expensive VU meter or a 0-100 microampere DC meter.

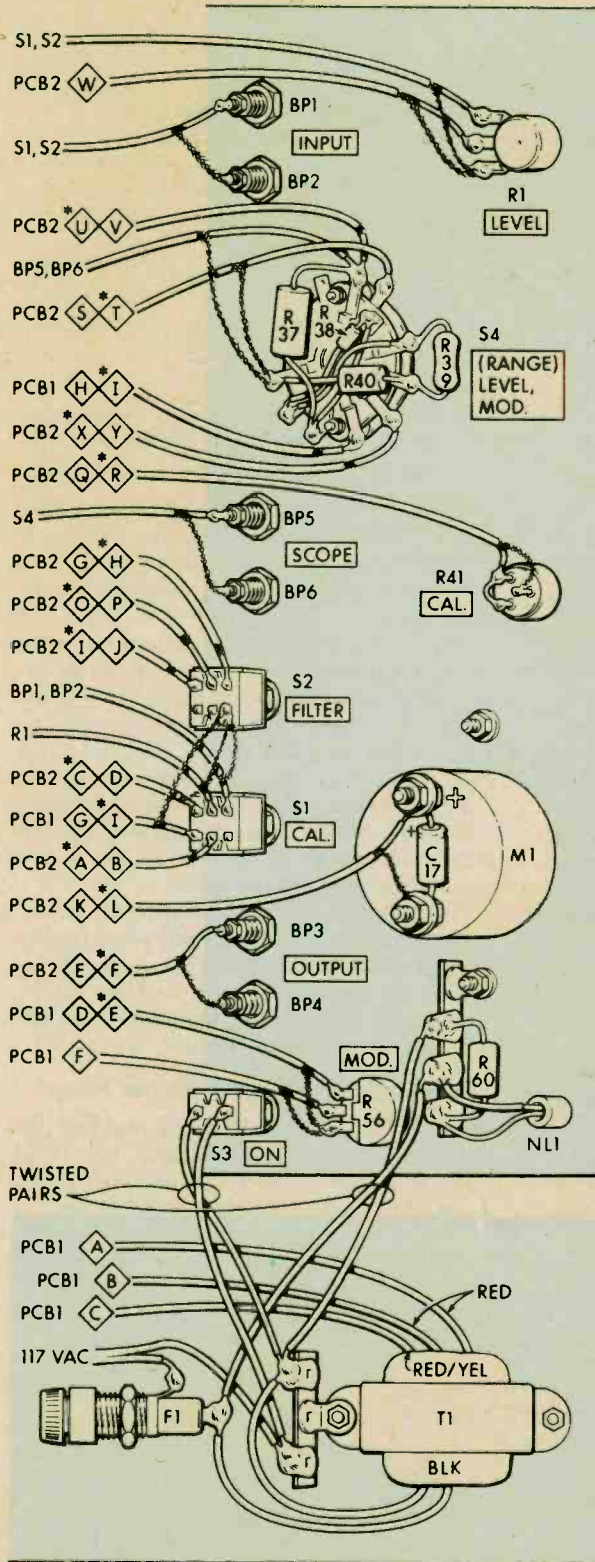In either case, you will have to draw your own meter dial. Use the scale shown in Fig. 2



only as a guide. Also, all internal resistors and the rectifier assembly will have to be removed from the substitute VU meter. You probably will find that the value of electrolytic capacitor C17 has to be changed if a non-specified movement is used. Try increasing the value of C17 to 50  $\mu$ f, 25V if a microampere meter is used instead.

### Building the Wow & Flutter Meter

First prepare both printed-circuit boards from the full-size templates. For best results, a reasonably close copy should be made of both boards. Perforated board and push-in terminal wiring is an alternate method but more care will have to be taken to insure that no connections are omitted.

After the pc boards (or their perfboard alternates) are cut to size and prepared, mount the components. Start with capacitor C1, the first board-mounted component shown in the schematic. Continue adding parts until all first-stage components are accounted for. Solder these parts to the board or push-in terminals.

Proceed to wire the next stage (IC1 and associated parts). Repeat this procedure until all components are mounted to PCB2. Do not forget to wire the six jumpers to the board, too. Then wire PCB1 in like manner.

No matter which wiring technique you choose to follow, make sure you observe that the only chassis ground for both pc boards is at the lug shown to the right of designation E on PCB1. Otherwise, ground loops and hum problems will plague instrument accuracy. Chassis ground is achieved by attaching PCB1 to the cabi-

Fig. 1—Top left box is pictorial of front panel wiring. Bottom edge corresponds to lefthand corner of cabinet. Power transformer, fuseholder and tie point mount to cabinet bottom and rear lip.

# Build a Direct-Reading Wow & Flutter Meter

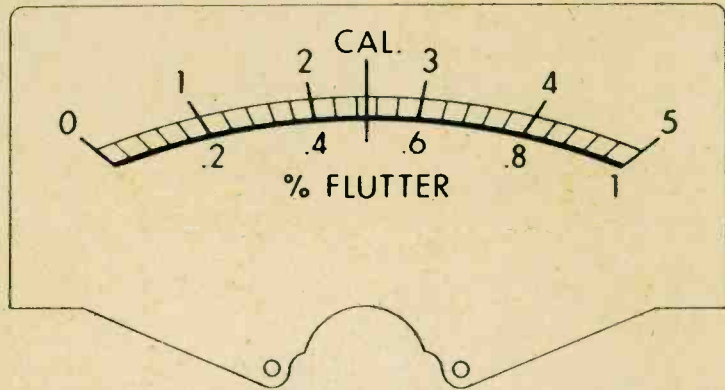


Fig. 2—If specified meter is purchased, glue this face over original dial. Redraw face to fit over dial of other than specified movements. See text.

net with a 1/2-in aluminum standoff.

After all of the components are soldered to both pc boards, inspect for solder bridging and cold joints. Make sure that all ICs are inserted and soldered properly into PCB2. Recheck all diodes and polarity-sensitive capacitors before you begin to drill holes for front-panel parts.

Lay out the front panel according to Fig. 1. The bottom of the pictorial corresponds to the left hand side of the cabinet. It is not mandatory to follow our parts placement. You should, however, mount each set of binding posts with 3/4-in. center spacing between each binding-post pair. This makes it possible to insert dual banana plugs into the binding posts later on.

After all holes are drilled, prewire switch S4 (Range). Don't solder those terminals which have shielded cable attached to them at this time. Since S4 is a 2-pole switch, use the lugs for the second pole as a virtual tie strip for resistors R37-40 and interconnecting wires. See Fig. 1.

Before mounting the meter into the cabinet, cut out the meter scale in Fig. 2, or use the markings as a guide when drawing your

own scale. Also remove the internal resistors and rectifier assembly. Glue the new scale over the original one in your meter and mount the modified meter assembly to the front panel.


After all components have been attached to the front panel, interconnect them to the pc board with shielded audio cable. Follow the guide shown in Fig. 1. Again, it must be stressed that the cable shields must *not* touch each other unless they are soldered together. Take particular care when wiring switches S1 and S2 to follow this precaution. The last step is to wire S4 to the rest of the circuit and then mount it to the panel.

After the power-supply transformer, fuse-holder and line cord have been connected to the rest of the circuit, label the control functions with press-on transfer lettering. Spray with a thin coat of clear laquer to bond the lettering to the cabinet surface.

## Calibrating the Wow & Flutter Meter

The following equipment is required for initial calibration: oscilloscope, an audio signal generator, audio voltmeter and VTVM. Set the W & F Meter's controls as fol-

Fig. 3—Power-supply pc board with component placement shown. View of board is front topside. Note that designations J, K, L do not make use of shielded wire. Ordinary hookup wire also is used at designation F. Ground chassis to cabinet where shown. Use an aluminum stand-off.

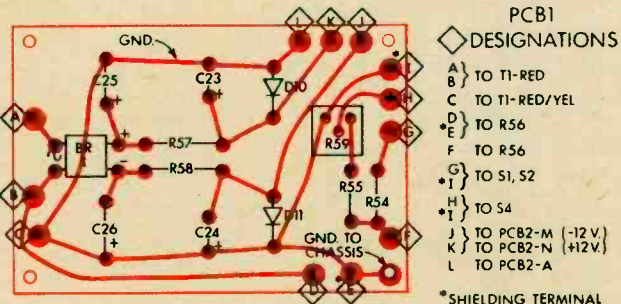



lows: the Level pot is turned fully counter-clockwise.

Range switch is set to the Level mode.

Filter switch turned off.

Calibrate switch is also turned off.

Internal adjustments are as follows: R7 and R56 full ccw. Pots R9,17,29,30,41,45, 48,51,59 set to 50% rotation.

Connect a 100-ohm resistor across M1. Turn the instrument on and adjust R45 for

a zero reading on the meter.

Turn on all test instruments listed. Wait until they have stabilized.

Adjust R29 for 0 VDC at pin 6 of IC3.

Adjust R9 for +0.05 VDC at pin 2 of IC1.

Adjust R51 for -9 VDC at the junction of components R52 and D9.

Wire a temporary jumper between test points (TP) B and C on PCB2. Similarly, wire a jumper between test points D and E.

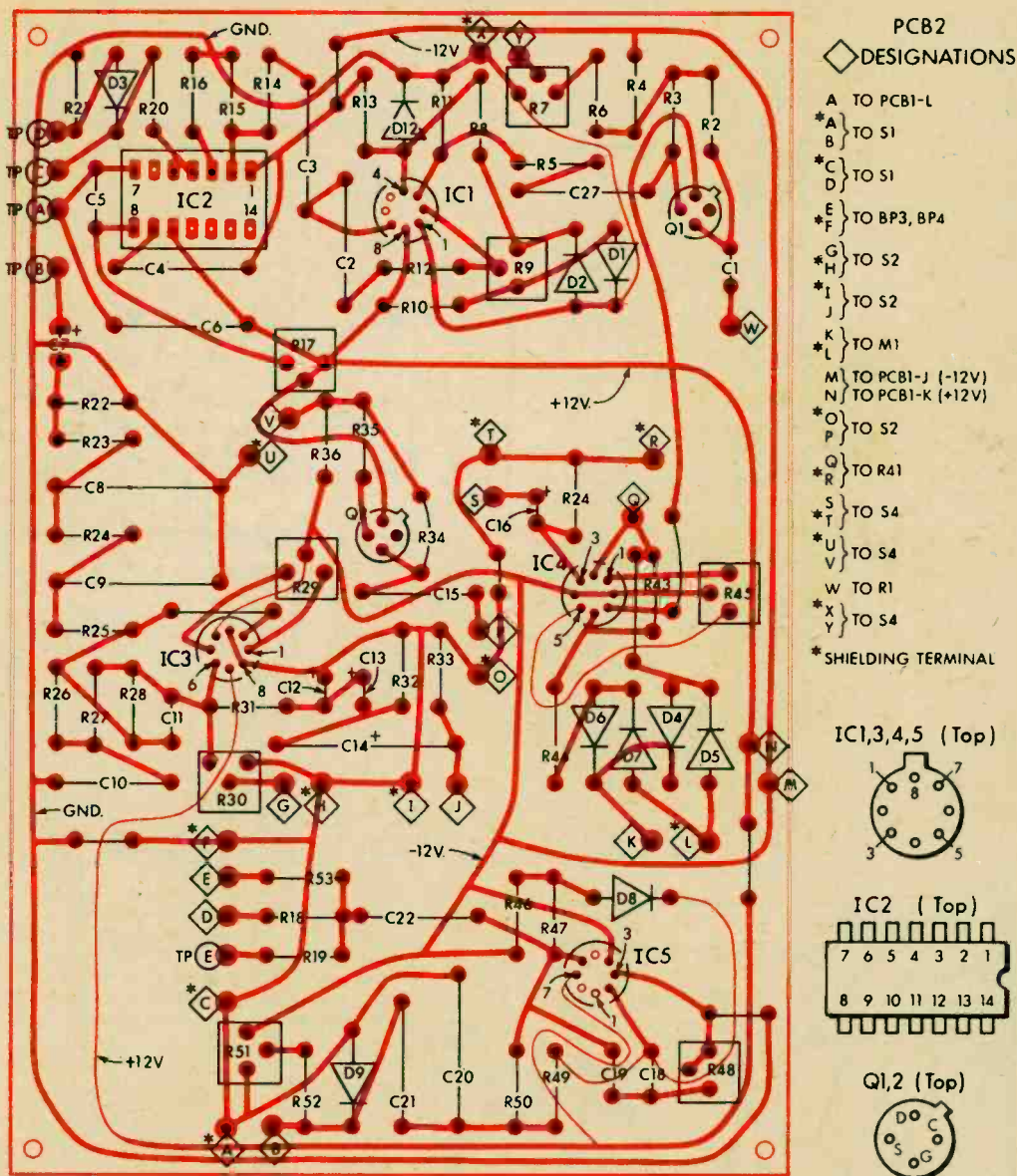


Fig. 4—Topside view of main circuit board. Cut off case (C) leads of Q1, Q2 before mounting transistors.

# Build a Direct- Reading Wow & Flutter Meter

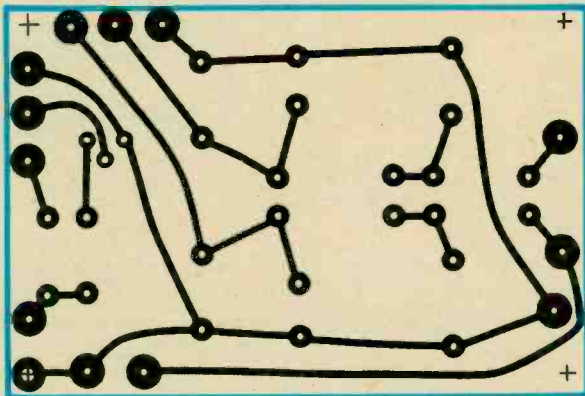
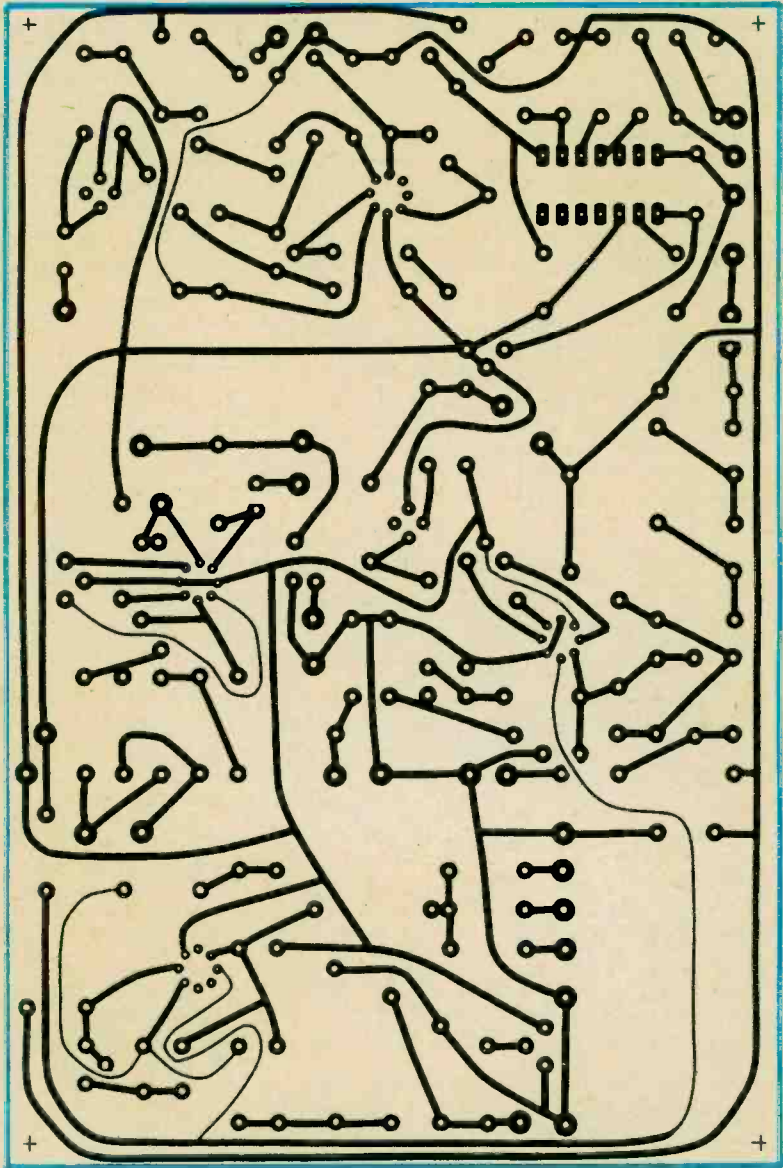


Fig. 5—Full-size template of pc boards. Copy onto board or use perfboard and push-in terminals. Crosshairs indicate position of mounting holes. Note that lower left mounting hole on PCB 1 also serves as circuit chassis ground.

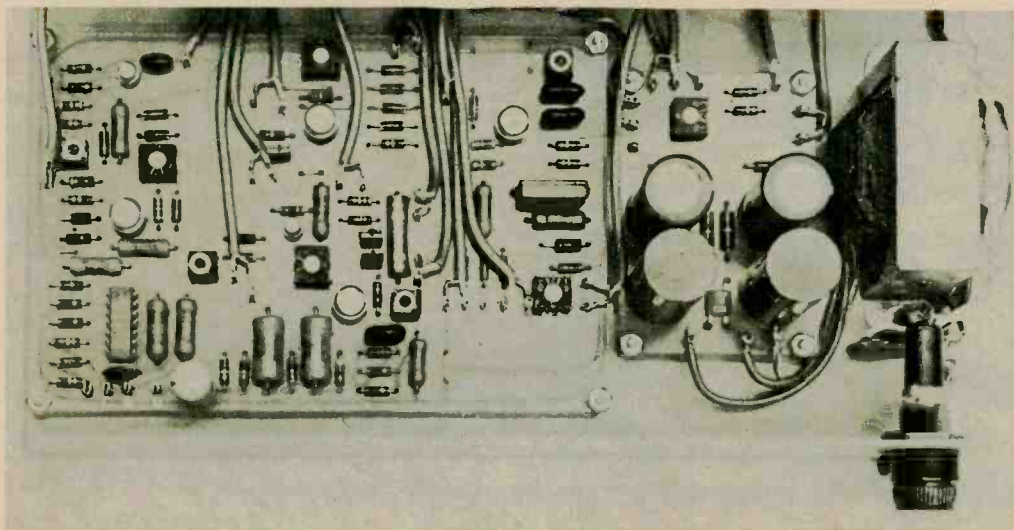


Fig. 6—Mount boards to chassis as shown. Test points A, B are jumpered after meter circuit is calibrated.

Connect the scope's vertical input to test point A and the horizontal input to the audio signal generator, which is set for 3,000 cps. Adjust R17 until a single circle (lissajous pattern) is seen on the scope.

The scope vertical input is attached to binding posts BP3 and BP4 (*Output*). Adjust R48 for a single-circle lissajous pattern on the scope.

Attach the scope vertical input leads to binding posts BP5 and BP6 (*Scope*). Reset the audio signal generator output frequency to 75 cps. It remains connected to the scope's horizontal input. Clip a lead from the VTVM to the junction of components R52 and D9. Adjust R51 ccw for a single-circle lissajous pattern and note the new voltage across D9.

Reset the output of IC5 to 3,000 cps by first readjusting R51 for a  $-9$  VDC reading at the junction of components R52 and D9. Then readjust R48 until a single-circle pattern reappears on the scope. The vertical input jack of the scope is connected to binding posts BP3 and BP4.

Divide the voltage difference previously noted across D9 by 1.41 to determine the rms modulation voltage.

Set S1 to its *Cal* mode. Connect the audio voltmeter to the wiper of R56. Adjust R56 to the rms reading computed in the last step.

Remove the jumpers between points B, C and D, E. Wire a permanent jumper across test points A and B. Remove the 100-ohm

[Continued on page 102]


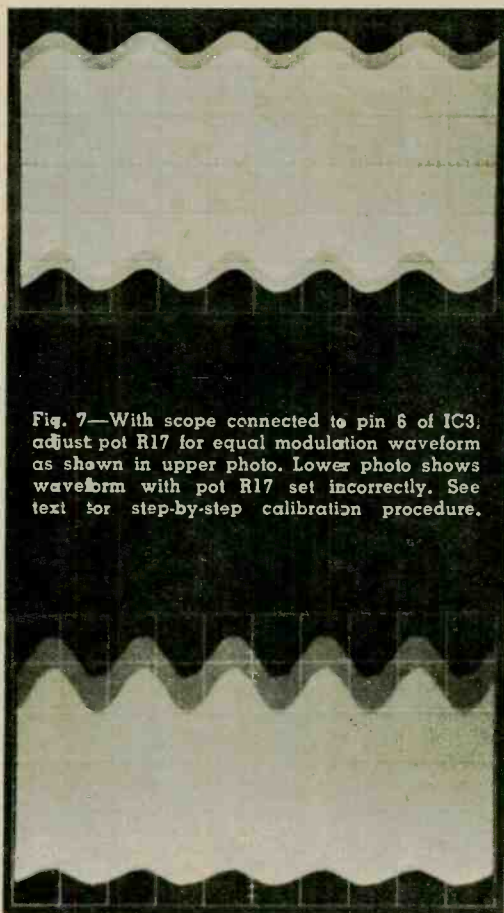


Fig. 7—With scope connected to pin 6 of IC3, adjust pot R17 for equal modulation waveform as shown in upper photo. Lower photo shows waveform with pot R17 set incorrectly. See text for step-by-step calibration procedure.

# Beginner's Guide to Basic Transistor Circuits

*Information you need to understand the theory and practice of using transistors and integrated circuits.*

By LEN BUCKWALTER

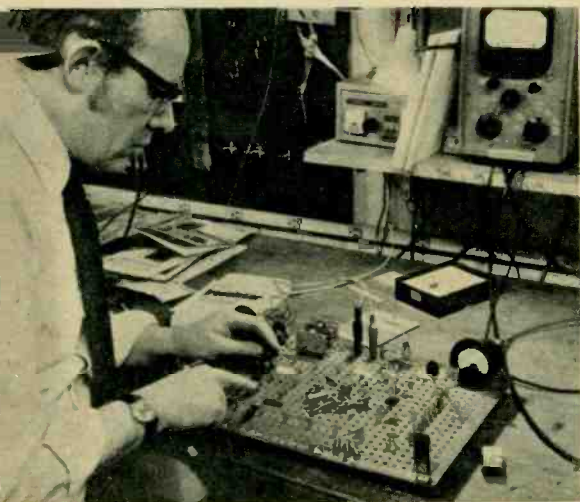

**W**ANT to understand the secrets of the transistor? Build and study these six basic circuits and you'll be on your way. The circuits demonstrate the principles of amplification, oscillation and switching. Each circuit also is a practical project in its own right. Before considering how these circuits operate, let's quickly review what happens inside a semiconductor.

First, how do you get electrons moving inside semiconductor materials such as silicon and germanium? Let's examine a diode—the simplest semiconductor—to illustrate how the properties of pure silicon can be changed to enhance the flow of electrons. Remember that a diode acts like a one-way street to block electrons flowing in one direction while passing electrons flowing in the opposite direction.


Whereas an NPN transistor has two N (negative) regions separated by a P (positive) region, a diode has only one junction which separates an N region from a P region. To get electrons moving in a diode we need both P-type and N-type semiconductor material. Both types are made by mixing chemical elements—known as impurities—in small quantities with pure silicon. This process is called *doping*. It converts the silicon (an insulator) into a conductor.

Typical N-type dopants are antimony, phosphorous and arsenic. P-type silicon is manufactured by adding boron, gallium or indium. The amount of impurity added is small—something like one part impurity to 10 million parts of silicon—but it's enough to change the silicon into a conductor.


To see how this happens, let's study N-type silicon first. After the doping process, impurity atoms are scattered throughout the silicon-crystal lattice. The impurity atoms occupy locations normally filled by silicon atoms.

When the silicon crystal is doped with an N-type impurity there is a free electron in the outer orbit of every impurity atom. Each impurity atom shares four electrons in highly stable bonds with its silicon neighbors, but its *extra* electron is free to wander about between silicon atoms. The whole purpose of N doping is to create free electrons.

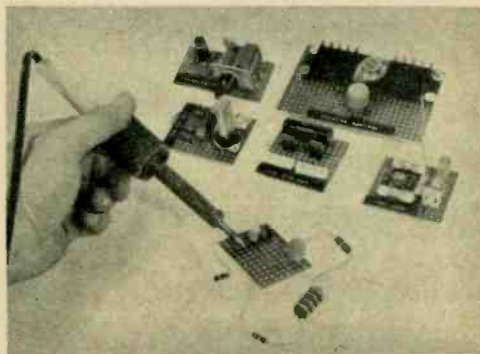How does N-type silicon conduct electricity? If you connect the terminals of an N-type silicon chip to a battery, electrons will be pumped into the semiconductor from one side and the free electrons created by the




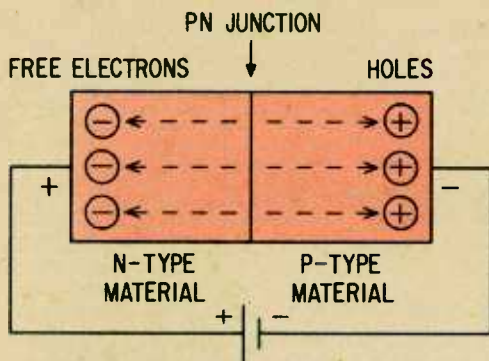Shown above are six practical projects you can build. They illustrate how basic transistor circuits operate. Schematics have parts information.



CURRENT CARRIERS DURING REVERSE BIAS

Fig. 1—Semiconductor diode has one P and one N region. During reverse bias, carriers are drawn away from PN junction, causing high resistance.

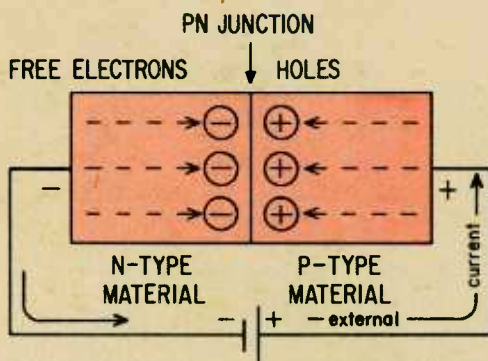

CURRENT CARRIERS DURING FORWARD BIAS

Fig. 2—Action of semiconductor diode during forward bias. Carriers are propelled towards the PN junction. They form a low-resistance bridge.

doping process will be withdrawn from the opposite side and returned to the battery.

To create P-type silicon, a minute amount of P-type dopant is added to the silicon crystal. The impurity atoms replace a small number of silicon atoms in the crystal lattice. Instead of donating an extra electron, the P-type dopant creates an electron deficiency in the crystal lattice. This deficiency is called a hole.

This hole is not a physical hole in the silicon chip. It's a location in the bonds between the atoms that has the potential to attract an electron. Electrons are attracted to these locations because each atom tries to stabilize by filling its outer orbit with the required number of valence electrons.

An atom can fill its outer orbit two ways. A hole either can capture a free electron that passes by or it can grab a bound electron from a neighboring atom. Whenever an electron does move into a hole location, a new hole is created in the crystal lattice at the point previously occupied by the electron.

Thus, if there is a continuous flow of electrons in one direction, there will be a corre-

sponding flow of holes in the opposite direction. Holes behave as if they were positively charged particles. They are the charge carriers in P-type semiconductors. (Free electrons are the charge carriers in N-type semiconductors.)

When the terminals of a P-type silicon chip are connected to a battery, electrons are pumped into the semiconductor. The flow of electrons in one direction is complemented by a flow of holes in the other direction. The more heavily silicon is doped with P-type material, the more holes are created. This enhances the flow of current inside the semiconductor.

Now let's examine a diode to see how the P-type and N-type regions work together to conduct electricity. (Remember that these regions are created by the diffusion of impurities into a bar of silicon—the layers are not constructed by joining separate pieces of semiconductor material.)

Fig. 1 shows a diode connected to a battery. The dividing line between the two regions is called the PN junction. To the left of the junction is N-type material, to the right is P-type material. It's the behavior of electrons and holes in the vicinity of the PN junction that gives a semiconductor its unique properties.

For a detailed discussion of how electrons and holes flow in solid-state circuits you had better turn to a textbook. We'll speed up now and see how semiconductors operate as devices.

Reverting back to Fig 1. In this circuit, free electrons in the N-type material migrate toward the positive terminal of the battery

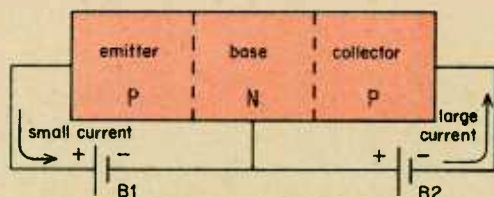


Fig. 3—PNP (or NPN) transistor can be seen as two diodes placed back-to-back. Emitter-base diode has forward bias; base-collector diode has reverse bias.

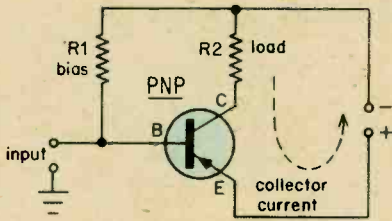


Fig. 4—PNP transistor amplifies when control current flowing through base regulates working current flowing to collector. Note its direction.

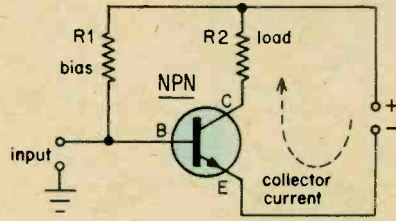


Fig. 5—NPN transistor amplifies in exact same manner only polarities are reversed and different charge carriers are responsible for current flow.

## Basic Transistor Circuits

because unlike charges attract each other. Meanwhile, in the P-type material, positively charged holes are pulled toward the negative terminal. This happens instantly so that the diode appears to the battery as a very high resistance (since the charge carriers have moved away from the junction). The diode blocks further current flow around the external circuit and it's said to be in a state of *reverse bias*.

The diode is switched to a *forward bias* condition by reversing battery polarity, as shown in Fig. 2. Now the rules of like and unlike charges dictate that the holes and free electrons be repelled by the battery voltages. Only now they pile up at the junction. By crowding either side of the barrier, they form an electrical bridge that greatly reduces resistance across the PN junction. Now the diode appears as a low resistance in the circuit and external current can soar.

To convert a diode into a transistor, we'll add a second junction. A transistor sometimes is described as two diodes placed back to back and Fig. 3 shows why. When three semiconductor regions are built up into a PNP sandwich, one diode (emitter-base)

forms at the left. Battery B1 causes current to flow because the forward bias overcomes junction resistance. Battery B2, however, prevents current flow between the base-collector regions because this diode is biased in the reverse direction.


This is the classic PNP transistor poised for action. A tiny current flowing between emitter and base will manipulate a much greater current flowing between emitter and collector.

Amplification (see Fig. 4) occurs when the base resistor R1 taps a small bias voltage from the power supply to create forward bias between emitter and base. The base current of any transistor is always limited to a small value because the base region is constructed of extremely thin material. Its job is to reduce junction resistance. This allows a very large collector current to pass through the base region and reach the emitter.


Since a small base current controls a large collector current, the transistor works as an amplifier. In a PNP transistor, current flow is mostly via holes—though these positive charges never travel outside the semiconductor material.

An NPN transistor (shown in Fig. 5) works according to the same rules except that all polarities are reversed and the major charge carriers are free electrons rather than

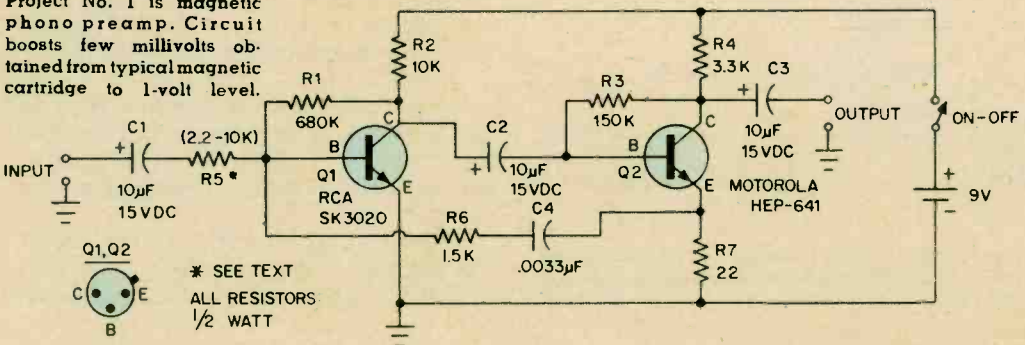Project No. 1 is magnetic phono preamp. Circuit boosts few millivolts obtained from typical magnetic cartridge to 1-volt level.



\* SEE TEXT  
ALL RESISTORS  
1/2 WATT

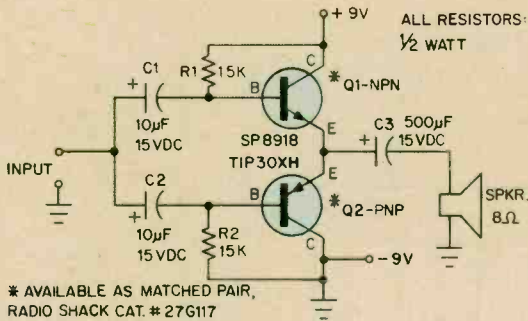


Project No. 2 is complementary-symmetry output stage found in solid-state audio amplifiers. NPN and PNP devices can be hooked up in series.

holes. In the early days of the transistor, most models were PNP types constructed from germanium. Today, silicon NPN types are more common.

**Magnetic Phono Preamp.** Project No. 1 is a circuit commonly found in hi-fi gear which raises the few millivolts obtained from a phono cartridge to the volt or so required by a solid-state power amplifier. Consider how the two NPN transistors are biased to bring them into operating condition.

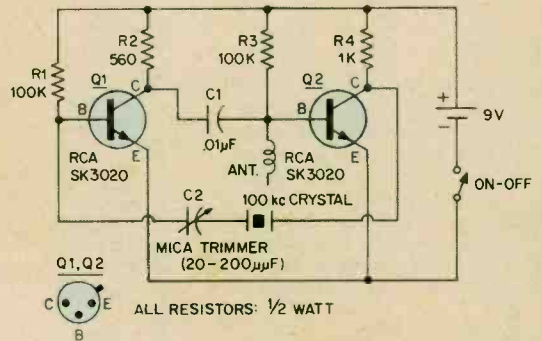R1 is a base-bias resistor which taps a tiny positive voltage from the battery (through R2). This assures a forward-bias condition between base and emitter and a continuous (and much larger) current flow between collector and emitter. When a signal from the phono cartridge arrives at the base of Q1, the audio swings positive and negative, thereby adding or subtracting from the bias volt-



Project No. 3 is 100-kc crystal calibrator. Circuit is called a multivibrator. Oscillator creates harmonics every 100 kc (up to 30 mc) in receiver.

age. These changes are impressed on the collector current and an amplified signal emerges. This process is repeated in Q2 for additional gain.

A special feature of this circuit is phono equalization. During a recording session engineers artificially boost high tones to protect a balance between highs and lows that could be upset during the manufacturing process. When the disk is played back, these highs must be reduced in the preamp with an equalizer circuit. This is done by negative feedback.

Note that a small resistor (R7) in the emitter lead of Q2 causes a small signal voltage to appear at this point. This sampling is fed back to the input of the preamp through C4 and R6. Since the feedback signal is always opposite in polarity to the input, it reduces the input signal by a slight amount.





Transistors switch on and off in multivibrator circuit when they reach saturation and cut-off points. Sine wave has flat top when transistor saturates.



Actual square wave produced by multivibrator. Clipping at top is due to saturation; clipping of bottom portion represents transistor's cut-off point.

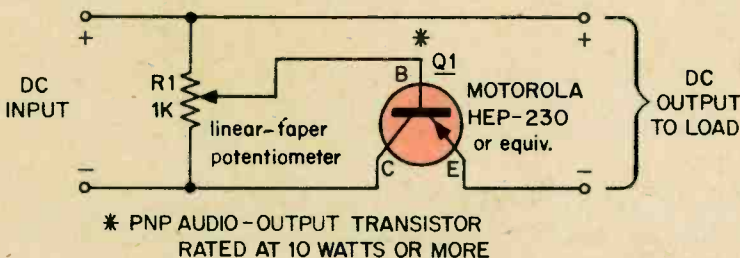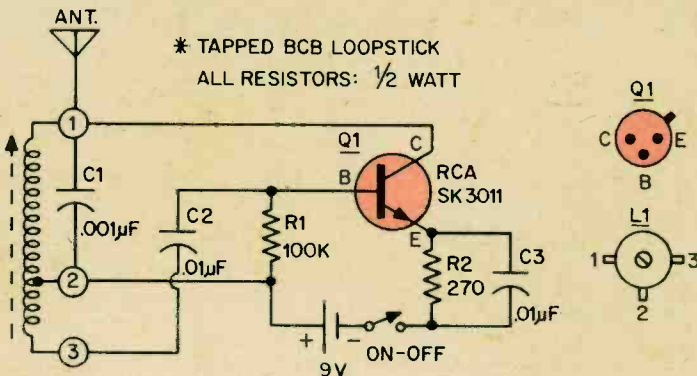Project No. 4 is RF oscillator which covers frequency range of 350 kc to 1000 kc. It will serve for troubleshooting and aligning AM radios. To use it as a BFO (beat-frequency oscillator), tune it to standard IF frequency of 455 kc so it beats against carrier.



Project No. 5 shows how power transistor can control flow of current to a working load. Load can be small DC motor, lamp, etc. This voltage-control device requires large transistor heat sink. It's shown in photo on first page.

## Basic Transistor Circuits


This only happens at high frequencies. The highs easily pass through capacitor C4, while low tones are blocked.

Some practical hints when you build this circuit. It is meant to handle a 5-millivolt cartridge signal (about average), so it may distort higher-level inputs. This can be cured by increasing the value of R5 within the range shown. You also can use this circuit

as a dynamic mike preamp by eliminating the two feedback components, R6 and C4. The transistors draw less than 2 milliamperes so any 9-volt battery will work.


**Complementary Symmetry.** Project No. 2's circuit may jolt anyone brought up solely on vacuum tubes. Standard description of a vacuum tube tells of negative electrons boiling off a hot filament and rushing toward a highly positive plate. Never the reverse. Transistors not only change this image but

[Continued on page 100]

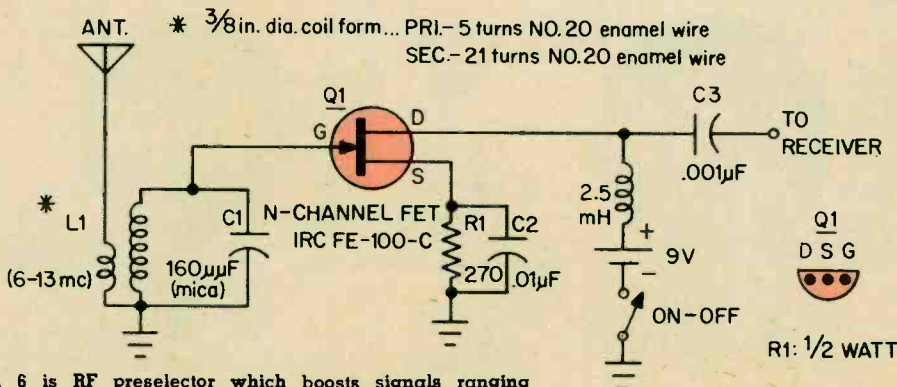

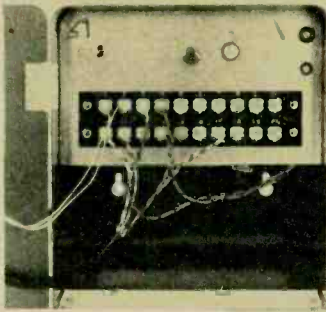Project No. 6 is RF preselector which boosts signals ranging from 6 to 13 mc to improve performance of ham and shortwave receivers. Extended coverage to 30 mc is possible if coil is modified.





## EICO FC-100

Wiring sensors and alarms to FC-100 control center, shown above with front panel open, is easy via screw terminals. Reset button is above terminal strips. Accessories for Eico system, seen from left to right, are: 8-in. bell, fire sensors, tamper switch, klaxon horn and a key-switch.



# A Home-Protection System

**P**ROTECTING your home used to mean building a fortress with moat and draw-bridge. While it might have kept the uninvited from scaling the walls, today's homeowner needs a different kind of setup. Modern electronic home protection with bells and buzzers should not only warn of would-be intruders but also alert the occupants of an emergency inside the home as well.

Furthermore, a good home security system must be able to summon help when needed. Most of all, the system must be reliable and tamper-proof, the protective circuits designed so they cannot be disarmed.


A home-security system offered by Eico can help the homeowner protect his property. Called Fail Safe, the entire system consists of a control center plus a wide variety of accessories enabling the homeowner to customize a protection system to meet his own needs. It requires no soldering to install.

Heart of the system is Eico's model FC-100 control center. This prewired box serves to terminate all sensor and alarm wiring. It also serves as a convenient place to house the power supply.

A wide assortment of sensors connected to the FC-100 gives the Eico system its versatility. Magnetic contact reed switches are available for doors and windows. A momentary key switch with signal light enables you to get into your home without setting off the alarm. Emergency buttons (commonly

known as panic buttons in home-security parlance) located around the home can sound the alarm and summon help. Aluminum foil is available and can be stuck around the windows.

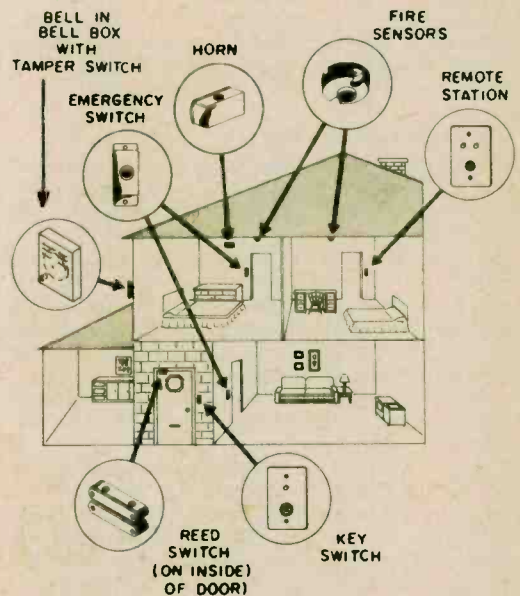Wiring the Eico system is a breeze. Route connections from the various sensors to the  
[Continued on page 103]



Locations of sensors and alarms in typical home.

# CIE graduate builds two-way radio service business into \$1,000,000 electronics company!

**How about YOU? Growth of two-way transmitters creates demand for new servicemen, field and system troubleshooters. Licensed experts can make big money. Be your own boss, build your own company. And you don't need a college education.**

Two-way radio is booming. There are already nearly seven million two-way transmitters for police cars, fire department vehicles, taxis, trucks, boats, planes, etc., and Citizens Band uses. And the number keeps growing by the thousands every month. Who is going to service them? You can — if you've got the know-how!

## Why You'll Earn Top Pay

One reason is that the United States Government doesn't permit anyone to service two-way radio systems unless he's *licensed* by the FCC (Federal Communications Commission).

Another reason is that when two-way radio men are needed, they're *really* needed! A two-way radio user must keep those transmitters operating at all times. And, they *must* have their frequency modulation and plate power input checked at regular intervals by licensed personnel to meet FCC requirements.

As a licensed man, working by the hour, you would usually charge at least \$5.00 per hour, \$7.50 on evenings and Sundays, plus travel expenses.

Or you could set up a regular monthly retainer fee with each customer. Your fixed charge might be \$20 a month for the base station and \$7.50 for each mobile station. Studies show that one man can easily maintain at least 135 stations—averaging 15 base stations with 120 mobiles! This would add up to at least \$12,000 a year.



Edward J. Dulaney, Scottsbluff, Nebraska, (above and at right) earned his CIE Diploma in 1961, got his FCC License and moved from TV repairman to lab technician to radio station Chief Engineer. He then founded his own two-way radio business. Now, Mr. Dulaney is also President of D & A Manufacturing, Inc., a \$1,000,000 company building and distributing two-way radio equipment of his own design. Several of his 25 employees are taking CIE courses. He says: "While studying with CIE, I learned the electronics theories that made my present business possible."

## Be Your Own Boss

There are other advantages, too. You can become your own boss — work entirely by yourself or gradually build your own fully staffed service company. Of course, we can't promise that you will be as successful as Ed Dulaney, or guarantee that you'll establish a successful two-way radio business of your own, but the opportunities for success are available to qualified, licensed men in this expanding field.

## How To Get Started

How do you break in? This is probably the best way:

1. Without quitting your present job, learn enough about electronics fundamentals to pass the Government FCC exam and get your Commercial FCC License.
2. Then get a job in a two-way radio service shop and "learn the ropes" of the business.
3. As soon as you've earned a reputation as an expert, there are several ways you can go. You can move *out* and start signing up and servicing your own customers. You might become a franchised service representative of a big manufacturer and then start getting into two-way radio sales.

Cleveland Institute of Electronics has been successfully teaching Electronics for over 37 years. Right at home, in your spare time, you learn Electronics step by step.



CIE's AUTO-PROGRAMMED\* Lessons remove the roadblocks by using simple, concise examples. You learn in small, compact steps — each one building on the other!

You'll learn not only the fundamentals that apply to all electronics design and servicing, but also the specific procedures for installing, troubleshooting, and maintaining two-way mobile equipment.

**You Get Your FCC License ... or Your Money Back!**

By the time you've finished your CIE course, you'll be able to pass the FCC License exam. A recent survey of 787 CIE graduates reveals that better than 9 out of 10 CIE grads passed the FCC License exam. That's why we can offer our famous Money-Back Warranty: when you complete any CIE licensing course, you'll get your FCC License or be entitled to a full refund of all tuition paid. This warranty is valid during the completion time allowed for your course. You get your FCC License — or your money back!

**It's Up To You**

Mail the reply card for two FREE books, "Succeed in Electronics" and "How To Get A Commercial FCC License." If card has been removed, mail coupon or write: Cleveland Institute of Electronics, 1776 E. 17th Street, Cleveland, Ohio 44114.

**APPROVED UNDER G. I. BILL**

All CIE career courses are approved for educational benefits under the G.I. Bill. If you served on active duty since January 31, 1955, OR are in service now with more than 180 days of active duty, check box for G.I. Bill information.

**CIE Cleveland Institute of Electronics**

1776 East 17th Street, Cleveland, Ohio 44114

Please send me your two FREE books:

1. Your book on "How To Get A Commercial FCC License."
2. Your new catalog "Succeed in Electronics" describing the job opportunities in Electronics today, and how your courses can prepare me for them.

I am especially interested in:

- |   |  |
|---|--|
| <input type="checkbox"/> Electronics Technology                 | <input type="checkbox"/> Electronic Communications |
| <input type="checkbox"/> Broadcast Engineering                  | <input type="checkbox"/> Industrial Electronics    |
| <input type="checkbox"/> First Class FCC License                | <input type="checkbox"/> Electronics Engineering   |
| <input type="checkbox"/> Electronics Technology with Laboratory |  |

Name \_\_\_\_\_ (Please Print)


Address \_\_\_\_\_

City \_\_\_\_\_


State \_\_\_\_\_ Zip \_\_\_\_\_ Age \_\_\_\_\_

Veterans & Servicemen: Check here for G. I. Bill information  
Accredited Member National Home Study Council EI-06

# Signal Injecting Pinpoints

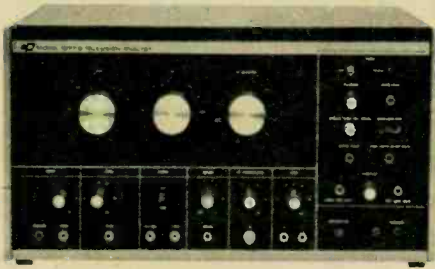

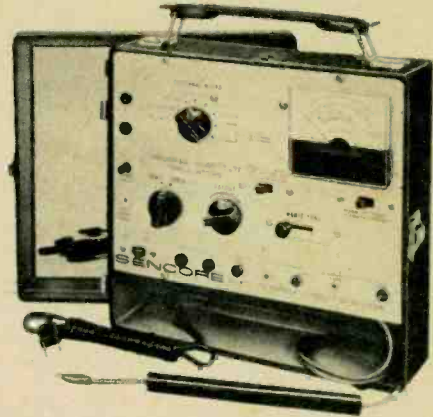B&K's Model 1077 Television Analyst (above) is a miniature TV station which provides signals for any circuit. Sencore's Model SS137 Sweep Circuit Analyzer (at right) provides signals only for horizontal and vertical sweep stages.



## Color TV Troubles

By **ART MARGOLIS** ONE of the quickest ways to locate troubles in color and b&w television receivers is to use the signal substitution technique. One generator can provide all of the TV signals broadcast by a television station and these can be injected into the appropriate circuits to pinpoint defects. The TV screen (CRT) displays the signals as they are developed in the set and gives an indication of what may be wrong.

Not only does signal injecting help you track down intermittents but it can save you time. Back in the Forties I realized that I either had to use signal-injection techniques or lose lots of money on each job. Since there were no all-purpose TV-signal generators available, I had to rig one up from an old TV chassis.

The set had a transformer for isolation, so all I had to do was tap into it to obtain the six test signals I wanted (see **HOW TO TURN A JUNKED TV INTO A SIGNAL GENERATOR**, July '71 EI). These included the tuner output, video output, vertical-grid output, vertical-plate output, horizontal-grid output and horizontal-plate output. Test probes plus a suitable ground brought these key substitute signals into the outside world.

During the Fifties, TV-signal injection gear

became available, notably B&K's Television Analyst, Sencore's Sweep Circuit Analyzer and various flying-spot scanners. Most of this gear has been updated and today it's the most strategic test equipment you can have on your bench.

At first glance, signal injecting may seem a complex procedure. It isn't. You start by tackling the set in block-diagram fashion and you don't worry about locating faulty components until the inoperative circuit is pinpointed. A few case histories will prove the value—and quickness—of this technique.

**Case of Collapsed Vertical.** I had a five-year-old Philco portable on the bench in front of me. Instead of getting a raster, all that appeared on the screen was a white line which ran from side to side. There was no vertical sweep.

I turned down the brightness control to reduce the strength of the electron beam concentrated in that one line. This would prevent burning of the phosphor. Despite the fact that an aluminized picture tube is supposed to stop the heavy ions in the electron beam from striking the phosphor, I've seen plenty of burn marks.

I put a couple of tubes into the set but the condition remained the same. Then I looked around for my B&K Analyst so I

could get a 60-cps sawtooth injection signal to troubleshoot the vertical stages. No luck. It was being used by another benchman across the room.

It isn't wise to begin without an injection test. The troublesome stage could be located anywhere from the vertical oscillator, the vertical output, on to the coils in the vertical deflection yoke. It's always best to narrow down suspects.

In this case, voltage readings with a VTVM would probably have been meaningless since with the lack of sweep the vertical oscillator would have lost its grid bias causing false voltage readings throughout.


Since I didn't want to wait for the Analyst I reverted to an old trick. I took a jumper lead and a 0.05-microfarad capacitor rated at 600 volts, soldered the jumper to a 6.3-volt heater terminal on the chassis and used the capacitor end as a probe. Then I turned on the TV.

I knew I had a 60-cps signal coming out of the capacitor. Of course, it was a sine wave rather than a sawtooth but I also knew it would produce some sort of sweep—even if it was goofy looking.

I injected the makeshift signal into the control grid of the vertical-output stage. The picture spread out pretty well. It was not linear due to the sine wave but the spread proved that everything from the vertical-output stage onward was cleared of suspicion. The trouble had to be in the oscillator.

I crossed over the grid coupling capacitor and touched down on the plate of the vertical oscillator. Again there was some sweep. This exonerated all the components in the output circuit. Then I touched down on the oscillator's control grid. The white line didn't spread a bit.

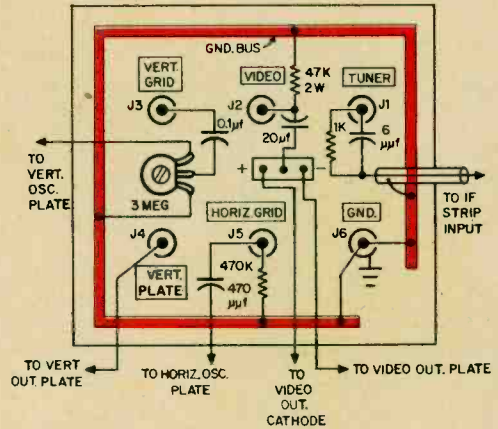I took the 0.05-mike capacitor lead and reattached it at the output. This caused the picture to spread again and restored most of the voltages. Otherwise I would have gotten




Test panel which author rigged up to tap signals from a junked TV set. Horizontal-output signal is tapped directly from metal cap on output tube.

false readings. Now that I had pinpointed the circuit I switched over to my VTVM.


There was low plate voltage on the oscillator. The B+ supply was being fed through a 1-megohm resistor so I read its value. It read about 15 megohms. After I replaced the resistor, sweep was restored and much time was saved by signal injection.

**Where's the High Voltage?** The high-voltage system also serves as the horizontal sweep. A defect in either one causes the loss of both. There's a lot of circuitry. It extends from the horizontal phase detector, horizontal oscillator and horizontal output stage on through to the high-voltage rectifier, focus rectifier, high-voltage regulator, the damper and the horizontal coils in the deflection yoke.

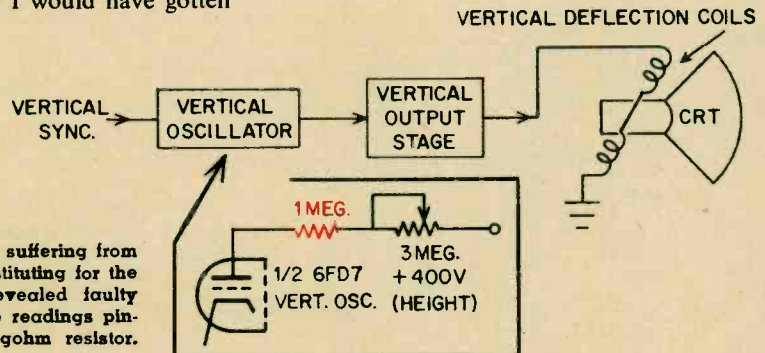While high-voltage problems can be tough, they can be sorted out by signal injection. I had a typical job just recently. It would have



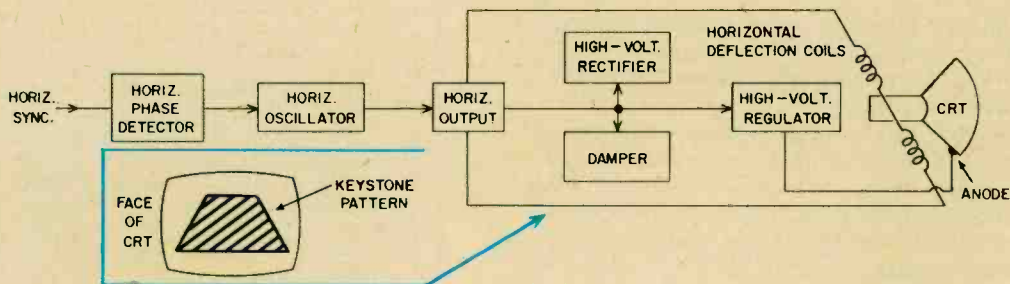In case of Philco portable suffering from loss of vertical sync, substituting for the 60-cps vertical signal revealed faulty vertical oscillator, voltage readings pinpointed defective one-megohm resistor.



Lack of high voltage in Zenith table model was due to bad deflection yoke. Fault was revealed by keystone pattern on set's picture tube. Horizontal sweep signals from B&K Analyst pinpointed defect.

## Signal Injecting Pinpoints Color TV Troubles

taken hours of labor if I hadn't used injection techniques.

The set was a b&w Zenith table model with a no-brightness problem. I measured the high voltage at the anode of the CRT and it read about 2 kv instead of the 18 kv specified. Anything in the entire system could have been the cause.

I put in a new set of tubes and then rolled the Analyst over to the bench. The B&K Analyst provides both a horizontal-grid-drive signal and a horizontal-output signal. It's best to use the output signal first since using the grid drive means getting under the chassis or using a tube socket adapter. The output signal can be injected right into the metal cap which crowns the output tube.

Once I had injected the output signal and turned on the TV, the picture tube seemed to bristle as if there were more high voltage. I was right. It now measured almost 10 kv.


I tried the brightness control. At one setting

some light started to appear on the screen. If I could get some kind of image, the picture defect would indicate the source of my problems. I turned out the room lights and gingerly adjusted for brightness. A wedge-shape picture appeared. The classic keystone pattern—narrow at the top and wide at the bottom.


This was a positive indication of a bad deflection yoke. There was a short in one of the horizontal coils. I took a replacement yoke and plugged it in. The high voltage returned to normal and a bright picture appeared.

**No Contrast, no Color.** The symptom of brightness only, with no sound or picture, is quite common. When it's not caused by a tube, tracking down this defect can be quite a chore. That is, unless you have a flying-spot scanner handy to pinpoint the faulty circuit. This kind of gear can be expensive and isn't easy to come by, but fortunately one is included in the B&K Analyst.

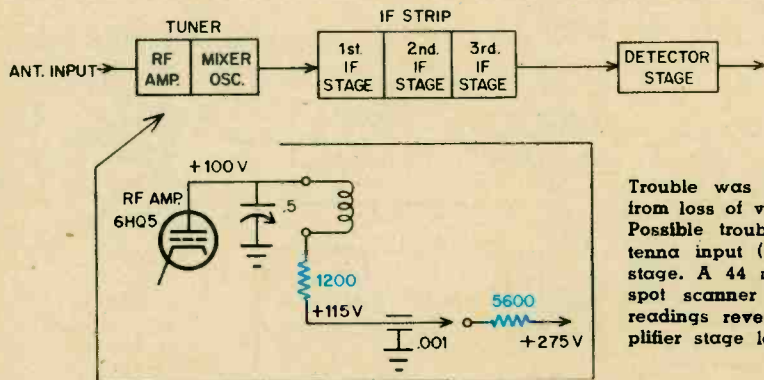A typical example of loss of video (the whole TV signal) stood before me in the form of a fairly new 23-in. color set. The raster shone brightly but no contrast or color



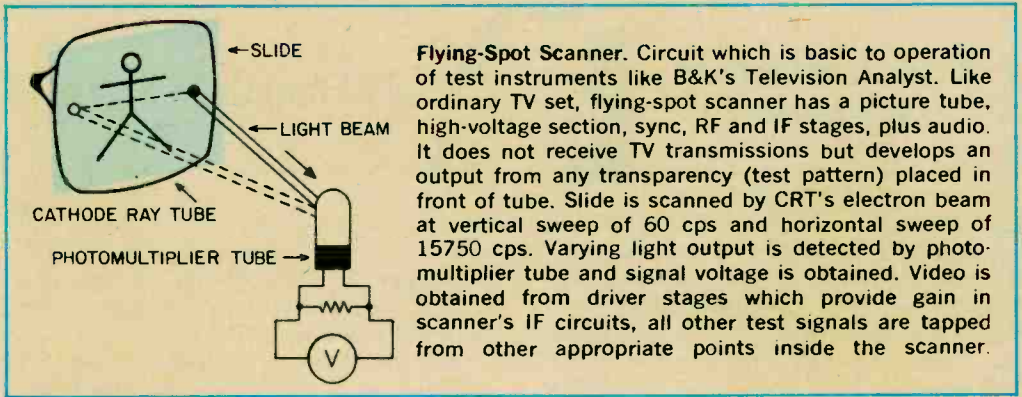Trouble was 23-in. color set suffering from loss of video (color, contrast, etc.). Possible troublespots ranged from antenna input (RF amplifier) to detector stage. A 44 mc IF signal from flying-spot scanner plus some DC voltage readings revealed a defective RF amplifier stage located in the set's tuner.



filled the screen and not a peep came from the speaker. The defective circuit could have been anywhere between the RF amplifier in the tuner to the video detector stage. This ballpark includes RF stages, IF stages, audio and video signals.

Since the IF stages used transistors I checked the only two tubes available but they were good. Then I brought over my flying-spot scanner to get some video into the set. I selected a 44-mc IF signal pattern and began looking for injection points.

You can inject IF signals anywhere in the strip. If you decide on a standard signal-tracing procedure, you might start at the output of the last IF stage and then work toward the input of the first stage. As you inject signals an image will or will not appear on the picture tube.


If an image does appear, the trouble is further back and all the circuitry from the point of injection to the picture tube is

cleared. If an image doesn't appear, the troublespot is further along the road toward the picture tube. For instance, should you be working backwards along the IF strip and injecting signals point by point, as soon as the image doesn't appear on the screen you know you have passed over a bad component. If you work the other way, you'll have passed over the defective component once the image does appear on the screen.

With this in mind, I decided to inject the 44-mc signal at the IF input. A display appeared on the CRT. This meant the entire IF strip was okay and that the trouble was in the tuner.

Next step was to take some DC voltage readings. I put a tube socket adapter into the RF amplifier socket and read the plate voltages. There was zero volts instead of the normal B+. A glance at the schematic showed two resistors in series with the B+

[Continued on page 95]

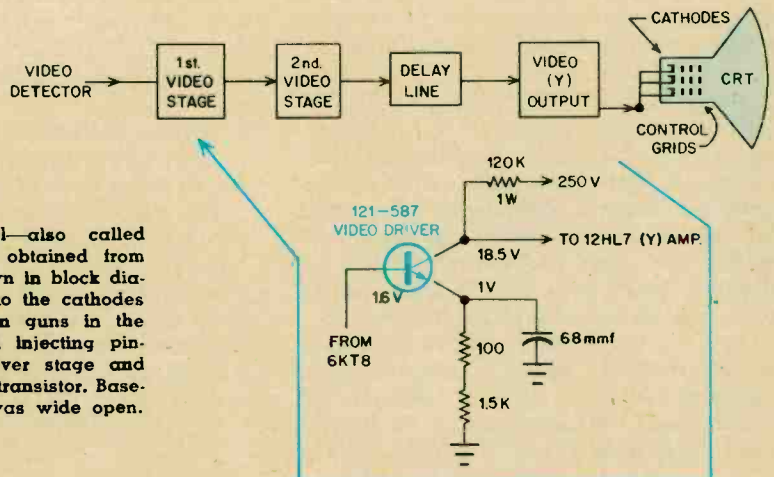

Luminance signal—also called the Y signal—is obtained from video stages shown in block diagram and is fed to the cathodes of all the electron guns in the color CRT. Signal injecting pin-pointed video driver stage and isolated defective transistor. Base-to-collector path was wide open.

# The Listener

By C. M. Stanbury II



## TV From Outer Space?

SOME time ago, North America was scheduled to get its first direct satellite-to-home TV station. Target date was 1973 with the launching of NASA's AT-S-F satellite. Parked in a synchronous orbit over the equator, it was supposed to beam educational TV programs into Alaska and the Rocky Mountain states on 850 mc (roughly UHF channel 77). Special receiving gear was to have been set up at schools and other public institutions, but any individual who wanted to tune in merely would have had to put down \$200 for a special antenna—not an unreasonable price to get in on the ground floor of a new broadcast medium. Now the script has been changed.

First, the atmosphere at the International Telecommunication Union's space conference held in Geneva during summer of 1971 was somewhat hostile. An example of this is a statement made by Radio Sweden's Edward Ploman, who proclaimed "... we wish to get away from abstract or misunderstood ideas about direct-broadcast satellites indiscriminately flinging programs around the earth, since in any case this is not the way such systems will function. Satellite broadcast systems will not be luxury articles, but will be set up for definite purposes in order to answer well-defined requirements. The lack of requirements is also the reason why at present there are no plans for the development of systems designed for broadcasting into augmented or unaugmented home receivers."

The ITU did allocate some UHF-TV frequencies for space (630-790 mc, UHF channels 40 thru 67), but decreed that the video portion of such transmissions must be frequency-modulated, a requirement for which no existing TV receiver is equipped. This clearly was a step backwards, although enthusiasts would have been able to receive the audio portion of AT-S-F programs.

NASA is going along with the ITU edict. In fact, the space agency is going even further and will switch satellite operations off conventional UHF channels to the Instructional Television Fixed Service band. The

video carrier will be on 2570 mc, audio will be on 2670 mc. According to a recent FCC report, only 16 ITFS systems are operating in the United States (none are equipped for frequency-modulated video).

Meanwhile, the 1974 AT-S-F satellite is scheduled to be moved to a spot over the Indian Ocean and will take part in an All India Radio educational TV experiment. AIR definitely favors conventional UHF broadcast channels for reasons of economy. The Russians also have considerable experience with these frequencies as their Molnya Communications Satellites use 800-mc channels.


**World's Oldest Daytime Station.** Station WDZ, Decatur, Illinois, according to our research, commenced operations in 1921 from nearby Tuscola. Despite its daytime status, WDZ has been one of the most progressive rural, pioneer broadcasters. Back in 1937, the station not only set up alternate studios at Danville, Mattoon and Effingham (all used daily), but was one of the first rural stations to use portable shortwave transmitters (with powers ranging from 2 to 30 watts) for remote broadcasts.

WDZ is not an easy logging for DXers, but because of its central location reception is remotely possible almost anywhere in North America at sunrise and sunset (local time). Exceptions are Toronto and New York City where stations CHUM and WHN hold down WDZ's 1050 kc frequency. Chances for success will depend on the quality of your receiver.

**DXing the Yemens.** Radio broadcasting in rural America was achieved prior to 1940. But in many parts of the world this process is just now taking place. In the Yemeni Republic (Aden), only two transmitters operate regularly—a 7½-kw outlet on 5060 kc (occasionally heard in North America at 2230 EST) and a 50-kw outlet on 755 kc. Under the terms of a pact recently signed with the Soviet Union, a new, more powerful station is on the way.

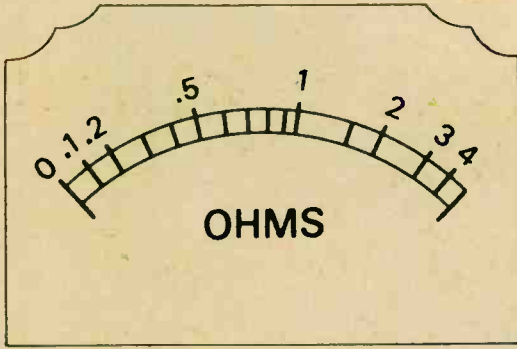In the neighboring Yemen Arab Republic  
*[Continued on page 103]*





# A Lo-Lo-Ohm Ohmmeter

By C. R. LEWART ANYONE familiar with trends in consumer electronics saw the chassis-mounted, plug-in circuit-board take shape some time ago. Plug-in boards obsolete the concept of individual component replacement. This time-saving feature simplifies and speeds up the repair of a TV or other appliance similarly built. Simply remove the defective stage and plug in a new board.

But quick-fix servicing isn't without its own peculiarities. Poor contact between the plug-in board and its mating connector provide the service technician with headaches similar to those experienced when tracking down a cold solder joint.

A bad connector will show an excessive resistance measurement typically from 10 to 50 milliohms between mating surfaces. Ordinary VOMs cannot resolve such low values of resistance for a variety of reasons.

Non-linearity of the ohmmeter scale, sensitivity of the meter and physical width of the meter needle all limit your ability to read low resistances. And the overall lack of scale divisions below a couple of ohms makes resistance readings worthless on a conventional VOM.

Our Lo-Lo-Ohms Ohmmeter lets you measure resistance between 10 milliohms and 40 ohms full-scale. Though precise measurement of contact resistance is a natural chore for our LLO instrument, the experimenter and serviceman also will find it useful in other applications where it is obvious that resistance is low but you need to know just how low.

Commercial milliohmmeters having similar specifications cost several hundred dollars. Even if they were cheaper, none of these lab-grade instruments is readily available to



the electronics experimenter. If all new components are used, cost of our milliohmmeter will be approximately \$20. And if your junk-box is well stocked, you can built it for considerably less.

Current used to measure resistance of a connector assembly or similar low-value resistance component with our ohmmeter will not exceed 15 ma on any of the instrument's three ranges. Voltage between the meter's probes is limited to 15 mv on the most sensitive (10-400 milliohm) range, 150 mv on the 0.1- to 4-ohm range and 1.3 V on the 1-to-40-ohm setting.

**How It Works.** A small voltage is developed across probes P1 and P2 via resistors R11, R17 and one of the range resistors (R3 through R7) as selected by the S1A deck of the rotary switch. Amplitude of this voltage is approximately proportional to the parallel combination of resistance selected by S1A and the component being measured.

This voltage is amplified by integrated circuit IC1. Overall gain of this IC is about equal to the ratio of the particular range resistor selected by deck S1B of the rotary switch (R8 through R10) and resistor R1.

The amplified signal drives meter M1. It is calibrated so that measured resistance can be read directly in ohms.

The components at input terminals 4 and

# A Lo-Lo-Ohm Ohmmeter

5 (resistors R2, R21, diodes D1 and D2) protect the IC against excessive input voltages. Germanium diodes limit the voltage across the amplifier input to about 0.3 V. Resistor R13 and capacitors C1 and C2 prevent IC1 from oscillating.

Pot R18 (*Calibrate*) is used for initial circuit calibration and to help compensate the circuit for low battery voltage. Pot R14 (*Null*) and resistors R12, R15 and R16 adjust the meter for zero null and compensate for

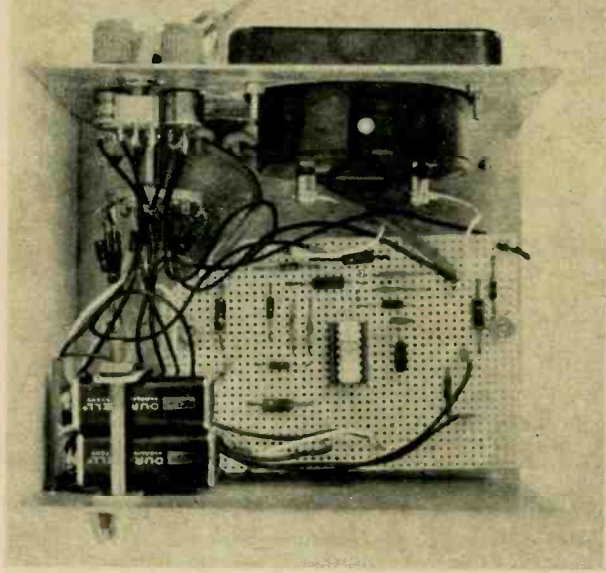


Fig. 1—Ohmmeter layout shown above. Test prod lead is 18-ga. stranded similar to Belden 8898. Battery bracket is made from U-shape sheet aluminum strip. Two battery holders work as well.

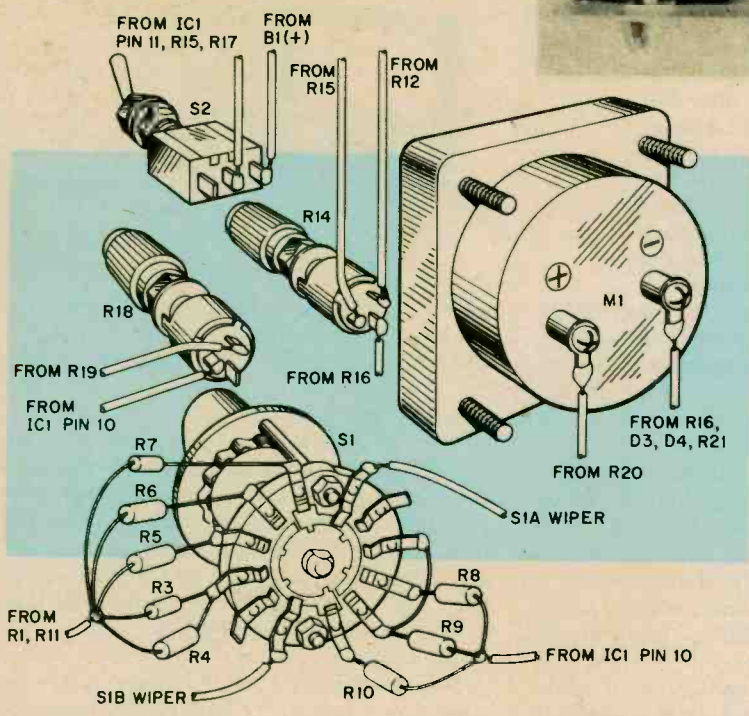


Fig. 2—Take care not to short ends of resistors R8, R9 going to lugs on S1A. Wiring isn't critical and substitutions in component tolerance can be tolerated if less accuracy is all right.

## PARTS LIST

- |   |   |
|---|---|
| B1—Two 9-V transistor radio batteries wired in series     | R9—6,200 ohms   |
| Capacitors: all 20% tolerance, 1000 VDC                   | R10—62,000 ohms   |
| C1—470 $\mu$ f disc ceramic                               | R12—470,000 ohms, 1/4 watt  |
| C2—22 $\mu$ f silvered mica                               | R13—1,500 ohms  |
| D1-D4—General-purpose germanium diode (IN34A or equiv.)   | R14—100,000-ohms, linear-taper pot  |
| IC1—Integrated circuit (Motorola MC1709CL) see text       | R15—100,000 ohms  |
| M1—0.1 ma. DC milliammeter (Lafayette 99R 50403)          | R16—470,000 ohms (see text)   |
| P1, P2—Needle-point test prod (Calectro 33-384 or equiv.) | R18—500-ohm, linear-taper pot   |
| Resistors: 1/2-watt, 5% unless otherwise noted            | R19—750 ohms  |
| R1, R5—100 ohms   | R20—200 ohms  |
| R2, R21—1,000 ohms, 1/4 watt                              | S1—Two-pole, six-position shorting-type rotary switch (Centralab PA-2002 or equiv.) |
| R3, R7—1 ohm, 1/4 watt                                    | S2—SPDT miniature toggle switch   |
| R4, R6—10 ohms  | 2—1-in. spacers   |
| R8, R11, R17—620 ohms, 1/4 watt                           | 1—14-pin IC socket  |
- Misc.—6 x 5 x 4-in. aluminum cabinet, perfboard, push-in terminals, rubber grommets, hardware, knobs, decals, etc.

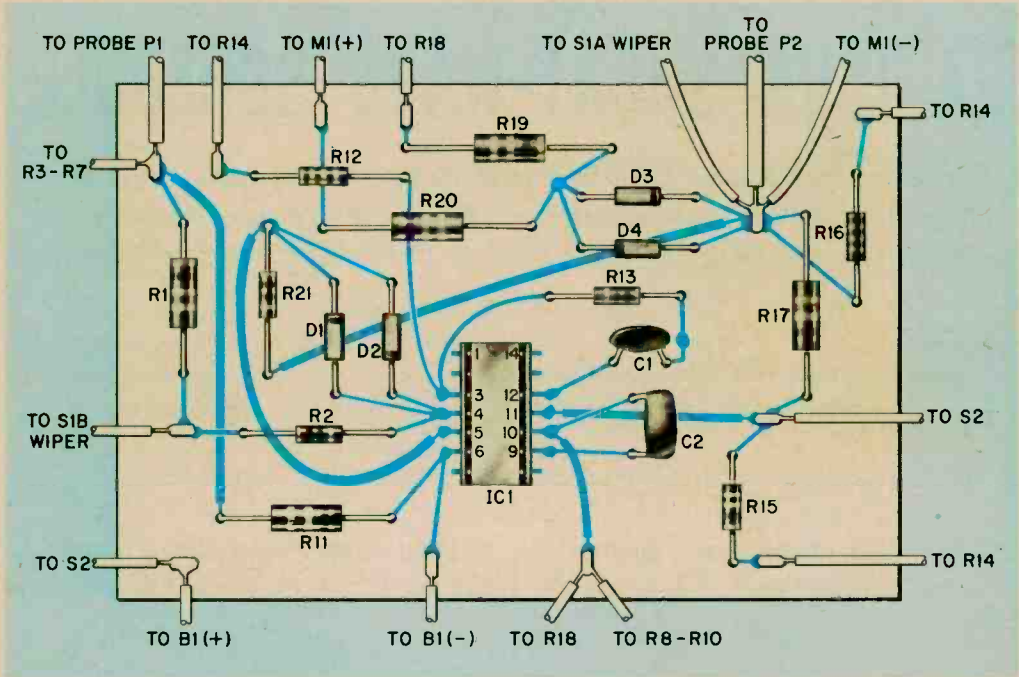


Fig. 3—Observe diode polarity and IC index tab positioning when wiring perfboard. Note 12 push-in lugs.


the resistance of the probe lead. Components R19, R20, D3 and D4 protect M1.

**Building the Ohmmeter.** Component selection, except for meter M1, is not critical. If you substitute another IC for the specified

one, check the substituted IC's socket diagram against that of the MC1709CL. If you wire the socket correctly, the substitute IC should work, too.

[Continued on page 104]

Fig. 4—Schematic of ohmmeter. Check pin connections against ones shown if another IC is used. See text.

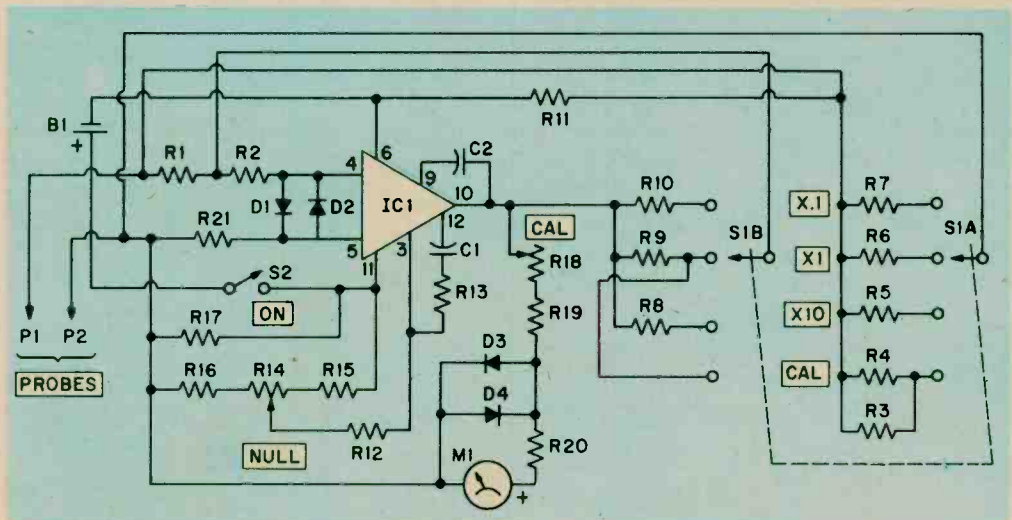

# 24-HOUR SHORT-WAVE SCHEDULE

It presents an updated Fifth Edition of its famous tabulation of English language short-wave broadcasts for 24 hours of the day—from nearly 100 countries. Keep it near your receiver to help you tune in the world.

## ABBREVIATIONS USED IN THIS SCHEDULE

- |   |                               |                       |                           |
|---|-------------------------------|-----------------------|---------------------------|
| A.—Authority                                | E.—East                       | sion, Radiodifusora)  | *—Beamed to North America |
| Af.—African                                 | Is.—Island(s)                 | S.—South              | +—Beamed to western U.S.  |
| B.C.—Broadcasting Co. (Corp.)               | N.—National (Nacional), North | Terr.—Territory       | #—Beamed to eastern U.S.  |
| B.S.—Broadcasting Service (System, Station) | Neth.—Netherlands             | TV.—Television        |                           |
|   | R.—Radio (Radiodiffu-         | V.—Voice (Voz) of the |                           |
|   |                               | W.—West               |                           |

All times listed are Eastern Standard Time. To convert, subtract 1 hour for Central Standard Time, 2 hours for Mountain Standard Time and 3 hours for Pacific Standard Time. Schedules are daily, except when noted parenthetically, i.e., (1)—Sunday transmission, (2)—Monday transmission, etc. All frequencies are in kilocycles.

TIME (EST)	FREQ.	STATION (CALL)	LOCATION	TIME (EST)	FREQ.	STATION (CALL)	LOCATION		
12 MIDN.	3,346	Zambia B. S.	Lusaka, Zambia	2:30 A.M.	3,925	Australian B. C., VLK3	Port Moresby, Papua Terr.		
	3,380	Malawi B. C.	Blantyre, Malawi		4,890	Australian B. C., VLT4	Port Moresby, Papua Terr.		
	4,925	R. Clube Mocambique	Lorenco Marques, Mozambique		5,975	Canadian B. C.	Montreal, Canada		
	4,976	R. Uganda	Kampala, Uganda		7,245	Austrian R.	Vienna, Austria		
	6,090	R. Clube Mocambique	Lorenco Marques, Mozambique		9,540	R. New Zealand	Wellington, New Zealand		
	6,145	Deutsche Welle, DMQ9	Cologne, W. Germany		9,570	R. Australia	Melbourne, Australia		
	9,545*	Deutsche Welle, DMQ6	Cologne, W. Germany		11,735	V. Andes, HCJB	Quito, Ecuador		
	11,715+	R. Nederland Relay	Bonaire, Neth. Antilles		17,880	R. Portugal	Lisbon, Portugal		
	12:15 A.M.	11,910*	Thai N. B. S.		Bangkok, Thailand	21,495	R. Portugal	Lisbon, Portugal	
		4,144	Nigerian B. C.		Calabar, Nigeria	3,995	Solomon Is. B. S.	Honiara, Solomon Is.	
		4,205	R. Nordsee International		International Waters	5,960	V. Andes, HCJB	Quito, Ecuador	
		12:30 A.M.	3,396		Rhodesia B. C.	Gwelo, Rhodesia	6,175	V. Malaysia	Kuala Lumpur, Malaysia
			4,915		R. Ghana	Accra, Ghana	7,290	Trans World R.	Monte Carlo, Monaco
	6,090		RTV Kaduna		Kaduna, Nigeria	11,730	R. Nederland Relay	Bonaire, Neth. Antilles	
	6,155		Swazi Commercial R.		Mbabane, Swaziland	11,780	R. Prague	Prague, Czechoslovakia	
17,840	R. Sweden		Stockholm, Sweden	11,900	V. Malaysia	Kuala Lumpur, Malaysia			
12:45 A.M.	4,795	R. Brazzaville	Brazzaville, Congo Rep.	3 A.M.	4,890	Australian B. C., VLT4	Port Moresby, Papua Terr.		
	11,890	R.V. Gospel, ETLF	Addis Ababa, Ethiopia		5,980	R. Sierra Leone	Free Town, Sierra Leone		
	15,115	V. Andes, HCJB	Quito, Ecuador		6,540	R. Pyongyang	Pyongyang, N. Korea		
	15,190	R. Brazzaville	Brazzaville, Congo Rep.		15,150	R. Pyongyang	Pyongyang, N. Korea		
	1 A.M.	3,316	R. Sierra Leone		Freetown, Sierra Leone	17,815	R. RSA	Johannesburg, South Africa	
4,900		Nigerian B. C.	Maiduguri, Nigeria	21,545	R. RSA	Johannesburg, South Africa			
4,915		R. Ghana	Accra, Ghana	3:15 A.M.	3,995	Solomon Is. B. S., VQ04	Honiara, Solomon Is.		
4,932		Nigerian B. C.	Benin City, Nigeria		4,890	Australian B. C., VLT4	Port Moresby, Papua Terr.		
9,540		R. New Zealand	Wellington, New Zealand		9,520	R. New Zealand	Wellington, New Zealand		
1:15 A.M.	9,720	Deutsche Welle Relay	Kigali, Rwanda		11,850(1)	R. Norway	Oslo, Norway		
	3,255	Liberian B. C., ELBC	Monrovia, Liberia		15,165	R. Denmark, OZFT	Copenhagen, Denmark		
	6,070	CFRB, Ltd., CFRX	Toronto, Canada	15,175(1)	R. Norway	Oslo, Norway			
	7,275	V. Nigeria	Lagos, Nigeria	3,322	R. Bougainville, VLB4	Kieta, Bougainville			
	7,290	Trans World R.	Monte Carlo, Monaco	11,890	Far East B. C.	Manila, Philippines			
1:45 A.M.	15,115	V. Andes, HCJB	Quito, Ecuador	17,830	R. Pakistan	Karachi, Pakistan			
	3,220	R. Fiji	Suva, Fiji	17,880	R. Portugal	Lisbon, Portugal			
	3,227	Sudan Interior Mission, ELWA	Monrovia, Liberia	21,590	R. Pakistan	Karachi, Pakistan			
	6,175	V. Malaysia	Kuala Lumpur, Malaysia	5,970	Canadian B. C., CKNA	Montreal, Canada			
	15,250	R. Bucharest	Bucharest, Rumania	9,625	Canadian B. C., CKLO	Montreal, Canada			
2 A.M.	3,316	Sierra Leone B. C.	Freetown, Sierra Leone	11,765	R. Australia	Melbourne, Australia			
	3,995	Solomon Is. B. S.	Honiara, Solomon Is.	4 A.M.	3,230	R. Fiji	Suva, Fiji		
	4,820	R. Gambia	Bathurst, Gambia		3,290	Guyana B. S.	Georgetown, Guyana		
	9,505*	R. Japan	Tokyo, Japan		5,980	R. Demerara	Georgetown, Guyana		
	9,590	Swiss B. C.	Berne, Switzerland		7,225	Far East B. C.	Manila, Philippines		
5,990	Canadian B. C., CKNA	Montreal, Canada	11,750		United Nations R.	New York, USA			
2:15 A.M.	6,155	Far East Network	Tokyo, Japan	9,505	British B. C. Relay	Tebrau, Malaysia			
	6,205	R. Nordsee International	International Waters	9,585	R. Japan	Tokyo, Japan			
					9,585	V. Indonesia	Djakarta, Indonesia		

TIME (EST)	FREQ.	STATION (CALL)	LOCATION
	11,850	British B. C. Relay	Tebrau, Malaysia
4:30 A.M.	15,430	V. Free Korea	Seoul, South Korea
	11,875	R. Japan	Tokyo, Japan
	11,940	R. Singapore	Singapore
4:45 A.M.	6,130	Maritime B. C., CHNX	Halifax, Canada
	7,131	V. Free China	Taipei, Taiwan
	7,295	V. Malaysia	Penang, Malaysia
	11,795	Deutsche Welle	Cologne, W. Germany
<hr/>			
5 A.M.	3,995	Solomon Is. B. S.	Honiara, Solomon Is.
	6,800	V. Prairies, CFVP	Calgary, Canada
	6,140	Canadian B. C., CKZN	St. Johns, Canada
	9,585	R. Japan	Tokyo, Japan
	15,220	R. RSA	Johannesburg, South Africa
	17,820	R. RSA	Johannesburg, South Africa
	21,520	R. RSA	Johannesburg, South Africa
5:15 A.M.	9,570	R. Australia	Melbourne, Australia
	11,705	R. New Zealand	Wellington, New Zealand
5:30 A.M.	11,740	R. Australia	Melbourne, Australia
	9,522	R. Singapore	Singapore
	7,115	Thai National B. S.	Bangkok, Thailand
	9,520	R. New Zealand	Wellington, New Zealand
5:45 A.M.	11,905	Thai National B. S.	Bangkok, Thailand
	7,145	V. America Relay	Okinawa
	9,560	R. Pakistan	Karachi, Pakistan
	11,672	R. Pakistan	Karachi, Pakistan
	11,785	Deutsche Welle Relay	Kigali, Rwanda
	15,155	V. America Relay	Tianguang, Philippines
	15,190	All India R.	New Delhi, India
	15,410	Deutsche Welle Relay	Kigali, Rwanda
<hr/>			
6 A.M.	4,950	R. Malaysia Sarawak	Kuching, Sarawak
	4,985	R. Malaysia Sarawak	Penang, Malaysia
	7,160	R. Malaysia Sarawak	Kuching, Sarawak
	7,145	V. America Relay	Okinawa, Ryukyu Is.
	7,235	British B. C. Relay	Tebrau, Malaysia
	7,200	All India R.	Gauhati, India
	9,585	V. Indonesia, RFB2	Diakarta, Indonesia
	11,920	R. Bucharest	Bucharest, Rumania
	11,935	Springbok R. Africa	Johannesburg, South Africa
6:15 A.M.	15,250	R. Bucharest	Bucharest, Rumania
	3,990	American Forces Network Taiwan	Taipei, Taiwan
	6,155	Far East Network	Tokyo, Japan
	7,115	Thai National B. S.	Bangkok, Thailand
6:30 A.M.	9,500	R. Australia	Melbourne, Australia
	17,830	Ceylon B. C.	Colombo, Ceylon
	21,490*	R. Sweden	Stockholm, Sweden
	3,335	R. Wewak, VLPD	Wewak, Papua Terr.
	4,890	Australian B. C., VLT4	Port Moresby, Papua Terr.
	4,920	Australian B. C., VLM4	Brisbane, Australia
	9,610	Australian B. C., VLV9	Perth, Australia
6:45 A.M.	11,725	All India R.	Delhi, India
	5,947	R. Republik Indonesia	Josjakarta, Indonesia
	6,120	R. 4VEH, 4VE	Cap Haitien, Haiti
	7,140	R. Malaysia Sarawak	Kuching, Sarawak
<hr/>			
7 A.M.	4,950	R. Malaysia Sarawak	Kuching, Sarawak
	4,985	V. Malaysia	Penang, Malaysia
	5,852	R. Singapore	Singapore
	7,160	R. Malaysia Sarawak	Kuching, Sarawak
	7,295	V. Malaysia	Penang, Malaysia
	9,580*	R. Australia	Melbourne, Australia
	9,660	R. Tashkent	Tashkent, USSR
	9,660	V. Malaysia	Kuala Lumpur, Malaysia
	11,710*	R. Australia	Melbourne, Australia
	11,925	R. Tashkent	Tashkent, USSR
	15,115	R. Berlin	Berlin, E. Germany
7:15 A.M.	6,092	V. Khmer Republic	Phnom Penh, Cambodia
	6,136(1)	R. Norway	Oslo, Norway
	7,225	Far East B. C.	Manila, Philippines
	8,890	Ulan Bator R.	Ulan Bator, Mongolia

TIME (EST)	FREQ.	STATION (CALL)	LOCATION
	9,625*	Canadian B. C., CKLO	Montreal, Canada
	11,720	Canadian B. C., CHSB	Montreal, Canada
	11,820*	Trans World R.	Bonnair, Neth. Antilles
	15,195	R. Nederland Relay	Malagasy Republic
	15,325	Canadian B. C.	Montreal, Canada
7:30 A.M.	21,455(1)	R. Norway	Oslo, Norway
	6,805	R. Sweden	Stockholm, Sweden
	6,890	Australian B. C., VLV6	Sydney, Australia
	7,155	R. Amman	Amman, Jordan
	9,430	R. Sweden	Stockholm, Sweden
	9,440	V. Free Korea	Seoul, S. Korea
	9,770	R. 4VEH, 4VEH	Cap Haitien, Haiti
7:45 A.M.	15,319	R. Bangladesh	Dacca, Bangladesh
	15,405	Marconi R., CFCX	Montreal, Canada
	6,130	R. National Lao	Vientian, Laos
	6,140	Australian B. C., VLV6	Perth, Australia
	9,400*	R. Peking	Peking, China
	11,835	Far East B. C.	Manila, Philippines
	15,095*	R. Peking	Peking, China
	15,445	Ulan Bator R.	Ulan Bator, Mongolia
	17,790	Ulan Bator R.	Ulan Bator, Mongolia
<hr/>			
8 A.M.	6,140	Australian B. C., VLV6	Perth, Australia
	6,155	Far East Network	Tokyo, Japan
	6,160	Canadian B. C., CKZU	Vancouver, Canada
	9,450	S. East Asia R. V.	Manila, Philippines
	9,770	R. 4VEH, 4VEH	Cap Haitien, Haiti
	15,130	R. Pakistan	Islamabad, Pakistan
	15,250	R. Bucharest	Bucharest, Rumania
	15,440	Far East B. C.	Manila, Philippines
	17,710	R. Bucharest	Bucharest, Rumania
	17,935	R. Pakistan	Islamabad, Pakistan
	25,790	R. RSA	Johannesburg, South Africa
8:15 A.M.	4,890	Australian B. C., VLT4	Port Moresby, Papua Terr.
	11,745	V. Andes, HCJB	Quito, Ecuador
	11,810	All India R.	Delhi, India
	17,935	R. Pakistan	Islamabad, Pakistan
	21,725	Swiss B. C.	Berne, Switzerland
8:30 A.M.	6,590	R. Peking	Peking, China
	9,770	R. 4VEH, 4VEH	Cap Haitien, Haiti
	11,450	R. Peking	Peking, China
	11,835	R. 4VEH, 4VEJ	Cap Haitien, Haiti
	15,240	R. Peking	Peking, China
	15,200	R. 4VEH, 4VWI	Cap Haitien, Haiti
	15,315	R. V. Gospel, ETLF	Addis Ababa, Ethiopia
	15,335	All India R.	Delhi, India
8:45 A.M.	17,845	Swiss B. C.	Berne, Switzerland
	11,820	V. Andes, HCJB	Quito, Ecuador
	15,100	R. V. Gospel, ETLF	Addis Ababa, Ethiopia
<hr/>			
9 A.M.	4,775	R. Afghanistan	Kabul, Afghanistan
	4,950	R. Malaysia Sarawak	Kuching, Sarawak
	9,560	R. Japan	Tokyo, Japan
	9,660	R. Tashkent	Tashkent, USSR
	11,900	R. RSA	Johannesburg, South Africa
	11,940	R. Singapore	Singapore
	17,810	R. Nederland	Hilversum, Netherlands
9:15 A.M.	6,130	R. Ghana	Accra, Ghana
	7,215	R. Brunel	Tutong, Brunei
	15,260	R. Nederland Relay	Malagasy Rep.
	17,825*(1)	R. Norway, LLN	Oslo, Norway
	17,870	R. Ghana	Accra, Ghana
9:30 A.M.	9,585*	V. Indonesia	Djakarta, Indonesia
	11,795*	V. Indonesia	Djakarta, Indonesia
	21,505	R. Sweden	Stockholm, Sweden
	21,520	R. Berlin	Berlin, E. Germany
9:45 A.M.	9,515	R. Pyongyang	Pyongyang, N. Korea
	9,610	Australian B. C., VLV9	Perth, Australia
	15,150	R. Pyongyang	Pyongyang, N. Korea
<hr/>			
10 A.M.	5,040	Burma B. S.	Rangoon, Burma
	4,130	R. Ghana	Accra, Ghana
	6,160	Canadian B. C., CKZU	Vancouver, Canada
	6,235	R. Pakistan	Karachi, Pakistan
	9,585	V. Indonesia	Djakarta, Indonesia
	9,675	R. Pakistan	Karachi, Pakistan
	11,795	V. Indonesia	Djakarta, Indonesia
	11,800	Ceylon B. C.	Colombo, Ceylon
	11,810	All India R.	Delhi, India
	15,320*	Canadian B. C.	Montreal, Canada

TIME (EST)	FREQ.	STATION (CALL)	LOCATION
10:15 A.M.	11,810(4)	Vatican R.	Vatican City
	11,865	Swiss B. C.	Berne, Switzerland
	15,305	Swiss B. C.	Berne, Switzerland
	17,810	R. Nederland	Hilversum, Netherlands
	17,830	Swiss B. C.	Berne, Switzerland
10:30 A.M.	6,055	R. Prague	Prague, Czechoslovakia
		R. Belgrade	Belgrade, Yugoslavia
		V. Vietnam	Hanoi, N. Vietnam
		R. Belgrade	Belgrade, Yugoslavia
		V. Vietnam	Hanoi, N. Vietnam
10:45 A.M.	15,240	R. Belgrade	Belgrade, Yugoslavia
		V. Nigeria	Lagos, Nigeria
		R. Prague	Prague, Czechoslovakia
		R. Ghana	Accra, Ghana
		21,545	R. Ghana

11 A.M.	9,595	R. Kuwait	Kuwait
	11,900	R. RSA	Johannesburg, South Africa
	15,220	R. RSA	Johannesburg, South Africa
	15,345	R. Kuwait	Kuwait
	17,880	R. Berlin	Berlin, E. Germany
11:15 A.M.	9,675	R. Warsaw	Warsaw, Poland
		Vatican R.	Vatican City
		Far East B. C.	Manila, Philippines
		R. Omdurman	Omdurman, Sudan
		R. Amman	Amman, Jordan
11:30 A.M.	9,735	Deutsche Welle	Kigali, Rwanda
		Relay	Kigali, Rwanda
		Deutsche Welle	Kigali, Rwanda
		Relay	Kigali, Rwanda
		R. Grenada	St. George's, Grenada

12 NOON	6,065	R. V. Gospel,	Addis Ababa, Ethiopia	
	9,915	British B. C.	London, England	
	11,765	Deutsche Welle	Cologne, W. Germany	
	15,275	Deutsche Welle	Cologne, W. Germany	
	15,345	Kuwait B. S.	Kuwait	
	17,845	R. New York World-wide, WNYW	New York USA	
	21,525	R. New York World-wide, WNYW	New York USA	
	12:15 P.M.	9,735	Deutsche Welle	Kigali, Rwanda
		11,735	RTV Marocaine	Rabat, Morocco
		11,855	B. S. Kingdom	Djeddah, Saudi Arabia
11,965		Deutsche Welle	Kigali, Rwanda	
15,345		Kuwait B.S.	Kuwait	
21,720		R. Ghana	Accra, Ghana	
9,605		R. Prague	Prague, Czechoslovakia	
11,790		American Forces RTVS	Washington, USA	
11,855		B. S. Kingdom	Djeddah, Saudi Arabia	
11,950		Far East B. Associates	Victoria, Seychelles	
12:30 P.M.	11,995	R. Prague	Prague, Czechoslovakia	
	15,265	R. Prague	Prague, Czechoslovakia	
	15,275	Deutsche Welle, DMQ15	Cologne, W. Germany	
	17,655	R. Cairo	Cairo, Egypt	
	15,080	All India R.	Bombay, India	
	15,345	Kuwait B. S.	Kuwait	
	12:45 P.M.	9,530	R. Afghanistan	Kabul, Afghanistan
		9,550	Finnish B. C., OIX2	Pori, Finland
		9,685	V. Free China	Taipei, Taiwan
		9,705	R. V. Gospel, ETLF	Addis Ababa, Ethiopia
11,755		Finnish B. C., OIX8	Pori, Finland	
11,780		R. Clube	Lorenco Marques, Mozambique	
15,125		V. Free China	Taipei, Taiwan	
15,185		Finnish B. C., OIX5	Pori, Finland	
9,530		R. Afghanistan	Kabul, Afghanistan	
9,765		V. Free China	Taipei, Taiwan	

1 P.M.	9,530	R. Afghanistan	Kabul, Afghanistan
	9,550	Finnish B. C., OIX2	Pori, Finland
	9,685	V. Free China	Taipei, Taiwan
	9,705	R. V. Gospel, ETLF	Addis Ababa, Ethiopia
	11,755	Finnish B. C., OIX8	Pori, Finland
1:15 P.M.	11,780	R. Clube	Lorenco Marques, Mozambique
	15,125	V. Free China	Taipei, Taiwan
	15,185	Finnish B. C., OIX5	Pori, Finland
	9,530	R. Afghanistan	Kabul, Afghanistan
	9,765	V. Free China	Taipei, Taiwan
	11,780	R. Clube	Lorenco Marques, Mozambique
	11,825	V. Free China	Taipei, Taiwan
	11,855	B.S. Kingdom	Djeddah, Saudi Arabia
	11,935	R. Portugal	Lisbon, Portugal
	21,495	R. Portugal	Lisbon, Portugal

TIME (EST)	FREQ.	STATION (CALL)	LOCATION
1:30 P.M.	7,215	RTV Ivorienn	Abidjan, Ivory Coast
	7,240	R. Belgrade	Belgrade, Yugoslavia
	9,620	R. Belgrade	Belgrade, Yugoslavia
	11,705	R. Lebanon	Beirut, Lebanon
	11,920	RTV Ivorienn	Abidjan, Ivory Coast
1:45 P.M.	11,925	Kuwait B. S.	Kuwait
	15,420	British B. C. Relay	Cyprus
	21,570	R. Nederland	Bonaire, Neth. Antilles
	7,065	R. Tirana	Tirana, Albania
	9,695	R. RSA	Johannesburg, South Africa
	11,940	Kuwait B. S.	Kuwait
	15,320	Canadian B. C., CKCS	Montreal, Canada
	15,420	British B. C. Relay	Cyprus
	17,720	V. Free China	Taipei, Taiwan
	21,595	Canadian B. C.	Montreal Canada

2 P.M.	6,540	R. Pyongyang	Pyeongyang, N. Korea
	7,195	V. America Relay	Monrovia, Liberia
	7,215	All India R.	Delhi, India
	9,515	R. Pyongyang	Pyeongyang, N. Korea
	11,875	R. Portugal	Lisbon, Portugal
2:15 P.M.	11,950	Trans World R.	Monte Carlo, Monaco
	15,105*	R. Japan	Tokyo, Japan
	15,435	R. Tanzania	Dar es Salaam, Tanzania
	4,885	V. Kenya	Nairobi, Kenya
	7,240	V. Kenya	Nairobi, Kenya
2:30 P.M.	11,815	R. Japan	Tokyo, Japan
	11,940	Sudan Interior	Monrovia, Liberia
	15,200	Mission, ELWA	Lagos, Nigeria
	4,070	R. Sofia	Sofia, Bulgaria
	6,150	R. Bucharest	Bucharest, Rumania
2:45 P.M.	7,195	V. America Relay	Monrovia, Liberia
	9,500	R. Tirana	Tirana, Albania
	9,700	R. Sofia	Sofia, Bulgaria
	9,715	R. Nederland	Hilversum, Netherlands
	9,745	R. Baghdad	Baghdad, Iraq
	17,800	Vatican R.	Vatican City
	21,570	R. Nederland	Hilversum, Netherlands
	4,770	Sudan Interior	Monrovia, Liberia
	4,800	R. Lesotho	Maseru, Lesotho
	7,275	RAI	Rome, Italy
9,670	IBRA Radio	Sines, Portugal	
9,710	RAI	Rome, Italy	
11,670	All India R.	Delhi, India	
11,800	RAI	Rome, Italy	
11,910	R. V. Gospel, ETLF	Addis Ababa, Ethiopia	

3 P.M.	6,040	V. America Relay	Monrovia, Liberia
	6,090	R. Baghdad	Baghdad, Iraq
	9,575	RAI	Rome, Italy
	11,850*	R. Ghana	Accra, Ghana
	11,910	R. V. Gospel, ETLF	Addis Ababa, Ethiopia
	11,930	R. Grenada	St. George's, Grenada
	15,084	R. Iran	Teheran, Iran
	6,205	R. Nordsee Int.	International Waters
	9,690	R. New York World-wide, WNYW	New York, USA
	9,760*	R. Ghana	Accra, Ghana
3:15 P.M.	11,620	All India R.	Delhi, India
	11,850*	R. Ghana	Accra, Ghana
	5,038	R. N.	Bangui, Central Af. Rep.
	9,655	Centrafricaine	Damascus, Syria
	11,890	Syrian B. S.	New York, USA
	11,920	R. New York World-wide, WNYW	New York, USA
	15,145	RTV Ivorienn	Abidjan, Ivory Coast
	15,185	R. N. Espana	Madrid, Spain
	15,340	Office RTV Francaise	Paris, France
	15,425	R. WINB	Red Lion, USA
3:30 P.M.	15,425	R. Habana Cuba	Havana, Cuba
	17,725	R. Cairo	Cairo, Egypt
	21,525	R. New York World-wide, WNYW	New York, USA
	5,038	R. N.	Bangui, Central Af. Rep.
	6,065	Centrafricaine	Damascus, Syria
	6,170	R. Sweden	Stockholm, Sweden
	6,205	Israel B. A.	Jerusalem, Israel
	9,640	R. Nordsee Int.	International Waters
	9,460	R. Pakistan	Karachi, Pakistan
	9,625	Israel B. A.	Jerusalem, Israel
3:45 P.M.	9,640	Vatican R.	Vatican City
	11,970	Sudan Interior	Monrovia, Liberia
	15,100	Mission, ELWA	St. George's, Grenada
	15,100	R. Grenada	St. George's, Grenada

TIME (EST)	FREQ.	STATION (CALL)	LOCATION	
<b>4 P.M.</b>	5,026	R. Uganda	Kampala, Uganda	
	9,650	Canadian B. C.	Montreal, Canada	
	15,295	R. Australia	Melbourne, Australia	
<b>4:15 P.M.</b>	15,325	Canadian B. C.	Montreal, Canada	
	15,340	R. WINB	Red Lion, USA	
	6,005	Marconi R., CFCX	Montreal, Canada	
	7,125	V. Revolution	Conakry, Guinea	
	9,009	Israel B. A.	Jerusalem, Israel	
	9,625	Israel B. A.	Jerusalem, Israel	
	9,650	V. Revolution	Conakry, Guinea	
	11,905	United Nations R.	New York, USA	
	17,760	R. New York World-wide, WNYW	New York, USA	
	<b>4:30 P.M.</b>	6,025	R. Budapest	Budapest, Hungary
6,110		British B. C.	London, England	
9,580		British B. C.	London, England	
11,780		British B. C.	London, England	
15,300		V. Andes, HCJB	Quito, Ecuador	
<b>4:45 P.M.</b>	17,740	V. Andes, HCJB	Quito, Ecuador	
	15,300	V. Andes, HCJB	Quito, Ecuador	
	17,790	American Forces RTVS	Washington, USA	
<b>5 P.M.</b>	3,316	R. Sierra Leone	Freetown, Sierra Leone	
	4,770	Sudan Interior Mission, ELWA	Monrovia, Liberia	
	6,130	R. Ghana	Accra, Ghana	
	7,130	British B. C.	London, England	
	7,150	R. Moscow	Moscow, USSR	
	9,515	R. Ankara	Ankara, Turkey	
	9,545	R. Ghana	Accra, Ghana	
	9,570	RTV Kaduna	Kaduna, Nigeria	
	9,620	R. Belgrade	Belgrade, Yugoslavia	
	11,780	British B. C.	London, England	
	11,860(1)	R. Norway	Oslo, Norway	
	15,195	R. Ankara	Ankara, Turkey	
	15,205	V. America Relay	Tangier, Morocco	
	15,285	R. Ghana	Accra, Ghana	
	17,820	V. America	Dixon, USA	
	3,255	Liberian B. C.	Monrovia, Liberia	
	4,820	R. Gambia	Bathurst, Gambia	
	6,010	R. Moscow	Moscow, USSR	
	9,695*	R. RSA	Johannesburg, South Africa	
	9,715*	R. Nederland	Hilversum, Netherlands	
9,805	R. Cairo	Cairo, Egypt		
11,730*	R. Nederland	Hilversum, Netherlands		
11,970*	R. RSA	Johannesburg, South Africa		
<b>5:30 P.M.</b>	6,110	British B. C.	London, England	
	9,560	R. RSA	Johannesburg, South Africa	
	9,580	British B. C.	London, England	
	9,645	R. Norway	Oslo, Norway	
	9,710	R. Nederland	Hilversum, Netherlands	
	11,730	R. Nederland	Hilversum, Netherlands	
	11,850	R. Norway	Oslo, Norway	
	11,970	R. RSA	Johannesburg, South Africa	
	<b>5:45 P.M.</b>	3,316	R. Sierra Leone	Freetown, Sierra Leone
		4,900	Nigerian B. C.	Maiduguri, Nigeria
4,980		R. Ghana	Accra, Ghana	
5,015		R. Grenada	St. George's, Grenada	
6,050		Western Nigerian B. S.	Ibadan, Nigeria	
9,610		R. Vilnius	Vilnius, USSR	
<b>6 P.M.</b>		6,015	V. America Relay	Rhodes, Greece
		7,235	All India R.	Delhi, India
		9,530	All India R.	Delhi, India
		9,550	RTV Belge	Brussels, Belgium
	11,710	All India R.	Delhi, India	
	11,945	Canadian B. C.	Montreal, Canada	
	15,235	RTV Belge	Brussels, Belgium	
	15,345	Trans World R.	Bonaire, Neth. Antilles	
	<b>6:15 P.M.</b>	5,015	R. Grenada	St. George's, Grenada
		6,015	V. America Relay	Rhodes, Greece
		7,038	V. Vietnam	Hanoi, N. Vietnam
	<b>6:30 P.M.</b>	7,130	British B. C.	London, England
		10,040	V. Vietnam	Hanoi, N. Vietnam
		11,970	R. RSA	Johannesburg, South Africa
		15,435	British B. C. Relay	Tebrau, Malaysia
6,035		R. Warsaw	Warsaw, Poland	
9,560*	R. RSA	Johannesburg, South Africa		
9,695*	R. RSA	Johannesburg, South Africa		
10,006	Liberation Radio	Clandestine		

TIME (EST)	FREQ.	STATION (CALL)	LOCATION	
<b>6:45 P.M.</b>	11,970*	R. RSA	Johannesburg, South Africa	
	15,185	V. America Relay	Tinang, Philippines	
	6,080*	R. RSA	Johannesburg, South Africa	
	9,695	R. RSA	Johannesburg, South Africa	
	11,745	V. Andes, HCJB	Quito, Ecuador	
<b>7 P.M.</b>	7,065	R. Tirana	Tirana, Albania	
	9,700	R. Sofia	Sofia, Bulgaria	
	9,780	R. Tirana	Tirana, Albania	
	15,095	R. Peking	Peking, China	
	15,435	British B. C. Relay	Tebrau, Malaysia	
	17,673	R. Peking	Peking, China	
	17,860	British B. C. Relay	Tebrau, Malaysia	
	7,150*	R. Moscow	Moscow, USSR	
	9,610(1)	R. Norway	Oslo, Norway	
	9,790	R. Tirana	Tirana, Albania	
	11,675	R. Peking	Peking, China	
	11,835	R. AVEH	Cap Haitien, Haiti	
	11,935*	R. Portugal	Lisbon, Portugal	
	6,025*	R. Portugal	Lisbon, Portugal	
	6,175#	R. Sweden	Stockholm, Sweden	
<b>7:15 P.M.</b>	7,150(2,6,7)	R. Kiev	Kiev, USSR	
	7,175	R. Nederland	Malagasy Rep. Ascension Is.	
	9,510	British B. C. Relay	Kiev, USSR	
	9,665(2,6,7)	R. Kiev	Kiev, USSR	
	9,685(2,6,7)	R. Kiev	Kiev, USSR	
	9,770	Austrian R.	Vienna, Austria	
	11,970	R. RSA	Johannesburg, South Africa	
	11,975	R. Grenada	St. George's, Grenada	
	15,145	V. America Relay	Tinang, Philippines	
	15,290	V. America Relay	Tinang, Philippines	
<b>7:30 P.M.</b>	5,990	Vatican R.	Vatican City	
	6,125	RTV Belge	Brussels, Belgium	
	9,615	Vatican R.	Vatican City	
	9,770	R. Tirana	Tirana, Albania	
	11,725	Vatican R.	Vatican City	
	11,815	Trans World R.	Bonaire, Neth. Antilles	
	11,875	RTV Belge	Brussels, Belgium	
	15,235	RTV Belge	Brussels, Belgium	
	<b>7:45 P.M.</b>	6,010	RAI	Rome, Italy
		6,075	Ceylon B. C.	Colombo, Ceylon
6,090		R. Luxembourg	Villa Louvigny, Luxembourg	
6,130		Maritime B. C., CHNX	Halifax, Canada	
6,165*		R. Budapest	Budapest, Hungary	
7,200*		R. Moscow	Moscow, USSR	
9,540		R. Prague	Prague, Czechoslovakia	
9,575*		RAI	Rome, Italy	
9,625		Canadian B. C.	Montreal, Canada	
9,715		R. New York World-wide, WNYW	New York, USA	
9,720		Ceylon B. C.	Colombo, Ceylon	
15,120		Ceylon B. C.	Colombo, Ceylon	
15,320*		R. Australia	Melbourne, Australia	
17,795*		R. Australia	Melbourne, Australia	
17,880		R. Japan	Tokyo, Japan	
21,740*	R. Australia	Melbourne, Australia		
3,300	R. Grenada	St. George's, Grenada		
<b>8 P.M.</b>	5,930*	R. Prague	Prague, Czechoslovakia	
	6,040	Deutsche Welle	Cologne, W. Germany	
	6,090	R. Luxembourg	Villa Louvigny, Luxembourg	
	7,200*	R. Moscow	Moscow, USSR	
	9,510	R. N. Espana	Madrid, Spain	
	9,540	R. Prague	Prague, Czechoslovakia	
	9,560	R. RSA	Johannesburg, South Africa	
	9,575*	RAI	Rome, Italy	
	9,690	R. RSA	Johannesburg, South Africa	
	11,815	Trans World R.	Bonaire, Neth. Antilles	
<b>8:15 P.M.</b>	11,865	Canadian B. C.	Montreal, Canada	
	11,990*	R. Prague	Prague, Czechoslovakia	
	15,320*	R. Australia	Melbourne, Australia	
	17,795*	R. Australia	Melbourne, Australia	
	21,740*	R. Australia	Melbourne, Australia	
	5,980#	R. Bucharest	Bucharest, Rumania	
	6,040*	Deutsche Welle	Cologne, W. Germany	
	6,075*	Deutsche Welle	Cologne, W. Germany	
	6,150#	R. Bucharest	Bucharest, Rumania	
	9,625*	Canadian B. C.	Montreal, Canada	
	9,690#	R. Bucharest	Bucharest, Rumania	
	9,735*	Deutsche Welle	Cologne, W. Germany	
	11,715	Swiss B. C.	Berne, Switzerland	
	11,865*	Canadian B. C.	Montreal, Canada	
	11,940#	R. Bucharest	Bucharest, Rumania	
15,235	R. Japan	Tokyo, Japan		

TIME (EST)	FREQ.	STATION (CALL)	LOCATION
8:45 P.M.	15,250#	R. Bucharest	Bucharest, Rumania
	17,795*	R. Australia	Melbourne, Australia
	21,740*	R. Australia	Melbourne, Australia
	6,080*	R. RSA	Johannesburg, South Africa
	6,120	Swiss B. C.	Berne, Switzerland
	6,200	R. Tirana	Tirana, Albania
	7,300	R. Tirana	Tirana, Albania
	7,345*	R. Prague	Prague, Czechoslovakia
	9,535	Swiss B. C.	Berne, Switzerland
	9,560	R. RSA	Johannesburg, South Africa
	9,630*	R. Prague	Prague, Czechoslovakia
	9,695*	R. RSA	Johannesburg, South Africa
9,750	Swiss B. C.	Berne, Switzerland	
9,780	R. Tirana	Tirana, Albania	
11,715	Swiss B. C.	Berne, Switzerland	
11,970*	R. RSA	Johannesburg, South Africa	
15,320*	R. Australia	Melbourne, Australia	
15,519	R. Bangladesh	Dacca, Bangladesh	

9 P.M.	FREQ.	STATION (CALL)	LOCATION
9 P.M.	6,025	R. Portugal	Lisbon, Portugal
	6,035*	R. Warsaw	Warsaw, Poland
	9,585	Finnish B. C.	Porl, Finland
	9,675*	R. Warsaw	Warsaw, Poland
	9,680#	R. Moscow	Moscow, USSR
	11,730	R. Nederland Relay	Bonaire, Neth. Antilles
	11,840*	R. Warsaw	Warsaw, Poland
	11,855	R. New York Worldwide, WNYW	New York, USA
	11,925	R. N. Espana	Madrid, Spain
	15,510#	R. Peking	Peking, China
	17,490#	R. Peking	Peking, China
	17,533#	R. Peking	Peking, China
9:15 P.M.	2,450	R. 4VEH	Cap Haitien, Haiti
	6,025#	R. Portugal	Lisbon, Portugal
	6,040	Deutsche Welle	Cologne, W. Germany
	6,175#	R. Sweden	Stockholm, Sweden
	11,745	V. Andes, HCJB	Quito, Ecuador
	11,935#	R. Portugal	Lisbon, Portugal
	15,345	V. Free China	Taipei, Taiwan
	17,720	V. Free China	Taipei, Taiwan
	6,200	R. Tirana	Tirana, Albania
	7,300	R. Tirana	Tirana, Albania
	9,475*	R. Cairo	Cairo, Egypt
	9,545*	R. Lebanon	Beirut, Lebanon
9,550*	R. Cairo	Cairo, Egypt	
15,320*	R. Australia	Melbourne, Australia	
17,795*	R. Australia	Melbourne, Australia	
9,510	R. Tirana	Tirana, Albania	
9,510	British B. C. Relay	Ascension, Iles	
9,680	R. Habana Cuba	Havana, Cuba	
11,795	R. V. Gospel, ETLF	Addis Ababa, Ethiopia	
11,830	R. Habana Cuba	Havana, Cuba	
15,125*	V. Free China	Taipei, Taiwan	
15,345*	V. Free China	Taipei, Taiwan	
17,720*	V. Free China	Taipei, Taiwan	
17,780*	V. Free China	Taipei, Taiwan	
17,890*	V. Free China	Taipei, Taiwan	

10 P.M.	FREQ.	STATION (CALL)	LOCATION
10 P.M.	4,820	V. Evangelica, HRVC	Tegucigalpa, Honduras
	5,980#	R. Bucharest	Bucharest, Rumania
	6,035*	R. Warsaw	Warsaw, Poland
	6,037	Faro del Caribe, TIFC	San Jose, Costa Rica
	6,150#	R. Bucharest	Bucharest, Rumania
	7,170*	R. Moscow	Moscow, USSR
	7,285*	R. Warsaw	Warsaw, Poland
	7,345	R. Prague	Prague, Czechoslovakia
	9,525	R. Cairo	Cairo, Egypt
	9,520#	R. Bucharest	Bucharest, Rumania
	9,616	V. Andes, HCJB	Quito, Ecuador
	9,640*	V. Free Korea	Seoul, S. Korea
9,645	Faro del Caribe, TIFC	San Jose, Costa Rica	
9,660#	R. Moscow	Moscow, USSR	
9,675*	R. Warsaw	Warsaw, Poland	
9,690	RAE	Buenos Aires, Argentina	
9,700*	R. Moscow	Moscow, USSR	
9,730*	R. Moscow	Moscow, USSR	
11,840*	R. Warsaw	Warsaw, Poland	
11,890	R. Berlin International	Berlin, E. Germany	
15,120	R. Warsaw	Warsaw, Poland	
15,140+	R. Moscow	Moscow, USSR	
15,320#	R. Australia	Melbourne, Australia	
15,335+	V. Free Korea	Seoul, S. Korea	
17,795#	R. Australia	Melbourne, Australia	
4,925	R. Clube	Lorenco Marques, Mozambique	
5,930*	R. Prague	Prague, Czechoslovakia	
5,980+	R. Bucharest	Bucharest, Rumania	
6,130*	R. N. Espana	Madrid, Spain	
6,150+	R. Bucharest	Bucharest, Rumania	
6,165	R. Budapest	Budapest, Hungary	

10:15 P.M.

TIME (EST)	FREQ.	STATION (CALL)	LOCATION
10:30 P.M.	9,505	R. Cultural, TGNA	Guatemala City, Guatemala
	9,570+	R. Bucharest	Bucharest, Rumania
	9,630*	R. Prague	Prague, Czechoslovakia
	9,680*	R. Habana Cuba	Havana, Cuba
	9,690	RAE	Buenos Aires, Argentina
	11,830*	R. Habana Cuba	Havana, Cuba
	11,850	R. Erevan	Erevan, USSR
	11,880	R. Japan	Tokyo, Japan
	6,037	Faro del Caribe, TIFC	San Jose, Costa Rica
	6,140	R. N. Espana	Madrid, Spain
	7,110+	R. Moscow	Moscow, USSR
	7,345*	R. Prague	Prague, Czechoslovakia
9,540+	R. Moscow	Moscow, USSR	
9,630*	R. Prague	Prague, Czechoslovakia	
9,645	Faro del Caribe, TIFC	San Jose, Costa Rica	
9,730+	R. Moscow	Moscow, USSR	
11,705+	R. Sweden	Stockholm, Sweden	
11,840	R. Portugal	Lisbon, Portugal	
11,990*	R. Prague	Prague, Czechoslovakia	

10:45 P.M.	FREQ.	STATION (CALL)	LOCATION
10:45 P.M.	12,050+	R. Moscow	Moscow, USSR
	15,140+	R. S. C.	Moscow, USSR
	3,346	Zambia B. S.	Lusaka, Zambia
	6,037	Faro del Caribe, TIFC	San Jose, Costa Rica
	7,200	R. Moscow	Moscow, USSR
	7,285*	R. Warsaw	Warsaw, Poland
	9,580+	R. Moscow	Moscow, USSR
	9,645	Faro del Caribe, TIFC	San Jose, Costa Rica
	9,680*	R. Habana Cuba	Havana, Cuba
	11,760*	R. Habana Cuba	Havana, Cuba
	11,815*	R. Warsaw	Warsaw, Poland
	11,830*	R. Habana Cuba	Havana, Cuba
12,080*	R. Peking	Peking, China	
15,060*	R. Peking	Peking, China	
15,095+	R. Peking	Peking, China	

11 P.M.	FREQ.	STATION (CALL)	LOCATION
11 P.M.	3,396	Rhodesian B. C.	Gwelo, Rhodesia
	4,875	R. South Africa	Johannesburg, South Africa
	4,965	R. South Africa	Johannesburg, South Africa
	6,025#	R. Portugal	Lisbon, Portugal
	7,150#	R. Moscow	Moscow, USSR
	7,200#	R. Moscow	Moscow, USSR
	7,245	Austrian R.	Vienna, Austria
	9,505*	R. Japan	Tokyo, Japan
	9,535*	Swiss B. C.	Berne, Switzerland
	9,680	R. South Africa	Johannesburg, South Africa
	9,700	R. Sofa	Sofia, Bulgaria
	9,730	R. V. Gospel, ETLF	Addis Ababa, Ethiopia

11:15 P.M.	FREQ.	STATION (CALL)	LOCATION
11:15 P.M.	11,935#	R. Portugal	Lisbon, Portugal
	3,285	R. South Africa	Johannesburg, South Africa
	4,845	R. Botswana	Gaberones, Botswana
	6,025*	R. Portugal	Lisbon, Portugal
	6,120*	Swiss B. C.	Berne, Switzerland
	6,130*	R. Norway	Oslo, Norway
	7,115*	Thai N. B. S.	Bangkok, Thailand
	7,170+	R. Moscow	Moscow, USSR
	7,270	R. RSA	Johannesburg, South Africa
	7,275	RAI	Rome, Italy
	9,540+	R. Moscow	Moscow, USSR
	9,550*	R. Norway	Oslo, Norway
9,610*	R. Norway	Oslo, Norway	
9,730+	R. Moscow	Moscow, USSR	
11,905*	Thai N. B. S.	Bangkok, Thailand	
11,935*	R. Portugal	Lisbon, Portugal	
4,800	R. Lesotho	Maseru, Lesotho	
6,025	Nigerian B. C.	Enugu, Nigeria	
6,050	R. Clube	Lorenco Marques, Mozambique	

11:30 P.M.	FREQ.	STATION (CALL)	LOCATION
11:30 P.M.	6,075	Deutsche Welle	Cologne, W. Germany
	6,140	R. N. Espana	Madrid, Spain
	6,145	Deutsche Welle	Cologne, W. Germany
	7,200#	R. Moscow	Moscow, USSR
	7,240#	R. Moscow	Moscow, USSR
	7,310#	R. Moscow	Moscow, USSR
	9,345	Deutsche Welle	Cologne, W. Germany
	9,370	R. Bucharest	Bucharest, Rumania
	9,660*	R. Moscow	Moscow, USSR
	9,760	R. Habana Cuba	Havana, Cuba
	11,760	R. Habana Cuba	Havana, Cuba
	5,955	R. South Africa	Johannesburg, South Africa

11:45 P.M.	FREQ.	STATION (CALL)	LOCATION
11:45 P.M.	6,025#	R. Portugal	Lisbon, Portugal
	7,115*	Thai N. B. S.	Bangkok, Thailand
	7,300	R. Tirana	Tirana, Albania
	9,780	R. Tirana	Tirana, Albania
	11,685	R. Peking	Peking, China
	11,790	R. South Africa	Johannesburg, South Africa
	11,905*	Thai N. B. S.	Bangkok, Thailand
	11,935#	R. Portugal	Lisbon, Portugal
	15,095	R. Peking	Peking, China



## CB Corner

By Len Buckwalter,  
KQA5012



## CB in the Big City

**T**HE 24th Precinct in New York City once boasted the second-highest crime rate in town. That's not surprising since it covers a wild area of teeming ghettos and ritzy high-rises beside New York's Central Park. What's remarkable is that 35 neighborhood CBers have invaded the station house and set up a communications center right on enemy turf. At least that's what I believed when I walked into the precinct one evening to investigate what could be billed as a marriage between a mongoose and a cobra.

"Citywide . . . a fight involving 12 persons on the corner of 104th St. and First Ave." This message wasn't crackling over the police radio but was coming from a CB rig parked in a corner of the station house. A CB operator logged the call from a CB mobile and fed it into the police network to be assigned a priority. If the message had been more serious—a case of someone being assaulted or a burglary in progress—the CBER in the precinct house would have dashed into the next room and delivered it directly to the police radio dispatcher. Cops would have been on the scene in seconds.

During the next two hours the Citywide call barked over the CB speaker a dozen times. It's the informal call of the New York Citizens Emergency Radio Service, first CB group in the city to establish a base inside a police station. There's plenty of action. They handle some 400 calls a month on daily shifts running from 4 p.m. to midnight. An antenna 50 ft. atop the station house affords good signal coverage over most of the city. The CB rig was donated by a manufacturer and (here's a surprise) a colinear antenna was purchased and erected for the group by the NYPD.

Most calls into the precinct originate from CBers summoning help on Channel 9. The Citywide network welcomes calls from anyone requiring assistance and often services other outfits—like a CB-equipped bike patrol in the nearby park. By far, disabled cars trigger the most cries for help. Next are auto accidents. A sudden change in the weather also spells trouble. Some 45 calls for help

arrived during one dousing downpour. The monitor on duty, with hundreds of phone numbers in a special directory at his side, can cope with anything from a sick animal to a poisoning, or matters for customs officials and the CIA.

Sometimes the scene is more like *The Godfather* than the Good Samaritan. Several months ago two cops were assigned to guard the residence of Manhattan's District Attorney, Frank Hogan. The DA had received threats on his life and the patrolmen were parked in front of his home. When the cops spotted a car going up a one-way street in the wrong direction, they tried to intercept it. As they approached the vehicle, a man in the car aimed a machine gun at the two men, fired and cut them down in the street. Critically injured, they were rushed to a hospital and word of the event hit the police radio in the 24th Precinct. CBers at the station heard the message—there was an urgent need for blood. An appeal broadcast on Channel 9 drew an overwhelming response. Donors drove in from as far as Westchester, in the next county.

Behind this extraordinary partnership of cops and CBers is Bill Wahlin, a psychology professor at a nearby community college. Bill enjoys electronics as a hobby and has a complete radioteletype receiving rig in his home. When Bill got a CB license he saw the medium's great potential for public service. He could also appreciate its seamy side. Volunteer groups too often fall apart because of internal rivalry and what Bill diagnoses as a lack of an institutional base. The institution he selected was the 24th Precinct. Bill presented the idea of internal CB monitoring to the cops and a stroke of coincidence led to its quick acceptance.


At that time the 24th Precinct was becoming a model precinct—an experimental lab the city could use to try out new ways of reducing crime. One of the most important of these developments was better police relations with the community. Bill rode into the station on that wave and today his CB group

[Continued on page 104]

**Let ICS mail  
you a FREE  
demonstration  
lesson without  
obligation...  
to prove that  
you can learn  
TV Servicing  
at home.**

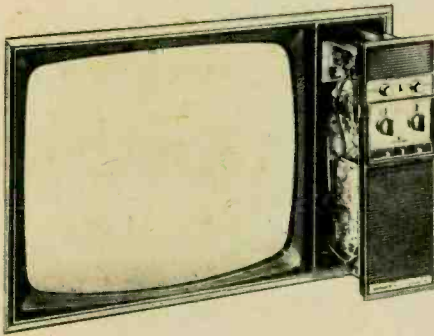Credit towards a Certified Electronic Technician (C.E.T.) rating will be granted by the National Electronics Association to ICS students upon completion of the ICS Career Program in TV Service/Repair.





**Practice on a new 25"  
MOTOROLA QUASAR II® chassis.**

TV Servicing is a satisfying career... and the pay is great. Qualified men are needed now to maintain the 93 million sets in U.S. homes. And prospects for the future are even brighter.

Now... here's an opportunity for you to prove to yourself that you can learn TV Servicing... at home, in your spare time. ICS, the world's most experienced home-study school, will send you a **FREE** Demonstration Lesson (complete with sample questions) if you will merely fill out the coupon below and mail it to us.

In addition to your free demonstration lesson, we'll send you... also **FREE**... a brochure that describes the 25" (diagonally measured screen) **MOTOROLA QUASAR II®** Color TV chassis that we include in our TV Service Training Program.

This chassis with automatic fine tuning control is ideal for training purposes because it combines solid state devices with vacuum tubes to give you both kinds of practical experience. All parts carry Motorola's two year replacement guarantee!

The **QUASAR II** chassis comes to you in three basic sub-assemblies... **NOT AS A KIT**... because we want you to learn how to *repair* TV sets, not build them.

Our free literature also describes the fully assembled test equipment you receive such as the Deluxe 5" Solid State Oscilloscope, the tools and the learn-by-doing kits, all of the finest quality.

And we're going to tell you about eight other career opportunities in Electronics and the ICS Career Programs that can help prepare you for them.

All you've got to do is mail the coupon.

**SEND IT TODAY!**

**ICS**

Since 1890  
**School of Electronics  
Scranton, Pa. 18515**

Canadian residents use above address for service from ICS Canadian Ltd in Hawaii; use Post Office Box 418, Honolulu

Approved for veterans under the new GI bill; approved for federally insured loans / Accredited by the Accrediting Commission of the National Home Study Council

**ICS School of Electronics  
Scranton, Pa. 18515**

**Dept. AA206W**

YES, I want you to mail to me without obligation, the **FREE DEMONSTRATION LESSON** and complete literature on the career program checked below. (Please check one.)


- |   |  |
|---|--|
| <input type="checkbox"/> Color TV Servicing   | <input type="checkbox"/> FCC License                     |
| <input type="checkbox"/> Computer Maintenance | <input type="checkbox"/> Communications/<br>Broadcasting |
| <input type="checkbox"/> CATV Installation    | <input type="checkbox"/> Hi-Fi Sound Systems             |
| <input type="checkbox"/> Telephony            | <input type="checkbox"/> Industrial Electronics          |

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

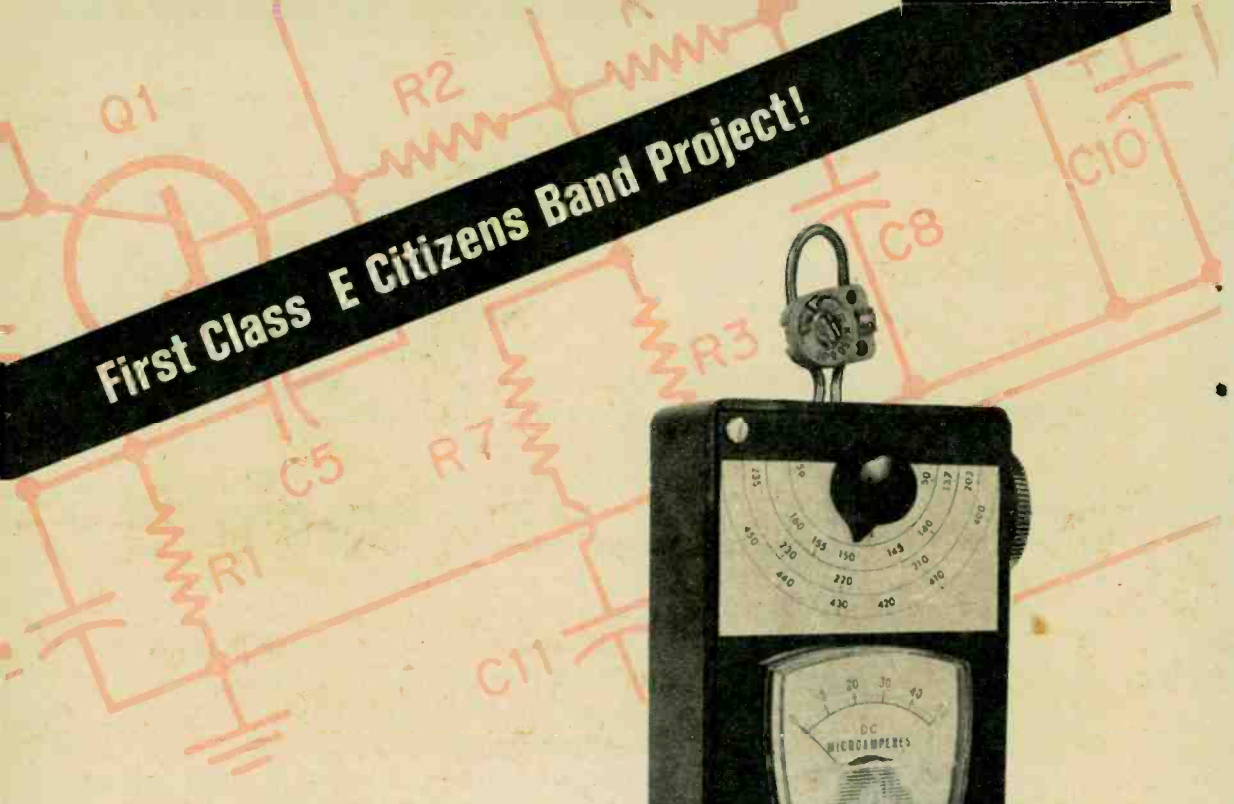

# First Class E Citizens Band Project!

By HERB COHEN



## The E-Dipper

*... Hams can use it on VHF & UHF, Too!*

**T**HOUGH the Class E Citizens Band, up there at 220 mc, is still in proposal form, Electronics Illustrated looks into the future and presents the first Class E project.

It's a grid-dip oscillator, one of those all-purpose types of gear the CBer, or anyone else interested in this potentially lively new band, will need to get himself established on Class E. A grid-dipper can help the CBer tune his rig, make antenna adjustments and do the chores every CB enthusiast faces before he can punch the talk button.

Hams also will find our GDO a useful accessory around the shack. Our grid-dip oscillator, dubbed the E-Dipper, operates across three of the busiest VHF/UHF ham bands. One of these bands, it happens, includes Class E CB. The E-Dipper's highest

# The E-Dipper

band (400-450 mc) enables the ham to adjust his UHF gear. This band is of particular importance since no commercial dipper covers this portion of the spectrum.

The E-Dipper is an inexpensive solution

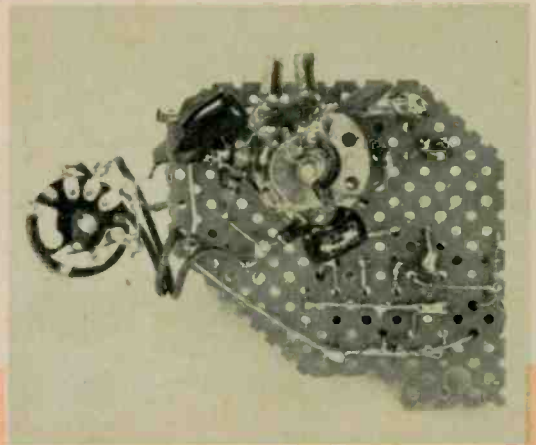


Fig. 1—RF wiring seen above. Lead lengths must be as short as possible. Perfboard is cut to shape shown to make room for battery B1.


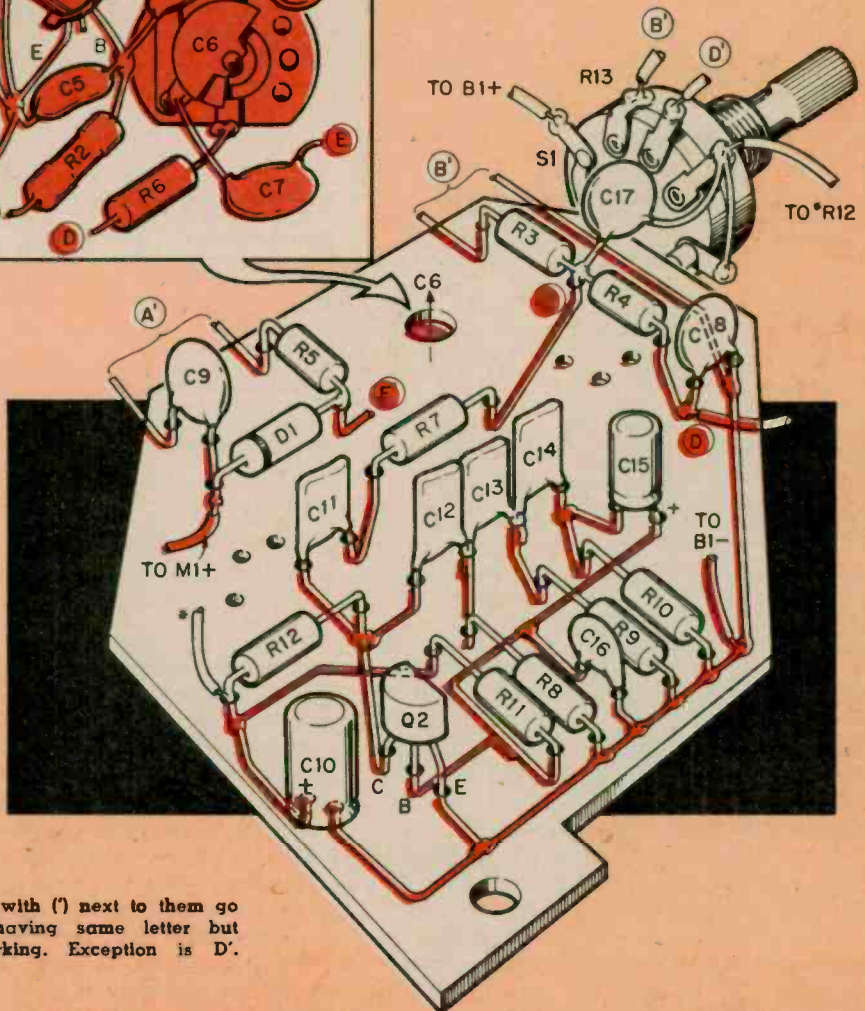
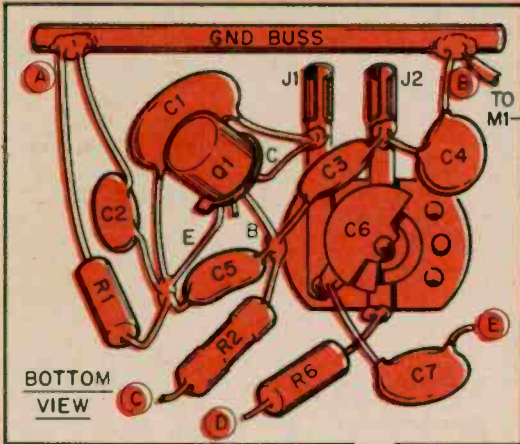


Fig. 2—Leads with (') next to them go to terminals having same letter but minus (') marking. Exception is D'.

Fig. 3—E-Dipper's wiring diagram. Compare schematic with pictorial on opposite page for exact lead placement. Lead lengths must be as short as possible. Cut off Q1's case lead before soldering transistor to components.

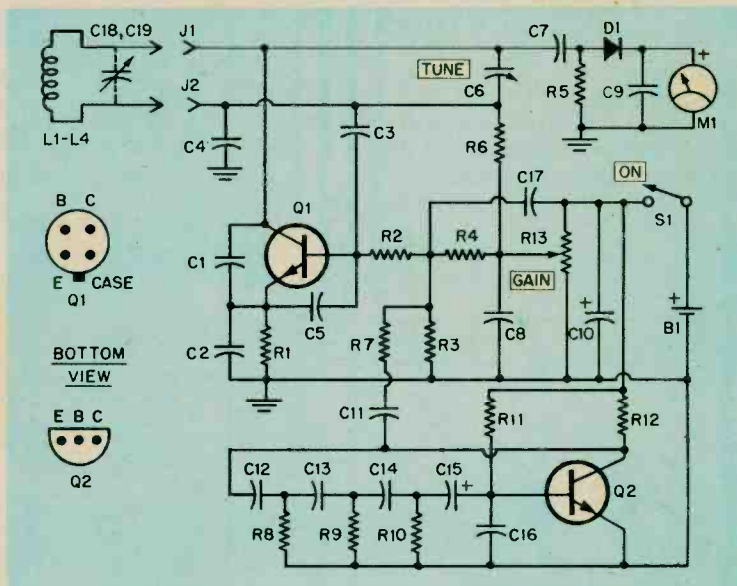

#### PARTS LIST

B1—9.8 V mercury battery (Mallory TR-177)  
 Capacitors: 1,000 V disc ceramic unless otherwise noted  
 C1—3.3  $\mu\text{f}$ , 5% silver mica  
 C2—15  $\mu\text{f}$   
 C3, C16—200  $\mu\text{f}$   
 C4, C17—0.001  $\mu\text{f}$   
 C5—10  $\mu\text{f}$ , 5% silver mica  
 C6—1.5-5.0  $\mu\text{f}$  variable (E. F. Johnson 167-102-1)  
 C7—10  $\mu\text{f}$ , 5% silver mica  
 C8—0.001  $\mu\text{f}$   
 C9—0.001  $\mu\text{f}$   
 C10—100  $\mu\text{f}$ , 10 V electrolytic  
 C11-14—0.01  $\mu\text{f}$   
 C15—1  $\mu\text{f}$ , 50 V electrolytic  
 C18, C19—4-30  $\mu\text{f}$  variable trimmer  
 D1—1N60 diode  
 J1, J2—Octal tube pin jacks (see text)  
 L1-4—see text

M1—0.50 ua. DC microamp meter (Lafayette 99R 50494 or equiv.)  
 Q1—Npn transistor (RCA SK-3019)  
 Q2—Npn transistor (Motorola MPS-2924)  
 Resistors:  $\frac{1}{4}$  watt, 10% unless otherwise noted  
 R1—470 ohms  
 R2, R6—150 ohms  
 R3, R5, R8-10, R12—5,600 ohms  
 R4—12,000 ohms  
 R7—100,000 ohms  
 R11—1,000,000 ohms  
 R13—5,000 ohms, audio-taper miniature pot with SPST switch  
 S1—SPST switch (mounted on R13)

Misc.—No. 10 copper buss wire, 4 x 3 x 1  $\frac{3}{4}$ -in. bakelite case and front panel,  $\frac{3}{8}$ -in. insulated standoff,  $\frac{3}{8}$ -in. i.d. plastic tubing, knobs, perf-board, etc.

to the problem of trying to adjust gear with a dipper at VHF or UHF frequencies. Basically, it spans three frequency ranges, all of which are of current interest to the ham. Starting with the lowest, or 2-meter band, the other popular frequencies covered are 220-225 mc (Class E) and 420-450 mc. All frequencies are amplitude-modulated.


Our E-Dipper departs from standard GDO design. This dipper uses a regenerative amplifier instead of the more common oscillator/wave-trap circuit. Reason is that sensitivity and selectivity of the dipper can be varied with pot R13 (*Gain*). The sensitivity of a standard GDO is fixed and this can be a

problem around low-Q traps or transmitter tank circuits. The selectivity of the E-Dipper's tank circuit also may be varied with R13 in order to simulate a wave-meter.

**How the E-Dipper Works.** Heart of the circuit is transistor Q1. It is operating as a conventional common-base, collector-to-emitter-feedback oscillator circuit. This enables maximum output power to be developed across the highest frequency range. Capacitors C1 and C2 form the RF feedback network and power match for the oscillator.

All ground symbols in the circuit eventually connect to a piece of No. 10 copper buss. Since this buss appears to be a high impedance

Fig. 4—Wind coils to dimensions as shown. Capacitor soldered to L4's leads is C19. See text for winding data.

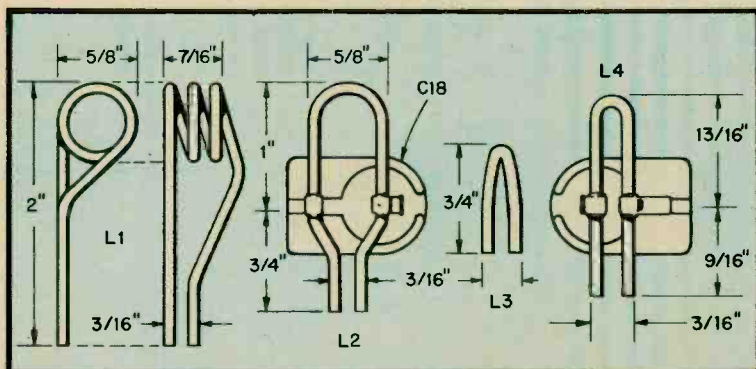

## The E-Dipper

in the UHF range, the base of Q1 must be bypassed directly to jack J2 through capacitor C3.

Part of the RF voltage appearing at Q1's collector is sampled via capacitor C7. The RF voltage is rectified by diode D1 and is used to drive meter M1.

Potentiometer R13 controls the collector base current to Q1. In the fully clockwise position, Q1 receives maximum voltage and current and oscillates at peak strength. When you back off the control until the meter reads about two-thirds full scale, the E-Dipper simulates a conventional grid dip.

If the control is turned back until the meter reads about 20 on the scale, the circuit becomes a very sensitive wave meter. Transistor Q1 is still oscillating very slightly, making it very sensitive to any RF in the vicinity. The oscillation cancels the losses in the plug-in coil assemblies, giving the meter a very sharp Q and high sensitivity.

Transistor Q2 is a phase shift oscillator

circuit. Output frequency is set for about 1,000 cps. This audio oscillator produces a clean sine wave which is coupled to the base of Q1 via components C11, R7 and R2. Result is a clean 1,000 cps signal modulating the RF waveform.

**Building the E-Dipper.** Jacks J1 and J2, the coil socket pins, are cannibalized from an old octal tube socket. They are the wrap-around variety and are soldered directly to variable capacitor C6. Line up the pins so they are spaced exactly 3/16-in. apart. They will eventually slide into a couple of holes in the plastic case.

Once capacitor C6 is mounted to the perfboard and the pins mounted to C6, wire the RF circuit. A No. 10 piece of buss wire serves as ground. It is 1 3/4-in. long and is fitted to the bottom edge of the perfboard.

All RF wiring around transistor Q1 must be made as short as possible. The transistor's leads must be especially short. The collector of Q1 should be soldered directly to the tab of J1, with a lead length of less than 1/4-in. Cut off the case lead of Q1 before mounting it.

Next step is to wire the phase shift oscillator. Though wiring is not critical, keep the leads of capacitor C16 as close to the base and the emitter of Q2 as possible.

Since the tuning capacitor's shaft is too short, a 3/8-in. dia. plastic sleeve is epoxied to the shaft. Attach the knob to it after assembly. This piece of plastic not only extends the shaft but also decreases stray capacitance.

Final step is to connect meter M1 and mercury battery B1 into the circuit. Then cement the frequency dial scale (Fig. 5) to the cabinet. Adjust capacitor C6 for full mesh. Then mount the perfboard into the cabinet with a 3/4-in. insulated standoff. Place

[Continued on page 98]

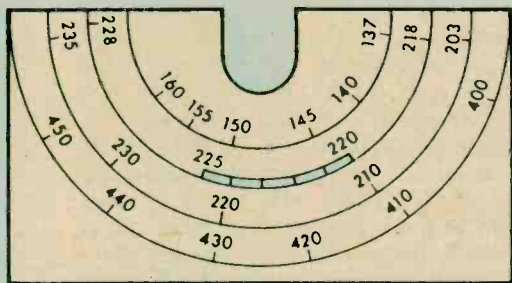


Fig. 5—Class-E band is colored area of dial.

# El's Hi-Fi Contest



\$200 First Prize goes to R. Iozzo, Mt. Vernon, N.Y., for an elaborate conventional hi-fi layout.



\$50 Third Prize is won by Richard Packer, Salt Lake City, Utah, for an ingenious hi-fi coffee table.

**O**UR new Hi-Fi Contest begins in this issue with the first group of cash-prize winners. Because of a magazine's far-ahead publishing schedule, the prize installations were chosen from only a small group.

However, we believe these four entries represent some of the criteria we are trying to employ in choosing prize-winning hi-fi installations. The sheer mass of equipment and money spent on audio gear should, we figure, be largely ignored. Otherwise, it becomes a matter of who has the most money.

Instead, we look with favor upon instal-



\$100 Second Prize is awarded to Robert Johnson of Bethany, Okla., for compact rec-room installation.



\$25 Fourth Prize is awarded to C. A. Simmons, Bakersfield, Calif., for a novel treasure-chest stereo.

lations which obviously have been the object of much thought and ingenuity by the owner. Thus, an unusual setup that is pleasing to the owner may get the nod over one that looks like a listening room at an audio store.

To enter your installation in our contest, send us one or more good black-and-white photos (8x10s preferred), a list of your equipment and a description of what you've done. Pack the pictures well to avoid damage. We will return unused photos. Mail your entry to: El's Hi-Fi Contest, 1515 Broadway, New York, N.Y. 10036. —



## Hi-Fi Today

By Robert Angus



## Matrix or Discrete 4 Channel?

**R**EADERS will recall the bitter battles between CBS and RCA over the long-playing record vs 45-rpm discs and over rival systems for color TV. Corporate prestige was at stake and no holds were barred. History will record that CBS won the record battle—though it took nearly ten years to do so—while RCA walked away with the color TV honors.

Now they're at it again. The latest contest over four-channel records is regarded by each side as the tie-breaker. For the short term, CBS is the obvious winner with its SQ system of matrixed four-channel sound. Just about every major manufacturer of stereo receivers and amplifiers has at least one model with a built-in SQ decoder. The system has become so popular (in less than a year) that some manufacturers touting their own matrix systems either have modified their own equipment (as Electro-Voice has done) or have a two-position, four-channel switch on their equipment—one for their own system, the other for SQ.

Columbia Records, meanwhile, has culled its catalogue for best-selling albums by artists like Santana, Blood Sweat & Tears, Leonard Bernstein and others, and has persuaded independent labels like Vanguard to go along with the SQ system. In terms of numbers of records sold, SQ has long since passed Sansui and Electro-Voice.

Now RCA enters the scene with a discrete



Combination record changer and discrete four-channel demodulator plus cartridge. Model 4VC-5244, made by JVC America, will cost \$189.95.

four-channel record. RCA, along with Panasonic and JVC (the latter actually developed the discrete system in Japan), first took the wraps off the record late last year. At that time, they hinted that it would be several months before all the bugs were ironed out. Now, say JVC and Victor, the bugs are out and the records are ready to go.

Because of the mechanics of the hi-fi component business, this means that if you want to play back an RCA record—assuming you can find one by the time you read this—you'll have to buy the equipment from Panasonic or JVC. Nobody else has any. Fortunately for you, JVC has been selling playback equipment in Japan for the past year or two, so there really are some decoders and receivers built for the system. At the same time, the rest of the industry will be pushing SQ for all it's worth. It's simply too late for most American manufacturers to include a multiplex decoder for the RCA system in this year's product line, even if they wanted to.

RCA and JVC will have to wait until next year to test their system in competition with CBS. Meanwhile, RCA's record company promises to build up a library of records to rival CBS, and JVC presumably will be trying to prove to the trade and to audiophiles that bugs like degradation of the four-channel signal and problems with broadcasting the discs over stereo FM stations have indeed been solved. If they're successful, next year's components from Japanese and American manufacturers may feature a multiplex decoder instead of—or in addition to—the SQ circuitry.

It's worth noting that in the LP-45 battle of 1948-1951, RCA was the largest record company, with most of the desirable artists. Columbia was in second place. By lining up support from just about every independent record company, however, Columbia carried the day for the LP. Now Columbia is on top, both in terms of record sales and big-name artists. RCA isn't even second—which means the company will have to try very much harder. —

# A TV Antenna System That Lasts & Lasts & Lasts

**W**HAT happens to old TV antennas? Unlike old soldiers, they don't just fade away. No, they tend to hang around—sometimes in shreds from a chimney mast, unfortunately. And with TV coming up on a quarter century of intense popularity, there are a lot of old antennas on the housetops of the world.


We set out to put together a TV antenna system that would give maximum usefulness during the longest life possible. The result is a broadband VHF/UHF/FM setup with a respectable amount of gain for primary viewing areas and the near fringes that should still be going strong when television is beginning to run golden-anniversary programs. Equipment from several manufacturers was used, nearly every piece having some special characteristic to recommend it.

The problem at the top of any system is corrosion, particularly in areas where the air contains a lot of salt. Antenna components made of ferrous metal tend to rust and fall away. The oxidation process on aluminum is slower, but thin-gauge parts do eventually pit badly and weaken. A first step to longer life is to select an antenna with the heaviest-

gauge aluminum available. Even better results are possible with gold-anodized elements (and as many related components of plastic as possible). We went even further, however, and selected an antenna made of fiberglass and thin foil conductors made by the Shakespeare Co. of Columbia, S.C. This rig, called the Model 426, has been turned out in limited numbers for use in high-corrosion areas such as coastal New England. The 426, which has moderate gain, sells for \$60 to \$80 (discounting being what it is) and probably will be around when the houses holding it up have become bug food.

Moving on down, we chose a heavy-gauge steel mast over aluminum. Steel may rust but it holds up better against twisting, turning and bending forces. Our mast and chimney straps came from Lafayette Radio.

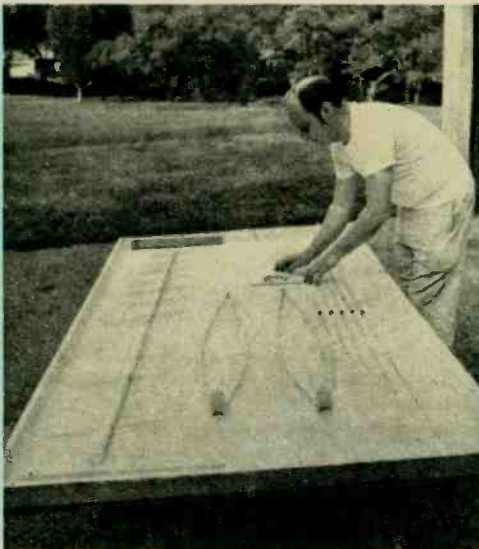
Most rotor systems today are pretty rugged affairs. We wanted one with simple controls and minimum whip and backlash action so we chose the AR-33 made by Cornell-Dubilier Electronics. We found the AR-33 to have good mechanical action but at the same time it's light enough to be easily handled on the roof. There are bigger rotors with



Cross and conical elements are laid out and then assembled in fiberglass antenna by Shakespeare.

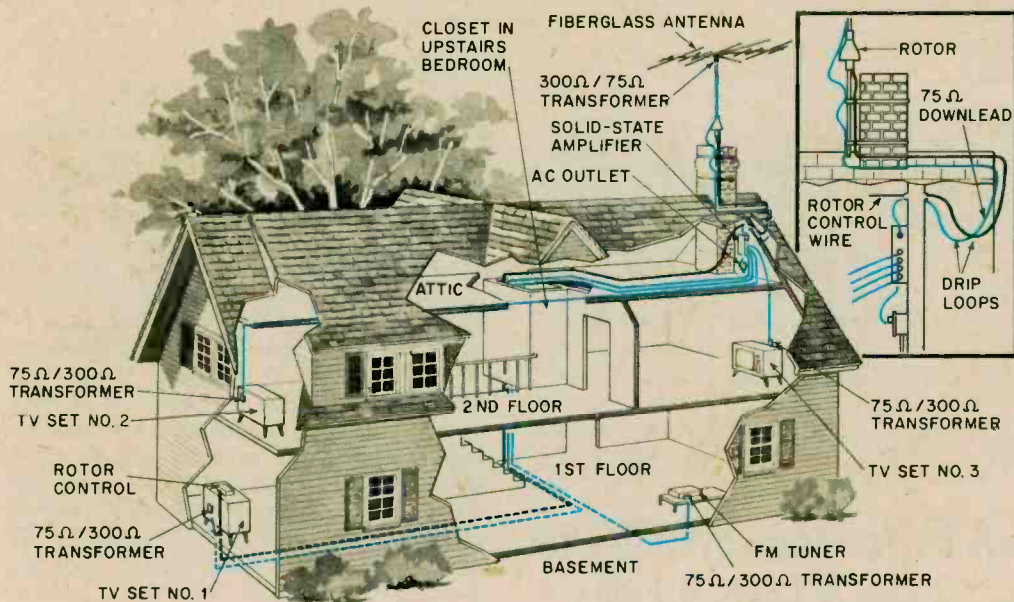The antenna has been assembled in photo below. Fiberglass and foil conductors make for long life.





TV antenna system designed to last for many years led to this kind of a layout in an old New England house of two stories, attic and basement. Setup would be somewhat different in other kinds of home designs.

enough power to turn a house around but they are used mainly to hold up large ham arrays—and they weigh enough to give you a hernia.

Everyone seems to agree these days that for the biggest and cleanest signal at the TV set, coax downloads and matching transformers are called for. Our choice was RG-59/U coax with a nominal impedance of 75 ohms (though you may see a listing of 72,

73 or even 70 ohms) and again it was a Lafayette product.

Since TV antennas have an impedance of 300 ohms, it is necessary to have a 300/75-ohm transformer at the antenna and a 75/300-ohm transformer at each TV or FM receiver. We installed the outdoor 300/75 transformer from the Winegard Co. on the antenna's boom as close as possible to the connecting points. The transformer (T-28M)

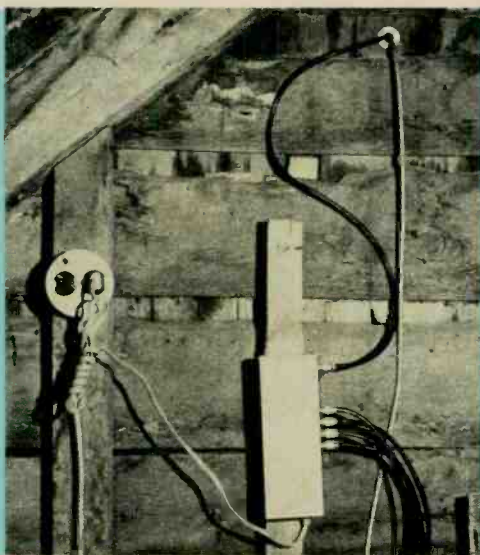


Photo at left shows inside of attic; coax and rotor cable come through wall, connect to booster.

Seen from outside (below) coax and cable form drip loops outside attic; plastic tube goes through wall.



Two Antenna Systems: Old vs New				
TV Channel	Signal Strength ( $\mu\text{V}$ )			
	New System		Old System	
	pix	sound	pix	sound
2	12,200	8,000	7,000	3,600
4	6,000	6,800	2,500	3,250
5	12,000	6,000	6,000	4,500
7	5,000	2,500	3,000	1,100
9	6,000	6,000	1,800	1,700
11	5,500	3,400	1,400	1,700
13	3,500	2,250	1,200	1,100

## A TV Antenna System That Lasts & Lasts & Lasts

has a snug rubber boot but we also daubed liquid rubber on the seal edges because it's exposed to moisture, wind, ice and the other baddies, and replacement means taking down the whole antenna.

For a signal amplifier and distributor, several choices are available. For instance, there's a wide selection of mast-mounted amplifiers. However, we were looking for maximum life with minimum service so we chose an indoor model, Winegard's BC-782, which is an 82-channel booster-coupler. The BC-782 has an impedance of 75 ohms to match the coax we were using, offers a gain of 6.5db and feeds four TV or FM receivers. Its solid-state circuitry means a long and trouble-free operating life (we trust) up there in the attic. The temperature around it in summer never gets to great heights (over 85°), which is fortunate. Neither tube nor transistor models can stand up to high temperatures for long and a really hot attic usually means moving the booster farther down the line to a closet or some other living area of the house.

The selection of equipment from there on down was pretty obvious (coax, 75/300 transformers at the sets, etc.), with one exception: we decided to run the coax directly to the sets in all but one case rather than  
[Continued on page 95]

1. Checking Cornell-Dubilier rotor and control. 2. 75/300-ohm JFD transformer on back of TV set.

3. Reading signal strength with Jerrold 718 meter. 4. Outlet in floor couples coax and rotor cable.



# The El Ticker

**A**CCORDING to figures released by the Electronic Industries Association, imports of color television sets in a particular month early this year were 77.9 percent above the figure for the same month last year.

★ ★ ★

Manufacturers of electronic equipment recently polled by the EIA say they back legislation currently being considered by Congress which would set up a National Metric Conversion Board whose job would be to convert measurements in the U.S. to the metric system. Big incentive for manufacturers is prospect of more sales abroad, where most countries do use metric system.

★ ★ ★

Whatever be the plans of the FCC, the EIA wants to look into the problems of transmission of four-channel FM broadcasts to see what can be done to establish performance standards. EIA expects to conduct the study with the help of the FCC and National Association of FM broadcasters.

★ ★ ★

Don't hold your breath, but new FCC study of Citizens Band radio may be around the corner. Complaints are coming fast and furious while FCC's hands are tied.

★ ★ ★

FCC is holding hearings on a proposal for a domestic satellite service which would permit all qualified applicants to own and operate domestic communications satellite systems. General expectation is, there will eventually be four systems (not including international systems already in use). Categories of these systems would be telephone usage, international common carrier, data transmission and

television broadcast. Should these services link up to expanding cable television (CATV) operations, a whole new world of home services could be coming.

★ ★ ★

FCC has allocated seven pairs of frequencies in the 460-mc band to improve services for emergency medical communications. Such services telemeter a patient's vital signs—such as an electrocardiogram—through an ambulance telemetry unit to a hospital so doctors can communicate instructions immediately.

★ ★ ★

Electronics division of North American Rockwell Corp. (NRMEC) will start delivering electronic mini-calculators this June to Sears Roebuck, Lloyds of California and other consumer outlets. Machines will be sold under customer labels, but are based on advances made recently by NRMEC in liquid-crystal technology and large-scale integrated circuits.

★ ★ ★

Prices of monochrome television receivers may go up substantially if new ruling by the FCC regarding TV tuners is implemented, according to some consumer electronics manufacturers. Major complaint is that the FCC, when requiring 70-position TV tuners having detent for both VHF and UHF channels to be installed in all sets after July 1, 1974, also required that receivers be equipped with circuits for automatic frequency control (AFC)—seldom included up to now in monochrome sets. Should AFC become mandatory, manufacturers say they'll take small b&w sets off the market and raise prices of the rest.

# A Triggered Sweep Scope

AS a general rule, oscilloscopes built from kits have minimal pretensions to life in the laboratory. They can be useful to the experimenter and the serviceman but they don't as a rule run with the Ferraris and the Lotuses of their tribe.

Heath's new IO-103 kit scope is an exception to the rule of thumb we just reeled off. This instrument is the peer of much of the high-high-price lab gear being sold today. Which helps to explain why so much attention was lavished on it after its arrival in EI's lab. When Heath introduced this 5-inch rig we really wondered whether as a kit it could meet its impressive list of specifications. On paper, at least, the IO-103 looked good and maybe it was the answer to every electronics experimenter's dream of owning a low-cost, high-quality scope.

The IO-103 didn't disappoint us. This instrument met—and exceeded—every spec set forth by Heath. Just for openers, stated frequency response is from DC to 10 mc, plus or minus 3db. That's for at least 3-cm deflection. For input signals that yield 6-cm deflection, Heath states that the IO-103's frequency response is DC to 8 mc,  $\pm 3\text{db}$ .

We did not expect this \$229.95 kit scope to knock out ruler-flat DC-to-13-mc response with only 3-cm's worth of deflection. With a 6-cm signal fed into the BNC-type vertical input jack, overall response was DC to 10 mc within 3db.

Many criteria are vital to the successful operation of a scope. When all is considered, frequency response doesn't mean a thing if the scope has an ineffective sweep circuit. The IO-103 has a topnotch deflection setup that rivals that of the \$2,000 scope we used to test the IO-103.

Besides being triggered, the IC-based sweep circuit is switch-selected over a seven decade range. Sweep speed can be varied from 100 milliseconds to 100 nanoseconds per centimeter. Furthermore, a horizontal expansion control lets you magnify the signal




## Heathkit IO-103

seen on the screen to twice normal size. So the Heath IO-103 really has 14 ranges overall.

Triggering modes can either be set to auto or normal positions, plus- or minus-going inputs, AC or DC and internal or external triggering. Overall accuracy of the time base is 2 percent, against 5 percent as stated by Heath.

Actually, the triggered timebase feature of the IO-103 is almost reason enough to make a hobbyist shell out for this scope. A triggered-sweep scope means that, if you're a ham, SSB output and frequency measurements can be made directly in the shack without extra gear adding to the complexities or expense.

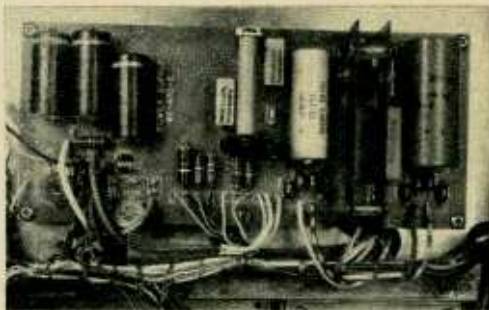This scope also is an invaluable item to have when you work on hi-fi. Couple it to the output of an audio amplifier and feed the amp with a swept-tone audio signal. The



Both high- and low-voltage power supplies are regulated. Fin-like structures are heat sinks.


bandwidth of the hi-fi rig is immediately made apparent on the scope's screen. Fact is, swept-audio tests are impossible to make with an ordinary recurrent-sweep scope.

The biggest difference between triggered- and the older recurrent-sweep scope is the ability to measure the frequency of an input voltage directly from the face of the graticule. This means that comparing input frequencies to standards via lissajous patterns is a measurement technique of the past. Merely count off the number of graticule divisions a complete waveform spans and multiply by the sweep setting. Reading frequency on the IO-103 is like reading volts, ohms or amps on a VOM.

Though the Heathkit IO-103 is a good performer, it required some troubleshooting on our part to achieve the figures mentioned. A power transformer with an open high-voltage secondary winding was supplied with the kit. A bad zener diode and open timing capacitor also were wired into the circuit before all three defective components were discovered during the alignment procedure.

At first, this didn't look like an easy kit. After all parts were taken out of the boxes and bags and checked against the parts list, we found there was a total of 56 transistors, 44 diodes and one IC. All these, plus other componentry have to be mounted on four circuit boards and the chassis. We originally thought that the IO-103 was for the intermediate- or advance-level hobbyist.

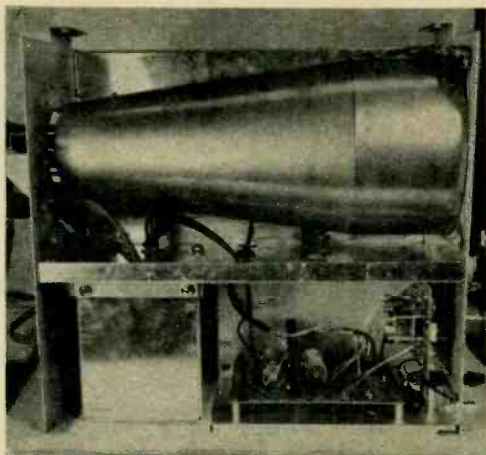But a person having no knowledge of electronics could, we came to believe, tackle portions of this scope kit. After learning the color code and reading the instruction manual and kit-builder's guide, we turned loose




Both power transformer and crt are magnetically shielded from circuit via large metal enclosures.


a novice who wired all components to the four circuit boards without a hitch.

After the four boards (power supply, vertical amplifier, attenuator, and combined horizontal amplifier-timebase) are wired, the main chassis wiring is completed. The majority of chassis components are mounted and interconnected to the front panel. A prewired and laced cable harness comes with the IO-103. This shortens construction time and also makes it more difficult to make wiring mistakes.

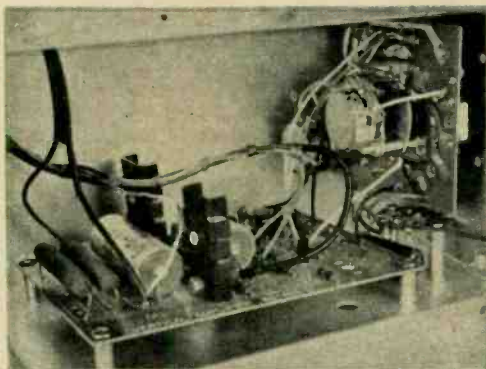All of the wiring steps outlined by Heath  
[Continued on page 99]



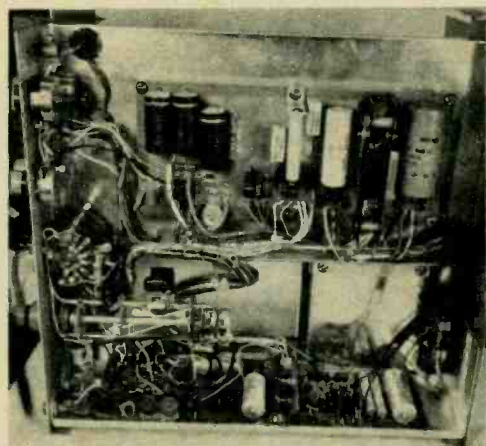Standoffs secure vertical amp to chassis. Attenuator pc board is attached to front panel.



Bottom pc board holds sweep generator, horizontal amp. Prewired harness saves wiring time.

## Good Reading

By Tim Cartwright



Books, Pamphlets,  
Booklets, Flyers,  
Bulletins and  
Application Notes.

FROM McGraw-Hill Inc., long a leading source for intermediate and advanced electronics texts, two books worth noting. One is **Solid-State Electronics Concepts** by John I. Matthews (406 pages, \$8.95), the other is **Instruments and Measurements for Electronics** by Clyde N. Herrick (560 pages, \$13.95). The Matthews book is a down-to-earth treatment of such topics as DC and AC circuits, diodes, transistors, FETs and typical applications. The presentation, which includes in each chapter a summary of concepts, glossary, references, review questions, plus problems and answers, seems to make it perfect for home study.

For those involved in servicing, experimenting or any kind of work that involves test gear, Clyde Herrick's book is a must. While it offers only limited information about troubleshooting procedures and applications of test instruments, it does offer excellent descriptions of how the gear operates and details about circuits. VOMs, VTVMs, bridges, scopes, generators, transistor testers, DVMs—they're all there.

Now that I've applauded some basic texts for beginners, I'd like to mention the latest in the series of superb RCA manuals. It's the **Solid-State Power Circuit Designer's Handbook** (SP-52, \$7.50). If you're an experimenter or other ampere-pusher, this 704-page powerhouse could surpass your wildest expectations. You won't find delicate receiving circuits here but rather brute power supplies, control systems, ultrasonic equipment and automobile ignition systems. The text grips each circuit, tells how it works, what it's made of and how to design one. If this handbook isn't in a local store, you can order it from: RCA Solid-State Div., Box 3200, Somerville, N.J. 08876.

Think Mallory, and capacitors, batteries and resistors come to mind. It's a surprise to learn that the company's latest catalog covers some 10,000 items. Besides offering many electronic components for project-building, Mallory has new items like security systems, cassette recorders and recording tapes. The **Mallory General Catalog**, which

describes them all, should be available from any distributor that carries Mallory products.

The more you tell, the more you sell, so goes the salesman's old saw. General Electric has decided to tell all in its **Nickel-Cadmium Battery Application Engineering Handbook**. The company believes it's the first comprehensive report on these cells. The manual is a bargain if you intend to select a ni-cad for a project, or design one into a new product. Coverage is exhaustive—ranging from theory and cell construction, to selection and application. The word engineering shouldn't put off the hobbyist because the text is written for newcomer and seasoned hand alike. Copies are available at \$2.50 each from: Battery Products Section, General Electric Co., Box 114, Gainesville, Fla. 32601.

Some writers of books for electronics experimenters are as about as close to their subject as an ulcer patient is to a hot pepper. Not so with Jim Ashe, whose new book is **Electronics Self-Taught With Experiments and Projects**. (TAB Books, \$4.95). He delivers hard-hitting information on setting up a home lab, laying out a workbench and lighting it. He offers valuable tidbits on handiest hardware sizes and parts assortments. Some advice, though, is controversial. Mr. Ashe is utterly opposed to soldering guns and recommends irons controlled by a Variac. He urges an oscilloscope with triggered sweep—while many hobbyists have yet to acquire the simplest service-type scope. He's also on shaky ground when he says, "A voltage regulator (to stabilize the AC line feeding your workbench) has more going for it than an impedance bridge or a sweep generator."

Since most test equipment tolerates almost any line-voltage swing in most localities, Mr. Ashe must be getting his juice from Afghanistan Alternator and Treadmill. He also takes a vicious swipe at QST magazine by calling their construction projects "frozen," then intimating that the more beautiful they look, the worse they perform. The opposition might say QST projects often work better than a brick outhouse (and that's a compliment)! —



## The Ham Shack

By Wayne Green  
W2NSD/1



## The Chips are Down on 220!

**T**HE Electronic Industries Association is keeping up a brave front, assuring everyone that its proposal for 80 new CB channels in the present 220-mc amateur band is a sure thing. But amateurs aren't at all convinced and are getting set for a real fight.

There has been relatively little ham activity on 220 in past years for a number of reasons . . . lack of military surplus equipment for these frequencies . . . lack of commercial gear such as mobile FM transceivers for business . . . lack of equipment designed for the amateur . . . severe power limitations, and considerable radar activity in the band—making much of it useless in large parts of the country.

It is interesting that the revival of interest by hams in 220 has coincided with the plot by the EIA to turn it into a big moneymaker for manufacturers who see the Citizens Band as a source of enormous profits. The rapid growth of 146-mc FM tipped the scales. Fact is, the FM part of the 146-mc band is not just full, it's overflowing and room for expansion is desperately needed. Only 220 mc holds promise for growth. If amateurs lose even part of this relatively narrow band (it's one-sixth the width of the next higher band), it could have serious consequences.

Through a series of FM symposiums being held across the country, FM amateurs and repeater operators are being alerted to the seriousness of the situation and are being offered a constructive counter-offensive. The basic theme: 220, Use it or Lose it. At the eastern symposium, users of over 50 repeaters pledged they would set up repeaters on 220 mc as soon as possible. The first repeater went into action a few days after the symposium. A few weeks later, a Midwest symposium was held and the 43 repeater groups represented there also agreed unanimously to set up 220-mc repeaters quickly.

In a few weeks, a third symposium will be held in California. It is hoped that 100 percent cooperation again will be the order of the day. If between 500 and 1000 220-mc repeaters are on the air by this fall, it will be exceedingly difficult for the FCC to go

along with the EIA proposal, no matter how strong lobby pressures in Washington are on the Congress . . . and they are strong. Money talks in Washington and there seems to be plenty of CB money. CB manufacturers are thinking of selling about \$500 million in equipment for the new band every year.

It's interesting to note that CBers do not want 220. In our opinion, at least. It is only the manufacturers, looking for big profits, who are trying to take the band away from amateurs. There is no skip on 220 . . . which takes away a lot of the fun. Direction finding is infinitely simpler there, which means that CBers will have to buy those \$20 licenses which many of them have been skipping for the last couple of years.

The shortage of equipment for 220 is about over. Three manufacturers already have introduced very nice 220-mc transceivers. These rigs will sell in the \$220-\$300 range and they're quite similar to the present 146-mc FM transceivers. Several other manufacturers are working round the clock to have models available for 220 by fall.

The first 220 rig announced is made by TPL Communications of Hawthorne, Calif. The AM/FM transceiver will sell for about \$220, will have crystal-controlled channels and a tunable receiver and transmitter—the best of both worlds. It is being marketed through Henry Radio as the Tempo Model 220. The driving force behind TPL is Tom Litty, K6RAD. Tom designed and builds the Tempo VHF power amplifiers.

Ed Clegg, W2LOY, the man behind the Clegg Division of ISC, returned from the first FM symposium to start work on a 220-mc transceiver. At the second symposium, he had a sample in hand and promised production several weeks later. His unit has many interesting features and will cost \$300.

Engineers in Japan have not ignored the fight for 220 and several rigs are in the offing. The first to arrive is made by the same company which makes the Market Luxury 2-meter FM rig and will be marketed by Drake. Standard and SBE are expected to have similar units soon. —

# Let Bell & Howell Schools help you prepare for a profitable electronic communications business of your own!

Announcing a unique, at-home training program that starts you on your way to a successful business — servicing two-way radio systems for planes ... boats ... fleets of taxis and trucks!



Two-way radio communications is one of the fastest-growing, most lucrative fields in electronics today. Almost two million commercial two-way radio systems now serve as vital communications links for trucks, planes, boats and taxis. And the FCC requires each system to have its equipment serviced regularly by a licensed technician. That's where *you* come in.

To get ready for a business of your own in two-way radio, you need: 1) career-oriented training; 2) FCC License; 3) "hands on" experience with commercial-grade equipment. Bell & Howell Schools offers a unique new at-home training program that gives you

*all three.* (See FCC License Guarantee on attached card.)

Find out more about this exciting new Bell & Howell Schools program. There's no obligation.



## The new at-home training program that gives you "hands on" experience with \$1,500.00 worth of actual commercial-grade equipment — right in your own home!

Knowing how to put an amateur radio kit together won't help when you're "on the job" —servicing two-way radio systems for aircraft or advising trucking companies about their land-mobile communications system. For that, you need "hands on" experience with the real thing. This new Bell & Howell schools learn-at-home program gives you just that.

Use a genuine commercial band FM transceiver. Test it for frequency, modulation and power output using sensitive professional instruments—right in your own home—as you prepare for a brighter future.

Bell & Howell Schools has helped many thousands of people prepare for careers —and businesses of their own—in electronics. You can have absolute confidence in the training you get.

Expert instructors at Bell & Howell Schools plan each program to answer a single question: "What qualifications will you need to take advantage of *actual career opportunities* in electronics?" They then build each program to give you those exact qualifications.

### HERE'S THE EQUIPMENT YOU'LL WORK WITH AT HOME

**Commercial-band FM transceiver** . . . exactly the kind of two-way radio you'll service throughout your career.

**Deviation meter** . . . model favored by many working technicians to check modulation of transmitted signal.

**Frequency meter** . . . highly sensitive instrument used to check signal frequency within precise tolerances established by government standards.



**Power output meter** . . . meter used almost universally by trained and licensed technicians to check power output—or wattage—of signal.

**Alignment generator** . . . a custom-designed unit you use to generate test signals for transceiver alignment.

### FCC REGULATIONS GIVE YOU THE OPPORTUNITY TO START YOUR OWN BUSINESS

The Federal Communications Commission requires that all commercial two-way communications systems be checked and serviced by a licensed technician at regular intervals.

As a Bell & Howell Schools graduate, you'll have the technical know-how you need. With your FCC license, you can go out and eventually build your own business—signing contracts with companies that use two-way radio. FCC regulations could mean *security and regular income for you!*

### BELL & HOWELL SCHOOLS OFFERS YOU THESE SPECIAL ADVANTAGES:

**Help Sessions** Scheduled regularly every few Saturdays at the Bell & Howell Schools and in many other cities throughout the U.S. and Canada. Top instructors give you personal help and guidance.

**Transfer Privileges** After completion, you can transfer to any of the resident schools for more advanced study, if you wish.

**Lifetime National Placement Service** Helps you locate a job any time after you complete your program.

**Veterans' Benefits** We are approved by the state approval agency for Veterans' Benefits.

**Student Financial Aid** We are an eligible institution under the Federally Insured Student Loan Program.

### EXCLUSIVE ELECTRO-LAB®— YOURS TO KEEP

To make sure you get practical experience with instruments used daily by professionals, we've integrated into your program three precision instrument kits you assemble yourself and keep:

**Design Console** Use this to rapidly "breadboard" circuits without soldering.

**Oscilloscope** Offers bright, sharp screen images, 3-way jacks for leads, plugs.

**Transistorized Meter** Registers current, voltage and resistance.

### FOR FULL INFORMATION, MAIL THE ATTACHED CARD TODAY!

DEVRY INSTITUTE OF TECHNOLOGY

ONE OF THE  
**BELL & HOWELL SCHOOLS**


4141 Belmont Avenue, Chicago, Illinois 60641 401



"... Aside from that, Al, it's a good buy..."

# Over and Out

*rodriguez*

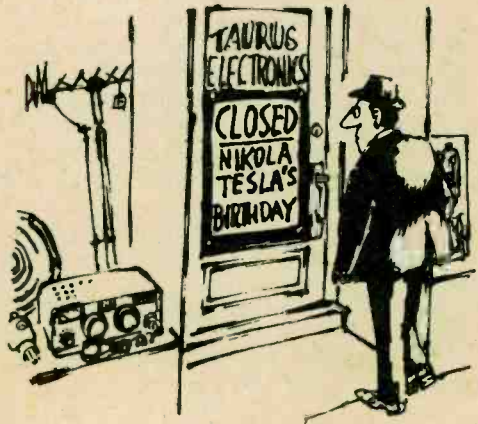

## Color TV Troubles

Continued from page 61

supply. I looked. They were both charred.

It was a classic case of the RF amplifier tube shorting out and burning up the resistor in the B+ leg. Two new resistors and a new tube restored all.

**Lacks the Basics.** My next-door neighbors are gift givers. If they happen to be in a store and see something appropriate for a friend they'll buy it and present it as a gift. When their TV went on the blink I was kind of glad. At least now I could do something for them.

The symptom was no Y signal (luminance). The sound was good but only a smeary color picture was displayed. There are four components in every color TV picture: a red signal, a blue signal, a green signal and the Y signal which makes up the b&w picture.

The Y signal has all the required frequencies to display a good b&w picture. Since the frequencies of the color signals are restricted they only fill in the b&w picture with color. Color signals are unable to construct a whole TV picture. When the Y signal is lost, the colors remain but are smeared.

In the color picture tube there are separate control grids in each electron gun for the three primary colors. The Y signal from the video circuits goes into all three cathodes simultaneously. If the Y signal should be absent, signal injecting can pinpoint the defective components in short order.

I brought over my flying-spot scanner from next door and began injecting. First setdown point was the cathode input to the CRT. Often a heater-to-cathode short in the CRT causes loss of Y signal. This wasn't the case here. When I touched down on the cathode a good b&w picture appeared.

I moved back into the Y circuits and began hitting one component after another. First a coupling capacitor, then a series resistor, then the delay line, etc. A good Y display kept reappearing.

I reached the plate of the video amplifier, then the control grid . . . still a good picture. Next came the video driver. The collector came through okay but when I hit the base of the transistor the picture disappeared.

I unsoldered the transistor and resistance measurements revealed the base-to-collector path was open. A new transistor revitalized the TV and the favor to my friends made my day. —

## Antenna System That Lasts

Continued from page 84

trying for wall outlets. The outlets are neat and handy but in an existing house it is difficult to snake either coax or twinlead in between the studs and to the electrical boxes. In our case, we did mount one box in the floor, behind the most-used TV set, which offers coupling for both the coax line and the five-wire rotor cable.

The antenna itself is folded out (in our case, with the fiberglass model, we worked with the individual elements) and mounted on the main mast. The rotor is mounted on a stub mast that gets the rotor just above the chimney (putting the weight as low as possible). The top bracket of the rotor, which comes off, then is mounted on the bottom of the main mast and, finally, the two halves of the rotor go together and you have a kind of a Christmas tree with coax and rotor cable dangling down like spaghetti.

The rotor and its control are preset by you to a particular direction (such as north) and then you point the antenna in that direction when you mount it. Thus, north at the controls downstairs also means north at the top. Some kind of through-wall tubing (we used Javex Tenna-Tube) is advisable to get coax and rotor cable through and into the attic.

Inside the attic, we cut a BX cable and installed a drop line and outlet box to power the booster/coupler, which we placed on the wall near the entry tubes. Unless you use splitters farther down the line to divide the signal between sets (and thus weaken it), you must run individual coax lines from the amplifier's outputs to each set.

Coax takes careful cutting and stripping before connectors are installed at the ends. The job is not difficult but requires patience. We used a cable cutting and stripping tool and a ferrule crimping tool from Winegard.

As a last step, the mast should be grounded as lightning protection. We used heavy aluminum wire running to a copper stake driven into the ground as far as we could get it—which was about 4 ft.

By the way, the system works. Our chart shows signal strengths we were getting with our old single-conical antenna and what we're getting now. In short, now is better. The figures were obtained from Jerrold's Model A.I.M. 718 antenna-installer's meter, which we found exceptionally sensitive. —

## One-IC Signal Tracer

Continued from page 35

you need to track down the signal. It's built in one package, and has a high-gain, high-input impedance amplifier with an RF probe, audio probe and built-in power supply.

Our signal tracer basically consists of gain control R1, emitter-follower amplifier Q1 and integrated circuit IC1. The overall input impedance is approximately 280,000 ohms. The IC power amplifier is rated for a maximum of 1 watt output into 8 ohms.

The RF probe consists of DC blocking capacitor C8 and diode detector D1. The capacity of the shielded cable serves as the RF filter. This assembly must be built in a shielded probe to avoid capacity-induced hum pickup from the user's hand. The audio probe consists of capacitor C9 and is housed in a shielded probe.


The signal-tracer circuit board is mounted to the main section of a 3 x 5 x 7-in. aluminum cabinet. A small section of perfboard approximately 2½ x 2¾-in. holds the amplifier.

First assemble the amplifier. While standard board can be used, construction will be easier if you use G-pattern perfboard. Although IC1 is round, its correspondingly round socket would be almost impossible to use for point-to-point wiring.

Form IC1's leads so they fit an in-line socket. Carefully bend leads 1 through 5 to one side and leads 6 through 10 to the other side. Note that lead No. 10 is directly opposite the tab. Form two sets of lead groups so they form a straight line. Next, separate out each lead so there is approximately ⅛-in. between leads. They should now fit into the socket. When wiring the amplifier, take care to note that two of the IC socket terminals on each side remain unused.

As long as you wire the layout according to the schematic, there are no special precautions. Make certain the polarities of the electrolytic capacitors are correct. The component leads can be soldered directly to the IC socket terminals but push-in terminals should be used for all other connections. Do not wire without these push-in terminals. Otherwise, complete amplifier instability can result.

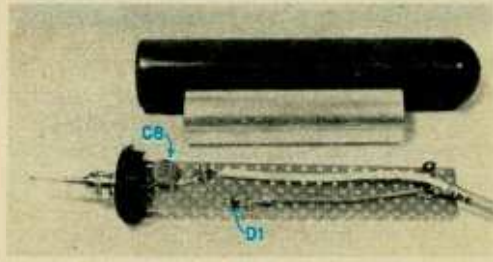When you wire both speaker terminals, make sure that only one connects directly to the positive battery supply. You cannot use a speaker that has one terminal connected



RF probe assembly. Add ground wire before you add metal shield. handle is slipped over perfboard.

to the speaker frame. This terminal would be grounded by the mounting screws to the cabinet, shorting out the battery supply. Both terminals must be insulated from ground.

Though IC1 is rated for an 8-ohm speaker, a 16-ohm type can be substituted with no appreciable loss in output power. Mount the speaker to the cabinet with a piece of scrap G-pattern perfboard serving as grille.

Leave sufficient space for the amplifier assembly and then mark the position of gain control R1, input jack J1 and B1 holder. Remove the speaker and drill the remaining component holes. Don't attempt to drill the cabinet with the speaker in position. Metal chips will most likely fall into the speaker cone and create a raspy sound.

After all cabinet-mounted components are installed, finish the tracer by mounting the amplifier. Secure an L shaped ground bracket to the perfboard amplifier. Fasten the other end of the bracket under one of the speaker mounting screws. Then interconnect all necessary wires.

Except for the connection between components J1 and R1, no shielding is required. The shield is formed by wrapping a section of insulated No. 20 or 22 solid wire around the wire leading from J1's center terminal to R1. Connect one end of the home-brew shield to R1's grounded terminal. Leave the other end of the shield free.

The battery can be fastened to the cabinet with an ordinary metal clamp or battery holder specifically designed for the standard 9 volt transistor radio battery.

The RF test probe is assembled from Keystone's type 1810 test probe kit. It consists of the probe case, an internal perfboard and shield. Screw the test probe tip into the front cap and insert a 0.001  $\mu$ f disc capacitor into the tip as far as it will go. Wrap the lead protruding through the tip once around the

groove at the base of the tip and cut off the excess lead. Tighten the knurled tip nut to secure the lead.

Position the supplied perfboard against the cap and insert one of the supplied terminals into the board about 1/2-in. from the capacitor. Solder the free capacitor lead and D1's cathode lead to this terminal.

At one end of the 36-in. length of shielded audio cable, trim back the shield and outer insulation. When the shield is soldered to the small solder lug which is already factory-mounted to the perfboard strip, the center conductor will reach the push-in holding down components C8 and D1. Insert the shield into the rivet hole on the solder lug. Solder a short length of wire from this hole to D1's anode lead using a push-in terminal. Bend the solder lug at right angles and slide the shield over the perfboard.

Straighten the solder lug, slide the shield back to the lug and solder the lug to the shield. At the same time, solder about 12 in. of flexible insulated wire to the solder lug. This will be the probe's ground lead.

Cut a small notch about 1/2-in. deep in the front end of the probe body and slide it over the shielded wire and probe. Bring out the ground lead through the notch and fasten the probe body to the cap with screws. Apply a phono plug to the free end of the shielded wire to complete the RF probe.

Assemble the audio probe the same way. You can use an identical test probe kit for this probe.

Overall gain is very high so all tests should start with the gain control no more than a quarter open. If you are tracing RF circuits, use the RF probe from the antenna through the RF and IF stages to the detector. From the detector to the loudspeaker, use the audio probe.—By *Herb Friedman*

### One-tube Radio

Continued from page 30

tank circuit is controlled by pot R2 (*Regeneration*). Sufficient positive feedback reduces losses in the tank. Too much feedback forces the receiver to oscillate.

Coil L1 is a standard ferrite loopstick antenna which covers the broadcast band. The secondary is ten turns of No. 22 wire wound tightly on top of the primary winding. Coil L2's primary winding consists of 22 turns of No. 24 enamelled wire. The secondary is

wound with six turns of the same gauge wire. Coil L3's primary is 12 turns of No. 24 gauge wire, while the secondary consists of six turns. After wiring the coils, coat with coil dope and let them dry.

After building the radio, advance R2 on each range and listen for an increase in noise level as the pot wiper is turned. If nothing happens, reverse the secondary leads of the coil.

Make your own dial scale and label it by marking down the frequencies of logged stations. Mount the radio in a cabinet if desired. For best results, connect a long-wire antenna and external ground. By *Herb Cohen*

### One-tube Amplifier

Continued from page 31

closer to ground via R5's wiper arm. Tone becomes bassy since more highs are diverted to ground.

Power amplification occurs in the pentode section labelled 1/2 V1(P). Unbypassed cathode resistor R8 introduces a small amount of negative feedback to reduce distortion and improve fidelity.

The secondary of the output transformer drives either a speaker via J2 or headphones through 100-ohm limiting resistor R9.

Power transformer T1 can be any unit having the specifications shown in the Parts List. The colors keying T1's leads are specifically for the transformer in the prototype.

Power supply rectification is full-wave with resistor-capacitor brute-force filtering. High voltage across capacitor C4B is 125 VDC. Total current to both tube plates is 18 ma.

Output power of the amplifier is nearly 1 watt to the load before distortion appears. High-frequency response is good and extends to 20,000 cps before dropping 3db.

Low-frequency response is not as good. The small size of the output transformer hampers bass response.

If a ceramic phono cartridge sounds too tinny, the problem can be cured by adding more capacity across the primary winding of the output transformer.

Though a test ceramic cartridge did not overload the amplifier input, some models may do so. This is remedied by increasing the value of R1. Also, if resistor R9 fails to reduce earphone volume sufficiently, increase R9's resistance. It was selected to drive 8-ohm phones comfortably. By *Len Buckwalter*

## CB Converter

Continued from page 33

as the secondary winding of L1. Two turns of the same wire wound next to the secondary is the primary half of the transformer. Coupling transformer L3 consists of a three-turn primary winding and 11-turn secondary. Both coil windings are wrapped around a 7/32-in. ceramic form. Again, use No. 24 gauge wire.

For best performance, make all component leads as short as possible. Point-to-point wiring with perfboard and push-in clips is a satisfactory wiring method. The prototype model was built on a 2 x 4-in. piece of perfboard. Layout is not critical.

To align the CB converter, tune the broadcast band receiver to 1500 kc (or any other frequency that is unoccupied on the band). Turn L2's slug until a rushing sound is heard. Then turn variable capacitor C6 and listen for an incoming call. While a transmission is in progress, adjust input RF transformer L1 for maximum signal. If the converter only monitors channel 9, peak L1 for maximum response at this frequency and substitute a trimmer capacitor having the same specifications for capacitor C6.—By Herb Cohen

## Home Intercom

Continued from page 34

muffled. The transformer corrects the frequency response.

The master station is housed in a 5½ x 3¼ x 7-in. aluminum cabinet. The amplifier we show is built on a 1¾ x 3-in. piece of perfboard. Push-in terminals are used for all tie points.

When installing IC1, take extra care that you solder to the correct terminals. Note that one end of IC1 has a tab, to which a heat sink will be soldered.

Carefully bend IC1's tab upright and coat it with solder. Cut a ½ x ¾-in. piece of metal from a tin can. Solder the metal to the tab. Follow the schematic and complete the sub-assembly wiring.

Do not eliminate capacitor C2. The amplifier might break into oscillation without it. Make certain capacitor C3's and C4's polarity is correct.

You may have to adjust the value of R2. Temporarily connect B1 to the amplifier. Measure the voltage from IC1 pin 12 to

ground with a VOM. If the voltage is approximately one half of the full supply voltage, R2's value is okay. If the voltage at pin 12 is less than 7 volts, change R2 for a lower value (50,000 ohms or so) until the voltage at pin 12 is about half the supply voltage.

Speaker SPK1 (and remote speaker SPK2) can be any intercom-type speaker of 30- to 45-ohm impedance. Any size from 2½-in. and up will handle IC1's output power.

Transformer T1 is soldered directly to the case of gain control R1. To avoid heat damage to T1, first coat R1 with solder where T1's mounting tabs will touch the case. Then coat the transformer tab with solder.

The remote station consists of a speaker and jack installed in a cabinet. The speaker can be cemented to the inside of the cabinet, a model supplied predrilled for speaker grille material and jack J2's mounting hole. Any cabinet can be substituted for the remote unit.—By Leslie Powell

## The E-Dipper

Continued from page 79

a knob over the plastic extension shaft glued to C6 and orient the pointer at the 137 mc marking on the lowest frequency band. If you built the E-Dipper exactly as shown, the knob pointed should indicate the appropriate frequency as selected by the plug-in coil. Of course, a signal generator is required for a more accurate calibration.

**Winding E-Dipper's Coils.** Four coils cover the bands described. All are made from No. 10 copper buss wire, the same type used to form the E-Dipper's ground buss.

The 400 to 450 mc coil, labelled L3 in Fig. 4, is a U-shaped piece of wire. Start with a 1-in. long coil and cut off the ends with a pair of nippers until the frequency rises to 450 megahertz at the minimum setting of capacitor C6.

The 203 to 235 mc winding, coil L2, is a larger U-shaped coil. The ends taper down to fit into the socket pins. Trimmer capacitor C18 is soldered across the base of the coil as shown and later adjusted to give the dipper's capacitor the correct frequency range.

The 2-meter coil, L1, is made from three turns of copper buss. It is wound to a ½-in. inside dia. and spaced so the length of L1 is 7/16-in. total.

The 218-228 mc. coil, L4, is a U-shaped coil. Solder C19 in place at the points indicated



## A Triggered Sweep Scope

Continued from page 87

in the assembly manual correctly match the component to be wired to the corresponding circuit-board position. A few steps, however, presented more-than-average difficulty to complete. Heatsinks on the power-supply board are referred to in the instructions as having a front and rear surface. We could not tell which side was front and which was rear.


The graticule lamps presented us with difficulties, too. The problem was finally solved by removing the already-mounted tie points which hold the lamp wires and gently pushing the lamps through a couple of rubber grommets which hold the lamps to the front panel. Then we remounted the tie points and soldered the lamp leads to the tie-point terminals. All of this extra work was done so that the extra-fine leads of the graticule lamps were not broken.

One error in the assembly manual that has nothing to do with wiring the kit should be pointed out. The right-hand column in pictorial 2-1 shows a 10  $\mu$ f electrolytic capacitor being soldered to the vertical-amplifier circuit board. If you later have reason to check circuit-board wiring against the schematic, you will find that the position of this electrolytic (capacitor C102) in the schematic is incorrect. The positive lead of this capacitor should connect to the shield terminal of transistor Q105 instead of the gate, as shown. Otherwise, the schematic is correct.

The final wiring chore consists of assembling an uncompensated coaxial test lead. It has the proper BNC plug on one end and a pair of alligator clips on the other. But don't think for a moment that this hunk of wire with attaching clips can be substituted for a compensated scope probe if you seriously want to make accurate measurements with your IO-103. Only use the supplied coax cable when you're working on low-impedance, low-frequency voltages. For accurately measuring signals, you'll have to invest in Heath's compensated scope probe. It costs \$19.95 and comes assembled.

To sum up, the Heathkit IO-103 is a kit scope that is well worth the initial outlay. It will take time to build and properly calibrate. But once these chores are completed, the IO-103 will more than reward the experimenter's or service technician's efforts.

## the EL SOCKET

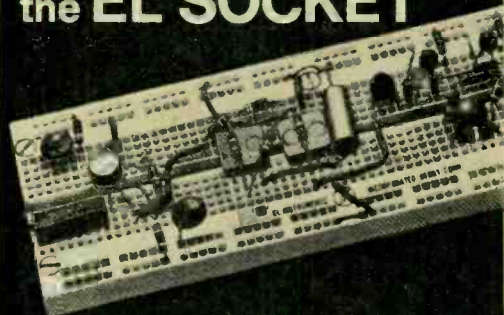

Test new circuit ideas...  
I.C. circuits...  
discreet components...  
at no risk!  
Money back guarantee!

**\$17<sup>25</sup>**

All you need are #4 mounting screws . . . just plug-in components . . . like 1/4 watt resistors, ceramic capacitors, diodes, I.C.s, transistors and more . . . and your circuit's built! No special patch cords needed! Components interconnected with any solid No. 22-26 gauge wire.

And you can try it with absolutely no risk for 5 days. If not satisfied, just return your EL Socket and receive a full refund. Trying is believing. How can you go wrong? Order your EL Socket now!

- Mickel/silver plated terminals — very low contact resistance
  - Low insertion force
  - Mounts with #4 screws
  - Initial contact characteristics beyond 10,000 insertions
  - Vertical, horizontal interconnecting matrices
  - Accommodates wide range of wire and component leads from .015"-.032"
- Send check or M.O. today!
- Add 50¢ for postage and handling
  - 25% deposit on C.O.D.s



EL INSTRUMENTS, INC  
61 First St., Derby, Conn. 06418  
Telephone: 203/735-8774

## Basic Transistor Circuits

Continued from page 52

are basic to an intriguing circuit widely used in push-pull audio stages.

If you recall the conventional push-pull output stage, the grids of the tubes are fed signals of opposite polarity via a phase inverter. One tube pushes while the other pulls. An output transformer having a center tap is required so that each tube can add its share of power to the output. Using transistors, the complementary symmetry circuit eliminates tubes, transformers and phase inverters.

The schematic diagram shows one NPN and one PNP transistor connected in series across the power supply. Let's assume the input signal is positive and that it's simultaneously applied to the bases of Q1 and Q2. Since transistor Q1 is an NPN type, a positive-going base signal causes an increase in collector current. At the same time, the positive signal causes a decrease in Q2's collector current (a PNP type).

This circuit draws about 80 ma. So an AC-operated supply of 9 VDC is recommended instead of a battery. The amplifier develops about a half-watt output in an 8-ohm speaker and requires several volts of audio drive. When we connected the amplifier to an FM tuner having a 1-volt output it produced good sound.

**Crystal Calibrator.** Almost all transistor circuits work as amplifiers even when they're called oscillators and switches. Project No. 3's circuit is a good example of how these various functions intermingle. If you recall the phono preamp, negative feedback was used to reduce high-frequency levels (equalization). In this circuit, we'll use positive feedback so the transistor goes into oscillation.

The oscillator produces a continuous signal when the power is turned on. When a surge of current causes the base of Q1 to become positive, it is instantly amplified as a large collector current. The signal will have its polarity reversed, however, as a consequence of its passing through the transistor. So a negative signal is applied to the base of Q2 which similarly amplifies it and reverses its phase.

A positive signal at the collector of Q2 is fed back to the base of Q1 through a quartz crystal. The result is that a tiny positive input signal to Q1 is rapidly reinforced by positive

feedback. This quickly drives Q1 beyond its ability to amplify—its saturation point—and no further signal reaches the base of Q2. This momentarily kills the positive feedback and Q1 starts conducting again.

The overall effect is that the transistors repeatedly switch each other on and off. For this reason, the device is called a multi-vibrator. It generates a square wave (see photo). Because the transistors alternately are driven into cut-off and saturation, the sine wave signal is clipped on both its positive and negative sides.

A special component is the 100-kc crystal. Since the crystal will pass only one frequency, the transistors are forced to switch at a 100-kc rate. This is the only signal permitted to deliver feedback. The square waves generated by this circuit are extremely rich in harmonics.

**RF Oscillator.** Millions of solid-state receivers have a radio-frequency oscillator similar to the one shown in the schematic for project No. 4. The tapped coil furnishes the important ingredient for any oscillator—a positive feedback signal of correct polarity. When the switch is turned on, collector current surges through the main winding of coil L1. Electromagnetic flux cuts across the lower coil and induces a current flow which reaches the base of Q1. This secondary flow serves as the positive feedback signal. It causes the base to pass more current.

The transistor quickly saturates, cannot amplify further and positive feedback halts. The coil's electromagnetic field then collapses and the stage drops back to its original state. The process is repeated as RF currents circulate at the resonant frequency determined by L1 and C1.

Selected component values permit the oscillator to operate over a range of 350 kc to 1000 kc. One valuable frequency in this band is 455 kc. You can place your RF oscillator next to a radio and use it as a BFO (beat-frequency oscillator). This will make code stations and single-sideband signals audible. The oscillator also can serve as a signal generator to provide a steady carrier for troubleshooting or receiver alignment.

**Voltage Control.** The circuit for project No. 5 shows how semiconductors can replace bulky tubes and rheostats in power control. It's also a handy item to have on a workbench.

Basically, the transistor serves as a variable resistance in series with a load. It's easy to

control many watts of working power by merely varying the tiny base current with a small potentiometer. The transistor shown is a PNP type, so collector current rises as R1 is rotated toward the negative side of the input. Emitter-collector resistance drops and more current reaches the load. Rotating R1 to the positive side reduces base bias until no current flows to the collector.

This circuit was tried with several loads. It can vary the speed of a small DC motor or the brightness of a pilot lamp. Also, a 6-volt high-intensity lamp was controlled over a range of 0 to 4 amperes. To prevent thermal damage, the transistor is mounted on a heat sink. Any PNP audio-output transistor capable of handling several amperes should work in this circuit.

**RF Preselector.** The circuit for project No. 6 features a field-effect transistor (FET). The transistors used in our other projects are called *bipolar* because they depend on charge carriers of two types, free electrons and holes. An FET is *unipolar* because it depends on only one carrier. (We will use an N-channel FET. P-channel FETs also are available.)

The two main terminals of an FET are called the source and drain. They lie at either end of a channel. The charge carriers (free electrons in N-channel devices) are drawn from the source to the drain because of a positive voltage applied to the drain. A third terminal, the gate, controls the flow of current.

As a signal on the gate becomes increasingly negative, its electrical field creates a *depletion* region in the channel. This constricts the current. It's comparable to the effect of a vacuum-tube grid. Amplification results when a tiny gate voltage controls a large drain current.

An important characteristic of the FET is that no current flows in its gate circuit. Control is exerted via electrostatic charges, not via a control current. Thus, input resistance is extremely high. This is an advantage in RF amplifiers since it prevents unwanted mixing of signals and annoying crosstalk.

Our RF preselector is designed to boost the performance of a shortwave or ham receiver that works poorly on the higher bands. The coil specified covers 6 to 13 mc, but you can place a tap in the coil or reduce the number of turns for extended coverage up to 30 mc. Keep your leads short for best performance and observe the manufacturer's precautions about handling the FET. —

## AT LAST! PROFESSIONAL HOME PROTECTION EVERYONE CAN INSTALL AND AFFORD.

Model FC-100  
**69<sup>95</sup>**

WIRED

- Start your custom Burglar/Hold-up/Fire Alarm System with the FC-100. Add on Sensors, Alarms and Accessories to suit your own needs.
- "Do-it-Yourself" Installers Handbook included. No technical knowledge needed — No soldering.
- 100% Professional in Design, Reliability, Performance.



**'Fail Safe'-SYSTEM BY EICO**

A New Concept in "Do-it-Yourself" Home Protection

### FREE 32 PAGE EICO CATALOG

For latest catalog on EICO Test Instruments, Stereo, EICOCRAFT Projects, Environmental Lighting, Burglar/Fire Alarm Systems, and name of nearest EICO Distributor, check Reader Service Card or send 25c for First Class mail service.

EICO, 283 Malta Street, Brooklyn, N.Y. 11207



## LOW COST DIGITAL CLOCK KITS (12 OR 24 HOUR)



Easy reading 7 segment display tubes. Solid state components. Printed circuit. Accurate 60 cycle line, time reference. Simple, push button settings. Displays hours, minutes and seconds. Easy step by step instructions.

USE YOUR MASTER CHARGE OR BANKAMERICARD  
Order or write for details:

Kit price: \$74.50  
Choice of cases extra:  
Metal — \$10/Walnut — \$20  
Calif. residents add 5% tax.  
Money back guarantee.



506 Main St. • El Segundo, CA 90245/772-6176

**ANOTHER SUPERB VALUE**

from **Olson**  
Electronics



ONLY **\$19<sup>95</sup>**

**ELECTRIC EYE  
WARNING  
SWITCH**

Multi-purpose warning system for business, home, warehouse or industry. Electric Eye is used to signal or count someone entering or breaking the beam. You need only plug in a bell, buzzer, counter or any other device.

Olson Electronics, Dept. D9, 260 S. Fargo St.,  
Akron, Ohio 44308

- I enclose \$19.95 plus \$1 for postage and handling. Send me the SW-364 Electric Eye Warning Switch.
- Send me the next seven issues of the Olson Catalog, without cost or obligation. **FREE**

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_  
State \_\_\_\_\_ Zip \_\_\_\_\_

new dimensions



in electronics

the versatile PHASE solid state

### AUDIO SWEEP GENERATOR

ELECTRONICALLY SWEEPS  
THE ENTIRE AUDIO  
RANGE CONTINUOUSLY!

OR USE IT AS A  
FUNCTION GENERATOR



Here are some of the professional features:

variable sweep control; no external input required; vco access; accurate linear dial; choose sine, square, triangle, positive sawtooth or negative sawtooth waveform with rapid function switch; sawtooth slope control.

The incredibly low price of **\$108.09**

includes factory assembly and testing, a two year warranty, and a ten day, money-back guarantee if not satisfied for any reason.

Also available as kit: \$84.85

PHASE CORPORATION, Dept. 920  
315A Boston Avenue  
Medford, Mass. 02155

## Wow & Flutter Meter

Continued from page 47

resistor from M1's terminals and readjust R45 for a zero reading on M1.

Connect the audio voltmeter to the junction of R3 and the source terminal of Q1. Adjust R1 for a 0.1 V reading. Place S2 in its *On* mode and S4 in the 1.0% position. Adjust R41 for a 0.8% reading on M1. Reset S4 for its 5% position and switch off S2. Adjust R30 for a half-scale (2.5%) meter reading.

Place S4 in the *Level* mode and set R7 for a half-scale reading on M1.

Place S4 in the *Modulation* position and adjust R59 for a half-scale reading.

Connect the scope's vertical input to pin 6 on IC3 (point A). If the scope is triggered, set its sweep rate to 10 milliseconds/centimeter. Readjust R17 so that there is equal modulation at the top and bottom of the 3,000-cps envelope. See Fig. 7 for the proper waveform shape. The Wow & Flutter Meter is now calibrated and ready for use.

### How to Use the Wow & Flutter Meter

Most tape decks have internal adjustments for wow & flutter correction. These adjustments usually are of a mechanical nature, affecting pinch pressure on idler wheels, capstan drive belt tension and the like.

Although each manufacturer shows (in his service manual) a complete procedure for adjusting these screws, it is almost always possible to better his specification by patiently trying various combinations of tensions and pressures on those components that directly affect wow & flutter.

The easiest way to improve wow & flutter is to give the tape transport mechanism a thorough cleaning. Bearings must be dust-free. And if you must oil your machine, sparingly apply what came with the deck.

Turntables have no provision for wow & flutter adjustments. One of the ways wow & flutter can increase is if dust and dirt enter the mechanism.

Idler wheels are especially prone to excessive wear and should be suspected if wow & flutter for a particular machine far exceeds a manufacturer's specs. Also check a turntable's spindle by substituting a known good one in its place. If wow & flutter drop significantly, replace the spindle. ●

## The Listener

Continued from page 62

two parallel outlets also are operating presently, one on 5804 kc (rated at 25 kw, sign-on around 2230) and one on 881 kc. A new 100-kw shortwave transmitter is soon to be donated by the recently formed United Arab Emirates, a federation of Persian Gulf principalities.

**Propagation Forecast.** During daylight hours, the 15-, 17- and 21-mc bands will provide good listening; the 6-, 7-, 9- and 11-mc bands will be best for DX during evening hours. Decreasing noise levels will result in an improvement in BCB DX, while decreasing sporadic-E activity will mean fewer FM- and TV-DX openings.

In September and October, daytime is nearly equal in the northern and southern hemispheres. Because of this, very long DX circuits between hemispheres open up for longer periods of time. Reception of signals from Australia, New Zealand, India, Ceylon and other South Asian countries will be best during the equinox months.

## A Home-Protection System

Continued from page 53

control box with ordinary lamp cord. Wires are fastened to appropriate screw terminals.


Although Eico sells all components of the Fail Safe system individually, it offers a complete starter package for \$109.95. Called the SS-500, this home-protection kit includes the FC-100 control center, AC power supply, alarm bell, key switch, remote stations, fire sensors for normal room use and an assortment of tamper and contact switches.

All sensors and bells operate from a 6-volt lantern battery or optional AC power supply. If batteries are the sole source of power, the Eico system can provide fail-safe operation only if the cells are fresh. For this reason we recommend Eico's optional power supply.

One of the nice features of the Eico system is a circuit-test and alarm-indicator light. A white lamp located at each remote station and on the control-center front panel indicates that all sensors are energized and the system ready. A red light also is mounted at each remote station and control-box panel. When lit, it indicates that the system will sound the alarm if a door or window is disturbed.

A monitor receiver  
without a professional  
monitor antenna is  
like a kite without  
a tail:

way  
down

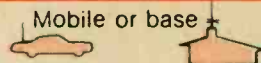

Want the high performance you paid for? Choose a professional A/S monitor antenna. Over 20 models, one for your exact need. Let us send our catalog.

**the antenna  
specialists co.**



Div. of **allen** Electric & Equipment Co.  
12435 Euclid Avenue • Cleveland, Ohio 44106

**ELECTRONICS  
and AVIATION  
Go "Hand in Hand"  
Be an "AVIONICS"  
Technician!**

*Combine Your Interest  
in Electronics With the  
Opportunities in Aviation*



**AVIATION ELECTRONICS offers you  
a whole new career opportunity:  
Exciting! Fast-growing! High Pay!**

Learn how you can train—in 12 months—to repair, maintain and calibrate sophisticated electronic navigation, control, environmental and communications systems now used in modern aircraft. Mail Coupon for Free "Career Kit" on AVIONICS.

**FREE  
"Aviation  
Career Kit"**

.....  
• SPARTAN SCHOOL OF AERONAUTICS Dept. 22879  
• International Airport, 8820 E. Pine St., Tulsa, Okla. 74151  
• Rush me full information on your AVIONICS course.  
.....  
• Name \_\_\_\_\_ Age \_\_\_\_\_  
• Address \_\_\_\_\_  
• City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_  
.....

## YOU CAN BUILD THIS HOME...



**FOR \$1,500!**

Learn how in the July issue of **MECHANIX ILLUSTRATED** along with many fascinating and interesting economy ideas...

- A ride in a hot-air balloon!
- A preview of '73 cars!
- A home-made patio serving cart!
- A profile on truck drivers!
- A 3-in-1 patio table

### EXTRA!

Tom McCahill falls for the loveliest Swede of all... the Saab Sonett III.

Pick up a copy of the July issue of **MECHANIX ILLUSTRATED** wherever magazines are sold. It's the how-to-do magazine for the budget minded home.



## CB Corner

Continued from page 71

is accepted by police officials as a valuable resource. The precinct's commanding officer knows the value of CB as a reporting medium and the set-up has been working well for more than a year.

I asked Bill if he could see the day when ordinary people walking the streets in high crime areas might carry handie-talkies for security. He replied that Channel 9 still isn't completely clear and is occasionally jammed by other signals. He wouldn't bet his life on it. His immediate goal is to help similar groups make contact with police officials in other areas. Three other boroughs of the city soon will have comparable monitoring services, with instant radio communications linking them all. This successful experiment in public service has other implications. As Bill Wahlin remarked, "This is one way to civilize CB!"

## A Lo-Lo-Ohm Ohmmeter

Continued from page 65

The circuit is built on a piece of 3x4½-in. perfboard. See Fig. 3. Twelve push-in lugs located around the perimeter of the perfboard, as shown in Fig. 3, terminate all wires which are to be connected to front-panel mounted components and probes P1 and P2.

After completing initial perfboard wiring, drill out two holes in the bottom of the aluminum cabinet and mount the wired perfboard to the chassis, using 1-in. spacers.

Next, replace the original meter dial with the one shown on the first page of this article. Remove the four screws securing the front cover of the meter and remove its cover. Remove both screws holding the dial and carefully lift it out. Cut out the new dial, paste it over the old one and reassemble M1.

After inserting two rubber grommets into holes drilled in the front panel for the probe leads cut and dress a couple of 1½-ft. leads.

**Calibrating the Ohmmeter.** Turn S1 to its *Cal* position. Short P1 and P2 and null M1 to read zero with pot R14. Then separate the probes and turn the calibrate pot until M1 reads exactly 1. If you can't null the meter when you try it the first time, substitute a higher or lower resistance value for R16. If R18 doesn't bring the meter needle up to 1, it is time to change batteries.

# Classified Ads

## ELECTRONICS ILLUSTRATED

Your advertisement can reach this mail-buying audience for only 50¢ per word . . . payable in advance (Check or M.O. please) . . . minimum 10 words. Closing dates are the 20th of 4th preceding month i.e. copy for the January issue must be in our office by September 20th. Mail to ELECTRONICS ILLUSTRATED, 1515 Broadway, New York, N. Y. 10036. Word count: Zipcode number free. Figure one word: Name of state (New Jersey), name of city (New York); sets of characters as in key (14-O); also abbreviations as 35MM, 8x10, A.C.

### SAVE MONEY • ORDER BY MAIL

#### • • • FOR SALE

**ANTIGRAVITY, EXPERIMENT and theory;** Rushed—\$2.00. Intertech 4A3, Box 5373, Station F, Ottawa, Canada.

**SOUND-TO-Light Converter—Complete plans, schematics, and operating theories.—Converter, \$1.50—Seven Segment Digital Clock, \$3.00—Understand Digital Circuits, Logic Theory. . . Complete Course in Digital Electronics, all you need to know for Logic Designs, \$10.00 Dynasign—A World of Dynamic Designs—P.O. Box 60-B, Wayland, Mass. 01778.**

**110 VOLTS, 3,000 WATTS** from your car, truck, or boat alternator. Unit operates most power tools & some household appliances. Simple to install. You can weld with it and charge batteries! Only \$17.50. 1922 PennMar, So. El Monte, Calif. 91733. Dealer inquiries welcome. Free brochure—send stamp.

**DISCARD TUBES,** solid state plug-ins, send stamped envelope for list. Precision Specialties, Box 912, Waco, Texas 76703.

**ELECTRONICS REFERENCE Chart.** Formulas for power, frequency, reactance, resonance, voltage divider etc. fully derived. Plus transistor base diagrams, frequency/time conversion scale, much much more. \$3.00. J. Denslow, 11771 National Blvd., L.A. Calif., 90064.

**TREASURE HUNTERS!** Prospectors! Rockhounds! Hobbyists! Find gold, silver, relics with world famous Detetron Metal Detectors. Free information. Delivery immediate. Detetron, Dept. 9-EI, Box 243, San Gabriel, California 91778.

**DO YOU drive a car?** Then you are breathing dirty air. (Automobile air conditioners do not clean particles out of air). Safe, reliable, effective Car Air Purifiers remove 90%+ of smog particles from air. Free Catalog. CSDC, 15446 Sherman Way, 222E1, Van Nuys, Calif. 91406.

**MAGNETS.** ALL types. Specials: 20 disc magnets, or 2 stick magnets, or 10 small bar magnets, or 8 assorted magnets, \$1.00. Maryland Magnet Company, Box 192-F, Randallstown, Maryland 21133.

**TREASURE FINDER** locates buried gold, silver, coins, treasures, 5 powerful models. \$19.95 up. Free Catalog. Relco A-192, Box 10839, Houston, Texas 77018.

**MAGNETIC-PICKUP CD** ignition plans. Write SES Enterprises, Box 607, Ferndale, Wash. 98248.

**FREE! GIANT** Electronics Catalog. McCord Electronics, Box 41-E, Sylvania, Ohio 43560.

**INVESTIGATORS, LATEST** Electronic Aids. Free Literature. Clifton, 11500-X NW 7th Ave., Miami, Florida 33168.

**IDEAL 5-ACRE** Ranch, Lake Conchas, New Mexico. \$2,975. No Down, No Interest, \$25.00 Monthly. Vacation Paradise. Money Maker. Ranchos, Box 1095E1, Alameda, California 94501.

**SKILL-RATED** construction plans. Free catalog. Systems-Mart, Dept. 315, Box 25280, Portland, Oregon 97225.

**FREE CATALOG.** The most unusual electronic kits available. Bird, Surf and Wind synthesizers, electronic wind chimes, many more. PAIA Electronics, Box H14359, Oklahoma City, Okla. 73114.

**MAKE BIG** Money Radio, Television Broadcasting Information \$2.00. Box 374, Canoga Park, California 91305.

**CONVERT ANY** television to sensitive, big-screen oscilloscope. Only minor changes required. No electronic experience necessary. Illustrated plans, \$2.00. Relco, A-19, Box 10563, Houston, Texas 77018.

**NEW AMAZING** telephone recorder. Automatically records every word each time your telephone is used. Only \$24.95. Amplicom, 4334 Tujunga Avenue, North Hollywood, Calif. 91604.

**POWER SUPPLIES:** input 117vac. Transformer isolated, 2.5watts output. Model 104A ± 25vdc. at 50 ma. Model 104B 25vdc at 100 ma. Ripple < 5%, \$15.00 plus postage. Manchester Electronics, 20 Meadow St., Manchester, N.H. 03103.

**ANY QUANTITY,** \$1.00 each IN830, IN830A, IN831, IN831A. Mitef, Box 82, Melrose Highlands, Mass. 02177.

**PRINTED CIRCUIT** Drill Bits. Trumbull, 833 Balra Drive, El Cerrito, Calif. 94530.

**TOOL KIT,** (9 pc.) For Bench or Mobile. Sat. guar. \$2.98 Ppd. Renco (EI), P.O. Box 4411, Hayward, Calif. 94544.

**CANADIANS:** FREE bargain packed electronics catalog. ETCO, 464 McGill, Montreal, Canada.

**AUTHENTIC JAPANESE** mailorder companies list. Save money; cameras, recorders, etc. 20 addresses \$3.00. Louts, Box 10, Elcajon, Calif. 92022.

#### • • • PRINTING

**STILL PUTTING** this off? \$1.00 buys 1,000 gummed address labels. Why not order right now? Decco, Box 745, Blanco, Texas 78606.

#### • • • GOVERNMENT SURPLUS

**GOVERNMENT SURPLUS,** How and Where to buy in Your Area. Send \$1.00, Surplus Information, Headquarters Bldg., Box 30177-E1, Washington, D. C. 20014.

**MANUALS** For surplus electronic equipment. List 25¢. Books, 4905 Roanne Drive, Washington, D.C. 20021.

**JEEPS TYPICALLY** From \$53.90 . . . Trucks From \$78.40 . . . Boats, Typewriters, Airplanes, Multimeters, Oscilloscopes, Transceivers, Electronics Equipment. Wide Variety, Condition. 100,000 Bid Bargains Direct From Government Nationwide. Complete Sales Directory and Surplus Categories Catalog \$1.00 (Deductible First \$10.00 Order From Our Separate Included Catalog.) Surplus Service, Box 820-T, Holland, Michigan 49423.

#### • • • BUSINESS OPPORTUNITIES

**JAPAN HONG** Kong Directory. World products information. \$1.00 today. Sekal Shogyo Annai, Hillyard, Washington 99207.

**HOW MUCH** does being your own boss or making \$25,000.00 per year interest you? The Warner breakthrough in the Engraving field could be your future. Write: Warner, Room EC-120-BJ, 1512 Jarvis, Chicago, Ill. 60626.

**MAILORDER—CARRY** no stock. Companies will pack, ship under your label. One-man operation capable of \$10,000-\$20,000 year. Details Free! Distributors, Box 9-J, East Rockaway, New York 11518.

**1,000 IMPORTED TOYS,** gifts and novelties at below wholesale prices. Catalog \$1.00 plus 50¢ postage, refunded on first order. JAD Enterprises, P.O. Box 13251, Sacramento, Calif. 95813.

**311 FAST, EASY** ways to make money! Free! Rush name, address, zip. Perry, 13263V Ventura Blvd., Studio City, Calif. 91604.

**VENDING MACHINES.** No selling. Routes earn amazing profits. Big catalogue free. Parkway Corporation, 715E1 Ensor Street, Baltimore, Maryland 21202.

**MAKE \$1.00 PER** Sale selling engraved metal Social Security plates. Free Sales Kit. Engravaplates, Box 10460-81, Jacksonville, Florida 32207.

**\$200.00 DAILY** In Your Mailbox! Your Opportunity To Make Money Like Mailorder Experts. Free Details. Associates, Box 136-E1, Holland, Michigan 49423.

**START SMALL,** highly profitable electronic production in your basement. Investment, knowledge unnecessary. Postcard brings facts. Barta-Elmon, Box 248, Walnut Creek, California 94597.

**AT LAST** Complete 24 Lesson Mail Order Course. Everything you need to know to begin making money immediately. Send \$2. Satisfaction Guaranteed. Family Enterprises, 1000 Cypress Ave., Ridgewood, N.Y. 11227.

#### • • • EMPLOYMENT INFORMATION

**EXCITING OVERSEAS** jobs. Directory \$1.00. Research Associates, Box 889-FW, Belmont, California 94002.

**PRINTING—ADVERTISING** Salesmen. Excellent moneymaking sideline selling Decalomania Name Plates. Advertising Specialties. Sign Letters, Automobile initials. Free Samples. **Ralco** El, Box L, Boston, Mass. 02119.

**EUROPEAN-FOREIGN** (Employment). Listing of currently available technical positions. Europe, Australia, Africa. \$3.00. Eurojob Report, Box 52634-Y, Lafayette, Louisiana, 70501.

### • • • EDUCATION AND INSTRUCTION

**HIGHLY EFFECTIVE** home study courses in Electronics Engineering Technology and Electronics Engineering Mathematics. Earn your Degree. Write for Free Descriptive Literature. Cook's Institute of Electronics Engineering (Dept. 14), P.O. Box 10634, Jackson, Miss. 39209. (Established 1945.)

**LEARN CARTOONING** At Home. Free booklet: "Key to Cartoon Career." Approved for G. I. Bill. Write: Cartooning, Box 7049X, Colorado Springs, Colorado 80907.

**BOOKKEEPING SELF-TAUGHT** quickly. Complete cost only \$3.95. Sample lessons \$1.00. Satisfaction assured. Details Free. **Badlers Digests**, 2063 E. 18, Brooklyn, N.Y. 11229.

**SERCOLAB. PHYSICS** and E.E. experiments, models. P.O. Box 78A, Arlington, Mass. 02174.

**FREE INFORMATION.** Get FCC license new, easy way. Academy of Communications Technology, El-3, Box 389, Roswell, New Mexico 88201.

**HIGHLY EFFECTIVE, Profitable Short Courses** (65 Choices). Free Literature. CIEE-C, Box 10634, Jackson, Miss. 39209.

### • • • BUILD-IT-YOURSELF (OR DO-IT-YOURSELF)

**AUDIO BUFFS** who build their own are wildly enthusiastic about **The Audio Amateur**, new quarterly exclusively dedicated to audio as craft. \$5.00 a year, prospectus free. **Audio Amateur**, 307A Dickinson, Swarthmore, Penna. 19081.

**LINEAR AMPLIFIERS:** Build your own 250 Watt 10-15 Meters Linear. Plans \$1.00. **Roberts**, Box 8791, Ft. Lauderdale, Florida 33310.

**FISHWORMS** AT your fingertips. Easy illustrated instructions, \$1.00. Its'a, P.O. Box 135, Martinsville, Indiana 46151.

**HOME SECURITY** and safety book, featuring installation and procedure description of burglar alarms. Send \$1.00 to **Bradley Electronics Inc.**, Dept. 108, 15 Gaval Road, Sayreville, New Jersey 08872.

**THE BOOK** about PC Boards. A simplified & comprehensive explanation of the processing procedures and equipment used to make prototype printed circuits. \$9.50. Order from **DAS**, 4329 Agnes St., Studio City, Cal. 91604.

**UNIQUE THREE-Channel Color Organ.** Features: Independent channel control, unaffected by changes in output volume control, 300 watts per channel, high input impedance. Complete plans and instructions available for \$1.00 from **H&R Electronics**, Box 134, Dept. 2A, Annapolis Jct., Md. 20701.

**NEW LOCATOR** indicates difference in metals detected. Plans \$4.00. **Taylor Electronics**, P.O. Box 253, Cape May, New Jersey 08204.

**PROVED SCHEMATICS:** Audio mixer, \$3.00. Microphone line amplifier, \$1.00. Sound-actuated burglar alarm/tape-slide synchronizer, \$2.00. **Millers**, 1896 Maywood, Cleveland, Ohio 44121.

**ELECTRONIC FEVER** Thermometer. Functionally similar to unit described in Jan. 1972 issue. Complete kit, \$14.95, or assembled and calibrated, \$19.95. **ESP Inc.**, 472 Westover Road, Stamford, Conn. 06902.

**PROJECT MODULES** Free Flyer. UTI, POB 252, Waldwick, N.J. 07463.

### • • • HI-FI, STEREO

**STEREO COMPONENTS** at lowest prices. Send for free catalog. **Carston**, Box 1094B, Danbury, Conn. 06810.

**DISCOUNTS—STEREO** components & Systems. Lowest possible prices on quality brands. For fastest service, Lowest cost—get our quote! **Redwood Stereo Co.**, P.O. Box 2794, San Rafael, Calif. 94902. (415) 472-2255.

### • • • TAPE RECORDERS

**WRITE FOR** our free 32 page catalog. It lists resistors (14 different types, in kits and singly), 1,542 tube types, 3,024 different transistor types, many transistor kits, rectifiers in kits and singly, condensers of various types, tools, wire, antennas, phonograph cartridges and needles, speakers, CRT boosters, controls, switches, i.v. tuners, yokes, flybacks, etc. **Hytron Hudson**, Dept. E, 2201 Bergenline Ave., Union City, N.J. 07087.

**RENT 4-TRACK** open reel tapes—all major labels—3,000 different—free brochure. **Stereo-Parti**, 55 St. James Drive, Santa Rosa, Calif. 95401.

**LEARN WHILE Asleep** with your recorder, phonograph or amazing new "Electronic Educator" endless tape recorder. Details free. **Sleep-Learning Research Association**, Box 24-El, Olympia, Washington 98501.

**RADIO RERUNS** catalogs \$1.00 (refundable). Box 724, Dept. El, Redmond, Wash. 98052.

### • • • RADIO & TV

**FREE! BARGAIN** Catalog. Fiber optics, LED's, resistors, diodes, rectifiers, SCR's triacs, parts. **Poly Paks**, Box 942, Lynnfield, Mass. 01940.

**TV TUNERS** rebuilt and aligned per manufacturers specification. Only \$9.50. Any make UHF or VHF. We ship COD. Ninety day written guarantee. Ship complete with tubes or write for free mailing kit and dealer brochure. **JW Electronics**, Box 51K, Bloomington, Indiana 47401.

**TELEVISION HIGH Voltage** Test Probe Only \$2. No meter or electronic experience needed. **Schek Television Company**, 8101 Schrider Street, Silver Spring, Maryland 20910.

**REPAIR TV Tuners—High Earnings.** Details of Complete Course, 12 Repair Tricks, Many Plans, Two Lessons, all for \$1. Refundable. **Frank Bocek**, 3236 Enterprise Branch, Redding, Calif. 96001.

**RADIO & TV Tubes—36¢.** Free List. **Cornell**, 4213-15 University, San Diego, Calif. 92105.

**BUILD DISTANCE** Crystal Sets. 10 plans—25¢; 18 different—50¢; 20 different—50¢. Catalog 25¢, refundable. **Laboratories**, 1477-K, Garden Grove, Calif. 92642.

### • • • ELECTRONICS SUPPLIES & EQUIPMENT

**KITS AND EQUIPMENT** FM Wireless microphone transmitters, FM Telephone transmitters, Infinity transmitters. **Security Electronics**, P.O. Box 265, Huntington, W. Va. 25707.

**WHOLESALE C.B.** transceivers, multi-band receivers. Lowest prices. Dealers welcome. List 25¢. **G-Enterprises**, Box 14E, O'Fallon, Ill. 62269.

**SUPREME TWENTY** different radio-television volumes, \$50 value, only \$19.95, postpaid. **Supreme Publications**, 1760 Balsam, Highland Park, Illinois 60035.

**MEMORIES SEMICONDUCTORS** Free Flyer, UTI, P.O. Box 252, Waldwick, N.J. 07463.

**INTEGRATED CIRCUITS.** Highest Quality Lowest Cost. 7400N Gates from 26¢. Free Catalog. **Digkey**, Box 126X, Thief River Falls, Minn. 56701.

**CB—SBE'S** brand new 23 channel mobile transceiver by **Linear Systems**. All Crystals Supplied. Fully warranted. \$99.95 check or MO. **CB Radio Equipment**, P.O. Box 611, Fairfield, Connecticut 06430.

**ELECTRONIC HOBBYIST** and professional builders love our 3¢ film resistors; 16¢ electrolytics and 1% micas. Great catalog 35¢. **Electrovalue-America**, Box 27D, Swarthmore, Pa. 19081.

**FREE ILLUSTRATED** catalog! covering wide range of low-cost stock business forms from 2-Way Radio to TV Service. Write today. Free catalog; samples, too. **Oelrich Publications**, 4040 N. Nashville East, Chicago, Illinois 60634.

**I'M SELLING** out my electronic business. All or part. Includes parts and equipment too numerous to list, 50% to 70% below wholesale. For itemized inventory and price list send \$1.00, deductible from order. **Aktronics**, 2333 E. Bugle Drive, Chesapeake, Virginia 23321.

**POWER SUPPLIES** dc output from \$9.90, 120 models. **Automatic**, Box 292, Butler, N.J. 07405.

**EICO—460 TRIGGERED** Sweep conversion kit \$29.95; **Digiswitch—Displays** Four Digital Signals on Scope \$9.95. **HW Electronics**, Bloomfield, Ontario Canada.

### • • • INVENTIONS & INVENTORS

**MANUFACTURERS** NEED New Products. Your ideas and inventions developed for commercial appeal and cash/royalty sales. Free "Invention Record" and "Product Marketing" brochure. **Raymond Lee Organization**, 230-X Park Avenue, New York City 10017.

**INVENTORS! SELL** your invention for cash or royalties! Our client manufacturers eagerly seek new items. Patented. Unpatented. Financial assistance if needed. 25 years proven performance. For free information, write Dept. 27, **Gilbert Adams**, Invention Broker, 80 Wall St., New York, N.Y. 10005.



**PATENT SEARCHES** including maximum speed, full airmail report and closest patent copies \$6.00. Quality searches expertly administered with complete secrecy guaranteed. Free Invention Protection forms and "Patent Information." Write Washington Patent Search Bureau, Dept. 20, Benjamin Franklin Substation, P.O. Box 7167, Washington, D.C. 20044.

• • • **PHOTOGRAPHY**

**PHOTOGRAPH HOBBYISTS** and professionals: Substantially improve the colour, detail, and depth of focus of your close up and far off photographs through a very simple and inexpensive process of photon multiplication. The process is applied during the actual faking of the photograph, not during the development. For plans send \$1.00 to J. Mulligan, 8346 N. Dwight Ave., Portland, Oregon 97203.

• • • **ROCKETS**

**ANTIGRAVITY DEVICE.** Brochure 35¢. AGD, Box 3062-E, Bartlesville, Okla. 74003.

• • • **MUSIC**

**SONGPOEMS NEEDED**, all types, Country, Western, Popular, Romantic, Folk, Rock, Religious, etc. Possible Recording/Publishing—Rush to Betty's Music Makers, 1417 Park Bldg., Dept. H, Pittsburgh, Penna. 15222.

**POEMS AND Lyrics** of religious, reverent, inspired nature wanted for immediate recording. We are only interested in songs of hope, God's love, the comfort of His words and wisdom. Cathedral Recording, P.O. Box 78-EI, North Weymouth, Mass. 02191.

**FREE CATALOG.** Electronic Musical accessory kits, Sustain, Waa-Waa, automatic drums and many others. PAIA Electronics, Box G14359, Oklahoma City, Okla 73114.

• • • **PERSONAL**

**LIFETIME SOCIAL Security plate and ID card.** Encased name and Social Security number engraved \$2.00. R. Manzi, 5-D, 2307 Morris Ave., Bronx, New York 10468.

**VACATIONING? RETIRING?** Read "Bargain Paradises of the World"; or "Off the Beaten Path," (America). Either book \$2.50. Both only \$4.75. Calif. residents add 5% tax. Spectrum Enterprises, 7650 Isabel Drive, Cotati, Calif. 94928.

• • • **MISCELLANEOUS**

**NOW! ENJOY** the great outdoors in comfort with your pocket size electronic Skeeter Skat mosquito repeller. \$9.95 postpaid, U.S.A. Satisfaction guaranteed. Detectron, Dept. C-9, P.O. Box 243, San Gabriel, California 91778.

**YOUR OWN Electronic Business.** Easy—lucrative. Details Free. Barta-ELAS, Box 248, Walnut Creek, California 94597.

**USED MYLAR Tapes.** 1800'. 50 reels for \$35.00 postpaid. Send check with order to Fremmerman, 4041 Central, Kansas City, Mo. 64111.

**IF YOU** like the convenience of buying by mail, thumb through my catalog of Specialties and Gadgets for everyday use. Sent free on request. Wagner, Dept. EI, 264 Eckford Street, Brooklyn, N.Y. 11222.

People  
start  
pollution.

People  
can  
stop it.

Kids, cops, comptrollers.

Butchers, bakers, businessmen.

Mommies, models, mayors.


Violinists, vice presidents, workmen

Keep America Beautiful

advertising contributed for the public good



# Changes come fast in electronics.

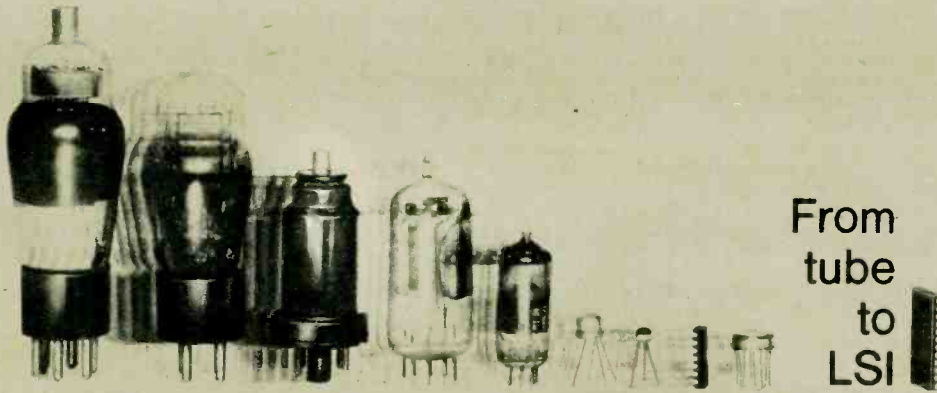


From  
tube  
to  
LSI

Take a look at the race in circuit technology. In the 1960's the tubes at the left made way for the transistors at the right. Today, transistors are surpassed by the large scale integrated circuit (LSI) at the far right. This circuit, less than a quarter inch square, replaces over 6000 transistors!

There's big money to be made by the men who stay ahead of this technology race. Put yourself

ahead with NTS Home Training! You get the latest, most advanced equipment (at no extra cost). More solid-state units, and more advanced technology. Plenty of training with integrated circuits, too! As an NTS graduate, you enter a world of electronics you're familiar with. You have a thorough working knowledge of solid-state circuitry. You're ready to tackle bigger jobs at higher pay!

## NTS COLOR AND B & W TV SERVICING

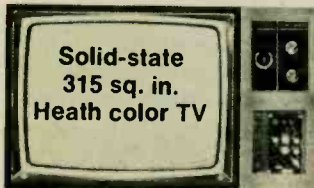

Solid-state  
315 sq. in.  
Heath color TV

Build and keep the largest, most advanced color TV made! Over-all solid-state design, ultra-rectangular screen, matrix picture tube, built-in self-servicing features, "Instant On," A.F.T., solid-state, 24-channel detent UHF/VHF power tuning, and much more! Also build and keep AM-SW Radio, Solid-State Radio, FET Volt-Ohmmeter, and Electronic Tube Tester. Learn trouble-shooting, hi-fi, stereo, multiplex systems, radio, color and B & W TV servicing.

Learn sophisticated solid-state circuitry as you build this B & W TV receiver. Lo-Silho "Superhet" Radio, FET Volt-Ohmmeter, Solid-State Radio, Electronic Tube Checker, and Signal Generator. TV

and all other equipment are yours to keep.

Solid-state  
B & W TV,  
74 sq. in.  
picture  
(cabinet  
included)



## NTS ELECTRONICS & COMPUTER TECHNOLOGY

Build and keep this exclusive NTS Compu-Trainer. It teaches you the

Solid-state  
Compu-Trainer  
14 integrated  
circuits replace  
198 transistors!



same principles used in million-dollar systems. Contains 14 inte-

grated circuits! All Solid-State! You perform all wiring and patchcording. No shortcuts. No pre-wired circuit boards. Your training is complete! Also receive an FET Volt-Ohmmeter and a 5" wide-bar Solid-State Oscilloscope.

## NTS ELECTRONICS COMMUNICATIONS

Gain the prestige and earning power of owning an F.C.C. First Class Radio-Telephone License. Two comprehensive NTS courses cover the big opportunity field of transmitting and receiving.

You build and keep 14 kits, including this amateur phone 6-meter VHF Transceiver, NTS's exclusive 6-transistor Solid-State Radio, and a fully transistorized Volt-Ohmmeter. Also, learn 2-way radio, Citizens Band microwaves, and radar.

5-watt AM  
transmitter/  
receiver




# NTS Home Training puts you in the lead.


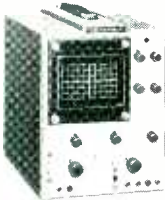
## NTS INDUSTRIAL & AUTOMATION ELECTRONICS

Automation is the future of industry and you can play an important part! Learn industrial controls by training on the NTS Electro-Lab (a complete workshop). You also build and operate this 5" Solid-State oscilloscope. And you perform experiments that involve regulating motor speeds, temperature, pressure, liquid level, and much more. All equipment is yours to keep.



## NTS AUDIO ELECTRONICS SERVICING

Learn basic sound theory—how it works in home radio, car tape

decks, stereo multiplex component systems, and more! Set up a spectacular music system. Learn about



Build and keep this famous Heath Stereo Receiver and Speakers.

sound distortion, amplification and control, loud-speaker baffles, problems of system installation, etc. Included is Volt-Ohmmeter, In-Circuit Transistor Tester, and Solid-State

Radio. Prepare yourself for great opportunities in the Home Entertainment Industry!

## CLASSROOM TRAINING AT LOS ANGELES

You can take classroom training at Los Angeles in sunny Southern California. NTS occupies a city block with over a million dollars in technical facilities. Check box in coupon below.

## NATIONAL TECHNICAL SCHOOLS

WORLD-WIDE TRAINING SINCE 1905

4000 S. Figueroa Street  
Los Angeles, California 90037

## APPROVED FOR VETERANS

Accredited Member: National Association of Trade and Technical Schools; National Home Study Council.

Big, Colorful NTS Guide to new opportunities in Electronics. Yours FREE!



NATIONAL TECHNICAL SCHOOLS  
4000 S. Figueroa Street  
Los Angeles, California 90037

Please rush me FREE Color NTS Electronics Guide & FREE lesson, plus information on course checked at right. No obligation. No salesman will call.

- MASTER COURSE IN COLOR TV SERVICING
- COLOR TV SERVICING (FOR ADVANCED TECHNICIANS)
- MASTER COURSE IN B&W TV & RADIO SERVICING
- MASTER COURSE IN ELECTRONIC COMMUNICATIONS
- PRACTICAL RADIO SERVICING
- FCC LICENSE COURSE
- MASTER COURSE IN ELECTRONICS TECHNOLOGY
- AUTOMATION & INDUSTRIAL ELECTRONICS
- COMPUTER ELECTRONICS
- BASIC ELECTRONICS
- AUDIO ELECTRONICS SERVICING

Dept. 213-082

NAME \_\_\_\_\_ AGE \_\_\_\_\_



ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_

STATE \_\_\_\_\_ ZIP \_\_\_\_\_

- Check if interested in Veterans Training under new G.I. Bill.
- Check if interested ONLY in Classroom Training at Los Angeles

# Build

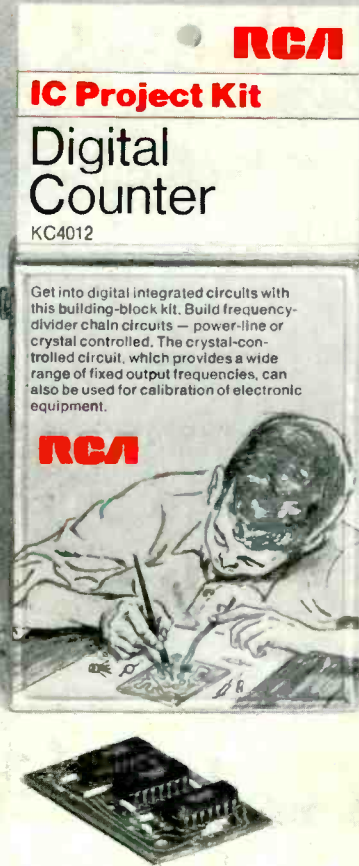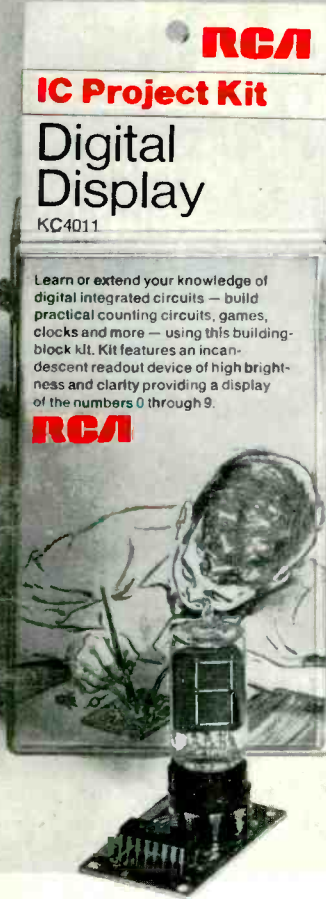

Go digital with RCA KC4011 and KC4012 display and counter kits... newest in a series of RCA project kits designed to provide an introduction to practical applications of Integrated Circuits.

With KC4011 and KC4012, individually or in combination, you can build many functional projects such as binary counter, photoelectric counter, dice game, 12- or 24-hour clock, power-line divider chain, and frequency divider chain. Easy-to-follow instructions, too, of course.

For experimenters and profession-

als interested in learning more about IC's, these kits offer an innovative approach to solid-state know-how. At the same time, you can build projects for use on the workbench, in the shop, or around the home.

Your RCA Distributor has KC4011 and KC4012 along with dozens of other RCA Project Kits, Variety Packs, Add-on Kits, Hardware, and Accessories, plus the RCA Solid-State Hobby Circuits Manual, HM-91. See him about the solid-state circuit you have in mind. Ask him, too, for your copy of 1L1350A, a brochure detail-

ing all RCA IC Kits, Experimenter's Kits, and support information. Or, write RCA, Commercial Engineering, Section 721, Harrison, N.J. 07029. Do it today.

**RCA**  
Electronic  
Components