

TV & RADIO ENGINEERING

Feb.-Mar. 1953

MILTON B. SLEEPER, Publisher

Price 65 Cents

Established as
RADIO
Engineering
1921



Texas Instruments'

POINT CONTACT


TRANSISTORS

now available!

TEXAS INSTRUMENTS makes available to industry Type 100 and 101 point contact transistors. Type 100 is designed for use in switching circuits. Type 101 is a high-efficiency, low-drain transistor for low frequency (below 1 mc) application. It is designed to operate at low voltage and power levels with a good, large signal performance. Both have the usual high temperature limitations of germanium semi-conductor devices. *Uniform characteristics are assured.* Write for bulletin with complete information.



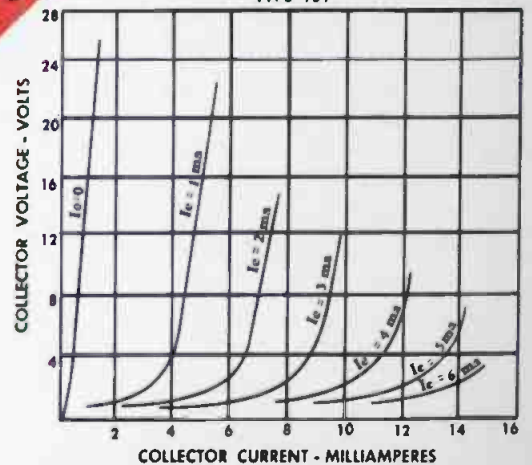TYPICAL COLLECTOR CHARACTERISTICS
TYPE 101



★
ACTUAL SIZE



★ Point contact transistors Type 100 and 101 ready for immediate delivery. ★ Junction transistors will be available in developmental quantities in May. ★ Be sure to watch for announcement concerning new semi-conductors later this year.

TEXAS INSTRUMENTS

6000 LEMMON AVENUE

INCORPORATED

DALLAS 9, TEXAS



Three Specialized Magazines

Each One Is The Leading Publication in Its Own Field:



COMMUNICATION ENGINEERING is the only magazine concerned exclusively with the development and design of components and equipment for civilian and military communications, and the planning, installation, operation, and maintenance of fixed, mobile, and microwave relay systems. Edited by Roy F. Allison, it is the principal source of information on new techniques, equipment, and system engineering for the public safety, public utility, petroleum and pipeline, special industrial, transportation, air-ground, and common carrier services. **COMMUNICATION ENGINEERING** also carries the basic system statistics, and reports on FCC actions concerning the entire field of safety and special services communication systems. It is published on the 20th of January, March, May, July, September, and November. \$3.00 per year, or \$6.00 for 3 years.

TV & RADIO ENGINEERING is the only magazine concerned exclusively with the development and design of TV, AM, and FM receivers, and broadcast studio and transmitting equipment. Edited by Roy F. Allison, this magazine, from issue to issue, is a complete what's-new record of video and audio progress from receiver components to transmitting antennas. You will find this magazine of special value as a source of ideas that can be adapted to solving your particular problems, whether they concern apparatus design or manufacturing techniques, the installation of studios and transmitters, or improved performance of present facilities. In short, if it concerns TV, AM, or FM, you find what you want to know in **TV & RADIO ENGINEERING**. It is published on the 20th of February, April, June, August, October, and December. \$3.00 per year, or \$6.00 for 3 years.

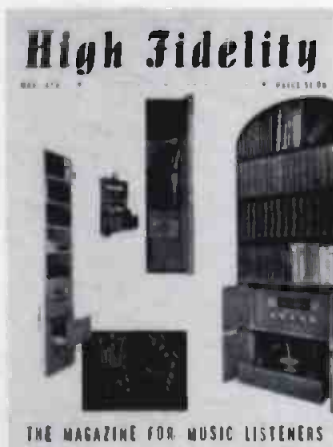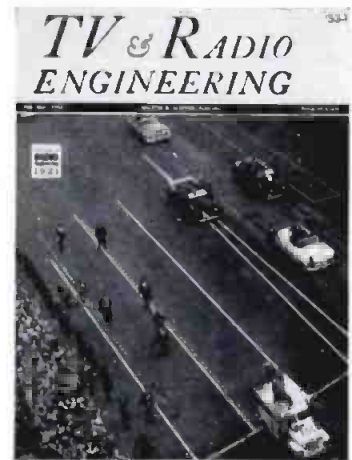

HIGH FIDELITY is the only magazine edited for people who enjoy music from FM, records, and tape. It is planned both for those whose primary interest is in music itself, and for those to whom high-fidelity reproduction is of paramount importance. With Charles Fowler as editor, and John Conly as associate editor, **HIGH FIDELITY** has really become the bible of these fast-growing groups. LP record reviews, contained in a special 32-page section, are written by nationally-known critics. These are supplemented by feature articles and news of artists and studio activities. For hi-fi enthusiasts, this magazine is the principal source of information on new equipment and its proper use, methods of improving reproduction from FM, records, and tape, and ideas for simple as well as elaborate custom installations. All articles are written in non-technical language, handsomely illustrated, and printed on fine paper. **HIGH FIDELITY** is also of great value to music teachers, educators, architects, and decorators. Published on the 1st of January, March, May, July, September, and November. \$5.00 per year, or \$10.00 for 3 years.

RADIOCOM, INC., The Publishing House, Great Barrington, Mass.
Please find enclosed my remittance for:

COMMUNICATION ENGINEERING	REDUCED RATE FOR BOTH MAGAZINES
<input type="checkbox"/> 3 years \$6.00 <input type="checkbox"/> 1 year \$3.00	<input type="checkbox"/> 3 years \$10.00 <input type="checkbox"/> 1 year \$5.00
TV & RADIO ENGINEERING	Name
<input type="checkbox"/> 3 years \$6.00 <input type="checkbox"/> 1 year \$3.00	Address

AUDIOCOM, INC.
The Publishing House, Great Barrington, Mass.
Please find enclosed my remittance for:

HIGH FIDELITY MAGAZINE

<input type="checkbox"/> 3 years \$10.00	<input type="checkbox"/> 1 year \$5.00
Add \$1.00 per year for foreign postage.	
Name	
Address	

Completely



New accessibility puts every component at your fingertips. One latch opens both hinged sides and top. Dual bar handles provide better grip and easier carrying.

New!

RCA TV CAMERA

TYPE TK-11A

Here is the all-new TV camera the industry is talking about. The camera the leading networks are planning to use in their new Hollywood studios! The camera which will be used in most of the new stations this year—and next!

Leading network engineers (after

NEW 7-inch viewfinder picture tube produces larger, brighter, and sharper pictures to help the cameraman.

NEW plug-in, high-stability video amplifier—with frequency response uniform to 8.5 Mc.

NEW fixed-position alignment coil for the Image Orthicon. Electrical control of coil eliminates all mechanical adjustments!

careful tests) have proclaimed the TK-11A the finest camera ever produced, easiest in the world to handle, and the simplest one to get at.

The TK-11A has all the proven performance of the world-renowned RCA TK-10—plus these new features:

NEW plug-in blower for cooling the deflection coil and the Image Orthicon!

NEW electronic-protection system guards your Image Orthicon against deflection failure, or loss of driving signals.

NEW "overscan" control takes burden off Image Orthicon during warm-ups and rehearsals; new vertical reverse switch for film pick-ups.

For complete information on the TK-11A,
call your RCA Broadcast Sales Representative.



RADIO CORPORATION of AMERICA
ENGINEERING PRODUCTS DEPARTMENT
CAMDEN, N.J.

3 EIMAC KLYSTRONS

FOR UHF-TV

Eimac announces the availability of the 3K20,000L type of five kilowatt klystrons, the most practical and dependable tubes ever developed for high power UHF-TV. With only three klystrons covering the entire UHF-TV spectrum (470-890 mc), manufacturing and supply is no problem, and equipment design is simplified.


Along with these attributes go exclusive Eimac features such as ceramic cavities, external tuning, and true metal to ceramic seals that give the 3K20,000L series a quality of construction that fulfills the rigorous demands of television transmitting. As a performer, each of these new klystrons has a power gain of 20 db., and will deliver five to six kilowatts peak sync output when driven by an Eimac 4X150G.

3K20,000LA — Channels 14 thru 32

3K20,000LF — Channels 33 thru 55

3K20,000LK — Channels 56 thru 83

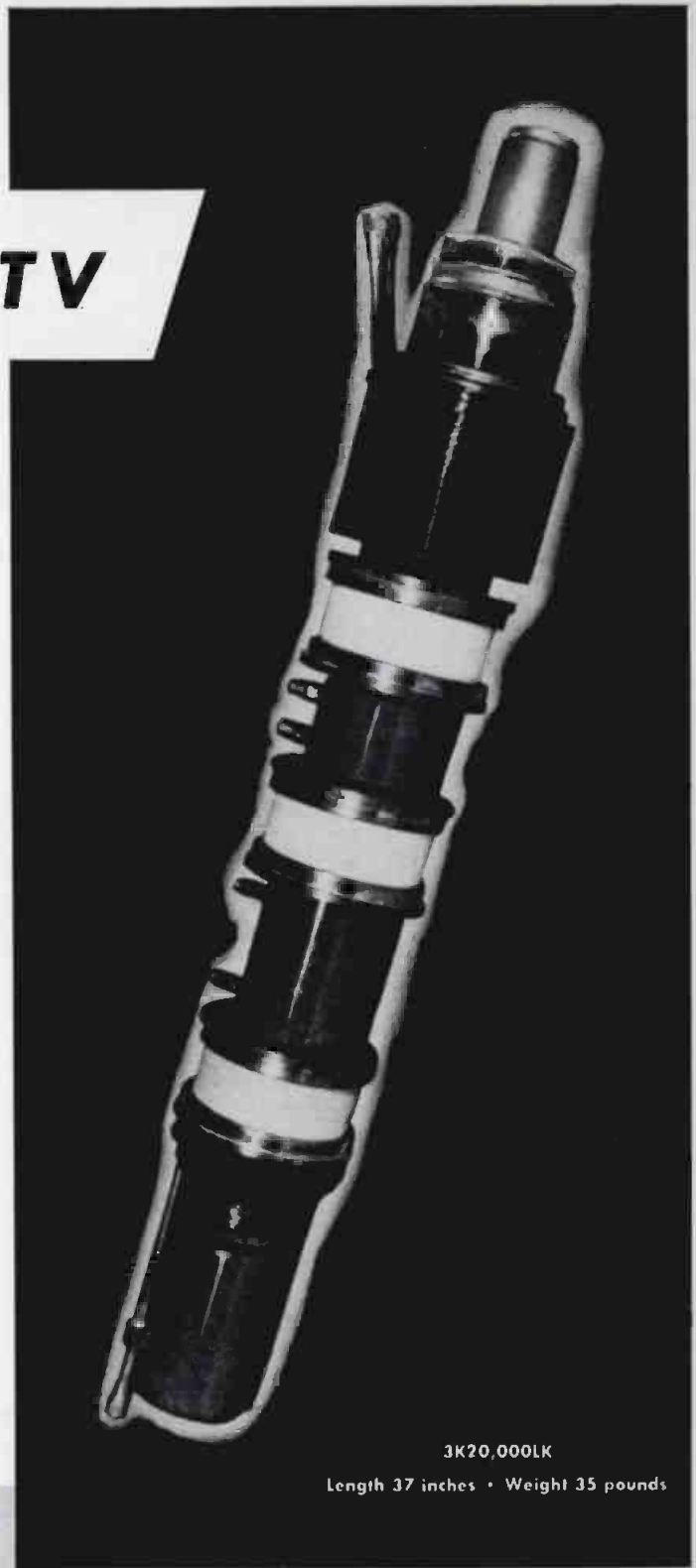- For more information about the five kilowatt klystrons write to our application engineering department
- Visit the Eimac display at the March I. R. E. show



3K20,000LK

Length 37 inches • Weight 35 pounds



EITEL-McCULLOUGH, INC.
SAN BRUNO, CALIFORNIA

Export Agents: Frazer & Hansen, 301 Clay St., San Francisco, California

The five kilowatt klystrons are another Eimac contribution to electronic progress

TV & RADIO ENGINEERING

VOL. 23

FEBRUARY - MARCH, 1953

NO. 1

COPYRIGHT 1953, by RADIOCOM, INC.

DEPARTMENTS

TV-AM-FM Set Production	
Compiled from figures released by RTMA	6
Product Information	
News of new products and literature	7
Companies and People	
Expansions, activities, appointments, awards	10
Meetings and Events	
Schedule of important shows and conferences	11
TV & Radio Review	
General news of the industry	12

ARTICLES

Noise and NTSC Color Standards	
C. H. Jones	14
Report on Spurious Radiations	
How industry is meeting the problem	21
Staging a Closed-Circuit Plant Tour	
L. W. Bidwell	22
Pattern for TV Profit	
Part 6 — Studio-transmitter and remote-pickup links	24
Head-End Design for FM Tuners	
H. H. Cross	27
Phonograph-Stylus Drag Distortion	
Little-known effects of tangential compliance	33
Increased VTVM Sensitivity	
Joseph Gluffrida	34

THE COVER DESIGN AND CONTENTS OF TV & RADIO ENGINEERING MAGAZINE ARE FULLY PROTECTED BY U. S. COPYRIGHTS, AND MUST NOT BE REPRODUCED IN ANY MANNER OR IN ANY FORM WITHOUT WRITTEN PERMISSION

ROY F. ALLISON, *Editor*

MILTON B. SLEEPER, *Publisher*

FRED C. MICHALOVE
Eastern Manager

CHARLES KLINE
Western Manager

EDWARD BRAND
West Coast Manager

MIRIAM D. MANNING
Production Manager

LILLIAN BENDROSS
Accounting

WARREN SYER
Director of Circulation

ELEANOR GILCHRIST
Art Director

Publication Office: The Publishing House, Great Barrington, Mass. Tel. 1300.

Chicago Office: Charles Kline, 426 North Pine Avenue. Tel. Columbus 1-1779.

New York Office: Fred C. Michalove, 6 East 39th Street, Room 1209. Tel. Murray Hill 5-6332.

West Coast Office: Edward Brand, 1052 West 6th Street, Los Angeles. Tel. Michigan 1732.


TV & RADIO ENGINEERING Magazine is mailed on the 20th of February, April, June, August, October, and December. Allow two weeks for West Coast delivery.

Subscriptions: Should be sent to Publishing House, Great Barrington, Mass.

Single copies 65¢—Subscription rates: \$6.00 for 3 years; \$3.00 for 1 year.

Contributions will be neither acknowledged nor returned unless accompanied by adequate postage, packing, and directions, nor will TV & RADIO ENGINEERING Magazine be responsible for their safe handling in its office or in transit.

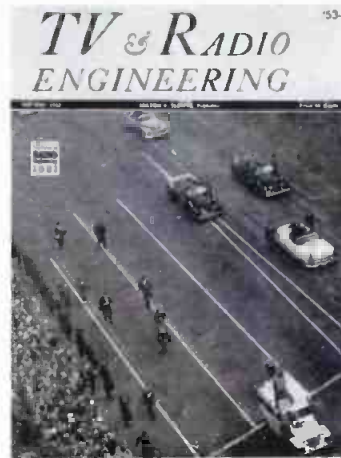Application for entry as second-class matter at Great Barrington, Mass., with additional entry at Boston, Mass., is pending. Printed in the U. S. A.



THIS MONTH'S COVER

One of the most useful pieces of equipment a television station can own is a mobile remote-pickup unit, with which on-the-spot coverage of civic, sports, and news events of local or national interest can be obtained. Such equipment is discussed in the current and concluding installment of "Pattern for TV Profit," beginning on page 24.

The remarkable cover photograph, showing an ABC mobile unit covering the recent Presidential inaugural parade, was taken by Joe Lewis of—right the first time—the American Broadcasting Company.

AUTHORS & ARTICLES

The lead article in this issue is, we think, a good one for many reasons. First, it does a thumping good job in its primary purpose—to evaluate the performance of the NTSC color system in the presence of noise. Second, it serves to give those unfamiliar with color TV techniques some idea of the nature of the general problems involved. Third, it clarifies basic color theory and the specific philosophy of the NTSC signal for those who have only general knowledge of its workings. Mr. Jones is to be congratulated on a well-written and informative work.

"Pattern for TV Profit" is concluded with this, the eleventh installment. We hope that it has been of real value to those who subscribed to RADIO COMMUNICATION primarily for this series, and we hasten to assure that other articles on station planning, operation, and maintenance will comprise an important part of the coverage of TV & RADIO ENGINEERING.

WHAT'S COMING NEXT

The article in this issue on FM head-ends, by Henry Cross, is the first of a series on FM tuner design. Next will come a superlative treatise on IF, limiter, and detector sections by Roy Paananen. Messrs. Cross and Paananen did the research work described while at Massachusetts Institute of Technology and, in fact, these articles are developed from their theses. Mr. Cross is now with Pickard and Buras, Needham, Mass.; Mr. Paananen is at Lincoln Laboratory, MIT.

This is the oldest magazine in the radio field published by its founder. It was established as RADIO ENGINEERING in 1921 by Milton B. Sleeper. Subsequently it was sold and published under the title of COMMUNICATIONS until 1950, when it became TELEVISION ENGINEERING. It was purchased by Radiocom, Inc. in 1952, combined temporarily with RADIO COMMUNICATION, and then published separately again under the present title.

TELEVISION ENGINEERING

CIRCULATION AUDITED BY
HENRY R. SYKES
CERTIFIED PUBLIC ACCOUNTANT
SYKES, GIDDINGS & JOHNSON
PITTSFIELD, MASSACHUSETTS

5



RADIO ENGINEERING LABS., Inc.

PIONEERS IN THE CORRECT USE OF ARMSTRONG FREQUENCY MODULATION

FOR FM NETWORKING OR MONITORING

The REL 722 Relay Receiver

All kinds of public service and special events programs can be handled over local FM and FM-AM networks with REL 722 Crystal-controlled FM receivers.

Model 722 is a fixed-frequency type of receiver, furnished for operation on any channel in the 88 to 108-mc. band. It is intended for picking up FM programs, and rebroadcasting them from FM or AM stations. This receiver is widely used to provide additional audience coverage for baseball, basketball, and football games, boxing matches, and other sporting events. It is also used for the reception of such programs over public address systems in public halls, theatres, and at outdoor gatherings.

Built to the highest standards of commercial performance and long-time stability, the 722 receiver has a frequency response flat to 1/2 db from 50 to 15,000 cycles, with less than 1/2 % distortion. Sensitivity is such that the sputter point is under 2 microvolts, and spurious response more than 70 db below the desired signal.

The complete receiver and power supply are mounted on a standard rack panel 19 ins. wide by 12 1/4 ins. high. For engineering data, price, and delivery schedule, write:

Engineers and Manufacturers of Broadcast, Communication, and Associated Equipment since 1922

RADIO ENGINEERING LABORATORIES, Inc.

TEL. STILLWELL 6-2100 TELETYPE: N. Y. 2816
36-40 37th Street, Long Island City 1, N. Y.

TV-AM-FM SET PRODUCTION

IN 1952, RTMA statistics reveal that TV set production increased 10% over 1951, while AM sets dropped 22%. Dollar-wise this change resulted in a substantial net increase for the industry.

During the first half of '52, however, average monthly TV production lagged behind the '51 average, but the last four months, with an all-time high in December, finally put 1952 slightly ahead of 1950, when the previous record was set, as shown by the Monthly Averages in the accompanying Production Barometer chart.

Surprisingly, AM production in December, topping 1 1/4 million, was the highest since May, 1951, although average monthly figure for '52 was down 1/4 million sets.

It appears entirely possible that TV production may run ahead of AM sets in 1953. During the last four months of '52, the TV figure was only 15% below AM. Now, with new television stations scheduled to come on the air each month, it would hardly be unexpected if TV sets take the lead.


Currently, a considerable part of TV sales is accounted for by replacements of old types with small picture tubes, up to 12 ins. Big tubes have so changed viewing habits that few people are content to watch images on small screens.

TV interference was reduced to some

extent in the past year, but that caused by receiver radiation is still a serious problem, and it will continue to plague viewers for as long as the great number of offending sets are in use.

Considering that manufacturers have concentrated their advertising and promotion on TV to the virtual exclusion of audio receivers, it is surprising that the sales of the latter held up so well. Some effort has been put behind clock radios, but there is a question as to whether they were bought as clocks with radio as an extra feature, or radios with clocks as a plus value! Zenith was the only company to promote FM sets consistently through the year. That accounts for the relatively small number of FM cabinet models produced. RTMA figures do not include FM and FM-AM tuners, since they are not classified as factory-built types.

Nevertheless, the number of FM tuners built in '52 was several times that in '51, and it will be much higher in '53. The older companies are steadily increasing their output, and others are planning to enter the market this spring. Sales, it should be noted, are being handled by mail order houses, dealers specializing in high-fidelity equipment, and the parts jobbers, rather than the conventional outlets for factory-built radio and TV sets.

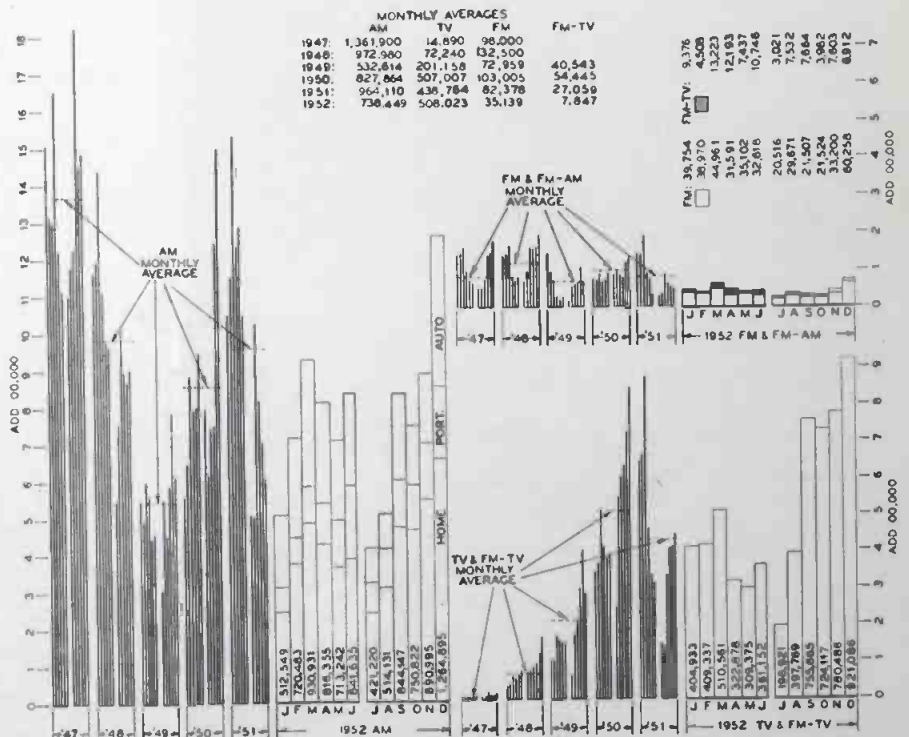

TV, FM, and AM set Production Barometer, prepared from RTMA figures

TV & RADIO ENGINEERING

PRODUCT INFORMATION

Sound Effects Filter: Built on a standard slotted rack panel 3½ ins. high, this versatile sound-effects filter has 8 high and low cut-off frequencies from 100 to 5,000 cycles, and flat positions at both ends. Cutoff rates are 16 db per octave on all positions. Toroid coils are used for hum-pickup immunity. All




inductors and capacitors are hermetically sealed, so that aging effects are negligible. Input and output impedances, 500/600 ohms. Hycor Company, Inc., 11423 Vanowen Street, North Hollywood, Calif.

Miniature Electrolytics: Claimed to be the smallest ever made, a new line of metal-encased electrolytic capacitors has been developed for hearing-aids and similar applications. These Microlytic series 999 units are .175 in. O.D. and 11/32 to 1 1/32 ins. long, rated at .05 to 3 mfd., 3 to 50 WVDC. Other types can be supplied to specifications. Micamold Radio Corp., 1087 Flushing Avenue, Brooklyn 37, N. Y.

High-Output Tape: Greater dynamic range than ever before obtained on magnetic recording tape is provided by a new line of tape introduced recently. Designated Scotch No. 120 High-Output tape, it will accept recording levels of 8 db over conventional red-oxide tape at a given distortion level, thus bettering the signal-to-noise ratio by 8 db. Same bias methods are used. Minnesota Mining and Manufacturing Company, 900 Fauquier Street, St. Paul, Minn.

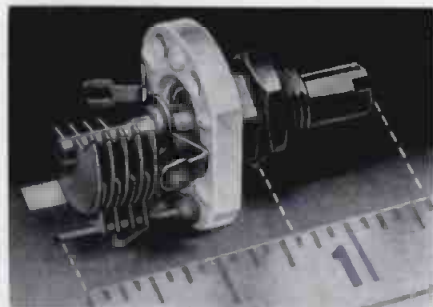VHF Trimmer Capacitor: Measuring only 3/4 by 5/8 in. and with a range of 1.4 to 19.6 mmf., type MAC variable capacitor is intended for miniaturized VHF equipments.




Rotor and stator are of silver-plated brass. The wiper rotor contact is of silver-plated beryllium-copper. Hammarlund Manufacturing Company, Inc., 460 West 34th Street, New York 1, N. Y.

CRO Table: A movable table for mounting oscilloscopes has just been made available. Table top is adjustable in height and can be tilted 0 to 20° backward. Lower shelf and large drawer are provided for storing auxiliary equipment. The table is mounted on large swivel-type rubber-tired casters. A. B. DuMont Laboratories, Inc., Instrument Division, 1500 Main Avenue, Clifton, N. J.

Capacitor Catalogue: Dimensions, prices, and specifications are given for virtually all types and sizes of transmitting and receiving capacitors in Catalog C-10, available from Wells Sales, Inc., 833 West Chicago Avenue, Chicago 22, Ill.

Reverberation Unit: A multiple-head magnetic tape loop recorder-reproducer, occupying only 8 3/4 ins. of standard rack space, has been developed to replace the space-wasting and expensive echo chamber. Amazingly flexible and effective, the unit contains equalizer controls and incorporates a zero-loss straight-through channel. Model 40 contains 5 heads with reverberation time adjustable to 6 seconds; model 42, 7 heads and 10 seconds. Audio Instrument Company, Inc., 133 West 14th Street, New York 11, N. Y.

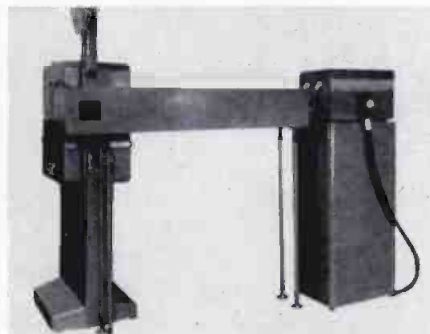TV Film Shadow Box: This new film multiplexer and shadow box permits film pickup by standard image orthicon TV cameras. Assembly consists of light-tight wooden shadow box with apertures for two 16-mm. film pro-



jectors and the TV camera. Inside the box are a mirror multiplexer and a high-resolution screen upon which the camera is focussed. Unit is mounted on four adjustable legs to provide easy leveling. Federal Telecommunication Laboratories, Inc., Nutley, N. J.

Miniaturized Potentiometers: Designed for use in TV receivers and small radios, a line of dime-sized composition variable resistors is rated at .3 watt below 10,000 ohms and .2 watt above. These type 70 units are available in various tapers and shaft styles. Chicago Telephone Supply Corp., Elkhart, Indiana.

New Slide Projector: Standard 2 by 2 in., or 35-mm. transparent slides in unlimited number can be projected automatically by remote or local control with the Teloprojector. This unit provides lapped, superimposed, or divided images through the use of two turrets. Additional pre-loaded turrets can be exchanged with used turrets in seconds. Gray Research and Development Company, Inc., 16 Arbor Street, Hartford 1, Conn.

Parabolic Reflectors: Complete mechanical dimensions and specifications for over 100 types of stock parabolic reflectors are given in a catalog just prepared and available on request from Workshop Associates Division, The Gabriel Company, Endicott Street, Norwood, Mass.

Continued on page 8

From Alden's Line of Ready-made Components for Unitized Plug-in Unit Construction:

Miniature Sensing and Indicating Components by


ALDEN

PATENTS PENDING



TOPS IN QUALITY & APPEARANCE
SAVE INSTALLATION COST & SPACE

ALDEN "PAN-i-LITE"

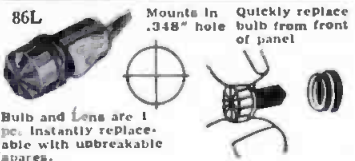

Bulb and Lens are 1 pc. Instantly replaceable with unbreakable spares.

You can use this new tiny Alden Pan-i-Lite indicator where never before possible. Easily serviced one-piece lens-bulb replaceable from front of panel. Mounts simply by pushing into .348" hole. Gives beautiful indication; glows like a red hot poker. Tiny spares can always be kept ready in kit or taped in recess of equipment. Available in 6V, 12V and 28V, various colors.

ALDEN "FUSELITE"



440-3/7 FH

to each unitized circuit. Available for 28V, 110V and 250V.

ALDEN TEST POINT JACK



Fits Anywhere
Takes Up to 8,000V.

Provides a quick front panel check point for any circuit voltages in your equipment. This tiny Jack fits .257" hole and takes only 29/32" behind panel. Beryllium copper contact withstands hundreds of insertions. Phenolic or nylon insulation, many colors.

SEND FOR FREE SAMPLES

— also request free "Alden Handbook" 226 pages of techniques and components for Unitized Plug-in Unit Construction.




ALDEN PRODUCTS CO.

145 N. Main St., Brockton 64, Mass.

February-March, 1953

TRANSMISSION LINES FOR AM-FM-TV-MICROWAVE ANTENNA EQUIPMENT • ANTENNA TUNING UNITS • DOWNING EQUIPMENT

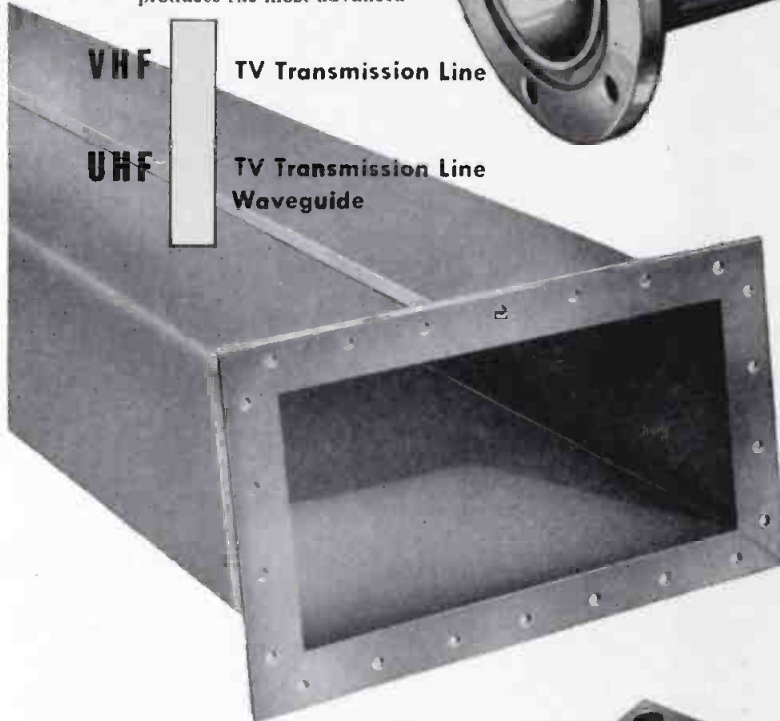Andrew's vast experience produces the most advanced




Request Andrew Nomographs in Bulletin 81 for direct graphical computation of efficiency of 10 to 2000 foot runs of line.

Andrew
CORPORATION

363 EAST 75TH STREET, CHICAGO 19
ANTENNA SPECIALISTS

ANDREW Type Number	Size	Impedance	Insulator Bead Material
TRANSMISSION LINE FOR VHF-TV			
451	1 3/8"	51.5 ohms	steatite
551-4	1 3/8"	51.5 ohms	Teflon*
452	3 3/8"	51.5 ohms	steatite
552-1	3 3/8"	51.5 ohms	Teflon*
T-453	6 1/8"	51.5 ohms	steatite
TRANSMISSION LINE FOR UHF-TV			
561	1 3/8"	50.0 ohms	Teflon*
562	3 3/8"	50.0 ohms	Teflon*
563	6 1/8"	75.0 ohms	Teflon*
WAVEGUIDE FOR UHF-TV			
M-14710	Aluminum 7 1/2" x 15" rectangular cross-section, RTMA designation WR-1500, 12 foot section		
M-14715	Aluminum waveguide WR-1150, 11 1/2" x 5 3/4" inside dimensions, 12 foot section		

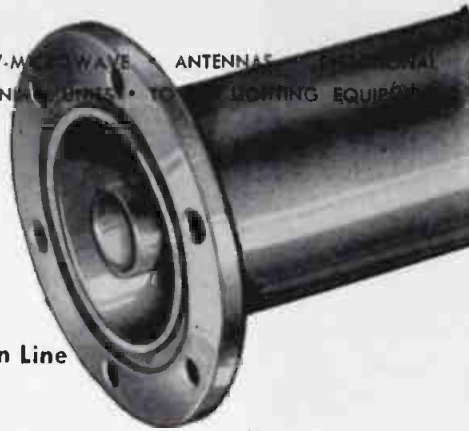*trademark for DuPont tetrafluoroethylene




NEW PRODUCTS

(Continued from page 7)

Hybrid Junctions: A new type of broad-band matched hybrid junction for X band wave-guide is available in aluminum or brass, with choke or flange connections. VSWR ranges from 1.08 to 1.20, depending on frequency, for the series arm; 1.05 to 1.175 for other arms. General Precision Laboratory, Inc., Pleasantville, N. Y.

Insulating Resin: A remarkable new electrical insulating resin, Silicone Varnish 994, retains 65% of initial dielectric strength after 2,000 hours at 250°C. According to manufacturer, craze life is longer by 4 times than that of best previous materials. For coating glass cloth and sleeving, and for bonding mica and glass. Dow Corning Corp., Midland, Michigan.

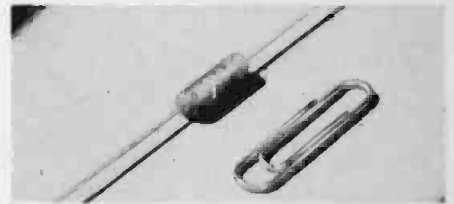Molded Paper Capacitors: Type 85-P molded paper capacitors, said to be the smallest available, are rated for continuous operation at 125°C. They are now available for




general use in two mould sizes, .175 by 5/8 in. and .200 by 5/8 in., and in 20, 10, and 5% tolerances. Bulletin 205E sent on letterhead request to Sprague Electric Company, 243 Marshall Street, North Adams, Mass.

90° Deflection Yoke: With horizontal inductance of 45 millihenries, a new cosine deflection yoke produces 90° deflection for 27-in. picture tubes. Sharp focus across entire screen is maintained, according to maker. DX Radio Products Company, 2300 West Armitage Avenue, Chicago 47, Ill.


Decade Amplifier: Type 140-A miniaturized laboratory voltage amplifier has frequency response flat within .1 db from 2 cycles to 1 mc., and stabilized voltage gains of 10 or 100. Straight RC coupling is used without peaking coils or compensators, hence transient and phase responses are excellent. Undistorted output, 40 volts max. Self-contained power supply. H. H. Scott, Inc., 385 Putnam Avenue, Cambridge 39, Mass.

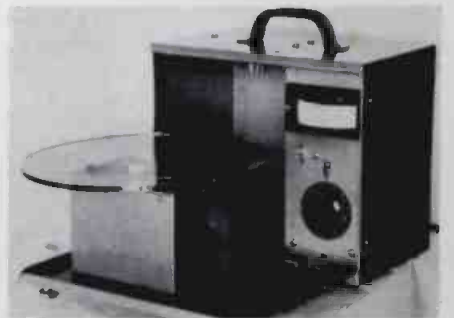CRT Glossmeter: Developed for the CRT committee of RTMA, this instrument measures reflectance from any type of tube face with radius of curvature greater than 12 ins. Consists of a light source, a photocell to



pick up light reflected as glare, a power supply, a calibrating variac, and a direct-reading microammeter indicator. Gardner Laboratory, Inc., Bethesda, Md.

UHF Transmission Line: New weather-proof 270-ohm UHF transmission line, type ATV-270, consists of two conductors surrounded by polyethylene spiral threads which act as centering mediums, permitting the conductors to float within individual polyethylene tubes. Outer jacket is constructed so that these tubes also are virtually suspended in air but are held to rigid spacing from one another. Efficiency at UHF is

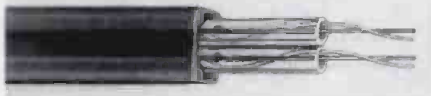

claimed to be 55 times that of standard flat ribbon line. Attenuation at 500 mc., 3.6 db/100 ft.; at 900 mc. 5.1 db/100 ft. Dimensions, 1/2 by 3/8 in. Developed by RCA Service Company and Anaconda Wire & Cable Company, New York 4, N. Y.

UHF-VHF Field Strength Meter: Covering 52 to 218 mc. and 470 to 890 mc. in 2 continuous ranges, a new field strength meter has a minimum sensitivity of 100 mv. for 50% meter deflection. Unit is portable, measuring 10 3/4 by 11 1/4 by 14 1/4 ins. Erwood, Inc., 1770 Bertenu Street, Chicago 13, Ill.

Closed-Circuit TV: Designed particularly for industrial applications, the TV camera shown is stated to be no more difficult or complicated to operate than the standard TV receivers which can be used with it. The camera is completely self-contained,



with all adjustments on the viewing panel. Over-all size is 14 by 9 3/4 by 4 3/8 ins. Dage Electronics Corp., 69 North 2nd Street, Beech Grove, Indiana.

Tantalum Foil Electrolytics: Polarized and non-polarized electrolytic capacitors of wound tantalum foil construction are described in a new bulletin, No. 523. Compactness, ruggedness, non-corrosive electrolyte, extremely low leakage current, long shelf life, low power factor, high operating temperature, and good frequency characteristics are claimed for these units. Cornell Dublier Electric Corp., Industrial Division, South Plainfield, N. J.

UHF Signal Generator: Model 612A generator, covering 450 to 1,200 mc. continuously, provides up to 5 volts output into 50 ohms. Broadband internal modulation up to 5-mc. can be obtained, or the instrument can be AM or pulse-modulated externally by pulses of 2 microseconds or more. Frequency and output are set directly and read on large

dials. Hewlett-Packard Company, 395 Page Mill Road, Palo Alto, Calif.

Transistor Batteries: A line of miniature low-voltage mercury batteries has been designed for junction transistor power supplies. Single cells of various sizes, called Energy Capsules, and cell combinations called Power-Pak batteries, are available in a wide range of voltages and ampere-hour capacities. P. R. Mallory & Company, Inc., Battery Division, North Tarrytown, N. Y.

Tubes and Sockets: Literature and technical data is available on the following tubes, germanium diodes, transistors, and sockets:

Amperex Electronic Corp., 230 Duffy Avenue, Hicksville, L. I., N. Y. — Type 5894-A UHF-VHF twin tetrode, 45 watts at 500 mc., wide-band RF amplifier, modulator, frequency multiplier.

Beam Instruments Corp., 350 Fifth Avenue, N. Y., N. Y. — Miniature CRT type 1CP1, for monitoring and similar purposes. Automatic focussing, only 1 anode potential required, cathode bias.

Hugh H. Eby, Inc., 4712 Stenton Avenue, Philadelphia 44, Pa. — New line of sub-miniature tube sockets meeting recognized industry standards and dimensions. Rectangular and round sockets.

International Rectifier Corp., 1521 East Grand Avenue, El Segundo, Calif. — Novel germanium diode assemblies, in double housings of phenolic material and glass. Excellent shock and vibration resistance claimed.

Lewis and Kaufman, Ltd., 62 El Rancho Avenue, Los Gatos, Calif. — Technical data sheet available on 4D21 power tetrode as Class AB1 or AB2 AF amplifier and modulator. Class C RF oscillator and unmodulated or high-level modulated amplifier.

Mycalex Tube Socket Corporation, 60 Clifton Boulevard, Clifton, N. J. — Transistor sockets molded of Mycalex 410 glass-bonded mica insulation, available in quantity. Contacts are of brass or beryllium copper. Also 7 and 9-pin miniature tube sockets for UHF applications.

Radio Receptor Company, Inc., 251 West 19th Street, New York 11, N. Y. — New and complete line of germanium diodes, including preferred JAN types. Tapered hexagonal bodies facilitate handling and indicate polarity at a glance.

Rauland Corporation, 4245 North Knox, Chicago, Ill. — Two new 21-in. rectangular TV picture tubes with spherical faceplates, 21YP4 and 21ZP4A, now in production. Former has electrostatic focus, latter magnetic focus.

Raytheon Mfg. Company, Receiving Tube Division, Newton 58, Mass. — Junction transistors CK721 and CK722, now available. CK721 has power gain of 38 db; CK722, 30 db.

Sylvania Electric Products, Inc., Radio Tube Division, Emporium, Penn. — Two new damping diodes for TV, 6AX4GT and 12AX4GT. Miniature high-perveance double triode for TV vertical deflection circuits, 12BH7. Sharp-cutoff high-transconductance video pentode, 12BY7, with miniature T-6 1/2 construction, separate suppressor grid connection. Rectangular 17-in. TV picture tube, magnetic focus, cylindrical faceplate, 17QP4. Miniature 9-pin triode-pentode, type 6U8, designed for oscillator-mixer service in FM and TV receivers.

Texas Instruments, Inc., 6000 Lemmon Avenue, Dallas 9, Texas — Point-contact transistor types 100 and 101. Former is for switching-circuit applications. Type 101 is high-efficiency amplifier for use below 1 mc. capable of handling large signals.

PHONE WELLS FOR ANY ELECTRONIC COMPONENTS

IMMEDIATE DELIVERY


FROM WORLD'S LARGEST STOCK . . . Seeley 8-4143

STOP COSTLY SHUT-DOWNS!

Write for Catalog

WELLS SALES INC. 833 W. Chicago Ave., Chicago 22, Ill.

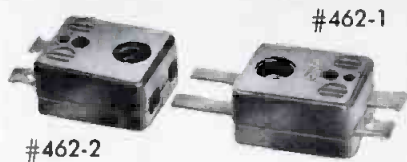
From Alden's Line of Ready-made Components
for Unitized Plug-in Unit Construction:




ALDEN PATENTED

BACK CONNECTORS

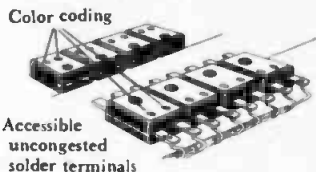
Get accessible central
check point for incoming
and outgoing leads



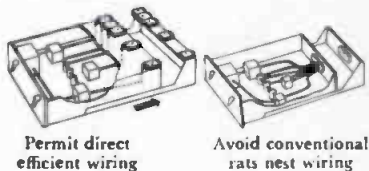
EASY SERVICING AND RAPID CIRCUIT CHECKS
Solder terminals easily accessible and uncongested for multiple contact wiring. Color-coding on back connector, corresponding to lead color, identifies each lead for instantaneous check to main circuit or trunk line.



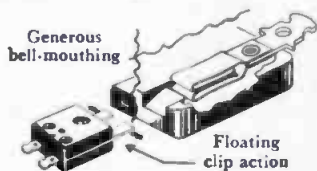EFFICIENT CIRCUIT WIRING
Connectors can be mounted where desired — to allow for isolation of critical voltages or frequencies — to provide most direct wiring from component to connector — to eliminate rat-nest wiring of conventional methods.



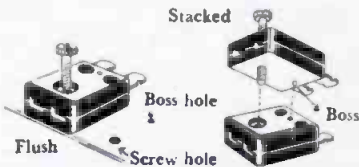EASY INSERTION AND REMOVAL
Made possible by large bell-mouth entries and ample float of rugged live-action beryllium copper contacts. Wide mating tolerances eliminate critical unit alignment problems.



EASY MOUNTING
Single screw for mounting flush or stacked. Molded locating boss positions and locks connector in place on unit when flush mounted — boss accurately lines up and positions connectors together in stack mounting.

SEND FOR FREE SAMPLES

— also request free "Alden Handbook" 226 pages of techniques and components for Unitized Plug-in Unit Construction.



ALDEN PRODUCTS CO.

145 N. Main St., Brockton 64, Mass.

COMPANIES and PEOPLE

\$8.5 Million for WPTZ:

Philco's TV station, started as an experimental transmitter in 1932, has been purchased by Westinghouse Radio Stations, Inc. It is understood that there will be no changes in the WPTV staff.

William P. Maginnis:

Elected vice president and chief engineer of Federal Telephone & Radio Corporation, Clifton, N. J. Prior to joining Federal in 1951, he was with RCA for 21 years. Mr. Maginnis will direct the telephone, radio, and vacuum tube engineering activities.

UHF Survey at Portland:

RCA has issued a very complete report on the coverage furnished by KPTV, now operating on 548 to 554 mc., with 16 kw. effective radiation. The report, of 24 pages, is profusely illustrated with photographs and charts. Copies can be obtained from the Engineering Products Division at Camden, N. J.

Relay Plant:

A new factory of 50,000 square feet, designed specifically for the manufacture of telephone relays, has been completed by C. P. Clare & Company, at 3101 W. Pratt Avenue, Chicago. Of windowless construction, it is provided with air conditioning, electrostatic air cleaning, humidity control, and shadowless lighting.

See You at the IRE Show:

TV & RADIO ENGINEERING, together with COMMUNICATION ENGINEERING and HIGH FIDELITY, will be represented at booth 3-310. We shall be glad to greet all our friends, and to discuss editorial material with those who are interested in preparing articles for any of our three magazines.

Speaker Magnet Requirements:

The RTMA Speaker Section, of which Russell Fenton is chairman, has submitted an estimate of Alnico 5 magnets which will be required for 1953 speaker production. The figure is 2,110,000 lbs., allowing 1½ oz. for each of 22,500,000 speakers. Last year, 18,807,515 speakers were manufactured in this Country.

Radio Industry Statistics:

Data on the radio industry by the Bureau of the Census has lacked certain significant information in the past, because it has been handled as a subclassification

of electrical machinery. RTMA is now seeking to obtain more adequate recognition of the radio industry in the Bureau's industrial classifications.

L. W. Teegarden:

RCA vice president in charge of technical products has been elected executive vice president, a post made vacant when Joseph H. McConnell resigned to become president of Colgate-Palmolive-Peet.

West Coast Components Plant:

Construction has been started by Aero-vox Corporation on a new plant at Monrovia, Calif. Manufacturing operations are scheduled to start early this summer.

North Adams, Massachusetts:

Robert C. Sprague, founder of Sprague Electric Company, has resigned as president. He has been succeeded by Julian K. Sprague. Also elected to the board of directors are Ernest L. Ward, William J. Nolan, George B. Flood, and Robert C. Sprague, Jr. Neal W. Welch has been appointed director of sales.

Radio Club of America:

Officers elected for 1953 are: John H. Bose president, Ralph R. Batcher vice president, Joseph Stantley treasurer, Frank H. Shepard, Jr. secretary, Frank A. Gunther recording secretary. Also elected to the board of directors are Ernest V. Amy, Edwin H. Armstrong, George E. Burghard, Alan Hazeltine, Harry W. Houck, Jerry Minter, and Harry Sadenwater.

Cleveland, Ohio:

Construction has been completed on Hickok Electrical Instrument Company's new assembly plant at 10626 Leuer Avenue. New techniques and facilities have been worked out for continuous workflow in such a manner as to permit quick changeover in response to demands for the 60 instruments which now comprise the line. Engineering and meter manufacturing will continue at 10514 Dupont Avenue.

Dr. Gordon K. Teal:

Has joined Texas Instruments, Inc. as assistant vice president in charge of materials and components research. Before he assumed this post, he had been with Bell Laboratories since 1930 where, in recent years, he had a part in the development of transistors and resistors.

Professional Directory

Jansky & Bailey

Consulting Radio Engineers

EXECUTIVE OFFICES:

970 National Press Bldg.
Washington, 4, D. C. ME 5411

OFFICES AND LABORATORIES:

1339 Wisconsin Ave., N.W.
Washington, 7, D. C. AD 2414

Member AFCE

WELDON & CARR

Consulting
Radio & Television
Engineers

Washington, D. C. Dallas, Texas
1605 Connecticut Ave. 4212 So. Buckner Blvd.

MICROWAVE SERVICES, INC.

"Architects of Modern Communications"

Independent Consultants,
Engineers, Constructors

Wire, Carrier, Radio — Transmission, Distribution
— Inside and Outside Plant Facilities —
Appraisals, Surveys, Specifications, Design,
Construction

Circle 7-4953 45 Rockefeller Plaza, New York 20



SINCE
1931

Professional 16mm Sound-On-Film Motion
Picture Cameras for Television Newsreels,
Commercials and other Television Filming.

Write for free illustrated catalog.

BERNDT-BACH, Inc.

7349 Beverly Blvd., Los Angeles 36, Calif.

RUSSELL P. MAY

CONSULTING RADIO ENGINEERS

★ ★ ★

1422 F Street, N.W., Wash. 4, D. C.
Kellogg Building Republic 3984

Member AFCE

WORKSHOP ASSOCIATES DIVISION

THE GABRIEL COMPANY

Specialists in
High-Frequency
Antennas



Endicott Street Norwood, Massachusetts
Norwood 7-3300

An Interesting Opportunity:

There's a very interesting position open at The Publishing House for an engineer who is interested in technical writing. It is an opportunity for diversified experience on COMMUNICATION ENGINEERING, TV & RADIO ENGINEERING, and HIGH FIDELITY Magazines. For a man who wants to work and live in the country, and yet keep up with city activities by making trips to various places where interesting things are going on, this is an ideal situation. If you are interested, write to Milton Sleeper, The Publishing House, Great Barrington, Mass.

NARTB Los Angeles Conference:

Program for the annual Broadcast Engineering Conference is being planned by a guidance committee comprised of Raymond Guy NBC, chairman, Frank Marx ABC, William B. Lodge CBS, Rodney D. Chipp, Dumont, Earl M. Johnson MBS, A. James Ebel WMBD, and Carl Nopper WMAR-TV. This group is working with Neal McNaughton, NARTB.

Color TV Research:

Admiral Corporation is operating a color research laboratory at Palo Alto, Calif., staffed under Robert M. Jones.

1952 Tube Production:

RTMA reports production of 7.6 million cathode ray tubes valued at \$170.6 million in 1952, and 368.5 million receiving type tubes valued at \$259.1 million.

MEETINGS and EVENTS

MARCH 23-26,
IRE NATIONAL CONVENTION & SHOW
Grand Central Palace, New York City

APRIL 11,
NEW ENGLAND RADIO ENGINEERING MEETING
Univ. of Connecticut, Storrs, Conn.

APRIL 16-17,
JOINT RTMA CONFERENCE, U. S. & CANADA
Ambassador Hotel, Los Angeles

APRIL 18,
CINCINNATI SECTION IRE CONFERENCE
Cincinnati, Ohio

APRIL 26-30,
73RD CONVENTION SMPTE
Hotel Statler, Los Angeles

APRIL 28-MAY 1,
NARTB BCST. ENGINEERING CONFERENCE
Philharmonic Auditorium, Los Angeles

APRIL 29-30, MAY 1,
ELECTRONIC COMPONENTS SYMPOSIUM
Shakespeare Club, Pasadena, Calif.

MAY 11-13,
IRE AIRBORNE ELECTRONICS CONFERENCE
Dayton, Ohio

MAY 18-21,
1953 ELECTRONICS PARTS SHOW
Conrad Hilton Hotel, Chicago

JULY 13-16,
MUSIC INDUSTRY TRADE SHOW
Palmer House, Chicago

AUGUST 19-21,
WESTERN ELECTRONIC SHOW
San Francisco Auditorium, San Francisco

SEPTEMBER 1-3,
INT'L SIGHT AND SOUND EXPOSITION
Palmer House, Chicago

SEPTEMBER 28-30,
9TH NATIONAL ELECTRONICS CONFERENCE
Hotel Sherman, Chicago

OCTOBER 26-28,
RTMA-IRE RADIO FALL MEETING
Toronto, Ontario, Canada

Professional Directory

KEAR & KENNEDY

Consulting Radio Engineers

1302 18th St., N. W. HUDSON 9-9000

Washington, D. C.

GEORGE P. ADAIR

Consulting Engineers

Radio, Communications, Electronics

1610 Eye St., N.W. EXECUTIVE 1230

Washington 1, D. C.

Paul W. Klipsch
Professional Engineer
Acoustic development
and consulting

Klipsch and Associates
building the authentic
KLIPSCHORN
world's finest sound reproducer

Hope, Arkansas

Tel. Hope 995



16-MM Professional Motion Picture
Production Equipment

J. A. MAURER, Inc.

37-07 31st Street, Long Island City 1, N. Y.
Tel. Stillwell 4-4601

MEASUREMENTS CORPORATION



Research &
Manufacturing
Engineers

Harry W. Houck Jerry B. Minter
John M. van Beuren
Specialists in the Design and
Development of Electronic Test Instruments
BOONTON, N. J.

JOHN D. TRILSCH CO.

TOWERS for
RADIO • TELEVISION
COMMUNICATION

1310 McKinney Ave., Houston, Texas
Phone: ATwood 9351

TV & RADIO REVIEW

PERHAPS this first Review should, like Janus, look back toward the past, and forward toward the future. But can it be said that radio broadcasting, and particularly television, has had time to acquire a past? And how, with the short focus of a few years, can we expect to get a sharp picture of the future?

These questions were brought to mind by the address which Dr. Lloyd V. Berkner, president of Associated Universities, Inc., delivered before the Radio Club of America last December. By way of introducing his discussion of the world's sources of energy, Dr. Berkner said: "Aside from the energy needed for food and minimum of warmth that is common to all biology, it is energy under man's control that forms the very basis of his civilization. In his quest for better living, and for time to follow intellectual pursuits, which are the bases of civilization, man first used slaves, both human and animal, as his principal energy-source. Then man learned to use the wind to sail his ships, and a little waterpower to grind his flour. But until two centuries ago, this was about the limit. The man without slaves, or without the favor of a court that had slaves, was poor indeed.

"The industrial revolution and, with it, the revolution in our civilized habits was started by James Watt [in 1769], who with his steam engine contrived to make controlled energy abundant. With the coming of simple electrical transmission of energy over great distances by fixed conductors, the first stage of the industrial revolution was complete. Each man, woman, and child in the United States now has the equivalent of 200 slaves at his disposal. Energy has made each of us king in contrast to the miserable situation of our forebears.

"This change has not been a slow evolution. It has been, rather, a sudden revolution. Man's written history is but 300 generations old. [For statistical purposes, a generation is considered to be 30 years.] So close are we to the beginning of civilization that about 7% of all men born throughout history are still living. Power in substantial quantities under man's control goes back only 6 or at the most 7 generations. Yet we routinely accept the mechanical slaves that power gives us as though they had always been present."

It seems impossible to believe now, in a land where there is available the work output of 200 slaves for each man, and woman, and child, that human slavery could have been an issue in a civil war less than three generations ago! And as we make plans today for the progress of tomorrow, we can see by looking at the past how short-sighted must be our view of things to come.

FOR example, there is the current philosophy that regards some 125 stations as the limit of TV network expansion, a figure indicated by operational economics. That figure may stand, of course, but its acceptance presumes that people who are now satisfied with the present picture quality of fringe-area reception from metropolitan stations will not prefer to tune in local stations, as they go on the air, in order to get the sharper pictures provided by stronger signals. Listeners, as we know, become conditioned to inter-station interference, static, and fading. But those viewers who have been putting up with the visual uncertainties of poor TV reception will quickly reject images that are less than clear and steady once they become available from new, nearby stations.

While broadcasters may be right in assuming that audio signals must be good enough because people listen to them,

whatever the quality of reception may be, television signals from one station are good enough *only* if they are better than those from other stations picked up in a given area. The hand may be quicker than the eye, but the eye is more critical than the ear. Moreover, high-power TV, like FM, does not have the secondary coverage that AM broadcasting provides. Also, as time goes on, if TV stations spring up in a considerable percentage of the areas where frequencies have been allocated, present fringe-area coverage may be reduced by interference. The final answer as to the number of stations which should comprise a TV network depends in part, at least, on factors not yet finalized, such as receiving conditions when another 500 transmitters are on the air, audience viewing habits, and the possible reduction of networking rates.

PROGRESS in color television highlights the antagonism which has always existed between those whose interests lie in regulation, and those who insist that they be free to conquer limitations. The extent to which government agencies can be legally right and factually wrong was never demonstrated as clearly and quickly as when our Federal Communications Commission attempted to dictate the course of advancement that color television should take. An interesting aspect of this case was that the public, the industry, and the scientists all rejected the Commission's purely legalistic stand.

There is no timetable yet for the introduction of color. Even if it were completely ready now, it would be too early to start transmission, and to offer receivers to the public. That will be the logical next step after the basic black-and-white method of broadcasting has been established on a national basis. It is only sound procedure to solve problems first in their simpler forms, with the least number of undetermined variables. The time to undertake color will come when the industry has completed its job of furnishing satisfactory monochrome service on a national basis for, until then, we shall not have encountered and solved all the basic problems of TV transmission and reception. At that point a compatible color system will be required, not only because it will facilitate the introduction of color but because, certainly at the beginning, programming will be switched back and forth between monochrome and color.

One important point about color was not established in the FCC tests, nor has it been subsequently: what will be the difference in the service areas of black-and-white and color transmission? Many viewers are now satisfied with substantially deteriorated picture quality. What will they see when their same stations switch to color? Will the images be more or less acceptable? To put it another way: How will people choose between sharp monochrome pictures from a local station, and less-than-perfect images in color provided by weaker signals from distant, high-power stations? Color will undoubtedly be an important factor in the competition for audiences, but only time will assign values to these presently-unknown quantities.

Educational television is a subject about which differences of opinion are drawn sharply. In theory, it has almost unlimited possibilities as an effective means of mass education. Practical-minded educators, on the other hand, recognizing that television is not a substitute for classroom instruction, view with alarm the possible diversion to television of funds

which, if and when available, are so sadly needed for additions to already inadequate school facilities. In some instances, it is held that support to educational television is being given by those whose real purpose is to confuse the issue of increased appropriations for new schools and more capable teachers, in order to postpone action on increasing funds for any educational purpose.

In any case, it is obvious that neither the FCC nor the educators who are actively supporting educational television have a realistic attitude toward the problems of producing effective program material, and the cost of programming and operating such stations.

And behind all that is being said about the potential values of educational television on a national basis, as envisioned by the FCC's plan of frequency allocations, there is the question in many minds as to the possibility that, somewhere in the background, lurks the undisclosed purpose of using such stations for government-controlled education, to be directed at children and adults alike.

Perhaps the wisest decision that can be made about educational television at this time is to make no decision at all and to let the right answer make itself evident, as it certainly will if it is allowed time to do so.

IN the field of scientific progress, one of the most interesting developments is that of recording TV shows on tape. If the work now being done was started from the point of basic research into the nature of the electrical impulses to be recorded, there is every reason to expect that tape can produce the visual equivalent of a live show, just as it is doing now in audio programs.

The use of TV tapes will probably be as an adjunct to film, however, because the latter has a practical advantage in editing. That is because film provides a record that can be seen, while tape does not. Interestingly enough, tape may eventually bear the same relation to film that disc records now bear to tape!

Television tapes may offer an important advantage to small stations, since the cost of equipment should be lower than that required for programming from movie film. Thus it may come about that TV shows will be taped from master films, just as phonograph records are made from master tapes.

EQUIPMENT is now available for theatre television, but this project is confronted with problems of frequency allocation and frequency utilization. There is keen competition for the channels being sought by the National Theatre TV Committee and the Motion Picture Association of America. The need for radio operation, according to representatives of these groups, is due to the fact that common carrier service is not available for network connections. On the other hand, while the theatres are asking for exclusive frequency allocations, their ultimate expectancy for using the channels they want is limited to 5 hours per day.

Considering the aspects of public interest, convenience, and necessity, the FCC is also concerned with the possibility of direct competition between the present TV broadcasting service and theatre television, since the movie producers might favor the latter at the expense of the former.

From the point of view of frequency utilization, it is argued that theatre television is a point-to-point service to be operated only a few hours a day, and should, therefore, be handled over a common carrier relay system, with wire-line connections to the theatres. Certainly the economics favor that plan, for part-time use of a microwave system might well run into such expense as to preclude any boxoffice profit. That seems particularly so if, as some experts contend, present TV

standards are not high enough to give the degree of definition needed for satisfactory theatre projection.

RELAXATION of FCC operator requirements and the authorization of remote controls promise a measure of relief to the smaller audio broadcasting stations. Under the Report and Order issued on January 27, "holders of commercial radio operator licenses of any class except aircraft radiotelephone operator authorizations or temporary limited radiotelegraph second-class licenses may be employed to stand regular watches and perform limited duties at all AM broadcasting stations with operating power of 10 kw. or less when employing non-directional antennas, and at all FM and non-commercial educational FM stations with operating power of 10 kw. or less. However, at least one person holding a radiotelephone first-class operator license is required to be employed as a regular full-time operator at all AM and FM stations affected, to supervise and insure the proper functioning of the station equipment.

Further: "At non-commercial educational FM stations of 1 kw. or less, but above 10 watts, the operator may be a person holding a radiotelephone second-class license. At non-commercial educational FM stations of 10 watts or less, the operator may be a person holding a radiotelephone or radiotelegraph second-class operator license, but he is not required to be a regular full-time employee of the station, although he must be available on call."

Use of remote controls for transmitters is another means of reducing the expense of operating small stations. The Report and Order referred to above provides that: "A station which is authorized for non-directional operation with power of 10 kw. or less may, upon prior authorization from the Commission, be operated by remote control at the point(s) which shall be specified in the station license. . . . Operation by remote control shall be subject to the following conditions:

"(1) The equipment at the operating and transmitting positions shall be so installed and protected that it is not accessible to or capable of operation by persons other than those duly authorized by the licensee.

"(2) The control circuits from the operating position to the transmitter shall provide positive on and off control, and shall be such that open circuits, short circuits, or other line faults will not actuate the transmitter, and any fault causing loss of such control will automatically place the transmitter in an inoperative condition.

"(3) Control and monitoring equipment shall be installed so as to allow the licensed operator, either at the remote control point or at the transmitter, to perform all the functions in a manner required by the Commission's Rules and Standards."

A remote control installation has already been made at KEAR San Mateo, Calif., and another is under way at KSON San Diego, using equipment furnished by The Rust Industrial Company of Manchester, N. H. Of relatively inexpensive design, the Rust system provides for as many as nine meter readings and nine transmitter adjustments over two telephone pairs. Thus, as a transmitter function is adjusted from the remote point, the corresponding meter-reading can be observed.

Principal argument advanced against the relaxation of the Rules was that some engineers will lose their jobs. While it is true that stations will be able to reduce their payrolls, the change may be a blessing in disguise for the operators. There is a large unfilled demand for licensed operators to take charge of radio communication systems, and at wages substantially higher than those paid by the smaller broadcast stations. Quickest way to locate those positions is to inquire of the companies manufacturing communication equipment, for they get the information from their field engineers.

Noise and NTSC Color Standards

PRACTICAL EFFECTS OF NOISE ON TENTATIVE NTSC COLOR SIGNAL UNDER VARIOUS CONDITIONS OF CHROMATICITY AND LUMINANCE—By C. H. JONES*

ABSTRACT

The purpose of this paper is to evaluate the efficiency with which the NTSC color television system transmits color information in the presence of noise.

For such an analysis, it is convenient to use the concept of a three-dimensional color solid. One dimension is determined by the amplitude of the black-and-white modulation envelope. The other two dimensions, in polar form, are determined by the magnitude and phase of the 3.9-mc. color subcarrier signal. The Munsell Color Solid specifies in an ideal way the visual relationship that exists among colors, because equal distances have equal visual meanings. In order to compare the NTSC solid with the ideal, contours of Munsell hue, value (related to luminosity), and chroma (saturation) have been plotted. An examination of these contours shows quantitatively what colors are most influenced by noise. The effects of placing the Z-Y and X-Y axes 119° apart are discussed. The proposed gamma of 2.75 is examined to determine whether or not it gives the best luminosity signal-to-noise ratio. The effect of applying gamma correction to each of the colors is analyzed.

While the tentative NTSC color signal is undergoing field tests, it is advisable to examine this signal theoretically to determine how it is affected by noise. Comparison with similar systems should reveal the strong and weak points of the proposed signal. In order to make such an examination, quantitative information is needed as to just how well the normal eye is able to perceive changes in brightness, changes in hue, and changes in saturation. Fortunately, such data is available in the form of Munsell^{1,2} Value, Hue, and Chroma specifications.

When dealing with different types of color specifications, the concept of a color solid is often very helpful.^{3,4,5} Five different color solids are discussed in this paper, but they are all of the general form shown in Fig. 1. The vertical axis is a measure of brightness; the radial distance from this axis, saturation; and the angular position on any plane, hue. Shape of the

color solid and the units used for the three dimensions vary from one solid to another. Fig. 2 shows a three-dimensional model of one color solid.

Munsell Colors: The three scales shown for the Munsell system are intended to agree as closely as possible with a normal observer's perception of the three dimensions of the color solid. Lightness differences that are equally perceptible are spaced equally along the vertical axis, and are measured as Munsell Value.^{**} Hue differences that are equally perceptible are separated by uniform angles, and are specified as Munsell Hue. Saturation steps are measured radially in uniformly perceptible steps as Munsell Chroma. A typical color specification would be 5R 4/8, which is a Hue of 5R, a Value of 4, and a Chroma of 8. Dorothy Nickerson⁶ has suggested that the Munsell Renotation Values⁷ be used to study systems that are based on the CIE (ICE) system of colorimetry.

CIE Diagrams: The CIE or ICI diagram⁸ is by now familiar to color television engineers.^{9,10} If the spectral response of a surface is known, the tristimulus values X, Y, and Z can be obtained. By multiplying points on the sample curve by corresponding points of the standard |X| curve, Fig. 3, and integrating, X is obtained. Y and Z are obtained by using the curves |Y| and |Z| in the same way. The sum of the tristimulus values X, Y, and Z gives the color mass or color weight.

$$W = X + Y + Z \quad (1)$$

The quantity W can be obtained directly by multiplying the spectral curve of the sample by curve |W| shown in Fig. 3. It will be noted that blue colors, or those with wavelengths near 445 millimicrons, have relatively low luminosity but high color mass. Therefore, reflected energy in this region has little effect on brightness but a great effect on chromaticity. In the field of color television, there seems to be some tendency to underestimate the importance of blue.

*Research Laboratories, Westinghouse Electric Corp., East Pittsburgh, Pa. This paper was presented at the eighth National Electronics Conference in Chicago, Ill., December 29, 1952.

¹Munsell Book of Color, Munsell Color Company, 10 East Franklin St., Baltimore, Maryland; 1929.

²A Color Notation, 9th Edition, by A. H. Munsell, Munsell Color Company; 1941.

³"Colorimetry in Television", by F. J. Bingley, a paper presented at the 1951 Convention of the I.R.E., New York.

⁴"Color Systems and Their Inter-Relation", by Deane B. Judd for the National Bureau of Standards, a paper presented at the 1940 Annual Convention of the Illuminating Engineering Society, Spring Lake, New Jersey.

⁵Color in Business, Science, and Industry, by Deane B. Judd, Wiley and Sons, Inc., New York. Part II, pp. 80-296.

**In this paper, when the words Value, Hue, and Chroma are capitalized, Munsell Value, Munsell Hue, and Munsell Chroma are implied.

⁶"Munsell Renotations Used to Study Color Space of Hunter and Adams", by Dorothy Nickerson, *J. Opt. Soc. Am.*, vol. 40, No. 2, pp. 85-88; February, 1950.

⁷"Final Report of the OSA Subcommittee on the Spacing of the Munsell Colors", by S. M. Newhall, D. Nickerson, and D. B. Judd, *J. Opt. Soc. Am.*, vol. 33, p. 385; 1943.

⁸Handbook of Colorimetry, Massachusetts Institute of Technology.

⁹Television Engineering, by Donald G. Fink, McGraw-Hill Book Company, Inc., New York, Chapter 8; 1952.

¹⁰"Color Fundamentals for Television Engineers", by Donald G. Fink, *Electronics*, vol. 23, pp. 88-93, December 1950; vol. 24, pp. 78-83, January 1951; pp. 104-109, February 1951.

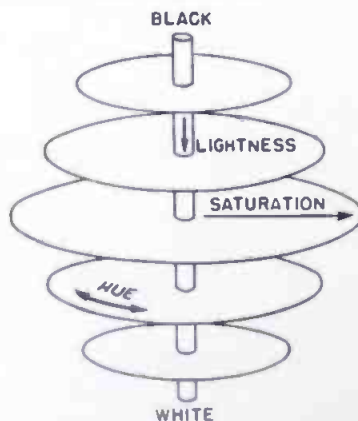


FIG. 1. DIMENSIONS OF A COLOR SOLID.

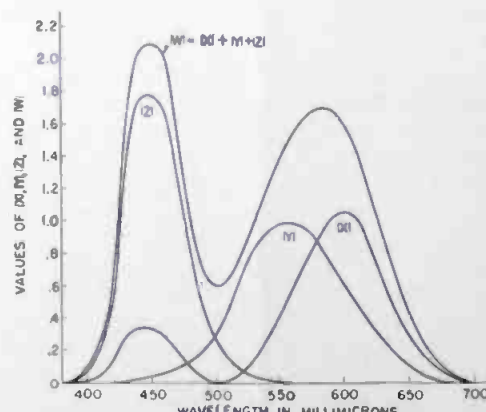


FIG. 3. STANDARD CIE CURVES FOR X, Y, Z, AND W.

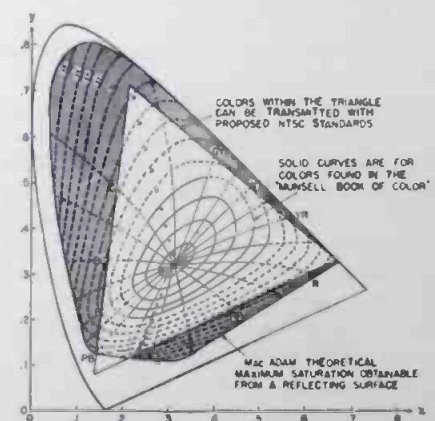


FIG. 4A. A CHROMATICITY DIAGRAM FOR MUNSELL VALUE 5

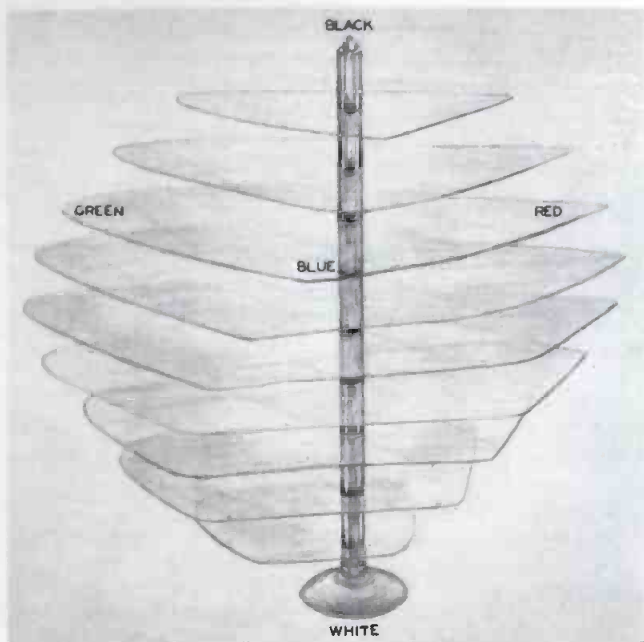


FIG. 2. A MODEL OF JUDD'S MODIFIED HUNTER ALPHA-BETA COLOR SYSTEM

The trichromatic coefficients are obtained by simply normalizing the tristimulus values as follows:

$$x = \frac{X}{W}, \quad y = \frac{Y}{W}, \quad \text{and} \quad z = \frac{Z}{W} \quad (2)$$

$$\text{Since } x + y + z = 1, \quad (3)$$

it is customary to specify only x and y . In making additive color mixtures, a plot of colors on an x, y chromaticity diagram is very useful. By considering a weight proportional to the color weight W at each color, the resulting chromaticity of the mixture can be found by simply calculating the center of gravity of the system.

Response of the eye is not uniform in different parts of the diagram. Fig. 4A shows the Munsell colors plotted on the chromaticity diagram for Value 5. Both Hue and Chroma contours are close together in the blue region and are spread out in the green. This means that the eye is able to detect chromaticity changes in the blue more easily than in the green. Also, on the left side and bottom of the diagram the Munsell colors do not extend all the way to the spectral locus, but only as far as the maximum-demand contour.¹¹ At this specified brightness level, it is theoretically impossible to obtain a reflecting surface having a chromaticity outside this contour. As the luminosity becomes greater, the demand curve becomes smaller, Fig. 4B, until at white it is only a point.

At least a dozen different transformations of the ICE diagrams have been made in attempts to obtain spacings that more nearly correspond to the perceptibility of the eye.^{6,12} These transformations are of all sorts and complexities; some are linear homogeneous transformations,^{4,5} and others are not. Some almost succeed in making the Munsell Chroma loci concentric circles and in making the angular separation of the Munsell Hues uniform. Just how complicated a transformation is justified for a particular color problem depends on the way in which the transformed color solid is to be used. In color television, the optimum color solid depends primarily on two factors: the effect of noise, and the complexity of the receiver required to decode and present the color information.

Color Transmission: Consider now the problems of color television. Basic requirements are that the information be pack-

aged in such a way that it can be transmitted in the available spectrum, that it can be received by present black-and-white receivers, that it undergoes a minimum of damage from noise in transmission, and that color receivers can use the received information. The color information to be transmitted is three-dimensional, so that three parameters are necessary. Some of the possible combinations that specify a color completely are:

$$X, Y, Z \quad Y, (X-Y), (Z-Y)$$

$$Y, x, y \quad Y, \frac{x}{y}, \frac{z}{y}$$

$$W, x, y \quad R, B, G$$

$$Y, S, \Theta_H$$

where S = saturation

Θ_H = hue angle

R, B, G = red, blue, and green primaries.

Since the only information required at black-and-white receivers is the luminosity signal Y , it would seem logical to modulate the black-and-white carrier with Y or some function of it. It has been found by experiment that a signal located 3.6 to 3.9 mc. above the picture carrier is not noticeable on most black-and-white receivers, particularly if the exact frequency is chosen such that the intensity modulation cancels out on successive pictures. Therefore, it has been proposed that chromaticity information be applied to this color subcarrier. If both sidebands of the subcarrier are transmitted, then the signal can be modulated in amplitude and phase simultaneously so that two independent types of information can be transmitted. By utilizing the oscillating color sequence¹³ technique, one set of sidebands can be transmitted during one picture interval and the other set during the next picture interval.

Tests have been made¹⁴ which indicate that sufficient chromaticity information can be conveyed if the color subcarrier is modulated only at frequencies up to 1 mc. Fig. 5A is a diagram of the video waveform as various colors are transmitted according to tentative NTSC standards. Gamma was set at 1.

¹³"Color Television Systems with Oscillating Color Sequence", by B. D. Loughlin, Report No. 7116-2, Hazeltine Corporation; May 7, 1951.

¹⁴"Requisite Color Bandwidth for Simultaneous Color-Television Systems", by Knox McIlwain, *IRE Proceedings*, vol. 40, No. 8, pp. 909-912.

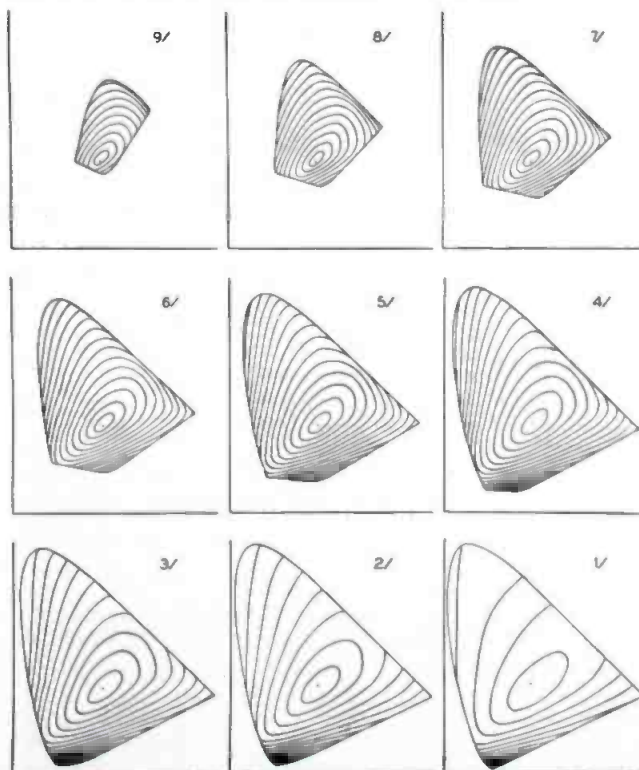


FIG. 4B. SCALED CHROMATICITY DIAGRAMS FOR MUNSELL VALUES 1 TO 9

¹¹"Maximum Visual Efficiency of Colored Materials", by D. L. MacAdam, *J. Opt. Soc. Am.*, 23, p. 361; 1935.

¹²"Comparison of Color Systems with Respect to Uniform Visual Spacing", by Robert W. Burnham, *J. Opt. Soc. Am.*, vol. 39, No. 3, pp. 387-392; May, 1949.

The corresponding colors are shown in Fig. 5B. All chromaticities are at maximum saturation.

All the color systems discussed in this paper employ phase modulation of the color subcarrier for hue transmission, and amplitude modulation of the subcarrier for saturation transmission. From the standpoint of noise, it is important to know in precisely what manner the phase varies with hue, the amplitude varies with saturation, and the DC level varies with luminosity.

The Brightness Signal: Brightness or luminosity transmission will be considered first. Let it be assumed that the transmitting equipment is capable of transmitting any function of Y , and that the receiver is capable of decoding this and reproducing the original Y values on the picture tube. If noise were not important, then it would be logical to transmit the function of Y that could be most easily decoded. For example, if receiver circuits were all linear, except for the picture tube which had a gamma of 2.75, then it would be sensible to transmit $Y^{1/2.75}$. Unfortunately, this is not the optimum characteristic for best performance with noise.

If it were desired to transmit ten brightness levels with noise noticeable equally at any level, ten brightnesses separated by intervals that are equally perceptible to the eye would be chosen. Those brightnesses should correspond to ten equally-spaced¹⁵ modulation voltage levels. This assumes a large signal-to-noise ratio. The problem then, reduces to that of determining the function of luminosity, $f(Y)$, which approximates the response curve of the normal eye in the range of brightnesses

to show how well this approaches an ideal straight line. Since the slope of this curve is nearly constant from gray to white, noise should be noticeable equally well throughout this region. In the very dark region the slope of the curve is large, so that noise should be less noticeable in that range.

For any function of Y , a comparison of the effects of noise at two brightness levels A and B can be obtained by comparing the slopes of the curves at the two points.

$$\text{db difference} = 10 \log \left(\frac{\text{slope at } A}{\text{slope at } B} \right)^2 \quad (5)$$

R. S. Hunter⁶ gives an expression that approximates the ideal Value curve rather well:

$$\frac{V}{10} \sim Y \frac{.51(20 + 20Y)}{(1 + 20Y)} \quad (6)$$

This is plotted in Fig. 6. Although it provides excellent correction, it might be more difficult to use in color receivers than a simple exponential gamma correction.

Even though a gamma of 2.75 is not as good as 2.34 from the standpoint of noise, it may be close enough to the ideal curve to be acceptable.

Munsell Chromaticity: The relative importance and frequency of occurrence of the different colors has a bearing on the best way to transmit the chromaticity signal. Probably the colors of skin complexions are of most importance. Colors of low saturation are more common than those of high saturation; in fact,

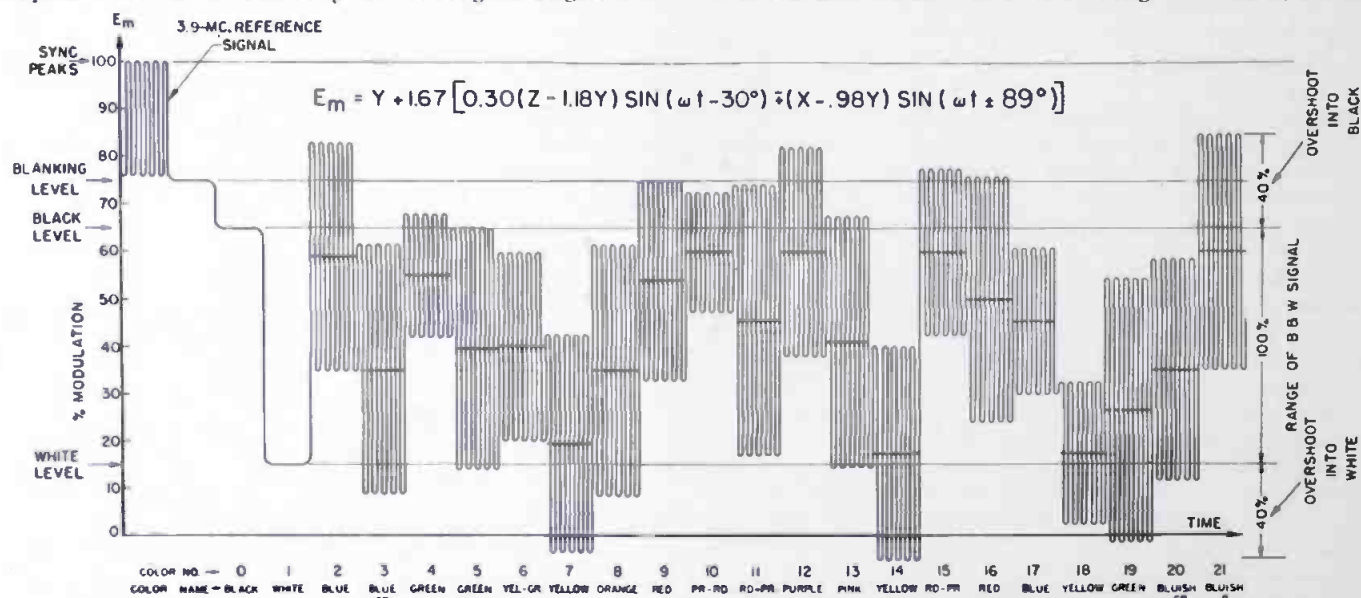


FIG. 5A. MODULATION ENVELOPE FOR VARIOUS COLORS WITH TENTATIVE NTSC STANDARDS. GAMMA IS 1. DC LEVEL, 3.9-MC. PHASE AND AMPLITUDE VARY

reproducible by a TV screen. Considerable study and experimentation^{7,16} has been done in an effort to obtain an ideal value scale. The Munsell Value scale is one result. Value is defined as the brilliance of the colors of a series of standards, varying in reflectance from zero to unity, in such a way that all the visual intervals are uniform. Munsell Value, V , is shown in Fig. 6 plotted as a function of Y . The curve does not obey any simple exponential or logarithmic law. An approximation is:

$$Y = 1.2219V - 0.23111V^2 + .23951V^3 - 0.021009V^4 + 0.008404V^5 \quad (4)$$

If it be assumed that a simple exponential relation is desirable for television, then it is obvious that $Y^{1/2.34}$, Fig. 6, gives a good approximation to the ideal straight line except at the lower end, near black. The curve $Y^{1/2.75}$ has been plotted also

some colors near the maximum demand contours occur very rarely. It is probably safe to assume that all hues are equally important and that they occur with equal frequency.

If it is assumed that all the Munsell colors are equally important, that they all occur equally often, and that noise should be equally perceptible for all colors, then the Munsell color system could, theoretically, be transmitted. That is, the average video level over .25 microsecond or more would be proportional to Munsell Value, the phase angle of the color subcarrier at 3.9 mc. would be proportional to Munsell Hue, and the amplitude of the color subcarrier would be proportional to Munsell Chroma. The modulation voltage might then be

$$E_m = M_v + M_c \sin(\omega t + 3.6 M_H) \quad (7)$$

where E_m is the modulation potential

M_v is the Munsell Value

M_c is Munsell Chroma

M_H is Munsell Hue (1 to 100)

¹⁵Frequency Analysis, Modulation, and Noise, by S. F. Goldman, McGraw-Hill Book Company, Inc., New York, Chapter VI; 1948.

¹⁶"Neutral Value Scales I, Munsell Neutral Value Scale", by A. E. O. Munse, L. L. Sloan, and I. H. Godlove, J. Opt. Soc. Am., 23, p. 394; 1933.

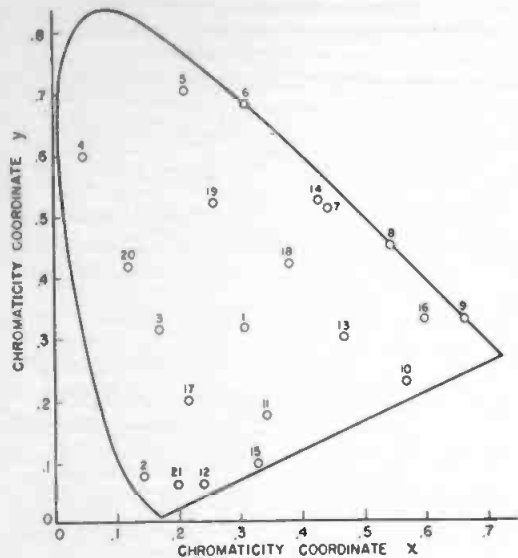


FIG. 5B, LEFT. THESE COLORS ARE TRANSMITTED BY CORRESPONDINGLY NUMBERED SECTIONS, AS SHOWN IN FIG. 5A

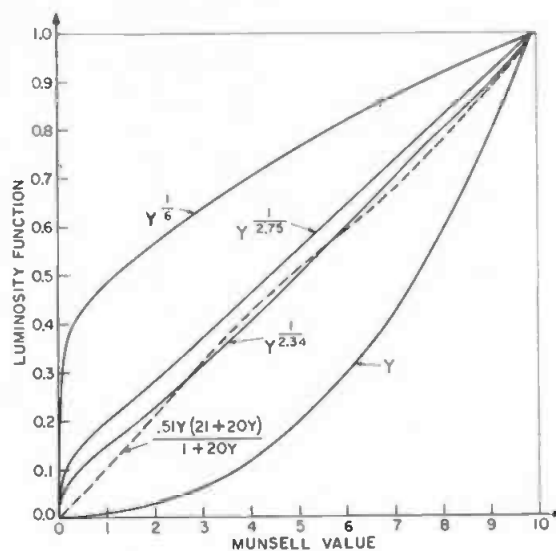


FIG. 6, RIGHT. HOW VARIOUS FUNCTIONS OF Y AFFECT THE LINEARITY OF THE LUMINOSITY SIGNAL-TO-NOISE RELATION

If the bandwidth of the chromaticity signal were a quarter of that of the luminosity signal, the RMS noise would be only half as much. Thus, the signal could be

$$E_m = M_V + .5 M_C \sin(\omega t + 3.6 M_H) \quad (8)$$

With such a signal, the noise in hue and brightness would be about equally noticeable, and chroma noise would be slightly less^{17,18}, about 1 db. At all brightness levels, noise would be equally perceptible; at all hues, noise would be equally perceptible; and at all saturations, noise would be equally perceptible.

It would probably be rather difficult to code color information into this form at the transmitter and to decode it into a usable form at the receiver. Also, it would not be practical to use a color subcarrier of such large amplitude because the modulation would extend too far below the white level, producing negative modulation.

CIE Chromaticity: The possibility of transmitting CIE chromaticity information alone on the color subcarrier has been suggested. Such a signal might be of the form

$$E_m = Y^{1/\gamma} + k(x \sin \omega t + y \cos \omega t) \quad (9)$$

where γ is the gamma used for the brightness
 k is a constant
 x and y are trichromatic coefficients
 ω is 2π times the frequency of the color subcarrier.

However, since x and y are always positive, the color subcarrier always lies in the first quadrant. A better system is obtained by translating the origin of the coordinate system to white, Illuminant C. The signal is then

$$E_m = Y^{1/\gamma} + k[(x - .310) \sin \omega t + (y - .316) \cos \omega t] \quad (10)$$

Means for generating such a signal at the transmitter and using it at the receiver have been worked out.¹⁹ A unique advantage of this method is that the luminosity and chromaticity components are completely independent. The signal disappears at white, and is relatively small at high luminosities because of the small area of the demand contour. At very low luminosities, on the other hand, the chromaticity signal for saturated colors is large, and the signal would extend into the blanking and sync regions. Chromaticity noise is less noticeable in dark regions than in light, because the eye is less able to detect chromaticity changes at low luminosities than at high luminosities. This is evident by comparing Munsell plots of low and high-Value colors, Fig. 4B.

The chromaticity signal can be made to decrease with decreasing luminosity by multiplying it by some function of luminosity. For example, suppose the signal

$$E_m = Y^{1/2.34} + 1.5 Y^{1/2.34} [(x - .310) \sin \omega t + (y - .316) \cos \omega t] \quad (11)$$

were transmitted. The constant in front of the chromaticity term was chosen such that the amplitude of the chromaticity signal is within reasonable limits. Fig. 7 shows how various Munsell colors are transmitted. All the colors at five dif-

¹⁹New Television Systems, by C. H. Jones, thesis for M.S. degree, University of Pittsburgh; 1951.

¹⁷"Colorimetry", by Deane D. Judd, National Bureau of Standards Circular 478; March 1, 1950.

¹⁸"Color Television Specification", by D. Nickerson and K. F. Stultz, *J. Opt. Soc. Am.* 34, p. 550; 1944.


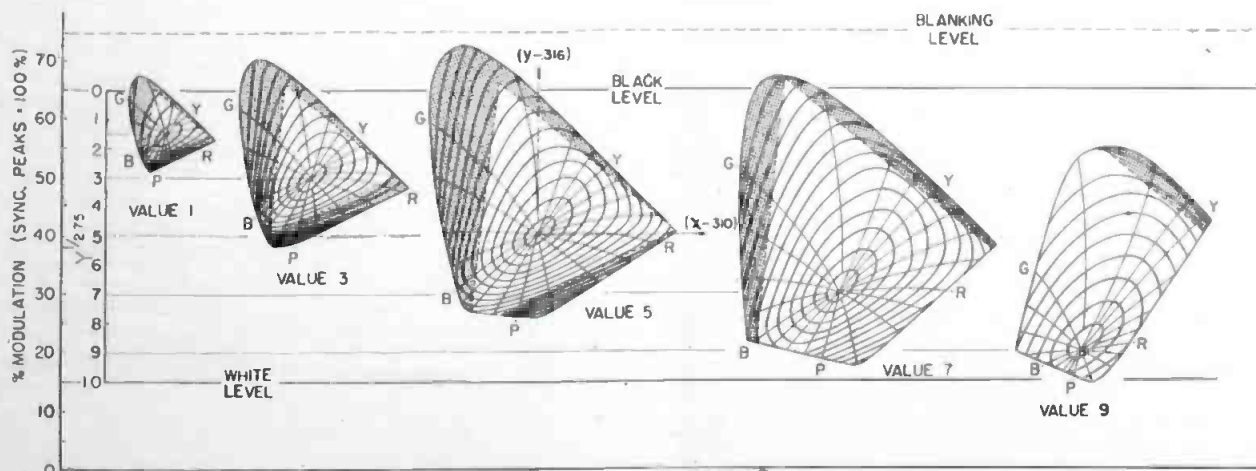


FIG. 7. DIAGRAMS OF COLOR SIGNALS TRANSMITTED IN ACCORDANCE WITH EQUATION 11. PLOTS ARE DRAWN FOR VALUES 1, 3, 5, 7, AND 9

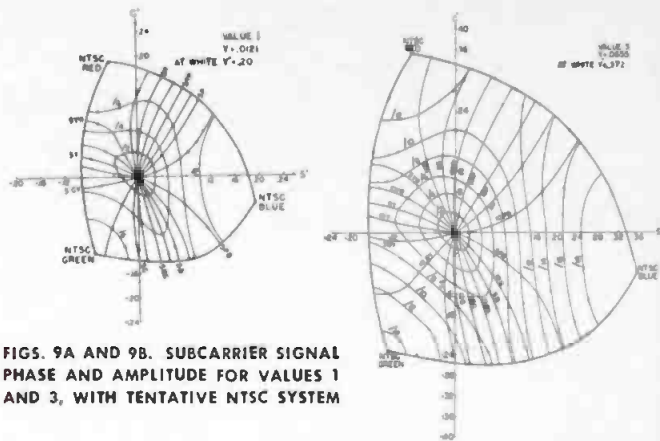

FIGS. 9A AND 9B. SUBCARRIER SIGNAL PHASE AND AMPLITUDE FOR VALUES 1 AND 3, WITH TENTATIVE NTSC SYSTEM

ferent brightness levels are illustrated. The amplitude and phase of any color can be found simply by drawing a vector from the center of the appropriate diagram to the color. Swinging this vector downward, it is easy to determine if the 3.9-mc. modulation would extend below the white level and, if so, by how much. Similarly, swinging the vector so that it points upward reveals whether or not the modulation would extend above the black level, and by how much.

Hunter's Alpha-Beta Diagram: The possibility of transmitting a transformed version of the ICI system should be examined. The general aim of such transformation¹² is to make the Munsell Chroma loci approach more closely a set of concentric circles, and to make the Munsell Hues have equal angular separations.


Dr. D. B. Judd has developed a three-dimensional figure to represent colors and to serve as a guide for estimating the perceptibility of color differences.^{5,17} A slightly modified form of this color solid could be used as a basis for transmitting a compatible color television signal. For a signal of the form

$$E_m = Y^{1/2.31} + 2.3 Y^{1/4} (\alpha \sin \omega t + \beta \cos \omega t), \quad (12)$$

the chromaticity portion inside the brackets is multiplied by the fourth root of Y. This has been done to make the diameter of the Munsell Chroma loci remain about constant as brightness varies from white to black.

The part of the signal inside the brackets represents the alpha-beta diagram developed by Hunter.^{20,21,22} These co-

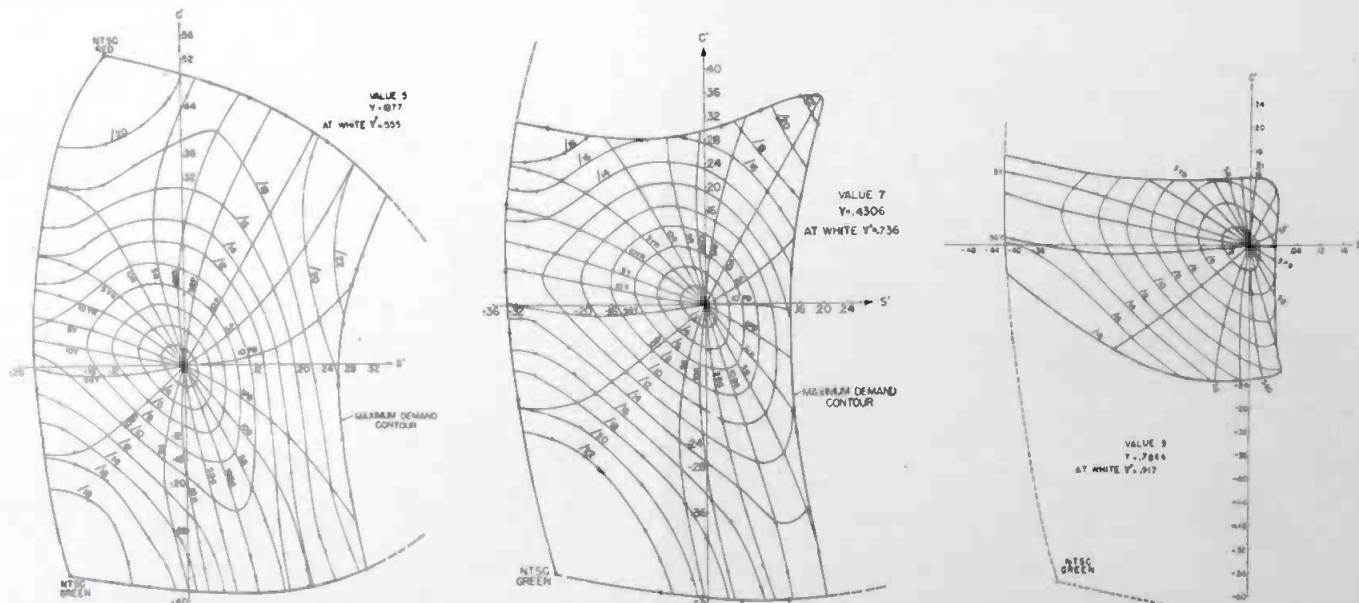¹²"Multipurpose Photoelectric Reflectometer", by R. S. Hunter, *J. Research NBS* 25, p. 581; 1940, RP1345; also *J. Opt. Soc. Am.* 30, p. 536; 1940.



FIGS. 9C, 9D, AND 9E. AMPLITUDE AND PHASE OF COLOR SUBCARRIER FOR VARIOUS COLORS AT VALUES 5, 7, AND 9, UNDER TENTATIVE NTSC SPECS

ordinates, Fig. 8, are related to the standard CIE chromaticity coordinates by the formulas:

$$\alpha = \frac{2.427x - 1.363y - 0.921}{1.000x + 2.236y + 1.105} \quad (13)$$

$$\beta = \frac{0.571x + 1.245y - 0.571}{1.000x + 2.236y + 1.105} \quad (14)$$

These signals could be obtained by using three color cameras with Hunter amber, green, and blue filters, and a matrix, since

$$\alpha \sim \frac{A - G}{A + 2G + B} \quad (15)$$

$$\beta \sim \frac{0.4(G - B)}{A + 2G + B} \quad (16)$$

where A, G, and B are the outputs of the amber, green, and blue cameras respectively.

NTSC Tentative Standards: Color field test specifications were released by the National Television Systems Committee on November 26, 1951.²³ The video voltage specified was

$$E_m = Y' + \frac{1}{1.14} \left[\frac{1}{1.78} (E'_B - Y') \sin \omega t + (E'_R - Y') \sin (\omega t \pm 90^\circ) \right] = Y' + S' \sin \omega t \pm C' \cos \omega t \quad (17)$$

The symbols S' and C' are used to denote the coefficients of the sine and cosine portions of the signal.

The luminosity part is defined by the equation

$$Y' = 0.59E'_G + 0.30E'_R + 0.11E'_B, \quad (18)$$

and the other terms are defined by these equations:

$$E'_G = E_G^{1/2.75} = (0.212W_G)^{1/2.75} = (-0.985X + 2.00Y - 0.028Z)^{1/2.75} \quad (19)$$

$$E'_R = E_R^{1/2.75} = (1.103W_R)^{1/2.75} = (1.908X - 0.531Y - 0.288Z)^{1/2.75} \quad (20)$$

$$E'_B = E_B^{1/2.75} = (0.699W_B)^{1/2.75} = (0.058X - 0.118Y + 0.896Z)^{1/2.75} \quad (21)$$

The chromaticities of the three primaries are plotted in Fig. 4A.

In order to examine more closely the transmitted signal, the

¹⁷"Photoelectric Tristimulus Colorimetry with Three Filters", by R. S. Hunter, NBS Circular C429; July 30, 1942.

²⁰"A Proposed Method of Designating Color", by F. Scofield, D. B. Judd, and R. S. Hunter, *ASTM Bulletin*, p. 19; May 1941.

²³National Television System Committee, Panel 13, Color Video Standards, "Report of Panel Actions"; 1951.

expression given in Equation 17 was evaluated for Munsell colors at various values by taking X, Y, and Z values from a table,⁷ and performing the indicated operations. The amplitude and phase of the color subcarrier are shown for Values 1, 3, 5, 7, and 9 in Figures 9A, 9B, 9C, 9D, and 9E. Constant Chroma and constant Hue loci have been plotted. The points marked were simply the calculated points, and have no special significance.

Equation 17 can be written in slightly different form:

$$E_m = Y' + .593E'_G \sin(\omega t \pm 119.4^\circ) + .632E'_R \sin(\omega t \pm 103.6^\circ) + .409E'_B \sin(\omega t \pm 12.4^\circ) \quad (22)$$

which, in terms of color weights of the primaries, becomes

$$E_m = Y' + .635W_G^{1/2.75} \sin(\omega t \pm 119.4^\circ) + .655W_R^{1/2.75} \sin(\omega t \pm 103.6^\circ) + .394W_B^{1/2.75} \sin(\omega t \pm 12.4^\circ) \quad (23)$$

If a color lies outside the triangle formed by the primaries, then W_G , W_R , or W_B will be negative. From Equation 23 it is evident that a negative quantity raised to the 1./2.75 power cannot be transmitted. A comparison of Figs. 4A and 9C illustrates this.

Since many colors near the maximum demand locus¹¹ seldom occur in practice, this limitation is not too serious. Examination of Fig. 9 reveals that the Chroma loci are not ideal circles, although at very low saturation levels they are reasonably round. As the saturation increases, the circles become more distorted until, near maximum saturation, many Chroma loci are almost parallel to the Hue loci. The diameters of Chroma² circles are about the same for all Values, and other Chroma loci also remain about the same size at different brightness levels.

TABLE 1

AMPLITUDE OF Y' FOR SATURATED COLORS

COLOR	MUNSELL VALUE				
	1	3	5	7	9
White	.200	.370	.554	.736	.916
NTSC Blue	.048	.090	.134	—	—
Cyan	.159	.295	.440	.584	—
NTSC Green	.144	.265	.402	.527	—
Yellow	.188	.345	.516	.685	.843
NTSC Red	.094	.172	.258	—	—
Magenta	.122	.209	.312	—	—

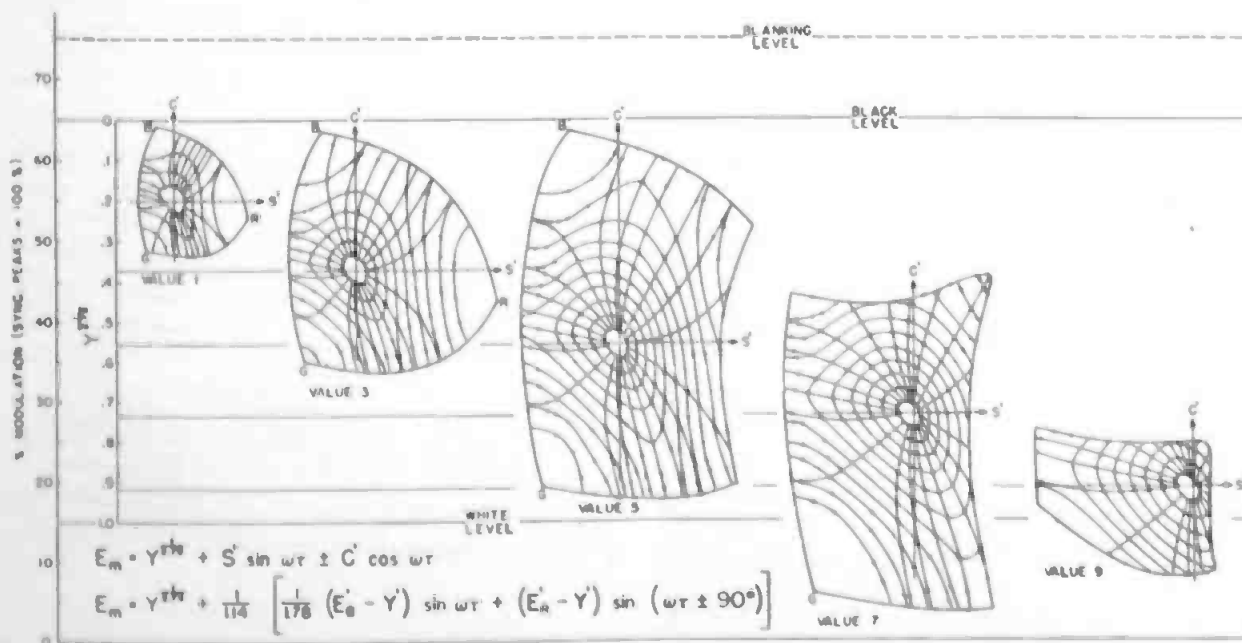


FIG. 9. THE DIAGRAMS OF FIGS. 9A TO 9E TRANSFERRED TO A TRANSMITTER MODULATION CHART. NO OVERMODULATION IS POSSIBLE

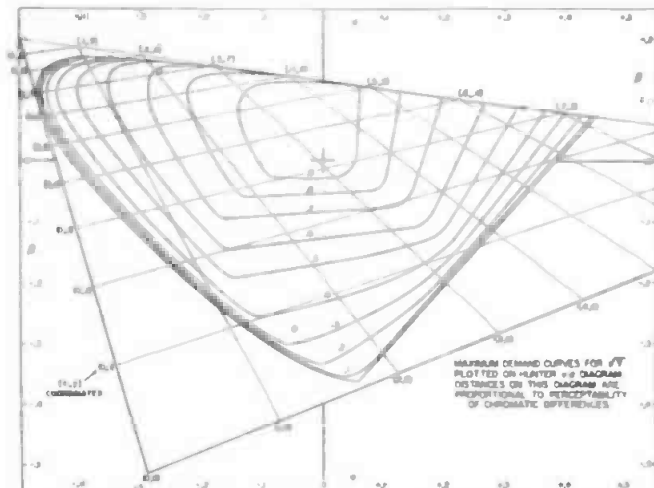


FIG. 8. DIAGRAM OF HUNTER'S ALPHA-BETA COLOR DESIGNATION SYSTEM

From the standpoint of noise performance, this is good. The spacing between Chroma circles is reasonably uniform, although it tends to become greater at high saturations. This is unfortunate, because high saturations are transmitted less frequently than low saturations.

For Hue loci, consider the Value 5 diagram in Fig. 9C. If the 20 Hues shown were spaced at equal angles, then the separation between adjacent Hues would be 18°. The angular separation between B5 and 10BG at Chromas up to 6 is about 9°. This means that the effect of noise is 6 db worse than it would be with uniform angular spacing. At high Chromas the angular separation is as low as 5.5° in some regions, so that noise is 10 db worse than ideal. Of course, there are regions where the angular separations are quite large, and noise in those regions has little effect on hue.

The equations shown in Fig. 9F indicate an average level of $Y'^{1/2.75}$ rather than Y' . For all shades of gray along the neutral axis, the two quantities are equal. At all colors of low saturation the two are almost equal²⁴; Y' is a little less than $Y'^{1/2.75}$. At high saturations, however, there can be considerable differences between the two, as shown in Table 1.

Modified NTSC Signal: The distorted shape of the NTSC color solid is determined in considerable measure by the way in

²⁴"Gamma Correction in Constant-Luminance Color Television Systems", by S. Applebaum, a paper presented at the 1953 IRE Convention, New York.

which the gamma is applied to the chromaticity portion of the signal. Suppose that Equation 17 is rewritten, assuming a gamma of 1 applied to the color part of the signal and a gamma of 2.34 applied to luminosity:

$$E_m = Y^{1/2.34} + \frac{1}{1.14} \left[\frac{1}{1.78} (E_B - Y) \sin \omega t + (E_R - Y) \sin (\omega t \pm 90^\circ) \right], \quad (24)$$

which can be written as¹³

$$E_m = Y^{1/2.34} + 1.67 \left[.030 (Z - 1.18Y) \sin (\omega t \pm 30^\circ) + (X - .98Y) \sin (\omega t \pm 89^\circ) \right] \quad (25)$$

or

$$E_m = Y^{1/2.34} + 1.67Y \left[.30 \left(\frac{Z}{Y} - 1.18 \right) \sin (\omega t \pm 30^\circ) + \left(\frac{X}{Z} - .98 \right) \sin (\omega t \pm 89^\circ) \right] \quad (26)$$

Note that the terms inside the brackets contain only chromaticity information. A plot of the Munsell colors using this equation reveals that half the Hues are squeezed into two 60° sectors, while the other half are in the other two 120° sectors. Therefore, the phase of one term should be shifted 29° with respect to the other in order to improve the angular spacing of the Munsell Hues. The amplitude of the first terms are thereby slightly increased, also, which makes the Chroma circles more nearly round. This yields:

$$E_m = Y^{1/2.34} + kY \left[\frac{1}{3} \left(\frac{Z}{Y} - 1.18 \right) \sin \omega t + \left(\frac{X}{Y} - 0.98 \right) \sin (\omega t \pm 90^\circ) \right], \quad (27)$$

where k is an arbitrary constant.

Such signal is very similar to one suggested by F. J. Bingley³ some time ago. If Munsell colors are plotted on a color solid based on this equation, it is found that the Chroma circles for low brightness are smaller than the same Chroma plots

for high brightness. This situation can be remedied by applying an exponent to the Y coefficient of the term in brackets, which does not distort the chromaticity diagram at all. The modulation signal would then be

$$E_m = Y^{1/2.34} + .56Y^{1/2.34} \left[\frac{1}{3} \left(\frac{Z}{Y} - 1.18 \right) \sin \omega t \pm \left(\frac{X}{Y} - .98 \right) \cos \omega t \right] = Y^{1/2.34} + S \sin \omega t \pm C \cos \omega t \quad (28)$$

where S and C are simply the coefficients of the sine and cosine portions of the signal. The constant 0.56 was chosen rather arbitrarily to make the diameter of the Chroma circles, Fig. 10, roughly the same as those in Fig. 9F. Provided that colors more saturated than the NTSC primaries need not be transmitted, this constant can be increased by 50%. Even then the modulation does not go as low as zero nor as high as blanking level. A 3.5-db improvement in chromaticity signal-to-noise ratio can be realized. Plots of the Munsell colors for transmitting this sort of a color system are shown in Fig. 10. It is evident that the spacing of the Hue angles is quite uniform. As illustrated in Fig. 6,

$$Y^{1/2.34} \sim \frac{.51Y(21 + 20Y)}{(1 + 20Y)}, \quad (29)$$

so that Equation 28 bears a close resemblance to the Hunter alpha-beta color solid.

Conclusions: The present NTSC proposed system is a fairly good one from the standpoint of noise effects on brightness and chromaticity. The signal-to-noise ratio for brightness would be improved slightly by employing a gamma a little lower than 2.75. The chromaticity signal-to-noise ratio can be improved appreciably by adjusting the amplitude and phase of the three color components, and by applying the gamma to the Y coefficient of the chromaticity part of the signal rather than to the individual parts of the chromaticity expression. This would also permit transmission of a wider range of colors, and would remove the limitation on primaries for use at the receivers.

The author wishes to thank L. Johnson and C. Carpenter for their calculations to obtain data for the figures and table.

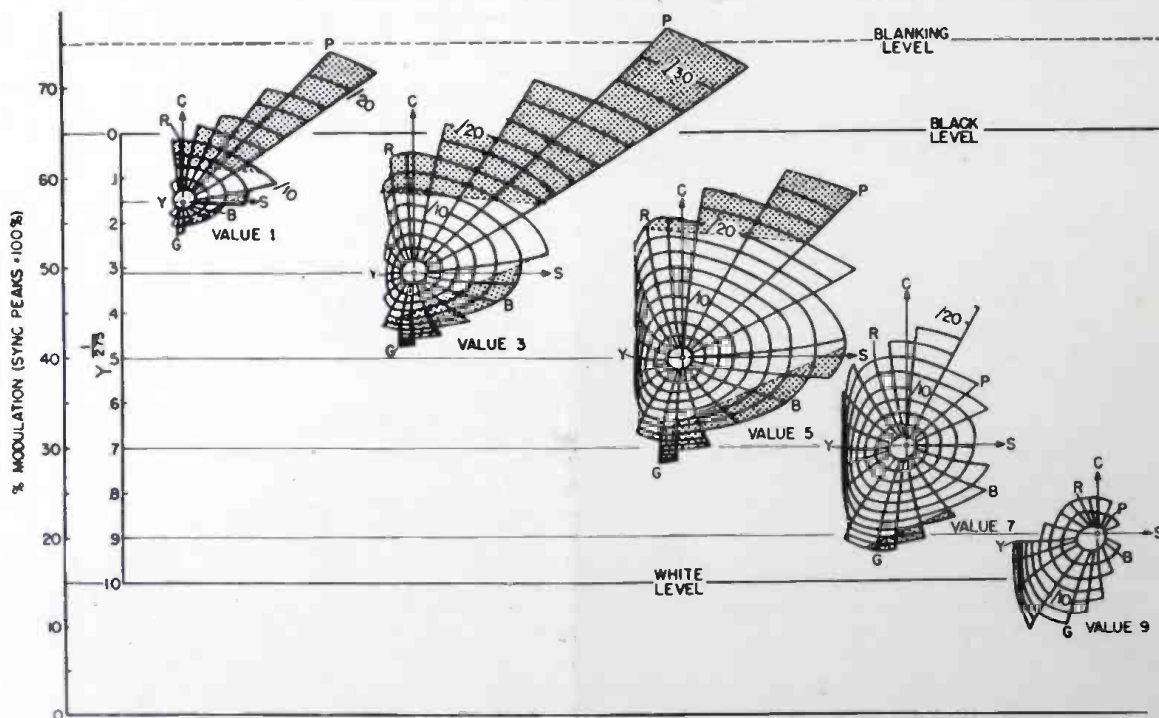


FIG. 10. PLOTS OF MUNSELL COLORS FOR 5 VALUES USING A MODIFIED VERSION OF THE NTSC COLOR SPECIFICATION

Report on Spurious Radiations

A RESUME OF INDUSTRY PROGRESS AND PROJECTED PLANS FOR REDUCTION OF SPURIOUS RADIATIONS FROM FM AND TV RECEIVERS AND TRANSMITTERS

AN industry-wide meeting on the problems of spurious radiations from FM and TV receivers and transmitters was held at the Hotel Biltmore, New York City, on January 9, 1953. The meeting was called by Dr. W. R. G. Baker, director of RTMA's Engineering Department. Members and non-members of RTMA in the radio and television industry were invited, and the Joint Technical Advisory Committee.

Genesis of the meeting was a letter from the FCC to JTAC, requesting that body to study the problem of interference from spurious radiation, which information the FCC would use in determining methods and limiting values for its regulatory functions. Ralph Bown of JTAC then wrote to Dr. Baker, asking for information on RTMA views concerning the practical problems of the spurious-radiation situation, and any operating or proposed plans for establishing standards and performance limits to keep interference from spurious radiations within "sound engineering bounds." The January 9 meeting was called in order to review what has been done by the industry since initiation of the 41.25-mc. IF standard, determining the progress to date; to impress on the industry the seriousness of the problem and its own responsibility; and to appoint task forces on transmitters and receivers to guide future progress.

Standard IF Frequency: I. J. Kaar, chairman of RTMA Receiver Committee R4, gave a brief talk on the work of his committee with regard to the standard television IF. He reviewed the history of the old standard IF, 21.25 to 21.9 mc., which was not entirely satisfactory. When the FM band was moved to its present range, consideration was given to the 40-mc. band for a new television IF. In 1949, the RTMA adopted 41.25 mc. for the sound IF as a new standard. Experience has shown, said Mr. Kaar, that this is a better choice than the old standard. Manufacturing costs are about the same. Interference to TV receivers using the new IF, however, can be caused by high-power state police transmitters. This fact, in addition to natural reluctance to discard a debugged design, has prevented the adoption of the new IF by some manufacturers.

Oscillator radiation from sets using a 41.25-mc. IF can interfere with FM broadcasting, some air services, amateurs, and some government bands. However, no IF choice can eliminate all interference if local oscillators are permitted to radiate to an unreasonable extent, Mr. Kaar pointed out. The proper solution to the interference problem lies in 1) limiting oscillator radiation as much as is practical, and 2) insuring that services interfered with use reasonably adequate transmitter power.

Progress Since 1950: Chairman L. M. Clement of the RTMA Receiver Executive Committee reported on previous spurious-radiation recommendations and the degree to which they have been followed.

On Sept. 12 and Nov. 19, 1950, meetings of FCC and RTMA personnel were arranged as the result of a proven case of FM receiver radiation interference with an air VOR system in Indiana. A resolution was adopted which stipulated the following limits on radiation effective June 30, 1951:

- FM — 50 microvolts/meter at 100 ft.
- TV, Channels 2-6 — 50 microvolts/meter at 100 ft.
- TV, Channels 7-13 — 150 microvolts/meter at 100 ft.

An IRE subcommittee has set up standards for such measurements.

Subsequent tests showed that these limits were adequate for protection to VOR systems, which operate sometimes with signal levels of 1 microvolt/meter.

A report of progress made by manufacturers toward meeting the RTMA recommendations, which was sent to the FCC on Oct. 7, 1952, showed the following figures:

	TV CHANNELS 2-6		TV 7-13		FM	
	WITHIN LIMITS	OUTSIDE LIMITS	IN	OUT	IN	OUT
1950 Sets	2	23	1	24		
1951 Sets	20	5	18	7	2	17
1952 Sets	23	4	19	8	12	2

At about the same time, the FCC sent a letter to RTMA expressing concern about increasing evidence of problems arising from oscillator and sweep-circuit radiation from VHF and UHF receivers and converters, and receiver spurious responses. The letter emphasized again the importance of adequate spurious-radiation suppression, and the use of the standard IF. UHF oscillator radiation was discussed at a meeting of the RTMA Committee on Radio Interference on Oct. 20, 1952, and limits of 500 microvolts/meter at 100 ft. were proposed for all UHF-TV equipments. Radiation from typical UHF units is considerably in excess of that value at the present time, as the following table shows:

		UHF OSCILLATOR RADIATION, MICROVOLTS/METER AT 100 FT.	
		AVERAGE	MAXIMUM
Converter	1	820	1,290
	2	550	980
	3	600	900
	4	1,180	1,400
	5	5,000	9,500
	6	500	820
	7	760	1,490
	8	2,180	4,400
	9	3,200	6,270
	10	1,900	2,560
Receiver	1	2,500	6,000
	2	360	615
	3	2,750	6,270
	4	1,310	2,260
Tuner	1	1,800	4,600

A continuous program of checking on performance is planned.

At the same meeting, interference from high-power state police transmitters was discussed. Interference is serious now in some areas, and it is expected that more trouble will be experienced as new TV stations begin operation. There are authorized presently some 46 five-kw. police transmitters, 5 ten-kw. transmitters, and 10 one-kw. transmitters, in 12 states. It is for this reason primarily that some manufacturers have been reluctant to employ the 41.25-mc. IF. Of 34 manufacturers replying to a questionnaire, 17 used the old IF in all 1952 receivers, 8 used the new IF in some 1952 receivers, and 9 used the new IF in all sets produced late in 1952.

Twenty-seven expect to use the new IF in 1953 sets. Of the 17 major manufacturers, 4 used the old IF in all 1952 sets.

Concluded on page 36

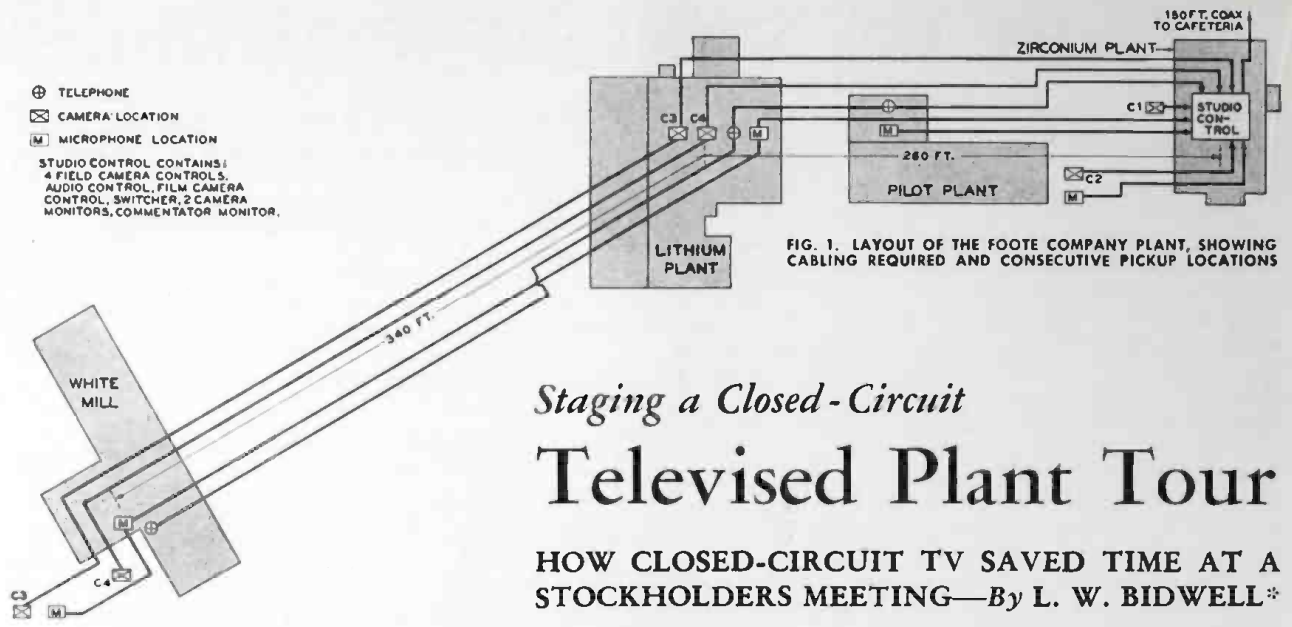


FIG. 1. LAYOUT OF THE FOOTE COMPANY PLANT, SHOWING CABLING REQUIRED AND CONSECUTIVE PICKUP LOCATIONS

Staging a Closed-Circuit Televised Plant Tour

HOW CLOSED-CIRCUIT TV SAVED TIME AT A STOCKHOLDERS MEETING—By L. W. BIDWELL*

MOST owners of television receivers are quite aware of the great potentialities of TV broadcasting for entertainment and education. It is common knowledge also that this medium has affected profoundly the American living pattern. Less well-known, however, is the fact that non-broadcast or closed-circuit television can provide services just as valuable and significant to our way of life. The field of potential applications is so broad that it can be encompassed only by the most general descriptive terms, i.e., wherever efficiency would be increased by some means to display a scene or event to many persons at one time, or to show an event occurring at some inconvenient or dangerous location. Closed-circuit systems are being used now in many industrial and research applications, and more uses are being found every day. A typical application of this equipment was the recent televised plant tour for a stockholders' meeting at the Foote Mineral Company in Exton, Pennsylvania. Because many unusual problems had to be solved for this project, it is described and shown in the photographs on these pages.

Plan of Operation: The physical layout of the Exton factory is diagrammed in Fig. 1. Four separate plants and the cafe-

*Press Division, RCA Victor, Camden, New Jersey.

teria, where the stockholders' meeting was held, stretch out over an area of 81 acres. Since there were over 250 at the meeting, it would have been a gigantic task to conduct the entire group on a tour through the factory. Instead, a closed-circuit TV system was set up to show the stockholders new facilities and key operations at widely-separated locations by means of television sets placed at strategic points in the cafeteria.

The idea of the TV tour originated with Robert Drake, Foote's advertising manager, who saw RCA's see-yourself television demonstration at the 23rd Exposition of the Chemical Industries in New York. He discussed the possibilities with Richard Hooper, manager of the Shows and Exhibits Division of RCA Victor's Public Relations Department, and Douglas Deakins, of Mr. Hooper's staff. Detailed plans, charts, and script were then worked out by Messrs. Drake, Deakins, and Otto Renner, Jr., of Renner Advertisers, who handle the Foote account. Television, they reasoned, would obviate the expenditure of effort, the inevitable confusion, and the inconvenience involved in taking a large body of people over long treks through the plant from one key installation to another. As it turned out, it also afforded the stockholders a clearer and more concise picture of the operation of their company than they could have obtained by making a physical tour.

FIG. 2, BELOW: SOME OF THE EQUIPMENT IN THE STUDIO CONTROL SETUP



FIG. 4. L. G. BLISS, AT THE COMMENTATOR'S DESK, PROVIDED CONTINUITY



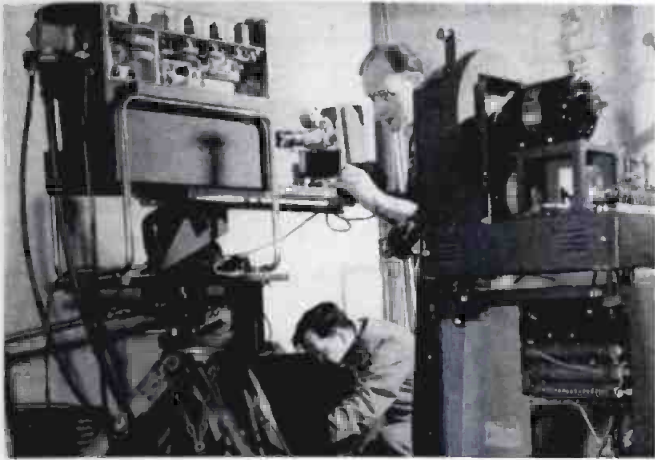


FIG. 3. FILM OF NORTH CAROLINA PLANT WAS INTEGRATED INTO PROGRAM

Four image orthicon field cameras, twelve 17-inch home-type receivers, 1,800 ft. of 24-conductor camera cable, 1,200 ft. of microphone line, a TV film camera chain consisting of a 16-mm. film projector and an iconoscope film-pickup TV camera, and field equipment required for a complete control and monitoring station, were used on the project. Total value of the installation was more than \$80,000.

Ten receivers were mounted on stands about 6 ft. high and lined up around three sides of the meeting room, and the other two were placed in an adjoining coattroom to take care of the overflow audience. The field cameras were set up in four strategic locations. Fig. 1, and a carefully charted plan of movement, integrated with the script and bound to precision timing, permitted coverage of seven plant locations without interruption of the show.

The power supply, monitor and control units for each camera, a switcher and fader with its own power supply, and a sync generator were installed in the zirconium processing plant building, near the cafeteria. This is shown in Fig. 2. Also located in this building were the TV film camera chain, Fig. 3, and the narrator's desk, Fig. 4, which was covered by one of the field cameras. From this point L. G. Bliss, Foote's vice president in charge of sales, supplied the commentary and introductions that tied together the remote pickups making up the show.

The equipment installation and the staging were handled by a crew of eight, including six RCA Service Company engineers led by Frank Helgeson, and two members of the RCA Victor shows and exhibits group — Mr. Deakins, as producer, and G. E. Ryan, his assistant. Members of this group have pioneered new applications of television and demonstrated the medium throughout the United States and in many foreign countries.



FIG. 7. ONE OF THE OUTDOOR SCENES, BEING COVERED BY TWO CAMERAS

Special Problems: Chief problems encountered in the Foote project, Mr. Helgeson said, were the necessity for stringing a total of about 3,000 ft. of cable and microphone line, most of it overhead; split-second timing of camera movements, which meant shutting down a camera, moving it to a new location, and putting it back in operation without the customary allowance for warm-up time; and quick shifts from indoor to outdoor light levels, and vice versa, with little time for camera adjustment.

Nothing could be done about warm-up time, but the problem caused more worry than difficulty, since all four cameras performed extremely well without it. The problem of compensation for varying light levels was met by supplementing quick lens adjustments with electrical compensation. A camera operating in one of the plant buildings with the lens


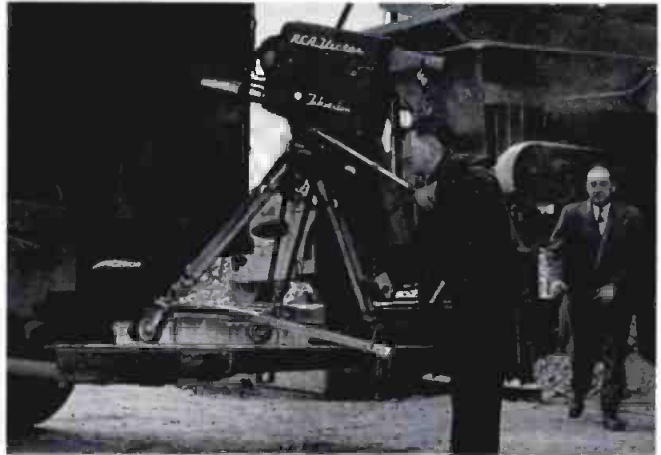


FIG. 5, ABOVE: CAMERAS WERE MOVED BY TRUCK WITH A HYDRAULIC LIFT

FIG. 6, BELOW: ROBERT DRAKE, FOOTE ADV. MGR., DESCRIBING ORE PROCESS

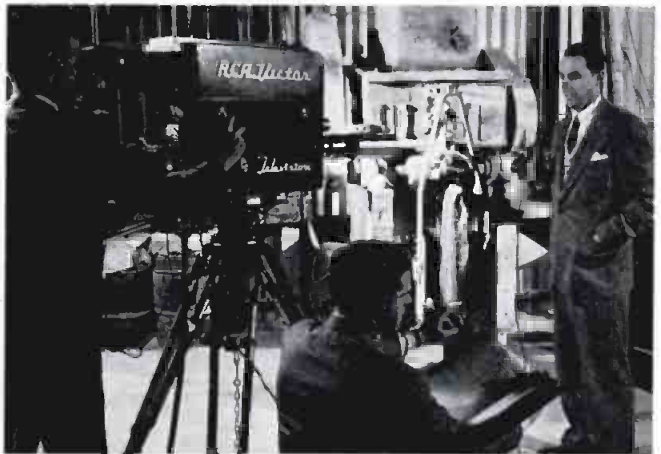

adjusted to f:5.6, for example, would be moved hastily to an outdoor location and stopped down to f:22. When this was found insufficient, the control operator would compensate for excessive highlights by adjusting the target voltage.

Target voltage adjustment was accomplished at the control station if it was observed that objectionable highlights persisted in the monitor image after the lens adjustment had been made. In such instances, the operator at the camera control would adjust the target voltage toward cutoff until the highlights were reduced satisfactorily. The effect of this measure was to reduce the flow of electrons away from the target in the pickup tube, thus reducing the intensity of the charge pattern on the target and, in turn, limiting the modulation of the beam which generates the signal.

It was pointed out that target voltage adjustment for such

Continued on page 38

PATTERN FOR TV PROFIT

PART 6—MICROWAVE EQUIPMENTS FOR NETWORK HOOKUPS, MOBILE PICKUPS, STUDIO-TRANSMITTER LINKS, AND OTHER POINT-TO-POINT APPLICATIONS

By Roy F. Allison, in collaboration with A. B. Chamberlain, Rodney D. Chipp, Raymond F. Guy, Thomas E. Howard, and Frank L. Marx*

A TELEVISION station manager may be confronted with any or all of 4 operating problems which make necessary the transmission of program material over relatively long distances outside the studio or transmitter building. First, it is probable that interconnection is desired between the nearest network access point and the station master control. Second, where studios are located in widely-separated buildings, some special means must be provided to bring the remote studio originations to master control. Third, wherever mobile pickup units are used by the station, their program originations must be sent to the master-control point. Finally, if the transmitter is not at the same location as the master control, the two must be interconnected.

Facilities for such interconnections may be installed and operated by the station, the AT&T Long Lines Department, or the local telephone company, depending on a number of circumstances. Although the telephone companies may find it

*Collaborators are, respectively; Chief Engineer, CBS Television, New York; Director of Engineering, DuMont Television Network, New York; Manager, Radio and Allocations Engineering, NBC, New York; Chief Engineer, WPIX, New York; and Vice President in charge of Engineering, ABC, New York.

advisable to use either coaxial cable or point-to-point radio links, the private operator does not, in general, have this choice. He is restricted by practical considerations to microwave radio equipment. This fact, combined with the circumstances involved in each application, determines the best solution to each interconnection problem.

Network Connections: Most connections to intercity network lines are installed and operated by the telephone company concerned, although some stations do operate private facilities. Cost is a major consideration here, particularly when the station is situated at some distance from an available AT&T terminal or relay station.

When making negotiations with a network (or networks) the station may decide to install its own link to the nearest city served by the AT&T system, which involves an appreciable expenditure on its part but which has long-term advantages. Alternatively, the network may arrange for the connection, dealing with the local telephone company or, if an intercity link is required, with AT&T. Terms of agreement between the network and the station may vary according

to the market served by the station, by its competition, and other local factors.

Remote Studios: Especially at the larger stations, and those which originate network programs, one or more permanent studios may be required in addition to those available at the main studio and control building. In New York, for instance, the networks have taken over several theatres for large-scale TV productions. Such remote studios can be connected to the master-control headquarters by lines leased from the local telephone company or by private short-hop microwave circuits installed permanently. The choice is dependent on long-range plans for the remote studio, by the availability of line-of-sight paths between such studios and control-center buildings, by the time of availability of coaxial lines, and other economic factors.

Mobile Pickups: Remote pickups using field equipment are usually of great programming value, and are extremely important to the successful operation of even small stations. As was pointed out previously, however, extra operating personnel, equipment, and maintenance costs are involved.

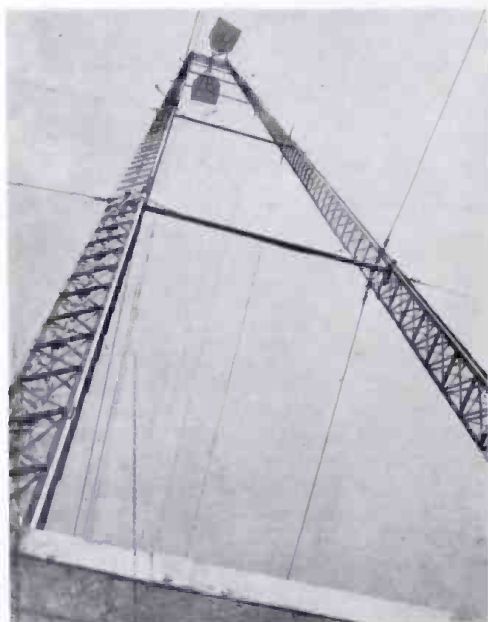


FIG. 1. MOTOROLA MICROWAVE REPEATER TOWER.

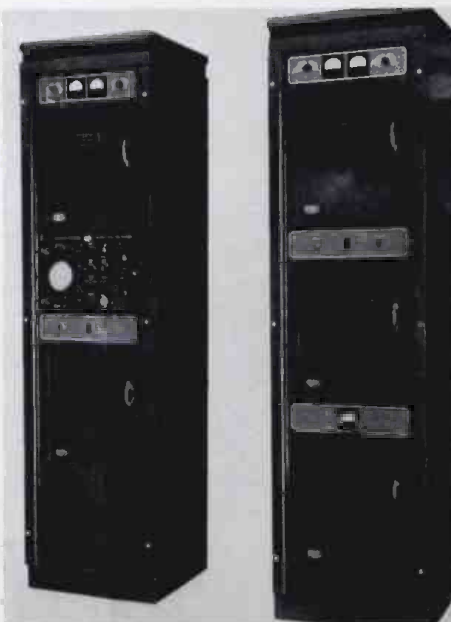


FIG. 2. DUMONT LINK EQUIPMENT FOR FIXED INSTALLATIONS.

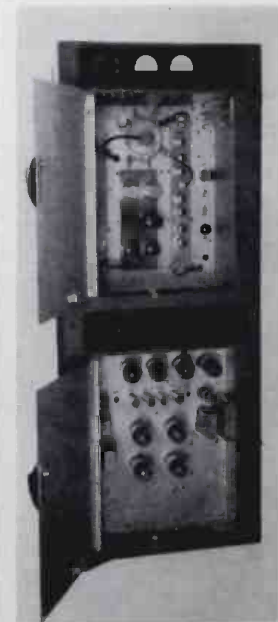


FIG. 3. FEDERAL MICROWAVE RECEIVER

Many scheduled events of local interest can be covered by remote-pickup equipment without a mobile microwave link, since the telephone company can often provide the required facilities if they are requested far enough in advance. However, for on-the-spot news coverage, pickup of events requiring camera mobility, and for general flexibility and versatility, microwave equipment is invaluable. Probably the most important advantage of the portable radio link is the mobility it provides, permitting pickups from anywhere within its operating range that the TV field equipment can be carried on short notice.

Whenever it is possible to do so, the site of the proposed remote pickup should be tested before the broadcast to determine that satisfactory operation of the link can be obtained. Also, as will be explained later, relay link equipment may or may not be capable of handling the audio part of a pickup. If it is not, arrangements must be made with the telephone company to obtain a telephone line for the audio. This can usually be made available with much less delay than a coaxial line, of course. Preliminary planning and survey work is always advisable when the time is available for it, in order to avoid unforeseen difficulties.

Studio-Transmitter Links: As with other point-to-point connections, this service can be handled privately or by the local telephone company. Basis of the choice seems to consist primarily of the relative desirability of a large initial expenditure and the maintenance of a private link or a long term of line-charge payments.

Link Equipment: Because it is quite likely that a station will require at least one microwave link circuit in its daily operation, descriptions of the equipments available for these applications are given in the following section.

FCC frequency allocations which became effective July 1, 1949, provide 3



FIG. 5. TWO VIEWS OF A MOTOROLA 7,000-MC. TRANSMITTER-RECEIVER-ANTENNA COMBINATION UNIT

specific operating ranges for TV remote-pickup and studio-transmitter links. They consist of the following frequency bands:

- 1,990 to 2,110 mc.
- 6,875 to 7,125 mc.
- 12,700 to 13,200 mc.

Commercial equipments are available which operate in the lowest two bands. All utilize frequency modulation of the carrier, and klystron tubes in the transmitter output stage. All except one are designed for either mobile or fixed application, and all can be used in multi-hop applications; that is, where the distance to be covered is too great for a direct transmitter-to-receiver path, additional units can be used as intermediate repeater stations.

The links are used with parabolic reflector antennas which provide extremely high power gains. The actual power

from the transmitter in the 2,000-mc. band may be from 5 to 10 watts. At these frequencies, the gain obtainable from a 4-ft. parabola is 25 db; from a 6-ft. parabola, 29 db. Since these antennas are normally used at both receiving and transmitting locations, the effective radiated power is at least 500,000 watts if the two antennas are aimed precisely at one another! Thus, distances up to 45 miles may be covered by these equipments.

There is a distinct disadvantage to such high power gains in that the antennas must be aimed with great accuracy, because the radiated beams are so narrow. For that reason, separate voice communication channels must be provided on remote pickups so that the operator at the transmitter end of the link can adjust his antenna for maximum signal strength at the receiver, in accord-

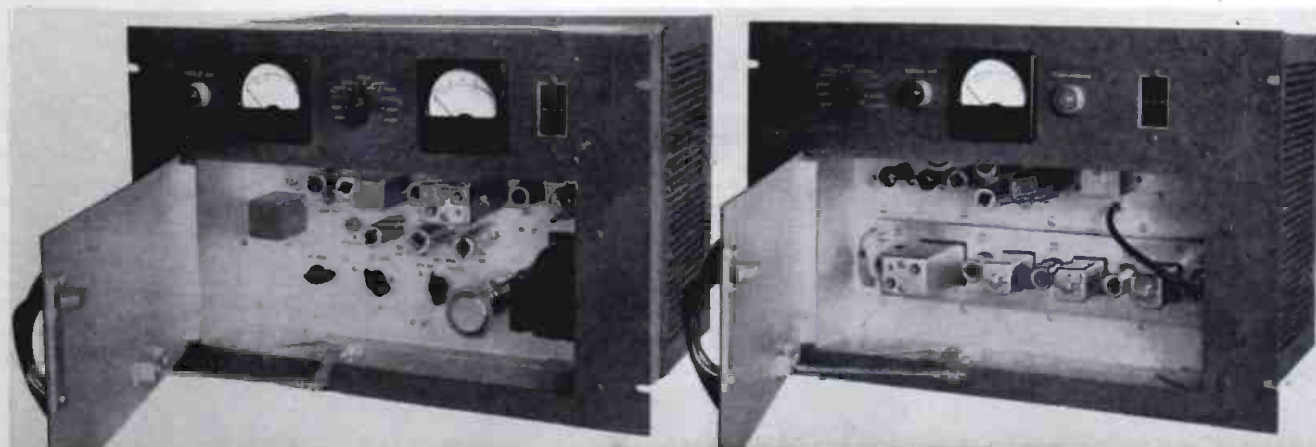


FIG. 4. SUBCARRIER TRANSMITTER AND RECEIVER UNITS PERMIT SUPERIMPOSITION OF AN AUDIO SIGNAL ON A STANDARD VIDEO MICROWAVE CHANNEL

ance with instructions from the receiver operator. Antenna mountings must be easily and precisely adjustable over wide ranges in order that aiming can be accomplished quickly and smoothly. When the receiving antenna is mounted in an inaccessible location, such as on the station transmitting antenna tower, a remote positioning device must be utilized. Four-ft. parabolas are ordinarily used on mobile installations. The 6-ft. models have considerably more gain, but are much heavier, more unwieldy, and have narrower beams, so that aiming is a good deal more difficult.

The preceding considerations point up the desirability of making preliminary surveys at sites of proposed mobile pickups, wherever possible. With equipment for the 7,000-mc. band, transmitter outputs are lower and antenna gains even higher.

Where direct line-of-sight paths are not available, it is often practical to use towers on permanent or semi-permanent installations for repeater or terminal stations. The towers may be large enough to mount the equipment at the top, or passive 45° reflector antennas can be employed, as in Fig. 1. The transmitter or receiver antenna, or both in the case of a repeater, are aimed directly upward at the reflector, which is then positioned so that the beam is reflected toward the remote antenna.

Low-Band Units: Links for the 2,000-mc. range is available from DuMont and Federal. Fig. 2 shows the DuMont fixed-station receiver on the left and the transmitter on the right. Both are equipped with metering facilities for all tubes. The transmitter has equipment for measurement of frequency and power output, and output waveform. A built-in test oscillograph can be provided on the receiver rack, and test signal sources for system lineup are included. The Federal receiver can be seen in Fig. 3. Both



FIG. 6. AN RCA MOBILE MICROWAVE LINK UNIT. THE TRANSMITTER IS IN CYLINDRICAL HOUSING

types of equipment can be furnished in mobile cabinets.

These units are designed basically for video transmission. Audio subcarrier modulator and demodulator sections can be added, however, as shown in Fig. 4. They can be obtained in portable carrying cases also.

7,000-Mc. Links: Motorola and RCA link equipments operate in the 7,000-mc. band. The Motorola transmitter-receivers, shown from two angles in Fig. 5, are designed for fixed installations only. The video signal is applied directly to the RF modulator. Separate subcarriers are

used for the audio program signal and a 2-way service channel or order-wire channel.

RCA equipment is quite compact and portable, although it can be used at fixed locations, of course. The transmitter, as shown in Fig. 6, is located in a cylindrical enclosure directly behind the parabolic antenna. A small, portable control unit, Fig. 7, is connected to the transmitter and provides for the necessary operating adjustments. The receiver is similar in operation and appearance. Fig. 8 shows the receiver chassis removed from its cylindrical cover.

Costs: Total cost of microwave link equipment required for a single hop may range from \$15,000 to \$20,000. This includes transmitter, receiver, control and test units, antennas, cabinets, and transmission lines. If sound channel equipment is provided, those figures may be increased by about \$5,000. Multi-hop systems will cost more, of course, although not in direct multiples of the single-hop cost. For mobile installations, the vehicle may cost from \$3,000 to \$10,000 or more, in addition. Camera chains, other video equipment, and audio pickup equipment are not included in these figures.

Microwave link equipment for TV applications can be obtained from the following sources:

Allen B. DuMont Laboratories, Inc., 1500 Main Avenue, Clifton, New Jersey.

Federal Telecommunication Laboratories, Inc., 500 Washington Avenue, Nutley, New Jersey.

Motorola, Inc., Communications & Electronics Division, 4515 Augusta Blvd., Chicago 51, Illinois.

RCA Victor, Engineering Products Division, Camden, New Jersey.

EDITOR'S NOTE: This concludes the "Pattern for TV Profit" series, which will be published soon in revised and expanded form as a book.

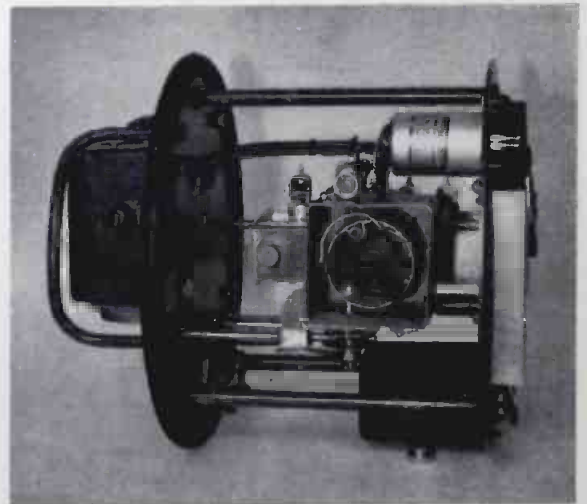


FIG. 7. RCA MICROWAVE TRANSMITTER CONTROL UNIT. FIG. 8. RECEIVER CHASSIS, DESIGNED SAME WAY AS TRANSMITTER, WITH SIMILAR CONTROL UNIT

Head-End Design for FM Tuners*

A DETAILED ANALYSIS OF THE PROBLEMS ASSOCIATED WITH THE DESIGN OF FM TUNER HEAD-ENDS, WITH PRACTICAL SOLUTIONS — By H. H. CROSS**

This paper is based on a B.S. thesis in the Department of Electrical Engineering, M.I.T. 1952

Abstract

The design of signal-frequency and frequency-changing sections of narrow-band VHF superheterodyne receivers for the FM broadcast band is analyzed. It is shown that, since noise factor varies inversely as the power efficiency of the input network, any finite-Q input network must compromise between noise factor and selectivity. For a given number of tuned circuits, the best arrangement is one which utilizes one tuned circuit for the input network and the rest to obtain interstage selectivity.

Mixer operation is considered, and the optimum adjustment is found to be relatively low oscillator injection combined with RF gain sufficient to make the amplifier input noise one to ten times the power of the noise generated in the mixer tube.

Tuners built in accordance with these principles are described briefly. Experimental data show that their performances compare favorably with those of medium-frequency receivers.

Introduction: The fundamental task of any receiver is to receive one and only one station at a time. In superheterodyne receivers, the task of separating two signals differing by only a small increment of frequency is made easier by changing the desired signal, along with its interference, to lower fixed frequencies, for which fixed-tuned amplifiers and selective networks can be used. Most of the signal amplification occurs in this intermediate frequency (IF) amplifier.¹

A major disadvantage of this system is that the converter circuits tend to change several discrete frequencies to the IF frequency, while only one is wanted. Selective circuits, therefore, are ordinarily used between the antenna and the converter. One or more RF amplifier stages may be used also. The selective circuits are supposed to pass the desired signal and attenuate the undesired signals which may appear on the spurious-response frequencies. In the usual case these spurious-response frequencies are separated from the desired signal by at least half the IF frequency so that, if the IF frequency is not too small a fraction of the signal frequency, several sharply-tuned circuits accomplish this separation fairly well.^{2,3}

This paper describes the development and construction of a tuning head suitable for use in a high-performance receiver for reception of FM broadcasts. The rest of the receiver was designed by Roy Paananen. A discussion of the basic problems peculiar to the FM broadcast band in metropolitan areas will be found in his thesis.⁴

Design Considerations: Once the IF frequency and required performance are determined, the receiver design can be resolved into sections. For instance, the gain of the RF section

is determined by the overload level of the mixer, not by the signal level the designer of the IF amplifier would prefer at its input; and the level of audio from the IF portion is determined by the limiter and detector circuitry, not by what is convenient in an audio system.

The plan of attack was to build the best receiver we could with components which were at least potentially adaptable to mass production or, better yet, used widely in present-day commercial equipment. In the event that the resulting performance was more than adequate, it should have been possible to effect economies in cutting back. On the other hand, if we had underestimated the problem, the extra performance would be available. The best justification for this procedure lies in experience in the communication field, where it is often found that only the over-designed unit is left when others have been rendered obsolete by ever-worsening channel congestion. It turned out that the best we could do was about right. Tests show that most commercial units are annoyingly deficient, by comparison, in one respect or another.

The intermediate frequency was fixed at 10.7 mc. Better control of selectivity in the IF amplifier can be obtained by using a lower frequency; however, spurious-response frequencies are separated more widely from the desired signal with a high-frequency IF. The RTMA standard frequency is quite suitable as a compromise.

It was decided to use an ordinary transformer-rectifier power supply, providing low-voltage AC for the tube heaters and 225 volts DC for the plate supply. Most low-level tubes give full performance with plate potentials of 100 volts or more, but there seemed to be no reason for conserving power and there were some advantages to be obtained from the higher B+ value.

For best receiver performance the limiters should limit well, but the selective circuits should be free from overload. This requires high maximum gain for weak signals and, in order to prevent overloading on very strong signals, some automatic gain control must be used. Provision for bias control of gain was made accordingly in this tuning head.

Some other tentative requirements were: Input suitable for unbalanced 75-ohm lines; less than 30 kc., or .03%, frequency drift during warm-up; FM noise 60 db below full program modulation, or about 50 cycles RMS; gain of tuning head, as high as seems practicable; tuning range, 88 to 108 mc. with some to spare; little variation of gain as the receiver is tuned through the range; sensitivity at least as good as any commercial receiver; reasonably low oscillator radiation; low spurious responses, few in number; and reasonable size and cost. A tuning head meeting the spirit of these specifications should be quite satisfactory.

Tuned-circuit components of the best design can be expected to have warm-up drifts corresponding to the linear expansion coefficients of the materials. Compensating capacitors commercially available have temperature coefficients of the same order of magnitude. Permissible warm-up drift is 300 parts per million, however, so that a change of from 10 to 20°C. will be required to give this drift, if compensation is correct plus or minus the usual commercial tolerances. By individual adjustments, the compensation can be made much closer.

*This work was supported in part by the Signal Corps, the Air Material Command, and the Office of Naval Research.

**Research Laboratory of Electronics, Massachusetts Institute of Technology, Cambridge, Mass. Mr. Cross is now with Pickard and Burns, Needham, Mass.

¹"General Superheterodyne Considerations at Ultra-High Frequencies," L. Malter, *IRE Proceedings*, Oct. 1943.

²*Radio Receiver Design*, K. R. Sturley, London, Chapman & Hall Ltd., 1943, Ch. 5.

³*Vacuum Tube Circuits*, L. B. Arguimbau, John Wiley & Sons, 1948, p. 422.

⁴M.I.T. Electrical Engineering Thesis, 1952, Roy Paananen. This will be published in TV & RADIO ENGINEERING in a forthcoming issue.

To keep oscillator noise at least 60 db below program level, the FM on the oscillator must be limited to 50 cycles RMS or 75 cycles peak. The way to obtain this performance is simple: build a good oscillator, make it mechanically and thermally stable, and supply it with well-filtered plate voltage. In some cases, filtered DC might be required for the heaters. Then the only source of noise would be the tube itself, as even a poor oscillator will be hum-free if supplied only from batteries.

The author has had some experience with oscillators in the VHF range which employ modern high-transconductance miniature triodes in Colpitts' circuits,⁵ Fig. 1. The grid-cathode condenser, C2, is made as large as possible without stopping the oscillations at low line voltage, in order to adjust the feed-back to optimum and to keep the influence of the rather variable input capacitance on the tuned circuit as low as possible. The FM hum in such an oscillator at 100 mc. can be much less than ten cycles when AC is used to heat the cathode. F. B. Llewellyn⁶ has shown that plate and grid lead inductances in a Colpitts oscillator can be arranged to reduce the shifts in frequency with changes in tube voltages. This may be considered a point in favor of this arrangement, as lead inductances are appreciable at VHF. Lea⁷ has shown that it is not possible to neglect the resistance-temperature coefficient of copper if the tuned circuit is not operating at true resonance. Any measures which decrease the stray detuning effects of parasitic elements better the stability. Colpitts or ultra-audio circuits will oscillate at true resonance at VHF.

Gain obtained in the tuning head should be fairly high, so that less gain is required in the IF amplifier. But strong signals when amplified may overload the mixer stage, even though the receiver is not tuned to them. Thus, there should not be too much gain.⁸ This is a true dilemma, and it will be considered in detail later.

The FM broadcast band is narrow in tuning ratio; its range of 1.23:1 in frequency requires only 1.5:1 variation in tuning inductance or capacitance. Because the mechanical action of a multisection variable capacitor is better and smoother than that of most inductance-tuning devices, capacitance tuning was used in this design.

Amplification should be kept as nearly constant as possible throughout the band, for the lowest gain may limit the sensitivity, while the point of highest gain will be more subject to overload on strong signals. Tracking errors vary the gain as a function of tuning frequency, but any single-range receiver can be made to track very well by bending the plates of the tuning capacitor slightly.

In some receivers, the gain is not sufficient for proper limiting action on weak signals; in others, capable of proper limiting, sensitivity is determined by the noise generated internally which is strong enough to mask signals below a certain strength. The average commercial receiver falls in the first group, as it is neither simple nor inexpensive to build a receiver having an overall power gain (in the absence of limiting) from antenna to detector of 130 db. 100 db must ordinarily be provided by the IF stages.

The experimental tuners were designed on the assumption that the receivers should have enough gain for proper limiting on input-circuit noise. In such a case, the weakest usable signal is determined by the signal-to-noise ratio of the first stage or stages of the receiver, and care should be taken to see that this section has the proper characteristics for good sensitivity. Practically, it is possible to build a receiver which,

with a directive antenna of reasonable size, will provide good-quality reception of 1 to 5-microvolt-per-meter signals, in the absence of any local noise sources outside the receiver. This would be an ideal design for perhaps 5% of the people likely to buy FM receivers. But to obtain this sensitivity, almost everything else important to the other 95% would have to be sacrificed. Therefore, it is believed that special cases should be accommodated by adding some sort of low-noise preamplifier to a well-designed receiver.

Oscillator radiation from FM and television receivers has become a source of annoyance, and some effort has been made to reduce this effect in recent commercial products. One or two RF amplifiers with tuned interstage coupling circuits give attenuation of oscillator energy in the reverse direction sufficient so that, with proper shielding and filtering, the leakage is tolerable.

Oscillator radiation may affect the frequency stability also. It is found that those receivers which have excessive radiation

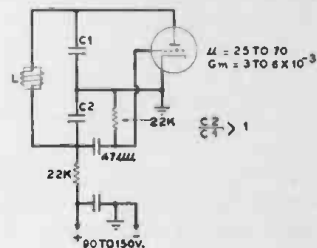


FIG. 1. A VHF OSCILLATOR DESIGNED FOR VERY STABLE OPERATION & LOW FM HUM

become detuned slightly when the antenna or antenna feeder is moved about, as by the wind, when the input circuits are adjusted, or even when a hand is put near them.

A dozen or more receivers of various makes were tried out for spurious responses. Some were tested in detail, and measured performances were compared with subjective ratings. The tests were made with a reference level of 10 microvolts RMS in 300 ohms, and a maximum generator output 92 to 98 db higher, roughly equivalent to a field strength of .25 volt per meter. One receiver was installed in an automobile; it was found that almost everywhere in the greater Boston area there is a possibility of spurious-response trouble from very strong signals, while the desired signal may be fairly weak on the average and may occasionally drop to zero because of destructive reflections.

Only one commercial receiver tested was judged to be adequate in this test. However, it still showed some repeat tuning points when tested in a private home which was two miles from the nearest transmitting station. Stations outside the FM band do not give the same degree of annoyance. They can be trapped or filtered out, if need be, and are not so powerful as the broadcast transmitters, so that lower limits can be put on the susceptibility of the tuner to out-of-band spurious pickup. The experimental units showed us what could be done.

Keeping costs down in commercial production is often accomplished at the expense of performance. This is more prevalent in the radio industry than, say, in the automobile business. The features immediately apparent to the customer are the logical place to spend development money. Since, in the case of a well-designed tuner the proof of performance is what is not heard, why bother? On the other hand, there is often room for improvement in the utilization of circuits already in the equipment. The rejection of spurious responses can sometimes be much improved by small changes, without appreciable degradation of either noise figure or net useful sensitivity.

The Input Circuit: From the foregoing survey, the reduction of spurious tuning points seems to be the major problem in tuner design. This checks the observation that most commer-

⁵"A Cascade Converter for 144 Mc.," H. H. Cross, *QST*, Oct. 1949.

⁶*Bell System Technical Journal*, F. B. Llewellyn, Jan. 1932.

⁷"Notes on the Stability of LC Oscillators," Norman Lea, *Journal I.E.E.*, Vol. 92, pt. III, Dec. 1945.

⁸"Adjacent Channel Operation of Mobile Equipment," D. E. Noble, *Electronics*, June, 1949, p. 90. Also "Adjacent Channel Rejection Receiver," H. Magnusky, *Electronics*, Jan. 1951, p. 100.

cial receivers are deficient in this respect to some extent.

If cost were of no importance, almost any desired degree of protection could be obtained by preceding the first tubes in the receiver with some sort of tunable filter which would offer high attenuation to undesired signals, while passing the proper ones with much less attenuation. This is actually a possibility because, for the case of an IF frequency less than one-fourth the signal frequency, the first spurious response point of importance is separated from the desired signal by one-half the IF frequency or, in this case, 5.35 mc.^{2,3} A filter at the signal

adds attenuation, then the noise figure of the system will be the noise figure of the receiver times the reciprocal of the power efficiency of the network. A 6-db noise figure for the receiver alone is changed to 16 db when a 10-db attenuator is inserted ahead of the RF stage.

This suggests that a low-noise receiver should be designed for high tank and coupling-circuit power efficiencies. For best efficiency, high-*Q* selective circuits should be employed. They should be loaded by the antenna resistance until their working *Q*'s are fractions of the unloaded values. Because typical

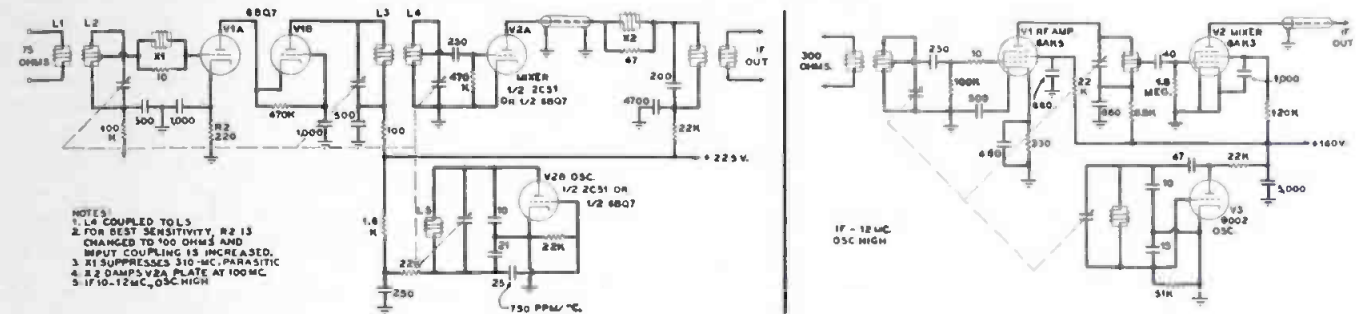


FIG. 2, LEFT: THE 4-GANG TUNING HEAD. FIG. 5, RIGHT: A 3-GANG EXPERIMENTAL TUNING HEAD. NOISE FIGURES ARE 12 AND 20 DB, RESPECTIVELY

frequency consisting of two loosely-coupled circuits, the *Q* of each being 100, provides about 40 db discrimination between desired and spurious responses, but the desired signal will be weakened also. As a practical matter, it is not possible to make such a filter in small size at reasonable cost without considerable attenuation of the desired signal.

Unfortunately, there is a limit to the attenuation that can be tolerated.^{9,10} An FM signal contains many frequencies, so that a finite band of frequencies must be passed in its transmission and reception. For any band *B* cycles wide, a resistor at temperature *T* (degrees Kelvin) delivers a thermal noise power $P = E^2/R = kTB$ when suitably matched, or twice the square root of $kTRB$ volts open-circuit for a resistance of *R* ohms. This is true also of any circuit components which introduce loss, and of antenna radiation resistance, where *T* is the temperature of the region with which the antenna is in thermal equilibrium. In these formulas, *k* is Boltzmann's constant, 1.38×10^{-23} watts per cycle-degree. If *B* is 2×10^5 , as for an FM broadcast receiver, a 50-ohm resistor will produce about 0.4 microvolts RMS at ordinary temperatures. If the receiver were otherwise free of noise, a 2 microvolt or .02 microwatt signal would be received satisfactorily in the absence of any other noise interference. An actual receiver we have tested did as well with 6 microvolts open-circuit RMS.

Rather than microvolts sensitivity at some particular bandwidth and impedance level, it is convenient to use a dimensionless number, first proposed by D. O. North,⁹ known as the noise factor. This is the ratio of the noise power from an actual receiver to that from an otherwise identical noise-free receiver, measured at a point in the system before any overloading or nonlinearity occurs. This noise factor, or noise figure, can be measured directly or indirectly by several methods.¹¹ It provides an absolute basis for comparing the performances of sensitive receivers.

Since any receiver has some noise originating in the first stages, a weak signal which is attenuated further by going through a lossy network will not be relatively so noise free after amplification. In general, if inserting the network, assumed to have rather more bandwidth than the receiver as a whole, does not disturb the impedance relationships but only

ganged resonant circuits have unloaded *Q* values of 100 to 200, however, this procedure makes them tune so broadly as to be useless for discrimination against the spurious response frequencies.

If a *Q* of 100 per tuned circuit is assumed, with an interfering signal removed in frequency by 5%, the performances of a few simple input-circuit configurations are as shown in Table 1. The rest of the system is assumed not to load the network, and to be adjustable to a noise factor of 4 (6 db).

TABLE 1

PERFORMANCES OF SIMPLE INPUT NETWORKS

CIRCUIT ARRANGEMENT	OVERALL NF	ATTEN. 5% dNF	OFF FREQ.
1—Single-tuned, ideally mismatched	6 db	0 db	0 db
2—Single-tuned, matched	9	3	14.2
3—Double-tuned, both mismatched	6	0	0
4—Double-tuned, pri. mismatched, sec. matched	9	3	14.2+
5—Double-tuned, pri. loaded to half <i>Q</i> by ant., sec. coupled to half <i>Q</i> _w L	12	6	27.4
6—Single-tuned, loaded to 3/4 <i>Q</i>	12	6	17.6
7—Single-tuned, virtually unloaded	very poor	(do.)	20

For best signal-to-noise ratio, cases 1 and 3 are best. If both sensitivity and selectivity are desired, some compromise is necessary. For a given noise figure increment, 5 gives more selectivity than 6, though at greater cost. Economically, the choice is between 1, 2, and 5.

The figures in Table 1 suggest that, in order to obtain much selectivity from the antenna coupling circuits, some sensitivity must be sacrificed.

In calculating the table above, it was assumed that loading of the tuned circuits by the first tube could be neglected. This is not quite true, in general, and is particularly in error at frequencies around 100 mc. For grounded-grid operation of the

⁹"The Absolute Sensitivity of Radio Receivers" D. O. North, *RCA Review*, Jan. 1942.
¹⁰Also *IRE Proceedings*, H. T. Friis, July, 1944.
¹¹*Vacuum Tube Amplifiers*, E. J. Schremp, McGraw-Hill Book Co., 1948. Vol. 18 of the MIT Radiation Laboratory Series.
¹²*Vacuum Tube Amplifiers*, Y. Reers, Ch. 14.

first tube, the optimum source impedance may be about 600 ohms, while the input impedance may be some 400 ohms. With a 6AK5 pentode, the input impedance will be 8,000 to 12,000 ohms at 96 mc.,^{12,13} and the optimum source impedance for best noise figure, some 1,900 ohms.^{12,14} In the first case, loading is severe, and in the second, it is about 20%. The cascode circuit, in which a 6AK5 might be used as a triode, would have an optimum source impedance on the order of 800 ohms. The loading effect would be around 10%.¹⁴

If a grounded-grid stage is not employed, then Table 1 is reasonably valid. The unloaded impedance of the tuned circuit would be around 5,000 ohms. If it were matched, as in the second case, the impedance across its terminals would be 2,500 ohms. A pentode RF stage, using a 6AK5, would have a grid connection to the top terminal. When the coupling is arranged so as to provide the maximum gain, the source impedance will be about optimum. If a triode stage or connection were utilized, the grid lead might be tapped down on the tuned circuit to obtain the desired grid-to-cathode impedance. The voltage applied to the grid would be reduced, of course, but the noise from the stage would decrease proportionally more than the signal.¹⁵

For a 3-db deterioration in noise figure, the single-tuned matched input circuit appears to be a reasonable compromise between cost and selectivity. This is the circuit most used at the input of VHF receivers. Two tuned circuits at the input do very little better in attenuating the response at 5% off-frequency, unless a further loss of sensitivity is permissible. For signals off-tune by 20% or more, however, this is not true. For cases in which circuit losses are so low that power efficiency is good at working *Q* values of 50 or 100, there may be an advantage in adding selective circuits between the antenna and the first tube, since the loss of sensitivity is not then appreciable; on the other hand, more benefit can invariably be derived by adding more resonant circuits to the interstage couplings.

Because the cost per gang-tuned circuit is fairly high, and for the same expense the extra tuned circuits might be used

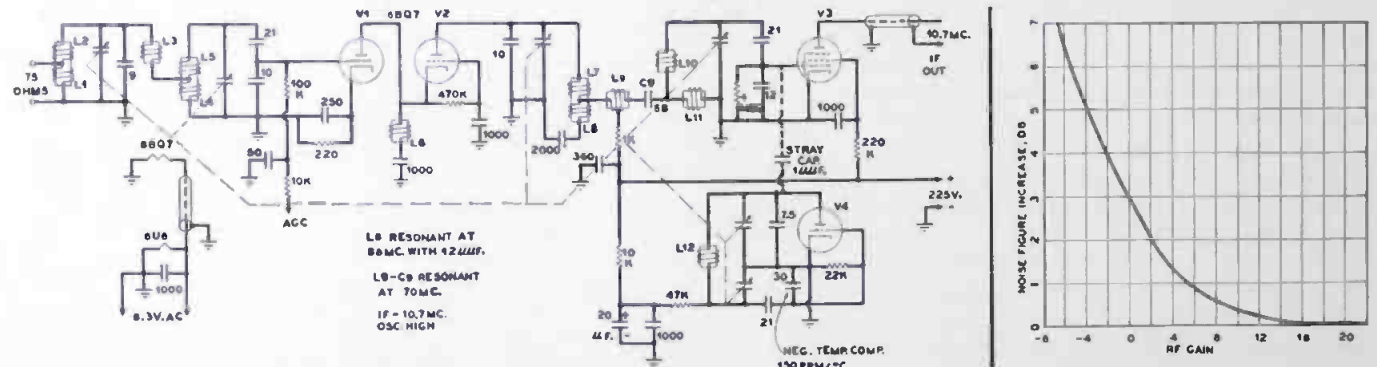


FIG. 3, LEFT: 6-GANG EXPERIMENTAL TUNING HEAD. FIG. 4, RIGHT: NOISE FIGURE INCREASES ABOVE INPUT STAGE NOISE WITH DECREASING RF GAIN

as interstage RF couplings, where they would contribute to the RF selectivity without degrading the sensitivity, a double-tuned input circuit is not ordinarily worthwhile. If signals far off the desired frequency are likely to overload the first tube, the most practical means of protecting a receiver with a narrow tuning range is passive wave filters inserted between the antenna and the receiver. Experimental data supports these conclusions, as will be shown later.

The Input Tube: The following points should be considered

¹²"Characteristics of Vacuum Tubes for Radar Intermediate Frequency Amplifiers," G. T. Ford, *B.S.T.J.*, XXV, 1946. Also "The Radar Receiver," L. W. Morrison, *B.S.T.J.*, Oct. 1947.
¹³*Introduction to Television Receiver Design*, Philco Corp., Vol. I, 1951, p. 100.
¹⁴*Vacuum Tube Amplifiers*, R. Q. Twiss and Y. Beers, Ch. 13, esp. p. 645.
¹⁵"An Analysis of the Signal-to-Noise Ratio of Ultra-High Frequency Receivers," E. W. Herold, *RCA Review*, Jan. 1942, esp. eq. 10.

in the selection of a tube for the RF stage: First, if the input circuits are gang-tuned, tube loading lowers the selectivity at that point, and tends to handicap spurious-signal rejection. Second, the noise figure obtainable with low-cost tubes. Third, the tube screening, which not only limits the maximum stable gain¹⁶ but controls oscillator radiation as well. Finally, the overload point, and the possibility of bias control of gain.

A grounded-grid triode is ruled out by the first consideration, as explained previously. The second restricts the choice to types developed for the television market. The third excludes neutralized triodes, other than the cascode, and the fourth suggests a direct-coupled cascode or a pentode with a screen-dropping resistor.

It is well known that a pentode tube is less noisy when connected as a triode amplifier than when operated as a pentode, if the plate current is the same in each case. Also, with low load impedances, a triode can handle the same grid swing as an equivalent pentode for a given amount of distortion. Because the noise generated by the triode is lower, and the overload point the same, the triode has a greater useful dynamic range.

If the noise figure is 10, there are about 1.2 microvolts equivalent open-circuit noise at a 50-ohm input. Transformed to a grid impedance of 800 ohms, this would be about 4.8 microvolts for a bandwidth of 200 kc. Signals weaker than this are masked by noise.

For grid-cathode structures similar to that of the 6AK5, including the 2C51, 6N4, and 6BQ7, the third-order characteristic curvature is tolerable over a grid range of 2 to 3 volts for 100 volts on the screen and plate. About 1 volt RMS is the overload point, then, if a bias slightly higher than normal is used. The dynamic range is then about 100 db. More plate voltage would increase the permissible bias and signal.

Because of the advantage with respect to noise and overloading, it was decided to use a triode in the RF stage. Other factors, as explained earlier, suggested some sort of cascode circuit, consisting of a grounded-cathode stage driving a grounded-grid stage. The arrangement described by Cohen¹⁷

was tried initially. The neutralizing condenser had to be omitted, and it was found that adding an inductor to tune out the stray capacitance in shunt with the plate of the first section gave a slight improvement in sensitivity, about 1 db. Another db could probably be obtained by tuning out the grid-to-plate capacitance of the first triode,¹⁸ but this inductor is less convenient to add in the series arrangement, and there is no room for it.




The 6BQ7 was considered to be nearly ideal for our purpose since it was reputedly designed on the basis of the grid-cathode structure employed in the 6AK5. Previous tests of various tube-types in the first stage of a cascode amplifier at 145 mc. showed that types 6AK5 and 6AS6, triode-connected, had no-

¹⁶*Microwave Receivers*, A. B. MacNee, McGraw-Hill, 1948. Ch. 5, p. 126. Vol. 23 of MIT Radiation Laboratory Series
¹⁷"Use of New Low-Noise Twin Triode in Television Tuners," R. M. Cohen, *RCA Review*, March 1951.

tably lower noise figures than those tubes having circular-cylinder elements such as the 6BH6 or 6AU6, or the wider-spaced 6AG5, 6CB8, or 6AH6, all circuit-connected as triodes. The 6BQ7 is rated for use in the Cohen series circuit, wherein relatively high voltage may appear across the heater-to-cathode insulation of the second triode section. Finally, in the series circuit, the 6BQ7 has reasonably good bias-control characteristics.

In the Paananen receiver⁴ automatic gain control voltage is applied to the RF stage and to the 6AU6 first IF amplifier. A design precept for the IF system was that no overloading

FIG. 6, LEFT: SENSITIVITIES OF THE 4 AND 6-GANG TUNERS WITH SAME IF AND DETECTOR. FIG. 7, CENTER: RF SELECTIVITY FOR 4 TUNED CIRCUITS. FIG. 8, RIGHT: TUNING HEAD FOR CAR RECEIVER

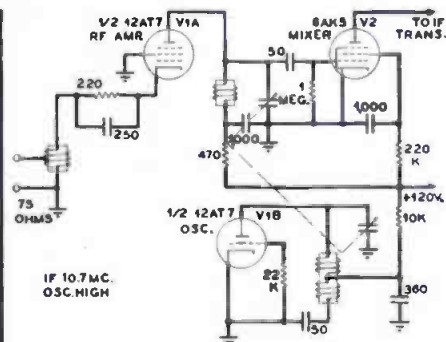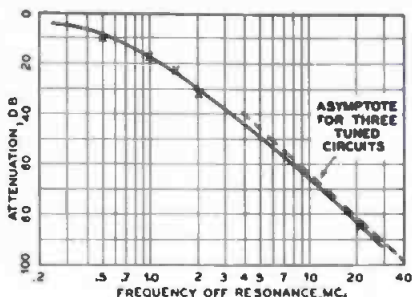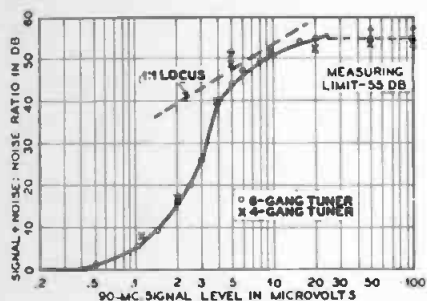

was to take place within the selective portion of the receiver, while the limiters were to have wide bandpass and very short time constants, so as to provide proper capture of a signal only slightly stronger than noise or interference.¹⁰ The range of gain control required in these two stages is approximately the same as the voltage gain from RF grid to the grid of the last IF amplifier. This is on the order of 60 db. In practice, satisfactory operation as planned was achieved over the usual range of signals. The AGC voltage is not effective on weak signals, and tests showed no significant change in signal-to-noise ratio on weak or moderate-strength signals with AGC on or off.

The values in Table 1 were based on the assumption that the first amplifying tube together with the remainder of the receiver could be adjusted to a net noise figure of 6 db. Cohen, for instance, reports this value measured on a television tuning head which used a cascode circuit with a 6BQ7 dual triode.¹⁷ There have been more sensitive receivers made for those frequencies.^{5,9,18,20} Presently available tubes appear to limit the performance at 100 mc. to a noise figure of about 2.3, or 3.6 db.^{18,21}

Two experimental tuners were built: a 4-gang unit, Fig. 2, and a 6-gang unit, Fig. 3. The sensitivity of each was poorer than would be expected from Table 1, for the following reasons: 1) tuned-circuit shunt loss from the fairly high-capacity input circuits lowered the efficiency; 2) the neutralizing circuits, and, in the 4-gang model, the plate coil, were omitted; 3) the gain of the RF section was kept low intentionally, so that the mixer noise was not negligible; 4) the plate supply voltage was lower than that of Cohen's circuit, and the 6BQ7 was operated at lower plate current, with resulting lower transconductance. The sensitivity could be improved by changing any of these factors, but this would involve a sacrifice in simplicity, spurious-signal rejection, or tube-life. Because tests show that the useful sensitivity is exceptionally good with the circuit as described, and better than most commercial receivers, no changes are planned.

Mixer Section: Design of the coupling network between the amplifier plate and mixer grid is not particularly involved. There should be two or more loosely-coupled circuits, for reasons given previously. Any amount of selectivity can be employed at this point, provided the overall bandwidth is not affected, without any basic effect on the noise figure. If the selective networks have excessive loss, it may be necessary to add a second stage of RF amplification in order to make up the gain, but there will not ordinarily be any need for this. The gain attainable from a single cascode amplifier is considerably in excess of that needed for good sensitivity,²² and the

insertion loss of the interstage coupling will not usually be more than 10 or 12 db.

For a direct-coupled 6BQ7 cascode stage, with no tuning inductor across the cathode-to-ground capacitance of the second triode, the effective output impedance will be about 9,500 ohms in shunt with .1 mnf. If the inductance is added, and the first section is coil-neutralized, the output appears as 250,000 ohms at midband; without the neutralizing coil, the output resistive term is around 100,000 ohms. With the self-shunt loss of the tuned circuits some 5,000 ohms at resonance, the loading effect will be moderate in the first case, and negligible in the last two. Tapping the plate terminal down on the tuned circuit might be desirable if the loading experienced in the first case was found to be excessive.

The RF input impedance of a silicon diode mixer may be as low as 50 ohms at microwaves. In the 100-mc. range, the triode or pentode mixers ordinarily used have some transit-time loading and, usually, feedback effects from cathode, plate, and screen impedances at signal frequency which may make the net input impedance either positive or negative. In some commercial television tuners, negative loading of a triode mixer with a plate circuit which was inductive at signal frequency was used to improve operation on the high channels. Experience shows that this sort of designing often makes for production trouble, as minor variations in lead lengths make large differences in tuning and loading of the mixer grid circuit.

In the six-gang experimental unit, the mixer was found to have an input impedance of only a few thousand ohms, probably because of the large grid-to-cathode loop inductance of the 6U8 pentode section. The grid was, therefore, fed from a capacitive voltage divider, so as to reduce the load on the tuned circuit and to maintain the selectivity of the interstage network.

It should be noted that with a loosely-coupled pair between RF stage and mixer there is a possibility of the mixer grid circuit impedance being *too* high, in which case thermal and induced grid noise terms might become excessive. The voltage gain between antenna and the mixer grid should be kept low; for a given gain, it is best to keep the mixer source impedance as low as possible. This is another reason for using a capacitive tap feed.

The gain over the tuning range may vary with changes in

¹⁸"A Low Noise Amplifier," Wallman, MacNee, and Gadsden, *IRE Proceedings*, June 1948.

¹⁹"Sky-Wave FM Receiver," L. B. Arguimbau and J. Granlund, *Electronics*, Dec. 1949.

²⁰"Radar Echoes from the Moon," J. Mofenson, *Electronics*, April 1946, p. 92. Also "Detection of Radar Signals Reflected from the Moon," J. H. DeWitt and E. K. Stodola, *IRE Proceedings*, March 1949.

²¹*Microwave Receivers*, A. B. MacNee, McGraw-Hill, 1948, Ch. 5, p. 131.

²²*Microwave Receivers*, A. B. MacNee, Ch. 16, p. 419.

circuit characteristics. Because of lead-inductance effects and stray couplings, the situation is complicated. Once the variations have been determined by observation, however, it is not difficult to compensate for them in part. In the six-gang experimental tuner the compensation consisted of inductive coupling so arranged that K increased considerably at the low-frequency end of the range, with a circuit resonant about 15% below the band. This can be seen in Fig. 3.

The gain from antenna to mixer is controlled easily by varying the coefficient of coupling and the voltage divider at the mixer grid. The proper amount of gain is a matter for experimental investigation. At 100 mc., 100 db of gain can be obtained easily, if there is need of it.²³ It is important to find out the variation of noise figure and spurious-response rejection with changing RF gain.

The noise figure of the combination can be calculated as described previously. Curves showing how the overall noise figure increases over RF stage noise with decreasing RF gain can be seen in Fig. 4.

Performance of a single-input mixer, in which both oscillator and signal voltages are applied to the same pair of terminals, is generally better than that of a multigrad tube at VHF. Also, less power is generally required from the oscillator.

Some extremely high responses to spurious signals were discovered in the experimental work. This was traced to two mechanisms: 1) the presence of UHF resonance in the wiring, causing a single high-order term to be emphasized unduly, and 2) leakage of oscillator voltage and harmonics to the grid of the RF stage, and there mixing with strong signals in such a way as to give an output at the frequency of the desired signal. In the second case, no amount of selectivity subsequent to the mixing process will help, although RF selectivity at the plate of the amplifier may reduce the amount of oscillator energy leaking back. Both these effects are reduced by having two tuned circuits before the first tube.

Morgan²⁴ and Sturley² classify the possible ways a mixer can receive the wrong signal by the algebraic expression for the conversion process. A flaw is inherent in this neat system, however, since a signal at $2f_0 - \text{IF}$ passed into our experimental receiver by a process which was entirely different from the way that its algebraic counterpart at $2f_0 + \text{IF}$ was received. The design steps which reduced one actually made the other a little worse.

The requirements for image suppression have been mentioned briefly. If RF selectivity is adequate to protect the mixer from other interference, the image response, unless the situation changes, will be down far enough. A 60-db image ratio seems to be adequate. The response depends only on the number and Q of the tuner's selective circuits.

Intermediate frequency suppression is more important. This interference is not tunable, and there is no way to escape, short of realigning the IF section, should a strong station appear on 10.7 mc. Even the cheapest receiver should have 60 db of IF rejection, and 90 db is a minimum for good design. Fortunately, a 60-db high-pass 75 or 300-ohm filter can be constructed for about a half dollar, and adding such a device to an existing receiver should be very simple. Most of the IF attenuation should be obtained ahead of the first tube, since the IF frequency may beat with oscillator voltage at the RF amplifier. It could then pass through the interstage circuits, for it would be at signal frequency. This is the means by which IF interference most often enters a VHF receiver, probably because most VHF receivers have considerable leakage from the local oscillator.

The circuit of the mixer stage may take several forms. In general, what is shown in a schematic diagram is much less

important than what is not shown, because the arrangement of the wiring is crucial. The mixer bias, ideally, should be set at the point where the second derivative of the mutual characteristic is a maximum; actually, it is set somewhere between the class A bias point and cutoff, for reasons given above. It may be obtained from a cathode resistor whose resistance is on the order of four times the proper value for an amplifier, or by means of a grid-leak and capacitor, with series resistance in the screen or plate circuits sufficient to limit the current to a safe value if oscillations should stop. In the latter case, the grid resistor must be of high value so that only a few microamperes of grid current can be drawn at the most positive excursion of the oscillator excitation, and the bias developed is governed mainly by the magnitude of that excitation. This tends to compensate in part for variations in oscillator voltage. The coupling capacitor should be fairly small, although if it is too small it may cause the mixer to oscillate at the intermediate frequency. This is not common in pentode mixers, but high-transconductance triodes may be unstable with grid coupling capacitors of less than 50 mmf.

Mixer plate lead configuration must be attended to carefully. Unless the first IF transformer is immediately adjacent to the mixer tube, this wire may be resonant at the signal or oscillator frequency. One way to remove the strong VHF currents flowing in this lead is to put the IF tuning capacitor at the socket of the mixer tube. A better solution, and one which avoids much leakage and feed-back, is to run the mixer plate lead to the first IF transformer through a shielded wire with the outside braid grounded at the socket. The shield provides an excellent bypass for signal-frequency components in the mixer plate current. Its capacitance is calculated as part of that in the tank circuit.

The proper oscillator injection is a compromise between poor signal-to-noise ratio on the one hand, and too many spurious responses or repeat points on the other. There is seldom a sharp line between the two, but a fairly safe rule is that the injection should be slightly less than the value

Continued on page 36

TABLE 2
MEASURED PERFORMANCES OF FM RECEIVERS

TUNER	IF, Mc	IMAGE RATIO	IN-BAND SP. RESP.	REMARKS
1 — 6-gang metal shaft	10.7	85 db	92 db	NF 11 db
2 — 4-gang, cer. shaft, adjusted for low sp. resp.	12	87	92	NF 12 db
3 — 4-gang, cer. shaft, adjusted for best sensitivity	10.7	72.5	90	N F 9 db
4 — 3-gang, cer. shaft	12	60	88	N F 20 db (est.)
5 — Comm. rcvr. 1 3-gang	10.7	54	82	Sp. resp. satisfactory
6 — Comm. rcvr. 2	10.7	41	69	S. R. poor
7 — Comm. rcvr. 3	10.7	49	73	S. R. poor
8 — Comm. rcvr. 4	10.4	42	65	S. R. bad
9 — Auto. rcvr.	10.8	33	69	S. R. bad

In each case, oscillator was above signal frequency, and worst in-band response was at signal frequency + $\frac{1}{2}$ IF. Reference level for 75-ohm input receivers, 5 μv ; for 300-ohm inputs, 10 μv . Units 5, 6, 7, and 8 are commercial models. Others built by author.

²³Vacuum Tube Amplifiers, H. Wallman, p. 196.

²⁴IRE Proceedings, H. M. Morgan, Oct. 1935, p. 1164.

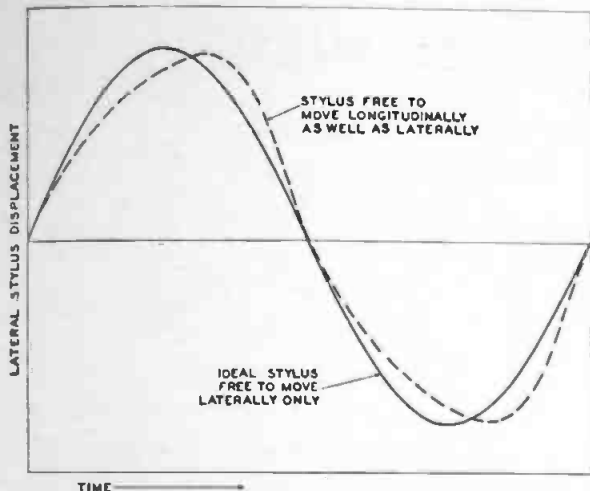


FIG. 1. DISTORTION OF SINE WAVE BY LONGITUDINALLY COMPLIANT STYLUS. FIG. 2. APPARATUS FOR MEASURING LONGITUDINAL STYLUS EXCURSION

Phonograph Stylus Drag Distortion

HOW HARMONIC DISTORTION IN DISK RECORDING AND PLAYBACK CAN BE REDUCED SIGNIFICANTLY BY LIMITING LONGITUDINAL STYLUS MOVEMENT

A recent study by Jacob Rabinow and Ernest Codier, of the National Bureau of Standards, demonstrates the existence of a type of distortion often found in phonograph reproducers that has, apparently, not been treated in available literature. The Bureau's study discloses that if a phonograph stylus can move longitudinally with respect to the groove of an ordinary laterally-recorded disk, the needle will not follow perfectly the lateral excursions of the groove, and drag distortion will result. On playback of recorded music, this distortion can produce spurious tones of greater amplitude than the true ones.

Nature of Drag Distortion: The mechanism of drag distortion is not difficult to understand. The usual type of disk phonograph record is recorded laterally; that is, the audio-frequency motion of the recording stylus is at right angles to the record groove. For ideal distortion-free reproduction, the motion of the playback stylus tip should duplicate exactly the original lateral motion of the recording stylus. Provided the electrical output of the pickup is proportional to the lateral displacement of the stylus, there is then no distortion. However, if forces acting on the stylus cause longitudinal motion, its lateral motion does not follow exactly that of the recording stylus, and distortion is introduced. The two conditions are shown in Fig. 1.

Many possible causes for such longitudinal motion can be suggested. One is the well-known pinch effect caused by uneven width of the record groove. Another is the varying force which the sides of the record groove exert against the stylus.


A third is the change in friction with changes in the pressure and velocity of the stylus within the groove.

The NBS study included both mathematical analysis and laboratory experimentation. Mathematical treatment indicates that if the recording consists of a pure tone of constant amplitude, drag distortion can produce only even harmonics, with the second harmonic predominating. A sudden transition from one amplitude to another will produce a large change in the longitudinal force on the stylus, and this can be expected to give rise to transient distortion if the stylus is not properly restrained longitudinally.

Test Results: A conventional crystal pickup with a replaceable steel stylus was used in experimental work. For some tests, a thin steel wire was spot-welded to the stylus near the tip; by tying the tip back with this wire, longitudinal motion could be minimized. A dual-beam oscilloscope was used to indicate simultaneously the waveform of the pickup output and the longitudinal displacement of the stylus tip.

Two methods of measuring the longitudinal motion were tried. The first consisted of a photoelectric arrangement in which spurious motion of the stylus modulated a beam of light. In the second, more satisfactory method, longitudinal motion of the stylus frequency-modulated a 50-mc. oscillator. Two small metal plates were mounted near the steel shank in such a way, Fig. 2, that the capacity between the plates varied with longitudinal motion of the stylus but not with lateral motion. The plates were connected across the tank coil of the oscillator.

Concluded on page 40

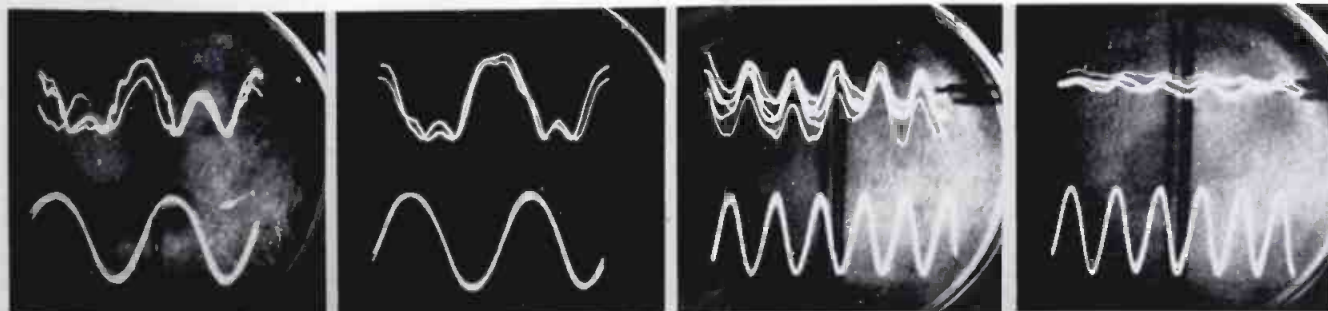

FIGS. 3, 4, 5. LONGITUDINAL MOTIONS (ABOVE) AND PICKUP OUTPUTS FOR 40, 50, AND 300-CYCLE GROOVES. FIG. 6. 300 CYCLES, STYLUS TIED BACK

Increased VTVM Sensitivity

NEW VACUUM-TUBE VOLTMETER CIRCUIT EMPLOYING 12A4 TUBES INCREASES SENSITIVITY 15-20 TIMES — By JOSEPH GIUFFRIDA*



FIG. 2. THE 12A4

IN conventional vacuum-tube voltmeters, maximum sensitivity is hardly ever realized because the tubes employed exhibit imbalance, instability, and nonlinearity when operated at the large plate currents necessary for high sensitivity. However, by employing tubes designed for normal high-plate-current operation with low grid currents, the Commercial Engineering Department of CBS-Hytron has developed a simple VTVM circuit, described here, which has a sensitivity 15 to 20 times that of conventional circuits.

VTVM Bridge Operation: The elementary VTVM bridge circuit consists of four resistances arranged in series-parallel, as shown in Fig. 1. Resistances R1 are the plate load resistors for the two tubes in the bridge, and R2 represents the static impedances of the tubes. The meter is normally connected across the two tube plates. Delta E, then, is a measure of circuit sensitivity. The potential difference across the bridge is:

$$\Delta E = E \text{ IN } \left(\frac{R2 + \Delta R}{R1 + R2 + \Delta R} - \frac{R1}{R1 + R2} \right)$$

The curve at the right in Fig. 1 shows that delta E approaches zero asymptotically as R2 is increased, corresponding to the use of conventional vacuum tubes with low plate currents. Maximum delta E occurs when R2=0. This indicates

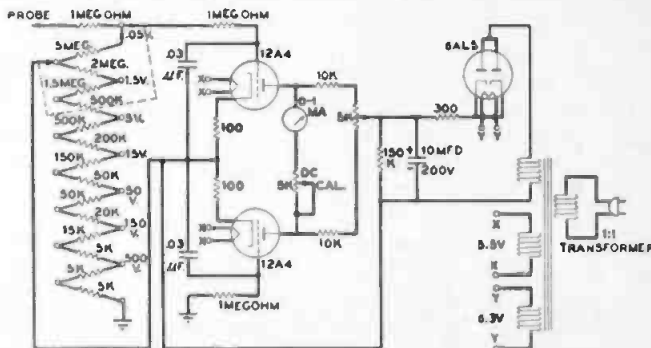


FIG. 4. COMPLETE BASIC CIRCUIT DIAGRAM OF THE NEW VTVM DESIGN

that tubes used in a VTVM bridge circuit must have very low resistance at the operating point in order to achieve high sensitivity. As a corollary, they must have a dissipation rating sufficiently high to permit their use with low-resistance plate loads, and low bias voltages.

Use of the 12A4: The Hytron type 12A4 vacuum tube, while designed for use as a vertical output tube in television receivers, is virtually ideal for VTVM service because of its high permeance and uniformly small grid current. This 9-pin medium-mu miniature triode, with connections as shown in Fig. 2, has the following characteristics:

TYPICAL CHARACTERISTICS, 12A4

Heater volts	12.6 or 6.3
Heater current, ma.	300 or 600
Plate volts	250
Grid bias, volts	-9
Amplification factor	20
Transconductance, umhos	7800
Plate current, ma.	21
Grid cutoff, volts (Eb=500 v.)	-33

*Commercial Engineering Department, CBS-Hytron, Salem, Mass.

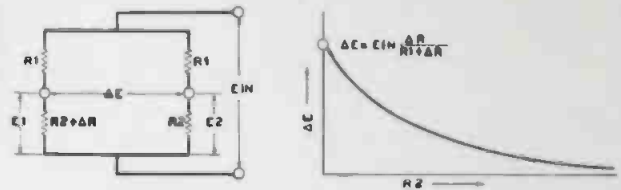


FIG. 1. OPERATING PRINCIPLE OF THE STANDARD VTVM BRIDGE CIRCUIT

By using cathode resistors of low value, the static operating point of each tube can be set at 5 milliamperes, which is a much higher current than is usual in VTVM circuits. The grid current that accompanies such operation can be balanced out by means of a center-tapped dividing network, as Fig. 3 shows. Resistance between the common cathode return and the two grids is kept constant by using an ordinary 2-wafer ganged switch for the voltage-divider network. The two functions of dividing input voltage correctly and maintaining equal grid-to-cathode resistances can be accomplished by substituting two resistors for each resistor in an ordinary divider. These two resistors have the same total resistance as the original, but are connected to the 2-gang switch, Fig. 3, so that the resistor connected to the high VTVM grid has a value half that of the total resistance in the divider below that particular tap. Resistor values shown in the diagram will make this clear. The range switch is in the 15-volt position.

Fig. 4 is a diagram of the complete basic circuit, with typical component values. This circuit has a sensitivity of .5 volts full-scale on a 0 to 1-milliamper meter, with stability comparable to conventional less-sensitive VTVM's. Input resistance is 10 megohms for any range, and the source resistance makes no practical difference in the reading obtained.

Heater voltage is limited to 5.5 volts, at which level operation is still quite satisfactory. However, tube life is extended significantly, and circuit stability is further improved by this reduced heater voltage. No difficulty was caused by operation of the power supply above ground potential. Ordinary power transformers have sufficient insulation resistance for this application.

Only the DC section of the circuit is shown, since this is the foundation of most VTVM's. Peak-to-peak or RMS diodes for AC scales, and an additional divider for ohmmeter scales, can be added easily.

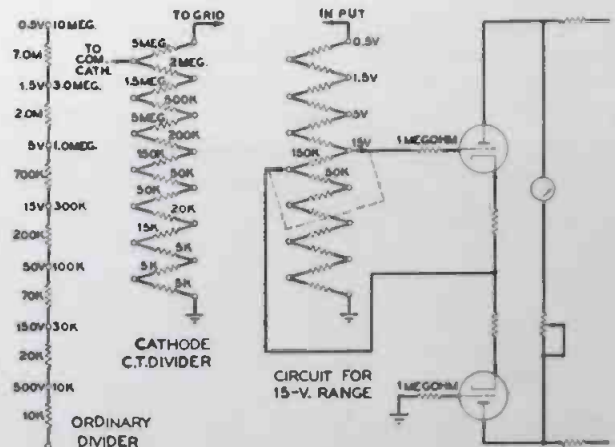


FIG. 3. STANDARD AND CONSTANT-RESISTANCE VOLTAGE-DIVIDERS



Now...

PACKAGED REMOTE CONTROL for Commercial Broadcast Transmitters AM — FM

THE RUST INDUSTRIAL COMPANY'S REMOTE CONTROL SYSTEM

The Rust System is the *only* transmitter remote control system *proven* in service in United States Commercial AM Broadcasting installations. *It meets all FCC requirements.*

REMOTE CONTROL

of transmitters means more effective station operation. Attending personnel may be utilized more efficiently. More convenient location of studio is made possible. Transmitter may be located where transmitting conditions are ideal and real estate costs low.

THE RUST SYSTEM

consists of a studio unit and transmitter unit connected by two telephone pairs. Up to nine meter readings can be made and up to nine operations can be controlled by simply dialing desired functions. Transmitter adjustment is made remotely while simultaneously observing readings of appropriate meter.

The transmitter unit is connected to any one of a number of tuning motors or contactors used for controlling transmitter tuning or other switching functions. Use of various shunts and multipliers permits the metering of several circuits at the remote control point. Any failure of the system immediately removes all power from the transmitter.

The complete system is sold on an installed basis with all components guaranteed for one year. Price includes any necessary modification of the transmitter. Savings can pay for entire cost in as little as ten weeks.



STUDIO UNIT
(Type RI-1080)



TRANSMITTER UNIT
(Type RI-1081)

WRITE FOR DETAILED INFORMATION.

the rust industrial

610 WILLOW ST.



company, inc.

MANCHESTER, N. H.

C-D and



C-D transmitting capacitors and Faradon* capacitors manufactured exclusively by Cornell-Dubilier, available through all Authorized C-D Distributors. Write for Catalog to: Dept. TV 23, Cornell-Dubilier Electric Corp., South Plainfield, N. J.



CONSISTENTLY DEPENDABLE
CORNELL-DUBILIER
 CAPACITORS

Plants in South Plainfield, N. J.; New Bedford, Worcester, and Cambridge, Mass.; Providence, R. I.; Indianapolis, Ind.; Fuquay Springs, N. C.; and subsidiary, The Radiant Corp., Cleveland, Ohio

SPURIOUS RADIATION

(Continued from page 21)

7 used the new IF in some 1952 sets, and 6 used the new IF in all late 1952 sets. All expect to use the 41.25-mc. IF in all 1953 models, although 2 stated that its use depends to some extent on interference experienced from the state-police transmitters. Means have been suggested to the FCC to eliminate or reduce such interference.

It was decided at the Oct. 20 meeting that recommendations on TV sweep circuit radiation would be postponed until the IRE subcommittee on sweep radiation completed its work on measurement

standardization. Preliminary standards have been developed, and are now ready for distribution, it was stated.

Television Transmitters: J. E. Keister, Chairman of RTMA Transmitter Committee RT-4, spoke on the status of his committee's work on harmonic radiation from television transmitters. Because a typical single-ended TV output circuit provides about 30 db second-harmonic suppression without a harmonic filter, this figure was incorporated into TR-104B, RTMA Electrical Performance Standards for Television Broadcast Transmitters. Subsequently, it was decided to change this figure to 60 db.

and the new figure is given in the C issue of TR-104.

For complete installations, the "radiation outside the assigned channel shall be as low as possible and in any case shall not disturb other services." This places the responsibility for suppressing spurious radiation on the industry, even when adjustments must be made in the field. All actual cases of TV transmitter interference have been corrected satisfactorily, Mr. Keister said.

On Nov. 28, 1952, the FCC published Docket No. 10353, in which 60-db harmonic suppression was proposed, and greater suppression where necessary to protect other services. RTMA filed a request that the effective date of such a Rule amendment be specified as at least a year after its formal adoption, because of the time necessary to prepare for production of the low-pass filters required. The following Schedule was estimated to represent the least possible times required for development, procurement, and manufacturing of such filters:

FILTER TYPE	CHANNELS	TIME
2nd. harm. only	2-3	3 mos.
2nd. harm. only	4-6	4 mos.
Low-pass	2-6	8 mos.
Low-pass	7-13	11 mos.
Low-pass	14-83	1 year

UHF Receivers: Chairman of IRE Committee on Spurious Radiation R. F. Shea reported that the IRE standard method for measuring local oscillator radiation from FM and VHF-TV receivers has been used with good results for UHF receivers also. Such measurements are handicapped to some extent, Mr. Shea noted, by the commercial availability of only one type of UHF field-strength meter. Consequently, deliveries are slow. Others are in development, however, and should be in production by this fall.

Three task forces were then set up for further work on these problems. No. 1, under chairman K. A. Chittick, is to be concerned with determining the maximum practical reduction of receiver spurious radiations, and establishing a schedule for compliance by the industry. No. 2, under J. E. Keister, is charged with the same task on TV transmitters. No. 3, under chairman D. G. Fink, is to act as coordinator between RTMA and JTAC, FCC, and IRE.

FM TUNER HEAD

(Continued from page 32)

giving maximum conversion gain, if there is such a maximum. The IF output on the desired signal will be roughly proportional to both signal and to oscillator magnitude, for low oscillator injections, and the nearby beat responses increase

as some higher power of each. Therefore, when the conversion gain is no longer proportional to the oscillator injection, it is more advantageous to increase the RF gain, if it is required for maximum sensitivity than to increase the injection.

For experimental adjustment, the RF gain should be held fixed while the oscillator injection is adjusted by setting the oscillator plate-supply voltage and the coupling to the mixer for the best operation, as explained above. Then the RF gain, which is most likely excessive, should be reduced until the measured noise figure is degraded by $\frac{1}{2}$ to 3 db. This gives best rejection of the most annoying beat, $f_0 \pm \frac{1}{2}IF$, when referred to standard sensitivity rather than to an absolute level. The proper way to reduce the RF gain is not by changing the transconductance but by decreasing the coupling between tubes and resonant circuits, or between circuits, so that gain is traded for selectivity.

The method by which oscillator voltage can be supplied to the mixer is mostly a question of convenience. Ref. 8 describes a mixer using cathode injection; ref. 22, a low-impedance link; in ref. 5 and Fig. 3, the coupling is accomplished by circuit stray capacitances; and in Fig. 2, the oscillator and mixer grid inductors are coupled magnetically. In each instance, the amount of oscillator injection can be varied over a fairly wide range by one means or another.

Performance Checks: If the ultimate truth of a theory cannot be verified, experimental evidence is at least a consolation. The foregoing discussion is in part the result of experiment, so that the correlation between theory and practice should be fairly direct.

Three examples of FM broadcast tuning heads designed for low spurious responses are shown in Figs. 2, 3, and 5. Their measured performances are shown in Table 2, where they are numbered 2, 1, and 4, respectively. No. 3 is No. 2 modified for better sensitivity. The other receivers are representative of lower-priced equipment, and should be compared only among themselves.

Fig. 6 shows the performances of Nos. 1 and 2 (as complete receivers) for weak signals. It can be seen that a signal of 4 microvolts at 75 ohms is sufficient for a 40 db overall signal-to-noise ratio on either receiver. This exceeds the signal-to-noise ratio of the average living room, and should be considered noise-free enough for good listening.

If the same tuning heads were used with an AM receiver with a bandwidth of 10 kc. rather than 200 kc., the standard sensitivity would be on the order of two microvolts. This is typical of MHF

Concluded on page 38

to the

ELECTRICAL ENGINEER

or

PHYSICIST

with experience in

RADAR

or

ELECTRONICS

Hughes Research and Development Laboratories, one of the nation's leading electronics organizations, are now creating a number of new openings in an important phase of their operations.

Here is what one of these positions offers you:

THE COMPANY

Hughes Research and Development Laboratories, located in Southern California, are presently engaged in the development and production of advanced radar systems, electronic computers and guided missiles.

THE NEW OPENINGS

The positions are for men who will serve as technical advisors to government agencies and companies purchasing Hughes equipment—also as technical consultants with engineers of other companies working on associated equipment. Your specific job would be essentially to help insure successful operation of Hughes equipment in the field.

THE TRAINING

On joining our organization, you will work in the Laboratories for several months to become thoroughly familiar with the equipment which you will later help users to understand and properly employ. If you have already had radar or electronics experience, you will find this knowledge helpful in your new work.

WHERE YOU WORK

After your period of training—at full pay—you may (1) remain with the Laboratories in Southern California in an instructive or administrative capacity, (2) become the Hughes representative at a company where our equipment is being installed, or (3) be the

Hughes representative at a military base in this country or overseas (single men only). Compensation is made for traveling and moving household effects, and married men keep their families with them at all times.

YOUR FUTURE

In one of these positions you will gain all-around experience that will increase your value to our organization as it further expands in the field of electronics. The next few years are certain to see large-scale commercial employment of electronic systems. Your training in and familiarity with the most advanced electronic techniques now will qualify you for even more important future positions.

How to apply:

HUGHES

RESEARCH AND
DEVELOPMENT LABORATORIES

Engineering Personnel Department
Culver City,
Los Angeles County, California

If you are under thirty-five years of age, and if you have an E.E. or Physics degree, write to the Laboratories, giving resumé of your experience.

Assurance is required that relocation of the applicant will not cause disruption of an urgent military project.



Announces

a NEW 90° YOKE for 27" TUBES



It's Engineered for TOP PERFORMANCE ... in Production NOW!

This new DX 90° Deflection Yoke has everything a television receiver manufacturer wants . . . a sharp full-screen focus, a minimum of pincushioning, the ultimate in compactness and a price that's downright attractive. Because this yoke has been brilliantly designed for mass production on DX's specialized equipment, it warrants immediate consideration in your 27" receiver plans. Write us today.

DEFLECTION YOKES . . . TOROID COILS . . . CRYSTALS
I. F. TRANSFORMERS . . . R. F. COILS . . . DISCRIMINATORS
SPEAKERS . . . TV TUNERS . . . ION TRAPS . . . TRANSFORMERS

DX RADIO PRODUCTS CO.

GENERAL OFFICES: 2300 W. ARMITAGE AVE., CHICAGO 47, ILL.



MOBILE RADIO HANDBOOK

Practical Working Data on Mobile and Point-to-Point Systems

EDITOR: MILTON B. SLEEPER — ASSOCIATES: JEREMIAH COURTNEY, ROY ALLISON

PLANNING: How to plan a mobile or point-to-point communications system. This chapter covers the overall problems of power and topography, interference, city ordinances, public liability, operation, maintenance, expansion, and interconnection.

FREQUENCIES: FCC rules and allocations which became effective in July, 1949 provided for many new services. Complete details are presented on every service in the common carrier, public safety, industrial, and transportation groups.

LICENSES: How to apply for a construction permit, license, and renewal for a communications system. Complete FCC forms, filled out in the correct manner, are shown. This is of the utmost importance; incorrect forms may cause months of delay.

EQUIPMENT: Three chapters are devoted to the problems of selecting the right equipment for a particular system, specifications on transmitters and receivers of all makes, selective calling and fleet control and adjacent-channel operation.

ANTENNAS, TOWERS: The problems of planning antenna installations are covered very thoroughly in two chapters which explain the various special-purpose types of radars, and the correct method of erecting a standard guyed, steel antenna tower.

MAINTENANCE: How to keep a communications system at peak performance. Methods and record forms that have been perfected by years of experience are described in detail. Proper balance between essential and superfluous maintenance is explained.

OPERATORS: The FCC is becoming increasingly strict about the observance of rules relating to operator requirements at communications systems. Official information is given, with a detailed explanation from FCC Secretary T. J. Slowik.

HOW FM WORKS: Advantages of FM over AM, coverage, interference, and static elimination, and circuit functions are explained pictorially in 83 illustrations. The use of mathematics has thus been avoided in this clear, practical presentation.

An elaborately illustrated reference book for executives, communications engineers, system supervisors. 190 pages, 8 1/4 by 11 1/2 ins.

\$4.00 Cloth Bound - \$2.00 Paper Cover Postpaid in the U.S. Elsewhere, 25c Postage

Published by Radio Communication Magazine

THE PUBLISHING HOUSE, GREAT BARRINGTON, MASS.

FM TUNER HEAD

(Continued from page 37)

communication receivers. The image ratios also compare favorably with good MHF receivers in the 5-mc. region.

No. 4 receiver, Fig. 5, is considered the best confirmation of the methods outlined here. When first checked, the sensitivity was excellent, but image and spurious-response ratios were 40 and 67 db respectively. As modified, the figures were increased to 60 and 88 db, at no cost for parts (none were added), and with no perceptible difference in sensitivity. Previously, interference from two nearby stations had been very annoying; now, there is no interference in the entire band. The RF gain was reduced 10 or 12 db, but the overall gain was still sufficient for adequate limiting, so the changes were an unqualified improvement.

RF selectivity for the 6-gang tuner is shown in Fig. 7. It can be seen that, for the region of interest, only 3 of the 4 tuned circuits contribute to selectivity. This confirms previous deductions.

Figure 8 is a diagram of the tuning head used in receiver No. 9, Table 2. Simplicity and maximum RF gain per milliamperere of plate current were the design objectives. The noise figure of a similar tuner has been measured as 3 db at 30 mc. and 9 db at 150 mc. It is better than a straight mixer without an RF stage in this respect, but worse for spurious responses.

TV PLANT TOUR

(Continued from page 23)

a purpose is a compromise measure which is not recommended, except where adequate optical adjustment is impossible, since the reduction of peak signal strength may involve a sacrifice of signal-to-noise ratio. To be preferred is the use of lenses which can be stopped down to the desired value or, where this is impracticable, the use of a neutral-density filter which cuts down the overall light input without discriminating against any particular wavelengths.

Quick movement of the cameras was facilitated by using a special truck with a hydraulic lift on the rear end, shown in Fig. 5. This truck stood by with the lift lowered until a camera completed one sequence and a camera in another location took over. The first camera was then rolled onto the lift, tripod and all, hoisted to the truck floor, hauled to the next location, lowered, and rolled into position. Toughest haul was about 450 ft., with only 10 minutes available from the instant it was shut down to the time when it had to be putting out a signal from the next location.

The five tons of equipment, consisting of 49 separate units, was trucked to the plant from Camden in 38 large wooden boxes. Uncrating and setting up the equipment took about four hours. Only two hours were required after the show to knock it down and crate it, ready for the trip back to Camden.

Stringing the half-mile of cable, however, was another matter. That took about eight hours in itself. To protect the insulation from puddles and wet ground, in many cases bearing lithium salts and other chemicals, and to avoid blocking plant streets and drives or the risk of damage to the cable by passing vehicles, it was decided best to string most of it overhead. Where it crossed a spur of railroad track, the railroad required that it be suspended a minimum of 8 ft. above the tops of freight cars. This was accomplished without raising poles by stringing it from one to another of the plant buildings and tanks. For the longest run, a 100-ft. stretch from one support to another where the cable crossed the railroad, it was necessary to use a catenary steel support cable to prevent sagging.

Two 800-ft. lengths of camera cable were used to carry signals from the two most remote cameras to the control station, and 100-ft. lengths were required for each of the two remaining cameras. Four microphones were used, three in the field and one at the narrator's desk. These required microphone-line runs of 800, 200, 100, and 50 ft., respectively.

Six floods provided lighting for the indoor sequences. One special lighting problem was engendered by the presence of an open doorway and two windows near one side of the narrator's desk. This was solved by hanging white muslin over the openings to diffuse the outside light, and using a flood to balance lighting in the rest of the scene.

The floods employed Westinghouse lamps rated at 500 watts, with filaments adjusted to burn at about 2,800° Kelvin. This supplied the equivalent of 750 watts, and produced a very white light. In most instances, one or more floods were placed within a range of 10 to 15 feet of the subject or main objects in the scene, the distance depending on the nature of the shot and the effects desired.

Little in the way of special effects was attempted, but one measure that was tried proved quite effective. This consisted of fading in the opening frames of the film part of the program behind an image of Felix Shay, vice president in charge of production for Foote, as he sat at the narrator's desk after being introduced. Mr. Shay furnished the commentary for the film, which was concerned with the Kings Mountain, North

Concluded on Page 40

February-March, 1953



FAS Air-Coupler for Bass Reinforcement

Good News . . . The Dual Air-Coupler for bass reinforcement is in stock, ready for delivery. This is the improved model described in *Radio Communication* last October, and in the Winter Edition of *High Fidelity*.

As more and more of the most critical audio experts install Air-Couplers in extended-range systems, reports of remarkable performance continue to pour in. One of the most enthusiastic owners is Paul deMars, former chief engineer of the Yankee Network, and a pioneer in high-quality reproduction. He said: "I have never heard such magnificent tone from records and live-talent FM as I am getting from my Air-Coupler in combination with a dual speaker for intermediate and treble frequencies."


For your convenience . . . the Air-Coupler is available in both knock-down form, so that you can assemble it with a screwdriver, or completely assembled, ready to mount the speaker. Made entirely of first-quality 3/4-in. plywood, with each piece cut to precision fit.

DUAL AIR-COUPLER, COMPLETELY ASSEMBLED . . . now only 47.50
The Air-Coupler is supplied completely assembled and finished in a truly professional manner, with front panel in place, ready for the speaker. Illustration shows assembled Air-Coupler, before front panel is mounted. Opening is cut for any 12-in. speaker, the recommended size.

DUAL AIR-COUPLER, IN KNOCK-DOWN FORM . . . now only \$34.50

MISCELLANY: we carry in stock . . . Altec 600-B 12-in. speaker for the Air-Coupler, \$46.50; Peerless S-230Q output transformer, \$26.00; Peerless R-560A power transformer, \$16.00; Peerless C-455A power choke, \$10.00; English KT-66 output tube, \$4.95; Racon CHU2 tweeter, \$23.10.

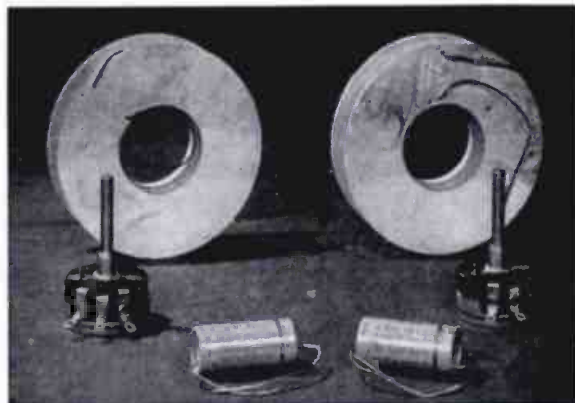Crossover Networks for Any System of Two or More Loudspeakers



By a judicious selection of associated components, the three coil sizes on which G.A. has standardized enable our customers to secure low-cost crossover networks which will operate at 14 different crossover frequencies! For the experimenter, that means a wide range of choice without having to break the bank to buy dozens of coils. For the man who wants to install his system once and for all, it means money saved, because G.A. saves money by making only three coil sizes (10.2, 5.1, and 1.6 Mh) — and it passes on those savings direct to its customers.

If you want to use three speakers with crossover points at 350 and 1,100 cycles, for example, just order two of the networks listed above (for an 8-ohm system, with rapid crossover attenuation, it would be No. 6 and No. 8).

As most everyone has found out by now, G.A. is headquarters for crossover networks. As far as we know, we're the only organization stocking networks specifically designed for use with Air-Couplers.

If you are in doubt about the selection of a network for your particular speakers, send 10c for the G.A. Network Data Sheet, from which you can determine your requirements exactly.

RAPID ATTENUATION NETWORKS

12 db droop per octave. These networks use two inductance coils.

Impedance of low frequency speaker	Crossover Frequency	Order by Number	Price 2 Coils Only	Price Complete*
16 ohms	2,200	No. 1	\$7.00	\$11.50
		2	7.00	12.00
		3	12.00	16.00
		4	12.00	17.50
		5	20.00	24.00
8 ohms	1,100	6	7.00	12.00
		7	7.00	13.00
		8	12.00	17.50
		9	20.00	24.00
		10	20.00	26.50
4 ohms	550	11	7.00	13.00
		12	7.00	15.00
		13	12.00	19.00
		14	20.00	26.50

* Complete networks include necessary capacitors and level controls. Be sure to indicate whether you want just the coils or the complete network.

Air-Couplers are shipped via Railway Express, FOB South Egremont, Mass.

Other items shipped FOB unless 75c is included to cover parcel post and insurance charges.

General Apparatus Co.


South Egremont, Massachusetts

**FOR PUBLIC
ADDRESS, RADIO,
and kindred fields,
JONES 400
SERIES
PLUGS & SOCKETS**

of proven quality!



P-406-CCT

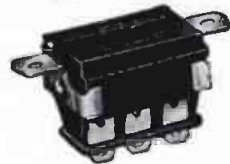

S-406-AB

Socket contacts phosphor bronze cadmium plated. Plug contacts hard brass cadmium plated. Insulation molded bakelite. Plugs and sockets polarized. 2, 4, 6, 8, 10, 12 contacts. Steel caps with baked black crackle enamel.

Catalog No. 18 gives full information on complete line of Jones Electrical Connecting Devices — Plugs, Sockets and Terminal Strips. Write



HOWARD B. JONES DIVISION
CINCER MANUFACTURING CORPORATION
CHICAGO 24, ILLINOIS
SUBSIDIARY OF UNITED-CARR FASTENER CORP.

**ZOPHAR
WAXES**

COMPOUNDS

Zophar Waxes, resins and compounds to impregnate, dip, seal, embed, or pot electronic and electrical equipment or components of all types, radio, television, etc.

Cold flows from 100°F. to 285°F.

Special waxes non-cracking at -76°F.

Compounds meeting Government specifications plain or fungus resistant.

Let us help you with your engineering problems.



ZOPHAR MILLS, INC.
112-130 26th Street,
Brooklyn 32, N. Y.

TV PLANT TOUR

(Continued from page 39)

Carolina plant of Foote. Here spodumene, a source of lithium salts, is quarried and processed. The film reproduction, incidentally, was unusually clear because the film camera had been modified with the latest laboratory improvements, and shading was not necessary.

Program: On the receiver screens in the cafeteria, the stockholders saw first the processing of lepidolite ores from Africa to obtain lithium products used for many industrial purposes, including the preparation of special types of glass for TV picture tubes. In Fig. 6, Mr. Drake explains the ore-bagging process.

Next, the Kings Mountain film was run, with commentary by Mr. Shay. More lithium processing operations were then shown, followed by the activities in progress at the pilot plant, Fig. 1, where a new process was being evaluated.

Detailed close-up action views were then presented of complex operations and equipment used in processing zirconium, a metal employed in radar and television manufacturing and for jet engines, atomic reactors, and the fabrication of vacuum tubes. The tour closed

with a visit to the plant area, Fig. 7, where various minerals are processed to produce welding electrode coating materials.

Commenting on Foote's introduction of this new use of television, Mr. Bliss predicted that closed-circuit TV will become a valuable tool of business and industry for such purposes.

"It provides a unique means of showing stockholders what is being done with their money, and how their investments are being protected," he said, "without wasting their valuable time and energies and those of company officials in traveling from point to point.

"Further, it makes it possible to present a dramatic vignette of highlights in a company's operations that is more impressive and understandable than a physical tour of the plant. It presents the company's story with more realism and conviction than film can achieve, since it is recognized that there is no window-dressing in a TV presentation, and no opportunity for cutting and editing.

"It may even be found practicable for firms with plants in different cities to bring live TV pickups from various plants to a stockholders' meeting in one convenient location."

DRAG DISTORTION

(Continued from page 33)

and the resulting FM signal was picked up on a standard FM receiver a few feet away. With proper tuning, the instantaneous output of the receiver varied with the instantaneous longitudinal position of the stylus tip.

Various test records were reproduced with this experimental equipment. Tests were made with recordings of pure tones ranging from 20 to 10,000 cycles per second, of two different tones recorded simultaneously, and of music. The unrestrained stylus showed significant longitudinal motion, substantially verifying the original hypothesis. Figs. 3 and 4 show the results at 40 and 50 cycles respectively, with the upper waveforms representing longitudinal motion and the lower waveforms the pickup output. Longitudinal motion was not restrained. Figs. 5 and 6 are similar views of 300-cycle waveforms, with the stylus restrained longitudinally in Fig. 6.

With the equipment available, it was not possible to measure electrically the amount of distortion caused by this motion, because of the simultaneous presence of other forms of distortion. It was possible, however, to determine the magnitude of the longitudinal motion, and by computation to arrive at the character and amount of distortion attributable to this motion.

Although it was pointed out that the effects of drag distortion can be serious with some pickups, it was shown also that the styli in the better modern pickups have high longitudinal stiffness; with such pickups, drag distortion is probably negligible.

Conclusion: Both the mathematical analysis and the laboratory work were necessarily limited in scope. However, the NBS work may serve as the basis for more rigorous investigation elsewhere. Although no tests were made on vertical records and pickups, the same general considerations should apply as with lateral recordings and reproducers. It is probable also that a form of drag distortion can occur in the recording operation if the recording stylus is not sufficiently rigid longitudinally.

This investigation of phonograph drag distortion was a by-product of the Bureau's military research program. Telemetered information from experimental weapons is frequently recorded on disks in the NBS ordnance development laboratories, and the distortions introduced in the recording and reproducing processes are sufficiently serious at times to cast doubt on the significance of indicated measurements. Analysis of possible sources of error in these recorded measurements led to the study of distortion introduced by phonograph-stylus drag.

IMPORTANT BOOKS

for your

REFERENCE LIBRARY

To help you in your selection of basic reference works, we have checked hundreds of engineering and technical books. One or more of these will provide the answer to your questions and problems in radio, television, UHF, mobile radio, microwaves, and sound reproduction. For prompt delivery, use the coupon below.

TELEVISION

- TV Standards and Practice**—by *Donald Fink*. No. 40...\$6.50
405 pages, 5½ by 8¼ ins., cloth. Official standards set by NTSC for use by engineers in the TV industry.
- Practical TV Engineering**—by *Scott Helt*. No. 41...\$7.50
708 pages, 6 by 9 ins., cloth. Fundamentals and methods of efficient TV practice for engineers, students, and technicians.
- Television**—by *Zvorykin and Morton*. No. 42...\$7.50
646 pages, illus., 6 by 9¼ ins., cloth. An authoritative treatment of fundamentals and practice for TV engineers and service men.

FREQUENCY MODULATION

- Frequency Modulation**—by *August Hurd*. No. 43...\$6.75
375 pages, 6 by 9 ins., cloth. An engineering text covering basic principles as well as design of commercial apparatus.
- FM Simplified**—by *Milton S. Kiver*. No. 44...\$6.50
347 pages, 5½ by 8 ins., cloth. An excellent book for the layman who wants to learn about FM transmission and reception.
- Frequency Modulation**—by *Nathan Marchand*. No. 45...\$5.00
409 pages, illus., 6 by 9, cloth. The fundamentals, circuits, and equipment used in FM explained using a minimum of mathematics.

UHF

- UHF Techniques**—*Edited by J. G. Brainerd*. No. 47...\$6.50
534 pages, 6½ by 9½ ins. cloth. A text designed primarily to train engineers and physicists in ultra-high-frequency research work.
- UHF Transmission**—by *Nathan Marchand*. No. 48...\$4.50
322 pages, 6 by 9¼ ins., cloth. For practicing engineers using UHF. The principles given are applicable to particular problems.
- Communication at UHF**—by *John Thomson*. No. 49...\$4.50
203 pages, 5½ by 8½ ins., cloth. Covers radio communications at these frequencies with emphasis on development possibilities.

MICROWAVES

- Introduction to Microwaves**—by *Simon Ramo*. No. 50...\$4.00
138 pages, 5½ by 8½ ins., cloth. An excellent non-mathematical treatment of the concept of microwaves for the novice.
- Understanding Microwaves**—by *V. J. Young*. No. 51...\$6.00
385 pages, 5½ by 8¼ ins., cloth. The underlying principles thoroughly explained for engineers, researchers, and students.
- Microwave Electronics**—by *John C. Slater*. No. 52...\$6.50
406 pages, 6 by 9 ins., cloth. A highly technical treatment of war-time and post-war development in microwaves.

RADIO COMMUNICATION

- Mobile Radio Handbook**—by *M. B. Sleeper*. No. 54...\$2.00
185 pages, 8¼ by 11½ ins., paper. Invaluable references for all concerned with mobile radio and point-to-point communications.

AUDIO REPRODUCTION

- Pianos, Pianists, and Sonics**—by *G. A. Briggs*. No. 55...\$2.50
192 pages, 5½ by 8¾ ins., cloth. The evolution and construction, touch, tuning, and toning of pianos. Of interest to music lovers.
- Sat. Rev. Book of Recorded Music & Sound Reproduction**—by *E. T. Canby, C. G. Burke, & I. Kolodin*. No. 98...\$4.50
320 pages, 6¼ by 9¼ ins., cloth. Complete analyses on all phases of the high-fidelity field. Includes equipment reports.

- Sound Recording**—by *Frayne and Wolfe*. No. 53...\$9.50
686 pages, illus., 6 by 9¼, ins., cloth. For designer, engineer, and technician, covers basic problems in recording and reproducing.
- Loudspeakers**—by *G. A. Briggs*. No. 56...\$1.60
88 pages, 5 by 8 ins., paper. A thorough yet concise account of the "why" and "how" of good reproduction in simple language.
- Musical Engineering**—by *Harry F. Olson*. No. 95...\$7.00
369 pages, 6 by 9 ins., illustrated. Interrelated engineering treatment of sound, speech, music, musical instruments, acoustics and sound reproduction.

INSTRUMENTS

- Modern Oscilloscope**—by *J. A. Ruiter, Jr.* No. 58...\$6.00
326 pages, 5¾ by 9 ins., cloth. A description of equipment and operational methods for engineers, servicemen, and teachers.
- Vacuum-Tube Voltmeters**—by *John F. Rider*. No. 59...\$4.50
432 pages, 5½ by 8¼ ins., cloth. Only source book devoted exclusively to this subject. For engineers, technicians, and teachers.
- Encyclopedia on Oscilloscope**—by *J. F. Rider*. No. 60...\$9.00
992 pages, 8½ by 11 ins., cloth. Truly encyclopedic in coverage. This book shows, in detail, efficient use of the scope.

ACOUSTICS

- Acoustic Measurements**—by *Leo L. Beranek*. No. 61...\$7.00
914 pages, 5½ by 8½ ins., cloth. Discusses techniques, apparatus, and theory of acoustic measurements for technicians.
- Acoustic Design in Architecture**—by *Knudsen & Harris*. No. 62...\$7.50
457 pages, 5½ by 8¼ ins., cloth. For engineers and students, a discussion of principles, procedures, and specific applications.
- Acoustic Design Charts**—by *Frank Massa*. No. 63...\$4.00
228 pages, 6 by 9 ins., cloth. Quick, handy reference for those interested in design or construction of electro-acoustic apparatus.

REFERENCE BOOKS

- The Radio Handbook**—*Edited by R. L. Dawley*. No. 64...\$6.00
726 pages, 6½ by 9½ ins., cloth. Detailed constructional information on a wealth of radio communication equipment; all new.
- Broadcast Operators Handbook**—by *H. E. Ennes*. No. 65...\$5.40
265 pages, 5¼ by 8½ ins. cloth. A complete guide to operating and maintenance practice for broadcasters and technicians.
- Data for Radio Engineers**—*Federal T. & R.* No. 66...\$3.75
675 pages, 5½ by 8½ ins., cloth. Revised edition of this comprehensive reference giving data on all phases of radio engineering.
- Radio Eng. Handbook**—by *Keith Heuney*. No. 67...\$10.00
1,197 pages, 6 by 9 ins., cloth. The 4th edition contains the latest revisions on all material pertaining to electronics and radio.
- Electrical Eng. Handbook, Vol. 2**—*Pender*. No. 68...\$8.50
1,564 pages, 5½ by 8½ ins., cloth. Covers field of communications, including facsimile, FM, TV, and latest pulse techniques.
- Radio Engineers Handbook**—*Terman*. No. 69...\$9.00
1,019 pages, 6 by 9 ins., cloth. A wealth of technical information. Specially selected for application toward practical radio problems.
- Microphones**—by *Engineering Staff, BBC*. No. 73...\$3.25
114 pages, 5½ by 8½ ins., cloth. Covers the theory, design, and characteristics of all standard microphone types.

MISCELLANEOUS

- Radio and TV Almanac**—by *O. E. Dunlap*. No. 71...\$4.00
211 pages, 5¼ by 8 ins., cloth. A chronological record of facts, dates, and people important in the history of radio and television.
- Short-Wave Radiation Phenomena**—*Hurd*. No. 72...\$20.00
1,382 pages, 6 by 9¼ ins., cloth. Two volumes, not sold separately. A comprehensive treatment of propagation theory and applications.

Book List Department, RADIO COMMUNICATION, Great Barrington, Mass.

I enclose \$..... for which please send me the books indicated by circled numbers below. (No. C.O.D.'s, please.)

40	41	42	43	44	45	47	48	49	50	51
52	53	54	55	56	58	59	60	61	62	63
64	65	66	67	68	69	71	72	73	95	98


Name

Address

THE **complete answer** TO **uhf** SOCKET PROBLEMS—

“MYCALEX 410”

7- AND 9-PIN UHF SOCKETS

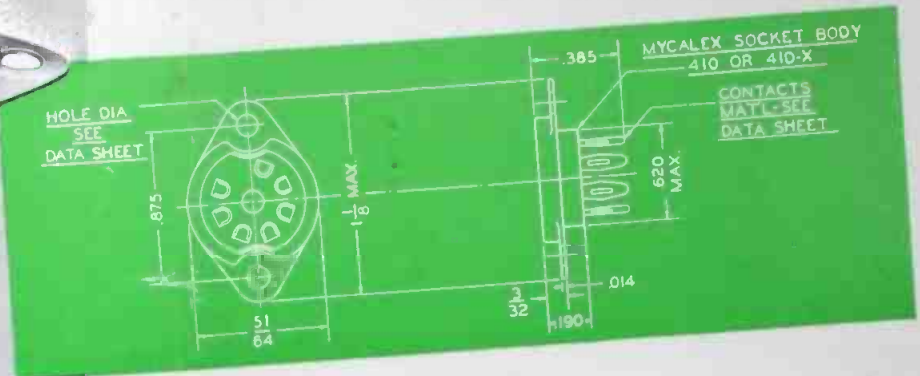

... ELECTRICALLY EFFICIENT!

... MECHANICALLY PERFECT!

- LOW INTER-ELECTRODE CAPACITANCE
- VERY LOW DIELECTRIC LOSS
- HIGH DIELECTRIC STRENGTH
- PERMANENT DIMENSIONAL STABILITY
- NON-HYGROSCOPIC, NON-WARPING

INFORMATIVE DATA SHEETS AVAILABLE!

Write for your complete set, together with loose-leaf binder for instant, easy reference. Your request will automatically assure prompt forwarding of all subsequent Mycalex data sheets and catalog material. Write on company letterhead please.

MYCALEX engineers designed these sockets to provide a complete, yet economical, solution to UHF tube mounting problems. Exhaustive tests have proven their mechanical excellence and high electrical efficiency. The use of “MYCALEX 410” (injection molded glass-bonded mica) with its great dimensional stability permits a minimum amount of dielectric to be used in the body structure. This plus other unique design features results in extremely low inter-electrode capacitance. In addition to its other advantages—high arc resistance, high dielectric strength, non-porosity, etc., “MYCALEX 410” has very low dielectric loss at all frequencies including UHF and thereby offers great advantage over phenolic materials. “MYCALEX 410” operates continuously in temperatures up to 650° F with practically no change in electrical properties or mechanical structure. Soldering operations will not cause body distortion.

MYCALEX TUBE SOCKET CORPORATION

Under exclusive License of Mycolex Corporation of America • 30 ROCKEFELLER PLAZA, N. Y. 20

TROUBLE-FREE CONTACT TERMINALS!

Contact terminals on these sockets are so designed that the effective inductance from soldered connection to the tube base is no greater than if the connection was made directly to the tube pin. Special design results in high contact area pressure that effectively reduces contact resistance. Contact terminals are secured in the body in a manner that permits 90° bending of the tab without weakening.

ALL TYPES OF MOUNTING HARDWARE!

“MYCALEX 410” UHF Sockets, 7 or 9 pin, can be furnished mounted in various standard saddle hardware—regular saddles (top or bottom mounted), saddles with ground lugs, snap or JAN types, permitting the use of radio tube shields.



MYCALEX CORPORATION OF AMERICA

Owners of ‘MYCALEX’ Patents and Trade-Marks

Executive Offices: 30 ROCKEFELLER PLAZA, NEW YORK 20 • Plant & General Offices: CLIFTON, N. J.