

ELECTRONIC

Servicing & Technology

APRIL 1986/\$2.25

TV camera test bench • Constant-current generators

Servicing Penney's vertical and luminance circuits

Oscilloscope gives paper copy



LEADER



Sometimes it's hard to go back for a scope!

60-MHz full-function field-service Attache Case Oscilloscope is so light and small it will be taken everywhere, every time.

LBO-325 packs all the power and performance of a cumbersome, backbreaking, 60-MHz workbench oscilloscope into an easy-to-carry, ultra-compact, featherweight unit. Although its 3½-inch CRT is as big and clear as screens on large field-service scopes—LBO-325 weighs only 9 lbs. So it won't weigh field-technicians down, no matter how far afield they go! LBO-325 is so small it fits inside a 3-inch deep attache case with room to spare for a multimeter, service manuals and some tools. The ideal full-function scope for a cramped work area or crowded bench.

Reduces the cost of service calls.

Time is money. A scope left in the vehicle takes time to retrieve. One kept in the shop causes repeat service calls. The LBO-325




Attache Case Oscilloscope is so easy to carry and use, techs will take it everywhere, every time. And the time saved translates into extra profits for years to come.

Outperforms all other portables:

- 60 MHz • Dual channel • ALT TIME BASE simultaneously displays main waveform and any expanded portion
- ALT TRIG for stable display of 2 asynchronous signals • Bright, sharp 12-kV trace • Large 3½-inch PDA CRT • Illuminated graticule
- Comprehensive triggering • TV-V and TV-H sync separators • Variable trigger hold-off • Delay line shows sharp leading edges • CH-1 output drives low-sensitivity instruments
- Measures only 3 x 9 x 11¾ inches • Weighs 9 lbs.

Two-year warranty.

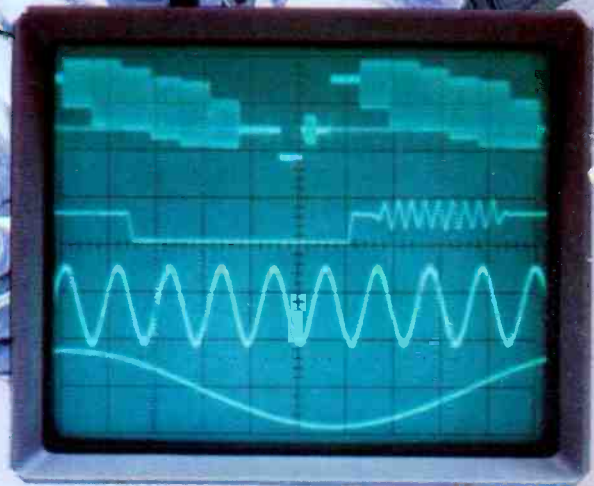Built tough to provide long use, LBO-325 is backed by Leader's 30-year reputation for reliability and by factory service depots on both coasts.



LBO-325 CRT is shown actual size.

Call toll-free
(800) 645-5104
In NY State
(516) 231-6900

Request an evaluation sample, or our latest Test Instrument Catalog with over 100 outstanding products, the name and address of your nearest "Select" Leader Distributor or additional information.

For professionals who know the difference.

LEADER
Instruments Corporation

380 Oser Avenue
Hauppauge, New York 11788
Regional Offices: Chicago, Dallas
Los Angeles, Boston, Atlanta
In Canada call Omnitronix Ltd.
(514) 337-9500

For Information Circle (1) On Reply Card
For Demonstration Circle (2) On Reply Card



Advanced Chemistry for Advanced Technology



Advances in engineering and design create constant challenges for the assembly, maintenance and repair of electronic equipment. To meet those challenges, Chemtronics is dedicated to providing you with only the finest, state of the art products. Each year, our R & D staff spends hundreds of hours testing and improving each product to ensure that your electronic components, systems and equipment perform at their designed rate of efficiency.

In production and rework... engineers depend on Chemtronics UL approved conformal coatings, QPL approved solders and masking agents, high purity degreasers, flux removers, anti-static sprays and non-contaminating desoldering braids. In field service... engineers and technicians depend on Chemtronics magnetic head/disc cleaners, non-residual wipes, foam swabs, dust removers, circuit refrigerants and contact cleaners.



Chemtronics

Keeping pace with advanced technology.

To help determine the Chemtronics products that are right for you, write us or call 800-645-5244, in New York 516-582-3322.

Chemtronics Inc.
681 Old Willets Path
Hauppauge, New York 11788
Circle (4) on Reply Card

ELECTRONIC

Servicing & Technology

Volume 6, No. 4 April 1986

10

Test your electronic knowledge

By Sam Wilson

Questions this month are based on 1985 issues of **Electronic Servicing & Technology**; attentive subscribers have the edge when mind-searching subjects such as materials technology, high-definition television (HDTV), and a new noise-reducing technique for FM stereo, all subjects that have been featured in **ES&T**.

12

TV camera test bench — a setup to speed checks and adjustments

By Gerald P. McGinty

Faced with so much technology compacted in such small space, technicians often find TV camera adjustments inhibiting unless they capitalize on the fullest capabilities of their test equipment such as the delayed-sweep scope, vectorscope and B&W picture monitor.



page 8

There are a number of convenience features on new oscilloscopes, not the least of which being a printed record of on-screen displays. (Photo courtesy of BBC-Metrawatt/Goerz.)



page 12

Proper equipment and a well-organized test bench can reduce technicians' frustrations and save time when testing TV color cameras.

22

Servicing Penney's vertical and luminance circuits

By Homer L. Davidson

A servicing pattern evolves after a period of time for every model of electronics equipment — a fact exemplified by the trend-setting, trouble-making vertical and luminance circuits of J C Penney's 685-2039 color receiver, for which a modification kit is now available because of the secondary effects of these problems.

58

What do you know about electronics — constant-current generators


By Sam Wilson

Some electronic circuits must be supplied with current that does not vary even though the load resistance may change. This constant current may be provided by a constant-current generator. Sam Wilson describes circuits that deliver constant current and discusses several of their applications in today's electronics.

Departments:

- 4 Editorial
- 6 News
- 8 Technology
- 66 Symcure
- 67 Products
- 69 Photofact
- 72 Literature
- 73 Books
- 74 Reader's Exchange

TECHNICAL QUESTIONS?

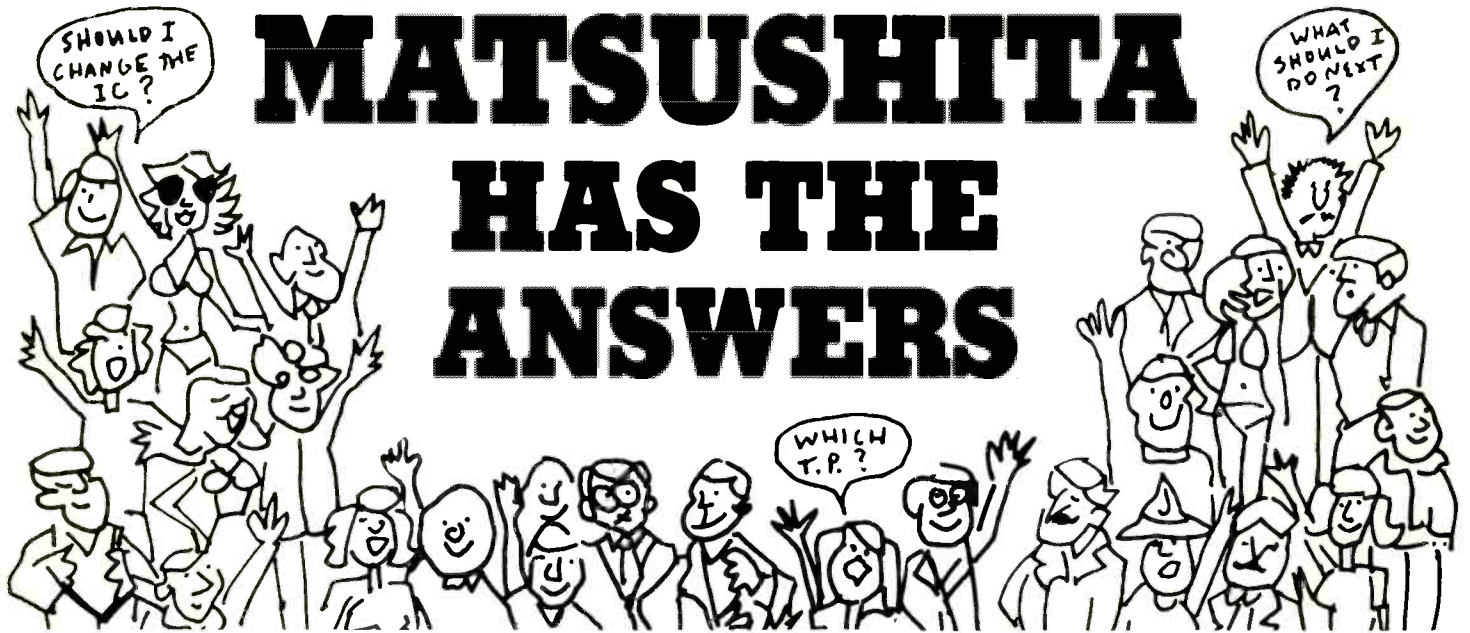

The questions asked by service technicians concerning today's higher technology products need answering now! Over the past few years, the technological advances made by MATSUSHITA in the areas such as video, audio, telephone, office products, home appliances and the like have been astounding, and will continue to be so!

These advances appear in many of the newer MATSUSHITA products from **Panasonic**, **Technics**, and **Quasar**. The knowledge and skills required for today's service is more advanced than 5 or 10 years ago.

The MATSUSHITA SERVICES COMPANY fully realizes the urgency of the situation. With more than 20 years experience in the service and parts business, we feel that no one understands the needs of today's technicians any better than we do.

The MATSUSHITA SERVICES COMPANY publishes a wide range of technical training material intended to serve the technician. These video tapes, training manuals, troubleshooting guides and sets of service bulletin manuals are written with the technician in mind.

A booklet listing all of our video tapes and book titles, along with pricing and ordering information is available at no cost by completing and returning the form below.

We are more than just a leader in the service and parts industry, we're leading the way in technical training too!

MATSUSHITA SERVICES COMPANY

Engineering Support Division
50 Meadowland Parkway
Secaucus, New Jersey 07094

Attn: Publications Department

PLEASE SEND ME YOUR CATALOG LISTING ALL MATSUSHITA TRAINING LITERATURE

Name _____

Company _____

Address _____

Circle (5) on Reply Card

Practice makes perfect

There's an old joke about a young violinist who was scheduled to perform at Carnegie Hall. He was walking to get there and became hopelessly lost. As the time for his performance came closer, he became increasingly agitated. In desperation, he approached an old derelict and asked, "How do I get to Carnegie Hall?" The unfortunate one looked at the musician and said without hesitation, "Practice, my boy, practice."

It may be a dumb joke, but it's excellent advice, and it's advice that's followed every day. Musicians and other performing artists practice every day, frequently for hours on end. Golfers, whether professional or amateur, may be seen anywhere they can find a few square yards of grass, or even carpet, practicing their putts. It's generally true that the more performers practice, the better they'll be and the greater their chances of success.

What's true of performers is also true of technicians. The more technicians practice their craft, intelligently, the better practitioners they'll be.

Perhaps it is stretching things a bit to compare a technician's oscilloscope with the violinist's violin, or the golfer's set of clubs. Still, the oscilloscope is the technician's most versatile instrument and his most valuable tool, just as the violin is the musician's instrument and the golf clubs are the golfer's tool set.

But how many technicians take the time to practice using the oscilloscope under known conditions so they'll be prepared to apply it when they face a faulty unit? How many technicians

take the time to experiment with all of the controls, and study the instructions so that they know all the *functions* of all the controls, and are truly capable of a virtuoso performance? Not many, we would guess.

At this moment, the world of test equipment, and oscilloscopes in particular, is changing. Paradoxically, oscilloscopes are becoming both easier and harder to use. Some of today's more sophisticated oscilloscopes include a digital readout that tells the operator what the peak, average and RMS values of the waveform are, making it unnecessary for the operator to count graticule divisions and perform the elementary calculations to determine the waveform's parameters.

On the other hand, some of today's oscilloscopes are more complex to use and to understand simply because they can do so much more than the earlier models. Digital storage oscilloscopes, for example, can store a waveform indefinitely, and later return it to the screen where the operator can manipulate it in a number of ways to determine the condition of the circuit under study *at the time the waveform was stored*.

Golfers practice wherever they can find a flat surface, musicians practice constantly to be the best that they can be, football players, baseball players, writers, singers and many more experts practice constantly so that they will be at their best when they perform. Should we ask less of electronics servicing technicians?

Mike Conrad Pearson

If you can't fix your board with the enhanced 9000 Series, it's beyond repair.

Introducing a new dimension of test capabilities for the Fluke 9000 Series Micro-System Troubleshooter line.

Finally there's a way to conquer some of the most difficult board testing problems imaginable. Take control of the situation with Fluke's 9000 Series and new **Asynchronous Signature Probe** option. You'll be able to pinpoint virtually every digital hardware fault on the entire board. Even those frustrating faults in circuits that operate independently of the microprocessor bus cycle.

Begin testing boards with the 9000 Series' built-in, preprogrammed test routines. In a single keystroke, you can automatically check the entire microprocessor kernel—Bus, ROM, RAM and I/O.

For testing beyond the bus, Fluke's new probe option eliminates the need for a logic analyzer or scope to test asynchronous circuits. One complete package, easily installed into either new or existing 9000 Series units, offers signature analysis, waveform capture and event counting. These three vital troubleshooting functions give any 9000 Series the power to diagnose:

- DMA Controllers
- Disk Controllers
- Video Controllers
- Video-Generation Circuits
- Communication Circuits
- Peripheral Controllers
- Dynamic RAM timing relationships

Not only does the 9000 Series test more of the board, it also supports more 8-bit and 16-bit processors than any other tester on the market.

Call Fluke toll-free **1-800-426-0361** or contact your local representative, and put your most challenging board to the 9000 Series test. If it can't be fixed with the enhanced 9000, it's probably beyond repair.

FLUKE®

Circle (6) on Reply Card

President Reagan cites Electronics Technicians

Electronics technicians were honored nationally on March 4 with the inauguration of the first National Electronics Technicians Day. This special day recognizes the 20th year of the certification program, which is sponsored by the International Society of Certified Electronics Technicians, and the certification of the 20,000th electronics technician.

In his proclamation announcing National Electronics Technicians Day, President Reagan saluted the high standards of performance and excellence maintained by professional technicians and by ISCET in its 20 years of distinguished service to the electronics industry. He paid tribute to the vital part that electronics technicians play in helping to assure our country's continued technological and economic leadership as a formidable international competitor. In extending his personal congratulations to technicians who have met the demanding

criteria for certification, he recognized the individual skills, talent and expertise that make electronics technicians one of the country's most important technological resources.

In citing ISCET's significant growth and professionalism, ISCET Chairman Jim Parks applauded the many dedicated individuals who have devoted countless hours of their time to honor electronics technicians in a very tangible way. "The instructors, certification administrators, and the general membership of ISCET have, in their own way, honored the technician; ISCET's day of honor is only a small step toward recognizing their work," Parks said.

ISCET set aside March 4 as a national testing day for certification of electronics technicians. Many of the volunteer corps of ISCET test administrators used that day to encourage technicians all over the nation to demonstrate their own professionalism by taking the CET exam.

In order to make National Electronics Technicians Day an official commemorative holiday, people involved in the electronics industry are asked to contact their senators and representatives to request their support for House Joint Resolution 507 (HJRes507) in-

troduced by Representative Martin Frost, D-TX.

For more information on National Electronics Technicians Day or House Joint Resolution 507, contact the ISCET offices at 2708 W. Berry St., Fort Worth, TX 76109; 817-921-9101.

1985 outstanding for VCR sales

With sales of videocassette recorders topping 1.9 million units in December (the equivalent of more than 60,000 per day), VCR sales during 1985 soared to 11.8 million units, a 55% jump over 1984's 7.6 million. That total surpassed EIA's forecast that 11.5 million would be sold to dealers in 1985. At Winter Consumer Electronics Show in Las Vegas, EIA predicted that, in view of the fact that VCRs are now in 30 percent of American households, sales in 1986 are expected to grow at a more modest rate, to approximately 12.5 million units.

Color TV sales in 1985 numbered nearly 17 million units, easily the best year in the 32-year history of that product. With 5.7% growth, color TV sales far exceeded the 16.1 million unit figure posted in 1984.

Projection television registered even more dramatic growth last year, increasing 36% to about 266,000 units.

ELECTRONIC

Servicing & Technology

Editorial, advertising and circulation correspondence should be addressed to: P.O. Box 12901, Overland Park, KS 66212-9981 (a suburb of Kansas City, MO); (913) 888-4664.

EDITORIAL

Nils Conrad Persson, *Editor*
 Carl Babcoke, *Consumer Servicing Consultant*
 Dan Torchia, *Group Managing Editor*
 Marjorie Riggan, *Associate Editor*
 Joy Culver, *Editorial Assistant*
 Darryll Fortune, *Editorial Assistant*

CONSULTING EDITORS

Homer L. Davidson
 Christopher H. Fenton
 Bud Izen
 Victor Meeldijk
 Kirk G. Vistain
 Sam Wilson

ART

Kevin Callahan, *Art Director*
 Tim Lynch, *Graphic Designer*

BUSINESS

Cameron Bishop, *Group Vice President*
 Eric Jacobson, *Publisher*
 Greg Garrison, *Sales Manager*
 Stephanie Fagan, *Promotions Manager*
 Kelly Hawthorne, *Marketing Assistant*
 Dee Jinger, *Advertising Supervisor*
 Karen Royall, *Advertising Coordinator*

ADMINISTRATION

R. J. Hancock, *President*
 John C. Arnst, *Circulation Director*
 Jo Ann DeSmet, *Circulation Manager*
 Dee Manies, *Reader Correspondent*



Member, Audit Bureau of Circulation



Member, American Business Press



Member, Electronic Servicing Dealers Association

ELECTRONIC SERVICING & TECHNOLOGY is the "how-to" magazine of electronics. It is edited for electronic professionals and enthusiasts who are interested in buying, building, installing and repairing consumer electronic equipment. This includes audio and video equipment, microcomputers and electronic games.


SUBSCRIPTION PRICES: one year \$18, two years \$30, three years \$38 in the USA and its possessions. Foreign countries: one year \$22, two years \$34, three years \$44. Single copy price \$2.25; back copies \$3.00. Adjustment necessitated by subscription termination to single copy rate. Allow 6 to 8 weeks delivery for change of address. Allow 6 to 8 weeks for new subscriptions.

PHOTOCOPY RIGHTS: Permission to photocopy for internal or personal use is granted by Intertec Publishing Corp. for libraries and others registered with Copyright Clearance Center (CCC), provided the base fee of \$2 per copy of article is paid directly to CCC, 21 Congress St., Salem, MA 01970. Special requests should be addressed to Eric Jacobson, publisher.
 ISSN 0278-9922 \$2.00 + 0.00



©1986 All rights reserved.

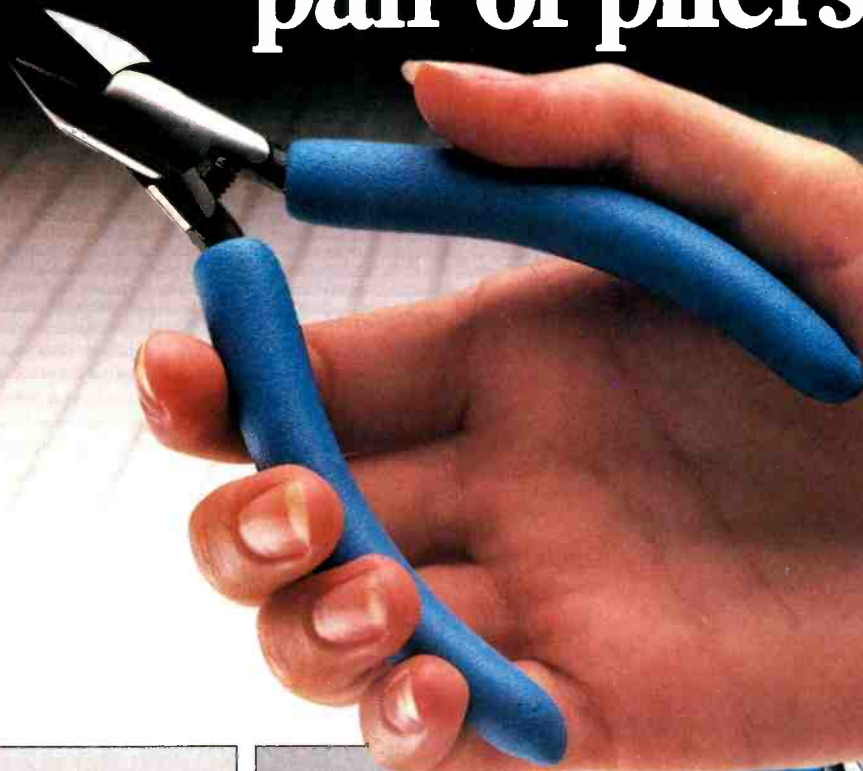For all those hands aching for a more comfortable pair of pliers.



The non-slip cushioned foam grips will give day long comfort from assembly fatigue.



The streamline cross sections have been designed to allow easy access to tight working areas. The unique oval joints look good, too.



With this wide variety of designs, Xcelite® can come to grips with any electronics task, comfortably! Check with your Electronics Distributor.



Xcelite® Electronics Pliers.

CooperTools



CRESCENT® LUFKIN® NICHOLSON® PLUMB® TURNER® WELLER® WIRE-WRAP® WISS® XCELITE®
The Cooper Group PO Box 728 Apex NC, 27502 USA Tel (919) 362-7510 Telex 579497

Circle (7) on Reply Card

BACK AMERICA

Digital oscilloscope gives paper copy of information on scope face

Oscilloscopes have undergone considerable change and improvement in the last few years. Bandwidths have increased greatly, trace rise times have become even smaller, the addition of digital circuitry has made it possible to capture a waveform and store it for any length of time, manipulate it, compare it with other waveforms and learn just about everything there is to know about it.

Other recent innovations have made the oscilloscope easier to use. On-screen or meter displays give readings directly in volts, time or frequency, eliminating the need to count graticule divisions, factor-in control settings and calculate parameters.

A recently introduced oscilloscope provides many innovations such as these and *in addition*: A.) makes it possible to display logic timing signals instead of, or

in addition to, analog signals, B.) will give a paper hard copy of what was displayed on the scope face and C.) store the information in a non-volatile memory for later recall.

The SE 571 Digitalscope by BBC-Metrawatt/Goerz is a 2-channel oscilloscope when used to analyze signals. When digital circuits are encountered it will function as an 8-channel logic timing analyzer.

Because this is a digital oscilloscope, a number of convenience features have been made possible. For example, the amplifier sensitivity and timebase are automatically selected based on the nature of the waveform to be studied. In addition, there are two cursors that are used to determine waveform values.

If you want to determine voltage between two points on the waveform, for example, you merely



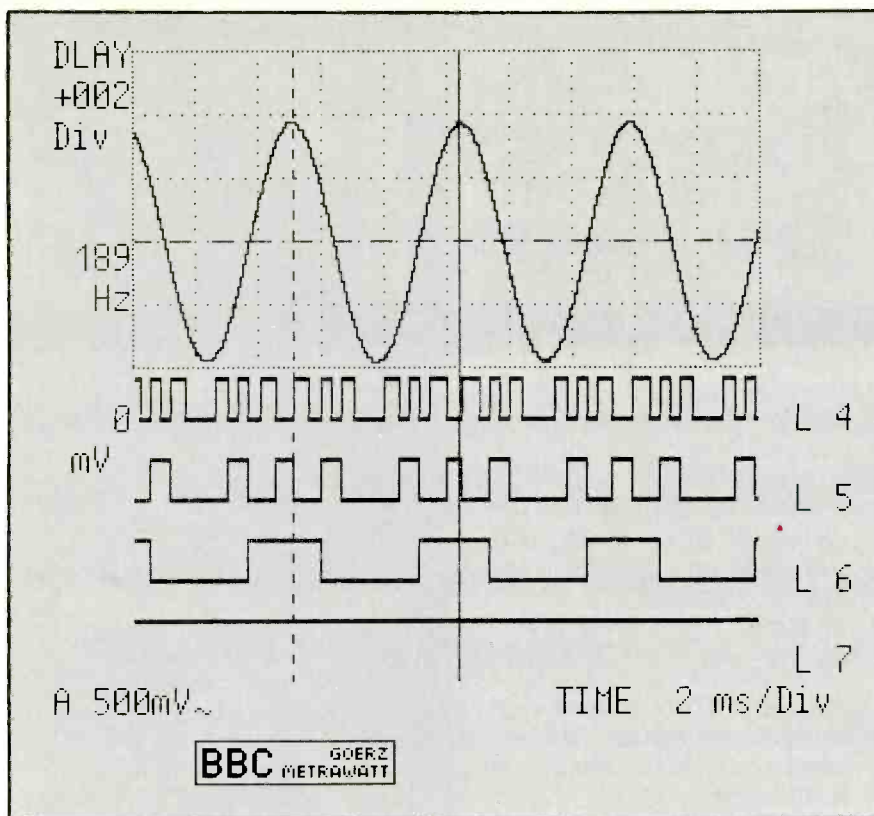


Figure 1. Oscilloscope paper copy looks like this. All information displayed on the screen is printed out on paper. This same information may be stored in a non-volatile memory. The paper copy requires about 10 seconds to produce.

place the reference cursor on one of the points of interest, move the main cursor to the other point and observe the numerical readout on the scope face. The readout will give you voltage difference and the time difference (or frequency) between the two cursors, and the voltage at the main cursor.

The display can be selected in a number of ways, depending on the circuitry to be tested. For analog signals only, the unit may be set up as a dual trace scope, allowing the user to examine a single waveform or to compare two waveforms. For examining digital circuits, the unit can be used to view up to eight logic timing diagrams. If the circuit under test requires analysis of both analog and digital waveforms at the same time, the instrument will display an analog signal on the A channel and the timing diagrams of up to four digital circuits.

When it becomes desirable to make a paper copy of the waveform and other information displayed on the scope face, all that's necessary is to select this feature, and in about 10 seconds the thermal printer produces an exact copy of what is on the scope face along with the date and time.

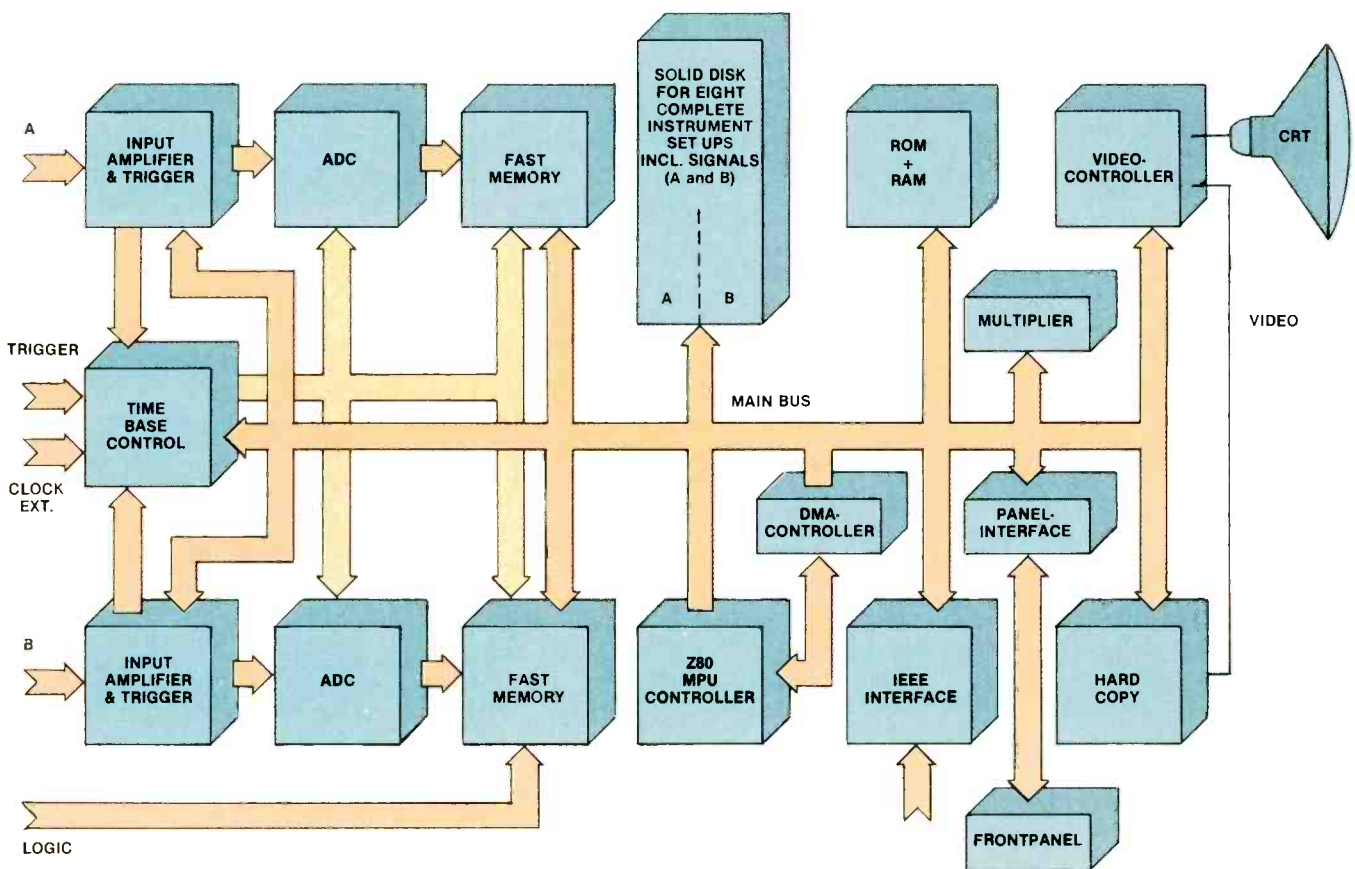


Figure 2. Block diagram shows major subsystems of printing digital oscilloscope.



TV camera test bench

A setup to speed checks and adjustments

By Gerald P. McGinty

TV cameras, especially those made for the consumer market, are forbidding to servicing technicians in terms of the wealth of technology packed into an extremely small package. A lot of time is wasted searching for test points; a job that is doubled in many cases because the service manual directs the technician to a second TP for scope trigger purposes. Some important routine checks like the accuracy of the sub-carrier frequency may not be made simply because the sync generator board is fully shielded or difficult to get to.

Much of the frustration associated with camera checks and adjustments can be eliminated if test equipment is used to the fullest. This article discusses using the scope, pattern generator, vectorscope, frequency counter and picture monitor to speed and simplify the job.

The video route

Figure 1 shows a block diagram of a suggested route for video from the camera to the picture monitor. Let's look at each of the components in the chain. The signal is first bridged to one of the vertical inputs of a dual-trace scope. The scope must be near the camera so it is nearest along the signal path. I use Channel 2 for this purpose and route video in via a BNC T connector. From the T the signal is routed to the picture monitor and terminated there.

Trigger the scope from CH-2 at all times. The camera puts out composite sync even when the lens is capped so a positive source for line and field-rate triggering is present whenever power is turned on at the camera. The scope should have H and V TV-sync separators so that you can change from H-rate to V-rate waveforms simply by flipping the sync coupling switch on the scope and making

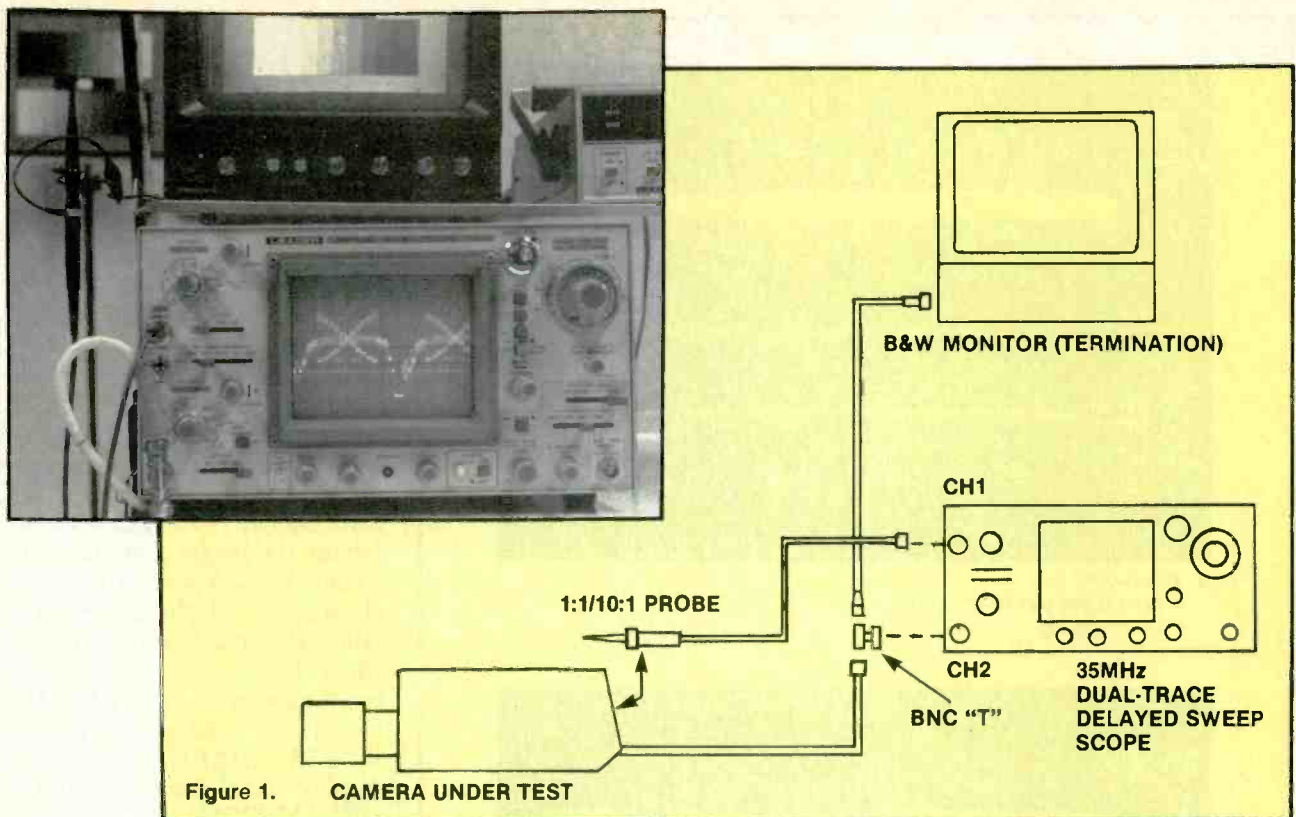


Figure 1. When you're setting up a video camera test bench, connecting video test equipment as shown here results in efficient testing with a minimum of frustration.

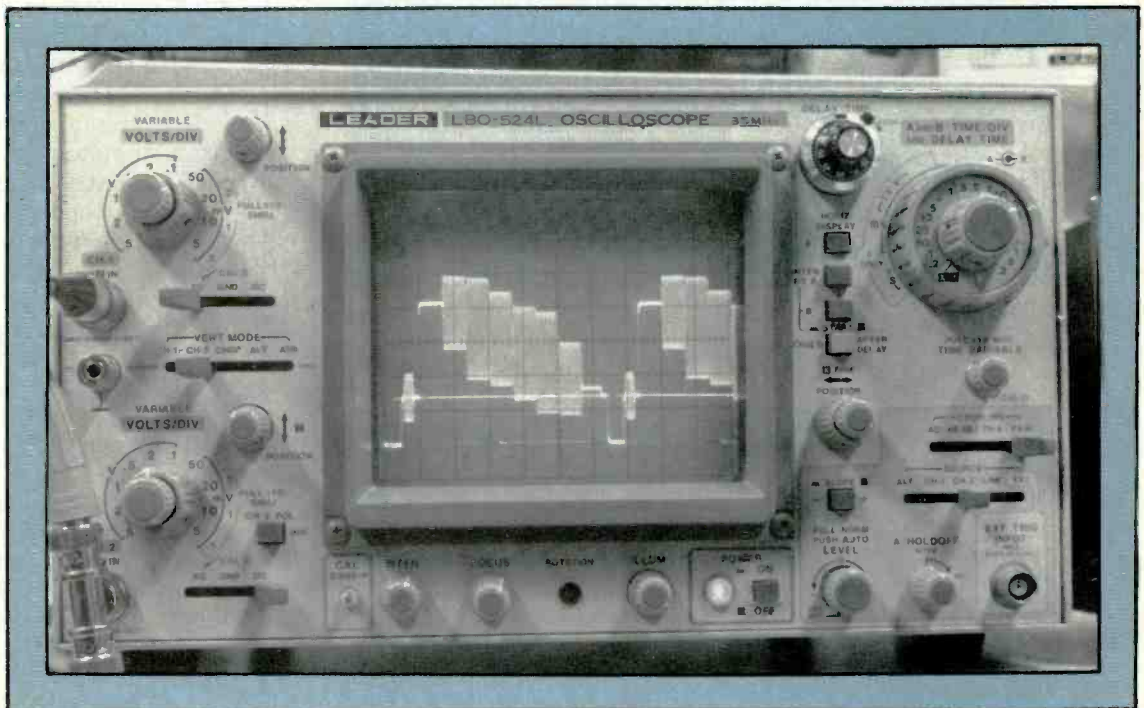


Figure 2. Connecting the scope in this manner (see text for details) gives you a source of positive trigger without having to search. It also makes it easy to switch back and forth from internal- to camera-output waveform.

the necessary change on the time-base selector (2ms/cm for V and 10 μ s/cm for H-rate displays).


Connect a switchable 10:1/1:1 probe to the CH-1 input jack. Use this probe for all camera internal waveform checks, but continue to trigger from CH-2 for all H and V

related signals. See Figure 2.


With this setup, you always have positive trigger with no need to search for a separate trigger source. Furthermore, you easily can switch back and forth from internal waveforms to the camera output waveform by flipping the

VERT MODE switch. And, of course, you can view both waveforms simultaneously.

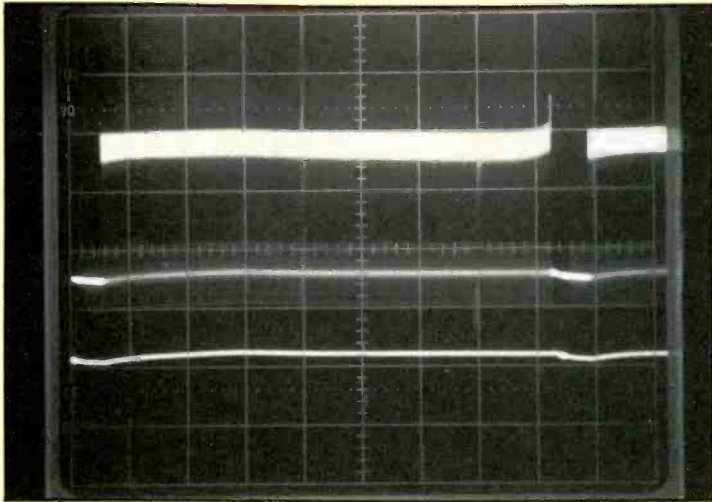
Delayed sweep is needed for many adjustments in single-tube color cameras because it is necessary to look at one or two raster lines in the vertical center



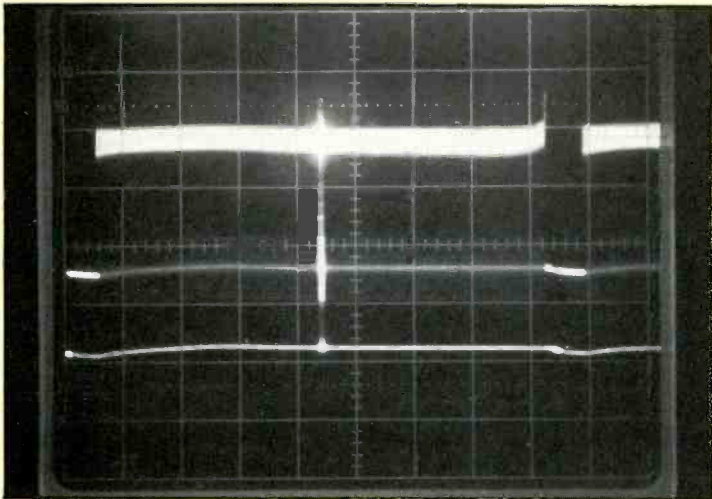a. Video out
A time base set to 2ms/cm
TV-V coupling



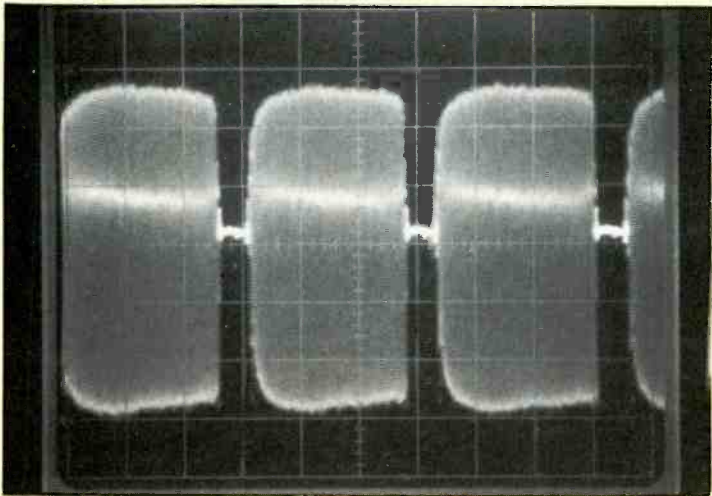b. Video out
A intensified by B
B time base set to 20μs/cm



c. B time base
Camera pre-amp output
Camera framed on white card

Figure 3. Steps in viewing three raster lines near the center of the picture.

of the picture. Figure 3 shows the steps involved in viewing three lines in the vertical center of the raster. In this case, the waveform is pre-amp output.

Start by observing video output by setting the scope's VERT MODE switch to CH-2. Trigger the scope as usual from CH-2. Set the COUPLING switch to TV-V, and set the A time base to 2 ms/cm. See Figure 3a. Now set the HORIZ DISPLAY for A intensified by B, and set the B time base to 20μs/cm. A bright vertical line representing the B time base will appear on the waveform. Adjust the DELAY TIME control to center the bright zone midway between the vertical sync pulses as shown at b of the figure. At this point you can connect the CH-1 probe to the pre-amp output test point, and set the VERT MODE switch to view CH-1. Reset the HORIZ DISPLAY switch to display the B time base and reset DELAY TIME as needed. The final waveform, three raster lines in the vertical center of the picture, is shown in Figure 3c.

Do you need a waveform monitor?

Not in my opinion. The waveform monitor is certainly convenient, but it is basically a special-purpose scope. Your 35MHz (or better), dual-trace delayed-sweep scope will do everything a waveform monitor will do except facilitate certain operational uses. What the waveform monitor cannot do for you is go inside the camera. It is made to handle standard level (1Vp-p) signals at 75Ω. One thing the waveform monitor *does* do is read out in IRE units for standard level signals. If levels are given in the service data in IRE units, you will have to convert them to volts for scope readings. This is done with the formula:

$$V_x = \text{Value in IRE}/140$$

Table 1 lists some key video voltage values for equivalent IRE values.

Adding a vectorscope

Although a waveform monitor can be left out of the setup, there really is no substitute for a vectorscope. The vectorscope is needed to adjust the camera color encoder. It provides a polar display

Simpson Electric Co.
Introduces

mercer

The Ultimate in Low-Cost Test Equipment

At last! Here is your opportunity to take your pick from a new test equipment line that has all the features you need and more... and at a price that is unbelievably low.

MODEL 9340
Pocket size 3½-digit
DMM with 20 megohm
range and 10 megohm
input resistance
\$44⁰⁰

MODEL 9670
Digital capacitance
tester covering 0.1 pF
to 20,000 µF
\$99⁰⁰

MODEL 9101
Compact VOM with 27
ranges, including a
100 megohm range
\$29⁰⁰

MODEL 9301
3½-digit, hand-held
DMM with 0.25%
basic accuracy and
2,000-hour battery life
\$69⁰⁰

MODEL 9120
Analog VOM with 12 A
DC range and output
jacks
\$35⁰⁰

MODEL 9401
4½-digit, full function,
hand-held DMM with
.05% accuracy and
data hold
\$129⁰⁰

MODEL 9701
digi-clamp™ compact
AC clamp-on volt-ohm-
ammeter with data hold
\$69⁰⁰

MODEL 9370
3½-digit autoranging
DMM with a memory
mode and 0.5% basic
DC accuracy
\$59⁰⁰

mercer

ELECTRONICS

Division of Simpson Electric Company

859 Dundee Avenue, Elgin, IL 60120-3090
(312) 697-2265 • Telex 72-2416

Mercer Electronics products reflect the design and quality standards established by Simpson Electric Company, an industry leader for over 70 years and known worldwide for its integrity and product excellence.

In Stock... Available Now! Stop in at your nearest distributor and see this new, complete line of Mercer test instruments. For the name of the MERCER distributor in your area, call (312) 697-2265, or send for our new line catalog.

in which the phase angle of each of the color bars (except white) is shown as an angle measured from burst and amplitude as the length of the vector measured from the origin. For color bars generated from electronic color-bar generators built into the camera, the display shows up as bright spots that should be within the small targets on the vectorscope graticule. See Figure 4. The small targets represent a tolerance of $\pm 2.5^\circ$ in phase and ± 1.5 IRE units in amplitude. The encoder is aligned to place each of the primary and complementary dots as well as the dots for burst at the designated locations on the vectorscope graticule. The vectorscope shown in Figure 4 makes use of electronically generated targets as well as a conventional, internally etched graticule. However, the electronic targets make encoder-alignment much easier because they are unaffected by centering controls and can be seen from a distance. It is usually necessary to fuss with centering controls and align your eye with the long axis of the CRT when using many vectorscopes.

For consumer cameras that do not use built-in electronic color-bar generators, the service data usually specifies angle and amplitude data for the color bars obtained when the camera is framed on a specified reflective or transparent color-chip test chart. In this case, the graticule targets cannot be used. Fully saturated colors cannot be obtained from any sort of test chart, so you have to use the phase angle and amplitude data published in the service data. Phase is measured CCW from the B-Y axis (burst is at 180°). The large increments on the outer graticule scale are 10° . Amplitude is somewhat more difficult because there are no scale readings outwards from the origin. To solve this problem, some manufacturers specify vector length in terms of the length of the burst vector. This amplitude is marked in the $-(B-Y)$ axis. A particular vector can thus be identified as a specific phase angle (with a tolerance given) and length with respect to burst. A color amplitude of $1.5B$ should read 1.5 times the length of the burst vector measured outwards from the origin. On the graticule of my

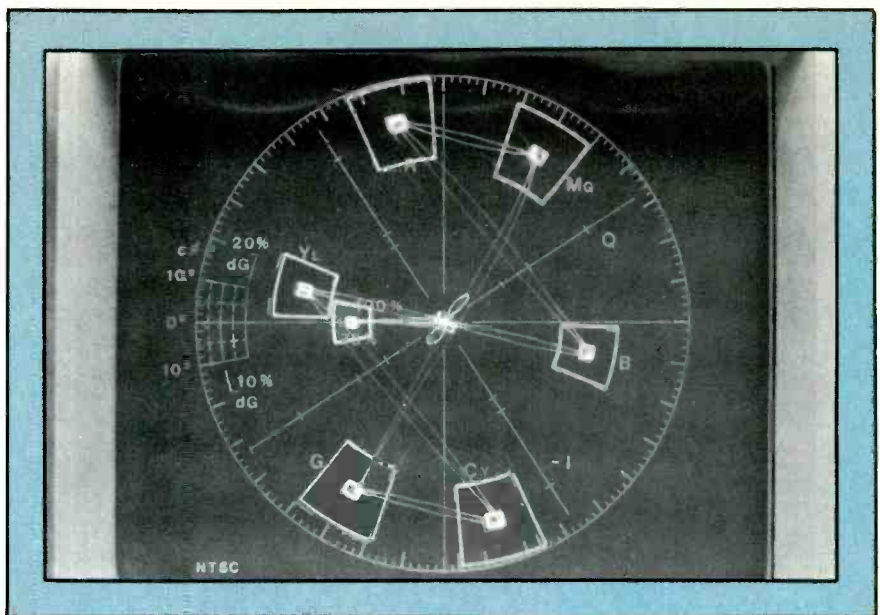


Figure 4. The vectorscope provides a polar display in which the phase angle of each of the color bars is shown as a dot at an angle measured from burst, and an amplitude of the length of the vector measured from the origin.

vectorscope, the burst vector is 15mm long, so it's easy enough to use a metric scale to measure vector amplitudes.

The vectorscope also helps when white-balancing the camera. This is done by making red and blue equal to green when the camera is

framed on a neutral gray scale chart illuminated by quartz-iodine lamps (3200K). When the three primaries are equalized, the color signals R-Y/B-Y or I and Q go to zero. Because the modulators in the encoder are balanced, subcarrier output disappears on all steps

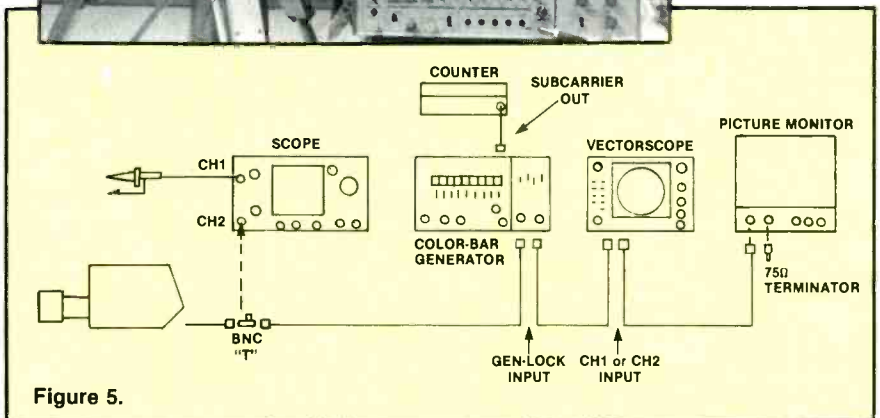
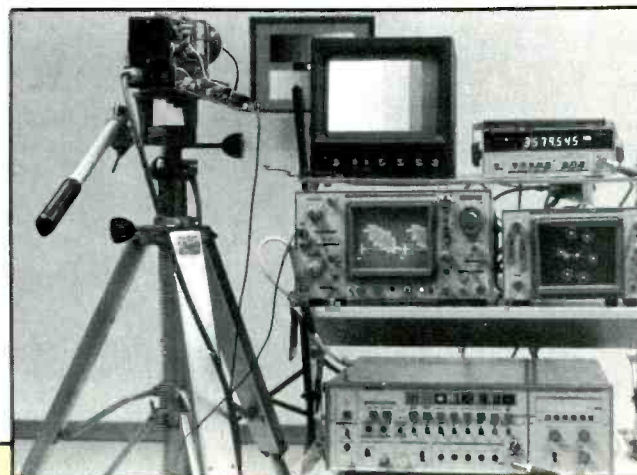


Figure 5. This more elaborate test setup provides for maximum versatility and efficiency for consumer color camera maintenance.

CIE CATALOG

Rush me CIE's COLOR CATALOG with complete details on electronics independent study. I understand there is no obligation. For your convenience, CIE will try to have a representative contact you — there is no obligation.

Name _____
(Please Print)

Address _____ Apt. _____

City _____ State _____ Zip _____

Age _____ Phone (area code) _____ / _____

Check Box For G.I. Bill Information: Veteran Active Duty

ES&T

ES-04

Detach and Mail This Postage-Paid Card Today



NO POSTAGE
NECESSARY
IF MAILED
IN THE
UNITED STATES

BUSINESS REPLY MAIL

FIRST CLASS PERMIT NO. 8685 CLEVELAND, OHIO


POSTAGE WILL BE PAID BY ADDRESSEE

CIE

Cleveland Institute of Electronics, Inc.

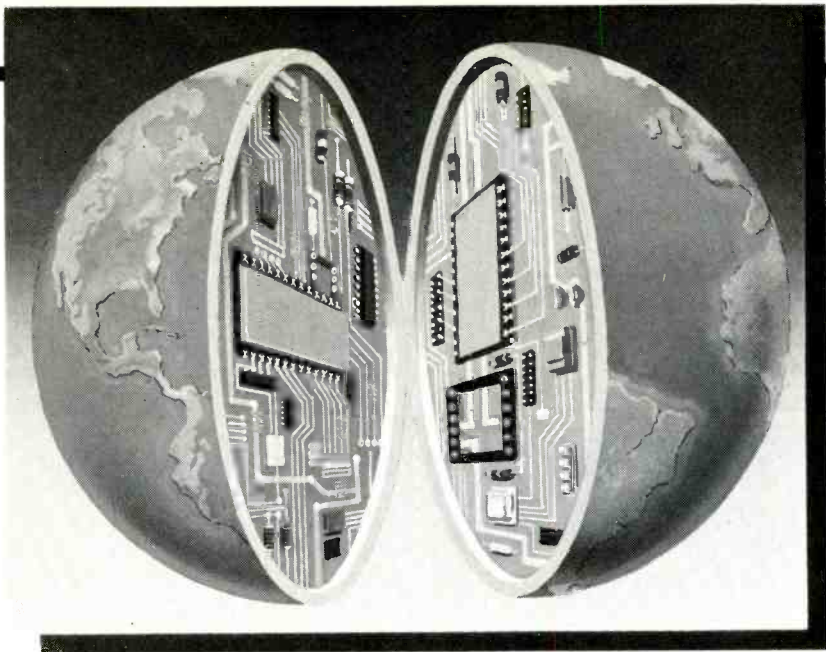1776 East 17th Street
Cleveland, Ohio 44114





CIE MAKES THE WORLD OF ELECTRONICS YOURS.

Today's world is the world of electronics. But to be a part of it, you need the right kind of training, the kind you get from CIE, the kind that can take you to a fast growing career in business, medicine, science, government, aerospace, communications, and more.

Specialized training.

You learn best from a specialist, and that's CIE. We're the leader in teaching electronics through independent study, we teach only electronics and we've been doing it for over 50 years. You can put that experience to work for you just like more than 25,000 CIE students are currently doing all around the world.

Practical training.

You learn best with practical training, so CIE's Auto-Programmed® lessons are designed to take you step-by-step, principle-by-principle. You also get valuable hands-on experience at every stage with sophisticated electronics tools CIE-designed for teaching. Our

4K RAM Microprocessor Training Laboratory, for example, trains you to work with a broad range of computers in a way that working with a single, stock computer simply can't.

Personalized training.

You learn best with flexible training, so we let you choose from a broad range of courses. You start with what you know, a little or a lot, and you go wherever you want, as far as you want. With CIE, you

can even earn your Associate in Applied Science Degree in Electronics Engineering Technology. Of course, you set your own pace, and, if you ever have questions or problems, our instructors are only a toll-free phone call away.

The first step is yours.

To find out more, mail in the coupon below. Or, if you prefer, call toll-free 1-800-321-2155 (in Ohio, 1-800-523-9109). We'll send you a copy of CIE's school catalog and a complete package of enrollment information. For your convenience, we'll try to have a representative contact you to answer your questions.



ES-03

CIE Cleveland Institute of Electronics

1776 East 17th St., Cleveland, Ohio 44114

YES! I want to get started. Send me my CIE school catalog including details about the Associate Degree Program. I am most interested in:

- | | |
|--|---|
| <input type="checkbox"/> computer repair | <input type="checkbox"/> television/high fidelity service |
| <input type="checkbox"/> telecommunications | <input type="checkbox"/> medical electronics |
| <input type="checkbox"/> robotics/automation | <input type="checkbox"/> broadcast engineering |
| <input type="checkbox"/> other _____ | |

Print Name _____

Address _____ Apt. _____

City _____ State _____ Zip _____

Age _____ Area Code/Phone No. _____

Check box for G.I. Bulletin on Educational Benefits

- Veteran Active Duty

MAIL TODAY!

OR CALL TOLL FREE 1-800-321-2155 (In Ohio, 1-800-523-9109)

Circle (13) on Reply Card

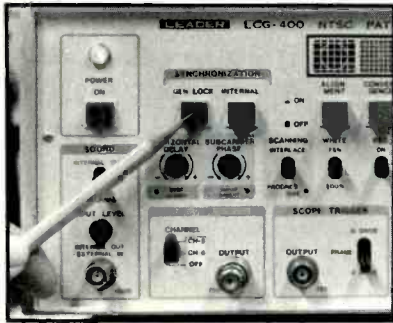


Figure 6. The GEN-LOCK feature on this pattern generator allows the generator's signal to be locked to the subcarrier frequency of the camera being tested, enabling you to check and adjust this signal without going inside the camera.

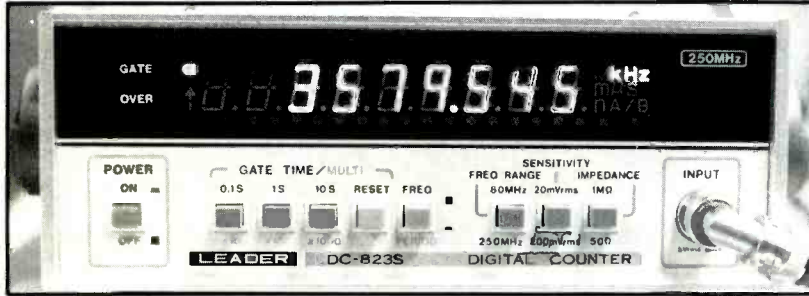


Figure 7. This frequency counter shows the reading from the color-bar generator locked to the camera output.

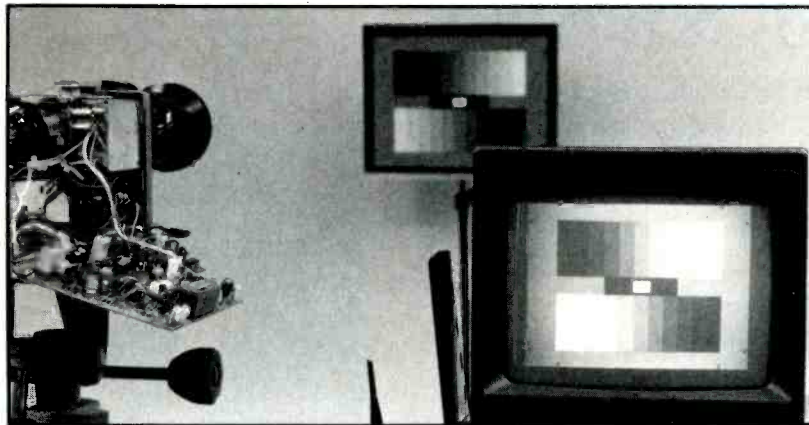


Figure 8. Picture monitor underscans for test-chart accuracy.

of the output waveform. On the vectorscope, deflection collapses to the origin.

The vectorscope is added to the test setup as shown in Figure 5 by making use of CH-1 or CH-2 loop-through connectors. A gen-lock pattern generator is also added in the figure. Here's why.

Measuring subcarrier frequency the easy way

Before any camera departs the shop, the frequency of its subcarrier oscillator should be checked and adjusted if necessary. A large error will prevent the monitor from locking to it. Even a small error will result in phase (hue) errors on the color monitor. The easiest way to check subcarrier frequency is to make use of the gen-lock

facility found in some pattern generators. Camera output is looped through the gen-lock jacks on the pattern generator as shown in Figure 5, and the generator set for GEN LOCK operation (the internal subcarrier clock is not used). See Figure 6. Now the generator phase locks to the burst signal produced by the camera under test. CW subcarrier output, available from a jack on the rear panel of the generator, then can be used to drive a frequency counter. In this way, the subcarrier frequency of the camera under test can be read and adjusted without going inside the camera for a CW feed. There is no reason to avoid this check. You can even do it with all the camera covers in place. See Figure 7.

There's a bonus from the hookup shown in Figure 5. That is, you can use off-air decoded video output of a VCR in place of a camera video to check the accuracy of your counter. By setting the tuner in the VCR to a network channel, you have a source of subcarrier frequency as accurate as ABC, CBS or NBC: 3.579545MHz on the nose. This makes it easy to know exactly where your counter is; you can check it as often as you like.

The picture monitor

The last item in the chain shown in Figure 5 is the picture monitor. Oddly enough, it should be a B&W monitor with a wideband video system. This permits accurate optical and electrical focus adjustments. (For single-tube cameras, electrical focus is extremely critical, and usually is set for maximum coded output from the pre-amp. The frequency of this signal, which carries the color information, is determined by the pitch of the color stripes on the faceplate of the pick-up tube.)

One prime requirement of the picture monitor is that it must be capable of *underscanned* operation. This makes the true sides, top and bottom of the visible (unblanked) raster visible. For the camera test charts to have any meaning, the test chart must be framed in the camera's field of view so that those arrows on the sides of the test pattern just touch the visible edges of the raster on the monitor screen. See Figure 8. The monitor shown in Figure 8 also has pulse cross-operation, which permits the sync and blanking signals to be observed. This also is handy for checking VCR video head switching points that usually are set for three lines above the start (top edge) of vertical blanking.

Since the picture monitor is the farthest from the camera along the cable route, it must terminate the line. Put a 75Ω terminator in the unused loop-through connector or switch on the internal terminator. All other equipment in the setup should be unterminated.

Video output from consumer cameras

The source of CH-2 signals described so far has been camera video output. This is easy to find in



ARM YOURSELF AGAINST STATIC WITH NTE'S NEW PATENTED FIELD SERVICE KIT.

Static electricity is a real hazard to sensitive electronic equipment. Now you can protect valuable components in the field and in the plant with NTE's new Field Service Kit. Our Kit includes everything you need to keep your equipment free of static — a 24" x 24" table top work mat, wrist strap with 8' coil cord, 15' clip-on grounding line and anti-static component storage bags. Both the wrist strap cord and grounding cord contain integral current limiting resistors.

Unlike other kits currently on the market, NTE's patented* three-layer construction produces controlled static drain,

eliminating the danger of sparking and the chance of additional component failure during the repair operation. The static-dissipative, vinyl work surface is durable and its bright green color enhances visibility. The entire Kit folds down into a compact unit and comes with its own zip-close bag.

Look for NTE's new Field Service Kit and our other static control products — including our anti-static foam, for shipping and storing equipment, and separately packaged wrist straps — at your local NTE distributor.

*Patent issued November 8, 1983.
U.S. Patent No. 4,414,260.



NTE ELECTRONICS, INC.

44 Farrand Street, Bloomfield, New Jersey 07003 • 201-748-5089
(Outside N.J.) 1-800-631-1250 • (N.J. only) 1-800-624-2624

Circle (14) on Reply Card


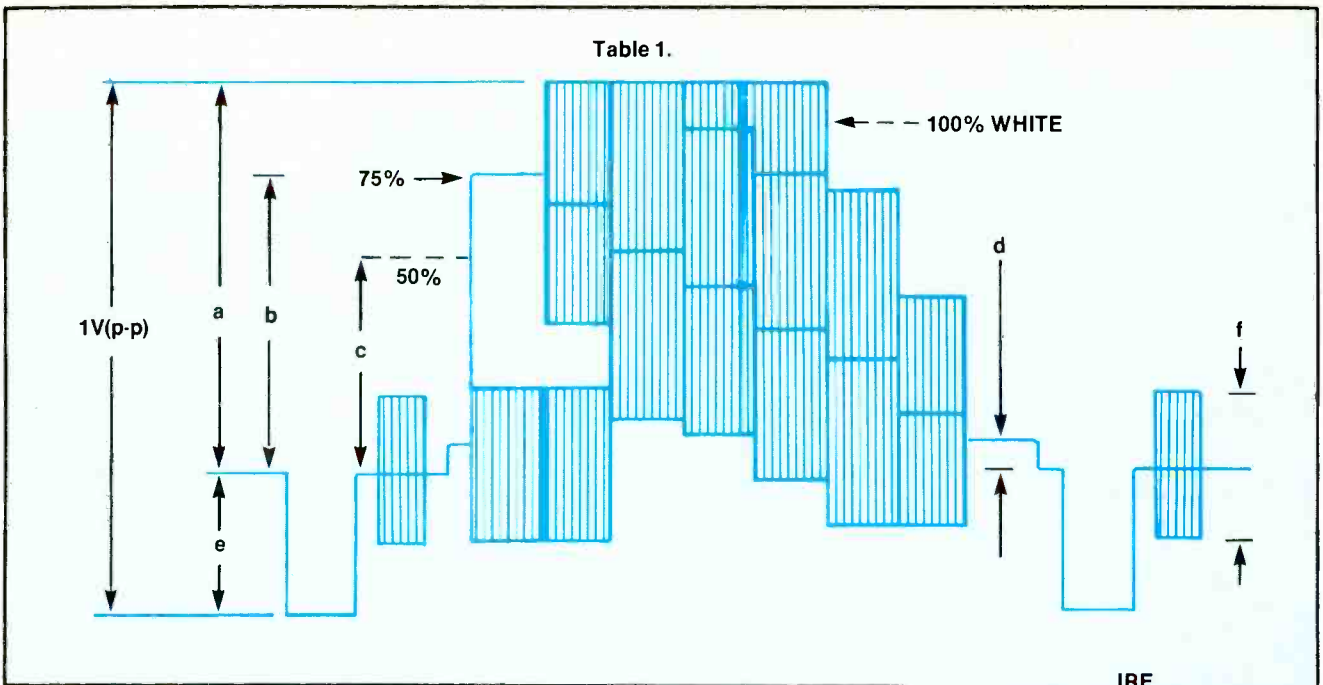


Table 1. Some key video voltage values for equivalent IRE unit values.

	ITEM	IRE UNITS	mV
a	100%	100	714
b	75%	77	550
c	50%	54	384
d	SETUP	7.5	54
e	SYNC	40	286
f	burst p-p	40	286

Figure 9. Camera cable branch-out provides separate output lines for video, audio and VCR control (pause) as well as 12Vdc input.

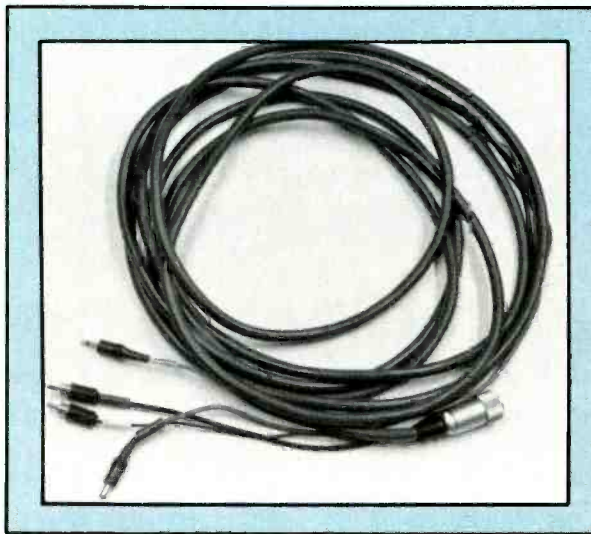

broadcast/industrial color cameras. They all have BNC VIDEO OUT connectors. For consumer-grade cameras it's not so easy: You have to make provision to branch out from the multi-pin connector at the end of the camera cable.

The simplest way to get video out from consumer cameras is to connect the camera cable to a matching VCR and take the video feed from the video out jack on the VCR. The VCR also supplies power (+12Vdc) in this case. However, the signal does pass through some processing in the VCR (video AGC) and this masks proper adjustment. An alternative is a branch-out cable like the one shown in Figure 9. These are available from the camera manufacturers. A separate 12Vdc supply is needed to supply power. Separate camera power supplies are available that output video directly (Ambico Model V-0605). An alternative is a test jack wired as shown in Figure 10. This provides video and audio out, dc power and a check of the camera VCR record stop-start system. The unit accommodates most VHS-compatible cameras. **ES&T**

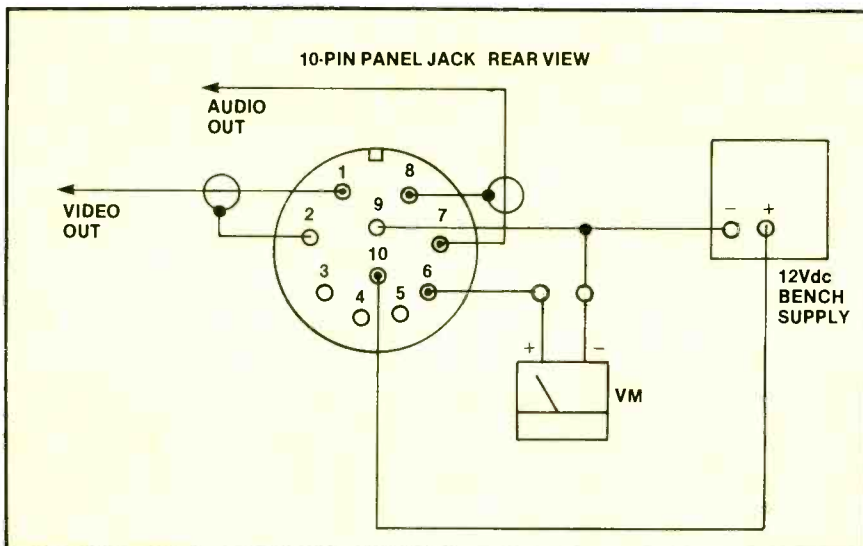


Figure 10. A test jack wired like this provides video and audio out, dc power and a check of the camera VCR record stop-start system.

ADVERTISEMENT



In less time than it took you to read just the first ten words of this sentence - - -

You could have diagnosed any problem, in any brand, solid state TV set down to circuit level, with 100% accuracy.

By simply plugging the set's AC cord into a self programming Mark VII computer, pushing one test button, and noticing which one of sixty lights are lit.

The light that is lit tells you which circuit or stage is not functional.

In nine out of ten instances, you can do so without even removing the back of the TV set! (Talk about fast estimates)

— INTERMITTANTS —
NO PROBLEM WHATEVER !

Leave the TV set's AC cord plugged into your Mark VII, leave the computer turned on, and go home for the weekend!

As soon as the set shuts down, or otherwise fails, the Mark VII will "Zero In" on **why** it failed, lite and latch the proper indicator light, automatically turn itself and the TV set off, then, sit there idle (with one light lit) awaiting your return.

All this by just plugging in the AC cord.
No other connections are required.

(In certain cases of low end, LV regulator shut down, you may have to bridge the LV regulator with an LV rect. other than this occasional inconvenience, no other connections are required. An adapter plug is provided for such instances.)

With a Mark VII you could accurately diagnose 400 TV sets down to circuit level in one 8 hour day. Unfortunately, you won't be able to replace the defective parts that quickly!

DIEHL

Call (806) 359-0329 for more info

6661 Canyon Dr. • Amarillo, TX 79110

Circle (15) on Reply Card

ADVERTISEMENT

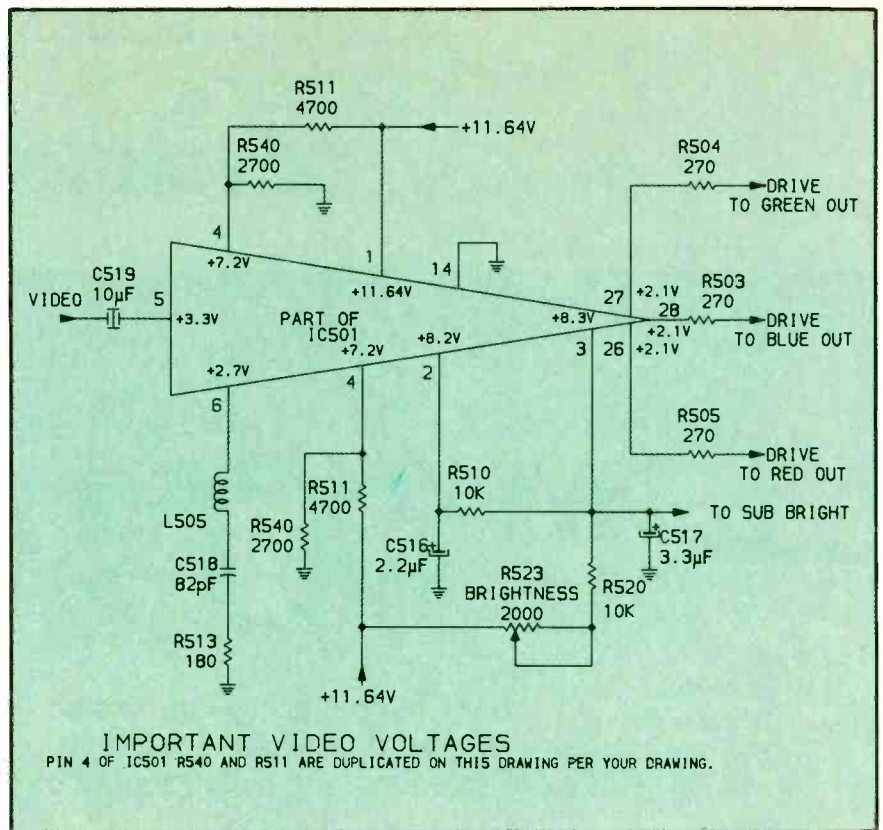



Figure 2. Video (luminance) enters IC501 at pin 5, and (except for being scoped at the pin 6 trap) is never found again without chrominance. Base signals for the red, blue and green color-output transistors come from IC501 pins 26, 28 and 27.

Any device that performs so many functions might be suspected of experiencing more than the usual amount of failures, and that is true here. A defective IC501 might cause loss of color, false color bars, loss of video, incorrect screen colors or a bright raster with retrace lines.

In early JC Penney 685-2039 models, replacing IC501 cured most luminance problems. However, the cure lasted only 30 days or so before IC501 went bad again, ruined by picture-tube arcs. A modification kit of zener diodes is available to protect the new IC501. This is described later.

My method of removing video/chroma IC501 is with solder wick and a 250W soldering gun. Suck up the solder from the rows of terminals along the IC's two sides. Look for bent terminals that might be holding the pins to the board. With some stubborn pins, try to slide a small knife blade under the pin as you apply heat to the pin's top. Finally, flick the end of each terminal with the small blade of a pocket knife or screw driver to make sure each terminal is loose before lifting off the IC.

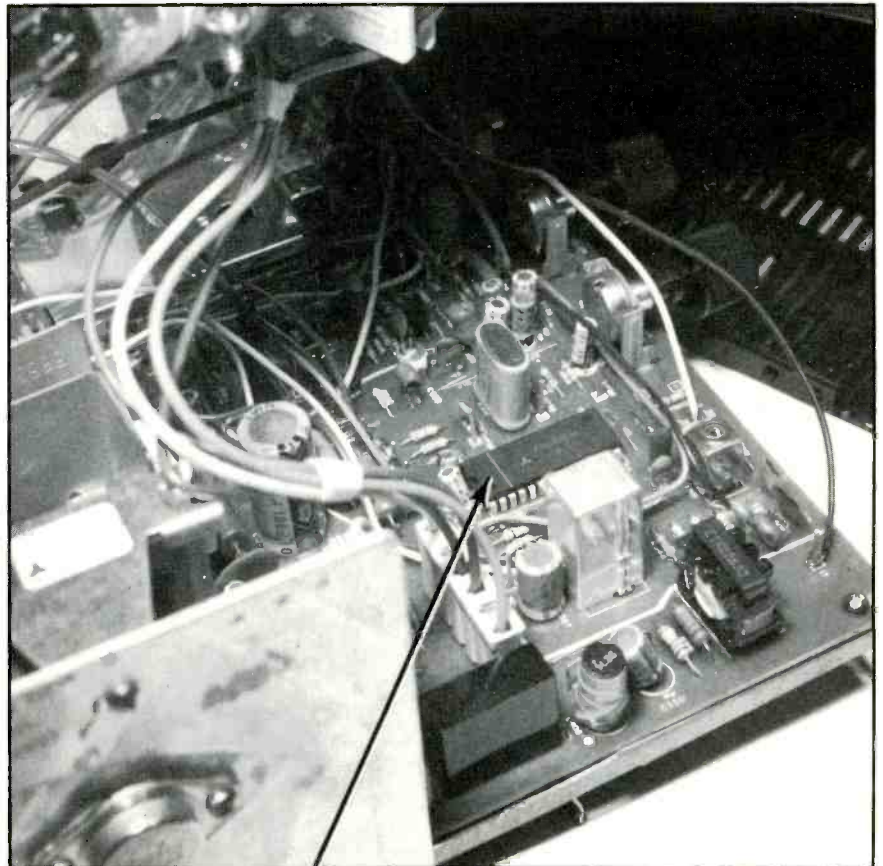After the IC is removed from the board, clean off all excess solder from the pads using solder wick. *Note: it is physically possible to in-*



An arrow points to the location of IC501 on the JC Penney circuit board. IC501 is under the IF shield, in the upper left corner of the photograph.

WARRANTY WORK

When you compare time spent to pay received, you might find it difficult to survive on some of the warranty allowances in today's market.

If so, this ad will serve as a reminder - - -

In less time than it takes you to print the customer's name on a warranty tag, a Mark VII computer will diagnose the failure down to circuit level. In most cases it will do so - - - without even removing the back!

If your local factory field service representative says it can't be done, remind him that **Diehl** will pay any engineer / technician a year's wages who can troubleshoot just three of his most familiar TV sets, before a Mark VII can troubleshoot thirty!! Hopefully, this challenge will either cause him to take his foot out of his mouth, - - - or finish putting it in!

— INTERMITTENTS POSE NO PROBLEMS —

(See our display ad on page 21)

DIEHL

Call (806) 359-0329 for more info.

6661 Canyon Drive • Amarillo, TX 79110

stall this large IC backwards. Be careful not to do so or the result will be catastrophic failure. Check for correct positioning of terminal 1. Solder all terminals with a low-wattage soldering iron to prevent heat damage to the new IC. A battery-operated iron is fine if it becomes hot enough. (Insufficient heat requires the iron to be on the joint too long, thereby transferring excessive heat to the IC's internal components.)

Troubleshooting video

When the picture tube shows no picture, check for good or bad video and luminance stages by taking a scope waveform at IC501 pin 5. No waveform indicates defective video. If the pin 5 waveform is normal, the tuner, picture-IF stages, AGC circuits and video detector are performing correctly.

When there is no picture, check for operating or non-operating video stages in IC301 by scoping IC501 pin 5. If the pin 5 waveform is normal, the tuner, picture-IF stages, AGC circuits and video detector in IC301 must be working correctly. An absence of pin-5 waveform indicates a defect in those stages just mentioned. Check the AGC-control voltage at pin 25; it should be between +4.7V and +7V depending on strength of the signal being received. The tuner AGV is at IC301 pin 5, and it should measure between +2V and +10V. As in Figure 1, modulated-RF signals can be injected at pin 28, pin 9 or pin

18 and the output viewed by scope at IC101 pin 19 or IC501 pin 5.

If the problem is IC501, the difficulties for testing are multiplied, because very few color or video signals are brought out to the pins until the three color signals exit at pins 26, 27 and 28. However, much useful information can be obtained by checking the dc voltages and the signal waveforms at IC501 pins 5, 13, 6, 19, 20 and 24 plus the three color-drive signals at pins 26, 27 and 28. All waveforms can be checked against those in Photofact 2145-1.

Pin 1 and TP59 bring the +11.64V supply into IC501. If this voltage is low, suspect leakage in zener D504 (that regulates the voltage) or in IC501.

If the three color-drive waveforms are normal at pins 26, 27 and 28, and there is no picture on the screen, suspect problems in one or more of the three color-output amplifiers or the picture tube. Scope all three collector waveforms. Perform in-circuit transistor tests of each power transistor. If one or more of the color amplifiers is defective, these tests should find it. However, a single defective color-output transistor usually will provide clear evidence in a B&W picture with one color missing.

Bright retrace lines

When the raster is extremely bright and has bright retrace lines, or the brightness cannot be reduced enough with the brightness

control, suspect IC501. Check the voltage and waveforms at terminals 1 through 6, 10 and 24. Sometimes this high brightness will drive the circuits into shutdown. Of course, you must get the receiver to operate in order to make dynamic tests, such as voltage tests.

Be certain pin 1 has adequate voltage (+11.64V). Measure the dc voltages at all luminance pins. If any voltages are too low, check the components connected to those pins. Check R510, R520, R514 and R516 for correct resistance. Test capacitors C516 and C517 in-circuit using a capacitance meter.

In a case when all active components and dc voltages appear to be normal, but the problem still persists, replace IC501.

Unusual luminance problem

To confuse the technician, some TV receivers develop more than one problem at one time. In one 2039 chassis, the brightness and retrace lines could not be turned down with the R523 brightness control. We automatically replaced the IC501, which corrected the brightness problem but brought to light a second one: The tuner could not tune in one station.

Accurate voltage tests on the tuner's memory board showed the +23.5V source had dropped to +13.6V. No negative pulses from the flyback were scoped at PA105 on selector board PWB (Figure 3). Tests of the +23.5V-source com-


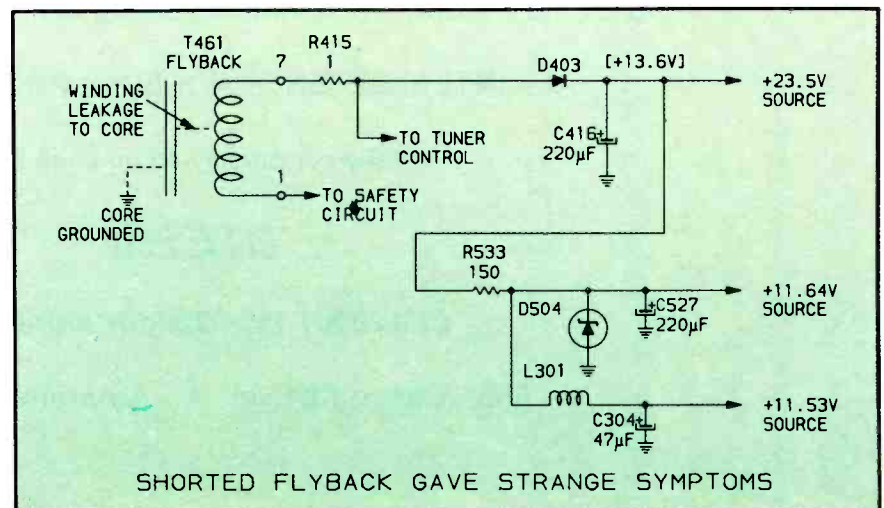


Figure 3. The +23V source is rectified from the pin-7 flyback signal, then the other two voltages are stabilized by D504 zener. In this receiver, a short between the flyback winding and the core grounded the winding incorrectly, thus reducing the dc-voltage output from D403. This interfered with the tuner station selection. The flyback was replaced.

2 SIMPLE SOLUTIONS TO 227,000 PROBLEMS.

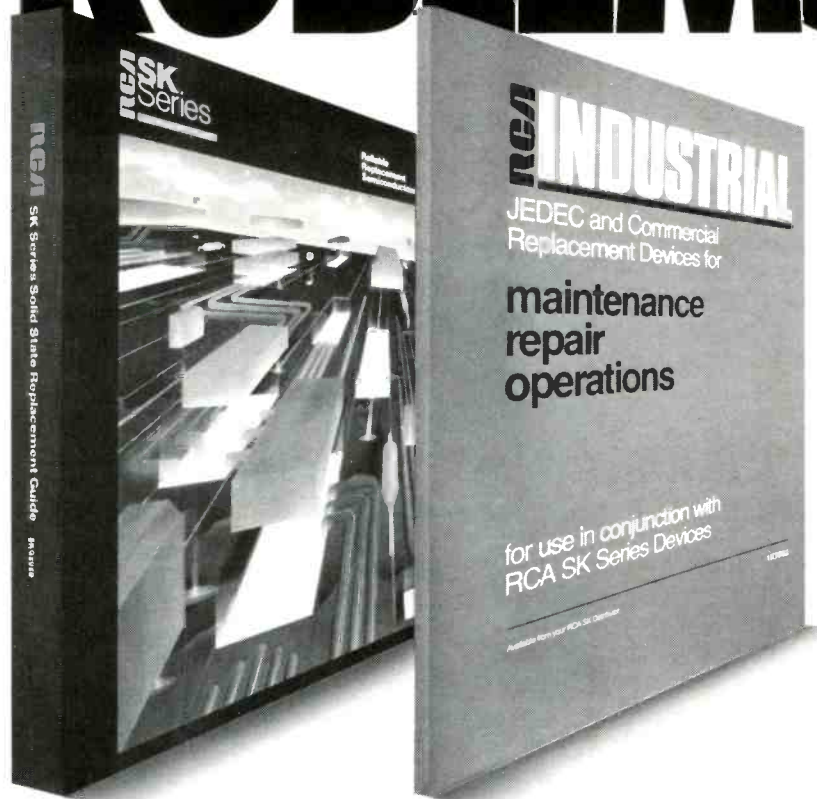

RCA's SK Series Replacement Guide (SKG202D) is your one source for over 206,000 solid state replacements using 2,500 SK and KH types. Integrated circuits, thyristors, rectifiers, transistors, microprocessors — RCA has them all.

Likewise, RCA's Industrial MRO Guide (1K7862) lists over 4,000 devices that replace more than 21,000 JEDEC* and Commercial types. The Guide also includes Power MOS/FETs, QMOS Integrated Circuits, a combined index/cross reference, and a section on high-reliability devices.

Together, these RCA Guides provide fast, easy answers for 227,000 solid state replacement problems.

For copies, see your local RCA distributor. Or write: Sales Promotion Services, RCA Distributor and Special Products Division, 2000 Clements Bridge Rd., Deptford, NJ 08096-2088.

*Joint Electron Device Engineering Council

RCA SK Replacement
Solid State

Circle (16) on Reply Card

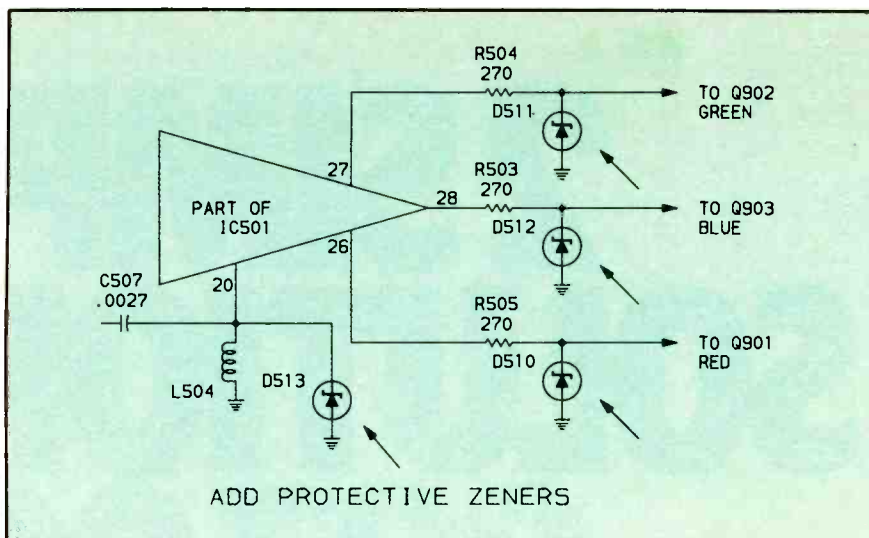


Figure 4. A 1206-8565 kit containing a new AN5310M IC and four zener diodes can be ordered from JC Penney stores or the RCA Service Company. These zeners are soldered to the foil side of the circuit board, and they absorb the transients that are produced when the picture tube arcs internally, thus protecting the IC. This should be done whenever a replacement IC501 has not operated more than a few weeks before failure.

ponents showed D403 and R415 were normal, and C416 (220 μ F) filter capacitor was paralleled with a similar capacitance but without any improvement.

The next possibility was that some overload on the +23.5V source was dragging down the voltage. With all loads disconnected from the supply, the voltage increased only to about +16V; not enough to be significant.

Resistance of the flyback winding was 21 Ω , which apparently is normal. But a dead short existed either from pin 1 or pin 7 to chassis ground. All wires on pin 1 and pin 7 were removed, but the short remained at the flyback pins.

Installation of a new flyback (part No. 1177-1557) solved the problem with the tuner.

Kit for modification

Because the secondary effects of picture-tube internal arcs can destroy IC501, a modification kit was designed to eliminate the problem. The 1206-8565 kit can be ordered through JC Penney stores or the RCA Service Company (which now is doing warranty repairs for the JC Penney stores).

The kit includes a new AN5310M IC and four zener diodes. As shown in the Figure 4 schematic, solder three zeners on the foil side of the board from terminal 26 to ground, 27 to ground and 28 to ground. The last zener must be connected between the ground foil and pin 20. Remember, all zener anodes go to ground. Locate the curved ground foil and scrape away the green coating where the new zeners should be


soldered. Grasp the wire lead of the zener in pliers, or a soldering heat sink as it is being soldered to minimize the possibility of heat damage to the diode.

Loss of height


When the vertical sweep has collapsed into one horizontal line, scope the IC301 pin 17 waveform

expecting to find about 1.3Vp-p. If it is there, the cause of loss of height must be in the vertical output or yoke stages. If it is missing or is weak or distorted, check pin 20 for the +11.53V source voltage. A loss of this voltage changes the next test to the power supplies. If the source voltage at pin 20 is correct, inject a vertical test signal

Continued on page 50

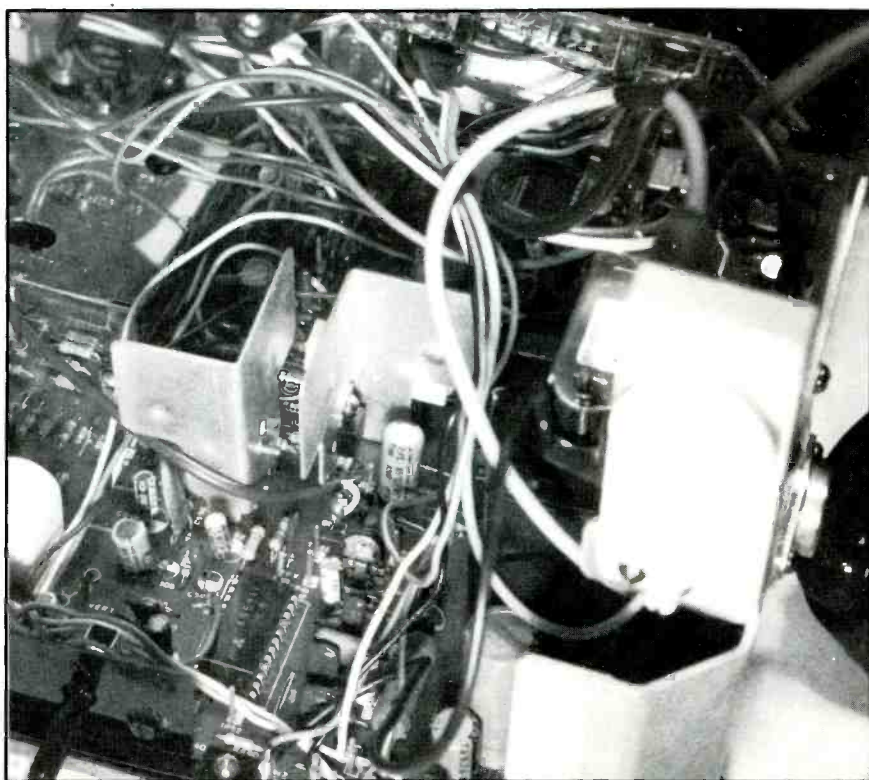

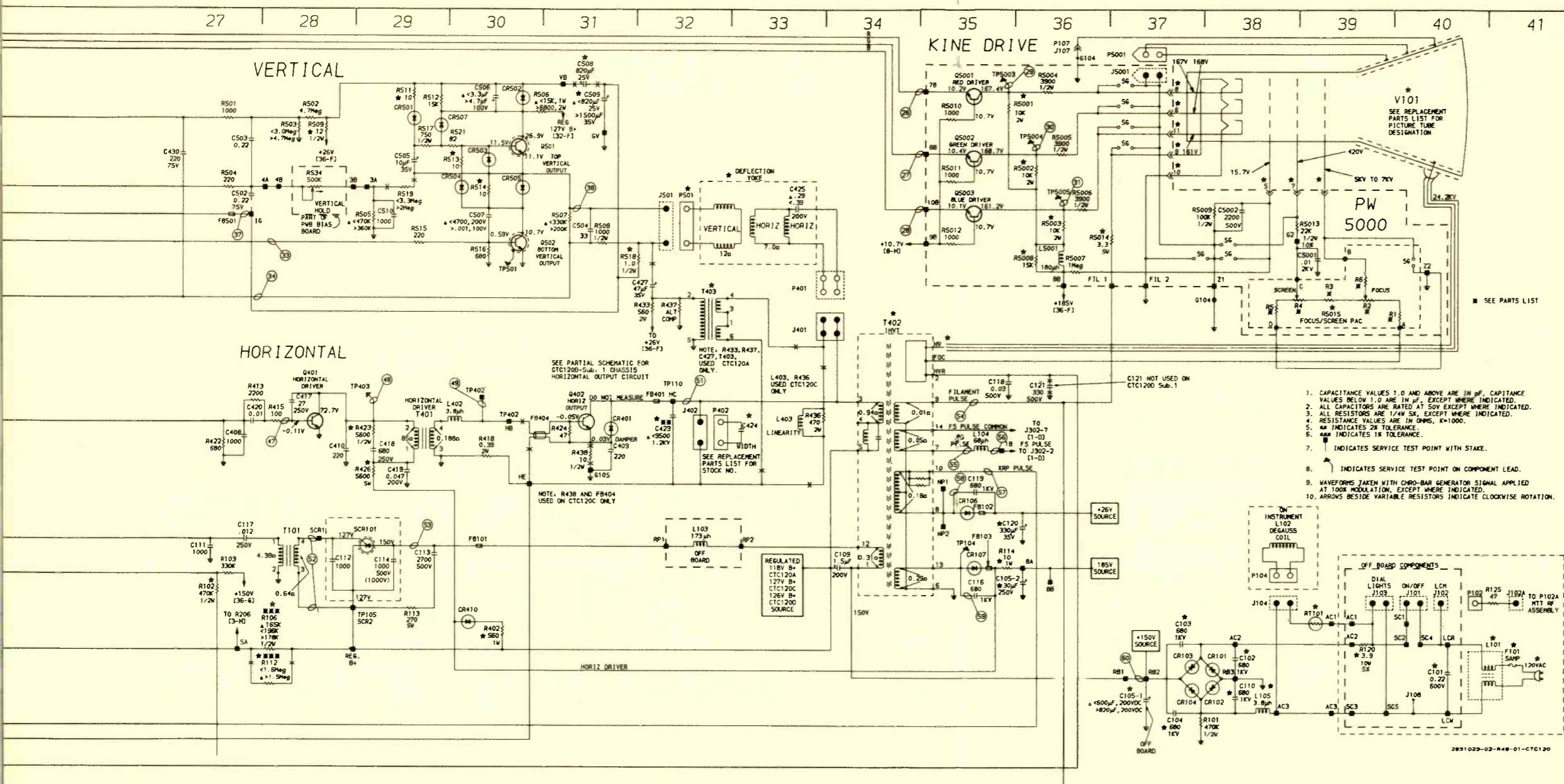The two right-angle pieces of metal near the photograph's center are the heat sinks for Q301 and Q302; Q302 is on the left, and Q301 is on the right. The IC at the lower center in the photograph is IC301.




Product safety should be considered when component replacement is made in any area of a receiver. The shaded areas of the schematic diagram designate the components in which safety is of special significance. It is recommended that only exact cataloged parts be used for replacement of these components.

Use of substitute replacement parts that do not have the same safety characteristics as recommended in factory service information may create shock, fire, excessive x-radiation or other hazards.

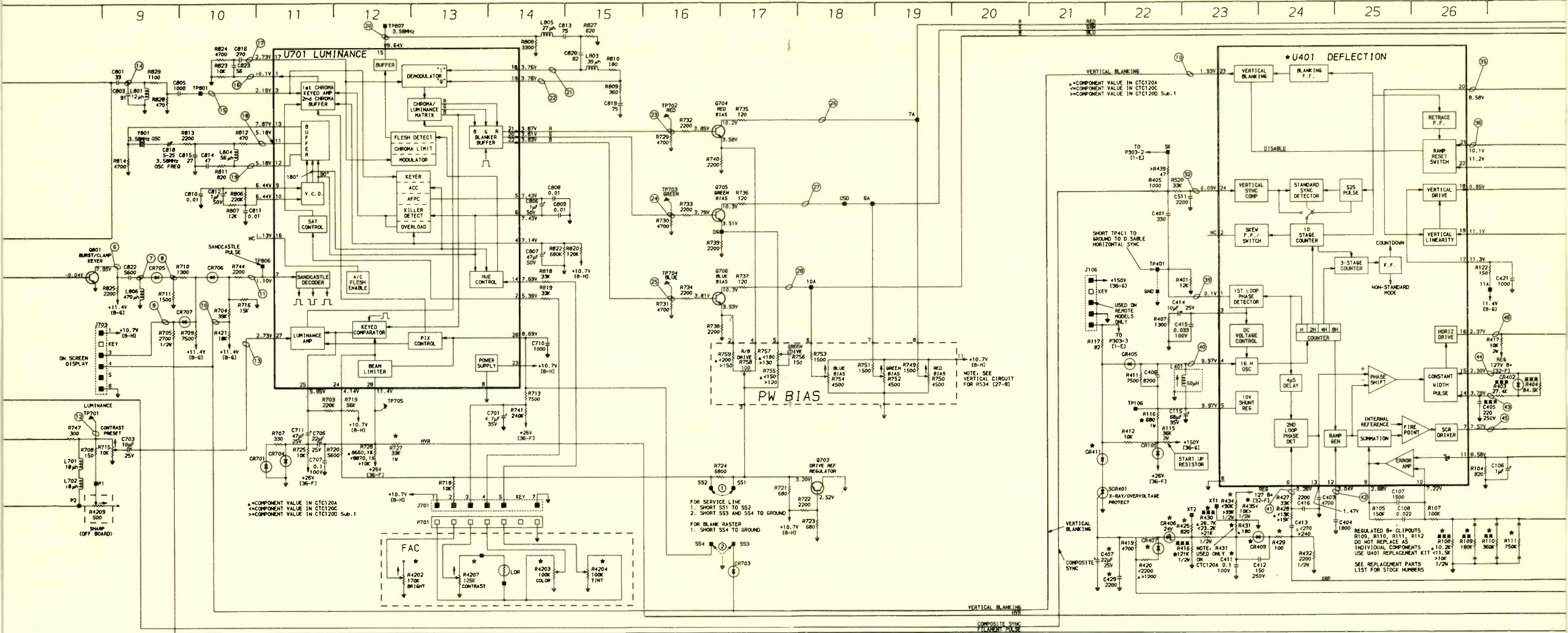1. CAPACITANCE VALUES 1.0 AND ABOVE ARE IN μF . CAPACITANCE VALUES BELOW 1.0 ARE IN pF , EXCEPT WHERE INDICATED.
2. ALL CAPACITORS ARE RATED AT 50V EXCEPT WHERE INDICATED.
3. ALL RESISTORS ARE 1/4W 5%, EXCEPT WHERE INDICATED.
4. RESISTANCE VALUES ARE IN OHMS, K=1000.
5. \star INDICATES 2% TOLERANCE.
6. $\star\star$ INDICATES 1% TOLERANCE.
7. ∇ INDICATES SERVICE TEST POINT WITH STAKE.
8. ∇ INDICATES SERVICE TEST POINT ON COMPONENT LEAD.
9. WAVEFORMS TAKEN WITH CHRO-BAR GENERATOR SIGNAL APPLIED AT 100% MODULATION, EXCEPT WHERE INDICATED.
10. ARROWS BESIDE VARIABLE RESISTORS INDICATE CLOCKWISE ROTATION.

This schematic is for the use of qualified technicians only. This instrument contains no user-serviceable parts.

The other portions of this schematic may be found on other Profax pages.



Product safety should be considered when component replacement is made in any area of a receiver. The shaded areas of the schematic diagram designate the components in which safety is of special significance. It is recommended that only exact cataloged parts be used for replacement of these components.

Use of substitute replacement parts that do not have the same safety characteristics as recommended in factory service information may create shock, fire, excessive x-radiation or other hazards.

This schematic is for the use of qualified technicians only. This instrument contains no user-serviceable parts.

The other portions of this schematic may be found on other Profax pages.


Product safety should be considered when component replacement is made in any area of a receiver. The shaded areas of the schematic diagram designate the components in which safety is of special significance. It is recommended that only exact cataloged parts be used for replacement of these components.

Use of substitute replacement parts that do not have the same safety characteristics as recommended in factory service information may create shock, fire, excessive x-radiation or other hazards.

This schematic is for the use of qualified technicians only. This instrument contains no user-serviceable parts.

The other portions of this schematic may be found on other Profax pages.


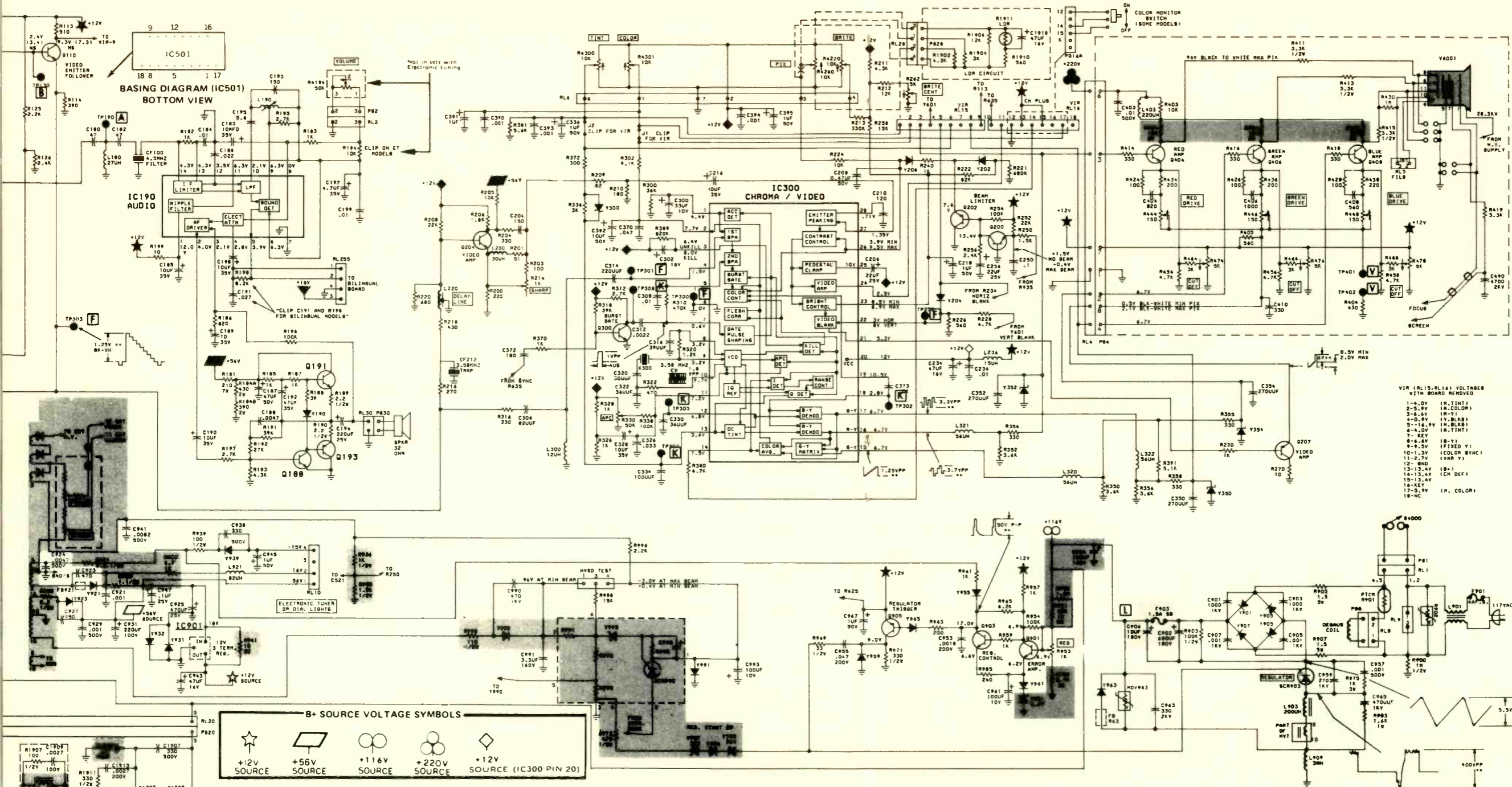
The other portions of this schematic may be found on other Profax pages.



Product safety should be considered when component replacement is made in any area of a receiver. The shaded areas of the schematic diagram designate the components in which safety is of special significance. It is recommended that only exact cataloged parts be used for replacement of these components.

Use of substitute replacement parts that do not have the same safety characteristics as recommended in factory service information may create shock, fire, excessive x-radiation or other hazards.

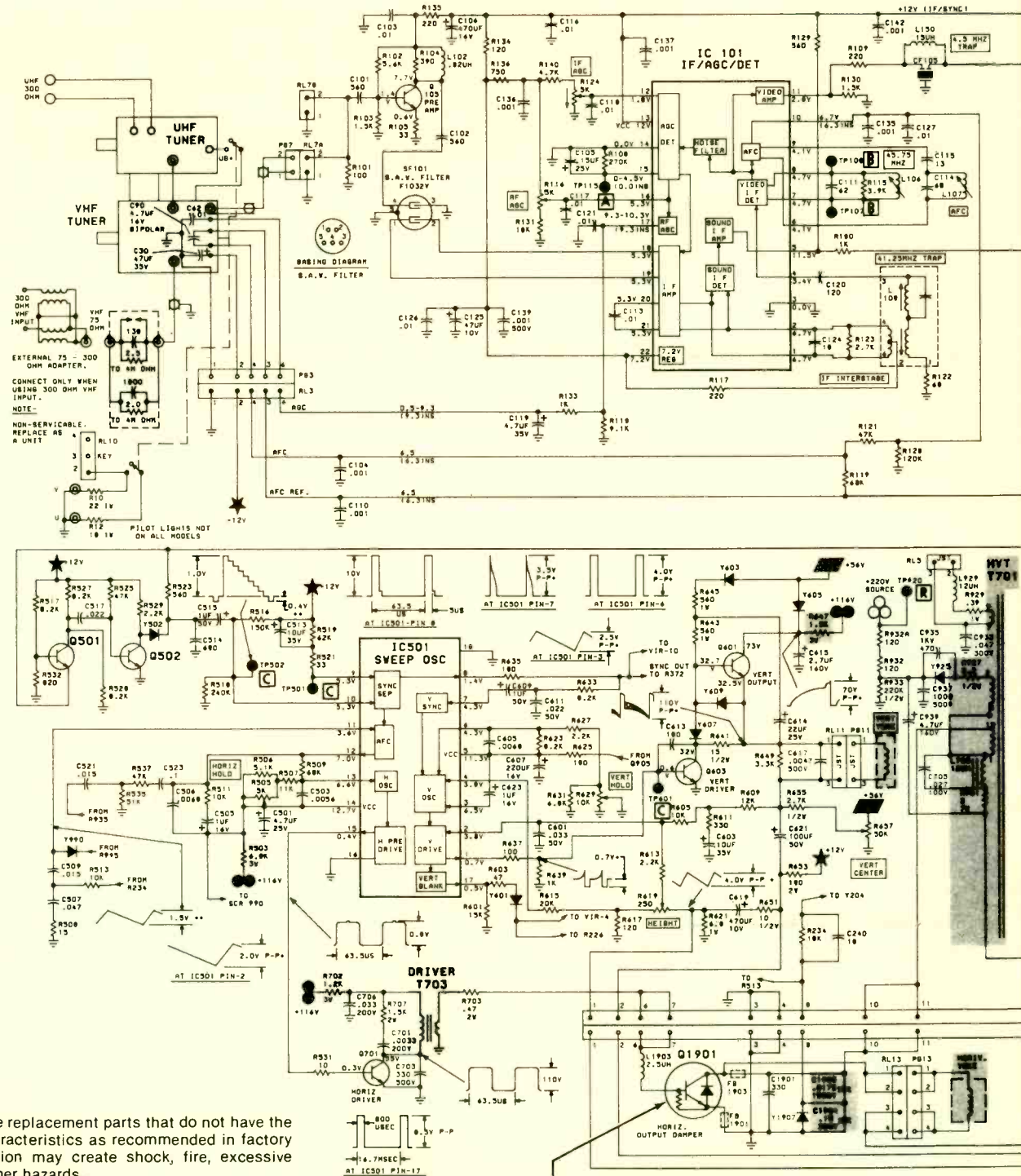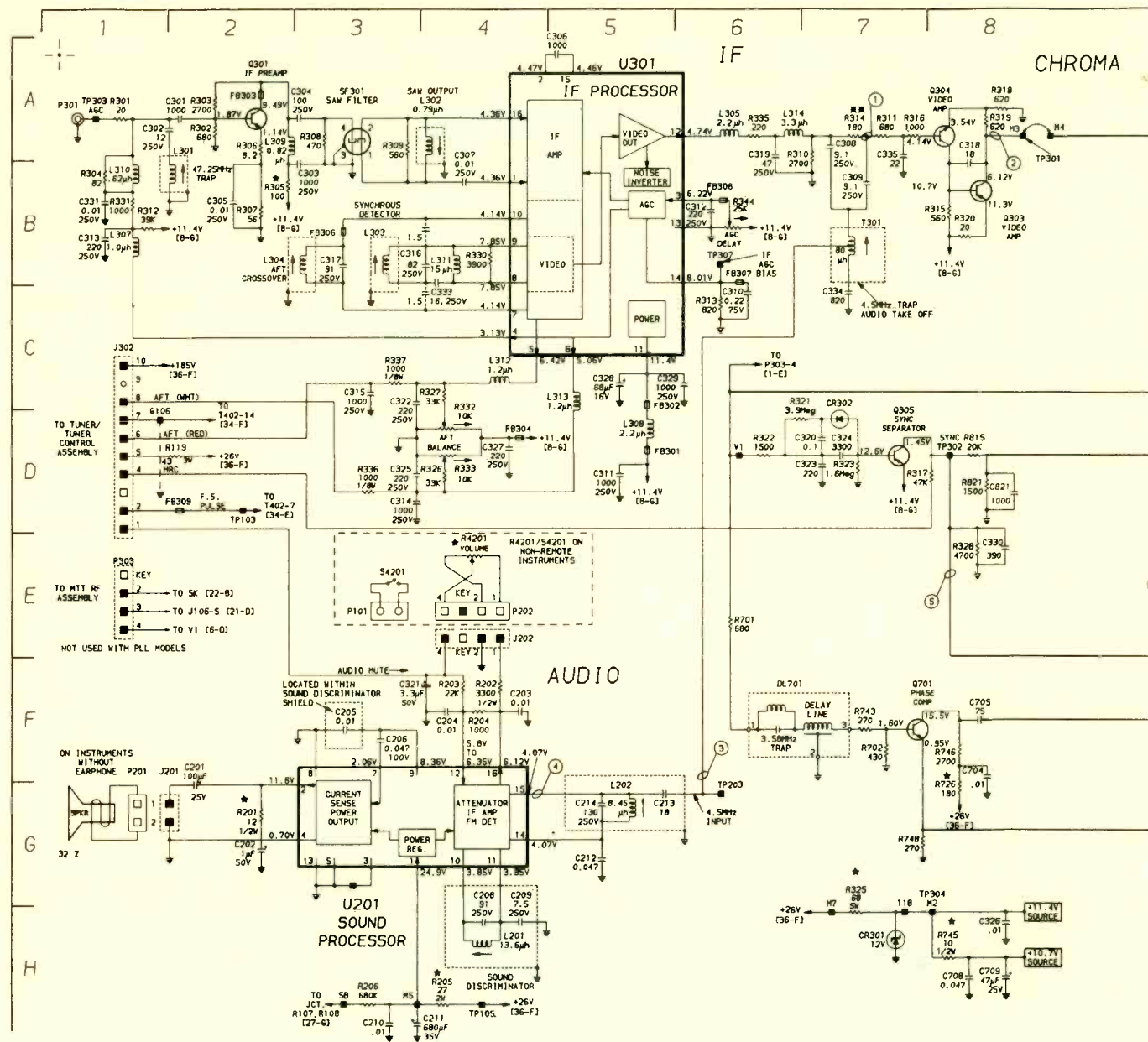This schematic is for the use of qualified technicians only. This instrument contains no user-serviceable parts.



The other portions of this schematic may be found on other Profax pages.

Product safety should be considered when component replacement is made in any area of a receiver. The shaded areas of the schematic diagram designate the components in which safety is of special significance. It is recommended that only exact cataloged parts be used for replacement of these components.

Use of substitute replacement parts that do not have the same safety characteristics as recommended in factory service information may create shock, fire, excessive x-radiation or other hazards.

Use of substitute replacement parts that do not have the same safety characteristics as recommended in factory service information may create shock, fire, excessive x-radiation or other hazards.

This schematic is for the use of qualified technicians only. This instrument contains no user-serviceable parts.

The other portions of this schematic may be found on other Profax pages.

HORIZ. OUTPUT RESISTOR AND DAMPER DIODE ARE INCLUDED IN THE SAME UNIT. REPLACE ONLY WITH ORIGINAL EQUIPMENT GE CATALOG REPLACEMENT PART NUMBER EPT58213.

Product safety should be considered when component replacement is made in any area of a receiver. The shaded areas of the schematic diagram designate the components in which safety is of special significance. It is recommended that only exact cataloged parts be used for replacement of these components.

Answers to the Quiz

By Sam Wilson

1. C. **ES&T**, December 1985, page 7.

The tone arm carriage is driven across the record by a servo motor. The LED scanning system tracks the disc. Variations in groove spacing are reported to a microcomputer for controlling the carriage drive servo motor.

2. D. **ES&T**, November 1985, page 4.

3. D. **ES&T**, October 1985, page 6.

4. A. **ES&T**, September 1985, page 20.

Begin with the rough adjustments and use the scope to fine tune. Never use electronic adjustments to compensate for mechanical problems.

5. B. **ES&T**, August 1985, page 42.

The letters stand for Schotz Noise Reduction.

6. C. **ES&T**, July 1985, page 48.

7. A. **ES&T**, June 1985, page 23.

Rosin-type fluxes are safest to use, but are relatively poor cleaners. Their intended purpose is to remove only minor oxidation.

8. D. **ES&T**, May 1985, page 5.

9. C. **ES&T**, April 1985, page 51.

See Figure 1.

10. D. **ES&T**, March 1985, page 16.

The questions are on page 10.


The New Powers of VIZ



LABORATORY AND INDUSTRIAL DC POWER SUPPLIES

WP-707A

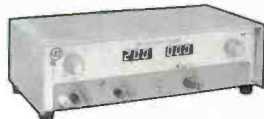- * Dual DC power supply, 0-25V 0-2A
- * Automatic Short Circuit Shutdown with Reset Button.
- * Excellent Line & Load Regulation.
- * LED overload indicators.
- * Two digital voltmeters with range of 0 to 99.9 VDC. May be used to measure DC source voltage or current.
- * May be used in series to provide 0-50V DC @ 0-2A



WP-712A Single output 20V, 2A with excellent line and load regulation.



WP-705A 0-50V, 2A regulated output, DC voltmeter, continuously variable between ranges.

VIZ's line of DC power supplies have a contemporary new design along with up-to-date features and specifications which offer you laboratory and industrial type performance—with style. This line of DC power supplies is well suited for servicing a wide variety of electronic equipment as well as production testing, circuit design, quality inspection and educational applications. Single, Dual & Triple output units are available.

The WP-707A dual power supply has two digital panel meters which can be switched to monitor voltage and, or current of either output.



The New Power in Test Equipment

VIZ TEST EQUIPMENT division of **VIZ Manufacturing Co.**
335 E PRICE STREET, PHILADELPHIA, PA 19144
215/844-2626 TLX. 710-670-2626 800/523-3696

Circle (17) on Reply Card

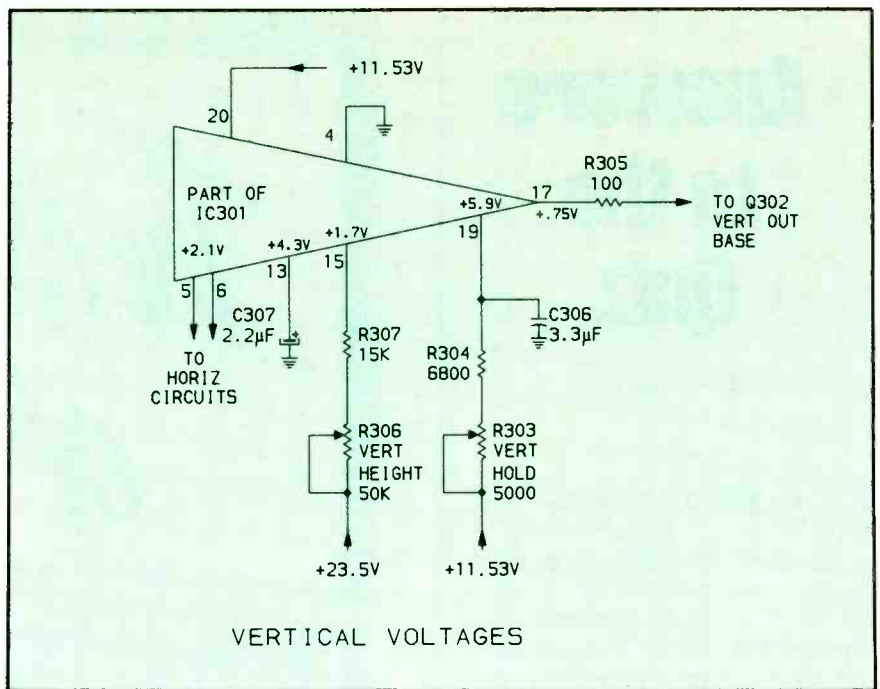


Figure 5. IC301 contains the vertical oscillator and driver stages. Vertical hold and vertical height controls are supplied, but there is no need for a vertical linearity control. The signal at pin 14 is produced by the vertical yoke current flowing through resistor R317, and this gives excellent linearity without adjustments. Scope pin 17 to determine whether or not IC301 is giving out the vertical-drive signal. If you verify that it is not, inject a vertical test signal there. It should give vertical deflection if the Q302 and Q301 stages are normal.

Continued from page 28


at pin 17 of IC301. If the IC is bad, but the following circuits are normal, a test pattern should appear on the TV screen and on the scope (Figure 5).

Very low voltage at pin 20 might indicate either a leaky IC301 or a defect in the power supply. Measure the resistance from pin 20 to chassis ground. If the reading is below 450Ω, disconnect pin 20 from the circuit board. Now measure pin 20 alone. The resistance will be low if IC301 is leaky internally. If so, IC301 must be replaced.

A normal sawtooth waveform at pin 17, but no height on the screen or waveform at C310 (Figure 6), changes suspicion to the vertical-output circuit. Vertical outputs Q301 and Q302 have a history of failures. First, take dc voltage measurements of Q301 and Q302. If that doesn't reveal anything significant, check both transistors in-circuit.

If the in-circuit tests give questionable results, remove the transistor from the circuit and from the heat sink and test thoroughly. If either check shorted, also test R308 or R309 because the overload usually causes the emitter resistor to become open.

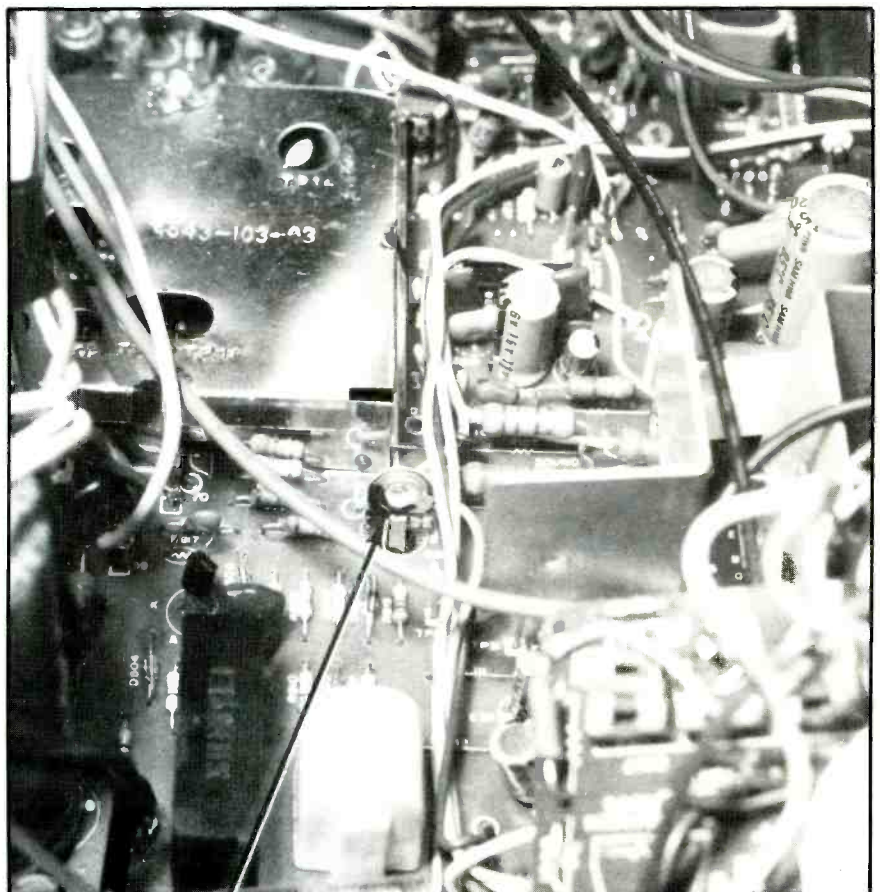A technician can go through a complicated series of dc voltage tests with calculations to show which resistors are open or have changed value, but this is seldom necessary in these circuits. Figure 6, for example, shows only nine



R851, the adjustment potentiometer for the +112V supply, is located as shown by the arrow, between the IF shield and Q302.


Check out the #1 source for technical support: RCA.

- Valuable, time-saving parts literature
- Nationwide distribution with super-fast delivery
- Highest quality exact replacement parts

1F7827 VCR Key Items Cross Reference from Manufacturer's Model Numbers to RCA Stock Numbers — Covers Magnavox, Panasonic, Philco, Sylvania and RCA.



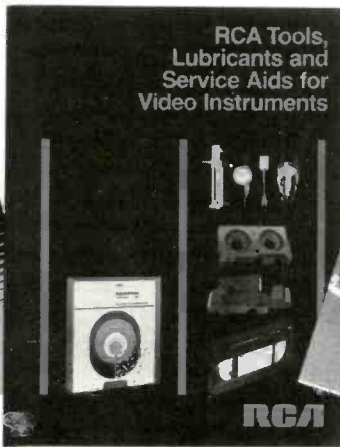RCA Tools, Lubricants and Service Aids for Video Instruments



1F6857 RCA Tools, Lubricants and Service Aids for Video Instruments — Illustrations and descriptions.

1F6870 Cross Reference TV Modules to RCA Chassis Vol. II — Lists replacement modules by number and functions for most recent color chassis.



RCA offers a wide range of literature highlighting our exact replacement parts. Each booklet is designed to make your job easier and more profitable. They're comprehensive and continually updated. Best of all, they're free. So check off the ones you want to check out. Then send in this coupon/ad today.

- | | |
|--|---|
| <p><input type="checkbox"/> 1F7297 Fastest Moving VHS VCR Parts Chart — Helps you establish and minimize VCR parts inventory.</p> <p><input type="checkbox"/> 1F6627 Replacement Parts for RCA Video Cassette Recorder Instruments — Helps determine RCA stock number when you know original manufacturer's number.</p> <p><input type="checkbox"/> 1F6932 RCA Drawing Number to Stock Number Cross-Reference — Relates RCA's manufacturing type number to RCA replacement stock number for all consumer products.</p> <p><input type="checkbox"/> 1F5790 RCA Remote Controls for TV, VCR, VideoDisc Instruments — Includes illustrations; cross-references stock numbers and instrument model numbers.</p> <p><input type="checkbox"/> 1F6541 RCA Replacement TV Antennas — Actual size illustrations.</p> | <p><input type="checkbox"/> 1F5345 QT Parts List — Quick turnover list of the 150 fastest-moving consumer parts.</p> <p><input type="checkbox"/> 1F7148 Replacement IHVT Chart — Cross-references chassis to replacement integrated high voltage transformer.</p> <p><input type="checkbox"/> 1F4163 RCA Exchange Program Eligibility List — Lists parts eligible for dud return allowance.</p> <p><input type="checkbox"/> 1F3588 RCA TV Tuner to Replacement Stock Number Cross-Reference — Lists RCA mechanical tuners and exact replacement stock number.</p> <p><input type="checkbox"/> 1F4786 Cross-Reference TV Modules to RCA Chassis Vol. I — Lists replacement modules by number and functions for earlier color chassis.</p> |
|--|---|

Please send the RCA Parts literature checked above to:

Firm

Address

City State Zip

Attention

Fill in information at left and mail entire page to:
RCA Distributor and Special Products Division
2000 Clements Bridge Road
Deptford, NJ 08096-2088
Attn: Sales Promotion Services

RCA

Offer expires July 31, 1986.

All New

Dynamically test all caps & coils 100% reliably!



**LC75 "Z METER 2"
Patented
\$995**

Finds them all because the "Z METER" is still the only LC tester that enables you to test all capacitors and coils dynamically — but now it's faster, more accurate and checks ESR (Equivalent Series Resistance).

- **Find Defective Capacitors That All Others Miss**
Want to dynamically test capacitors for value, leakage, dielectric absorption, and ESR with up to 600 volts applied with 100% reliable results?
- **Test Inductors In- Or Out-Of-Circuit And Save Time**
Looking for a sure fire way to dynamically test inductors for value, shorts, and opens?
- **Reduce Costly Inventory**
Tired of stocking a large inventory of caps, coils, flybacks, and IHVTs because you don't have a proof positive way of testing them?
- **Test SCRs & TRIACs Without Investing In A Second Tester**
Need a way to test SCRs, TRIACs, and High-Voltage Diodes dynamically with up to 600 volts applied?
- **Turn Chaos Into Cash By Quickly Locating Transmission Line Open & Shorts**
Like to be able to pinpoint distance to a short or open, to within feet, in any transmission line?

Call WATS Free, 1-800-843-3338, to try the world's only Dynamic LC Tester for yourself for 15 days FREE.

**CALL TODAY
WATS Free, 1-800-843-3338**



SENCORE

ELECTRONIC TEST EQUIPMENT
Innovatively Designed With Your Time In Mind
3200 Sencore Drive
Sioux Falls, South Dakota 57107
Circle (19) on Reply Card

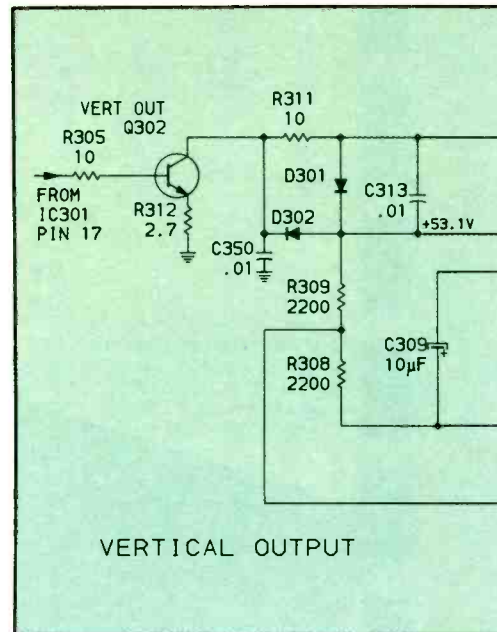



Figure 6. There are a few components in the Q301/Q302 vertical-output stage. If necessary, test all of them. The sawtooth of vertical yoke current across R317 is modified by C312 and R315 and again by the "S" filter R313, C311, and R314 before the shaped waveform is sent to IC301 pin 14 where it automatically corrects the linearity. These values are fairly critical.

resistors (including the first base resistor, the S filter resistors and the yoke-return resistor). Only five resistors are vital to the output stage, so just test them while the transistors are out of the chassis. Measure each with the test leads in one polarity and then exchange the test leads and make the measurement again. The higher reading probably is the correct one. If the reading swings (from some capacitor charging), just hold the probes there a little longer.

Resistances of R312, R310, R308 and R309 are critical, so tolerance should be a consideration when replacements are selected.

An open C310, R317 or L462 (vertical-yoke coils, Figure 6) removes all vertical sweep from the picture tube. R317 is a large part of the automatic linearity system and must not be tampered with. A quick test is from the negative terminal of C310 to

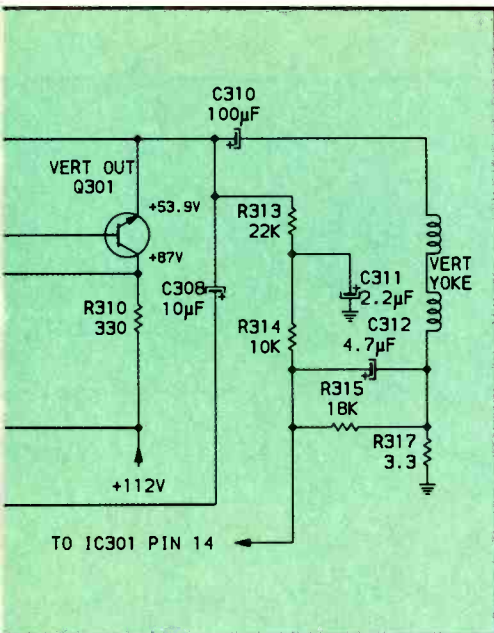Faster, more accurate, and more confident measurements you can trust every time . . . or your money back.




ground; a normal receiver will show about 5.3Ω . Another $100\mu\text{F}$ capacitor can be paralleled across C310 temporarily as a test for an open capacitor. (Turn off the ac power before adding the capacitor.)

Insufficient height

Scope waveforms can be very helpful in identifying stages with defects. For example, a weak drive voltage (should be 1.3Vp-p) at IC301 pin 17 might be caused by a defective IC301 integrated circuit or an insufficient $+11.53\text{V}$ supply voltage. Also check (to find if Q302 is loading down the drive signal) by disconnecting the emitter terminal of Q302 and trying the test again. A normal drive signal indicates excessive loading. No change proves IC301 is not operating correctly, and should be replaced.

Measure the $+11.53\text{V}$ source at pin 20 and the $+23.5\text{V}$ source at

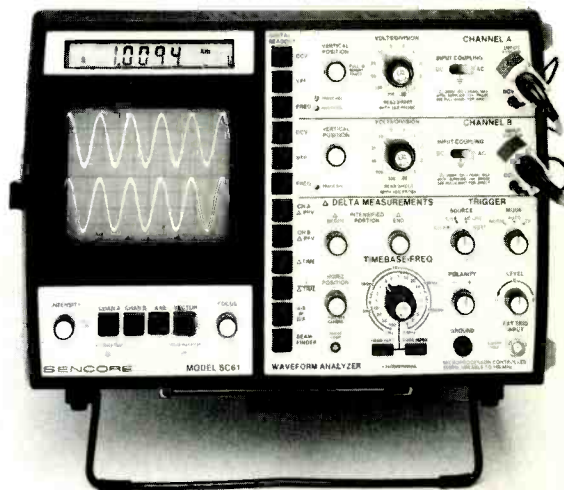

**SC61
Waveform Analyzer
Patented
\$2,995**

If you value your precious time you will really want to check out what the exclusively patented SC61 Waveform Analyzer can do for you . . .

- **No More Fiddling With Confusing Controls**
Exclusive ultra solid ECL amplifiers, simplified controls and bright blue dual trace. You'll measure signals to 100 MHz easier than ever.
- **Exclusive 3000V Protection For Fearless Circuit Measurements**
Accurately and confidently measure from 5mV all the way to 2000V without hesitation — While 3000V protection eliminates expensive "front end" repairs and costly equipment downtime.
- **Guaranteed Faster, More Accurate, More Confident Measurements**
You'll be amazed that by making only one circuit connection and pushing one button for each test, you can instantly read out DC volts, Peak-To-Peak volts and frequency with digital speed and accuracy. It's a real troubleshooting confidence builder.
- **Confidently Analyze Complex Waveforms Quickly**
Exclusive Delta measurements let you intensify any waveform portion. Examine glitches, interference signals, rise or fall times or voltage equivalents between levels instantly at the push of a button.
- **Speed Your Digital Logic Circuit Testing**
Analyzing troublesome divide and multiply stages is quicker and error free — No time-consuming graticule counting or calculations.

To see what the SC61 can do for your troubleshooting confidence CALL TODAY, WATS Free, 1-800-843-3338, for a FREE 15 day Self Demo.

CALL TODAY
WATS Free, 1-800-843-3338



SENCORE

ELECTRONIC TEST EQUIPMENT

Innovatively Designed With Your Time In Mind

3200 Sencore Drive
Sioux Falls, South Dakota 57107
Circle (20) on Reply Card

Now test every CRT on the market
 ... without ever buying another adaptor
 socket or coming up embarrassingly
 short in front of your customer ...



CR70
"BEAM BUILDER"
 Patented
 \$995

Have you ever:

- Thrown away a good TV, data display, or scope CRT that could have been used for another two or three years because you had no way to test it?
- Lost customers because you advised them that they needed a new CRT when another technician came along and restored the CRT for them?
- Lost the profitable extra \$35 or more that you could have gotten for restoring a CRT while on the job?
- Avoided handling trade-ins or rentals because you were afraid you'd have to replace the picture tube?
- Had a real need to test a CRT on the job, but didn't have the right adaptor socket or setup info in your setup book?

If any of these things have happened to you, you'll want to try the CR70 Universal CRT Tester and Restorer for 15 days, FREE OF CHARGE — with no obligation.

CALL TODAY
WATS Free, 1-800-843-3338



SENCORE

ELECTRONIC TEST EQUIPMENT
 Innovatively Designed With Your Time In Mind
 3200 Sencore Drive
 Sioux Falls, South Dakota 57107
 Circle (21) on Reply Card

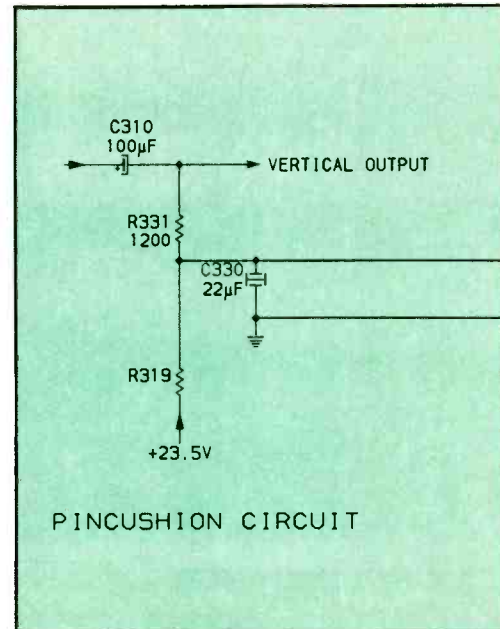


Figure 7. Side pincushioning is corrected by sending the horizontal yoke current through the secondary of T460 whose inductance is varied by the ac and dc voltages at the primary. R331 and R319 apply some of the vertical-sweep output, C330 filters it before it reaches the T460 primary. R319 also brings in dc offset current to move the primary inductance where it operates best.

the height control, and make power supply repairs if either is low. Check for correct waveforms at pins 14, 15, 18 and 19 of IC301, and be certain R306, R307, R304 and R303 have the correct resistance.

Check these components when the sweep is insufficient: R312, R308, R310, Q301, Q302, C309 and C310. Replace any that are defective or questionable. C309 or C310 also can be checked as stated before by paralleling a similar capacitor across it during operation. If the paralleled capacitor produces a large improvement, it is clear the original capacitor is open.

Do not overlook the pincushion-transformer circuits (Figure 7) for vertical height (or horizontal width) problems. There are just a few components there; check them all and be certain. Also, the P/J401

Walk out "tough dog" TV & VCR troubles in half the time . . . or your money back.



**VA62
Video Analyzer
Patented
\$3,295**

Would you like to . . .

- Increase your service profits by isolating any problem to one stage in any TV or VCR in minutes, without breaking a circuit connection, using the tried and proven signal substitution method of troubleshooting?
- Cut costly call-backs and increase customer referrals by completely performance testing TVs & VCRs before they leave your shop? Check all standard and cable channels? Check complete RF, IF, video and chroma response of any chassis in 60 seconds without taking the back off the set?
- Take the guess work out of costly service parts with the patented Ringing Test? Run dynamic proof positive test on any yoke, flyback and integrated high voltage transformer . . . in the circuit?
- Protect your future by servicing VCRs for your customers before they go to your competition. Walk out "tough dog" troubles in any VCR chrominance or luminance circuit — stage by stage — to isolate problems in minutes? Have a proof positive test of the video record/play heads before you replace the entire mechanism?
- Increase your business by meeting all TV and VCR manufacturers' requirements for profitable warranty service work with one up-to-date system?

If you answered yes to any of these questions, you'll want to put the VA62 Analyzing System on your bench for a 15 day FREE trial . . .

CALL TODAY
WATS Free, 1-800-843-3338




SENCORE

ELECTRONIC TEST EQUIPMENT

Innovatively Designed With Your Time In Mind

3200 Sencore Drive
Sioux Falls, South Dakota 57107

Circle (22) on Reply Card

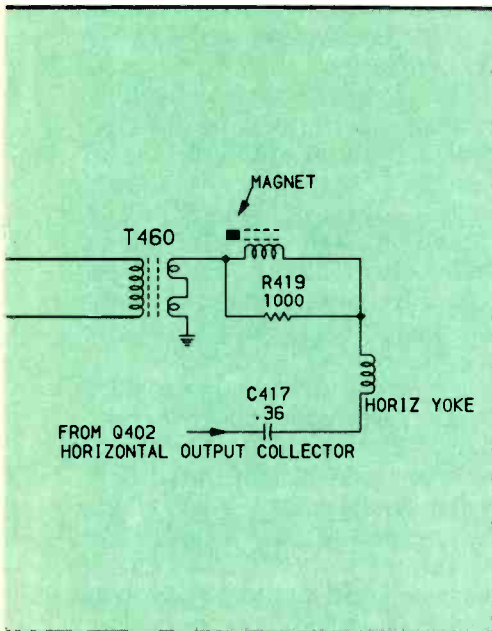

yoke plug might be another possible source of mysterious intermittent problems. Keep it in mind.

Vertical foldover

Most cases of foldover and poor vertical linearity originate in the vertical-output circuit. So first check both output transistors for leakage. Test diodes D301 and D302 for leakage or being shorted. If all other tests fail, replace Q302 and Q301, in that order. (A universal transistor replacement chart is included in this article.) Use a capacitance meter to check in-circuit these capacitors: C307, C308, C309, C311 and C312. Replace or temporarily substitute any that are low in capacitance.

Intermittent height

With a dual-trace scope, monitor the IC301 pin 17 signal with one

probe and the output signal at C310 with the other probe. Then wait until the intermittent occurs, or until you can find a way to trigger it. Several dc voltages also could be monitored, such as IC301 pins 15 and 20, and +87V at the Q301 collector.

The components most likely to produce intermittent height (vertical deflection) are IC301, Q301 and Q302. Remember that canned coolant sometimes triggers an intermittent *on* or *off* when sprayed on the offending part. Just be sure that only one component at a time is cooled if you want to be sure that the test will be accurate.

If a waveform remains at C310 but the screen shows only one horizontal line, suspect a defective yoke, the yoke plug or the wires to these components. Poor socket connections at pins 4 and 5 can cause the open circuit and loss of vertical. Incidentally, the vertical yoke coils should measure 56Ω.

COMPONENT	NUMBER IC	MFG. NUMBER	RCA	PHILIPS
IC301	AN-5411	1177-1169	SK-9314	ECG-1417
IC501	AN-5310	1177-1151	SK-9016	ECG-1410
Q301 & Q302	2SC-2073	1178-7538	SK-3929	ECG-375


Table 1. These replacements have been tested and found satisfactory for use in the JC Penney model 685-2039.

TEST INSTRUMENTS Lowest Prices Off-The-Shelf Directly To You

HITACHI 35 MHz DUAL TRACE OSCILLOSCOPE

Model V-355
\$599⁹⁵

(Reg. \$899.95)
Probes included

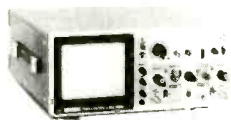

- Thin, lightweight, compact • Large 6" rectangular, internal graticule CRT
- Autofocus


FREE!

**LOGIC PROBE
BP LP189
(\$40.00 VALUE)**
with purchase of
Model V-355

B&K 60 MHz TRIPLE TRACE OSCILLOSCOPE

Model 1560
\$899⁹⁵

(Reg. \$1150)
Probes included

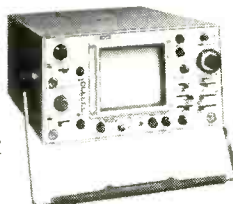

- 1 mV/div sensitivity
- 22 calibrated sweeps • Rectangular CRT
- w/internal graticule & scale illumination • Autofocus

FORDHAM SWEEP FUNCTION GENERATOR

Model FG-801
\$199⁹⁵

(Reg. \$289.95)
Test Leads included.



SPECIAL PRICE!

- 7 frequency ranges, 0.2 Hz to 2 MHz
- Accuracy to ±5%

FORDHAM 550 MHz FREQUENCY COUNTER

Model FM-8
\$169⁹⁵

(Reg. \$249.95)



Completely assembled, pre-tested, pre-calibrated • High intensity 8-digit LED display

FLUKE 3½ DIGIT MULTIMETERS & VOLTMETERS

Model 73 **\$74⁹⁵**

Model 75 **\$89⁹⁵**

Model 77-F **\$119⁹⁵**




HITACHI 100 MHz QUAD TRACE DELAYED SWEEP OSCILLOSCOPE

Model V-1050F
\$1249⁹⁵

(Reg. \$1980)
Probes included.

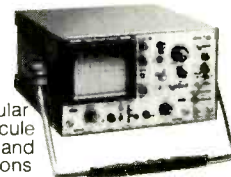- Large 6" rectangular CRT w/internal graticule
- Delayed alternate and single sweep functions
- Autofocus



☎ ☎ ☎ Phone orders accepted.

Fordham **ASK FOR OUR FREE CATALOG!**
Toll Free **800-645-9518**
260 Motor Parkway, Hauppauge, NY 11788 In NY State 800-832-1446

Service & Shipping Charge Schedule Continental U.S.A.

FOR ORDERS	ADD
\$25-100	\$4.50
\$101-250	\$6.00
\$251-500	\$8.00
\$501-750	\$10.50
\$751-1,000	\$12.50
\$1,001-1,500	\$16.50
\$1,501-2,000	\$20.00
\$2,001 and Up	\$25.00

Vertical voltage sources

A complete loss of height, intermittent height or insufficient height can be caused by abnormal conditions in any or all of the three voltage sources. The +112V source supplies the horizontal-output transistor and Q301, plus the base voltage for Q401, the horizontal-driver transistor. Therefore, any significant increase of this voltage would produce shutdown and remove all power; this would remove the voltage and all danger to Q301. A reduced +112V source voltage probably would produce a picture with reduced width and height.

When the +11.53V at IC301 pin 20 is missing, check for an open R415 (1 Ω fuseable surge resistor) and a shorted or open D403 diode rectifier (Photofact 2145-1). If the +11.53V source is higher than usual, check zener diode D504; it might be open. Or in the opposite

direction, leakage in D504 can produce excessive heat and reduce the voltage source.

Remember that insufficient vertical height and rolling problems might be caused by a defect in the low-voltage supply circuits.

Comments

This JC Penney's 685-2039 model is somewhat typical of many that extensively use integrated circuits. Questions arise during troubleshooting because very few stages are brought out to external pins. Therefore, the usual resistance and dc voltage tests cannot always identify a defective IC. Sometimes it is necessary to replace the integrated circuit. That's costly and time consuming, but necessary in many cases.

We hope the suggestions in this article will help the technicians, and result in avoiding unnecessary IC replacements.

ES&T

SAVE TIME

For fast, accurate service, please remove the Peel-Off Label (which is used to address your magazine) and affix it to the Reader Service Card, the Address Change Card, or to any correspondence you send us regarding your subscription.

Coming in...

MAY

Ups and downs of vertical sweeps—Homer L. Davidson describes 10 vertical problems that exemplify the wide variety of malfunctions commonly occurring in several color-TV-receiver brands. Although most vertical problems are easy to repair, a few require persistent, sometimes creative, testing. The author recommends using a good VOM or DMM with your scope, and points out that a schematic or Photofact is necessary reinforcement.

Test components and ICs with your scope—According to the author, Al Kovalsky, a component test feature is found on some scopes. Jacks on the scope provide output of low-current sine wave voltage that can be applied across component contacts. With a single-channel scope, the input is accepted and the trace displayed from one source. For comparison testing, as detailed in the article, a dual-channel scope is required.

Field-strength meter or signal-level meter?—The characteristics and purposes of these two testing devices are dissimilar, although they frequently are confused even by experienced technicians. James Kluge explains why the two meters are not interchangeable.

What do you know about electronics?—**Visual modulation.** Oscilloscopes, certainly the best instrument to use when visualizing waveforms, unfortunately show the waveforms as 2-dimensional when, in reality, waveforms have three dimensions: amplitude, frequency and time. These can be displayed graphically today with a personal computer, a great advance from the *granddaddy* 3-dimensional display described by the author.

What do you know about electronics?

Constant-current generators

By Sam Wilson

The idea of a constant-voltage generator, one that produces a fixed value of voltage across a load regardless of the amount of the load's resistance, is widely understood. Today's stiffly regulated power supplies can approximate closely a constant-voltage generator within a given range of output currents.

A less familiar concept is the constant-current generator. It produces current through a load resistance even though that load resistance may change. The constant current also can be simulated using electronic control circuitry.

The simplest component that can be used for constant-voltage generation is the zener diode. There also is a constant-current diode available. It maintains a constant-current flow despite variations in applied voltage or load resistance. The constant-voltage and constant-current diode symbols and their characteristic curves are shown in Figure 1.

The author is indebted to Motorola for much of the technical information presented in this article.

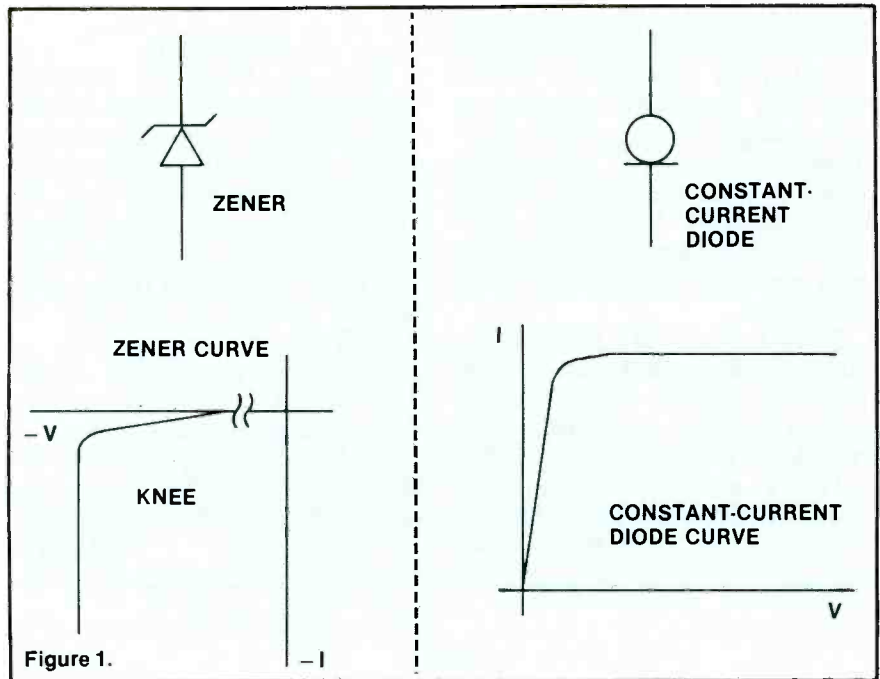


Figure 1. These are the symbols and the characteristic curves for the constant-voltage and constant-current diodes.

Use in network analysis

The concept of constant-voltage and constant-current generators existed before electronic components could be made to approximate their characteristics. As a matter of fact, they were considered to be imaginary generators used in Thevenin's and Norton's theorems. These theorems are still used to simplify circuit calculations. The following statements of the theorems are applicable to dc circuits. (Resistances must be replaced with impedances in ac systems.)

THEVENIN'S THEOREM: Any two-terminal network composed of linear bilateral circuit elements and one or more sources of voltage can be replaced with a simple constant-voltage generator in series with a resistor.

NORTON'S THEOREM: Any two-terminal circuit composed of linear bilateral circuit elements and one or more sources of voltage

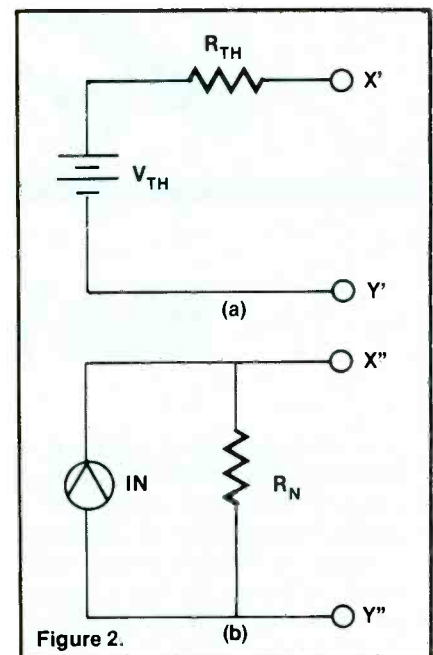


Figure 2. In network analysis, these simple circuits, the Thevenin and Norton generators, can be used to replace more complex combinations of sources and resistances.

can be replaced with a constant-current generator in parallel with a resistor.

Figure 2 shows Thevenin's (a) and Norton's (b) generators as they usually are depicted.

Figure 3 shows a complex dc circuit consisting of linear, bilateral circuit elements (resistors) and several sources of voltage. This circuit, according to Thevenin's and Norton's theorems, can be replaced with either of the two circuits shown in Figure 2. It follows that if either of the circuits in Figure 2 can be used to replace the circuit of Figure 3, as far as calculations of load voltage and load current are concerned, then the two circuits also must be equivalent to each other.

We are more interested here in the concept of the constant-current generator (I_m). But let's first

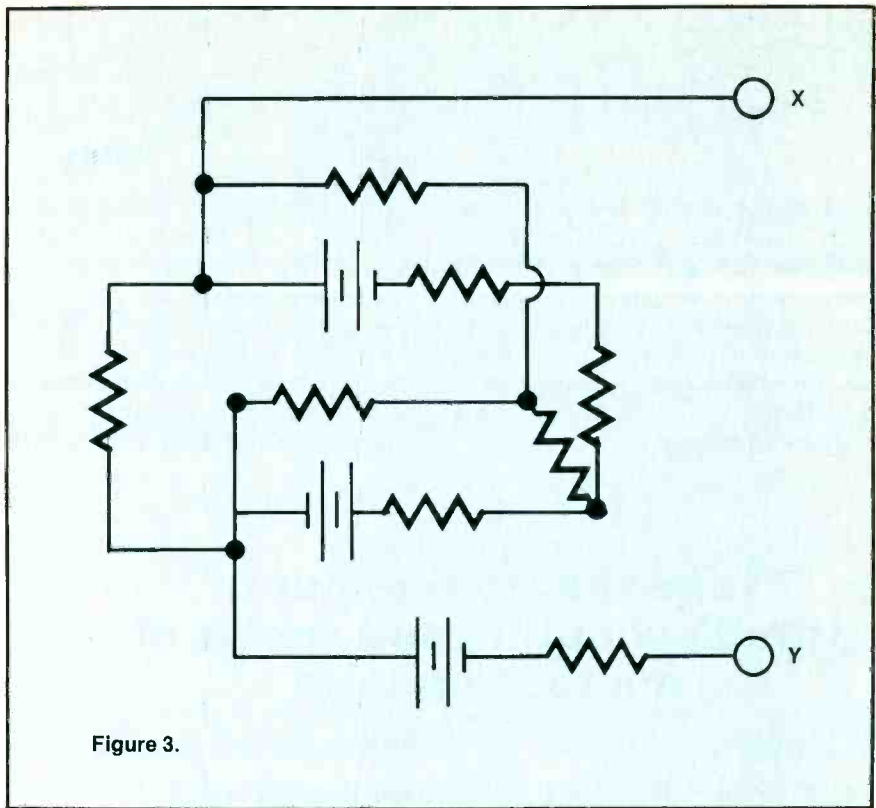


Figure 3.

Figure 3. This circuit, according to Thevenin's and Norton's theorems, can be replaced with either of the two circuits shown in Figure 2.

- **Delayed Sweep**
- **20MHz, Dual Trace**
- **Component Tester**
- **Much More**



Beckman Industrial

Instrumentation Products Division • Beckman Industrial Corporation • A Subsidiary of Emerson Electric Company
630 Puente Street • Brea, California 92621 • (714) 671-4800 T/WX: 910-592-1260 Telex: 188790

Circle (24) on Reply Card

look at the circuit of Figure 2(a). This Thevenin generator has a constant voltage source (V_{th}) in series with the Thevenin equivalent resistance. If you are looking into terminals X' and Y', you will see an open-circuit voltage that is identical to the open-circuit voltage in Figure 3.

Also, if you short the sources of voltages, then the resistance looking into the Thevenin's generator will be identical to the resistance looking into the circuit of Figure 3.

Because of the way the equivalent Thevenin generator circuit is calculated, it is necessary that the internal resistance of V_{th} must be

zero. If the resistance was any other value, then the voltage would change under varying load current conditions and it would no longer be a constant-voltage generator.

For the constant-current generator of Figure 2(b), it is also necessary to see the same terminal voltage and the same resistance looking into terminals X'' and Y''. The Norton resistance (R_n) is numerically equal to R_{th} and it is calculated in the same way.

A moment's reflection will show that if R_n and R_{th} are equal, then it is necessary that the internal resistance of I_n must be infinite. If this were not so, the resistance of I_n would be in parallel with R_n . That would reduce the resistance as seen looking into terminals X'' and Y''.

The Thevenin constant-voltage source can be very closely approached by using a closed-loop voltage regulator. Likewise, the Norton generator can be simulated using electronic circuitry. Later in this article, we will discuss an electronic constant-current generator.

Take the trouble out of troubleshooting and repair of microcomputers

Computerfacts

Choose Sams Computerfacts for detailed schematics, circuit board photos, troubleshooting tips, and replacement parts cross references covering more than 50 different microcomputers, printers, disk drives, and monitors. Sams works from actual production models disassembling each unit and testing each board. Every component location, every circuit track, and every waveform is checked and rechecked.

Coverage includes IBM, Apple, Commodore, Radio Shack, ATARI®, Texas Instruments, AT&T Computers, Epson®, Okidata, C.I.T.O.H., NEC® printers; Shugart, Tandon, Rana disk drives, and Hitachi®, Amdek®, Panasonic® monitors... and many more. Call 800-428-SAMS to order the Computerfacts you need.

Troubleshooting and Repair Guides

These easy-to-understand repair and maintenance guides provide the instructions you need to solve problems unique to the Apple® II+ / IIe, IBM® PC, Commodore™ 64, and Commodore 1541 disk drive. The books contain schematic diagrams, block diagrams, photographs and troubleshooting flowcharts to trace the probable cause of failure. A final chapter on advanced troubleshooting shows you how to perform more complicated repairs.

Apple II+ / IIe, No. 22353, \$19.95
 IBM PC, No. 22358, \$19.95
 Commodore 64, No. 22363, \$19.95
 Commodore 1541 Disk Drive, No. 22470, \$19.95

To order call
800-428-SAMS
 Ask for Operator 803
 In Indiana call 317-295-5566



The constant-current diode

Figure 4 compares the constant-current diode with the simplest JFET construction used to make such a diode. Note that the JFET gate is connected to the source so

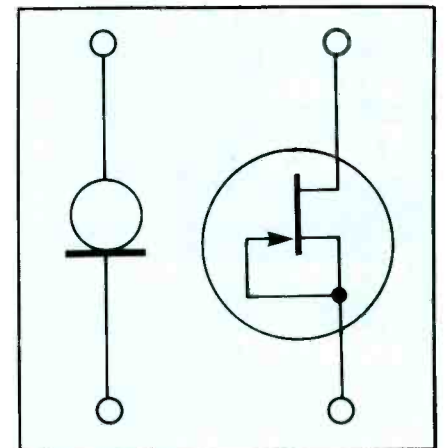


Figure 4. The symbol for the ideal constant-current diode along with the simplest JFET (junction field-effect transistor) construction of an actual device with a characteristic that approaches that of the ideal device.

Book No.	Quantity	Price
Shipping & Handling		\$ 2.50
AK, CA, FL, IN, NC, NY, OH, TN, WV residents add local sales tax		\$
Total		\$
Name		
Address		
City		
State	Zip	

Bill me credit card VISA MC AE


Account No. Exp. Date

Signature (required)

Check or money order enclosed. Make checks payable to Howard W. Sams & Co. Mail this form with payment to Howard W. Sams & Co., Inc., Dept. DM • 4300 West 62nd Street • Indianapolis, IN 46268

SAMS

Circle (25) on Reply Card

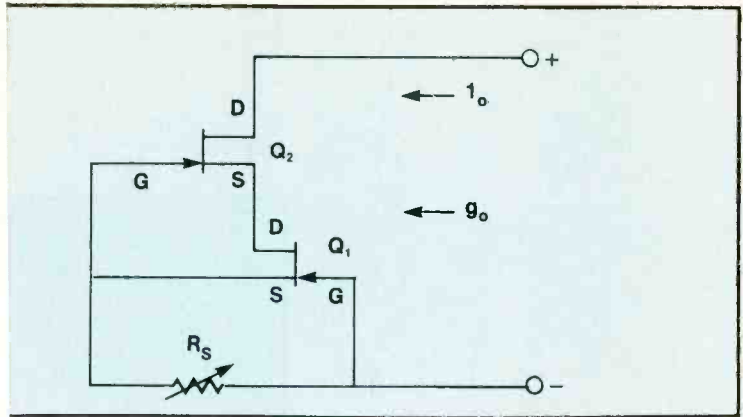

her constant-current device, this circuit using two FETs has the advantage of a higher impedance.

you could make your own constant-current diode by using a saturated JFET. It is only necessary to pick the right JFET with the right saturating current. The real problem is that the current may not be related to the actual current that you desire.

A better version is shown in Figure 5. With this arrangement, it is possible to select the desired operating current. Another version is shown in Figure 6. It uses two JFETs and it has the advantage of having a higher impedance. Also, it is adjustable. When experimenting with this constant-current generator, you must be sure that both JFETs are conducting when the circuit is in operation.

TOTAL SERVICE FOR THE VIDEO REVOLUTION.

Now you can offer fast total service for all the products of the video revolution. Increase service business without increasing overhead.

Depend on PTS for quality replacement parts and fast repair service.



Send more... information on total service for these video products!

TV PRODUCTS
Tuners and Modules

MATV/SMATV
Converters and Amplifiers

REMOTES

PRO LINE
Alignment Tools, Tuner-lube and more.

VCR Total Unit Service

TVRO
Receivers, Downconverters, Actuators and Arms

Name _____

Company Name _____

Address _____

City _____ State _____

Zip _____ Phone _____

For the name of the PTS Servicenter or Authorized Distributor nearest you call or write:



PTS CORPORATION
CORPORATE HEADQUARTERS
P.O. Box 272
Bloomington, IN 47402
(812) 824-9331



Figure 5.

Figure 5. This arrangement yields a nearly constant current that may be selected by varying the resistance.

Circle (26) on Reply Card

The very earliest electronic constant-current generators used pentode vacuum tubes because of their high impedance and constant-current output after the saturation point has been reached. Pentodes, of course, have the disadvantage that they require filaments and additional electrode connections. So, it was not possible to buy off-the-shelf constant-current diodes similar to the ones now available with JFETs. An additional advantage of using JFETs is that there are both N-channel and P-channel devices. Therefore, it is possible to use either (with corresponding changes in polarities).

Circuits

Constant-current diodes can be connected in parallel to increase the current rating, or in series to increase the voltage rating. (See Figure 7.) When connected in series, it is necessary to use parallel resistors across each diode to assure that they are all operating under identical voltage conditions.

Some practical applications of constant current diodes are shown in Figure 8. For the application shown in (a), a constant-current diode is used to produce a linear charging voltage on the capacitor. This causes any sawtooth waveform at the base of the UJT (uni-junction transistor) to have a linear ramp. Without the constant-current diode, the sawtooth ramp will be a time-constant curve.

Figure 8(b) shows how the constant-current diode can be used in conjunction with a zener diode to produce a very accurate reference voltage. This circuit utilizes diodes that have a zero temperature coefficient so that the output voltage does not change as a result of changes in operating temperature. This circuit configuration also is

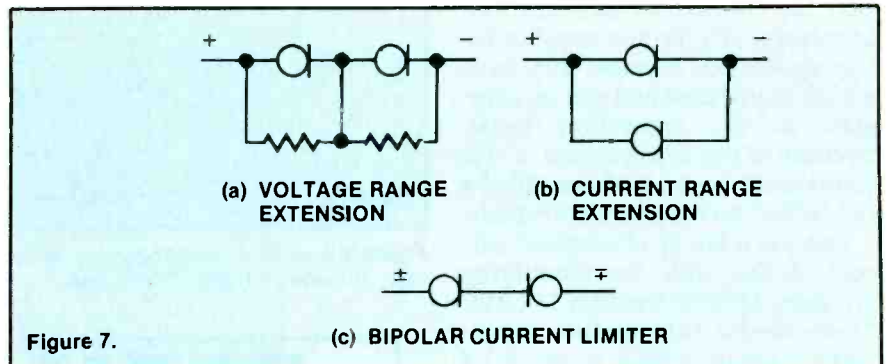


Figure 7.

Figure 7. Constant-current diodes can be connected in series to extend the voltage range, or in parallel to extend the current range.

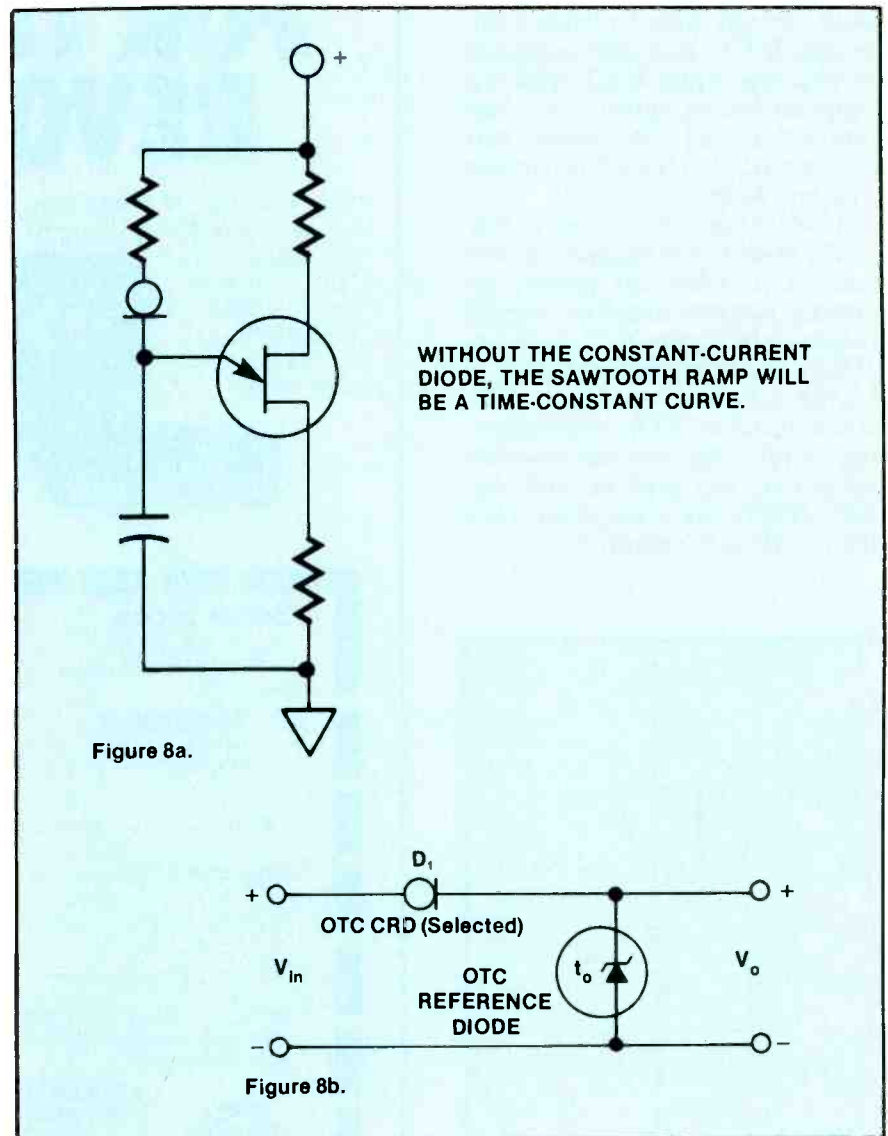


Figure 8. In (a), the constant-current diode in the circuit will cause any sawtooth waveform appearing at the base of the UJT to have a linear ramp rather than a time-constant curve. In (b), a constant-current diode in conjunction with a zener diode produces a highly accurate reference voltage.


A.W. Sperry Instruments introduces
**The 4½ digit DMM with
 the 3½ digit price.**

Another A.W. Sperry Instruments first! Our new **AWS DM-7010** combines the precision of 4½ digit readings with all the most-wanted features you've been looking for. We've even included a built-in frequency counter (up to 200KHz)! With 9 functions and 33 ranges, the **AWS DM-7010's** expanded capability can't be beat!

And that's not all! Included among the special functions built into the **DM-7010's** small, self-contained housing are: conductance, diode test and an instant audible continuity check. The **DM-7010** has a basic DC Volt accuracy of 0.05% and loads of built-in safety features.

You'd expect to pay \$300 or more for an instrument boasting this kind of performance, yet the **AWS DM-7010** can be yours for a low **\$170!** Now there's no need to pay more for the accuracy and quality you need in a DMM.

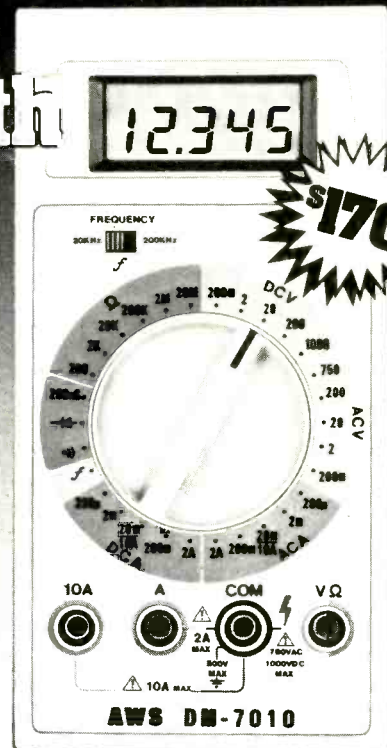For more information, call your distributor or A.W. Sperry Instruments, Inc., P.O. Box 9300, Smithtown, N.Y. 11787. **800-645-5398** Toll-Free (N.Y., Hawaii, Alaska call collect 516-231-7050).



A.W. SPERRY INSTRUMENTS INC.
The Measurable Advantage.

Circle (27) on Reply Card

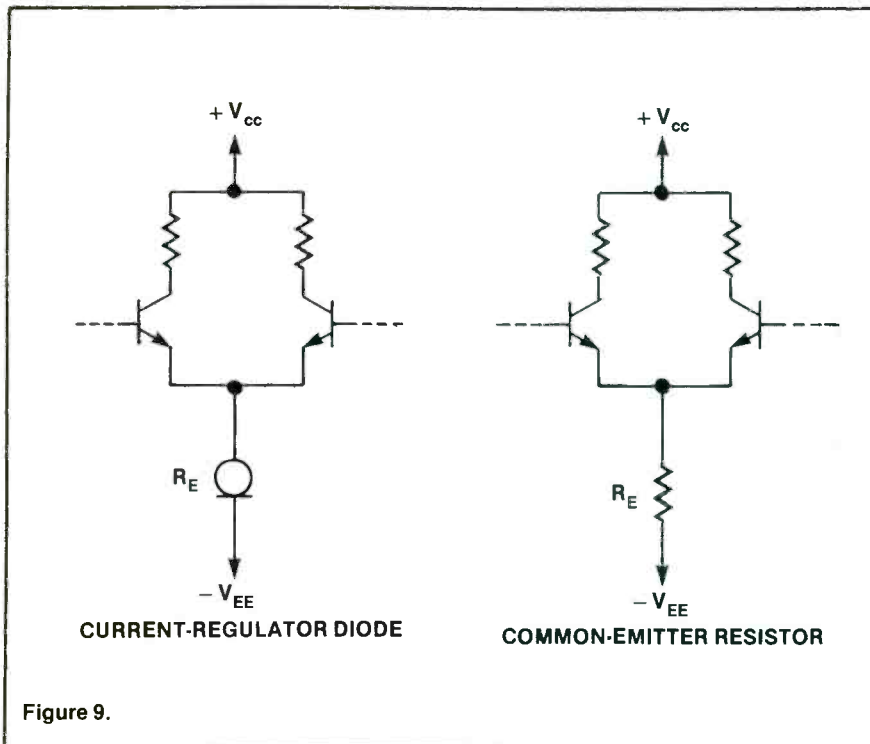


Figure 9.

Figure 9. A differential amplifier must be fed a constant current in order to operate properly. This may be accomplished by using a large-value resistance, or, preferably, a constant-current diode.

effective for removing noise and ripple voltages from the input voltage. An attenuation of about 100dB can be attained for frequencies up to several hundred kilohertz!

Figure 9 shows the use of a constant-current diode for the current sourcing of a differential amplifier. In order to operate effectively, a differential amplifier must be fed a constant current to the emitter junction. The constant current diode is ideal for this application. You will sometimes see a large resistance value being used to simulate a constant-current source. A good example of this application is evidenced when a high resistance is substituted for the constant-current diode. This also is shown in Figure 9. A simple Ohm's Law analysis will show how this works. (See Figure 10.)

Capacitance, logic and more. For less.

Now, a fully-loaded DMM combines a capacitance meter, logic probe, and an hFE meter, all for the price of a DMM.

TTL Logic Probe: 20 MHz

Hi/lo/off indications

Detects 25nS pulse width

Capacitance: 5 ranges (2nF to 20μF)

hFE (NPN or PNP): 1 range (1000)

DMM: DCV-5 ranges (.2V to 1kV)

ACV-5 ranges (.2V to 750V)

DCA-4 ranges (200μA to 10A)

ACA-3 ranges (20mA to 10A)

Ohms-7 ranges (200 Ohms

to 2000 Megohms)

Continuity beeper


Diode check

Built-in bail

Anti-skid pads

See one now at your local Beckman Industrial distributor.

DM25L... \$89.95*

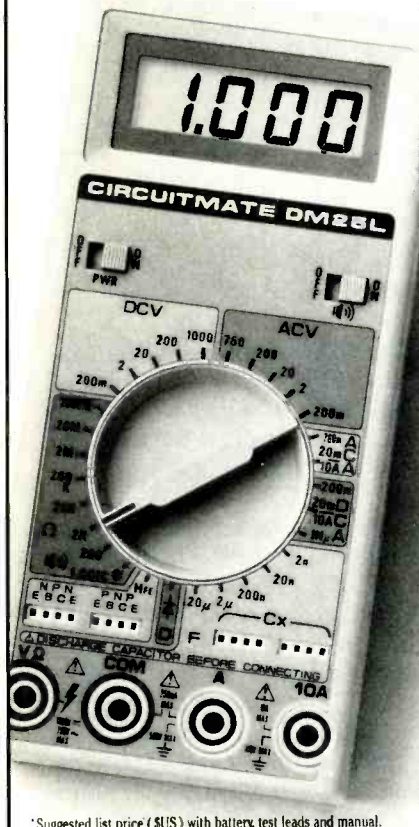

*Suggested list price (\$US) with battery, test leads and manual.

Beckman Industrial™

Beckman Industrial Corporation
A Subsidiary of Emerson Electric Company
630 Puente Street, Brea, CA 92621
(714) 671-4800

© Copyright 1985 Beckman Industrial Corporation

Circle (28) on Reply Card

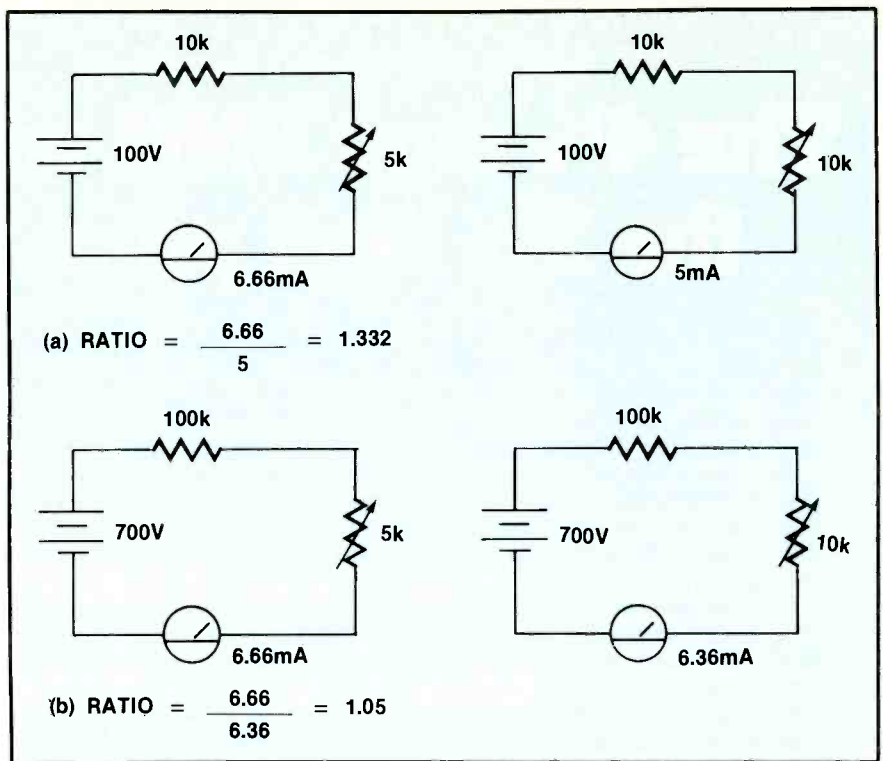


Figure 10. Analyzing this circuit in terms of Ohm's law explains why use of a large series resistance provides relatively constant current.

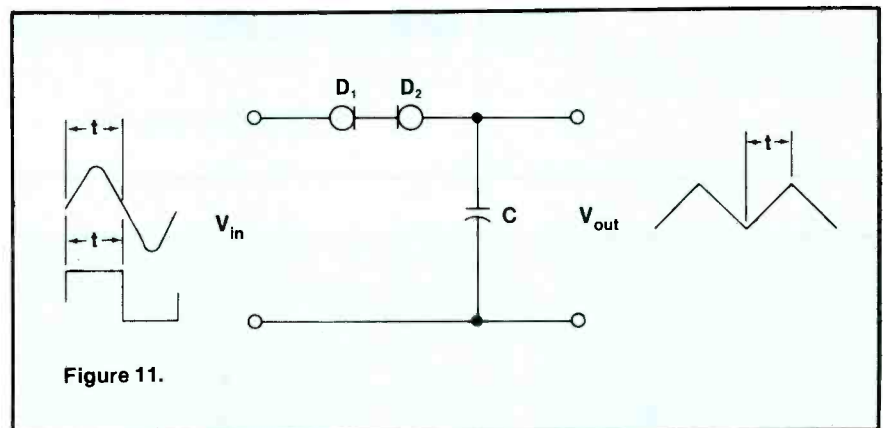


Figure 11.

Figure 11. Two constant-current diodes connected back-to-back yield a very linear triangular output waveform with an input of a sine or square wave.

In Figure 10(a), there is a 100V supply in a series with a 10k resistor. The resistance across the source is varied from 5k to 10k. Note that this causes the output current to vary from 6.66μA to 5μA. The ratio of maximum to minimum current in this case is 1.332.

When the series resistance is increased to 100k, as shown in Figure 10(b), it is necessary to use a voltage of 700V so that the maximum current (6.66μA) will be the same as for the circuit of Figure 10(a). Now when the resistance is changed from 5k to 10k, the ratio of maximum-to-minimum current is only 1.05.

Clearly, the higher resistance results in a more nearly constant current. If the resistance is raised even higher—above 100k—it will be more effective in producing a regulated output current.

This simple problem helps to explain why high-impedance devices such as pentodes and JFETs are preferred for constant-current work. It also shows why a high resistance value may be used in place of a constant-current diode.

Figure 11 shows how two constant-current generators, connected back-to-back, can be used to make a linear triangular output waveform. Either a sine wave or a square wave can be used as the in-

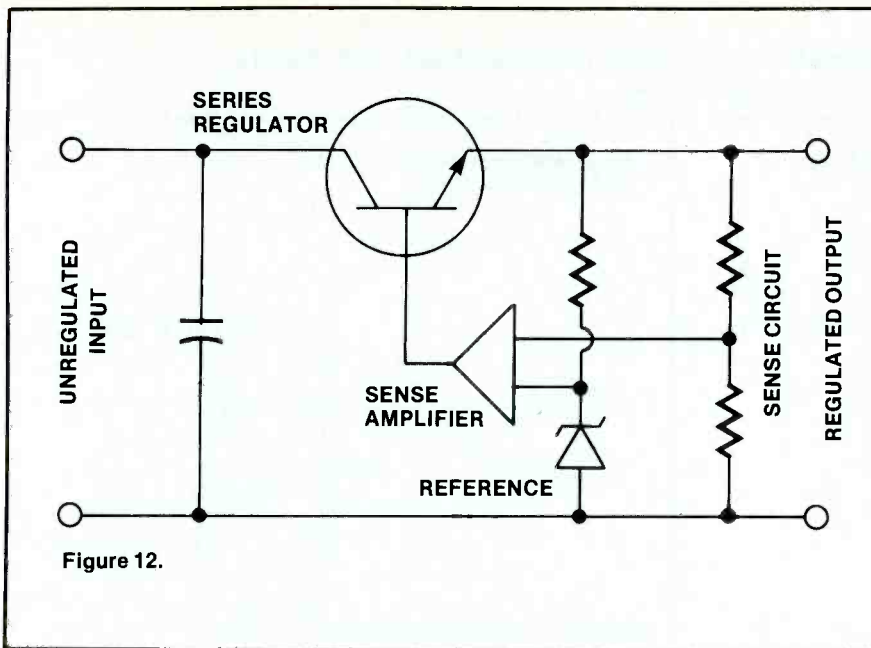


Figure 12.

Figure 12. A zener diode can be used to make a constant-voltage regulator when connected like this.

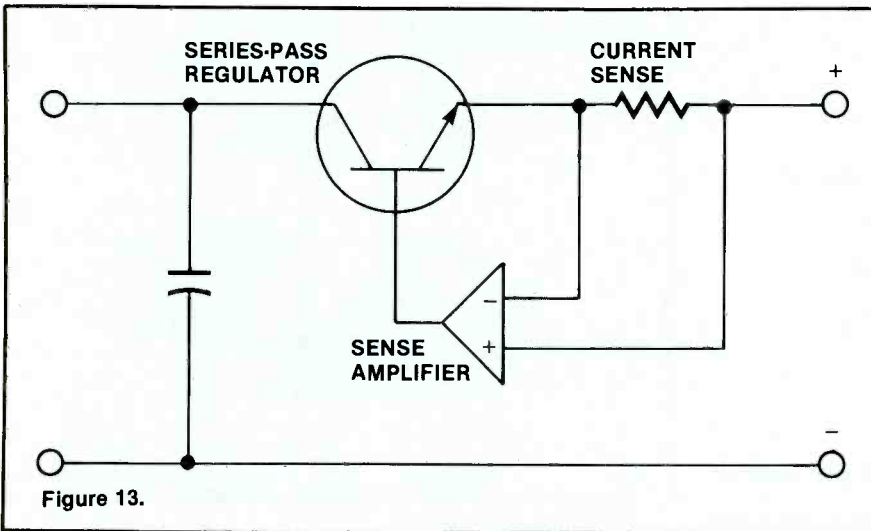


Figure 13.

Figure 13. In this constant-current regulator, the voltage drop produced by the current is sensed and used to control the output current.

put waveform. This circuit is useful for making an inexpensive function generator.

Of course, there are many other applications of constant-current devices and supplies. When you see the diode symbol, think of a high-impedance device that holds the current constant over a range of values stipulated by the manufacturer.

An electronic constant-current generator

To make a constant-voltage supply, it is necessary to use a sense circuit to monitor the output voltage. This sense circuit often is made of two or three resistors in

series across the supply output. This is shown in Figure 12. The sensed voltage is compared with the reference voltage, and a correction is made when the voltages are not the same.

Figure 13 shows how an electronic constant-current regulator is made. In this case the current being regulated flows through a series resistor. The drop across the resistor represents the supply current. That voltage drop is amplified and used to control the series regulator. A change in current is sensed by R and used to correct the output current. The overall effect is to hold the output current constant.

ES&T

DISCOVER PROFITS WITH THE PRB BELT SYSTEM



PROJECTOR RECORDER BELT offers you the world's most complete inventory of replacement belts for all types of electronic equipment including . . .

- Video Recorders
- Turntables
- Cassette Recorders
- Projectors
- 8-Tracks
- 102 Video Belt Kits

PRB has the replacement belt you need in just the right shape, size and material. PLUS . . . our system helps you find that "perfect" replacement belt easily and fast. DISCOVER . . . The PRB Belt System for maximum convenience that assures profitable returns.

PRB . . . THE SOURCE FOR OVER 10,000 ELECTRONIC COMPONENTS

We stock virtually every electronic component. These are all high quality electronic components at everyday low prices backed by personalized service you can depend on. PRB will even pay the freight on your 1st pound of the UPS charge (ground only).

For details on our profitable belt system and a FREE copy of our 98 page 30th Anniversary Catalog, just write or call toll free . . .

NATIONAL 1-800-558-9572 IN WISCONSIN 1-800-242-9553

BUSINESS NUMBER

1-414-473-2151

In Canada call collect: 1-613-225-5003
TLX 4994411 PRB USA

"See Us at Booth A-14
Ed Show-Las Vegas




PROJECTOR RECORDER BELT
200 Clay Street, Whitewater, WI 53190

Circle (29) on Reply Card

Chassis—Magnavox E31
PHOTOFACT—2257-2


1

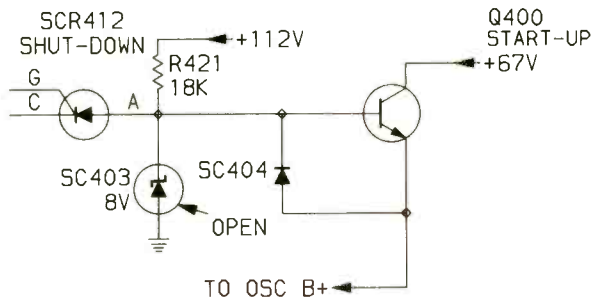

Symptom—Horizontal foldover and/or slow or no start-up
Cure—Check 8V zener SC403, and replace it if open.

Chassis—Magnavox E31
PHOTOFACT—2257-2


2

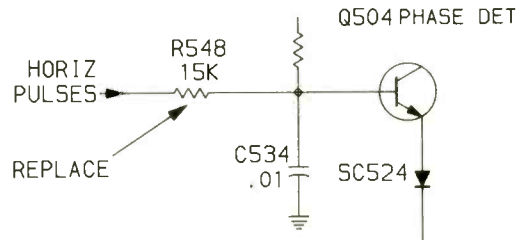

Symptom—Erratic shut-down
Cure—Check R548, and replace it with a 15k 1W carbon-film resistor.

Chassis—Magnavox E31
PHOTOFACT—2257-2


3

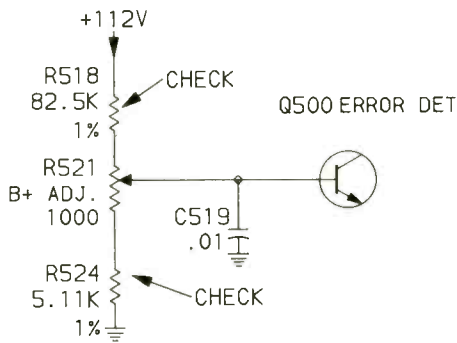

Symptom—Regulated B+ is high, sometimes triggering shutdown
Cure—Check R518 and R524, and replace any that are out of the 1% tolerance.

Chassis—Magnavox E31
PHOTOFACT—2257-2


4

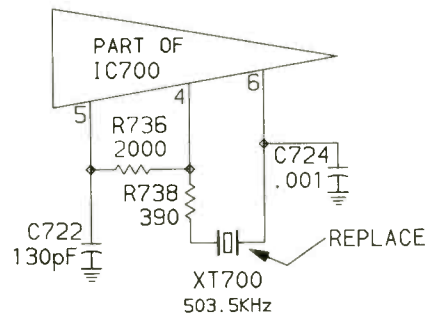

Symptom—Intermittent start-up, shutdown or loss of horizontal locking
CURE—Replace resonator XT700.

Chassis—Magnavox 13C2
PHOTOFACT—1940-1


5

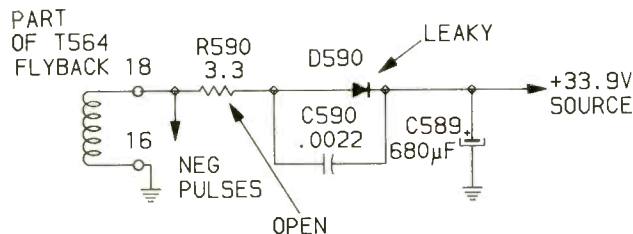

Symptom—Constant shutdown
Cure—Check R590 and D590 and replace both, if the resistor is open and the diode is leaky or shorted.

Chassis—Magnavox E51
PHOTOFACT—2189-2

6

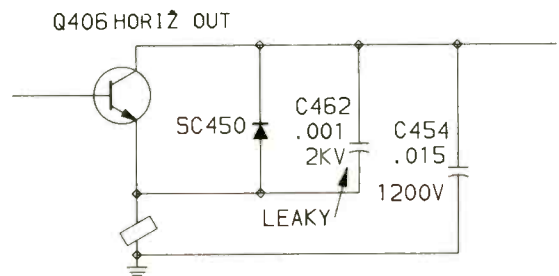

Symptom—Immediate shutdown
Cure—Check capacitor C462 and replace it if leaky or shorted.

Products

Hand-held dual trace scope

Soar Corporation is introducing model 1000 Soar Scope that may be hand-held, is small in size and can be used in a variety of light ambients including bright sunshine. There is a built-in battery back-up memory and a 128x160 dot LCD with variable contrast




control and 6 hours battery operation. This scope features dual trace with 10mV per division sensitivity, ± 3 dB or less for dc 200kHz and has a sampling rate of 3.2MHz.

Circle (75) on Reply Card

Floppy disk drive repair tool

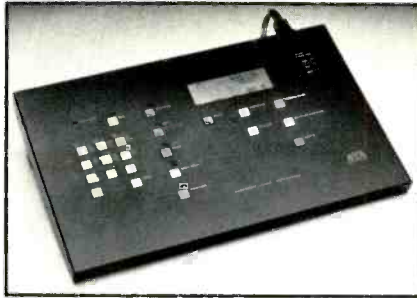The model 803XP exerciser/alignment scope by AVA Instrumentation incorporates the functions of an oscilloscope and a programmable drive exerciser in



one portable instrument that is dedicated to floppy drive head alignment. All alignment information is presented pictorially and numerically on a solid-state flat panel LCD display. All parameters necessary for proper alignment are displayed, with 1-button operation.

The built-in programmable exerciser is compatible with all sizes of floppy drives, including 8-, 5¼- and 3½-inch, and can be programmed to test in any sequence of steps.

This repair tool was designed to help technicians perform drive preventive maintenance without any additional test equipment.

Circle (76) on Reply Card

Analog oscilloscope conversion

Sibex is offering the model 602 Scope Memory, an add-on device that converts an analog oscilloscope into a dual channel digital storage scope. Connect to any standard dual channel scope; the unit is an alternative for users who



cannot justify the expense of purchasing a complete new scope. The model 602 stores both analog and digital signals in a single sweep. It features 18 selectable sample times with a 1.4MHz maximum sampling rate. Each input is selectable in eight ranges. A comparison mode is an additional feature.

Circle (77) on Reply Card

Send Purchase Order
Check, Money Order, or C.O.D.
or Call Toll Free
800-223-0826
in N.Y. State (212) 865-5580
Nobody Beats Us!



\$69⁹⁵ JERROLD CORDLESS
CABLE T.V. CONVERTER
Model DRX3-105/400 (58 CHANNELS)

ALSO AVAILABLE TEKNICA - Model 6510 with volume control \$139⁹⁵

CO-AXIAL CABLE

Braided bare
Copper Shield



RG 59/u

\$44⁵⁰/1000 Foam polyethylene dielectric

RG-6/u 69⁹⁵/1000
Add \$5.00 per Roll for Shipping

SANYO
2SC1308K
ORIGINAL

TOSHIBA
2SC1172B
ORIGINAL

100 up **\$1.49**
10-29... \$1.99 30-99... \$1.69

\$10⁹⁹
each

RCA
Triplers
SK3306/Equivalent to ECG-523
ECG-526
SK3304/Equivalent to ECG-500A

2 WAY - 75 ohm u/v
Splitter
49¢/100 lot
99¢ each
MT-2

21¢/100 lot
MATCHING
TRANSFORMER MT-1

"F" - FITTINGS
F-59ALM with attached
1/2" ring for RG-59/u cable
12¢/100 9¢/1000 **7¢/5000**

F-56ALM with attached
1/2" ring for RG-6/u cable
15¢/100 10¢/1000 **8¢/5000**

WELLER
WTCP R CONTROLLED OUTPUT
SOLDERING STATION

Model
WTCP-R

\$69⁹⁵

HITACHI 20 Mhz Dual
Trace Scopes

V-212-**\$439⁹⁵** Probes included
V-222-**\$489⁹⁵**
V-223-**\$539⁹⁵** DELAYED SWEEP

■ MASTER CARD ■ VISA

OMNITRON

ELECTRONICS

770 Amsterdam Ave., New York, NY 10025

SHIPPING CHARGES

For Orders	Add
\$25-100	\$6.50
\$100-500	\$8.50
\$500-750	\$10.50
\$750 and up	\$20.00

Write for
FREE
CATALOG
136 page

Circle (30) on Reply Card

Check Digital IC's in-circuit Fast!

In the field or on the bench. B&K-PRECISION gives you the answers for TTL or CMOS



Model 550 (for TTL) \$395
Model 552 (for CMOS) \$395

New B&K-PRECISION IC Comparator Testers/Logic Monitors put you on the fast track to digital troubleshooting. IC's are tested by comparison to a known good device, allowing you to test hundreds of types with one simple operation.

As logic monitors, they simultaneously indicate the logic states of up to 20 IC pins. No need to check pins singly with a logic probe.

Tests most 14 to 20 pin, 54 and 74 Series TTL (Model 550) or 4000 and 74C Series CMOS (Model 552) devices.

- Convenient one button testing
- Reverse polarity and overvoltage protection
- Uses power from equipment under test
- Memory stores short duration pulses and intermittent events
- Zero insertion force reference IC socket
- LED at each IC pin identifies where fault exists
- Includes 16 and 20 pin DIP clips
- Compact hand-held size

Available from stock at your local B&K-PRECISION distributor. For more information contact your distributor or:

BK PRECISION
DYNASCAN
CORPORATION

6460 West Cortland Street
Chicago, Illinois 60635 • 312/889-9087
International Sales, 6460 W. Cortland St., Chicago, IL 60635
Canadian Sales: Atlas Electronics, Ontario
South and Central American Sales,
Empire Exporters, Plainview, NY 11803

Circle (31) on Reply Card

Built-in Component Checker

The model 620C oscilloscope by A.W. Sperry Instruments incorporates a special built-in circuit called the Component Checker that is designed to test single or multiple components, in or out of circuit.



The display obtained will show component faults, size and characteristics, thus allowing troubleshooting and tests of solid-state circuits and components without circuit power.

Component Checker specifications include maximum 9Vac at terminal, no load, maximum 2mA current, with terminal shorted. Internal resistance: 4.7kΩ.

Circle (78) on Reply Card

Dual trace portable scope

Ballantine Laboratories' enhanced model 1024B Travelscope, a dual trace portable oscilloscope, is a field instrument with laboratory and bench instrument applications.

This bright, high acceleration, high resolution scope uses a flat-face CRT with a built-in internal graticule to help eliminate parallax. Further, the 1024B's



CRT is a post-accelerated type with total accelerating voltage raised to 2kV, providing a brighter, higher resolution trace than mono-accelerated types. The 25MHz frequency response extends the 1024B's use to fast signals and the passive delay line permits display of the leading edge of fast rise time signals and pulses.

Circle (79) on Reply Card

Digital storage, auto setup scope

Model 4500 digital oscilloscope from Gould Electronics is controlled exactly like a conventional oscilloscope, using familiar volts and seconds per division control terminology. The automatic setup mode finds repetitive signals on an input and sets sensitivity, offset and sweep speed to display several repetitions of the signal. After automatic setup is complete, the




user can modify the settings as required. There is a floppy disk option in use any time waveforms must be logged.

Circle (80) on Reply Card

Dual-beam oscilloscope mainframe

The Iwatsu dual-beam 100MHz oscilloscope mainframe, model DS-8122, was designed to accept up to three plug-in units. A 1-gun, 2-beam system makes it possible to observe two high-speed single-shot phenomena simultaneously or to observe four traces at the same time when two vertical dual-input units are plugged in. The mainframe itself incorporates a character generator to display the data from the plug-in units on a 6-inch dome-mesh, high luminance CRT.

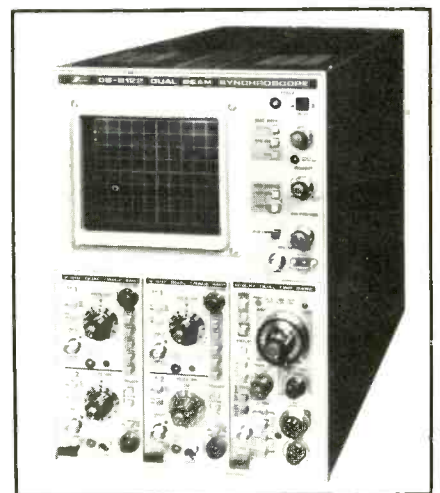

Continued on page 70

Photofact

These Photofact folders for TV receivers and other equipment have been released by Howard W. Sams & Co. since the last report in ES&T.

ADC

Chassis M9C2-1K1, M9C2-1K2, M9C2-1K 2391-1

MAGNAVOX

Chassis 19C112-00BA, 19C122-00CA,
19C123-00CA, 19C124-00CA 2390-1

MAGNAVOX

Chassis 19C501 through 19C519-00AA/BA 2394-1

PRODUCTION CHANGE BULLETIN

RCA

FKR485S, FKR485W, GKR637PR, GKR639P,
GKR650T, GKR654H, GKR658P,
GKR671TR, GKR696PR 2391-3

SEARS

564.42610450 2392-1

SEARS

564.42680450 2395-1

SHARP

19J79, 19J81 2390-2

SHARP

13J330 2392-2

SHARP

19J69 2393-1

SHARP

25J01 2394-2

SHARP

13J41 2395-2

SONY

Chassis SCC-548P-A/Q-A/S-A/T-A 2391-2

SONY

Chassis SCC-595A-A 2393-2


VIDEO CASSETTE RECORDERS

SANYO

Models VCR3900/II, VCR4000/-2

SEARS

S64.53110250

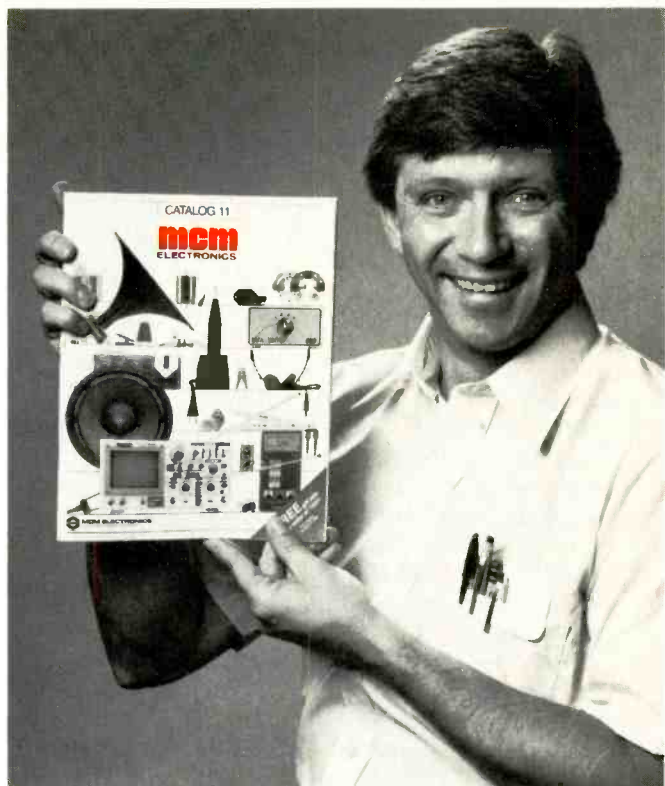

There's Always One Catalog You Can Count On- **MCM** **ELECTRONICS!**

You want a company you can depend on for quality.

You want a company that's famous for fast service.

And you want a company that's known for great, low prices.

What you want is **MCM Electronics**.

Because if you want to get the best out of your business, it only makes sense to order from the best.

Nobody will serve you better.

CATALOG #11 NOW AVAILABLE

CALL TOLL FREE
1-800-543-4330

(IN OHIO, 1-800-762-4315)
(IN ALASKA AND HAWAII, 1-800-858-1849)



MCM ELECTRONICS
A DIVISION OF PREMIER INDUSTRIAL
858 E. Congress Park
Centerville, OH 45459

Circle (32) on Reply Card

Continued from page 68

Signal output terminals also are provided for outputs of vertical signals, timebase signals, gate signals and calibration voltages, which extend the versatility of the model DS-8122.

Circle (81) on Reply Card

Analog/digital storage scope

Kikusui International announces its 40MHz dual-channel, portable analog/digital storage scope. The DSS 5040's sine interpolation capability offers the user a higher single-occurrence capture capability: 10MHz. Most scopes in this range use linear techniques, resulting in 2MHz to 4MHz.

The function selection controls are identical to those on an analog scope. The only additional controls are a push-button selector for sine or pulse interpolation, and the push-button controls for store, erase and reference memory. Circuitry within the scope eliminates the multistep, function-select sequence. Kik cameras attach easily for photographic records.



Constant resetting of the trigger level is eliminated by a patented level-lock circuit that controls the trigger signal and automatically adjusts the trigger level. To simplify triggering on complex waveforms, a variable trigger hold-off function is available.


Circle (82) on Reply Card

Soldering iron's cermet element

Oryx has introduced an electronically controlled soldering iron, the Oryx Platinum 45, which incorporates a thick film cermet element and an ultra stable platinum resistance temperature sensor, together with miniaturized electronic control circuitry. The control circuit is built into the handle of the iron.

This soldering iron runs direct from a 115V supply. It is rated at 45W and is supplied with a burn-proof power cord and molded 3-pin

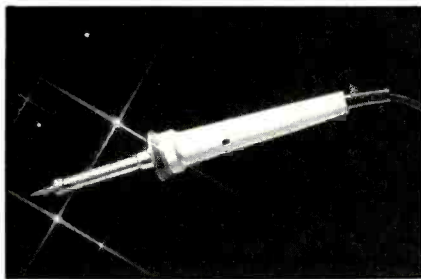plug. Its tip temperature is controlled to within $\pm 5^\circ\text{F}$ over the range 490°F to 750°F . The operating temperature is adjustable by the user.



The electronic control circuitry features zero-point switching to ensure spike-free operation of the heating element, and temperature overshoot is avoided by means of a proportional control circuit.

Circle (83) on Reply Card

Isolated ac power source

VIZ Test Equipment, a division of *VIZ Manufacturing* introduced model WP-32, Monitor ISO-V-AC III that provides isolated ac output from 0V to 150V and 10A continuous output to a maximum 1,300VA, at 60Hz. This isolated ac power source is designed to provide isolated power to equipment in fixed or variable output voltages. These features offer safety to individuals and equip-



ment, and provide a broad range of output voltages should input vary. The WP-32 can be used in incoming or outgoing quality control testing, in-line and final production environments, and in maintenance and service of a variety of electronic products. Additional uses include circuit design work when checking operation at voltages higher or lower than normal. This technique also can be used to help detect intermittent circuit defects.


Circle (84) on Reply Card

Data line monitor

A pocket size monitoring tool

provides a means of determining the status or condition of the RS-232 communication ports. This advanced model has bipolar LEDs that indicate *red* or *green* to show if the signal is high, low, or off, if in an illegal condition.

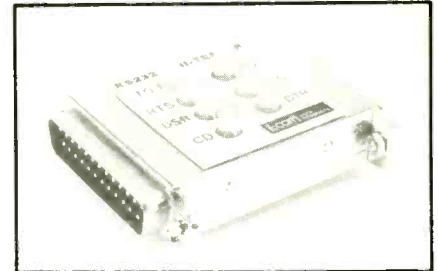The Mark II data line monitor, *L-com Data Products*, installs in series between the terminal and the CPU equipment. The seven



LEDs allow continuous sources of trouble in about 95% of the problems associated with data communication networks, according to the company.

No external power is required as the DLMS-2 derives its power from the RS-232 interface. Each LED draws a nominal 3mA and operates with signals as low as 3V to 26V. Equipped with male/female RS-232 connectors. Size: $2\frac{1}{2}'' \times 2\frac{1}{8}'' \times \frac{3}{8}''$.

Circle (85) on Reply Card

One tube radio kit

A one tube radio kit providing the experimenter or antique radio buff the opportunity to experience early radio construction and operation is available from *Antique Electronic Supply*.

The kit comes complete with breadboard, tube and other parts. Batteries and headphones are optional. A 20-page catalog covering parts such as tubes, parts and books is included.

Circle (86) on Reply Card.

Test equipment update

Huntron Instruments has introduced improved models of its Tracker 1000 and 2000 test instruments. The most notable new features are redesigned carrying cases and modernized front panels. A stronger, reinforced carrying handle that doubles as an adjustable tilt bail also has been added. The front panel layout has been simplified, and color coding added. LEDs are used to identify the test range selected.

This equipment tests boards or

components without system power being applied, generating a current limited sine wave that is injected across two points of any device under test, creating a unique current vs. voltage signature that is displayed on the CRT.



Circle (87) on Reply Card

Telephone loop tester

The new model 5, three-in-one local loop tester, introduced by *Triplet* (a *Penril Company*), has an LCD display with a front panel color-coded guide to transmission test limits. The tester provides local loop test capabilities most often needed by installation and repair personnel plus an ac/dc voltmeter and multitone generator.

Constructed per AT&T Sub-

scriber Loop Transmission Test Set publications 41009 and 55020, model 5 utilizes a tone generator and transmission test set to measure power influence, circuit noise, circuit loss or line milliamp checks on telephone company or privately installed telephone lines.

The tone generator has 15 switch-selectable frequencies.




Two other frequencies may be obtained with an optional kit that includes precision resistors to achieve any tone between 100Hz and 5kHz.

Circle (88) on Reply Card

Autoranging DMM with memory

EXTECH introduces its rotary dial digital multimeter with large LCD display that measures Vdc,

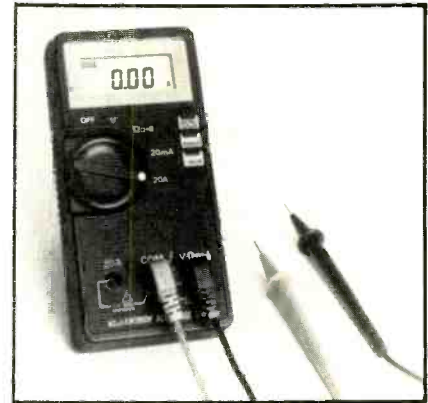Vac, dcA, acA resistance and diodes. Features include instant autoranging range hold and manual ranging when required; autopolarity auto-zero accuracy and resolution. This DMM with memory is housed in a sturdy soil-resistant case, and powered by a 9V battery. Eighteen ranges, including five Vdc and ohm ranges, and four Vac and low power ohm



ranges with 2,000 counts per range, improve resolution. Pressing the MEM key stores the last two significant digits and subtracts them from subsequent measurements.

Circle (89) on Reply Card



ATTENTION TECHNICIANS

- ★ JOB OPENINGS
- ★ MONTHLY TECHNICAL TRAINING PROGRAM
- ★ BUSINESS MANAGEMENT TRAINING
- ★ LOW COST INSURANCE
- ★ CERTIFICATION
- ★ TECHNICAL SEMINARS


All of this in a nonprofit international association for technicians

FIND OUT MORE:



604 N. Jackson St.
Greencastle, IN 46135

LOW COST PROBES FOR ALL SCOPES

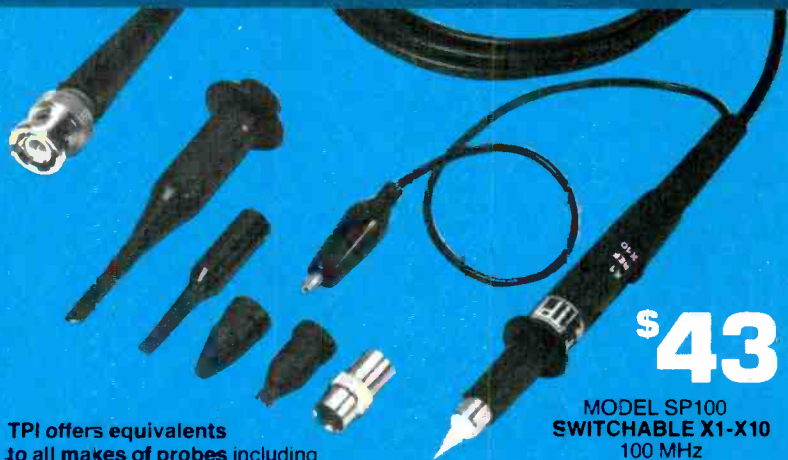

\$43

MODEL SP100
SWITCHABLE X1-X10
100 MHz

TPI offers equivalents to all makes of probes including modulators, at savings up to fifty percent. TPI probes compensate to all scopes. Slender, flexible cables are easier to handle yet more durable because of their unique center conductor. Performance is guaranteed.

FOR FAST RESPONSE CALL

800-368-5719

In Calif. 800-643-8382

**TEST
PROBES, INC.**



Your Probe Specialists
COLINE U.S. SALES & STOCKING SOURCE

P.O. Box 2113, LA JOLLA, CALIFORNIA 92038 (619) 459-4197

Circle (38) on Reply Card

Literature

New-Tone Electronics offers literature on its new line of NTE static control products. Included are descriptions for a field service kit, wrist straps, mats and anti-static foam. Also available is the Technical Guide and Cross-Reference manual, which cross-references more than 3,200 parts to 220,000-plus industry part numbers.

Circle (125) on Reply Card

Tools and test equipment expressly for servicing electronics and telecommunications equipment, including computers, is described according to category in the **W.S. Jenks & Son's** 1986 catalog. The 96 pages and four-color cover are profusely illustrated and more than 1,000 manufacturers are represented.

Circle (126) on Reply Card

Technical information is combined with cartoon-style characters in the **PTI Industries** Datashield booklet, which emphasizes the need for protection against dirty power.

Circle (127) on Reply Card

Five major product categories of automatic cord control reel products highlight the **Cordomatic** catalog, which contains comprehensive descriptions and full-color illustrations of the company's complete product line.

Circle (128) on Reply Card



Circle (129) on Reply Card

Minitool offers a folder showing precision miniature hand tools for fine assembly work, delicate deburring, and printed circuit design and repair. The folder includes technical data as well as prices and ordering information.

"The Monitor," a quarterly newsletter, is available from **Dranetz Technologies**. Covering a range of topics from monitoring and analysis of power line problems, complex operations and processes, to effective energy cost reduction techniques, this publication includes ap-



plication information, new product announcements and service and maintenance techniques.

Circle (130) on Reply Card

HIGH VOLTAGE TRIPLERS/MULTIPLIERS

REPLACEMENT FOR

ECG®/GE®/SK®

500A/GE527 & SK3304	8.75	6.95
523/GE528 & SK3306	8.85	7.20
526A/SK3306	8.85	7.20
528/SK3906	10.70	8.70
529/GE529 & SK3307	9.99 3 MIN.	7.95 100 MIN.

OUTPUT TRANSISTORS

165/SK3115 & GE38	2.25	1.95	1.75
238/GE37 & SK3710	2.25	1.95	1.75
283/SK3467	2.75	2.35	1.80
2SD1341P	2.25	1.95	1.75
2SC1172B	2.25 5 MIN.	1.95 50 MIN.	1.55 100 MIN.

AUDIO POWER

TYPE	10 min	50 min	100 min	TYPE	10 min	50 min	100 min	TYPE	10 min	50 min	100 min
152/SK3893	.30	.25	.21	196/SK3054	.49	.44	.39	291/SK3440	.49	.44	.39
153/SK3274	.30	.25	.21	197/SK3083	.59	.54	.49	292/SK3441	.49	.45	.40

RECTIFIER DIODES

125	1000V/2.5A	7C	6C	5C
156	1000V/5A	18C	16C	13C
506	DAMPER/HI-VOLT—FAST RECOVERY	29C	24C	19C

\$\$\$ ADDITIONAL SAVINGS \$\$\$

TYPE	10 min	50 min	100 min	TYPE	10 min	50 min	100 min
102A	.35	.32	.29	171	.49	.44	.38
123A	.18	.16	.14	184	.38	.33	.28
123AP	.13	.11	.09	185	.38	.33	.28
128	.38	.35	.29	198	.60	.54	.49
129	.38	.35	.29	199	.18	.15	.12
130	.59	.55	.49	234	.19	.16	.13
159	.16	.13	.11	375	.44	.42	.39
162	2.25	1.95	1.49	712	.75	.69	.60
163A	2.35	1.99	1.55				

FOR A COMPLETE LIST CALL OR WRITE—C.O.D. Orders Welcome (Min. Order \$25)

DIGITRON ELECTRONICS
110 HILLSIDE AVENUE, SPRINGFIELD, NEW JERSEY 07081
Toll Free 1-800-526-4928 In NJ 201-379-9016 Telex 138441
PRICES SUBJECT TO CHANGE WITHOUT NOTICE. OFFER GOOD WHILE SUPPLY LASTS.
ECG is a Trade Mark of Philips ECG. Digitron Ele. not associated with Philips ECG.

Circle (36) on Reply Card

NESDA Computer Group

COMPUTER SALES AND SERVICE DEALERS
WORKING TOGETHER

NESDA

- Service training.
- Assistance in selecting in-house equipment and software.
- Specialized software for service management.
- Factory contacts for service literature and parts.
- Involvement in a stable and productive national trade association.

FOR MORE INFORMATION SEND BUSINESS CARD TO:
**NESDA COMPUTER GROUP, 2708 WEST BERRY STREET
FORT WORTH, TEXAS 76109; PHONE (817) 921-9061**

Books

Editor's note: Periodically *Electronic Servicing & Technology* features books dealing with subjects of interest to our readers. Please direct inquiries and orders to the publisher at the address given, rather than to us.

Electronic Techniques: Shop Practices and Construction, third edition, by Robert S. Villanucci/Alexander W. Avtgis, William F. Megow; Prentice-Hall; 619 pages; \$32.95 hardbound.

The progression of new devices for high-density packaging of electronic systems requires that today's technicians develop more sophisticated construction and packaging techniques. This edition of two previous, familiar texts has been designed to reduce the gap between industry and the educational environment as well as to

provide a possible update for technicians already in the field. Clear, detailed explanations for laying out and fabricating electronic systems are accompanied by 500-plus visual and graphic aids. No prerequisite knowledge of electronic circuits is necessary, according to the authors, but a deeper insight of the material presented may be realized if the technician has a fundamental background in electronics.

Published by Prentice-Hall, Englewood Cliffs, NJ 07632.

The CLR200 "ProWonder" Camcorder Technical Training Manual, by RCA; RCA Technical Training; \$7.95 paperback.

Anyone expecting to service RCA's newest video product will consider this training manual a useful tool. The manual is illustrated with simplified schematics, block diagrams and circuit board photos that show component and test point locations. Explanations of how circuits and systems function are included, as well as descriptions of common trouble symptoms and their most probable

causes. The manual addresses these major topics in detail: tape transport mechanism; microcomputer system control; servo system; signal processing and color camera overview.

Published by RCA Technical Training, 1-450, P.O. Box 1976, Indianapolis, IN 46206.

Designing IC Circuits...with Experiments, by Delton T. Horn; Tab Books; 364 pages; \$16.45 paperback, \$24.95 hardbound.

The ability to design integrated circuits will significantly increase the capabilities for building advanced electronics devices that promise customized usefulness beyond the usual kit projects. The author has avoided heavy emphasis on theoretical rhetoric and complex mathematical equations, stressing, instead, practical applications of the basic concepts used in IC technology. The reader is guided into designing practical circuits, using op amps, 555 timers, voltage regulators, linear ICs, digital ICs and other commonly available IC devices.

Published by Tab Books Inc., Blue Ridge Summit, PA 17214.


ES&T

★ QUALITY PARTS ★ DISCOUNT PRICES ★ FAST SHIPPING!

SEND FOR FREE NEW 1986 CATALOG... 48 PAGES!

ALL ELECTRONICS CORP.
905 S. VERMONT • P.O. BOX 20406 • LOS ANGELES, CA 90006


10 AMP SOLID STATE RELAY
CONTROL: 3 - 32 vdc
LOAD: 140 vac 10 amp
SIZE: 2 1/2" x 3/4" x 7/8"
\$9.50 EACH 10 FOR \$90.00




13.8 VDC REGULATED POWER SUPPLY
These are solid state, fully regulated 13.8 vdc power supplies. Both feature 100% solid state construction, fuse protection and L.E.D. power indicator. U.L. listed.

2 amp constant, 4 amp surge \$18.00 each
3 amp constant, 5 amp surge \$25.00 each


RECHARGEABLE NI-CAD BATTERIES
AAA SIZE 1.25V 500mAH \$1.85
AA SIZE 1.25V 500mAH \$1.85
AA with solder tab \$2.00
C SIZE 1.2V 1200mAH \$3.50
D SIZE 1.2V 1200mAH \$3.50




STANDARD JUMBO DIFFUSED T 1-3/4
RED 10 for \$1.50
100 for \$13.00
GREEN 10 for \$2.00
100 for \$17.00
YELLOW 10 for \$2.00
100 for \$17.00




COMPUTER GRADE CAPACITORS
2,000 mfd. 200 VDC
1 1/4" DIA. x 5" HIGH \$2.00
3,600 mfd. 40 VDC
1 3/8" DIA. x 3 3/4" HIGH \$1.00
6,400 mfd. 60 VDC
1 3/8" DIA. x 4 1/4" HIGH \$2.50
9,700 mfd. 50 VDC
1 3/8" DIA. x 4 1/2" HIGH \$3.00
31,000 mfd. 15 VDC
1 3/4" DIA. x 4" HIGH \$2.50
72,000 mfd. 15 VDC
2" DIA. x 4 3/8" HIGH \$3.50
185,000 mfd. 6 VDC
2 1/2" DIA. x 4 1/2" HIGH \$1.50




EDGE CONNECTORS
ALL ARE 1.56" SPACING.
22/44 EDGE CONNECTOR
PC style \$2.00 each
22/44 EDGE CONNECTOR
solder lug style \$2.50 each
28/56 EDGE CONNECTOR
PC style \$2.50 each




FLASHER LED
5 volt operation
red jumbo T 1 3/4 size
\$1.00 each
NEW GREEN FLASHER
CAT # LED-4G \$1.00



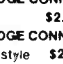
MINIATURE TOGGLE SWITCHES
S.P.D.T. (on-on) Solder lug terminals \$1.00 each
S.P.D.T. (on-off-on) Solder lug terminals \$1.00 each
10 for \$9.00 100 for \$80.00




XENON FLASH TUBE
3/4" long X 1 1/8" dia. Flash tube designed for use in compact camera flash units. Ideal for experimenters.
CAT# FLT-1 2 for \$1.00




D.P.S.T. LIGHTED ROCKER SWITCH
115 vac lighted rocker snap mounts in 3/8" x 1 1/8" hole.
Orange lens. 16 amp contact \$1.50



ULTRA-MINIATURE 5 VDC RELAY
Fujiitsu # FBR211NED005M20
High sensitivity
COIL: 120 ohms \$1.25 each
CONTACTS: 1 amp 10 for \$10.00
Mounts in 14 pin DIP socket



MINI-PUSH BUTTON
S.P.S.T. momentary normally open 3/8" bushing Red button 35¢ each 10 for \$3.00



TOLL FREE ORDERS • 1-800-826-5432
(IN CA: 1-800-258-6666)
INFO • (213) 380-8000
TWX - 5101010163 ALL ELECTRONIC


● QUANTITIES LIMITED ● MINIMUM ORDER \$10.00 ● USA \$3.00 SHIPPING NO C.O.D. ● FOREIGN ORDERS INCLUDE SUFFICIENT SHIPPING CALIF. RES. ADD 6 1/2

Durable Desoldering Tools

Sterling™ Brand from Wahl Clipper Corporation

- High quality at a low price. You pay a little and get a lot.
- Anti-static or static-free desoldering tools available. End all worries about static electricity harming your components.
- Replaceable tips last twice as long as regular teflon tips (approximately 2,000 suction).
- Easy one-hand operation. Grooved handgrip and curved thumb-holder reduce fatigue during long desoldering operations.
- Self-cleaning. Plunger clears the tip of hardened solder. You'll always get a high-vacuum suction.

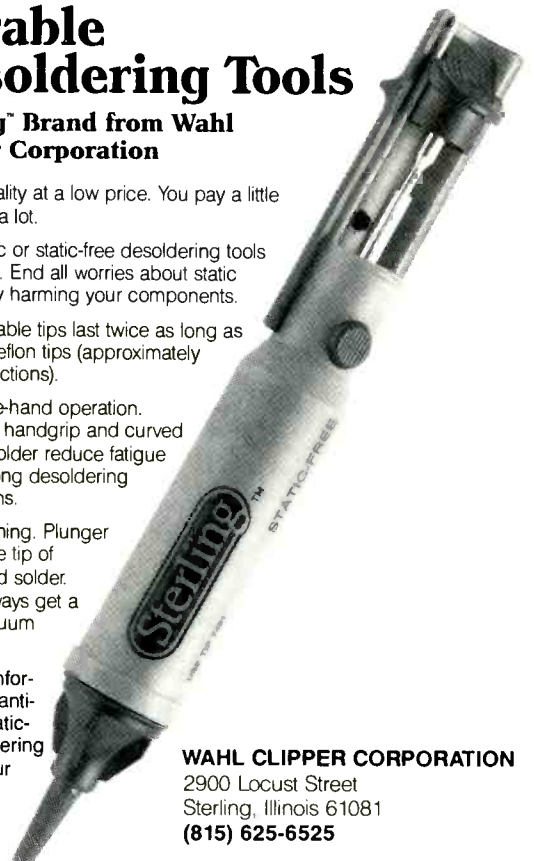For more information on anti-static or static-free desoldering tools, or our full line of soldering irons, call or write.



WAHL CLIPPER CORPORATION
2900 Locust Street
Sterling, Illinois 61081
(815) 625-6525

Sterling™ is a trademark of Wahl Clipper Corporation.

Circle (33) on Reply Card

Circle (37) on Reply Card

Readers' Exchange

Wanted: Supremes' TV-1, TV-2, TV-16 and R-1 manuals; also Knight 83YX137 AF generator, and RF generator, with manuals; 83Y135 signal tracer manual. *C.T. Huth, 229 Melmore St., Tiffin, OH 44883.*

For Sale or Trade: Telematic jig adaptors: SYA-885, 887, 888, 889, 891 and YA-35, never used, still in original package. Sell or trade for RCA 10J...series adaptors. *Dan Schafer, 4215 Buechner Ave., Cleveland, OH 44109; 216-351-4446.*

Wanted: Test adaptor socket end for small-diameter-neck CRT: 7 GR basing plug end. 12L duo-decal-basing, Pomona Electronics model 2713 or its equivalent. *Joseph A. Gontarz, JAG's Radio & TV, 14 Rudolph Road, Forestville, CT 06010; 203-583-7532.*

Needed: RCA manual for CTC chassis 72C. Please send price and ship to *Leo E. Smith, P.O. Box 945, Veteran's Home Section J, Yountville, CA 94599.*

Wanted: Manuals on B&K Precision models 650 and 1075, Sencore TC131 and CG153, RCP804A. **For Sale:** B&K model 1076, \$100, model 415, \$200; Heath IO-101 vectorscope, \$75. IG-28 color-bar generator, \$50; Tektronix model 545 oscilloscope, \$100. *Jim Corliss, 2446 Vista Drive, Upland, CA 91786; 714-985-9967.*

For Sale: Sams AR volumes - AR19, 20, 26, 28, 30, 31, 33, 35, 36, 50, 83, 96, 184, 185, 186, 190. TSM 72 - \$4 each prepaid. **Need:** 243, 262, 266, 293, 299 through 311. **Wanted:** Tube-type TV sound tuners. *Jim Farago, P.O. Box 65701, St. Paul, MN 55165.*

Wanted: Broken Telequipment D54 oscilloscope for parts; must be intact. Also need Tekfax manuals from *E.T.D.* magazine, and a Sylvania D16-05 color TV classic. *M.T. Shelton, 2708 May Drive, Burlington, NC 26215; 919-227-2908.*

Wanted: For VCR repair - tape tension and spindle gauge, VCR service manuals, Panasonic 12-inch picture tube No. A26JA531X, Diehl Mark III, IV or V. *Ed Herbert, 410 N. Third St., Minersville, PA 17954.*

For Sale: (Clarification of previous ad) Sams Photofact folders in the 600s, 700s, 800s and 900s, \$1 each, postage not included. Send s.a.s.e. for exact numbers. *David Muratore, 27 Clarkview Road, New Windsor, NY 12550.*

Needed: High school electronics program needs donations of equipment, parts, Photofacts, ham gear, etc. All donations tax deductible. Please ship to *Payson High School Electronic Dept., 1050 South Main St., Payson, UT 84651, or call Robert Strange, K7VVU, 801-465-2568, ext. 117.*

Needed: Schematic for Foxx Company sound-effects pedal, Foxx Fuzz-WA-Volume. *P. Wells, 449 S. Canyon Drive, Redmond, OR 97756.*

For Sale: B&K Precision model 415 sweep and marker generator, excellent-plus condition, \$350 plus shipping, or will trade for Sencore model TF46 transistor tester in same condition. *Paulmer L. Williams, 322 N. Court St., Lewisburg, WV 24901; 304-647-5414.*

For Sale: Service manuals, textbooks, magazines and assorted parts; 1,000 tubes, 85% off list price. Send large s.a.s.e. for list. *M. Seligsohn, 1455 55th St., Brooklyn, NY 11219.*

For Sale: Old tubes and parts, too many to list. Send s.a.s.e. to *Doc's Music Center, 72-5 Greenville St., Neunan, GA 30263.*

Needed: Horizontal output transformers No. 77x35 for General Electric 19YA chassis, new or used, in working condition. *Larry Huckeba, 6 Buchanan St., Neunan, GA 30263; 404-253-6566.*

For Sale: Sencore PR57 variable isolation transformer and safety analyzer, 1 year old, \$300; Telematic VHF-UHF tuner sub- and digital generator, \$30; Heathkit VTVM IM5228, \$40; Sams Photofact folders, miscellaneous, 1037-2254, 100 total, \$500; NRI Master Course video-audio books, \$100. *City Radio & TV, 135 S. Second, Rogers City, MI 49779; 517-734-4300, 517-734-4325.*

Needed: New or used - Panasonic ESB11500S24T control; Panasonic on/off switch, model RF-850HB; Sony green dial bulb, model 8FC-69WA radio; cartridge EO511-A1 (or similar); Delmonico SRC-6(4), 246, 642, V.C. *Williams, TV Central, 870 Pio Nono Ave., Macon, GA 31204; 912-748-1451.*


ES&T

SPRING SALE \$		\$ SPRING SALE	
Popular	Min. Spcs. P/Type	Min. Spcs. P/Type	Min. Spcs. P/Type
Flybacks & Triplers	AN-214 0.88	LA-4460 1.25	
FO-1123 11.00	AN-240 0.75	LA-4461 1.10	
FB-1108 11.00	CX-143 4.50	MB-3712 0.95	
4-2751-48500 7.50	CX-186 3.00	MB-3713 1.10	
4-2751-48600 7.50	HA-1377 1.30	TA-7205 0.57	
Z-0040 9.50	HA-1388 1.50	UPC-1181 0.45	
Z-0064 9.50	HA-1398 1.70	UPC-1182 0.45	
		UPC-1185 1.40	
Min. Spcs. P/Type	Min. Spcs. P/Type	Min. Spcs. P/Type	Min. Spcs. P/Type
STK-437 3.30	2N-3055 0.50	2SD-355 0.20	
STK-2129 4.80	2SA-634 0.29	2SD-600 0.25	
STK-3042 3.08	2SA-473 0.25	2SD-613 0.40	
STK-3082II 2.75	2SC-1172 1.55	CX-187 3.90	
STK-4141II 5.90	2SC-1384 0.20	CX-188 2.60	
STK-4362 3.00	2SC-1413 1.55	IN-4007 0.07	
STK-7216 1.40	2SC-1318 0.09	IN-4148 0.04	
STK-8250II 9.00	2SC-1675 0.08		
Matching Transformer Min. 100pcs		0.19	
2 Way Splitter Min. 20pcs.		0.39	
F Type Female Splice Min. 100pcs.		0.11	
Deluxe Desoldering Gun		1.85	
Video Cassette Rewinder		11.00	
UHF/VHF/FM Dist. Amplifier		9.50	
Car Antenna (Honda) Min. 3pcs.		1.00	
Top of Line Wire/Wireless Microphone		10.40	

* Call or write for our current flyer
 * Quantity prices available
 * C.O.D. orders welcome (Min. Order \$25.00)
 PRICE SUBJECT TO CHANGE WITHOUT NOTICE. OFFER GOOD WHILE SUPPLIES LAST.

NIPPON AMERICA, INC
 call 9600 n.w. 12 st. miami fl 33172
 toll free 800-327-7522
 305-592-2616

Circle (34) on Reply Card



Plug in!

To the NESDA system.

YOUR BUSINESS is in the world's fastest changing industry. If you're not careful, you could find your business in the dark.

But, you don't have to stay there.

Through a system of local, state, and regional groups, the **National Electronics Sales & Service Dealers Assn.** (NESDA) keeps members up-to-date with the fast pace of advancing technology while offering:

- ◆ Managerial and technical training.
- ◆ Business contacts.
- ◆ Technical and management certification.
- ◆ Information on new products.
- ◆ Legislative activities that affect the industry.

Don't be left in the dark. Let the NESDA system work **FOR YOU!**

For more information and an application, write to:
NESDA, 2708 W. Berry St., Ft. Worth, TX 76109; Ph (817) 921-9061

Name _____

Bus. Name _____

Address _____

State _____ Zip _____ Phone _____

Member of State Local Assn. _____

Tech's Guide To Pricing
 updated new 5th edition...a framework for setting rates that apply to Hi-Tech products...a formula that guarantees SUCCESS!
 Call Toll Free for details 8/5
1-800-228-4338 CST

Circle (42) on Reply Card

DANDY-DAPTER™
 PATENTED CRT ADAPTER—Don't buy another socket for your CRT Tester! This is the **Only** way you can win the Socket War! Guaranteed to fit your tester & allow you to test/clean/restore ANY Color, B/W, Projection, Scope or Camera CRTs. Visa/M-Card, Checks, CODs. New Low Price \$59.95 (We pay UPS) 1(800) 331-9658. DANDY ELECTRONICS, 2323 GIBSON, MUSKOGEE, OK 74403.




Circle (39) on Reply Card

**NATIONAL REBUILT HEADQ. FOR—
 SONY REBUILT
 PICTURE TUBES**
 2 YR. WARR. — FREE U.P.S.-DEL.
 716-621-5250

Circle (40) on Reply Card

ELECTRONIC SERVICING & TECHNOLOGY Volume 6, No. 4, (USPS 462-050) is published monthly by Intertec Publishing Corp., 9221 Quivira Road, P.O. Box 12901, Overland Park, KS 66212. Second Class Postage paid at Shawnee Mission, KS, and additional mailing offices. POSTMASTER: Send address changes to ELECTRONIC SERVICING & TECHNOLOGY, P.O. Box 12952, Overland Park, KS 66212-9981.

Classified



Advertising rates in the Classified Section are 75 cents per word, each insertion, and must be accompanied by payment to insure publications.

Each initial or abbreviation counts a full word.

Minimum classified charge is \$15.00.

For ads on which replies are sent to us for forwarding (blind ads), there is an additional charge of \$25.00 per insertion to cover department number, processing of replies, and mailing costs.

Classified columns are not open to advertising of any products regularly produced by manufacturers unless used and no longer owned by the manufacturer or distributor.

FOR SALE

AUTOMOBILE RADIO and tape replacement parts. Delco, Chrysler, Philco-Ford, Motorola, Panasonic and many others. Large inventory. Laran Electronics, Inc., 3768 Boston Road, Bronx, NY 10469. (212) 881-9600. National (800) 223-8314, NY State (800) 446-4430.
1-85-tfn

BOOTLEGGERS BIBLE for CB Modification \$12.95, CB Radio Repair \$10.95. Linear Amplifier Planbook \$14.95, kits, etc. Catalog \$1.00 refundable — APS, POB 263 Newport, R.I. 02840 401-846-5627.
12-84-tfn

SCRAMBLED TELEVISION, encoding/decoding. New book. Theory/circuits, \$9.95 plus \$1 shipping. Workshop, Box 393ES, Dept. E, Bethpage, NY 11714.
1-85-tfn

TV TROUBLE ANALYSIS TIPS. Over 300 symptoms/remedies by circuit area; tough ones over the years. Save time and money. Send \$12.50 to CHAN TV, 8151 Grandview Rd., Chanhassen, MN 55317.
1-85-tfn

CABLE CONVERTERS. Lowest price. Dealer inquiries accepted. Quantity Discounts. FREE CATALOG. P.G. Video Corp, 61 Gatchell St., Dept. ES&T, Buffalo, NY 14212.
5-85-tfn

CABLE TV CONVERTERS & EQUIPMENT. Plans and parts. Build or buy. Send S.A.S.E. C&D Electronics, P.O. Box 1402, Dept. ES&T, Hope, Arkansas 71801.
1-86-tfn

CONVERT ANY SCOPE into a spectrum analyzer/receiver. Send stamp, self-addressed envelope for details. Workshop, Box 393ES, Bethpage, N.Y. 11714
03-86-3t

HEWLETT PACKART (608D) 10-420MHz signal generator \$650. 707-545-0285.
4-86-1t

INDIVIDUAL PHOTOFAC FOLDERS (not sets) #1 to #1400, \$3.00 first-class postpaid. Loeb, 414 Chestnut Lane, East Meadow, NY 11554.
4-86-3t

REPAIR OF ZENITH CIRCUIT BOARD 9-160-ALL; with dud exchange \$33.00. One year guarantee. Kinirral Electronics, 68-26 64th Place, Glendale, N.Y. 11385. (718) 366-3859.
4-86-3t

VCR VIDEO HEAD TEST. Use standard shop equipment to thoroughly check VCR video heads and associated circuitry. For complete details send \$5.00 to: APG ELECTRONIC SERVICE, Box 7, Whitehall, NY 12887.
4-86-1t

TUBES: \$2.49, many discontinued types, SASE brings lists. Old Photofacts, to #1000, \$4.00. Binders, \$3.50. EDNF, 6690 7 Mile, S. Lyon, MI 48178.
4-86-1t

MAKE ANY TELEVISION OUTPUT STEREO SOUND!!

Increase your profit margins by selling and installing this unique device.



Model SS-2001: The TELEVONIC™ implant unit, installed directly into any Television, creates synthesized stereo output from any channel. When connected with a stereo amplifier or receiver, it will provide a sound system found only in expensive stereo Televisions, at a fraction of the cost.

Works on any TV • Easy to install • 100% Solid State • Microchip technology • Superior Sound quality • 1 year warranty.

REQUIRES QUALIFIED TECHNICAL INSTALLATION.

DISTRIBUTOR INQUIRIES WELCOMED.

For Information Contact: Mr. Ernest C. Hassell • Director of Marketing
 • Spectrum 2000, Inc. • 4854 Sterling Drive • Boulder, CO 80301
 • (303) 444-2828 (Call Collect)

TELEVONIC is a trademark of Spectrum 2000, Inc.
 Manufactured in the U.S.A. by Spectrum 2000, Inc.

Circle (35) on Reply Card

BUSINESS OPPORTUNITIES

3 HOURS FROM SAN FRANCISCO! Town of paradise in pine forested foothills. Electronic repair business. Building/shop/equipment/7 room residence with large garden. \$165K, (916) 872-1962.
12-85-tfn

FT. LAUDERDALE. Diversified electronic business located in busy shopping center. Old established with steady clientele. Reasonably priced for quick sale. \$85,000. Call 305-776-4941.
4-86-2t

ELECTRONICS REPAIR SHOP. TV, stereo, VCR, microwave repair. Established 10 years in Wichita. \$20,000. Will trade. Eugene Faber, 2527 W. Pawnee, Wichita, KS 67213.
4-86-2t

3 HRS FROM SAN FRANCISCO in pine forested foothills, electronic repair business. Poor health forces sale. Bldg./shop/equipmt. & 7 rm. residence w/lg. garden, was \$165K, now \$155K. (915) 872-1962.
4-86-1t

TV SALES & SERVICE RCA-Equipment, parts, truck & customer records. \$40,000/yr. net potential, asking \$20,000. Owner retiring after 30 years serving Tampa Bay Area. Showroom, work shop & house \$140,000. Call Jim Wolfston, CENTURY 21 G.M. GROUP, INC. 813-535-4646.
04-86-1t

HELP WANTED

CAMERA-VIDEO Technicians needed. Top pay and benefits for well trained and experienced technicians who are expert with consumer and/or industrial cameras and VCR's. Training by manufacturers such as Sony, Hitachi, Panasonic, etc., are necessary for job experience. Come to sunny Florida and enjoy your work & leisure time. Write or call ATLANTIC ELECTRONICS INC., 1881 NE 26 St., Ft. Lauderdale, FL 33305. (305) 564-8274 10 AM to 6:30 PM. Ask for Dave or Joe.
8-85-tfn

HELP WANTED (CONT.)

TELEVISION TECHNICIAN NEEDED. Must be experienced with American & Japanese televisions. Excellent benefit package and incentive plan. Send resume to P.O. Box 894, Union, N.J. 07083. 4-86-2t

EDUC.-INSTRUCTION

UNIVERSITY DEGREES: Economical home study for Bachelor's, Master's, Doctorate. Prestigious faculty counsels for independent study and life experience credits. Free information—Richard Crews, M.D. (Harvard), President, Columbia Pacific University, 1415 Third St., Dept. 2B84, San Rafael, CA 94901; Toll Free: 800/227-0119; California: 800/552-5222; or 415/459-1650. 4-86-1t

ELECTRONIC TECHNICIANS AVAILABLE: The Willmar Area Vocational-Technical Institute will graduate Electronic Service Technicians in June, 1986. Graduates have received training in consumer electronic equipment, such as VCR's, satellite television, and television receivers. In addition, the graduates have received the PACE training program on soldering and PC board repair. Their training involves hands-on experience of analyzing and troubleshooting, and repairing microcomputers, disk drives, printers, and video monitors. Training covers operation of recent model personal computers, microprocessors, digital electronics, data communications systems, and BASIC programming. For further information, contact Fred Hanson, Placement Coordinator, Willmar AVTI, P.O. Box 1097, Willmar, MN 56201, telephone (612) 235-5114, extension 118. 4-86-2t

**Use ES&T
classified ads**

**SAVE
TIME**

*For fast, accurate service,
please remove the peel off label
used to address your magazine,
and attach it to the Reader
Service Card, the Address
Change Card or to any
correspondence you send us
regarding your subscription.*

Advertisers' Index

	Page Number	Reader Service Number	Advertiser Hotline
Adatron Electronics	IBC	3	800/222-8782
All Electronics Corp.	73	37	800/826-5432
B&K Precision Dynascan Corp.	68	31	312/889-9087
Beckman Industrial Corp.	59,64	24,28	714/671-4800
Chemtronics, Inc.	1,43-44	4	800/645-5244
Cleveland Institute of Electronics	17	13	800/321-2155
Cleveland Institute of Electronics	16A,16B		800/321-2155
Contact East	29,30		800/225-5370
Cooper Group	7	7	919/362-7510
Dandy Mfg. Co.	75	39	800/331-9658
Diehl Engineering	21,23,15	15	806/359-0329
Digitron Electronic	72	36	800/526-4928
E-Z Hook	45,46		818/445-6175
ETA	71		
Fluke, John Mfg. Co., Inc.	5	6	800/227-3800
Fordham Radio Supply Co.	56	23	800/645-9518
Hitachi-Denshi America, Inc.	10,11	8,9,10,11	516/921-7200
Jensen Tools Inc.	33,34		602/968-6231
Leader Instrument Co.	IFC,33,34	1,2	516/231-6900
Matsushita Engineering & Service Co.	3	5	201/392-4281
MCM Electronics	69	32	800/543-4330
NAP Consumer Electronic Corp.	31,32		615/639-1121,
NESDA	72,74		817/921-9061
Nippon American Inc.	74	34	800/327-7522
NRI Schools-Electronics Division	29,30		202/244-1600
NTE Electronics, Inc.	31,32		800/631-1250
NTE Electronics, Inc.	19	14	800/631-1250
Omnitron Electronics	67	30	800/223-0826
Pace, Inc.	43,44		301/490-9860
Philips ECG	45,46		800/225-8326
Precision Picture Tubes	75	40	716/621-5250
Prentice-Hall Inc.	31,32,33,34		
Projector Recorder Belt Corp.	65	29	800/558-9572
PTS Corp.	61	26	812/824-9331
RCA Distributor and Special Products	27,51	16	
RCA Distributor and Special Products	43,44		
Howard W. Sams & Co., Inc.	60	25	800/428-SAMS
Sencore, Inc.	54,55	21,22	800/843-3338
Sencore, Inc.	52,53	19,20	800/843-3338
Simpson Electric Co.	15	12	312/697-2265
Spectrum 2000 Inc.	75	35	303/444-2828
Sperry AW Instruments Inc.	63	27	800/645-5398
Sperry Tech, Inc.	75	41	800/228-4338
Tab Books	45,46		800/233-1128
Tentel	29,30		800/538-6894
Test Probes, Inc.	71	38	800/368-5719
Viz Test Equipment	49	17	800/523-3696
Wahl Clipper Corp.	73	33	815/625-6525
Zenith	BAC		

ARTICLE REPRINTS

Interested in ordering custom reprints of an article from this issue?*

Reprints of articles about your company or products can be valuable sales and marketing tools. For information, call or write Kelly Hawthorne, Intertec Publishing Corp., P.O. Box 12901, Overland Park, Kansas 66212; (913) 888-4664.

*minimum order 1,000 copies

**LOWEST POSSIBLE PRICES
FROM THE ELECTRONIC
INDUSTRY'S LARGEST
WHOLESALE SUPPLIER!**

**ABATRON
ELECTRONICS**



CALL TODAY FOR SAME DAY SHIPPING ON ORDERS, LARGE OR SMALL, AND YOUR FREE CATALOG.

1-800-222-8782 in N.J. 201-687-4215

Second Edition

64A

Circle (3) on Reply Card

Go for 'em! Solid margins year-around! They're yours in the video aftermarket! With this new VCR Care Kit by Zenith!

You bet there's a VCR aftermarket out there! A sizeable one. Perhaps as big as *twenty million plus* households. So that capitalizing on it with VCR accessories like this beautifully packaged Zenith VCR Care Kit can be very, very profitable.

Look and see for yourself!

Inside this kit, latest in a long line of Zenith video accessories – and available separately, too – are a great new VCR Head Cleaner. A T-120 VHS Blank Video Tape. A VCR Dust Cover. And a clear VHS Tape Storage Cover. All proudly bearing and backed by Zenith, a name renowned for superb product performance and reliability.

They are at your Zenith distributor's place now, these new Universal VCR Care Kits, ready for immediate delivery to heads-up service techs alert to the money to be made in the overall video aftermarket.

Actually, there's more in store than ever before in this expanding line of Zenith video accessories. More than just this new Universal VHS VCR Care Kit. Solid margins, for example. The kind that can turn some 6, 7 or 8 feet of your floor space into a video accessory profit center right before your eyes.

So hurry! Quit second-guessing yourself! Neither this video accessory business nor VCR aftermarket is going to wait for you. Call your Zenith distributor's Parts & Accessories Sales Manager!

Besides being an integral part of Zenith's new VCR Care Kit, this VCR Head Cleaner is also available separately as Model T-HC from your Zenith distributor.



ZENITH
UNIVERSAL VCR CARE KIT

- Use top quality Zenith blank video tape to help prevent excess build up of oxides on your VCR heads and damage to capstan and pinch rollers.
 - Cover your VCR machine when not in use to prevent dust which can damage the internal components of your VCR.
 - Clean your VCR head with a Zenith VCR Head Cleaner once a month.
 - Cleaning may be required more frequently when rental tapes are used.
 - Keep VCR cassettes in dust proof cassette case; never leave cassette unprotected.
- By following these preventive maintenance tips, you can extend the interval between professional cleanings.

ZENITH
UNIVERSAL VCR CARE KIT

Universal VHS VCR Care Kit
Contents:
1 ea. VCAe144-C
Clear VHS Tape Storage Cover
1 ea. B45-501
Dust Cover
(17" x 14" x 4")
1 ea. T-120
Zenith VHS Blank
Video Tape
1 ea. T-HC
Zenith Video
Head Cleaner
Kit Number
845-511

Zenith VCR care products are designed to enhance your viewing pleasure. See back panel for additional VCR accessories.



Zenith Service, Parts & Accessories
11000 Seymour Avenue, Franklin Park, Illinois 60131
A Division of Zenith Electronics Corporation