


RADIO — ELECTRONICS

MARCH 1953

LATEST IN TELEVISION • SERVICING • AUDIO

HUGO GERNSBACH, Editor

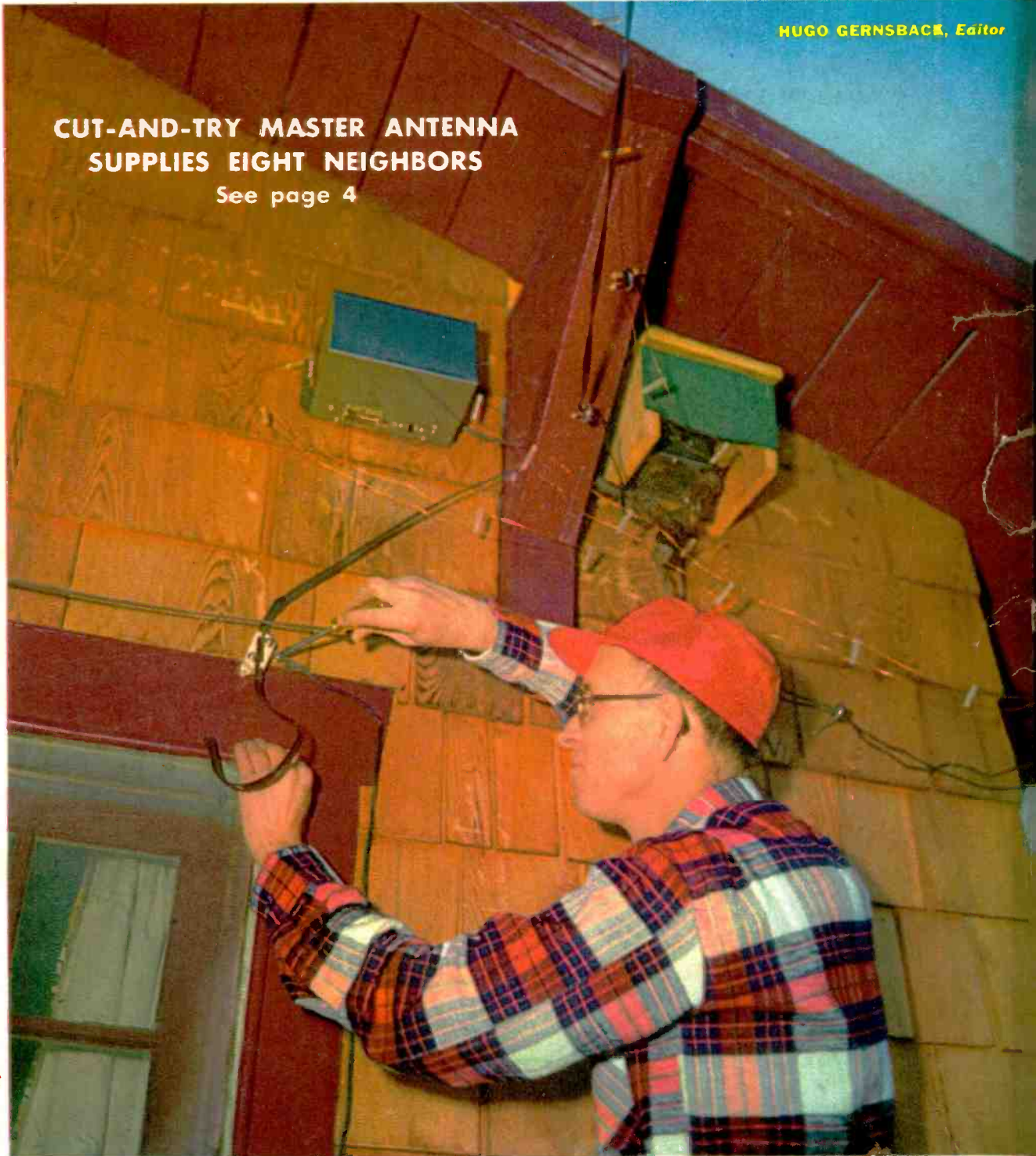CUT-AND-TRY MASTER ANTENNA
SUPPLIES EIGHT NEIGHBORS
See page 4



30¢

U. S. and
CANADA

**In this issue: High-Speed Remote Mike Control •
Video Amplifier Design • A Transistor Receiver**



for that **NEW-SET** performance
INSIST ON GENUINE

DUMONT
*Original Television Parts and Teletrons**

Use the components designed, specified and insisted upon by Du Mont receiver engineers. They account for that universally acknowledged Du Mont quality. Now these same Du Mont Original Television Parts and Teletron picture tubes are made available through selected distributors for top-quality TV servicing.

Replacement Sales Cathode-Ray Tube Division
ALLEN B. DUMONT LABORATORIES, INC.
Clifton, New Jersey

*Trade Mark

NEW



I'LL TRAIN YOU FOR YOUR FCC LICENSE

A Federal Communications Commission Commercial Operator's License puts you in line for a good job in Radio or Television Broadcasting, Police, Marine, Aviation, Two-way, Mobile or Micro-wave Relay Radio. Mail coupon below for 64-page book FREE. It will give you complete facts about my NEW Communications course.



YOU BUILD THIS TRANSMITTER

with parts I send. With this Transmitter you practice how to put a station "on the air." You perform procedures demanded of Broadcast Station Operators, conduct many experiments, make many practical tests.

LEARN COMMUNICATIONS by PRACTICING at Home in Spare Time

Get Practical Experience on Circuits Common to Radio & TV

Ever think HOW FAST Radio-Television Communications is changing, developing, growing? Have you considered what this amazing progress can mean to you? Even without Television the industry is bigger than ever before. 105 million home and auto radios, 2900 Radio Broadcasting Stations, 108 TV Stations with 1800 more now authorized. Expanding use of Aviation and Police Radio, Micro-Wave Relay, Two-Way Radio for buses, taxis, etc. makes opportunities for Communications Technicians and FCC Licensed Operators. New jobs, more jobs for beginners! Better jobs, better pay for experienced men!

Television Is Today's Good Job Maker

In 1952, over 18,000,000 homes had TV sets. More are being sold every day. The "Freeze" on building new TV stations has been lifted. The time to act is NOW! Start learning Radio-TV communications. America's fast growing industry offers good pay, a bright future, security. If you are a beginner, my course can help you get FCC License, prepare for the job you

J. E. SMITH, President National Radio Institute Washington, D. C.

For 38 years, the leader in training men for Radio-Television.



MY COURSE INCLUDES TELEVISION


want. If you've had some training in Radio or Radar, or as a Licensed Operator, my course modernizes, increases the value of your knowledge.

Includes New Developments

Mail coupon now for facts about my practical course in Radio-Television Communications. Let me send you my FREE book. See the nine big Kits of Parts I send that "bring to life" theory you learn. You get practical experience by working on circuits common to both Radio and Television; also lessons on TV principles. Read about the Transmitter you build and operate, about the Electronic Multitester you get. All equipment is yours to keep. My graduates are filling jobs, making good money in both Radio and Television. Remember, the way to a successful career in Television is through experience in Radio.



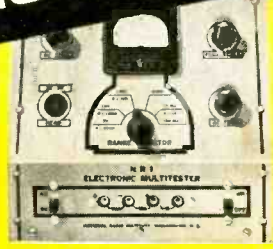YOU BUILD this Transmitter Power Supply used in the basic experiments in RF and AF amplifiers, frequency multipliers, buffers, etc.



YOU MEASURE current, voltage (AC, DC and RF), resistance and impedance in circuits with Electronic Multitester you build. Shows how basic transmitter circuits behave; needed to maintain station operation.



YOU PRACTICE setting up code, amplitude and frequency modulation circuits (put voice, music, etc., on "carrier signals" you produce). You learn how to get best performance.



YOU BUILD this Wavemeter and use it to determine frequency of operation, make other tests on transmitter currents.

Training Leads to Jobs Like These

- | | | |
|---|--|---|
| BROADCASTING
Chief Technician
Chief Operator
Power Monitor
Recording Operator
Remote Control Operator | GOVERNMENT RADIO
Operator in Army,
Navy, Marine Corps,
Coast Guard
Forestry Service
Dispatcher | AVIATION RADIO
Plane Radio Operator
Airport Transmitter Operator |
| SHIP AND HARBOR RADIO
Chief Operator
Assistant Operator
Radiotelephone Operator | AIRWAYS RADIO
Operator
Voice Transmitter Operator
TV Technician
Remote Control Operator | |





Servicing Training Also Offered by N. R. I.

If you prefer a good-pay job in Radio-Television Servicing or your own money-making Radio-Television Sales and Service Shop, I'll train you at home. My famous Servicing Course also includes many Kits of Radio Parts. You use them to get PRACTICAL EXPERIENCE with circuits common to Radio and Television. I also show you how to make \$5, \$10 a week or more EXTRA MONEY fixing neighbors' Radios while training. Full information in my 64-page book. Mail coupon.

Mail Coupon for Book FREE

Send today! See what my Communications course is like. Find out how I get you ready for a brighter future, better earnings, more security in Radio-Television. Send coupon now in envelope or paste on postal. NO OBLIGATION, NO SALESMAN WILL CALL! My book, sent to you FREE, tells the full story. J. E. SMITH, President, Dept. 3CF, National Radio Institute, Washington 9, D. C. Our 39th year.

I TRAINED THESE MEN


 "My position with WNBZ is video color engineer on the RCA color project. I owe a lot of my success to your textbooks."—Warren Deem, Malverne, N. Y.	 "I am a technician at WTOP in Washington and I like it very much. Most of my radio knowledge was from N.R.I."—John Britto, Hyattsville, Md.
 "My first job was with KDLL, obtained for me by your Graduate Dept. Now in charge of Radio Equipment for Police Dept."—T. S. Norton, Hamilton, O.	 "A former employer recommended N.R.I. training. Now employed as transmitter operator at WKBO."—Albert Herr, New Cumberland, Pa.

MAIL NOW-BOOK FREE

MR. J. E. SMITH, President, Dept. 3CF National Radio Institute, Washington 9, D. C.

Mail me your 64-page Book about Radio and Television Communications opportunities and training. (No salesman will call. Please write plainly.)

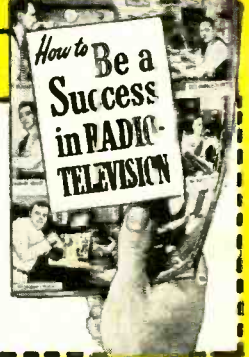Name.....Age.....
Address.....
City.....Zone.....State.....
Approved Under G. I. Bill



RADIO - ELECTRONICS

Formerly RADIO-CRAFT • Incorporating SHORT WAVE CRAFT • TELEVISION NEWS • RADIO & TELEVISION*

Hugo Gernsback
Editor and Publisher

M. Harvey Gernsback
Editorial Director

Fred Shunaman
Managing Editor

Robert F. Scott
W2PWG, Technical Editor

Mortimer Bernstein
Associate Editor

I. Queen
Editorial Associate

Matthew Mandl
Television Consultant

Angie Pascale
Production Manager

Wm. Lyon McLaughlin
Tech. Illustration Director

Sol Ehrlich
Art Director

Lee Robinson
General Manager

John J. Lamson
Sales Manager

G. Aliquo
Circulation Manager

Robert Fallath
Promotion Manager



Member
Magazine Publishers
Association

ON THE COVER
(Story on page 44)
Installing a distribution amplifier on the Mount Baldy system's transmission line.

Color original by John Gartner

CONTENTS

MARCH, 1953

"WHAT IS ELECTRONICS?"

Due to the large number of definitions received, it has not been possible to complete judging the entries in the "What Is Electronics?" contest. Prizes will be paid immediately the judging is finished, and the winners will be announced in the April issue.

Editorial (Page 33)			
Radio Astronomy	by Hugo Gernsback		33
Audio (Pages 34-43)			
Rapid Remote Microphone Control	by N. H. Crowhurst		34
Voltage Regulators for High-Fidelity Amplifiers	by Joseph Marshall		36
Push-Pull Drivers, Part IV	by George Fletcher Cooper		38
Volume Expanders and Compressors	by Robert F. Scott		41
Television (Pages 44-53)			
TV Comes Over the Mountain (Cover Story)	by Douglas W. Stephens		44
Design Data on Video Amplifiers, Part I	by Alan G. Sorensen		46
Television? ... It's a Cinch!	by E. Aisberg		48
Antenna Reference Chart			51
Television Service Clinic	Conducted by Matthew Mandl		52
Electronics (Pages 54-56)			
U.H.F. Treatments to Improve Wines	by M. Lafargue		54
Servicing—Test Instruments (Pages 57-62)			
Communiclip	by Milton Lowens		57
Canvassing Builds Business	By Jim Kirk		58
Subminiature Tube Tester Design	by Richard J. Sandretto		60
R.F. Circuit Tester	by I. Queen		62
FM (Pages 63-66)			
FM Broadcasting in Western Germany	by Prof. Werner M. Nestel		63
Theory and Engineering (Pages 78-97)			
Test Techniques for Transistors	by Rufus P. Turner		78
Detector-Amplifier with Germanium Diodes	by Irving Gottlieb		86
Artificial Delay Lines	by R. C. Payne		92
Construction (Pages 99-100)			
Transistor Receiver Operates Loudspeaker	by W. H. Grace, Jr.		99
Departments			
The Radio Month	14	Radio-Electronic	
Radio Business ..	20	Circuits	117
With the		Try This One ...	123
Technician ...	102	Question Box ...	126
New Devices ...	109	Technotes	131
New Patents ...	112	People	133
		Miscellany	136
		Communications	138
		Electronic	
		Literature ...	139
		Book Reviews ..	142



MEMBER Audit Bureau of Circulations

Vol. XXIV, No. 3


EXECUTIVE, EDITORIAL and ADVERTISING OFFICES: 25 West Broadway, New York 7, N. Y. Telephone REctor 2-8630. Gernsback Publications, Inc. Hugo Gernsback, President; M. Harvey Gernsback, Vice-President; G. Aliquo, Secretary.

SUBSCRIPTIONS: Address correspondence to Radio-Electronics, Subscription Dept., Erie Avenue, F to G Sts., Philadelphia 32, Pa., or 25 West Broadway, New York 7, N. Y. When ordering a change please furnish an address stencil impression from a recent wrapper. Allow one month for change of address.

SUBSCRIPTION RATES: In U. S. and Canada, in U. S. possessions, Mexico, South and Central American countries, \$3.50 for one year; \$6.00 for two years; \$8.00 for three years; single copies 30c. All other foreign countries \$4.50 a year, \$8.00 for two years; \$11.00 for three years.

BRANCH ADVERTISING OFFICES: Chicago: 100 E. Ohio St., Tel. Superior 7-1796. Los Angeles: Ralph W. Harker, 1127 Wilshire Blvd., Tel. MADison 6-1271. San Francisco: Ralph W. Harker, 582 Market St., Tel. GARfield 1-2481. **FOREIGN AGENTS: Great Britain:** Atlas Publishing and Distributing Co., Ltd., London E.C.4. **Australia:** McGill's Agency, Melbourne. **France:** Brentano's, Paris 2e. **Belgium:** Agente et Messageries de la Presse, Brussels. **Holland:** Trilectron, Heemstede. **Greece:** International Book & News Agency, Athens. **So. Africa:** Central News Agency, Ltd., Johannesburg. **Cape Town:** Durban, Natal. **Universal Book Agency, Johannesburg. Middle East:** Steimatzky Middle East Agency, Jerusalem. **India:** Broadway News Centre, Dadar, Bombay #14. **Pakistan:** Paradise Book Stall, Karachi 3. *Trademark registered U.S. Patent Office.

RADIO-ELECTRONICS

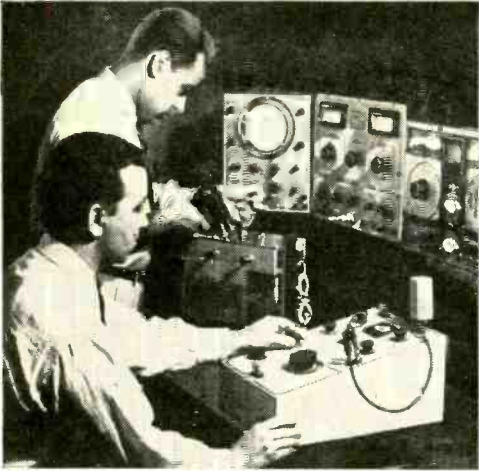

EARN MORE MONEY AS AN EXPERT

Get Shop-Method Training at Home in **RADIO TELEVISION ELECTRONICS**

One Master Course - One Low Tuition
LEARN ALL PHASES - EARN WHILE YOU LEARN

AS A NATIONAL SCHOOLS GRADUATE THERE'S A PLACE FOR YOU IN THIS EXPANDING INDUSTRY...Never before such a demand for *you!* For *never before* such a *growing* industry as today's Television, Radio and other Electronic fields. This industry needs *you*... **TODAY**... and it needs you as a *trained* man... the kind of man you will be as a National Schools graduate. So don't wait. Start your National Schools training **NOW**...and enjoy big money, job security, **SUCCESS!**

LEARN from EXPERTS! BE A SUCCESSFUL MAN YOURSELF! You learn from men who are themselves successful Radio, Television and Electronics technicians. You learn the *practical* way... by *doing*... with equipment we send you. And you advance *quickly, step by step*. Get **ALL** the facts from **FREE** book and sample lesson. Mail coupon below **NOW**. Absolutely no obligation.

You can qualify FAST for these big-pay jobs...plus many more

Radio Station Technician • Your own Sales and Service Shop • District Service Manager • Inspector Technician • Aircraft Radio Inspector • Special Govt. Positions • Service Specialist • Sound Truck Operator • and many others!

ONLY NATIONAL SCHOOLS GIVES YOU THIS PROFESSIONAL MULTI-TESTER



Ready to use. Easy to operate. Light enough to carry on service calls.

DRAFT AGE? National Schools training helps you get into special service classifications—get higher grades, better pay!



FREE!

Radio-TV Book & Sample Lesson **JUST MAIL COUPON!**

NATIONAL SCHOOLS GRADUATES IN BIG DEMAND. You'll find National Schools graduates in good jobs everywhere. For these are the jobs National Schools *trains* you for. Such complete, shop-method home training can be *your* ticket to success...your key to the job happiness you've always wanted. It's up to you. Mail coupon **NOW!**

FRIENDLY GUIDANCE AS STUDENT AND GRADUATE. Our special Welfare Department is constantly at your service. Helps you with your technical and personal problems. Gives you the benefit of its wide industry contacts and experience in helping you after graduation. Both resident and home study courses offered.



All yours at no extra cost!

GET YOUR TRAINING FROM THE RADIO-TV CAPITAL OF THE WORLD

Let National Schools —a resident technical trade school for nearly 50 years—train you at home for today's unlimited opportunities in Radio-TV.



NATIONAL SCHOOLS APPROVED FOR G. I. TRAINING

Los Angeles, Calif. • Est. 1905 • In Canada: 193 Hastings St., Vancouver, B.C.

YOU GET ALL THE PARTS INCLUDING TUBES for this superheterodyne receiver... and lots of other equipment...to keep!

NATIONAL SCHOOLS, Dept. RG-33
4000 South Figueroa Street
Los Angeles 37, California

Mail in envelope or paste on postal card

Send me **FREE** book "My Future in Radio-Television and Electronics." Also a **FREE** sample lesson. I understand no salesman will call on me and that there is no obligation.

NAME _____ AGE _____

ADDRESS _____

CITY _____ ZONE _____ STATE _____

VETS! Check here if you are a veteran.

ACT NOW

Don't put it off! Mail coupon NOW!

This name spells Quality and Profits



UNBEATABLE quality is built into every Sylvania product. Even beyond that, Sylvania quality goes back to its essential metals, chemicals, and materials.

Sylvania quality is fundamental


Sylvania grinds and formulates its own phosphors, and applies them by improved methods which assure maximum uniformity and fine picture-tube performance. Sylvania draws its own high-quality tungsten filaments and winds and tests its own coils.

Naturally, this far-reaching quality control results in an enviable nation-wide reputation. Today 7 of the top 10 television set makers use Sylvania Picture Tubes and Receiving Tubes. Naturally, too, Sylvania quality pays off in fewer call-backs, more satisfied customers . . . and *more profits for you.*

You'll find your friendly Sylvania Distributor a mighty high quality man to do business with, too. Call him today!



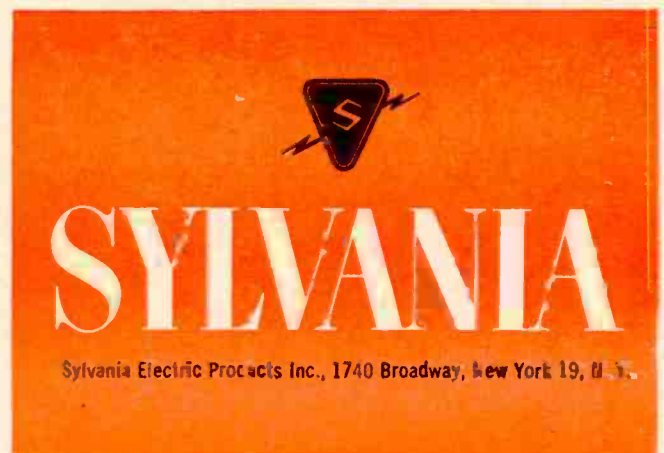Be sure to install Sylvania Picture Tubes and Receiving Tubes in all the sets you service. Your customers know about Sylvania's fine quality and they'll appreciate your selection of Sylvania products for their sets.



RADIO TUBES; TELEVISION PICTURE TUBES; ELECTRONIC PRODUCTS; ELECTRONIC TEST EQUIPMENT; FLUORESCENT LAMPS, FIXTURES, SIGN TUBING, WIRING DEVICES; LIGHT BULBS; PHOTCLAMPS; TELEVISION SETS

RADIO-ELECTRONICS

NOW! DTI's GREATEST TRAINING OFFER IN 22 YEARS!

IT'S NEW! IT'S PRACTICAL! IT'S DIFFERENT!

DTI's NEW 1953 HOME TRAINING PROGRAM

has been re-designed to
**GET YOU FURTHER
FASTER**


in



21 INCH

NOW . . . as a part of our training, you build and keep this outstanding 21-inch—steady — sharp image — D.T.I. quality-engineered TV set. Can be readily converted to receive U.H.F.

TELEVISION RADIO AND ELECTRONICS

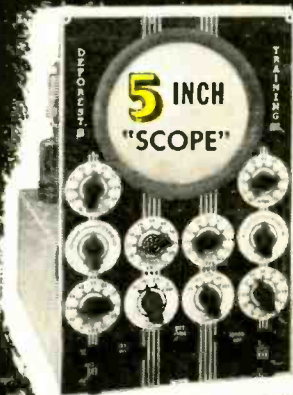


5 INCH "SCOPE"

NEW 5-INCH "SCOPE"

D.T.I. now also makes it possible for you to build and keep this big 5-inch commercial-type oscilloscope, one of the most useful and versatile pieces of testing equipment used in television today. In fact, it's almost a "must" for the serious-minded TV technician.

IMPROVED HOME MOVIES

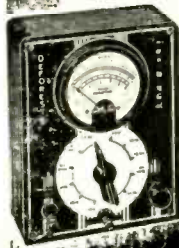D.T.I.'s new 1953 Master Home Training Program provides you with the use of 16 Hollywood-produced reels of film and a 16 mm. motion picture projector to speed your progress.



MULTIMETER



HOME MOVIES

MILITARY SERVICE!

If you're subject to military service, the information we have for you should prove very helpful.

ONE OF AMERICA'S FOREMOST
TRAINING CENTERS

— Established —

1931



Here, we believe, is one of the most **PRACTICAL** . . . most **HELPFUL** . . . most **EFFECTIVE** home training programs ever offered to prepare you to earn real money in America's amazing multi-billion dollar opportunity field of **TELEVISION-RADIO-ELECTRONICS**. Now, at home, you can get real practical experience from working on high quality, **FULL SIZE Commercial type equipment**—much like you'll handle when later working in the TV field. Here's the **REAL THING**—nothing else like it!

You get interest-packed lessons. You get 21 shipments of parts—working over 400 construction and test procedures that include building and keeping D.T.I.'s big, new, 5-INCH Oscilloscope and a jewel bearing Multimeter—followed by building D.T.I.'s wonderful new 21-inch tube TV set. You get shop method training—right at home. And to help you understand all-important fundamentals **FASTER** . . . **EASIER** . . . you use D.T.I.'s unique and effective **HOME MOVIES**. Then upon completing your training, D.T.I.'s Employment Service helps you **GET STARTED** in a good job or your own sales and service business. Get the facts—including the thrilling story of the opportunities ahead in Television.

OTHER TRAINING PROGRAMS AVAILABLE

D.T.I. also offers home training in (a) Television-Radio-Electronics—but without the TV set, (b) full time training in D.T.I.'s big **CHICAGO TRAINING LABORATORIES**—one of the nation's finest. Mail coupon today.

**89 WAYS
TO
EARN
MONEY
IN TELEVISION
RADIO ELECTRONICS**

Get this publication FREE!

DeFOREST'S TRAINING, INC. Dept. RE-3-J
2533 N. ASHLAND AVE., CHICAGO 14, ILL.

I would like your Opportunity News Bulletin showing "89 Ways to Earn Money in Television-Radio-Electronics"; also, complete facts about the training opportunity made possible by your organization.

Name _____ Age _____

Address _____ Apt. _____

City _____ Zone _____ State _____

DeFOREST'S TRAINING, INC.

AFFILIATED WITH

DeVRY Technical INSTITUTE

CHICAGO 14, ILLINOIS

ASTRON

SAFETY MARGIN




CAPACITORS

Cut Callbacks!

When you install ASTRON Capacitors, you're insuring against call-backs, building your reputation for *reliable* service.

Through the use of an improved electrolyte, and an exceptionally high-purity anode foil—plus rigid quality control and exhaustive multiple testing techniques—ASTRON electrolytic SAFETY-MARGIN capacitors mean longer life and maximum performance under every condition. Unexpected surges of voltage, undue heat or moisture—conditions that might spell failure in an ordinary capacitor—rarely affect an ASTRON.

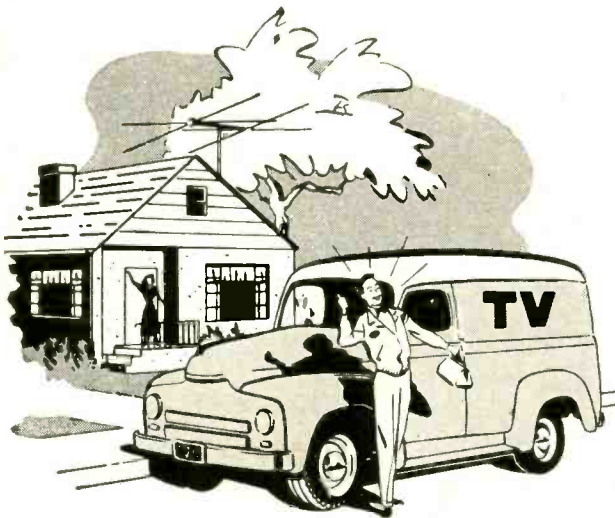So next time ask for ASTRON—the capacitor with the "safety margin" that protects your service reputation. And ask for Astron Type AM molded paper tubular capacitors to complete your service job. *Individually tested—individually guaranteed.*



Depend On—Insist On



Write for Catalog AC-3 and
Name of Jobber Nearest You


Visit Astron at the IRE Show, Booth 4-707,
Grand Central Palace

ASTRON

CORPORATION

255 Grant Avenue, E. Newark, N. J.

RADIO-ELECTRONICS

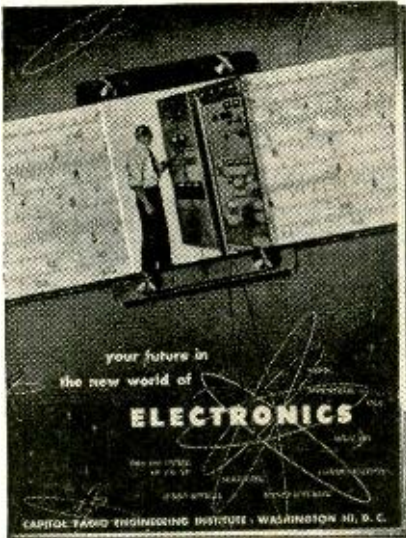

← The data that Launched Thousands of Careers is yours FREE . . .

to show

HOW YOU CAN BE SUCCESSFUL IN RADIO-TV-ELECTRONICS

YOU CAN plod along for years, getting a paltry increase now and then, enjoying little security, finding your work dull and drab.

Then something happens. Things look up. You become more confident. Your earnings rise. You feel more important.

"Luck," some may say.

"Contacts," others may suggest.

But in your heart, you will know the answer: "Training." And it all may have started the moment you filled out a coupon requesting a copy of a free booklet named "Your Future in the New World of Electronics." From this data you get knowledge of where you stand in Electronics. Tremendous expansion leaves this gigantic industry pleading for trained men. In the defense build-up alone, more than \$7 billion in electronics contracts have been awarded. Top manufacturers sold about \$3 billion worth of electronic merchandise in 1951. By 1960, the radio-electronics industry should do no less than 10 billion dollars per year, not counting military orders.

Today there are over 50,000 radio-equipped police cars; an even larger number of taxis are radio equipped (at least 65,000); 28,000 civilian planes have radio; 27,000 American ships have radio; there are 9,200 industrial radio network installations.

Today there are over 100,000,000 radios in use. There are over 20,000,000 TV sets and 121 TV stations in operation. 175 new stations have received the FCC's go-ahead signal. 823 more TV station applications are awaiting FCC action. Countless positions must be filled—in development, research, design, production, testing and inspection, manufacture, broadcasting, telecasting and servicing. To fill these posts, trained men are needed—men who somewhere along the line take time to improve their knowledge, their skills—men who today perhaps take two minutes to send for a booklet.

"Your Future in the New World of Electronics" shows you how CREI Home Study leads the way to greater earnings through the inviting opportunities described above.

However, CREI does not promise you a "snap." With an accredited technical school such as this, you must *study* to convert your ambition into technical knowledge you can sell in the fabulous Electronics market.

CREI resident instruction (day or night) is offered in Washington, D. C. New classes start twice a month.

VETERANS: If you were discharged after June 27, 1950—let the new G.I. Bill of Rights help you obtain resident instruction. Check the coupon for full information.

Since its founding in 1927, CREI has provided thousands of professional radio men with technical educations. During World War II CREI trained thousands for the Armed Services. Leading firms choose CREI courses for group training in electronics at company expense, among them United Air Lines, Canadian Broadcasting Corporation, Trans Canada Airlines, Sears, Roebuck and Co., Bendix Products Division, All-American Cables and Radio, Inc., and RCA Victor Division.

CREI courses are prepared by recognized experts, in a practical, easily understood manner. You get the benefit of time-tested materials, under the personal supervision of a CREI Staff Instructor, who *knows* and *teaches* you what industry wants. This is accomplished on your own time, during hours selected by you, and controlled by your own will power. This complete training is the reason that graduates find their CREI diplomas keys-to-success in Radio, TV and Electronics. CREI alumni hold top positions in America's leading firms. At your service is the CREI Placement Bureau, which

finds positions for advanced students and graduates. Although CREI does not guarantee jobs, requests for personnel far exceed current supply.

Now is the time of decision for you. Luck will not propel you forward unless it finds you trained. Contacts won't budge you an inch unless you have the skill to back them up. The answer is: Technical Training . . . and willingness to learn. Together they will bring you increased earnings in this new Age of Electronics. Fill out the coupon and mail it now. We'll promptly send you your free copy of "Your Future in the New World of Electronics." The rest—your future—is up to you.

MAIL COUPON FOR FREE BOOKLET

CAPITOL RADIO ENGINEERING INSTITUTE

Dept. 143 3224 16th St., N.W., Washington 10, D. C.

Send booklet "Your Future in the New World of Electronics" and course outline.

CHECK TV, FM & Advanced AM Servicing Aeronautical Radio Engineering
 FIELD OF Practical Television Engineering
 GREATEST Broadcast Radio Engineering (AM, FM, TV)
 INTEREST Practical Radio Engineering

Name.....

Street.....

City..... Zone..... State.....

Check Residence School Veterans


ENGINEERED FOR BRILLIANT PERFORMANCE



REVOLUTIONARY
VEE-D-X
Q-TEE


BY ANY STANDARD OF COMPARISON

The Finest All-Channel Antenna

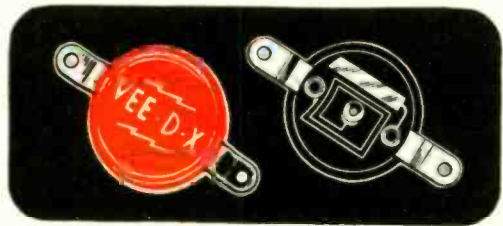

Secret of the Q-Tee all-channel operation is the patented printed circuit electronic channel separator in this colorful red plastic housing. Lic. A.A. K. Pat. 2,422,458; 2,282,292; 2,611,086, others pending.

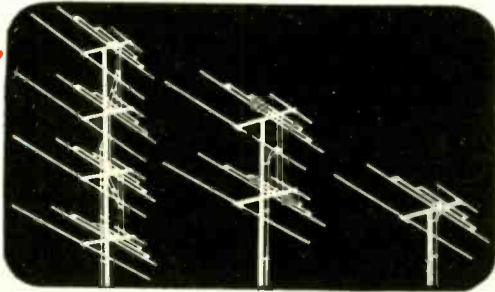Easy stacking makes the Q-Tee a pleasure to install especially when in combination with new UHF antennas. Three series: Q-Tee single bay for primary areas; Q-Tee double (two-bay) for near-fringe areas; Q-Tee quad (four-bay) for fringe areas.



There is only one Q-Tee! It's powerful — it's revolutionary — it's patented — it's made only by Vee-D-X. Embodying an entirely new engineering approach to all-channel reception, the Q-Tee has met with sensational success. Its brilliant performance, ease of installation, ease of stacking and clean-cut appearance have won for it the reputation of "Antenna of the Year". Ideal for all multi-channel areas (primary, near-fringe and fringe), the Q-Tee provides the high front-to-back ratio found in no other broadband antenna. In areas of co-channel interference this often means the difference between a good picture and none at all. The Q-Tee is an excellent basic VHF antenna for use in combination with UHF antennas.

THE LaPOINTE-PLASCOMOLD CORPORATION
 ROCKVILLE, CONNECTICUT

Send full information on Q-Tee

NAME

STREET

CITY ZONE..... STATE.....

RADIO-ELECTRONICS



Where Will You Be
in **ELECTRONICS**
6 Months from Today?

ADD TECHNICAL TRAINING to your practical experience
Get Your FCC License In A Hurry!

Then Use Our Amazingly Effective
JOB FINDING SERVICE

Get This Valuable Booklet **FREE**



TV ENGINEERING INCLUDED IN OUR TRAINING & COACHING

TELLS HOW—

HERE IS YOUR GUARANTEE

If you fail to pass your Commercial License exam after completing our course, we guarantee to continue your training without additional cost of any kind, until you successfully obtain your Commercial license, provided you first sit for this examination within 90 days after completing our course.

WE GUARANTEE

TO TRAIN AND COACH YOU AT HOME IN SPARE TIME UNTIL

YOU GET **YOUR FCC LICENSE**

If you have had any practical experience—Amateur, Army, Navy, Radio repair, or experimenting.

TELLS HOW—

Our Amazingly Effective **JOB-FINDING SERVICE**

Helps CIRE Students Get Better Jobs

Here are a few recent examples of Job-Finding results:

GETS JOB WITH CAA

"I have had a half dozen or so offers since I mailed some fifty of the two hundred employment applications your school forwarded me. I accepted a position with the Civil Aeronautics Administration as a Maintenance Technician. Thank you very much for the fine cooperation and help your organization has given me in finding a job in the radio field."
Dale E. Young, 122 Robbins St., Owosso, Mich.

GETS FIVE JOB-OFFERS FROM BROADCAST STATIONS

"Your 'Chief Engineer's Bulletin' is a grand way of obtaining employment for your graduates who have obtained their 1st class license. Since my name has been on the list I have received calls or letters from five stations in the southern states, and am now employed as Transmitter Engineer at WMMT."
Elmer Powell, Box 274, Sparta, Tenn.

GETS CIVIL SERVICE JOB

"I have obtained a position at Wright-Patterson Air Force Base, Dayton, Ohio, as Junior Electronic Equipment Repairman. The Employment Application you prepared for me had a lot to do with me landing this desirable position."
Charles E. Loomis, 4516 Genesee Ave., Dayton, Ohio.

Your FCC Ticket is recognized in all radio fields as proof of your technical ability.

TELLS HOW— Employers make **JOB OFFERS** Like These to Our Graduates Every Month

Letter from Chief Engineer, Broadcast Station, North Carolina, "Need men with radiotelephone 1st class license, no experience necessary. Will learn more than at average station for we are equipped with Diesel Electric power, transmitting and studio equipment."

Telegram from Chief Engineer, Broadcast Station, Wyoming, "Please send latest list available first class operators. Have November 10th opening for two combo men."

These are just a few examples of the job offers that come to our office periodically. Some licensed radioman filled each of these jobs . . . it might have been you!

HERE'S PROOF FCC LICENSES ARE OFTEN SECURED IN A FEW HOURS OF STUDY WITH OUR COACHING AT HOME in Spare Time.

Name and Address	License	Lessons
Lee Worthy 2210 1/2 Wilshire St., Bakersfield, Calif.	2nd Phone	16
Clifford E. Vogt, Box 1016, Dania, Fla.	1st Phone	20
Francis X. Foerch, 38 Baucier Pl., Bergenfield, N. J.	1st Phone	38
S/Sgt. Ben H. Davis, 317 North Roosevelt, Lebanon, Ill.	1st Phone	28
Albert Schoell, 110 West 11th St., Escondido, Calif.	2nd Phone	23

CLEVELAND INSTITUTE OF RADIO ELECTRONICS
CARL E. SMITH, E.E., Consulting Engineer, President
Desk RE-50, 4900 Euclid Bldg., Cleveland 3, Ohio

MARCH, 1953

OURS IS THE ONLY HOME STUDY COURSE WHICH SUPPLIES FCC-TYPE EXAMINATIONS WITH ALL LESSONS AND FINAL TESTS.



GET ALL 3 FREE!
MAIL COUPON NOW

CLEVELAND INSTITUTE OF RADIO ELECTRONICS
Desk RE-50—4900 Euclid Bldg., Cleveland 3, Ohio
(Address to Desk No. to avoid delay)

I want to know how I can get my FCC ticket in a minimum of time. Send me your FREE booklet, "How to Pass FCC License Examinations" (does not cover exams for Amateur License), as well as a sample FCC-type exam and the amazing new booklet, "Money-Making FCC License Information."


Be sure to tell me about your television engineering course.



Name.....
Address.....
City..... Zone..... State.....

Paste on 2-cent postcard or send air mail.

No fuss No cuss

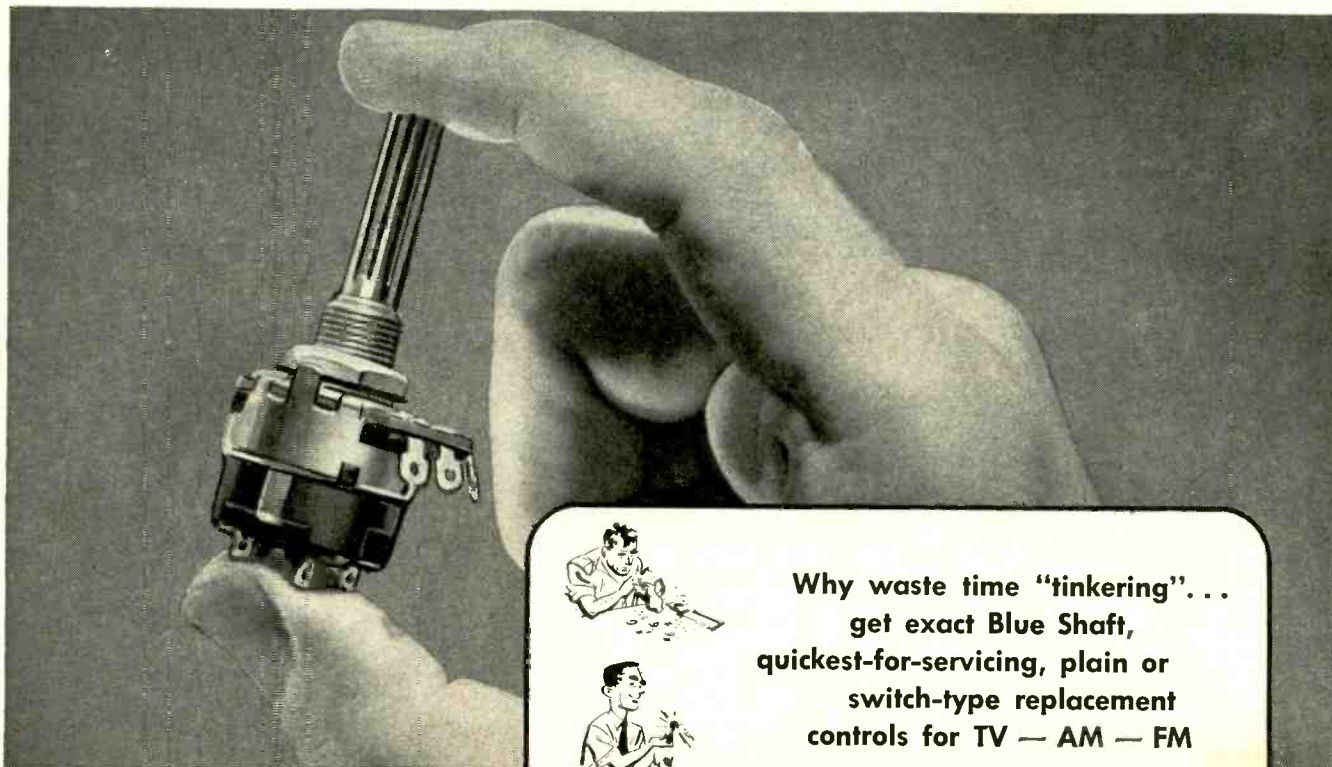When you use Centralab Blue Shaft Controls



 Why waste time "tinkering"...
 get exact Blue Shaft,
 quickest-for-servicing, plain or
 switch-type replacement
 controls for TV — AM — FM


**Don't fuss with an assembly job
 the factory does better, faster,
 and guarantees-at no extra cost.**

Yes, Blue Shaft Controls are your smartest service buy! Why? Because these *exact*, quickest-for-servicing replacements not only save you valuable bench-working time, but they're guaranteed *right* every time!

Why it pays to standardize on Blue Shaft

Centralab's famous Blue Shafts, plain or switch-type, are exclusive service items. The factory-attached and tested, high-amperage universal switches are *exact* for SPST — DPST or 3-wire. Blue Shafts are available in a range from 500 ohms to 10 megs in a wide variety of tapers and tapped units. All Centralab Blue Shaft Controls are packaged singly, or in handy kit assortments in plastic boxes of 12. You can

also get a special metal cabinet containing 22 controls. NO EXTRA CHARGE for the cabinet.

Flexible "Fastatch,"† type KB, converts any plain type control with blue and white label on back cover to switch type . . . in seconds.



SERVICE ENGINEERS — here's more good news
 — 26 new Blue Shafts added in '53 line!

Centralab

A Division of Globe-Union Inc.
 Milwaukee 1, Wisconsin
 In Canada, 635 Queen Street East, Toronto, Ontario

Blue Shafts give you exactness plus LOW COST

Cat. No.	Ohms Max. Resistance	Taper	Circuit Location	List Price
B-60	500,000	C-2 (audio)	Volume or Tone	\$1.00
B-60-S*	500,000	C-2 (audio)	Volume or Tone	\$1.50
B-70	1 megohm	C-2 (audio)	Volume or Tone	\$1.00
B-70-S*	1 megohm	C-2 (audio)	Volume or Tone	\$1.50

*Switch Type †Trademark

CENTRALAB, A Division of Globe-Union Inc.
 922 East Keefe Avenue, Milwaukee 1, Wisconsin

Ask your jobber or write direct for Cat. 28.

Name.....Position.....

Company.....

Address.....

City.....State.....

RADIO-ELECTRONICS

**ELIMINATE
CORROSION OF
ANTENNAS**

**HELP PREVENT
CORONA WITH**

KRYLON®

100% ACRYLIC



**JUST PRESS
THE
BUTTON**

Krylon is a tough, quick-drying Acrylic coating that has become a "must" in TV service. Because of its high dielectric strength it helps prevent corona. Spray it on high voltage coil and insulation, the socket of the high voltage rectifier and component parts of the rectifier circuit.

Krylon is nationally advertised.

USE THE KRYLON FAMILY



CLEAR rustproofs, waterproofs, insulates. Goes on clear and stays clear.



ALUMINUM is non-conductive. Protects and insulates.



WHITE is popular for touching up chipped white goods. Will not discolor.



BLACK is newest Krylon product. Use for touch-up, stenciling and marking.

**TECHNICAL
CHARACTERISTICS**

Dielectric constant—2.8 to 3.4 (1,000 cycles)
Dielectric strength—400 to 800 (number of volts necessary to cause electric arc through Krylon coat one mil thick)
Electrical resistance— 10^{10} ohms/cm²

In U.S.A. and CANADA
SEE YOUR JOBBER
Or Write Direct
Department 3103

KRYLON, Inc.

2601 N. Broad St., Philadelphia 32, Pa.



"AUDREY"—Bell Laboratories' Automatic Digit Recognizer—selects the right circuits automatically when numbers are spoken distinctly into the telephone.

BELL LABS' "AUDREY" (automatic digit recognizer) translates spoken numbers directly into selective switching operations. Audrey now responds dependably only to clearly enunciated syllables, but may some day do away entirely with dials and even operators—you may literally "call" a number merely by speaking into your telephone.

The recognizer compares speech sounds with electrical equivalents of standard phonetic patterns stored in memory cells. The appropriate circuit—an indicator lamp at present—is energized when the waveform of the spoken numeral matches one of the stored standards.

A TRANSISTOR TRANSMITTER on the 146-mc amateur band, operated by George M. Rose of K2AH, Mountain Lakes, N. J., worked three stations—the farthest over 25 miles away—with power supplied only by a tiny 22½-volt hearing-aid battery. According to Mr. Rose, who manages the advanced development group at RCA's transistor laboratory, the entire transmitter, including the quartz frequency-control crystal, takes up no more space than a pack of cigarettes. Transmissions were reported strong and clear, even at W2UK in New Brunswick, N. J., more than 25 miles from Mountain Lakes.

THE ARMSTRONG MEDAL for outstanding achievement in radio was awarded to a Briton, Capt. Henry J. Round, by the Radio Club of America at its 43rd Annual Banquet in December. Captain Round, one of the few surviving pioneers who aided Marconi in his early work, developed radio direction-finding equipment which enabled the British to intercept the German fleet in World War I, and bring on the Battle of Jutland. Captain Round

is well known to radio old-timers throughout the world as an operator at the first commercial radio station in the United States, at Babylon, N. Y., from 1905 to 1907.

A YEAR-END SURVEY OF TV production released by Admiral Corporation points out that nearly 20% of all TV and radio receivers made in the United States are produced in the Chicago area. Philadelphia, New York City and Syracuse follow in that order as electronic manufacturing centers.

TV's biggest year was 1950, when nearly 7,500,000 receivers were sold, with a value of \$2,000,000,000.

Of the 19,000,000 TV receivers in use in the United States at the end of 1952, 9,000,000 were over 4 years old, and had screens smaller than 16 inches. The survey estimates the replacement market alone will hit 5,000,000 sets a year when television reaches all sections of the country (See P. 26 for NBC estimates).

COMMITTEES to study television-interference problems were recently named by the RTMA. Acting on the FCC's request that the industry take steps to standardize receiver i.f.'s and reduce oscillator radiations, Dr. W. R. G. Baker, director of the RTMA Engineering Department, appointed the groups to work with the Joint Technical Advisory Committee and the Institute of Radio Engineers.

One task committee, headed by J. A. Chittick of RCA, will tackle receiver problems. A second group, under J. E. Keister of G-E, will work on transmitter interference. The third committee, headed by Donald G. Fink of Philco, will co-ordinate the work of the first two, and act as liaison with the JTAC, I.R.E. and FCC.

Mr. Ray Snyder
General Manager
Educ. Book
Division

You Get
This Valuable Book

FREE

Just for Examining
COYNE'S NEW 6-VOLUME SET

"Applied Practical Radio-Television" ON 7 DAYS FREE TRIAL!



Now! The most liberal "get-acquainted offer you've ever seen! Think of it—Coyne gives you this big, brand new book, "150 Radio-Television Picture Patterns and Diagrams Explained", ABSOLUTELY FREE. This up-to-the-minute, practical book gives you complete wiring circuits and diagrams on the leading Radio and Television Sets. Also many trouble-shooting picture patterns. Large 8½ x 11" pages. Full instructions show you how to read and use the diagrams. This valuable book is a FREE GIFT to you, for just asking to see the great new Coyne 6-book set, "Applied Practical Radio-Television"!

OVER 2500 FACT-PACKED PAGES OF TV SERVICING "KNOW-HOW"!

You get all the right answers to today's TELEVISION-RADIO servicing problems—and get them quickly—in Coyne's great new 6-volume set. Right at your finger-tips is the TV-Radio knowledge that makes you worth more money! Over 5,000 practical facts and data are fully covered in easy-to-understand fashion in volumes 1 through 5. Every step is completely explained—from principles of radio and television to installing, servicing, trouble-shooting and aligning including full facts on COLOR TV and UHF, adapters and converters. Also includes very latest information on TRANSISTORS. Hundreds of photos, illustrations, charts and diagrams help you understand quicker. For speedy on-the-job use, I'll also include the famous 762 page Coyne TELEVISION SERVICING CYCLOPEDIA—covering today's television problems in easy-to-find a alphabetical order. Use this complete 6 volume TV-RADIO LIBRARY FREE for 7 days. Get the valuable Picture Pattern-Diagram Book ABSOLUTELY FREE!

ACT NOW—SEND NO MONEY!

Just mail the coupon for Coyne's 6-volume set on 7 days free trial. I'll include the book of 150 TV-RADIO Patterns & Diagrams. If you keep the set, pay \$3 in 7 days and \$3 per month until \$22.50 plus postage is paid. (Cash price, \$20.95.) Or you can return the library at our expense in 7 days and owe nothing. Either way, the book of TV-Radio Patterns is yours to keep FREE! Take advantage of this offer AT ONCE!

A WORLD OF PRACTICAL RADIO AND TELEVISION FACTS AT YOUR FINGER TIPS!

- Vol. 1. APPLICATION OF TELEVISION-RADIO PRINCIPLES:** 300 pages, covers resonance & tuning, amplifiers, oscillators, etc.
- Vol. 2. RADIO, TELEVISION & FM RECEIVERS:** 403 pages, covers rectifiers, high frequency, short wave, FM, antennas, etc.
- Vol. 3. RADIO-TELEVISION CIRCUITS:** 336 pages, covers power tubes, de-coupling, distortion, photo-tubes, phase inverters, etc.
- Vol. 4. LATEST INSTRUMENTS FOR SERVICING RADIO-TELEVISION:** 343 pages, covers all types of testing instruments, their use in service work.
- Vol. 5. TELEVISION SERVICING & TROUBLE-SHOOTING MANUAL:** 400 pages, practical servicing of all types of TV sets, UHF, boosters, color TV printed in 4 colors, etc.

★ PLUS TV CYCLOPEDIA!

A "must" for the TV serviceman. Quick answers to all TV problems in A-B-C order, cross-indexed. 762 pages, fully illustrated; covers hundreds of facts on servicing, installation, alignment, UHF, transistors much more.

MAIL COUPON TODAY

FREE BOOK—FREE TRIAL COUPON!

Mr. Ray Snyder, Technical Book Manager
COYNE ELECTRICAL & TELEVISION-RADIO SCHOOL
500 S. Paulina St., Dept. 33-T1, Chicago 12, Ill.

O.K., Mr. Snyder! I'll take advantage of your Get-Acquainted Offer! Send new, 6-book set, "Applied Practical Radio-Television" for 7 days FREE TRIAL per your offer. Include TV-RADIO Patterns & Diagrams Book FREE!

Name _____ Age _____

Address _____

City _____ State _____

Where Employed _____ Zone _____

Check here if you want library sent C.O.D. You pay postman \$20.95 plus C.O.D. postage on delivery. 7-day Money Back Guarantee.

COYNE

ELECTRICAL & TELEVISION — RADIO SCHOOL
500 South Paulina Street
Dept. 33-T1, Chicago 12, Illinois

take the
kick
out of
TV



Burton Browne advertising



**CORONA FREE HVO-X7
FLYBACK TRANSFORMER**

Merit's famous HV07 is now treated to a miracle-tough, new non-hygroscopic insulation. Liquid-molded, this latest development in insulating materials encloses the high voltage winding, is impervious to moisture and high humidity and forms a watertight seal for the high voltage lead. Unaffected physically or electrically by cycles of heat and cold, it will withstand operating temperatures 50% above normal without change. Its high dielectric constant affords maximum protection with minimum distributive capacity.

MERIT COIL AND TRANSFORMER CORP.
4425 NORTH CLARK ST., CHICAGO 40



Above—Hearing aid models of the past 15 years, terminating in the new Maico transistor type. The model at rear is using a still older type. Right—The new Sonotone transistor hearing aid.

TRANSISTOR-EQUIPPED hearing aids have been offered to the public for the first time. Weight and operational costs are greatly reduced. Their small size may be seen from the photographs of the Maico aid, which uses three transistors, and the Sonotone model, which uses a transistor to replace the power tube and retains two voltage amplifier tubes.


NEW GERMANIUM SOURCE—the richest found thus far—has been discovered in a Kentucky coal deposit by prospectors seeking new supplies of the urgently needed substance. Worth \$350 a pound in pure metallic form, the germanium is little more than a trace in the coal and must go through an elaborate process of extraction and refining before it is suitable for use in transistors, diodes, and power rectifiers. Despite the new find, the tremendous increase in the demand for the valuable metal will probably bar any immediate decrease in cost.

THE 1953 I.R.E. SHOW and convention will be held at Grand Central Palace, New York City, on March 23, 24, 25, and 26. In anticipation of an even larger attendance than the 28,000 who visited last year's I.R.E. show, the layout has been improved and simplified to enable visitors to circulate more comfortably among the exhibits. **RADIO-ELECTRONICS** extends a cordial invitation to visit its exhibit on the second floor—Booth 2-141—directly opposite the elevators on the 46th Street side of the building.

Technical sessions in connection with the show will take place at the Waldorf-Astoria.

TV SETS OUTNUMBER PHONES in many leading U. S. cities. Baltimore, Boston, Cleveland, Los Angeles, Philadelphia, and St. Louis already have given TV a comfortable lead, while in New York, Chicago, Detroit, and Washington the two vital services are running just about even. Opening of u.h.f. channels and new assignments in the v.h.f. band are expected to pull TV far out in front in cities that have had at least one channel for five years or more.

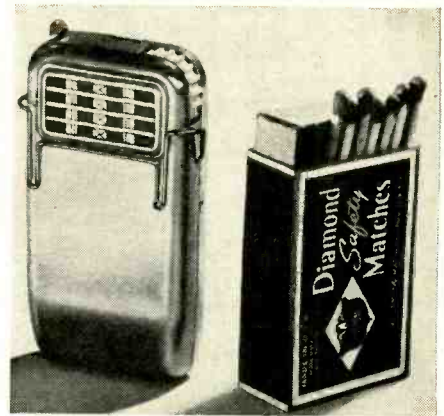THE SERIAL-NUMBER RACKET, which has victimized thousands of pur-



chasers of radios, television sets, and other appliances over many years, is being fought vigorously by Better Business Bureaus through proposed legislation already submitted in New York, Nebraska, and other states. Unscrupulous dealers remove or deface manufacturers' serial numbers on equipment to evade warranty obligations, transfer merchandise irregularly to non-franchised, cut-price channels, or conceal stolen merchandise. The bill introduced in New York calls for a fine of \$50 for the first offense, with penalties up to \$1,000 for subsequent convictions. Nebraska's proposed legislation goes even farther, carrying cash penalties of \$50 to \$5,000, and prison terms of 6 months to 5 years.

EUROPEAN TV has been further expanded with the opening of a television station by the Northwest German Radio Network, which has been in operation since the beginning of the year.

The station is so located as to cover about 60% of northwest Germany, and reaches West Berlin. The audience is still limited—official estimates state that about 5,000 sets are in use in West Germany. Many are leased rather than sold outright, as the prices (ranging from \$300 to \$600 in American money) are from three to six times the average worker's monthly salary.

Broadcasts are reported to consist of 2-hour daily programs. No commercials are carried.

There is a monthly television tax of five marks (\$1.25 approximately) on each set. The Northwest German Radio Network and the Post Office radio administration share the proceeds.

EDUCATIONAL TV has been given the support of no less an authority than Dr. W. R. G. Baker, vice-president of the General Electric Company and one of the country's television pioneers.

"To my mind it is not a question of whether we can afford television," Dr. Baker said in a statement to the New York State Temporary Commission on the Use of Television for Educational Purposes, which is holding hearings to determine whether New York State should embark on a program of educational television. "Instead, I believe we cannot afford, if we have the least concern for our country's future and for the future of our children, to pass up the opportunity offered us." **END**

THE ONLY COMPLETE CATALOG FOR
EVERYTHING IN TV, RADIO AND
INDUSTRIAL ELECTRONICS

get your 1953 **FREE**

ALLIED


236-PAGE CATALOG

it's complete
it's value-packed

THE WORLD'S LARGEST STOCKS

- TV and Radio Parts
- Test Instruments
- Hi-Fi and P.A. Equipment
- Custom TV Chassis
- AM, FM Tuners & Radios
- Recorders and Supplies
- Amateur Station Gear
- Builders Supplies
- Equipment for Industry


**QUICK
EXPERT
SERVICE**

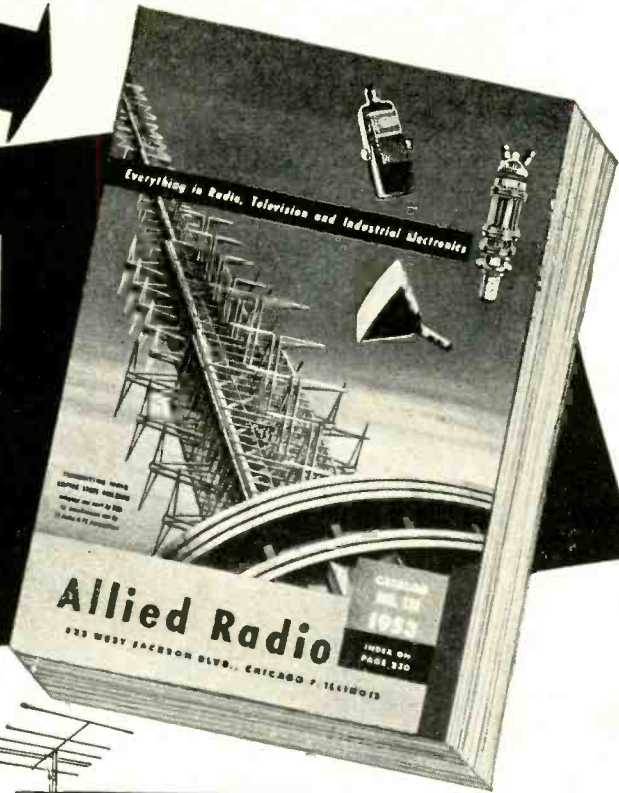

Send for it today!

Here's the *one* authoritative, complete Buying Guide to *Everything in Electronics*—packed with the world's largest selections of quality equipment at lowest money-saving prices. See the latest in TV custom chassis, TV antennas and accessories; AM and FM tuners and radios; High-Fidelity Custom Sound components; latest P.A. Systems and accessories; recorders; Amateur receivers, transmitters and station gear; specialized industrial electronic equipment; test instruments; builders' kits; huge listings of parts, tubes, tools, books—your choice of the world's *most complete stocks* of quality equipment.

ALLIED gives you every buying advantage; speedy delivery, expert personal help, lowest prices, liberal time payment terms, assured satisfaction. Get the latest 1953 ALLIED Catalog. Keep it handy—and save time and money. Send for your **FREE** copy today!

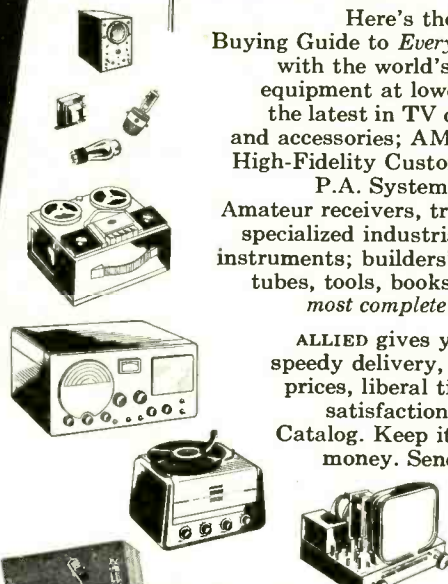

**EVERYTHING IN
ELECTRONICS**

**SEND TODAY FOR RADIO'S
LEADING BUYING GUIDE**

free

ALLIED RADIO

World's Largest Electronic Supply House

EASY-PAY TERMS

Take advantage of ALLIED's liberal Easy Payment Plan—Radio's best terms—only 10% down, 12 months to pay—no interest if you pay in 60 days. Available on Hi-Fi and P. A. units, recorders, TV chassis, test instruments, Amateur gear, etc.

TV & HI-FI SPECIALISTS

To keep up with developments in TV and High-Fidelity, look to ALLIED! Count on us for *all* the latest releases and largest stocks of equipment in these important fields. If it's *anything* in Television or High-Fidelity equipment—we have it in stock!

ALLIED RADIO CORP., Dept. 2-C-3
833 W. Jackson Blvd., Chicago 7, Illinois

Send **FREE** 236-Page 1953 ALLIED Catalog.

Name

Address

City Zone State

INCREASED SERVICE BUSINESS 123%!



Miami TV-radio
service dealer
L. T. Sample
proves that
promotion
pays off!

"Because of our summer promotion, June service sales were 194 per cent of May; July sales 223 per cent. August service will equal or exceed July. Newspaper ads, mailing cards, television spots, radio announcements—we used them all successfully."

LAURENCE T. SAMPLE
Electronic Television of Florida, Inc.
1003 S. W. 27th Avenue, Miami, Fla.

Follow L. T. Sample's lead . . . use G-E promotion aids
to get more service business!

BEGINNING the first day you use them, these 1953 promotion helps work hard to bring you more service business—bigger profits! See your General Electric tube distributor for your copy of G. E.'s new catalog! Or write direct to *General Electric Company, Tube Department, Schenectady 5, New York.*

You can put your confidence in—

GENERAL  ELECTRIC

161-1A1



RADIO-ELECTRONICS



Now you can do it!

. . . with the sure-fire promotion aids described in General Electric's brand-new catalog for 1953—

- Identification aids, such as decals, clock, signs, and tube display cartons.
- Advertising aids, such as mailing pieces, newspaper ad mats, doorhangers, and streamers.
- Business aids, such as job tickets, calling cards, letterheads, and tube-test stickers.
- Service aids, such as tube puller, jumper cord, drop cloth, and shop garments.
- Technical manuals and publications.




NEW! FREE!

CARTRIDGE DISPENSER

PLUS


THESE E-V SALES AIDS

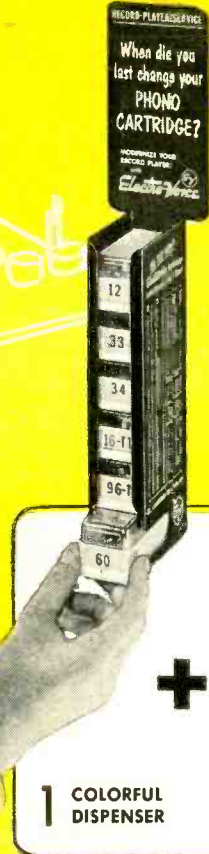

1 COLORFUL DISPENSER

2 UNIQUE DECAL

3 SET MODEL REPLACEMENT GUIDE

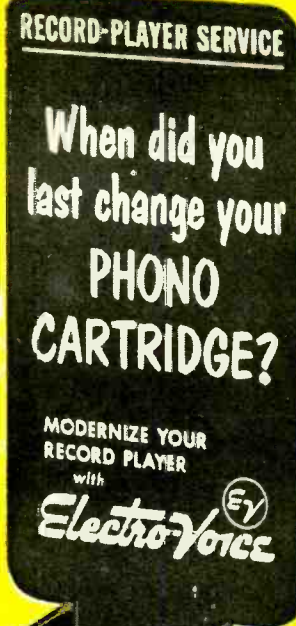

USE this handsome, all-metal dispenser in your store or shop. It catches the eye and makes your customers want to buy!

This modern merchandiser is the *new way*, the *positive way* to cash in on the \$70,000,000.00 phono-cartridge modernization-replacement market.

Not only does it sell cartridges, but the handy Cartridge Interchangeability Chart on each side makes your replacement service quick and easy.

In addition, the unique colorful, transparent Decal and the complete Manufacturers Set Model Replacement Guide make *you* the authority on Phono Service in your community.


All three are Free, without extra cost, from your E-V Distributor with every purchase of any 6 E-V Phono Cartridges. (The 6 basic Preferred E-V Models shown here, of course, enable you to make over 92% of all replacements.)

Use this profit key to '53! Open up the treasure that holds 10,000,000 Phonograph Modernization Sales. Make money selling Cartridge replacements now the E-V way.

Electro-Voice



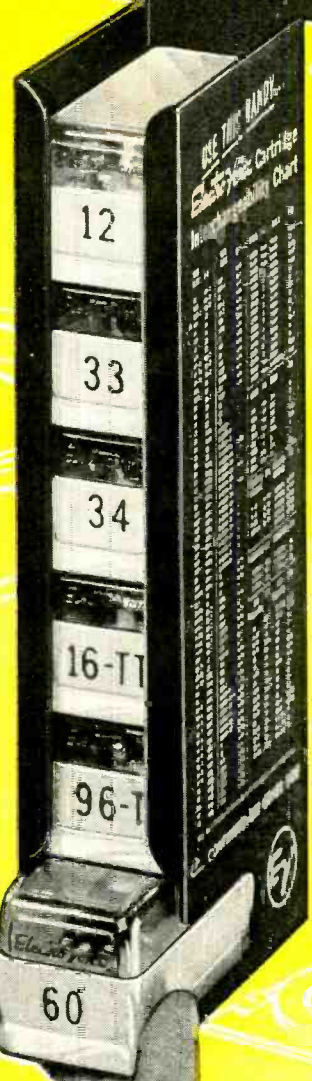Send Now For
FREE BOOKLET SCP 1-2
"YOUR PROFIT KEY TO '53"



Handsome All-Metal Maroon, Yellow and White Dispenser. Holds any 6 E-V Cartridges in their New Jewel-Like Golden Yellow Plastic Boxes.

Hang it on a Wall or Shelf. Cartridge Boxes Easily Removed from Bottom or Top.

Complete Cartridge Interchangeability Chart on Both Sides of Dispenser

ELECTRO-VOICE, INC.
421 Carroll St., Buchanan, Mich.
Send Free Booklet SCP 1-2
"YOUR PROFIT KEY TO '53"

NAME _____
ADDRESS _____
CITY _____ ZONE _____ STATE _____



BAROMETER of the PARTS INDUSTRY

During January, 54 of the leading 400 manufacturers of Radio-Television-Electronic parts and equipment made changes in their lines. Actually there was a decrease in "change activity" as compared to December. In price revisions by the number of manufacturers and products affected, the following summary illustrates the comparative trend for the months of December and January.

	No. of Manufacturers			No. of Products	
	December	January		December	January
Increased prices	18	19	Increased prices	265	207
Decreased prices	10	14	Decreased prices	88	123

For a summary of the most active product categories, see the following table:

Product Group	Increased Prices		Decreased Prices		New Products		Discontinued Products	
	No. of Mfrs.	No. of Products	No. of Mfrs.	No. of Products	No. of Mfrs.	No. of Products	No. of Mfrs.	No. of Products
Antennas & Access.	3	17**	3	38*	7	117**	8	75**
Capacitors	0	0**	0	0	1	44**	0	0
Controls & Resistors	0	0**	1	45*	1	4**	1	1**
Sound & Audio Prod.	5	8*	3	9**	14	47**	13	40*
Test Equipment	2	2*	0	0	8	49*	5	17*
Transformers	2	2	1	1	2	4**	0	0**
Tubes	7	178*	6	30*	5	19**	5	29**
Wire & Cable	0	0	0	0	1	2**	1	4*

* Increase over December
** Decrease from December

* Increase over December
** Decrease from December

Comment: Since the last reported period, fewer manufacturers were engaged in "change activity." TV and radio receiving tube manufacturers are continuing their tendency toward increasing prices, while other product group price changes remain spotty with no apparent trend.

This data is prepared by the staff of United Catalog Publishers, Inc., 110 Lafayette Street, New York, publishers of RADIO'S MASTER, the Official Buying Guide of the parts industry.

Merchandising and Promotion

Channel Master Corp., Ellenville, N. Y., presented the 200th performance of its film, "The Antenna is the Payoff," at Philadelphia's Benjamin Franklin Institute under the sponsorship of Radio Electric Service Co., Channel Master's Philadelphia distributor, and leading dealer associations in that area. Following the film, Sam Schlusel, Channel Master u.h.f. engineer, addressed the group.

The General Electric Tube Department will continue its consumer advertising program in support of television service technicians with a series of consumer magazine ads in 1953.

Merit Coil & Transformer Corp., Chicago, is packing a new form in each HVO-7 flyback box. The form provides complete hookup data and five applicable schematics to cover various chassis. The company plans to include similar information in future TV "Repl" Guides. The forms are also available from the company for counter distribution.

Simpson Electric Co., Chicago, has made reprints of an article on efficient TV installation techniques by two of its engineers, Jack Whiteside and L. J. Austin, available in Instruction Forms No. 19 and No. 20.

(Continued on page 26)




TUNG-SOL statistical quality control methods produce the industry's most reliable tubes for all uses.


Tung-Sol makes: All-Glass Sealed Beam Lamps, Miniature Lamps, Signal Flashers, Picture Tubes, Radio, TV and Special Purpose Electron Tubes.

TUNG-SOL ELECTRIC INC.
Newark 4, N. J.

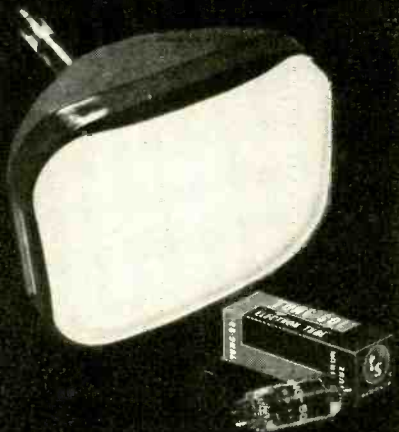Sales Offices: Atlanta, Chicago, Culver City (Los Angeles), Dallas, Denver, Detroit, Newark



TUNG-SOL
RADIO, TV TUBES, DIAL LAMPS

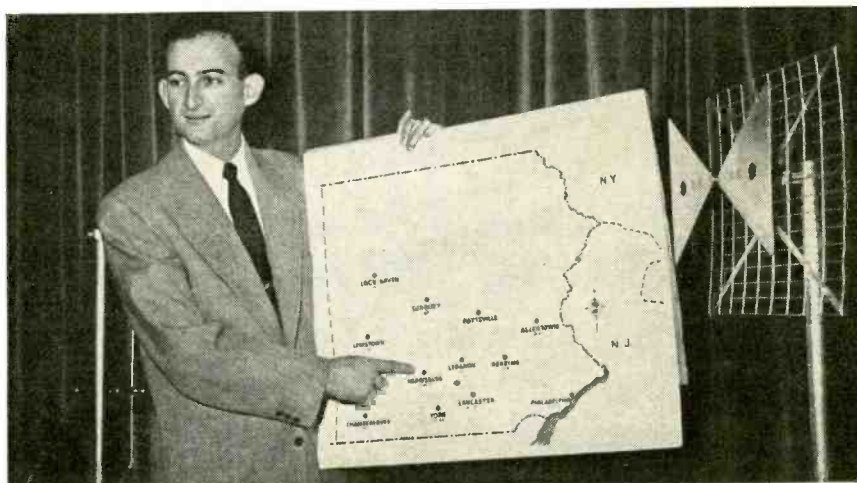


Sam Schlusel, Channel Master u.h.f. development engineer, at a demonstration.

RADIO-ELECTRONICS

For opportunities within your reach

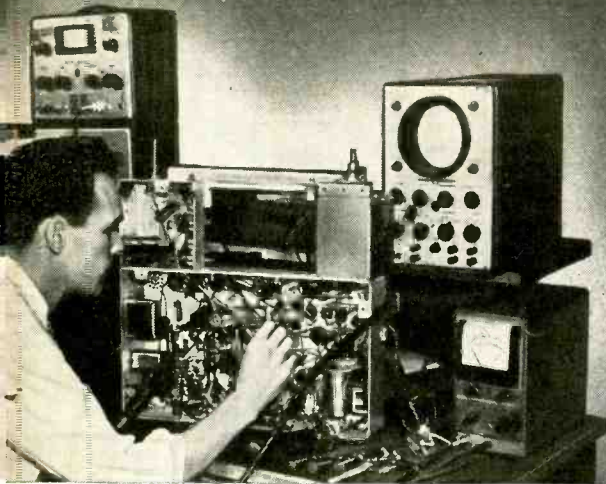See what the RCA TV Servicing Course offers you



Good-pay jobs. A business of your own.

OPPORTUNITIES FOR GOOD-PAY JOBS in Television are within your reach when you study TV Servicing by the RCA Institutes Home Study Method. Or perhaps you would like to start a TV Service business of your own.

If you are not satisfied with the way your future now stacks up, see how easily

you can change the course of your career. RCA Institutes Home Study Course in TV Servicing is helping thousands of other people to better jobs. It can help you. Right now thousands of opportunities are going begging. There is a critical shortage of trained TV servicemen. This is *your* big opportunity.

Easy-to-understand, illustrated lessons



The entire course is divided into ten units of several individual lessons. You study them at home in your spare time. Lesson-by-lesson you learn

the theory and step-by-step procedures of installing TV antennas, of servicing and trouble-shooting TV receivers. Hundreds of pictures and diagrams help you understand the how-it-works information and the how-to-do-it techniques. You will be amazed how easily you absorb the knowledge of each lesson, how quickly you train yourself to become an experienced technician.

Experienced engineers and faculty prepared the course, grade your lessons



The RCA Institutes course was written and planned by instructors with years of specialized experience in training men by home-study and resident-school methods. The course embodies RCA's background of television experience plus knowledge gained in training several thousand technicians. A study of the course parallels an apprentice's training. Your lessons are carefully examined and accurately graded by friendly teachers who are interested in helping you to succeed.

One of the leading and oldest Radio-Television training schools



Founded in 1909, RCA Institutes, Inc. has been in continuous operation for the past 44 years. Its wide experience and extensive educational facilities give students, just like you, unsurpassed technical training in the highly specialized field of radio-television-electronics.

RCA Institutes is licensed by the University of the State of New York . . . an affiliate member of the American Society for Engineering Education . . . approved by the Veterans Administration . . . approved by leading Radio-Television Service Organizations.

It costs so little to gain so much

RCA Institutes makes it easy for you to take advantage of the big opportunities in TV Servicing. The cost of the TV Servicing Home Study Course has been cut to a minimum. You pay for the course on a pay-as-you-learn unit lesson basis. No other home study course in TV Servicing offers so much for so little cost to you.

RCA Institutes conducts a resident school in New York City offering day and evening courses in Radio and TV Servicing, Radio Code and Radio Operating, Radio Broadcasting, Advanced Technology. Write for free catalog on resident courses.



RCA INSTITUTES, INC.
A SERVICE OF RADIO CORPORATION of AMERICA
350 WEST FOURTH STREET, NEW YORK 14, N.Y.

SEND FOR FREE BOOKLET—Mail the coupon—today. Get complete information on the RCA INSTITUTES Home Study Course in Television Servicing. Booklet gives you a general outline of the course by units. See how this practical home study course trains you quickly, easily. Mail coupon in envelope or paste on postal card.



MAIL COUPON NOW!

RCA INSTITUTES, INC., Home Study Dept. RE-353
350 West Fourth Street, New York 14, N.Y.

Without obligation on my part, please send me copy of booklet "RCA INSTITUTES Home Study Course in TELEVISION SERVICING." (No salesman will call.)

Name _____ (please print)

Address _____

City _____ Zone _____ State _____



Bonded!
... sign of Service Dealers
who are *Building for Tomorrow*



RIGHT... FOR SOUND AND SIGHT!

WHEREVER you see Service Dealers who are featuring the Raytheon Bonded Electronic Technician Program, you're looking at good businessmen who are as interested in tomorrow as in today. True, the cash-protection of the Raytheon Bond (backed by Continental Casualty Company) and the Raytheon "Code of Ethics" create initial customer confidence and thus stimulate sales right now.

But, more important, the sound, sensible way *Raytheon Bonded Electronic Technicians* do business insures future profits from an ever-increasing backlog of satisfied customers.

Your Raytheon Tube Distributor will be happy to give you the whole story on the Raytheon Bonded Program, and tell you whether or not you can qualify for this double-barreled asset. Call him today.



RAYTHEON MANUFACTURING COMPANY

Receiving Tube Division
 Newton, Mass., Chicago, Ill., Atlanta, Ga., Los Angeles, Calif.

RAYTHEON MAKES ALL THESE

RECEIVING AND PICTURE TUBES - HELIX AND SHIELDING TUBES - RECTIFIERS AND THERMISTORS - DIODES - MICROWAVE TUBES

Excellence in Electronics

RADIO-ELECTRONICS



Leonard C. Lane,
B.S., M.A.
President of Radio-Television
Training Association,
Exec. Dir. of Pierce School
of Radio and Television

AMAZING NEW TRAINING PLAN

NOW . . . YOU CAN BECOME A

LICENSED* TV TECHNICIAN

LICENSED TV MEN MAKE MORE MONEY

**AT NO EXTRA COST!
YOU GET A ROUND TRIP TO
NEW YORK CITY**

FROM ANYWHERE IN THE U.S. OR CANADA—I pay your way to New York and return, PLUS 2 FREE weeks, 50 hours of advanced instruction and shop training at the **PIERCE SCHOOL OF RADIO & TELEVISION**. You use modern electronics equipment, including student-operated TV and Radio ment, including behind the scenes of New York's stations. You go behind the scenes of New York's big Radio-TV centers, to study first hand. And I give you all this **AT NO EXTRA COST!** (Applies to complete Radio-TV course only.)

Only RTTA makes this amazing offer.

EXTRA FEATURES THAT MEAN MORE MONEY FOR YOU!

Thousands of new job opportunities will be available for you right in your own state, now that the government has lifted restrictions on new TV stations. My simple, successful methods can PREPARE YOU NOW to take your place in America's booming TELEVISION and Electronics industries . . . help you get the success and happiness that you always wanted out of life. You learn the practical, easy way by using actual parts and equipment in the 15 big Radio-TV kits I send you, including a COMPLETE TV RECEIVER . . . yours to build and keep.

My Advanced Training Prepares You For Better Jobs

Then, after you finish your training for a position as a full-fledged TV Technician—where you can write your own ticket and choose from dozens of fascinating careers—I don't stop there! I continue to train you—AT NO EXTRA COST—to qualify for even better pay in the BETTER JOBS that demand FCC licenses, with my . . .

FREE FCC COACHING COURSE
PREPARES YOU AT HOME FOR YOUR
FCC LICENSE
THE BEST JOBS IN TV AND RADIO
REQUIRE AN FCC LICENSE

Given to every student at NO EXTRA COST after TV Theory and Practice is completed.

**SET-UP YOUR OWN HOME LABORATORY
WITH THE 15 BIG TELEVISION-RADIO
KITS WE SEND YOU (At No Extra Cost)**

**YOU BUILD
AND KEEP
ALL THESE
UNITS**

- INCLUDING BIG SCREEN TV RECEIVER,
- plus Super-Hot Radio Receiver,
- R.F. Signal Generator, Combination
- Voltmeter-Ammeter-Ohmmeter,
- C-W Telephone
- Receiver, AC-DC
- Power Supply.
- Everything
- Furnished
- Including
- All Tubes, and
- Big TV Tube



NOW! Advanced FM-TV Training
For Men Who Know Radio
Prepares You For Higher Pay Jobs
In A Few Months
COMPLETE theory and practical training
course . . . complete with kits
including large screen TV receiver.
FCC License Coaching Course Included FREE.

ATTENTION! VETERANS!

MY SCHOOLS FULLY APPROVED TO TRAIN VETERANS UNDER NEW G. I. BILL!
If discharged after June 27, 1950—CHECK COUPON BELOW! Also approved
for RESIDENT TRAINING in New York City . . . qualifies you for full subsistence
allowance up to \$160 per month.



I GET MY GRADUATES GOOD PAYING JOBS

"As Merchant Ship Radio Officer, I receive \$867. for 40-day trip. Your training helped me get this fine position."
—Stanley Nawrocki

I now hold a fine airlines position at LaGuardia Field, New York City, thanks to your excellent training."
—Joseph Rosenberg

"Your excellent instruction helped me get my present job as an airport radio mechanic for American Airlines."
—Eugene E. Basko

"Thanks to your training, I qualified for a good job as a Receiver Tester at Federal Telephone and Radio."
—Paul Frank Seier

Many others working at NBC, RCA, CBS, Dumont, Philco, Emerson, Admiral and other leading firms.



**BOTH
FREE
New
Illustrated
Book plus
Sample
Lesson**

NO SALESMAN WILL CALL!

Mr. Leonard C. Lane, President
RADIO-TELEVISION TRAINING ASSN.
1629 Broadway, Radio City Station
New York 19, N. Y. Dept. R-3

Dear Mr. Lane:
Mail me your NEW FREE BOOK and SAMPLE LESSON that will show me how I can make BIG MONEY in TELEVISION. I understand I am under no obligation and no salesman will call.


Name _____ Age _____
Address _____
City _____ Zone _____ State _____

I am interested in: Radio-TV Advanced FM-TV
VETERANS: If qualified under new G.I. Bill, check here


RADIO-TELEVISION TRAINING ASSOCIATION

1529 Broadway, Radio City Station, New York City 19, N. Y.
Approved as a Correspondence School
under the laws of the State of New York.

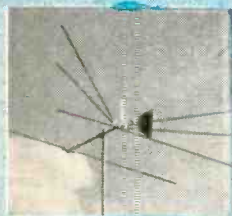ULTRA FAN series — Complete VHF-UHF coverage




single bay — model no. 413

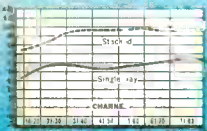

Today's most sensitive All-VU[®] antennas! The Ultra Fans actually operate on three separate electronic principles — automatically:

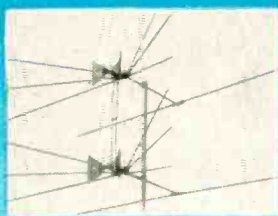1. Low Band VHF (Channels 2-6) ... Conical antenna with parasitic reflector
2. High Band VHF (Channels 7-13) ... Large diameter Y-antenna
3. UHF (Channels 14-83) ... Triangular dipole with show reflector


One set of All-VU[®] stacking rods provides highest VHF and



stacked — model no. 4132

UHF gain. Each Ultra Fan has its own 2-stage inter-action filter, so that only one transmission line to the set is required.

*All VHF, all UHF

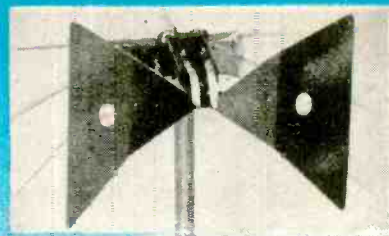

ULTRA DAPTER
model no. 414

Instantly converts all Channel Master Super Fans into high gain, all-channel, VHF-UHF antennas. Features a built-in inter-action filter.

Your best bet for UHF!

CHANNEL MASTER Ultra-Tennas

America's most complete — most effective — UHF antenna line.

Channel Master's advanced engineering pays off again! While rain caused hundreds of UHF antennas to fail recently in Portland, not one Channel Master antenna dimmed or shorted out a picture! The facts speak for themselves: Rain or shine, Channel Master antennas out-perform all others.

Only Channel Master Antennas are designed to eliminate the "TWIN TERRORS" OF UHF RECEPTION:

- Vibration, which causes picture flicker.

Eliminated by Channel Master's Ultra-Rigid construction and advanced mechanical design.



- The accumulation of dirt or moisture around the antenna terminals, which dims and eventually shorts out the TV picture.

Eliminated by Channel Master's sensational "free-space" terminals which prevent the accumulation of foreign deposits at the feed points.





ULTRA BOW
model no. 401

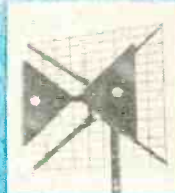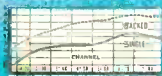The basic UHF antenna for primary signal areas, and the outstanding member of the bow-type antenna family.





ULTRA BOW
with
SCREEN REFLECTOR
model no. 403

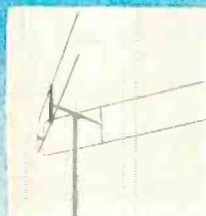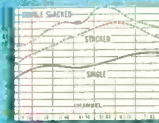Can be stacked in 1, 2, and 4 bays. High, all-channel UHF gain, excellent front-to-back ratio.



ULTRA VEE
model no. 404

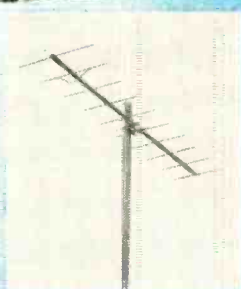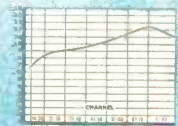- Good UHF gain
- Low VHF gain
- The most rigid UHF antenna of its type and size.




Gain: 11 DB, single
14 DB, stacked

DELTA WELD


Wide Band
10 Element
UHF Yagi

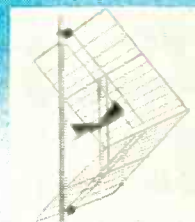Custom-designed for full coverage of your specific area! Brilliant high gain performance across as many as 23 different channels.



CORNER REFLECTOR
model no. 405

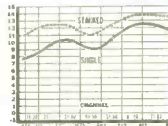The outstanding all-channel UHF FRINGE antenna. Now — can be stacked for even greater gain.



Sold through the nation's leading distributors

CHANNEL MASTER CORP.
KINGSTON, N.Y.

Write for complete technical literature



ULTRA-TIE model no. 9034
Electronic Inter-Action Filter

JOINS separate antennas into a single VHF-UHF antenna system, for use with a single transmission line.

SEPARATES VHF and UHF signals at the set or converts where separate inputs are provided.

The only filter with "free-space" terminals.

NOW — read this true story of

UHF ANTENNA FAILURE IN PORTLAND!

GARRETSON RADIO SUPPLY, INC.

INDUSTRIAL DIVISION
2416 SECOND AVENUE



SEATTLE 1, WASHINGTON
SE. 0640 • MU. 0422

January 22, 1953

Channel Master Corporation
Napanoch Road
Ellenville, New York

Attn: Harold Harris

Dear Harold:

Now that the UHF station, KPTV in Portland, Oregon has been on the air for a few months, it may interest you to know some of the results of antenna performance.

Antennas of all descriptions, both multi-channel and single channel UHF have been installed in the Portland area. The results in most cases were fair, however in some instances certain types of antennas specifically for the UHF channels failed completely to perform. Several of the so called "all channel" antennas performed in strong signal areas, but failed completely where gain was needed, or ghost problems were encountered. These results were obtained while the weather in Portland was good.

For the past few weeks it has been raining consistently in the Portland area and the antenna failures have been numerous, due to the shorting out of the terminal connection at the antenna. The result -- antenna crew men have been out drilling small holes in the terminal blocks trying to provide as much air insulation as possible. Certain types of antennas, which used an isolation filter at the antenna also had their troubles. In many cases this filter broke down and moisture leaked into the filter, causing it to short out at the terminal.

Many of the Channel Master UHF antennas have been sold and installed by our dealers in Portland, with no complaints whatsoever. In all cases, the antennas have given excellent performance and provided clean pictures, regardless of weather conditions. This, we feel, is the result of research and engineering, and the foresight to foresee the many problems which would confront the UHF antenna.

The use of your free-space terminals has forestalled any problems of signal loss due to moisture conditions and in all cases, our dealers tell us that the Channel Master antennas live up to the published catalog information.

May we offer our congratulations on an excellent unit - and let's keep them rolling!

Very truly yours,

GARRETSON RADIO SUPPLY, INC.

Paige C. Lundberg
BY: Paige C. Lundberg

VMH/pl

Look to Channel Master for UHF— IT PAYS OFF!

HICKOK

NEW Video Generator



MODEL 650

**VISUALLY IDENTIFIES
TROUBLE IN ANY SECTION
OF A TV RECEIVER**

The HICKOK Model 650 Video Generator is the first instrument of its kind to accurately and rapidly solve your servicing problems with the necessary tests to visually identify trouble in any section of a TV receiver.

FEATURES:

- An all-purpose video generator. Provides an electronically accurate bar or dot pattern on the screen of any TV receiver—independent of station operation.
- Can be used as a TV transmitter to simultaneously transfer a program to any number of TV receivers—on any desired channel.
- RF output, directly calibrated in microvolts for sensitivity measurements.
- Substitute Video Amplifier with gain of 0 to 10.
- Crystal controlled timer for greater accuracy.
- Fast, accurate, the ideal instrument for all area servicing.
- Increases TV maintenance profits—allows you to trouble shoot many more installations per day.
- Built only by HICKOK. Contains highest quality components throughout for lasting accuracy and dependability.

Write for the new, complete Hickok Test Instrument Catalog today.

THE HICKOK ELECTRICAL INSTRUMENT CO.

10531 Dupont Avenue • Cleveland 8, Ohio

(Continued from page 20)


Jensen Manufacturing Co., Chicago, developed a new 9-way merchandising package as a high-fidelity selling aid. The plan includes counter cards, folders, catalog material, etc.

Weller Electric Corp., Easton, Pa., designed a new crowd-stopping display for use in regional and local dealer trade shows which it lends, free, to its distrib-



utors. Built around a shooting-gallery theme, the display uses audience participation to gain additional appeal.

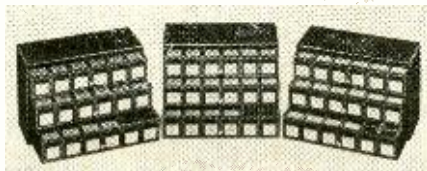P. R. Mallory & Co., Inc., Indianapolis, designed three new kits for its controls. Any one of the three permits servicing of over 50 different models of radio and TV sets. Individual kits are recommended for Western, Central, and Eastern states.



Precision Apparatus Co., Inc., Elmhurst, N. Y., manufacturer of radio and TV test equipment, opened its 1953 series of lectures on television circuitry and servicing in New York City recently. The lectures and demonstrations are scheduled to be presented in 110 cities throughout the United States and Canada during 1953.

Permo, Inc., Chicago, manufacturer of phonograph needles, recording tape and wire, and record brushes, released a new brochure to distributors showing photographs of the representatives who handle the Permo line.

Radio Merchandise Sales, Inc., (RMS), New York City, held another in its series of forums on TV antennas in Quebec. The company also participated in a forum at Bridgeport, Conn., conducted by the local station WICC-TV.

Production and Sales

The RTMA estimated TV set production for 1952 at approximately 6,000,000 and radio set production at 9,500,000. Officially, the RTMA reported production of 5,175,194 TV sets and 8,386,-

076 radios for the first 11 months of 1952, as compared with 4,798,056 TV sets and 11,701,115 radios produced in the 1951 period.

The NBC Research and Planning Department reported that there were 20,439,400 TV sets installed in the United States as of December 1. New York had over 3,000,000 and Chicago, Los Angeles and Philadelphia over 1,000,000 each. Boston was close to the million mark, and the new TV areas of Denver, Colo., and Portland, Ore., rang in with 70,000 and 35,000 respectively.

New Plants and Expansions

Aerovox Corp., New Bedford, Mass., purchased the entire outstanding stock of Acme Electronics, Inc., Pasadena, Calif., designer and manufacturer of filters. Acme will be operated as a wholly owned subsidiary of Aerovox under the continuing management of Hugh P. Moore, president.

Radio Apparatus Corp., Indianapolis, has transferred the national sales offices of its Monitoradio line of receivers and transmitters for mobile or stationary communications systems to Chicago, according to an announcement by Roy True, corporation president. At the same time he announced the appointment of Verne Roberts and Paul Redhead as director of sales and sales manager, respectively, of the newly formed group. Both are well known in the industry.

General Cement Manufacturing Co. opened an additional plant in Rockford, Ill., according to R. G. Ellis, general sales manager. This is the company's third plant in that city. Main offices remain at 919 Taylor Ave. in Rockford.

Granco Products, Inc., 36-17 20th Ave., Long Island City, N. Y., was established as a new firm in the electronics field. The company will design, manufacture, and distribute u.h.f. converters for TV and u.h.f. measuring instruments.

Radio Corporation of America announced plans to build a factory in Spain for the production of phonograph records, record players, and TV home receivers.

Crest Laboratories relocated its factory and offices in expanded facilities in Rockaway Beach, N. Y. The new facilities, quadrupling the company's former space, will produce transformers.


Blonder-Tongue Laboratories, Inc. completed its new factory and office building in Westfield, N. J. It will be used for the manufacture of TV boosters and distribution amplifiers.

David Bogen Co., manufacturer of sound systems, moved to new and larger quarters occupying the entire six-story building at 29 Ninth Ave., New York City.

Radio Craftmen, Inc., Chicago, established the Hi-Fidelity Manufacturing

HICKOK

Choice of the Experts

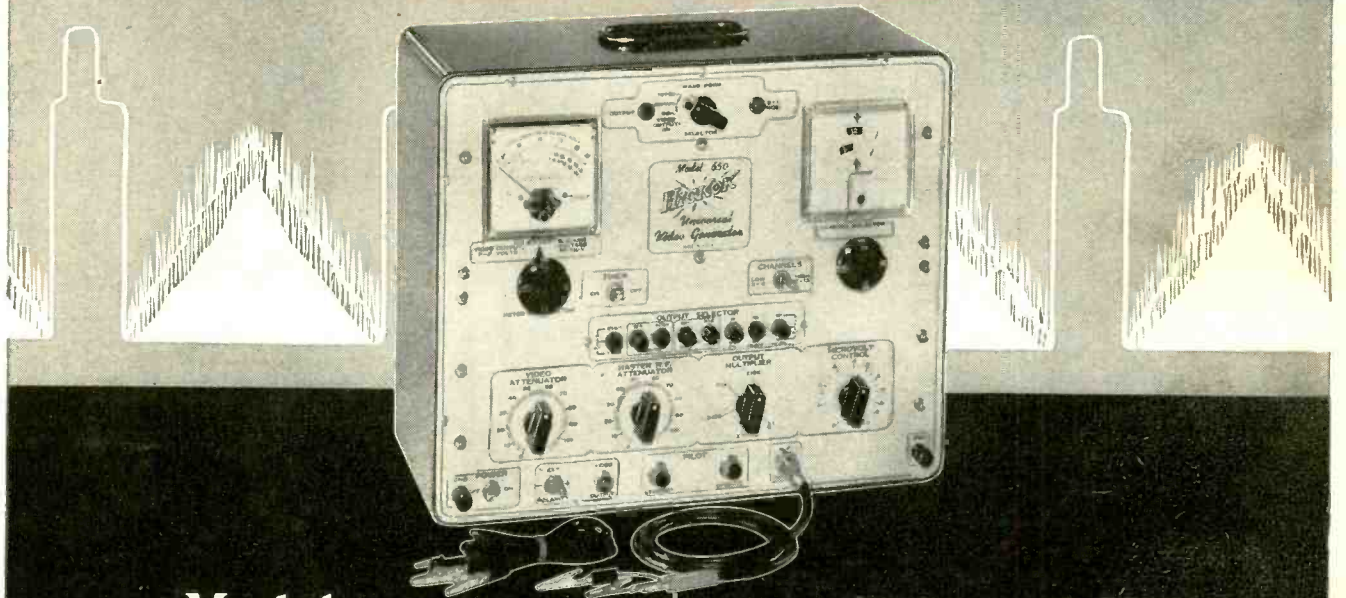

**Model
650**

**Universal Video
Generator**

Hickok, through 42 years of uninterrupted quality production has pioneered and developed numerous well-known electrical and electronic equipments now recognized as standards for the industry.

The newest Hickok contribution is the Model 650 Universal Video Generator. It accurately and rapidly localizes trouble in any stage of a TV receiver. Its use accomplishes in minutes tasks that normally take hours.

THE HICKOK ELECTRICAL INSTRUMENT COMPANY

10514 Dupont Avenue • Cleveland 8, Ohio

MARCH, 1953




“Check your air, Sir?”



To keep voices traveling strongly through telephone cables, you have to keep water *out*. This calls for speed in locating and repairing cable sheath leaks—a hard job where cable networks fork and branch to serve every neighborhood and street.

At Bell Telephone Laboratories, a team of mechanical and electrical engineers devised a way to fill a complex cable system with dry air under continuous pressure. Pressure readings at selected points detect cracks or holes, however small. Repairman can reach the spot before service is impaired.

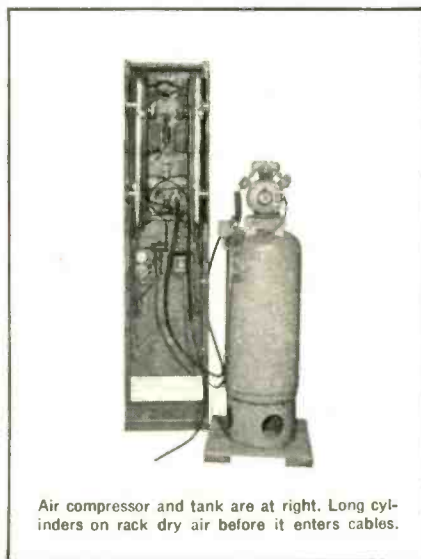It's another example of how Bell Laboratories works out ways to keep your telephone service reliable—and to keep down the cost to you.



Air compressor and tank are at right. Long cylinders on rack dry air before it enters cables.

He's checking the air pressure in a branch cable, one of scores serving a town. The readings along the cable are plotted as a graph to find low-pressure points which indicate a break in the protecting sheath.



Master meters keep watch over the various cable networks which leave a telephone office in all directions to serve a community. Air enters the system at 7 pounds pressure, but may drop to 2 pounds in outermost sections—still enough to keep dampness out.





BELL TELEPHONE LABORATORIES

Improving telephone service for America provides careers for creative men in mechanical engineering

RADIO-ELECTRONICS

SPRAGUE

SERVICEMAN'S DIARY... by Ben Grim

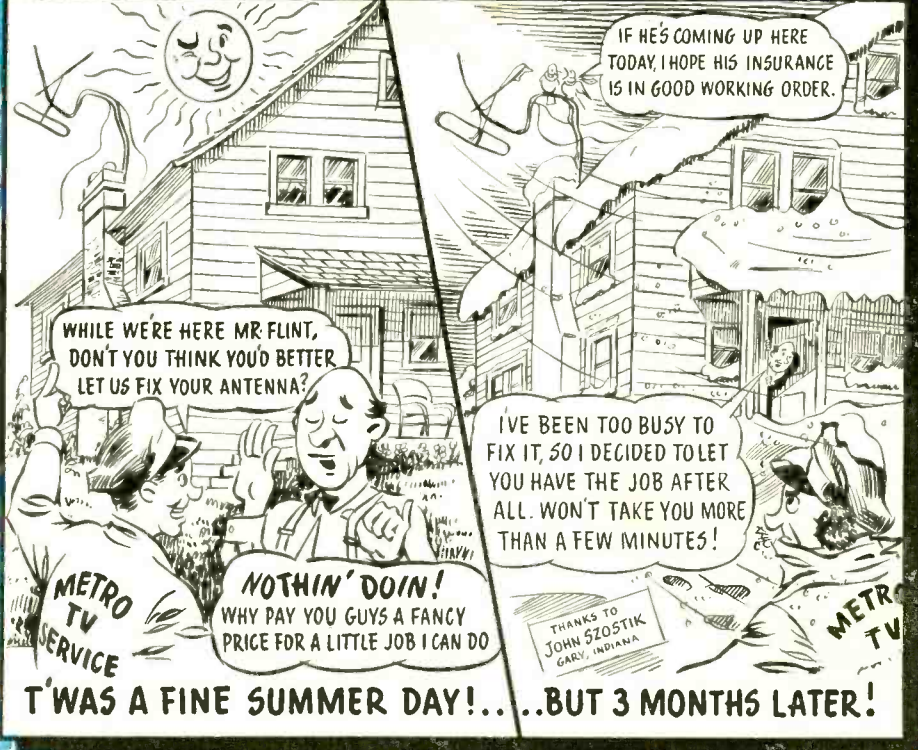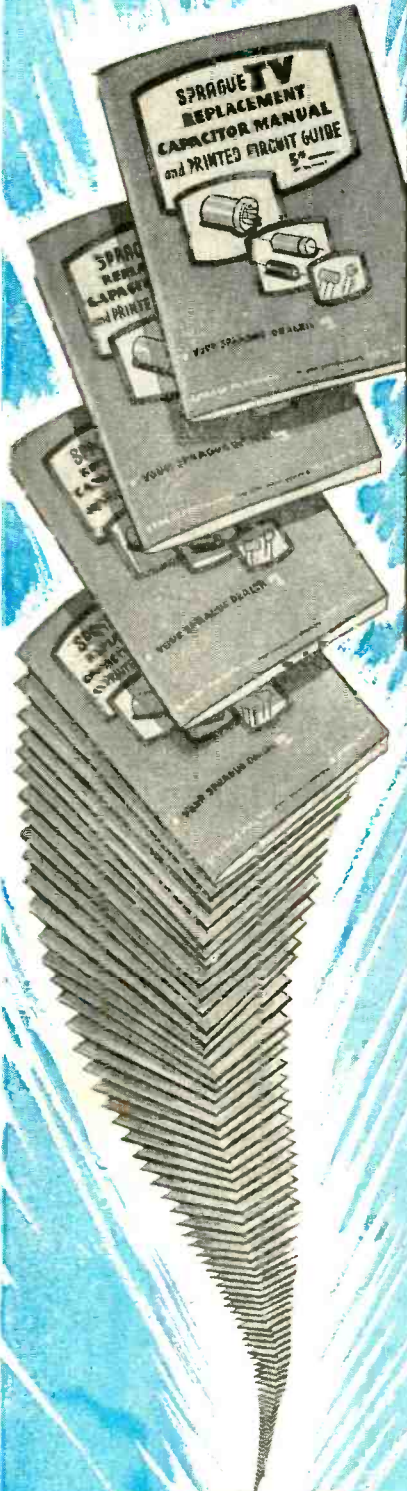

Do you have the **NEW** 5th Edition of the **SPRAGUE TV REPLACEMENT CAPACITOR MANUAL?**

If not, get your copy from your distributor without delay!

This 44-page reference guide shows the accurate, up-to-the-minute Twist-Lok[☆] and Atom[☆] Electrolytic Capacitor replacements for 2460 receiver models by 78 set manufacturers. It's the most comprehensive of all such manuals and it's yours FREE!

Also included for the first time in this new edition is a Printed Circuit Guide for the resistor-capacitor plates used by 46 manufacturers as well as a complete capacitor color code chart, two extra features to make the Sprague TV Replacement Capacitor Manual even more invaluable to every television technician!

P.S. If your distributor is temporarily out of stock, you can also get copies by writing Sprague Products Co., 81 Marshall St., North Adams, Mass. Please enclose 10c to cover handling and postage.

[☆]Trademark




WORLD'S LARGEST CAPACITOR MANUFACTURER

NEW! 2ND EDITION
of the only complete
reference on **AUDIO!**

**"The Recording &
Reproduction
of SOUND"**

by **OLIVER READ**

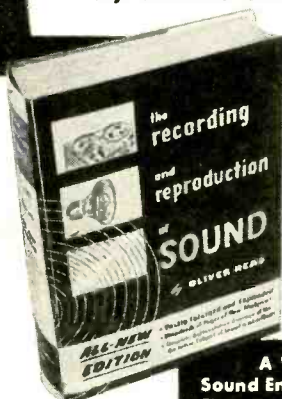

Completely
revised and
vastly en-
larged new
edition

**OVER
800
PAGES**

A "Must" for
Sound Engineers, Hi-
Fi Enthusiasts, P. A.
Men, Broadcasting
Stations, Recording
Studios, Students

largest selling
book in its field

CONTENTS:

A Partial List of Authoritative Chapters:
Behavior of Sound Waves; Basic Recording
Methods; Lateral Disc Recording; Microgroove
Recording; The Decibel; Phono Reproducers;
Styli; Microphones; Loudspeakers and En-
closures; Dividing Networks and Filters; At-
tenuators and Mixers; Home Music Systems;
P.A. Systems; Amplifiers; AM and FM Tun-
ers—PLUS HUNDREDS OF OTHER SUBJECTS

Now you can have all the *right* answers to
any subject in the field of Audio. Learn how
to select and get the most out of recording
equipment. Tells you how to select the
proper amplifier for given applications, how
to test amplifier performance, how to elimi-
nate hum. Explains microphone, speaker
and pickup principles and selection factors.
Shows how to utilize inverse feed-back, ex-
panders and compressors. Covers hundreds
of subjects—a vast wealth of reliable infor-
mation found in no other single volume. If
you work in the field of Audio, this book be-
long in your library. Order your copy today!

6" x 9" **ONLY \$7.95**
Hard Covers
800 pages 700 illustrations

**ORDER
TODAY**

Order from your Parts
Jobber, or write direct to
HOWARD W. SAMS & CO., INC.
2205 E. 46th St., Indianapolis 5, Ind.
My (check) (money order) for \$.....
is enclosed.

Send copy(ies) of *The Recording &
Reproduction of Sound (RR-2)*. \$7.95 per copy.

Name.....

Address.....

City..... State.....

Corp. in West Palm Beach, Fla., to
manufacture tuners, amplifiers, and
eventually television chassis as subcon-
tractors for Radio Craftsmen.

Arcturus Electronics, Inc., Newark,
N. J., has been merged into General
Electronics, Inc., Paterson, N. J., with
Delbert E. Replogle as president and
Frederick D. Gearhart, Jr., as chairman
of the Board.

Stromberg-Carlson opened a sales
and sales engineering office for its
Sound Division in Dallas to serve an
eight-state area in the South.

American Phenolic Corp., Chicago,
signed a licensing agreement with the
Cornish Wire Co. of New York, giving
Cornish rights to manufacture, package,
and sell tubular twin-lead under Am-
phenol's Krueger patent.

Sarkes Tarzian, Bloomington, Ind.,
is expanding its Rectifier Division, with
the addition of a two-story structure
to its present plant. When completed
the building will double the company's
production capacity.

Business Briefs

... International Resistance Co., Phila-
delphia, presented a lecture to over 150
executives, engineers, supervisors, and
other plant personnel, by Jack Lacy,
widely known sales-training lecturer.
The talk was part of IRC's long-range
plan to increase customer service.

... The 1953 Electronic Parts Show
management reports that 234 compa-
nies, with a total of 374 display units,
reserved space at the annual show to be
held in Chicago May 18-21.

... The RTMA held an industry-wide
engineering conference in New York
City to explore all phases of the prob-
lem created by spurious receiver and
transmitter radiations.

... General Electric will double its
production of germanium diodes this
year to meet the rising demand by
television manufacturers.

... L. B. Calamaras, executive vice-
president of NEDA, reported that a
program has been outlined for the 1953
NEDA Convention and Conference to be
held September 14-16 at the Chase
Hotel in St. Louis, Mo.

... Electronic Instrument Co., Brook-
lyn, N. Y., announced the production of
its 250,000th Eico instrument since the
company began business in 1945.

... Howard W. Sams & Co., Indi-
anapolis, announced that RCA, Hatti-
son, N. J., Sarkes Tarzian, Inc., Bloom-
ington, Ind., and the J. W. Miller Co.,
Los Angeles, have become participants
in the Sams Photofact service for trans-
former components, selenium rectifiers,
and coils, respectively.

... John F. Rider Publisher, Inc., New
York City, announced that Merit Coil
& Transformer Corp., Chicago, is now
participating in the Rider Replacement
Parts Listing Program. **END**

**NEW! GONSET
UHF-TV
PRODUCTS**

VHF/UHF GONSET LINE

Another First!
by the originators
of prefabricated
open wire line. Gonset Part #1499



Closer spacing restricts r.f. field at UHF.
375 ohm surge impedance requires no
special matching to 300 ohm circuits. Un-
like "ribbon" type line using either con-
tinuous or perforated polyethylene web,
the UHF attenuation of VHF/UHF GON-
SET LINE increases only moderately when
it is wet.

UHF RHOMBIC




High gain and ex-
cellent directivity
characteristics to-
gether with a rugged
mechanical struc-
ture, all at a modest

Gonset Part #1529
price are obtained in
this optimized GONSET UHF RHOMBIC.
Uniform gain of approximately 8 db from
channel 14 through 65 (compared to a
matched, resonant dipole). Sharp forward
pattern minimizes the need for "probing"
when installing. Amplitude of spurious
lobes is sufficiently low to reject ghosts in
over 99 per cent of installations.

UHF PARABOLIC

A parabolic sheet type an-
tenna using a folded di-
pole. Construction avoids
use of insulation. Ideal for
use in locations where very
strong rear reflections pro-
duce unusually difficult
ghost problems. Gain 4 to
5 db over specified fre-
quency range (referred to
a resonant half wave di-
pole). Not intended for fringe area use,
but rather as a moderately priced antenna
having excellent rear rejection.

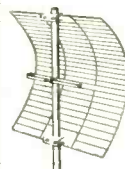

Gonset Part #1531-A	Channels 14-42
" " #1531-B	" 25-65
" " #1531-C	" 42-83

UHF CORNER REFLECTOR



A sturdy, well designed
array of the corner re-
flector type, using a folded
dipole and 90 degree re-
flector. Gain of approxi-
mately 8 db is comparable
to that of the GONSET
UHF RHOMBIC, but for-
ward response is somewhat
broader and back response
somewhat lower. Use of a

folded dipole eliminates the need for an
insulator, and permits a good impedance
match to 300 ohm or 375 ohm line. Ideal
for use where high gain is required and
strong reflections from the rear make
necessary an antenna which is virtually
"dead" off the back.

Gonset Part #1535-A	Channels 14-42
" " #1535-B	" 25-65
" " #1535-C	" 42-83

GONSET CO.

RE



801 S. Main St.
Burbank, Calif.

Please RUSH new UHF-TV ENGINEERING BROCHURE

Name.....

Address.....

City..... Zone..... State.....

Depend on Mallory
for
Approved Precision Quality



The Vibrator Preferred by 5 out of 6 Service Men



How do we know? We surveyed hundreds of service men like yourself . . . maybe you were one of them. We found that Mallory Vibrators were preferred over others because of their long life and dependability.

There is good reason for that vote of confidence. It is the same reason why more Mallory Vibrators are used as original equipment than all other makes combined. The patented, tuned mechanism in Mallory Vibrators assures completely dependable performance, every time . . .

Less wear because of slow contact

Low resistance because of high contact pressure

Reduced arcing because of clean, fast break

You can depend on Mallory Vibrators for highest quality . . . yet they cost no more. Ask for Mallory, by name, the next time you call your distributor. It is a sure way to beat the call-back problem . . . make sure every job is right the first time.

MALLORY

CAPACITORS • CONTROLS • VIBRATORS • SWITCHES • RESISTORS
RECTIFIERS • POWER SUPPLIES • FILTERS • MERCURY BATTERIES

APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO., Inc., INDIANAPOLIS 6, INDIANA



320K SIG. GEN.
KIT \$19.95 WIRED \$29.95


145K SIG. TRACER
KIT \$19.95 WIRED \$28.95

950K R-C BRIDGE &
R-C-L COMP. KIT \$19.95
WIRED \$29.95

360K SWEEP GEN.
KIT \$34.95 WIRED \$49.95

New 214K VTVM KIT
\$34.95 WIRED \$34.95

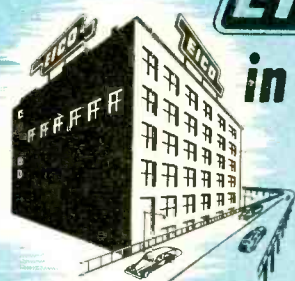OVER 1/4 MILLION
EICO INSTRUMENTS
in use the world over!




EICO new modern facilities for research, development and production—your greater assurance of . . .

LABORATORY PRECISION AT LOWEST COST



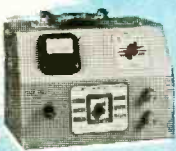New 377K SINE & SQUARE
WAVE AUDIO GEN. KIT \$31.95
WIRED \$49.95



1040K BATTERY ELIM.
KIT \$25.95 WIRED \$34.95



New 536K MULTIMETER
KIT \$12.90 WIRED \$14.90
1,000Ω/v; 31 ranges



1171K RES. DECADE BOX
KIT \$19.95 WIRED \$24.95



625K TUBE TESTER
KIT \$34.95 WIRED \$49.95



CRA PIX TUBE ADAPTOR
for Tube Tester \$4.50



New 565K MULTIMETER
KIT \$24.95 WIRED \$29.95
20,000Ω/v; 31 ranges




315K DELUXE SIG. GEN.
KIT \$39.95 WIRED \$59.95



HIGH VOLTAGE
PROBE \$6.95



221K VTVM \$25.95
WIRED \$49.95

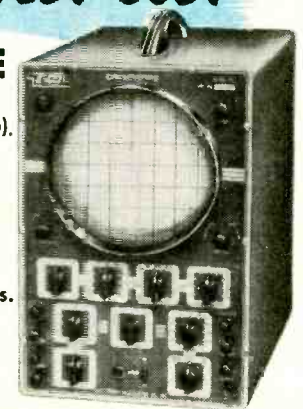

470K KIT \$79.95 WIRED \$129.50



425K 5" PUSH-PULL SCOPE
KIT \$44.95 WIRED \$79.95

- NEW 7" Push-Pull OSCILLOSCOPE**
- Boosted vert. sensitivity: 10 mv rms/in.
 - Extended flat freq. response: 10 cps—1 MC (±2 db).
 - 3-step freq.-compensated attenuator; cathode follower input.
 - Internal voltage calibrator; dir.-cal. screen.
 - Extended sweep range: 15 cps—100 kc.
 - Int. pos. or neg., ext. & line sync.
 - On front panel: sawtooth, 60 cps outputs; intensity mod. & ext. sync inputs.
 - Var. phasing of int. 60 cps sweep.
 - Direct connection to CRT plates.

You Build EICO Kits in One Evening, but . . . They last a Lifetime! and You SAVE OVER 50%

YOU be the judge. See the famous EICO line TODAY — in stock at your local jobber — and SAVE!

Write NOW for FREE newest Catalog 3-C.

America's greatest instrument values bear the name—



ELECTRONIC INSTRUMENT CO., Inc., 84 Withers Street, Brooklyn 11, N. Y.

See EICO'S Exhibit Booth No. 4-401 at the I. R. E. Show

RADIO ASTRONOMY

... *Newest and Fastest-Growing Science* ...

By HUGO GERNSBACK

RADIO Astronomy, a comparatively new branch of radio electronics, dates back only to about 1931. At that time Dr. Karl G. Jansky, of the Bell Telephone Laboratories of New York, discovered that unusual and previously unobserved radio signals, emanating from the direction of the Milky Way, were received on Earth.

Astronomers and physicists alike paid little attention to the new discovery. But a radio amateur, Grote Reber, before World War II, set up a rotating 30-foot antenna in his back yard. This antenna, bowl-shaped like a searchlight, could be pointed into any direction in the sky, like a telescope.

Reber, like Dr. Jansky, found that the strongest signals originated somewhere in a plane near the center of our galaxy. He soon noted that the signals *did not* seem to come from the biggest or brightest stars.

Reber at the time theorized that the radio signals really did not come from the stars themselves, but that they originated in the huge hydrogen gas clouds which we know exist in interstellar space.

With better modern instrumentation that was not available in 1931, a great deal of progress has been made toward solving many unsolved riddles of the cosmos. Today we know that most stars—including our own sun—give out radio energy at various frequencies.* In the near future we are certain to learn a great deal more about the mysterious behavior of matter. Man once more realizes that even one of his greatest achievements, radio, is old (and ancient) hat! Radio waves, it now appears, have existed for at least *five billion years*—perhaps longer.

This, then, explains the sudden and feverish international activity in radio astronomy. Nearly all the major countries are in the race. Much of the work unquestionably is going on in secret, much of it behind the Iron Curtain.

Large radio telescopes are now installed at the National Bureau of Standards, Naval Research Laboratory, Harvard Observatory (under construction), and Cornell University (Sacramento Peak, N. M.), in the United States; in England at Manchester University and Cambridge University; in France, at the École Normale Supérieure (Laboratoire de Physique); in Holland at Leyden University; and in Australia at the Radio Physics Laboratory.

How important the subject is can best be expressed by

the generous funds that are being poured into the various installations. Thus, Great Britain will be spending over one million dollars on the world's largest and most modern radio telescope at Manchester University. Its huge parabolic lattice-bowl antenna measures 250 feet in diameter. It swings in a cradle between metal-lattice towers which are 180 feet high. The whole assembly is mounted on a metal platform which runs on a circular railroad track. Thus the telescope antenna can be pointed toward any region in the sky. Clockwork then guides the telescope and will keep it on any selected point in the heavens.

Why all this great and feverish activity on such a seemingly highly scientific and improbable endeavor? Why, on top of spending millions on radio telescopes, do all the above-mentioned countries add extensive—and expensive—faculty centers of radio astronomy to their present seats of learning?

The answer is not difficult to find. Radio astronomy is in an exactly parallel position today to that which existed in atomic science in the twenty years before 1945, the date of the first atomic explosion.

Many scientists realize that reception on Earth of interstellar radio signals, which have taken from one hundred to one billion years to reach us, poses important problems concerning their origin. At present there is some indication that a solution of such problems may be of vast scientific importance, contributing to the understanding of many fields of science—even the atom. This may in time open the road to entirely new sources of *energy*—POWER.

Scientists, too, suspect that there may be an important connection between cosmic rays and radio energy—both may turn out to be closely related.

What does man stand to gain by the understanding of the origin of radio waves from interstellar space? No one can tell. We do not immediately expect to gain from it vast amounts of power—this lies in the future. We are, however, certain that the knowledge of cosmic radio manifestations is as fundamental to the future of science as was Maxwell's electromagnetic theory to the development of our present radio communication.

By 2023, the present population of the Earth (1949-2,367,737,000) will have doubled to 4¾ billion humans. To feed and clothe them, man will require more and still cheaper power. Only by understanding Nature's still unknown, immense energy sources can we hope to achieve prosperity for all mankind and consequently a real planetwide Peace.

*See also the writer's editorial "Our Electronic Universe", October 1952, RADIO-ELECTRONICS.

RAPID REMOTE MICROPHONE CONTROL

By N. H. CROWHURST

REMOTE microphone control in PA work has obvious advantages, and once you try it you'll find it indispensable. The control panel can be moved to any convenient point where the operator can hear what the audience hears, and can watch the stage for cues. The simplest method of remote control is *electronic mixing*, using d.c. bias on the control or suppressor grids of the individual microphone-input stages. The chief advantages of this method are that low-level audio signals go *direct to the amplifier inputs* instead of first passing through noisy switching circuits, and the control lines carry only hum-free d.c.

The d.c.-bias supply can be a dropping resistor in the common negative return, or a well-filtered-d.c. heater supply for the first stages can be used. Either way there must be sufficient decoupling and filtering to keep hum or noise off the grid used for gain control. Simple resistor-capacitor filters are sufficient.

On PA jobs where two or more microphones are required there will be less danger of acoustic feedback if only one microphone is alive at any time, or at least if only those microphones actually needed at the moment are alive. This is no problem with direct microphone switching, but a *remote-control switching circuit* is not easy to design. If bias voltage is switched, loud clicks or plops come from the system. One alternative is to change the bias quickly with fader-type controls, but this can cause peculiar effects until a great deal

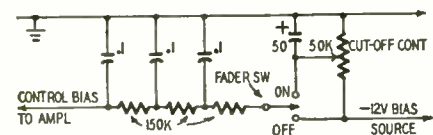


Fig. 1—Circuit of the basic bias-control unit for one microphone. The three-section filter eliminates audible switching transients without noticeable delay.

of skill is acquired; and with nice fat decoupling capacitors in the circuit,


there can be a disconcerting delay in the microphone changeover action.

The problem is to provide the quickest possible change of bias without any audible effect. The solution is an *automatic switching circuit*. See Fig. 1.

Various arrangements were tried for smoothing out the switching clicks, from a single R-C combination to a multisection low-pass filter. A single resistor-capacitor section produced a loud click unless the values were made so large that the time delay became unbearably long; with multisection filters the click was transformed into a *plop*—the filters changed the proportions of the component frequencies in the switching voltage transient.

High-speed switching means that some disturbance—in the form of a simple step transient—is bound to get into the amplifier. The problem is to make this transient inaudible, while still attaining satisfactory operating speed. To do this, all the component frequencies in the step must be inaudible. We dug out an old copy of Fletcher-Munson loudness contours, from which we found that the slope of the curves at the low-frequency end is approximately 18 db per octave near the threshold of audibility. The answer obviously was to use three R-C stages—each with a slope of 6 db per octave—to produce an inverse modification of the step response. This should give the highest possible speed of action without producing any audible effect—and it worked! When this system is in use there is not the slightest indication that at one instant a certain mike is dead, and a second later it is alive.

Two systems were modified to incorporate this method of switching. The first was simply a twin version of Fig. 1 for switching two microphone circuits; the second is far more versatile, and is shown in block form in Fig. 2. There are three remote-control microphone inputs with universal input transformers so that microphones of any impedance can be used. After mixing, the frequency spectrum is divided into

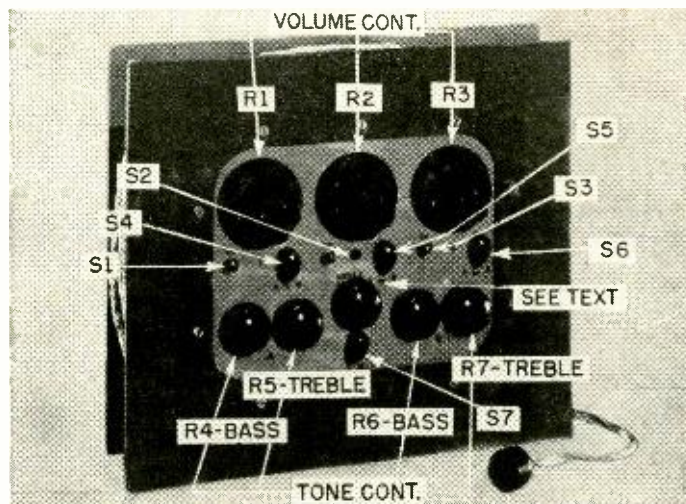

The completed remote-control panel does double duty as a reel for control cable. The "Middle" control was transferred to the amplifier in later models.

three channels, with individual low-, medium-, and high-frequency amplifiers. Two of the channels have remote gain control (operating the middle channel at fixed gain eliminates an extra control).

6J7's are used in the input and tone-control stages. Tubes were scarce over here when the original amplifier was built, and the 6J7 and the Z63 (a British type) can be used interchangeably. With the control bias applied to grid 1, 12 volts provides complete cutoff. This is much less than would be needed with remote-cutoff tubes, and no microphone has large enough output to produce appreciable distortion due to the curvature of the tube characteristic even in the second stages.

Grid 1 control was chosen in preference to suppressor control because the earlier KTZ63, for which the Z63 is now a replacement, was a tetrode.


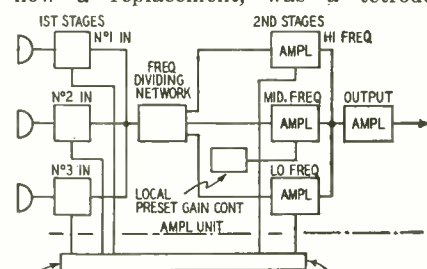


Fig. 2—Block diagram of the de luxe remote-control amplifier described in the text. One or more microphone inputs may be selected, mixed, and divided into low-, medium-, and high-frequency amplifier channels with independent gain controls.

Use care in selecting tubes, to find suitable nonmicrophonic samples. Special low-noise pentodes such as the 1620, 7000, and British EF37A might be better for this application, but this does not invalidate the method. Fig. 3 is the complete amplifier circuit.

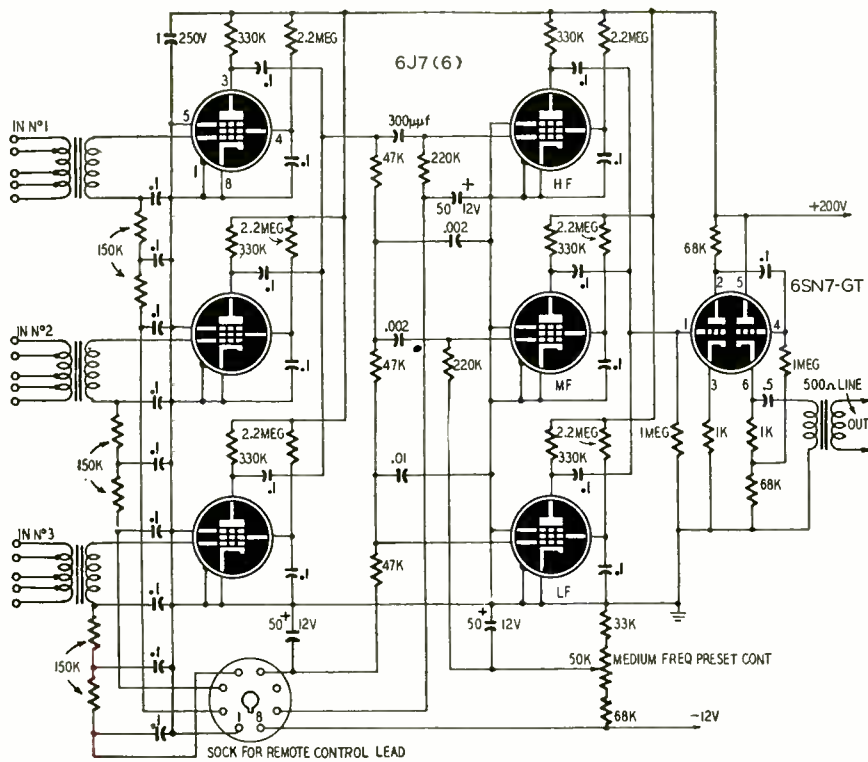The control-panel circuit is shown in Fig. 4, and the panel in the photo. The remote-control connection is through an octal plug and socket on a 7-wire cable.



Figs. 3 and 4—Schematic of controlled system (above) and control unit (below).

There are two switches with each microphone gain control. The lower one (S1, S2, or S3 in Fig. 4) is a simple on-off toggle switch: when it is OFF, that mike circuit is definitely off. When it is ON, the mike is controlled by the remaining switches and controls. The additional switch above each gain control (S4, S5, or S6) has three positions, marked A, ON, B; in the center (ON) position, the mike circuit is on, subject to control only by gain controls R1, R2, or R3. But in either side position A or B it is further subject to control by the tone-control switch S7.

Two pairs of tone-compensation controls—one pair shown as R4 and R5, and the other pair shown as R6 and R7—are provided for low- and high-frequency gain. (The mid-frequency gain is preset in the amplifier.) Between these pairs is a two-way switch

S7 whose positions have been marked A and B. When this switch is in the A position R4 and R5 control tone, while in B position R6 and R7 control tone. Besides selecting tone-control settings, this switch will also select mike circuits set to position A or B on the individual mike-circuit switches.

This layout may seem complicated, but a little thought will show that it provides extremely versatile control. Suppose two individuals are talking alternately into two different mikes. Using S4 and S5, one mike can be set to A position and the other to B position, and the master tone-control switch S7 can be used to switch from one to the other as each speaks in turn; tone-control group A can be set to give the most pleasing result with mike and voice A, independent of the B position

setting. S7 changes the tone setting automatically every time the mikes are switched. If desired, a third mike can cut in on either A or B position, by having its three-way circuit switch S6 in the ON position, and just bringing it in with its ON-OFF switch S3. It is best to keep any circuit not in use with its ON-OFF switch on OFF, and its selector switch in the middle ON position. Then it can be cut into the circuit instantly, simply by throwing the ON-OFF switch. The high- and low-frequency tone controls can be used to create special effects such as artificial distance, by accenting or attenuating extreme frequencies. (This system can be adapted for use with an echo chamber like the one described by Charles L. Hansen in RADIO-ELECTRONICS for July, 1952.—Editor)

One feature of the panel's versatility is that a new tone-control setup can be prepared while one or two mike circuits are being used. At the right moment the changeover between the tone controls is made with a flick of the A-B switch S7. If for any reason the new arrangement would be better on B circuit, and the present arrangement is already on B circuit, then the present setup can be transferred to A circuit first. Set the live mike-selector switches to the middle ON position, set both tone controls in the same position, and change over from B to A with S7. Then switch the live mike-selectors to A. Now preparation can proceed on the B circuit. This does not interfere with the program. A little thought is needed to master the principle of operation, but once understood, its extreme versatility is ample reward.

Two more points should be made clear before concluding. The values used for the switching-filter circuits, three 150,000-ohm resistors and three 0.1-µf capacitors, proved adequate for practically all jobs. But if more than usual gain is required, due to using a low-sensitivity microphone at long range, switching clicks may come through, particularly when switching off. One method of preventing this without modifying the circuit, is to turn the gain control down first; then switch off; and then reset the gain control to the desired level ready for the next switching on. If the operator finds this difficult, further controls could be added to reduce the gain by a fixed amount in the OFF position (just enough to render the microphone insensitive), instead of cutting the tube off completely. Less switching voltage will be needed with this method, but the first method has been found satisfactory for the comparatively few occasions where clicks are audible.

Some readers may feel that 6J7's will not give much range of control, but will act like on-off switches. Try it. You will find that any tube can be used as a variable-mu tube, provided the signal level is small enough so the tube curvature does not cause distortion. The range of gain variation is as great as can be obtained with a remote-cutoff tube. END

VOLTAGE REGULATORS

*VR tubes decrease hum
and improve amplifier
stability and response*

By JOSEPH MARSHALL

VOLTAGE-REGULATED power supplies find considerable application for stabilizing high-frequency oscillators in receivers and transmitters. Their purpose is to minimize frequency drift if the line voltage varies. Less well known, but of even greater value, is the use of voltage regulators, especially gas-tube types, as hum and decoupling filters in high-fidelity audio amplifiers. They provide a highly effective and low-cost method of improving the hum level and transient response, and can transform an excellent amplifier into a superlative one. I have used this device for many years and it is one of the features of the *Golden Ear* amplifier. ("For Golden Ears Only," by Joseph Marshall. *Audio Engineering*, April, 1950.)

A voltage regulator is the equivalent of a highly effective low-pass filter consisting of a series impedance A and a shunt impedance B (Fig. 1). We know from Kirchoff's law that when a current is introduced at a junction of several branches it will divide among the branches in inverse proportion to their resistances or (in the case of a.c.) their impedances. In the low-pass filter, part of the current will go through series element A and part through shunt element B. If the combined resistance or impedance of the series element and the load is 10 times greater than the impedance of the shunt element, 90% of the current will flow to ground through B and only 10% will flow through A and the load.

In a power supply we are dealing with both d.c. and a.c. The d.c., of course, is what we want to apply to the load, while the a.c. is the ripple we want to suppress or bypass to ground. We need a series circuit, which will offer a high impedance to the a.c. and a low resistance to the d.c., and a shunt circuit with high resistance to the d.c.

and a very low impedance to the a.c. We achieve it by using either resistance or inductance for the series element and capacitance for the shunt element. The capacitor has very high resistance to d.c. and relatively low opposition to a.c., while the inductance has high impedance to a.c. and a low resistance to d.c. Thus we can bypass a good deal of the a.c. without reducing the d.c. too much. Unfortunately, it takes very bulky inductors and capacitors to do the job at hum frequencies (60 and 120 cycles). And when the hum level must be held to 60 db or more below the signal level—which means reducing the ripple to one-ten-thousandth or even one-hundred-thousandth of its value at the rectifier output, four or five filter sections are required.

This is where the VR tube can perform a valuable service. It is an ideal hum filter, and it is very much less costly and bulky than any combination of capacitors and inductors or resistors capable of equal filtering action.

The use of VR tubes as hum filters combines perfectly with their use as decoupling filters.

Amplifier "definition"

The ideal amplifier delivers an exact counterpart of the input signal to the load. It neither adds to nor subtracts anything from the *form* of the signal. An amplifier may distort a signal by subtracting some of the tonal values through frequency discrimination, or by adding harmonic distortion and intermodulation. Another addition affects the *definition* of the amplifier.

An amplifier with good definition maintains the distinctness of the individual elements of the signal. Definition in an amplifier can be compared to resolution in a camera. A camera with good resolution will show individual blades of grass and individual hairs

in a coiffure; a camera with poor resolution blurs the separate components so that they cannot be distinguished. Similarly, an amplifier with good definition reproduces the individual notes and instruments distinctly; one with poor definition will blur the individual tone elements and instruments until they cannot be distinguished separately.

Definition in an amplifier is very largely a function of transient response. An amplifier with good transient response is nonresonant, nonregenerative and nonoscillating. It is always merely a reproducer, never a generator. Unfortunately, this is much easier to stipulate than to achieve. Most amplifiers are regenerators or oscillators of the triggered type. At some point in the frequency range they are resonant, possess a feedback loop, and will break into momentary oscillation if triggered by a strong-enough impulse. These oscillations are not always audible as such in the output. They are manifested not as constant tones but as "hangover" effects, and consist of a series of echoes of the signal. They may even be pleasing to some because they give a resonant effect which sometimes simulates room resonance. But they reduce the definition of the amplifier, blurring the individual elements and instruments instead of maintaining their distinctness.

Transient oscillations

Fig. 2 shows what happens. The figure at *a* represents the wave-train of a damped (soft pedal) piano trill plotted on amplitude-time co-ordinates. There are definite valleys between the separate tones in the original signal. An oscillating or regenerative amplifier, however, will prolong each pulse with a series of spurious pulses—hangovers or echoes—which not only change the shape of the original pulse, but also

FOR
HIGH-
FIDELITY
AMPLIFIERS

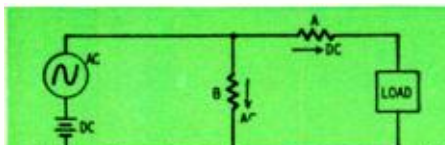


Fig. 1—Functions of series-element "A" and shunt element "B" in low-pass filter.

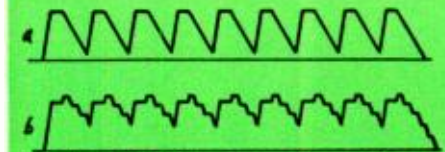


Fig. 2—(a) Original waveform of piano trill. (b) Oscillations in amplifier add "hangover" pulses to each trill cycle.

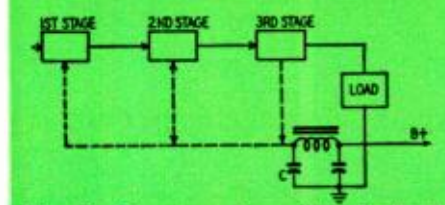


Fig. 3—Diagram of possible feedback loops in a three-stage amplifier with one B supply and no decoupling.

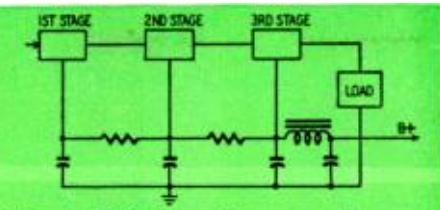


Fig. 4—R-C decoupling networks.

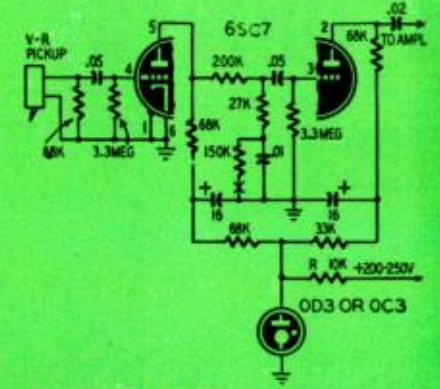


Fig. 5—Adding voltage regulation to a variable-reluctance pickup preamplifier.

fall into and partially fill the valleys between pulses. The result is indicated at *b*. The separation between pulses is no longer distinct and sharp, and the total effect is blurred. In fact, the effect is very much like that of playing the same trill undamped—that is, with the loud pedal depressed.

Moreover, if the amplifier is resonant at any frequency, it can be triggered into oscillation at this point by any strong transient regardless of its frequency. In good amplifiers the resonant points will be at the inaudible extremes of the frequency range and the oscillations themselves will not be audible. Nevertheless the oscillations will have two disastrous effects: first, they create intermodulation distortion; second, they are usually of much higher amplitude than the signal and may drive one or more stages of the amplifier into the nonlinear regions of their curves and produce violent distortion of every possible form, even at low signal levels.

To be a true reproducer, an amplifier must be as nearly nonresonant, non-regenerative and nonoscillating as possible. To achieve these qualities we make the amplifier frequency response flat away below and away above the audible range (from 10 to 100,000 cycles in good amplifiers). We also try to eliminate or reduce the bad effects of feedback loops in the amplifier.

Feedback loops are inescapable in any amplifier when several stages are fed from the same power supply. Fig. 3 is a block diagram of a three-stage audio amplifier with a common power supply and no decoupling filters. The dashed lines are the feedback loops created by the common plate-supply line. If capacitor *C* does not bypass all audio voltage on the line to ground, part of the audio voltage in the output stage will be fed back to the first and second

stages. Regeneration will occur where the feedback is in phase with the stage signal, and oscillation will start if the amplifier has a resonant point.

With 3 resistance-coupled stages or 2 transformer-coupled stages the feedback will always be in phase over some portion of the frequency range. To minimize feedback we must insert low-pass filters in the feedback loops—filters which will pass the d.c. plate currents but will bypass most if not all of the signal frequencies. Typical R-C decoupling networks are shown in Fig. 4. These will reduce feedback at normal frequencies; but adequate bypassing below 50 cycles calls for enormous values of shunt capacitance. For this reason cheap amplifiers cut off the low-frequency response very sharply at about 100 cycles.

But as we have already noted, really high-fidelity amplifiers must be designed for a pass-band from 10 to 100,000 cycles. How are we going to decouple effectively at a frequency as low as 10 cycles? One way is to use two or more power supplies. Some expensive amplifiers actually do this. A much simpler and equally effective device, is to use one or more VR tubes at appropriate points in the power-supply loop.

VR decoupling

Any regulator which holds a d.c. voltage absolutely constant, is a perfect bypass for a.c. As a shunt unit a VR tube is effective down to subaudible frequencies. The installation of VR tubes for decoupling and hum filtering is simple and inexpensive. Only one VR tube is necessary in most amplifiers. The need for decoupling and hum filtering is progressive; we need much less attenuation of hum and feedback in the final stages of an amplifier than in the input stages. By combining brute-force inductance-capacitance filters with

a single VR tube we can usually achieve almost complete hum and feedback suppression in amplifiers of five or even six stages (assuming that the final stage and the drivers are push-pull and that no interstage transformers are used).

The most effective point for a VR tube is the input stage, or the pre-amplifier for a low-level phono pickup. Fig. 5 shows how to use a VR tube with a G-E-type preamplifier. If a commercial amplifier is used, the 10,000-ohm resistor and VR tube can be inserted at the B plus-input point. If the preamp is home-built, the 16- μ f filter capacitors and 33,000-ohm series resistors can be eliminated. In any case, the 150,000-ohm resistor in the frequency-correction network can be removed. This resistor limits the bass compensation at very low frequencies to guard against motorboating. With the much better decoupling provided by the VR tube, this limitation is no longer necessary, and removing the resistor extends the effective range of the bass boost circuit.

Application to any other input circuit is just as simple. The VR tube is simply inserted in the B plus line in place of the usual decoupling network. The stage in which the VR tube is connected should be designed for a plate supply of 150 volts. Most amplifiers designed for a 250-volt plate supply will work all right with a 150-volt supply. In any case, the improved decoupling extends the low-frequency limit and a larger cathode bypass capacitor (at least 25 μ f), and a larger grid-coupling capacitor should be installed. In all cases the series resistor *R* should be adjusted so that a minimum current of 10 ma flows through the VR tube. Two or more stages may be fed by one VR tube provided the total current does not exceed 30 or 40 ma.

The addition of a VR circuit to a well-designed audio amplifier with a very wide, flat frequency range will produce a marked improvement in transient response, especially at very low frequencies. The "Golden Ear" amplifier—although transformer-coupled—will reproduce the 1/4-cycle wave of a phonograph record with an off-center hole without any tendency toward oscillation or instability. In large part this is due to the use of two VR tubes—one at the phono-preamp and one at the stage feeding the push-pull drivers. The expedient is highly recommended to high-fidelity enthusiasts and designers.

Audio amplifiers using Class AB pentodes and beam power output tubes require a regulated screen voltage for maximum output. This can be supplied by one or more VR tubes operated in series. Use tubes whose total operating voltages equal or approximate the required screen operating voltage. The 0B3 operates at 90 volts, the 0B2 and 0C3 at 105 volts, and the 0A2 and 0D3 operate at 150 volts. The VR-75 (obsolete but often available on the surplus market) supplies 75 volts. END

PUSH - PULL DRIVERS

Part IV—This circuit, the "long-tailed pair," is considered by the author to be the best of the phase-splitters.

By GEORGE FLETCHER COOPER

IN this series of four articles about the phase-splitting stage which must provide the link between a single-ended amplifier and a push-pull stage we have examined several bad circuits and two classes of good circuits. As we have seen, the single tube with a split load is good if you do not need too much drive; and the anode-follower or *see-saw* circuit gives more output, but less gain. For conventional audio work the tubes and supply voltages you plan to use will determine whether you take the single-tube or two-tube phase-splitting circuit.

There are some special jobs, though, for which these push-pull driver types are not suitable. The most important of these is when you want to go down to extremely low frequencies, or even all the way to zero frequency. The anode follower (see Part III, in the February issue) includes one coupling capacitor, so that it will not stay balanced once the capacitor starts to take control; the split-load circuit (Part II, January, 1953) has the disadvantage that the two output terminals are at different d.c. potentials. A symmetrical direct-coupled deflection amplifier for a cathode-ray oscilloscope calls for a phase splitter which provides two out-

puts at the same average d.c. potential, because any unbalanced difference will pull the undeflected spot away from the center of the tube.

"Long-tailed pair"

One phase-splitting circuit is particularly good for cathode-ray oscilloscope work. It has other uses too, but we shall come back to those after we have examined its characteristics. The circuit itself is known as the "long-tailed pair," or more prosaically, as the Schmitt cathode-coupled phase inverter. If you look at the basic circuit in Fig. 1, you will see why the name "long-tailed pair" was adopted. This circuit is related to the anode-follower discussed last month in a rather interesting way. The anode-follower circuit, you may remember, could be described simply by saying that the second tube is driven by the *difference* in the *plate-voltage* swings of the two tubes. The second tube of the long-tailed pair has its grid grounded, and the effective drive to this tube is applied at the cathode. The driving voltage is equal to the cathode resistance R_k multiplied by the *difference in plate currents* of the two tubes.

Suppose we raise the potential of grid 1 by 1 volt, causing an extra cur-

rent I_1 to flow through tube 1. The current in tube 2 will *drop* by an amount I_2 , and the cathode potential will change by $(I_1 - I_2)R_k$. This *change* is the input to tube 2, and if R_k is very large, we can have $(I_1 - I_2)$ very small and still get some drive into tube 2. In fact, we can draw Fig. 2-a, for comparison with Fig. 2-b, which is the *see-saw voltage* diagram from last month's article. If you look at Fig. 2-a you will notice that in order to get any drive at all for tube 2 it is necessary to have unequal values of I_1 and I_2 ($C_1 - R_k$ and $C_2 - R_k$). Drive for tube 2 is Og . The only way to get equal swings at the two plates is to use slightly different plate-load resistances R_{L1} and R_{L2} .

We can do some very simple calculations to see the sort of difference.

At plate 1 we have a swing of $I_1 R_{L1}$. The input to tube 2 is $(I_1 - I_2)R_k$, which gives a plate current of $gm(I_1 - I_2)R_k$ and, therefore, a swing at the plate of tube 2 equal to $gm(I_1 - I_2)R_k R_{L2}$, which is, of course, also equal to $I_1 R_{L2}$. Therefore $gm I_1 R_k R_{L1} = I_2 (1 + gm R_k) R_{L2}$, and

$$I_1 / I_2 = 1 + \frac{1}{gm R_k}$$

Since we want

$$I_1 R_{L1} = I_2 R_{L2}$$

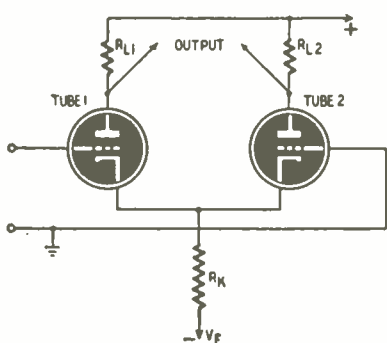


Fig. 1—Circuit of the "long-tailed pair" cathode-coupled phase inverter.

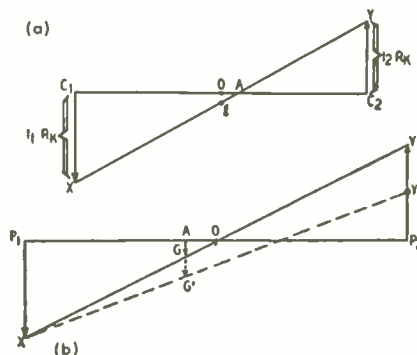


Fig. 2—(a) Current see-saw diagram of the "long-tailed pair". (b) See-saw diagram of balanced-voltage phase inverter reprinted from last month's article for comparison with balanced-current type.

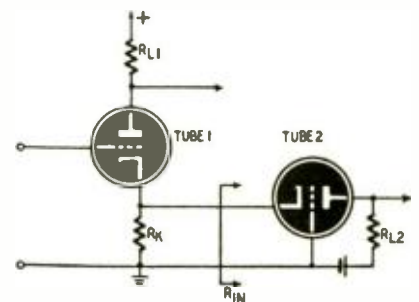


Fig. 3—"Long-tailed pair" redrawn to show grounded-grid operation of Tube 2.

we have

$$\frac{R_{L1}}{R_{L1}} = \frac{I_1}{I_2} = 1 + \frac{1}{gmR_k}$$

Typical values for this circuit are $R_k = 5,000$ ohms and $gm = 5ma/v$ (5,000 μ mhos), giving a ratio $R_{L2}/R_{L1} = 1.04$.

This means that even without unequal load resistors we get a balance correct to 4%, which is quite good.

The rigorous approach

This result, obtained by very simple reasoning, applies quite well if tube 1 and tube 2 are pentodes, though it leaves a rather tricky gap if you wonder how to bypass the screen grids right down to zero frequency. It shows that the circuit looks good, anyway. And now we come up against the main problem of the writer of technical articles: do you want it easy, or do you want it right? Sometimes the writer can put in all the mathematics—if he is French he seems to put in nothing but the mathematics—sometimes he collects a dense mass of small-print equations at the end. Usually he must tack between the Scylla of editorial condemnation and the Charybdis of long-haired readers who write and point out the smallest deviation from rigor.

My own preference is to start off with the exact mathematical solution, and then simplify. Any reader who wants to get more detail can then build up on the sound foundations I have provided. If you try to simplify *first*, you will have nothing to build on later.

It will be much easier to understand the long-tailed pair if we redraw the circuit in the form of Fig. 3. This is not as elegant and symmetrical as Fig. 1, but it is a good deal more useful. Tube 2, you now see, is a grounded-grid stage, a subject we discussed recently in RADIO-ELECTRONICS (October, 1952, issue). I shall save myself a lot of trouble by using some of the results I worked out in that article. In particular, the input impedance (R_{i2}), looking in at the cathode, is $R_{L2} + R_{p2}/1 + \mu_2$ and the gain is $(1 + \mu_2) R_{L2}/R_{L2} + R_{p2}$.

Let us look at the first stage first. The tube has a plate load R_{L1} , and there

is some negative feedback because of the unbypassed cathode resistor. If we represent the cathode circuit (R_k in parallel with the input resistance of tube 2) as R_x the gain is just $\mu_1 R_{L1}/[R_{L1} + R_{p1} + (1 + \mu_1) R_x]$ and the voltage across the cathode circuit is R_x/R_{L1} times the voltage at the plate. So if we have 1 volt at the grid of tube 1 we have $\mu_1 R_{L1}/[R_{L1} + R_{p1} + (1 + \mu_1) R_x]$ volts at plate 1, $\mu_1 R_x/[R_{L1} + R_{p1} + (1 + \mu_1) R_x]$ volts at the common cathode, which we can write as V_x , and $[(1 + \mu_2) R_{L2}/R_{L2} + R_{p2}] V_x$ at plate 2.

We want the voltage at plate 1 to be the same as the voltage at plate 2, so we put

$$\frac{\mu_1 R_{L1}}{R_{L1} + R_{p1} + (1 + \mu_1) R_x} = \left(\frac{(1 + \mu_2) R_{L2}}{R_{L2} + R_{p2}} \right) V_x$$

and $V_x = \mu_1 R_x / [R_{L1} + R_{p1} + (1 + \mu_1) R_x]$

There is one more equation, because R_x is made up of R_k in parallel with $R_{i2} = [(R_{L2} + R_{p2}) / (1 + \mu_2)]$ —so $R_x = R_k (R_{L2} + R_{p2}) / (R_{L2} + R_{p2} + \mu_1 R_k)$.

That last paragraph is tough but true. Assume the two tubes are similar and struggle with it for a while and you will come out with the equation for true push-pull balance,

$$R_{L1}/R_{L2} = (1 + \mu) R_k / R_{L2} + R_{p2} + \mu R_k$$

This doesn't look too bad, and if we assume further that we have pentodes, so that μ and R_{p2} are very large, $1 + \mu \approx \mu$ and

$$\frac{\mu}{R_p} = gm$$

we arrive at $R_{L1}/R_{L2} = gmR_k / (1 + gmR_k)$ which is equivalent to the answer given by our very simple treatment.

It is interesting to compare the exact solution with the simple one for a typical case: consider a 12AT7, with $R_p = 10,000$ ohms, $\mu = 50$, $gm = 5,000$ μ mhos and $R_k = 5,000$ ohms. We can choose $R_{L2} = 50,000$ ohms and we obtain $R_{L1}/R_{L2} = 51 \times 5,000 / 50,000 + 10,000 + (50 \times 5,000) = \frac{255,000}{310,000}$

This is about 0.825, whereas with the simple formula we had

$$R_{L1}/R_{L2} = 1/1.04 = 0.96$$

There is quite a difference between a 17% unbalance and a 4% unbalance, and obviously we are justified in adopting a more rigorous approach. Ener-

getic readers may care to consider what happens if Tube 2 ages and R_{p2} gets bigger: as R_{p2} represents only 10,000 in the total 310,000 of the numerator it cannot be a very serious factor. If μ_2 gets smaller, things are rather more complicated, because μ_2 appears in both denominator and numerator; anyway, μ_2 is more nearly constant during the life of the tube.

Oscilloscope applications

For applications in which a good stable balance is needed, a much higher value of R_k would be used. As an example, we might take $R_k = 50,000$ ohms, when

$R_{L1}/R_{L2} = 2,550,000 / 2,560,000 = 0.996$ and the unbalance is only about 1/2%. Changes in tube characteristics can only unbalance the circuit to the same limited extent, assuming that we start with correctly proportioned load resistors, so that we have a very satisfactory circuit here. But 50,000 ohms is a very long tail.

The reader who has been watching these numbers carefully may be getting a little worried. If each tube draws 5 ma there will be a total of 10 ma through the cathode resistor. All this talk of 50,000 ohms implies a drop of 500 volts across R_k , and even if we cut R_k to 20,000 ohms, we need a -200-volt supply if we are to work with the grids around ground potential. This is not a serious matter in oscilloscope circuits, because negative high-voltage supplies are generally used. In some other circuits, where the grid of tube 1 is connected directly to the plate of a preceding tube it is an advantage to have the whole tube circuit lifted up above ground. But 200-500 volts is rather high, and when an extra-large cathode impedance is needed for special high-balance jobs, special circuit tricks are usually adopted.

One very important circuit uses a pentode in place of R_k . A 6AQ5, for example, will pass 10 ma with only 20 volts on the plate, but the impedance so far as constancy of current is concerned will be very high, certainly above 100,000 ohms. This means that we can make $R_{L1} = R_{L2}$, and still have a virtually perfect balance. The form the circuit takes is shown in Fig. 4, which

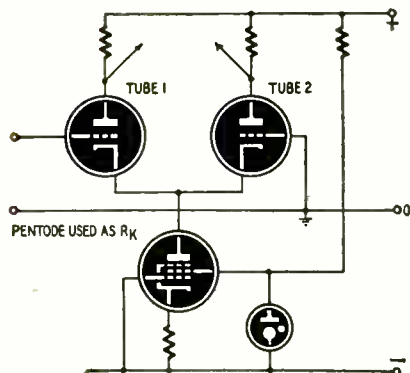


Fig. 4—A high-impedance pentode as a common cathode resistor swamps out variations in Tube 1 or Tube 2 that might unbalance the phase-inverter currents.

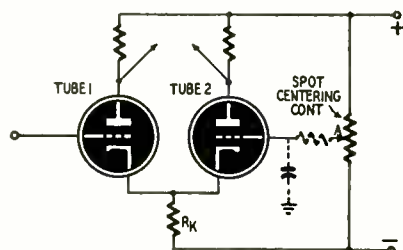


Fig. 5—When using the "long-tailed pair" to feed the balanced deflecting plates of a cathode-ray oscilloscope the grid of Tube 2 may be returned to an adjustable d.c. divider to restore the beam to the center of the scope screen.

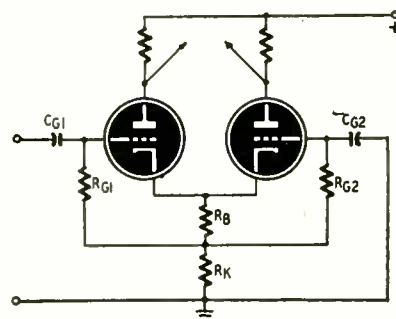


Fig. 6—One method of eliminating the negative voltage supply for the cathode return. R_k is tapped off the total cathode resistance at the desired bias point.

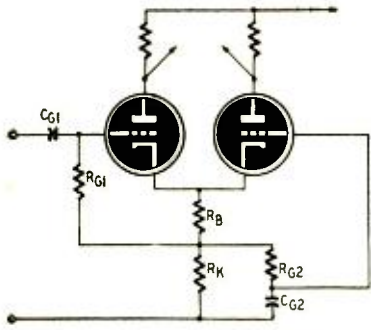


Fig. 7—The circuit of Fig. 6 redrawn to show the high-frequency shunting effect of C_{G2} , the coupling capacitor to Tube 2.

also shows a voltage-regulator tube as a screen bypass, to insure operation down to zero frequency.

Another way of providing the necessary high impedance in the cathode circuit is to use a saturated diode for R_k . The tungsten-filament diodes used as noise sources in receiver testing give full emission (saturate) at a relatively low plate voltage, and increases in plate voltage give almost no change in current. The only disadvantage in using them is that the diode current depends on the filament temperature, so that the filament current must be stabilized.

Our purpose in seeking such highly accurate balance is not to get 10.01 watts from an amplifier instead of 10 watts, but to meet the requirements of some special measuring instruments. If you look back at Fig. 1, you will see that apart from the ground connection of the grid of tube 2, the circuit is absolutely symmetrical. In fact, this ground connection is there only because we assumed a grounded input: we are really using the voltage G_1-G_2 as the input, and deriving two equal antiphase outputs from this. Suppose, however, that we connect both grids together, and then apply a signal. There will be an in-phase signal at the plates, but it will be relatively small, since the large cathode resistance R_k provides a great deal of feedback. We can easily calculate what will happen, because we can assume that each tube has $2R_k$ in its cathode and then treat one tube alone. The gain from grid to plate is $\mu R_1 / [R_1 + R_k + (\mu + 1)2R_k]$.

With a 12AT7, $R_1 = 50,000$ ohms, $R_k = 10,000$ ohms, $\mu = 50$, $R_k = 50,000$ ohms.

This gives a gain of about 0.5, so for *push-push* input the gain from grid to plate is less than unity. For *push-pull* input, applied *between* the grids instead of to grids in parallel, the gain is 30, so the balance ratio is 30: 0.5, or 60 to 1. If a pentode is used for the cathode resistor this figure can be increased still more.

This circuit is used in electroencephalography: the two grids are connected to electrodes applied to the head of the patient, and the tiny brain currents produce a *push-pull* voltage between the electrodes. Stray 60-cycle fields produce a relatively large *push-push* voltage which must be eliminated, of course,

because it would mask the brain signals even if it did not overload the final stages of the recording amplifier.

For use with oscilloscopes there are two possibilities. In the first, the two grids can be regarded as the two input terminals, and we have the feature that *push-push* voltages are discriminated against, while *push-pull* voltages are applied to the deflecting plates of the oscilloscope tube. This is excellent if you wish to work around zero voltage. But if you are interested in the variations of a voltage which is always well away from zero, this push-pull input is not very satisfactory, because the d.c. component of the input will deflect the spot away from the center of the screen. The arrangement of Fig. 5 is then more useful. The grid of Tube 2 is connected to point A, which provides a positioning voltage to bring the spot near the center of the screen. The grid of tube 1 takes the input signal, which is converted to push-pull to avoid defocusing and trapezium distortion (keystoning). A capacitor (shown in dotted lines) may be added to keep supply hum off the grid of tube 2, where it would be amplified as an ordinary signal. A resistor (also shown dotted) is sometimes added to improve the smoothing. (In some oscilloscopes the time constant of this R-C filter is so long that the spot goes on drifting long after you have taken your hand off the positioning control.

Stages of this kind can be connected in cascade if you have generous power supplies. The subject is slightly outside our present field, but you can see that if the first pair is to operate at about zero grid volts, the plates will be up at about + 100, while the cathode resistor is returned to, say, -150 volts. The second stage grids are then at + 100, so we have a 250-volt drop in the second cathode resistor (assuming this also goes back to -150 v). The second-stage plates will be at + 200-250 volts, so that the supplies needed will be +400 v, 0 and -150 v. You just apply Ohm's Law to find the resistance values.

Although this circuit is not used much for audio amplifiers, we should examine how it can be used, and in particular how we can get away from this negative voltage line. A simple and apparently symmetrical form of circuit is shown in Fig. 6. Bias is provided by R_B , which has its usual value for the tubes (about 100-500 ohms) according to the operating conditions, and the grids return to the bottom of R_B through R_{G1} , R_{G2} . The coupling resistor R_k lifts the whole group of resistors up to perhaps +100 volts, so that blocking capacitors C_{G1} , C_{G2} are needed to connect the input and to provide the a.c. ground on grid 2. This circuit is not as symmetrical as it looks, as you will see if you consider it as redrawn in Fig. 7. At high frequencies the grid of tube 2 is grounded, but at low frequencies, when C_{G2} is no longer a low impedance, the grid is returned to somewhere between ground and the top of R_k . At zero frequency, the coupling resistance is


down to R_B , which is too small to provide any satisfactory sort of balance. In practice this means that we must make $2\pi f C_{G2} R_{G2} \gg 1$ at the lowest frequency we intend to use. We also need $2\pi f C_{G1} R_{G1} > 1$ if we are to get the signal into the circuit at all. At high frequencies the only sources of trouble are tube capacitance, in particular the grid-cathode capacitance which is effectively in parallel with R_k , since grid 2 is grounded.

If you now look back at Fig. 1 you will, no doubt, admire the elegant simplicity of the circuit: just three resistors, a pair of tubes, and that little $-V_c$ sign. Every few years I come back to this point of indecision. It's a good simple circuit, but where will I get that negative supply? For special jobs, with double input, it is possible to elaborate the long-tailed pair to give a really well-balanced system, though the balance is usually not as good as you can get with a transformer. But the long-tailed pair stays balanced down to zero frequency.

I hope that in these four articles I have succeeded in making it clear that it doesn't cost any more to make your push-pull circuit really balanced. The shoddy circuits described in Part I will add to your troubles if you want to use a reasonable amount of negative feedback, and as far as I can see they amount to nothing more than a public avowal that you "couldn't care less." If an amplifier is designed on that basis I would expect it to be pretty badly constructed, too, and I should stay well clear of it. END

LOW-HUM AMPLIFIER

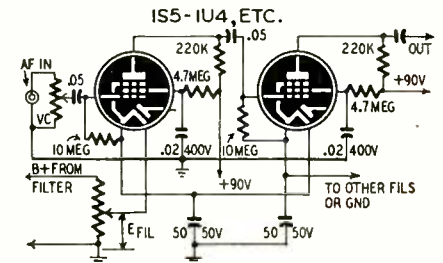
While constructing a high-gain a.f. amplifier for minute input voltages, I was faced with the problem of 60-cycle heater hum. Unable to lick the problem using 6.3-volt tubes, I switched to 1.5-volt, 50-ma, battery-type tubes, wired the filaments in series and connected them to a bleeder on the power supply. The circuit shown does all



that was expected of it. The control grids are operated with zero bias in this circuit. Fixed bias can be applied by inserting dropping resistors in the heater line and returning the grids to the point which gives the desired bias with respect to its negative heater pin. The tap on the bleeder must be adjusted so the voltage does not exceed the sum of the voltage drops across the tubes. If biasing resistors are used this voltage must be raised accordingly.—David Simon.

Volume Expanders and Compressors

By ROBERT F. SCOTT

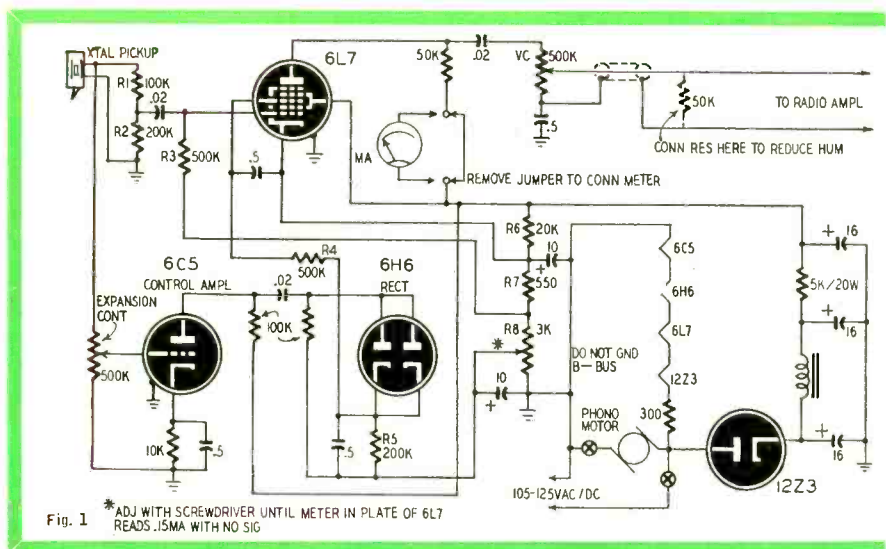

AUTOMATIC volume expanders (also called contrast expanders) were developed in an effort to restore the original dynamic volume range to broadcast and recorded music which had been limited or compressed to prevent overmodulating the transmitter or overcutting the record. While FM broadcasting and LP and 45 r.p.m. records have reduced the need for expansion (little or no compression is used at the studios), the technician still runs across the circuits in older or special equipment. Commonly used volume expanders are of three basic types, namely: variable-gain, constant-gain variable-output, and inverse-feedback. An example of the variable-gain type is shown in Fig. 1.

Ansley Phantom Conductor

Fig. 1 is the circuit of the Ansley model DA-PC *Phantom Conductor*, a volume expander similar to the one which was described in several editions of the RCA Receiving Tube Manual. This unit is designed for use between a crystal pickup and audio amplifier.

The variable-gain expander tube is a 6L7 pentagrid mixer, a tube designed for superheterodyne circuits having separate oscillators and for other applications where dual gain control circuits are desired in a single tube. In audio applications, grids 1 and 3 may be used as separate control grids. The amplification of a signal applied to either grid can be controlled by varying the bias voltage applied to the other grid.

The full output of the pickup is developed across the expansion control and R1 and R2 in series. A portion of the a.f. signal is tapped off the junction of R1 and R2 and is applied to the signal grid (grid 1) of the 6L7. Operating voltages for cathode and signal grid are taken from taps on a voltage divider consisting of R6, R7, and R8. The bias voltage for the injector grid (grid 3) is obtained from a movable slider on R8 and is applied to it through R4 and R5 in series.

The signal appearing across the expansion control is amplified by the 6C5 control amplifier and then rectified by the 6H6. When the 6H6 conducts, it develops a positive voltage across R5 which adds to the fixed bias to reduce the potential difference between grid 3 and the cathode and to increase the amplification of the signal applied to grid 1.

The tap on R8 is adjusted so the 6L7 plate current is 150 microamperes with no signal input. The setting of the expansion control determines the amount of signal applied to the 6C5 and subsequently, the amount of dynamic d.c. bias applied to grid 3 of the 6L7.

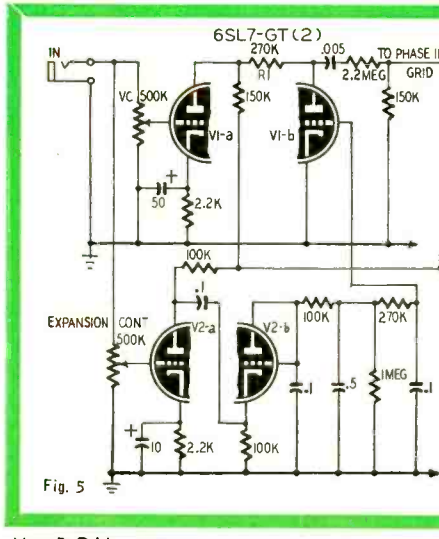
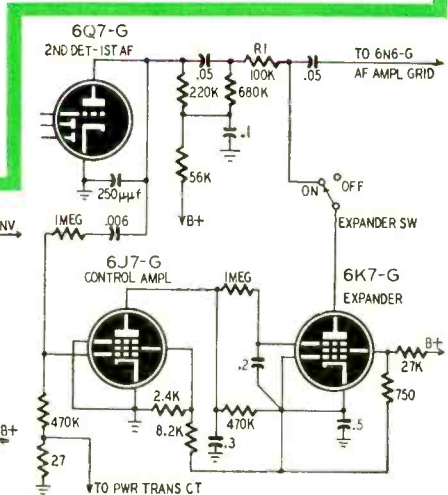
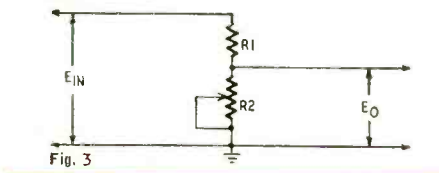
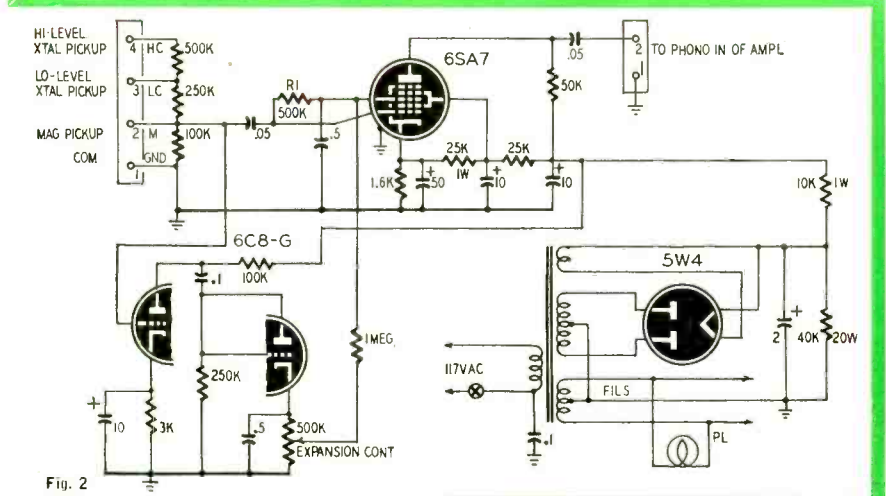


Fig. 1—The Ansley *Phantom Conductor*. Fig. 2—The Bogen model SLX volume expander. Fig. 3—Equivalent circuit of a constant-gain expander. Fig. 4—An early Spartan circuit. Fig. 5—Masco's constant-gain volume-expander circuit.

Bogen model SLX expander

The Bogen model SLX expander shown schematically in Fig. 2 is fundamentally similar to the unit shown in Fig. 1. A 6SA7 replaces the 6L7 as the variable-gain amplifier. One triode of the 6C8-G replaces the 6C5, the other has its plate and grid strapped together as a substitute for the 6H6.

In this unit, the signal voltage is applied to grid 1 of the 6SA7 and to the control grid of the triode section of the 6C8-G. The dynamic bias voltage from the rectifier is applied to grids 1 and 3 to provide a greater control over the available amplification. The 0.5- μ f capacitor bypasses the a.f. voltage to ground so it will not reach grid 3. The 500,000-ohm resistor R1 isolates the grids and prevents the a.f. signal on grid 1 from being bypassed to ground.

Single-ended variable-gain volume expanders produce a peculiar form of distortion when the incoming signal is modulated by the ripple and harmonic content of the dynamic bias developed by the control rectifier. Ripple and harmonics cannot be readily removed from the bias signal by filtering because this increases the time constant of the circuit to the point where the expander will not follow staccato passages.

To eliminate this effect and to permit the use of a short time constant, Amplifier Corp. of America has used a circuit which is basically a push-pull version of the single-ended expanders in Figs. 1 and 2. A push-pull audio signal is applied to the control grids in each of the push-pull variable-gain tubes and the dynamic bias is applied to the tubes in parallel. In this way, transients, ripple, and harmonics are balanced out because they are in phase on the grids and out of phase in the plate circuit. A modern version of the push-pull expander is used in the model 100-DC amplifier produced by Amplifier Corp. of America.

Constant-gain expanders

In a constant-gain variable-output expander, the output of a constant-gain stage is applied to a voltage divider in which one element is variable from zero to infinite resistance. The principle of this very interesting type of expander is illustrated by Fig. 3. The input voltage (from a constant-gain source) is applied across a voltage divider consisting of R1 and R2. The output voltage E_o can be varied from approximately E_{in} when R2 is infinite to zero when R2 is zero. In practice, R2 is replaced by the plate-cathode resistance of a vacuum tube. A control amplifier and signal rectifier supply dynamic bias to the tube represented by R2.

Fig. 4 shows the volume expander used in the Sparton 827X, 997X, 1167 and similar receivers, which were manufactured about 15 years ago. A part of the voltage output of the 6Q7 is fed into the grid of the 6J7 expander-amplifier (control tube) which is biased to cutoff by returning its grid to the center tap on the power transformer.

The plate of the 6J7 is coupled

directly to the suppressor grid of the 6K7 expander stage through a 1-meg-ohm resistor. The control grid of the 6K7 is tied to the suppressor through a filter consisting of 0.2- and 0.3- μ f capacitors and a 470,000-ohm resistor. The time constant of this filter network permits only very large changes in 6J7 plate current to affect the grid voltage of the 6K7.

The 6K7 and 6J7 are connected in series across the B supply. The 6J7 plate receives much of its voltage from the 470,000-ohm resistor connected to the 6K7 cathode. The voltage drop across this resistor biases the suppressor of the 6K7 expander tube.

Since the 6J7 expander amplifier is biased to cutoff, a fairly large signal must be applied to its grid to produce an appreciable change in plate current. With low signals, the 6J7 remains cut off, and there is no voltage drop across the 470,000-ohm plate resistor. Since there is no voltage drop across the resistor, the 6K7 suppressor is at cathode potential and the tube conducts heavily. Under these conditions, the plate-cathode resistance of the 6K7 is low compared to R1 and much of the output of the 6Q7 is lost in the voltage divider consisting of R1 in series with the plate-cathode resistance of the 6K7.

On loud passages, the 6J7 draws heavy current and the voltage drop across the 470,000-ohm plate load resistor is sufficient to place a heavy bias on the suppressor of the 6K7. This increases the plate-cathode resistance of the 6K7 and permits a greater voltage to be fed to the grid of the 6N6 a.f. amplifier.

Masco constant-gain circuit

Fig. 5 shows a simpler version of the variable-output constant-gain expander circuit, as used in recent Masco amplifiers. V1-a and V2-a are conventional voltage amplifiers. V2-b is the bias rectifier, and V1-b is the expander tube whose plate-cathode resistance is represented by R2 in Fig. 3.

When the signal applied to the grid of control amplifier V2-a is low, the dynamic bias voltage developed by V2-b is not high enough to cause a substantial increase in the plate-to-cathode resistance of V1-b. The resistance of V1-b is low and a large part of the signal developed in the plate circuit of V1-a is dissipated across R1. When a strong signal reaches the grid of V2-a, the dynamic bias reduces the plate current and increases the internal resistance of V1-b so that a greater portion of the output of V1-a reaches the grid of the following stage. The attack and release times of the expander are determined by the charge and discharge time-constants of the capacitors connected between the plate of the rectifier V2-b and the grid of V1-b.

Inverse-feedback expanders

If inverse feedback is applied to one or more stages in an amplifier, the gain of these stages may be varied by varying the feedback voltage. Fig. 6 is the diagram of the Thordarson T-31W11

and T-31K11 audio amplifiers designed for use with a radio tuner. These units use an inverse-feedback type of expander.

The output of V1-a is applied simultaneously to the variable-gain stage V1-b and to control-voltage amplifier V2-a. V2-b is a half-wave shunt rectifier connected to develop a positive output voltage. This voltage is filtered by R1, R2, and C1 and fed to the parallel grids of V3, the feedback control stage, which is initially biased to cutoff by a positive voltage on its cathode taken from the 6B4 bias resistor.

The cathode of V1-b is unbypassed and its grid is returned to a point on the cathode biasing resistor. This causes degenerative feedback which reduces the gain of the stage to a level considerably below that which would be obtained without feedback. The amount of feedback depends on the a.c. cathode impedance of the stage.

The plate-to-plate impedance of V3 is reflected into the secondary of T1 which parallels the cathode resistance of V1-b. When V3 is cut off, its plate-to-plate impedance is so high that it has little or no effect on the cathode impedance of V1-b.


When the positive dynamic bias voltage on the grids of V3 reaches a point which permits conduction, the plate-to-plate impedance drops. Since this impedance is in parallel with the cathode impedance of V1-b, the amount of cathode feedback decreases and the gain of V1-b rises.

The grids of V3 are fed in parallel and the plates work in push-pull. In this way, the feedback control stage effectively eliminates thumps and transients which would normally be caused by rapid rises in the dynamic bias voltage.

Fig. 7 shows another Thordarson inverse-feedback expander circuit. In it we have a two-stage variable-gain amplifier with a 25-db feedback loop (R1, R2, and C1) connected between the plate of V2 and the cathode of V1. The secondary of the feedback control transformer is connected between ground and the junction of R1 and R2 to form a T network.

The control amplifier circuit is similar to that used in Fig. 6. However, this circuit was used in a recording-playback amplifier so it incorporates volume compression as well as expansion. The control amplifier V3-a is connected to the phono-radio input when used as an expander and to the second variable-gain stage when used as a compressor. This switching is handled by section S1-b of the EXPAND-COMPRESS switch. Switch sections S1-a, S1-c and S1-e reverse the polarity of the rectifier and cut in separate filter circuits for compression and expansion.

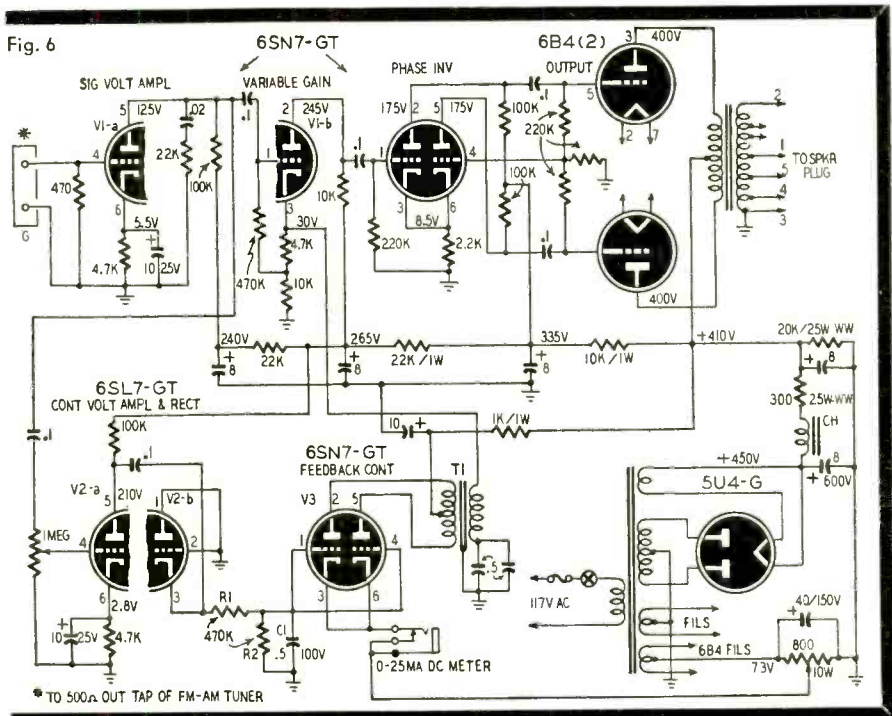When the switch is set for expansion, the rectifier V3-b develops a positive control bias and V4 is biased to cutoff. When the input signal level is low, little or no voltage is developed by the control rectifier and the plate-to-plate impedance of V4 is high. This high impedance is reflected into the secondary of T1,



where it forms a high-impedance shunt path in the inverse-feedback loop.

A sudden rise in signal voltage produces a high positive bias voltage at the output of V3-b. The positive voltage on the grids of V4 causes the plate-to-plate impedance to drop and lower the impedance reflected into the secondary of T1. This decreases the impedance of the shunt leg of the T, reduces the voltage fed back to the cathode of V1 and allows the gain to rise.

When the circuit is used as a volume compressor, the cathode biasing voltage across R5 limits the total plate current of V4 to about 16.5 ma and keeps the plate dissipation just within its maximum permissible value. The high plate current results in a very low plate impedance being reflected into the shunt leg of the T feedback loop. This reduces the voltage being fed from the plate of V2 to the cathode of V1 so the amplification of V1 and V2 is about normal.

When the audio signal rises above a given level, V3-b develops enough *negative* bias voltage to reduce the plate current and increase the plate-to-plate impedance of V4 and the impedance that is reflected into the shunt leg of the feedback loop. The increase in the shunt impedance increases the feedback voltage and causes a corresponding decrease in the gain of V1.

The attack-time of the compressor is about .03 second and the decay time is 0.25 second. This compares favorably with the 0.25-second attack and decay times of the expander circuit. The decay or *hangover* time of the expander circuit can be increased by replacing the 500-000-ohm bleeder resistor with a higher resistance.

A 1,000-ohm resistor is switched into the circuit to replace the secondary of T1 when the EXPAND-COMPRESS-NORMAL switch is turned to NORMAL.

Lamp-operated expander

Fig. 8 shows the novel inverse-feedback volume expander circuit used in the Silvertone model 8160 audio amplifier. Inverse feedback for the cathode of the driver stage is obtained from a voltage divider (R1 and R2) across the secondary of the output transformer. R2 is paralleled by two type 47 pilot lamps in series. When the signal level is low, there is comparatively little voltage across the lamps and their resistance is low enough to practically short-circuit R2 and permit maximum voltage to be fed back into the cathode of the driver stage. Loud passages increase the voltage in the transformer secondary and cause the lamps to heat. Their resistance rises and decreases the amount of feedback applied to the driver cathode. END

Fig. 6—The schematic diagram of the Thordarson model T-31K11 and T-31W11 amplifiers using an inverse-feedback type volume expander. Fig. 7—Another adaptation of the Thordarson inverse-feedback expander. Fig. 8—A lamp-operated type of inverse feedback volume expander used in Sears Roebuck Silvertone type 8160 audio amplifier.


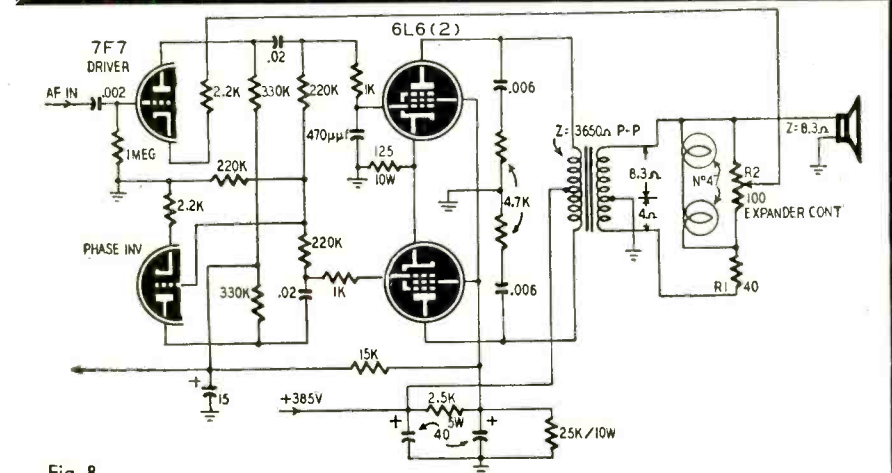
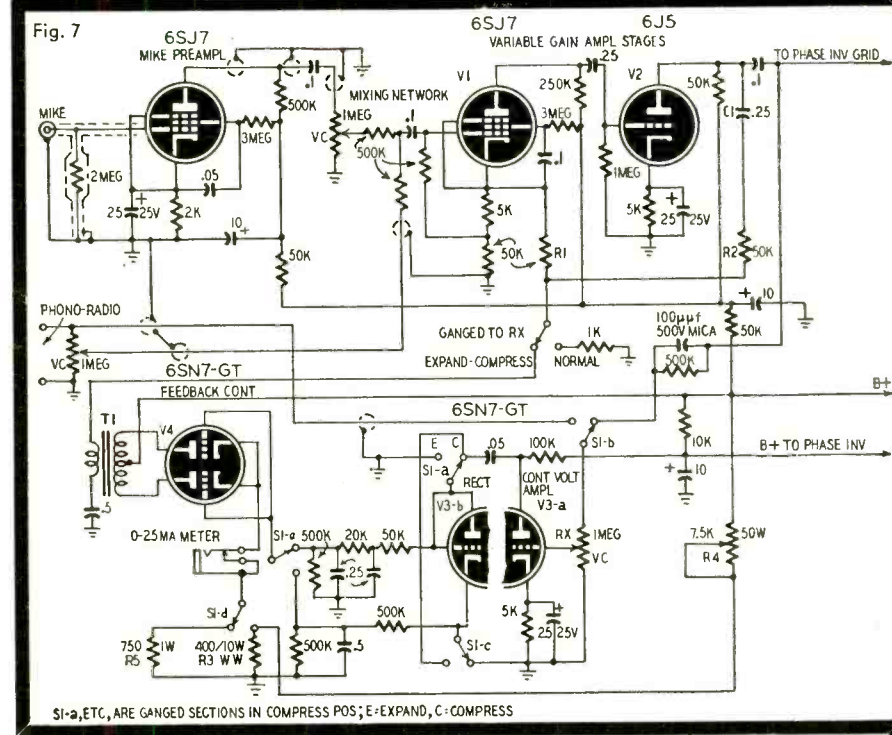


Fig. 8
MARCH, 1953

TV COMES OVER THE MOUNTAIN

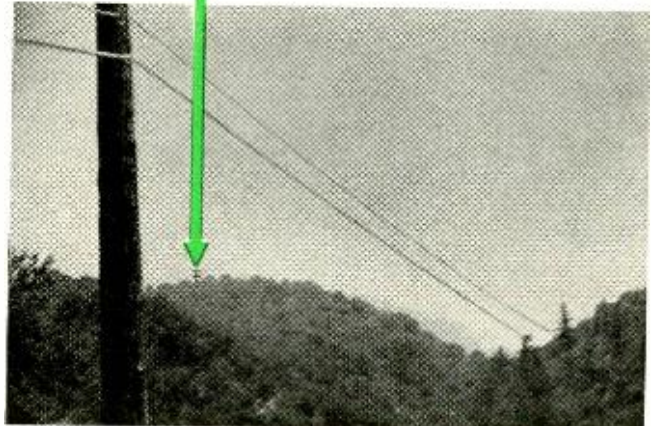Distribution
antenna systems
are critical, but
“technical sense”
can make them work



Part of the transmission line. Arrow points at antenna.

By DOUGLAS W. STEPHENS

WITH the surging wave of television station construction and installation, which will eventually give us more than 1,900 new transmitters, TV will be brought to many who have before been without this new wonder of our age.

But, because TV, unlike radio, will not go up, over, or around mountains, hills, or even large buildings, many new problems are encountered.

In towns which are large enough to support elaborate layouts and in other areas where the expense of coaxial cables, aerial towers, master amplifiers, and distribution units can be borne by large groups, the problem presented will be only one of engineering.

The television lessons learned by residents of Mount Baldy, a resort community deep in the Sierra Madre of Southern California, may be helpful to many small groups living in locations where TV reception is hindered by geographical reasons and where funds available are limited because of the size of the group.

This picturesque mountain resort is situated in a deep canyon at an elevation of 4,500 feet, a scant hour drive from the heavily populated Los Angeles area.

At first glance the TV problem at Mount Baldy did not look difficult. Mount Wilson, the site of all seven transmitters for the Southern California area, was only 25 miles away. But when Cecil May and E. Leslie, full-time residents, tried out antennas on their cabin roofs, they found that Mount Sunset and Lookout Peak, towering 3,000 feet above the valley, blocked off the Mount Wilson transmitters. Channels 4 and 5, full of snow and ghosts,

could be viewed by pointing the antennas toward 9,000-foot Mount Ontario to their rear, but as the signal bounced from one peak to the other, back and forth across the valley, the picture was far from satisfactory.

Hearing that some residents at the lower end of the valley could bring in TV signals over a saddle connecting Sunset and Lookout, these men conceived the idea of putting an antenna on the top of Signal Rock across the stream and to the back of their cabins 2,500 feet up the steep side of the mountain. Here Mount Wilson could be seen over the saddle. The lower valley group, however, was situated closer to the saddle, and the line from their antenna was less than 1,500 feet long. As the distance from the antenna on Signal Rock to the last cabin on the line was close to 4,500 feet, the cost of engineering such a project with coaxial cables, 200-foot towers, large amplifiers, and other equipment such as Panther Valley used, would be prohibitive.

The problem then was to find an *inexpensive* way to bring the signals down the mountain. Finding two other cabin owners, Jack Fountain and Mr. Garrison, who also wanted television, the four put up \$120 each to purchase materials.

Four V-cone antennas in a stacked array were installed on the summit of Signal Rock. Fifteen feet of 300-ohm flat ribbon line was used to connect the antenna to two No. 14 insulated copper wires which were run, 12 inches apart, down the mountain, attaching the wires enroute to trees with insulators on wood cross-bars. Across the stream the line ended at the junction, a tree centrally

located to the cabins. Four separate 330-ohm flat lead-in lines were run from this point to the cabins.

Reception fair to middling

With this long setup, the Baldy men found channels 4 and 5 came in from fair to good, while channels 2 and 9 could be viewed occasionally late in the evening. But even at best there were heavy ghosts on these channels, the reception was subject to every whim of the weather, and the sets interfered with each other. There was no picture on channels 7, 11, and 13.

This was the situation from November 1951 until March 1952, when a heavy, wet snow broke down the 300-ohm flat leads connecting the cabins with the junction. Viewing the breakdown, the group decided to consult Roger Howell, owner of the Reliable Radio and TV Service Co., at Long Beach, 50 miles away. Howell was an old-timer in radio and television, having built one of the first television sets, in 1931.

Realizing the limited financial structure of the undertaking, Howell came up to Mount Baldy and with Jack Fountain and Leslie climbed Signal Rock to the antenna. This trip, 2,500 feet almost straight up through snow and thick underbrush, took several hours. On reaching the summit, Howell found all four antennas were hooked up in such a manner that they were working out of phase and the connections were badly corroded. As they had no way of soldering, they scraped the wires, reattached them in the conventional parallel-series hookup—which properly harnessed the stack so each antenna worked in phase with the

RADIO-ELECTRONICS



Jack Fountain, in the picture above, resolders the transmission line with the assistance of a split coffee can.

Right, above—Snowy picture received before soldering the antenna; below—moving parallel lines cleared up ghosts.

others—and taped the connections. Jack Fountain took the hard way down, following the line, taking up the slack where the heavy snow had stretched it and repairing it in one place where it had been broken.

Nothing else could be done for a couple of weeks until the snow melted. In the meantime, four other cabin owners joined the group, each new man putting up another \$120. With this additional money the group bought enough 450-ohm Gonset line to run from the junction to the eighth house, each member attaching to this main line with 300-ohm flat lead. Howell estimated the No. 14 line down the mountain being a foot apart would have an impedance of about 750 ohms. To compensate for this, he advised tapering the last few feet of the No. 14 line before it joined the Gonset at the junction.

This improved the pictures so that channels 4 and 5 came in with only a slight ghost, and channel 2, though not quite as good, was satisfactory. There was not too much snow on these channels, but only sound was present on 7, 9, 11, and 13. However, there was a great deal of set interference and the reception was bad in the daytime.

As there was still money in the treasury, Howell installed a booster amplifier (amplifying the signal 30 db) 2,000 feet down the mountain from the antenna where a near-by cabin could be tapped for power. Four distribution boxes were put in the line at the cabins, two lead-in lines coming out of each box. This improved the pictures already received and eliminated set interference. However, there was a loss of 3 db on the low channels and 6 db on the

high channels at each box. This resulted in a poorer picture being received as the signals moved down the line until at the last two sets there was a loss of 12 db on the low channels and 24 db on the high ones. Howell advised Jack and Leslie to check the main line and the connections at the antenna. Lower channels, he told them, would come in even though there were great signal losses on the line, but if there were any losses due to unsoldered joints or other causes, the high channels would be held back.

Cleaning up the line

On climbing the mountain, the two men found the connections at the antenna corroded. Inserting new 10/32 brass bolts at all eight connections, they attached Gonset between the antenna and the No. 14 wire, replacing the 300-ohm line at that point. The Gonset and No. 14 wire connection was soldered and the eight connections at the antenna were sprayed with Krylon plastic spray to prevent further corrosion.

On following the line down the mountain—a difficult descent through heavy brush and down steep cliffs—Leslie noticed several places where the No. 14 wire had been wound around insulators to tighten the line. As Howell had warned them that all loops in the line would result in a weaker signal (acting as r.f. chokes), they straightened these out and soldered all connections that had previously been taped. This last was done by cutting a slot in either side of a coffee can and slipping it over the wire to protect the soldering flame from the wind.

When they got back to the first cabin they found they could bring in all channels except 7 with very little snow and practically no ghosts. Channel 7 was too weak for good viewing. Checking the line from the junction, they found that the lead from the first box ran parallel to the main Gonset line and only a few inches below it for 75 feet before going to the first cabin. Paralleling of lines for such a distance put the line out of phase. To correct this, they raised the Gonset on the pole and moved the lead-in four feet away and out of parallel to the Gonset. This strengthened channel 7, but when they checked the other sets down the line, they found signals were progressively weaker until at the last set, channels 7, 9, and 11 were too weak for good viewing. As there were two more cabin owners who wanted television, \$120 was collected from each, and another large amplifier (30 db), like the one on the hill, was put at the junction and a distribution box was installed to take care of the two new members. This resulted in clear pictures all down the line on channels 4, 5, 11, and 13. Channels 2, 7, and 9 were not quite as good as the others, showing slight ghosts and snow. It is hoped to run Gonset later all the way up to the antenna and thereby strengthen the signals on these last three channels.

The story of Mount Baldy proves that by taking advantage of the skilled knowledge and modern equipment available at their local distributors, small groups, even though located in so-called blind TV areas, can bring the wonders of television into their homes without overtaxing the family budget. END

Part I

How to overcome the inherent circuit characteristics that limit h.f. response

Design Data

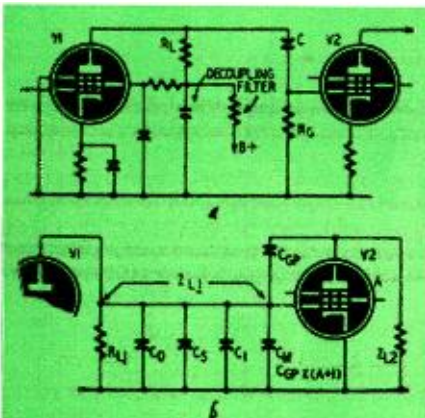


Fig. 1

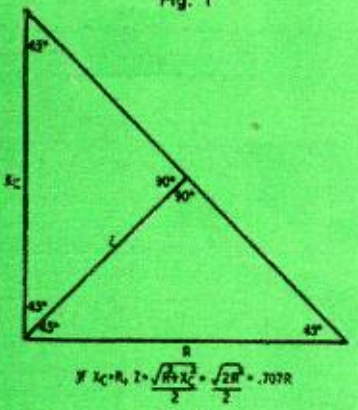


Fig. 2

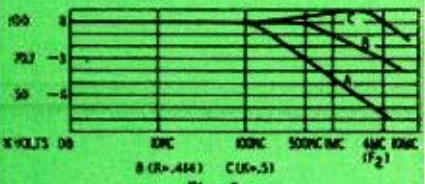


Fig. 3

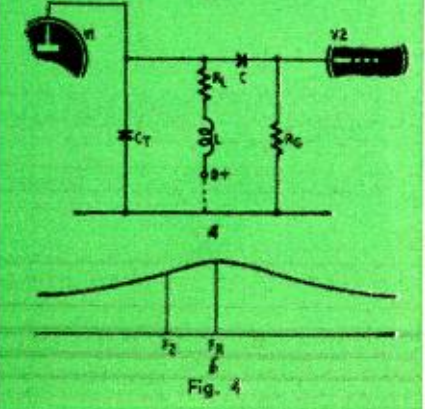


Fig. 4

MANY present-day applications of electronic equipment call for uniform amplification over a very wide range of frequencies. The video amplifier in a good television receiver must pass all frequencies from 30 cycles to 4 mc with equal gain. Laboratory oscilloscopes must be able to reproduce frequencies from 0 cycles (pure d.c.) to 10 mc and higher, and other types of equipment cover even wider frequency ranges.

Ordinary amplifier stages cannot handle these wide ranges. Special circuits are required. This series of articles will try to reduce to simple terms the complete design procedure for wide-range amplifiers.

To begin with, let's take a look at a typical R-C-coupled amplifier, and some of its shortcomings. Fig. 1-a is a typical pentode voltage-amplifier circuit. With parts values normally used in audio circuits (see *RCA Receiving Tube Manual RC-16*, pages 246 to 261), the response will be substantially flat from about 100 cycles to 15,000 cycles. This is nowhere near the response required of a video amplifier. What causes this drop in gain below 100 and above 15,000 cycles?

At the low end the major factor responsible for this is the grid-to-plate coupling capacitor C. This capacitor and R_i form a voltage divider across the output of V1. The reactance of the capacitor increases as the frequency is lowered

$$X_c = \frac{1}{2\pi FC}$$

thereby reducing the signal voltage available at the grid of V2. The V1 screen- and cathode-bypass capacitors and the B+ decoupling filter also affect the low-frequency response. At the moment, though, we are more interested in what happens at the h.f. end of the amplifier response curve. The low end will be taken up in full detail later in this series.

Fig. 1-b is the equivalent circuit of

the amplifier at high frequencies. (Coupling-capacitor C can be omitted because its reactance at high frequencies is so low that it can be considered a dead short.) The loss in gain at this end is caused by the combined shunting effect of all the capacitances shown. C_0 is the output capacitance of V1; C_s is the total stray capacitance to ground of all the components and wiring except the tubes; C_i is the input capacitance of V2; and C_M is the Miller-effect capacitance of V2. (When a tube operates as a grid-to-plate amplifier, the input capacitance is increased by $C_{gp}(A + 1)$, where C_{gp} is the grid-plate capacitance, and A is the tube gain. This comprises what is known as the Miller effect. In triodes, which have relatively high grid-plate capacitance, and very-high-gain pentodes, the Miller-effect capacitance is large. In low-gain pentodes the effect is almost negligible.)

Since these capacitances are all in parallel, their total C_T is found by simply adding them together:

$$C_T = C_0 + C_s + C_i + C_M$$

The shunting effect of C_T across R_i decreases the output voltage as the frequency rises. When the reactance of C_T is equal to the resistance of R_i , the net load impedance Z_{L1} will be $0.707 R_i$ and the output voltage will be reduced by the same amount, or 3 db. See Fig. 2.

One way of reducing this effect is to use a smaller value of R_i . The equation for the gain of a pentode ($A = gm \times Z_{L1}$) shows that the maximum gain of the stage will be reduced, but in this case, flat frequency response is much more important than gain.

In the actual design we must first decide what tubes we want to use. A point of caution here: The tubes selected must have high gm and low interelectrode capacitances. Types like the 6AC7, 6CB6, and 6AH6, were designed especially for this application. For the output stage, types 6AG7, 6CL6, or 12BY7 are recommended. The average gain per stage will be rather

Fig. 1—(a) Typical R-C coupled pentode amplifier stage discussed in the text. (b) Equivalent circuit of the amplifier showing circuit capacitances that affect the response at high frequencies. Fig. 2—Impedance diagram for resistance and capacitive reactance in parallel. Fig. 3—Response with and without compensation. Curve A shows response without shunt peaking. B and C show improvement with different peaking-coil factors. Fig. 4—(a) Inserting a peaking inductance L in the load circuit cancels the shunting effect of C_T . (b) Resonating the circuit at a frequency above F_0 increases the high-frequency response of the amplifier stage.

ON VIDEO AMPLIFIERS

By ALAN G. SORENSEN

low. Decide what total gain you require and what tube line-up you want to use. For demonstration we will assume a total gain of 100 and use a 6AH6 followed by a 6AG7.

The next step is to find the shunt and stray capacitances. A tube manual will be needed here. According to the manual, the output capacitance of a 6AH6 is 2 μmf , and a 6AG7 has an input capacitance of 13 μmf . So, in substituting numbers for letters in the equation, C_0 and C_1 will be 2 and 13 μmf , respectively.

C_s includes the capacitance to chassis of the wiring, sockets, and components. Keep this capacitance as small as possible, by using low-loss sockets, and point-to-point wiring, and mount the parts up off the chassis. A perpendicular parts layout is best. Or even a nonmetallic chassis-strip. C_s is much too small to be measured easily. For the time being we'll estimate it at 10 μmf . In order to find C_M we must first know the gain of V2.

According to the tube manual, a 6AG7 has a transconductance of 11,000 μmhos (.011 mhos), and a grid-plate capacitance of .06 μmf . We will assume the 6AG7 plate-load impedance (Z_{L1}) is a resistance of 3,000 ohms. Then the gain of the 6AG7 is

$$A_2 = g_m \times Z_{L1} \\ = .011 \times 3,000 \\ = 33$$

The Miller-effect capacitance is

$$C_M = C_{gp} \times (A + 1) \\ = .06 \times (33 + 1) \\ = .06 \times 34 \\ = 2.04, \text{ or approximately } 2 \mu\text{mf}.$$

Then $C_T = 2 + 10 + 13 + 2$, or 27 μmf .

This value of 27 μmf is the *estimated* total shunt capacitance C_T . Now we can proceed to find the correct load resistance R_L .

As mentioned earlier, the response of the amplifier will not begin to drop off noticeably until the reactance of C_T equals R_L . R_L must have a value that will keep the response up to at least the 70.7% point at the highest frequency the amplifier is expected to handle without discrimination. This frequency is called F_2 , and if the circuit we are working on is a television video amplifier, it would have a value of about 4 mc. R_L , then, must be equal to the total shunt reactance X_C at 4 mc.

With C_T in μmf , and F_2 in mc, we use this formula:

$$X_C = \frac{1.59 \times 10^5}{F_2 \times C_T} \\ X_C = \frac{1.59 \times 10^5}{4 \times 27} \\ X_C = 1,472 \text{ ohms} \\ R_L = 1,472 \text{ ohms}$$

The nearest standard RTMA values are 1,300 ohms and 1,500 ohms. There will be only a slight difference in gain between the two, and in a conservative design it would be better to choose the lower value.

Now we can find the maximum gain of the 6AH6 stage ($A_1 = g_m \times Z_{L1}$). The tube manual gives the gm of a 6AH6 as 9,000 μmhos , and Z_{L1} is 1,300 ohms.

$$A_1 = .009 \times 1,300 \\ = 11.7$$

Checking results

If we now set the circuit up for an operating test and measure the actual frequency response, we find that instead of being flat all the way out to 4 mc, the response begins to drop at only 500 kc. See Fig. 3. Apparently, a low-value load resistor was not the complete answer to our problem. What we need is a means of *cancelling* the effect of C_T .

We know that inductance and capacitance have opposite characteristics. If we insert a small inductor L between the load resistor and the B supply, we create the broadly tuned parallel-resonant circuit shown in Fig. 4-a. The impedance of a parallel-resonant circuit rises as we approach the resonant frequency. If we choose a value of L that will resonate with C_T at a frequency F_R somewhere above F_2 , the impedance of the load circuit will increase as the frequency rises and will compensate for the original drop in response. See Fig. 4-b.

This system is known as *shunt peaking*. L can be varied to give flat response to F_2 , or even raise the output at that frequency. But the value of L must be held within certain limits to avoid excessive phase shift.

When the load of an amplifier contains either inductive or capacitive shunt reactance the input and output voltages will never be exactly 180° out

of phase. In the mid-frequency range, where the reactances have negligible effect, the phase shift will be practically 180°, but at the high-frequency end, where capacitive reactance begins to dominate, the output voltage will be shifted more than 180°. At the low end, inductive reactance shifts the output voltage less than 180°.

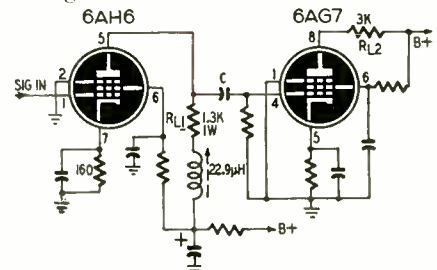


Fig. 5—Final interstage circuit of the video amplifier with values derived from the text for flat response to 4 mc.

In a TV receiver with excessive phase shift, a low-frequency video component which follows immediately after a high-frequency component may actually reach the picture-tube screen first. This gives pictures a smeary quality.

The ratio between the peaking inductance L and the shunt capacitance C_T determines this phase shift. Various ratios (K) have been worked out for specific applications. For ideal phase characteristics, at the expense of a slight drop in response, K should have a value of 0.34. Values of K above 0.414 introduce a peak just below F_2 . A good compromise for a video amplifier is to use a K value of 0.5. This gives a rise of about 3% just below F_2 .

To find L in μH , where C_T is given in μmf we use the formula:

$$L = K \times C_T \times 10^{-9} \cdot (R_L)^2$$

In our sample problem, taking $K = 0.5$ we have:


$$L = 0.5 \times 27 \times 10^{-9} \times 1,300^2 \\ = 22.9 \mu\text{H}.$$

If the peaking coil L is wound on a small slug-tuned coil form, its inductance can be adjusted to the exact value.

Fig. 5 is the final circuit. The components which have not been given values do not affect the high-frequency response. These parts control the low-frequency response and will be dealt with in Part II of this series.

TO BE CONTINUED

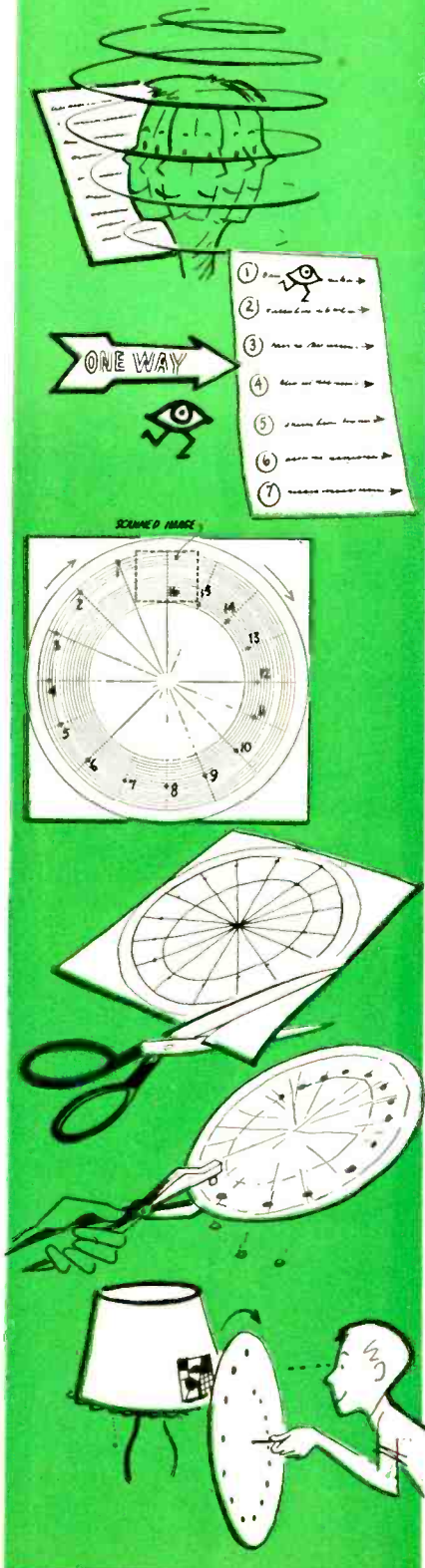From the original "La Télévision? ... Mais c'est très simple!" Translated from the French by Fred Shunaman. All North American rights reserved. No extracts may be printed without the permission of RADIO-ELECTRONICS and the author.



TELEVISION?

...it's a cinch!

By E. AISBERG

Second Conversation—
The Nipkow Disc

Our hero's dizzying adventure

Ken—Don't bother telling me what you're trying to do, Will. Either you're practicing to become a whirling dervish, or TV has you going around in circles!

Will—Wrong on both counts, Ken! I'm just trying to read without having to jerk my eyes back from right to left at the end of each line.

Ken—I know I'll regret asking, but why?

Will—Because I've been thinking about the way a scene is scanned in television. You remember, the last time we talked you said it was like reading a book—line by line. But when you think of how fast the TV camera has to read, it seems there ought to be some way to save the waste of time getting back from the end of one line to the beginning of the next. So, when I finish one line, I spin rapidly round so my eyes fall on the beginning of the next one without having to snap back from the end of the last!

Ken—Bright idea, but I don't think you're going to save much time that way. You *can* get pretty dizzy, though! But you might be interested to know that your continuous-scanning method was the one they used in most of the early mechanical television systems.

A little geometry

Will—I'd like to hear a little more about some system that really was used! All you've told me about "scanning" and "image analysis" so far has been pretty much up in the air. But just how do you "explore successively the elements of the image" in real live television?

Ken—I hadn't figured on telling you how mechanical television worked, because it's been abandoned entirely in favor of electronic methods. But maybe you'll be able to understand the more advanced systems better if we start in with the simplest—and the oldest—system: the Nipkow disc!

Will—The Nipkow disc? I've heard about it somewhere. What is it?

Ken—We're going to make one right now! Take a look at this piece of thin Bristol board. We'll cut a circle about 16 inches across out of it. Now I'm going to lay out a series of concentric circles on it. The first will be 13 inches in diameter, and each one will be an eighth of an inch bigger, till we have 16 circles. Then we proceed to divide up the circumference of our disc into 16 equal parts. . . .

Will—This is fine! We've been going through arithmetic and algebra—now we're getting a geometry exercise. When do we start integral calculus?

Ken—Never mind the calculus—I'll be satisfied if you learn television! Now let's get back to our disc. We have 16 radii, or arms, going to equally-spaced points on its circumference. I needed all these lines so I could lay out a spiral. I just mark the point where the first radius crosses the first circle, another point where the second radius crosses the second circle, and so on, going around the circle clockwise.

Will—That gives you 16 points arranged in a spiral. What do you intend to do with them?

Pinhole view of life

Ken—You'll see in a minute. First let's make—with a very small punch—a series of holes, one at each point on our spiral. And here is our Nipkow disc!

Will—And you really think you can use this for scanning television images?

Ken—I do, and what's more, I'm going to prove it! Let's make a little design—something very simple in black and white—about two by three inches. Fasten it on the bottom of the lampshade here. Now put the disc on this knitting needle, hold it in front of the design, and spin it!

Will—I see your design just as though the disc were transparent!

Ken—Now—just so we can see what's going on—let's turn the disc a little slower.

Will—I get it! This is just a big improvement on the piece of paper with the window in it we had last time. When the disc turns the first hole scans a line across the design. (Not exactly a straight line either, it's an arc of a circle, but that doesn't seem to make any difference.) Just as it finishes its line, the second hole starts across the picture and scans a line just below the first. And each hole follows (beginning at the outside of the circle or top of the design) and scans a line, till the whole design is covered.

Ken—And then the whole thing starts again with the second revolution of the disc. You see that if you turn the disc fast enough you apparently see the whole image, though really only one of its elements is visible at any one instant through one of the holes in the disc.
 Will—I see too that the disc reads in the whirling-dervish style, without having to make any backward movement to get to the beginning of each line. And I can see that it has to turn pretty fast before the eye blends all the elements into a single picture.

Reading—the hard way

Ken—Yes, and when I let the disc slow down just a little, the image shimmies as if light and dark waves were going across it. That's because the sensation produced in the eye by the light from each hole doesn't last very long.
 Will—Just how fast does the disc have to turn to get rid of this flickering?
 Ken—You know—to do a good job you need 30 complete images a second.
 Will—Yes, that's our television standard. You told me before the Europeans get by with fewer. But is 30 really enough? Wouldn't it be a good idea to scan even faster?
 Ken—Don't forget that your video frequency is proportional to the number of images you transmit a second. It's not a good idea to do anything that will increase that frequency too much. Fortunately, there's a way you can kill the flicker without increasing the band of frequencies you have to transmit. It's called *interlacing*.
 Will—This TV business really has a language of its own! What's interlacing?
 Ken—Instead of starting at line No. 1 and transmitting all the lines of the image one after the other, you transmit all the odd-numbered lines first: 1, 3, 5, etc.; then go back and transmit all the even ones. The whole scanning time is 1/30 second. That means that half the lines, covering the whole surface of the image, are transmitted in 1/60 second, and the rest of the lines are transmitted during the next sixtieth.
 Will—If I tried to read a book that way, I wouldn't get much out of it.
 Ken—If it were an ordinary book, you wouldn't! But try this little sheet; you'll have to "interlace" to read it. Your eye will follow the exact course that would be followed by the scanning beam of a modern television camera.


To read this text correctly, you must *ner in scanning first the group (or first peruse the odd lines, then the field) of odd lines, then afterward even ones. Interlaced sweep permits the even ones. To sweep the image 30 "reading" the lines in the same man-times a second, 60 fields are scanned.*

Will—This is interesting, to say the least. Maybe it was turned out by a drunk compositor! But can you really scan that way in television? It sounds awfully complicated.
 Ken—No problem at all! Suppose we make a Nipkow disc with two spirals, one on each half of the disc. We'll have lines 1, 3, 5, etc., on one spiral and lines 2, 4, 6, and the rest on the other.
 Will—Of course! It can't help but work! But now that we've proved that we can scan a picture—interlaced or otherwise—with a Nipkow disc, where do we go from here? How does it help to transmit a television program?

Now a little chemistry

Ken—Do you know anything about photocells?
 Will—Of course! I use an exposure meter when I take photographs. It's a photo-cell connected to a meter. The meter is calibrated to show how much light there is on the subject being photographed.
 Ken—Then the photocell is a device for changing light energy into electric energy. The current from the cell is proportional to the amount of light that falls on it. The photocells (or rather phototubes) used in television are the *photo-emissive* type. The simplest phototubes of that kind are little glass vacuum tubes with one inside wall covered with *photo-emissive* material.
 Will—Is that material that emits light?
 Ken—On the contrary. It's material that emits electrons when struck by light rays.
 Will—What kind of substances do that?
 Ken—Most of the so-called alkaline metals: cesium, sodium, potassium, rubidium and lithium, as well as some of the rare earths, though they're not as commonly used.
 Will—I've got an idea! If all these metals give out electrons when you turn a light on them, you could use them for vacuum-tube cathodes! Then you could get along without filament supplies. In the daytime, just keep the tubes in the light. And at night, put your radio near a lamp!
 Ken—Believe it or not, the idea isn't absurd! Unfortunately, the number of electrons emitted wouldn't give you enough current to be of much practical value. But to get back to our television—if we are going to have current in our phototube, we need one thing more. The photoactive surface is the cathode. . . .



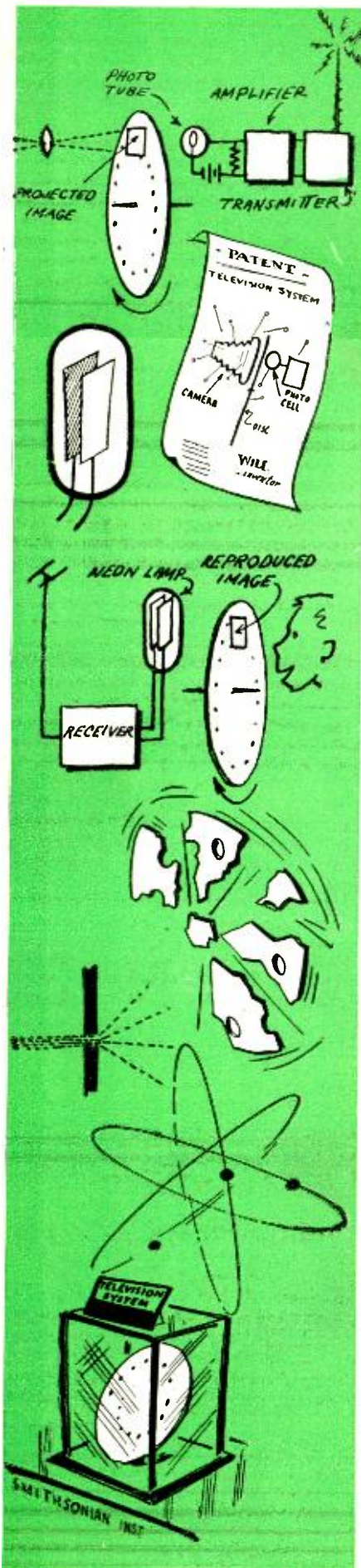

Will—I see! We need an anode. We'll have to put a plate in our tube and put a positive voltage on it to attract the electrons.

Ken—That's the idea, but a "plate" would block off the light. So our anode will be a wire ring or a fine grid.

The image is scanned

Will—Now I think I see how to make a TV transmitter. I'll take my camera, but in place of the ground glass I'll put the outer part of our Nipkow disc. Then it'll be right where the lens forms its image. And behind the disc, I'll put a phototube. What do you think? Will it work?

Ken—Absolutely! You're practically reinventing television! Your phototube is now receiving—from instant to instant—the light from each successive element of the picture being scanned, and translating it into an electric current of proportional intensity. That gives us a video-frequency signal that can be amplified easily and used to modulate the v.h.f. or u.h.f. carrier that takes it out into space.

The image is reproduced

Will—How about the receiver?

Ken—It has to have a Nipkow disc like the one at the transmitter, and moving in exact step with it.

Will—Is that what they call synchronization?

Ken—Right! And that's another word for your technical vocabulary.

Will—But how do we get the variations in current back into light again?

Ken—Very simply—with a neon lamp. You understand them, of course?

Will—Oh, yes! I even engineered an accident to the one on the restaurant across the street when it began putting out more static than light.

Ken—I'm not interested in your criminal record. The lamps most commonly used in television in this country had two plates about the size and shape of the image to be reproduced. When you put enough voltage between the two electrodes, one of the plates glows over its whole surface. A large d.c. voltage makes a bright glow. . . .

Will—And less d.c. means a weaker one, I suppose. But how . . . ?

Ken—Let me finish! If we add the varying voltage of the video signal onto the d.c. we started with, the brightness of the plate varies with the instantaneous signal voltages.

Will—Yes, but how do we manage to light each point of the plate to the brightness of that exact spot in the televised scene?

Ken—You don't have to! Your Nipkow disc in front of the neon lamp will show you each point on the plate at the instant it has the right brightness.

Will—Of course! At any instant the disc lets us see just one element of the surface of the plate. And at that same instant, the brightness is just right for that spot in the televised scene. For instance, when the first element of the picture is transmitted, the whole neon lamp is lighted to the brightness of that point. But we can see only that one spot through the hole in the disc. And when the hole passes to the next element, the whole plate is just as bright as *that* spot ought to be, and so on. So we see all points of the scene in their proper places and with their proper brightnesses, and the whole image is reproduced!

Ken—Bravo! You have described exactly the system of television first outlined about the end of the 19th century and put into practice around 1924 by Jenkins, Baird, and others.

Mechanics vs electronics

Will—It looks like a very simple and practical system to me, and I doubt if it would be easy to improve it!

Ken—Pull in your hat-band, chum! They gave up that idea years ago! They couldn't get enough detail with it—180 lines was about the most you could get in a single image.

Will—Couldn't they get more lines by using bigger discs with more holes?

Ken—No. At the speed the discs would have to turn, centrifugal force would tear them apart.

Will—Couldn't you make the holes smaller?

Ken—Not very much smaller. You would cut down the amount of light that could get through, and after a certain point you'd be up against the very disagreeable phenomenon of diffraction.

Will—It seems I don't have any good ideas today!



Ken—No matter how good they might be, you wouldn't be able to save mechanical television. It had other bad faults. For example, the phototube at the transmitting end received the light from each point of the image for such a short time you had to use very high illumination on the subject to get enough photoelectric current to use. And the efficiency at the receiving end was very low, because you can see only a very small part of the neon lamp's plate at any instant. And finally, we're living in the age of electronics now!

Will—Then why did you take time off to explain a system that belongs in a museum?

Ken—Because once you understand a simple system of television, your brain cells will find it easier to absorb the more complex details of the electronic systems.

Will—I've got a feeling I'm letting myself in for something awfully complicated!

ANTENNA REFERENCE CHART

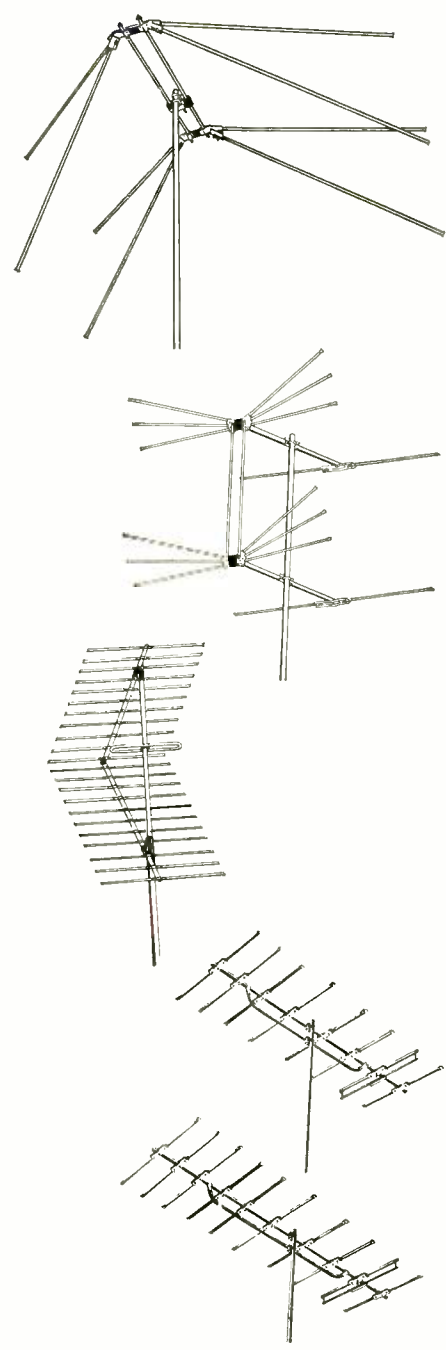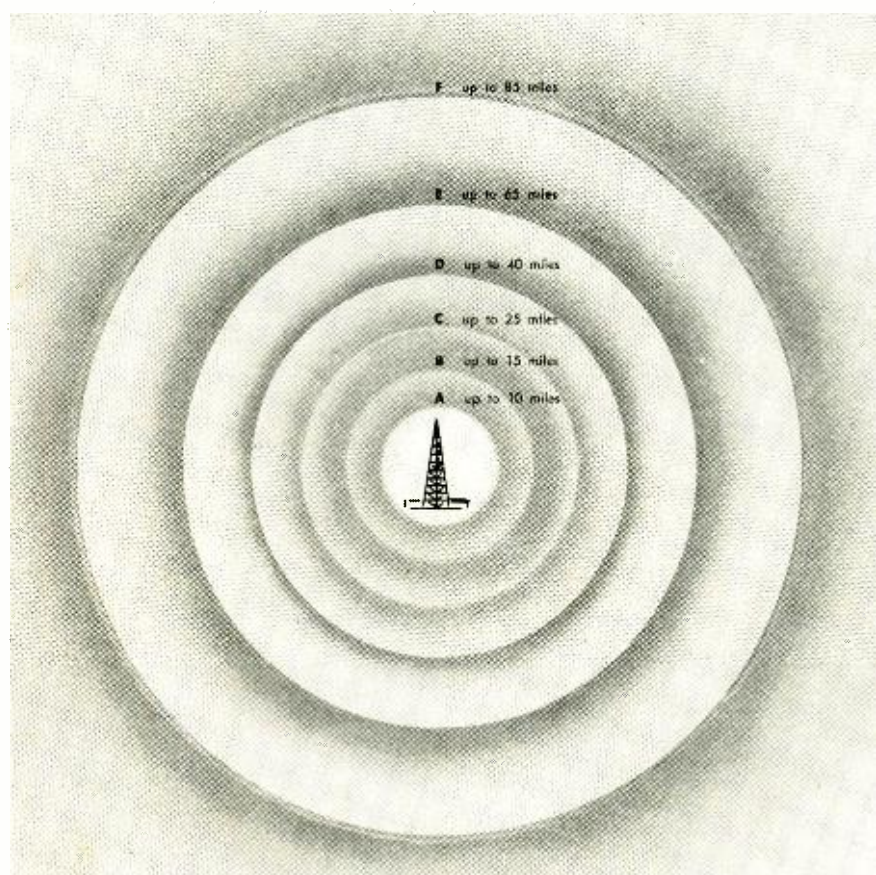

This chart takes into consideration only proportional signal strength over unobstructed terrain at given distances from the transmitter, based on the effective radiated power of the average v.h.f. television transmitter. It **does not** cover the possible effects of natural obstacles or buildings on the path or strength of the received signal.

For example: the single-bay in-line antenna has fairly high forward directivity, and works best at distances up to 25 miles from the transmitter (B and C). Where you want to receive **two** stations from different directions at this distance, select an antenna that has the necessary gain without the sharp forward directional characteristic, such as the 8-element conical V. (The ranges given are for v.h.f. only, and will be much shorter on u.h.f. due to increased ground attenuation on the higher frequencies.)

In built-up areas close to the transmitter, there may be difficulties from rear and side reflections, especially where tall buildings are involved. Use a conical with a large number of reflector elements (a 6-front, 6-back type for example) to raise the forward gain and reduce signal pickup from the rear and sides.

Our thanks to *Radio Merchandise Sales*, for permission to reproduce this chart, which was prepared by their engineering department.

Gain Reference Code Letter	Television Antenna Types
A	Built-in or indoor ("rabbit-ears")
A	Window
A and B	Piggy-back
A and B	V type (4-element end-fire array)
A	Conical (4 directors—4 reflectors)
B	Conical (6 directors—2 reflectors)
B and C	Single-bay in-line
C	Conical V (8-element end-fire array)
C and D	2-bay in-line
C and D	2-bay V type
C	2-bay conical (6 directors—2 reflectors)
D	5-element Yagi
D and E	2-bay conical V
E	8-element Yagi
D and E	4-bay conical (6 directors—4 reflectors)
D and E	4-bay conical V
F	10-element Yagi
E and F	Corner array
E and F	Rhombic antennas

TV SERVICE CLINIC

Conducted By
MATTHEW MANDL*

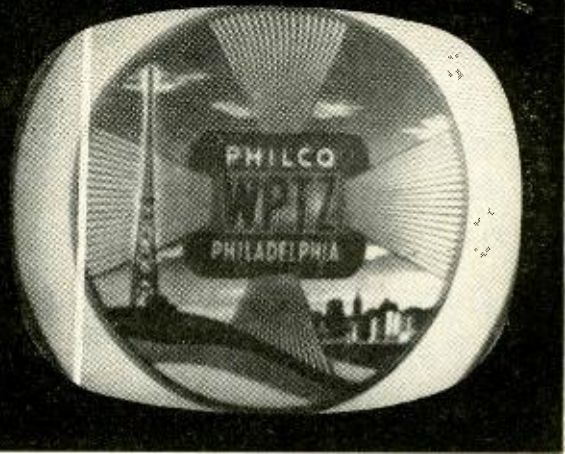


Fig. 3—Effect of transient oscillation.

THE voltage boost circuit of the horizontal flyback system is a simple circuit consisting of a pair of capacitors and a coil. These are connected to the cathode of the damper when the horizontal output transformer has a secondary winding for the deflection coils. On occasion, however, the

insufficient damping of the transient oscillations developed during collapse of the fields in the yoke during retrace.

The transient oscillations occur at the beginning of the sawtooth sweep and thus are usually positioned near the left of the screen. They interrupt the gradual incline of the sawtooth sweep one or more times for each line traced on the screen. A single dip as shown in Fig. 2 means that the forward trace is slowed down, then reversed as the sawtooth dips. When the waveform comes out of the dip the beam within the tube moves across the screen again. This reversal of the beam at the beginning of the trace makes this section of the scan brighter, and successive horizontal trace lines produce the vertical bar down the screen. This appears (in exaggerated form) in Fig. 3. Often the bar (or bars) may be just barely visible. (Fig. 3 has been retouched for better reproduction.)

bridging with new ones is a useless test. If the capacitor is shorted, it also shorts the shunting capacitor. If leaky, the leak still exists despite the shunting capacitor. If off value, the shunting capacitor adds additional capacitance beyond the required amount for normal function of the circuit. Disconnect the capacitor, then try the known good one.

Picture tube leakage

In a GE 14T2 receiver brightness is excessive and can't be reduced by the brilliancy control. A test showed B plus voltage on the control grid of the picture tube even with the coupling capacitor disconnected. I checked the socket and found nothing wrong. It appears that the picture tube is defective, but was wondering if there is any remedy other than replacement.—N. T., Brooklyn, N. Y.

Your checks indicate a defective picture tube which should be replaced. Some technicians, on occasion, have been able to correct the internal defect by high voltage arcing. They remove the picture tube socket and ground pin 2, the control grid. They then connect a high-voltage insulated probe to the high-voltage connector (this is removed from the tube and connected to the probe). The probe is applied to pin 11 of the tube. This causes an intense high-voltage arc between the cathode and grid of the tube and often burns away any shorting flakes of conductive material or any coatings which have formed between terminals. This is repeated by applying the high-voltage probe to pin 10 (grid 2). This arcs between grid 2 and grid 1 and helps eradicate any leakage.

This procedure is of course dangerous because of the high voltage. And no guarantee of success can be made. I've tried this on a 10-inch tube lately and good results were secured for only about three weeks, when leakage again developed.

Barkhausen

In a GE 803 receiver I am getting severe Barkhausen effects (black vertical bars as shown in Fig. 5). I've replaced the 6BG6 horizontal output tube,

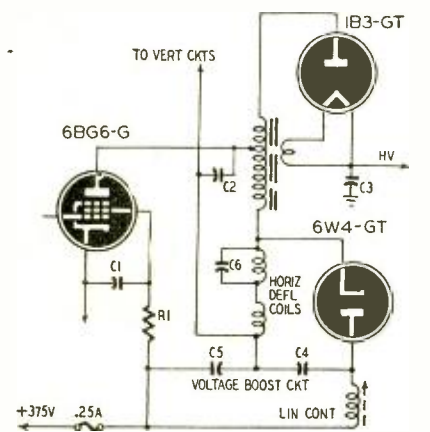


Fig. 1—Voltage boost circuit in the RCA 6T53 direct drive sweep system.

boost circuit may be in the plate side of the damper as shown in Fig. 1. This is a partial schematic of the direct drive type of horizontal output system, in which the deflection coils are in series with the transformer primary. The only secondary winding is for the filament of the high-voltage rectifier.

Despite the simple circuit, the voltage boost system contributes a good percentage of the many troubles which occur in horizontal sweep stages. A gassy or shorted rectifier can mean raster loss, while defective capacitors and coil affect linearity. Defective tube and components can also produce white vertical bars on the screen which denote

If damping is exceptionally poor, the bar interference becomes more visible. Since the bar is caused by poor sweep linearity a similar symptom may be observed if the horizontal output tube or circuit develops defects. If, for instance, the drive control is advanced too far, sweep linearity is affected and a bar can be produced. Usually, however, it is located nearer the center of the screen and is often the result of a misadjustment in both linearity and drive controls.

If components in the boost circuit open, much more serious symptoms are produced. Fig. 4, for instance shows the multiple bar interference which occurs when C4 of Fig. 1 opens. Besides the bars, horizontal shrinkage and foldover at the left are also present.

Initial trouble-shooting procedures consist of replacing the damper tube. If this fails to correct the defect, check the linearity coil for continuity and shorted turns, and check capacitors (C4 and C5 of Fig. 1) for leakage and off values. If a capacitor checker isn't available, try direct substitutes with values agreeing with the schematic. Off-value capacitors are a common cause of poor linearity and white vertical bars. Unless the capacitors are open,

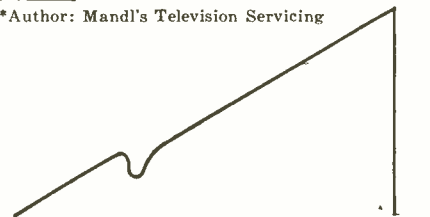


Fig. 2—Transient oscillation in sweep.

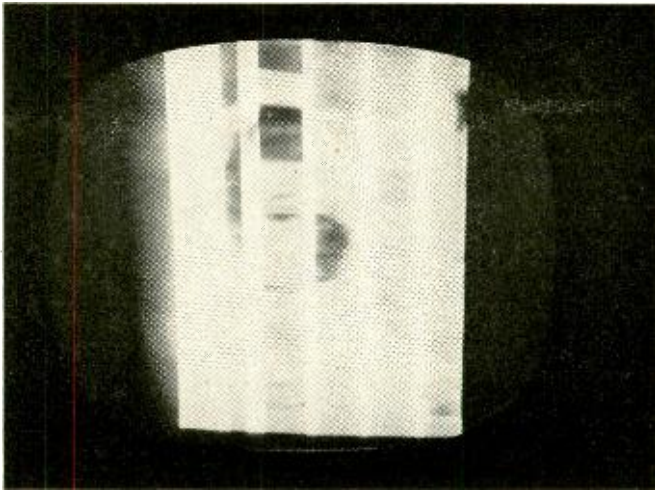


Fig. 4—Effect of an open capacitor.

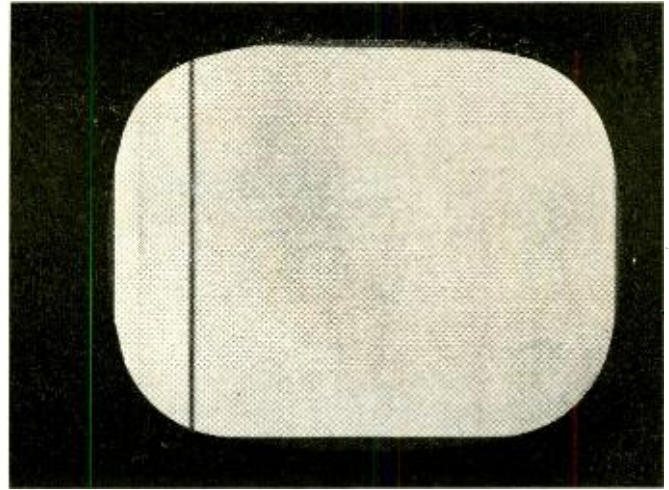


Fig. 5—Barkhausen effect (retouched).

and tried a magnet type eliminator on the tube without success. What other remedies are there?—R. B., Haver-town, Pa.

You should try 75- or 100-ohm resistors in series with the control and screen grid leads. Wire the resistors as close to the tube as possible. Also check lead dress. If this fails, the trouble may be in the tuner, which picks up the radiated signals from the horizontal output tube and permits their final appearance at the grid of the picture tube.

Often Barkhausen effects can be eliminated by tuner tracking to bring performance up to peak sensitivity for the incoming signal. The video i.f. stages should also be aligned with an accurate marker, sweep generator, and oscilloscope. (Many new receivers now use double shielding in the tuner to minimize Barkhausen and other undesirable signal pickup.)

Interlace

In several receivers lately I've noticed what appears to be interlace trouble. The horizontal trace lines seem split up instead of being clearly defined. I notice that if the vertical hold is adjusted slightly the lines are much clearer and more visible. Could you give me some information on this?—J. K., Chicago, Ill.

You are misinterpreting the appearance of true interlace. Without interlace, line pairing results with the horizontal line structure more coarse and better defined. With proper interlace, however, horizontal line structure is much fainter in appearance. When the vertical hold is set just at the point where vertical sync loss is about to occur (or during loss of sync when picture rolls) interlace is lost and the lines actually look clearer and more visible. But since coarse line structure is undesirable, an interlaced raster is preferred.

In most instances interlace is lost on occasion because of the nature of the transmitted signal or because of noise interference. Proper interlace is aided by the *integrator* circuit of resistors and capacitors at the input to the ver-

tical oscillator. Definite loss of interlace calls for a check of these components. (Some sets have poor interlace due to faulty design. This is beyond the technician's control.—Editor)

Excessive picture tube bias

In a Westinghouse H-630T14 receiver there is sound but no raster. The picture tube has 275 volts on the cathode instead of 120. Also, with no raster I still get a flash of light on the screen when the receiver is shut off. I am assuming, therefore, that high voltage is present. What causes raster loss?—J. K., Grand River, Mich.

The excessive cathode voltage indicates excessive bias which is cutting off tube emission. First take a voltage reading between the picture tube grid and cathode as the brilliancy control is varied. The voltage should vary from a low value to well over 50 volts (grid minus with respect to cathode). In all probability you will find the grid-cathode voltage relationship remains unchanged because of a defective brilliancy control, or bad resistors and capacitors in these circuits. Use an ohmmeter for isolation of the component which is causing the trouble.

Conversion parts

In a conversion job on an RCA 9TC247K, can I use a Merit HV07 horizontal output transformer in the same manner as the autotransformer in the receiver by connecting terminals 4 and 1? If this is possible, I can avoid extended circuit changes.—A. F., Baltimore, Md.

The direct-drive type of horizontal output system in this receiver cannot be replaced with a similar circuit unless a direct-drive type of transformer is used. The conventional two-winding type of transformer such as the Merit HV07 is not suitable for this job. The direct-drive transformer permits matching the output tube impedance to a *high-impedance* yoke, while the secondary type of transformer steps down the tube impedance to match a low-impedance yoke. Wiring the transformer as you suggest would not give proper impedance transfer characteristics.

Defective a.g.c.

In an RCA 9T79 receiver the picture becomes poor and excessively dark on strong stations. On weak signals picture quality is good. I've tried a new 6AL5 (second detector and a.g.c.) but this didn't help. Could this be a leaky capacitor somewhere in the a.g.c. line?—C. H., Leroy, N. Y.

Yes, a leaky or shorted capacitor in the a.g.c. bus could cause this trouble, as could an open series resistor. Check all such parts from the 6AL5 a.g.c. detector to the various feed points ending at the grids of the r.f. and i.f. tubes involved. A v.t.v.m. placed from any a.g.c. point to ground will show the amount of bias. This negative potential should increase as a strong local station is tuned in, and decrease for a weak station. It should also vary as the fine tuning is adjusted when a station is tuned in. Also check the 6AV6 first sound amplifier, as this is also the bias clamp for the a.g.c.

Lead losses

Would running the flat 300-ohm ribbon type of transmission line through four feet of mast affect performance? The installation consists of a 37-foot mast with the antenna mounted above an Alliance motor. The lead is run through the four-foot mast as an expedient way to get around the motor. The mast is grounded. With similar antennas (but with the line running outside the mast) neighbors get better reception. Their receivers, when used with my antenna, also perform poorly. I suspect the four-foot section, but would appreciate your advice.—L. S., White House Station, N. J.

As you suspect, there is loss when a ribbon line is run through a mast section. When the transmission line carries signals, a field is set up around it, and the capacitance effect between the line and the metal of the mast creates losses which get worse at the higher frequencies. The longer the run inside a metal enclosure, the greater the loss. You will find that signals will improve when the lead is installed properly with standoffs. Keep the line away from large metal objects. END

U.H.F. TREATMENTS TO IMPROVE WINES



Ewing Gallotay

*Irradiation
reduces acid
content and
contamination*

By M. LAFARGUE
Central Radio School Paris, France

EXPERIMENTS in the field of preservation of foodstuffs by exposing them to radio waves during varying periods of time have been made at different times since 1925, by such workers as Lakhowsky, Foyaz, Copin, and others. This has always been an important problem, since refrigeration as the solution has always been an expensive one. On the other hand, certain products must live and age as part of the process of preservation. Wine is one of these products, and because of its economic importance in France, experiments to determine the effect of short-wave radiation in its processing have been carried out to considerable length in this country.

In our experiments, wavelengths of 10 centimeters, several millimeters, and between 90 centimeters and 1.20 meter were used, most of the work being done on the 1.20-meter wavelength, just below the edge of the ultra-high-frequency region.

A transmitter with a range from 0.9 to 1.50 meters was constructed. Since a stable or exact frequency is not necessary, a simple long-lines oscillator worked satisfactorily. There are three methods of operation. At switch position A in Fig. 1, 500 volts d.c. is applied to the plates, and the output is 45-48 watts. In position B, pulsating current at 4,000 volts is supplied. The pulsations are controlled by square positive 400-volt pulses on the grid. Waveform and other characteristics are precise, controllable, and stable. In position C, only the voltage peaks (10 kv) are stable, and the pulses have no special form.

The useful peak power in position B is 1.8 kw and in position C, 5.7 kw.

Radiation methods

In most of the tests, a setup like that of Fig. 2 is used. The antenna is a half-wave dipole fed directly by a two-wire line which is coupled to the transmitter by the usual adjustable hairpin link placed below the plate circuit of the oscillator.

Glass vessels of special construction fit over the ends of the dipole and hold the wine. Note that, as in Fig. 2, two experiments (such as treating two kinds of wine) can be carried out during the

same transmission. In all these experiments, the degree of heating was negligible, being less than 1 degree C.

Much of the energy from the dipole radiates into the surrounding space and is lost. To increase efficiency, a waveguide was next tried.

Wine, being mostly water, has a dielectric constant a trifle over 80. The length of a wave in wine therefore is its length in air divided by the square root of 80 (8.944). Thus, a circular waveguide of 9 cm diameter can easily operate on waves in the $TE_{1,1}$ mode throughout the transmitter's frequency range.

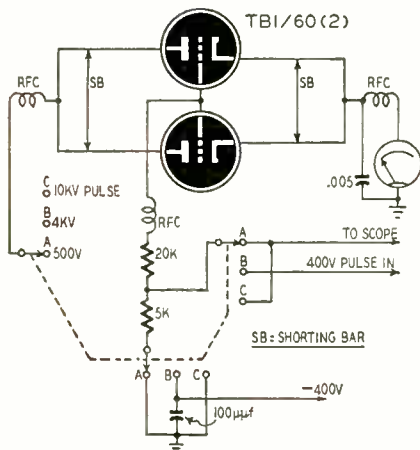


Fig. 1—The transmitter output stage.

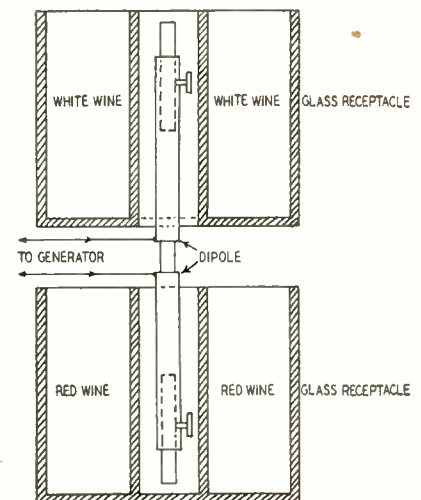


Fig. 2—The simplest radiating system.

The liquid waveguide has its own problems. Coupling cannot be adjusted by slits or movable wires, because of leakage. Silvered waveguides cannot be used, as silver dissolves in the wine. Therefore the impedance of the transmitter was matched with a double-stud coaxial line (Fig. 3). The coax is of the air-dielectric type (except at the joint where it enters the wave-

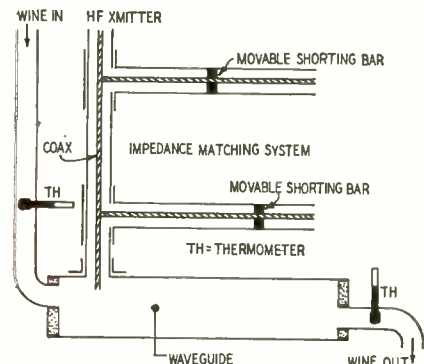


Fig. 3—A more complex, but more controllable method of irradiating wine.

guide) to keep losses down. The insulation must be capable of withstanding pulsed energy. The coupling loop to the transmitter is of the symmetric-asymmetric (balun) type. (Fig. 4). The coax has an impedance of 50 ohms.

The "wine circuit" is so arranged that the same wine can be recirculated for treatment several times. There is also a control circuit in which wine is circulated in exactly the same manner without being exposed to r.f. energy, to indicate effects caused simply by the handling.

The pulse generator

This generator (Fig. 5) has an oscillator stage, a peak clipper, a monostable multivibrator producing the pulses, and a power amplifier. The oscillator is of the low-frequency Wien-bridge type, using an ECH21. Pulse

frequency is variable from 1 to 1,000 per second without affecting the output power. Coarse frequency setting is by changes in capacitance, controlled by ganged switch S1, and fine tuning by the ganged potentiometers P1 and P2. The signal goes to a peak-clipping tube (EF50), whose voltages are so adjusted that only the part of the wave with the steepest slope is retained. The differentiator which controls the multivibrator has a single fixed resistor and a separate capacitor for each band. If the sides of the square signal thus differentiated are not sharp enough there is danger that the multivibrator either will not work on the lowest frequencies, or that it will supply two successive pulses per cycle for the weakest voltages.

The 6N7 monostable multivibrator has one grid biased to cutoff while the other has a variable positive voltage (through P4) which controls the width of the pulses (variable control of power output). A variable resistor in this circuit (P3) is ganged to P1 and P2. Thus for a given setting of the power output, the width of the pulses varies with frequency, maintaining output power constant.

The output amplifier consists of an EBL21 first stage and an EL39 final. The square-wave output signal goes direct to a 5,000-ohm load. Very narrow (though not rectangular) pulses can be obtained by differentiation with a small coupling capacitor.

60-kilovolt generator

A generator which delivered 60-kv peaks for transmission as damped waves through a Hertzian discharger also was designed for higher-frequency work. The circuit (Fig. 6) was the one that seemed most economical. A 6N7 multivibrator controls a Philips TB 2/500 transmitter tube operated as a blocking oscillator. (A blocking oscillator without control was first tried,

but was unstable and at times erratic.) The high-voltage coil operates on the principle of a television high-voltage transformer, and is constructed of six large honeycomb coils from old Philips superregenerative receivers, well spaced along a cylindrical bakelite form with an iron-wire core. Double discs of bakelite between the coils insulate the leads between coils from both the coils between which each lead was attached. The Q and inductance-capacitance ratio of such a coil is important, and its insulation is a delicate task not to be entrusted to inexperienced hands.

Conclusions

Some interesting results were obtained. Some of the more important were:

1. A decrease of 10 to 20% in the volatile acid content was noted in wine that had been subjected in small quan-

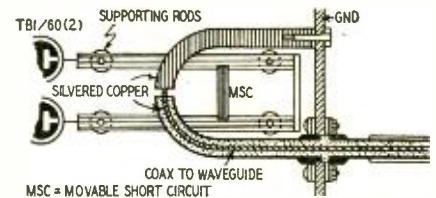


Fig. 4—Balanced-unbalanced transformer matching push-pull tubes to coax.



ties to the action of *damped waves* of 1 millimeter wavelength (approximately) over a period of 3 to 11 days.

2. A decrease of 34% was noted in the volatile acidity of wine (original acidity 0.58 gram per liter) was noted after subjecting it to the action of *continuous waves* for 17½ hours over a 3-day period.

3. Absolute cessation of specks and considerably less "turning" of the wine.

The following further features were noted:

1. There was an excitation thresh-

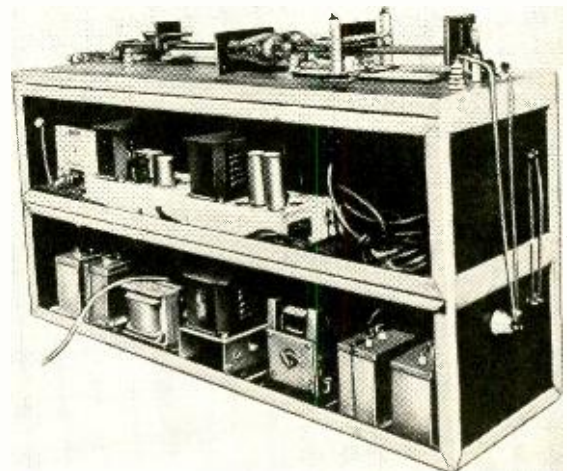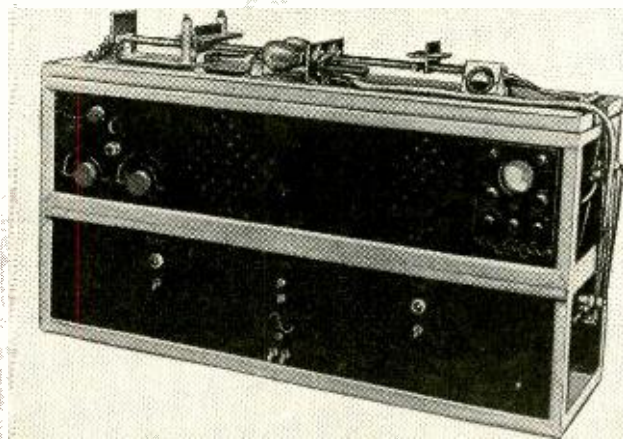

The transmitter used in most of the experiments. It is a long-lines, push-pull circuit with provision for various means of excitation. Power can be varied, but control over the output waveform decreases as power is increased.

A rear view of the equipment. Dimensions of the long-lines circuit are well shown here. Power supplies, excitation apparatus and even an oscilloscope for checking pulse waveforms are also built into the two sections of the equipment.

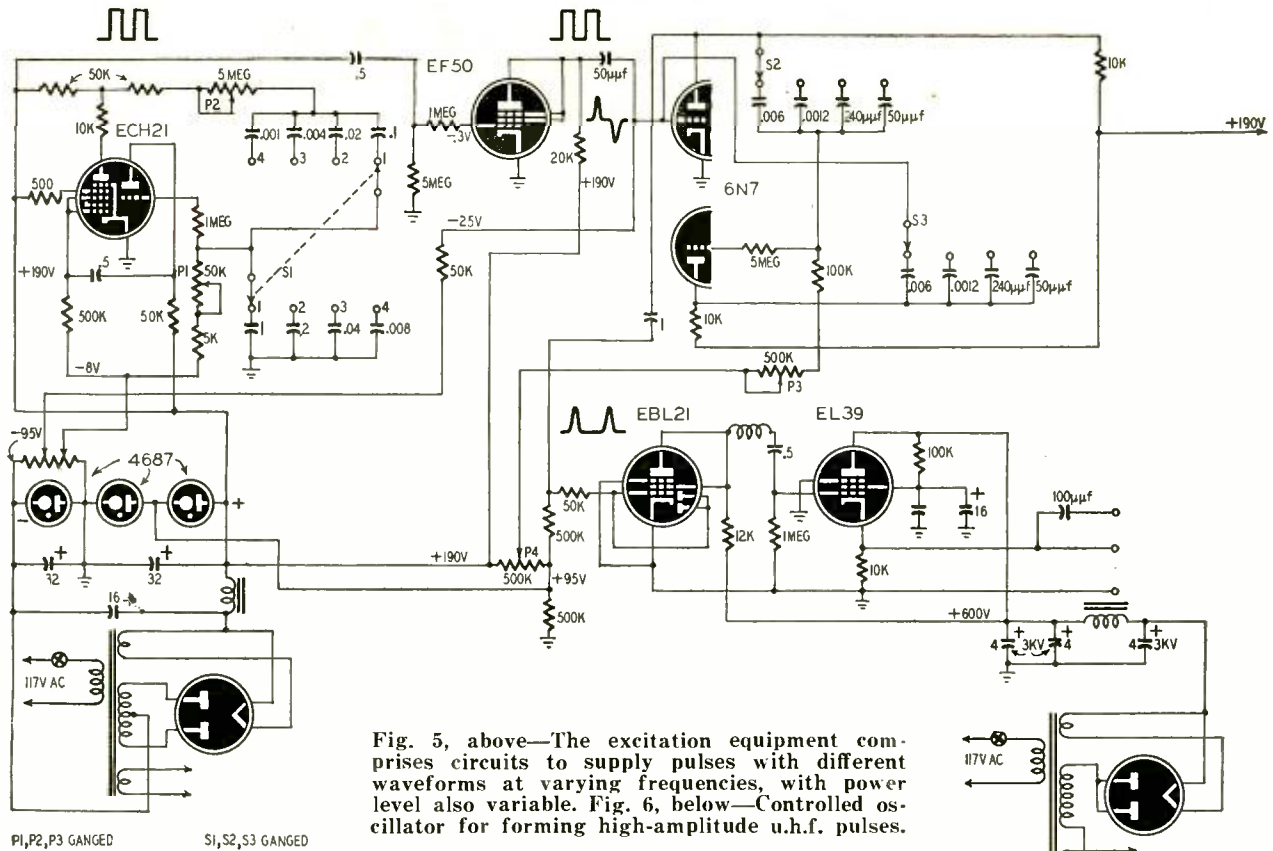


Fig. 5, above—The excitation equipment comprises circuits to supply pulses with different waveforms at varying frequencies, with power level also variable. Fig. 6, below—Controlled oscillator for forming high-amplitude u.h.f. pulses.

old; radiation below a certain power produced no effect whatever on wine.
 2. The treatment must be spaced—for example, one hour out of every three.

3. Improvement was not always noticeable until several days after treatment.

The above discoveries, as well as the techniques worked out for irradiating liquids, may be useful in the treatment of other foodstuffs and beverages, as well as for performing operations on liquids consisting mostly of water. One

Characteristics of the tubes

EBL21—Duo-diode and output pentode. Plate dissipation (pentode) 11 watts. Transconductance is 9,000, plate resistance is 50,000 ohms with 250 volts on plate and screen.

ECH21—Triode-heptode converter tube. Similar to 6J8, 7J7, and 7S7 except that each grid has a separate pin terminal and the oscillator (triode) grid is not connected internally to any of the grids in the heptode section. A triode-pentode such as a 6X8 will probably work in this circuit.

EF50—High-transconductance pentode. A 6AC7 is probably the best American substitute in this application.

EL39—Power-amplifier pentode. Plate resistance is 30,000 ohms and gm is 4,000 with 600 volts on the plate. A 6L6 or 807 is probably applicable.


4687—Voltage regulator tube. Operating voltage 95.

TB1/60—50-watt transmitting triode. Amplification factor is 10.5.

TB2/500—300-watt transmitting triode. Amplification factor is 30 with 2-kv plate supply.

may well hope that a cure for the maladies that occur in wine and other products which require aging or fermentation may be evolved.

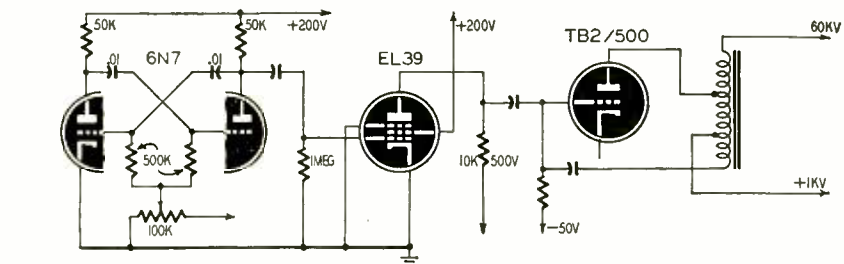On the other hand, we still do not know just how the ultra-high-frequency waves produce their effect on wines and other living organic matter. To us, it seems that this scientific aspect of the problem is by no means unimportant. END



SONIC DELAY LINES

MODERN electronic computers, radar equipment, and oscilloscopes for observing high-speed transient phenomena need some way to delay a signal for a definite time interval. One of the most practical methods is to feed the signal into a sonic delay line. It can handle a wide range of frequencies and can be adjusted to give various time delays.

With this system the electrical signal travelling through the circuit at a little less than 186,000 miles per second, is applied to a quartz or rochelle-salt crystal fitted to one end of a long, narrow metal tube. The tube may be folded to provide the required overall length in the smallest possible space. It is filled with water, mercury, or some other liquid. The far end is fitted with another crystal identical to the one at the input end.

The input crystal changes the electrical signal into a mechanical vibration, which travels down the fluid column as a sonic wave. Since the velocity of sonic waves in water is approximately 5,000 feet per second, the signal takes about .001 second to reach the far end of a 5-foot line and strike the receiving crystal. This crystal then converts the sonic wave back to an electrical signal, which is applied to the output circuit.

Lines can be made longer or shorter for other delay intervals; and mercury, which has a higher velocity of propagation than water and is not subject to evaporation, can be used where extremely short delays are needed.

The high attenuation in the liquid absorbs reflections from the walls of the tube, so that only the main signal reaches the receiving end. END

*TV installation
intercommunicator
uses the lead-in
as a phone line.*

By MILTON LOWENS

MOST service technicians have grown up with the feeling, at one time or another, of a strong urge to communicate with others over a distance. We recall our first experiments—the signal flags, the string stretched between the ends of two cans (or were they oatmeal boxes?), the telegraph lines to the neighbor's house, the toy telephone, and finally (in many cases) amateur radio.


Possibly forgotten is a very simple and inexpensive communication arrangement which can now be used by TV antenna installation teams. The essential component, which practically all service technicians already have, is a pair of headphones. Connect two phones together through any reasonable length of wire as shown in Fig. 1 and you have a sound-powered telephone system: no batteries, microphones, transformers, or amplifiers are required. No wire is required either—the antenna down-lead serves the purpose.

The phone is one of the simplest radio devices and its normal operation is well known. Send audio current into its electromagnet and the resulting variations in pull will cause the steel diaphragm to vibrate, producing sound. Not so readily remembered is the fact that the operation is reversible; make the diaphragm vibrate—as by speaking into the phone—and a small audio voltage will appear across the coil terminals. The reason is that as the steel diaphragm changes its distance from the pole pieces of the permanent magnet upon which the coil is always wound, the strength of the magnetic field varies because of the changing reluctance of the magnetic circuit. Going back to fundamentals: whenever the strength of a magnetic field around a coil changes, a voltage is induced. Thus the headphone is really a dynamic microphone. Although its output—like all dynamic mikes—is rather low, it is great enough to operate another phone to produce a “readable” signal. Since two identical units are used at both ends of the line, the impedance match is good and power transfer is optimum.

Putting it into practice

The usual TV antenna installation team consists of two men; one at the set, the other on the roof. If each clips his phones to the two wires of the TV

COMMUNICLIP

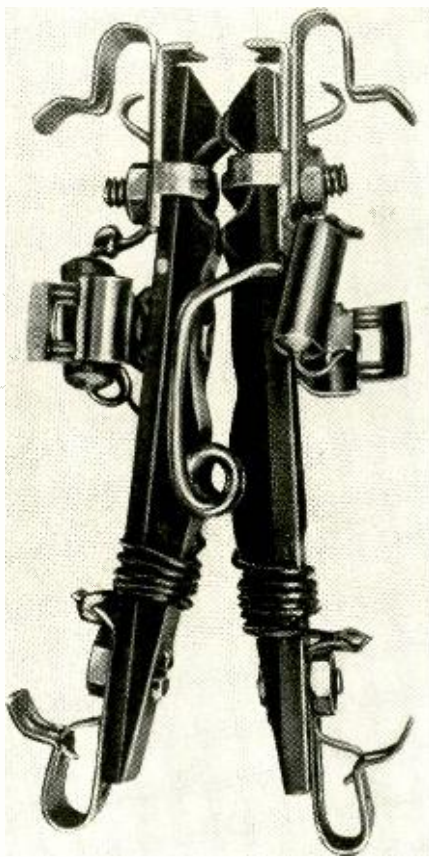

Though the Communiclip looks formidable, it is just a plastic clothespin.

transmission line (lead-in), communication theoretically is possible. Actually there are a number of problems to be overcome before the system is practical:

1. If a folded dipole antenna is used, the phones would be shorted out.

2. The antenna coil in the TV set will in most cases also short-circuit the phones;

3. Even if the above were corrected, attaching phones directly to the line could interfere with antenna performance and make adjustments difficult.

The solution to the problem is shown in Fig. 2. The capacitors prevent short-circuiting the low-frequency audio by low-resistance antenna and set components without interfering with TV signal frequency transmission. The chokes RFC isolate the phones for r.f. without interfering with audio currents. Values of the capacitors and r.f. chokes are not critical: about 500 μf and 6 turns of No. 22 wire on a $\frac{3}{8}$ -inch dowel will do nicely.

The Communiclip

While almost any arrangement of parts will work, the assembly should be rugged so as to be trouble-free despite the hard use it is likely to get, especially on the roof. The design shown

in Fig. 3 is suggested. It is built around a plastic clothespin, of the type that sells for about two for 5 cents in most hardware stores. Fig. 3 shows only half the clip—the other half is identical.

In use, the clip is left attached to the phone tips, using the proper Fahnestock terminals. The man at the set attaches the ends of the lead-in to the center terminals, and clips the whole “clothespin” onto the teleaset's antenna terminals by means of the ears K improvised from a piece of light metal. At the antenna, the lead-in is cut at a convenient point and its ends are clipped to the proper terminals. Communication is then established. The man at the set, whose hands are free, does most of the talking. His partner on the roof wears his phones, leaving his hands free for shifting or turning the antenna as directed by the man at the set. Whenever he wishes, however, the man on the roof may speak to the other by talking into one of the phones.

A few final precautions: Any kind of phones may be used as long as both pairs are electrically similar. They must be in good condition; weak magnets will not produce sufficient output. Single phones at each end are somewhat more effective than pairs because when one phone is used as a mike, the generated energy must drive three other receivers when pairs are used. However, the received signal is quite adequate even with pairs, and a pair of phones is more comfortable. END

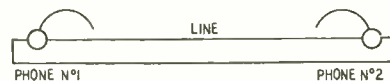


Fig. 1—Simple sound-powered phone.

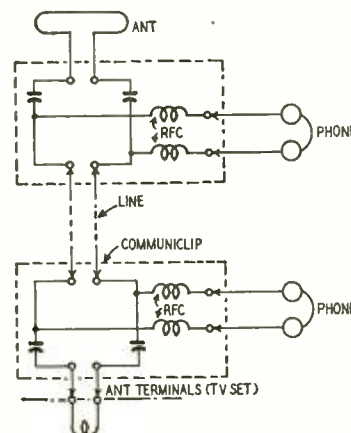


Fig. 2—The intercommunicator circuit.


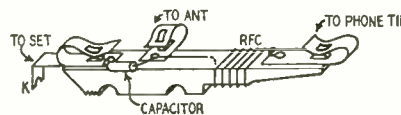


Fig. 3—Drawing of one half of the clip.

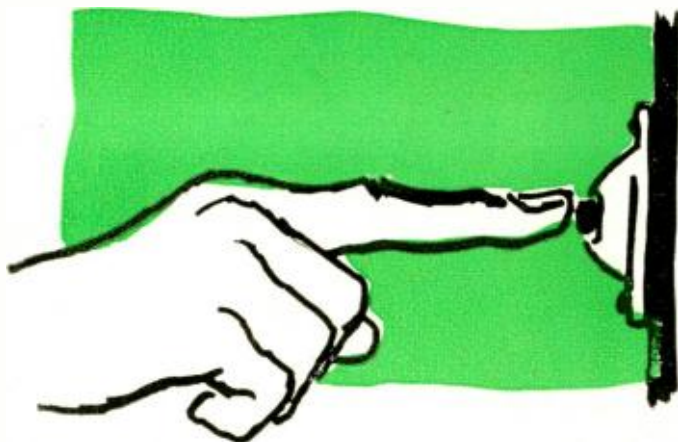

CANVASSING BUILDS BUSINESS

By JIM KIRK

WHENEVER salesmen visit me, or telephone solicitors call me, I try to be always polite and friendly. I remember the times when I wished I might have been treated that way but wasn't. Sometimes, the salesman himself is to blame for the way he is treated; sometimes he abuses privileges. But oftener, it is the other way around.

I don't mean to infer that canvassing, by ringing door bells or telephones is on the whole an unpleasant business. On the contrary, 99% of the prospects are kindly, friendly, and anxious to be helpful. Canvassing is the backbone of my present business and is the way I started two other businesses in two other cities.

In 1929, I was working from my garage on Edenhurst Street, Los Angeles. That business was built entirely by canvassing, door to door. The canvassing was done methodically. I drew a large map of the vicinity and began ringing doorbells on the streets nearest my shop. I kept a notebook with every street number in it and made back calls where no one was home the first visit. By 1934 the business was well established and I had moved to a store on Glendale Boulevard. However, I wanted to leave Los Angeles. Each summer I spent my vacations in the San Francisco Bay area, so I sold and gave away radio parts and moved to Oakland. I had a salaried position until 1939 when I deliberately moved to a neighborhood where there was no radio shop. I canvassed nights and Saturdays until there was so much radio business that I could not handle both jobs. I gave up the job that paid me the most money (my salaried position) but I was happy!

In Oakland I drew a large map to scale (drawing is a hobby of mine) of the territory in a mile radius from my location, and moved to a store a block from my home on West 14th Street. I canvassed every morning, and it was the backbone of a business, which in 1946 was soundly established and paying well. But I always did like dear

old S. F. better than any city I have ever seen. In 1946, there was a neat, clean, little store for rent in an attractive neighborhood in San Francisco (Church Street). I rented it and hired help in both shops. (Oakland shop was paying well, then.)

I drew another large map, to scale, of the territory within a mile radius of the S. F. shop. (That map is still hanging on the wall of my reception room and excites favorable comment from customers.) While my employees handled the radio work, I did the canvassing for my San Francisco shop. That canvassing is still the backbone of this business.

Time and again, my card index shows that old canvass customers are returning. I couldn't make a living on simply new, drop-in business.

Chasing back and forth between the two cities was driving me frantic. Besides, I had unhappy experiences with employees. Business prospered when I was on the ground but went back when the employee was alone. I didn't blame anyone, but I decided I must drop one shop and go back to a one-man business again. I hated to turn either shop loose. I loved San Francisco and the new location, but the Oakland shop was really paying. I put the Oakland business in the hands of two real-estate operators. One actually brought around *one* prospect but all either operator ever did for me was to take my money. It seems that just anyone can't operate a radio service shop. What I was looking for was a radio man with money. Ever see one? I finally regretfully abandoned Oakland.

The effective opener

I have experimented with various approaches, but my favorite is the one I was using in 1932 and am using today:

"How does your radio work?"

(The prospect will ask you if you do television work, also.)

Having done no canvassing in this city since my first campaign six years

ago, I decided recently that business could stand a tonic. What better method than the tried and true results that canvassing brings? However, in life's twilight, Grandpa could not see fun in climbing hills and steps and taking a lot of exercise for small results. My business had progressed from exclusively radio work to mostly television work. Why not progress from ringing doorbells to ringing telephones? I found it best of all, because more people could be contacted in a given amount of time.

I got out my card index of customers and looked up their phone numbers, where I did not have them already. I asked the same old question, quoted above. I received some orders to pick up radios that I would not have had without reminding the customers. I also received television service work. I got some unexpected replies, such as:

"My radio hasn't worked since you fixed it. I am thoroughly disgusted with your service!"

My card index showed that the service was rendered three years ago, so I doubted the veracity of the statement, but did not say so. I do not suppose I made a friend of the customer, but I tried my best to do so. I explained that the parts I installed were guaranteed for three months, and that if he had brought in the set during that time, I would have been happy to look it over without charge. If any part I had installed was defective, there would be no charge whatsoever for a replacement, even though it would take time and work to locate it and replace it. In three years, everything could happen, so I could not give free inspection at this late date.

(My fellow service technicians will agree with me, that we give the customer a better break than other kinds of service businesses do. Take the auto repair shops, for example. You have your valves ground this week, and next week the rear end of the car drops out. Does the mechanic install a rear end free? No. He not only charges you for new parts; he adds a towing charge

and a labor charge for installing the new rear end. A radio and TV repairman, however, is something different. He should guarantee everything about the set the minute he touches it. I have had customers hit the ceiling and threaten to sue, because I would not replace—free of charge—an old tube that happened to burn out the day after I repaired the set. I asked the customer if he would expect an auto mechanic to supply a tire free because the old tire blew out the day after he had changed the crankcase oil. Of course, an appeal to reason is hopeless in such cases.)

Customers are nice people!

I don't want to give the impression that all customers are chiselers—that



the technician must be careful to hold onto his eye-teeth. The big majority are fine people, but when I get a chiseler—I get a dilly! To illustrate how wonderful some people can be, just take the case I got last week. I completely overhauled an old set, even supplying some parts that were not necessary, simply to have it play for the time being. The customer returned next day, and I said, under the breath that I was holding (along with my stopping heart): "Oh-oh. Now, what the . . . ?"

The customer said:

"We just want to compliment you on how well you made that radio play. It never worked so well when it was new! Thank you for your thorough service."

They didn't *have* to say that. I was well paid for my work. Just wonderful people!

Another unexpected reply to my phone call was:

"We certainly won't ever patronize you again! We think your price is away out of reason. You took us for plenty!"

Again, I looked at the card-index record. The customer called Saturday afternoon and insisted the TV be back Sunday morning. I picked up the set in my truck, and to make a good impression with a new customer, I had it back and installed Sunday morning. A shorted capacitor had been replaced and the charge was around \$10. Well, I don't want that kind of customer, but again, I didn't say so.

MARCH, 1953

"Don't let these few undesirables throw you! On the whole, canvassing is an enjoyable business," I tell myself.

A phoning list

Next I rented, from the telephone company, a list of phone numbers listed by street addresses. I copied them off for a half-mile radius round my shop, and after deleting names of my present customers, started cold-turkey canvassing. This, I told myself, would be 100 percent pleasant. No one could say what the two customers quoted above had said. And I did talk to some fine people and created some friends and customers. It takes all kinds to make a world, some wise-cracker has said. Here are three of the other kind:

"No-no-no! Don't bother me."

"I do *not* like telephone solicitors!"

"I didn't call a radio man. What right have you to call me?"

(I could think of some appropriate answers, but they would only lead to mayhem.)

It is good discipline to practice not getting hot under the collar with that small minority of . . . (can I call them people?).

Technique and consideration count

I learned some things about the telephone approach, by experience. Don't ask, "Is this Mrs. Jones?" It may be Miss Jones, or some other member of the family, and they will hang up, right away. You don't care what the name is, anyway. You want to talk to any radio or television set owner. The right opener is:

"Is this Valencia four one three five six?"

That will *always* keep the prospect on the phone (if you have dialed the right number). The next words I use are:

"This is the radio shop on the corner of Church and Duncan. How does your radio work?"

From there on, you are on your own, but *keep it short* and *do not hang on* and insist. In most cases, if they say everything is working fine (to background music of noisy and horribly distorted radio) I say, quickly:

"I'd like to leave my phone number, to use in case of an emergency. I have a truck to pick up your radio and TV and save you the trouble of bringing it in."

I started the telephone canvassing in April of this year. I set an hour a day aside for this work and it brought in too much business. I'm not kidding! I want time to play with my hobbies. I agree with Frank L. Moch in his letter to RADIO-ELECTRONICS, October, 1952, issue. I close at 5:00, and *do not* work evenings, Sundays, or holidays. Not for customers, that is. For myself, plenty! Ham radio is one of my main hobbies, but by no means my only one. I like singing, dancing, drawing, playing the organ, making tape recordings, and experimenting with electronic equipment, too!

END

MAKING METER SCALES

SPECIAL meter scales are often required for field-strength meters, v.t.v.m.'s, and other types of special equipment. Inking in new markings on the original meter scale leaves the finished apparatus with an unprofessional appearance. An amateur photographer with a good camera and enlarger can make special meter scales which are as neat and clear-cut as that supplied with the meter. If photographic equipment is not available, a professional photographer will do the work at a very reasonable price.

We constructed a new face for a 1-ma meter used in a pH electrometer which required two special scales. The

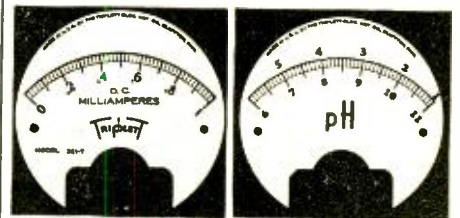


Fig. 1, left, and Fig. 2, right, show the transformation in the meter scale.

original dial scale was removed and photographed full size on Contrast Ortho film. The scale was flat-lighted to prevent reflections, and the camera stopped down. The photograph was then enlarged to about 8 inches (exact size unimportant). A camera with a ground glass is best. Otherwise center the scale to reduce distortion, and focus very carefully. A photograph of the original scale is shown in Fig. 1.

New numbers were cut from an old calendar and pasted in place on the dried enlargement of the meter scale. In cutting out numbers for this purpose, it is sufficient to cut rough squares around them because all roughness will fade out and be lost in the subsequent steps.

The completed paste-up was photographed on Contrast Ortho film to a size slightly smaller than that required for the meter. The negative was processed in D-8 developer as before. The resulting negative is a considerable reduction from the 8-inch paste-up, and therefore slight imperfections are reduced to the point where they are not noticeable.


This negative was enlarged to the exact size required by placing the original dial on the enlarging easel while adjusting the enlarger. The negative was printed on contrasty enlarging paper. Fig. 2 is the finished scale for the pH meter.—Paul Halmbacher.

(Scales which have fine graduations close together will reproduce clearer if they are photographed on Kodalith Ortho film type 2—available only as cut film in 5 x 7 inches or larger—and processed in Kodalith developer. Kodalith Fine-Line developer should be used where the scales have extra-fine line work.—Editor)

END

subminiature TUBE TESTER design....

By RICHARD J. SANDRETTO

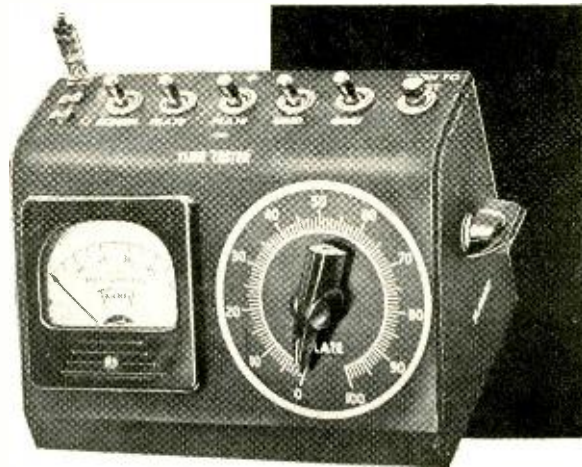

The completed tester is compact and easy to use.

SUBMINIATURE tubes are becoming increasingly popular, yet there are very few tube checkers on the market which will test them. The checker described here tests battery-type subminiatures for filament continuity, internal shorts and opens, filament emission, effectiveness of control grid, and microphonics. It features small size, light weight, and simplicity of design and construction.

This tester was built especially for hearing-aid tubes, but it will test many other types without modification. Extra grid and plate switches have been provided to accommodate multisection tubes; and, since some tube manufacturers use different base-pin arrangements, suitable sockets properly connected can be added or substituted to adapt the tester for any filament-type subminiatures.

One of the basic considerations in the design of this tester was that the tubes should be tested at approximately their normal low operating voltages. Most modern tube testers cannot be adapted easily to meet this requirement, due to the need for relatively high electrode voltages to produce readable indications on the meter. With subminiature tubes, the electrostatic charges developed by higher-than-normal voltages may attract the elements to each other to such an extent that they short out.

Circuit details

The tester schematic is given in Fig. 1.

The 50-microampere meter is placed in the circuit in such a manner that it reads filament current when the d.p.d.t. push-button switch S1 is in its normal (UP) position. Pressing the push-button switches the meter out of the filament circuit, and connects it in series with the B supply line to the plate and screen circuits.

Because filament-type subminiature tubes have widely different filament voltage and current requirements—ranging from 0.625 to 1.25 volts, and from 10 to 50 milliamperes—a 50-ohm rheostat (R1) is connected in series with the filament line. This rheostat is adjusted until the filament current is the value given in the manufacturer's data for the particular tube under test. When this control is turned past its

minimum-current (maximum resistance) position, the arm slides off the resistance element onto the insulating strip, thereby serving as an on-off switch for the entire tester.

The s.p.d.t. switches S2 and S3 were inserted to shift the control-grid d.c. potential from zero to minus $1\frac{1}{2}$ volts. The change in plate and screen current when the bias is shifted indicates the effectiveness of the control grid. When S1 is pressed down, the meter and B supply line are connected in series with the plate and screen switches S4, S5, and S6. Plate and screen currents can then be read separately or in combination by closing one or more of these switches.

A plate-screen-voltage control in the form of a voltage divider across the B battery is necessary. This control (R2) is a wire-wound potentiometer of about 30,000 ohms resistance. A large bar knob and calibrated scale permit adjusting this control to a predetermined value for the particular tube under test. The method of determining this value is explained later in this article.

Construction

The checker is assembled as shown in the photograph. The cabinet is a standard, sloping-front type, approximately seven inches wide and four inches high. While not shown in the diagram, the meter may be fused if desired.

The only critical component is the meter-shunting resistor R3. This resistor multiplies the meter reading by

1,000 when the push-button switch is in the UP position for measuring filament current. The value required is approximately 4.7 ohms, but the specific resistor for each tester must be selected as described below.

Wire the tester, with any 4.7-ohm, 10% resistor connected temporarily for R3. Caution: *Never disconnect this meter-shunting resistor unless the filament rheostat is in its OFF position.* Otherwise, a dangerously high current will flow through the meter. Connect a resistor of known value—preferably between 50 and 100 ohms—across the filament pins of one of the tube sockets; then turn the filament rheostat all the way up and measure the voltage across the known resistor. This voltage reading divided by the known resistance (E/R) gives the current flowing through the filament circuit. The meter reading multiplied by 1,000 should be the same as this calculated current. If it is not, try several 4.7-ohm (nominal value) resistors as meter shunts until you find one that makes the meter reading agree with the calculated current.

Most battery-operated subminiature tubes with the same number of base pins have the same base-pin-to-tube-element arrangement. For the very few exceptions, however, it will be necessary to wire a few sockets especially for these tube types. Provision should also be made on the panel for future socket types, because simply wiring in additional sockets later is less of a problem

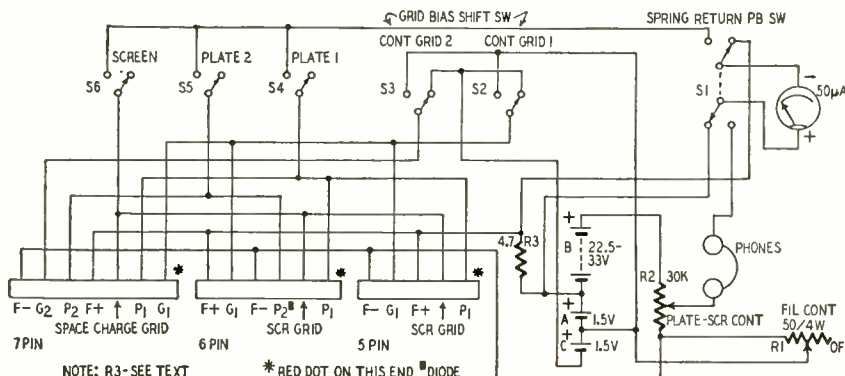


Fig. 1—Schematic of the subminiature tube tester. Extra sockets for tubes with special basing may be added as required. The duplicate plate and grid switches permit the operator to test twin-triodes, converters, and other multi-element types.

SUBMINIATURE TUBE TESTER CHART

TUBE TYPE	FIL. (ma)	PLATE-VOLTAGE CONTROL SETTING	SWITCH POSITIONS S P2 P1 G2 G1	METER READS	SWITCH POSITIONS S P2 P1 G2 G1	METER READS	SWITCH POSITIONS S P2 P1 G2 G1	METER READS
CK501AX	30	32	P * P * P	45	P * N * P	38	P * N * N	0
CK503AX	30	21	P * P * P	45	P * N * P	36	P * N * N	0
CK505AX	30	52	P * P * P	45	P * N * P	38	P * N * N	0
CK506AX	50	15	P * P * P	45	P * N * P	36	P * N * N	0
CK507AX	45	20	P * P * P	45	P * N * P	38	P * N * N	0
CK509AX	30	85	** P * P	45	** P * N	0.5		
CK510AX	50	6	P P P P P	45	P P P P N	41	P P P N N	37
CK512AX	20	39	P * P * P	45	P * N * P	36	P * N * N	0
CK516AX	20	36	** P * P	45	** P * N	0.5		
CK518AX	30	15	P * P * P	45	P * N * P	39	P * N * N	0

A specimen calibration chart for testing battery-type subminiature tubes. Other types may be substituted and new ones added as the need arises. Asterisks indicate that there is no element connected to that base pin in that type of tube. Letters under SWITCH POSITIONS headings: S—screen or space-charge grid; P2—plate 2; P1—plate 1; G2—control grid 2; G1—control grid 1.

than trying to find room for them a few years after the tester has been completed.

Flat-type subminiature tubes have a red mark at one end to indicate the proper way of inserting the tube in its socket. Mark the corresponding side of each tube socket in the same way or with some unmistakable label. Then, when inserting a tube, make the marks coincide.

Calibration and operation

Make up a chart like the one shown for calibration and testing. The chart data will vary, of course, depending on the voltage of the B battery used. To simplify directions for calibrating the tester, each of the five element switches is specified as having a POSITIVE and a NEGATIVE position. Therefore, the P and N symbols shown opposite meter readings on the chart indicate the positions of the corresponding element switches when each meter reading was obtained. Where an asterisk is shown, there is no element connected to that base pin in that tube type, and it makes no difference what position the corresponding switch is in.

Take a group of new tubes of each type you will want to test, make the necessary readings on each one, and set down the average readings for that type in the chart. Also, by comparing readings on known good tubes and known bad tubes, you can figure out what variation from the average readings a tube may have in order to still be considered good.

In using the tester, always start with the filament-current control in its OFF position. Otherwise, it may be set at a value much too high for the tube to be tested and may burn out the filament. Also make sure the plate-voltage control (R2) is at its minimum position before the tube is inserted. A pair of high-impedance headphones must be plugged into the tester, or the headphone terminals shorted out, to complete the plate circuit. (In this connection, results will be more accurate if calibration and testing are done under

the same conditions. For example, if the instrument is calibrated with the headphone terminals shorted out, and a tube of the same type is tested later with headphones plugged in, the headphone resistance may reduce the plate current below the normal value for that tube type.)

Next, insert a tube in its proper socket, aligning the plate-end markings. Now advance the filament-current control (R1) until the meter reads as close as possible to the value specified by the tube manufacturer. Let's assume the tube we are checking is a pentode. Throw the screen switch S6, plate 1 switch S4, and control-grid 1 switch S2, to their POSITIVE positions. Next, press down the meter switch S1, and advance the plate-voltage control R2 slowly until the meter reads 45 microamperes. Record the R2 setting on the chart. Now throw S4 to its NEGATIVE position, and record the new meter reading. Then throw grid switch S2 to its NEGATIVE position, leaving the plate switch alone, and record this new reading, which should be close to zero. (If the control grid connection of the tube is open, there will be no change in the screen current.) It is entirely normal for the meter to show more screen or space-charge-grid current than plate current on some tube types.

Tubes to be tested are handled the same way as for calibration purposes, except that the plate voltage control is advanced slowly with the meter switch pressed down, to the setting given in the chart. The actual reading is then compared with the standard value of 45 to see whether the variation is too great for the tube to be good. The importance of always bringing R2 up slowly from its lowest position cannot be overemphasized. If the tube under test has a screen-to-control-grid short, this fact will be shown almost instantly by a large deflection of the meter long before the plate-voltage control has been brought up to the setting shown on the chart. Remember, if this control is brought up to setting before pressing the meter switch, excessive current will

flow through the meter circuit when S1 is pressed.

To test tubes for microphonics, set the filament control, throw all element switches to their POSITIVE positions, and press the meter switch. Now, tap the tube gently while you listen in the headphones. If you hear loud ringing sounds, the tube is microphonic. Practically all tubes are microphonic to some degree, but some are so much so that

Materials for tester

Resistors: 1—30,000-ohm wire-wound potentiometer; 1—50-ohm 4-watt potentiometer; 1—4.7-ohm, 1/2-watt resistor (see text). Miscellaneous: 1 d.p.d.t. spring-return push-button switch; 3 s.p.s.t. toggle switches; 2 s.p.d.t. toggle switches; 1—0.50 microammeter; subminiature tube sockets as required; 1 pair high-impedance headphones; 1—1 1/2-volt A battery; 1—1/2-volt C battery; 1—22 1/2-volt, 30-volt, or 33-volt B battery; dial plate; meter fuse and fuse holder if desired; cabinet; knobs; hardware; wire; solder.

they are very objectionable, and this test will indicate these quickly.

Once the chart has been made up, and you have a little experience, it takes only a few seconds to check the condition of a tube. The time required for testing is much less than with most other types because these tubes are instant-heating. END

TROUBLE IN ADMIRAL TV SETS

Vertical white bars at left of the picture in Admiral 24D1, 24E1, 24F1, 24G1, and 24H1 chassis may be minimized by inserting a filter between the horizontal output transformer and the yoke. The filter consists of the following parts connected in parallel: Width coil (part No. 94A4), .01-μf, 600-volt capacitor (part 64B5-10), and a 470-ohm, 1-watt resistor (part 60B14-471). Connect the filter in series with the lead between terminal 4 of the horizontal output transformer and pin 5 of the damper tube.


Adjust the slug in the coil until the vertical bars are reduced to a minimum. In some instances, leaving off the 470-ohm resistor may provide a greater reduction.

Note: Do not confuse this trouble with the vertical bars produced by misadjustment of the horizontal drive control.—Admiral TV Service Hints.

R. F. Circuit Tester



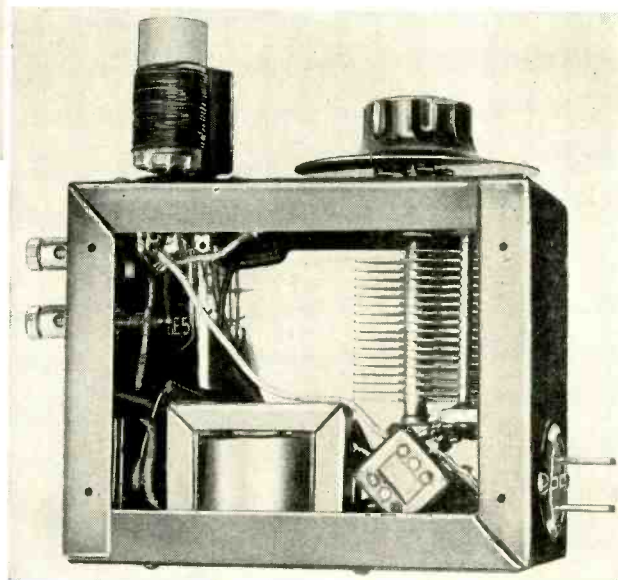Above, coil and crystal mount in the same socket.



Right, an inside view of the handy little instrument.

THIS instrument is designed to test crystals and measure coils and capacitors. It is built into a 3 x 4 x 5-inch box and has its own self-contained power supply. Only one tube is used, a 6E5 combination oscillator-electron-ray indicator. The triode section of the tube is the oscillator.

An octal socket is wired to receive crystals which are either FT-243-mounted or octal-mounted. When an octal is plugged in, it is automatically connected into a Pierce-type circuit requiring no tuning. A type 243 (1/2-inch pin spacing) is plugged into terminals 3 and 5 of the socket for the Pierce connection. In either case C should be left at minimum capacitance for the Pierce circuit.

For a conventional tuned circuit crystal oscillator, plug the crystal into terminals 1 and 3 of the octal socket, and plug a coil into 6 and 7. As seen in Fig. 1 the coil is resonated with capacitor C to the crystal frequency. This coil may be wound on a miniature 5-prong Amphenol polystyrene form (3/4-inch diameter). Three prongs of the form are cut off, leaving only pins 3 and 4. There is ample room on the octal socket for both coil and crystal.

When the circuit is in a nonoscillating condition the triode grid is at zero bias and the magic eye shadow is open. The grid goes negative during oscillation, so the angle is reduced. The more intense the oscillation is, the smaller the angle. Resistor R may be varied slightly until the angle is at or near zero when an active crystal is plugged in and when a high-Q coil is used. Sluggish crystals cause only partial closing of the eye.

To measure capacitance a "standard" coil is wound. It should resonate at the desired crystal frequency when C is set at maximum capacitance (0 on the dial). We use a 3750-kc crystal with a coil wound with 23 turns of No. 22 enameled wire to extend about 7/8 inch.

Having adjusted the eye to close with

the main dial at 0, connect an unknown capacitor across the binding posts. The circuit is thrown out of oscillation. Then rotate the main dial to restore resonance. It is better to approach from the low end of the dial (high-capacitance end) because this gives a much sharper indication on the eye. The circuit oscillates again when the unknown capacitance equals the change in C.

The main dial may be calibrated by connecting various known capacitors across the binding posts and noting the dial readings for resonance. Use a straight-line-capacitance capacitor at C to obtain a linear calibration. A curve or chart may be drawn up from the data. The instrument used here shows about 2.5 μf per dial division. A maximum of about 260 μf may be measured.

The circuit may be padded for greater capacitance values. Connect a known capacitor of 250 μf across the binding posts and use a coil which will resonate when C is at maximum setting. Remove the 250- μf and substitute the unknown, rotating C for resonance. The unknown capacitance equals 250 plus the change in C (which may be determined from the calibration curve). A maximum of 500 μf may then be measured. A bridge is more convenient if still larger capacitors are to be measured (see "Linear Resistance Bridge," RADIO-ELECTRONICS for July, 1949).

It is seldom necessary to know the exact inductance of a coil. More often it is simply desired to know the frequency range when it is tuned with a given capacitor. To check a coil, connect it across the binding posts, insert a crystal into 1 and 3 of the octal socket and then tune to resonance. The capacitance of C at any position may

be determined from its calibration chart and its known maximum capacitance. If needed, the inductance may also be calculated since the crystal frequency and the capacitance are known.

The circuit becomes an excellent r.f. signal generator by plugging a center-

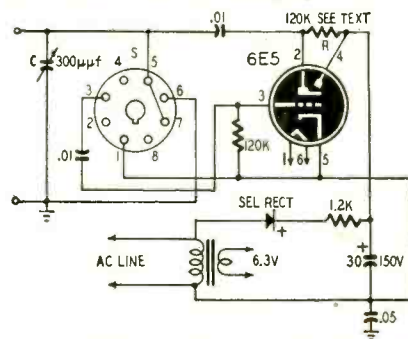


Fig. 1—This circuit can check crystals or coils and measure capacitors. tapped coil into the octal socket. The center-tap goes into terminal 1, the ends into 5 and 3. The coil may be wound over the base of a glass octal tube or an octal plug.

We have also used this circuit to

Materials for the circuit tester

Resistors: 1—1,200, 2—120,000 ohms, 1/2 watt.
Capacitors: (Mica or paper) 2—.01, 1—.05 μf , 400 volts. (Electrolytic) 1—30 μf , 150 volts. (Air-type variable) 1—300 μf , straight-line capacitance.
Miscellaneous: 1—6.3-volt filament transformer, 2—octal sockets, 1—75-ma selenium rectifier, 1—3 x 4 x 5-inch metal utility box. Dial, binding posts, hookup wire, and assorted hardware.

check points on a v.f.o. To do this, use the tester as a Pierce oscillator and couple its hot binding post to a low power transmitter. A piece of wire connected to the binding post and left near the transmitter is sufficient. As the v.f.o. is tuned through the crystal frequency, the eye shadow will show a change.

END

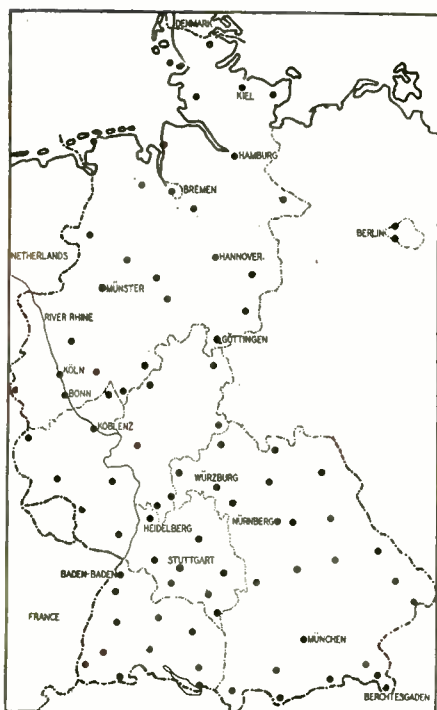


Fig. 1—Locations of stations in Western Germany's nationwide FM network.

FM BROADCASTING IN WESTERN GERMANY

Blanketing a nation with high-level signals brings FM benefits to 50 million

By PROFESSOR WERNER M. NESTEL*

BRROADCAST-FREQUENCY assignments in Europe are based on two international agreements:

1—The Atlantic City Agreement (1947), which assigned the frequency band 525-1605 kc for "medium-wave" broadcasting. (Europe also has a number of "long-wave" broadcast sta-

ble frequencies at the high-frequency end of the medium-wave band. These were all shared channels, with unreasonable power limitations, and had to compete with very powerful stations in other countries operating on the same frequencies and on adjacent channels. The fact that Western Germany, with about 50 million inhabitants and some 10 million listeners, would be open to Communist propaganda by radio as long as its own broadcasting system did not work effectively, was not taken into account at this conference.

Faced with the difficult situation, Western Germany had to devise a means of serving all its listeners through a new system of program distribution, if broadcasting as one of the most effective and important modern instruments of culture and education was not to be given up entirely. In seeking a satisfactory solution, the following possibilities were considered, and each method was tested by thorough experiments:

- b. Carrier-current distribution of programs over power lines.
- c. A combination of methods *a* and *b*.
- d. Low-power common-frequency broadcasting (on various frequencies).
- e. Short-wave broadcasting.
- f. V.h.f. AM broadcasting.
- g. V.h.f. FM broadcasting.

System *g* (FM) proved so superior to all the others that it was decided to make it available to the public as fast as possible. Much of the experience gained with FM broadcasting in the United States was utilized, but in many respects new techniques had to be developed.

The basic plan

In general, FM receiver circuits developed in the United States have such high sensitivities that large areas can be served by low-power transmitters. The comparatively low prices of sets, tubes, and parts in the United States make it possible to manufacture and sell the elaborate multitube receivers needed there. In spite of these favorable

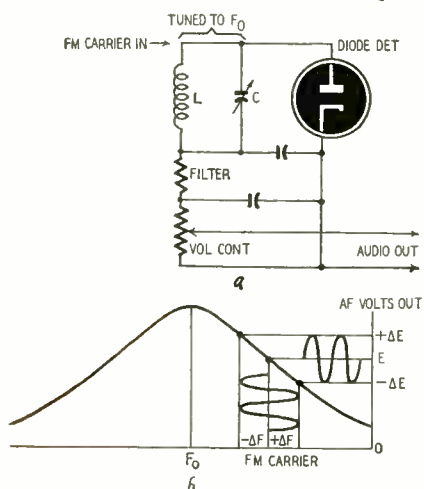


Fig. 2—(a) FM slope detector circuit. (b) Peaking the tuned circuit below the FM carrier converts carrier-frequency deviations to audio voltage variations.

tions on various frequencies between 150 and 530 kc.)

2—The Copenhagen Agreement (1948), which assigned specific channel frequencies to nearly 600 European stations operating within a relatively small geographic area.

Western Germany, which was not represented at the Copenhagen conference, was allotted only a few undesir-

- a. Carrier-current distribution of programs over telephone circuits.


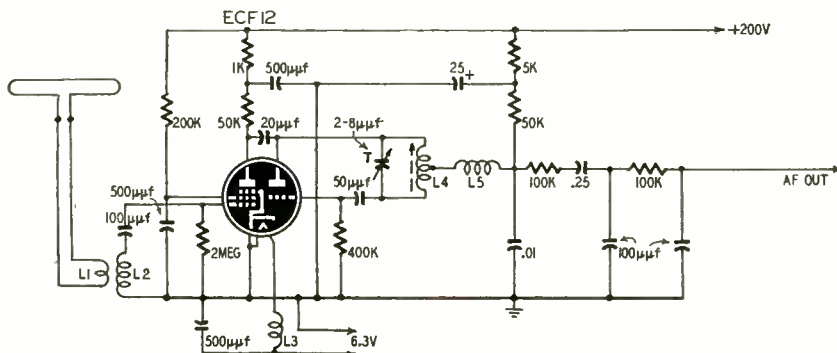


Fig. 3—Low-cost superregenerative FM adapter developed for the NWDR national network. The 6U8 and 6X8 are approximate American equivalents of the ECF12.

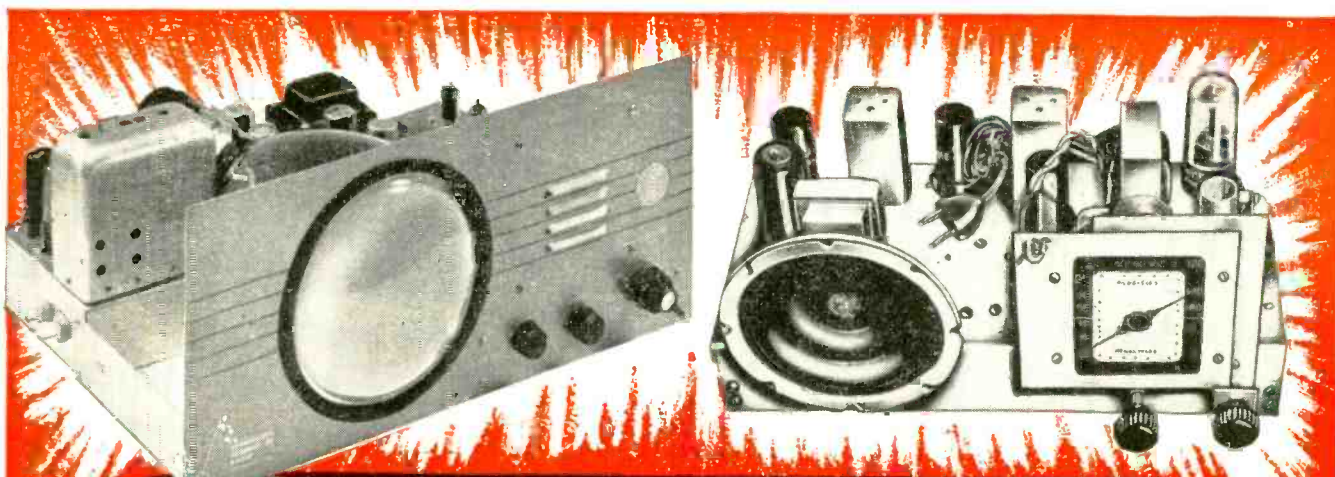*Technical Director, Nordwestdeutscher Rundfunk (Northwest German Radio System).



**TRAIN FASTER—TRAIN BETTER—TRAIN EASIER
IN 10 MONTHS—OR LESS—FOR
RADIO-TELEVISION**

Our 21st Year Training Men for Greater Incomes and Security in Radio-Television

**I SEND YOU
18 BIG KITS**

of Radio-Television parts and equipment. Much of your training will be actual construction and experimentation... the kind of truly PRACTICAL instruction that prepares you for your Radio-Television career.



Frank L. Sprayberry
President
Sprayberry Academy
of Radio

NEW! NO OBLIGATION PLAN

**You Have No Monthly Payment Contract to Sign
Pay For Your Training as You Earn and Learn**

You can get into Radio-Television, today's fastest growing big money opportunity field, in months instead of years! My completely new "package unit" training plan prepares you in as little as 10 months or even less! *No monthly payment contract to sign—thus NO RISK to you!* This is America's finest, most complete, practical training—gets you ready to handle any practical job in the booming Radio-Television industry. Start your own profitable Radio-Television shop... or accept a good paying job. I have trained hundreds of successful Radio-Television technicians during the past 21 years—and stand ready to train you, even if you have no previous experience! Mail coupon and get all the facts—FREE!



**Valuable Equipment Included
With Training**

The new Sprayberry "package" plan includes many big kits of genuine, professional Radio-Television equipment. You perform over 300 demonstrations, experiments and construction projects. You build a powerful 6-tube 2-band radio set, multi-range test meter, signal generator, signal tracer, many other projects. All equipment and lessons are yours to keep... you have practically everything you need to set up your own profitable Radio-Television service shop.

Earn Extra Money While You Learn!

All your 10 months of training is IN YOUR HOME in spare hours. Keep on with your present job and income while learning. With each training "package" unit, you receive extra plans and "Business Builder" ideas for spare time Radio-Television jobs. New television stations everywhere, open vast new opportunities for trained Radio-Television Technicians—and those in training. If you expect to be in the armed forces later, there is no better preparation than practical Sprayberry Radio-Television training.

YOU BUILD the Television set and the powerful superhet radio receiver shown above. **NO ADMISSION** to the other test units shown here (many are not shown because of lack of space). All equipment I send you is **YOURS TO KEEP.**

SPRAYBERRY ACADEMY OF RADIO 111 NORTH CANAL ST. Dept. 20-U, Chicago 6, Ill.

**MAIL COUPON
TODAY!
NO OBLIGATION**

**SPRAYBERRY ACADEMY OF RADIO, Dept. 20-U,
111 North Canal St., Chicago 6, Ill.**

Please rush to me all information on your 10-MONTH Radio-Television Training Plan. I understand this does not obligate me and that no salesman will call upon me. Be sure to include 3 books FREE.

Name..... Age.....
Address.....
City..... Zone..... State.....

**I invite you to get all the facts—
FREE TO YOU 3 BIG
RADIO-TELEVISION BOOKS**

I want you to have ALL the facts about my new 10-MONTH Radio-Television Training—without cost! Rush coupon for my three big Radio-Television books: "How to Make Money in Radio-Television." PLUS my new Illustrated Television Bulletin PLUS an actual sample Sprayberry Lesson—ALL FREE. No obligation and no salesman will call. Mail coupon NOW!



feasible, German manufacturers then were able to use two very simple receiving circuits which do not require one single component more than similar AM circuits. These are the *superregenerator*, and the *slope detector* (Fig. 2).

The cheapest receivers and adapters are superregenerators. In this connection the broadcasting authorities and the Post Office (which has the same authority over broadcasting here that the FCC has in the United States) made very strict regulations requiring that the interference produced in the superregenerative circuit must not get into the antenna. Out of this were developed 2-tube adapter circuits, with both tubes—a pentode and a triode—in a single envelope.

The circuit of a typical adapter is given in Fig. 3. One of the tubes has a fixed-tuned grid circuit and merely serves to isolate the antenna from the actual receiving tube. It blocks oscillator radiation and reduces the effects of variations in the antenna circuit on receiver tuning. The actual FM de-

10.7-mc i.f. transformers in addition to the 470-kc transformers already in the receiver. The price differential between a 3-band AM superhet and one with the added FM range is only about 10 marks (\$3).

Fig. 4 is the circuit of a typical receiver of this type. Whereas during the first year of FM broadcasting in Western Germany only one-third of the receivers made had an FM band, the current public demand is so great that now over 90% of all sets produced are equipped for FM.

In addition to these inexpensive sets, a group of first-class receivers selling at higher prices was developed. The FM sections of these receivers have r.f. amplifier stages, and limiter-discriminator-type detection, and give very high-grade reception even at great distances.

It is now an accepted fact in many parts of Western Germany that long-distance FM reception is practicable, and there are many districts where the owner of one of these FM receivers can pick up several—often as many as

selectivity, have a restricted r.f. bandwidth, which limits the sideband response to about 3 or at most 4 kc. The audio stages of such sets, including the loudspeakers, generally have reasonably good response to 8 kc. Therefore even the simplest and cheapest adapter, selling for only about 27 marks (\$6), extends the audio response from an upper limit of 3 kc to 8 kc, which is such a very great improvement that every listener is impressed.

The reduction in harmonic distortion—from 4% at 100% modulation with AM to only ½ of 1% with FM—means a corresponding improvement in audio quality at the receiving end.

Another advantage is the reduction in interference. Even receivers without noise limiters do not suffer the interference—from electrical devices or natural static—which frequently ruins medium-wave reception.

Transmission up to 15 kc over long-distance phone lines is still not practicable except at prohibitive cost. High audio quality is maintained over the entire network by a novel method of rebroadcasting from station to station. Each station is equipped with a special FM receiver and directional pickup antenna. (The usual 8-kc long-distance wire lines are provided as a standby.) The relay receiver contains the r.f. and i.f. sections of a normal receiver, but the i.f. is transposed by means of an 0.8- or 1.2-mc crystal oscillator to a frequency 0.8 or 1.2 mc higher or lower than the original r.f. carrier. See Fig. 5. This new frequency is amplified and then radiated. Receiver and transmitter thus have very simple design.

In planning the network, the channel separation and the geographic distances between transmitters were co-ordinated with the designs for very cheap and simple receivers.

The great success of FM broadcasting in Western Germany has led many other European countries to start or at least to plan FM broadcasting, and a European conference on FM and TV frequencies was held at Stockholm in June, 1952. The frequency plan decided upon at Stockholm provides for 2,000 FM stations in Europe.

Summary

In summing up, it may be said that: All the individual technical problems of FM broadcasting from the transmission, propagation, and reception points of view, have been solved in every way. FM broadcasting is economically and technically beyond reproach. In many ways it is cheaper than other systems.

If the deterioration in medium-wave reception throughout Europe since the adoption of the Copenhagen Plan is to be overcome, then thought must be given right away to the outcome of the next Wavelength Conference. Only one path will lead to improved broadcasting. Only if as many countries as possible adopt FM for all local and regional programs will it be possible to reduce the number of medium-wave transmitters. END

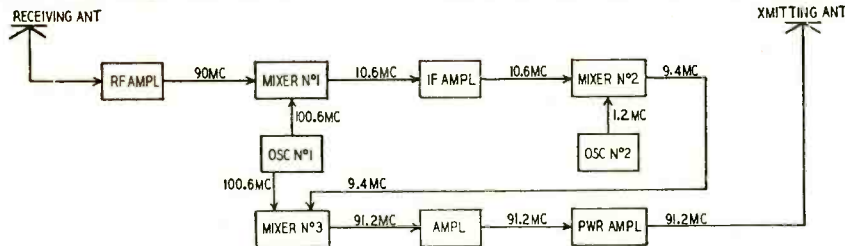


Fig. 5—Block diagram of the unique relay-receiver-transmitter which eliminates wire lines and special point-to-point links in the West German FM network.

detector is the triode section, in a superregenerative circuit. The production of the auxiliary (quench) frequency is completely reliable, even during line-voltage fluctuations. Following the superregenerative stage is a simple RC h.f. de-emphasis filter. The output is adequate for feeding the audio sections of existing receivers.

The sensitivity of these simple FM adapters is about 0.1 mv—that is, at this input voltage the “no-signal” noise is suppressed satisfactorily.

Adapters of this type, which cost between 27 and 50 German marks (\$6-\$12) can be added to any existing receiver, and the availability of such inexpensive units probably is the underlying reason for the popularity of FM broadcasting. The obsession that expensive receivers are absolutely essential no longer exists, but—curiously enough—the cheapest adapters are by no means the most popular. Most listeners prefer a slightly higher quality signal, but it was imperative psychologically to make such very inexpensive adapters available.

The second type of receiving circuit mentioned above (slope detection) is used to provide 3-band (short-, medium-, and long-wave) receivers with an additional range for FM broadcasting. Compared with the usual superhet circuit, this type requires only few additional components: a band switch with four positions instead of three; and

seven—different stations.

Another circumstance has helped in the very quick swing toward FM broadcasting in Germany. During the war and post-war years (from 1938 to 1948) German listeners could not buy receivers. When FM started, home receivers were completely out of date. Everyone was in the market for a new receiver, and it was possible to get one incorporating FM immediately.

Other advantages

FM broadcasting fulfills the two main requirements which led to its adoption.

- Coverage of areas not reached by medium-wave stations.
- Giving all listeners a choice of programs not available on medium waves under the Copenhagen plan.

Beyond this, however, it has become very evident that FM broadcasting gives the public a very welcome improvement in audio quality, and has helped to overcome certain misconceptions. According to popular belief, standard AM stations have an audio limit of about 5 kc, while FM transmits everything up to 15 kc. But since very few loudspeakers will reproduce such high frequencies satisfactorily, FM was held to be of no value from the point of view of improved quality.

The true picture is quite different. Most European medium-wave receivers, to provide adequate adjacent-channel

Let HEATHKITS CREATE AN ELECTRONICS LABORATORY OR SERVICE SHOP FOR You

New Free

MANUALS SHOW YOU HOW!

Here is visual proof of the top-dollar value offered only by Heathkits. Think of the tests made possible through the use of suggested combinations as shown below. When more instruments are required, additional Heathkits can be selected from the greatest kit instrument line ever offered.

PLANNING YOUR SERVICE SHOP


BY JOHN T. FRYE



Here is complete first-hand information written in a refreshing authoritative style by a man with over a quarter century of experience in radio and TV work. In this booklet John T. Frye discusses all factors involved in establishing a service business. Consideration is given to the type of business, location, selection of tools and instruments, bookkeeping procedures, job records, business promotion, and other similar subjects. Full explanation of the method used in computing service charges and how to establish a rate which will insure a fair and profitable return on your investment will prove very helpful. This booklet is available to Heathkit customers at no charge. Write for your free copy.


ESTABLISHING THE INDUSTRIAL ELECTRONICS LABORATORY

BY LOUIS B. GARNER, JR.

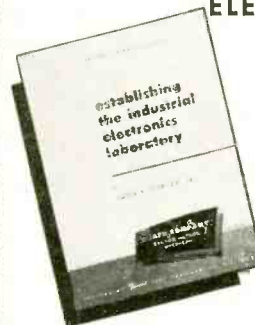

A service offered by the Heath Company for the direct assistance of those involved in laboratory work. In this booklet, by Louis B. Garner, Jr., full consideration has been given to all factors required in establishing an electronics laboratory. Information regarding the type of laboratory—laboratory layout—space allotment—lighting and service facilities—personnel—heating and air conditioning, etc. Work benches, as well as other details such as desks, shelves, cabinets, drafting tables, stools, etc., are discussed. This valuable booklet is offered to Heathkit customers at no charge. Write for your free copy.

BASIC SERVICE SHOP

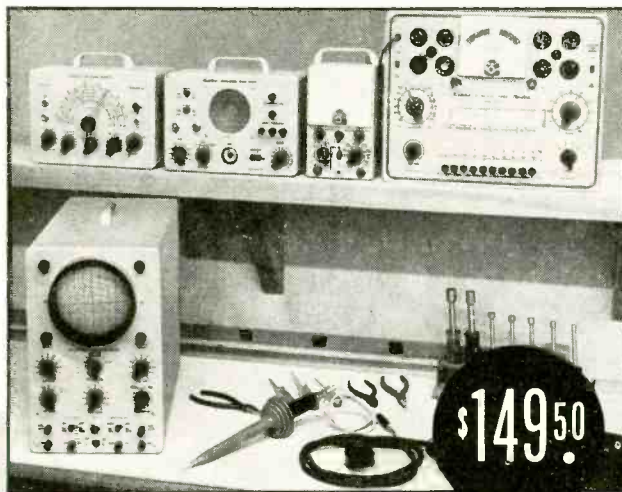

\$149.50

This group of instruments represents a typical combination of basic test equipment required for Radio and TV service work. Here is emphatic proof of the tremendous economy offered only by Heathkits. Seven basic equipment items for less money than the price quoted for a single commercially available instrument such as a general purpose oscilloscope. A serviceman can easily assemble this entire group of instruments in 45 actual working hours.

7 Complete KITS

- Oscilloscope
- VTVM
- Signal Generator
- Signal Tracer
- Tube Checker
- TV Picture Adapter
- High Voltage Probe


TYPICAL LABORATORY

11 Complete KITS

- Oscilloscope
- Voltage Calibrator
- Electronic Switch
- VTVM
- AC VTVM
- Power Supply
- Q Meter
- Decade Resistance
- Decade Condenser
- Resistance
- Substitution Box
- Audio Oscillator

This combination of eleven typical instruments, required for any Electronics Laboratory, clearly illustrates the economy offered by the purchase of Heathkit equipment. Practically an entire basic laboratory for the price of one piece of factory built equipment. These instruments can be assembled by a laboratory technician in approximately 55 actual working hours.

\$263.50

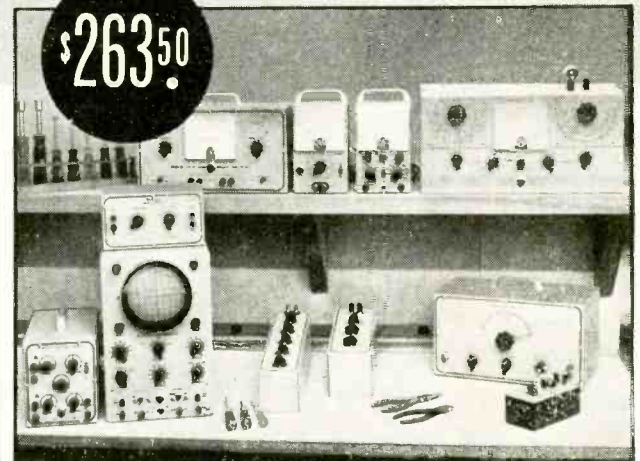

Additional information regarding these instruments will be found on the following pages. Write to the Heath Company for a free

catalogue listing all Heathkits—schematics—specifications and applications.

REPORT AGENT
ROCKE INTERNATIONAL CORP.
85 E. 40th ST.
NEW YORK CITY (16)
CABLE: ARLAB, N.Y.

The HEATH COMPANY

... BENTON HARBOR 20, MICHIGAN

NEW Heathkit "Q" METER KIT

• A HIGH QUALITY Q METER AT LOW COST.

MODEL QM-1

SHIPPING
WT. 12 LBS.


\$39.50



Measures Q and inductance of coils.



Measures Q and capacity of capacitors.

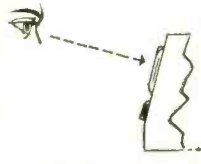

Slant face cabinet for ease in reading the meter.



• First Q METER within the price range of all.

• Read Q's of 0-500 directly on calibrated scale.

• Stable oscillator supplies R.F. frequencies of 150 kc to 18 megacycles.

• Calibrated capacitor with range of 40 mmf to 450 mmf with vernier of ± 3 mmf.

• Simple, easy operation.

• Can be used to measure small inductances or capacitors.

• Measures Q of condensers, RF resistance and distributed capacity of coils.

• Measures capacity by substitution, capacity by resonance, inductance by resonance.

• Slanted panel for convenient operation.

Another outstanding example of progressive HEATHKIT engineering. Now a highly desirable Q METER within the price range of all laboratories, schools and experimenters. No longer is it necessary to deny yourself the many measurement advantages offered by this instrument.

Use the new HEATHKIT Q METER for the following simple basic measurements: capacity by substitution, capacity by resonance, inductance by resonance and Q at the OPERATING frequency all can be read on the calibrated scales. The method used to obtain information regarding the Q of condensers, RF resistance, distributed capacity in coils, etc., is only slightly more involved. In the HEATHKIT Q METER, the generated RF signal is coupled through a cathode follower and injected across a low impedance condenser which is included in the resonant circuit under test. Large $4\frac{1}{2}$ " 50 microampere Simpson meter reads Q directly. The resonating condenser and vernier condenser are calibrated in mmf for substitution method capacity tests. The resonating condenser is also calibrated in effective capacity for resonance tests. The inductance calibration serves for rapid determination of the approximate inductance of a coil. The HEATHKIT Q METER has a generator frequency range of 150 kc to 18 megacycles. Vernier capacity covers ± 3 mmf and the resonating condenser is calibrated from 40 mmf to 450 mmf actual capacity or 40 mmf to 350 mmf effective capacity. Meter reads Q directly up to 250. Higher and lower full scale readings can be obtained by varying the injection voltage levels.

The entire kit consists of 12AT7, 6AL5, 6C4, OD3 and 6X5 tubes, 50 microampere Simpson meter, power transformer, cabinet and all other parts necessary for construction as well as instructions for assembling, testing and operation of the completed instrument.

Heathkit DECADE RESISTANCE KIT

The HEATHKIT DECADE RESISTANCE KIT is widely used by schools, experimenters and laboratories because of the extremely wide resistance range offered and the useful, dependable service provided. The DECADE consists of 5 rotary 2 deck ceramic wafer switches with silver plated contacts and twenty 1% precision resistors in a circuit which provides the resistance range of 1 ohm to 99,999 ohms in 1 ohm steps. The HEATHKIT DECADE RESISTANCE KIT is simple to construct and is housed in a beautiful polished birch cabinet with an attractive panel. The DECADE will furnish years of accurate trouble-free service.

Individual decade sections of above can be purchased separately for special applications.



MODEL DR-1
SHIPPING
WT. 4 LBS.

\$19.50

NEW Heathkit DECADE CONDENSER KIT

Extremely useful in all experimental and design work such as determination of condenser values for: compensating networks, filters, bridge impedances, tuned circuits, etc. Uses all precision silver mica condensers within $\pm 1\%$ accuracy. Values run in three decades from 100 MMFD to 0.111 MFD in steps of 100 MMFD. Smooth acting, positive detent, highest quality ceramic wafer switches make all capacitor values easy to set up and keep losses to a minimum. Low loss dielectric terminal board mounts on outside of panel for easy cleaning. Heathkit binding posts accommodate a wide variety of test leads. Comes complete with all parts, including polished birch cabinet.

Individual decade sections of above can be purchased separately.



MODEL DC-1
SHIPPING
WT. 4 LBS.

\$16.50

EXPORT AGENT
ROCKE INTERNATIONAL CORP.
13 E. 40th ST.
NEW YORK CITY (16)
CABLE ARLAB N.Y.

The **HEATH COMPANY**

... BENTON HARBOR 20, MICHIGAN

NEW *Heathkit* OSCILLOSCOPE KIT

• NEW WIDE BAND VERTICAL AMPLIFIER ± 2 DB 10 CYCLES TO 1 MC.



Direct plate connections for modulation tests.



Displays TV sync pulses correctly.



Useful to 5 mc.



Good square wave response at 100 kc.

MODEL O-8


SHIPPING
WT. 29 LBS.

\$43.50



- New wider band vertical amplifier ± 2 db from 10 cycles to 1 megacycle useful to over 5 megacycles.
- High sensitivity in vertical amplifier. .025 volts RMS per inch deflection.
- New 3 step input attenuator input ranges X1, X10, X100.
- Terminal board and rear cabinet opening provisions for direct connections to deflecting plates.
- Newly styled formed and ventilated aluminum cabinet.
- Wide band sweep generator, 15 cycles to over 100 kc. Will synchronize with 5 megacycle signal.
- 10 tube circuit featuring push pull operation of vertical and horizontal amplifiers.
- Internal synchronization on either positive or negative peaks.
- Reproduces faithfully the front and back porches of TV sync pulses. Excellent square wave reproduction to over 100 kc.
- Optional Intensifier kit available for 2200 volt operation.

Proudly announcing the new 1953 HEATHKIT Model O-8 OSCILLOSCOPE featuring the finest performance ever offered in this extremely popular kit instrument. Improved wider band vertical amplifier featuring a new 3-step input attenuator affording smooth control of the excellent .025 volts per inch vertical sensitivity. Possibility of overloading the vertical input circuit is minimized. Greater band width in the vertical channel is a decided advantage to TV service men. Permits clear observation of all TV sync pulse detail and excellent square wave reproduction over 100 kc. A handsome, ventilated cabinet with smooth rounded corners and a snug fitting drawn panel adds to the smartly styled professional appearance. Longer life is assured through cooler instrument operation. Push pull output stages in both vertical and horizontal amplifiers for balanced deflection of the spot. All of the many fine features of the previous model have been retained. Rear cabinet access to terminal board for direct connection to CR plates. The entire kit of all 10 tubes, parts, cabinet and panel as well as detailed construction manual for assembly and operation of the instrument included.

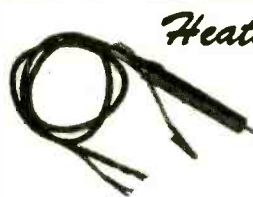


Heathkit

SCOPE DEMODULATOR PROBE KIT

Trouble shooting or aligning TV, RF, IF and video stages requires demodulation of high frequency signals before Oscilloscope observation. The HEATHKIT SCOPE DEMODULATOR PROBE KIT was specially developed for this application. Kit consists of a probe housing, crystal diode detector circuit, shielded cable and spade lugs. Assembly is simple and the probe will quickly prove its usefulness as an Oscilloscope accessory.

No. 337
SHIP. WT. 1 LB.
\$4.50

NEW *Heathkit* VOLTAGE CALIBRATOR KIT

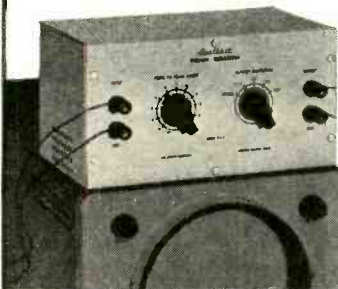


MODEL VC-1
SHIPPING
WT. 5 LBS. **\$9.50**

Use the Heathkit Voltage Calibrator with your oscilloscope to measure peak-to-peak TV complex waveshapes. TV manufacturer's specifications indicate correct peak-to-peak voltages and this kit will permit making these important measurements.

A big help to engineers in circuit work. Makes peak-to-peak voltage measurements of complex waveshapes of all kinds. Flat topped semi-square wave output of calibrator assures fast and easy measurement of any voltage between .01 and 100V peak-to-peak. The Voltage Calibrator can remain connected to your oscilloscope at all times for instant use. "Signal" position connects signal under study directly through calibrator and into scope input circuit for direct observation. Eliminates transferring leads from calibrator. *A wonderful scope accessory.*

Heathkit ELECTRONIC SWITCH KIT

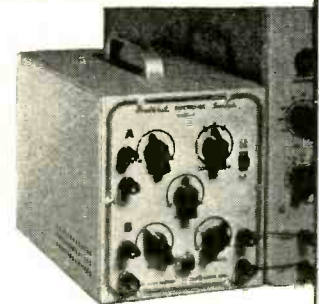

MODEL S-2
SHIPPING
WT. 11 LBS.

\$19.50

A few dollars spent for this accessory will increase the usefulness of a scope immeasurably. An electronic switch will open up a whole new field of scope applications for you. The S-2 allows TWO SIGNALS to be observed at the SAME TIME — this important feature allows you to immediately spot phase shift, clipping, distortion, etc. The two signals under observation can be superimposed or separated for individual study. Each signal input has an individual gain control for properly adjusting scope trace patterns. Has both coarse and fine frequency controls for adjusting switching time. Multivibrator switching frequency is from less than 10 cps to over 2000 cps in three overlapping ranges. Kit comes complete including 5 tubes, power transformer, all controls, instruction manual, etc. *Every scope owner should have one!*

EXPORT AGENT
ROCKE INTERNATIONAL CORP.
13 E. 40th ST.
NEW YORK CITY (16)
CABLE: ARLAS-N.Y.

The **HEATH COMPANY**

... BENTON HARBOR 20, MICHIGAN



Heathkit VACUUM TUBE **VOLTMETER KIT**

• NEW 1½ VOLT RANGE ON 1953 VTVM.

MODEL V-6

SHIPPING
WT., 7 LBS.

\$24.50

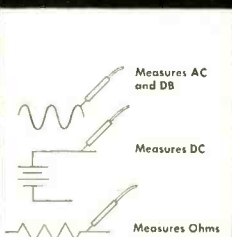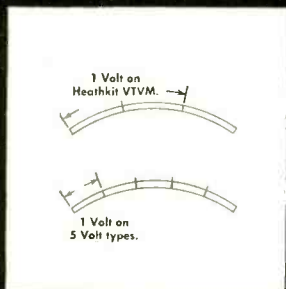

- New 1½ volt low range gives over 2" of scale per volt instead of less than ¾" found on 5 volt range type.
- Increased accuracy due to expanded scales.
- New 1500 volt DC high range gives 50% greater coverage.
- Seven ranges in all, 1½, 5, 15, 50, 150, 500 and 1500 volts DC (1000 volts maximum AC only).
- Provides proper service ranges 150 volts for AC DC work and 500 volts for AC type service.
- High input impedance, 11 megohms minimizes circuit loading.
- Variety of accessory probe kits available.
- 1% precision resistors in multiplier circuits.
- 200 microampere Simpson meter.
- Center scale zero adjust.
- Transformer operated.
- Test leads included.
- New cabinet styling.
- Large, clearly marked meter scales indicate ohms, AC volts, DC volts and DB.

The 1953 Heathkit V-6 VTVM has improved ranges! The lowest range has been moved way down to 1.5V full scale. This gives 3½" of actual scale length for the 1.5V covered — that's 2½ inches per volt!! Now you can make your low level measurements faster and with greater accuracy.

And the upper range has been moved up. Readings up to 1500V DC can be readily made with new, improved VTVM — plus readings up to 1000V on AC. Higher ranges for extended use.

New vertical chassis mounting gives added chassis space for really easy wiring — no tight corners to worry about. Uses only highest quality components throughout. Simpson 200 microampere meter movement combined with 1% precision resistors in multiplier circuit insure highly accurate and dependable readings.

AC and DC voltage ranges are 0-1.5V-5V-15V-50V-150V-500V-1500V. (1000V max. reading on AC) — a total of seven ranges for convenient, accurate readings. Instrument also measures resistance from .1 ohm to over 1 billion ohms in seven handy ranges of RX1, X10, X100, X1000, X10K, X1 Meg., — all convenient multiples of 10 with no skips. Has Db scale in red for easy identification.

New panel has tough baked on enamel finish for freedom from scratches and maximum durability. Modern styled, formed, compact cabinet with rounded edges and crackle finish is truly handsome.

Comprehensive, detailed instruction manual with step-by-step instructions, figures, pictorials, etc. makes assembly a cinch.

Be sure and look over the special accessory VTVM probes below — for added usefulness.

Heathkit R. F. PROBE KIT

SHIP. WT. 1 LBS. **\$5.50**
No. 309
Extends RF range of HEATHKIT 11 megohm VTVM to 250 megacycles ± 10%.

Heathkit 30,000 V. D.C. PROBE KIT

SHIP. WT. 2 LBS. **\$5.50**
No. 336
Provides DC multiplication factor of 100 for any 11 megohm VTVM.

Heathkit PEAK TO PEAK VOLTAGE PROBE KIT


SHIP. WT. 2 LBS. **\$6.50**
No. 338
Reads on DC scale of any 11 megohm VTVM 5 kc to 5 megacycle range.

NEW Heathkit BATTERY TESTER KIT

The new Heathkit Battery Tester measures all types of dry batteries between 1½ volts and 150 volts under actual load conditions. Readings are made directly on a three-color GOOD-WEAK-REPLACE scale that your customers can readily understand. Operation is extremely simple and merely requires that the leads be connected to the battery under test. Only one control to adjust in addition to a panel switch for A or B battery types.

The Heathkit Battery Tester features compact assembly. An accurate meter movement and wire wound control mount in the portable, rugged plastic case.

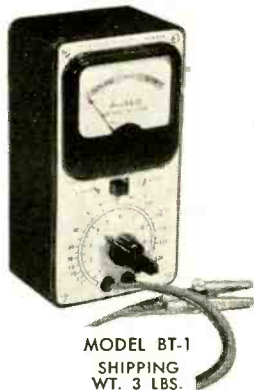Use the BT-1 to check portable radio batteries, hearing aid batteries, lantern batteries and photo flash gun batteries.



MODEL BT-1
SHIPPING
WT. 3 LBS.

\$7.50

Heathkit AC VACUUM TUBE VOLTMETER KIT

A new AC VTVM that makes possible those sensitive AC measurements required by laboratories, audio enthusiasts and experimenters. Ten full scale ranges of .01, .03, .1, 3, 1, 3, 10, 30, 100 and 300 volts RMS. 10 DB ranges from -52 to +52 DB. Frequency response within 1 DB from 20 cycles to 50 kc. Simpson 200 microampere meter with large plainly marked meter scales. Precision multiplier resistors. Two amplifier stages using miniature tubes. A unique bridge rectifier meter circuit and a clean layout of parts. Order the AV-2 today and become acquainted with the interesting possibilities offered by this instrument.



MODEL AV-2
SHIPPING
WT. 5 LBS.

\$29.50



EXPORT AGENT
ROCKE INTERNATIONAL CORP.
13 E. 40th ST.
NEW YORK CITY (16)
CABLE: ARAS-N.Y.

The HEATH COMPANY

... BENTON HARBOR 20, MICHIGAN

NEW *Heathkit* GRID DIP METER KIT

• CONVENIENT ONE HAND OPERATION.

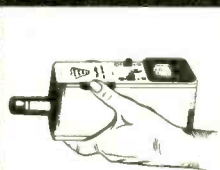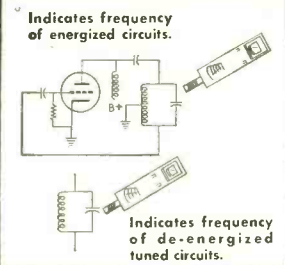

Complete unit easily held and operated with one hand.

MODEL GD-1

SHIPPING
WT. 4 LBS.

\$19⁵⁰



- New GRID DIP METER with assembled calibrated coils.
- Uses quality Simpson 500 microampere meter.
- One hand operation, extremely compact. Only 2½" wide by 3" high by 7" long.
- Variable meter sensitivity control.
- Uses newest type 6AF4 high frequency triode in a Colpitts oscillator circuit.
- Continuous coverage from 2 megacycles to over 250 megacycles in 6 ranges.
- Head phone monitoring jack.
- AC power transformer operated for maximum safety.

Here is the GRID DIP METER KIT you have been asking for. This new HEATHKIT instrument is compact, highly sensitive and easy to use. Housed in a handsome formed aluminum cabinet—rounded corners—durable oven baked finish on panel and cabinet. The entire instrument can be easily held and operated in one hand, tuning accomplished with the thumb wheel drive. This excellent design feature leaves the other hand entirely free for making circuit adjustments. The instrument with many applications — with oscillator energized, use it for finding the resonant frequency of tuned circuits, locating parasitics, determining characteristics of filter circuits, roughly tuning transmitter stages with power off, and neutralizing transmitters. Useful in TV and radio repair work for alignment of traps, filters, IF stages, peaking and compensation networks within the 2 to 250 megacycle range. With the oscillator not energized, the instrument acts as an absorption wave meter and indicates the frequency of radiating power sources. Locates spurious oscillations, as a relative indication of power in various transmitter stages, etc. Phone jack permits monitoring of AM transmitter for determination of radiated hum, audio quality, etc. (Head phones not included). Complete kit includes plug-in coils, tube, all necessary parts and detailed assembly and instruction manual.

Heathkit IMPEDANCE BRIDGE KIT



MODEL IB-1B
SHIPPING
WT. 15 LBS.

\$69⁵⁰

The HEATHKIT IMPEDANCE BRIDGE is especially useful in educational training programs, industrial laboratories and for experimental work. Use it for measuring AC and DC resistance value of resistors,

determination of condenser capacitance and dissipation factor, finding coil inductance and storage factor, electrical measurements work, etc. Quality components: GR 1000 cycle hummer, GR main control, Mallory ceramic wafer silver plated contact switches, ½% precision resistors, etc. The basic circuit is a self powered, 4 arm bridge. Choice of Wheatstone, Capacitance comparison, Maxwell or Hay bridge circuits. Resistance from 10 milliohm to 10 megohm. Capacitance 10 mmf to 100 mfd. Inductance 10 microhenry to 100 henries. Dissipation factor .002 to 1. Storage factor (Q) 1 to 1000. The IMPEDANCE BRIDGE has provisions for external generator use for measurement at other than the 1000 cycle level. Take the guess work out of electrical measurements. The HEATHKIT IMPEDANCE BRIDGE mounted in a beautiful polished birch cabinet with large easy reading panel calibrations will furnish years of accurate, trouble free measurement service.

Heathkit HANDITESTER KIT

The HEATHKIT Model M-1 HANDITESTER fulfills requirements for a portable volt ohm milliammeter. This kit features precision 1% resistors, 3 deck switch for trouble free mounting of parts, specially designed battery bracket, smooth acting ohms adjust control, beautiful molded bakelite case and a 400 microampere meter movement. 5 convenient AC and DC voltage ranges as follows: 10 - 30 - 300 - 1000 - 5000 volts. Ohms ranges 0 - 3000 and 0 - 300,000. DC milliamperes ranges 0 - 10 milliamperes and 0 - 100 milliamperes. The instrument is easily assembled from complete instructions and pictorial diagrams. Test leads are included. Carry the HEATHKIT M-1 HANDITESTER in your tool box at all times for those simple jobs and eliminate that extra trip for additional testing equipment.



MODEL M-1
SHIPPING
WT. 3 LBS.

\$13⁵⁰

EXPOSURE AGENT
ROCKE INTERNATIONAL CORP.
13 E. 40th ST.
NEW YORK CITY (16)
CABLE: ARLAB, N.Y.

The **HEATH COMPANY**

... BENTON HARBOR 20, MICHIGAN

NEW
Heathkit


AUDIO GENERATOR KIT

• RANGE EXTENDED TO 1 MEGACYCLE

MODEL AG-8

SHIPPING
WT. 16 LBS.

\$29.50

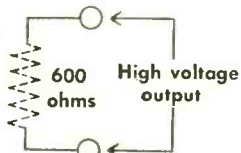

Low impedance output
High voltage output



Sine wave output
from 20 cycles to 1
megacycle.

- Improved design — new low price.
- Frequency coverage in five ranges from 20 cycles per second to 1 megacycle.
- Response flat 1 DB from 20 cycles to 400 kilocycles. Down 3 DB at 600 kilocycles. Down only 8 DB at 1 megacycle.
- Five calibrated output voltage ranges, continuously variable 1 mv, 10 mv, 100 mv, 1 v, 10 v.
- Low impedance output circuit. 600 ohms.
- Distortion less than .4 of 1% from 100 cycles per second through the audible range.
- New HEATHKIT universal type binding posts.
- Durable infra-red baked enamel panel.
- Transformer operated for safe operation.
- Sturdy, ventilated steel cabinet.

A new Audio Generator with features heretofore found in only the most expensive generators. Such features as complete coverage from 20 cycles to 1 Mc — response flat ± 1 db from 20 cycles to 400 Kc, down 3 db at 600 Kc and down only 8 db at 1 Mc.

And it has calibrated output . . . Calibrated continuously variable and step attenuator output controls allow you to easily set calibrated output voltage. Moreover, distortion is less than .4 of 1% from 100 cps through the audible range.

Oscillator section consists of a two stage resistance coupled amplifier (6SJ7 and 6AK6) utilizing both positive and negative feedback for oscillator operation and reduction of distortion. Oscillator section drives a cathode follower output power amplifier (6AK6) which isolates the oscillator from variations in load and presents a low impedance output (600 Ohms). Power supply is transformer operated and utilizes 6X5 rectifier with 2 sections of RC filtering.

An unbeatable dollar value — for here is an audio generator with wide frequency coverage, excellent frequency response, stepped and continuously variable calibrated output, high signal level, low impedance output, and low inherent distortion.

Heathkit AUDIO FREQUENCY METER KIT




MODEL AF-1

The HEATHKIT AUDIO FREQUENCY METER provides a simple and easy way to check unknown audio frequencies from 10 cycles to 100 kc between 3 and 300 volts RMS. The instrument features 7 ranges for accuracy and wide coverage. The meter itself has a quality 200 microampere Simpson movement and large clearly marked scales. The AUDIO FREQUENCY METER is transformer operated and features a voltage regulator tube to maintain constant plate voltage on the second stage. Kit supplied complete with all necessary construction material and a detailed construction manual.

SHIPPING
WT. 15 LBS.

\$34.50

NEW *Heathkit* AUDIO OSCILLATOR KIT

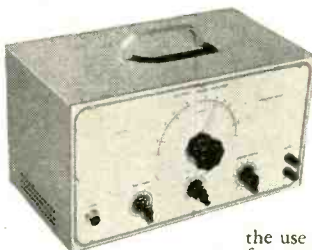

MODEL AO-1
SHIPPING
WT. 14 LBS.

\$24.50

A new Audio Oscillator with both sine and square wave coverage from 20 to 20,000 cycles . . . An instrument designed to completely fulfill the needs of the audio engineer and enthusiast — Has numerous advantages such as high level output (up to 10V obtainable across the entire range), distortion less than .6%, and low impedance output.

Special design features include the use of a thermistor in the second amplifier stage for keeping the output essentially flat across the entire range.

A cathode coupled clipper circuit produces good, clean, square waves with rise time of only 2 microseconds. Oscillator section uses 1% precision resistors in range multiplier circuit for greatest accuracy.

You'll like the operation of this fine new kit.

Heathkit SQUARE WAVE GENERATOR KIT



MODEL SQ-1
SHIPPING
WT. 14 LBS.

\$29.50

The HEATHKIT SQUARE WAVE GENERATOR is an excellent square wave frequency source with wide range coverage from 10 cycles to 100 kc continuously variable. This feature makes it useful for TV and wide band amplifier work as well as audio experimentation. The output voltage is continuously variable between 0 and 20 volts. The circuitry consists of a multivibrator stage, a clipping and squaring stage and a cathode follower low impedance output stage. The power supply is transformer operated and utilizes a full wave rectifier circuit with two sections of filtering. Another excellent HEATHKIT value at this remarkable low price. Kit includes all necessary construction material as well as complete instruction manual for assembly and operation.

ROCKE INTERNATIONAL CORP.
13 E. 40th ST.
NEW YORK CITY (16)
CABLE ARLAB-N.Y.



The **HEATH COMPANY**

... BENTON HARBOR 20, MICHIGAN

RADIO-ELECTRONICS

NEW *Heathkit* VISUAL-AURAL SIGNAL TRACER KIT

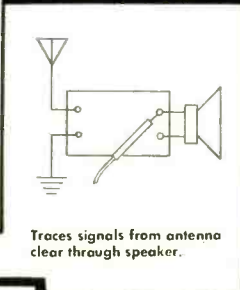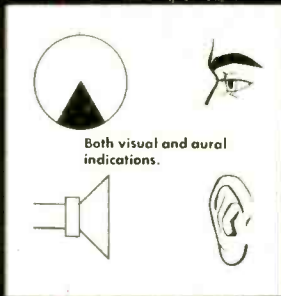• NEW NOISE LOCATOR AND WATTMETER CIRCUITS.



MODEL T-3

SHIPPING
WT. 8 LBS.


\$22.50



- Permits visual signal observation as well as aural operation.
- Two separate input channels.
- Tremendous RF channel sensitivity. Adequate for actual signal detection at receiver input.
- Separate high gain RF and low gain audio channels.
- A unique and useful noise locator circuit.
- Built-in calibrated wattmeter.
- Two separate shielded probes for RF and audio application.
- Additional test leads supplied.
- Substitution test speaker and output transformer eliminates necessity for speaker removal in service work.
- Utility amplifier. Check record changers, tuners, microphones, instrument pickups, etc.
- VTVM and Scope panel terminals.
- 5 tube transformer operated circuit.

The new HEATHKIT VISUAL AURAL SIGNAL TRACER represents one of the most convenient and useful instruments the service man can use in AM, FM and TV service work. The electron ray beam indicator constantly monitors both input channels for visual observation of the signal. Now, see and hear the signal level for easier estimation of signal strength and gain per stage in a receiver circuit. Separate high gain channel and special shielded demodulator probe for RF circuit work. Low gain channel for audio circuit investigation and for use as a noise locator. In this feature, approximately 200 volts DC is applied to a suspected circuit component and the action of the voltage in the component can be seen and heard to determine satisfactory operation. This feature alone will prove tremendously helpful in locating the source of objectionable noises in coils, transformers, resistors, condensers, cold solder joints, controls, etc. A convenient wattmeter permits rapid preliminary check for voltage distribution circuit breakdown as well as transformer failures. Use the T-3 as a universal test speaker and substitution transformer and save service time by eliminating the necessity for speaker removal on every service call. Additional service uses are: as a utility amplifier for checking the output of record changers, tuners, microphones, instrument pickups, etc. Separate panel terminals permit utilization of other shop equipment such as your Oscilloscope or VTVM. Entire kit supplied complete with 5 tubes, all necessary construction material along with a detailed step by step instruction manual for the assembly and operation of the instrument.

NEW *Heathkit* CONDENSER CHECKER KIT

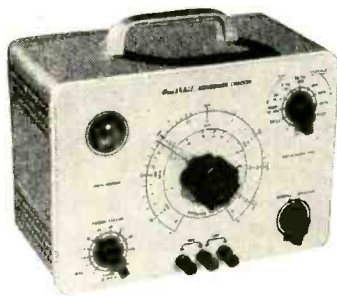

MODEL C-3
SHIPPING
WT. 7 LBS.


\$19.50

Announcing the new improved Model C-3 HEATHKIT CONDENSER housed in a new smartly styled professional appearing cabinet featuring rounded corners and snug fitting drawn panel. Adequate provisions for ventilation insures longer instrument life through cooler operation. Use the C-3 to accurately measure those unknown condenser and resistor values. All readings of condensers and resistors are read directly on the calibrated scales. Range of condenser measurements is from .00001 mfd to 1000 mfd. Calibrated resistance measurements can be made from 100 ohms to 5 megohms. A leakage test with a choice of 5 DC polarizing voltages will quickly indicate condenser operating quality under actual voltage load conditions. The spring return leakage test switch automatically discharges the condenser under test and eliminates shock hazard. An electron ray beam indicator tube is used in a new leakage test circuit for added sensitivity. The instrument is transformer operated for safety and will prove an extremely welcome addition to your shop equipment. The kit is furnished complete with all necessary parts, test leads and includes a step by step detailed construction manual for assembly and operation.

Heathkit TV ALIGNMENT GENERATOR KIT

MODEL TS-2
SHIPPING
WT. 20 LBS.

\$39.50

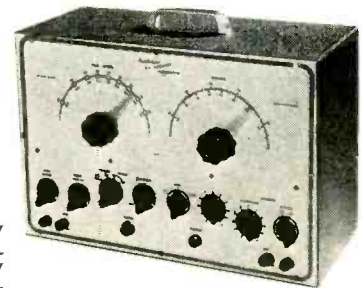

Here is an excellent TV ALIGNMENT GENERATOR designed to do TV service work quickly, easily and properly. The Model TS-2 when used in conjunction with an Oscilloscope provides a means of correctly aligning TV receivers. The instrument furnishes a frequency modulated signal covering in 2 bands the range of 10 to 90 megacycles and 150 to 230 megacycles. An absorption type frequency marker covers from 20 to 75 megacycles in 2 ranges; therefore you have a simple, convenient means of checking IF's independent of oscillator calibration. Sweep width is variable from 0 to 12 megacycles. Other excellent features are horizontal sweep voltage controlled with a phasing control — both step and continuously variable attenuation for setting the output signal to the desired level — a convenient stand by switch — and blanking for establishing a single trace with a base reference level. Make your work easier, save time and repair with confidence. Order your HEATHKIT TV ALIGNMENT GENERATOR now.

EXPORT AGENT
ROCKE INTERNATIONAL CORP.
13 E. 40th ST.
NEW YORK CITY (16)
CABLE: ARIAS, N. Y.

The **HEATH COMPANY**


BENTON HARBOR 20, MICHIGAN

Heathkit TUBE CHECKER KIT


MODEL TC-1

SHIPPING
WT. 12 LBS.

\$29.50

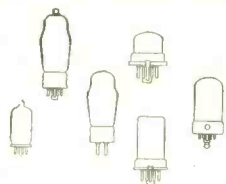

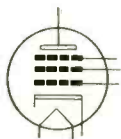Checks 7, 8, 9 prong tubes, octals, loctals, 7 and 9 prong miniatures, 5 prong Hytrons, pilot lights.



Checks for opens, shorts, emission, filament and filament tap continuity.



- Beautiful counter type birch cabinet.
- 4½" Simpson 3 color meter.
- Simplified setup procedure.
- Built-in gear driven roll chart.
- Checks emission, shorted elements, open elements and continuity.
- Complete protection against obsolescence.
- Sockets for every modern tube.
- Blank for new types.
- Individual element switches.
- Contact type pilot light test socket.
- Line adjust control.

PORTABLE TUBE CHECKER KIT MODEL TC-1P

Same as TC-1 except supplied with polished birch cabinet (with removable lid) instead of counter type cabinet. Shipping weight 14 lbs. **\$34.50**

No. 365 Polished Birch Tube Checker Cabinet only. Shipping Weight 7 lbs. **\$7.50**

With the HEATHKIT TC-1 TUBE CHECKER test all types of tubes commonly encountered in AM-FM and TV receiver circuits. Test setup procedure is simplified, rapid and flexible. Tube quality is read directly on a beautiful 4½" Simpson three color BAD - ? - GOOD scale that your customers can readily understand. Panel sockets accommodate 4, 5, 6 and 7 prong tubes, octals, loctals, 7 and 9 prong miniatures, 5 prong Hytrons, a blank socket for new tubes and a contact type socket for quick checking of pilot lights. Built-in gear driven roll chart for instant reference. Neon short indicator, individual three position lever switch for each tube element, spring return test switch, line set control to compensate for supply voltage variations. At this low price, no service man need be without the advantages offered by the HEATHKIT TUBE CHECKER.

Heathkit TV PICTURE TUBE TEST ADAPTER

Use your HEATHKIT TUBE CHECKER with this new TV TEST ADAPTER to determine picture tube quality. Check for emission and shorts, independent of TV power supply. Consists of standard 12 pin TV tube socket, 4 feet of cable, octal socket connector and data sheet. Quickly prove TV picture tube condition to yourself and your customer.



No. 355
Ship. Wt. **\$4.50**
1 lb.

Heathkit RESISTANCE SUBSTITUTION BOX KIT

MODEL RS-1
SHIPPING
WT. 3 LBS.

\$5.50

NEW HEATHKIT RESISTANCE SUBSTITUTION BOX KIT provides switch selection of any single one of 36 RTMA 1 watt 10% standard value resistors, ranging from 15 ohms to 10 megohms. This coverage available in 2 ranges in decades of 15, 22, 33, 47, 68 and 100. Housed in rugged plastic cabinet featuring new HEATHKIT universal type binding posts. The entire kit priced less than the retail value of the resistors alone.

Heathkit BATTERY ELIMINATOR KIT

A clean 6 volt d-c supply source is definitely required for successful automobile radio servicing. Has a continuously variable d-c output from 0 to 8 volts. It can be safely operated at a steady 10 ampere level and will deliver up to 15 amperes for intermittent periods. The voltage output terminals are completely isolated from the chassis to accommodate additional service applications such as supplying bias voltages or d-c substitution voltages for battery operated tube filament circuits.

The output of the Battery Eliminator is constantly monitored by a d-c voltmeter and a d-c ammeter. The circuit features an automatic overload relay of self resetting type. For additional protection, a panel mounting fuse is provided. Build this kit in a few hours and pocket a substantial savings.

MODEL BE-3
SHIPPING
WT. 20 LBS.


\$24.50

Heathkit VIBRATOR TESTER KIT

Repair time is valuable, and the Heathkit Vibrator Tester will save you hours of work. Instantly tells the condition of the vibrator under test — and the check is thorough and complete. Checks vibrator for proper starting, and the easy-to-read meter indicates the quality of output on large BAD-GOOD scales. Tests both inter-rupter and selfrectifier types of vibrators. Five different sockets for checking hundreds of vibrators.

Operates from any battery eliminator capable of delivering continuously variable voltage from 4-6V at 4 amps. The Heathkit BE-3 Battery Eliminator is ideal for operating this kit.

Faulty vibrators can be spotted within seconds and you're free to go on to other service jobs.

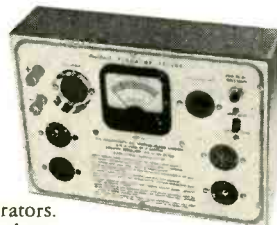MODEL VT-1
SHIPPING
WT. 7 LBS.

\$14.50

EXPORT AGENT
ROCKE INTERNATIONAL CORP.
13 E. 40th ST.
NEW YORK CITY (16)
CABLE: APLAS, N.Y.

The HEATH COMPANY

... BENTON HARBOR 20, MICHIGAN

RADIO-ELECTRONICS

Heathkit SIGNAL GENERATOR KIT

MODEL SG-7

SHIPPING
WT. 7 LBS.

\$19.50



Modulated or unmodulated RF output.



400 cycle sine wave output.

- Step attenuated RF output.
- 6 to 1 vernier dial ratio.
- Turret mounted coil sub-assembly.
- Pre-calibrated and adjusted coils.
- Hartley RF oscillator circuit.
- Colpitts oscillator 400 cycle sine wave output.
- Modulated or unmodulated RF output.
- Frequency coverage on fundamentals 160 kc to 50 megacycles in five ranges. 51 megacycles to 150 megacycles on calibrated harmonics.
- RF output in excess of 100,000 microvolts.
- Audio output 1 1/2 to 2 volts.
- AC transformer operated.
- Professionally styled cabinet.
- Infra red baked enamel panel.

The new HEATHKIT Model SG-7 SIGNAL GENERATOR easily fulfills requirements for a controllable, modulated or unmodulated source of variable frequency. A convenient 400 cycle sine wave output is available for audio work. All RF oscillator coils are precision wound and adjusted to calibration before shipment thereby assuring maximum accuracy. The coils, band switch and tuning condenser all mount as a turret assembly so as to offer the advantage of short wiring leads and easy mounting of parts. The RF output circuit is of the low impedance type obtained by the use of cathode coupling to the output jacks. The level of RF output is varied by means of the RF step and RF output control. Use the HEATHKIT SG-7 as an RF signal source modulated or unmodulated for radio repair, laboratory work, experimental testing, 400 cycle sine wave audio testing, checking RF stages, alignment of both AM and FM IF stages, marker generator for TV alignment, etc. The kit is transformer operated and utilizes miniature tubes for ease in handling high frequency. Panel jacks and a convenient switching system permit either external or internal modulation. The entire kit is supplied complete with tubes and all necessary material as well as a detailed step by step instruction manual for the assembly and operation of the instrument.

Heathkit INTERMODULATION ANALYZER KIT



MODEL IM-1
SHIPPING WT. 18 LBS.

\$39.50

The HEATHKIT MODEL IM-1 is an extremely versatile instrument specifically designed for measuring the degree of interaction between two

signals caused by a specific piece of apparatus, or a chain of equipment. It is primarily intended for tests of audio equipment but may be used in other applications such as making tests of microphones, records, recording equipment, phonograph pickups and loud speakers. Use it for checking tape or disc recordings, as a sensitive AC voltmeter, as a high pass noise meter for adjusting tape bias, cutting needle pitch or other applications. High and low test frequency source, intermodulation section, power supply and AC voltmeter all in one complete unit. Percent intermodulation is directly read on three calibrated ranges, 30%, 10% and 3% full scale. Both 4 to 1 and 1 to 1 ratios of low to high frequencies easily set up. At this low kit price YOU can enjoy the benefits of Intermodulation analysis for accurate audio interpretations.

Heathkit LABORATORY REGULATED POWER SUPPLY KIT



MODEL PS-2
SHIPPING WT. 20 LBS.

\$29.50

New HEATHKIT LABORATORY POWER SUPPLY provides continuously variable regulated DC voltage output

from 160 volts to 400 volts depending on load. Panel terminals supply separate 6.3 V. AC supply at 4 amperes for filament circuits. A 3 1/2" plastic cased panel mounted meter provides accurate metered output for either voltage of current measurements. Exceptionally low ripple content of .012% admirably qualifies the HEATHKIT LABORATORY POWER SUPPLY for high gain audio applications. Ideal for laboratory work requiring a reference voltage for meter calibration or for plotting tube characteristics. In service work, it can be used as a separate variable voltage supply to determine the desirable operating voltage in a specific circuit. Use it as a DC substitution voltage in trouble shooting TV circuits exhibiting symptoms of extraneous undesirable components in plate supply circuits. Entire kit, including all 5 tubes now available at this low price.

EXPORT AGENT
ROCKE INTERNATIONAL CORP.
13 E. 40th ST.
NEW YORK CITY (16)
CABLE: ARAMNY

The **HEATH COMPANY**

... BENTON HARBOR 20, MICHIGAN

Heathkit WILLIAMSON TYPE AMPLIFIER KIT


The new HEATHKIT WILLIAMSON TYPE AMPLIFIER incorporates the latest improvements described in Audio Engineering's "Guiding the Lily." 5881 output tubes and a new Peerless output transformer with additional primary taps afford peak power output of well over 20 watts. Frequency response ± 1 db from 10 cycles to 100 kc. allows reproduction of highs and lows with equal crispness and clarity. Harmonic and intermodulation distortion have been reduced to less than $\frac{1}{2}$ of 1% at 5 watts. This eliminates the harsh unpleasant qualities which contribute to listening fatigue. Make this amplifier the heart of your radio system to achieve the fine reproduction that is the goal of all music lovers.

The HEATHKIT PREAMPLIFIER (available separately or in combination with the amplifier kit) features inputs for magnetic or low level cartridges, crystal pickups and tuners, turnover control for LP or 78 type records, individual bass and treble tone controls each providing up to 15 DB of boost or attenuation. Special notched shafts on preamplifier controls and switches adaptable to custom installation. The preamplifier can be mounted in any position and a liberal length of connecting cable is supplied. No radio experience is required to construct this amplifier. All punching, forming, or drilling has already been done. The complete kit includes all necessary parts as well as a detailed step by step construction manual with pictorial diagrams to greatly simplify the construction.

ACROSOUND TRANSFORMER OPTION. If desired, the output transformer with the kit will be the Acrosound output transformer, type TO-300. The use of this transformer permits ultra-linear operation as described in Audio Engineering's "Ultra-Linear Operation of the Williamson Amplifier."



Heathkit FM TUNER KIT

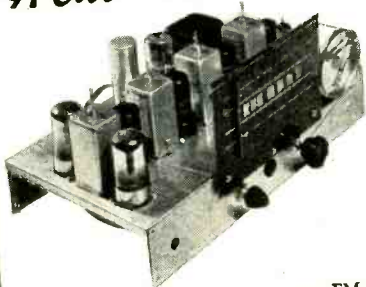

MODEL FM-2
SHIPPING
WT. 9 LBS.

\$22⁵⁰

The HEATHKIT MODEL FM-2 TUNER specifically designed for simplified kit construction features a preassembled and adjusted tuning unit. Three double tuned IF transformers and a discriminator transformer are used in an 8 tube circuit. Smooth tuning is obtained through a 9 to 1 ratio vernier drive using a calibrated six inch slide rule type dial. The usual frequency coverage of 88 to 108 megacycles is provided. Experience the thrill of building your own FM tuner. Operate it through your amplifier or radio and enjoy all the advantages of true FM reception. Transformer operated power supply to simplify connections to all types of audio systems. The kit is supplied complete with all 8 tubes and a necessary material required for construction. A complete instruction manual simplifies assembly and operation.

PRICES OF VARIOUS COMBINATIONS

- W-2 Amplifier Kit** (Incl. Main Amplifier with Peerless Output Transformer, Power Supply and WA-P1 Preamplifier Kit) Shipping Weight 39 lbs. **\$69⁵⁰**
- W-2M Amplifier Kit** (Incl. Main Amplifier with Peerless Output Transformer and Power Supply) Shipping Weight 29 lbs. Shipped express only **\$49⁷⁵**
- W-3 Amplifier Kit** (Incl. Main Amplifier with Acrosound Output Transformer, Power Supply and WA-P1 Preamplifier Kit) Shipping Weight 39 lbs. Shipped express only **\$69⁵⁰**
- W-3M Amplifier Kit** (Incl. Main Amplifier with Acrosound Output Transformer and Power Supply) Shipping Weight 29 lbs. Shipped express only **\$49⁷⁵**
- WA-P1 Preamplifier Kit only.** Shipping Weight 7 lbs. Shipped express or parcel post. **\$19⁷⁵**

Heathkit ECONOMY 6 WATT AMPLIFIER KIT



MODEL A-7
SHIPPING
WT. 10 LBS.

\$14⁵⁰

The HEATHKIT Model A-7 amplifier features beam power, push pull output with frequency response flat $\pm 1\frac{1}{2}$ DB from 20 to 20,000 cycles. Separate volume, bass and treble controls. Two input circuits, output impedances of 4, 8, and 15 ohms. Peak power output rated at full 6 watts. High quality components, simplified layout, attractive gray finished chassis, break off type adjustable length control shafts and attractive lettered control panel.

THE MODEL A7A amplifier incorporates a preamplifier stage with special compensated network to provide the necessary voltage gain for operation with variable reluctance or low output level phono cartridges. Excellent gain for microphone operation in a moderate powered sound system..... **\$16.50**

Heathkit HIGH FIDELITY 20 WATT AMPLIFIER KIT

The HEATHKIT MODEL A-8 amplifier kit was designed to deliver high fidelity performance with adequate power output at moderate cost. The frequency response is within ± 1 DB from 20 to 20,000 cycles. Distortion at 3 DB below maximum power output at 1000 cycles is only .8%. The amplifier features a Chicago power transformer in a drawn steel case and a Peerless output transformer with output impedances of 4, 8, and 16 ohms available. Separate bass and treble tone controls permit wide range of tonal adjustment to meet the requirements of the most discerning listener. The amplifier uses a 6SJ7 voltage amplifier, a 6SN7 amplifier and phase splitter and two 6L6's in push pull output and a 5U4G rectifier. Two input jacks for either crystal or tuner operation. The kit includes all necessary material as well as a detailed step by step construction manual.



MODEL A-8
SHIPPING WT. 19 LBS.

\$33⁵⁰

MODEL A8-A features an added 6SJ7 stage (preamplifier) for operating from a variable reluctance cartridge or other low output level phono pickups. Can also be used with a microphone. A 3 position panel switch affords the desired input service. **\$35.50**

EXPORT AGENT
ROCKE INTERNATIONAL CORP.
13 E. 40th ST.
NEW YORK CITY 10 (16)
CABLE: ARAB-N.Y.


The **HEATH COMPANY**

... BENTON HARBOR 20, MICHIGAN

Heathkit SUPERHETERODYNE RECEIVER KITS

- High gain dual iron core tuned type IF transformers
- AC transformer operation for safety
- Continuously variable tone control
- Sturdy punched and plated steel chassis
- Ideal for custom installation
- Full AVC action
- Inverse feedback for improved frequency response
- Kit supplied with all necessary construction material except speaker and cabinet. (Available separately if desired).

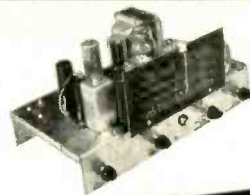6 tube all wave circuit.
3 ranges, continuous coverage 550 kc to over 20 megacycles, shipping wt. 11 lbs.



Model AR-1
\$23.50

5 tube broadcast band
550 to 1600 kc coverage,
shipping wt. 11 lbs.

Model BR-1
\$19.50



Two excellent radio receiver kits featuring clean design and open layout for simplified construction. Satisfy that urge to build your own radio receiver and select the model which meets your requirements. Both receivers feature continuously variable tone control, a radio phono switch and phono input and an AC receptacle for the phono motor. A six inch calibrated slide rule type dial with a 9 to 1 ratio vernier dial drive insures easy tuning.

SHIPPING INFORMATION

ON PARCEL POST ORDERS include postage for weight shown and insurance. (We insure all shipments.) Don't worry about sending more than the correct amount — if you send us too much, every extra cent will be promptly returned.

ON EXPRESS ORDERS do not include transportation charges. They will be collected by Express Agency on delivery.

ORDERS FROM CANADA must include full remittance for merchandise.

Orders processed on the same day received. Customers notified of unavoidable delay.

U. S. postal or express money orders, bank drafts or checks are acceptable. Do not send loose coins or stamps.


ALL PRICES SUBJECT TO CHANGE WITHOUT NOTICE

EXPORT AGENT
ROCKE INTERNATIONAL CORP.
12 E. 40th ST.
NEW YORK CITY (10)
CABLE: ARIAD-NY

The HEATH COMPANY

... BENTON HARBOR 20, MICHIGAN

ORDER BLANK

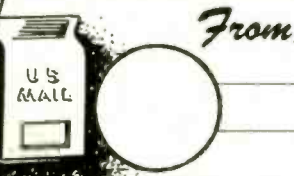

From _____

SHIP VIA

- Parcel Post
- Express
- Freight
- Best Way

(PLEASE PRINT)

QUANTITY	ITEM	PRICE	QUANTITY	ITEM	PRICE
	Heathkit Oscilloscope Kit—Model O-8 (29 lbs.)	\$43.50		Heathkit Square Wave Gen. Kit—Model SQ-1 (14 lbs.)	\$29.50
	Heathkit Intensifier Kit (O-8 only) No. 339 (1 lb.)	7.50		Heathkit AC VTVM Kit—Model AV-2 (5 lbs.)	29.50
	Heathkit Voltage Calibrator Kit—Model VC-1 (5 lbs.)	9.50		Heathkit Intermodulation Analyzer Kit—Model IM-1 (18 lbs.)	39.50
	Heathkit Electronic Switch Kit—Model S-2 (11 lbs.)	19.50		Heathkit Regulated Power Supply Kit—Model PS-2 (20 lbs.)	29.50
	Heathkit Scope Demodulator Probe Kit No. 337 (1 lb.)	4.50		Heathkit Handitester Kit—Model M-1 (3 lbs.)	13.50
	Heathkit T.V. Alignment Generator Kit—Model TS-2 (20 lbs.)	39.50		Heathkit Decade Resistance Kit—Model DR-1 (4 lbs.)	19.50
	Heathkit Q Meter Kit—Model QM-1 (12 lbs.)	39.50		Heathkit Decade Condenser Kit—Model DC-1 (4 lbs.)	16.50
	Heathkit Grid Dip Meter Kit—Model GD-1 (4 lbs.)	19.50		Heathkit Impedance Bridge Kit—Model IB-1B (15 lbs.)	69.50
	Heathkit VTVM Kit—Model V-6 (7 lbs.)	24.50		Heathkit Battery Tester Kit—Model BT-1 (3 lbs.)	7.50
	Heathkit RF Probe Kit No. 309 (1 lb.)	5.50		Heathkit Resistance Substitution Box Kit—Model RS-1 (3 lbs.)	5.50
	Heathkit HV Probe Kit No. 336 (2 lbs.)	5.50		Heathkit F.M. Tuner Kit—Model FM-2 (9 lbs.)	22.50
	Heathkit Peak-to-Peak Volt. Probe Kit No. 338 (2 lbs.)	6.50		Heathkit Broadcast Receiver Kit—Model BR-1 (11 lbs.)	19.50
	Heathkit Visual-Aural Signal Tracer Kit—Model T-3 (8 lbs.)	22.50		Heathkit Three Band Receiver Kit—Model AR-1 (11 lbs.)	23.50
	Heathkit Condenser Checker Kit—Model C-3 (7 lbs.)	19.50		Heathkit Amplifier Kit—Model A-7 (10 lbs.)	14.50
	Heathkit RF Signal Generator Kit—Model SG-7 (7 lbs.)	19.50		Heathkit Amplifier Kit—Model A-7A (10 lbs.)	16.50
	Heathkit Tube Checker Kit—Model TC-1 (12 lbs.)	29.50		Heathkit Amplifier Kit—Model A-8 (19 lbs.)	33.50
	Heathkit T.V. Tube Adapter No. 355 (1 lb.)	4.50		Heathkit Amplifier Kit—Model A-8A (19 lbs.)	35.50
	Heathkit Battery Eliminator Kit—Model BE-3 (20 lbs.)	24.50		Williamson Type Amplifier Kit (Type:)	
	Heathkit Vibrator Tester Kit—Model VT-1 (7 lbs.)	14.50		Shipped express only	
	Heathkit Audio Generator Kit—Model AG-8 (16 lbs.)	29.50		WA-P1 Preamplifier Kit (7 lbs.) (Shipped exp. or p.p.)	19.75
	Heathkit Audio Oscillator Kit—Model AO-1 (14 lbs.)	24.50			
	Heathkit Audio Frequency Meter Kit—Model AF-1 (15 lbs.)	34.50			

*Please ship C.O.D. Postage enclosed for _____ lbs. Enclosed find Check Money Order for _____

TEST TECHNIQUES FOR TRANSISTORS

The experimenter is in a helpless position when it comes to checking his transistors. This article gives him needed information.

By RUFUS P. TURNER

RIDER TEK- FILE*

packaged

tv

service

information—

factory—

authorized

factory—

approved

for easy

tv servicing...

tailor-made

for over

2800

receivers...

only

\$2 per pack

(at your jobbers)

*dependable replacement parts listing beginning with Pack 57

JOHN F. RIDER

Publisher, Inc.

480 Canal Street
New York 13, N. Y.

In a vacuum tube, there is no physical connection, as such, between the grid and plate. In a transistor, on the other hand, a definite amount of resistance appears between the emitter and collector. The transistor in a grounded-base circuit may be considered as a 3-terminal resistance network having direct and transfer resistances. Output changes in the transistor affect the input.

Because of the differences between

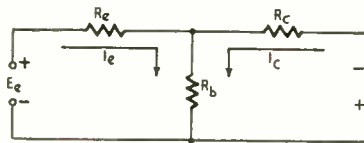


Fig. 1—Transistor equivalent circuit.

tubes and transistors, common tube-testing techniques are not always applicable or adequate for checking transistors. In checking transistors, attention often must be paid to the values of input, output, and transfer resistances.

Measuring resistances

Fig. 1 shows the equivalent 3-terminal resistance network of a transistor when the unit is connected in a ground-base circuit. (E , I , and R represent voltage, current, and resistance. Subscript letters b , c , and e refer to base, collector, and emitter, respectively.) Polarities of emitter voltage E_e and collector voltage E_c are shown in this illustration for the point-contact transistor. The op-

posite polarities are employed with junction-type transistors.

Resistance R_e represents the emitter resistance, R_c the collector resistance, and R_b the base resistance. The input resistance of the transistor is equal to $R_e + R_b$ and lies between 150 and 1,000 ohms in commercial point-contact transistors. The output resistance is equal to $R_c + R_b$ and is between 10,000 ohms and 1 megohm or more in commercial point-contact types.

Four distinct resistances should be checked in a d.c. test of transistor characteristics. We will designate these as R_1 , R_2 , R_3 , and R_4 . These resistances have definite relationships to R_b , R_c , R_e , and transfer resistance R_m . Since transistor resistance values are never measured with a bridge or ohmmeter—to do so would probably seriously damage the transistor—we calculate the resistance values from measured voltages and currents.

The table lists R_1 to R_4 , showing the transistor resistance values to which these parameters correspond and the voltage and current characteristics which determine their values. It is important to note that either the input or output circuit is open in each of the resistance measurements.

Fig. 2 shows four circuits for measuring transistor voltages and currents for calculating the values of R_1 , R_2 , R_3 , and R_4 . Operation of each of these circuits is discussed separately in the following paragraphs.

Resistance R_1 . See Fig. 2-a. This meas-


TRANSISTOR TEST RESISTANCES

$$R_1 = R_e + R_b = \frac{E_e}{I_e} \quad \text{Measured with output circuit open.}$$



$$R_2 = R_b = \frac{E_e}{I_e} \quad \text{Measured with input circuit open.}$$

$$R_3 = R_b + R_m = \frac{E_e}{I_e} \quad \text{Measured with output circuit open.}$$



$$R_4 = R_c + R_b = \frac{E_c}{I_c} \quad \text{Measured with input circuit open.}$$




Now I've got a
HIGH PAYING CAREER in
TELEVISION
RADIO & ELECTRONICS
—thanks to the famous
CRESCENT SCHOOL
Home Study Course!

Yes, a brilliant future
awaits you in **TELEVISION**.
My advice is to send for the
details now about the
CRESCENT course!

It's the **CRESCENT**
SCHOOL
FREE sample
lesson. Boy!
That was fast!



Gosh—I can actually earn while
I learn with the practical
CRESCENT SCHOOL course!



Learning in my
spare time is so
easy with these
illustrated,
simplified
lessons!



Wow! I built this swell TV
set myself with my complete
CRESCENT kits!



I'm sure proud of my
CRESCENT SCHOOL certificate
...now I can really start
on a big career!



Imagine—my own business, a home,
a new car—and the **CRESCENT**
SCHOOL course started it all!

Also Day and Evening Classes
Trained at our School.

Approved under the G.I. Bill,
CRESCENT SCHOOL has trained
thousands for **BIG** careers in the
fast-growing **TELEVISION**
industry.



CRESCENT SCHOOL
"One of the largest
schools of its kind"

ACT TODAY to start on a profitable
career in **TELEVISION!**
Get your
sample lesson **FREE!**

SEND COUPON TODAY!

CRESCENT SCHOOL Dept. E3
500 Pacific St., B'klyn 17, N. Y.

Sirs: Rush your **FREE** sample lesson and full details about
the **CRESCENT SCHOOL** Course—at no obligation to me!
 Home Study Course Residential Course


NAME

ADDRESS

CITY ZONE STATE



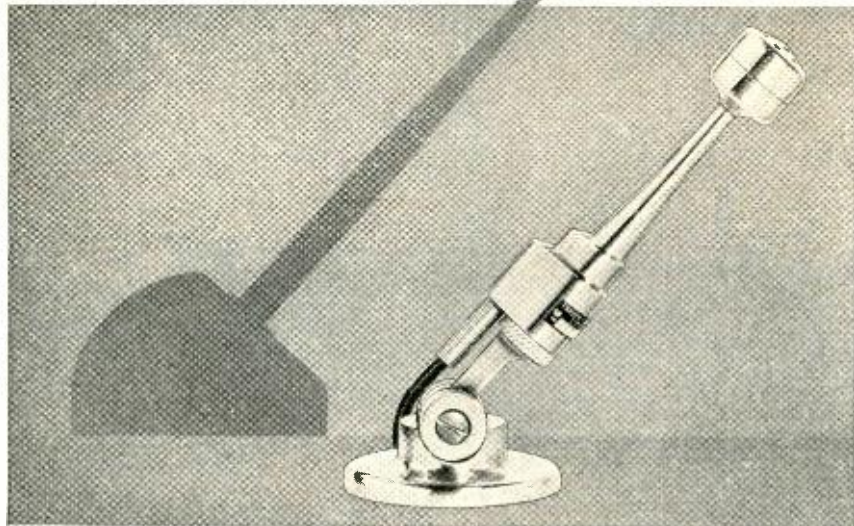Smaller than a desk pen — just as convenient



The NEW Turner C-4 Stand for Model 80 Microphone

The new C-4 stand gives complete maneuverability and convenience with the Model 80. It pivots the microphone in a 135° arc for any operational angle — swings parallel to base needing little more packing space than two packs of cigarettes.

The microphone is held firmly by the unique, positive-action hinge, yet moves smoothly and easily to any desired position without adjustment. Microphone quickly and easily removed.

This new, matching stand is solidly built of die-cast zinc overlaid with beautiful satin chrome plate. It is heavy enough to prevent tipping — it will not slide with the weight of the cord. The C-4 stand complements the graceful shape of the Model 80; the combined unit is an attractive but inconspicuous addition to a speaker's table. Ideal for use with wire recorders, public address systems, pulpits, office and factory call systems, amateur operators and other similar uses.

Model C-4 matching stand. 3/8" — 27 thread. List Price.....\$ 5.75
 Model 80 Microphone. List Price.....\$15.95



THE TURNER COMPANY

933 17th St., N. E. Cedar Rapids, Iowa
 In Canada: Canadian Marconi Company, Toronto, Ont., and Branches
 Export: Ad Auriema, Inc., 89 Broad Street, New York 4, N. Y.

OVER 50,000
 TECHNICIANS
 HAVE LEARNED

HOW TO GET
 THE MOST OUT
 OF BASIC TEST
 EQUIPMENT

for A.M. - F.M. - TV



ONLY 40¢
 103 pages. Invaluable information that will help you re-double the value of your basic test equipment.

'SERVICING BY
 SIGNAL SUBSTITUTION'
 A BEST SELLER FOR OVER 12 YEARS!
 (NEW, UP-TO-DATE, 12th EDITION)

The Modern, Simplified, Dynamic Approach to Receiver Adjustment & Alignment Problems.

- ★ Nothing complicated to learn
- ★ No extra equipment to purchase
- ★ Universal... non-obsolete
- ★ Employs only Basic Test Instruments

Ask for "S.S.S." at your local Radio Parts Jobber or remit 40¢ in small stamps or coin directly to factory.

PRECISION APPARATUS COMPANY, INC.
 92-27 HORACE HARDING BLVD., ELMHURST 4, N. Y.

urement is made with the transistor output circuit open. Starting from zero, increase the d.c. voltage until emitter current I_e , indicated by the d.c. milliammeter, corresponds to the maximum value specified by the transistor manufacturer for grounded-base operation. The high-resistance d.c. vacuum-tube voltmeter then reads the emitter voltage E_e . The value of R_1 is calculated from the emitter current (in amperes) and the emitter voltage: $R_1 = E_e / I_e$.

Resistance R_2 . See Fig. 2-b. Standard test procedure requires that this measurement be made with the transistor input circuit open. By using a high-

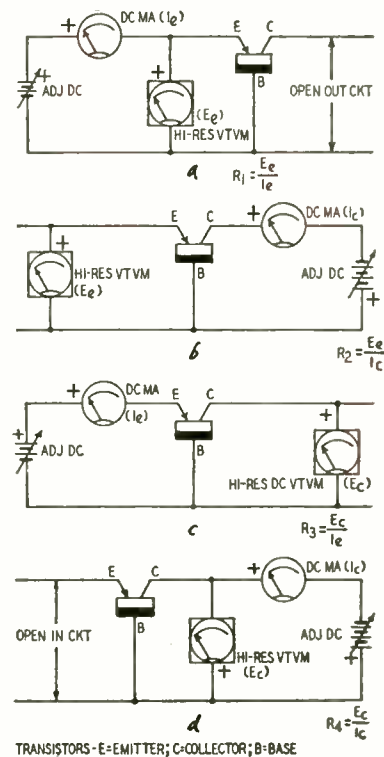


Fig. 2—Connections for the various measurements described in the text.

resistance d.c. vacuum-tube voltmeter to measure E_e , the equivalent of an open input circuit is obtained. For the highest resistance, it is advisable to use a meter which has no input resistors at all (such as General Radio type 1800-A) if such an instrument is available.

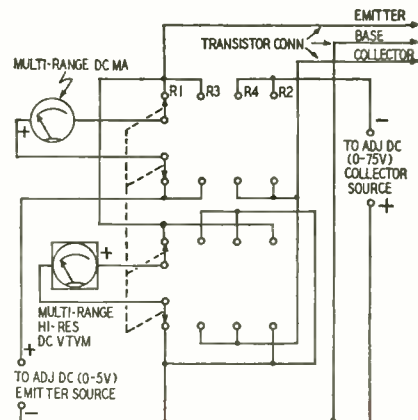



Fig. 3—A quick and efficient set-up for making the tests indicated in Fig. 2.

THE *Original* AND *Only*

CO-Lateral

TV ANTENNA

PATENT NO. 2,566,287

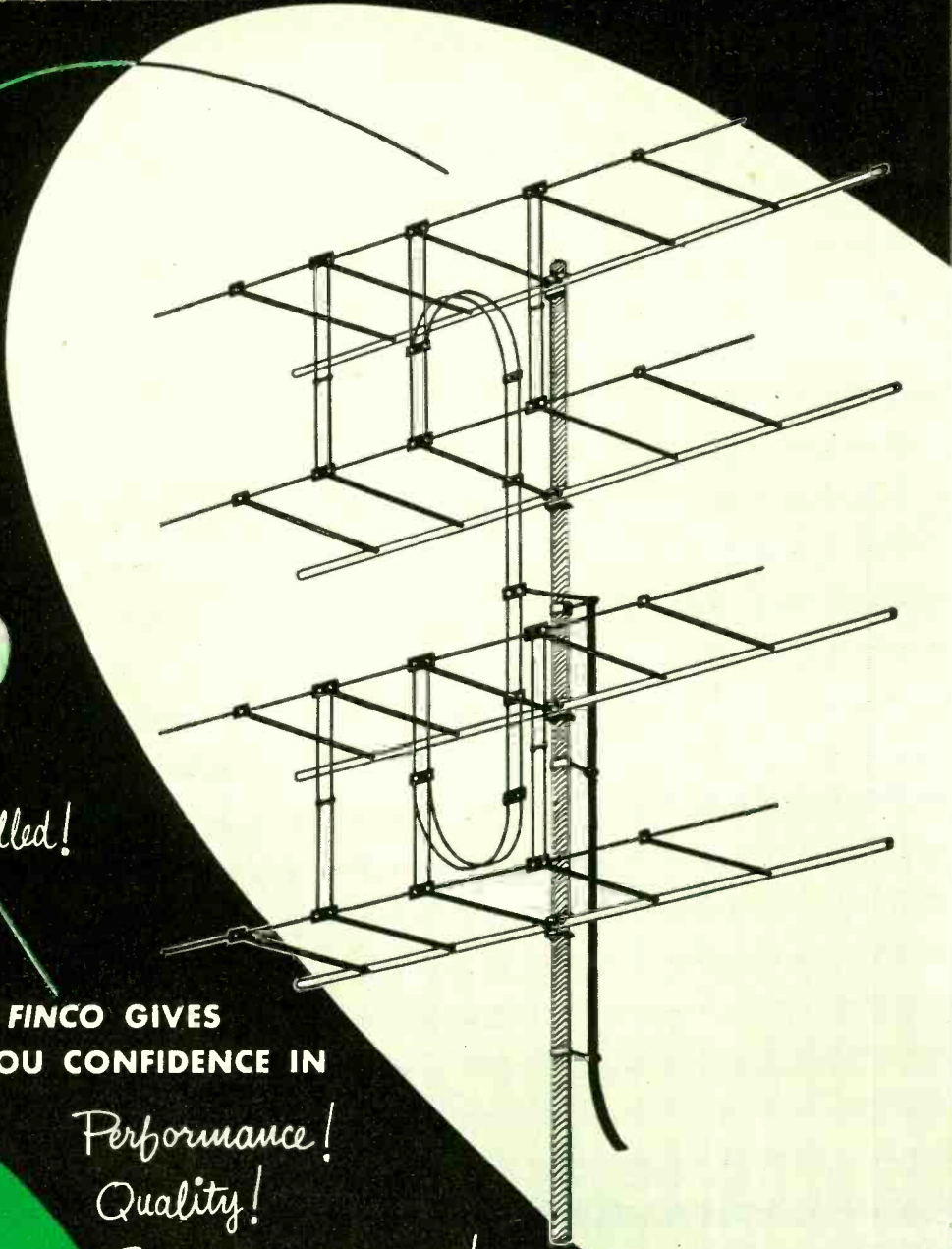

FINCO

PATENTED

*imitated but
never equalled!*

**ONLY FINCO GIVES
YOU CONFIDENCE IN**

*Performance!
Quality!
Sales Reputation!*

● in fringe areas
tens of thousands
of **FINCO CO-Lateral**
installations have proved
FINCO superiority!



The FINNEY Company

4612 ST. CLAIR

CLEVELAND 3, OHIO

COMPLETE TRAINING FOR BETTER RADIO-TV SERVICE JOBS



Let these two great new Ghirardi training books teach you to handle all types of AM, FM and TV service jobs by approved professional methods—and watch your efficiency and earnings soar!

Completely modern, profusely illustrated and written so you can easily understand every word, these books pave the way to fast, accurate service on any type of home radio-TV-electronic equipment ever made. Each book is brand new. Each contains the latest data on the latest methods and equipment—NOT a re-hash of old-out-of-date material. Each is co-authored by A. A. Ghirardi whose famous RADIO PHYSICS COURSE and MODERN RADIO SERVICING were, for 20 years, more widely used for military, school and home study training than any other books of their type!

THE NEW Ghirardi RADIO-TV SERVICE LIBRARY

Almost 1500 pages and over 800 clear illustrations show step by-step how to handle every phase of modern troubleshooting and servicing.

1—Radio and Television Receiver TROUBLESHOOTING & REPAIR

A complete guide to profitable professional methods. For the novice, it is a comprehensive training course. For the experienced serviceman, it is a quick way to "brush up" on specific jobs, to develop improved techniques or to find fast answers to puzzling service problems. Includes invaluable "step-by-step" service charts. 820 pages, 417 illus., price separately \$6.75.

2—Radio and Television Receiver CIRCUITRY AND OPERATION

This 669-page volume is the ideal guide for servicemen who realize it pays to know what really makes modern radio-TV receivers "tick" and why. Gives a complete understanding of basic circuits and circuit variations; how to recognize them at a glance; how to eliminate guesswork and useless testing. 417 illus. Price separately \$6.

New low price . . . easy terms

If broken into lesson form and sent to you as a "course", you'd regard these two great books as a bargain at \$50 or more! Together, they form a complete modern servicing library to help you work faster and more profitably. Completely indexed so you can look up needed facts in a jiffy. Under this new offer, you save 75¢ on the price of the two books—and have the privilege of paying in easy installments while you use them! No lessons to wait for.

10-DAY EXAMINATION PRIVILEGE

Dept. RE-33, Rinehart Books, Inc. Technical Division, 232 Madison Ave., New York 16, N. Y.

Send me GHIRARDI'S NEW 2-VOL. SERVICE LIBRARY. I enclose \$3 and will send you \$3 a month for three months until the total price of only \$12.00 plus a few cents postage is paid. It is understood I may read the books for 10 days. Then, if not satisfactory, I will return them postage paid and you agree to refund my \$3 and cancel the remaining installments. (Books shipped postpaid if full remittance accompanies order. Same return privilege.)

Name _____
 Address _____
 City, Zone, State _____
 Employer's Name & Address _____

OUTSIDE U.S.A.—\$13.00 cash only. Same 10-day return privilege with money refunded.

Starting from zero, increase the voltage until I_c , (indicated by the milliammeter) corresponds to the maximum value specified by the transistor manufacturer for grounded-base operation. The v.t.v.m. then indicates emitter voltage E_e . The value of R_2 is calculated from the equation $R_2 = E_e / I_c$, where I_c is in amperes.

Resistance R_3 . See Fig. 2-c. This measurement is made with the transistor output circuit open. As in measuring R_2 , a high-resistance d.c. v.t.v.m. keeps the output circuit resistance high enough to simulate an open circuit while measuring collector voltage E_c .

Starting from zero, increase E_c until the milliammeter indicates an emitter current, I_e , corresponding to the maximum value specified by the manufacturer for grounded-base operation. The d.c. v.t.v.m. then indicates the resulting collector voltage, E_c . R_3 is calculated from the emitter current (in amperes) and the collector voltage: $R_3 = E_c / I_e$.

Resistance R_4 is measured using the setup in Fig. 2-d. This test is made with the input circuit open. Starting from zero, increase the voltage until I_c corresponds to the maximum value specified by the transistor manufacturer for grounded-base operation. The d.c. vacuum-tube voltmeter then indicates the collector voltage, E_c . $R_4 = E_c / I_c$.

The following values are specified for the Raytheon point-contact transistor

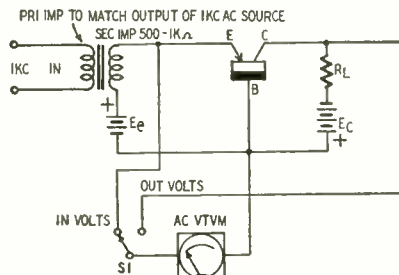


Fig. 4—Circuit for directly checking the voltage amplification of transistors.

type CK716: $R_1 = 150$ to 450 ohms, $R_2 = 25$ to 140 ohms, $R_3 = 15,000$ to $70,000$ ohms, and $R_4 = 10,000$ to $40,000$ ohms.

Practical d.c. tester

Fig. 3 shows a practical arrangement for quickly setting up the test circuits shown in Fig. 2 for transistor resistance measurements.

The 4-pole, 4-position rotary selector switch switches the d.c. milliammeter and v.t.v.m. to the proper transistor electrodes, and shifts the polarity of the instruments and opens the input or output circuit of the transistor to correspond with the circuits in Fig. 2. Rotating the selector switch through positions R_1 , R_2 , R_3 , and R_4 automatically sets up the test circuits in Figs. 2-a, 2-b, 2-c, and 2-d, respectively. Meter and power-supply polarities are shown for point-contact transistors. Reverse both meter and power supply polarities when checking N-P-N junction transistors. The switching circuit, meters, and power supplies might be combined into a single, self-contained transistor d.c. tester

BLAK-RAY SELF-FILTERING ULTRA VIOLET LAMP



BLAK-RAY 4-watt lamp, model X-4, complete with U-V tube. This lamp gives long-wave ultra-violet radiation having a wave-length of 3654 to 4000 angstrom units. Some of the substances made to fluoresce visibly when illuminated by U-V light are certain woods, oils, minerals, milkstone, cloth, paints, plastics, yarn, drugs, crayons, etc. This lamp is self-filtering and the invisible U-V rays are harmless to the eyes and skin. Equipped with spectral-finish aluminum reflector. Consumes only 4 watts and can be plugged into any 110 volt 50-60 cycle A.C. outlet. Will give 2000 to 3000 hours of service. It weighs but 1 3/4 lbs. Approved by the Underwriters Laboratories and has a built-in transformer so that it may be safely used for long periods when necessary. Extra U-V tubes are available.

Ship wt. 4 lbs. ITEM NO. 125 UNUSUAL BUY \$14.75

POWERFUL ALL PURPOSE MOTOR

Sturdy shaded pole A.C. induction motor. 15 watts, 3000 rpm. 3"x2"x1 3/4". 4 mounting studs; 3/8" shaft, 3/16" diameter; 110-120 volts, 50-60 cycles, A.C. only. When geared down, this unit can operate an 18" turntable with a 200 lb. dead weight. Use it for fans, displays, timers and other purposes. Ship wt. 2 lbs. ITEM NO. 147 UNUSUAL BUY \$2.45

WATTHOUR METER

Leading makes—reconditioned. Ideal for trailer parks. 100-110 volts, 60 cycles, 2-wire A.C. 5 amp. Heavy metal case 8 1/2" x 6 1/4" x 5". Easy to install. Ship. wt. 14 lbs. ITEM NO. 33 NOW ONLY \$4.50

WESTERN ELECTRIC BREAST MIKE

Lightweight 1 lb. carbon microphone. Aircraft type. Breastplate mounting, adjustable 2-way swivel. Easily fastened straps. For home broadcasts, communications etc. Complete with 6 foot cord, hard rubber plug. Sherardized plate, non-rusting finish. Ship. wt. 2 lbs. ITEM NO. 152 NEW LOW PRICE \$1.75

AMAZING BLACK LIGHT

250-watt ultra-violet light source. Makes fluorescent articles glow in the dark. Fits any lamp socket. For experimenting, entertaining, unusual lighting effects. Ship. wt. 2 lbs. ITEM NO. 87 A SAVING AT \$2.45


250 POWER TELESCOPE LENS KIT

Make your own high powered 6 ft. telescope! Kit contains 2" diam., 75" focal length, ground and polished objective lens and necessary eye pieces. Magnifies 50x to 250x. Full instructions. Ship. wt. 1 lb. ITEM NO. 123 YOU SAVE AT \$2.95

HUDSON SPECIALTIES CO. 40 West Broadway, Dept. RE-3-53 New York 7, N. Y.

I am enclosing full remittance for items circled below. (Be sure to include shipping charges.) OR, my deposit of \$_____ Ship balance C.O.D. MINIMUM C.O.D. ORDER \$5.00. C.O.D. ORDERS ACCEPTED ONLY WITH 20% DEPOSIT INCLUDE SHIPPING CHARGES.

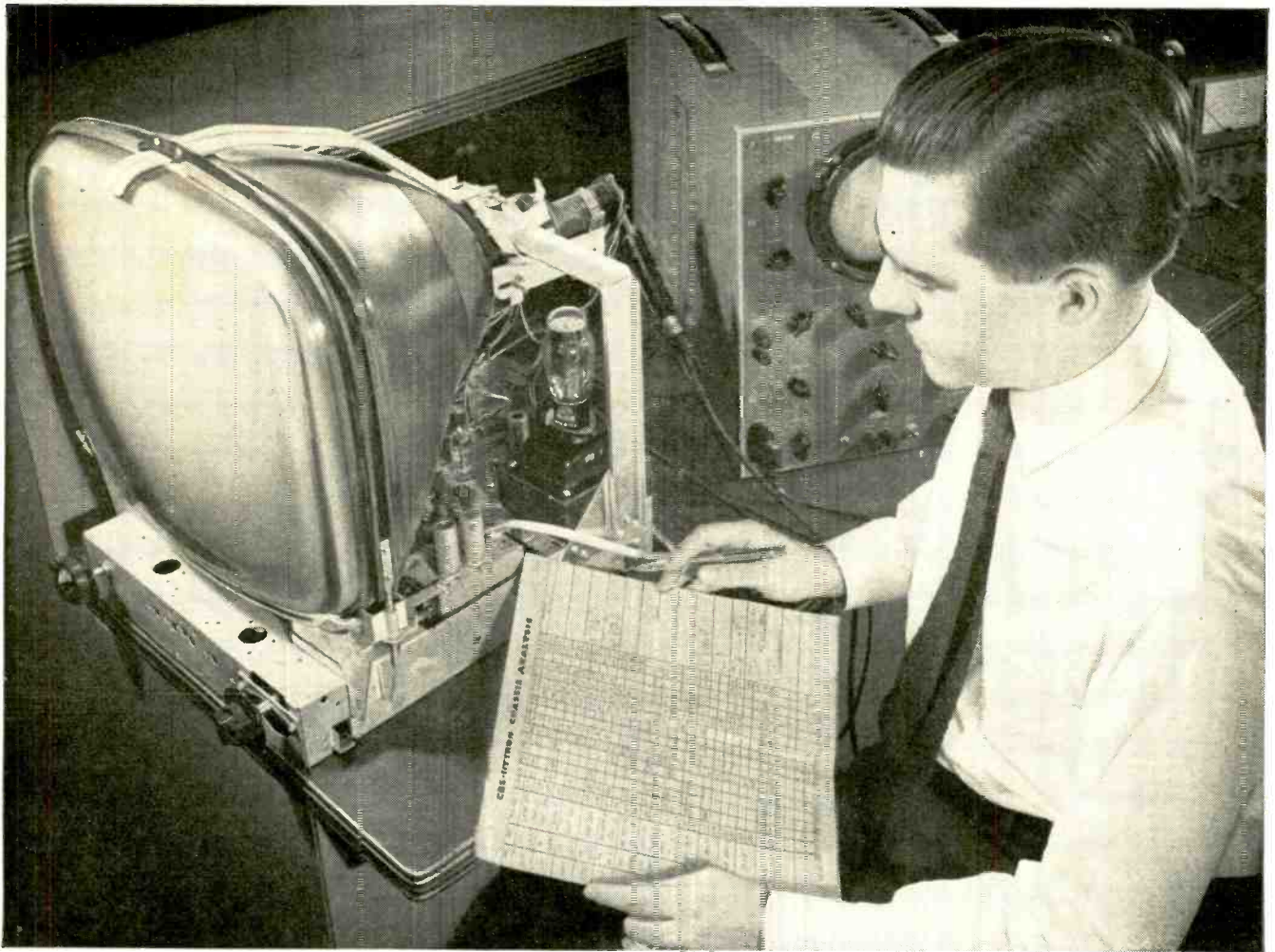Circle Items Wanted
 87 147 33 152 125 123
 Name _____ Please Print Clearly
 Address _____
 City _____ Zone _____ State _____



Bring back that New-Set Sparkle with **Performance-Tested Tubes**

Meet John Cunningham, a CBS-Hytron Commercial Engineer. John is beginning at the beginning for you. Socket by socket, he is analyzing the tube requirements of a brand-new TV set design.

John knows the superior performance demanded. He concentrates his know-how on insuring top tube operation within standard specification limits. He tests sample tubes . . . checks analysis data. Working hand-in-glove with the set designer . . . and with CBS-Hytron engineers . . . he assures control of the characteristics of all tubes for this new chassis. Finally he achieves . . . from rectifiers to picture tube . . . the perfect performance all of this engineering team (and you) seek.

Constantly CBS-Hytron carries on teamwork like this. Socket by socket analysis. Day in, day out — with 9 out of 10

leading TV set makers. Both tube and set engineers pool their specialized skills. Scores of the nation's foremost TV set engineers help make endless CBS-Hytron improvements. Help assure you of unsurpassed performance in virtually *all* leading TV sets.

Small wonder that your CBS-Hytron replacement tubes recapture that new-set sparkle. Please *your* customers. Cut *your* call-backs. Profit more. Take advantage of CBS-Hytron engineering. Demand CBS-Hytron . . . your logical replacement tube, because it is performance-tested *all* the way . . . from original to replacement.



MANUFACTURERS OF RECEIVING TUBES SINCE 1921
HYTRON RADIO AND ELECTRONICS CO.

A Division of Columbia Broadcasting System, Inc.
Main Office: Danvers, Massachusetts

NEW... BIGGER... BETTER

FREE!

6th Edition

**CBS-HYTRON
Reference Guide
for
Miniature Electron
Tubes**



- A CBS-Hytron original . . . it's unique.
 - All miniatures, regardless of make.
 - 250 miniature types . . . 87 new.
 - 111 basing diagrams . . . 34 new.
 - Similar larger prototypes indicated.
 - 8 packed pages of data you need daily.
 - And it's FREE!
- Get your copy of this old friend brought up to date now. Ask your CBS-Hytron jobber or write direct . . . today!



Don't spoil the reflection

Your reputation as a skilled Service Man depends a great deal on your choice of replacement parts. The performance of replacement speakers reflects upon your ability and knowledge. Be sure the reflection is favorable. Specify Utah* speakers—and your customers will say "That Service Man Knows His Business!"

*All Utah speakers have exclusive Utah Universal Angle Mounting.



FREE . . . WRITE TODAY FOR THE NEW UTAH REPLACEMENT SPEAKER CATALOG 5201
Export Dept. Rocke International Corporation, N. Y. C.

RADIO PRODUCTS CO., INC.
HUNTINGTON, INDIANA

A WHOLLY OWNED SUBSIDIARY OF NEWPORT STEEL CORPORATION

CODE SENDING RECEIVING SPEED

Be a "key" man. Learn how to send and receive messages in code by telegraph and radio. Commerce needs thousands of men for jobs. Good pay, adventure, interesting work. Learn at home quickly through famous Candler System. Qualify for Amateur or Commercial License. Write for FREE BOOK.

CANDLER SYSTEM CO.
Dept. 3-C, Box 928, Denver 1, Colo., U.S.A.

MAGNETIC PICKUP LOOP

Pickup phone conversations without connecting. Make your own Electric Guitar Pickup. Produce your own Electric organ tones. An ideal tool for experimenters—extremely sensitive—Put your inventive genius to work. . . . Supplied with full instructions on its various interesting possibilities together with schematic for a 3-tube amplifier to work with Loop or can very easily be attached to Radio. . . . ORDER NOW—\$3.95 COD plus postage or send \$3.95 we pay postage.

GALVANICS
Dept. T-10 Box 158 Hackensack, N. J.

FREE! from KLIPZON
Write today for folder.
"THE VERSATILE CRYSTAL PROBE"

Tells how to get V.H.F. performance from your V.T.V.M. or V.O.M. by using KLIPZON SELFHOLDING CRYSTAL PROBES. How to make "one man" TV antenna orientation easy!

Other valuable information on timesaving and convenient SELFHOLDING PRODS, CONNECTORS, SHIELDED LEADS and ADAPTORS. See KLIPZON at your local distributor.

UNITED TECHNICAL LABORATORIES
204 LITTLETON RD. • MORRISTOWN, N. J.

somewhat similar in function and operation to a laboratory tube tester.

Current amplification

The *current amplification figure*, designated by α , the Greek letter *alpha*, is an important property of the transistor. It may be determined in two ways. One way is in terms of the resistance values measured according to the instructions in the preceding paragraphs: $\alpha = R_c/R_e$. The other involves setting up the transistor with rated d.c. emitter and collector voltages for grounded-base operation, and with separate milliammeters for the simultaneous reading of emitter and collector currents. The static values of I_e and I_c are recorded. Then, without changing the collector voltage E_c , shift the emitter current a small amount (dI_e) and observe the resulting shift (dI_c) in collector current. Current amplification, α , may be calculated from these readings: $\alpha = dI_c/dI_e$.

A minimum current gain α of 1.2 is specified for the CK716 transistor.

A.c. voltage gain

In some instances, it will be important to check directly the performance of the transistor with an a.c. input signal. The circuit shown in Fig. 4 may be used to measure a.c. voltage amplification. A test-signal frequency of 1,000 cycles is recommended. E_c and E_e are adjusted to give the emitter and collector currents, respectively, (in the absence of a.c. signal input) specified by the transistor manufacturer for grounded-base operation. Load resistance R_L should be not less than the specified output impedance or the measured R_o value of the transistor under test. In most instances, the a.c. input signal (E_i) between emitter and base should not exceed 0.1 volt r.m.s.


When switch S1 is thrown to INPUT VOLTS, the a.c. v.t.v.m. reads the input signal voltage. When S1 is thrown to OUTPUT VOLTS, the meter reads the output signal voltage (E_o). The a.c. voltage gain is equal to E_o/E_i . The voltage gain in decibels is equal to $20 \log_{10} E_o/E_i$.

In the test circuit similar to the one shown in Fig. 4, the CK716 point-contact transistor gives a voltage gain of 50 at 1,000 cycles when E_c is 0.25 volt, E_e is 67½ volts, R_L is 4,000 ohms, and $E_i = 0.1$ volt. END

SALE!

WORLD'S MOST POWERFUL TV SET SUPER DUPER

Suggested by E. Bruno, Brooklyn, N. Y.

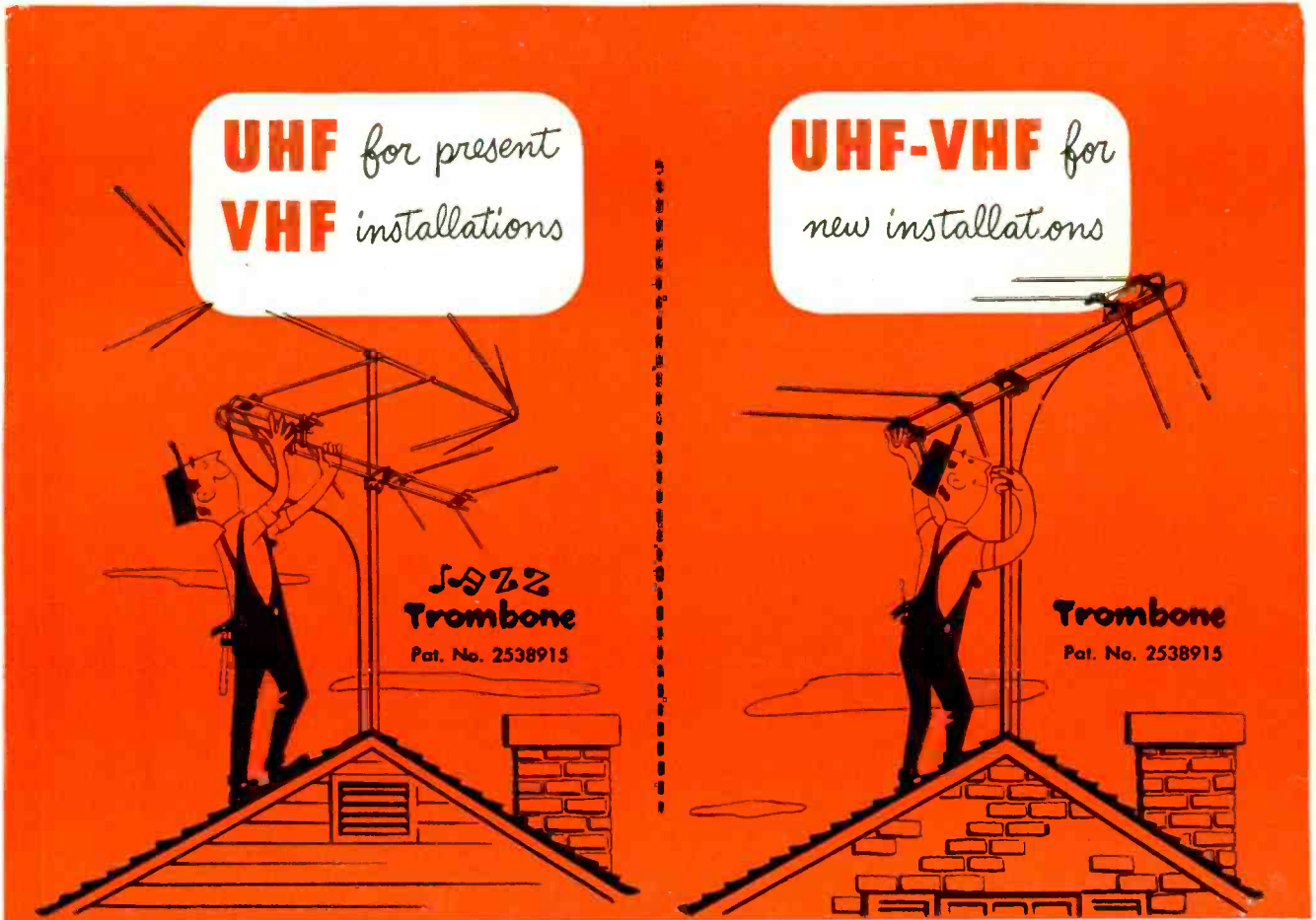

new WARD antennas give everybody everything in television UHF and VHF!

WARD'S newest, exclusive contribution to Television — the JAZZ TROMBONE — is a small, light-weight, auxiliary antenna designed for UHF only. When attached to any present day VHF antenna, it creates a complete UHF-VHF antenna. Low cost, streamlined, fully preassembled, easily installed. JAZZ TROMBONE is the ideal change-over auxiliary Antenna for all present installations.

For all new installations, nothing compares with the sensational, new WARD TROMBONE, engineered and designed to bring in all channels, all frequencies, both UHF and VHF, with one single antenna. — The WARD TROMBONE is the completely universal Antenna that provides clear, sharp reception in any location; outstandingly effective in fringe areas.

Write for Catalog Sheets

THE DIPLEXER



Another new WARD exclusive — the DIPLEXER — completely solves the problem of two lead-in lines, where separate UHF and VHF Antennas are used. — Simply connect the two lines to the DIPLEXER and extend one single line to the Television receiving set.




THE WARD PRODUCTS CORP.

DIVISION OF THE GABRIEL COMPANY

1148 EUCLID AVENUE • CLEVELAND 15, OHIO • In Canada: Atlas Radio Corp., Ltd., Toronto, Ont.

Like money in the Bank...

WALSCO UHF-VHF

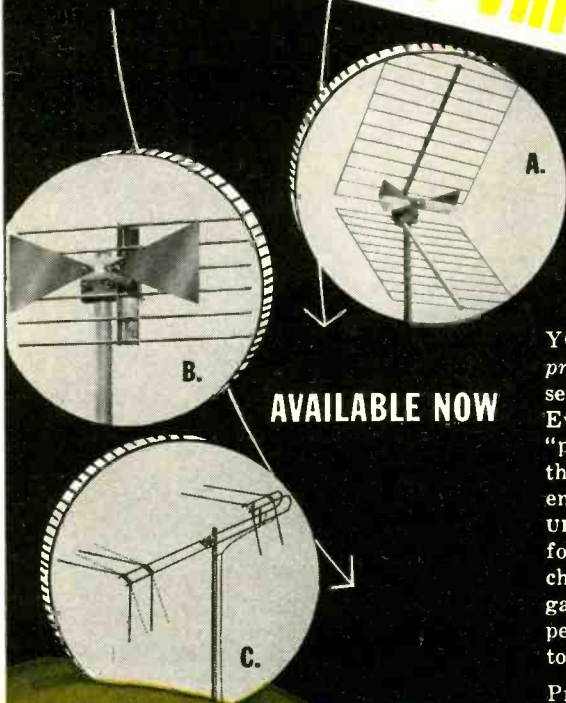

- A. CORNER REFLECTOR
For fringe and ghost area reception
- B. REFLECTO-FAN
For local reception
- C. TROMBONE
For combination UHF-VHF reception

AVAILABLE NOW

YOU are completely protected when you buy, sell or install WALSCO. Every model is now a "proven performer"... thoroughly tested and endorsed in all the new UHF-VHF areas. Designed for all present and future channels. The best high gain, all channel performance and a model to fit every installation

Protect your profit... eliminate costly call-backs. Install WALSCO, America's most dependable TV antennas. It's like money in the bank!

WALSCO

Walter L. Schott Co.
3225 Exposition Place
Los Angeles 18, Calif.
Overseas Representative:
Ad Auriema, Inc., 89 Broad St.,
New York 4, N.Y.

WRITE FOR COMPLETE PRICE AND CATALOG INFORMATION—Dept. P-53

A DETECTOR-AMPLIFIER WITH GERMANIUM DIODES

By IRVING GOTTLIEB

GERMANIUM diodes can be used as simultaneous detectors and amplifiers. Fig. 1 is the circuit of such a simple detector-amplifier. It will be recognized as the familiar half-wave voltage quadrupler often used for transformerless voltage multiplication at power-line frequency.

The time constant of the R-C elements is made high with respect to the radio frequency, but low compared to audio frequencies. The r.f. is therefore rectified and filtered out, and the audio modulation appears across the output terminals.

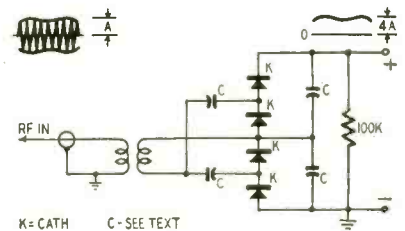


Fig. 1—A simple detector-amplifier, useful in telemetering applications.

The circuit of Fig. 1 is useful for signalling and telemetering applications in which r.f. is available from a coaxial cable. The input impedance of the detector-multiplier is comparable to that of the coax, and a good match can be obtained with closely coupled links made of several turns of wire on a 1-inch diameter form.

Size of the capacitors C will depend on the kind of operation desired. To obtain the modulation at a voltage amplitude nearly four times that on the r.f. carrier, they should be about 250 μf in all circuits. If it is desired to rectify unmodulated r.f. and step up the resultant d.c. voltage, the capacitors may be 0.1 μf or larger, depending upon the current consumption of the load. Gain is actually about 90% of the theoretical value, due to diode back resistance.

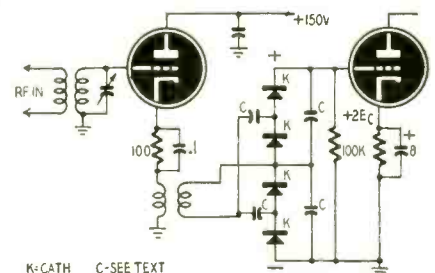


Fig. 2—Circuit with unique features.

In Fig. 2 a detector-amplifier circuit with several unique features is illustrated. It combines the signal-handling capacity of the diode detector, the no-loading of the input circuit characteristic of the plate detector, the audio



did you know...

that Rauland made the first rectangular tube in 1925?
everybody knows... that engineering leadership means
sales leadership... and that means RAULAND

THE RAULAND CORPORATION, 4245 N. KNOX AVENUE, CHICAGO 41, ILLINOIS • MULBERRY 5-5000

RAULAND



did you know...

that Rauland was the first company to produce the
electrostatic low focus voltage tube?
everybody knows... that engineering leadership means
sales leadership... and that means RAULAND



THE RAULAND CORPORATION, 4245 N. KNOX AVENUE, CHICAGO 41, ILLINOIS • MULBERRY 5-5000




DID YOU KNOW


that Rauland was the first company to manufacture
clemitized tubes on a production basis?
everybody knows... that engineering leadership
means sales leadership... and that means RAULAND

THE RAULAND CORPORATION, 4245 N. KNOX AVENUE, CHICAGO 41, ILLINOIS • MULBERRY 5-5000

Burton Brown Advertising

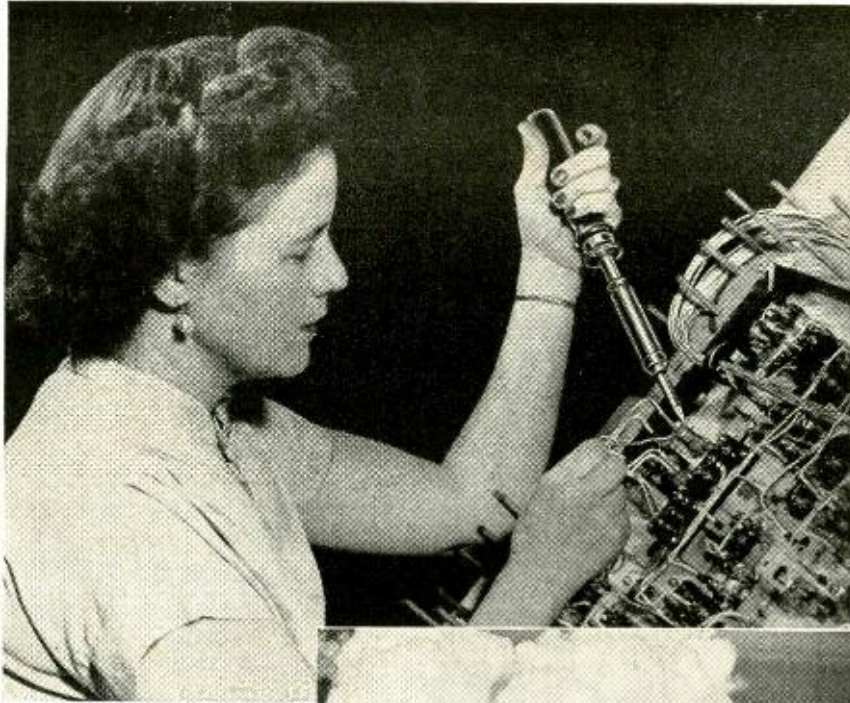

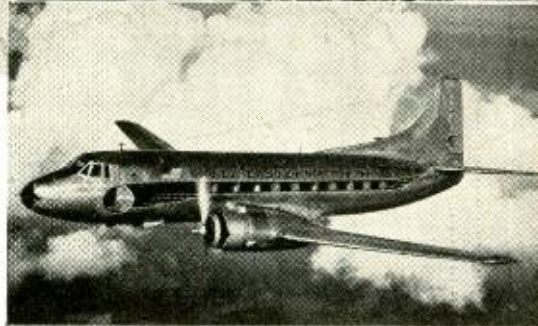At the Glenn L. Martin Co., Baltimore, Md., American Beauty Soldering Irons are used to fasten parts to an overhead switch control panel for the pilot's compartment of Martin 4-0-4 twin-engine commercial transports.



American Beauty makes perfect Soldered Connections

FOR THE GLENN L. MARTIN CO.

HERE'S WHY AMERICAN BEAUTY is the Standard-of-Perfection on the world's production lines . . . where dependability, long life and efficiency are demanded . . .



TEMPERATURE REGULATING STAND

Thermostatically controlled to maintain heat of Iron at any desired temperature while at rest.

Write for
Free Literature

- Nickel-coated, corrosion-resistant tips, easily and quickly replaced
- Super-flexible cord, American Beauty made, resists wear due to flexing
- Heating element of chrome-nickel ribbon resistance wire
- Insulated with pure mica
- Built-in adapter for ground wire
- Five sizes . . . from 50 to 550 watts

AMERICAN BEAUTY Electric Soldering
Irons are Service Proven . . .
since 1894

A-104

AMERICAN ELECTRICAL HEATER CO.
DETROIT 2, MICH.

frequency response of direct interstage coupling, and the voltage boosting of transformer coupling. This is done by using the r.f. voltage multiplier with a cathode-follower r.f. amplifier. (The low input impedance of the multiplier prevents direct connection to a resonant circuit.)

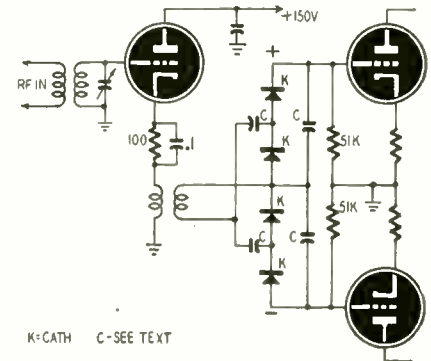


Fig. 3—Push-pull version of Fig. 2.

The audio output amplifier should be operated with a negative grid bias twice that corresponding to the operating point of the same tube in a conventional class-A amplifier with the same plate voltage. This enables Class-A operation over the same grid-voltage swing as the conventional amplifier even though the operating point will be determined by the unmodulated carrier amplitude and will therefore be subject to variation. A strong carrier will shift the operating point down toward zero bias; a weak carrier pushes it toward twice conventional bias voltage. Thus, the grid operating range is between $-2E_c$ and $0E_c$, just as in a conventional class-A amplifier. Over-all voltage gain is about 3.3 ($0.9 \times 0.9 \times 4$).

For push-pull operation of the output audio amplifier, the diode connections are altered as shown in Fig. 3. The gain from the push-pull diode demodulator is only half that of the single-ended circuit, so except for the merits of push-pull amplification, its use is not advantageous.

To obtain a voltage gain of 0.9 or better in the cathode-follower stage, a tube with high transconductance is needed. The 6J4 and the 6Q4 are good tubes for this purpose. The cathode bias resistor is 100 ohms and is bypassed with a $0.1\text{-}\mu\text{f}$ capacitor. The output resistance of the cathode follower is determined by the impedance of the coupling link in the cathode circuit in conjunction with the input impedance of the voltage multiplier. Tight coupling is necessary to make this impedance mainly resistive. The number of turns will depend somewhat upon the radio-frequency range, but is not critical. For intermediate frequencies of several hundred kc, 10 to 20 turns on a 1-inch form will be suitable. For higher frequencies, fewer turns should be used. In any case, a voltage gain of less than 0.9 from the cathode follower indicates the need for more turns.

The crystal diodes may be any of the germanium elements intended for r.f. applications. Best results will be obtained with the 1N54. END

FAR BETTER RECEPTION

IN EVERY LOCATION

with Sensational New

TRIO ZIG-ZAG

Patent Pending

TV ANTENNAS



ZZ4A



ZZ6A

SUBURBAN MODELS

Models ZZ4A and ZZ6A give you all-channel (2 thru 13) reception in ONE SINGLE BAY ANTENNA. The Model ZZ4A has excellent gain and is designed for suburban areas. Model ZZ6A has even greater gain and provides excellent all-channel reception in near fringe areas.




ZZ6L

ZZ6H

NEAR FRINGE MODELS

For near fringe area reception, the Models ZZ6L and ZZ6H are recommended. Model ZZ6L covers Channels 2 thru 6, Model ZZ6H is for Channels 7 thru 13. Both antennas offer high gain with patterns and front-to-back ratios similar to cut-to-channel yagis.

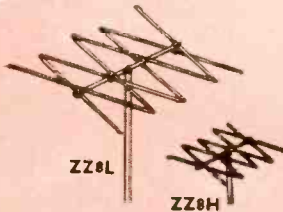


ZZ8L

ZZ8H

FRINGE MODELS

Models ZZ8L and ZZ8H were designed for normal fringe area reception and provide clear, snow-free pictures. Forward lobe patterns and front-to-back ratios are similar to a good single channel, multi-element yagi.

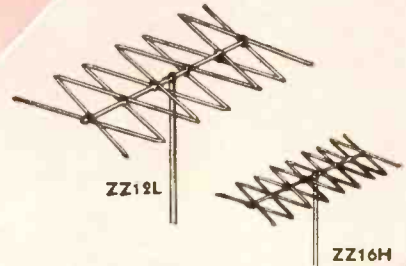


ZZ12L

ZZ16H


ULTRA FRINGE MODELS

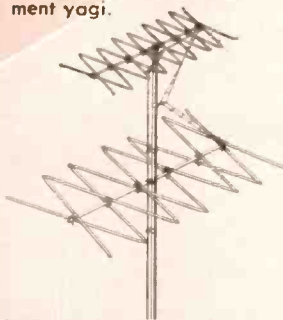The extremely high gains of the ZZ12L and the ZZ16H models provide unequalled reception in ultra-fringe areas. Model ZZ12L covers Channels 2 thru 6 and Model ZZ16H, Channels 7 thru 13. These two models when stacked, are fed with only one 300 ohm line and provide ALL VHF CHANNEL RECEPTION. Line match is excellent and front-to-back ratios are unusually high.



ZZ12L and ZZ16H are stacked for all VHF Channel Reception

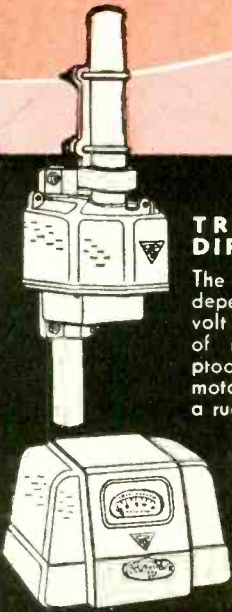* To provide even greater strength, TRIO Antennas now have stamped steel element clamps.



TRIO ROTATOR AND DIRECTION INDICATOR

The TRIO Rotator is America's most dependable — has two powerful 24 volt motors — one for each direction of rotation. Absolutely weather-proof, permanently lubricated. All motors, shafts and gears mounted on a rugged, one-piece casting for true alignment, strength and longer life. Every TRIO Rotator fully guaranteed for two years! Beautiful Direction Indicator has "finger tip" control — no need to hold knob for rotation. A touch of the finger starts it — a touch stops it!



TRIO

TRIO MANUFACTURING COMPANY

GRIGGSVILLE, ILLINOIS


Dealers find
the **NEPCO** line

*Reduces
Stocks*

*Reduces
Call Backs*

*Increases
Goodwill*

*Increases
Profits*

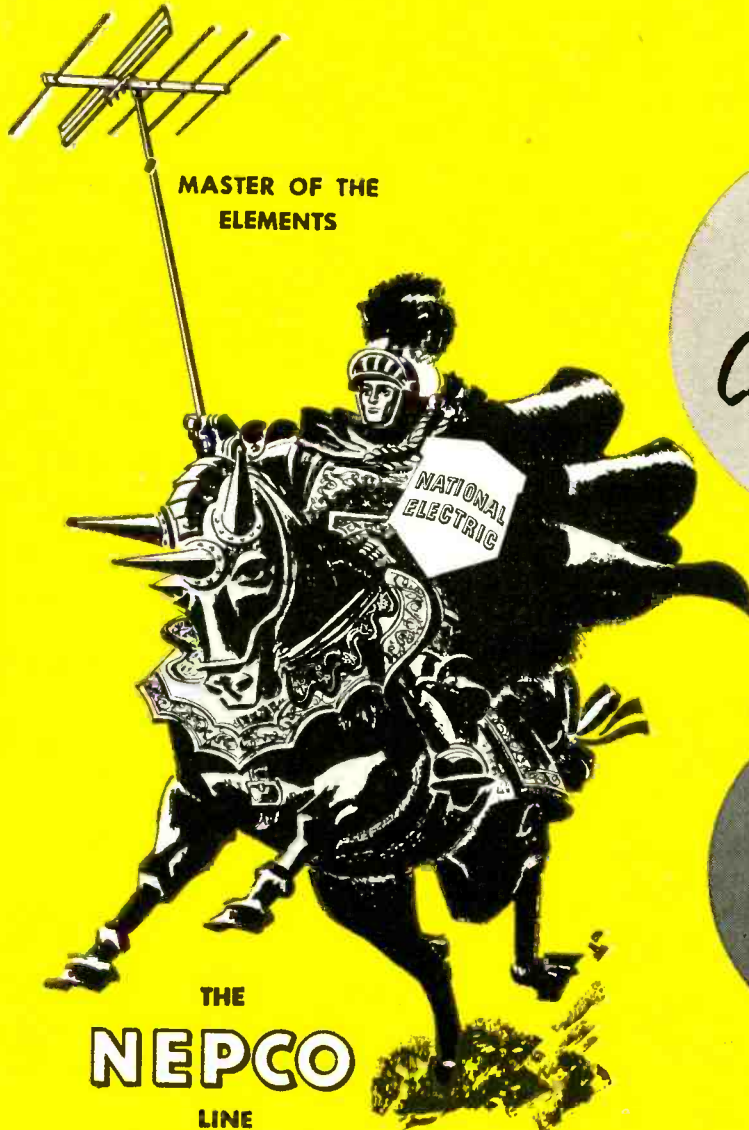

MASTER OF THE
ELEMENTS

THE
NEPCO

LINE

INCLUDES:

- YAGI ANTENNAS ● CONICAL ANTENNAS
- UHF ANTENNAS ● MASTING ● EAVE MOUNTS
- WALL BRACKETS ● VENT MOUNTS ● ROOF MOUNTS
- CHIMNEY BANDING ● CHIMNEY MOUNTS ● GUY RINGS
- BANDING & MAST CLAMPS ● ADD-A-TOWER PLATES ● TV WIRE

National Electric Products

RADIO AND TELEVISION DEPARTMENT, PITTSBURGH, PA.

TV set owners want
a better picture, longer
Here is the answer

Today, TV set owners are demanding better reception. Often the *trouble is in the antenna installation, not the set*. A corroded antenna (and most antennas are corroded if they have been up a while) or cracked and crazed down-leads (and most polyethylene leads are faulty after 10-12 months) can cause a deteriorated picture. *Nothing* you do to the set can correct this condition. A *new and better* antenna installation is the answer.

The NEPCO Line of antennas and TV installation materials eliminates this condition.

It was designed to meet the pressing demand for *better* electronic equipment—with more built-in ruggedness and corrosion-resistance than any line now known.

The NEPCO line was designed with YOU in mind:

- Provides *maximum* number of installations with a *minimum* number of parts from jobbers. Your stocks are kept at a minimum.
- Its high quality eliminates costly call backs . . . saves you time, trouble and tempers . . . improves customer goodwill.
- Eliminates rust streaks—a common customer complaint.
- Provides *quicker* installations . . . goes up fast . . . easy to handle . . . easy to carry.


Remember, a better installation using better materials will insure more satisfied customers.

These other features will "spark" your TV sales:

**ORDER A BALANCED STOCK
FROM YOUR JOBBER TODAY**

CHIMNEY MOUNTS

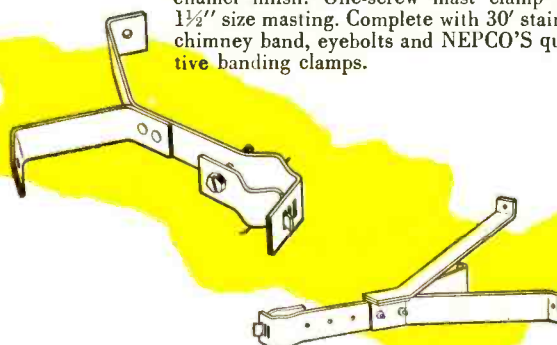Made of $\frac{1}{8}$ " x $1\frac{3}{4}$ " steel, zinc-coated plus baked-enamel finish. One-screw mast clamp adapts to $1\frac{1}{2}$ " size masting. Complete with 30' stainless steel chimney band, eyebolts and NEPCO'S quick, positive banding clamps.




WALL BRACKETS

Fabricated of $\frac{1}{8}$ " x $1\frac{3}{4}$ " steel, heavily zinc-coated with baked-enamel finish. One-screw mast clamp adjustable to $1\frac{1}{2}$ " masting. Hex head slotted bolts to speed erection time.



**SPACE SAVER—
BIG, FLAT BOXES FOR TV WIRE**

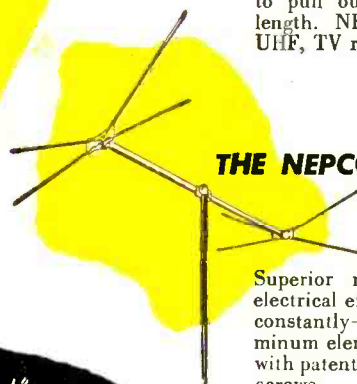NEPCO "Zee" Line comes in strong, flat cartons. Easy to stack, easy to handle, easy to pull out for cutting to any desired length. NEPCO "Zee" Line is low-loss UHF, TV receiving wire.



**THE NEPCO CONICAL ANTENNA
IMMEDIATE
DELIVERY**


Superior mechanical features maintain electrical effectiveness and performance—constantly—regardless of conditions. Aluminum elements are permanently secured with patented "vibration-proof" imbedding screws.

- All parts heavily zinc-coated plus baked-enamel finish.

- All mounts made of rigid, heavy gauge steel.
- Unique adjustable mast clamp with one-bolt mounting.
- Two 15' stainless steel chimney bands with each chimney mount.
- Over 100 installation combinations possible with minimum inventory.
- Slotted, hex-head bolts standard equipment . . . all zinc-coated plus baked-enamel finish.
- Exclusive antenna mast clamp with positive alignment in all planes.
- Patented imbedding type screw for positive electrical and mechanical locking.

ARTIFICIAL DELAY LINES

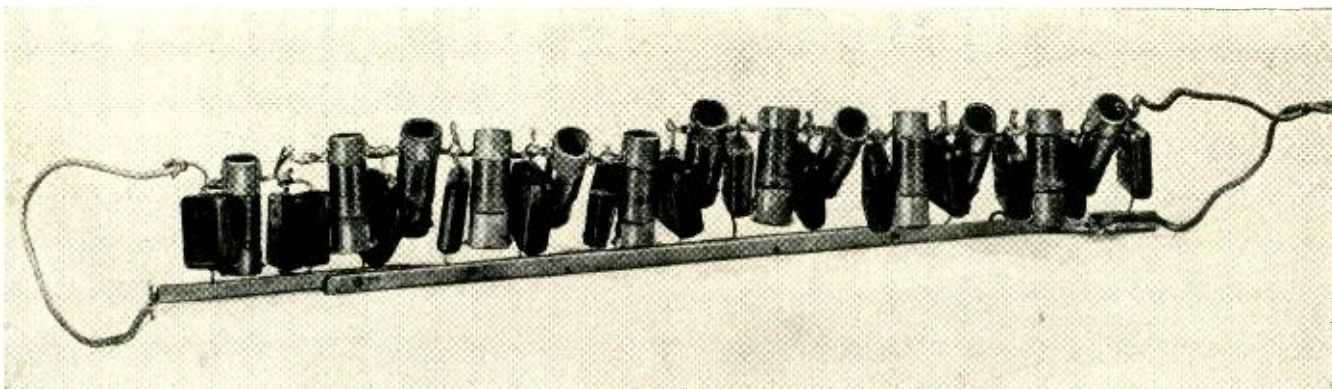Delay lines have many
electronic applications.
Construct yours
from low-pass filters
made with L-C components
By R. C. PAINE



One way of constructing a multisection delay line. The adjacent coils are mounted at an angle, to reduce coupling.

IN RADAR a distant plane is detected by radio waves reflected from the plane as a radio echo, just as sound waves reflected by a distant cliff create an acoustic echo. The audible echo is produced because the time it takes for the sound to travel out to the cliff and return is perceptible to the human senses. Even the radio echo requires a definite time for the waves to reach the target and return, though this time is measured in microseconds. Radio waves travel through free space at the speed of light—300,000,000 meters per second, or about 984 feet per microsecond. Distance can be determined by measuring the time of arrival of the reflected waves.

The time of travel of waves between points may be referred to as "delay time." For many purposes, such as range measurements in radar and loran, and storing information in calculating devices, circuits which produce definite

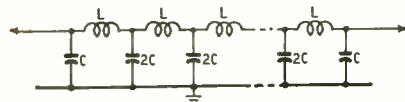


Fig. 1—An artificial transmission line assembled from identical low-pass-filter sections linked end to end. Input and output capacitors are each half the value of the internal capacitance elements.

time delays are required. Theoretically, it would be possible to use radio transmission line for delay circuits, because the speed of radio waves in ordinary transmission cable is less than in free space; but this approach is not very practical, since thousands of feet of line would be required to produce appreciable delay times.

To avoid the bulk of long transmission-cable delay lines, artificial transmission lines with lumped constants are constructed. Over a limited frequency range, a relatively compact network of coils and capacitors can simulate the distributed series inductance and parallel capacitance of a long transmission line. The more sections such a line has, the more nearly it duplicates the performance of a uniform line.

These artificial transmission lines are often used as delay lines to retard electrical impulses for a definite time (measured in microseconds, or millionths of a second) between points in a network. Such lines are used in radar and navigation systems, computing machines, and many other instruments.


The characteristics of a delay line are usually studied with pulse generators and special complex oscilloscopes. An experimental line, however, is easily constructed and its delay characteris-

tics can be observed readily with an ordinary oscilloscope.


A delay line is shown schematically in Fig. 1 as a series of pi sections. The end capacitors have a value C , but the intermediate capacitors combine two parallel C values into a single one.

One such line constructed by the author consists of thirteen sections and is shown above. The coils and capacitors are arranged in line and connected to a common grounding strip. Adjacent coils are tilted right and left at an angle of 45° to minimize coupling between them. The inductances L are wound on paper forms $\frac{7}{16}$ inch in diameter and about $1\frac{1}{4}$ inches long, as shown in Fig. 2. They are wound with about 28 turns of No. 22 enameled wire and have an inductance of 5 microhenries. The end capacitors, C , are nominal .001- μf units selected for an actual value of 925 μf each. The internal capacitors were selected from .002- μf units for a measured value of 1850 μf . The line has a characteristic impedance of about 50 ohms. That is, when it is terminated by this value of resistance all the energy that reaches the end of the line is absorbed by the load, and reflected waves are suppressed. This artificial line has a time delay of about 1.15 microseconds.

(CONTINUED ON PAGE 95)

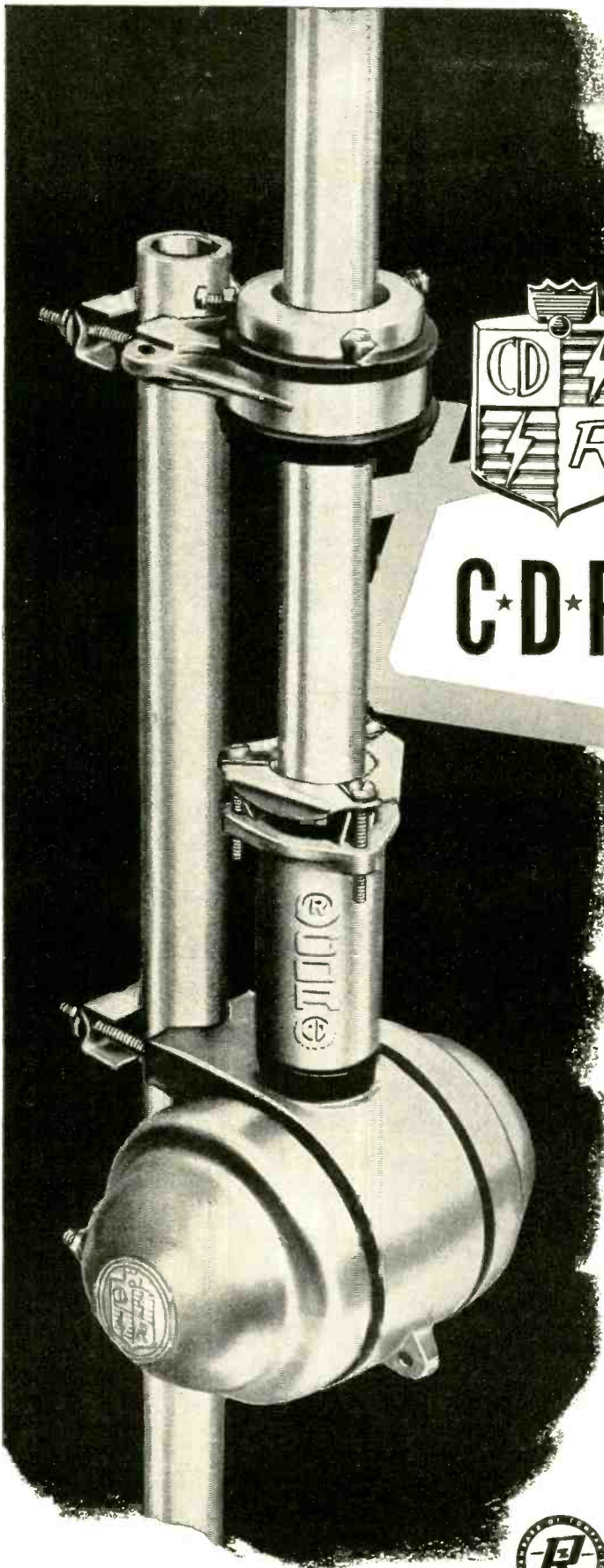

In a Class
by Itself

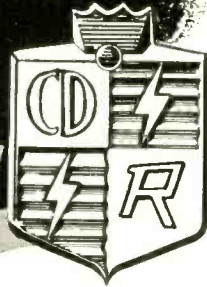

**the
C·D·R Rotor**

Speedy Installation ... the servicemen's dream come true! No loose parts to assemble...no kits with loose washers, nuts and bolts... quick mounting antenna mast collet plus four wire cable hookups!

Dependable ... experience has proven that once a CDR ROTOR is up... it's THERE TO STAY! No costly call-backs! Completely weather-sealed and streamlined... it's the outstanding value in the field!

Powerful ... sturdy in design to support and TURN ANY TV ANTENNA array... never a worry about the CDR rotor working! Locking instantly it will not drift! Instantly reversible... makes a complete revolution in 45 seconds!

MODEL TR-12 A special combination value consisting of complete rotor including thrust bearing... handsome modern design plastic cabinet with meter control dial, only... \$47.95



MODEL TA-6 Thrust bearing accessory, separately... \$4.95

MODEL TR-11 Same as TR-12 without thrust bearing... \$44.95



THE RADIART CORPORATION
CLEVELAND 13, OHIO

CORNELL-DUBILIER
SOUTH PLAINFIELD, NEW JERSEY

MARCH, 1953

- ★ **HOW** to do faster, better testing with fewer instruments
- ★ **HOW** to double the usefulness of your present instruments
- ★ **HOW** to choose the right instrument for each job
- ★ **HOW** to understand its operating principles



★ **HOW** to evaluate its readings and put them to practical use

BASIC ELECTRONIC TEST INSTRUMENTS

By RUFUS P. TURNER
254 pages, 171 illus., Price \$4.00

The Instrument Book Written Especially for
• SERVICEMEN • AMATEURS
• EXPERIMENTERS

★ HERE'S a brand new book that can save you money on instruments and help you use your present instruments lots more efficiently!

Over 60 instruments—from the most modern TV pattern generators to special-purpose bridges—are carefully described. Their uses are fully explained and valuable work-saving short cuts outlined.

Included are complete details on simple meters for current and voltage; ohmmeters and V-O-M's; V-T voltmeters; power meters; impedance meters; capacitor checkers; inductance checkers; special-purpose bridges; oscilloscopes (this material alone is worth the entire price of the book to busy servicemen!); r-f test oscillators and signal generators; audio test oscillators; radio frequency and audio frequency measuring devices; audio-amplifier testing devices; r-f signal tracers and tube testers.

Among other things, BASIC ELECTRIC TEST INSTRUMENTS is a complete training course in the latest instruments including grid-dip oscillators, TV sweep and marker generators; TV linearity pattern generators, square-wave generators, distortion meters and others.

SAVE ON INSTRUMENTS!

You are shown new uses for VOM's, 'scopes, signal generators and other old standbys. You learn how easy it is to extend the range of many old instruments; how power drain measurements can be used for fast TV troubleshooting; how a useful and accurate bridge can be built from a combination of familiar general-purpose instruments; how to calculate shunts and multipliers; how to measure r-f impedance with a simple T-network; how to measure inductance and capacitance with a grid-dip oscillator and scores of other money-saving "tricks".


Just off the press! Read BASIC ELECTRONIC TEST INSTRUMENTS for 10 days at our risk!

10-DAY FREE EXAMINATION

Dept. RE-33, Rinehart Books, Inc.
Technical Division,
232 Madison Ave., New York 16, N. Y.

Send Turner's BASIC ELECTRONIC TEST INSTRUMENTS for 10-day FREE EXAMINATION. If I decide to keep book, I will then remit \$4.00 plus postage. Otherwise I will return book post-paid promptly and owe you nothing.

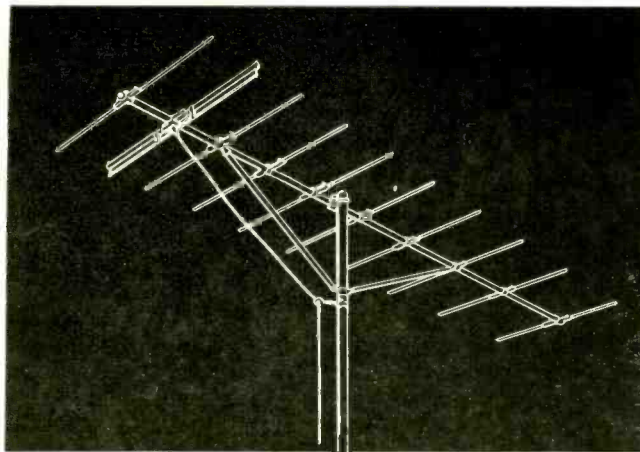Name _____
Address _____
City, Zone, State _____
Employers Name and Address _____
OUTSIDE U.S.A.—Price \$4.50, cash only.
Money back if book is returned postpaid in 10 days.



10-Element Yagi
Cut to specified channel
(Also Available Stacked)

- ✓ Amazingly Powerful Reception
- ✓ Rugged All-Aluminum Construction
- ✓ Lifetime Factory Warranty


a "TESCO" exclusive
the **ROCKETENNA**



by T-V PRODUCTS CO.

Complete factory Preassembly features sensational "Quick-as-a-Wink" construction. No Nuts or Bolts to Tighten... rugged rivet assembly prevents damage by wind and storm vibration.

ANOTHER "TESCO" PRODUCT

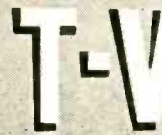

Write for New Complete Catalog R

PRODUCTS CO.

152 SANDFORD ST. • B'KLYN, N. Y.



SCIENCE-FICTION +

A NEW GERNSBACK PUBLICATION

Second issue, April, 1953

- Instructive
- Entertaining

ON SALE MARCH 11

Reserve a copy at your favorite newsstand now.

ANOTHER OUTSTANDING JOBBER PENN ELECTRONIC PARTS CO.

5303 Frankford Ave.
Philadelphia 24, Pa.

HAS THE SENSATIONAL NEW
TEICO 470-K 7" SCOPE KIT
IN STOCK!



\$79.95

Send for Free Flyer

ANOTHER OUTSTANDING JOBBER CERTIFIED RADIO SUPPLY

Wickham Ave. Ext. Route 84
Middletown, N. Y.
and: 130 South Ave., Poughkeepsie, N. Y.

HAS THE SENSATIONAL NEW
TEICO 470-K 7" SCOPE KIT
IN STOCK!



\$79.95

The time required for an impulse to go out and return as a reflected wave on this line is 2.3 microseconds. This is equivalent to quarter-wave-line resonance at 435 kilocycles, or half-wave resonance at 870 kilocycles. Resonance on this line can be demonstrated in an interesting manner. It can be driven by an oscillator operating at 870 kc. The line is coupled to the oscillator by a loop of a few turns connected across its input end as shown in Fig. 3. Its far end is short circuited.

Voltage and current ratios

The current distribution due to standing waves is at a minimum in the center of the network, but gradually increases to a maximum as each end is approached. Correspondingly, the voltage across each coil at the center of the network is low, but increases towards the ends of the line. A small flashlight bulb with probe terminals may be used to bridge each coil in succession. Near the center of the network the lamp glows dimly or not at all, but at the ends it lights brightly, and—unless caution is observed—it may even burn out.

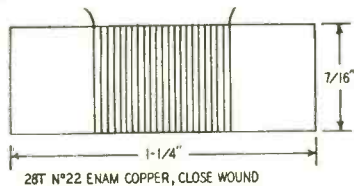


Fig. 2—One of the line-section coils.

To check the reflected waves in a line we feed in a pulse and observe its progress on an oscilloscope. By using the return sweep of the oscilloscope for the initial pulse the two functions are combined and synchronized automatically.

A portion of the sweep circuit of a typical scope is shown in Fig. 4. The input of the delay line is connected through a .001- μ f capacitor to the output of the sweep amplifier (a cathode

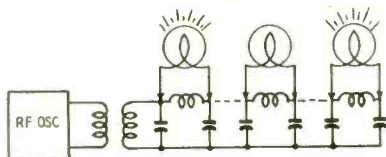



Fig. 3—Checking voltage distribution along the artificial transmission line.

follower in this case) and also to the vertical input terminals of the same scope. With other scopes it may be necessary to connect to different points in the horizontal sweep circuit, but a small capacitor should always be used for coupling. This capacitor, together with the low input impedance of the delay line, differentiates the retrace of the saw-tooth sweep wave and produces a sharp pulse for exciting the line.


Mismatched Impedances

When the delay line is connected in this manner, its input or "near" end is terminated by the relatively high impedance of the scope input amplifier. Thus, waves reflected from the open-circuited far end are re-reflected from the near end. Successive reflections take

TV SERVICEMEN

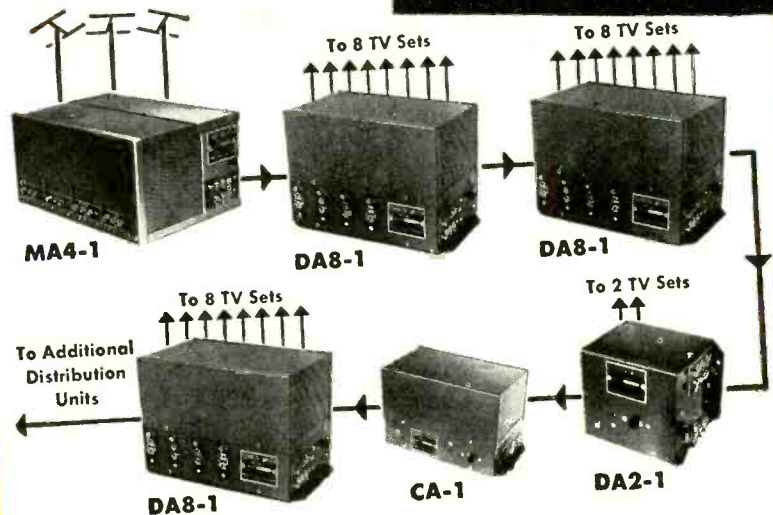

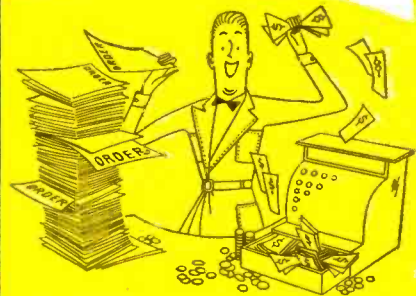**YOU CAN Easily
DOUBLE YOUR BUSINESS
AND YOUR PROFITS
IN VHF AND UHF
WITH B-T UNITS**



B-T UNITS are by far the most economical and reliable wherever the needs arise for TV Antenna Mixing, TV Signal Distribution, and TV Signal Amplification. They are ideal for Master Antenna Systems, Community Systems, and other Television Installations, whether they involve 1 or 2 or 2000 TV sets.

B-T UNITS are easier to install than TV receivers.

The **B-T MA4-1** is a Mixer-Amplifier. It is the perfect solution to all multi-antenna and multi-directional signal problems.

	LIST PRICE
MA4-1 Basic Chassis & Power Supply.....	\$52.50
CS-1 Single Channel Plug-in Strips.....each	19.50
UC-1 UHF Converter Strips.....each	34.50

The **DA2-1** is a no-loss Distribution Amplifier with two outlets and a through-line 39.50


The **DA8-1** is a no-loss Distribution Amplifier with eight outlets and a through-line 87.50

The **CA-1** is a highly efficient Line Amplifier with a gain in excess of 27 db over the entire VHF band..... 77.50

B-T ACCESSORIES include Line Splitters, a Matching Transformer, Line-Loss Equalizer, Attenuator, Remote Control Unit, Weather-Proof Housing, and others.

And then there are the **B-T BOOSTERS**, the 4 tube HA-2 with gain in excess 24 db., and the 3 tube HA-3 with gain in excess of 16 db. Both are Fully Automatic over the entire VHF band with no channel-tuning or band-switching.

Write for Manual GC-3

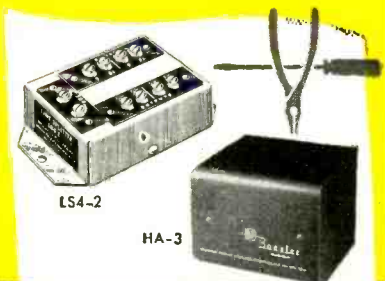


The Story of the **B-T UNIT SYSTEM** with Use and Installation Instructions ... designed to create more markets for the Serviceman than he has ever had before ... and to make his task easier and more profitable.

Sold through leading distributors
BLONDER-TONGUE LABORATORIES, INC.
WESTFIELD, NEW JERSEY



at Last!

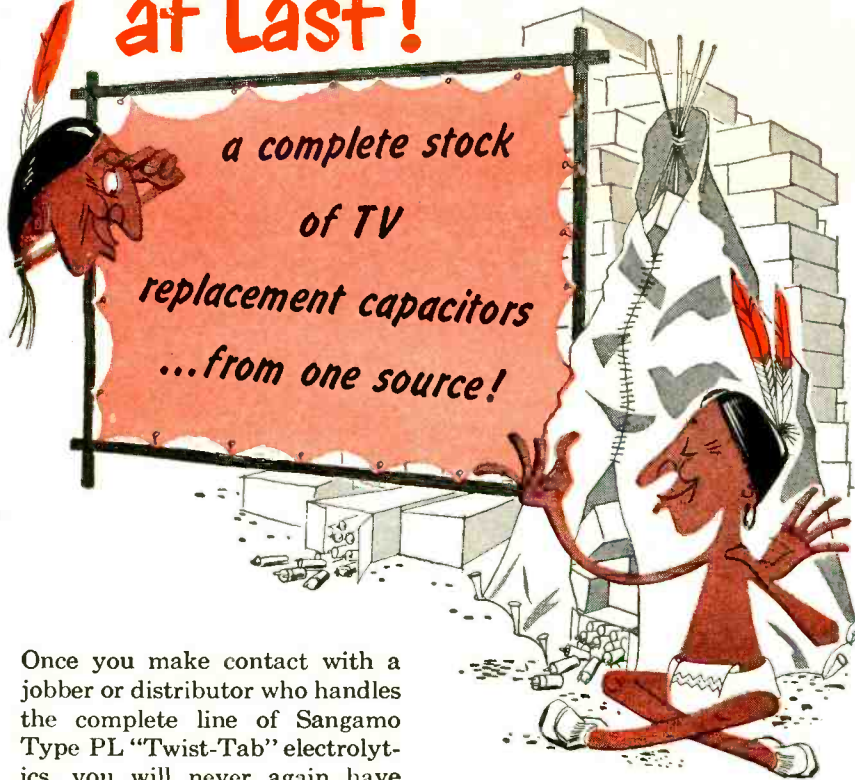a complete stock
of TV
replacement capacitors
...from one source!



Once you make contact with a jobber or distributor who handles the complete line of Sangamo Type PL "Twist-Tab" electrolytics, you will never again have to "shop around" for odd sizes or capacities. Why? . . . because the Sangamo line is the most complete in the industry.

Used by all leading manufacturers of TV sets, Sangamo Type PL "Twist-Tab" electrolytics are exact replacements. They assure long life and dependable performance at 85° C and under conditions of high surge voltages and extreme ripple currents often found in TV applications.

Ask your distributor for a copy of the Sangamo TV Replacement Catalog. It's easy to use and helps you choose the right replacement every time.

Deal with your Sangamo "Head-quarters."

Those who know... choose Sangamo



SANGAMO ELECTRIC CO. MARION ILLINOIS

You can't keep up with u.h.f. TV without reading the articles in future issues of RADIO-ELECTRONICS

place until the energy of the original pulse is dissipated in the resistance of the line.

If the far end of the line is open, or terminated in a *high impedance*, reflected waves are of the same polarity as the incident waves at each end and build up the voltage at each reflection (See "Transmission Lines Simplified," by Hector E. French, in the October, 1952, RADIO-ELECTRONICS). This is shown in the oscilloscope photograph Fig. 5, in which the line is terminated by a 500-ohm resistor. A carbon or "metallized" resistor should be used for the termination because of its negligible inductance. An inductive termination would upset the delay-line constants.

When the far end of the line is terminated by a *low impedance* or short circuit the polarity of the reflected wave is not the same as the incident wave at that end. This results in alternate recurring waves being reversed at the near end. This is shown in Fig. 6, in which the line is terminated in a 10-ohm resistor.

The value of the terminating resistance can be varied until the observed reflections are reduced to minimum. At this point the load is equal to the characteristic impedance of the line, the incident wave is completely absorbed at the far end, and no reflections take place. This is illustrated in Fig. 7, where the 50-ohm terminating resistor is thus shown experimentally to be equal to the characteristic impedance of the line.

Delay time

The delay time of the line can be estimated from the frequency of the oscilloscope sweep and the number of reflections as indicated by the total number of positive or negative peaks in Fig. 5. In this case the peaks (including one on the dim return trace) add up to nine. The frequency of the scope sweep was checked against an audio oscillator and found to be about 48,000 cycles, or 21 microseconds per sweep. This value divided by 9 gives 2.3 microseconds for each complete reflection, or transit in both directions. The observed delay for one way is thus 1.15 microseconds.

Delay lines of different properties can be designed by using the formulas for uniform lines. Thus the characteristic impedance Z_0 , in ohms, = $1,000\sqrt{L/C}$, where L is in microhenries and C is in micromicrofarads. The total delay time is equal to the number of sections mul-

ANOTHER OUTSTANDING JOBBER

NIDISCO

713 Newark Ave. Jersey City, N. J.
55 State St. Hackensack, N. J.
294 Passaic St. Passaic, N. J.
658 Anderson Ave. Cliffside, N. J.
126 So. Warren St. Trenton, N. J.

HAS THE SENSATIONAL NEW **EICO** 470-K 7" SCOPE KIT IN STOCK!

470K KIT \$79.95 WIRED \$129.50

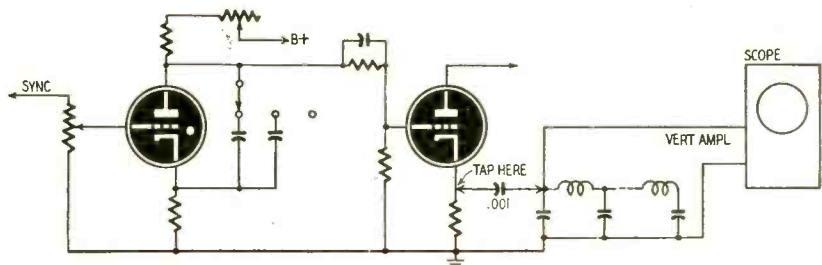


Fig. 4—Using the oscilloscope sweep as a pulse source for checking line characteristics. Reflections are observed and counted on the scope screen for different values of line-terminating resistance.

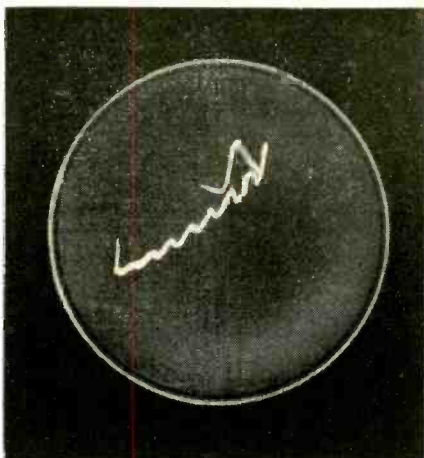


Fig. 5—Reflected signals on an open-ended line are in phase with the input, and cause the voltage to rise at the input end with each new reflected wave.

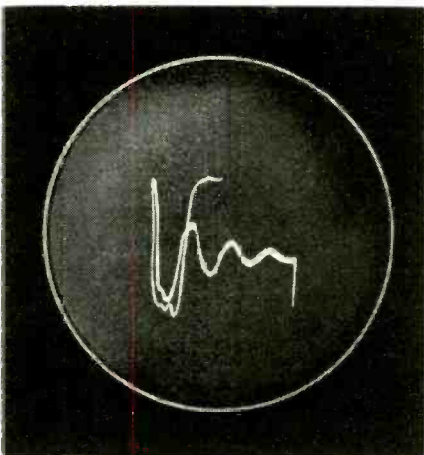


Fig. 6—A line terminated in less than its characteristic impedance creates multiple reflections which are damped out eventually by the line resistance.

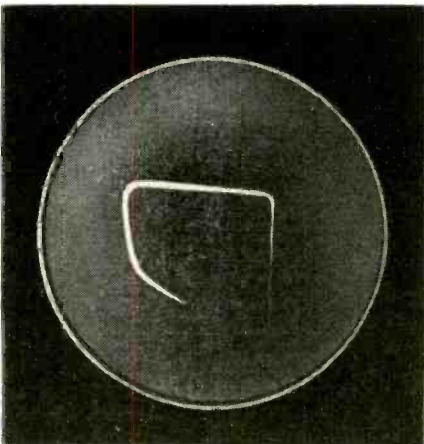


Fig. 7—Perfectly terminated line has no reflections. All energy is dissipated in the load connected across the far end.

multiplied by $\sqrt{LC}/1,000$. These formulas for uniform lines are approximately correct for lumped multisection lines. In the line described above the calculated values are $Z_0 = 1,000\sqrt{5}/1,850 = 52$ ohms and $t = 13\sqrt{5}(1,850)/1,000 = 1.25$ microseconds. These calculated values compare favorably with the corresponding experimental values, $Z_0 = 50$ ohms and $t = 1.15$ microseconds. END

MARCH, 1953



HAVING TROUBLE GETTING FAR AWAY TELEVISION STATIONS UP TO 125 MILES AWAY—OR MORE?


If you're in FRINGE area — not right next door or fairly close to the television stations you want to get, you need the DAVIS VHF SUPER-VISION ALL-CHANNEL ANTENNA. For ALL CHANNELS.

The DAVIS SUPER-VISION is one of the three basic elements necessary for FINE RECEPTION. It's actually as important as a fine television receiving set. So, when you buy, BUY RIGHT — all the way through: Set, Antenna and Leadline. And the services of a competent television technician to make the installation. If you miss on one, you'll miss what you're really buying: AMERICA'S FINEST TELEVISION RECEPTION.

The DAVIS STORY is a BIG STORY — in performance. Get all the facts. Aside from distance and DX reception, know about the "other ten" important features.

PRICED RIGHT for such fine reception. List only \$34.95. Worth every cent of its cost with "the price forgotten long after fine reception remains."

WHAT'S YOUR ANSWER TO THIS QUESTION?

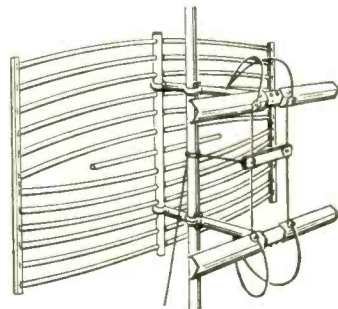

DAVIS SUPER-VISION FOR FRINGE AREA & DX

"The Original Antenna Sold With A Money-Back Guarantee"

Built By America's Fastest Growing Antenna Manufacturer

AT YOUR JOBBERS, or MAIL COUPON TO:

DAVIS ELECTRONICS 1-28
4313 West Magnolia Blvd., Burbank, California
SIRS: RUSH INFORMATION TO ME AS CHECKED BELOW:
 Send Free Technical Data on new SUPER-VISION ANTENNA.
 Send Name and Address of NEAREST JOBBER.
Name _____
Street _____
City _____ State _____

NEW IT'S TERRIFIC! EICO MODEL 470 7-INCH PUSH-PULL SCOPE



HIGHLIGHT FEATURES:

- Boosted vert. sensitivity: 10 mv rms/in.
- Extended flat freq. response! 10 cps—1 MC (± 2 db); useful to 5 MC.
- 3-step freq.-compensated attenuator; cathode follower input.
- Internal voltage calibrator; directly calibrated screen.
- Extended sweep range: 15 cps—100 kc.
- Sel. of int. pos. or neg., ext. & line sync.
- Sawtooth, line freq. outputs, intensity mod. & ext. sync. all on front panel.
- 60 cps sweep, var. phasing.
- Provision for direct connection to CRT plates

KIT \$79.95 Factory Wired \$129.50

ORDER NOW!

For full specifications on Model 470 and the complete EICO line, write for latest catalog.

Federated Purchaser INC 66 Dey Street New York 7, N. Y. DIgby 9-3050

- Newark, N. J., 114 Hudson St.,
- Allentown, Pa., 1115 Hamilton St.,
- Easton, Pa., 925 Northampton St.,
- Los Angeles 15, Cal., 911 So. Grand Ave.,

NEW
 These two TV-radio books
 show you over 900 ways to
 save time and money!

From the publishers of
**RADIO -
 ELECTRONICS**



112 Pages **\$1.00**
 132 Illustrations


RADIO & TV HINTS—No. 47

No matter what phase of electronics you're in—TV, radio, audio or amateur—you can work faster, better, and easier when you know the tricks of the trade. Here's a new and different kind of book which gives you over 300 hints, kinks and short cuts worked out by the experts and passed along to you for only a dollar. It would take you a lifetime to gather all the inside information which is handed to you here this easy way. Order your copy today.

RADIO & TV HINTS presents over 300 practical short cuts on just about every phase of electronics. Conveniently grouped in sections on Test Instruments, Tools, Television, Radio Servicing, Audio, Amateur and Miscellaneous.

TELEVISION TECHNOTES—No. 46

When you're servicing a TV set—time is money and too much of both are wasted in routine trouble-shooting. Here's a book that will cut that kind of time-wasting, nerve-wracking work to the bone. Lists over 600 actual troubles which have cropped up in scores of sets made by 27 leading manufacturers. Tells you what they look like, how they sound and how to put your finger on them and correct them quickly and painlessly. If you're in servicing, you need this book—Get a copy today.

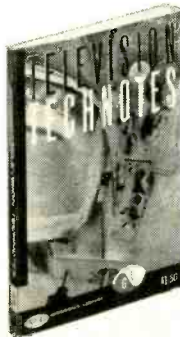

Helps you solve troubles like these: Sync Buzz • Hum • Poor Contrast • Horizontal Wiggle • Microphonics • Arcing • Vertical Jitter • Audio Buzz • Intermittent Picture Tubes • Ineffective A.G.C. • No Vertical Sweep • Blooming Picture • Noise in Picture • Vertical Roll • And many, many others.

128 Pages **\$1.50**
 58 Illustrations

Other GERNSBACK LIBRARY BOOKS
 You'll find helpful!

- Radio Tube Fundamentals • Bk. 45 \$1.00
- Basic Radio Course • Bk. 44 \$2.25
- Model Control by Radio • Bk. 43 \$1.00
- High-Fidelity Techniques • Bk. 42 \$1.00
- Public-Address Guide • Bk. 41 75¢
- The Cathode-Ray Oscilloscope • Bk. 40 75¢
- Practical Disc Recording • Bk. 39 75¢
- Amplifier Builder's Guide • Bk. 33 50¢
- Advanced Service Technique • Bk. 32 50¢
- Radio Questions & Answers • Bk. 31 50¢
- Unusual Patented Circuits • Bk. 30 50¢

See your distributor—or mail this coupon

GERNSBACK PUBLICATIONS, INC. Dept. 33
 25 West Broadway
 New York 7, N. Y.

Enclosed is my remittance of \$.....
 Please send me, postpaid, the books checked below.

- 47—RADIO & TV HINTS
- 46—TELEVISION TECHNOTES
- 45 44 43 42 41 40
- 39 33 32 31 30

Name _____
 (Please print clearly.)

Street _____
 City _____ Zone _____ State _____

AT WHOLESALE RADIO
SAVE MORE THAN 50%
AND OWN THE FINEST!

NEW! PRECISE INSTRUMENTS
MARKER GENERATOR KIT FOR RF-AF-TV



Fundamentals thru 110-300 MC on harmonics. Audio: 20-20,000 cycles. Cathode follower output; variable per cent modulation. Stepping attenuator. External modulation. Speech amplifier. Crystal marker.

Model
 630 A Kit \$33.95
 630KA Kit with pre-assembled RF Head. 38.95
 630W Factory Wired. 53.95

UNIVERSAL AF SINE & SQUARE PULSE GENERATOR

Efficiently and effectively ascertains audio and video troubles. Sine waves; square waves; pulses; Wein Bridge Oscillator; variable impedance output. Voltage regulator insures a veritabily constant output. Cathode follower output; square waves and pulses with minimum overshoot and roundoff through 30,000 cycles. Sine waves from 20 through 200,000 cycles.




Model
 635K Kit \$33.50
 635W Factory wired \$52.50
 VTVM Kit with 7 1/2" meter. 907K \$39.98
 New! Precise 7" Scope. Kit 89.50

Address Orders to Dept. RE 3
 Write for FREE F.Y.I. Flyer

WHOLESALE RADIO PARTS CO., Inc.
 311 W. Baltimore St.
BALTIMORE 1, MD.

FASTER STURDIER
 Lower Installed Cost

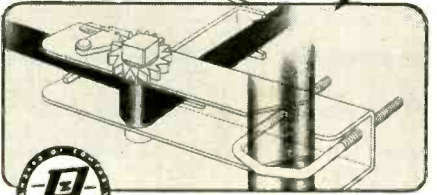

RADIART SPEE-DEE CHIMNEY MOUNT

Model AK 85 The fastest-installed chimney mount ever devised for TV antennas! Rugged in design—simple to install. Simply thread strapping through ratchet, around chimney and back through ratchet—wind up ratchet tight—and the job's done! Heavy gauge, zinc-plated steel with large "U" bolt for up to 1 3/4" O.D. mast and full length galvanized steel strapping.


THE RADIART CORPORATION
 CLEVELAND 13, OHIO
 RADIO-ELECTRONICS

TRANSISTOR RECEIVER OPERATES LOUDSPEAKER

By W. H. GRACE, JR.

THE simple circuit shown in the accompanying diagram, was assembled to determine the possibilities of a Western Electric A-1698 transistor as a detector-rectifier at standard broadcasting frequencies. This particular transistor is of the point-contact type and is made in cartridge form to fit the Cinch EXP8672 or equivalent socket. Connections may be soldered directly to the prongs and base of the device, but heat protection on the transistor side of the joint must be provided (as with a pair of flat-nosed pliers.) This requires extreme care, as the transistor can very easily be damaged by too much heat. The A-1698 model was designed to be used in switching circuits, not as a detector-rectifier. However, it functions very well in this capacity too. (A G-E type G11 transistor should also be usable in this circuit and may be easier to obtain commercially.)

The circuit components are self-explanatory to the experienced; a certain amount of elaboration seems appropriate for the tyros. The two inductances which comprise the L1 and L2 circuits are Ferri-Loopstick coils, available in radio supply stores as loop aerial replacements in a.c.-d.c. sets. Remove the short piece of enameled wire attached to one terminal before using. These coils have a very high Q and are inexpensive. The primary circuit is tuned by the series capacitor to ground, using both sections in parallel. The secondary circuit is aperiodic and is coupled to the primary by being placed parallel to it with about one-half inch

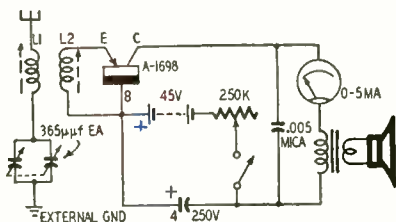

Materials for transistor receiver

Capacitors: 1—4-µf, 250-volt, electrolytic; 1—.005 µf mica; 1—2-gang variable receiving capacitor, 365 µf per section. Other parts: 1—250,000-ohm potentiometer; 1—Western Electric type A-1698 transistor or equivalent; 1—45-volt B-battery, 1—5-ma d.c. milliammeter, Ferri-Loopstick coils as per text, switch, headphones or speaker, wire, etc.

separation between coils. End-to-end coupling may be used with equal effectiveness if desired. Keep coupling as loose as possible for best selectivity compatible with ample volume. All point-contact type transistors appear to give best results with a grounded base type hookup. High impedance phones or output transformer winding will better match the impedance of the collector leg.

Operation of this receiver is conventional in most respects. All tun-

Carry This ONE Astatic Dual-Output Cartridge

AND YOU ARE READY FOR MOST 78 RPM REPLACEMENTS

Astatic Universal Model L-12-U Cartridge—Output Is Low (1.2 Volts) with Condenser Harness On; or Slip It Off when High Output (4.0 Volts) Is Needed.

YOU ARE virtually never at a loss when you carry the amazingly versatile Astatic L-12-U Crystal Cartridge. It's the one cartridge that replaces the great majority of 78 RPM units you encounter in your day-to-day business and, at the same time, gives assurance of reproduction qualities better or equal the previous cartridge when new! It isn't a CURE-ALL. But it is the closest thing to it that has been developed since the early days of the industry. It is your best answer for simplification of inventory, for avoiding lost time and problems of servicing, **WITHOUT SACRIFICE OF QUALITY RESULTS.** Performance, in every application, where recommended, is guaranteed by Astatic, the leader.

EXPORT DEPARTMENT

401 Broadway, New York 13, N. Y.
Cable Address: ASTATIC, New York

Astatic crystal devices manufactured under Brush Development Co. patents



SCOOP!

AM RADIO TUNER

made especially for any 630 or 630 DX Chassis. Complete, ready to install. Fits into well of TV chassis.

ROSE Special \$14.95 ea.

SUPER VALUE! SUPER VALUE! 630 DX-2 TV CHASSIS

Includes the same features as the 630 DX-1 chassis plus the following:

- ★ Keyed AGC level control
- ★ Cornell-Dubilier plastic molded condensers
- ★ 4.5 Megacycle wave trap to eliminate interference
- ★ Phono input & switch which cuts out high voltage supply
- ★ RCA matched 70° cosine yoke & Hi-Voltage transformer
- ★ RCA 12" PM Speaker

Net price Complete \$159.50 (less CRT)


New UHF Channel Strips! Another ROSE SCOOP!
Immediate \$8.95 complete Delivery strip

ROSE Co.'s Supermarket of SUPER VALUES

Wire, Call, Write, Come-in—Thousands of Bargains! 630-DX CHASSIS SUPER VALUE

1953 Model—Advanced Design—Great Saving!

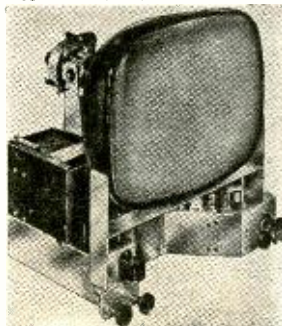
Includes newest developments—Cascade Tuner—30 Tubes—For 16" to 24" Picture Tube—Wonderful Saving! Adaptable for color & UHF!



The great 630 with all the up-to-date improvements! Wonderful reception on long range up to 200 miles, without a booster, is yours today at this low-low price. Gives 3-times normal reception. Special super high-gain standard coil tuner gives greater sensitivity, top performance on any channel. Aligned and tested for 5 hours, molded condensers, 4 microvolts sensitivity, FM sound system, horizontal & linear lock and is directly adaptable for color & UHF.

Model 630 DX-1: RMA Guaranteed—Factory Wired, ready to play. Complete with 12" speaker, hardware and knobs. \$149.50 (less CRT)

Universal Mounting Brackets...\$5.95 ea.

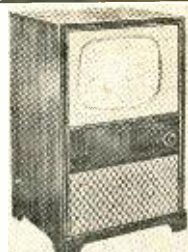

SAVE \$50 ON THIS DECORATOR TV CABINET For 17", 20" & 21" Picture Tubes—630 or other Chassis.

Every beautiful cabinet is richly finished of hand rubbed mahogany and made by our own cabinet-makers. They are custom styled, guaranteed new & perfect. Includes mask & mounting brackets. Cabinets are also available with blank control panel to fit any chassis.

Model 200: Original list \$99.95
Blonde finish, add \$10
Now! \$49.50

Also Deluxe Cabinets, write for catalog

SPECIAL LOW PRICES! SUPER VALUE

TV PICTURE TUBES

Full Year's Guarantee—Brand New—Black Face—Standard Brands
10BP4 \$19.95 20CP4A \$35.95
12LP4A 22.95 21EP4A 38.50
17BP4A 24.95 27EP4 99.50
All other sizes in stock—equally low priced!

THE ROSE COMPANY

100 Park Place—Dept. E-3—New York 7, N. Y. COrtlandt 7-6195.

PRICE REDUCTIONS

ON STANCOR YOKES and FLYBACKS

It's our way of saying, "Thanks for your confidence." Yes, thanks to you, the sale of these Stancor TV components has increased tremendously... our costs are lower... and we are passing these savings on to you.

These components are the same high quality, triple-tested units you have always received and come to expect from Stancor. At these new, low prices they are even better values than before.

DEFLECTION YOKES

PART NO.	OLD LIST PRICE	NEW LIST PRICE
DY-8	10.75	9.80
DY-8A	11.00	10.00
DY-9	10.75	9.80
DY-9A	11.00	10.00
DY-10	10.75	9.80
DY-10A	11.00	10.00
DY-11A	*	10.00
DY-12A	*	10.00

FLYBACKS

PART NO.	OLD LIST PRICE	NEW LIST PRICE
A-8128	10.50	10.00
A-8129	11.00	10.50
A-8130	11.00	10.00
A-8131	7.00	6.50
A-8132	*	10.50
A-8133	11.00	10.50
A-8134	11.00	10.50

STANDARD TRANSFORMER CORPORATION

3592 ELSTON AVENUE
CHICAGO 18, ILLINOIS



*New items: DY-11A is used in 172 models of 15 manufacturers. DY-12 is used in 160 models of 8 manufacturers. A-8132 is an exact replacement for Muntz TO-0031, used in over 300,000 sets. Ask your Stancor distributor for Bulletin No. 461 listing applications of these units, or write Stancor direct for your free copy.

Stancor Transformers are listed in Photofact Folders, Tek-Files and Counterfacts.

Export Sales: Roburn Agencies, 39 Warren Street, New York 7, N. Y.



Poof!
there goes
NOISE!

with
SPRAY KLEEN

contact cleaner & lubricant

- No More Eyedroppers
- Can't Spill
- Can't Break
- Can't Evaporate
- Cleans & lubricates in one operation

Available thru jobbers

WARD E. RICE INDUSTRIES
P.O. Box 1705, Glen Park Sta., Gary, Ind.

Only
\$1.00
Net
6 full ounces

ing is done with the single dial on the 700- μ f variable capacitor shaft with the variable resistance adjusted so that approximately 1 ma of current is flowing in the collector circuit. When a station is tuned in, the meter will indicate a slight rise; adjust the resistor knob to the position where 2 ma is shown by the meter dial. This will give the loudest signal for that frequency.

As the collector current is controlled by the amount of resistance in the collector circuit it is almost imperative to employ a meter with a 5-ma scale. Never allow more than about 2 ma to flow through the circuit, or the transistor may burn out. Do not apply power to the transistor without first setting the resistance to its highest value. Avoid excessive transients, as in plugging the transistor in or out of its socket with the power on. Remember that these devices, as far as the collector circuit is concerned, are merely diodes with a small amount of backward current flowing through the circuit. Naturally, the collector circuit must always be biased in the direction of high diode resistance, as a reversal will burn out the element forthwith. It is the presence of current from the incoming signal in the emitter circuit which affects the resistance of the collector reversed-diode circuit and thus accounts for the gain.

The receiver will operate a loud-speaker on several local stations at this location. Five or six stations can be heard with volume sufficient to be audible in every room of the house. *A good aerial and ground are required for speaker results.* Under favorable conditions the results compare quite well with those obtained with a single-tube receiver. The over-all sensitivity does not equal that of a grid-leak tube detector, but some dx (up to several hundred miles) has been recorded with headphones instead of speaker. Considering that less than 2 ma is drawn from the battery the volume is unusually good.

END

Loe E. Buresch



"Wottaya mean, the reception was better a minute ago? I had the lead-in attached to the lightning rod."

RADIO-ELECTRONICS

Buy on our radically new
NO INTEREST!! **Time Payment Plan** **NO CARRYING CHARGES!!**
— OUR POLICY —

All merchandise offered on a "try-before-you-buy" basis. If the item you order does not meet with your approval, you may return it, no explanation necessary.

All merchandise offered on easy terms at the net cash price with no interest charges added!

Superior's New Model 770

VOLT-OHM MILLIAMMETER
Sensitivity—1000 ohms per volt



Uses latest design 2% accurate 1 Mil. D'Arsonval type meter. • Same zero adjustment holds for both resistance ranges. It is not necessary to readjust when switching from one resistance range to another. This is an important time-saving feature never before included in a V.O.M. in this price range. • Housed in round-cornered, molded case. • Beautiful black etched panel. Depressed letters filled with permanent white, insures long-life even with constant use.

SPECIFICATIONS:
 6 A.C. VOLTAGE RANGES: 0-15/30/150/300/1500/3000 Volts.
 6 D.C. VOLTAGE RANGES: 0-7.5/15/75/150/750/1500 Volts.
 4 D.C. CURRENT RANGES: 0-1.5/15/150 MA. 0-1.5 Amps.
 2 RESISTANCE RANGES: 0-500 Ohms 0-1 Megohm.

Model 770 is an accurate pocket-size V.O.M. Measures only 3 1/2" x 5 7/8" x 2 1/4".

\$14.90
 NET

The Model 770 comes complete with self-contained batteries, test leads and all operating instructions.

Superior's New Model TV-11 TUBE TESTER



• Uses the new self-cleaning Lever Action Switches for individual element testing. Because all elements are numbered according to pin number in the RMA base numbering system, the user can instantly identify which element is under test. Tubes having tapped filaments and tubes with filaments terminating in more than one pin are truly tested with the Model TV-11 as any of the pins may be placed in the neutral position when necessary. • Uses no combination type sockets. Instead individual sockets are used for each type of tube. Thus it is impossible to damage a tube by inserting it in the wrong socket. • Free-moving built-in roll chart provides complete data for all tubes. • Phono jack on front panel for plugging in either phones or external amplifier detects microphonic tubes or noise due to faulty elements and loose external connections.

Operates on 105-130 Volt 60 Cycles A.C. Hand-rubbed oak cabinet complete with portable cover

\$47.50
 NET

Superior's New Model 670-A

SUPER-METER



A combination volt-ohm milliammeter plus capacity reactance inductance and decibel measurements

SPECIFICATIONS:
 D.C. VOLTS: 0 to 7.5/15/75/150/750/1,500/7,000 Volts
 A.C. VOLTS: 0 to 15/30/150/300/1,500/3,000 Volts
 OUTPUT VOLTS: 0 to 15/30/150/300/1,500/3,000 Volts
 D.C. CURRENT: 0 to 1.5/15/150 Ma. 0 to 1.5/15 Amperes
 RESISTANCE: 0 to 1,000/100,000 Ohms 0 to 10 Megohms
 CAPACITY: .001 to 1 Mfd. 1 to 50 Mfd. (Quality test for electrolytics)
 REACTANCE: 50 to 2,500 Ohms 2,500 Ohms to 2.5 Megohms
 INDUCTANCE: .15 to 7 Henries 7 to 7,000 Henries
 DECIBELS: -6 to +18 +14 to +38 +34 to +58

Comes housed in rugged, crackle-finished steel cabinet complete with test leads and operating instructions. Size 6 1/4" x 9 1/2" x 4 1/2".

\$28.40
 NET

ADDED FEATURE
 The Model 670-A includes a special GOOD-BAD scale for checking the quality of electrolytic condensers at a test potential of 150 Volts.

Superior's New

TV BAR GENERATOR

THROWS AN ACTUAL BAR PATTERN ON ANY TV RECEIVER SCREEN!!



CONNECTS DIRECT TO ANTENNA POST
NO CONNECTION INSIDE RECEIVER

Features—
 Can be used when no stations are on the air. • Provides linear patterns to adjust vertical and horizontal linearity • Provides vertical and horizontal sweep signals • Provides signal for testing video amplifiers.

TV Bar Generator comes complete with shielded leads and detailed operating instructions. Only

\$39.95
 NET

Superior's Model 660-A—A NEW A.C. OPERATED SIGNAL GENERATOR



Provides Complete Coverage for A.M.—F.M. and TV Alignment

• Generates Radio Frequencies from 100 Kilocycles to 60 Megacycles on fundamentals and from 60 Megacycles to 220 Megacycles on powerful harmonics. • Accuracy and stability are assured by the use of permeability trimmed Hi-Q coils. • R. F. available separately or modulated by the internal audio oscillator. Built in 400 cycle sine wave audio oscillator used to modulate the R. F. signal also available separately for audio testing of receivers, amplifiers, hard of hearing aids, etc. • R. F. Oscillator Circuit: A high transconductance heptode is used as an R. F. oscillator, mixer and amplifier. Modulation is effected by electron coupling in the mixer section thus isolating the oscillator from load changes and affording high stability. • A. F. Oscillator Circuit: A high mu triode is used as an audio oscillator in a high-C Colpitts Circuit. The output (over 1 Volt) is nearly pure sine wave. • Attenuator: A 5 step ladder type of attenuator is used.

• Tubes used: 1—6BE6 as R. F. Oscillator, mixer and amplifier, 1—6BE6 as Audio Oscillator, 1—6M6 as Power Rectifier.

The Model 660-A comes complete with coaxial cable, test load and instructions

\$42.95
 NET

NEW TIME PAYMENT PLAN
 ORDER BLANK

MOSS ELECTRONIC DISTRIBUTING CO., INC.
 Dept. B-52, 38 Murray Street, New York 7, N. Y.

Please send me the units checked below. I am enclosing the down payment with order and agree to pay the monthly balance as shown. It is understood there will be no carrying, interest or any other charges, provided I send my monthly payments when due. It is further understood that should I fail to make payment when due, the full unpaid balance shall become immediately due and payable.

- MODEL 770 Total Price \$14.90
 \$2.90 down payment. Balance \$2.00 monthly for 6 months.
- MODEL TV-11 Total Price \$47.50
 \$11.50 down payment. Balance \$6.00 monthly for 6 months.
- MODEL 670-A Total Price \$28.40
 \$7.40 down payment. Balance \$3.50 monthly for 6 months.
- TELEVISION BAR GENERATOR Total Price \$39.95
 \$9.95 down payment. Balance \$5.00 monthly for 6 months.
- MODEL 660-A Total Price \$42.95
 \$12.95 down payment. Balance \$5.00 monthly for 6 months.

- I enclose \$_____ as down payment.
- Ship C.O.D. for the down payment.

Signature _____

Name _____

Address _____

City _____ Zone _____ State _____

PERSONAL MUSIC

CHROME MUSIC BOX containing 5" Speaker and Coin Timer Motor. Can be used for remote speaker in Home, Car, Shop, Boat, Office, etc. Timer Motor operates from 24 Volt 60 cycle. Prices:



With 5" Dynamic Speaker \$3.55
 With 5" PM Speaker \$4.95

TRANSFORMER—24 Volt to operate Timer Motor from 110 V. 60 cycle \$1.50

ATTENTION!

TELEVISION FRINGE AREAS

AIRCRAFT GUY CABLE— $\frac{3}{32}$ " 7 x 7 Strand, Weatherproofed, Galvanized, Preformed—920 lb. Test. This cable has been tested and proven in many fringe areas over many years—millions of feet in use. PRICES: $4\frac{1}{2}$ ¢ per Ft.—1000 Ft. @ $4\frac{1}{2}$ ¢ per Ft.—5000 Ft. @ $3\frac{1}{2}$ ¢ per Ft.

REVERSIBLE MOTOR



Motor Reversible—3.7 RPM. 40 lb. torque. 24 Volts DC or AC. Motor size: $5\frac{1}{2}$ " x $4\frac{1}{2}$ " x $3\frac{3}{16}$ ". Shaft size: $2\frac{1}{32}$ " x $5\frac{1}{16}$ ". Philco No. 441-1008 NEW: \$5.95
 110 Volt AC TRANSFORMER to operate above \$4.95
 motor NEW:

AERIAL WIRE—Phosphorus Bronze #16 Stranded, 200 lb. test. Weatherproof, 150 Feet on Reel, RL-3 with Clips \$1.50
 Telephone Wire—3 Cond. copper & steel, 525 Ft. \$4.75

JUST WHAT YOU NEED . . .

Standard Test Leads, 4" x $1\frac{1}{2}$ " Prods. Pair 39¢
 3 for \$1.00
 Phone Plug—Nickel Plated, Screw Terminals. Each: 39¢ — 3 for \$1.00
 Instrument Knobs—Bar, Octagon, Round, Set Screw, Skirts—Asst. 10 for \$1.00
 Line Cord—Brown Rubber 7 Ft., Molded Rubber Plug Each: 29¢ — 4 for \$1.00
 Line Cord—Black Rubber 6 Ft. Angle Molded Plug Each: 39¢ — 3 for \$1.00
 Resistors Carbon—Asst. $\frac{1}{4}$, $\frac{1}{2}$, 1 and 2 Watt 100 for \$2.95
 Resistors—Wire Wound—Asst. 5 to 100 Watt 25 for \$2.95
 Mica Condensers—Asst. Values & Voltages—50 for \$2.95

PE-101C DYNAMOTOR

(Reprints of original CQ conversion articles, Oct. and Dec., 1952 issues, furnished.)



• This is the Dynamotor the Hams have been talking about. Easily adapted to supply 625 V. @ 150 MA. and 325 V. 125 MA. at 12 V.—or 300 V. 90 MA. and 160 V. 110 MA. at 6 V. (Illustration shows modified) NEW: \$4.95

BATTERY SWITCHING UNIT & METER

Used to switch load from one battery to another, or 6 to 12 Volts. Contains Weston 2" Meter, 0-15 Volt DC Scale for reading battery voltage, 20 Amp DPDT Switch & Indicator. Case size: 4" x $6\frac{1}{4}$ " x $2\frac{3}{4}$ ". NEW: \$2.95

TRANSFORMERS—110 V. 60 CYCLE PRIMARIES:

5 Volt CT-25A—10,000 V. Ins. OPEN FRAME—6" x 5" x $4\frac{1}{2}$ " \$7.95
 6.3 V. 1 Amp. \$1.25 24 V. 1 Amp. \$1.95
 24 V. $\frac{1}{2}$ Amp. \$1.50 24 V. 6.5 Amp. \$5.95
 6—24—or 30 Volt, 8 Amp. \$5.95
 Two 12 V. 4 Amp Windings—gives 12 V. 8 Amp or 24 V. 4 Amp. \$5.95
 325-0-325 V. 50 MA.—6.3 V. 2.5 Amp. 6.3 Volt .6 Amp (Rect. 6x5) Half Shell— $2\frac{7}{8}$ " x $3\frac{3}{8}$ " x 3". No. T-23-28 \$2.75
 440 VCT/70 MA.—5 V. 2 Amp.—6.3 V. 4 Amp \$3.35
 460 VCT/90 MA.—5 V. 3 Amp.—6.3 V. 4 Amp. \$3.75
 175-0-175 V. 40 MA.—6.3 V. @ 2.4 A.; 6.3 V. @ .6 A.; Halfshell: $2\frac{7}{8}$ " x $2\frac{3}{8}$ " x $2\frac{3}{8}$ ". No. T-23-40 \$1.75
 350-0-350 V. 90 MA.—6.3 V. @ 3 A.; 5 V. @ 3 A.; Upright— $3\frac{1}{2}$ " x $3\frac{1}{8}$ " x $3\frac{3}{8}$ " \$3.25

CHOKES:

15 Henries—165 MA. 125 ohms \$2.95
 5 Henries—150 MA. 85 ohms DC—Res. Cased \$1.95
 8 Henries—150 MA. 200 ohms \$1.95
 5-20 Henries—300 MA. 110 ohms, 1000 V. Ins. \$3.95

Address Dept. RE • Minimum Order \$5.00
 Prices F.O.B., Lima, O. 25% Deposit on C.O.D. Orders
FAIR RADIO SALES
 132 SOUTH MAIN ST. LIMA, OHIO

EDITOR TOURS PENNA.

RADIO-ELECTRONICS' Associate Editor, Mort Bernstein, had an opportunity to study contrasting TV service problems in York and Williamsport, Pa. recently. On January 6, despite snow, sleet, wind, and rain, York technicians were frantically busy, indoors and out, trying to solve two urgent—and profitable—problems at once: In one week, York's nearest v.h.f. station—WGAL-TV 25 miles away in Lancaster, Pa.—shifted from channel 4 to channel 8; and a new u.h.f. station—WSBA-TV on channel 43—opened up in York itself.

Almost every high-gain channel-4 antenna had to be replaced with one cut for channel 8, or relocated and reoriented to eliminate ghosts and the effects of changed transmission paths at the new frequency. In many cases—especially where the sets had been used solely on channel 4 for more than a year—the channel-8 segments of the tuner had to be realigned. One problem (and this is certain to crop up wherever high-band channels come on the air for the first time) was the apparent failure of sets that worked perfectly on channel 4 to work at all on channel 8. The answer was simple (after someone had thought of it): *Replace the local oscillator tube.* Most h.f. oscillators have much higher output on the low band than for channels 7-13. Normal loss of emission through use over a year or more is not generally severe enough to weaken low-band channels to the extent where they can't be brought in by turning up the contrast control; but when a high-band channel is tuned in for the first time—it just isn't there!

The problem of converting for u.h.f. channel 43 had plenty of headaches too. As could have been predicted, you couldn't predict anything! In some cases built-in antennas gave perfect results; in others—even closer to the u.h.f. transmitter—arduous hours of raising, lowering, shifting, and relocating were necessary to bring in anything at all. With some types of v.h.f. ribbon lead-in the u.h.f. signals faded out like the Cheshire cat when it started raining (leaving the grin, of course, on the face of the u.h.f.-lead-in manufacturer).

Where external converters were used, with output on channels 5 or 6, the v.h.f. receiver had first to be aligned precisely on the required channel to make sure signals could get through from the converter at all. This called for highly-accurate channel markers, since there were no stations available on these channels for reference.


With u.h.f. converters that have high-v.h.f.-band output (channel 10) the problem of the weak oscillator tube in the v.h.f. receiver was added to the complications. But these are jobs the technician gets paid for, so nobody was complaining except the customers, who face waits of two to five weeks for their antennas, converters, and installations.

At a meeting held in York on the evening of January 6, Bernstein spoke to the members of the Southern Pennsylvania Radio and Television Servicemen's Association on servicing problems, circuit analysis, and recent de-

THE NEW

Sky Hi

HYDRAULIC MAST

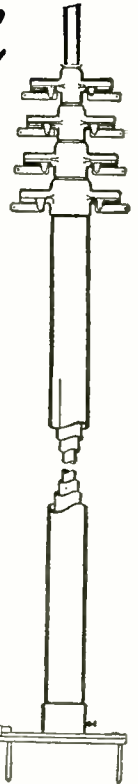

Now you can have the SKY-HI mast in steel or aluminum with latches or without, in any height up to and including 200 feet.

Your choice of hand pump, 110 volt or 6 volt electric driven pump, or in many cases available water pressure is sufficient for operating the aluminum mast.

Also complete trailer and mast assembly up to 100 feet for survey work ready to put into service.

These products are approved and used by many government and commercial agencies.

We welcome comparison with any other mast built when you are considering speed of erection and lowering, and all around versatility.

Write for details.

THOMAS MOLD & DIE CO.

WOOSTER, OHIO

OSCILLOSCOPES ARE "GOLD MINES"!



... if you learn how to use them fully on all types of service jobs!

Learn to handle the oscilloscope fully on all types of AM, FM and TV service work—and watch your efficiency and earnings soar!

MODERN OSCILLOSCOPES AND THEIR USES, a fact-jammed 326-page book by Jacob H. Ruiter, Jr., of the Allen B. DuMont Laboratories, contains exactly the help you need—written in a way you can clearly understand. It shows you how to use your 'scope for fast accurate work on all types of jobs from troubleshooting to realigning; how to make connections; how to adjust circuit components; how to set controls and how to analyze patterns fast and accurately. 370 helpful illustrations including dozens of pattern photos make things doubly clear.

No other type of specific service training stands to mean so much to you in terms of being able to do better, faster and more profitable work!

- V When, where, why and exactly how to use your oscilloscope
- V How to interpret patterns
- V How to handle tough jobs in less time

MAIL ORDER 10-DAY FREE EXAMINATION

Dept. RE-33, RINEHART BOOKS, Inc. Technical Division, 232 Madison Ave., New York 16, N. Y. Send MODERN OSCILLOSCOPES AND THEIR USES for 10-DAY EXAMINATION. If I decide to keep the book, I will then remit \$6.00 plus a few cents postage in full payment. If not, I will return book post-paid and owe you nothing.

Name _____
 Address _____
 City, Zone State _____
 Employer's Name & Address _____
OUTSIDE U.S.A.—Price \$6.50, cash only. Money back if book is returned in 10 days.

LEOTONE RADIO CORP.
67 Day Street
New York 7, N. Y.

!!MOTOR SPECIAL!! 1 40 H.P. AC Motor (Robbins & Myers) 115 V., 1650 RPM. 5/16" O.D. shaft. With condenser & SPDT switch. Shpg. wt. 7 lbs. C.O.D. 1 1/4" x 1 1/2" **4.95**
17 H.P. G.E. MOTOR (Type 50) 1725 RPM. 7 amp. Shunt wound. 3/8" shaft. 110 V. C.O.D. 4 3/4" x 5 1/2". Shpg. wt. 13 lbs. **2.95**

!!XMAS IN MARCH!! with the NEWEST "JUMBO RADIO PARTS KIT" "GOLD-MINE" of inventory cards & ends including:
CONTROLS
SOCKETS
SWITCHES
WIRE
CONDENSERS
RESISTORS
and M.U.C.H. MUCHE!
Shpg. wt. **3.95**
20 lbs.

2.5V. FIL. TRANSFORMER (1 1/2" x 1 1/2") 1 amp. **.79**

DPDT 12V. DC RELAY (1 1/2" sq. x 2") 70 ohm coil **.88**
6V. AC-DC PLUNGER SOLENOID (1 1/2" x 1 1/2" O.D.) **.89**
PHOTOELECTRIC CELL (selenium) 2 1/2" x 1 1/2" **.8**
BALL BEARINGS, O.D. 1/2", I.D. 3/16" ea. **22¢** 1.00
RADIO HARDWARE TREASURE FULL LB. CAN OF: Nuts, Screws, Lugs, Washers, etc. **89¢** 2.49
SOUND-POWER PHONE UNITS use as mike or recv. Sealed metal case. ea. **1.95** 2.39
DYNAMIC HEADSET & HAND MIKE (press-to-talk) Brand new (1 1/2" x 1 1/2" x 1 1/2") **3.75**
METAL UTILITY CAN (4" x 1 1/2" x 1 1/2") for Sm. Components, Hardware, etc. Moisture-proof snap lid. ea. **10¢** 1.00

!!TUBE CLEARANCE SALE!! 90 DAY GUARANTEE. Standard brands; unscathed cartons.
2B, 27, 31, 41, 42, 50, 50A, 50B, 50C or 6K7 ea. **29¢**
1E4, 1H6, 1J6, 6B7, 6F5, 6G5, 6SD7, 6SH7, 6RT or 7R **39¢**
5Y3, 5Y4, 5Y5, 7L, 7T, 7L4, 5Y3, 5Y4, 5U4, 6G6, 6J5, 6K6, 6SA7, 6SK7, 6SQ7, 6C5, 6U7, 7A4, 7B6 or 7C7 **59¢**
1A7, 1L6, 1L7, 2A5, 2A6, 6AG5, 6AG6, 6AR, 6B8, 6SC7, 6SN7, 7A7, 7AG7, 7C6, 7C7, 7Y1, 12SN7, 47, 50, 57, 58 or 81, ea. **69¢**
TUBE CARTONS plain white. Prices per 100:
Min (1 1/2" sq. x 3 1/2") **1.20**; GT (1 1/2" sq. x 3 1/2") **1.45**;
Med (1 1/2" sq. x 1 1/2") **1.65**; large (2" sq. x 5") **1.98**

CONNECTOR VALUES!! Jones 33 CONTACT (2333) Cable female; panel male. Off cable set **51.29** 5.00
PL-54 / JK-26 CONNECTORS, 2 wire, set **39¢** 10 / 3.49
PL-291 JK-48 MIDGET CONN., set **49¢** 10 / 4.49
4 WIRE PLUG JACK, cable-cable, set **59¢** 6 / 2.98
CABINET DRAW SLIDES, silent, ball-bearing: 1 1/2" (9" ext.) **2.10** pr.; 1 3/4" (11" ext.) **2.25** pr.; 1 1/2" (12 1/2" ext.) **2.39** pr.; hvy. duty, all-steel 1 1/2" x 1 1/2" slides, pair **53.25**

DIRECT FACTORY SPEAKER REPAIRS SINCE 1927. SPECIALISTS ON ALL TYPES OF "HIGH-FIDELITY" UNITS. Min. Order \$3.00. 20% deposit req. on all C.O.D.'s. Full remittance with foreign orders. Please add sufficient postage—excess refunded.

Leading ENGINEERS and TECHNICIANS Recommend...

TECH-MASTER CUSTOM-BUILT TV CHASSIS

GOLD MEDAL SERIES Deluxe TV Chassis

World's Most Sensible, Most Reliable TV Receiver—Truly custom-designed and custom-built to provide the ultimate in sight, sound, and value. Employs most advanced engineering methods, finest components, and most rigid alignment and test standards. Tech-Master improved 630-type chassis • Advanced Cascode Standard turret tuner, adaptable to UHF without tools • Full 4 Mc. bandwidth • Quick action keyed AGC circuit • New, Hi-sweep auto-transformer system • 5 microvolt sensitivity • For all picture tubes from 16" to 24".

MODEL 2430: with quality PM speaker, all tubes less picture tube, universal picture tube m't'g. brackets, phono-input jack. Equipped with audio take-off to feed sound thru external amplifier, if desired **\$189.50**

MODEL 2431P: Same as 2430, (less sound take-off), but with true fidelity Push-Pull Audio Amplifier **\$199.95**

Chassis plated, gleaming nickel finish... completely wired, aligned and tested, ready for installation.

BLUE RIBBON Custom-built TV Chassis

Designed for the utmost in value, with famous Tech-Master design features for high quality image and sound. Retains the outstanding characteristics of the RCA-630 circuitry, namely the 4-stage, full bandwidth picture 1F strip, and the 3-stage FM sound section • Latest innovations in synch and sweep circuits • Advanced Cascode turret tuner adaptable to UHF without tools • 5 microvolt sensitivity • Permanent magnetic focalizer • A.G.C. level control • 29 tubes (including 4 rectifiers). For all picture tubes from 16" to 24".

MODEL C-30: With quality PM speaker, and all tubes (less picture tube), completely wired, aligned and tested **\$149.50**

Sold by all leading Radio Parts Distributors.

Write for detailed literature

TECH-MASTER PRODUCTS CO.
443-445 BROADWAY, NEW YORK 13, N. Y.

Just Out

Most - Often - Needed

1953

Television

Servicing Information

This newest giant volume of the Supreme TV series covers 1953 factory data on all popular television sets of all makes. There are explanations of new circuits, 192 pages of alignment procedure, test patterns, response curves, pages of waveforms, voltage charts, service hints, production changes, and dozens of double-spread circuit diagrams. Manual-style binding (opens flat). Special price, only **3**

New SUPREME 1953 TV Manual


GET IT AT YOUR RADIO JOBBER OR SEND COUPON

COVERS ALL POPULAR SETS

This new Supreme 1953 TV manual has all the required service material on every popular television set of every important manufacturer. Here is helpful, practical, factory-prepared data that will really make TV servicing and adjustment easy for you. Benefit and save with this amazing manual scoop. This new giant TV manual, as well as the previous volumes for other years, has complete circuits, alignment facts, test patterns, response curves, service hints, recommended changes, voltage charts, waveforms, and many double-page diagram blueprints. Here is your TV service material to help you do more expert work quicker; and priced at only \$3 and \$2 per manual covering a whole year of material. See coupon below for the complete list of all seven TV volumes, from 1947 to 1953. Order at our risk for a 10-day trial.

AMAZING BARGAIN OFFER

The new 1953 TV manual is the most remarkable value offered by Supreme Publications in their 19 years of business. This mammoth television servicing manual at only \$3, or the TV manuals for previous years for only \$3 and \$2 each, are amazing bargains and defy competition. There is nothing else like them. Each manual is a virtual treatise on practical television repairs. By normal standards, each such large manual packed as it is with practical facts, hundreds of illustrations, diagrams, charts, photographs, and expensive extra-large blueprints, should sell for \$10—but as SUPREME special values they are priced at \$3 and \$2 each. Only a publisher who sold over one million TV and radio manuals can offer such bargains based on tremendous volume-sales. Be ready to repair any TV set by having in your shop all seven Television Manuals listed in coupon. Or try the new 1953 TV manual to see what an amazing bargain you get for only \$3. Send no-risk trial coupon.

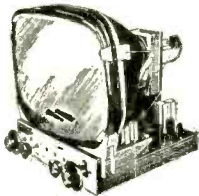

The repair of any television set is really easy with Supreme TV service manuals. Every set is covered in a practical manner that will simplify troubleshooting and repair. This is the help you need to find toughest faults in a jiffy. Each \$3 volume covers a whole year of material. Be wise, buy Supreme Manuals only once each year instead of spending dollars every week for not needed data.

Most - Often - Needed

1952

RADIO DIAGRAMS

Servicing Information

RADIO DIAGRAMS

Here is your complete source of all needed RADIO diagrams and service data. Covers everything from most recent radios to pre-war old-timers; home radios, auto sets, combinations, changers, and portable. Sensational values. Still sold at pre-Korean prices. Only \$2 for most volumes. Every Radio manual contains large schematics, all needed alignment facts, parts lists, voltage values, trimmers, dial stringing, and helpful service hints. Volumes are large in size, 8 1/2 x 11 inches, about 192 pages. See coupon at right for a complete list of these low-priced manuals.

NO-RISK TRIAL ORDER COUPON

SUPREME PUBLICATIONS, 3727 W. 13th St., Chicago 23, ILL.

Radio Diagram Manuals

- New 1952 Manual, \$2.50
- 1951 Radio EACH
- 1950 Manual } **\$2.50**
- 1949 Radio
- 1948
- 1947
- 1946
- 1942
- 1941
- 1940
- 1939
- 1926-1938 Manual, \$2.50

PRICED AT ONLY \$2 EACH

Send TV and Radio manuals checked below and at left. Satisfaction guaranteed or money back.


- New 1953 Television Servicing Manual, \$3.
- 1952 Television Manual, \$3.
- 1950 Television Manual, \$3.
- 1948 TV, \$3.
- 1951 TV, \$3.
- 1949 TV, \$3.
- 1947 TV & FM, only \$2.

I am enclosing \$..... Send postpaid.
 Send C.O.D. I am enclosing \$..... deposit.

Name:
Address:

Supreme Publications
Available from Leading Radio Jobbers
MARCH, 1953

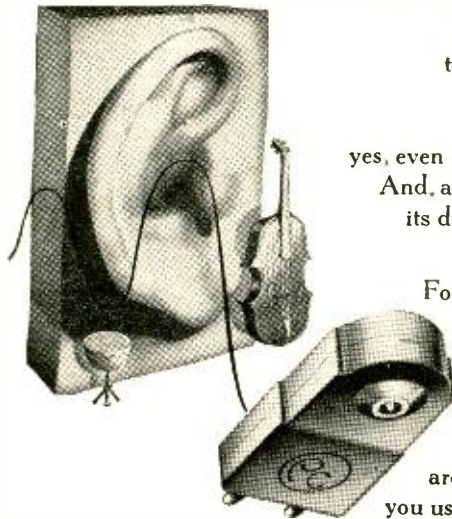"For those who can hear the difference"
Listen . . .



it comes to you
in the subtle shading of a piano . . .
in the clean brilliance of violins,
the purity of a flute. Your ear detects
the sweet mellowness of cellos,
the roundness of a clarinet . . .
yes, even the iridescence of clashing cymbals.
And, as the symphony swells to crescendo,
its dynamic energy adds a flood of color
to your musical canvas.

For those who can hear the difference,
these are the elusive pleasures
that often remain hidden
in the grooves of fine recordings.
These are the thrilling
new listening experiences that
are released for your enjoyment when
you use quality components by Pickering.


PICKERING and company, incorporated

Pickering High Fidelity Components are available through leading Radio Parts distributors everywhere; detailed literature sent upon request. Address Department P-1.


Oceanside, L. I., New York



ORIGINAL

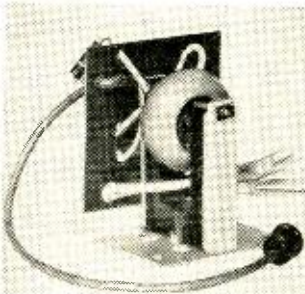

REPLACEMENT

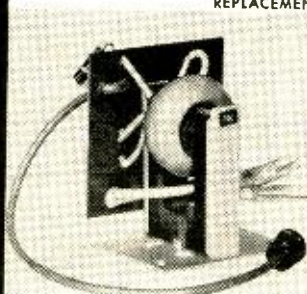

can you tell . . .

which transformer
is the RAM?

If you can't tell any difference between the original and replacement flybacks these days, there's good reason. They're TWINS—they're BOTH RAMS!

Yes, the great majority of famous TV set manufacturers order their original flybacks built to their own specifications by RAM. They know that a RAM-built original surpasses their every quality and performance standard.

Under the special RAM twin-transformer manufacturing technique, in most instances the originals destined for the TV set maker and the replacements destined for the RAM-brond and your jobber's shelf are both made at exactly the same time, during the identical production run!

That's why you can be certain—9 times out of 10—that a RAM-brand replacement is the best replacement, for highest efficiency and durability. And that's why RAM components are lowest-priced in the industry, for highest profits for you.

ONLY RAM manufactures 29 types of transformers, 10 types of deflection yokes and 15 types of linearity and width coils—the industry's most complete, most diversified sweep replacement line. See them at your local distributor.

FREE!

RAM 1953-edition Replacement & Conversion Manual—over 5000 sweep component listings—most complete in the industry. Write Dept. C-3.



Ram ELECTRONICS SALES CO.
IRVINGTON-ON-HUDSON, N. Y.
TEST-PATTERN TESTED COMPONENTS FOR TV

velopments in transistors, but he feels he owes them a debt of thanks for what they taught him about u.h.f.

Williamsport, Pa.

On January 7, our Associate Editor got the low-down on conditions in Williamsport, and that evening addressed the Central Pennsylvania technicians' group. Williamsport lies in a valley, about 100 miles north of York, surrounded by high parallel ridges of the Allegheny mountain chain. These ridges run generally in a northeast-southwest line and form a crude natural wave-guide for v.h.f. signals from Altoona, Johnstown, and Pittsburgh, in southwestern Pennsylvania. That is, the wave guide is effective as long as you're up on one of the surrounding ridges. Williamsport has no local TV station, but the city is fed by three competitive community antenna systems. These have their antennas, tuners, channel amplifiers, and main distribution equipment on various mountain tops surrounding the city, and run coaxial feeders on public-utility poles along the streets and local highways. Customers pay a substantial cash installation fee for a tie-in, plus a monthly rental charge.

Receiver service problems are routine, except for a.g.c. and sync difficulties, generally caused by excessive signal from the distribution lines. In some instances, the gain of the community systems on weak channels is raised by narrowing the r.f. bandwidth. This gives excessive boost to the picture carrier, and to the sync pulses which lie close to the carrier. Another undesirable effect of this practice—for which the set-owner generally blames the innocent service technician—is the loss in picture detail. With extremely limited bandwidth the pictures come out almost like simple animated cartoons—merely black and white.

The majority of the technicians' headaches are not the fault of the receivers, but they have a hard time convincing customers that they should be paid for diagnosing trouble in the community antenna systems.

LICENSING DEBATED

The question "to license or not to license" service technicians is getting intensified attention in New York, Philadelphia, Chicago, and other areas, with the result that spirited arguments and strongly worded articles on the subject are appearing in a number of trade papers. One such series—in the newspaper *Retailing Daily*, has taken almost the form of a debate.

Opener was Mort Farr, of Upper Darby, Pa., head of the National Appliance and Radio-TV Dealers Association. Opposing licensing, he pointed out that many of the complaints against TV service were due to the vast and rapid growth of the industry, which made it inevitable that technical know-how would lag behind demand, and cited surveys showing that today the average TV owner is satisfied with his service technician. The "dwindling number of


 TRIPLETT

650 VTVM

There's Nothing finer for

Television



This combination of features explains why

- Complete frequency coverage with one probe, 20 cps to over 110-mc. Insulated and shielded RF tube probe, found usually only with laboratory instruments, is included.
- Peak to Peak ACV and RF with one probe.
- One volt full scale reading on AC & DC.
- One main selector switch, all ranges.
- ACrms—Peak to Peak
- 32 Ranges
- Zero center mark for FM discriminator alignment plus any other galvanometer measurements.
- High input impedance 11 megohms on DC.

Suggested U.S.A. Dealer Net \$69.50 • Prices subject to change without notice.

TRIPLETT ELECTRICAL INSTRUMENT CO., BLUFFTON, OHIO

Triplet

TRIPLETT



70% to 90% off list! TOP TUBE BUYS

All Tubes Individually Boxed! Same Day Service!
Check this list for Fully 90-Day Guaranteed Tubes

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
0B3 VR90	.75	5V4	.73	6BH6	.46	6UB	.61	198G6G	.95
1A5GT	.30	5W4	.50	6BJ6	.39	6V3	.93	19C8	.70
1A6G	.30	5X4	.40	6BK7	.59	6V6GT	.39	19T8	.79
1A7GT	.47	5Y3G	.32	6BQ6GT	.59	6W4GT	.44	19V8	.89
1A8S	.30	5Y3GT	.32	6BQ7GT	.95	6W6GT	.44	24A	.63
1B3	.65	5Y4G	.35	6BZ7	.90	6X4	.37	25AV5	.83
1B5	.30	5Z3	.46	6C4	.37	6X5GT	.37	25BQ6GT	.62
1B7GT	.30	6A3	.59	6C5GT	.39	6Y6G	.48	25L6GT	.39
1C5GT	.43	6A7	.59	6C6	.58	7A4	.47	25Z5	.40
1E7	.29	6A8	.62	6C86	.44	7AF7	.53	25Z6GT	.37
1H4G	.30	6AB4	.44	6CD6G	1.11	7B4	.44	25W4	.56
1H5GT	.40	6AG5	.43	6D6	.45	7C6	.40	26	.45
1G6	.30	6AJ5	.90	6E5	.48	7E6	.30	27	.39
1L4	.46	6AK5	.75	6F5GT	.39	7X7	.70	32L7GT	.89
1L05	.51	6AL5	.38	6F6	.37	12A8	.61	35B5	.40
1N5	.46	6AQ5	.39	6G6G	.52	12A15	.37	35C5	.39
1P5	.57	6AQ6	.37	6H6GT	.41	12AT6	.37	35L6GT	.41
1Q5	.58	6AR5	.37	6J5GT	.37	12AT7	.56	35W4	.37
1R5	.45	6AS5	.50	6J6	.52	12AU6	.38	35Z4	.39
1S5	.39	6AT6	.37	6K6GT	.37	12AU7	.43	35Z5GT	.37
1T4	.45	6AUG	.38	6J7G	.43	12AV6	.39	36	.60
1T5	.53	6AV5	.83	6J8	.30	12AV7	.59	41	.42
1U4	.45	6AV6	.37	6K5	.47	12AX4	.48	42	.42
1U5	.39	6AX4	.53	6K7	.44	12AX7	.48	43	.55
1V	.60	6B4G	.64	6L6	.64	12AZ7	.69	45	.55
1X2	.63	6B5	.39	6Q7	.45	12BA6	.38	50B5	.39
2A3	.70	6BA7	.57	6S4	.38	12B6	.45	50C5	.39
2X2	1.50	6B8G	.44	6S8	.53	12B6G	.39	50C6	.59
3A4	.45	6BC5	.44	6SA7GT	.43	12BF6	.39	50L6GT	.41
3E5	.46	6BD5GT	.59	6SD7GT	.41	12BH7	.63	50V6	.46
3Q4	.48	6BD6	.45	6SF5GT	.46	12J5GT	.42	50Y7	.50
3Q5GT	.49	6BE6	.39	6SG7GT	.41	12Q7G	.39	57	.58
3S4	.46	6BF5	.41	6SH7	.73	12S8	.70	58	.60
3V4	.47	6BF6	.37	6SJ7GT	.41	12SA7GT	.44	70L7GT	1.09
5U4G	.45	6BG6G	1.25	6SK7GT	.41	12SF5	.50	75	.41
				6SL7GT	.48	12SG7GT	.52	76	.44
				6SN7GT	.52	12SJ7	.44	77	.57
				6SQ7GT	.37	12SX7GT	.48	78	.47
				6SR7GT	.45	12SL7GT	.47	80	.68
				6S7	.42	12SN7GT	.52	83	.35
				6TR	.56	12SQ7	.44	85	.59
				6U4	.60	12SR7	.49	117Z3	.37
				6U5	.44	14J7	.30	117L7	.99
				6U6	.63	14W7	.30	807	.99



TERMS: A 25% deposit must accompany all orders—balance C.O.D. All shipments F.O.B. Irvington warehouse. Orders under \$10—\$1.00 handling charge. Subject to prior sale. Don't Delay . . . Order Today!

115 COIT ST.
Dept. RE 353
IRVINGTON II, N. J.

Check JSC for Complete 300-Ohm TV Lead-In Wire

... for best results!



22 gauge copper

40 mil
55 mil
70 mil
80 mil
100 mil

20 gauge copper

40 mil
55 mil
70 mil
80 mil
100 mil

4-Conductor Rotor Wire
Perforated 300 Ohm Open Wire

JSC has highest quality wire at lowest possible prices.

Lithographic spools of orange and blue individually packed 1000 feet to the metal spool.

See your nearest JSC distributor who proudly displays the Blue and Orange disc of quality.

RADIO-ELECTRONICS APRIL ISSUE
ON SALE MARCH 25.

customer complaints" tends to prove the same thing, he stated.

Further, according to Mr. Farr, some of the strongest proponents of licensing favor it because they believe it will raise rates and reduce the number of technicians in the industry, thereby providing licensed operators with more income. He also pointed out that in many cases licensing may be favored purely for financial reasons by "municipalities (which) are hard pressed for funds to bolster the local treasury. They think the service field will be the most lucrative." He further stressed the point that licensing cannot possibly cure all the so-called evils, as some who are turning to it as a "last resort" apparently believe.

Mr. Farr believes much could be done to reduce the already dwindling number of customer complaints if set manufacturers would emphasize to the consumer the amount of time and skill needed to repair TV sets, and asked for "an educational program by the producers and service contractors."

In a statement published a few days later, Frank Moch of NATESA dismissed the argument that technicians were seeking licensing for selfish reasons as "unqualified baloney." He held that dealers' demands for kickbacks on service work are responsible for many abuses, since they put a financial squeeze on the service operator and make it impossible to give the customer the service he is paying for. He also branded as "absolutely ridiculous" the charge that licensing would raise present service rates, and stated "There is no movement afoot to reduce the number of technicians. Everyone agrees that there are not enough technicians to handle present business volume."

Paul Forte, executive secretary of the Television Contractors Association, attacked the anti-licensing groups in a long letter in which he declared that manufacturers, far from educating the public as to the complexity of TV installation and servicing, are following in effect an opposite course. "The public is being told" he said, "that for a few pennies and the use of a screwdriver they will have no problems in receiving the new u.h.f. signals. The public is not being told of the special antennas, the precise positioning, the new and special equipment, and the extremely high degree of technical knowledge, together with the cost, which will be needed before u.h.f. reception becomes a fact." The practice of parts distributors of selling to non-professional TV repairers or tinkerers at wholesale prices was another of the factors which Mr. Forte considered important in the demand for licensing made by sections of the service industry.

Mr. Forte ended with the statement that he too was opposed to licensing, but considered it necessary to recognize the real reasons why such a demand was supported before attempting to solve the problem. He says, however: "In recognizing it, I find myself helpless, because the answer does not lie with me or my associates, but with the people who created this atmosphere.

WITH THE TECHNICIAN

They can defeat licensing—with deeds, not words."

ASK NEDA TO ACT

The Television Contractors Association, of Philadelphia, has asked the Pennsylvania chapter of the National Electronic Distributors Association to prevent retail buyers from obtaining components at wholesale prices.

President of TCA, Albert Haas, pointed out in a letter to the president of the Keystone Chapter of NEDA that legitimate television contractors are seriously hurt by the fact that students, employees of TV service organizations working after hours on their own, and others, are able to purchase parts at the same rate as the legitimate TV service company. These operators, working without overhead or normal business expenses, are able to cut prices to a point where legitimate service business is imperiled. He requested that the Keystone Chapter "adopt a resolution calling for a halt to this type of unorthodox selling procedure," advocating that some independent group classify all who may rightfully buy electronic equipment wholesale.

NATESA'S NEW OFFICERS

The officers of the National Alliance of Television and Electronic Service Associations are Frank J. Moch, president; Bertram Lewis, Eastern vice-president; Fred Colton, East-Central vice-president; Vincent Lutz, West-Central vice-president; Jack MacDowell, secretary-general; John Hemack, treasurer; Harold Rhodes, Eastern secretary; W. A. Rosenberg, West-Central secretary; and Gerald Ratner, legal counsel.

The officers were elected at the NATESA convention held in Chicago during December. A number of other important actions were performed by the convention, among which were a redistricting of the organization to take care of the increase in membership, setting up a committee to determine a new dues structure, and amending the by-laws to permit voting by mail on important issues which might arise in the periods between conferences.

Committees were also set up to design and put into force a plan for manpower training and qualification; to organize a speaker's bureau and training coordination plan; to select a recipient for the "Friends of Service Management" award; and to work out a NATESA "Seal of Acceptance" plan.

A plan was presented for the various affiliates to "visit" each other through the medium of tape recordings. Another plan—for consumer education through lectures before various fraternal, business, and service organizations—was also approved. It was proposed that the Internal Revenue Department, OPS, FTC, local zoning boards, and other government agencies be used to clean out frauds in the TV and radio service industry. A proposal for the establishment of chapters in cities and areas not yet in NATESA and in those areas still without TV was also taken up. END

MARCH, 1953

THE SIMPSON MODEL 260 VOLT-OHM-MILLIAMMETER

*outsells all others combined
because...*


- A** covers all ranges necessary for Radio and TV set testing
- B** includes the Simpson 50 Microampere Meter Movement known the world over for its ruggedness
- C** no bulky harness wiring, thus eliminating all intercircuit leakage at this high sensitivity
- D** molded recesses for resistors, batteries, etc.
- E** easy battery replacement
- all components — including case and panels — are specially designed and completely tooled for maximum utility . . . not merely assembled from stock parts

ranges 20,000 Ohms per Volt DC,
1,000 Ohms per Volt AC
Volts, AC and DC: 2.5, 10, 50,
250, 1000, 5000
Output: 2.5, 10, 50, 250, 1000
Milliamperes, DC: 10, 100, 500
Microamperes, DC: 100
Amperes, DC: 10
Decibels (5 ranges):
-12 to +55 DB
Ohms: 0-2000 (12 ohms
center), 0-200,000 (1200 ohms
center), 0-20 megohms
(120,000 ohms center)

SIMPSON ELECTRIC COMPANY

5200 W. Kinzie St., Chicago 44 Phone COLUMBUS 1-1221

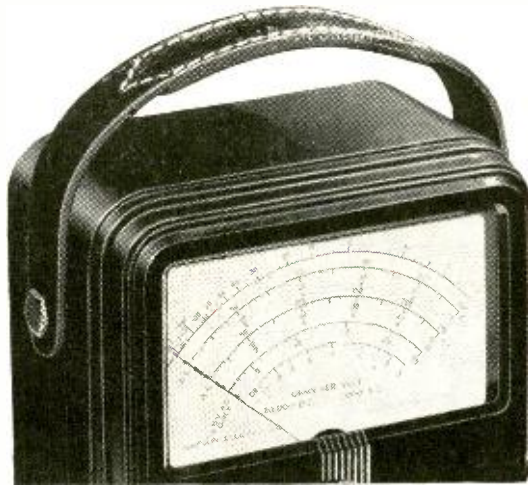In Canada: Bach-Simpson, Ltd., London, Ont.



BURTON BROWNE ADVERTISING

prices

Model 260 \$38.95;
With Roll Top \$46.90.
Complete with test
leads and operator's
manual. 25,000 volt
DC Probe for use with
Model 260, \$9.95.

Scala OSCILLOGRAPH PROBES

Complete with Coaxial Lead and Instruction Book

**A PRECISION INSTRUMENT THAT
WILL MAKE EVERY TV SERVICE
JOB EASIER, FASTER AND MORE PROFITABLE**

FULLY ADJUSTABLE TO OPERATE WITH ANY SCOPE MADE

See your local distributor or write factory and specify model number

BZ-1 Signal Tracing Probe

BZ-2 Low Capacity Probe

BZ-3 100:1 Voltage Divider Probe

SCALA RADIO CO. 2814-19th St., San Francisco 10, California



**Creating \$ALES for YOU
with Consumer
Advertising!**

with **Television Spots**
Throughout
the country

with **TV Consumer
Magazine Ads**
Throughout the country

\$9.95
LIST
PRICE

*U. S. Patent No. 2,495,579
Canadian patents 1951

Available at leading jobbers!

**The Genuine
HI-LO TV
Spiral-Tenna
Model 101 (indoor)**

Hi-Lo TV ANTENNA CORP.
3540 N. Ravenswood • Chicago 13, Illinois

Flying Saucers?




Frankly we don't know if they're fact or fiction... but if they are fact it wouldn't surprise us a bit to learn that some extra-terrestrial manufacturer has incorporated SELETRON Selenium Rectifiers and R. R. Co. Germanium Diodes into the design. That's because—as pioneers in the field of electronic development—we've had our hand in some of the most difficult projects and met some of the stiffest requirements ever cooked up! Making drawing board dreams come true are daily chores at Radio Receptor Co.!

GERMANIUM DIODES

Radio Receptor's new Germanium Diodes feature polarity at a glance combined with simplicity of construction and sound design principles. The tapered shape speeds assembly because operators can see at a glance the correct direction of assembly. Users are enthusiastic over the quality of the product which is currently being used in walkie-talkies, computers, TV sets, tuners and other electronic applications.



Germanium Diode (shown enlarged)

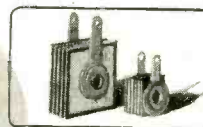

Our Germanium Diodes and Seletron Selenium Rectifiers may hold the answer to many of your problems. Radio Receptor Engineers will be glad to study your requirements and submit their recommendations on both of these products.

Germanium Transistors available in limited quantities.



SELETRON SELENIUM RECTIFIERS


Seletron Selenium Rectifiers, in both miniature and industrial types, are in constant demand by an increasingly large number of engineers throughout the world because they are completely dependable under the most grueling conditions. Years of experience have given Radio Receptor Co. a deep insight into the idiosyncrasies of rectification.

Seletron and Germanium Division

RADIO RECEPTOR COMPANY, Inc.

Since 1922 in Radio and Electronics
SALES DEPT: 251 West 130th Street, New York 11, N. Y. • FACTORY: 84 North 9th Street, Brooklyn 11, N. Y.

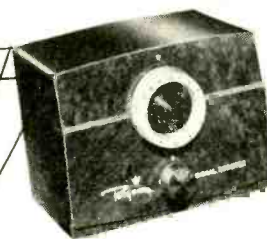GIVE BLOOD NOW • Call your Red Cross today • National Blood Program



Regency

LARGEST SELLING BOOSTER

at any price!

64-5618

RADIO-ELECTRONICS


burton brown advertising

TV LINE SPLITTERS

Blonder-Tongue Laboratories, Inc., 526 North Ave., E. Westfield, N. J., presents a new group of Line Splitters for dividing any TV transmission line into four branch lines. These units are available in the following models:

- Model LS4-1—Divides one 75-ohm line into four 75-ohm lines.
- LS4-2—Divides one 300-ohm line into four 75-ohm lines.
- LS4-3—Divides one 75-ohm line into four 300-ohm lines.
- LS4-4—Divides one 300-ohm line into four 300-ohm lines.

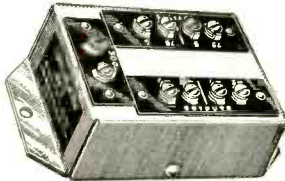The line splitters were designed to provide branch lines to distribution amplifiers in master TV systems. Requiring no power, they can be installed at remote locations. Precise impedance match and flat response over all v.h.f. channels are featured in these low-cost units.




They may also be used as an inexpensive means to provide reception for two to four TV sets, from one antenna. Interaction between TV sets, when present, can be eliminated by inserting attenuation pads between the line splitter and each TV set.

Each type is shipped with two resistors which provide proper termination of unused outlets.

UHF ANTENNAS

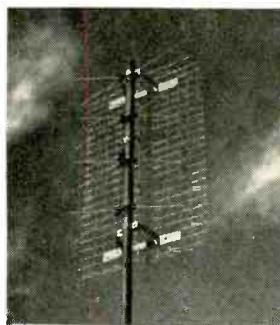Technical Appliance Corp., Sherburne, N. Y., has designed a new line of u.h.f. antennas. Parabolic-reflector types, Yagi, modified X (bow-tie), and V type antennas are included. With the exception of the modified X design, all




are of the sharp directivity type. The modified X will be marketed for areas where reception from channels in opposite directions is required. Tuning of all antennas is such that all operating u.h.f. channels will be within the bandwidth of the antenna.

FM-AM TUNER

Pilot Radio Corp., 37-06 36th St., Long Island City, N. Y., has announced an FM-AM radio tuner, for use as the central control head of a high-fidelity music system. The *Pilotuner* model AF-

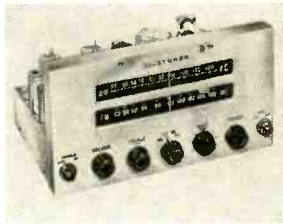821 is a 9-tube unit incorporating a two-stage preamplifier with adjustable equalization for various makes of reluctance phonograph cartridges, sepa-



rate input connections for phono and TV operation, extended range bass and treble controls, a temperature-compensated oscillator for drift-free FM reception, automatic frequency control, full shielding against radiation, built-in antennas, and high sensitivity on both the FM and AM bands. Over-all dimensions are 14 1/4 x 7 1/4 x 8 1/2 inches.

HIGH-VOLTAGE PROBE

Kapner Hardware, Inc., 2248 Second Ave., New York 29, N. Y., has introduced its *Defecto* probe which indicates the presence or absence of high voltage, and checks proper operation of the high-voltage supply.

The probe has a built-in lamp which lights up if high voltage is present.



HIGH-VOLTAGE PROBE

General Cement Mfg. Co., 919 Taylor Ave., Rockford, Ill., has announced a tester for checking high-voltage TV circuits. The tool, about 7 inches in length, glows when in contact with high voltage.


The probe has a metal pin which is put in contact with the component to be checked when testing rectifier tubes,



output and transmitter tubes, and high-voltage transformers. For testing high-voltage filter resistors, the tester is moved along the body of the resistor. If the resistor is open or cracked the tester glows at the trouble point.

U.H.F. ANTENNA

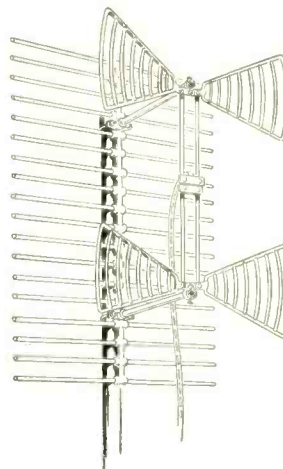Tel-a-Ray Enterprises, Inc., Henderson, Ky., has announced an all-channel u.h.f. antenna, the *Universal*. It is a fan-type model constructed from Dural and cast aluminum with noncorrosive hardware, giving a flat frequency response over the whole u.h.f. band. Single, double, and four-bay arrays are available.



BUILD 15 RADIOS

ONLY

AT HOME \$19.95

With the New Improved 1953 Progressive Radio "EDU-KIT"

**NOW INCLUDES
SIGNAL TRACER
and
CODE OSCILLATOR**



- FREE TOOLS WITH KIT
- ABSOLUTELY NO KNOWLEDGE OF RADIO NECESSARY
- NO ADDITIONAL PARTS NEEDED
- EXCELLENT BACKGROUND FOR TELEVISION
- 10 DAY MONEY-BACK GUARANTEE

WHAT THE PROGRESSIVE RADIO "EDU-KIT" OFFERS YOU

The Progressive Radio "Edu-Kit" offers you a home study course at a rock bottom price. Our Kit is designed to train Radio Technicians, with the basic facts of Radio Theory and Construction Practice expressed simply and clearly. You will gain a knowledge of basic Radio Principles involved in Radio Reception, Radio Transmission and Audio Amplification.

You will learn how to identify Radio Symbols and Diagrams; how to build radios, using regular radio circuit schematics; how to mount various radio parts; how to wire and solder in a professional manner. You will learn how to operate Receivers, Transmitters, and Audio Amplifiers. You will learn how to service and trouble-shoot radios. You will learn code. You will receive training for F.C.C. license.

In brief, you will receive a basic education in Radio exactly like the kind you would expect to receive in a Radio Course costing several hundreds of dollars.

THE KIT FOR EVERYONE

The Progressive Radio "Edu-Kit" was specifically prepared for any person who has a desire to learn Radio. The Kit has been used successfully by young and old in all parts of the world. It is not necessary that you have even the slightest background in science or radio.

The Progressive Radio "Edu-Kit" is used by many Radio Schools and Clubs in this country and abroad. It is used by the Veterans Administration for Vocational Guidance and Training.

The Progressive Radio "Edu-Kit" requires no instructor. All instructions are included. All parts are individually boxed, and identified by name, photograph and diagram. Every step involved in building these sets is carefully explained. You cannot make a mistake.

PROGRESSIVE TEACHING METHOD

The Progressive Radio "Edu-Kit" comes complete with instructions. These instructions are arranged in a clear, simple and progressive manner. The theory of Radio Transmission, Radio Reception, Audio Amplification and servicing by Signal Tracing is clearly explained. Every part is identified by photograph and diagram. You will learn the function and theory of every part used.

The Progressive Radio "Edu-Kit" uses the principle of "Learn by Doing". Therefore you will be building radios to illustrate the principles which you learn. These radios are designed in a modern manner, according to the best principles of present-day educational practice. You begin by building a simple radio. The next set that you build is slightly more advanced. Gradually, in a progressive manner, you will find yourself constructing still more advanced radio sets, and doing work like a professional Radio Technician. Altogether you will build fifteen radios, including Receivers, Transmitters, Amplifiers, Code Oscillator and Signal Tracer.

The Progressive Radio "EDU-KIT" Is Complete

You will receive every part necessary to build 15 different radio sets. Our kits contain tubes, tube sockets, chassis, variable condensers, electrolytic condensers, mica condensers, paper condensers, resistors, line cords, selenium rectifiers, tie strips, coils, hardware, tubing, hook-up wire, solder, etc.

Every part that you need is included. These parts are individually packaged, so that you can easily identify every item. Tools are included, as well as an Electrical and Radio Tester. Complete, easy-to-follow instructions are provided.

In addition, the "Edu-Kit" now contains lessons for servicing with the Progressive Signal Tracer, F.C.C. instructions, quizzes. The "Edu-Kit" is a complete radio course, down to the smallest detail.

TROUBLE-SHOOTING LESSONS

Trouble-shooting and servicing are included. You will be taught to recognize and repair troubles. You will build and learn to operate a professional Signal Tracer. You receive an Electrical and Radio Tester, and learn to use it for radio repairs. While you are learning in this practical way, you will be able to do many a repair job for your neighbors and friends, and charge fees which will far exceed the cost of the "Edu-Kit". Here is your opportunity to learn radio quickly and easily, and have others pay for it. Our Consultation Service will help you with any technical problems which you may have.

FREE EXTRAS IN 1953

- ELECTRICAL AND RADIO TESTER
- ELECTRIC SOLDERING IRON
- BOOK ON TELEVISION
- RADIO TROUBLE-SHOOTING GUIDE
- MEMBERSHIP IN RADIO-TELEVISION CLUB
- CONSULTATION SERVICE
- QUIZZES
- TRAINING FOR F.C.C. LICENSE

The Progressive Radio "Edu-Kit" is sold with a 10-day money-back guarantee. Order your Progressive Radio "EDU-KIT" Today, or send for further information.

We pay shipping charges all over the world, if you send check or money order with your order. On COD orders, you pay cost of delivery.

PROGRESSIVE ELECTRONICS CO.

497 UNION AVE., Dept. RE-69, Brooklyn 11, N. Y.

NEW DEVICES

HI-FI PACKAGE

Meissner Manufacturing Division, Maquire Industries, Inc., Mount Carmel, Illinois, has announced a matched high-fidelity radio-FM-phonograph system consisting of changer, tuner, amplifier, and coaxial speaker.

Changer pickup is the G-E triple play variable reluctance cartridge. Frequency response of tuner is ± 2 db throughout 50 to 15,000 c.p.s. range and it has a new type miniature tube lineup. The amplifier hum level is -70 db down, and its frequency response is flat ± 1 db throughout 20 to 20,000 c.p.s. Undistorted power output is 10 watts. Amplifier has built-in preamp.



TUNER

AMPLIFIER

CHANGER

Speaker uses two coaxially mounted cones driven from one voice coil. Frequency response is practically flat throughout range of 30 to 13,000 c.p.s. Built-in mechanical crossover at 4,500 c.p.s. permits each cone to work through its own tone range.

PAPER CAPACITORS

Cornell-Dubilier Electric Corp., Plainfield, N. J., now has 12 types of miniaturized, tubular metal-cased paper capacitors in its Demicon series.

These capacitors are hermetically sealed in metal cases, with glass-to-metal seal terminals, and are available in seven mounting and container styles. Impregnants, tolerances, and internal constructions are provided to




meet the most popular applications in modern engineering. All these capacitors comply with applicable parts specifications of JAN-C-25 and MIL-C-25A.

VOLTAGE BOOSTER

Crest Laboratories, Inc., 84-11 Rockaway Beach Blvd., Rockaway Beach, N. Y., has introduced its LVB-117 line-voltage booster. The unit is engineered to restore peak performance for TV sets or electrical appliances requiring 117 volts.

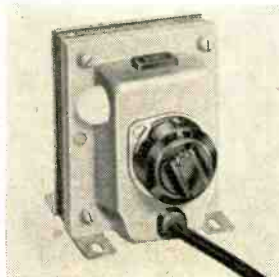
The LVB-117 has an overload cutout to protect against unsafe line voltage increases and has a multitap selector switch for exact selection and a visual indicator for precise determination of required boost.



ALL-CHANNEL ARRAY

Channel Master Corp., Ellenville, N. Y., has developed a stacked ultra-fan v.h.f.-u.h.f. array, model 4132.

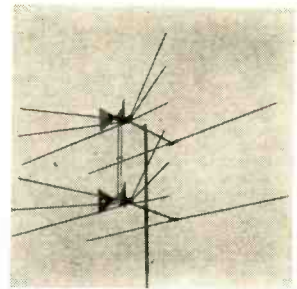
Two interaction filters separate the v.h.f. and u.h.f. bands, permitting the antennas to be used with one transmission line. Free space terminals prevent accumulation of dirt and moisture.



Based on a tuned reference dipole, its gain averages 6.5 db on low-band v.h.f., 10 db on high-band v.h.f., and a uniform 9.5 db on u.h.f. On low-band v.h.f. it is a conical antenna with parasitic reflector. On high-band v.h.f. it is a large-diameter V antenna. On u.h.f. it is a triangular dipole with the v.h.f. elements acting as a sheet reflector.

U.H.F. ANTENNA

Telrex, Inc., Asbury Park, N. J., is producing a new broad-band, stacked dipole antenna, the Conical-V-Beam. Completely factory-assembled, the array covers the full u.h.f. range at high signal-to-noise ratio.

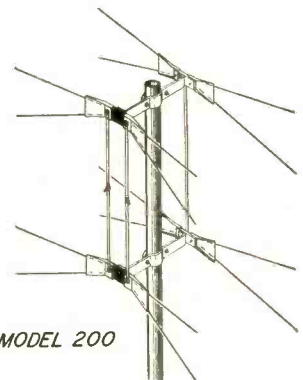

MODEL 200

SENSITIVITY TESTER


Service Instruments Co., 422 S. Dearborn St., Chicago 5, Ill., has announced a sensitivity tester to measure TV receiver sensitivity in microvolts.

The Sens/Meter microvolt scale is divided into very sensitive, medium sensitivity, and insensitive, and determines whether a receiver will operate in a weak-signal area.




LOUDNESS CONTROL

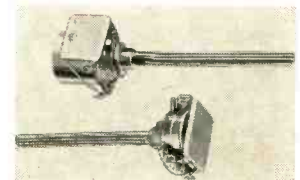Centralab, Division of Globe Union, 900 E. Keefe Ave., Milwaukee 1, Wis.,



RADIO-ELECTRONICS

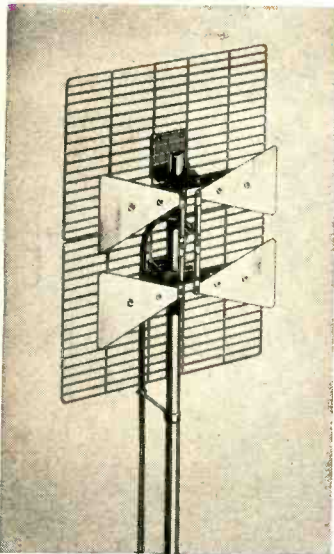

Two Amphenol 114-053 BO-TY Antennas stacked for greater gain, with 114-560 Reflectors.


AMPHENOL

UHF television antennas



The Amphenol 114-053 BO-TY Antenna carries the high standards of Amphenol quality into the field of UHF television. It is designed to give the maximum signal strength possible along with broadband reception.

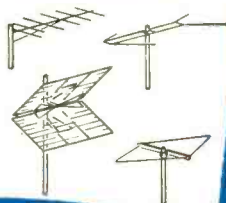In addition, Amphenol has available a complete list of accessories to adapt the BO-TY to any specific reception problem. These accessories include the 114-558 Stacking Rods for use when stacked array is desired to provide extra gain and the 114-560 Reflector which changes the bi-directional reception pattern of the BO-TY into a narrower, uni-directional pattern.



The UHF antennas previewed for you at the right will shortly be added to the BO-TY as available UHF antennas. They are in final development stages and will soon be in full production. They are designed to meet the specific reception problems that may be peculiar to any locality.

AMPHENOL

tubular twin-lead

U.S. Patent No. 2543696



Amphenol's patented 3-271 Tubular Twin-Lead is unequalled as an economic, low-loss lead-in for UHF television. As the illustrations at the left clearly demonstrate, the concentrated field of energy is largely contained and protected by the tubular construction. Rain, snow, dirt or salt deposits on the lead-in do not materially affect the impedance or electrical efficiency of Tubular Twin-Lead. Because of the high signal losses common to UHF television and because flat twin-lead does not afford this protection, flat lead-in is not suitable for UHF installations.

AMERICAN PHENOLIC CORPORATION
CHICAGO 50, ILLINOIS

NEW DEVICES


has developed a new compensated loudness control. The unit is a combination dual-tapped control and printed electronic circuit plate combining the compensating network. Since all components in the network are in shunt, there is no insertion loss, and no additional amplification is required.

Designed as a replacement for standard controls in all audio equipment, the unit compensates for the Fletcher-Munson hearing characteristic curves. It is available in 1/2- and 1-meg. values in both switch and non-switch types. Units are assembled and ready for installation.

NEW METER

Jerrold Electronics Corp., 26th and Dickinson Sts., Philadelphia 46, Pa., has developed a field strength meter, model 704, reading carriers in microvolts. The meter is accurate to plus or minus 0.8 db and has a continuous tuning range from 50-220 mc.

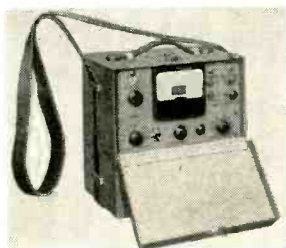
The model 704 separates and measures video, audio, and adjacent channel carriers, and locates r.f. interference.



WIRELESS INTERCOM

David Bogen Co., 29 Ninth Ave., New York 14, N. Y., has announced a new wireless communication system for home, office, factory, or institutional use.

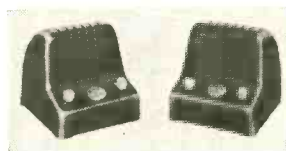
Designated model *Twin*, the unit can be used with two or more stations, with all conversation heard by all stations in the system. Each station contains a transmitter and receiver operating at 175 kc. Stations are placed in service by plugging them into a 117-volt a.c. or d.c. outlet.



DEFLECTION YOKES

Haldorson Transformer Co., 4500 N. Ravenswood Ave., Chicago 40, Ill., presents new 6,000-volt test deflection yokes DF603 and DF604, extra-heavily insulated for direct-drive TV service.

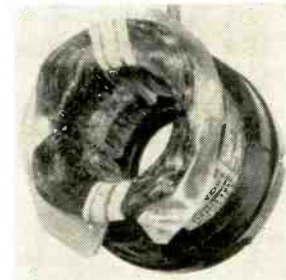Both yokes have 30-mh horizontal inductance, but to cover all direct-drive applications the vertical inductance of DF603 is 3.5 mh, while DF604 is 50 mh. They are supplied with 20-inch color-coded leads and networks.



"SUBURBAN" ANTENNA


LaPointe-Plascomold Corp., Rockville, Conn., has now in manufacture a new antenna, the *Ultra Q-Tee Suburban*. It is exactly the same as the present 2-83 Ultra except that the u.h.f. V portion of the antenna is replaced by a high-gain, broad-band, 8-element u.h.f. Yagi.

MARCH, 1953

The new model UQT-S was developed for critical areas and also fringe areas which will exist while many u.h.f. stations are operating temporarily on low power. UQT-S requires only a single transmission line and includes eight printed-circuit channel separators.

PULSE TRANSFORMER

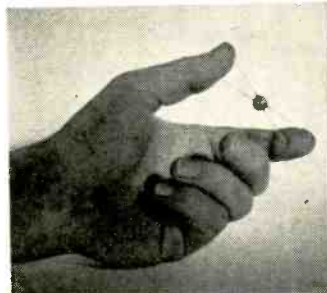PCA Electronics, Inc., 6368 De Longpre Ave., Hollywood 28, Calif., has developed a new pulse transformer, the MPT 101-0.1, which is the smallest pulse transformer now commercially available.



The unit weighs less than .03 ounce and meets MIL-T27 test specifications, including Table 1A humidity resistance tests. It can operate indefinitely at temperatures from -70° to +125° C., and will operate normally for a short time at +150° C.


It is resin-impregnated and imbedded and is hermetically sealed with transformer leads able to withstand a 5-pound pull. Although the MPT 101-0.1 is designed for pulse forming, it can also be used for pulse coupling.

TRANSFORMER CANS

Triad Transformer Mfg. Co., 4055 Redwood Ave., Venice, Calif., has introduced a line of deep-drawn transformer cans. They are seamless, drawn from cold-rolled steel. They meet the dimensional specifications of MIL-T-27. The lids are internal and require no stops. Cans are obtainable only for military contracts.

MOBILE MICROPHONE

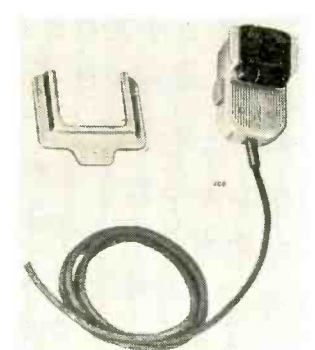
Electro-Voice, Inc., Buchanan, Mich., has designed a hand-held, differential type noise cancelling, high output, single-button carbon microphone. The model 208 has a flat 100-4,000 cycle frequency response to sounds of close origin, and an output of -50db. It measures 2/4 x 1 1/2 x 1 1/8-inches and weighs 3 ounces. Press-to-talk switch actuates button and relay simultaneously.



DOUBLE-O ANTENNA



Rytel Electronic Manufacturing Co. of 9820 Irwin Ave., Inglewood, Calif., announces a new u.h.f. antenna, the *Double-O*. Its circular construction makes for greater directivity in the horizontal plane and a 1-db gain over single dipole, together with low pick-up response in the vertical direction. With the two circle antennas fed 90 degrees out of phase an additional gain of 3.8 db is obtained. END

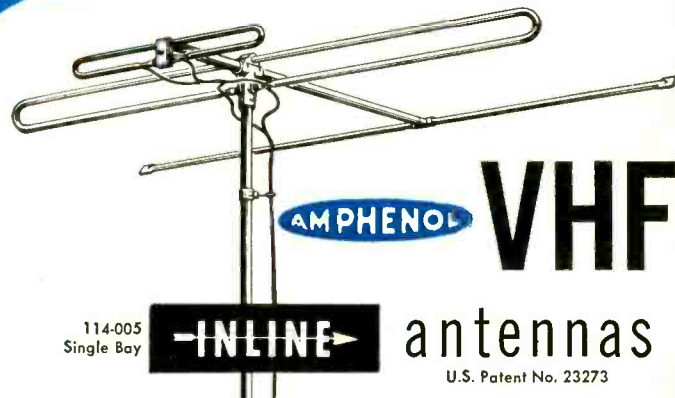All specifications given on these pages are from manufacturers' data.



Over four years in the tough competition of VHF television, subject to the critical eye of dealer, installer and set owner and still proclaimed to be the best all-channel VHF antenna—the Amphénol Inline Antenna.

The Inline Antenna is the net result of the coordinated efforts of designers and engineers who have won industry-wide acclaim for their research and construction of radar antennas and civilian and military antenna systems of all kinds. It is designed to give the best possible reception over the entire VHF spectrum. That it has succeeded is borne out by the thousands of testimonials and by the reputation it has established by its performance in "trouble areas."

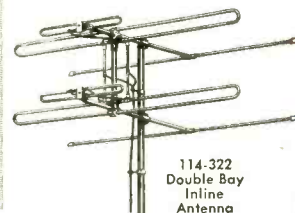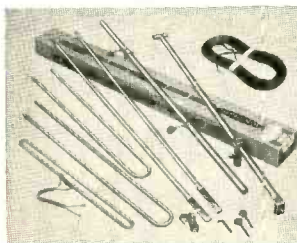

114-322 Double Bay Inline Antenna

Both the 114-005 single bay and the 114-322 double bay are packaged in Quick-Up Assemblies. Each antenna is shipped as a complete antenna system including mast, twin-lead, insulators, guying ring and mounting bracket. This makes the Inline Antenna the easiest to stock as well as the easiest to install.



114-040 Installers Economy Inline Antenna



Amphénol's 14-056 300-ohm flat twin-lead is the best in quality available anywhere. The seven stranded copper wire conductor is extruded in brown pigmented polyethylene. This pigmented polyethylene remains flexible at -70° C. and has a long life even under extreme exposure to sun, salt-air, chemical fumes or gas polluted air.

For Better TV Picture Quality, from Top to Bottom, make your antenna installation Amphénol.

AMERICAN PHENOLIC CORPORATION
CHICAGO 50, ILLINOIS

PERMO



PHONO



NEEDLES



SEE YOUR JOBBER
OR WRITE FOR
CATALOG

PERMO, INC. 


6415 Ravenswood,
Chicago 26, Illinois

AUTOMATIC RADIO POLL

Serge A. Scherbatsky, Tulsa, Okla.
Patent No. 2,618,743

(Assigned to A. C. Nielsen Co., Chicago, Ill.)

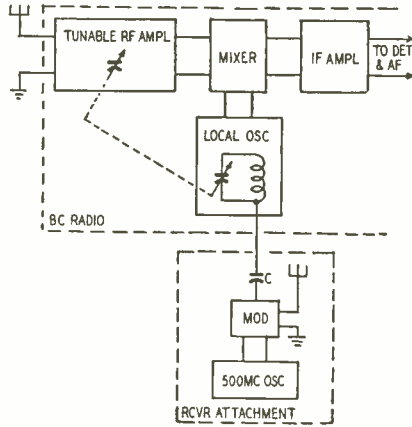Radio stations, advertising agencies, and sponsors try to put on the type of program that meets wide public approval. Surveys, polls, and interviews are undertaken from time to time to determine what people like. They are expensive and not altogether satisfactory. People don't like to be bothered, and may not always know the correct answers. Here is a new method for polling radio listening habits.



A special attachment is installed near or within the radio in a representative number of homes chosen on the basis of economic status, family size, education, and other factors. The attachment includes a 500-mc transmitter and an r.f. modulator. The latter is coupled to the radio local oscillator through a small capacitor (C). The receiver's oscillator modulates the 500-mc transmitter. (See the figure.)


In any superheterodyne, the local oscillator and signal frequencies differ by a constant i.f. Thus, by measuring the modulation frequency on the 500-mc carrier, we can determine the broadcast channel to which the radio is tuned.

At a convenient central location, a 500-mc receiver is set up to intercept the u.h.f. signals. These are demodulated and combined. The various r.f. channels are scanned by a sweep circuit and the amplitude of each channel is measured. If desired, a moving pen and chart is used to provide a continuous record of radio listening with respect to time.

"PROPELLER" TV ANTENNA

Patent No. 2,610,296

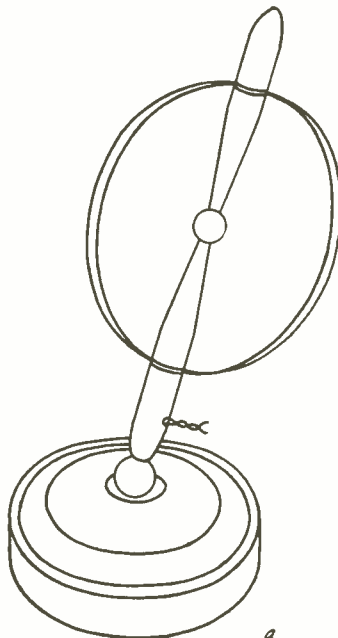John Drysdale Reid, Cincinnati, Ohio.
(Assigned to Avco Manufacturing Corp.)



Multiply your sales
with **AIM**

(AUTOMATIC
IMPEDANCE
MATCH)



No More "GHOSTS"

AIM eliminates all ghosts due to multi-path reflections.



No More "WEAK" Pictures

AIM increases db gain up to 80% signal strength increase. (Extremely high signal-to-noise ratio!)



No More PICTURE Flutter

AIM balances antenna system! Stops standing waves, line surges, distortions. 13 matching stubs in one!



AIM hits the PERFECT Vision Bullseye!

Easy, simple installation at receiver. Aim is not just a wave trap or booster, NOT a twin lead stub. A-I-M automatic impedance match automatically matches antenna lead-in with receiver impedance for all frequencies, for VHF and UHF.

ACT NOW! Handy counter display kit.
One sale means 20 more.
Write today!



RYTEL ELECTRONICS MFG. CO.
9820 Irwin Avenue • Inglewood, California
RADIO-ELECTRONICS

NEW PATENTS

Fig. a looks like a model propeller, but it is actually an efficient indoor TV and FM antenna. Signals are picked up by a split loop supported by a "propeller" of polystyrene or other plastic. The loop is only about 0.1 wavelength in diameter, but sensitivity comparable to a half-wave dipole is obtained by tuning it to each channel desired. Because of its small size, the loop may be oriented and positioned for minimum ghosts, interference, and body capacitance. It can be used for u.h.f. as well as v.h.f.

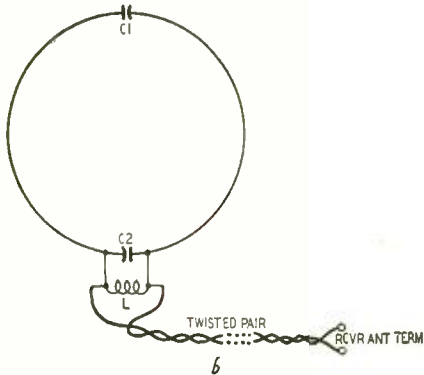


Fig. b shows the circuit. The loop, C1, C2 and L form a bandpass filter for the desired channel. Here are typical values for a 5-inch diameter loop:

C1	C2	Frequency
10 μmf	5 μmf	108 mc
5 μmf	75 μmf	69 mc

The loop is coupled to the receiver antenna terminals through twisted leads to reduce electrostatic pickup. Besides supporting the loop, the propeller improves the appearance of the device. Cups at the top and bottom cover the coil and the capacitors and keep them out of sight.


GAS TUBE AMPLIFIER

Patent No. 2,603,766


Jerome Kurshan, Princeton, N. J.

(Assigned to Radio Corp. of America)

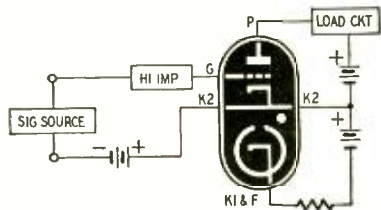Conventional gas tubes are never used to amplify, because there is no way of controlling conduction. Below the firing point, no tube current



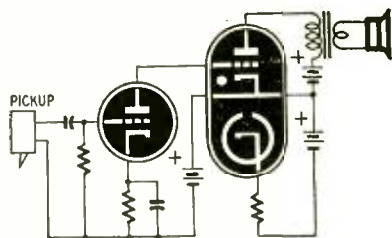
flows. When the gas is ionized the grid loses control and there is considerable plate current flow. A new type of tube has been designed to solve



this problem. The new tube has auxiliary elements which provide a stream of charged particles. The main elements function just like those of a vacuum tube triode. This tube can handle large amounts of power with little distortion.

The circuit of the tube is the upper figure. K1, K2 are the auxiliary and main cathodes, respectively. When the potential between them is high enough, the gas ionizes and separates into negative electrons and positive ions. This mixture is called a plasma. Focusing electrode F focuses the plasma into a narrow beam. The electrons are attracted to the positive plate P. Ions are drawn towards the negative grid G. A high-impedance element in the grid circuit minimizes distortion.

MARCH, 1953

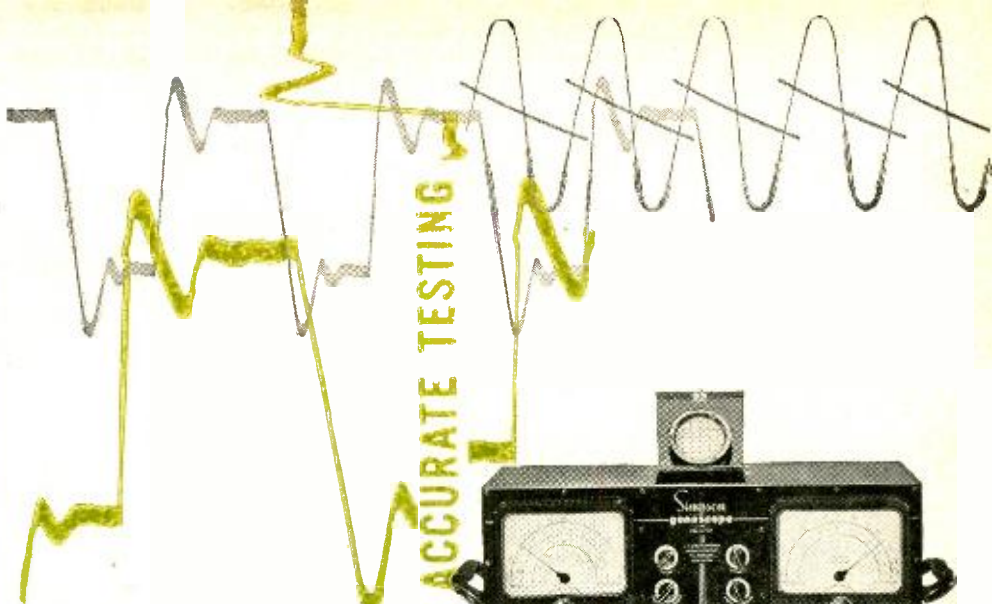

SIMPSON MODEL 480 GENESCOPE FOR ACCURATE TESTING

approved by
service managers of:

admiral


zenith

motorola

emerson


hoffman

hallicrafters

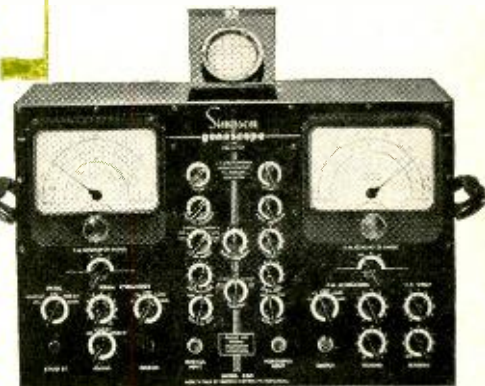

- All the necessary signal sources for alignment of FM and TV receivers • Includes the Simpson High Sensitivity Oscilloscope and high frequency crystal probe for signal tracing • Independent, continuously variable attenuators and step attenuators for both AM and FM units offer complete control of output at all times • 0-15 megacycle sweep is provided by a noiseless specially designed sweep motor based on D'Arsonval meter movement principles • The exclusive Simpson output cable (illustrated) includes a variable termination network, quickly adapted to provide open, 75 or 300 ohm terminations — the addition of a pad provides attenuation and isolation. Use of appropriate resistors across certain terminals will provide any other termination required. A .002 MFD blocking condenser can be added on any termination for use on circuits containing a DC component • The FM generator output voltage is constant within .2 DB per MC of sweep.

dealer's net \$395.00

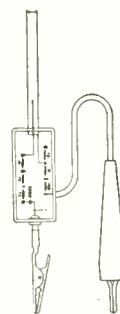

SIMPSON ELECTRIC COMPANY


5200 W. Kinzie St., Chicago 44, Illinois • Phone: COlumbus 1-1221 • In Canada: Bach-Simpson, Ltd., London, Ont.

BURTON BROWNE ADVERTISING

TRAIN At Home FOR OPPORTUNITIES IN

UHF-TV

SERVICING



Get in on the ground floor of this fast-growing field, with proven, practical T.C.I. training. Here is complete, non-mathematical training you take in your spare time, without leaving your present job! You learn TV set conversion, master antenna installation, the latest in UHF-TV, money-making short cuts and much more. You learn to trouble shoot, test and repair TV sets the only practical way by doing the work yourself!

LEARN BY DOING! You work on a large screen, modern TV receiver furnished with the course and yours to keep. As an optional feature, you get two weeks of field experience with one of Chicago's largest independent TV servicing organizations. *Age is no barrier.* Many T.C.I. students are over 40! Send for facts NOW!


VETERANS discharged since June 27, 1950 are eligible for G.I. benefits. Check coupon.

TELEVISION COMMUNICATIONS INSTITUTE
205 W. Wacker Dr., Dept. RE-15, Chicago 6, Ill.

MAIL NOW FOR FREE BOOKLET

TELEVISION COMMUNICATIONS INST. Dept. RE-15, 205 W. Wacker Dr., Chicago 6, Ill.

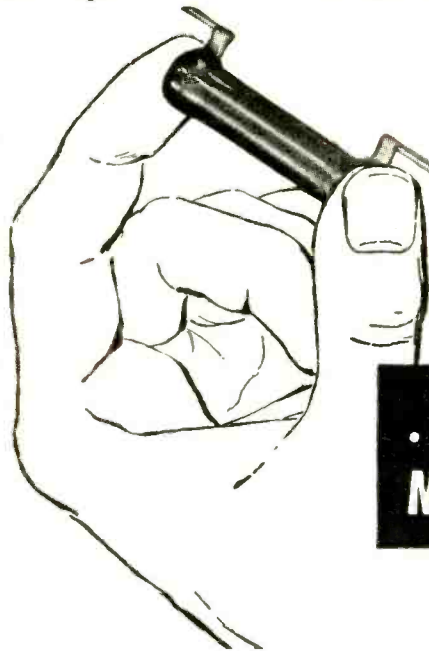Name.....
 Veterans Check Here
 Address.....
 City & Zone.....State.....
 BEGINNEES: Check for facts on Pre-TV Course.




OHMITE *resistors*

**... for that EXTRA
MARGIN OF SAFETY!**

Customers judge your service by the results they get. If a radio or TV repair job fails to stand up, they blame *you*, not the parts you used.

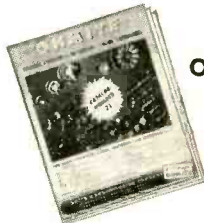Don't jeopardize your business reputation with "just-as-good" replacement parts. OHMITE resistors provide an extra margin of safety. You can depend on these quality resistors—wire-wound or composition—to give years of trouble-free service.




OHMITE MANUFACTURING COMPANY
4895 Flournoy Street, Chicago 44, Illinois

Send for stock catalog

*Be Right
with...*

OHMITE®

DEPENDABLE RESISTANCE UNITS

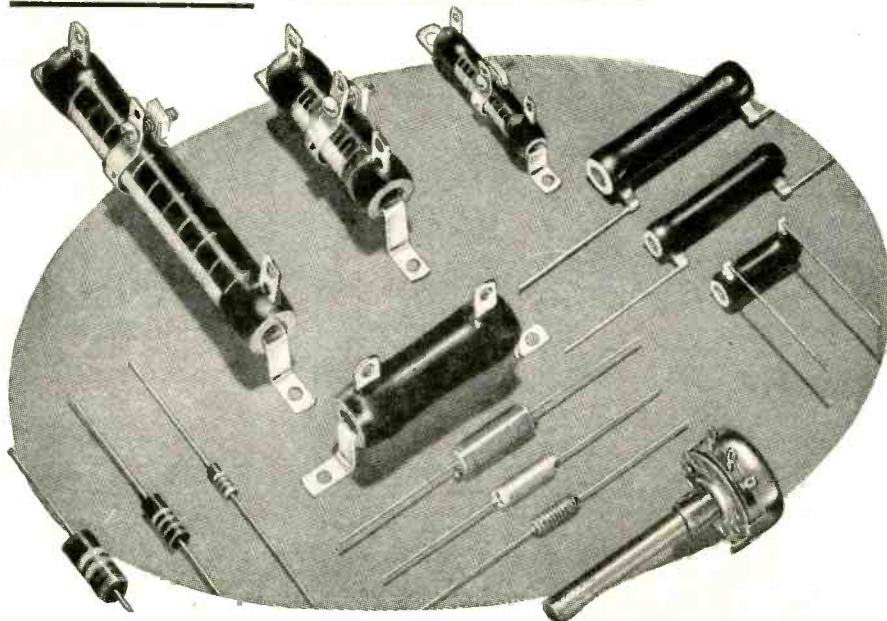

A phono amplifier schematic is also shown. Here a vacuum triode is used in the grid circuit of the gas tube. The triode amplifies the output of the photo pickup and provides the necessary high impedance in series with the grid of the gas tube.

SAWTOOTH GENERATOR


Patent No. 2,616,044

Kurt Schlesinger, New York, N. Y.
(assigned to Radio Corp. of America)

A sawtooth wave can be generated by differentiating a parabolic wave. This invention shows methods for forming the parabolic wave.

See the accompanying figure. An a.c. sine wave (which cannot be changed by differentiation) is applied to the full-wave rectifier through a transformer. The tube delivers the usual rectified sine-wave pulses shown. These are distorted by L and R1 to a rounded parabolic waveform. A differentiator made up of C and R2 converts the parabola to a sawtooth.

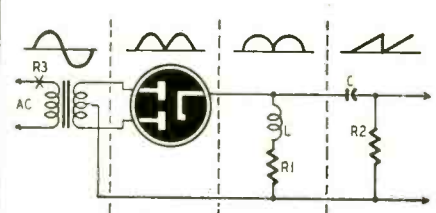In an alternate method, the parabolic wave may be formed by inserting a resistor (R3) in series with the input. When this is done, L and R1 may be eliminated.



U.H.F. CONVERTER FOR TV

Patent No. 2,616,037


Benjamin F. Wheeler and Howard R. Mathwich,
Haddonfield, N. J.

(assigned to Radio Corp. of America)

In this u.h.f converter, the incoming signal is mixed with a harmonic of the local oscillator. The oscillator tube may be a conventional type, operating with relatively high efficiency at less than half the frequency of the incoming signal.

The figure shows a cavity resonator Q tuned to the desired signal by a screw S. The signal frequency (F3) is coupled to the cavity through a loop. The local oscillator frequency (F1) is fed into the cavity at P. A 1N21B crystal distorts the oscillator current and generates a strong second harmonic 2F1. The difference between F3 and 2F1 is the i.f. (F2). The converter is followed by an i.f. stage.

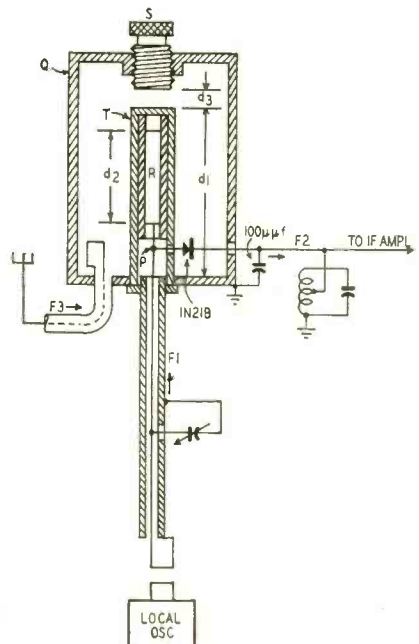The inner conductor T of the cavity is hollow. Within it is conducting rod R. A polystyrene tube separates R and T. Although R is much shorter than T, they can each be adjusted to an odd multiple of a quarter-wavelength at F3. This is be-



RADIO-ELECTRONICS

cause R and T are separated by polystyrene, which has 2.5 times the dielectric constant of air. Coax line R, T, is open as its far end, so the impedance at point P is very low with respect to F3. The incoming signal is shorted out by the low effective impedance at this point and is prevented

from entering the local oscillator circuit and affecting the oscillator frequency.

Here are typical dimensions and frequencies for the harmonic converter described above.

- d1 2.67 inches F1 416-442 mc
- d2 1.92 inches F2 88-76
- d3 .72-.18 inches F3 920-960

COMBINATION HEARING AID AND RADIO RECEIVER


Patent No. 2,618,707
Lemuel M. Temple, Scarsdale, N.Y.
(Assigned to Raytheon Mfg. Co., Newton, Mass.)

This circuit combines a radio and hearing-aid in a single unit. Thus a hard-of-hearing person may enjoy radio programs when he is not using the device as an ordinary hearing aid.

The set may use 6 miniature type tubes. Three of them may operate as r.f. amplifier, converter, and i.f. amplifier. One tube is the diode detector when the set is switched to RADIO. This tube becomes an amplifier when the switch is thrown to HA (hearing aid). The remaining tubes are the a.f. voltage amplifier and power output tubes, respectively.

The figure shows the audio section. S1, S2, S3, S4 is a ganged switch. The first two poles switch the control grid of V1 from microphone to the i.f. transformer. In the RADIO position, only the control grid and filament are in the circuit. Then the tube is a half-wave diode detector. When the switch is thrown to HA the tube is a pentode amplifier. V2 is the audio amplifier and V3 is the power tube.

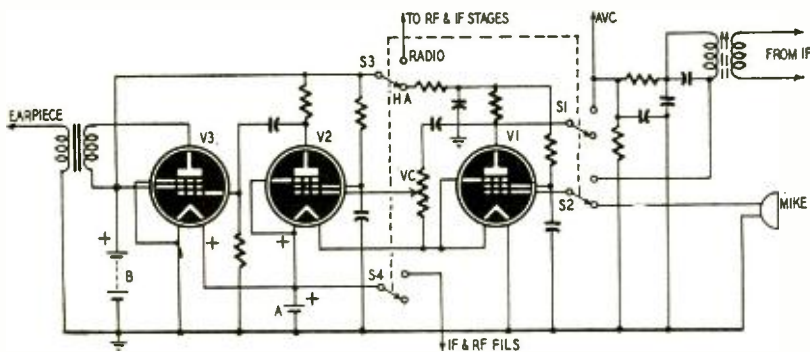A and B voltages are disconnected from the r.f. and i.f. stages when the set is in HA position. They are controlled by switch sections S4 and S3, respectively.



MAGNETOMETER

Patent No. 2,603,687
Lawrence J. Giacometto, Eatontown, N. J.
(Assigned to Radio Corp. of America)

This instrument measures the strength of a magnetic field by its effect on an electron stream. Electrons carry a magnetic charge and can be deflected from their normal paths by an external magnetic field. It can be used wherever space is limited, as in testing narrow air gaps. Readings are accurate and continuous. The circuit uses three tubes, one of which is a special magnetometer type shown schematically in the diagram below.

V1 is normally blocked by high negative grid bias from B1. When V1 conducts, its cathode current flows through meter M, which constitutes the entire tube load. During conduction, the voltage across the meter will nearly equal T, the peak-to-peak amplitude of the sawtooth plate potential.

V2 is an amplifier whose output is fed to the grid of V1.


V3 is the special magnetometer tube. It has a cathode K, plates P1 and P2, and a collector CO. P2 has two small apertures, one above K and the other above CO. V3 must be placed in the magnetic field to be measured. All other components may be located elsewhere, since the connecting leads to the magnetometer tube carry only d.c. supply voltages or low-frequency a.c.

Electrons from K pass through the first aperture and are attracted by P1, which is biased by the positive voltage T. If the tube is in a mag-

netic field, the electron stream will be deflected. A weak field produces only slight deflection, such as A. If the magnetic force is very strong there will be a greater deflection of the electrons—along a path like D. Possible intermediate paths produced by other magnetic field strengths are shown by the positions of the dashed lines at B and C.

If T is a positive-going sawtooth voltage, the electron beam will follow paths A to D progressively, as the sawtooth rises from zero to maximum. As electrons sweep along path B, they pass through the second aperture to CO and flow through R. This produces a negative pulse at the V2 grid which is amplified, inverted, and fed to V1. The positive grid pulse unblocks V1 momentarily, and M reads the instantaneous value of T. Capacitor C integrates the pulsating voltages appearing across the meter into a steady reading whose maximum value would be limited by the peak-to-peak amplitude of the sawtooth supply voltage T.

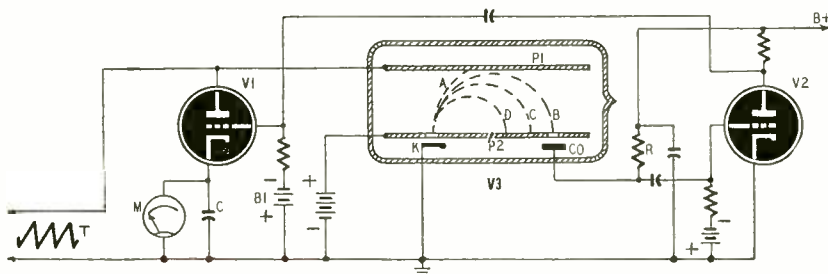The magnetic field strength can be determined from the reading of M. M reads a value closely equal to T, as we have already stated. For any particular value of T, only one definite magnetic-field intensity will guide the electrons along B. The strength of the magnetic field being explored can be computed from the meter readings or determined by comparison with known fields.



CONCORD TV CLINIC



NATIONAL TURRET BOOSTER
Finest turret tuner ever designed. Built-in Power supply. Brand New!
Lots of 6
3.....\$10.95 ea.
Singly ..\$11.95

10.00 ea.



GRAYBURNE TV-I.F. PLUG-IN BOOSTER

Just plug in this complete EXTRA I.F. stage. Improves pix and sound. No switches, no external connections, permanent installation. Shpg wt 2 lbs. Your Net Cost

\$5.60

Tele-Matic IGNITION FILTER

Compact, shielded, easy to install. Eliminates ignition "signal" interference from TV sets. Shpg wt 1 lb. Your Net Cost

\$1.18



TUBE BRIGHTENER

Extends pix tube life, improves emission by increasing fil. temperature. Just plug in. Shpg wt 1 lb. Your Net Cost ..

\$1.95

CLAROSTAT Automatic LINE VOLTAGE Regulator

For clear steady TV pictures in areas of fluctuating line voltage. Constant 115 V over variation between 90 and 140 volts. Shpg wt 6 oz. Net 300WattsMax,Net

\$1.18

\$1.47

ANTENNA SWITCH

\$2.91

Vee-DX. Handles 3 separate antenna leads with no capacity loss. Shpg wt 1 lb.



TELEVISION CLARIFIER

Two adjustable knobs tune out or reduce ghosts, tears, other interference. Easily installed in antenna line. 3 1/4" sq. x 1 3/4". Shpg wt 1 1/2 lbs. Your Net Cost

\$4.40

ALL CHANNEL "YAGI"

\$6.95 ea. Lots of 6 \$6.50 ea.

Optimum results on all channels. 6 aluminum elements. Fine for fringe areas. "Self-lock" design. 3/8" elements, 1" arm. Shpg wt 10 lbs.

10 CANDOHM RESISTORS

\$1.59 per kit

Shielded, insulated, wire-wound. 5 to 50 watt sizes, some tapped. In plastic utility box, shpg wt 2 lbs.

CONDENSER BARGAIN!



\$7.95 per kit

100 RESISTORS

Carefully selected popular assortment color coded. 1/2, 1, 2 watt sizes only. SPECIAL **98¢**

Surprise value, 75 asstd paper bypass, mica, electrolytic, all types, in utility plastic box, shpg wt 1 lb. Worth over \$20!

Send in your NAME AND ADDRESS and get on our mailing list for red hot "limited quantity" buys! Write today—Dept. C-3.

MINIMUM ORDER \$5.00
Address All Mail Orders to Dept. C-3

Concord Radio

55 Vesey Street. Phone
New York 7, N. Y. Dlgy 9-1132

The finest all-channel antenna ever made!

the **SKYLINE**

Amazing reception to 150 miles

For the same reasons installers spray antenna connections, we have eliminated them!

Our continuously formed antenna elements provide maximum signal gain—and maintain it indefinitely, because they eliminate 80% of the number of element connections common to this type.

Performance is assured. That's why the pre-assembled, foldable, quick-rig, all aluminum SKYLINE colinear antenna is fast replacing all other types in fringe areas.

SKYLINE MFG. CO., 1458C6 East 17th Street • Cleveland 14, Ohio

Patented

SKYLINE MFG. CO.
1458C6 East 17th Street, Cleveland 14, Ohio

FILL OUT AND MAIL

Send more information on the SKYLINE antenna to this address:

MY NAME _____

STREET AND NUMBER _____

CITY _____ STATE _____

Here's the name of my local Dealer or Serviceman Distributor

NAME _____

STREET AND NUMBER _____

CITY _____ STATE _____

METER SPECIALS

New Triplett Meters

Model	Description	Price
341	0-500 ma. RF. 3" rd.	\$6.50
232	0-10 V. AC. 2" rd.	6.50
327A	0-1 ma. DC. 0-100 good-bad scale. 3" sq.	6.50
327A	0-60 micro-amps. DC. 0-1000 ohm scale. 3" sq.	8.50
327A	0-400 micro-amps. DC. 3" sq. 0-25-50-100 V. AC scale.	8.50
221	0-8 ma. DC. 2" rd. 0-100 good-bad scale.	4.50
242T	0-1.2 ma. DC. 2" rd. 0-100 ma. scale.	4.50

Weston "S" Meter—Mod. 606. Type 234L. Tune for max. 2.5 ma. movement. Price \$3.50

Weston Volt-Ammeter—Mod. 606 Type 221-P. 0-60 Amps. DC and 0-30 volts DC. Normally reads current—depress switch for volts. Complete with shunt at \$9.50 each.

General Electric Model 53BAAL similar to above but less shunt—\$7.50 each.

Ampere Demand Indicator—Stewart Warner. Type 748A. 0-20 amps. High time lag. Indication follows for average reading as would affect supply transformers and motor windings. Separate pointer remains at maximum average reached during check period. Very special at \$3.95 each.

Write for free catalogue of Electronic, Aircraft, Hydraulic and other equipment.

Minimum order \$2.00

Prices F.O.B. Paterson, N. J.

Electro Devices
INCORPORATED
4 Godwin Ave. Paterson, N. J.

Examine FREE

PULSE TECHNIQUES

by S. Moskowitz and J. Racker

Get this new self-training book for 10 days' free examination



Here is everything you need to know about pulse techniques—a subject of increasing importance in television, communications, and all electronic equipment. This book covers transient response of linear networks, design of pulse networks, pulse shaping and clamp circuits, pulse generation, measurement, and instruments, pulse communication systems, and aerial navigations aids.

PARTIAL CONTENTS: Fourier-transform method. Response of an ideal low-pass filter to a step voltage. Physical significance of response curves. Response to a pulse series. Determination of network response by Fourier transforms. Use of partial fractions in the solution of transform problems. Laplacian transform and inverse Laplacian of a step voltage. Typical network problems using L transforms. High-pass RC filter. Pulse transformers. Step-voltage build-up time response of a step-down transformer. Delay-time response. Special coaxial delay lines. Design of lumped lines. Supersonic delay lines. Shunt-peaking amplifier. Four-terminal coupling networks. Transmission-line amplifiers. Cathode follower. Limiter circuits. Clipping circuits. Peak-riding clipper. Integrating circuits. Positive-bias restorer. Electron-coupled pulse oscillators. Relaxation oscillators. Multi-vibrators. Sweep circuits. Time calibration. Pulse-counting systems. Commutation. Modulation. Synchronization. Commercial pulse communication system. Introduction to radar systems. Timing unit. Radar receiver. Navar system. Loran system. Get this authoritative handbook today! Coupon below brings you "Pulse Techniques" on FREE trial for 10 days. Mail it NOW!

MAIL COUPON TODAY

Prentice-Hall, Inc., Dept. M-RE-353
70 Fifth Avenue, New York 11, N. Y.
Please send me a copy of PULSE TECHNIQUES for FREE examination. Within 10 days I will either return the book and owe nothing, or keep it and remit \$2.65 down (plus postage) and \$2 monthly for 2 months.

Name _____
Address _____
City _____ Zone _____ State _____

RADIO-ELECTRONICS

SIMPLE PHONO OSCILLATOR


Here is a neat little battery-powered phono oscillator which gives surprising results at distances up to 100 feet. Separate isolated inputs and volume controls are provided for operating the oscillator either from a low-level micro-

phone or from a high-output phono pickup.

Coil L1 is a single-layer type broadcast antenna or r.f. coil with a 20-turn tickler (L2) of No. 30 enameled wire, wound close to the bottom of the form. The tubes, tuning capacitor, and most

of the remaining parts were taken from a junked personal-type portable receiver.

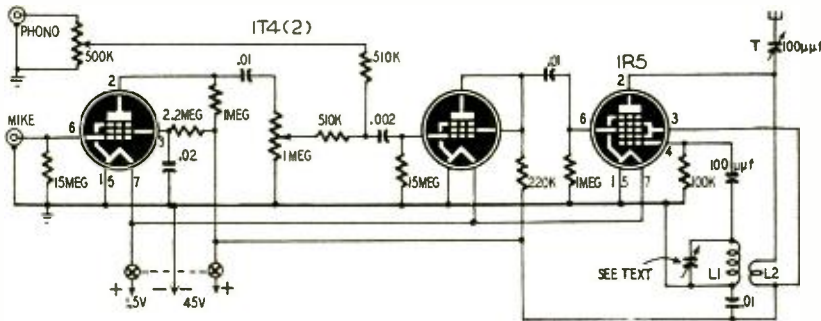If you don't care to use an antenna or r.f. coil, you can use the oscillator coil from a battery receiver. Keep the antenna as short as possible to avoid excessive radiation and possible interference with other broadcast-band receivers.—G. R. Anglado



CRYSTAL-DIODE TESTER

The usual method of testing crystal diodes is to measure the forward and backward resistances and the back current with a fixed voltage. The values thus obtained are then compared to those obtained with standard crystals. Although a diode may pass these tests with flying colors, the conversion loss, noise temperature, and other factors

TeleSound CUSTOM-BUILT TV CABINETS

Direct from MANUFACTURER to YOU!

Be Alert—be smart! Don't be misled by other offerings of cabinets similar to these original TeleSound creations, at lower prices. They are NOT the same quality. When you buy from TeleSound, you buy from the MANUFACTURER—at the lowest possible prices consistent with the high quality of these cabinets.

Be price and quality conscious! TeleSound wholesale prices enable you to sell more, make a BETTER PROFIT for yourself, with greater satisfaction to your customers. Compare price and quality—then—buy with confidence from TeleSound. Our factory-to-you shipments, and lowest wholesale prices, are your guarantee of satisfaction!

Nationally Advertis **SUPER DeLUXE TV CHASSIS**

VIDEO
MODEL 630K3C

SMASHINGLY LOW PRICED!
\$149.50

- 30 tubes—for 16" to 24" Picture Tubes
- High Efficiency High Voltage Circuit
- Keyed AGC
- Automatic brightness control
- Special extra high gain Cascade Standard Coil Tuner
- Directly adaptable for UHF.
- 12" Quality speaker
- Factory wired, aligned, tested.
- Complete, ready to play, including tubes, knobs and hardware
- Less CRT

Video 630DX DeLuxe Chassis for extreme fringe area. Complete, \$159.50
Techmaster C-30 Chassis, Complete with Tubes & Speaker, Less CRT, \$149.50

DeLuxe Techmaster 2431P Chassis. Complete less CRT\$199.95
FREE OFFER! Schematic Diagram and complete 24 page service manual FREE with any of these chassis!

GUARANTEED QUALITY & VALUE!



H:25", D:21 1/2", W:25" Wgt: 50 Lbs.
TABLE MODEL 500 **\$42.00**



As above, for 24" Picture Tube
H:31", D:24", W:27" Wgt: 60 lbs. **\$55.80**

H:40 1/4", D:22 1/2", W:25 1/4" Wgt: 60 lbs. CONSOLE MODEL 200 **\$47.50**

HERE'S THE "PACKAGE DEAL" YOU'VE WAITED FOR!

SAVE MONEY! Order the cabinet of your choice from the TeleSound models illustrated, in combination with the famous Video 630 TV Chassis, 12" speaker, and your choice of picture tube. If Video 630DX DeLuxe Chassis is desired, add \$10 to combination price. For DeLuxe Techmaster 2431P Chassis, add \$50. Check these sensationally low prices:

CABINET STYLE	COMBINED WITH Super 630 Chassis, 12" Speaker, and			
	17" CRT	20" CRT	21" CRT	24" CRT
500	\$216.25	\$222.70	\$227.00	\$272.50
200	\$221.50	\$227.90	\$232.25

FAMOUS MAKE TV PICTURE TUBES


ALL STANDARD BRANDS—NATIONALLY ADVERTISED
FULL ONE YEAR GUARANTEE

DON'T BE MISLED—DEMAND GUARANTEED STANDARD BRANDS

12 1/2" Black or White	\$22.55
14" Glass Rect. (Blk)	22.55
16" Glass Round (Blk)	33.55
16" Glass Rect. (Blk)	33.55
17" Rectangular (Blk)	32.45
19" Round (Blk)	36.85
20" Rectangular (Blk)	39.05
21" Rectangular (Blk)	43.45
24" Metal	76.45
27" Rect.	Wholesale Price on Request

Please include 25% deposit with orders, balance C.O.D. All shipments F.O.B., NYC "Designers & Manufacturers of Custom TV and Radio Furniture"

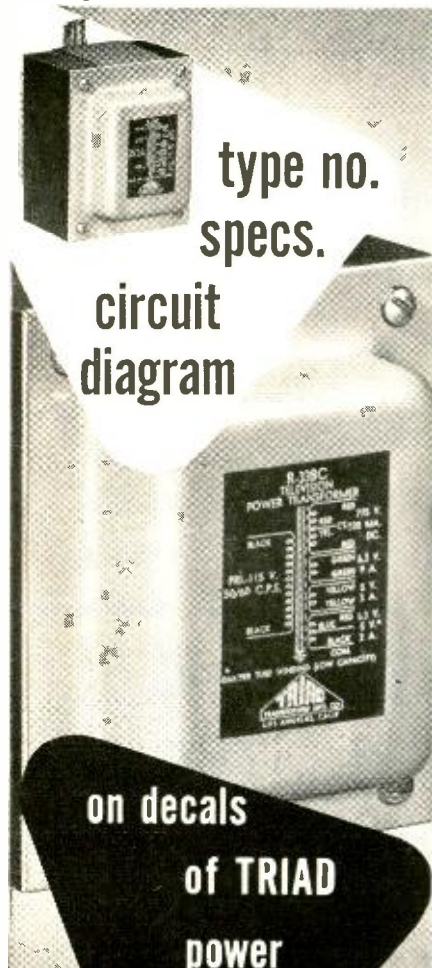TeleSound CORPORATION
421 West 28th Street
New York 1, N.Y.
Phone: WI 7-0719



Triad Power Transformers—like other Triad transformers—have the essential information right where you want it—on the decal. It simplifies installation—speeds servicing—makes reordering easy. Whether used for replacement, industrial applications, PA amplifiers or amateur gear, they offer small size, maximum efficiency, low temperature rise and low cost. Also, they are "Climatite" treated, both coil and core, for protection against moisture and for elimination of lamination chatter. Laminations are painted to prevent rust. Copper straps are used for static shields, grounded to case and core. Leads are color coded, UL approved. Final tests include checking for proper operation. Cases are finished in durable, attractive grey baked enamel.


Write for Catalogs TR-52B and TV-52B



may make it entirely unsuitable for many applications.

The crystal-diode tester shown in the diagram is the invention of Peter D. Strum and is described in Patent No. 2,585,353. The unit indicates conversion loss and noise temperature. Performance curves, calibration charts, and construction drawings will be found in the published patent.

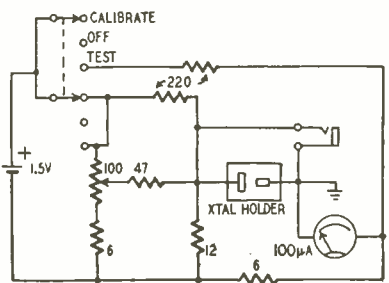The tester is calibrated initially by placing the switch in the TEST position with a fixed resistor between 300 and 3,000 ohms plugged into the crystal socket. The potentiometer is then ad-



justed so the meter reads full scale (100 μ a). Then, without varying the potentiometer, the switch is thrown to CALIBRATE. The meter reading is then marked on the dial of the potentiometer. Other resistors between 300 and 3,000 ohms are then used to calibrate the potentiometer dial throughout its range.


To check crystals, plug the crystal into the socket, throw the switch to CALIBRATE, and adjust the potentiometer so its dial setting corresponds to the meter reading. Switching over to TEST gives a new meter reading which is an indication of the quality of the crystal being tested.

NOVEL CAPACITOR CHECKER

I am one who likes to get as much use as possible from existing equipment so I developed this method of testing capacitors for shorts, opens, and leakage. For the test, I use a d.c. vacuum-tube voltmeter and a source of B voltage. The latter may be a bench power supply or the power supply in a piece of equipment under test.

From the supply, I tap off a d.c. voltage equal to the working-voltage rating of the capacitor to be checked. This voltage is applied to the capacitor and v.t.v.m. in series as shown in the diagram.

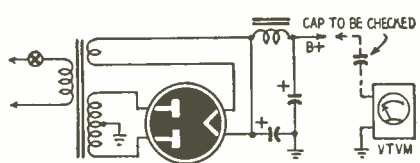
If the capacitor is good, the needle of the meter will immediately swing up scale as the capacitor charges; then it will drop to 1 or 2 volts. This indicates that the capacitor is good for blocking d.c. A leaky capacitor will show a much higher voltage reading—depending on the amount of leakage through the capacitor and on the test voltage.



RADELCO

LIGHTNING ARRESTOR

MODEL R-116

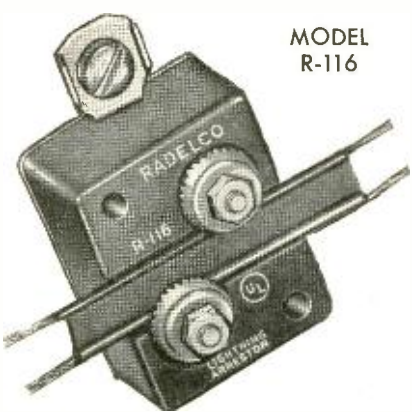

IT'S THE LOWEST PRICE UNDERWRITERS' LISTED ARRESTOR ON THE MARKET

ORDER FROM YOUR NEAREST PARTS JOBBER

LIST PRICE **90¢**

TV Receiver Sensitivity Measurements made Simple with

The New "SensiMeter"*

... a "must" in fringe areas



Net \$129.50
*Part. Applied For

- * Takes the guesswork out of TV service
- * Checks receiver from antenna terminals to picture tube
- * Microvolt scale is divided into 3 sections as a guide for the servicemen
- * Sensitivity testing is accepted by servicemen as the best method of determining the cause of bad pictures

Approved by leading television manufacturers!

Consult your jobber or write for further information

SI SERVICE INSTRUMENTS COMPANY
422 South Dearborn Street, Chicago 5, Illinois

G-C HAS MADE... 125 MILLION STAND-OFFS FOR THE TELEVISION INDUSTRY

125 MILLION STAND-OFFS! Yes, G-C recently completed the manufacture of its 125,000,000th Stand-Off . . . made possible by the fact that the entire radio-TV service industry recognizes the value, the top quality built into every G-C Stand-Off—available from your jobber in 24 popular styles.











All G-C Stand-Offs are supplied with genuine Polyethylene insulators like this . . . featuring the exclusive G-C reinforcing rib that keeps the insulator from collapsing.




G-C KANT-STRIP MAST STAND-OFFS

Exclusive, improved mast stand-offs with strip-proof extruded threads. Extra strong; no flimsy light metal used; no loose nuts to fall out. Galvanized strap has round end for easier threading. Genuine Polyethylene insulator, unique G-C design.

No.	Size
8253	3 1/2" Single
8257	7 1/2" Single

 <p>G-C UNIVERSAL STAND-OFFS (Machine Screw Type)</p> <table border="0"> <tr> <td>No.</td> <td>Length</td> </tr> <tr> <td>8031</td> <td>3 1/2"</td> </tr> <tr> <td>8032</td> <td>5 1/2"</td> </tr> <tr> <td>8035</td> <td>7 1/2"</td> </tr> </table>	No.	Length	8031	3 1/2"	8032	5 1/2"	8035	7 1/2"	 <p>G-C UNIVERSAL STAND-OFFS (Wood Screw Type)</p> <table border="0"> <tr> <td>No.</td> <td>Length</td> </tr> <tr> <td>8027</td> <td>3 1/2"</td> </tr> <tr> <td>8028</td> <td>5 1/2"</td> </tr> <tr> <td>8029</td> <td>7 1/2"</td> </tr> <tr> <td>8030</td> <td>12"</td> </tr> </table>	No.	Length	8027	3 1/2"	8028	5 1/2"	8029	7 1/2"	8030	12"	 <p>G-C NAIL-IN STAND-OFFS</p> <p>New, speed-type nail-in stand-offs save installation time, labor and cost on each job. Easy to use, Genuine Polyethylene insulators.</p> <table border="0"> <tr> <td>No.</td> <td>Length</td> </tr> <tr> <td>8343</td> <td>3 1/2"</td> </tr> </table>	No.	Length	8343	3 1/2"	 <p>G-C DUPLEX IN-LINE STAND-OFFS</p> <p>Two styles, wood screw and machine screw types. Heavily zinc plated to prevent rust.</p> <table border="0"> <tr> <td>No.</td> <td>Size and Type</td> </tr> <tr> <td>8225</td> <td>7 1/2" Wood Screw</td> </tr> <tr> <td>8226</td> <td>7 1/2" Machine Screw</td> </tr> </table>	No.	Size and Type	8225	7 1/2" Wood Screw	8226	7 1/2" Machine Screw
No.	Length																														
8031	3 1/2"																														
8032	5 1/2"																														
8035	7 1/2"																														
No.	Length																														
8027	3 1/2"																														
8028	5 1/2"																														
8029	7 1/2"																														
8030	12"																														
No.	Length																														
8343	3 1/2"																														
No.	Size and Type																														
8225	7 1/2" Wood Screw																														
8226	7 1/2" Machine Screw																														
 <p>G-C SNAP-ON STAND-OFFS</p> <p>NEW, improved snap-on that is easier to install, then stays on. Snap . . . and it's on; that's all there is to it! Two standard sizes. Feature exclusive G-C reinforced insulators.</p> <table border="0"> <tr> <td>No.</td> <td>Size</td> </tr> <tr> <td>8797</td> <td>For 1" Masts</td> </tr> <tr> <td>8798</td> <td>For 1 1/4" Masts</td> </tr> </table>	No.	Size	8797	For 1" Masts	8798	For 1 1/4" Masts	 <p>G-C "WIRE-GRIP" GUY WIRE STAND-OFFS</p> <p>TV lead-ins and rotator wires can be brought down long guy wires. Fasten permanently; easy to use. Genuine Polyethylene insulators.</p> <table border="0"> <tr> <td>No.</td> <td>Size and Type</td> </tr> <tr> <td>8255</td> <td>3 1/2" Single</td> </tr> <tr> <td>8256</td> <td>Double Type</td> </tr> </table>	No.	Size and Type	8255	3 1/2" Single	8256	Double Type	 <p>G-C DUPLEX KANT-STRIP MAST STAND-OFFS</p> <p>Heavy steel stand-off with strip-proof extruded threads. A deluxe stand-off at a really low price. Galvanized strapping. For both 300-ohm and coaxial lines.</p> <table border="0"> <tr> <td>No.</td> <td>Type</td> </tr> <tr> <td>8258</td> <td>Double</td> </tr> </table>	No.	Type	8258	Double	 <p>G-C EAVE TYPE CLAMP-ON STAND-OFFS</p> <p>New type, clamp-type stand-off that quickly fastens to eaves. Easy to install. Genuine Polyethylene insulators.</p> <table border="0"> <tr> <td>No.</td> <td>Type</td> </tr> <tr> <td>8811</td> <td>Single</td> </tr> <tr> <td>8812</td> <td>Double</td> </tr> </table>	No.	Type	8811	Single	8812	Double						
No.	Size																														
8797	For 1" Masts																														
8798	For 1 1/4" Masts																														
No.	Size and Type																														
8255	3 1/2" Single																														
8256	Double Type																														
No.	Type																														
8258	Double																														
No.	Type																														
8811	Single																														
8812	Double																														



G-C TEE-TYPE STAND-OFFS

Heavy zinc plated for permanent installation. Two types, wood screw and machine screw. For both 300-ohm and coaxial lines.

No.	Size and Type
8809	7 1/2" Wood Screw
8810	7 1/2" Machine Screw

FREE G-C's big, illustrated Catalog, chock-full of hundreds and hundreds of radio-TV service aids. Send a postcard for your copy today!



GENERAL CEMENT MANUFACTURING Co.
910 TAYLOR AVENUE ROCKFORD, ILLINOIS

TOP-SELLING TV-RADIO PUBLICATIONS distributed by **HOWARD W. SAMS & CO., INC.**

COYNE FAMOUS SHOP-TESTED REFERENCE BOOKS

"Latest Testing Instruments for Servicing Radio-TV"

New 1952 edition tells all about modern electronic testing equipment and how to use it most effectively. Packed with money-making short-cuts on trouble-shooting, servicing, construction and other subjects involving use of test instruments. Covers Multipliers, Resistors, Ohmmeters, Oscilloscopes, etc. All data shop-tested for practical application. Profusely illustrated, 350 pages. ORDER CTB-3. Only\$3.25




"TV Servicing Cyclopedia"—A Best Seller

The fact-packed TV reference book by H. P. Manly. Covers every phase of TV, including latest data on color and UHF. Shows you how TV works, how to service sets. Special sections on picture pattern servicing; testing and measuring; alignment; full treatment of amplifiers, antennas, controls, ion traps, sync. circuits, power supplies, video IF amplifiers, sweep oscillators, adapters, converters—covers everything. 750 pages. ORDER CTB-1. Only\$5.95



"Television and Radio Handbook"

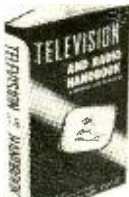1952 edition of the famous TV and radio "answer" book. Over 3000 facts packed into a single volume to speed trouble-shooting. Covers solutions to most frequent TV-radio service troubles; offers short-cut time-saving tips; data on TV boosters, latest UHF conversion methods, etc. 375 pages, hundreds of illustrations. ORDER CTB-5. Only\$2.75



BOYCE AUTHORITATIVE TV & RADIO HANDBOOKS

"Video Handbook"

Covers entire subject of TV; gives expert data on design, construction, production, installation, operation and servicing. Fourteen complete sections cover the field of TV exhaustively. All subjects treated practically and simply for easy understanding. A remarkable handbook widely used by schools, engineers, experimenters, and industrial technicians. 892 pages. ORDER BB-2. Only\$5.95



"Radio and Electronics Handbook"

Here is the basic knowledge and data of Radio and Electronics digested in 18 sections; complete, easy-to-locate data. Clearly explains radio and electronic theory, and covers all phases of the subject in detail. The most widely used handbook of its kind—absolutely invaluable to anyone interested in radio or electronics. 890 pages; illustrated. ORDER BB-1. Only\$4.95



HOWARD W. SAMS & CO., INC.

Order from your Parts Jobber today, or write direct to Howard W. Sams & Co., Inc. 2205 East 46th St., Indianapolis 5, Ind.

\$.....enclosed. Send the following books:

- CTB-3 CTB-1 CTB-5
- BB-2 BB-1

Name.....

Address.....


City.....Zone....State.....

A shorted capacitor will cause the meter to indicate the full value of the impressed supply voltage. An open capacitor will not cause the meter to kick when the voltage is applied and the reading will remain at zero volts.—*Leon Gold*

SIMPLIFIED METER SHUNTS

Very often we want to use a low-range sensitive milliammeter to measure a wide range of currents which may be found in the grid, filament, and plate circuits of transmitters, receivers, and similar equipment. When we use the average low-range meter, the shunt resistors may have values considerably less than 1 ohm. Precision resistors are expensive and easily damaged. It is a lot of trouble constructing and calibrating your own, so we increase the meter resistance and use standard stock resistors as shunts.

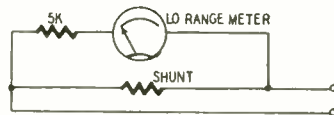To do this, we first connect a 5,000-ohm, 1-watt resistor in series with the meter and then shunt this combination as shown in the diagram. The resistance of the average meter is small compared to 5,000 ohms, so it can be disregarded.



Whatever the basic range of the meter, all you do to get the approximate shunt resistance is to divide 5,000 by the scale multiplication factor. Thus, if we start with a 1-ma meter and want to increase its range to 10 ma to measure grid current in a transmitter, we simply divide 5,000 by 10, and our shunt resistor becomes 500 ohms. To measure plate current, we might need a 500-ma shunt. In this case, we divide 5,000 by 500 and find that a 10-ohm resistor is required.

When selecting shunts, be sure that the resistors have an adequate wattage rating. For low current ranges, a 1-watt resistor may suffice. But, when extending the meter range to 500 ma or so, you may need a 10- or 20-watt resistor. The minimum wattage rating can be found by multiplying the resistance by the square of the current ($I^2 \times R$).

This method of shunting meters gives good results when used in constructing a multimeter.—*Mitchel Katz W2KPE*. (Be aware that by increasing the resistance of the combination the usefulness of the meter is reduced, often in direct proportion. For example, a meter-shunt combination with a range of 100 ma and a resistance of 50 ohms would be quite useless in measuring the current through the filament of the average 1.4-volt tube, as the meter would have more resistance than the filament, and the reading would therefore be less than half the normal current. In other applications it might be quite acceptable, as in the example of the 500-ma shunt. A resistance of 10 ohms in the plate circuit would make no noticeable difference.—*Editor*) END

Editors and Engineers PUBLICATIONS

RADIO HANDBOOK. GIANT 13TH EDITION. A one-volume library of radio information with extensive, simplified theory. Detailed how-to-build-it data on dozens of items of practical radio equipment. Book No. E&E-RH13...\$6.00*

BETTER TV RECEPTION (in fringe and low-signal areas). **NEW SECOND EDITION.** The standard guide for installation technicians. A popular text for TV enthusiasts. Book No. E&E-TR2.....\$2.50*

RADIOTELEPHONE LICENSE MANUAL. Typical study questions with concise answers for any commercial U.S.A. radiotelephone operators license. Book No. E&E-RL1.....\$3.75*

ANTENNA MANUAL. A practical, comprehensive book on antennas, for everyone interested in transmission and reception. Over 300 pages. Book No. E&E-AM1.....\$3.50*

RADIO HANDBOOK, 12TH EDITION. Selected constructional items; only. English edition. Book No. E&E-RH12.....\$3.00*

Spanish edition. Book No. E&E-RHSP12...\$4.00*

WORLD'S RADIO TUBES (BRANS' VADE MECUM). **NEW 9TH EDITION.** Lists over 15,000 tubes from every tube making country. Printed in 16 languages. Book No. E&E-VM9...\$5.00*

SURPLUS RADIO CONVERSION MANUAL. VOL. 1. Practical conversions. Write for list of contents. Book No. E&E-SM1.....\$2.50*

SURPLUS RADIO CONVERSION MANUAL. VOL. 2. Companion to Volume 1. Book No. E&E-SM2.....\$2.50*

*Plus any tax.

BUY FROM YOUR DISTRIBUTOR

ADD 10% ON DIRECT MAIL ORDERS TO EDITORS and ENGINEERS, LTD. BOX 689B, SANTA BARBARA, CALIF. (Registered under name BAKER & TAYLOR, Hillside, N. J.)



to add increased brilliance to any TV PICTURE TUBE

manufactured by **Perma-Power COMPANY**

Chicago 25, Illinois
Manufacturers of Electronic Equipment Since 1928
RADIO-ELECTRONICS


NEW... AMAZING... OSCILLOSCOPE by precise

(IN KIT AND WIRED FORM)


ACCEPT NO SUBSTITUTE—INSIST on this latest PRECISE Original—No other "scope" can compare with this newest test instrument—BECAUSE: PRECISE uses **NO SURPLUS**—only the finest components in our precision-engineered products. PRECISE offers an iron-clad guaranty with every purchase. AND PRECISE gives you an instructively illustrated, 3 color, "step-by-step" construction book—the most comprehensive in the market today!

HERE ARE A FEW OF THE NUMEROUS PRECISE FEATURES IN THE NEW OSCILLOSCOPE:

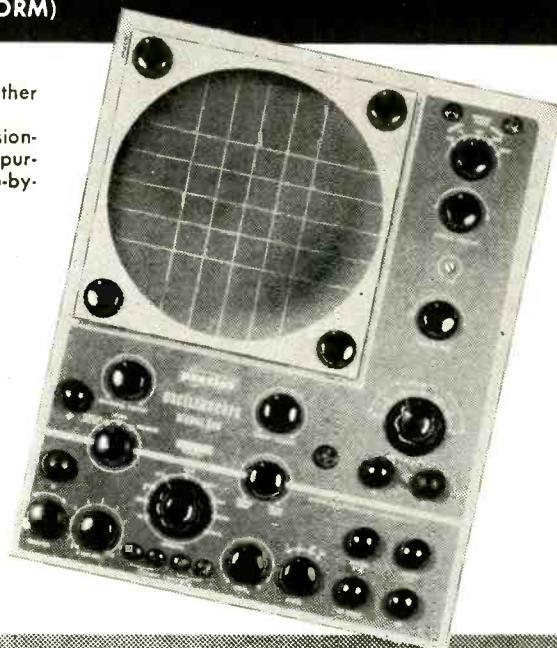1. True electronic sweep magnifier
2. Astigmatism control
3. Push-Pull vertical from input thru output; push-pull horizontal
4. Internal blanking and Z modulation with blanking amplifier
5. Driven and non-driven sweep
6. Over 5MC flat response—DC amplifiers
7. Cathode follower input on vertical and horizontal
8. Internal calibrator
9. Horizontal and vertical stepping attenuator
10. NEW 7" Tube to PRECISE specifications
11. Highest sensitivity available aside from finest laboratory scopes



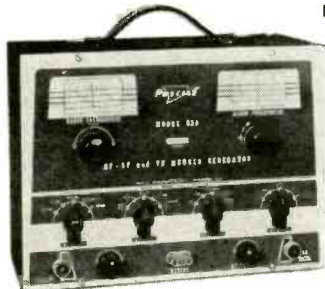PRECISE TEST EQUIPMENT AVAILABLE IN KIT AND WIRED FORM



MODEL 630 RF-AF-TV AND MARKER GENERATOR. For the first time in the history of the industry... **SO MUCH FOR SO LITTLE** 110 MC on fundamentals; 330 MC on harmonics; Pre-tuned RF (within 1% head); AF from 20 to 20,000 cycles; variable % and Ext. Mod.; Cathode-Follower and Constant Z output; Stepping attenuator; Speech Amp.; Xtal Marker with Amp. control; RF and AF Standby; Wien Bridge AF; Colpitts RF; Illuminated Drum Dials; Coax outputs; Separately tuned coils; Filtered AC; Vernier tuning; Separate RF; Shielded; 8" x 11" x 5"; Etched panel.

*Model 630KA \$38.95 (pre-assembled head) **Model 630K \$33.95**
Model 630W \$53.95 (Factory wired)



MODEL 635 UNIVERSAL AF SINE, SQUARE AND PULSE GENERATOR. For accurate testing audio and video circuits; 1% Ceramic precision resistors; Wien Bridge; variable Z and cathode-follower output; minimum overshoot and roundoff through 100,000 cycles; sine waves through 200 KC **\$33.50**
Factory wired \$52.50



MODEL 909 VACUUM TUBE VOLTMETER. 1% Ceramic precision Resistors; Coax DC connector; FM zero alignment scale; burn-out proof circuit. Rugged oversize 4 1/2" meter **\$25.98**
Factory wired \$44.98


FOR COMPLETE LINE OF PRECISE KITS MAIL COUPON BELOW

MODEL 912 RF PROBE. LOWEST PRICED, factory wired Probe in the industry. Individually calibrated at 75 MC for accuracy, impedance and shunt capacity. **Wired Only \$4.25**

MODEL 960 CAPACITY ATTENUATOR PROBE. Reduces input C. and loading effects of an oscilloscope by 10 to 1. Adjustable for any scope. Lowest priced in the field, but still using highest quality components. **Wired Only \$5.95**



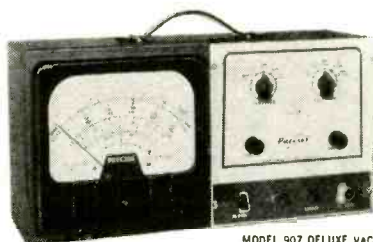MODEL 610 RF SIGNAL GENERATOR. The lowest priced signal generator in the field offering—Same RF head as Model 630; 110 MC on fundamentals; 330 MC on harmonics; 50 and 400 cycle AF; Cathode-follower output; Ext. Mod.; Speech Amp.; Individually tuned coils. **Model 610K \$23.95**
Model 610KA \$28.95 (pre-assembled head)
Model 610W \$39.95 (wired)



Prices slightly higher in the West. Prices and specifications subject to change without notice.

MODEL 907 DELUXE VACUUM TUBE VOLTMETER. Another PRECISE first! Vertical or Horizontal construction. GIGANTIC 7 1/2" meter movement; all the unusual values and features of Model 909 in a really DELUXE version **\$38.98**
Factory wired \$57.98

SEE US at the I.R.E. SHOW Booth 4-426 and 4-428

precise DEVELOPMENT CORP.
OCEANSIDE, NEW YORK

PRECISE DEVELOPMENT CORP. DEPT. RE-15
999 LONG BEACH ROAD • OCEANSIDE, L. I., NEW YORK

GENTLEMEN: Without any obligation on my part, kindly send me the following:

- PRECISE CATALOG
- NAME OF DISTRIBUTOR NEAREST ME

NAME _____
ADDRESS _____
CITY _____ ZONE _____ STATE _____

The world's most desirable oscilloscope for TV service.



JACKSON

MODEL CRO-2

Proved by the hundreds in use by TV manufacturers' and dealers' technicians

Judging by ratio of sales to market potential, this laboratory grade 5" oscilloscope is preferred by the great majority of television and electronic technicians. The specifications explain why such is the case.

Specifications

Vertical Amplifier—Push-pull amplifiers provide flat response within 1.5 db from 20 cycles thru 4.5 Mc.

Sensitivity Ranges—The sensitivity ranges are 0.18, .18, 1.8, .25, 2.5, 25 RMS volts-per-inch.

Horizontal Amplifier—Push-pull with sensitivity of .55 RMS volts-per-inch.

Input Impedances—Vertical 1.5 megohms shunted by 20 mmfd. Direct to plates, balanced 6 megohms shunted by 11 mmfd. Horizontal: 1.1 megohms.

Linear Sweep Oscillator—Saw tooth wave 20 cycles to 50 Kc in 5 steps. 60 cycle sine wave also available as well as provision for using external sweep.

Input Voltage Calibration—Provides a standard voltage against which to measure voltages of signal applied to vertical input.

Vertical Polarity Reversal—For reversing polarity of voltage being checked or for choosing either positive or negative sync. voltages.

Return Trace Blanking—Electronic blanking provides clear, sharp trace to prevent confusion in waveform analysis.

Synchronizing Input Control—to choose among INTERNAL, EXTERNAL, 60 CYCLE, or 120 CYCLE positions.

Intensity Modulation—60 cycle internal or external thru front panel binding posts.

Accessory—Model CR-P Probe for demodulating RF and IF voltages.

Prices: Model CRO-2, Users' Net \$197.50
Model CR-P Probe. Users' Net \$9.95

See your electronics distributor for more information, or write

JACKSON ELECTRICAL INSTRUMENT CO. • DAYTON 2, OHIO
"Service Engineered" Test Equipment
IN CANADA: THE CANADIAN MARCONI CO.

Standard Brand Radio & T.V.

TUBES

Convince yourself. Send TODAY for our bi-weekly Bulletin of Excellent Tube Values. Dept. "C"

KMA Guarantor
Current Listings

MANNFRED
Electronics Corporation

8 Barclay 7-4565 6544

EFFECTIVE IMMEDIATELY: ALL TUBES INDIVIDUALLY BOXED IN ATTRACTIVE TWO COLOR BOXES AT NO EXTRA CHARGE!

136 LIBERTY STREET N. Y.

AUDELS TV-RADIO SERVICE LIBRARY

HERE IS LATE INFORMATION IN A HANDY FORM FOR RADIO & TELEVISION REPAIRMEN, SERVICEMEN & STUDENTS



2 VOLS. \$6 COMPLETE \$1 A MO. PAY ONLY 1 MO.
IT PAYS TO KNOW!

AUDELS T.V.-RADIO SERVICE LIBRARY presents the important subjects of Modern Radio, Television, Industrial Electronics, F.M. Public Address Systems, Auto, Marine & Aircraft Radio, Phonograph Pick-Ups, etc. Covers Basic Principles—Construction—Installation—Operation—Repairs—Trouble Shooting. Shows How to get Sharp, Clear T.V. Pictures. Install Aerials—How to Test. Explains Color Systems & Methods of Conversion. 1001 Facts—Over 1260 Pages—625 Illustrations—Parts & Diagrams—Valuable for Quick Ready Reference & Home Study. Tells How to Solve T.V. & Radio Troubles—Answers T.V. & Radio Questions.

Get this information for Yourself.
7 DAY TEST — ASK TO SEE IT!


-----**MAIL ORDER**-----
AUDEL, Publishers, 49 W. 23 St., N.Y. 10
Mail AUDELS T.V. RADIO SERVICE LIBRARY 2 Vols. \$6 on 7 days free trial. If O.K. I will remit \$1 in 7 days and \$1 monthly until \$6 is paid. Otherwise I will return them.

Name _____
Address _____
Occupation _____
Employed by _____ RE

RADIO-ELECTRONICS

CHARGING DRY BATTERIES

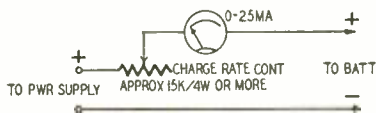
The life of 45- and 67½-volt batteries used in portable receivers and test instruments can be prolonged by the recharging scheme illustrated in the diagram. The charging current of about 15 ma can be obtained from any convenient power supply.



The batteries should be recharged before the terminal voltage drops below one-half its rated value. Check the voltage while recharging to prevent overcharging. Disconnect the battery from the power supply before checking the voltage. When the voltage has come up to normal, let the battery rest for about eight hours to allow the voltage to stabilize.—O. C. Vidden

ANCHORING CABLES

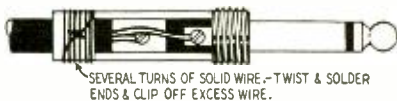The cables entering PL-55, PL-54, and PL-68 plugs and JK-26 jacks should be anchored to eliminate strains on the connections. The result of the special clamping bands manufacturers use can be duplicated easily. After connecting



the cable, wrap the clamping area with No. 20 or 22 solid wire. Then twist the two ends tightly together and apply a small spot of solder. The twisting of the ends gives a strong clamping action.—Richard Sandretto

QUICK MIP SOCKET REPAIR

While checking a piece of defective equipment, I found that one of the pin lugs of a MIP type octal socket had broken off flush with the bakelite body. The damaged socket was in a crowded section of the chassis where it would be extremely difficult to remove.

With a stiff piece of fine wire, I punched out the remaining piece of pin contact from the under side of the socket. Then I removed a perfect contact from a spare socket, slipped it into the slot, and seated it in place by inserting a tube into the socket. A slight bend on the underside of the socket locked the new contact firmly in place. I soldered on the lead from the broken lug and the job was done. This kink enabled me to make the repair in a few minutes without disturbing existing wiring. Replacing the whole socket would have taken much longer.—Alan Palmer

INSULATED CLAMPS

When an insulated, low-loss cable clamp is needed for unshielded grid leads (a metal one may cause detuning) and certain leads in TV high-voltage supplies, cut a small piece of 300-ohm ribbon lead and strip out the wires. When bent into a U-shape and the ends drilled for a bolt, it makes a nice non-conductive, low-capacitance clamp.—B. W. Welz

MARCH, 1953

BARGAINS • BARGAINS • BARGAINS

BARGAINS • BARGAINS • BARGAINS

BARGAINS • BARGAINS • BARGAINS

You can depend on STEVE-EL to come up with "terrific" buys! Here is just a "sample" of the hundreds of bargains. Our latest catalog is chock full of 'em. Write today!

TAPE RECORDERS

- Web-Cor tape recorder #210B..... \$146.50
- Pentron tape recorder #9T3C..... 117.50
- Tape Master tape recorder PT 125... 89.50
- Tape Master Power Amplifier #SA13 69.50

EXTRA SPECIAL

- 3 Tube 6 Watt Power Amplifier Kit..... \$9.39 less tubes
- 3 Tube Phono Amplifier, Wired — Amplifier uses 50C5, 35W4, 12AT6..... \$2.98 less tubes

PHONO EQUIPMENT

- 78 RPM Phono Motor..... \$2.59
- 3 Speed Phono Motor..... 5.25
- 78 RPM Pick up..... 2.19
- 3 Speed Twist Pick up..... 4.75

SPEAKERS

- Alnico #5 P.M.
- 4" PM..... \$1.33
- 5" PM..... 1.39
- 4x6" PM..... 1.89
- 5x7" PM..... 2.28
- 6" PM..... \$2.49
- 8" PM..... 2.99
- 10" PM..... 3.59
- 12" PM..... 4.25
- 4 Prong 6 Volt Auto Vibrators..... \$9.97
- "Kine-Lite" Renews brilliance and contrast of Picture Tube..... 2.49

OUTPUT TRANSFORMERS

- For 50L6, 25L6, 3Q5, 3V4, 6K6, 6F6... \$.46
- For pair 50L6, 25L6, 6F6, 6K6..... \$5.59

TUBES

1B3GT	.63	6S7	.42
1U4	.48	6T8	.74
1U5	.48	6U6	.57
1S5	.48	6U8	.78
1X2	.63	6V6GT	.46
5U4	.38	6V8	.83
5W4GT	.46	6W4	.45
5Y3GT	.29	6W6	.52
6A7	.62	6X4	.74
6A8	.51	7C6	.42
6AG5	.62	7X7	.62
6AK5	1.14	12AT6	.48
6AL5	.41	12AU6	.48
6AU6	.43	12A7	.56
6BC5	.58	12AV6	.52
6BC7	.86	12AZ7	.94
6BE5	.48	12BA6	.47
6BG6	1.21	12SA7	.52
6BH6	.62	12SK7	.49
6BJ6	.53	12SL7	.57
6BK7	.86	12SN7	.54
6BQ5	.76	12SQ7	.42
6BQ7	.86	14AF7	.59
6CB6	.48	19T8	.77
6F6	.49	25BQ6	.48
6J6	.79	25W4	.48
6L6G	.89	25L6	.48
6SA7	.52	25Z6	.42
6SG7	.49	35L6	.48
6SK7	.49	35Z6	.33
6SL7	.52	50L6	.48
6SN7	.54	80	.38

SPECIAL DISCOUNTS

- 50 Asst. { 5%
- 100 Asst. { 10%

STEVE-EL ELECTRONICS CORP.

Dept. RE-3, 61 Reade St., New York 7, N. Y. COrtlandt 7-0086

BRIGHTEN YOUR SALES PICTURE With The New **KINE-LITE** Picture Tube Pat. Pending
Brightener & Rejuvenator

VIDAIRE'S Kine-Lite operates on ANY cathode ray picture tube of 10" and larger, including electrostatic focus.

VIDAIRE's Kine-Lite brings new brightness to TV picture tubes having low emission—permanent installation — can be re-used — simple instructions with each unit. \$495 list

- ★ Renews brilliance and contrast of picture
- ★ Prolongs life of old picture tubes
- ★ Easy to install ★ No soldering necessary
- ★ For all standard tubes using duo-decal bases
- ★ No limit to tube size—10" to 30"
- ★ Standard Warranty ★ Two connecting plugs
- ★ Compact, attractive package
- ★ QUICK SELLER — EXCEPTIONAL PROFITS

Sold only through VIDAIRE distributors
Write for Catalog A

Vidaire Electronics Mfg. Co.
Mfrs. of TV color equipment, phono & TV amplifiers
6 E. 39th St., N. Y. 16, N. Y.
LExington 2-7372

Let me show you how EASY it is to **LEARN TV** the practical way—

ASSEMBLE A TRANSVISION TV KIT

Pay as You Wire \$ **39** Down Payment

I WILL HELP YOU to start learning TV the practical way — by assembling a TRANSVISION TV KIT in EASY STAGES. For only \$39 you get PACKAGE #1 (standard first pkg. for all of our kits). This package gives you the BASIC CHASSIS and over 450 TV COMPONENTS with complete Instructions, Drawings, Photos, Service Booklet, and a year's subscription to my "TV and Electronics Notes". When ready, you order the next stage (pkg. #2), etc. Low prices make your complete kit a terrific buy!

Your completed chassis is a superb 25 tube set (22 tubes plus 3 rectifier tubes), with 6"x9" p.m. speaker, Automatic Frequency Control, Automatic Gain Control. You have a CUSTOM-QUALITY TV SET worth up to 100% over your investment. Ideal for fringe areas. UHF and Remote Control may be had at a small additional cost. (Also adaptable to foreign TV systems). Used in Naval Reserve Training Program. Over 70,000 learners, including U. S. Naval trainees, have assembled our kits. No Previous Technical Knowledge or special tools required.

FAMOUS EDITOR of a national science magazine says: "... my own assembly (of the kit) produced top-quality results, comparable with any set I've seen and better than most!" So you see, you have everything to gain. Don't put it off — order your PACKAGE #1 today.

FREE CATALOG describes 6 great new Transvision TV Kits.

Write today to D. GNESSIN, EDUCATIONAL DIRECTOR, at: TRANSVISION, INC., Dept. RE, NEW ROCHELLE, N. Y.

ANACONDA UHF LINE

was adapted for use because it was found to be the most reliable available; had lowest losses under adverse weather conditions . . .

- high-strength conductor
- unique inner construction
- reliable over the entire range of both VHF and UHF channels

ORDER TODAY! Carried by leading jobbers.

Manufactured by Anaconda . . . supplied by "Columbia"




WIRE & SUPPLY CO. 2850 Irving Park Road Chicago 18, Illinois

New "UHF" Line
for the first commercial UHF Telecasts

"PERSONAL" HEADPHONES

Headphones have been with us for many years and are simple and efficient devices for those with normal hearing or those with equal hearing loss in both ears. However, there are many of us whose hearing is near normal in one ear while the other is only a fraction as sensitive to sound. For such people headphones can be easily improved to give the impression of normal hearing. The result is truly amazing to those who have become accustomed to "one-sided" sound.

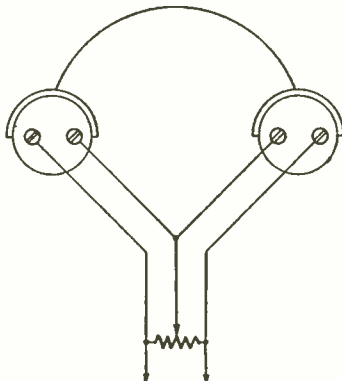

In a pair of magnetic phones, we find two identical units connected in series. Now if we connect a 50,000 or 10,000-ohm control across them, we can now proportion the voltage to each phone unit, giving the stronger or more sensitive ear less sound and the weaker ear more sound until the sensation is that of normal hearing in both ears.


It would appear from the drawing that an additional wire would be needed in the phone cord. This is not so. We need not change the appearance of the phones at all. The volume control is used just to find the value of resistance to place across each phone unit. Then it is removed and fixed resistors substituted. In many makes of phones there is space enough inside the phone housing for the resistors so that the external appearance is unchanged.

Most headphones are reversible, so a spot of paint may be added as a means of quickly determining the phone for the left or right ear.—E. E. Youngkin

MOUNTING ACORN TUBES

The 954 and other types of acorn tubes are useful in many types of u.h.f. and v.h.f. circuits. However, their unusual construction often makes it difficult to incorporate them into conventional circuit layouts. Try the following the next time you want to use an acorn tube:

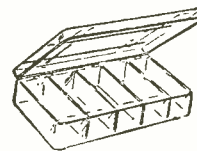Punch a 3/4-inch hole in the chassis at the desired place for the tube. Mount the acorn socket under the chassis, concentric with this hole. The tube is then installed in an upright position, but it is put in its socket from the bottom, with its envelope projecting through the 3/4-inch hole in the chassis. Since the tube is used in an upright position with the socket inverted, the



FREE WITH EVERY PURCHASE

Sparkling styrene utility box with every order this month. Quantity limited—so HURRY! Order now!

HANDY RADIO ASSORTMENTS

- 100 Insulated resistors \$2.39
- 100 Solderless terminals49
- 25 Tie lugs & terminal strips49
- 100 Tube sockets (mini, octal, etc.) 3.65
- 100 Knobs (set screw & push on) 2.95
- 100 Tubular condensers 4.69
- 50 Trimmer condensers79

EXTRA SPECIAL VALUES

- 300 Ohm twin lead—100 Ft. \$1.18
- GE RPX-050 reluctance cartridge 5.69
- ASTATIC "LQD" flip-over cartridge 2.95
- RCA 12" PM speaker 3.95
- Volume controls .18 w/sw. 500K Ea.29
- RCA pin plug & jack10 sets .95
- Superhet vari-cond. 365 µuf Ea.39

10 Lb. SURPRISE ASSORTMENT. Parts, assemblies, hardware, etc. You will like it and want more. \$4.95.

ALL PURPOSE AMPLIFIER

In leatherette box. Volume control—mike & phono input—3 tubes—5" alnico PM speaker. All electric. Complete, ready to operate. \$8.95 3 tube amplifier chassis only (as above) \$2.75.



GI 3 SPEED CHANGER

Special needle plays RCA, Columbia & standard records. 12 records at one loading. 12"x12 1/2". Wgt. 14 lbs. \$15.95
With flip-over cartridge \$19.95
Metal base for above \$3.50

SPECIAL! FAMOUS MAKE

Pocket V.O.M. with battery, test leads, guaranteed. Limited quantity. \$12.95

WRITE FOR FREE BARGAIN LIST NOW. IMPORTANT: 25% deposit on C.O.D. orders. Minimum order \$5.00.

JAN ELECTRONIC DISTRIBUTORS
222 FULTON STREET NEW YORK 7, N.Y.

ANOTHER OUTSTANDING JOBBER

BURROUGHS RADIO Inc.

711 Second Street N.W.
Canton, Ohio

HAS THE SENSATIONAL NEW

EICO

470-K 7" SCOPE KIT
IN STOCK!

470K KIT \$79.95 WIRED \$129.50


PLEASE MENTION RADIO-ELECTRONICS when answering advertisements

pin connections must be changed accordingly. In triodes, the plate and grid connections, and in pentodes, the screen and suppressor connections, must be transposed from their positions with the tube and socket in normal relationship. This is very easy to clear up with the help of suitable base diagrams.

Acorn tubes are excellent for converter and r.f. amplifier applications at v.h.f. and u.h.f. where gain is not critical. However, their transconductances are considerably lower than those of the more modern loctal and miniature tubes. Therefore, they should not be used in local oscillator circuits designed for these tubes. Erratic or poor operation may result.—*Charles Erwin Cohn*

CLOCK-RADIO MODIFICATION

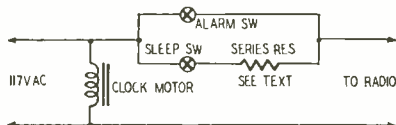One of the disadvantages of clock-radios is that when the volume is reduced sufficiently to provide soft music using the sleep switch on retiring, it is too low to waken one in the morning. Conversely, when the volume is set high enough for satisfactory waking operation, it is too loud the night before.



The diagram shows a simple circuit modification which can be applied to most clock-radios to remedy the situation. In many clocks the sleep switch is usually a separate unit in parallel with the alarm switch. The modification consists of introducing series resistance into the sleep switch circuit. The resistor drops the voltage to the radio, causing a reduction in volume. The resistance depends on the individual radio and on personal preference, and will have to be chosen by trial and error. However, for the a.c.-d.c. sets using 150-ma heaters, a value of between 100 and 200 ohms should be satisfactory. Wattage rating will be determined by the value of resistance used, and the current drain of the radio. A 10-watt resistor should handle the 150-ma heater sets, and a 20-watt resistor the 300-ma sets. Users of radios having transformer power supplies can calculate wattage dissipation. I have used a 150-ohm metal ballast tube on a set having 150-ma heaters with very satisfactory results.—*Thomas S. Ely, W3MJP*

GONSET NOISE CLIPPER

The hum level in Gonset noise limiters can be greatly reduced and the apparent effectiveness of the device can be increased by inserting an 8- to 10-ohm resistor in series with one of the heater leads supplying the clipper. The resistor reduces the heater voltage and minimizes hum introduced into the audio circuit by heater-to-cathode leakage.

This same procedure can be used to reduce hum in similar noise limiter circuits which use a separate clipper tube.—*G. P. Oberto*

(The installation of the series resistor is one of the first steps in the instruction sheets issued with late Gonset clippers.—*Editor*)

END


C-D does it again!

**6 capacitor assortments
in beautiful plastic cases!**

Ideal for storing screws, tubes, small parts of all sorts. Even fishing tackle. And you pay no more than if you bought the capacitors individually.

The majority of sets can be serviced with these six twist-prong electrolytic replacement kits. See your jobber today for full details. Cornell-Dubilier Electric Corp., South Plainfield, New Jersey.

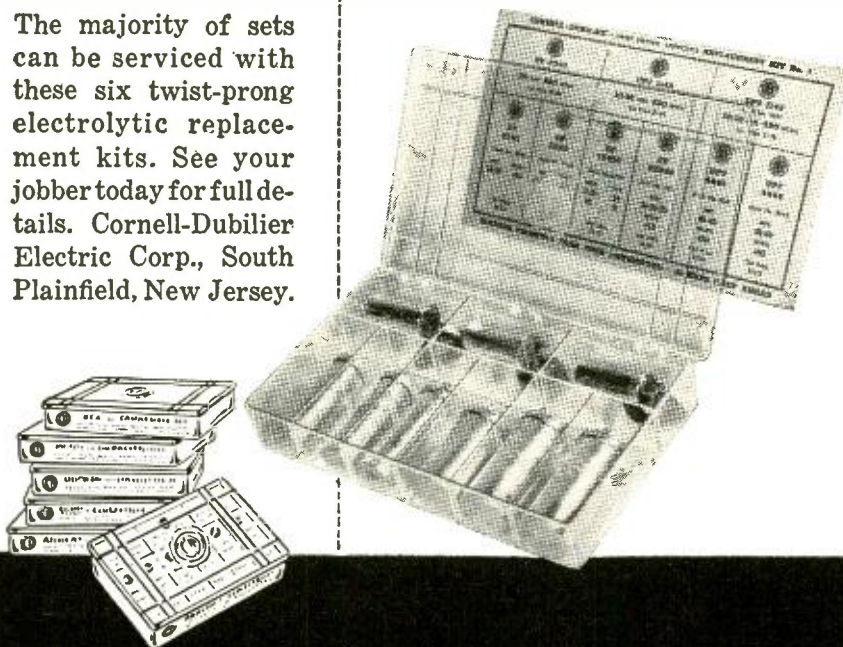- KIT #1 — UNIVERSAL
- KIT #2 — FOR RCA SETS
- KIT #3 — FOR PHILCO SETS
- KIT #4 — FOR MOTOROLA SETS
- KIT #5 — FOR GENERAL ELECTRIC SETS
- KIT #6 — FOR ADMIRAL SETS



A service of
CORNELL-DUBILIER
world's largest maker of capacitors

PLANTS IN SO. PLAINFIELD, N. J. • NEW BEDFORD, WORCESTER AND CAMBRIDGE, MASS. • PROVIDENCE, R. I. INDIANAPOLIS, IND. • FUGUAT SPRINGS, N. C. • SUBSIDIARY, RADIART CORP., CLEVELAND, OHIO

3 easy STEPS TO BETTER TV INSTALLATIONS

with **MOSLEY FLUSH SOCKETS**

1. Get the PK Package (right)—contains everything needed to complete installation!
2. No outlet box needed. Mounting brackets fit any type wall—easily, quickly installed!
3. Here's a neat, efficient installation. TV owners like the convenience of plug-in connection to lead-in!

Available at Radio Parts Jobbers

MOSLEY Electronics




2125 Lackland Rd.
Overland, Missouri

A.F. AMPLIFIER

? I get good results from this little receiver and would like to add a simple audio amplifier to it. Please show how I can add a 3Q5-GT as a power amplifier with sufficient power to drive a small PM speaker.—L. C., Texarkana, Ark.

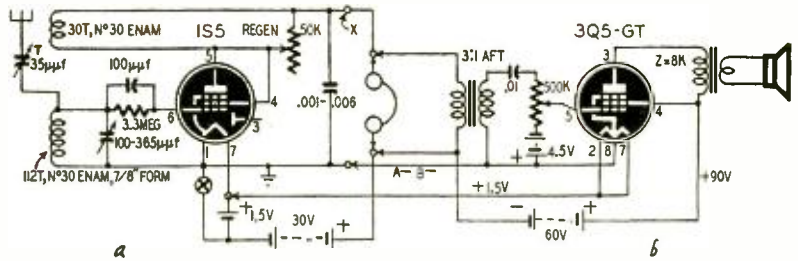A. The diagram of your set is shown at a and the diagram of the amplifier at b. The amplifier is hooked up to the receiver by making the connections shown in dashed lines. With these connections the amplifier and receiver are turned off with the switch in series with the common negative sides of the batteries.

(L. C. did not include the values of the resistors and capacitors in his set, so we have added typical values for those who may want to give the circuit a try. If the set does not go into and out of oscillation smoothly, try different values for the .001-.006- μ f capacitor and insert a 2.5-mh r.f. choke at X. The input coil consists of a 112-turn



grid winding and a 30-turn tickler. Both are wound on a 7/8-inch form with No. 30 enameled wire. The coils are wound in the same direction and spaced about 3/16 inch apart with the tickler at the bottom of the form. The plate lead connects to the outside end of the tickler and the grid lead connects to the outside end of the tuned coil. The tuning range of this coil is approximately 1100-3200 kc with a 144- μ f capacitor and 700-2100 kc with a 365- μ f unit. You can cover the range

of amateur and short-wave radio bands down to about 10 meters by using a 144- μ f tuning capacitor and a set of standard commercial all-wave plug-in coils, now obtainable from some of the radio mail-order houses.—Editor)

tone control for TV set

? I am enclosing a circuit of the audio section of a Magnavox CT-274 TV receiver. Please show how I can add a simple tone control to this receiver.—E. J. H., Plainfield, N. J.

BUY WITH CONFIDENCE FROM EDLIE

**ANOTHER GREAT EDLIE FIRST
SUTCO VHF-UHF BOOSTER CONVERTER**

This terrific unit enables any TV receiver now being manufactured to receive UHF signals and also have the booster necessary for VHF in fringe areas. It employs its own power, a crystal mixer, and two tubes, a 6AF4 and a 6J6. Operates on 110-115 volts AC. The 6J6 is used in a balanced push-pull amplifier circuit and in the converter I.F. The converted signal is then boosted and fed to the TV receiver. The booster is slug tuned and has a 75-300 ohm input and output. Provision for built in UHF antenna. Very simple to install.



ONLY
\$35.70

DON'T DISCARD THAT CRT

UNTIL YOU'RE SURE THAT IT'S DEAD. FIND OUT WITH THE NEC-INTENSITOR.



- Tests all TV picture tubes
- Automatic testing for shorts
- No extra power supply needed
- Shows hot tube shorts
- Checks tube quality in set or out
- Light and portable

YOUR PRICE **\$8.95**

**UHF IS HERE AND EDLIE HAS IT!!
VEE-D-X ULTRA Q-TEE**



Net
\$8.37

One antenna for both VHF and UHF. The Ultra Q-TEE is by far the most important antenna ever perfected. It solves one of TV's biggest problems by combining both VHF and UHF (all-channel 2-83) into a single antenna using a single transmission line. The Ultra Q-TEE employs eight patented printed circuit band reject filters that isolate the VHF and UHF portions of the antenna.

**VEE-D-X ALL CHANNEL Q-TEE
THE BEST ANTENNA THAT MONEY CAN BUY**

The outstanding new feature, patented Electronic Channel Separators, plus amazing, newly engineered all-channel power give the Q-TEE better gain and directivity, higher front to back ratio, increased mechanical strength and better appearance. Light in weight the Q-TEE has rugged VEE-D-X pre-assembled construction. Single Bay for primary areas; 2-stack array for near fringe areas; 4 stack array for ultra fringe areas. The Q-TEE's pronounced directivity minimizes co-channel interference and results in less noise pick-up since signals off the side and back are rejected to a much greater degree than in conical antennas.




Single
\$5.44

2 bay **\$11.49** 4 bay **\$24.34**

\$\$\$

MONEY SAVER KITS FROM EDLIE ELECTRONICS


\$\$\$

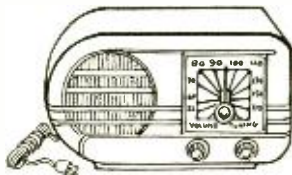

5 TUBE AC-DC SUPERHET KIT

Kit #1—Five Tube superheterodyne kit, A.C.-D.C. contains all components required to construct this latest design, highly sensitive superheterodyne broadcast receiver complete with black bakelite cabinet (excludes wire **\$7.95** and solder) Price

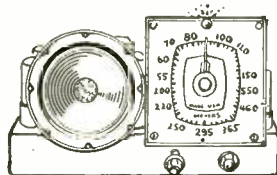Extra for a kit of 5 tubes (12AT6, 12BA6, 12BE6, 35WA, 50C5). Price **\$3.25.**



6-TUBE KIT

Kit #2—A low-priced 6 TUBE KIT designed for high sensitivity, excellent selectivity and good tone quality. Uses 25L6, 25Z6, 6SQ7, 6SA7, 6SK7, 6SK7 in an easily constructed circuit. The 6 Tube Kit is shipped with all parts, including punched chassis, resistors, condensers, coils, sockets, PM Speaker, hardware, etc.

And at a closeout price of only (less tubes and cabinet) **\$6.95**

Extra for matched set of six tubes for kit **\$3.25**

**Electronic Code Practice
Oscillator & Blinker Kit
AC/DC or Battery Operated!**

Kit #3—One of the most practical Code Practice Oscillators ever designed, yet one of the simplest to build and operate. Can be used with any number of headphones.

Adjustable Pitch Control—Any type of headphone can be used. No warmup time—ready to operate instantly. Simple and safe to operate. Operates anywhere—with AC or DC power, or from a 90 volt Miniature Battery. Learn Blinker Code with flashing light. Blinker can be used as signaling device. International Morse Code included.

Kit each **\$1.95** Assembled **\$2.95**

Kit #4—Basic 1 tube training kit. Simple to construct complete with all parts one tube and headset diagrams and instructions included. Use 1-354 tube and a 67½ volt Battery. Price— **\$3.95**

Kit #5—2 tube Amplifier Kit complete with 50L6, 35Z5, and 4" PM to convert Kit No. 1 to a 3 tube set for loud-speaker operation **\$4.95**

THREE TUBE PHONO AMPLIFIER

Not a Kit!
An assembled unit ready for installation using tone and volume control and six feet of rubber cord **\$2.95**

(Not including Tubes)
With Complete Set of Tubes **\$3.95**

PHONO OSCILLATOR

Not a Kit!
Wireless phono oscillator transmits recording for crystal pickups or voice from carbon mike through radio without wires. Can also be used as an intercom by using P.M. speaker as mike. Price (excluding **\$2.95** tubes)
With Complete Set of Tubes **\$3.95**

Satisfaction guaranteed on all merchandise. All prices subject to change without notice.

WRITE FOR FREE CATALOG

EDLIE ELECTRONICS • 154 Greenwich St. • New York 6, N. Y.

A. Fig. 1 shows a simple high-cut type of tone control. The 470,000-ohm grid resistor in the 6V6-GT circuit is replaced with a 500,000-ohm tone-control potentiometer with a .005-.01- μ f

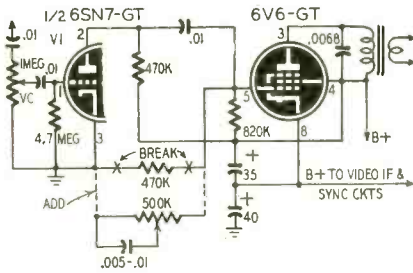


Fig. 1—A top-cutting tone control.

capacitor connected between the arm and ground. The 470,000-ohm fixed resistor must be removed since it is replaced by the resistance of the potentiometer.

The diagram in Fig. 2 is a more elaborate circuit which permits individual control of bass and treble notes.

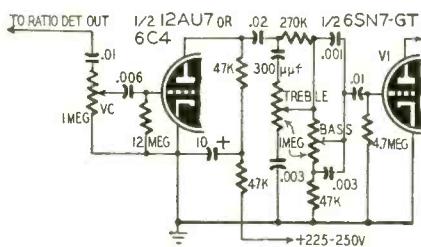


Fig. 2—Complete bass-treble control.

An extra triode stage is required to compensate for the insertion loss of the tone-control networks. You can mount the 6C4 on or under the chassis or you may replace the 6C4 vertical oscillator with a 12AU7 and use the remaining triode section as in Fig. 2.

YAGI ANTENNA PROBLEM

? I have single-channel, 300-ohm Yagis for channels 4, 5, 7, and 9. I would like to stack the high-band antennas and connect them to one lead-in and the low-band antennas to another. How should I space the antennas and what type of stacking bars should I use? What spacing should I use between the high- and low-band stacks?—R. T., St. Joseph, Mich.

A. Although the Yagis are single-channel models, you will probably find that all of them have considerable signal pickup on adjacent channels. For this reason, it may not be advisable to stack them and use a common transmission line. You may have interaction between the antennas which will result in reflections and ghosts. On the other hand, stacking may result in a gain of 2-3 db over a single antenna.

The spacing between the antennas in either pair should be approximately one-half wavelength at a frequency midway between the low-frequency end of the lower channel and the high-frequency end of the higher one. The low-band antennas should be spaced 78

ANOTHER *Brach* FIRST!

BRACH UNIVERSAL MODEL 482

the **ONE** Indoor Antenna
for **ALL** TV Channels!

VHF SWITCHES TO

UHF IN A JIFFY!

Locks in base at 90° angle for UHF

\$5.95
List

Only the Brach Universal Indoor Antenna 482 provides dual-purpose reception for all VHF and UHF channels. Revolutionary new design—an eccentric rotating joint in the base—permits switching from a vertical V for VHF to a locked horizontal V position for UHF. Available for immediate delivery!

CHECK THESE FEATURES

- Smooth ball-socket action and spring tension insure fixed location of elements and tight contact.
- Elements extended for VHF . . . fully retracted for UHF.
- VHF and UHF position markings are molded into base.
- Base is finished like fine furniture and is weighted to prevent tipping.

Write for details and prices. Technical article "How to Select UHF Antennas" also available.

MANUFACTURING CORP.
Quality-Engineered TV & Radio Products

200 CENTRAL AVENUE, NEWARK 4, NEW JERSEY

ANOTHER OUTSTANDING JOBBER
PENINSULA TELEVISION & RADIO SUPPLY
881 South First St.
San Jose, Calif.

HAS THE SENSATIONAL NEW
EICO 470-K 7" SCOPE KIT
IN STOCK!

\$79.95
3% higher on West Coast

ANOTHER OUTSTANDING JOBBER
VAN SICKLE RADIO SUPPLY CO.
1320 S. Calhoun St.
Fl. Wayne, Indiana

HAS THE SENSATIONAL NEW
EICO 470-K 7" SCOPE KIT
IN STOCK!

\$79.95

LEARN WITH "AMECO" COURSES
Simple, Low Cost, Home-Study Courses prepare you to pass F.C.C. Code and Theory license examinations.

BECOME A RADIO AMATEUR

Write for details and receive free sample F.C.C.-type questions and answers for all amateur examinations.

FREE →

AMERICAN ELECTRONICS CO.
1203 Bryant Ave. (Dept. RE-3), New York 59, N. Y.


ARKAY

world's finest radio kits

Write for free Brochure

RADIO KITS, INC., 120 Cedar St., N. Y. 6

HOTTEST TV PACKAGE for "ONE BUCK"!

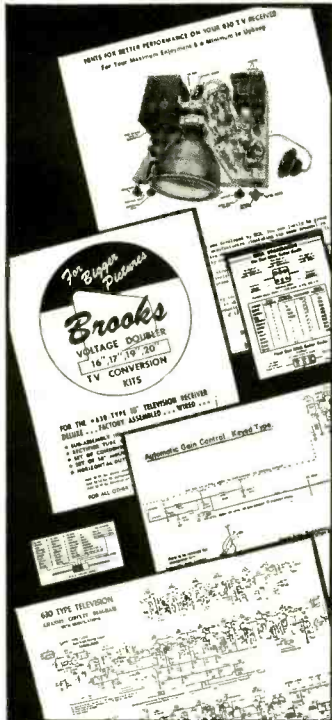

- Hints for Better Pictures on 630TV
- 630TV Diagram with Modifications
- Illustrated TV Conversion Manual
- Pulse Keyed AGC Circuit Diagram
- RMA Resistor & Mica Code Charts

All for only
\$1.00
Postpaid

EVERYONE INTERESTED IN TELEVISION should own this TV literature package . . . The information will be found useful on any make TV set. It's different and right to the point. It carries instructions that are up to the minute and not yet found in expensive text books. Indispensable to the TV technician yet easy enough for anyone with even a limited knowledge of TV to understand and follow.

SAVE MONEY ON REPAIRS—Important common occurrences are carefully analyzed and corrective procedures are suggested. You are told what to do—WHEN THE RECEIVER FAILS TO OPERATE, WHEN THERE ARE GHOSTS, INTERFERENCE, NO PICTURE, PICTURE FOLD-OVER, NO RASTER, PICTURE BLOOMS, DISTORTED PICTURE, PICTURE ROLLS, NO SOUND, DISTORTED SOUND, CORONA EFFECTS, ETC. PICTURE TUBE ASSEMBLY and PATTERN ADJUSTMENTS are outlined in detail (the ion trap adjustment caution may save you the price of a new picture tube). THE HORIZONTAL SYNC, RCA TUNER and STANDARD TUNER step by step adjustments alone are worth many times the cost of this package.

TUNING GUIDANCE and ANTENNA ADVICE will enable you to enjoy peak performance at its best. The HIGH VOLTAGE #630 CIRCUIT DIAGRAM, AGC DIAGRAM, RESISTOR & MICA CODE CHARTS need no emphasis as to their usefulness.

Brooks LIFE-SIZE TV Instructions for building any #630 TV RECEIVER only \$2.49 Postpaid

Brooks CASCODE MANUAL. How to install Cascode Tuner in any make TV set only 50¢ Postpaid

"HIGHLIGHTS of TV OFFERS for 1953" included with each order or on request.

BROOKS RADIO & TV CORP. 84 Vesey St., New York 7, N. Y.

LEARN
**Television-Radio
Electricity**
REFRIGERATION-ELECTRONICS
IN THE GREAT SHOPS OF **COYNE**

**TRAIN QUICKLY! OLDEST, BEST
EQUIPPED SCHOOL of ITS KIND in U.S.**

Come to the Great Shops of Coyne in Chicago. Get practical training in opportunity fields—TELEVISION-RADIO—ELECTRICITY—ELECTRONICS—vital in Defense Program. Prepare now for a better job in industry or better service rating.

Approved for Veterans

Finance Plan—Enroll now, pay most of tuition later. If you need part-time work to help out with living expenses while at Coyne, we'll help you get it. Special tuition plan for men of Draft Age.

FREE BOOK Clip coupon for Big Free Illustrated Book. No salesman will call. Act NOW.

B. W. Cooke, President
COYNE SCHOOL A TECHNICAL TRADE INSTITUTE CHARTERED NOT FOR PROFIT Established 1899 500 S. Paulina, Chicago

**ELECTRICITY ★ TELEVISION
RADIO ★ REFRIGERATION ★ ELECTRONICS**

B. W. COOKE, Pres.
COYNE School
500 S. Paulina St., Chicago 12, Ill. Dept. 33-81H

Send FREE BOOK and full details on:

TELEVISION-RADIO ELECTRICITY

NAME.....
ADDRESS.....
CITY..... STATE.....

CORNISH
Wires
have been identified with **QUALITY** since the swaddling days of Radio. The era of Television finds them, more than ever, the Serviceman's Friend.

**GLUTTONS for
PUNISHMENT**



Preferred for their
**Absolute Uniformity.
Superior Qualities
and
Ultimate Economy**

CORNISH WIRE COMPANY, INC.
50 Church Street. New York 7, N. Y.


inches apart and the high-band antennas 32 inches apart. Use 425-ohm stacking bars. You can use standard open-wire TV transmission line or 3/8-inch tubing spaced 6 1/4 inches apart.

The high- and low-band arrays should be spaced any convenient distance apart greater than 45 inches.

TV MATCHING PADS

? I would appreciate details on constructing resistive matching pads for connecting several receivers with 72-ohm antenna inputs to the 72-ohm output of a booster.—O. R. B., Greensboro, N. C.

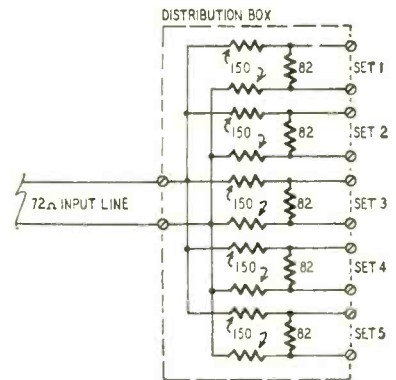A. The diagram shows a resistive pad for connecting five 72-ohm receivers to a common 72-ohm signal source. Val-



ues of the series and parallel resistors depend on the number of receiver outlets. Refer to the table for values for a different number of receiver outlets.

No. of Sets	TABLE	
	Series Resistors (ohms)	Parallel Resistors (ohms)
2	56	100
3	100	100
4	120	82
5	150	82
6	180	82
7	240	82
8	270	82

TRANSMITTING TUBE TESTS

? I service industrial and medical equipment which uses transmitting-type tubes. Since a defective component can quickly ruin a new tube substituted for the suspect, I am looking for details for testing tubes of these types. Can you supply a diagram of a tube checker or details on setups for testing industrial and transmitting tubes?—W. F. M., Oakland, Calif.


A. There are a number of procedures for testing transmitting and industrial tubes. One method is to run a series of characteristic curves and compare these curves with those given in manufacturers' data on the tube being tested. Another method is to use a C-R tube curve tracer (see "Versatile Tube Checker," RADIO-ELECTRONICS, August, 1951) which enables the operator to instantly compare a tube of unknown

SPECIAL THIS MONTH... 10% EXTRA OFF

On a COMBINED PURCHASE—Of a #630 TV CHASSIS or KIT with a MANHATTAN CABINET and any size PICTURE TUBE

#630 SUPER DELUXE 31-TUBE TV KIT

OPERATES ALL 16" TO 24" PICTURE TUBES

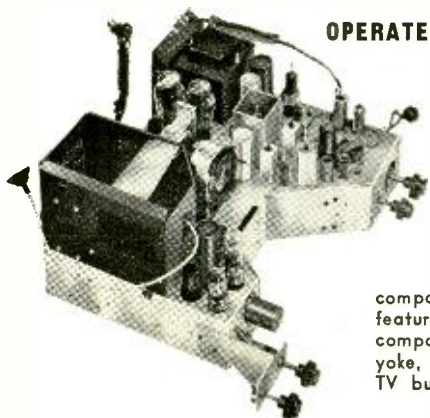

Engineered in strict adherence to the genuine RCA #630, plus added features ★ ★ ★ ★ ★

NOTHING BETTER AT ANY PRICE!

- Standard Cascode Turret Tuner for DX
- Cosine 70° Deflection Yoke for Definition
- Original 630 Synch. Chain for Stability
- 16 KV for Clarity and Brilliance
- Fast Action Pulse Keyed AGC
- Large Concert-tone 12" PM Speaker

COMPLETE SET OF PARTS including the components of the STANDARD KIT plus added features, more tubes, doubler components, AGC components, Cascode tuner, Cosine 70° deflection yoke, 12" speaker, etc., and the Brooks LIFE-SIZE TV builder instructions (less CRT & wire)

only... **\$119.44**

#630 SUPER DELUXE 31-TUBE TV CHASSIS KNOWN MANUFACTURER

Licensed under RCA patents

COMPLETE READY TO PLAY including all tubes, 12" speaker and CRT mounting brackets. No charges for extras of any kind. Each set is factory aligned and air tested. All parts are guaranteed 3 months. Our booklet "HINTS FOR BETTER PERFORMANCE ON YOUR #630 TV RECEIVER" is supplied with each set. You best buy at

\$167.97 (less C.R. Tube)

FINEST STANDARD GUARANTEED PICTURE TUBES

Most desirable 4 sizes . . . BRAND NEW in Sealed Cartons—With a Full Year Guarantee

17" Rect. \$29.63	20" Rect. \$39.74	21" Rect. \$44.68	24" Round \$79.49
-------------------	-------------------	-------------------	-------------------

SUPER DELUXE

#630 TV BASIC PARTS KIT

- PUNCHED & DRILLED CHASSIS PAN
- BRACKET & SHIELD KIT (18 items)
- VIDEO & I.F. KIT (19 items)
- POWER TRANSFORMER #201T6
- VERTICAL OUTPUT TRANSFORMER
- VERTICAL BLOCKING TRANSFORMER
- FLYBACK TRANSFORMER #211T5
- FOCUS COIL, 470 ohms #202D2
- COSINE DEFLECTION YOKE 70°

All for Only... **\$39.49** including LIFE-SIZE TV builder instructions

#630 TELEVISION PARTS

PUNCHED CHASSIS PAN, cadmium plated	\$ 4.87
STANDARD CASCODE TUNER compl.w/tubes	22.49
ESCUTCHEON PLATE, for tuner	.69
COMPLETE SET OF KNOBS, incl. decals	1.34
COMPLETE SET OF KNOBS, gold incl. decals	2.49
POWER TRANSFORMER, 295ma.	9.97
VERTICAL OUTPUT TRANS.	2.69
VERTICAL BLOCKING TRANS.	1.32
HORIZONTAL OUTPUT TRANS.	2.98
HORIZONTAL OUTPUT TRANS.	3.98
FOCUS COIL, 247 ohms.	2.29
FOCUS COIL, 470 ohms.	3.42
DEFLECTION YOKE, 60°	2.97
COSINE DEFLECTION YOKE, 70°	3.98
HORIZONTAL DISCRIM. TRANS.	1.49
FILTER CHOKE, 62 ohms	1.47
WIDTH CONTROL COIL, keyed AGC	.79
ION TRAP BEAM BENDER, (single) 203D1	.79
ION TRAP BEAM BENDER, (double) 203D3	.98
AUDIO OUTPUT TRANSFORMER (6K6)	.69
HV RECTIFIER, SOCKET ASSEMBLY, double	1.37

Modernize a #630 or any TV Set

With a New

STANDARD CASCODE TUNER

For better all around performance

Complete with tubes, and Brooks CASCODE MANUAL with step by step instructions **\$22.49**

PULSE KEYED AGC KIT


Finest, most accurate and the easiest Kit to install in a #630 or in any other make TV receiver. Improves performance, eliminates airplane flutter and picture jumping and insures a steady picture on all channels.

COMPLETE SET OF PARTS Including 6AU6 tube & Instructions **\$4.59**

#630 PARTS • IN SETS

TV WIRE & SOLDER KIT, for any Set	\$1.49
630-KIT, screws, nuts, rivets, washers, etc.	1.69
VIDEO AND I.F. KIT, 19 items	7.84
AGC KIT, complete with instructions	4.59
VARIABLE CONTROL KIT, 9 controls	5.83
CARBON RESISTOR KIT, 107 resistors	6.98
WIREWOUND RESISTOR KIT, 4 resistors	2.31
BRACKET AND SHIELD KIT, 18 items	8.63
ELECTROLYTIC CONDENSER KIT, 6 cond.	4.28
TUBULAR CONDENSER KIT, 38 condensers	7.37
CERAMIC CONDENSER KIT, 28 condensers	3.37
MICA CONDENSER KIT, 11 condensers	1.38
COMPLETE SOCKET KIT, 25 sockets	1.57

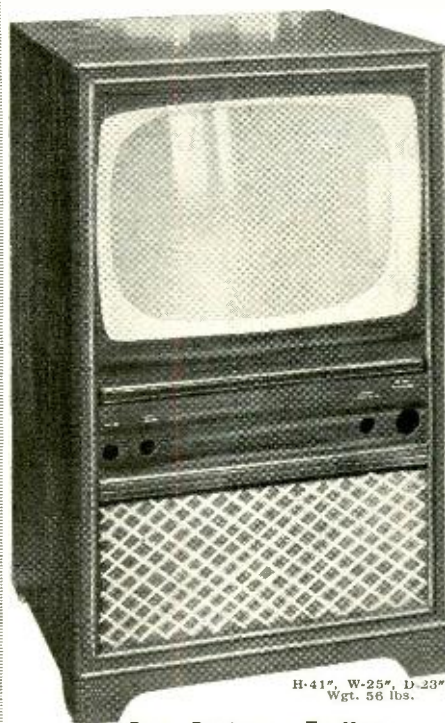The MANHATTAN CUSTOM-BUILT CABINET For #630 AND ALL OTHER TV SETS



H-41", W-25", D-23", Wgt. 56 lbs.

From Factory — To You

The MANHATTAN has everything

STYLE . . . QUALITY . . . PRICE

STYLED—to blend with any furniture setting, *it's a best seller.*

QUALITY—constructed of genuine mahogany or walnut, handrubbed to a fine piano finish.

LOW PRICE—made possible by our controlling interest at the factory.

THE MANHATTAN—Takes any TV set. The knob-panel and shelf are either drilled for a #630 chassis, or left blank for any other TV set. The picture tube cutout is any size you order (12½" to 21") and the mask and safety glass are included.

EVERYTHING NECESSARY—for an easy, perfect installation is included—assembly instructions, picture tube mounting brackets, hardware, decals, backboard, and as a finishing touch we even include a backup for recessing the picture tube neck.


EACH CABINET—is carefully packed in an air cushioned carton & shipped F.O.B. factory, N. Y.

\$59.37

(bland 10% extra)

Also available for 24" C.R.T. \$86.22

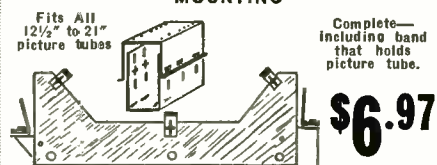UNIVERSAL Picture Tubes MOUNTING BRACKETS



Complete—including band that holds picture tube. **\$6.97**

BROOKS RADIO & TV CORP., 84 Vesey St., Dept. A, New York 7, N.Y.

TELEPHONE
COrtland 7-2359

**GREATEST NEWS
IN TV HISTORY!**
THE SENSATIONAL NEW
**RCP Model 8873
SERVISHOP
TV - FM - AM**



Never before has there been a Single instrument combination to match this!

- CATHODE RAY TUBE TESTER
- CR TUBE REACTIVATOR
- TUBE TESTER
- VACUUM TUBE VOLTMETER
- AM SIGNAL GENERATOR
- FM SIGNAL GENERATOR
- AF SIGNAL GENERATOR

This unit includes:

An up-to-date tube tester for testing and re-juvenating Cathode Ray Tubes as well as testing all modern, miniature, noval base and sub-miniature tubes. Uses the speedy Rollindex Tube Chart. A complete 17 range VTVM with exceptionally high input impedance (25 megohms). Check AC and DC volts with negligible loading of circuit. Accuracy $\pm 3\%$ DC, $\pm 5\%$ AC. Measures ohms from 2 to 1000 megohms. Includes High-Voltage Probe. The Signal Generator is a fixed frequency AM, FM generator and Audio Oscillator.

Advanced engineering results in the fine performance of the Model 888 combination Tube Tester-Reactivator and VTVM with the Model 730 AF-AM-FM Signalizer.

Complete with tubes, batteries, leads, etc. in beautifully finished oak portable case. Size 18 1/2" x 12 3/4" x 5 1/4". Weight 18 pounds.

\$139⁹⁵
NET

MAIL COUPON NOW FOR

FREE CATALOG

RADIO CITY PRODUCTS CO., Inc.
Dept. RE-3, 152 West 25th St., N. Y. 1, N. Y.

Please send me a copy of your new 1953 colorful, fully illustrated catalog featuring the top-quality RCP instrument line.

NAME.....

ADDRESS.....

CITY.....STATE.....

quality with a standard by comparing their traces on the curve tracer screen.


The May-June, 1951, issue of *G-E Ham News* is devoted almost entirely to procedures for testing 23 popular transmitting tubes including the 813, 4D21, 211, 807, 810, 811, and 2E26.

Copies of the May-June, 1951, issue of *Ham News* can be obtained from Tube Division, Bldg. 267, General Electric Co., Schenectady 5, N. Y.

ADDING A SHORTWAVE BAND

I want to convert a Fada model 740 5-tube, a.c.-d.c. broadcast receiver to a 2-band set for use on the broadcast and 6-15-mc bands. This can be done either by hand-switching or using plug-in coils. The latter is preferable if I can get coils about the size of a 50B5 tube. This will permit mounting the coil socket between the 12BE6 and the front of the chassis. Can you help with this problem?—R. F. G., Washington, D. C.

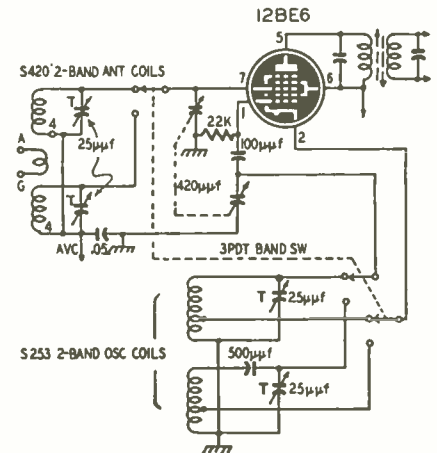A. If you want to use plug-in coils, we suggest that you purchase miniature antenna and oscillator coils for the bands that you want to cover. The coils should be about 1/2-inch diameter and not more than 2 inches long.



The present tuning capacitor has a 465-µf section for the antenna and a 184-µf cut-plate section for the oscillator. Replace this tuning capacitor with a unit of approximately the same over-all dimensions. The maximum capacitance of each section should be 420 to 467 µf.

Sockets for the plug-in coils may be installed on a metal bracket fastened to the right side of the chassis close to the tuning capacitor. The 25-µf trimmers and the oscillator padders can be mounted on top of or inside the small plug-in coil forms.

Band-switching coils will probably be just as easy to install and much more convenient for the operator. You can purchase 2-band coils which are about the same size as the broadcast oscillator and antenna coils that you are now using. You can use these as replacements and install a small switch to select the band that you want. The diagram shows how Stanwyck S-420 antenna and S-253 oscillator coils may be added to the set to give coverage on the broadcast and 6-18-mc bands. END

RADIO ENGINEERING DEGREE IN 27 MONTHS

Intensive, specialized course including strong basis in mathematics and electrical engineering, advanced radio theory and design, television, Modern lab. Low tuition. Self-help opportunities. Also B.S. degree in 27 months in Aeronautical, Chemical, Civil, Electrical, and Mechanical Engineering. G.I. Gov't approved. Enter March, June, September, December. Catalog.

INDIANA TECHNICAL COLLEGE
153 E. Washington Blvd., Fort Wayne 2, Indiana

TUBES

All receiving and special purpose types. Real values that will save you 10 to 70%. Call or write today for special price list. State type & quantity for additional discount.

METROPOLITAN SUPPLY CORP.
1133 Broadway, New York 10, N. Y. - CH 3-1105

Every RADIOMAN can use these SERVICE HINTS!

Valuable Manual Yours—FREE Write today, no obligation. **FEILER ENGINEERING CO., Dept. 3RC3-1** 8026 N. Monticello Ave., Skokie, Ill. (Suburb of Chicago)

Every page of "How to Simplify Radio Repairs" is packed with on-the-bench, practical ideas.

BUILD 'EM YOURSELF

it's fun...



it's easy...



Build your own radio, AM-FM tuner, phono pickup amplifier, disc recorder, power supply, public address amplifier and a host of other equipment at a fraction of the cost of assembled units. The new **MEISSNER "HOW TO BUILD"** Manual shows you how, with simple step-by-step instructions, fully illustrated with pictorial wiring and assembly diagrams and scores of photos. **IT'S EASY AS ABC.** The popular new 2-CW novice transmitter kit is illustrated above, also the T-2BK trainer kit. Both are included in the new manual.

A separate section on basic theory, tells you all about the construction and operation of different radio parts, in simple easy to understand language.

Whether you know nothing about radio, or are an advanced student or even if you are an instructor, the "HOW TO BUILD" Manual is worth its weight in gold. 160 packed-full pages written by the engineering staffs of THORDARSON and MEISSNER,

two great names in radio and electronics. Previous editions ran into tens of thousands of copies. This NEW enlarged issue is the best ever published. See your radio parts distributor or use coupon.

"HOW TO BUILD" Manual, # 53-1, Price \$1.50



MEISSNER
THORDARSON-MEISSNER
Dept. BL • Mt. Carmel, Illinois

Enclosed is \$1.50. Please send "HOW TO BUILD" Manual. THORDARSON-MEISSNER pays the postage.


Name.....

Address.....

City.....State.....

STEWART-WARNER TV SETS

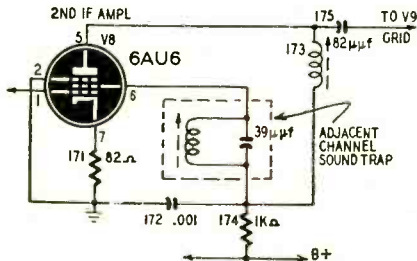Interference caused by the sound carrier of a lower frequency adjacent channel can be eliminated in the 26-tube chassis by installing an adjacent-channel sound trap. The trap (part No. 520131) is installed in the screen circuit of the second i.f. amplifier stage. The modified circuit is shown in the diagram. The installation can be simplified by following the procedure outlined below.



How the adjacent-channel sound trap is placed in 26-tube Stewart-Warner Sets.

1. Mount the trap coil in the hole directly in front of tube V9 (the 6AU6 third i.f. amplifier). (On the 9103, 9104, 9105, 9106, and 9108 series receivers, drill a $\frac{5}{16}$ -inch mounting hole for the trap.) Insert the coil from the under side of the chassis and push it through until the mounting clip snaps into place.

2. Disconnect resistor 174 (1,000 ohms) from pin 6 of V8, the second i.f. amplifier.

3. Carefully disconnect capacitor 172 (.001 μf) from the chassis ground and from pin 6 of V8.

4. Disconnect the second i.f. coil 173 from pin 6 of V8.

5. Connect one terminal of the trap coil directly to pin 6 of V8.

6. Connect the other end of the trap coil to the end of the second i.f. coil which was previously disconnected (in step 4.)

7. Connect the open end of resistor 174 to the junction of the second i.f. and the trap coils.

8. Connect one end of capacitor 172—removed in step 3—to the junction of the two coils. Ground the other end to the chassis at a point close to the second i.f. coil.

To align the circuit, rotate the trap-tuning adjustment until the stem of the slug is as far out as possible. Use the fine tuning control to tune in a normal picture. *Do not touch this control during the rest of the adjustment procedure.*

Then connect a standard signal generator through a 330- μf capacitor to point Q on the r.f. tuner and a v.t.v.m. across the video detector load resistor 196. (Refer to the manufacturer's diagram for proper connections.) Set the signal generator accurately to 28.25 mc. Adjust the adjacent-channel sound trap for *minimum* reading on the meter.

In fringe areas, it may be necessary to watch the screen and touch up the setting of the trap to reduce the interference to a minimum.—*Stewart-Warner Service Bulletin*

FM OSCILLATOR DRIFT

Excessive frequency drift in Motorola 1949, 1950, and 1951 FM receivers may be caused by a defective or incorrect temperature compensating capacitor in the FM oscillator circuit. This capacitor, located on the FM oscillator inductor assembly, has a value of 85 μf and a negative temperature coefficient of either .000750 μf per μf per degree Centigrade (N750), or .001500 μf per μf per degree Centigrade (N1500). Table model receivers, which are tightly enclosed, generate more heat and require more compensation than relatively open consoles.

If frequency drift is objectionable during the warmup period, change the compensating capacitor. It may not have the correct temperature coefficient. If the oscillator drift requires retuning to a lower frequency on the dial, the compensation is too great. Compensation is too small if the set must be retuned to a higher frequency on the dial during warmup.

Replacement capacitors may be disc or tubular types. On the latter type, the temperature coefficient is indicated by the end dot. It should be either purple (for 750 parts per million) or orange (for 1,500 parts per million.). Disc type capacitors are marked directly in parts per million (PPM).

Motorola's *Service and Installation Bulletin No. 3* (dated June 19, 1952), available from Motorola distributors, contains a printed table listing recommended compensating capacitors for all 1949, 1950, and 1951 Motorola FM receivers. This table should be taken as final authority for replacement capacitors, even though it may not agree in all instances with parts lists in the service manuals.—*Motorola Service Dept.*

OLYMPIC DX-621 COMBINATION

In the early models, hum may be heard occasionally on the AM-FM or PHONO positions. This can be eliminated by rerouting and shielding the three leads connected to the tone control-power switch. Disconnect the three leads from the a.c. switch and reroute them to run directly from the rear of the chassis to the switch. Cut off excess length of leads. Shield each lead with one 7 $\frac{1}{2}$ -inch length of spiral shielding (part SD-2340) and insulate with an 8-inch length of sleeving (part IT-1932). Ground rearmost end of shielding to the chassis. Connect a short jumper from the center lug (ground) of the three-terminal tie post under the record changer to the adjacent lug on which the shield braid of the phono pickup lead is soldered.

In these sets, bass response is normal when the set is operated on a hard-surfaced floor. On carpeted floors, low-frequency response may not be satisfactory. To increase it, mount a 3 $\frac{1}{2}$ x 10 $\frac{1}{2}$ -inch piece of $\frac{1}{8}$ -inch tempered Masonite to cover the hole in the speaker baffle next to the speaker. Mount a 17 $\frac{1}{2}$ x 16 $\frac{1}{2}$ -inch piece of the same material under the speaker on the shelf inside the speaker compartment.—*Olympic Television Service Bulletin*

PHYSICISTS
AND
ENGINEERS

ATTENDING THE

I.R.E.

CONVENTION

NEW YORK CITY

MARCH 23-26...

Inquiries are invited regarding openings on our Staff


- ▶ RADAR LABORATORIES
- ▶ GUIDED MISSILE LABORATORIES
- ▶ ADVANCED ELECTRONIC LABORATORIES
- ▶ ELECTRON TUBE LABORATORIES
- ▶ FIELD ENGINEERING DEPARTMENT

For the convenience of those attending the I.R.E. meetings and Radio Engineering Show, members of the Laboratory Staff will be available for interviews at the Convention hotel. For appointment telephone Hughes New York office, LACKAWANNA 4-9350.

HUGHES

RESEARCH AND DEVELOPMENT LABORATORIES
Scientific and Engineering Staff
CULVER CITY, LOS ANGELES COUNTY, CALIFORNIA

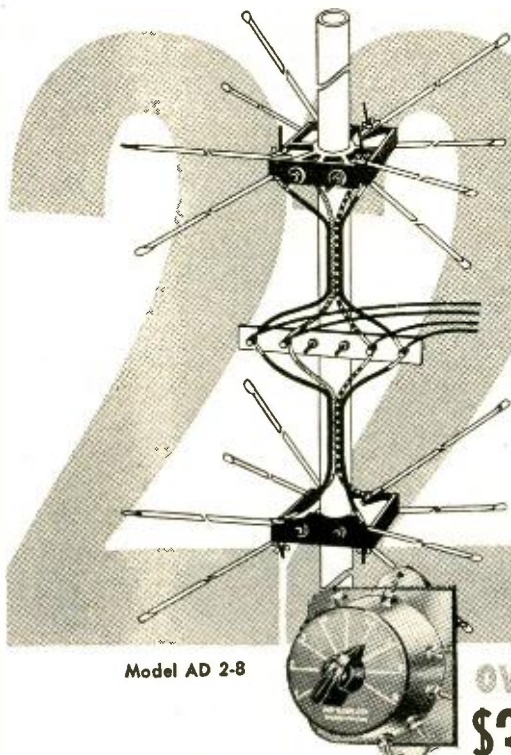Assurance is required that relocation of the applicant will not cause disruption of an urgent military project.



Model AD 2-8

World's most powerful TV Antenna!

over a tuned dipole

\$36⁵⁰ LIST PRICE

Includes Stacked Antenna Array, 9 Position Switch, Completely Wired Stacking Harness, A.I.M.—Automatic Impedance Matching Coupler.

Individually packaged with complete instructions.

- Guaranteed 10 times more powerful than stacked 10 element Yagis.
- Receives channel 2-83 from all directions without a rotor.
- Broadband UHF-VHF and FM, motorless all direction reception.
- Pat. # 2,585,670—2,609,503—2,625,655 others pending.
- All aluminum flip-out assembly.

The only TV antenna that instantly beams the television set directly to the signal without a rotor. This antenna brings strong signals from all directions to weak signal areas instantly . . . with a flick of the nine position switch located near the television set.

MONEY BACK GUARANTEE
To outperform any present day antenna array using a rotor motor, including stacked 10 element Yagis, 4 bay conicals, fans, double V's, etc.

Available at local jobbers or write for name of nearest representative

ALL CHANNEL ANTENNA CORP.
70-07 Queens Blvd., Woodside 77, N. Y. • Hickory 6-2304

CRYSTAL CARTRIDGE HINT

The output of a crystal pickup cartridge varies with temperature. Its output is higher at room temperature than at lower temperatures. Do not immediately reject a cartridge because of low signal output if it has been in cold storage or subjected to low temperatures. Wait until it has warmed up before passing final judgment.—*RCA Radio Phono Television Service Tips*

SPARTON 5006X AND 5007X

Reduced sensitivity and low audio output were encountered in the first production run of the 25TK10 TV chassis using a 6AX5 low-voltage rectifier for the 140-volt B-supply line.

The minimum allowable voltage on this line is 130. It has been found that the internal resistance of the 6AX5 increases enough to drop the voltage to 110-120 after the set has been operated for as little as 50 hours.

It is recommended that the 6AX5 be replaced with a 6X5 in cases where the voltage on the 140-volt line drops below 130. The 6AX5 has been replaced with a 6X5 in later production runs.—*Sparton Service Division Bulletin*

STANDARD COIL TUNER

Loss of sensitivity on all channels and split tuning on high-band channels have been encountered on several sets using Standard Coil type TV303 tuners.

In all cases, the trouble was caused by a break at the terminal on the converter plate coil.

The lead was resoldered to restore normal operation.—*A. D. Marikle*

PHILCO TV PRECAUTION

Always disconnect the outside antenna lead-in or pull the line cord from the outlet before replacing the back on Philco TV sets which use a tapered-line antenna circuit. Failure to observe these precautions may cause serious damage to the antenna input assembly.

If the antenna happens to be a folded-dipole type with a metal boom and a grounded mast, accidental contact between the high side of the power line and the chassis will cause the tapered-line assembly to become burned out.—*C. E. Wyatt*

ZENITH TV SETS

Smeary pictures in Zenith TV sets using the 24H20 chassis with interference in the form of horizontal lines, have, on several occasions, been traced to an open 10- μ f decoupling capacitor in the plate circuit of the 12AT7 noise limiter. The trouble clears up when the capacitor is replaced.—*Jim Cavesano*

PHILCO 45-131

If the set is dead, the trouble is most likely traceable to an open circuit in the primary of the output transformer which is mounted underneath at the back of the chassis. If the replacement does not fit the holes used to mount the original unit, you can probably use one or more of the holes which you will find close to the position occupied by the original component.—*Howard Simpkins*

END

WANTED

WE NEED YOUR SURPLUS ELECTRONIC EQUIPMENT

WE PAY TOP \$\$\$ FOR:

- ★ RADIO RECEIVERS
- ★ TRANSMITTERS
- ★ ARC-1
- ★ ARC-3
- ★ ART-13
- ★ CONTROL BOXES
- ★ INDICATORS
- ★ CLAMPS
- ★ PLGS
- ★ CORDS
- ★ RELAYS
- ★ TELEPHONE MATERIALS
- ★ AN CONNECTORS
- ★ WE BUY ANYTHING!

Write, Wire today! Tell us what you have.
TALLEN CO., Inc., Dept. RE
159 Carlton Ave., Brooklyn 5, N. Y.

LEARN CODE

No matter how difficult it has been for you to learn code before, I guarantee that you will memorize the Morse International Code in two hours or return method within 5 days and I will refund your money. Send one dollar for complete method. **NOTHING ELSE TO BUY!**

OTTO LUTHER, NEW PRESTON, CONN.

RADIO-ELECTRONICS is paying good rates on acceptance for original and unusual articles on audio, television, FM and AM servicing, as well as articles on industrial electronic equipment and applications. Send for a copy of our Authors' Guide. Address:

THE EDITOR
RADIO-ELECTRONICS
25 West Broadway, New York 7, N. Y.

TELEMATIC THE Professional LINE OF **CRT EXTENSIONS** MAKES SERVICING EASIER

Anode EXTENSION
CR-33.....3 ft
CR-33-6.....6 ft
Exclusive Non-Breakable Molded Ends


Socket EXTENSION
CR-35.....3 ft
CR-35-6.....6 ft
Exclusive One model for both Electrostatic & Electromagnetic CRT'S.

Yoke EXTENSION
CR-55.....3 ft
CR-55-6.....6 ft
Exclusive Leads pitched for Security

Free! Booklet on TV Interference. Just write.

TELEMATIC
ONE JOHANNESB. ST. • BROOKLYN 2, N. Y.

Now! HANDLE UP TO 90% OF TV TROUBLES

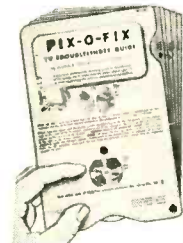

by the easy **PICTURE ANALYSIS METHOD!**

PIX-O-FIX TV TROUBLE FINDER GUIDE

By Ghirardi & Middleton

Only \$1.

Covers 24 common troubles identified by actual screen photos
• • • 190 possible causes of these troubles localized to receiver stage or section where they are most likely to occur.

• • • 253 step-by-step remedies for these troubles

• • • 4,500 words in CAUSE AND REMEDY section to show exactly what to do.

Cut hours of tedious TV troubleshooting to minutes! Make repairs twice as fast! Operation of Ghirardi's new PIX-O-FIX TV TROUBLE FINDER GUIDE is simplicity itself. Covers all TV receivers.

Just turn dial until actual TV screen photo appearing in PIX-O-FIX "window" matches distorted picture on set being repaired. PIX-O-FIX then gives you all possible causes for this trouble and just where in the receiver they are likely to be found. But that is only the beginning!

Step-by-step repair instructions follow. Components likely to be faulty are specified. Quick tests are outlined. PIX-O-FIX guides you every step of the way! Remember! PIX-O-FIX is NOT a "fix-it-yourself" gadget for consumers. It is a truly professional device for servicemen, apprentices and students—prepared by two of the nation's foremost service instructors—A. A. Ghirardi and R. G. Middleton.

MONEY BACK IF YOU'RE NOT SATISFIED!

Simply pin a \$1 bill to this ad. Mail with your name and address to the publisher. If not satisfactory, return PIX-O-FIX in 10 days and your \$1 will be refunded promptly. (Price outside U.S.A. \$1.25 same money-back guarantee).

Dept. RE-33, RINEHART BOOKS, Inc., Technical Div., 232 Madison Ave., New York 32, New York

G. W. Duckworth was named manager of the equipment sales field force of the RCA TUBE DEPARTMENT in a realignment of the company's equipment sales activities. At the same time, four veteran field representatives were made managers of newly created districts.



Left to right, rear: C. R. Klinger, J. W. Kirschen, L. D. Kimmel. Front: G. W. Duckworth and J. H. Mosher.

They are: J. W. Kirschen, Eastern district; C. R. Klinger, Western district; L. D. Kimmel, Central district; J. H. Mosher, Interdepartmental district.

William W. Taylor, formerly assistant sales manager of the Capacitor Division of the SANGAM ELECTRIC Co., Marion, Ill., was appointed sales manager. He succeeds John Giltner Twist who resigned to become a manufacturers' representative in Chicago. H. Laurence Kunz, general manager of the Division, was elected vice-president. He will continue as general manager of the Capacitor Division.

John H. Hauser joined HYTRON RADIO & ELECTRONICS Co., Danvers, Mass., as renewal tube sales manager, according to an announcement by John Q. Adams, vice-president in charge of sales. Mr. Hauser was formerly with Sylvania Electric.



J. H. Hauser

W. Walter Jablon was appointed vice-president in charge of sales of the DAVID BOGEN Co., New York City manufacturer of electronic equipment. He was formerly with Espey Manufacturing Co.



W. W. Jablon

Leon Golder joined CARBONNEAU INDUSTRIES, INC., Grand Rapids, Mich., as general sales manager. He was formerly chief of the Radio and Television Section, Electronics Division of the NPA. Prior to that he had been



L. Golder

ATR

Makes it easy to **DEMONSTRATE AND TEST D.C. APPARATUS FROM A.C. LINES**

"A" BATTERY ELIMINATORS
For DEMONSTRATING AND TESTING AUTO RADIOS
New Models . . . Designed for testing D.C. Electrical Apparatus on Regular A.C. Lines. Equipped with Full-Wave Dry Disc Type Rectifier, Assuring Noise-less, Interference-Free Operation and Extreme Long Life and Reliability.

NEW MODELS
NEW DESIGNS
NEW LITERATURE

ATR

"A" Battery Eliminator A-C D-C Inverters Auto Radio Vibrators
See your jobber or write factory

AMERICAN TELEVISION & RADIO Co.
Quality Products Since 1931
SAINT PAUL 1, MINNESOTA-U.S.A.

Find Out About These New **WEN** Products

The Better
**ELECTRIC
SOLDERING
GUN**

The
**EXTRA
LONG LIFE
TIP**

HEATS IN 3 TO 5 SECONDS—COOLS QUICKLY

- Better Designed
- Better Made
- Tips Rigid—Stay Tinned
- Easily Replaced



Underwriters' Approved

The 250 Watt electric soldering gun entitled to show this certification. Speaks well for the quality of the product and its safety. Users praise its balance, ease of handling, excellent performance.

NO DUTY CYCLE

Can be used almost constantly. Its excellent design and construction prevent overheating. Operating on 120 Volt AC, 60 cycle, the Wen Gun handles all soldering requirements 50 to 250 Watts.

A FINE PROFESSIONAL TOOL

Ideal for assembly, maintenance, service and repair. Retail for \$12.95 with discounts for quantities and to the trade. Individually boxed. Fully guaranteed.

EXPORT AGENTS, SCHEEL INTERNATIONAL, INC.—CHICAGO 18, ILL.

WEN PRODUCTS, INC.

5806 NORTHWEST HIGHWAY • CHICAGO 31, ILL.

**ACTUALLY LASTS
20 TIMES
AS LONG**

**50¢
LIST**

This Feraloy tip is same size as standard tip of the Wen Gun but specially coated to protect against corrosion and silver plated to insure best electrical contact and heat transfer. Stays tinned indefinitely, never requires dressing, extra rigid, retains full tip contact area.

BIG HELP IN SHOP, FACTORY

Where soldering is constant and tip life is important (as in factory production or bench work) this Wen Feraloy tip is terrific. One plant reports standard tips had to be changed every half hour—Wen Feraloys every two weeks.


AND NOW ANOTHER

A special tip for smooth, fast cutting of plastic tile, linoleum, asphalt tile. Cuts straight lines, curves, any shapes. Works in regular Wen Soldering Gun.

**A TIP
FOR CUTTING
PLASTIC TILE
—50¢ LIST—**

with the Rola Co. and Magnavox in executive positions.

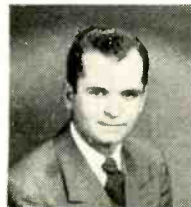Floyd A. Hayhurst was promoted to staff assistant to Edward C. Tudor,



F. A. Hayhurst

president of I.D.E.A. (REGENCY), Indianapolis, manufacturer of Regency boosters and converters. Hayhurst was formerly purchasing agent for I.D.E.A.

Lou Burzycki joined CREST LABORATORIES, Rockaway Beach, N. Y., as chief transformer engineer. He was formerly affiliated with Berkshire Transformer Co.



L. Burzycki

Personnel Notes

... Walter E. Peek has joined CENTRALAB, a division of Globe-Union, Inc., Milwaukee, as sales manager of the Mechanical Electronic Products Section, which covers variable resistors and wave-change switches, according to an announcement by W. S. Parsons, Centralab president.

... R. H. Siemens was appointed manager of kinescope equipment sales and J. T. Wilson, manager of receiving tube equipment sales of the RCA TUBE DEPARTMENT in a move to create separate kinescope and receiving-tube sales functions. Previously, Siemens had administered both kinescope and receiving tube sales. Wilson was formerly field application engineer for the Tube Department's Equipment Sales Section.

... A. D. Davis, president of ALLIED RADIO CORP., Chicago, presented a gold watch to Max Hechter, assistant purchasing agent, to mark his 25 years with the company. The presentation was made at a meeting to organize an Old-Timers Club of employees associated with the company 20 years or more.

... Kenneth A. Giffin was appointed district sales manager for the GENERAL ELECTRIC TUBE DEPARTMENT in the Western region. He was formerly with Aeronautical Radio, Inc.

... E. T. Spence of the Special Sales Division of ALPRODCO, INC., Mineral Wells, Texas, was appointed director of sales for all states along the Atlantic seaboard. The company manufactures aluminum TV towers and the Erector-tower, portable trailer-tower device for dealer use.

... Arthur L. Chapman, a vice-president of SYLVANIA ELECTRIC PRODUCTS, INC. for the past two years, was named vice-president in charge of electronics operations of the company.

... Charles Weyl, formerly executive vice-president of INTERNATIONAL RESISTANCE Co., Philadelphia, was elected president. Ernest Searing, former president, was elected chairman of the Board of Directors.

END

RADIO-ELECTRONICS

EASY TO LEARN CODE

It is easy to learn or increase speed with an Instructograph Code Teacher. Affords the quickest and most practical method yet developed. For beginners or advanced students. Available tapes for beginner's alphabet to typical messages on all subjects. Speed range 5 to 40 WPM. Always ready—no QRM.



ENDORSED BY THOUSANDS!

The Instructograph Code Teacher literally takes the place of an operator-instructor and enables anyone to learn and master code without further assistance. Thousands of successful operators have "acquired the code" with the Instructograph System. Write today for convenient rental and purchase plans.

INSTRUCTOGRAPH COMPANY

4701 Sheridan Rd., Dept. RC, Chicago 40, Ill.

**ANOTHER OUTSTANDING JOBBER
MERCURY ELECTRONICS DIST. CO.**

Corner Clinton & Wall Sts.
Binghamton, N. Y.

HAS THE
SENSATIONAL NEW
EICO 470-K 7"
SCOPE KIT
IN STOCK!



\$79.95

\$3.00 FOR CARTOON IDEAS

RADIO-ELECTRONICS prints several radio cartoons every month. Readers are invited to contribute humorous radio ideas which can be used in cartoon form. It is not necessary that you draw a sketch, unless you wish.

Address
RADIO-CARTOONS, RADIO-ELECTRONICS
25 West Broadway, New York 7, N. Y.

VEE GOT IT!

Check these tube prices against your last purchase order. We're positive you can't beat these prices for branded tubes, *fully guaranteed* and individually boxed.


0Z4A . . .68	6AV6 . . .41	6W4 . . .49
1B3 . . .68	6BA6 . . .48	6X4 . . .39
1R5 . . .61	6BC5 . . .56	6X5 . . .32
1S5 . . .52	6BG6 . .1.40	12AT7 . .73
1T4 . . .61	6BE6 . .49	12AU6 . .42
1U1 . . .60	6BQ6 . .90	12AU7 . .57
1X2 . . .68	6C4 . . .40	12BA6 . .48
3Q4 . . .65	6CB6 . .56	12BE6 . .48
3Q5 . . .70	6CD6 . .1.79	12SA7 . .57
3S4 . . .60	6J5 . . .40	12SK7 . .55
5U4 . . .45	6J6 . . .71	12SN7 . .57
5Y3 . . .35	6K6 . . .48	12SQ7 . .47
6AC7 . .80	6S4 . . .51	19BG6 . .1.44
6AG5 . .56	6SA7 . .57	25BQ6 . .90
6AK5 . .1.15	6SK7 . .55	25L6 . .50
6AL5 . .45	6SQ7 . .47	35W4 . .34
6AQ5 . .51	6SN7 . .57	35Z5 . .40
6AT6 . .41	6T8 . . .83	50B5 . .53
6AU6 . .45	6V6 . . .51	50L6 . .53

Jobber Inquiries Invited

All prices F.O.B., N.Y. Min. order \$5.00. C.O.D.'s, of course. 25% deposit with order. Pre-paid shipments if check in full with order.

VEE Dept. E
Box 134,
Queens Village 29, N.Y.

Fidelity

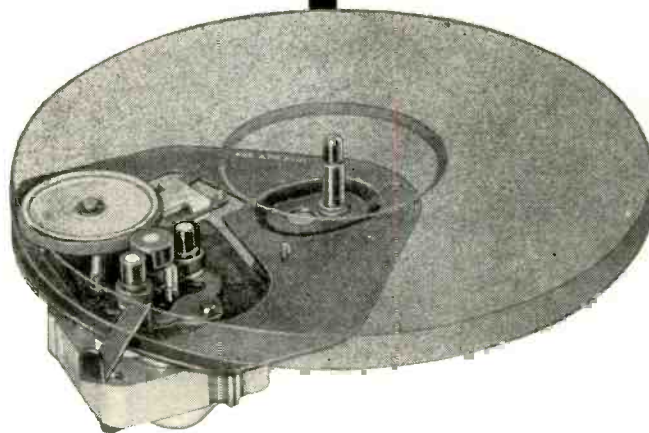

BEGINS HERE . . .

with General Industries' Phonomotors


The fidelity reputation of your record players, phono-combinations, and portables begins at the phonomotor. Be sure it's a good reputation that stays good . . . protected by General Industries' *Smooth Power* Phonomotors.

Complete data and specifications on the entire line of *Smooth Power* Phonomotors will be sent promptly on your request.



THE GENERAL INDUSTRIES CO.
DEPARTMENT ME • ELYRIA, OHIO

"HIGH FIDELITY Simplified"

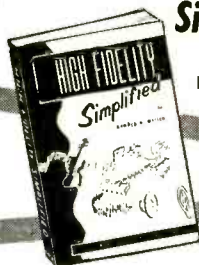

by
H. D. WEILER

Here is the complete story of high fidelity—clearly told, easily understood. This brand new, practical book covers everything from 'what high fidelity is' to the actual selection, purchase and installation of the proper high fidelity equipment. You'll find page after page of detailed, illustrated information concerning record players and changers, amplifiers, loudspeakers and tape recorders . . . it answers your questions on what to buy and do to obtain perfect results. Learn how you can enjoy the most lifelike musical reproduction possible. Order your copy of this valuable, new first edition today at your local bookstore . . . or simply send \$2.50 to—

John F. Rider, Publisher, Inc.
Dep't. T, 480 Canal Street
New York 13, N. Y.

THE DYNATRACER* NEW DYNATRACER FOR DYNAMIC SIGNAL TRACING AT LOW COST! REQUIRES NO AUXILIARY EQUIPMENT

Dynamic Signal Tracing is the fastest known method of trouble-shooting any radio or television set. "DYNATRACER" is designed to signal trace through any radio or TV audio, video, sync, AFC, vertical or horizontal sweep circuit, and instantly isolate trouble to a stage or component.

"DYNATRACER" is a Portable Self-Powered Instrument that is used under actual operating conditions. Ideal for home service calls and bench.

Complete Instructions and Trouble-Shooting Methods Enclosed.
Distributors Inquiries Invited

CENTURY ELECTRONICS CO.
8509-21st Ave., Dept. 101, Brooklyn 14, N. Y.



Check or M. O.
Postpaid U.S.A.

\$4.95

Satisfaction
Guaranteed

Used Recording Tape (plastic base)



1.99 for 7" 1200 foot.
1.09 for 5" 670 ft.
.69 for 4" 300 ft.
.29 for 3" 150 ft.
(plastic reel included
with all above sizes)

Money cheerfully refunded if you do not find this tape cleanly erased and as good as new. (if you are skeptical and from Missouri send us 12¢ in stamps and we'll roll you a sample).

New empty plastic reels in boxes for easy labeling
3"-10c; 4"-22c; 5"-24c; 7"-30c each. EMPTY
BOXES: 3"-3c; 4"-5c; 5"-5c; 7"-10c.

• We carry new recorders, recording blanks, tape, tape recorders, etc., at large savings. PLEASE INCLUDE SUFFICIENT POSTAGE.

COMMISSIONED ELECTRONICS CO.
2503 Champlain Street, N.W., Washington, 9, D.C.

Please mention **RADIO-ELECTRONICS**
when answering advertisements

New Portable Battery-Operated Spring-Motor Tape Recorder



The Magnemite*

For all field recording without AC power! Smaller and lighter than a portable typewriter, the Magnemite* actually makes field recordings that can be played on any studio console equipment. Completely self-powered, the Magnemite* does away with bulky and cumbersome generators, storage batteries and rechargers.

Just check these unusual features:

- Noiseless and vibrationless governor-controlled spring-motor assures constant tape speed.
- 100 operating hours per set of inexpensive flashlight-type dry cell batteries.
- Earphone monitoring while recording, and earphone playback for immediate quality check.
- Operates in any position, and is unaffected by movement or vibration during operation.
- Warning indicator tells when to rewind, and shows when amplifier is on.
- Broadcast models weigh 15 pounds. Slow-speed models weigh only 10 pounds.
- Requires no more desk space than a letter-head, measuring only 11 x 8½ x 5½ inches.

There's a choice of 5 different models for any recording need. High fidelity units, meeting primary and secondary NARTB standards, which record and play back frequencies up to 15,000 cycles, are available for broadcast stations, critical music lovers, and scientific research. For investigation, missionaries, reporters, and general dictation while traveling, there are units which play up to 2 hours per reel of tape.

Write today for complete descriptive literature and direct factory prices.



**AMPLIFIER CORP.
of AMERICA**

398 Broadway, N. Y. 13, N. Y.

*Trade Mark Reg.

THE FUND NEARS \$10,500



HELP - FREDDIE-WALK FUND

There is always a distinct feeling of anticipation when we here at RADIO-ELECTRONICS open the Help-Freddie-Walk Fund mail, for it's fun to meet at first-hand the many friends of little Freddie Thomason, four-year-old son of Herschel Thomason, radio technician of Magnolia, Arkansas. Freddie was born without arms or legs, but his faith and courage are mirrored in the hundreds of letters we have received.

The following are excerpts from letters received this month:

"As I looked through my RADIO-ELECTRONICS I noticed the Help-Freddie-Walk Fund. I brought it to the attention of our team chief, and he suggested I contact the other team members, who each donated \$2.00. They are: Lt. Col. Willis B. Scudder, Maj. Charles T. Boyle, Capt. Arthur E. Lomax, M/Sgt. Dewey Duckworth, M/Sgt. Robert F. Strosnider, and Sgt. Joseph T. Olwick." A picture of the entire team, all working with the Turkish Military in Erzurum, Turkey, was forwarded to Freddie.

"We are pleased to enclose our check in the amount of \$50.00, with our best wishes for Freddie and you all," from the Radiotelephone Communicators of Puerto Rico, San Juan, Puerto Rico.

With a check for \$10.00 comes a note: "Please accept this small contribution towards your fund. We all wish that we could contribute a whole month's pay—but we hope this will help just a little," from the 1st Inf. Div. Signal Repair Team #2, A.P.O. 1, c/o Postmaster, New York.

We should also like to mention the special Christmas greetings received from Linda Zeiher, age 4½, of Jackson Heights, N. Y., with her \$2.00 donation.

Although the Help-Freddie-Walk Fund has now topped \$10,400, the fight is just beginning. We urge each and every one to help this worthy cause by sending in his contribution, small or large, as soon and as often as possible. No donation is too small to receive our sincere thanks and acknowledgment. *Make all checks, money orders, etc., payable to Herschel Thomason.* Address all letters to:

HELP-FREDDIE-WALK FUND
c/o RADIO-ELECTRONICS Magazine
25 West Broadway
New York 7, New York

FAMILY CIRCLE CONTRIBUTIONS
Balance as of December 22, 1952 ... \$ 577.50
Anonymous, Washington, D. C. 1.00

FAMILY CIRCLE Contributions as of January 20, 1953 \$ 578.50

RADIO-ELECTRONICS CONTRIBUTIONS
Balance as of December 22, 1952 ... \$9,731.22
A. Friend, Worcester, Mass. 2.00
Anonymous, S. S. Irvingdale 2.00
Fred R. Courtney, Brooklyn, N. Y. ... 5.00
John Doe, Monterey Park, Calif. ... 10.00
1st Inf. Div. Signal Repair Team #2,

How much time will you
spend on your next job?

to spot the cause of
trouble quickly and
accurately on your
next service job, take
along a copy of



Mandl's TELEVISION SERVICING

- A master index shows the possible causes of 100 trouble symptoms in sound and picture, and refers directly to the page on which servicing instructions are given.
- You'll learn simple signal tracing procedures, essential factors for successful VHF and UHF servicing, how to improve reception in fringe areas, how to troubleshoot A.G.C. and synchroguide circuits, and many more trade tricks in diagnosing troubles in minimum time.
- You'll see how each unit in the TV receiver functions, how it is set up by the different manufacturers, what flaws may occur in it, what points in the circuitry cause these flaws, how they affect the other components in the unit and how they show up on the TV screen.
- You'll have clear illustrations of scope patterns and station defects as well as hundreds of schematics to help you check and locate trouble. Every practical aid is here to help you do the best, most satisfactory servicing job in the minimum time. Try it out free of charge. See below.

Do you know enough
about hearing aids?



Mandl's HEARING AIDS

tells you how to select and get the most out of a hearing aid, and how to service it. Here is badly needed, reliable information on the various types of aids being manufactured today, their components, and their adaptability to different types and degrees of deafness, together with instruction for the serviceman on testing, adjustment and repair.

SEE COPIES ON APPROVAL

The Macmillan Company, 60 Fifth Ave., N. Y. 11

Please send me the books checked below. I will either remit in full or return the books in 10 days.

- Mandl's Television Servicing \$5.50
- Mandl's Hearing Aids \$3.50

Signed

Address

This offer good only within continental limits of U.S.A.)


A.P.O. 1, N. Y.	10.00
Michael Gaffney, Lyndhurst, N. J. . .	1.00
P. Hoffman, E. Paterson, N. J.	5.00
M. Jarnagin, Arlington, Va.	1.00
Johns Radio Service, Griffith, Indiana	1.00
Edward T. Jones, RCA, Camden, N. J.	2.00
Sgt. Joseph T. Olwick, on behalf of his Team, working with the Turkish Military, Erzurum, Turkey	12.00
Radio Maintenance Shop, Augusta, Georgia	5.00
Radiotelephone Communicators of Puerto Rico, San Juan, Puerto Rico	50.00
Walter A. Upson, 16 Bateman St., Haverhill, Mass.	5.00
Linda Zeiher (age 4½), Jackson Heights, New York	2.00

RADIO-ELECTRONICS Contributions
as of January 20, 1953 \$9,844.22
FAMILY CIRCLE CONTRIBUTIONS 578.50

TOTAL CONTRIBUTIONS as of Jan-
uary 20, 1953 \$10,422.72

CORRECTION

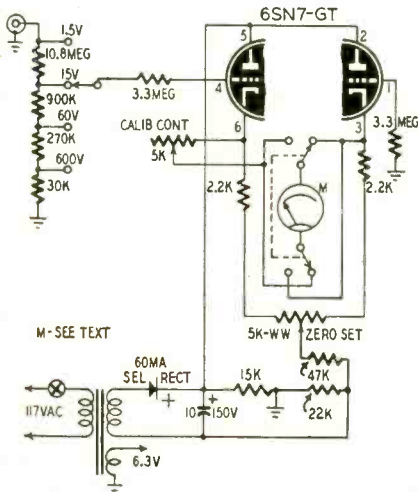When the "Low-Cost V.T.V.M." is connected according to Fig. 1 on page 46 of the December, 1952, issue, the meter will not operate. The corrected circuit is shown here.



The original schematic showed an excessively high cathode bias.

Radio Thirty-Five Years Ago
In Gernsback Publications


HUGO GERNSBACK Founder	
Modern Electrics	1908
Wireless Association of America	1908
Electrical Experimenter	1913
Radio News	1919
Science & Invention	1920
Television	1927
Radio-Craft	1929
Short-Wave Craft	1930
Television News	1931

Some of the larger libraries still have copies of ELECTRICAL EXPERIMENTER on file for interested readers.

**March 1919
ELECTRICAL EXPERIMENTER**

- Underground Wireless & Sub-sea Radio, by H. Gernsback
- My Inventions, by Nikola Tesla
- Amateurs Win; Wireless Bill is Killed, by H. Gernsback
- The Rogers Underground Wireless, by H. Winfield Secor
- How I Invented the Audion, by Dr. Lee de Forest
- Gigantic French Radio Station

MARCH, 1953

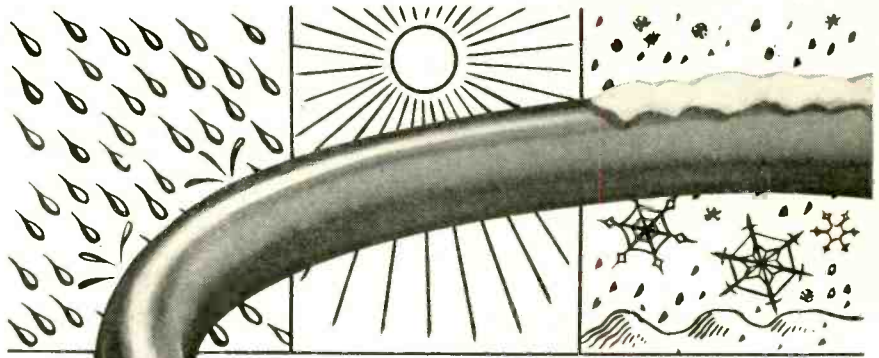

Sheath-Leed

**the all-weather lead line
for finest TV reception**

SHEATH-LEED—the DON GOOD super-fine leadline is built for use wherever tough weather conditions prevail. It's especially recommended for use in coastal areas where salt spray encrusts the regular leadline and devitalizes it. And also in hot humid areas, where much alternate rainfall and strong sunlight prevails, and where leadlines are subjected to frost, snow and icy conditions.

- PURE POLYETHYLENE TUBING — ENCASING GOODLINE AIRLEAD
- TWO COLORS — STANDARD BROWN or SILVER-GRAY TUBING
- RECOMMENDED FOR FINEST VHF or UHF RECEPTION
- GIVES MAXIMUM LONG-LIFE SERVICE VS WEEKS OF SERVICE WHERE A REGULAR TYPE LEADLINE IS USED

**Goodline Airlead — Nationally Accepted as the Basis
of Finest Television Reception**

- 80% OF LOSS PRODUCING DIELECTRIC WEB IS REMOVED
- CORRECT IMPEDANCE FOR SHARP, CLEAN, "SNOW-FREE" PICTURES
- PACKAGED: 100'—250'—500'—1000'—2500'

**GIVE TELEVISION SETS A CHANCE TO GIVE YOU FINEST RECEPTION
INSIST ON SHEATH-LEED or GOODLINE AIRLEAD**

Don Good, INC.

**SOLD BY LEADING
JOBBER & DEALERS**

Send coupon NOW for complete information. Get samples "in your hands" —you'll realize why Goodline Products give the finest possible in television reception.

DON GOOD, INC. 1.0
1014 Fair Oaks Ave., So. Pasadena, Calif.
Please rush Samples and Complete Information covering Sheath-Leed and Goodline Airlead.

Name _____
Street _____
City _____ State _____

COLOR TONE TELEVISION!
ON YOUR TELEVISION!

Simply attach TELECOLOR FILTER to front of set and enjoy programs in glorious color tones instead of dull black and white. GUARANTEED to give genuine color tone. Can also be used with any other filter. Once tried, you will never go back to old black and white. Write for FREE information. ORDER BY MAIL. NEW REDUCED PRICES!

Send check, M.O., cash, COD to Dept. RE-3

10 in. \$1	16, 17 in. \$3
12, 14 in. \$2	19, 21 in. \$5

HARVARD LAB. 659 FULTON ST. BROOKLYN 1, N.Y.

PRES-PROBE CONDENSER TESTER

Finds Intermittent Condensers Instantly


Pres-probe's sliding tip with variable resistance prevents condenser heating. Tests with power on. Requires no adjustment. Stops guesswork. Saves time. Convenient probe size (7¼" long). Satisfaction guaranteed.

795
Postpaid U.S.A.

See Your Dist. or Order Direct
PRES-PROBE CO.
4034 N. Sixth St., Milwaukee 12, Wisc.

Another **TACO** First...


The ALL NEW *Silver Streak* **BAZOOKA**

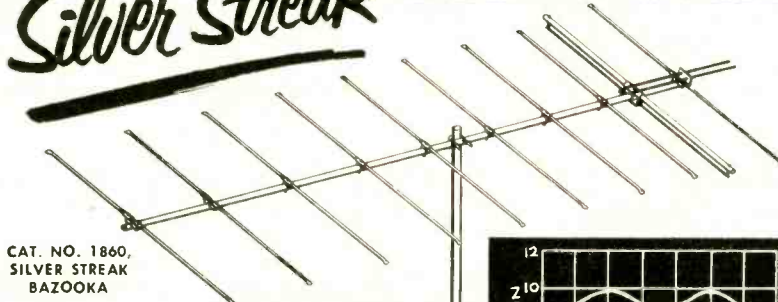

CAT. NO. 1860,
SILVER STREAK
BAZOOKA

Here is the first broad-band antenna that provides top performance on all seven channels (7-13). It's a BAZOOKA-TUNED yagi, incorporating all these advantages:

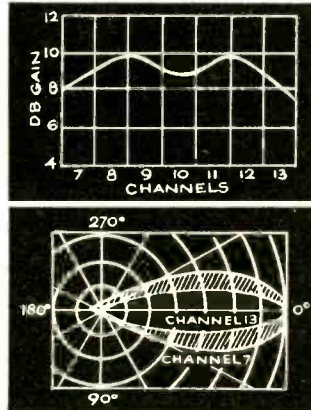- Single forward lobe.
- 13½ db front-to-back ratio.
- Snap-Spring assembly.
- Mechanically balanced—ideal for use with rotor.
- Extremely high, flat response throughout high-band VHF.



A NATIONWIDE NETWORK OF TOP DISTRIBUTORS CARRY TACO ANTENNAS

TECHNICAL APPLIANCE CORP. Sherburne, N.Y.
HACKBUSCH ELECTRONICS • TORONTO 4, ONT., CANADA

STANDARD BRANDS **TUBES** INDIVIDUALLY BOXED
STANDARD WARRANTY **NEW LOW PRICES** BRAND NEW!!

0Z4 \$.54	5Y3GT . . \$.39	6BA6 . . . \$.54	6F6GT . . \$.54	6W4GT . . \$.54	12SQ7GT \$.63
1B3GT87	6AB461	6BA776	6H657	6W6GT . . .65	19B66G . 1.75
1L465	6AC798	6BC565	6J5GT54	6X449	19T887
1R559	6AG564	6BE657	6J676	6X5GT . . .43	25AV5GT 1.05
1S476	6AG7 . . . 1.19	6BF569	6K6GT . . .54	12AT6 . . .47	25BQ6GT 1.08
1S564	6AH6 . . . 1.05	6BG6G . 1.69	6L6GA . 1.05	12AT7 . . .76	25L6GT . .54
1T464	6AK588	6BH672	6SA7GT . .61	12AU6 . . .54	25Z6GT . .49
1U469	6AL550	6BJ661	6SC776	12AU7 . . .65	35B561
1U561	6AQ5 . . .54	6BL798	6SF558	12AV7 . . .88	35C561
1X2A . . .75	6A06 . . .49	6BN6 . . .72	6SH7 . . .65	12BA6 . . .54	35L6GT . .61
3Q475	6AR5 . . .69	6BQ6 . . 1.08	6SJ754	12BE6 . . .58	35W441
3O5GT . .72	6AS5 . . .62	6BQ7 . . 1.08	6SL7GT . .64	12BH7 . . .82	35Z5GT . .39
3S465	6AT6 . . .46	6C449	6SN7GT . .69	12SA7GT .62	50B561
3V465	6AU6 . . .54	6C557	6SO7GT . .49	12SG7 . . .61	50C561
5T4 1.31	6AV5GT 1.05	6CB6 . . .65	6SR7 . . .49	12SH7 . . .49	50L6GT . .59
5U4G . . .54	6AV6 . . .46	6CD6G . 1.29	6T879	12SK7GT .63	117Z3 . . .54
5V4G . . .98	6B4G . . .98	6E576	6V6GT . . .57	12SN7GT .73	

Many other types equally low priced—include all your tube needs with your order.
One of the largest stocks in the country!
Min. Order \$25.00. Terms: 25% with order, balance C.O.D.
All prices subject to change without notice. F.O.B. New York City. Mail order division.

Television Materials Corp.
120 LIBERTY ST., NEW YORK 6, N.Y. • COlrandt 7-4307

ANOTHER OUTSTANDING JOBBER
PENINSULA TELEVISION & RADIO SUPPLY
42 West Gabilan St.
Salinas, Calif.

HAS THE SENSATIONAL NEW
TEGO 470-K 7" SCOPE KIT
IN STOCK!
\$79.95 (5% higher on West Coast)

You can't beat
Radio-Electronics
for complete coverage of
Radio, Television and Audio

TRANSFORMER POLARITY

Dear Editor:

In the article "Saturated-Core Light Flasher" by Erwin Levey on page 62 of the December issue of RADIO-ELECTRONICS, the author suggests a method for checking polarity of the transformers. For safety, a much lower voltage (any filament supply) could be used instead of 117 volts a.c. to obtain the same results. If 117 volts is used, the supply voltage should be connected to the high-voltage instead of the low-voltage winding to avoid stepping up the voltage during the test.

There are two other methods for checking polarity of transformers. The first uses a small pocket magnetic compass and a single 1.5-volt dry cell. The compass is placed above the iron core of the transformer and a 1.5-volt dry cell is connected to either winding. The movement of the compass should be noted and also which lead is connected to the positive pole of the battery. The leads are marked accordingly. The other winding can be tested in the same manner noting the direction of the flux around the core as indicated by the compass. Coil connections should be changed if necessary to obtain the same indication of flux direction as for the other winding. The low tension and high tension leads which were connected to the positive terminal +, or following the article's markings, of the dry cell can be marked A and C respectively. The other transformer can now be checked in the same manner. If the transformers are identical and the leads are colored, the positively connected leads will be the same on each transformer which is a further check as to correct polarity.

The second method calls for a dry cell and a 5-volt or 10-volt d.c. voltmeter. For a transformer with 450 volts total secondary voltage, a 1.5-volt meter is large enough, although higher range meters will give sufficient indication. Connect the voltmeter across one winding. Connect the 1.5-volt dry cell across the other winding through an s.p.s.t. switch. The switch should be left open until all other connections are made. Close the switch while watching the voltmeter. The voltmeter will either kick up momentarily in the positive direction or show reversed polarity. If the latter, reverse the connections to the dry cell. The voltmeter will now kick up when the switch is closed and immediately return to zero. On opening the switch, the meter will kick downward momentarily. Mark the transformer lead which is connected to the positive terminal of the dry cell. This lead becomes either A or C depending on which winding of the transformer is being checked. The other winding and the other transformer can be checked and leads marked in a similar manner. Then transformers can be connected in series or parallel as required, by simply observing the markings.

J. H. BROWNELL, VE4BU
Pointe du Bois, Manitoba

RADIO-ELECTRONICS

Any or all of these catalogs, bulletins, or periodicals are available to you on request direct to the manufacturers, whose addresses are listed at the end of each item. Use your letterhead—do not use postcards. To facilitate identification, mention the issue and page of RADIO-ELECTRONICS on which the item appears. All literature offers void after six months.

CAPACITOR CATALOG

Wells' 1953 capacitor catalog lists a wide variety of mica, paper, oil-filled, electrolytic, and variable capacitors.

Free of charge from Wells Sales Inc., 833 West Chicago Ave., Chicago 22, Ill.

JFD CATALOG

JFD's 1952-1953 "Television Almanac" is a well-illustrated 35-page catalog listing television antennas, mounts, boosters, masts, lightning arresters, and screw-eye standoffs. The antennas are fully described, and of special interest are the Jetenna conical and the Baline Yagi.

Request Catalog No. 450 from JFD Mfg. Co., Inc., 6101 16th Ave., Bklyn 4, N. Y.

TRANSFORMER CATALOG

A 15-page transformer catalog listing audio and power transformers and chokes has been released by Peerless.

Copies free on request to Peerless Electrical Products, 161 6th Ave., New York 13, N. Y.

MASTER TV SYSTEMS

A manual giving complete technical data on all types of master TV systems, *The B-T Unit System for Better Television*, has been issued by Blonder-Tongue. It describes the characteristics and functions of the various units and accessories and gives information on the layout of a master system, the locations and installation of various units, and the elimination of interference.

Gratis from Blonder-Tongue Laboratories, Inc., 526 North Ave. E., Westfield, N. J.

AUDIO CATALOG

Terminal Radio Corporation's new 128-page *Audio Catalog* is divided into five sections: home music, public address, recording, broadcast, and special equipment. Completely indexed, it should be of interest to music lovers, sound engineers, and installation men.

Copies may be obtained free of charge by writing to Terminal Radio Corp., 85 Cortlandt St., New York 7, N. Y.

MICROWAVE CATALOG

Titeflex, Inc. has issued a 12-page catalog describing its line of microwave components. The booklet includes specifications for both rigid and flexible waveguides, plus schematic diagrams and application charts.

Available free of charge from Titeflex, Inc., 500 Frelinghuysen Ave., Newark, N. J.

MARCH, 1953

TESTED . . . APPROVED

- High Gain over all UHF channels
- No Rust all aluminum construction
- Excellent vertical directivity
- Broad horizontal pattern
- Ideal front-to-back ratio
- Completely assembled for quick, easy installation

\$9.95 LIST

STACKED UHF TV ANTENNA

Cletron

CLEVELAND ELECTRONICS, INC.
6612 Euclid Avenue • Cleveland 3, Ohio
Morhan Exporting Corp.
458 Broadway, New York, N. Y.

SUBSCRIBERS

If you're moving, please don't forget to send us your address as it appears on the copy of the magazine, including the numbers shown beside your name, as well as your new address.

If we receive this information before the 20th of the month, you will continue getting the magazine without interruption.

Your cooperation will be most helpful and greatly appreciated.

COUPON-OF-THE-MONTH

AUTO RADIO FOOT CONTROL—List \$2.00 . . . 2 for \$0.99
TUBES—STD. BRAND 12SQ7 or 35Z5 . . . 2 for .99
VOL. CONTROLS—STD. BR. .5 Meg. W. SN . . . 3 for .99
CONDENSERS—40-40 Mfd. 150V . . . 2 for .99
CONDENSERS—20-20 Mfd. 150V . . . 3 for .99
LOOP ANTENNA—HI GAIN (5"x8") . . . 3 for .99
I.F. COILS 455 KC (1 1/4"x2 1/2") . . . 3 for .99
OSC. COILS 455 KC (for 125A7) . . . 4 for .99
BY PASS COND. KIT—18 Asstd.99
DIAL CORD KIT—100 Ft. Asstd. & 6 Springs99
GRILLE CLOTH—6 Asstd. 6"x6" & 10 Knobs99
● COMBINATION KIT—All Above Items—Only . . . 10.00

WITH THIS COUPON—ORDER AT ONCE
Write for Monthly Coupons and Bulletin
RADIO DISTRIBUTING CO. PASADENA 18, CAL.

You can't beat

Radio-Electronics
for complete coverage of
Radio, Television and Audio


UHF

UHF TELEVISION IS HERE!

Telecasting on the UHF channels is under way. Several stations are on the air now and, soon, almost every city will have two or more UHF stations in operation. Now you can get UHF antennas with the same durable construction that made the Tel-a-Ray Model T and Butterfly famous.

HERE ARE THE ANTENNAS TO RECEIVE IT BEST!


TEL-A-RAY UNIVERSAL

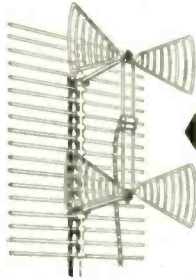

All-channel (14 through 83) antenna constructed from Dural and cast aluminum. Completely guaranteed against weather damage — can not corrode. Flat frequency response over entire band, provides brilliant reception in service and fringe areas. Quickly assembled. Single bay (UF1) \$3.75 list; Double bay (UF2) \$7.50 list; Four bay (UF4) \$14.95 list.

TEL-A-RAY ULTRA

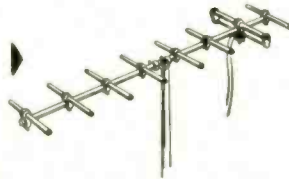Wide-spaced yagi peaked for single channel. Same durable construction as Universal, same guarantee. Folded dipole completely pre-assembled for lightning quick assembly — just tighten screws. Eight element single bay \$4.95 list; 12 element single bay \$6.50.




Order today from
TEL-A-RAY ENTERPRISES INC.
 BOX 332R • HENDERSON, KY.

now 2 specific type FLYBACKS by HALLDORSON

service

115 DIFFERENT ADMIRAL TV MODELS

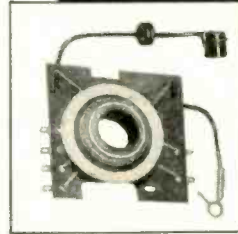

ECONOMY—With Halldorson FB405 and FB406 Flybacks you utilize costly Ferrite pieces and mounting brackets of Admiral part being replaced.

CONVENIENCE—Both units are completely wired to terminal boards with exact length plate leads and clips attached. New H. V. filament wires and easy assembly instructions supplied.

Think of it! Two parts that are not makeshift arrangements but specific replacements for 115 popular TV models made during the last two years by Admiral. You get them as complete coil assembly replacements ready for quick installation. Keep a few FB405's and FB406's on hand for quick service and extra profits! See your distributor today.

HALLDORSON TRANSFORMER COMPANY
 4500 N. Ravenswood Ave. Chicago 40, Illinois
 Write Dept. RE-3



HALLDORSON

QUALITY Transformers SINCE 1913

EXPORT: Intex Co., Inc., 130 Liberty St., New York 6, N.Y. Cable Address: Intexcom, N.Y.

GREYLOCK TERRIFIC TUBE BUYS!

All tubes listed below carry full ONE-YEAR GUARANTEE. All individually boxed, in attractive GREYLOCK Cartons.

1B3GT	.89	6CB6	.54	12BE6	.49
5U4G	.59	6CD6G	1.59	12BH7	.79
6AK5	.89	6JC	.69	12SA7GT	.79
6AL5	.49	6SN7	.59	12SK7GT	.79
6AQ5	.49	6T8	.79	12SN7GT	.79
6AU6	.49	6V6GT	.49	12SQ7GT	.69
6AV6	.49	6W4GT	.49	19BG6G	1.39
6BA6	.49	12AT7	.79	25BQ6GT	.79
6BE6	.49	12AU7	.59	35W4	.49
6BG6G	1.39	12AV7	.69	35Z5GT	.49
6BK7	.89	12AX7	.59	50L6GT	.59
6BQ6	.89	12BA6	.49	80	.59

EXTRA! 5% ADDITIONAL DISCOUNT on any assortment of 100 tubes or more.

SPEAKER SPECIALS

- All PM Speakers have
- Alnico V slugs.
- 3" PM 6.8 oz. \$1.29
- 4" PM 1.0 oz. 1.39
- 5" PM 1.0 oz. 1.39
- 6" PM 1.0 oz. 1.79
- 4"x6" PM 1 oz. 1.49
- 5"x7" PM 1.47 oz. 1.89
- 6"x9" PM 3.16 oz. with heavy duty output trans-former 2.99
- 8" PM 2.15 oz. 3.69
- 10" PM 6.8 oz. (extra heavy) . 5.95
- 12" PM 3.2 oz. 4.95
- 12" PM 6.8 oz. 5.95



TUBULAR ELECTROLYTIC KITS

Fine assortment, popular types for radio, TV service.

10 condensers... \$1.49
 25 condensers... \$3.69

TUBULAR PAPER BYPASS CONDENSER KITS


100 Asstd. 400 WV \$4.95
 100 Asstd. 600 WV \$5.95

INSULATED RESISTORS

1/4 & 1/2 Watt, Kit of 100 Asstd. \$2.25
 1/2 Watt A-B & IRC, separated, in plastic container, 20 popular sizes \$4.85

All prices F.O.B. N.Y.C. Please include postage and insurance with your remittance. 25% deposit on all C.O.O. orders. 50c handling charge on orders under \$5.00.

GREYLOCK CONICAL ANTENNAS

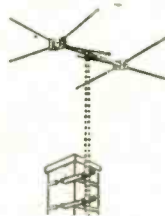

4x2 Element Conical Antenna, Aluminum, less mast. \$3.19

4x4 Element Conical Antenna, (illustrated) Aluminum, less mast. \$3.59

STACKING BARS for above conicals, per pair 75¢

STEEL ANTENNA MASTS

5-ft. Crimped at end for extending... 89¢ ea.

CHIMNEY MOUNT

As shown above... 99¢



300-OHM TWIN LEAD \$1.49 per C. ft. \$12.95 per M. ft.

GREYLOCK SPECIAL TV ANTENNA "PACKAGE" OFFERS

Complete Kit, 4X2 element conical antenna, including 5-ft. mast, chimney mount, 4 assorted standoffs, 75-ft. 300-ohm leadin, 1 lightning arrester, special \$6.98

Complete Kit, 4X4 Conical Antenna, other items as above, special \$7.38

Stacked 4X2 Array Kit, as above, including stacking bars, special \$14.49

Stacked 4X4 Array Kit, other items as above, special \$15.39

MANY THOUSANDS MORE!

Yes, you'll find many thousands more bargain buys in Radio & TV supplies that you use every day. In GREYLOCK's great new catalog. Order your free copy today!

GREYLOCK 1953 CATALOG



AN ESSENTIAL BUYING GUIDE for every RADIO & TV SERVICEMAN!

featuring:

- GREYLOCK TUBES, at new low prices!
- STANDARD BRAND TUBES, tremendous values!
- COMPLETE STOCKS OF STANDARD BRAND LINES

including:

INSTRUMENTS EICO Jackson EMC Oak Ridge	BOOKS Howard Sams Rider Coyne Editors & Engineers	OTHER TOP BRANDS C.D. Vibrators, Converters, Antenna Rotators Merit Transformers Sprague Condensers Stanwyck Coils GE Lamps Reconon Needles Shure Microphones RMS Antennas, Accessories Electrovoice Burgess Batteries Quam Nichols Speakers Regency Boosters
HARDWARE, TOOLS ICA Walco Jackson Irons Phillips Guns Xcelite Eby Myeller	RADIOS, SOUND EQUIPMENT Pentron Bogen Challenger Atlas Sound Steelman Phones Gen'l Industries Esquire Clock Radios	

GREYLOCK

ELECTRONICS SUPPLY CO.
 115 Liberty St., N. Y. 6
 Phone BE. 3-0224

GREYLOCK ELECTRONICS, Dept. C-3
 115 Liberty St., N. Y. 6

Send FREE Catalog #200 at once to

Name _____
 Address _____
 City _____ State _____

OPPORTUNITY AD-LETS

Rates—45¢ per word (including name, address and initials). Minimum ad 10 words. Cash must accompany all ads except those placed by accredited agencies. Discount, 10% for 12 issues. Misleading or objectionable ads not accepted. Copy for May issue must reach us before April 21, 1953.

Radio-Electronics, 25 W. Broadway, New York 7, N. Y.

SPEAKERS REPAIRED at wholesale prices. Guaranteed workmanship. Fast service. Amprite Speakers Service, 70 Vesey St., New York 7, N. Y.

YOUR TAPE OR WIRE RECORDINGS REPRODUCED onto Disc. 78RPM \$2.85 seven minutes, 33 1/3 microgroove \$3.50 fifteen minutes. Connecticut Recording Co., 15 Parklane, Wallingford, Connecticut.

TUBES AND EQUIPMENT BOUGHT, SOLD AND EXCHANGED. For a fair deal send details to B. N. Genster, W2LNI, 136 Liberty, N. Y. 6, N. Y.

EXPERIMENTER'S "RADIOBUILDER" 12 issues \$1.50; copy 15¢. Laboratories, 1131-B Valota, Redwood City, California.

WANTED TOP PRICES PAID—Navy Selsyns 1DG, 1F, 1GT, 1G, 5DG, 5D, 5CT, 5G, 6G, 7G, etc., and BC-348, BC-221, AN/ARP-13, AN/ARC-1, AN/ARC-3, RTA-1B, AN/APR-4. Electronic Research, 719 Arch St., Philadelphia.

BUY WHOLESALE—25,000 ITEMS CATALOG 25¢. Matthews, 1472-P6 Broadway, N. Y. C. 36.

FOR SALE: MATERIALS FOR BUILDING electronic organ. Console, tubes, relays, etc. V. R. Parker, Box 88, Fitchburg, Mass.

ALL TYPES OF ANTENNAS FOR AMATEUR AND TV. Aluminum Tubing, Willard Radcliff, Fostoria, Ohio.

FOR SALE: RADIO-CRAFT MAGAZINES Almost complete set. First issue July 1929 to December 1947. Alma Rutherford, 303 W. Court St., Doylestown, Pa.

SAVE 90% ON YOUR TEST EQUIPMENT. FREE information. Technological Developments, 475 Fifth Ave., New York 17, N. Y.

TV SET ANTENNAS. ALL TYPES INCLUDING UHF. Mounts, accessories. Lowest prices. Wholesale Supply Co., Lumburg 2, Mass.



The National Society for Crippled Children & Adults, Inc. 11 S. LaSalle St., Chicago 3, Ill.



EVERY RADIOMAN Can Use These SERVICE HINTS!

Valuable Manual Yours—FREE!

Every page of "How to Simplify Radio Repairs" is packed with on-the-bench, practical ideas. Contains photos, charts, diagrams—no fluff—no vague theory. In plain every-day language it gives you priceless suggestions—new servicing ideas. You'll use and benefit from the experience of experts. Partial list of contents: How to Localize Trouble; How to Service Amplifiers; How to Test for Distortion; How to Test Audio Circuits; How to Test Speakers; How to Find Faults in Oscillators; How to Test Radio Parts—and it's all yours—FREE! No obligation.



FEILER SEND COUPON OR GOVERNMENT POSTCARD FOR YOUR FREE COPY TODAY!

FEILER ENGINEERING CO., Dept. 3RC3
8026 N. Monticello Ave.
Skokie, Ill. (Suburb of Chicago)
Please RUSH my FREE copy of "How to Simplify Radio Repairs."

Name.....
Address.....
City..... Zone..... State.....

MARCH, 1953

TV TRANSMITTERS

A 12-page bulletin giving technical details of the complete range of TV transmitting equipment made by Standard Electronics Corporation is now available. It presents the electrical and mechanical specifications of the S-E 500-watt visual—250-watt aural—basic unit with final amplifiers providing complete transmitters of 5, 10, and 20 kw output.

Request Bulletin TTS-61 from Standard Electronics Corp., 285-295 Emmett St., Newark 5, N. J.

INDUSTRIAL RELAYS

Automatic Electric Co. has released a color-illustrated brochure describing its line of telephone-type relays, including hermetically sealed (in metal and glass containers) subminiature, plug-in types.

Request brochure 1702-A from Automatic Electric Co., 1033 Van Buren St., Chicago 7, Ill.

MASCO CATALOG

Mark Simpson has issued its new general catalog of 1952, revising catalog No. 50. The 24-page booklet describes high-power and high-fidelity amplifiers, transcription, mobile, and preamplification equipment, as well as institutional or school control amplifiers with microphone, radio, and phonograph inputs for up to 40 locations.

Separate individual catalogs list intercommunication equipment, tape recorders, television boosters, and the Masco economy line.

All available gratis from Mark Simpson Mfg. Co., 32-28 49th St., Long Island City 3, N. Y.

TRANSFORMER CATALOG

Stancor's revised 24-page catalog and replacement guide contains over 500 separate listings of transformers and related components and includes a separate TV component section. It is indexed. There are sections for hi-fi, input, interstage, output, driver, modulation, power, filament, plate, and isolation transformers and filter chokes. Also included is an output transformer chart, matched power supply chart, and data on the Stancor-Williamson amplifier.

Available free of charge from Standard Transformer Corp., 3580 Elston Ave., Chicago, Ill.

CIRCUIT BREAKERS

Manual 101, explaining operating principles of basic circuit-breaker designs and providing engineering data on factors of application, has been released by Heinemann Electric Co.

Simplified diagrams show the three basic types of circuit breakers in general use. There are explanations of temperature factors, inrush current effects, tripping and reset time, and time delay.

Available on request to Heinemann Electric Co., 342 Plum St., Trenton 2, N. J. END



Special Offer On This Complete RADIO ENGINEERING LIBRARY

New, Up-To-Date Edition of Famous Library Covers Whole Field of Radio Engineering. Places Latest Facts, Standards, Data Practice, and Theory At Your Fingertips

The five big volumes of the new edition of the Radio Engineering Library now include the very latest facts, standards, data, and practice. This Library will help solve hundreds of problems for designers, researchers, engineers, and students in any field based on radio.

Written by leading radio engineers, these books cover circuit phenomena, networks, tube theory, vacuum tubes, amplification, measurements, etc.—give specialized treatment of all fields of practical design and application. They provide you with a complete and dependable encyclopedia of facts.

- 5 Volumes, 3872 Pages, 2770 Illustrations
- Eastman's FUNDAMENTALS OF VACUUM TUBES, 3rd Edition.
- Terman's RADIO ENGINEERING, 3rd Edition.
- Everitt's COMMUNICATION ENGINEERING, 2nd Edition.
- Hund's HIGH FREQUENCY MEASUREMENTS, 2nd Edition.
- Henney's RADIO ENGINEERING HANDBOOK, 4th Edition.

SEND NO MONEY

Special Low Price—Easy Terms

On this special offer you get this Library for \$37.50, instead of \$43.50. You save \$6 and may pay on easy terms. Mail coupon below to examine the Library FREE for 10 days. No obligation. These books are recognized as standard works; you are bound to need them. So take advantage of this special money-saving offer. Mail coupon at once!

McGraw-Hill Book Co., Dept. RE-3
327 West 41st St., New York 36, N. Y.

Send for 10 days' FREE trial, the RADIO ENGINEERING LIBRARY. If not satisfied I will return books. Otherwise I will send \$7.50, plus delivery charges, then; and \$6 a month for 5 months. (Reg. price \$43.50, you save \$6).

Name.....
Home Address.....
City & State..... RE-3
Employed by.....
 We'll Pay Delivery Charges if you enclose \$7.50 first payment WITH coupon. Same return privilege for full refund.
(Offer applies to U.S. only.)

Thousands depend on PHOTOFACT! THEY TELL YOU WHY

Unsolicited letters tell what the world's finest TV and Radio Data means to Service Technicians



J. S. Hedges
Service Television Co.
514 Main
Beacon, N. Y.

"I have found your schematics most advantageous in my work. Your schematics are not mere diagrams. They rank with the best of instruments for servicing, not only for their preciseness, but also for their noted particulars of the various components employed in radio and TV receivers. Believe me when I say with all sincerity that I think you are the leaders in your field."



Jack Lapine
J & J Dist. Co.
3249 Kildare Road
Cleveland Heights, Ohio

"Words cannot express my appreciation for the wonderful service you have rendered me. It is no wonder that your concern is growing in popularity with the serviceman."



V. L. Bethea
Bethea Electric Service
108 E. Gibson Ave.
McCull, So. Car.

"I would like to express my pleasure at your new system of placing the voltages on the different points in the circuits... a great help... thanks again..."

NOW! GET THE PROOF FOR YOURSELF!

FREE

We'll send you a Free Photofact Folder on any receiver listed in "PF Index & Technical Digest."

Learn for yourself—at our expense—how PHOTOFACT pays for itself by earning bigger repair profits for you! Select any Folder from the PF Index (if you haven't an index, get a copy from your distributor). When you write us for your Free Folder, be sure to state Photofact Set and Folder Number as shown in the Index. Get your Free Folder now. Examine, use, compare—see why you can't afford to be without PHOTOFACT!

HOWARD W. SAMS & CO., INC.
2205 E. 46th St., Indianapolis 5, Ind.

HOWARD W. SAMS & CO., INC.

ESSENTIALS OF MICROWAVES, by Robert B. Muchmore. Published by John Wiley & Sons, Inc., 440 Fourth Avenue, New York 16, N.Y. 5 3/4 x 9 inches, 236 pages. Price \$4.50.

Every serious reader, whether novice or technician, can benefit from a book that features *logic* and *completeness*. This book gives a good physical explanation of the basic electromagnetic laws. Then it shows that waves and fields obey these laws. Math appears in only a few places. Illustrations appear throughout.

The practical and detailed approach of the author will make the book particularly useful to technicians lacking in mathematical training, or to engineers and scientists in other fields who may not have the time to plod through the demonstrations of a so-called "rigorous" work. The author has contented himself with simply presenting the information. The practical reader will be grateful for this, since in most cases he is much more interested in the facts than in knowing how they were developed.

Wave guides, cavity resonators, antennas and filters are developed from more conventional h.f. components. Slot antennas and microwave lenses are treated in detail. Then material is presented on tubes. Klystrons, magnetrons, lighthouse and travelling wave types are analyzed. Microwave applications and measurements follow.

This book should dispel much of the mystery that sometimes seems to surround microwaves.—*IQ*

EVERYBODY'S TELEVISION AND RADIO HANDBOOK. Published by Popular Science Publishing Co., New York 10, N. Y. 6 1/2 x 9 1/2 inches, 255 pages. Price. \$2.49.

This book is a compilation of approximately 200 hundred "how-to-do" and "how-it-works" articles and short items reprinted from *Popular Science* magazine.

Although a number of the articles are quite basic and would be of greater interest to the general public than to the average experimenter or technician, a number of articles describe the construction of items of interest to the radio and electronic experimenter and gadgeteer. Among these are:

A power converter which operates from 115-volt, 60-cycle lines and delivers 115 volts a.c. at frequencies which permit 78-r.p.m. synchronous phonograph motors to be operated at 45 or 33 1/3 r.p.m.

An electronic target range like those commonly seen in penny arcades and other amusement centers.

An induction-type model control system that does not require a licensed operator. Details include diagrams of the receiver and transmitter which operate on about 115 kc.

A vacuum-tube driven Tesla coil for experimental and demonstration purposes.

Also included is the usual array of receiver and TV booster diagrams along with short articles on simple servicing kinks and methods of improving reception.—*RFS* END

STAN-BURN E-P-A-R-K-E

ANTENNAE SPECIALS

DOUBLE V 3/8"	1-11	12 or more
DOUBLE V 3/8" Dowel	\$2.98	\$2.20
DOUBLE V 1/2" Dowel	3.45	2.45
10 Element Conical 3/8"	3.95	2.95
Folded Hi Straight Low Quick Rig	3.55	2.55
1/2" elements	4.25	3.25
WINDOW CONICALS	4.95	3.75

MASTS

5 FOOT SWEGDED	.79	.69
10 FOOT PLAIN	1.39	1.29

TV WIRE

42 Mil.	\$9.95 M Ft.
55 Mil. 300 OHM	14.95 M Ft.
72 OHM COAXIAL	45.00 M Ft.

CATHODE RAY TUBE SPECIALS

Standard Brands—Unconditionally Guaranteed	
GENERAL ELECTRIC	21EP4A 37.35
5TP4	43.55
7JP4	18.15
10BP4A	18.35
10FP4A	24.40
12KP4A	27.50
12LP4A	21.40
12UP4B	27.10
14CP4	20.60
16PA4A	29.10
16PP4A	26.65
16GP4	27.85
16KP4 / 16RP4	25.25
17BP4	23.90
17CP4	23.90
19AP4A	34.80
20CP4	35.45
20LP4	36.95
10BP4A	10BP4A \$14.30
12LP4A	12LP4A 17.80
14CP4	14CP4 20.35
15DP4	15DP4 22.55
16FP4	16FP4 24.85
16EP4A	16EP4A 24.85
16DP / HP4A	16DP / HP4A 24.85
16LP4A	16LP4A 24.85
16KP4A	16KP4A 24.85
17BP4	17BP4 26.05
19AP4	19AP4 28.50
20CP4	20CP4 30.80
21EP4	21EP4 32.45
16EP4A Rauland	42.00

* CHASSIS 630 REGAL with Cascade Tuner \$149.50

* OPEN FACE CABINET 39.00

SPECIALS

* 4 Prong Vibrators, each \$ 1.29

* Lots of 12 or more Special 1.19

* 12" Heavy Slug Speaker Special 4.98

* Audio Devices, Discs and Scotch Tape in Stock

* Audio Plastic Red Oxide Plastic tape—Half-hour spool \$2.30

* One-hour spool \$3.30

WIKE RECORDERS IN STOCK

* WILCOX GAY—Model 2A10 \$ 89.97

* PENTRON—Model 9T3C—2-speed Tape Recorder Net 134.50

* RADIO CRAFTSMAN Model RC2—Hi FI Amplifier Net 42.89

* Model RC10—AM-FM Tuner Net 130.84

* Model C5—Williamson Amplifier Net 99.45

AUTHORIZED DISTRIBUTORS for:

* General Electric, Kenrad, Tung-Sol, National Union, De Wald, Regal, Automatic and General Motors.

* We carry a complete stock of HI-FIDELITY and SOUND EQUIPMENT. Send us your requests. We also carry a complete line of popular makes of Radio and TV tubes, at 50% discount. Also many other special purpose and transmitting types, and all electronic parts and equipment at lowest prices.

* Send us a list of your requirements for prompt quotations.

* Terms: 20% with order. Balance COD. All prices FOB. NEW YORK Warehouse. Minimum order \$5.00.

* Write for our latest price list to Dept. RE-3 *

STAN-BURN RADIO and ELECTRONICS CO.
(C.B.S. THEATRE BLDG.)
1697 BROADWAY • NEW YORK 19, N.Y.

ON THE SPOT BATTERY RECORDER

WALKIE-RECORDALL 8 lb. miniature BATTERY RECORDER-PLAYBACK
Continuous, permanent, accurate, indexed recording at only 5c per hr. Instantaneous, permanent playback. Picks up sound up to 60 ft. Records conferences, lectures, dictation, 2-way phone & sales talks; while walking, riding or flying. Records in closed briefcase with "hidden mike"! Write for details.

MILES REPRODUCER CO., INC.
812 BROADWAY Dept. RE-3 NEW YORK 3, N. Y.

PEN-OSCIL-LITE

Extremely convenient test oscillator for all radio servicing; alignment • Small as a pen • Self powered • Range from 700 cycles audio to over 600 megacycles u.h.f. • Output from zero to 125 v. • Low in cost • Used by Signal Corps

Write for information

GENERAL TEST EQUIPMENT

38 Argyle Ave. Buffalo 9, N. Y.

FREE

Write today for "How to Service T.V. Receivers" with the HICKOK VIDEO GENERATOR.

Hickok Electrical Instrument Co.
10814 Dupont Ave., Cleveland, Ohio

LEARN TELEVISION
ELECTRONICS and RADIO
 Engineering Laboratory and Classroom
 Training, Day and Evening Classes.
Write for illustrated Catalog
ELECTRONICS INSTITUTE, Inc.
 21 HENRY, DETROIT 1, MICH.

**TV REPAIRMEN
 MAKE TOP MONEY!**
 In just 39 weeks, you can get complete TV training! Streamlined course gives you all the essentials for big job as service technician. Graduates in great demand; jobs are plentiful in this booming field. Other courses in electronics, radio operation and maintenance. Day or evening classes; modern equipment. Opportunity for employment in local industry.
Write for Catalog 111 Today
INDIANAPOLIS ELECTRONIC SCHOOL
 314 E. Washington, Indianapolis 4, Ind.

RCA INSTITUTES, INC.
 A service of Radio Corporation of America
 350 West 4th St., New York 14, N. Y.
**OFFERS COURSES IN
 ALL TECHNICAL PHASES OF
 RADIO, TELEVISION, ELECTRONICS**
 Approved for Veterans
 Write Dept. RC-53 for Catalog

RADIO-TV ELECTRONICS
 CREI graduates in big demand. Approved by Engineers' Council for Professional Development. New classes start every month. Free placement service for grads. (Courses offered—Radio Engineering (Practical or Broadcast) TV Engineering, TV, FM, AM Servicing.)
 Write for free catalog.
CAPITOL RADIO ENGINEERING INSTITUTE
 Dept. RE, 3224—16th St. N.W., Washington 10, D.C.

TELEVISION
Big demand for graduates
B.S. DEGREE IN 27 MONTHS in radio including TV engineering—VHF, UHF, AM and FM. Students use over \$100,000 worth of equipment including 2 large commercial type transmitters in new TV lab. Intense specialized course includes strong basis in mathematics, science and advanced design in radio and TV.
 Hundreds of young men each year are earning engineering degrees in this recognized institution. Start any quarter. Many earn a major part of expenses in this industrial center. Low tuition. Competent instruction. Thorough, intense, practical program.
 Also **B.S. DEGREE IN 27 MO.** in Aeronautical, Chemical, Civil, Electrical and Mechanical Engineering. G.I. Gov't approved. Enter March, June, Sept., Dec. Free catalog. **ENROLL NOW**
INDIANA TECHNICAL COLLEGE
 1733 E. Washington Blvd., Fort Wayne 2, Indiana

PHOTOGRAPHS
 RADIO-ELECTRONICS can use good photographs of service benches, service shops, high-fidelity audio layouts, and any other interesting and original radio-electronic photographs.
 We will pay \$6.00 each for good professional photos or equivalent, suitable for reproduction.
 Full information on subject photographed will increase their acceptability.
The Editor, RADIO-ELECTRONICS
 25 West Broadway, New York 7, N. Y.


**GET INTO
 ELECTRONICS**
 You can enter this uncrowded, interesting field. Defense expansion, new developments demand trained specialists. Study all phases radio & electronics theory and practice: TV, FM; broadcasting; servicing; aviation, marine, police radio. 18-month course. Graduates in demand by major companies. H.S. or equivalent required. Begin Jan., March, June, Sept. Campus life. *Write for catalog.*
VALPARAISO TECHNICAL INSTITUTE
 Dept. C Valparaiso, Ind.

Unlimited Opportunities in
RADIO ENGINEERING
DEGREE IN 27 MONTHS
 Complete Radio Engineering course including telev., U. H. F. and F. M. Bachelor of Science Degree also in Mech., Civil, Elect., Chem., and Aero. Eng.; Bus. Adm., Acct. Extensive campus, modern buildings, well equipped labs. Low cost. Prep courses. Personalized, practical instruction. Founded 1884. Placement service. Growing shortage of engineers. Prepare now. Approved for Korean vets. Enter March, June, September, January. *Write for catalog.*
TRI-STATE COLLEGE
 2433 College Ave. ANGOLA, IND.

RADIO COURSES
 • RADIO OPERATING • CODE
 • RADIO SERVICING • ELECTRONICS
 • F.M. TELEVISION
 Preparation for Civilian, Maritime, Army and Navy license requirements.
 Write for Catalog TE
YMCA TRADE & TECH. SCHOOL 15 W. 63 St., N. Y. 23
 ENdicut 2-8117

**EARN MORE MONEY—
 BE A PROFESSIONAL
 TELEVISION
 SERVICE
 TECHNICIAN**
**STEP INTO THE TOP PAY
 \$5,000—\$10,000 A YEAR
 CLASS. YOU CAN WITH
 WTI SHOP TRAINING.**
 If you want to reach your goal as a Successful Service Technician you will need plenty of "KNOW HOW" to qualify for the better servicing jobs or profitable shop ownership.
**SEND FOR
 FREE
 BOOK TODAY!**
 WESTERN TV offers real experience on live equipment in our BIG SHOPS AND LABORATORIES in the shortest practical time under expert instructors. Graduates are in big demand because they have the "field experience" necessary for immediate "bench" or supervisory positions. You learn every phase of Radio and TV servicing (AM, FM, VHF, UHF). WTI men win fast promotion... can demand better pay... develop highly profitable businesses of their own with the latest and most PRACTICAL PERSONALIZED TRAINING BEHIND THEM. You concentrate all your time on being a PROFESSIONAL TV SERVICE TECHNICIAN—non-essential math and engineering theory omitted. YOU CAN EARN WHILE YOU LEARN. Special Finance Plan. APPROVED FOR VETERANS. Find out how you can get into the TOP PAY GROUP—Send for this fact-packed book NOW!
WESTERN TELEVISION INSTITUTE America's Leading Television Servicing School
 Western Television Institute Dept. E-33
 341 W. 18th St., Los Angeles 15, Calif.
 Without obligation, please send FREE fully illustrated booklet. (No salesman will call.)
 NAME _____ AGE _____
 ADDRESS _____
 CITY _____ ZONE _____ STATE _____

Become an ELECTRICAL ENGINEER in 36 MONTHS
Bachelor of Science Degree — Major in Electronics or Power
 It is estimated by 1955 there will be at least two positions for every engineering and technician graduate. This college offers a tested plan that permits you to enter these vast employment opportunities at an early date. Save a valuable year through optional year-round study. Receive advanced credit for prior training gained in the armed forces, other schools or field experience.
ENTER BOTH RADIO AND TELEVISION 12 months or one-third of the B. S. degree course (Electronics major)—also brings you the Radio Technician's certificate. An added 6-month course qualifies you for the Radio-TV Technician's certificate. Recent developments open unlimited opportunities for TV technicians and engineers.
THE PROVEN "UNIT CHASSIS SYSTEM" of teaching was developed here. It "breaks down" the TV set by stages. You learn every component of all types and makes—and are prepared for future design changes, including the advent of color.
6 TO 12-MONTH TELEVISION SERVICE COURSE... trains for good servicing jobs and shop ownership in the shortest practical time under expert instructors.
Terms open April, July, October, January. Over 48,000 former students from all states and 23 overseas countries. Faculty of trained specialists. Modern laboratories and equipment.
 Write for free 110-page catalog, 48-page pictorial booklet "Your Career"—and "Occupational Guidance Bulletins."

MILWAUKEE SCHOOL OF ENGINEERING
 APPROVED FOR VETERANS • NONPROFIT • FOUNDED IN 1903

 Milwaukee School of Engineering
 Dept. RE-353, North Milwaukee
 Milwaukee 1, Wisconsin
 Without obligation send Catalog for Electrical Engineering, B. S. Degree, major in Electronics; Power; "Your Career"; Occupational Guidance Bulletin on: Radio-TV; Electrical Power; Welding; Heating, Refrigeration, Air Conditioning; Mechanical Engineering, B. S. Degree; Preparatory; Television Service.
 Name _____ Age _____
 Address _____
 City _____ Zone _____ State _____
 If veteran, indicate date of discharge _____

ADVERTISING INDEX

All Channel Antenna Corp.	132
Allied Radio Corp.	17
American Electrical Heater Co.	88
American Electronics Co.	127
American Radio Co.	110, 111
American Television and Radio Co.	133
Amplifier Corporation of America	136
Arky Radio Kits, Inc.	127
Astatic Corp.	99
Astron Corp.	8
Audel Publishers	122
Barry Electronics	144
Bell Telephone Labs.	28
Bionder-Tongue Labs.	95
Broach Manufacturing Co.	127
Brooks Radio and TV Corp.	128, 129
Burroughs Radio Inc.	124
Cardwell System Co.	84
Capitol Radio Engineering Institute	9
Centralab—Div. of Globe Union	12
Century Television Co.	135
Certified Radio	123
Channel Master Corp.	24, 25
Cleveland Electronics Inc.	139
Cleveland Institute of Radio Electronics	11
Columbia Wire & Supply Co.	124
Commissioned Electronics	135
Concord Radio	94
Cornell-Dubilier Electric Corp.	125
Cornish Wire Co.	128
Coyne Electrical & TV Radio School	15, 128
Crescent School	79
Davis Electronics	97
DeForest's Training, Inc.	2nd Cover
DuMont Labs., Inc.—Allen B.	120
Editors and Engineers	126
Edlie Electronics	116
Electro Devices, Inc.	19
Electro-Voice Inc.	32
Electro-Instrument Co., Inc.	102
Fair Radio Sales	3rd Cover
Federal Telephone & Radio Corp.	97
Federated Purchaser	130, 141
Filer Engineering Co.	81
Finney Co.	84
Galvanics	18
General Cement	135
General Electric Co.	142
General Industries Co.	137
General Test Equipment	140
Gonset Co.	137
Good, Inc.—Don	140
Graylock Electronic Supply Co.	137
Halldorson Transformer Co.	140
Harvard Labs.	137
Health Co.	67-77
Hickok Electrical Instrument Co.	26, 27, 142
Hi-Lo TV Antenna	108
Hughes Research and Development Labs	131
Hytron Radio & Electronic Corp.	2, 70
Indiana Technical College	130
Instructograph Co.	134
International Correspondence Schools	13
Jackson Electrical Instrument Co.	145
Jan Electronic Distributing Co.	124
Jerry Specialty Co.	106
Krylon, Inc.	14
LaPointe-Plascomold Corp.	10
Leotard Radio Corp.	103
Luther, Otto	132
Macmillan Co., The	136
Mallory and Co., Inc., P. R.	31
Manfred Electron	122
McGraw-Hill Book Co.	141
Mercury Electronic Supply	134
Merit Coil & Transformer Co.	16
Metropolitan Supply Corp.	130
Miles Reproducer Co., Inc.	142
Mosley Electronics	105
Moss Electronic Distributing Co.	121
National Electric Products Corp.	90, 91
National Radio Institute	3, 8
National Schools	5
Nidisco Radio Supply Co.	8, 25
Opportunity Adlets	141
Pennsylvania Television and Supply	127, 118
Penn Electronic Parts	94
Perma-Power Co.	120
Permo, Inc.	111
Pickering & Co.	104
Precision Development Corp.	121
Precision Apparatus Co., Inc.	107
Prentice-Hall, Inc.	116
Pres-Probe Co.	137
Progressive Electronics	109
RCA Institutes, Inc.	2
RCA Victor Division (Radio Corp. of America)	Back Cover
Radecco Manufacturing Co.	118
Radiart Corp.	93, 98
Radio City Products	130
Radio Distributing Co.	139
Radio Receptor Co., Inc.	108

RADIO SCHOOL DIRECTORY—PAGE 143

Capitol Radio Engineering Institute	9
Electronics Institute, Inc.	83
Indiana Technical College	130
Indianapolis Electronic School	131
Milwaukee School of Engineering	132
RCA Institutes, Inc.	2
Tri-State College	133
Valparaiso Technical Institute	134
Western Television Institute	135
YMCA Trade & Technical School	136
Radio-Television Training Assn.	23
Rad-Tel Tube Co.	106
Ram Electronics Sales Co.	104
Rauland Corp. The	87
Raytheon Manufacturing Co.	22
Regency Div. (I.D.E.A., Inc.)	108
Rice, Ward	100
Rider, Inc. John F.	94, 102, 133, 182
Rinehart Books, Inc.	99
Rose Co.	112
Rytel Electronic Manufacturing Co.	30, 120, 142
Sams and Co., Inc. H. W.	96
Sangamo Electric Co.	86
Scala Radio Co.	80
Schott Co., Walter	86
Service Instrument Co.	118
Skyline Manufacturing Co.	116
Simpson Electric Co.	107, 113
Sprague Products Co.	29
Sprayberry Academy of Radio	65
Stan-Burn Radio & Electronics Co.	142
Standard Transformer Corp.	100
Steve-EI Electronics Corp.	103
Supreme Publications	94
Sylvania Electric Products	6
TV Products Co.	146
Tab	132
Tallen Co., Inc.	103
Tech-Master Products	138
Technical Appliances Co.	103
Tel-Ray Enterprises, Inc.	140
Telematic Industries Inc.	133
Telesound Corporation	117
Television Communications Institute	113
Television Materials, Inc.	138
Thomas Mold and Die Co.	252
Thornton-Meister	130
Transvision, Inc.	123, 145
Triad Transformer Manufacturing Co.	89
Tri-County Manufacturing Co.	89
Triplet Electrical Instrument Co.	105
Tung-Sol Electric Co.	80
Turner Co.	80
United Technical Labs	84
Utah Radio Products Co.	84
Van Sickle Radio	127
Vee	135
Vee-D-X	10
Vidair Television Co.	123
Ward Products Corp.	85
Wells Sales	144
West Products Co.	14
Wholesale Radio Parts Co., Inc.	98

Radio-Electronics does not assume responsibility for any errors appearing in above index.

NEED ANY TUBES?

Barry for FAST-DELIVERY on all types. We carry all the standard brand Tubes individually cartoned and carry Standard RMA GUARANTEE.

Tube Orders Over \$8.00 with full remittance Prepaid To You in USA.

All tubes INDIVIDUALLY retested (not just spot-checked) on our Hickok Mutual Conductance Tube-Testers to insure you 100% perfect merchandise. For your maximum money's worth, buy in full confidence from TUBE-SPECIALISTS. Here is a partial listing of our large stocks. You may order types not listed at approx. same savings.

0A2	.90	6BE6	.55	35L6	.69
0A4G	1.00	6BG6-G	1.35	35Z5GT	.49
0B2	1.10	6BG6-G(RCA)	.42		.65
0C3 VR105	1.00		1.85	50C5	.50
0D3 VR150	.88	6BH6	1.60	50L6GT	.55
1A7GT	.89	6BQ6GT	1.20	FG-105	17.00
1AE4	.90	6BZ7	1.25	11Z26	1.00
1B3/9016	.80	6C4	.45	F-123A	6.50
1B22	2.00	6CB6	.55	211(GE)	.75
1B23	8.00	6CD6-G	1.60	250-TH(GE)	
1B27	12.50	6CMU			18.75
1L4	.60	6F8-G	.85	274-A&B	2.95
1LA6	.90	6G6-G	.85	275-A(WE)	3.00
1N21B(Syl.)	1.75	6J5GT	.45	304-TH	7.00
1N23A(WE)	2.25	6J6	.62	304-L	8.75
1N23B	3.49	6J7	.70	310-A(WE)	5.95
1N34	3.64	6K4(Syl.)	3.50	31-A(WE)	5.50
1N34A(Syl.)	.75	6K6GG	.59	328-A(WE)	5.00
1N44/400B	1.21	6K7-M	.70	349-A(WE)	1.35
1N45/400C	1.39	6L5-G	.49	359-A(WE)	4.00
1N48(GE)	.55	6L6-G	1.19	371-B	.65
1N54 (Syl.)	.77	6L6-GA	1.20	372-A(WE)	4.00
1X24	1.00	6L8-M	1.95	374-A(WE)	3.50
2C43(GE)	13.95	6L7	.80	387-A(WE)	2.50
2C52	5.50	6N7-M	.80	403-B(WE)	7.50
2D21	1.25	6Q7GT	.80	407-A(WE)	5.00
2E24	2.50	6S7-M	.98	408-A(WE)	2.75
2E30	1.95	6S7	.72	WL-417A	8.50
2J22	6.50	6S47	.69	GL-559	1.00
2J34	27.00	6S47	.62	725-A	5.50
2J49	34.00	6SK7GT	.60	805	3.25
2K25	29.50	6SL7GT	.70	807	1.59
3A4	.59	6SN7GT	.55	811	2.85
3AP1	9.00	6V6G	.55	812	2.70
3B28	7.50	6V6GT	.85	812-A	3.50
3B29	12.00	6W6GT	.88	816	1.10
3BP1	5.75	6Y6-G	.55	832-A	8.50
3BP11	9.50	6X5GT	.69	837	1.45
3C23(GE)	9.50	7A8	.69	861	15.00
3C27	7.50	7C6	.69	866A(Hyt.)	1.55
3C33	9.00	7C30	.85	872-A(GE)	3.95
3D6/1299	.50	7F7	.72	959	2.75
3E29	9.95	7H7	.50	1613	.70
3Q56T G	.99	12A6	.75	1616	1.95
3S4	.80	12A7	.62	1622(6L6M)	1.85
4C35	22.50	12A7U	.49	1625(RCA)	.70
4E27	13.00	12AV6	.57	1632	1.35
4-125A	22.00	12AX7	.57	2050(RCA)	1.10
4-250A	32.00	12BA6	.57	2051	4.50
5D21	16.75	12BE6	.75	5514(Hyt.)	3.00
5FP7	1.95	12BH7	.75	5608-A	3.95
5R4G	1.25	12SA7	.70	5645(Syl.)	8.25
5U40P4	2.15	12SF5	.65	5654	2.00
5V4G	.95	12SG7	.63	5702	3.23
5Y3GT	.42	12SJ7	.63	5744	2.25
6AB4	.75	12SK7	.60	5886	3.00
6AB7	.98	12SL7GT	.80	5814	2.95
6AC7	.77	12SN7GT	.80	5910	.75
6AG5	.65	12SR7GT	.44	8020	.98
6AG7	1.25	12SR7	.44	9001	1.85
6AH6	1.00	14F7	.44	9002	1.50
6AJ5	1.30	19AP4A(GE)	.67	9004	.35
6AK5	.70	25AV5	.67	9006	.25
6AK6	.25	25BQ6GT	.64	9003	1.50
6AN5-W	.60	25L6GT	.67	9004	.35
6AU6	.59	25Z6	.67	9006	.25
6AV6	.49	35B5	.40	AX9903	17.75
6BD6	.80	35C5	.40		

CBS—HYTRON CATHODE-RAY PICTURE TUBES

First Quality in factory-sealed cartons. Full Year Warranty Card on each tube. Remember—no seconds; no re-bins. Prices include Fed. Tax. C.R. Tubes via Express Collect.

7JP4	18.75	16KP4	28.75	17HP4	25.50
10BP4A	21.50	16TP4	30.00	20CP4A	38.50
12LP4A	21.50	16TP4A	24.75	21EP4A	38.50
14CP4	24.00	17CP4A	25.25	21FP4A	36.00
16AP4	31.00				

SELENIUM RECTIFIERS

Current (Continuous)	Full-Wave Bridge Types			
	18/14 Volts	36/28 Volts	54/42 Volts	130/100 Volts
1 Amp.	\$1.35	\$2.15	\$3.70	\$7.50
2 Amps.	2.20	3.60	5.40	10.50
2 1/2 Amps.	6.00	13.00
4 Amps.	4.25	7.95	12.95	25.25
6 Amps.	4.75	9.00	13.50	33.00
10 Amps.	6.75	12.75	20.00	40.00
12 Amps.	8.50	16.25	25.50	45.00
20 Amps.	13.25	25.50	39.00	79.50
24 Amps.	16.25	32.50	45.00	90.00
30 Amps.	20.00	38.50
36 Amps.	25.00	48.50

New, Selenium Rectifier Transformers
 PH11 115 V., 60 cycles in. } 4 Amps. \$ 8.75
 SEC-9, 12, 18, 24, and 36 } 12 Amps. 16.75
 volts } 31 Amps. 35.75

W.E. HERM. SLD. PWR XFR PRI-115V.—60 cy. SEC-930V. CT @ 520 ma and 5.2V. @ 4 amps. Brand New—Boxed—Hi-Voltage Insulation \$995

New Selenium Rectifier Chokes
 4 Amps.—.07 hy.—.6 ohm \$7.95
 12 Amps.—.01 hy.—.1 ohm \$14.95
 24 Amps.—.004 hy.—.025 ohm \$29.95

For other types of rectifiers and supplies, write

AR-11 Complete Station for 20, 40, or 80 meters Superhet Rcvr.—50 Watts CW w/built in 115 V.A.C. Pwr Supply. New—in compact suitcase (orig. cost over \$500) an excellent buy for only \$495

Trim. Model 100 "Featherweight" Headsets & Band. New, in orig. mfr.'s carton. \$495

BARRY ELECTRONICS CORP.

136 Liberty Street, N.Y. 6, N.Y. REctor 2-2562
 Terms: 25% with order, balance C.O.D.—Send a few cents for postage—All merchandise guaranteed. F.O.B. N.Y.C. *Please: minimum order \$25*

PHONE WELLS FOR ANY ELECTRONIC COMPONENTS
IMMEDIATE DELIVERY
 FROM WORLD'S LARGEST STOCK... SEELEY 8-4143

STOP COSTLY SHUT-DOWNS!
 Write for Catalog
WELLS SALES INC. 833 W. Chicago Ave., Chicago 22, Ill.



H. D. Suesholtz,
General Manager,
Transvision, Inc.

Servicemen, Technicians, secure your future —

I WILL START YOU in a WELL-PAYING TV SET BUSINESS

FOR THE AMAZINGLY SMALL INVESTMENT OF ONLY **\$9⁹⁵**

**Be a TRANSVISION Factory Agent —
and make good money full time or part time.**

Would you like to boost your income with at least \$2000 to \$5000 a year, or more? Then get on the *Transvision Factory Agent* band wagon. Here's a golden opportunity to get that extra income you've been dreaming of—without investing in merchandise or overhead.

That's right — I don't tie you up with inventory. **ALL YOU NEED** is my **SALES KIT** costing only \$9.95. This kit gives you our *3-Dimensional Illuminated Viewer*, *Natural-color Slides* displaying our complete line of gorgeous TV Sets; also our spiral-bound *Salesman's Catalog* and *price list*.

YOU CARRY NO STOCK: With my Sales Kit you sell from our million-dollar inventory. We ship either to you, or direct to your customer, as you wish. **YOU MAKE 2 INCOMES FROM EACH SALE** — profit on the set, and a fee for the installation (we expect all of our Factory Agents to be competent installation-and-service men).

YOU CAN BEAT COMPETITION: Our prices on giant screen TV sets will enable you to meet and best competition at a good profit.

YOU SELL THE FINEST SETS: You sell sets with the incomparable RCA-licensed 630 Chassis — the finest on the market — or the famous fine-quality Transvision A4 Chassis. You have a wider sales range — a greater choice of *Table Models*, *Consoles*, *Combinations*, in screen sizes from 17" to 21". You have a set and a price for every prospect.

SECURE YOUR FUTURE: Don't lose time. Get started making more money now. Fill out and mail the coupon to me — **TODAY!**




CLINCH SALES
in prospect's home
with my 3-Dimensional
Illuminated Viewer,
Natural Color Slides,
and Salesman's Catalog.



We offer the LATEST, 31-tube
630 TYPE RCA licensed CHASSIS
with High-Fidelity Sound

This famous Chassis offers many exclusive features, including . . . high-fidelity sound . . . flat response, 60-12,000 cycles . . . push-pull amplifier . . . 31 tubes (27 tubes, picture tube, 3 rectifier tubes) . . . designed for optimum UHF performance . . . handles all picture tubes up to 24" . . . made with only the finest parts . . . carries standard RMA Guarantee.

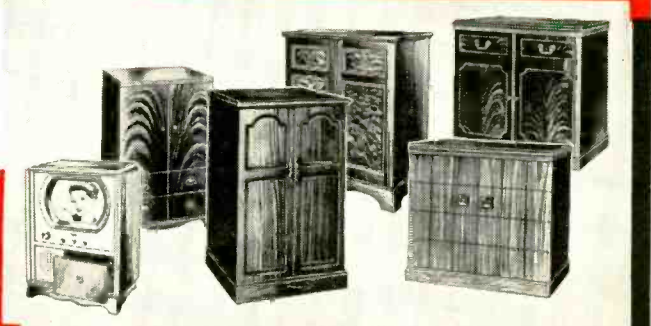Buy this great Chassis direct from my factory.



BEAUTIFUL, IRRESISTIBLE CABINETRY: This illustration is only suggestive of our vast line of gorgeous TV Sets. Get the **SALES KIT**. See the *Natural-Color Slides*. You'll agree that Transvision offers the hottest TV deal in the entire industry!



TRANSVISION, INC.
NEW ROCHELLE, N. Y.
NE 6-6000

**RUSH THIS
COUPON NOW** →

Mr. H. D. Suesholtz, Gen. Mgr.
TRANSVISION, INC., NEW ROCHELLE, N. Y. Dept. RE3T

I enclose \$9.95 for your complete SALES KIT.

I like the idea but would appreciate more details.

Name _____

Address _____

City _____ State _____

AUDIO AMPLIFIERS READY TO GO

Model 305MP 5 Watt Ampl. as Pictured Above Features Mike & Phono Inputs, W. 50db Gain Control, Latest Compensated Tone Control Design. Complete with Tubes. \$14.98
Model 2000M Mike OSC. Broadcasts Through Your Radio with No Direct Connection. \$6.98
Model 1000P Phono OSC. Phonograph Broadcasts Through Your Radio. No Direct Hookup. W/Tube. \$4.98
Model 302PA 3 Tube Phono Ampl. Ideal for Custom Building Your Phonograph. W/Tubes. \$4.98

AUDIO COMPONENTS

GE CRP3 Phono Cart. \$2.49
GE RPX05 Tone Play Cart. 5.69
Electrovoice Triple Play. 2.69
Pickup Arm & Xtal Hi-Output 2.39
PM 12" Hi-Fi Driver Speaker 4.98
PM 12" GE S120D Speaker 19.00
PM 8" Blue ST18-1 Permuflex 13.00
PM 5" Speaker-Gud Tone 1.98
PM 10" Hi-Fi Woofer & Separate Horn Tweeter. 10 Watt 40-20 Kc. 19.98
Crystal Mike. 1.98
Crystal Mike Cartridge (Label Type). 2.98
Crystal Mike Cart. Ceramic Wetpur. 3.98

TELEVISION ANTENNA

TV CONICAL ANTENNA All Channel Sturdy Prefab Const. Inclds 8 elements & 100 Ft. Copper Twinned Cross Bar & Hardware. Brand New \$15.98
DUBL-STACK CONICAL ARRAY. 16 Elements Hardware, 2 Crossbars & 100 Ft. All Copper Twinned. \$19.98
DOUBLE V Ant. All Channel. Sturdy Const. w/Mtg Clamps & 100 Ft. All Copper Twinned. \$14.49
WINDOW CONICAL ANT. All Channel. Hwy Duty Const. Mounts outside your windows. Special 12 Element. \$3.95
5 FOOT Interlocking Mast Sections. Hwy Duty Painted. rustproof. 95c

866A KIT and XFORMER
2 Tubes, Sects, xmfr, 115V/60Hz Inpt, output 2.5vct/10A, 3 Hivts. \$5.49

KITS AND COMPONENTS

SPRGE CRP3 Vert Integrator Netwk 3 Res CNDRSLT. \$2.49
CERAWIC 2X.004 mfd/500V 6 for 1.00
VARIAC 200CU 5A Reconditioned. 14.98
AC BUCCO BUZZER. 9 @ 5 for 2.00
10 PWR Magnifier & Condr. 2.00
100 Ohm to 2 Meg. 10 for 2.50
Resistors, 1/2 & 1W, to 2 Megs. 100 for 1.98
1/2 W. 100 Ohm to 2 Meg. 10 for 2.50
Resistors, Ass'd. B. 7, 5, 4P. 25 for 2.49
Rotary Switches, Ass'd. 6 for 1.75
Ceramic Condens. 12 for 1.98
Electrolytic Condensers, Ass'd. 25 for 4.98
Oil Condensers, Ass'd. 25 for 4.98
Resistors, 2 Watt, Ass'd. 25 for 2.49

METER SPECIALS

0-300DC Aircraft Type "AN" as illustrated. \$1.95; 3 for \$5.25
0-25 MA DC Weston. \$6.98
0-500AC AC type. \$3.25; 3 for \$9.00
0-240VAC "AN" type. \$3.49; 3 for \$9.75
0-20 3VU Weston 30V. \$1.98
Indicator. Brand New \$14.98

CIRCULAR SLIDE RULE

Equiv to 12"-Only 2 1/2" Radius. LAMINATED-Print Slides On Mult. Div. Scales. Cases & Books. Logarithmic Equiv. 98c
Parallel Rules. Precision Drafting Tool Mr. BRUNING 6" wide. For Radiomen, Engineers, Students-Unsurpassed for Quick CRT Diagrams. SPECIAL \$3.9c; 3 for \$11.00

TEST EQUIPMENT

Model 102-Pocket multimeter features: AC/DC 10 rngs to 3000V, AC current: 3 rngs to 600 ma, DC current: 4 rngs to 1.2 amps, ohms 10 to 1000hm. Compact, accurate & durable construction. Std mfr. "TAB" GTD display model. \$13.98
SPECIAL Post Paid. \$13.98
Model 106-Vacuum tube volt meter. Features include: AC/DC 10 rngs to 1000V, ohms 5 ranges to 1000 megohms, 5 dB ranges, AC freq. response 25 to 100,000 cycles. Designed for field alignment of Radio sets. Std mfr. "TAB" GTD display model. SPECIAL Post Paid. \$33.49
Model 106-10 kV Voltmeter. SPECIAL Post Paid. \$22.98
Model HVP-30,000 Volt probe for model 106. Display model "TAB" GTD. SPECIAL Post Paid. \$8.25
Model 206P-Real Mutual Conductance Tube Tester. Checks all latest tubes. Industrial, Radio & TV types. Tests all elements for gas, shorts, opens & leakage. Meter 4 1/2" reads Microhms, English Scales Reject & Good. Roller Chart. GTD Includes Factory Warranty & New Test Information as available. "TAB" GTD Display Model. \$80.00
Write For Test Equip Pamphlet

TELEVISION COMPONENT BUIS

Horiz Def Output & HiVols xmfr SIM RCA 211T5. For 12"-18" picture tubes. \$1.98
Width Control similar RCA 201R4. \$1.39
HiVoltage Condenser 500MFD 15KV. .65
HiVoltage Condenser 500MFD 20KV. .75
ION TRAP permit. \$1.00
RGS50 Cable per ft. .08; 100 ft. \$5.98
300 ohm All Copper TELEVISION TWIXEN SPECIAL-100 Ft \$1.49; 1000 Ft \$12.49

MODEL HF-1 OSCILLOSCOPE

Laboratory Features. 5 M C Bandwidth, 10V Sens. PP Horiz & Vert Amp. 5 Cathode Coupled Multi Vib. Swp. Int. Traces, Cathode Flyer Input Vert & Horiz Amp. Non-Freq Discrim Gain Control, Cal Compensated Attenuator, Sync Pos Neg Input or External. Inbuilt Cathode P1W for Sig Tracing with Phones, Integral Cath Voltage Tech Manual. All Data Diagrams, 13 Tubes. Complete-Incl 3HP C-Ray Tube. Write for Complete Data. A "TAB" SPECIAL only \$99.50

"TAB" THAT'S A BUY

FUSES & HOLDERS
3AG: 1/4, 1/2 Amp. Ea. 5c; 100 for 3.98
3AG: 1 1/2, 2, 3, 4, 15, 20 Amp. Ea. 3c
3AG: 50-100, 20 Amp. 7c; 100 for 5.98
4AG: BUSS 10 Amp. Ea. 7c; 100 for 3.98
4AG: 1/4, 1/2 Amp. Ea. 7c; 100 for 3.98
4AG: 3, 5, 10, 15 Amp. Ea. 5c; 100 for 3.98
4AG: 35, 40 Amp. Ea. 5c; 100 for 3.98
HOLDER 1075 Littlefuse 20c; 10 for 1.75
HOLDER Dual 3 or 4 Ag. 15c; 100 for \$1.00

ONE YEAR GTD PICTURE TUBES
10 B14 \$13.98
10 B14A 14.49
12" Glass 17.95
12" Metal 21.98
14" Rectangular 20.95
16" Glass 22.95
16" Metal 23.98
17" Rectangular 23.49
19" Round 27.98
20" Rectangular 29.95
21" Rectangular 30.95

Your old pict. tube is worth money, write for trade-in allowance on RMA coded and dated tubes with one year guarantee. Ship your defective tube, we'll refund only. When ordering metal tube, defective metal tube is required.

BENCH TOOLS

Pliers 6" Long Nose Side Cutters. 89c
Pliers 6" Bench Cutter. 89c
Pliers Linesman 7" Heavy Duty. 79c
All (3) Pliers Listed Above \$2.25
Screw Driver Set 6 Pcs. Plastic Handle, Hardened Tempered Steel. Special. 98c
Utility Screw Driver Set 3 Standard & 3 Special. Interchangeable Blades. \$1.98
W.Wrap Around Plastic Case. .79c
12 Piece Drill Set, 1/16" to 1/2" Vana-dium Speed Steel. Std. Length. \$3.49
29 Piece Drill Set, 1/16" to 1/2" Vana-dium Speed Steel. Std. Length. \$8.98
Spiral Ratchet Screw Driver & Drill, W/2 Inl Bits & 1 Sd Blade. \$2.25

PHOTOFLASH CONDENSERS

100MFD 500VDC C. Dubilier. \$2.69
200MFD 450VDC C. Dubilier. 2.89
300MFD 450VDC C. Dubilier. 4.29
15MFD 430VDC 1500VDC Intermitt. 2.38
45MFD 350VAC 1500VDC Intermitt. 6.49
16MFD 600VAC 2800VDC Intermitt. 6.95
16MFD 660VAC 3000VDC Intermitt. 7.95
32MFD 1.2KVDC 23W. Sec. 7.49
27MFD 1.2KVDC 24VDC Int. 54W. Sec. 8.95

TAB "SUN-FLASH" LAMPS

Replaces Max. Each
USW GE FT105 100 5.98
1110 GE FT114 100 7.25
1115 ANGLO 5804X 100 10.98
23ST GE FT 210 100 8.98
39GT GE FT 403 500 13.50
S1V SLV 4330 200 9.98
24MT FT 214 250 9.98
22ST FT 110 200 9.98
353GT FT 103 500 49.98
X100 X100 1000 49.98
SPRGFA100 1500 9.00

Write for Complete "TAB"FTLITE" Data Booklets. Ex. Hics. Units for Local parts centers & accessories. We Buy Sell & Swap.

TABOGRAM WRITE FOR IT WE STOCK LARGE VARIETY OF COMPONENTS, TELL US YOUR NEEDS, SEND US YOUR TUBES & EQUIPMENT

TUBES

Table listing various vacuum tube models and their prices, including 0A2, 6X4, 6AV6, 6BE6, 6BD5GT, 6BE6, 6BE5, 6BE4, 6BE3, 6BE2, 6BE1, 6BE0, 6BE, 6B5, 6B4, 6B3, 6B2, 6B1, 6B0, 6A5, 6A4, 6A3, 6A2, 6A1, 6A0, 6A, 6, 5, 4, 3, 2, 1, 0.

"HO" RAIL PACK
0 to 12 VDC/2 Amp. Variable DC supply, unregulated and completely built-inpt. 115V/60 cy. Usable LAB supply, eliminates D. C. plug-in, battery charging, model railroad, includes voltage or speed control and auto off reversing sw. Ideal for two "HO" locomotives. \$10.95 2 for \$20.00

SELENIUM RECTIFIERS

We specialize in Rectifiers and Power supplies to your specifications. Immediate delivery.
Current 18/14 36/28 54/40 130/100 (cont.) Volts Volts Volts
1AMP 1.35 2.15 3.70
2AMP 2.20 3.60 6.00
4AMP 4.25 7.95 12.95 10.50
10AMP 6.75 12.75 20.00 25.25
12AMP 8.50 16.25 25.50 45.00
20AMP 13.25 25.50 39.00 79.50
24AMP 16.25 32.50 45.00 90.00
30AMP 20.00 38.50
36AMP 25.00 48.50
Full-Wave Seton Rect & Trans. in Kit Form All 115V/60 cy inputs
up to 14VDC at 12 amps. \$18.98
up to 24VDC at 12 amps. \$28.98
up to 28VDC at 48 amps. \$117.00

RECTIFIER XFMRs

18.8-19.2-20.4-21.4Volts 12Amp \$10.98
31-32-34-36Volts 12Amp 2 Kvins. 13.98
12-18-24-30-36-42-48-60-72-84-96-108-120-132-144-156-168-180-192-204-216-228-240-252-264-276-288-300-312-324-336-348-360-372-384-396-408-420-432-444-456-468-480-492-504-516-528-540-552-564-576-588-600-612-624-636-648-660-672-684-696-708-720-732-744-756-768-780-792-804-816-828-840-852-864-876-888-900-912-924-936-948-960-972-984-996-1008-1020-1032-1044-1056-1068-1080-1092-1104-1116-1128-1140-1152-1164-1176-1188-1200-1212-1224-1236-1248-1260-1272-1284-1296-1308-1320-1332-1344-1356-1368-1380-1392-1404-1416-1428-1440-1452-1464-1476-1488-1500-1512-1524-1536-1548-1560-1572-1584-1596-1608-1620-1632-1644-1656-1668-1680-1692-1704-1716-1728-1740-1752-1764-1776-1788-1800-1812-1824-1836-1848-1860-1872-1884-1896-1908-1920-1932-1944-1956-1968-1980-1992-2004-2016-2028-2040-2052-2064-2076-2088-2100-2112-2124-2136-2148-2160-2172-2184-2196-2208-2220-2232-2244-2256-2268-2280-2292-2304-2316-2328-2340-2352-2364-2376-2388-2400-2412-2424-2436-2448-2460-2472-2484-2496-2508-2520-2532-2544-2556-2568-2580-2592-2604-2616-2628-2640-2652-2664-2676-2688-2700-2712-2724-2736-2748-2760-2772-2784-2796-2808-2820-2832-2844-2856-2868-2880-2892-2904-2916-2928-2940-2952-2964-2976-2988-3000-3012-3024-3036-3048-3060-3072-3084-3096-3108-3120-3132-3144-3156-3168-3180-3192-3204-3216-3228-3240-3252-3264-3276-3288-3300-3312-3324-3336-3348-3360-3372-3384-3396-3408-3420-3432-3444-3456-3468-3480-3492-3504-3516-3528-3540-3552-3564-3576-3588-3600-3612-3624-3636-3648-3660-3672-3684-3696-3708-3720-3732-3744-3756-3768-3780-3792-3804-3816-3828-3840-3852-3864-3876-3888-3900-3912-3924-3936-3948-3960-3972-3984-3996-4008-4020-4032-4044-4056-4068-4080-4092-4104-4116-4128-4140-4152-4164-4176-4188-4200-4212-4224-4236-4248-4260-4272-4284-4296-4308-4320-4332-4344-4356-4368-4380-4392-4404-4416-4428-4440-4452-4464-4476-4488-4500-4512-4524-4536-4548-4560-4572-4584-4596-4608-4620-4632-4644-4656-4668-4680-4692-4704-4716-4728-4740-4752-4764-4776-4788-4800-4812-4824-4836-4848-4860-4872-4884-4896-4908-4920-4932-4944-4956-4968-4980-4992-5004-5016-5028-5040-5052-5064-5076-5088-5100-5112-5124-5136-5148-5160-5172-5184-5196-5208-5220-5232-5244-5256-5268-5280-5292-5304-5316-5328-5340-5352-5364-5376-5388-5400-5412-5424-5436-5448-5460-5472-5484-5496-5508-5520-5532-5544-5556-5568-5580-5592-5604-5616-5628-5640-5652-5664-5676-5688-5700-5712-5724-5736-5748-5760-5772-5784-5796-5808-5820-5832-5844-5856-5868-5880-5892-5904-5916-5928-5940-5952-5964-5976-5988-6000-6012-6024-6036-6048-6060-6072-6084-6096-6108-6120-6132-6144-6156-6168-6180-6192-6204-6216-6228-6240-6252-6264-6276-6288-6300-6312-6324-6336-6348-6360-6372-6384-6396-6408-6420-6432-6444-6456-6468-6480-6492-6504-6516-6528-6540-6552-6564-6576-6588-6600-6612-6624-6636-6648-6660-6672-6684-6696-6708-6720-6732-6744-6756-6768-6780-6792-6804-6816-6828-6840-6852-6864-6876-6888-6900-6912-6924-6936-6948-6960-6972-6984-6996-7008-7020-7032-7044-7056-7068-7080-7092-7104-7116-7128-7140-7152-7164-7176-7188-7200-7212-7224-7236-7248-7260-7272-7284-7296-7308-7320-7332-7344-7356-7368-7380-7392-7404-7416-7428-7440-7452-7464-7476-7488-7500-7512-7524-7536-7548-7560-7572-7584-7596-7608-7620-7632-7644-7656-7668-7680-7692-7704-7716-7728-7740-7752-7764-7776-7788-7800-7812-7824-7836-7848-7860-7872-7884-7896-7908-7920-7932-7944-7956-7968-7980-7992-8004-8016-8028-8040-8052-8064-8076-8088-8100-8112-8124-8136-8148-8160-8172-8184-8196-8208-8220-8232-8244-8256-8268-8280-8292-8304-8316-8328-8340-8352-8364-8376-8388-8400-8412-8424-8436-8448-8460-8472-8484-8496-8508-8520-8532-8544-8556-8568-8580-8592-8604-8616-8628-8640-8652-8664-8676-8688-8700-8712-8724-8736-8748-8760-8772-8784-8796-8808-8820-8832-8844-8856-8868-8880-8892-8904-8916-8928-8940-8952-8964-8976-8988-9000-9012-9024-9036-9048-9060-9072-9084-9096-9108-9120-9132-9144-9156-9168-9180-9192-9204-9216-9228-9240-9252-9264-9276-9288-9300-9312-9324-9336-9348-9360-9372-9384-9396-9408-9420-9432-9444-9456-9468-9480-9492-9504-9516-9528-9540-9552-9564-9576-9588-9600-9612-9624-9636-9648-9660-9672-9684-9696-9708-9720-9732-9744-9756-9768-9780-9792-9804-9816-9828-9840-9852-9864-9876-9888-9900-9912-9924-9936-9948-9960-9972-9984-9996-10008-10020-10032-10044-10056-10068-10080-10092-10104-10116-10128-10140-10152-10164-10176-10188-10200-10212-10224-10236-10248-10260-10272-10284-10296-10308-10320-10332-10344-10356-10368-10380-10392-10404-10416-10428-10440-10452-10464-10476-10488-10500-10512-10524-10536-10548-10560-10572-10584-10596-10608-10620-10632-10644-10656-10668-10680-10692-10704-10716-10728-10740-10752-10764-10776-10788-10800-10812-10824-10836-10848-10860-10872-10884-10896-10908-10920-10932-10944-10956-10968-10980-10992-11004-11016-11028-11040-11052-11064-11076-11088-11100-11112-11124-11136-11148-11160-11172-11184-11196-11208-11220-11232-11244-11256-11268-11280-11292-11304-11316-11328-11340-11352-11364-11376-11388-11400-11412-11424-11436-11448-11460-11472-11484-11496-11508-11520-11532-11544-11556-11568-11580-11592-11604-11616-11628-11640-11652-11664-11676-11688-11700-11712-11724-11736-11748-11760-11772-11784-11796-11808-11820-11832-11844-11856-11868-11880-11892-11904-11916-11928-11940-11952-11964-11976-11988-12000-12012-12024-12036-12048-12060-12072-12084-12096-12108-12120-12132-12144-12156-12168-12180-12192-12204-12216-12228-12240-12252-12264-12276-12288-12300-12312-12324-12336-12348-12360-12372-12384-12396-12408-12420-12432-12444-12456-12468-12480-12492-12504-12516-12528-12540-12552-12564-12576-12588-12600-12612-12624-12636-12648-12660-12672-12684-12696-12708-12720-12732-12744-12756-12768-12780-12792-12804-12816-12828-12840-12852-12864-12876-12888-12900-12912-12924-12936-12948-12960-12972-12984-12996-13008-13020-13032-13044-13056-13068-13080-13092-13104-13116-13128-13140-13152-13164-13176-13188-13200-13212-13224-13236-13248-13260-13272-13284-13296-13308-13320-13332-13344-13356-13368-13380-13392-13404-13416-13428-13440-13452-13464-13476-13488-13500-13512-13524-13536-13548-13560-13572-13584-13596-13608-13620-13632-13644-13656-13668-13680-13692-13704-13716-13728-13740-13752-13764-13776-13788-13800-13812-13824-13836-13848-13860-13872-13884-13896-13908-13920-13932-13944-13956-13968-13980-13992-14004-14016-14028-14040-14052-14064-14076-14088-14100-14112-14124-14136-14148-14160-14172-14184-14196-14208-14220-14232-14244-14256-14268-14280-14292-14304-14316-14328-14340-14352-14364-14376-14388-14400-14412-14424-14436-14448-14460-14472-14484-14496-14508-14520-14532-14544-14556-14568-14580-14592-14604-14616-14628-14640-14652-14664-14676-14688-14700-14712-14724-14736-14748-14760-14772-14784-14796-14808-14820-14832-14844-14856-14868-14880-14892-14904-14916-14928-14940-14952-14964-14976-14988-15000-15012-15024-15036-15048-15060-15072-15084-15096-15108-15120-15132-15144-15156-15168-15180-15192-15204-15216-15228-15240-15252-15264-15276-15288-15300-15312-15324-15336-15348-15360-15372-15384-15396-15408-15420-15432-15444-15456-15468-15480-15492-15504-15516-15528-15540-15552-15564-15576-15588-15600-15612-15624-15636-15648-15660-15672-15684-15696-15708-15720-15732-15744-15756-15768-15780-15792-15804-15816-15828-15840-15852-15864-15876-15888-15900-15912-15924-15936-15948-15960-15972-15984-15996-16008-16020-16032-16044-16056-16068-16080-16092-16104-16116-16128-16140-16152-16164-16176-16188-16200-16212-16224-16236-16248-16260-16272-16284-16296-16308-16320-16332-16344-16356-16368

DOWN GO CALL-BACKS

UP GO PROFITS

That's why . . .



Federal **TV** PICTURE TUBES

**... ARE THE REPLACEMENT
CHOICE OF MORE AND MORE
SERVICEMEN**

**Federal tubes are designed right, made
right, factory-tested to the hilt . . . and
BACKED BY A YEAR'S GUARANTEE!**

FEDERAL is fast-growing in demand as a *profitable* picture tube replacement, because Federal goes the limit to assure your customers *steady satisfaction!*

Every Federal tube must measure up to exacting standards of efficiency for breakdown and stray emission (at max. ratings), ion trap current, central grid cut-off, zero bias beam current, focus voltage current, highlight brightness, leakages, shorts, gas ratio, screen and glass quality . . . plus other characteristics. Tests include the tough 500-hour operation run.

Moreover, a unique, prior-to-shipment check-up follows a 24-hour minimum storage period—*an extra provision for trouble-free performance!*

Start now to protect *your* replacement profits with Federal picture tubes . . . the tubes backed by decades of experience in producing highest-quality vacuum tubes for broadcast, military communications and other major uses.

Consult your Federal distributor for full information and prices.

FEDERAL POPULAR-SIZE TUBES INCLUDE: 12½ and 16-inch round; 14, 16, 17, 20 and 21-inch rectangular. Write for your free copy of Federal's Television Picture Tube Data Book.

Federal
Telephone and Radio Corporation



VACUUM TUBE DIVISION • 100 KINGSLAND ROAD, CLIFTON, NEW JERSEY
In Canada: Federal Electric Manufacturing Company, Ltd., Montreal, P. Q.
Export Distributors: International Standard Electric Corp., 67 Broad St., N. Y.

"Federal always has made better tubes"

AS A RESULT OF YOUR CALL

*The show
goes on...*

YOU'VE just finished a routine call. Just a few adjustments . . . a couple of tubes . . . and the set works as good as new. Nice the way folks smile appreciatively when you bring that missing picture back to their screen.

Now you've got yourself another steady customer. You know they'll remember you . . . and recommend you to their friends . . . because they're enjoying the finest picture their set can produce. And the RCA Tubes you installed will continue to provide them with long, faithful service. The superior quality of RCA Tubes and Kinescopes is your best measure of protection against the costliness and inconvenience of premature tube failures. It's good to know you can service a receiver . . . and forget about call-backs.

Safeguarding your reputation is a vital, everyday service of RCA Tubes. And that service is yours at no extra charge.



RADIO CORPORATION of AMERICA
ELECTRON TUBES

HARRISON, N. J.