

TRANSISTORIZED WIRELESS MIKE

JUNE 1956

# RADIO — ELECTRONICS

TELEVISION • SERVICING • HIGH FIDELITY

HUGO GERNSBACH, Editor

Simple Alignment  
of  
Broadcast Radios

•  
All-Transistor  
Amplifier  
Has High Gain

•  
Radiation Meter  
for Civil Defense

•  
Understand Your  
Color Bar Generator

•  
Servicing  
Intercarrier Buzz



**35¢**  
U. S. and  
CANADA


Now—A Module  
See p

FULTON T V 3-57  
% PAUL S BOLLARO  
434 FULTON ST  
ELIZABETH 1 N J



ANOTHER **FIRST** FOR **RAYTHEON**

**BONDED ELECTRONIC TECHNICIANS**

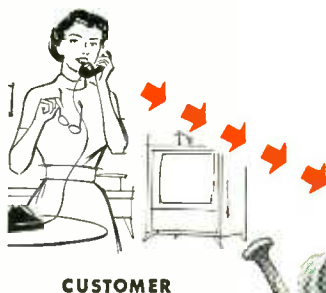

CUSTOMER



RAYTHEON BONDED SERVICE DEALER

**WESTERN UNION**  
**"Operator 25"**  
**will recommend them to more customers**

Something new — and very important — has been added to the sales force of Raytheon Bonded Electronic Technicians. It's "Operator 25". Customers seeking Radio-TV Service simply call Western Union by number and ask for "Operator 25". In answer to their request for a reliable source of bonded service, "Operator 25" gives them the name and phone number of the nearest Raytheon Bonded Dealer. That means more business — exclusive business — for Raytheon Bonded Electronic Technicians.

This customer producing new sales advantage, plus the cash-protection of the Raytheon Bond,

the Raytheon Bonded Certificate, ID Cards, Decals, Raytheon Creed Displays, the Raytheon Code of Ethics, Classified Telephone Directory listings, all backed by sound, hard-hitting national advertising in LIFE, TIME, NEWSWEEK and TV GUIDE — make the Raytheon Bonded Electronic Technician Program the most powerful sales force a service dealer can have.

Call your sponsoring Raytheon Tube Distributor and ask him if you can qualify as a Raytheon Bonded Dealer.

If you can, you're well on your way to more volume and profit.




**RAYTHEON MANUFACTURING COMPANY**

*Receiving and Cathode Ray Tube Operations*

Newton, Mass. • Chicago, Ill. • Atlanta, Ga. • Los Angeles, Calif.

Raytheon makes all these { Receiving and Picture Tubes, Reliable Subminiature and Miniature Tubes, Semiconductor Diodes and Transistors, Nucleonic Tubes, Microwave Tubes



*Excellence in Electronics*

# You Can Train at Home for Good Jobs, Career Opportunities

## Find out What N.R.I., Oldest, Largest, Home Study Radio-TV School can do for You

Whether you're on the "OUTSIDE" and want to get in; or on the "INSIDE" and want to advance, N.R.I. has specialized training for you.



J. E. Smith,  
Founder

Training plus opportunity is the ideal combination for success. And today's opportunity field is Radio-Television. Over 125 million home radios plus 30 million sets in cars plus 40 million TV sets mean top money, top jobs for trained Radio-TV technicians. More than 4,000 Radio and TV broadcasting stations offer interesting and important positions for technicians, operators. Color television, portable TV sets, Hi-Fi, other developments, assure future growth.

### N.R.I. is Tested Way to Better Pay

If you want to gain knowledge and skill for success and security, find out what N.R.I. offers. Since 1914—for more than 40 years—N.R.I. has specialized in training ambitious men at home in spare time for Radio-TV. As the outstanding leader, you are assured dependable training when you enroll with N.R.I. You are backed by the record and reputation of the oldest and largest home study Radio-TV school. With an N.R.I. diploma, you command respect because you are a skilled operator equipped to do important work.

### Add to Your Income Starting Soon

Whether you know very little or whether you have some knowledge of Radio-TV, N.R.I. training can help you. We send you easy-to-understand, illustrated texts. As part of our Servicing Course you get many kits to build Radio Receiver, Multi-tester, other equipment that "brings to life" what you study. Soon after starting many N.R.I. Students earn \$10, \$15 a week extra fixing neighbors' sets in spare time.



N.R.I. SUPPLIES EQUIPMENT FOR PRACTICAL EXPERIENCE. 17" picture tube, all tubes, parts to build UHF-VHF Television Receiver, a 5" high definition Oscilloscope and a Television Signal Generator supplied with Advanced TV Training.

N.R.I. Communications Training provides the practical knowledge you need for a career in Broadcasting. We send kits to build a Transmitter, Signal Generator, etc.; practice methods, procedures required of licensed Commercial Radio-TV operators.

### TV Service Experts Earn Top Pay, Top Jobs

N.R.I.'s All Practice Professional TV Servicing Course is designed for the man who wants to reach the top in TV Servicing. Not for beginners, this course is for the man with a knowledge of basic theory, either from Radio-TV servicing experience or planned training. We send

you 17" picture tube, components for TV Receiver, 5" TV Oscilloscope and a TV Signal Generator. You learn methods to diagnose and correct TV Service problems quickly, correctly, with confidence.

### Sample Lesson and Catalog Sent FREE

Mail coupon today. Check the Radio-Television Training that interests you. We will send you Sample Lesson and Catalog. Address: National Radio Institute, Dept. 6FF, Washington 9, D.C.

## MAIL COUPON NOW

**NATIONAL RADIO INSTITUTE, Dept. 6FF, Washington 9, D.C.**

Please send information on opportunities and training checked below. (No salesman will call.)

Radio-TV Servicing Training.

Radio-TV Communications Training.

Advanced TV Servicing.

Name-----Age-----

Address-----

City-----Zone-----State-----

**VETS: Write in date of discharge** . . . . .

Approved Member, National Home Study Council



# RADIO - ELECTRONICS

Formerly RADIO CRAFT • Incorporating SHORT WAVE CRAFT • TELEVISION NEWS • RADIO & TELEVISION\*

Hugo Gernsback  
Editor and Publisher  
M. Harvey Gernsback  
Editorial Director  
Fred Shunaman  
Managing Editor  
Robert F. Scott  
W2PWW, Technical Editor  
Jerome Kass  
Associate Editor  
I. Queen  
Editorial Associate  
Matthew Mandl  
Television Consultant  
Elizabeth Stalcup  
Production Manager  
Angie Pascale  
Editorial Production  
Wm. Lyon McLaughlin  
Tech. Illustration Director  
Sol Ehrlich  
Art Director

Lee Robinson  
General Manager  
John J. Lamson  
Sales Manager  
G. Aliquo  
Circulation Manager  
Adam J. Smith  
Director, Newsstand Sales  
Robert Fallath  
Promotion Manager

## GERNSBACK PUBLICATIONS, INC.

Executive, Editorial and Advertising Offices, 154 West 14 St., New York 11, N. Y. Telephone ALgonquin 5-7755.

Hugo Gernsback  
Chairman of the Board  
M. Harvey Gernsback  
President  
G. Aliquo  
Secretary

## ON THE COVER

(Story on page 37)

The new Emerson modular TV receiver, first of its kind to reach the public. In the foreground are two typical modular circuit boards.

Color original by Habershaw Studios



Average Paid Circulation over 175,000

JUNE 1956

Vol. XXVII, No. 6

## Editorial

Electronics in Space Flight.....by Hugo Gernsback 29

## Audio—High Fidelity

High-Gain Transistor Audio Amplifier.....by Joseph Braunbeck 30

Servicing Home Tape Recorders, Part II.....by Herman Burstein 32

For Golden Ears Only: Browning L-500 tuner; Crestwood 404 tape recorder and amplifier-speaker; tape splicer; two ribbon micro-phones.....by Monitor 34

Transistorized Wireless Mike.....by Elliott McCready 36

## Television

Modular TV Receiver (Cover Feature).....by Fred Shunaman 37

Government TV-Set Certification Program.....by David Lachenbruch 39

Troubleshooting AGC Circuits, Part II.....by Cyrus Glickstein 40

Servicing Intercarrier Buzz.....by James A. McRoberts 42

Dramatic High-Voltage Demonstrator.....by L. H. Wilson 43

TV Service Clinic.....Conducted by Jerry Kass 44

Most Useful TV Circuits of 1956.....46

## Test Instruments

Understand Your Color Bar Generator.....by Robert Middleton 52

Preset AF Calibrator.....by I. Queen 56

Hazard on the Bench.....by B. W. Welz 57

## Electronics

Electronics in the Air Force.....by Ronald A. Lane 58

Civil Defense Radiation Meter.....by Edwin N. Kaufman 73

## What's New

.....76

## Radio

Transistor Radios, Part I.....by I. Queen 78

Aligning Broadcast Receivers.....by James E. Dalley 80

50-240 mc Converter-Receiver Using Helical Type Inductuner.....84

Identifying Transistors.....by Henry A. Kampf 88

## DEPARTMENTS

Books.....124

Business.....116

Corrections.....120

Correspondence.....10

Miscellany.....93

New Devices.....94

New Records.....91

New Tubes and Transistors.....99

Patents.....103

People.....119

Question Box.....110

Radio Month.....6

Radio-Electronic Circuits.....113

Technical Literature.....122

Technicians' News.....101

Technotes.....105

Try This One.....108

Associate Member of Institute of High Fidelity Mfrs., Inc.



RADIO-ELECTRONICS, June, 1956, Vol. XXVII, No. 6. Published monthly at Mt. Morris, Ill., by Gernsback Publications, Inc. Second-class mail privileges authorized at Mt. Morris, Ill. Copyright 1956 by Gernsback Publications, Inc. All rights reserved under Universal, International and Pan-American Copyright Conventions.

SUBSCRIPTIONS: Address correspondence to Radio-Electronics, Subscription Dept., 404 N. Wesley Ave., Mt. Morris, Ill., or 154 West 14 St., New York 11, N. Y. When ordering a change please furnish an address stencil impression from a recent wrapper. Allow one month for change of address.

SUBSCRIPTION RATES: U. S., U. S. possessions and Canada, \$3.50 for one year; \$6.00 for two years; \$8.00 for three years; single copies 35c. Pan-American countries \$4.00 for one year; \$7.00 for two years; \$9.50 for three years. All other countries \$4.50 a year; \$8.00 for two years; \$11.00 for three years.

BRANCH ADVERTISING OFFICES: Chicago: 1413 Howard St. Tel. ROGers Park 4-8000. Los Angeles: Ralph W. Harker and Associates, 600 South New Hampshire. Tel. DUNkirk 7-2328. San Francisco: Ralph W. Harker and Associates, 552 Market St., Tel. GARfield 1-2481. FOREIGN AGENTS: Great Britain: Atlas Publishing and Distributing Co., Ltd., London E.C. 4. Australia: McGill's Agency, Melbourne. France: Brentano's, Paris 2e. Belgium: Agence et Messageries de la Presse, Brussels. Holland: Trilectron, Heenstede. Greece: International Book & News Agency, Athens. So. Africa: Central News Agency Ltd., Johannesburg; Cape Town, Durban, Natal. Universal Book Agency, Johannesburg. Middle East: Stinatz Middle East Agency, Jerusalem. India: Broadway News Centre, Dadar, Bombay #14. Pakistan: Paradise Book Stall, Karachi 3. POSTMASTER: If undeliverable send form #578 to: RADIO-ELECTRONICS, 154 West 14 St., New York 11, N. Y. \*Trademark registered U. S. Patent Office.



# NATIONAL SCHOOLS

*proudly presents*

**FOR MEN  
WHO WANT  
TO EARN  
MORE MONEY**

## TELERAMA • ALL 8 BRANCHES OF TELEVISION • ELECTRONICS • RADIO IN ONE DYNAMIC, MODERN SHOP METHOD, HOME TRAINING COURSE

\*Registration applied for

Another great advance in **HOME STUDY TRAINING**. Let National Schools, of Los Angeles, a practical Technical Resident Trade School for over 50 years, train you at home by Shop-Method, for today's unlimited opportunities in **ALL 8 BRANCHES** of the Television, Electronics, Radio Industry.

Check all you receive in *One Master Course* at One Low Tuition

1. Television — Including Color TV
2. Radio — FM and AM
3. Industrial Electronics
4. Sound Recording and Hi-Fidelity
5. Preparation for FCC License
6. Automation
7. Radar and Sonar
8. Communications

ALL OF THIS MODERN, NEWEST, PRACTICAL EQUIPMENT IS YOURS TO KEEP!

- Parts to Build a modern TV set, including large screen Picture Tube.
- Parts to build a powerful Superhet Receiver, standard broadcast and short wave.
- Parts to conduct many experiments and build Continuity Checker, RF Oscillator, TV Circuits, Audio Oscillator, TRF Receiver, Signal Generator.
- Professional Multitester
- These are a MUST for all technicians.

### YOU DO MANY PRACTICAL JOBS.

You do servicing, circuit analysis and many other down-to-earth experiments. You build a modern TV set from the ground up . . . with equipment kits we give you, including a new large screen picture tube and professional Multitester, at no additional charge.

**EARN AS YOU LEARN!** Many of our students earn their entire tuition and more in Spare Time jobs we show them how to do while learning. **YOU GET GRADUATE ADVISORY SERVICE, TOO.**

**ALL YOURS  
TO KEEP**



**L. J. ROSENKRANZ**  
President of NATIONAL SCHOOLS



This Master-Shop-Method course is completely up-to-date. Here in Los Angeles, the TV and Electronics center of the world, we are able to keep in constant touch with the industries' latest developments. As a student, you will quickly master all phases at home . . . in your spare time. Your earning power will grow with every lesson. Just as thousands of National Schools graduates do every day, you can handle servicing, manufacturing, repairing, hundreds of other jobs, or make good money in your own business. **SECURE YOUR FUTURE—NOW. SEND COUPON BELOW.**



IN THESE MODERN TV STUDIOS, SHOPS AND LABORATORIES, your Shop Method Home Study Course was developed by experienced instructors and engineers. What an advantage that is to you at home — each lesson is tested, proved, easy to understand. You can master the most up-to-date projects, such as color TV set repair, printed circuits — even prepare for F.C.C. License and industrial electronics without taking a special course. **TAKE YOUR FIRST STEP NOW TO A TOP-PAY JOB IN TV, ELECTRONICS, RADIO. SEND COUPON BELOW TODAY.**



**APPROVED FOR  
VETERANS  
AND  
NON-VETERANS**

## NATIONAL SCHOOLS

4000 S. FIGUEROA ST., LOS ANGELES 37, CALIF  
187 N. LA SALLE ST., CHICAGO 1, ILL.

IN CANADA: 811 W. Hastings St., Vancouver, B. C.

MEMBER



### FREE!

Fully illustrated "CAREER" BOOK in TV, Radio, Electronics. AND actual Sample Lesson—yours at no cost, no obligation **SEND COUPON NOW—TODAY!**



**NATIONAL SCHOOLS**  
TECHNICAL TRADE TRAINING SINCE 1905  
Los Angeles, California

**GET FAST SERVICE—MAIL NOW TO OFFICE NEAREST YOU!**

NATIONAL SCHOOLS, DEPT. RG-66

4000 S. FIGUEROA ST. OR 187 N. LA SALLE ST.  
LOS ANGELES 37, CALIF CHICAGO 1, ILL  
Rush free TV-Radio "Opportunity" Book and sample lesson. No salesman will call.


NAME \_\_\_\_\_ BIRTHDAY \_\_\_\_\_ 19 \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ ZONE \_\_\_\_\_ STATE \_\_\_\_\_

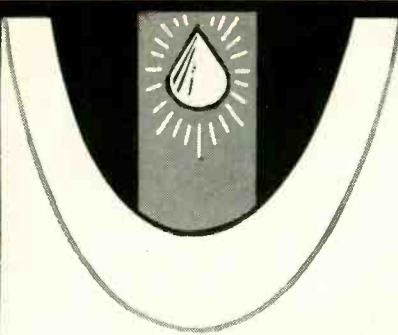VETERANS: Give Date of Discharge \_\_\_\_\_






**PROFIT COMES BACK!**

to phono cartridge and  
needle market with...

*Electro-Voice*®

**POWER-  
POINT**

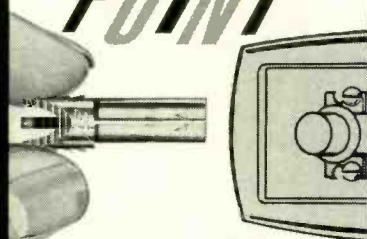

Power-Point replaces over 90% of all popular phono cartridges. Power-Point cuts inventory costs! Power-Point is easy to change! Power-Point sells on sight!

**What Power-Point is:** Power-Point is a ceramic phono-graph cartridge with jeweled\* playing tips in a SINGLE unit—replaceable in seconds without tools! Provides fresh cartridge and two needle-tips at less cost than comparable needles alone.

Four basic types provide Power-Points for any record speed. Just \$3.95 list.

Mail the coupon for complete information.

\*Superior synthetic sapphire or natural diamond.

*Electro-Voice*

Electro-Voice, Inc. • Buchanan, Michigan  
Please send me details and specifications  
of the NEW Electro-Voice Power-Point.

company \_\_\_\_\_


address \_\_\_\_\_

city \_\_\_\_\_ state \_\_\_\_\_

signed \_\_\_\_\_



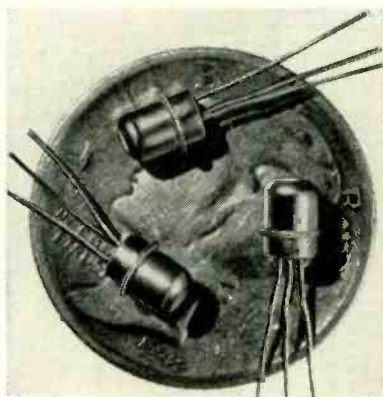
**SUBMINIATURE TRANSISTOR,** first unveiled by Philco at the recent Institute of Radio Engineers show and convention, is believed to be the smallest of its kind yet developed. The tiny



device (upper photo) is so small that more than 20 can be placed on a dime.

The new transistor, the M-1, is a p-n-p type having a 70-db gain, or a power gain of 10 million. Because of its tiny size—excess mass minimized—the M-1 can withstand an acceleration rate of 20,000 G's without change in characteristics. Power consumption is very low, with normal operation possible on as little as a ten-thousandth (.0001) watt.

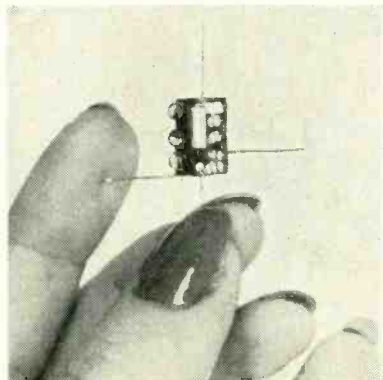Like most junction transistors, the basic operating portion of the M-1 consists of a wafer of germanium. In this case, however, the wafer is about the size of a pinhead. Leads are soldered to a dot of indium on each face of the wafer. Using M-1 transistors, a miniaturized amplifier about the size



of an ordinary pencil eraser (lower photo) has been assembled by Philco. Despite its tiny size, the M-1 is covered

by a metal can which is hermetically sealed.

**THREE NEW TV STATIONS** have gone on the air since last month's report:

- KSHO-TV Las Vegas, Nev.....13
- KETA Oklahoma City, Okla.....13
- WRVA-TV Richmond, Va.....12
- WROW-TV, Albany, N. Y., channel 41, has changed its call letters to WCDA; WAST, Hagaman, N. Y., channel 29, to WCDB; WXEL, Cleveland, Ohio, channel 8, to WJW-TV; WIRI, Plattsburgh, N. Y., channel 38, to WPTZ, and KFXI-TV, Grand Junction, Colo., channel 5, to KREX-TV.

**MUSICAL TONE** may soon replace the familiar telephone bell. Undergoing major field trials this spring, telephones that radiate various tones through the louvered area at the base of the set (see photo) will be tested for customer reaction. The experi-



mental site, Crystal Lake, Ill., was selected for the variety of telephone equipment it affords—some 300 customers on 100 telephone lines, ranging from individual to 8-party rural service.

In this experiment the tones will be transmitted (using transistorized equipment) with the same amount of power required for a telephone conversation—considerably less than is needed to make a telephone ring. The ordinary telephone bell requires 85 volts; the transistorized device less than 1.

An advantage rated high by Bell scientists is that the new device is an aid to the partially deaf. This is because the musical tone contains more energy in the middle-frequency range where there is ordinarily less loss of hearing.

The tone stands out above general room noise and can be distinguished from the ringing of doorbells, alarm clocks or fire alarms.



Prepare Now... in spare time at Home... for a New,

PROFITABLE, INTERESTING FUTURE  
*in* **AUTOMATION**  
 ELECTRONICS  
**TELEVISION**  
 RADIO-ELECTRONICS



**JACK DEMPSEY**

Former World's Heavyweight Champion  
 TELLS WHY HE'S PROUD

TO BE WITH **DTI**

- I have been greatly impressed with DTI's wonderful spirit of friendliness and sincere determination to help its students make good in Television-Radio-Electronics.
- I admire its remarkable 25 year record of helping men build brighter futures.
- I also admire the business policy of its management and the thoroughness of its large faculty of instructors.
- Never have I heard young men praise a school as enthusiastically as do the students and graduates of DTI. They are its best boosters.

RADIO CHIEF OF ILE DE FRANCE  
 FRENCH LUXURY LINER PRAISES DTI

Radio Chief—Jean Desmas Says:

"Your Training Organization in Chicago is known not only throughout Europe, but also in many parts of the world as one of America's finest Television, Radio and Electronics training centers."




**Prepare At Home Or In Our Chicago Laboratory!**

See for yourself how readily you may prepare at home, or in our modern Chicago laboratories, for a good job or business of your own in one of America's most promising, fast-growing fields—TELEVISION-RADIO-ELECTRONICS.

If you train at home you get (1) the use of a 16-mm. movie projector and 16 reels of animated movies to help you learn important points faster... easier, (2) modern, well illustrated lessons and (3) sixteen shipments of electronic parts enabling you to get valuable practical experience from over 300 projects—including building and keeping the electronic equipment shown below. And upon completing training, you have the optional privilege of building and keeping a big 21 INCH TV Set. (DTI offers another home training in Television-Radio-Electronics, but without the TV set.) Get the full story. Mail coupon today!



HOME MOVIES

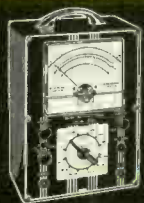

VACUUM TUBE  
 VOLTMETER



OSCILLOSCOPE



Build and keep this BIG DTI Engineered TV set—easily converted to U.H.F. (DTI offers another home training, but without the TV set.)

**LAUD DTI'S HOME MOVIES IN CONGRESS**

DTI's remarkable home training benefit of visual training MOVIES has been praised from the floor of the House of Representatives in Washington, D.C. and recorded in the Congressional Record.



MILITARY SERVICE!

If subject to military service, the information we have for you should prove very helpful. Mail coupon today.

"One of America's Foremost Electronics Training Centers"



**89 WAYS TO EARN MONEY IN TELEVISION RADIO ELECTRONICS**

MEMBER OF NATIONAL HOME STUDY COUNCIL

**MAIL COUPON TODAY!**

DEVRY TECHNICAL INSTITUTE  
 4141 BELMONT AVE., CHICAGO 41, ILL.

Dept. RE-6-M

I would like your valuable information-packed publication showing how I may get started toward a good job or my own business in Television-Radio-Electronics.

Name \_\_\_\_\_ Age \_\_\_\_\_  
(PLEASE PRINT)

Street \_\_\_\_\_ Apt. \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

1005

DTI's Training is Available in Canada

**DEVRY TECHNICAL INSTITUTE**

CHICAGO 41, ILLINOIS


FORMERLY

**DEFOREST'S TRAINING, INC.**





**TUBES FOR THE  
FINEST IN HI-FI**

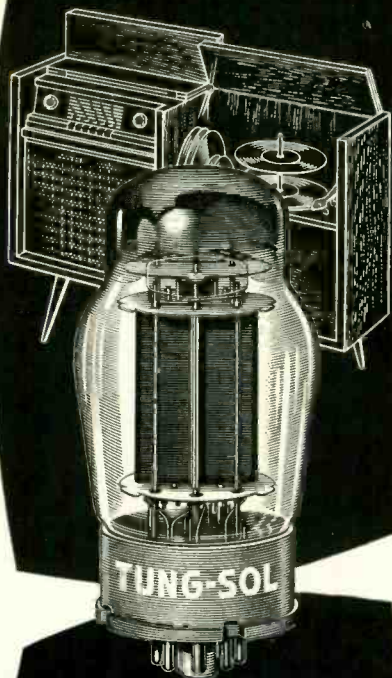


Almost without exception, makers of the finest high-fidelity sets depend upon Tung-Sol Audio Amplifier Tubes to help deliver the performance expected of their products.

Through these tubes—the "5881" and the "6550"—Tung-Sol clearly demonstrates its ability to meet and maintain high-fidelity's critical design requirements in volume production.

This achievement is indicative of the quality and dependability of Tung-Sol Hi-Fi, Radio and TV Tubes . . . products of America's largest independent electron tube manufacturer, Tung-Sol Electric Inc. Newark 4, N. J.

**TUNG-SOL**  
ELECTRON TUBES

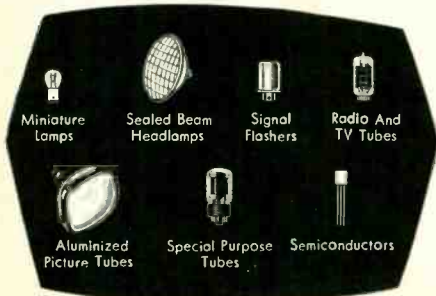**Tung-Sol Automotive & Electronic Products**



**TRANSISTORIZED RADIO PAGERS**

make private, individual paging of personnel possible. The new Handie-Talkie low-frequency radio paging system, announced by Motorola, does away with disturbing public-address, bell or



chime systems. No one except the paged is aware that a message is being transmitted.

The system consists of a selector console with individual buttons for key personnel, an FM transmitter that radiates alerting tones and voice messages within a confined induction-loop area, and the individual Handie-Talkie radio pagers. The selective calling method used in this device consists of matched precision vibrating reed mechanisms—one in each pocket receiver to correspond with another activated by the transmitting console selector button.

The portable receiver (see photo) weighs only 10 ounces and is powered by a 4-volt mercury battery. The system permits paging of several hundred persons individually.

Another paging system, produced by Stromberg-Carlson, is the Pagemaster which uses a small radio decoder (see photo). Each decoder responds to a certain coded radio signal. When receiving that signal it emits an audible tone, alerting the individual carrier. The unit weighs only 7 ounces and the system provides up to 64 channels. In larger installations, servicing a large metropolitan area, approximately 4,000 channels can be utilized.

The Pagemaster encoder transmitter is a small console, on the front of which are dials with which the coded signals are set up. Only 3 or 4 seconds are needed to set a coded signal into the transmitter. As many as four signals can be set up at once, and the transmitter automatically sequences them and continues to transmit each one until it is removed from the encoder by the operator.

**NEW TV TAPE PROCESS**

makes recording television programs on magnetic tape commercially practical. Developed by Ampex, the recorder will permit almost instantaneous playback through a normal TV system. Several other similar units have been demonstrated in the past, but the Ampex recorder is ready for use now and will be put into action by the Columbia

Broadcasting System immediately upon delivery, which is expected in August.

The Ampex device records both the television picture and sound on a strip of magnetic tape about 2 inches wide. The tape speed is 15 inches per second, and 65 minutes of program material can be recorded on a 14-inch reel of tape. The high-frequency response at a low tape speed was obtained with a magnetic head assembly which rotates at a high speed and which records across the tape and thus gives a much higher effective tape speed. The present Ampex recorder can be used for black-and-white only.

**TECHNICAL IMPROVEMENTS**

in radio broadcast services provided by its radio stations WWV near Washington, D.C., and WWVH in Hawaii have been announced by the National Bureau of Standards. Users may now make a better assessment of high-precision oscillators and clocks without waiting for correction data.

The broadcasts have been increased in accuracy from one part in 50 million to one part in 100 million. In addition, the broadcast frequencies at WWV are now normally held within plus or minus one part in a billion of the bureau's primary standard of frequency; this is done if necessary by making daily adjustments at 1900 Universal Time (2:00 p.m. Eastern Standard Time). The bureau's primary standard, which is now constant to one part in a billion, is derived immediately from standard quartz-crystal clocks which are evaluated over long intervals with reference to Standard Time from the U.S. Naval Observatory.

Time signals from WWV are kept in close agreement with Universal Time as determined by the Naval Observatory. This is done by occasional step-adjustments in time, when necessary, of precisely plus or minus 20 milliseconds. These adjustments may be necessary several times per year. When required, they are made on Wednesdays at 1900 Universal Time simultaneously at WWV and WWVH.

**A NEW TWIST**

in the used-tube racket was exposed with the sentencing of Joseph Lynch to two years in the Massachusetts House of Correction. The sentence was appealed and Lynch released on \$20,000 bail pending hearing on the appeal.

Police reported that Lynch bought large numbers of burned-out tubes from dealers at junk prices. The date code numbers on the tubes were then changed to indicate that they had become inoperative while in warranty. These tubes were then, according to Sergeant Barrett of the Boston police force, turned in to dealers in exchange for new ones, and the new tubes sold to other dealers.

Two separate sentences of 1 year each, on the charges of counterfeiting code numbers and of counterfeiting labels on tubes, were imposed. END




Let me send you FREE  
the entire story

Just fill out the coupon and mail it. I will send you, free of charge, a copy of "How to Pass FCC License Exams," plus a sample FCC-type Lesson, and the amazing new booklet, "Money-Making FCC License Information."



CARL E. SMITH, E.E.  
President

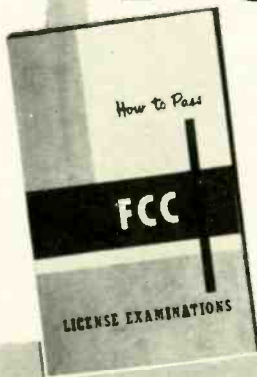I can train you to pass your FCC License Exams in a minimum of time if you've had any practical radio experience—amateur, Army, Navy, radio servicing, or other. My time-proven plan can help put you, too, on the road to success.



# How to Pass FCC COMMERCIAL Radio Operator License Exams

FREE

Tells where to apply and take FCC examinations, location of examining office, scope of knowledge required, approved way to prepare for FCC examinations, positive method of checking your knowledge before taking the examination.

GET YOUR FCC TICKET IN A MINIMUM OF TIME

Get this Amazing Booklet FREE



An FCC License Can Be Your Guarantee of Success in Electronics

TELLS HOW

HERE IS YOUR GUARANTEE

If you fail to pass your Commercial License exam after completing our course, we guarantee to continue your training without additional cost of any kind, until you successfully obtain your Commercial license.

WE GUARANTEE

TO TRAIN AND COACH YOU AT HOME IN SPARE TIME UNTIL YOU GET

YOUR FCC LICENSE

If you have had any practical experience—Amateur, Army, Navy, radio repair, or experimenting

TELLS HOW

Our Amazingly Effective JOB-FINDING SERVICE

Helps CIRE Trainees Get Better Jobs

Here are a few recent examples of Job-Finding results

ELECTRONICS TECHNICIAN

"I am now employed by the Collins Radio Company as a Lab Technician. (This job was listed in your bulletin). I have used the information gathered from your course in so many ways and I know that my training with CIRE helped me a great deal to obtain this job."

Charles D. Sindelar, Cedar Rapids, Iowa

AIRLINES

"I replied to the Job Opportunities you sent me and I am now a radio operator with American Airlines. You have my hearty recommendation for your training and your Job-Finding Service."

James A. Wright, Beltsville, Md.

INDUSTRIAL ELECTRONICS

"Upon my discharge from the Navy I used your Job-Finding Service and as a result I was employed by North American Aviation in electronic assembly (final checkout)."

Glen A. Furlong, Fresno, Calif.

Your FCC ticket is recognized by employers as proof of your technical ability.

TELLS HOW

Employers make

An Approved Member



JOB OFFERS Like These to Our Graduates Every Month

Transcontinental Airline: "American Airlines is very much interested in receiving applications from CIRE trainees. We have immediate need for technicians in many cities."

West Coast Manufacturer: "We are currently in need of men with electronics training or experience in radar main-

tenance, and we would appreciate if you will refer interested persons to us."

Letter from nationally-known Manufacturer: "We have a very great need at the present time for radio electronics technicians and would appreciate any helpful suggestions that you may be able to offer."

These are just a few examples of the job offers that come to our office periodically. Some licensed radioman filled each of these jobs . . . it might have been you!

HERE'S PROOF FCC LICENSES ARE OFTEN SECURED IN A FEW HOURS OF STUDY WITH OUR COACHING AT HOME IN SPARE TIME

Name & Address	License	Time
A/1C Ronald H. Person, St. Louis 20, Mo.	1st Class	25 Weeks
Milton L. Geisler, ET3, FPO, San Francisco, Calif.	1st Class	26 Weeks
Marvin F. Kimball, Lafayette, Ind.	2nd Class	21 Weeks
L. M. Bonino, Harlingen AFB, Tex.	2nd Class	16 Weeks
John E. Hutchison, Bluefield, W. Va.	1st Class	27 Weeks

CLEVELAND INSTITUTE OF RADIO ELECTRONICS

CARL E. SMITH, E. E., Consulting Engineer, President  
Desk RE-92 4900 Euclid Bldg., Cleveland 3, Ohio



Get All 3 FREE

MAIL COUPON NOW

CLEVELAND INSTITUTE OF RADIO ELECTRONICS

Desk RE-92, 4900 Euclid Bldg., Cleveland 3, Ohio  
(Address to Desk No. to avoid delay)

I want to know how I can get my FCC ticket in a minimum of time. Send me your FREE booklet, "How to Pass FCC License Examinations" (does not cover exams for Amateur License), as well as a Sample FCC-type lesson and the amazing new booklet, "Money-Making FCC License Information."

PLEASE PRINT CLEARLY

NAME..... AGE.....

ADDRESS.....

CITY..... ZONE..... STATE.....


FOR PROMPT RESULTS SEND AIR MAIL  
Special tuition rates to members of the U. S. Armed Forces  
Electronic Training Available to Canadian Residents





Model TK-155  
Three Speed  
Manual Portable

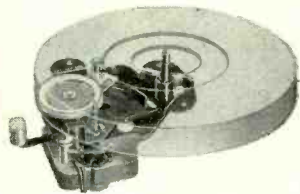**The Waters Conley Co.**  
manufacturer of the well known  
"PHONOLA" phonographs,  
... finds that



Model SS  
Three Speed Motor

... it pays to

**RELY on GI**

PHONOMOTORS

To maintain the high standards of performance expected of their fine "Phonola" line of portable phonographs, the Waters Conley Company has found that there is no substitute for the precision engineering of GI phonomotors. They know that for quality, performance and economy, GI phonomotors just can't be beat! They like GI's prompt, on-the-dot deliveries, too. When you have a phonomotor requirement, for original equipment or replacement purposes, take a tip from the Waters Conley Company. You'll find that you, too, can ... RELY on GI!

Other General Industries AC induction type motors for applications ranging from 1/40 HP to 1/1100 HP.

Write for specifications and quantity-price quotations.



**THE GENERAL INDUSTRIES CO.**

DEPT GR • ELYRIA, OHIO

**SENSATIONAL OFFER!**

ANOTHER GREAT "THOMPSON" PRODUCT  
**Superotor**

WORLD'S FINEST  
**ANTENNA ROTATOR**



MODEL M-100 An extremely attractive and effective mahogany tuning control—lights automatically when tuning—shuts off when rotator stops. Simple to operate. Built-in mast aligner and other features too numerous to list.

REG. 43.95  
NOW ONLY

**\$15<sup>95</sup>**



**Almo RADIO CO.**

509 ARCH ST. DOWNTOWN PHILA., PA.

Branches: Camden, N. J. Atlantic City, N. J. Trenton, N. J. Wilm., Del. Norristown, Pa. Salisbury, Md.

## Correspondence



### BUILDS HARTLEY BOFFLE

Dear Editor:

I have constructed a Hartley Boffle from the article in the February issue with terrific results. I have an Electro-Voice SP12B in thin housing which measures 28 x 24 x 17½ inches. The screens are of 1¾ x 5/8-inch unplanned wood covered with rug padding. The first frame fits the speaker chassis; the second has a 15-inch opening, the third 13 inches, the fourth 11 inches, the fifth 9 inches, the sixth 7 inches, the seventh 5 inches, the eighth 3 inches, with a solid felt screen over its back.

The Boffle works so well and has such striking presence that I have to pass this setup along since it can be had at so reasonable a cost.

The Boffle is used with a TM15A Techmaster Ultra-Linear, a self-powered preamp and a Collaro changer with a G-E RPX-050A cartridge. I tried the system on *Slaughter on Tenth Avenue* as sort of a test, and the reproduction from the lowest bass to the triangles is really fine. I hope this will help some other money-strapped audiophile.

R. MERTZ

Akron, Ohio

### BUSINESS VIEWS

Dear Editor:

I have for some time followed with interest the various letters in your magazine regarding screwdriver mechanics, publication of list and net prices and related topics. I suspect that if you publish this letter there will be repercussions, but I am sincere in my beliefs.

First, I am firmly convinced that much opposition to basement repairmen and part-time technicians by those engaged in the business at established locations is due to distrust of their own ability. Since when did a man's address add to his skill in a trade or profession? I have met many of the so-called established men and have noted that the loudest howl came from those whose own work was the sloppiest, highest priced and least satisfactory from a customer standpoint. Many of the men working at a regular service business have sufficient business to keep themselves and one or more hired technicians busy 15 hours a day, yet can't stand the often excellent competition offered them by these so-called part-time technicians. Tell me—did all of these worriers start in a modern, completely equipped shop, charging full "established" rates?



# ALLIED'S 1956

## value-packed 324-page CATALOG

FREE



the only **COMPLETE** catalog  
for everything in electronics

**FEATURING SUPER-VALUE knight-kits**  
BUY DIRECT AND SAVE! Select from America's top quality equipment in precision-designed kit form—everything in build-your-own Test Instruments, Hi-Fi kits, Hobbyist kits, Ham Gear—easiest to build and you SAVE MORE!

**FEATURING EVERYTHING IN HI-FI**  
Make your money-saving selections from the world's largest offerings of complete Hi-Fi music systems and components—all the quality lines available for immediate shipment from stock. Own the very best in Hi-Fi for less!

### World's Most Complete Stocks

Huge Listings of Parts, Tubes, Transistors, Tools, Books • TV Tubes, Antennas and Accessories  
• Test and Lab Instruments • P. A. Systems and Accessories • Recorders and Supplies  
• Amateur Gear • Specialized Industrial Electronic Equipment...

Get every buying advantage at ALLIED: fastest shipment, expert personal help, lowest prices, assured satisfaction. Make your selections from our 324-page 1956 Catalog packed with the world's largest selection of quality electronic equipment.

send for the  
leading electronic  
supply guide

FREE

### EASY-PAY TERMS

Use our liberal Easy Payment Plan—only 10% down, 12 months to pay—no carrying charges if you pay in 60 days. Available on all orders over \$45, including Hi-Fi, P.A., Kits, Recorders, Test Instruments, Amateur Gear, etc.

Our 35th year

## ALLIED RADIO

World's Largest Electronic Supply House



ALLIED RADIO CORP., Dept. 2-F-6  
100 N. Western Ave., Chicago 80, Ill.

Send FREE 324-Page 1956 ALLIED Catalog.


Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

# Give customers "hi-fi satisfaction" —profitably!
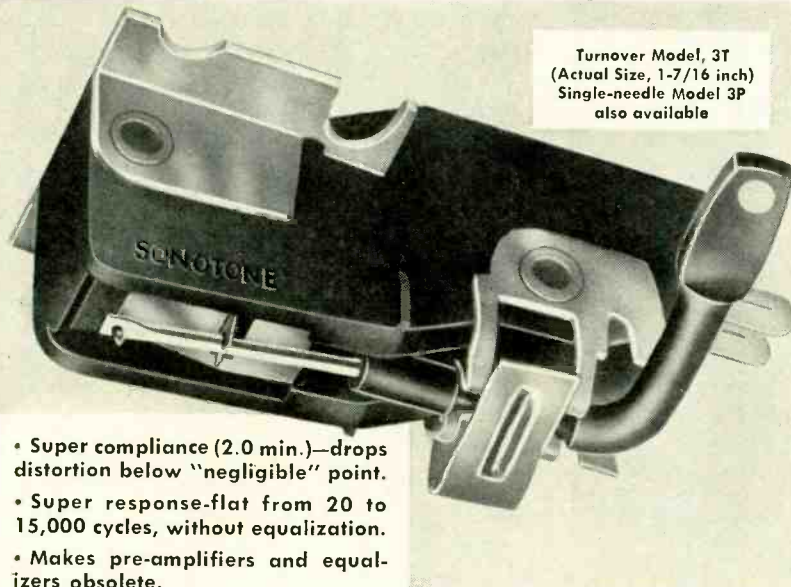
## THE BRILLIANT NEW "3" SERIES SONOTONE CERAMIC



- Super compliance (2.0 min.)—drops distortion below "negligible" point.
- Super response—flat from 20 to 15,000 cycles, without equalization.
- Makes pre-amplifiers and equalizers obsolete.

If you've followed the development of ceramic cartridges since Sonotone pioneered them in 1946, you know of their enormous advances.

Now Sonotone presents the "3" Series, which sets utterly new standards of performance and opens the door to profitable "hi-fi" business for you.

The Sonotone "3" Series ceramic cartridge can be used as a replacement in nearly any phonograph circuit. It delivers a brilliance and clarity of sound which will be noticed and commented upon by delighted customers. Because these cartridges deliver a whopping 0.5 volts (roughly 50 times as much as most velocity types), they do not need preamplification and equalization circuits. And naturally the non-magnetic structure eliminates motor hum.

There are two basic models, a turnover (3T-S) for all record speeds and a single-needle model (3P-1S) for 33 and 45 rpm records. They have standard  $\frac{1}{2}$  or  $\frac{5}{8}$  inch mounting centers and fit any of the widely used tone arms. Prices begin at \$12.50 list (sapphire needles).

Use the brilliant new Sonotone Series "3" on your next replacement job. You'll find yourself on the way to profitable "hi-fi" business.

# SONOTONE®

CORPORATION, ELMSFORD, N. Y.



Write Department CE-66 for free cartridge replacement chart.  
In Canada—Atlas Radio Corp. Ltd., 50 Wingold Ave., Toronto.

## CORRESPONDENCE (Continued)

Second, the complaint about the ability of nearly anyone to get a considerable discount on tubes and other components. So what? The principle upon which business competition in this country was based is the initiative of the individual in offering products to a large number of consumers, banking upon volume to offset a lower profit margin.

What the main gripe seems to boil down to is this: "We want all the business, regardless of our ability to handle it, at charges which we wish to collect."

It seems to me that this is making the set owner, who knows nothing of wholesale outlets and part-time technicians, the victim of one of the most highly organized monopolies in the country. Yet the "established" people claim they do not want monopoly. Show me the business man who won't buy the products he wants where he gets the best price. Show me, if you can.

BRIAN S. WARD

Gary, Ind.

## THE FINISHING TOUCH

Dear Editor:

With reference to my article "A Low-Distortion Amplifier," RADIO-ELECTRONICS, May, 1955, I have obtained an Acrosound TO-330 output transformer and a pair of Tung-Sol 6550 output tubes and installed these. I can report very favorably indeed on the results.

The power output before clipping is 48 watts and at that level IM distortion is below 0.25%. I no longer have available the fine spectrum analyzer I used for checking distortion on the original unit, but my makeshift tests indicate that it is still somewhere below 0.25% at full output.

The only changes in the circuit were: an Acro TO-330 for the TO-300, KT66's to 6550's, adding a pair of 1,000-ohm resistors in the grid circuit of the 6550's (between each grid and the V3 cathode bias resistor connection with the grid), and finally the exchange of R8 (8,200 ohms) for a 12,000-ohm pot which was adjusted to give the -48 volts bias for the output tubes. Plate current is then about 75 to 80 milliamperes for the pair of tubes.

I think that varying the 330-ohm feedback resistor a small amount to the optimum point may increase output power a few watts without increasing distortion. Personally, I don't feel the need for additional power at this point. I am, at last, satisfied.

HERBERT MALAMUD

New York City, N. Y.

## THE WORM TURNS


Dear Editor:

Always interesting are the TV service articles by Art Margolis and now that he has roundly scored the "scarcely able" do-it-yourself TV repairer (RADIO-ELECTRONICS, April, 1956, page 56), perhaps a sequel could be devoted to this subject: after the TV technician has been paid, the "able" do-it-yourselfer sometimes has to do the work!

Following are examples, all from my personal—and unpaid—experience:



# DYNAMIC SUSPENSION

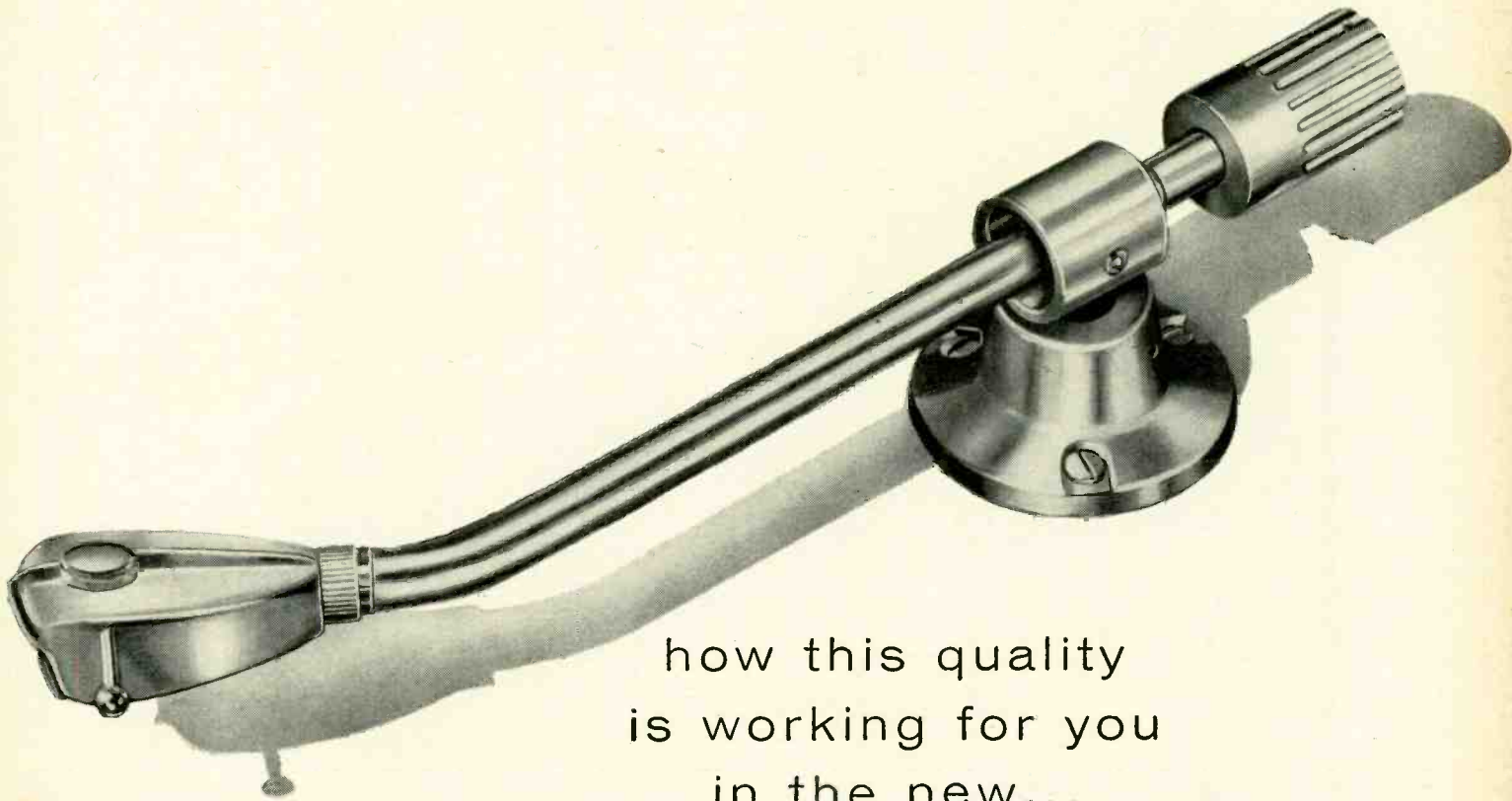

how this quality  
is working for you  
in the new...

## REK-O-KUT TURNTABLE ARM

*So free and effortless is the motion of this arm, so sensitive its suspension, that in a state of perfect balance, a mere feather can tip the scale.*

This wonderful quality has been put to work in a most useful and ingenious manner. With a cartridge mounted in the shell, and the shell secured to the arm, the counterweight is adjusted until the arm is suspended in perfect balance. Naturally, the stylus pressure is now zero.

By rotating the counterweight so that it moves towards the pivot, the cartridge dips downward and the stylus begins to develop pressure — at the rate of 1 gram for every  $1\frac{1}{4}$  turns. Thus, a cartridge calling for operation at 8 grams would require 10 complete turns of the counter-

weight to arrive at optimum stylus pressure.\*

The Rek-O-Kut turntable arm is well nigh the perfect unit — truly passive — following and responding to every movement of the cartridge without anticipating or resisting. This is poise — dynamic balance.

Model 120 for records up to 12"..... \$26.95  
Model 160 for records up to 16"..... 29.95

Additional Cartridge Heads  
Model PA-20..... each \$4.95  
*Slightly higher West of Rockies*




$1\frac{1}{4}$  turns per gram applies to Model 120 arms  
2 turns per gram applies to Model 160 arms.

For complete details, write Dept. UF-13

**REK-O-KUT COMPANY, 38-01 Queens Blvd., Long Island City 1, N. Y.**  
EXPORT: Morhan Exporting Corp., 458 Broadway, New York 13, N. Y.  
CANADA: Atlas Radio Corp., 50 Wingold Ave., Toronto 10, Ontario

# Merit

FIRST IN EXACT REPLACEMENT.

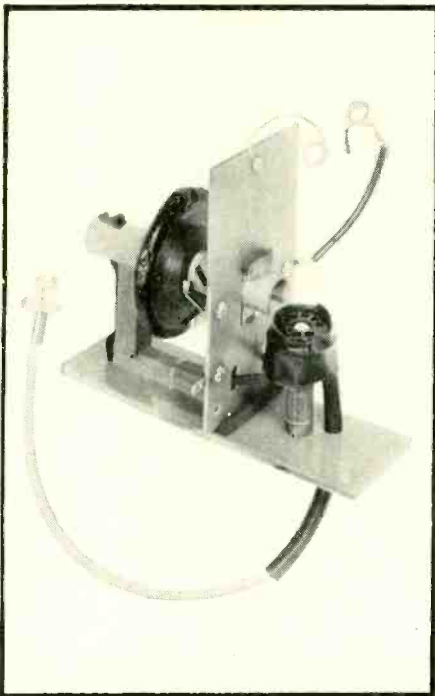

HVO-37 FOR EXACT REPLACEMENT IN over 125 models . . . CROSLY, HALLICRAFTERS, SENTINEL, SILVERTONE. Another in the complete Merit line of exact and universal transformers, yokes and coils. Merit is the only manufacturer of transformers, yokes and coils who has complete production facilities for all parts sold under their brand name.

# Merit

MERIT COIL & TRANSFORMER CORP.  
4127 N. CLARK ST., CHICAGO 40, ILL.

## CORRESPONDENCE

(Continued)

The first was on my own little TV set which, right out of the factory carton, had sound bars in the picture. On the advice of my retail dealer and after he had tried to correct the difficulty, I took the set back to the factory distributor who maintains an elaborate-looking service shop. But alas! their elaborate test equipment was not used on my set—all they did was to detune what I have since learned to call the *front end*. The sound bars were eliminated all right—but so was the clearest part of the picture! And the service charge for this shenanigan was \$7.50!

There were two alternatives: either trade in the set on a new one or else look into the difficulty myself. The latter seemed to be the least costly and might be instructive. So, after reading all I could of the manufacturer's and other literature, I decided: that the original picture clarity could possibly be restored by retuning the front-end slugs (about 2 minutes' work); that the original difficulty could possibly be repaired by twisting the sound-trap slugs. Both of these hunches paid off handsomely, proving that, if the do-it-yourself man does a little preliminary investigation, he can also become a "learn-to-do-it-right" man. Maybe my TV technician would have profited by the same procedure.

This experience was told to one of my friends and she asked me to look at her set—on which a TV technician had also been paid and failed. It had a very high-pitched intermittent oscillation. When the TV technician had left the set as repaired, he had somehow temporarily checked the oscillation, but, when I started poking around in the back, I found that I could make the set howl like a stuck pig merely by pressing on the 6AX4 damper tube. Since I am not a TV technician I am not at all sure what was happening. And I am not at all sure that my "cure" (a new 6AX4) was the proper one. But at any rate my wealth of inexperience has paid off in "customer" satisfaction, for the set has never howled again.

The next set at which I was asked to look—*after* a TV technician had been paid and failed—also had (as it turned out) a bad 6AX4 damper, an unstable vertical sync and a bad vertical output tube. When the technician was called in there was no picture, due (as I found out later) to an open Slo-Blo fuse in the damper circuit. The technician had put in a conventional fuse of higher wattage, had adjusted the vertical hold to a point of temporary stability, apparently ignored the poor vertical height and linearity, but had collected his service fee and left.

So this is the sad sad story to date of a poor do-it-yourselfer and I suggest to Art Margolis that not all of us are trying to beat the TV technician out of his service fees. Sometimes we are pressed into service *after* the TV technician has been paid and failed.

JOSEPH H. SUTTON

Kansas City, Mo.

END



new  
**AMERICAN**  
**"5-PAK"**  
SERVICE  
KIT

sells  
**9 out of 10**

CRYSTAL  
PHONOGRAPH  
REPLACEMENT  
CARTRIDGE  
CUSTOMERS!

Here's everything you need . . . in one convenient package!

American's high quality "Clear as Crystal" replacement cartridges are packed in this reusable plastic box . . . ideal as a small parts container. The box contains five of the most popular types of replacement cartridges . . . meets 90% of your customers' requirements.

In addition, you get an authorized repair service decal . . . five identification cartridge labels for your name . . . and a handy crystal cartridge replacement chart.

The whole package costs less, because you get more. And, you give your customers more, too. Why not call your nearby American distributor today and order the new "5-PAK" for yourself.



**American**  
replacement  
cartridges

ELECTRONICS DIVISION  
ELGIN NATIONAL WATCH CO.

370 South Fair Oaks, Pasadena, California


RADIO-ELECTRONICS



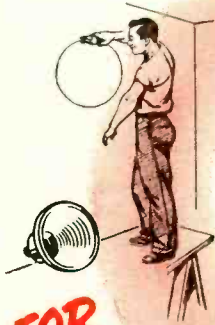
# Seen the Saw?

INDISPENSABLE FOR RADIO-TV

CUTS 2 x 4's  
IN SECONDS.  
CUTS  
1/2" STEEL.



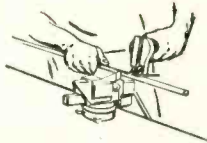**FOR** CUTTING PLASTER  
AND WOOD, INSTALLING  
SPEAKERS, ETC.



**FOR** CUTTING PIPES  
FOR ANTENNA,  
ELECTRICAL  
CONDUITS, ETC.



**FOR** PREPARING  
ELECTRICAL OUTLETS, ETC.








**FOR** SERVICE

**FOR** SELLING

Like other WEN tools, this new Power Saw is compact, handy, efficient, ideal for the Service Man. Has powerful AC/DC Universal motor. Delivers 2650 - 5/8" strokes per minute. Cuts wood, plastics, metals, composition, hard rubber, etc. Acts as jig, rip, crosscut, band, hack, coping, scroll or keyhole saw. Interchangeable blades. Air stream blows dust off work.

This is the hottest selling item in electrical power tools today. It's being snapped up by professionals and amateurs alike wherever shown. And no wonder—for this saw does the work of 8 saws—more swiftly, smoothly and safely than tools costing twice as much. EVEN CUTS HEAVY LUMBER—STEEL PLATE. Price complete with 3 blades.....Only \$29.95 LIST

THERE'S PERFORMANCE AND PROFIT IN EVERY WEN PRODUCT

"Quick-Hot" ELECTRONIC SOLDERING GUNS			ELECTRIC SANDERS—POLISHERS			POWER SAW
#199 K  KIT \$9.95	#288  \$9.95	#199  \$7.95	#202  \$13.95	#303  KIT \$16.95	#404 HEAVY DUTY  KIT \$19.95	#505  \$29.95

— ALL OPERATE ON 110-120 VOLT A.C. — 60 CYCLE —



**WEN**

**PRODUCTS, INC.**

5808 NORTHWEST HIGHWAY, CHICAGO 31, ILL.  
(Export sales, Scheel International, Inc., Chicago)



# 2 IMPORTANT DEVELOPMENTS

OF INTEREST TO EVERY  
HIGH FIDELITY ENTHUSIAST IN THE COUNTRY

**Collaro**  
ANNOUNCES

1. **NEW MODEL RC-456** — the first 4-speed high fidelity record changer for 78, 45, 33 1/3 and 16 2/3 rpm.

2. **NEW LOW PRICE of \$34<sup>50</sup>\***  
— the lowest in the field for a recognized high fidelity changer.

The New RC-456 Features:

*Manual Operation*

*Automatic Intermix*

*Pre-Wired for Easy Installation*



... plus all the other features  
that have made **Collaro** the fastest growing  
changer in the field.

\*less cartridge — slightly higher West of Rockies




For complete details, write to Dept. GF-16

**ROCKBAR CORPORATION**, 650 Halstead Ave., Mamaroneck, N.Y.



*Made in England*

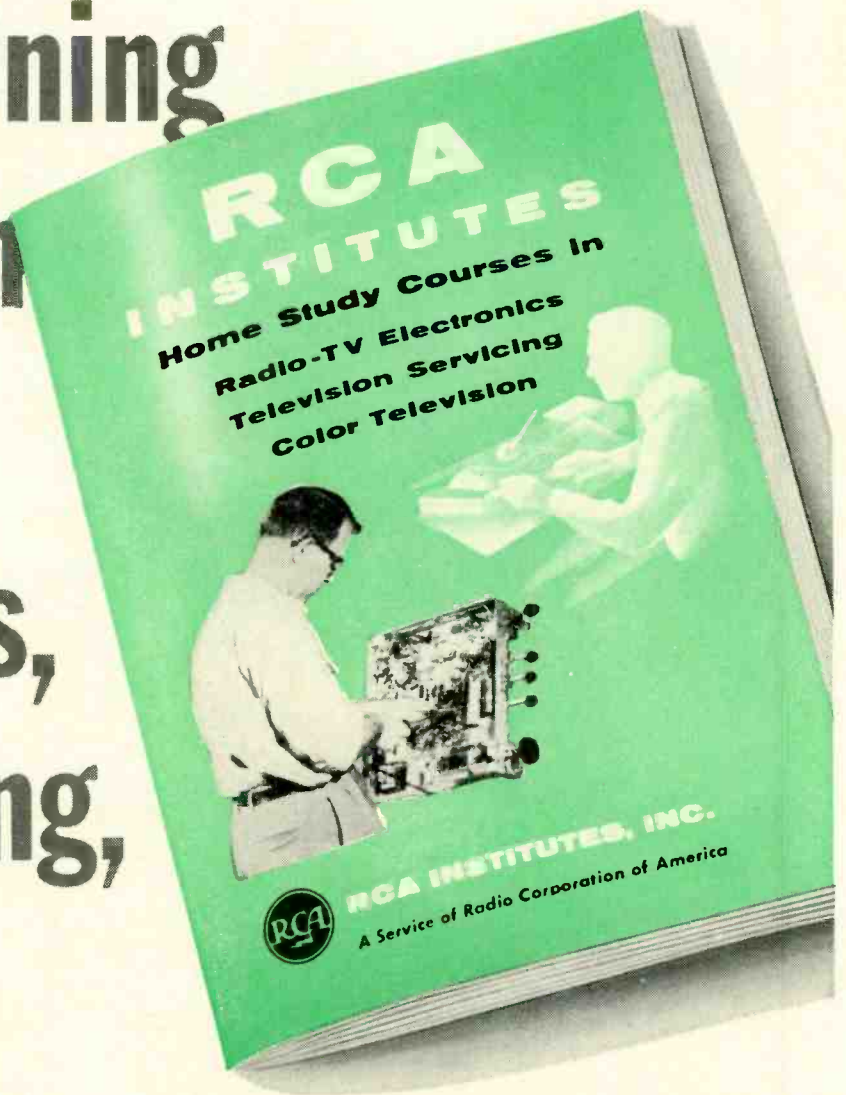**RCA** offers you the  
 finest training  
 at home in  
 Radio-TV  
 electronics,  
 TV servicing,  
 Color TV



**SEND FOR THIS FREE  
 BOOK NOW!**

The instruction you receive and equipment you get (and keep) will start you on your way. Pay-as-you-learn. You pay for only one study group at a time. This 52 page book contains complete information on Home Study Courses for the beginner and the advanced student.




**RCA INSTITUTES, INC.**  
 A SERVICE OF RADIO CORPORATION of AMERICA  
 350 WEST FOURTH STREET, NEW YORK 14, N.Y.

RCA Institutes, Inc., Home Study E-66,  
 350 West Fourth Street New York 14, N. Y.  
 Without obligation, send me FREE CATALOG  
 on Home Study Courses in Radio, Television  
 and Color TV. No salesman will call.

Name ..... Please Print  
 Address .....  
 City ..... Zone ..... State .....

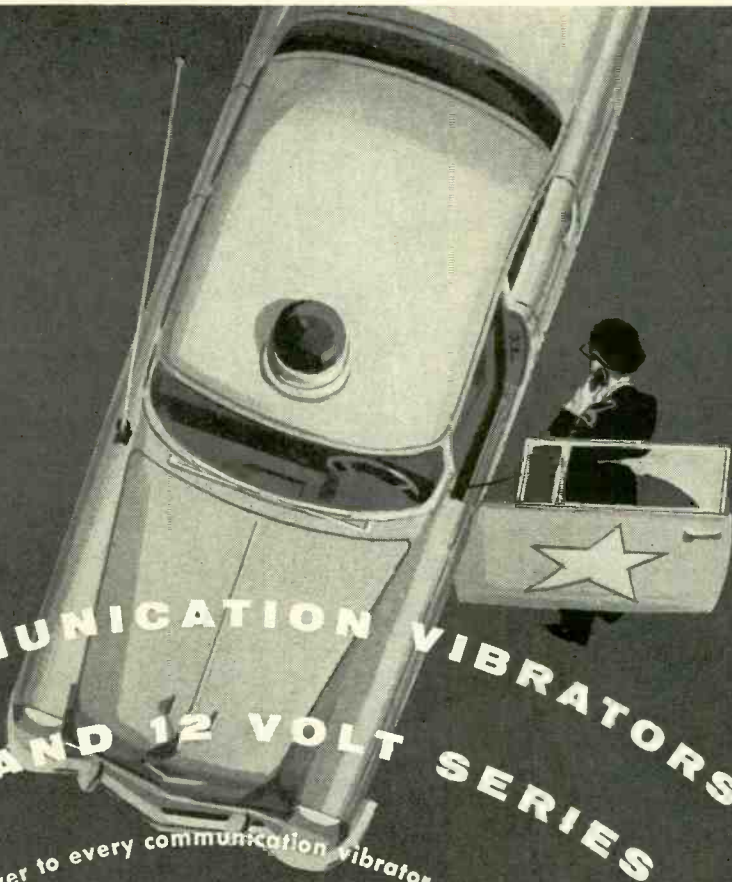**IMPORTANT**  
 Be sure to write  
 for RCA Institutes  
 catalog before  
 signing up for any  
 Radio-TV course





# RADIART COMMUNICATION VIBRATORS IN 6 VOLT AND 12 VOLT SERIES

Here is the ABSOLUTE answer to every communication vibrator replacement...  
 because NOW... you are ABSOLUTELY CERTAIN of the proper vibrator  
 replacement for EACH original type! And QUALITY you can depend  
 upon because of superior engineering... long lasting  
 dependable service because of quality controlled  
 manufacture which means MORE  
 performance hours per dollar!

### These 10 Types Offer Proper Replacement For Original Communication Equipment

Here is a 6 volt vibrator for EACH 6 volt operation  
and a 12 volt vibrator for EACH 12 volt operation!

Old Number	New Number 6 volt	New Number 12 volt
5515	<b>5715</b>	<b>6715</b>
5518	<b>5718</b>	<b>6718</b>
★	<b>5721</b>	<b>6721</b>
★	<b>5722</b>	<b>6722</b>
★	<b>5725</b>	<b>6725</b>
5605	<b>5805</b>	<b>6805</b>
5620	<b>5820</b>	<b>6820</b>
5621	<b>5821</b>	<b>6821</b>
5622	<b>5822</b>	<b>6822</b>
★	<b>5824</b>	<b>6824</b>



THE RADIART CORPORATION  
CLEVELAND 13, OHIO


VIBRATORS • AJTO AERIALS • TV ANTENNAS  
ROTORS • POWER SUPPLIES

"best shop investment I've ever made..."
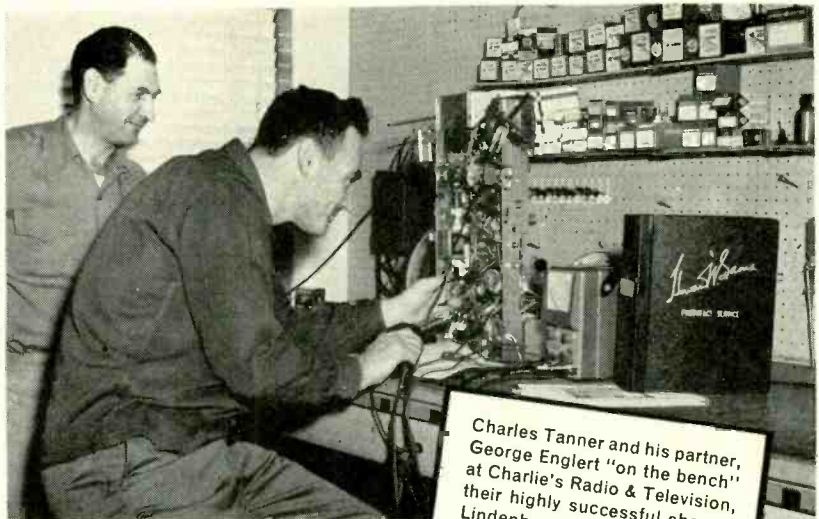
# PHOTOFACT

saves me time,  
helps me earn  
extra profits  
every day..."

SAYS Charles Tanner  
of Lindenhurst, L. I., N.Y.




Charles Tanner and his partner, George Englert "on the bench" at Charlie's Radio & Television, their highly successful shop at Lindenhurst, L. I., New York.

Writes Mr. Tanner: "The use of Sams' PHOTOFACT data saves me time on bench jobs, and that means *extra* profits every day, profits I can really measure. The big time-savers I especially like are the convenient Voltage Data\* and Waveforms\* shown directly on every PHOTOFACT TV schematic diagram. Because of PHOTOFACT'S size, too, it's possible to work on a set with that very fine Standard Notation Schematic\* lying easily accessible in front of the technician. In my opinion, PHOTOFACT is the best shop investment I've ever made."



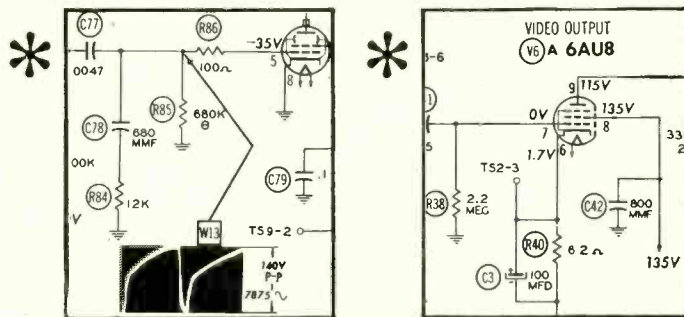George Englert stands near the shop's complete PHOTOFACT Library. Charles Tanner refers to his handy Sams PHOTOFACT Index for the time-saving Folder covering his next bench job.



From start to finish, you solve your service problems in just minutes... you service more sets and earn more daily with PHOTOFACT by your side!



**MONEY BACK GUARANTEE!**

Got a tough repair? Try this—at Howard W. Sams' own risk: see your Parts Distributor and buy the proper PHOTOFACT Folder Set covering the receiver. Then use it on the actual repair. If PHOTOFACT doesn't save you time, doesn't make the job easier and more profitable for you, Howard W. Sams wants you to return the complete Folder Set direct to him and he'll refund your purchase price promptly. **GET THE PROOF FOR YOURSELF—TRY PHOTOFACT NOW!**

free



Send for Sams' INDEX TO PHOTOFACT FOLDERS—your guide to virtually any receiver model ever to come into your shop; helps you locate the proper PHOTOFACT Folder you need to solve any service problem on any model. You'll want this valuable reference guide. Send coupon now.

\*One of 32 features found exclusively in Sams PHOTOFACT—the world's finest service data covering over 20,000 TV and radio models

## HOWARD W. SAMS & CO., INC.

Howard W. Sams & Co., Inc.  
2205 E. 46th St., Indianapolis 5, Ind.

- Send FREE Index to PHOTOFACT Folders  
 I am a Service Technician

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_





It's easier to sell CBS

# Silver Vision

the  
 "High-Fidelity"  
 .....

## Aluminized Tube

Your customer is aware that Hi-Fi does sound better . . . that it faithfully reproduces the original sound. And you can prove by demonstration that advanced-engineered CBS Silver Vision tubes can do for video what Hi-Fi does for audio.

You know Silver Vision's aluminization . . . silver-activated phosphors . . . and small-spot gun can accomplish this. But technical details do not interest the lady. She does appreciate Silver Vision's sparkling whites . . . deep blacks . . . and wide range of middle gray tones. She likes the way they can be blended to give her truly high-fidelity reproduction of the telecast picture.

Here's a tube whose performance sells it. And Garry Moore makes it still easier by convincing your women customers over the CBS Television Network: "There are no better tubes made than CBS tubes, the tubes with the Good Housekeeping Guaranty Seal." Sell the easy way, follow Garry's lead. Sell CBS Silver Vision . . . the "high-fidelity" aluminized picture tube.

*Always show her the CBS carton with the Good Housekeeping Guaranty Seal.*



**CBS-HYTRON**, Danvers, Massachusetts  
 A Division of  
 Columbia Broadcasting System, Inc.



**WANTED:  
200,000 TV  
SERVICE MEN!**

**VETERANS  
NON-VETERANS**



**GET IN ON THIS  
2 BILLION DOLLAR PLUM!**

200,000 — That's how many service men will be needed to handle television-radio-electronics industry requirements in the next few years. That's the figure given by the director of product service for CBS-Columbia — a man in a position to know.

2.7 billion dollars to be spent just for service and installation of TV sets in American homes by 1957! That's the figure given by one of the top men in the entire industry — the president of Radio Corporation of America.




L. C. Lane, B.S., M.A.  
President, Radio-Television  
Training Association.  
Executive Director, Pierce  
School of Radio & Television.

**Think What This Means For YOU!**

Here is a field still in its infancy — New jobs with top pay and a secure future are being created every day — Here is a chance for you to get into a growing field with unlimited opportunity for advancement — Here is your chance to set up your own business and be your own boss — Here is your opportunity to get in on a 2 billion dollar plum by becoming a Television Technician.

**LEARN BY DOING**

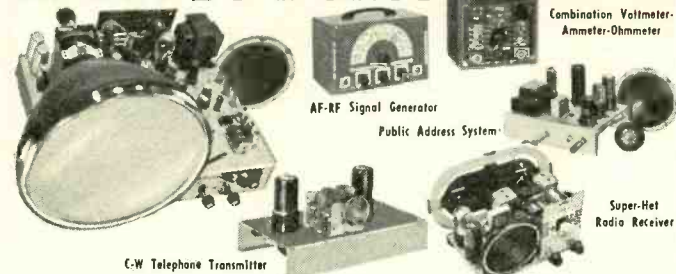

As part of your training, I give you the equipment you need to set up your own home laboratory and prepare for a BETTER PAY TV JOB. You build and keep a professional TV RECEIVER complete with big picture tube (designed and engineered to take any size up to 21-inch) . . . also a Super-Het Radio Receiver, AF-RF Signal Generator, Combination Voltmeter-Ammeter-Ohmmeter, C-W Telephone Transmitter, Public Address System, AC-DC Power Supply. Everything supplied, including all tubes.

**EARN WHILE YOU LEARN**

Almost from the very start of your course you can earn extra money by repairing sets for friends and neighbors. Many of my students earn up to \$25 a week . . . pay for their entire training with spare time earnings . . . start their own profitable service business.

**VETERANS**

My School fully approved to train Veterans under new Korean G. I. Bill. Don't lose your school benefits by waiting too long. Write discharge date on coupon.

**LEARN TELEVISION AT HOME  
IN YOUR SPARE TIME**

Trained men get the top jobs. You can qualify for one without giving up your present job or social life. My lessons are especially prepared for you to study at home — even if you have absolutely no experience in this field.

**CHOOSE FROM THREE COMPLETE COURSES**  
covering all phases of Radio, FM and TV

1. Radio, FM and Television Technician Course — no previous experience necessary.
2. FM-TV Technician Course — previous training or experience in radio required.
3. TV Cameraman and Studio Technician Course — advanced training for men with Radio or TV training or experience.

**EXTRA TRAINING IN NEW YORK CITY AT NO EXTRA COST!**

After you finish your home study training in Course 1 or 2 you can have two weeks, 50 hours, of intensive Lab work on modern electronic equipment at our associate resident school, Pierce School of Radio & Television. THIS EXTRA TRAINING IS YOURS AT NO EXTRA COST WHATSOEVER!

**FCC COACHING COURSE** — Important for BETTER-PAY JOBS requiring FCC License! You get this training AT NO EXTRA COST! Top TV jobs go to FCC-licensed technicians.

**FREE!**

I'll send you my new 40-page book, "How to Make Money in Television, Radio, Electronics," a Free sample lesson, and other literature showing how and where you can get a top-pay job in Television.



Mr. Leonard C. Lane, President  
RADIO-TELEVISION TRAINING ASSOCIATION  
Dept. R-6C, 52 East 19th Street, New York 3, N.Y.

Dear Mr. Lane: Send me your NEW FREE BOOK, FREE SAMPLE LESSON, and FREE aids that will show me how I can make TOP MONEY IN TELEVISION. I understand I am under no obligation.

(PLEASE PRINT PLAINLY.)

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

- I AM INTERESTED IN:
- Radio-FM-TV Technician Course
  - FM-TV Technician Course
  - TV Cameraman & Studio Technician Course

**VETERANS!**  
Write discharge date

**R**adio **T**elevision **T**raining **A**ssociation


52 EAST 19th STREET • NEW YORK 3, N. Y.

Licensed by the State of New York • Approved for Veteran Training

**MAIL THIS COUPON TODAY!**



# limitless

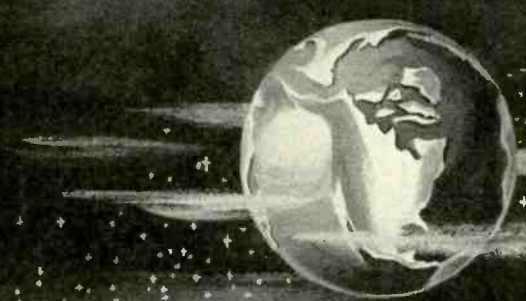

## as the future of UNIVAC<sup>®</sup>

When planning your future, it is necessary to choose that company which presents the most complete program for you. The opportunity at Remington Rand Univac can only be limited by the individual. Excellent salaries, benefits and educational programs are yours to guarantee this limitless future.


At UNIVAC you will be working with men who developed much of the basic knowledge of computers—who designed and produced components being used by the manufacturers in the field—who set the standards that the others follow.

Now is the time to come to Univac where ambition and professional skill find their reward in limitless opportunities in an expanding organization.
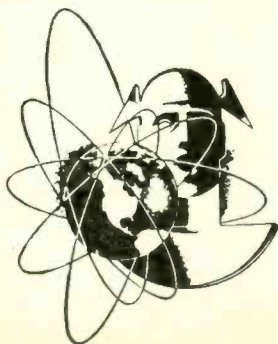
### Immediate openings for:

**FIELD LOCATION ENGINEERS** with a college degree in a scientific or engineering field and experience in electronics. Extensive electronic background may substitute for some college. Many opportunities for rapid advancement.

**FIELD LOCATION TECHNICIANS** Technical school background and preferably some experience in electronics. These positions can lead to full engineering responsibility.



Send complete resumé to

## *Remington Rand Univac*

DIVISION OF SPERRY RAND CORPORATION  
AT ANY ONE OF THESE THREE PLANT LOCATIONS


MR. D. A. BOWDOIN  
Dept. JP-10  
2300 W. Allegheny Ave.  
Philadelphia, Pa.

MR. KURT PINKE  
Dept. JS-10  
1902 W. Minnehaha Ave.  
St. Paul W4, Minn.

MR. FRANK KING  
Dept. JN-10  
Wilson Avenue  
South Norwalk, Conn.

© Registered in U. S. Patent Office



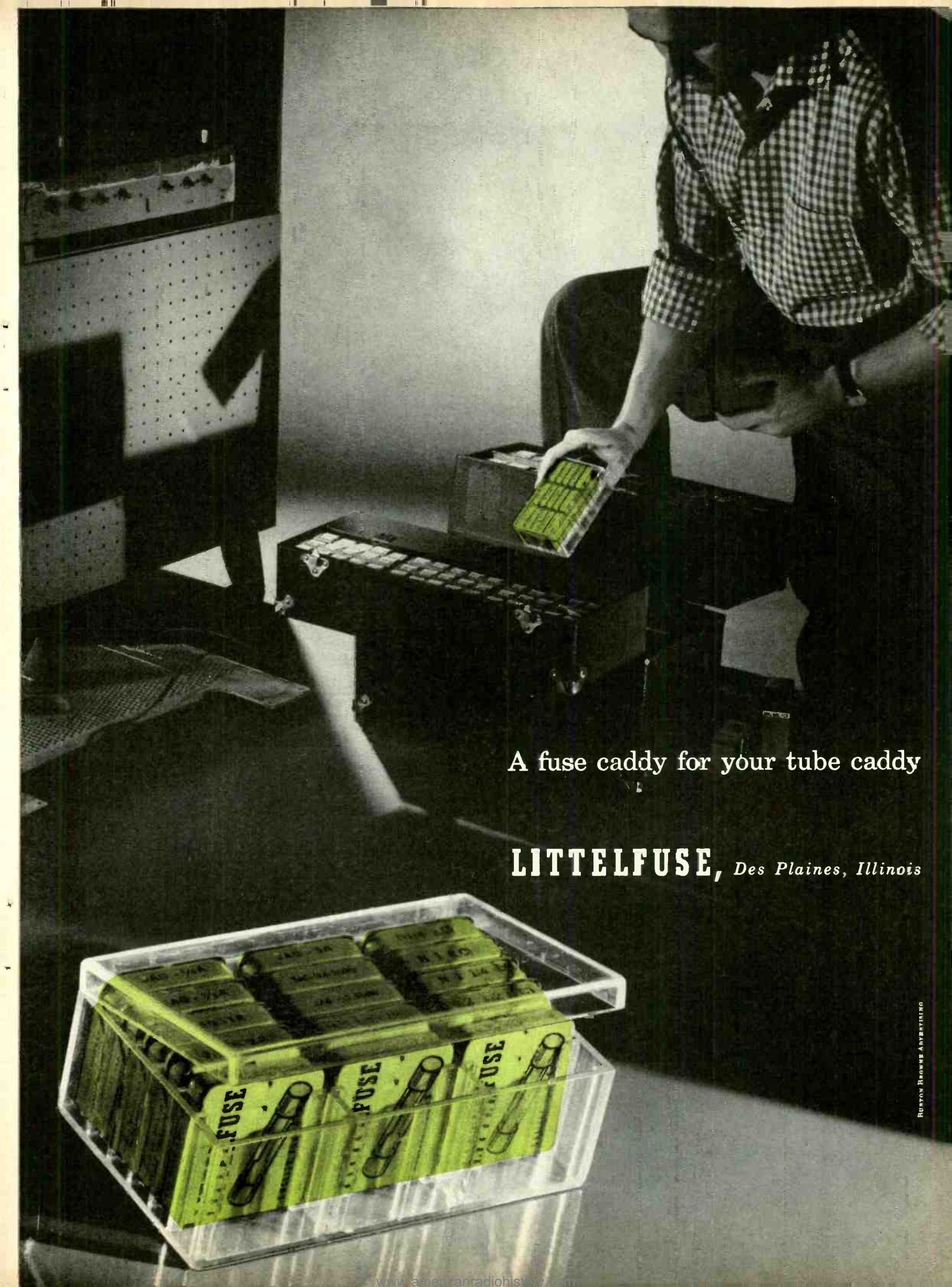


A fuse caddy for your tube caddy


**LITTELFUSE**, *Des Plaines, Illinois*





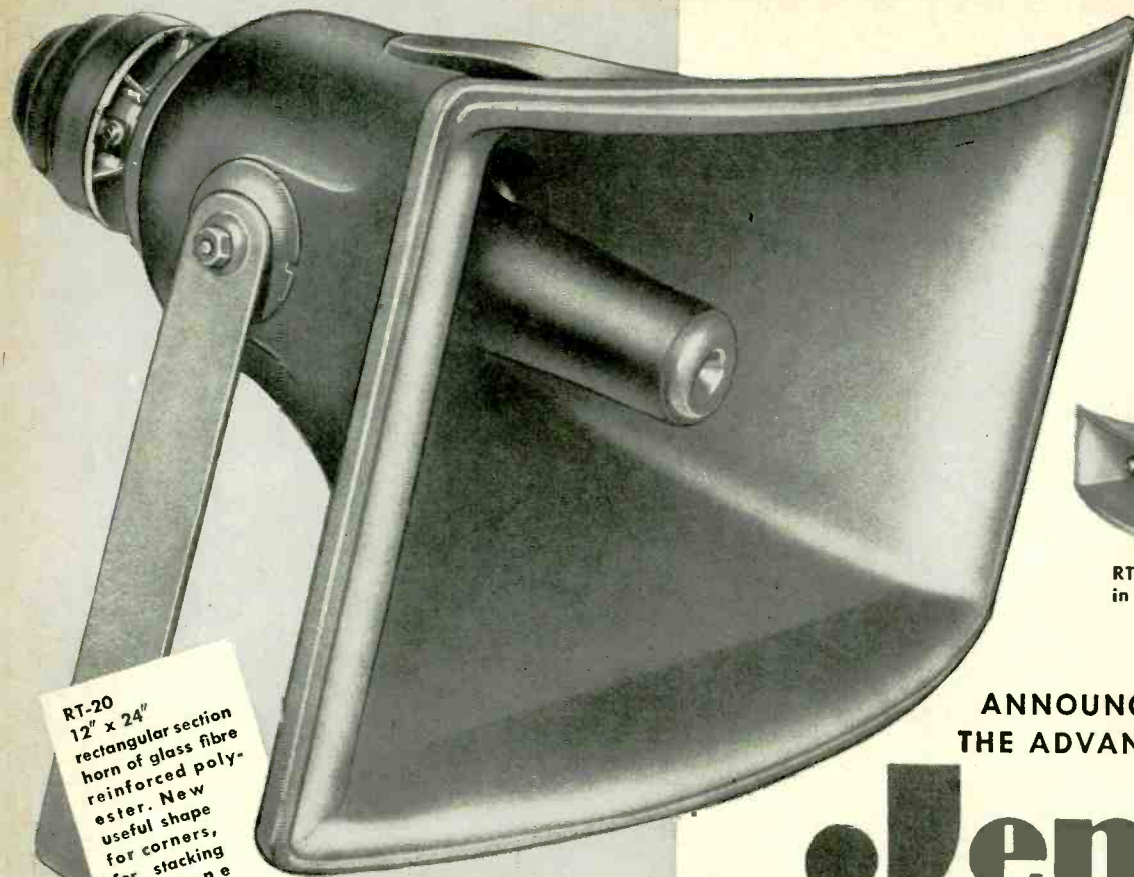

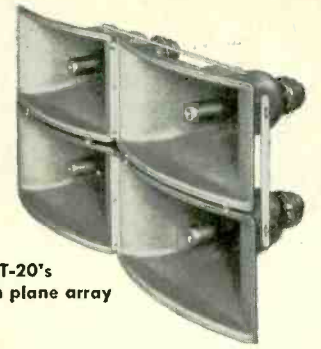RT-20  
12" x 24"  
rectangular section  
horn of glass fibre  
reinforced poly-  
ester. New  
useful shape  
for corners,  
for stacking  
in plane  
or circular  
arrays.



RT-20's  
in plane array



RT-20's  
in circular array

ANNOUNCING THE ADVANCED **NEW**


**Jensen**

**PROFESSIONAL  
SERIES** LOUDSPEAKERS

FOR INDUSTRIAL, COMMERCIAL, INSTITUTIONAL,  
CIVIL DEFENSE, AND MILITARY SOUND SYSTEMS


If sound is your business, here is big news for you . . . a complete new line of loudspeakers to meet for the first time every sound system need for both entertainment and efficient, effective communication. From a fraction of a watt to 1600 watts or even more . . . for high fidelity or high efficiency coverage . . . for distributed or concentrated source projection . . . indoors or out—there is a Jensen Professional Series loudspeaker that will do the job *better, more dependably, and more economically* than ever before. Just as an example, the new Hypex Lifetime Driver Units are *guaranteed indefinitely against failure under normal use!*

Three years of product design and a background of nearly 30 years of field experience and manufacturing know-how come to you in Jensen Professional Series loudspeakers. We can't begin to illustrate or describe all the items here—nor tell you about all the new features for convenience and performance which we've built into them. Catalog 1070 tells the whole story, including valuable information on sound system design. Send for your free copy today.

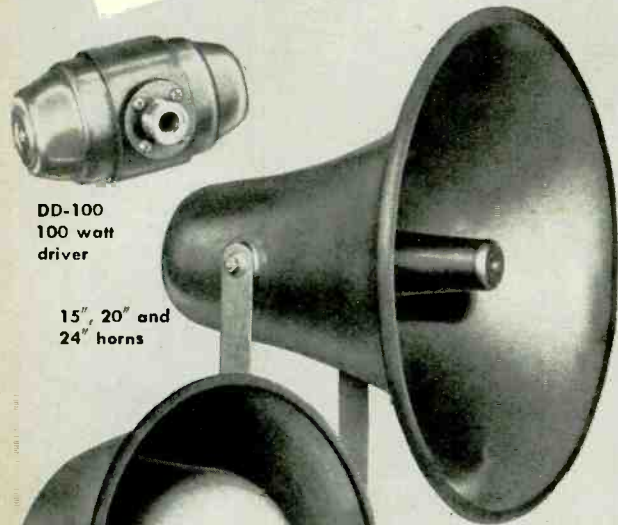


DD-100  
100 watt  
driver

15", 20" and  
24" horns

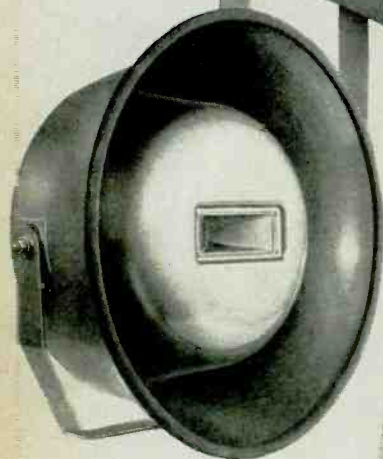

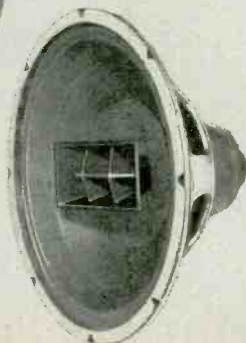HF-100  
weatherproof  
2-way HI-FI  
Projector



Four 12" and 15"  
2-way and 3-way  
speakers



D-30 and D-40  
30 and 40 watt  
drivers

**Jensen** MANUFACTURING COMPANY  
6601 S. Laramie, Chicago 38, Illinois

Division of The Muter Co. • In Canada, Copper Wire Products, Ltd. Licensee



**IF JOBS LIKE THESE ARE "ON YOUR MIND" . . .**

*. . . but you can't qualify because you lack*  
**ADVANCED TECHNICAL KNOWLEDGE . . .**

**SEND NOW FOR  
 CREI'S NEW FREE BOOKLET**

It's crammed with facts and data—containing a tested plan to make you ready for the big jobs and high-salaried careers now being offered in



**RADIO—TELEVISION—ELECTRONICS**

The want ads above are *real* ones . . . they appear almost daily in magazines and newspapers—all over the country. They show how desperately the electronic industry needs *trained* men. On the other hand, they give you a good idea of what opportunities await you—if you get advanced technical training *now*. And no wonder trained men are needed! Look what's happening in just a few phases of the booming world of electronics:

40,000,000 TV sets already in use—430 TV stations on the air—more coming. Color TV is coming ahead fast. More than 125,000,000 radios in use. More than 97,000 radio-equipped police cars. At least 87,000 radio-equipped American ships. Top manufacturers sold billions of dollars worth of electronic equipment in 1955. By 1960, the radio-electronic industry should do no less than 15 billion dollars of business per year, not counting military orders.

*What do these figures mean to you? They mean that thousands of new electronic jobs have been added to the great, expanding field of electronics.*

**LITERALLY THOUSANDS ARE NEEDED!**

You are needed—for development, research, design, production, testing, inspection, manufacture, broadcasting, telecasting, servicing. But you can qualify only if you take time to advance your knowledge . . . if you take 2 minutes right now to write for the free CREI booklet, with no obligation.

**SHORTEST DISTANCE TO A GOOD CAREER IS CREI TRAINING**

If you follow the plan outlined in our free booklet, you will be in line for promotion and pay increases in short order. Read what a typical CREI graduate has to say:

"In this time of less than two years, I have almost doubled my salary and have gone from wireman to engineering assistant and now to junior engineer. I have CREI to thank."—Frank A. Eckert, 22 Clover Lane, Levittown, Pa.

**CREI TRAINING—JUST WHAT INDUSTRY ORDERED**

By method, experience, and personnel—CREI is equipped to teach you what you will need when you translate your study into work. As proof that CREI knows what industry wants, many leading companies choose CREI to train their own technical staffs. Among them:

United Air Lines, Canadian Broadcasting Corporation, Columbia Broadcasting System, Glenn L. Martin Co., All-America Cable and Radio, Inc., Radio Corporation of America.

**TOP FIRMS LOOK FOR CREI MEN**

A CREI diploma itself is ample proof to many leading companies that a man is worth hiring. Moreover, employers contact us regularly for graduates to fill good jobs. Our placement bureau cannot keep up with the demands.

**Typical recent request:**

"In view of the fact that we have recently merged with the General Dynamics Corporation, we are entering a period of greatly expanded activity. Our need for the technical institute graduate is, therefore, greater than it has been, and we are interested in bringing our opportunities to the attention of your students."

Stromberg-Carlson Company  
 Rochester 3, New York

**NAME YOUR FUTURE—GO AFTER IT—GET IT**

What do you want? To pass FCC exams? Start your own business? CREI has helped others reach these goals, and can help you. Or, do you want to go after good-paying electronic jobs, secure, permanent careers like those advertised above? *Whatever* your

choice, CREI can help you as it has helped thousands of men—provided you have the ambition to follow the plan.

**NO COLLEGE DEGREE NECESSARY**

If you have the equivalent of a high school education, and are good at mathematics, and have had some electronic experience—you can qualify for CREI and for the fruits which await you upon graduation.

**CREI ALSO OFFERS RESIDENCE TRAINING**

CREI Residence School in Washington, D.C. offers training at same high technical level. Classes start at regular intervals. Qualified residence school graduates earn degree: "Associate in Applied Science." Check coupon if you prefer residence study.

**KOREAN WAR VETERANS:**

If you were discharged after June 27, 1950, let the new G. I. Bill of Rights help you obtain resident instruction. Check coupon for full information.

**DON'T WASTE ONE MINUTE, INVEST TWO MINUTES . . .**

. . . and fill out the coupon—mail it right away. No obligation—you have nothing to lose but your present job in exchange for more money, a bright future and job security in a wide choice of electronics fields. Act today—and you'll receive your free booklet and the CREI plan by return mail. No obligation.



**MAIL THIS COUPON Today!**

**CAPITOL RADIO ENGINEERING INSTITUTE**

Accredited Technical Institute Curricula • Founded 1927  
 3224 16th St., N.W., Dept. 146-C, Washington 10, D.C.

Please send me your course outline and FREE illustrated Booklet "Your Future in the New World of Electronics" . . . describing opportunities and CREI home study courses in Practical Electronic Engineering.

- CHECK FIELD OF GREATEST INTEREST**
- Practical Radio Electronic Engineering
  - Broadcast Radio Engineering (AM, FM, TV)
  - Practical Television Engineering
  - Practical Aeronautical Engineering
  - Electronic Engineering

To help us answer your request intelligently, please give the following information:

**EMPLOYED BY** \_\_\_\_\_

**TYPE OF PRESENT WORK** \_\_\_\_\_

**SCHOOL BACKGROUND** \_\_\_\_\_

**ELECTRONIC EXPERIENCE** \_\_\_\_\_

Name \_\_\_\_\_

Street \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

CHECK:  Home Study  Residence School  
 Korean Veteran





# RADIO'S ONE- WAY STREET



Dr. S. Weisbaum assembles an isolator which he developed for use in a new microwave system. Dr. Weisbaum is a Ph.D. in microwave spectroscopy from New York University. He is one of many young men at Bell Laboratories applying the insight of the physicist to develop new systems of communication.

New radio relay systems for telephone and television now in the making will employ an ingenious device invented by Bell scientists. The device, known as an "isolator," senses which way microwaves are traveling through a waveguide, and stops those going the wrong way.

In the new systems a klystron wave generator sends signals through a waveguide to the antenna. The klystron must be shielded from waves reflected back along the waveguide by the antenna. The isolator stops reflections, yet allows the transmitted signals to go through clear and strong.

This isolator is a slab of ferrite which is mounted inside the waveguide, and is kept magnetized by a permanent magnet strapped to the outside. The magnetized ferrite pushes aside outgoing waves, while unwanted reflected waves are drawn into the ferrite and dissipated. This "field displacement" action results from the interplay between microwaves and a ferrite's spinning electrons. Bell physicists discovered this action during their fundamental studies of ferrites.

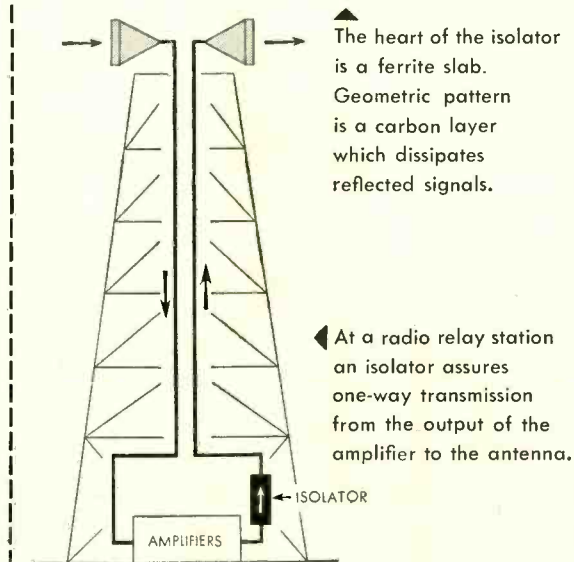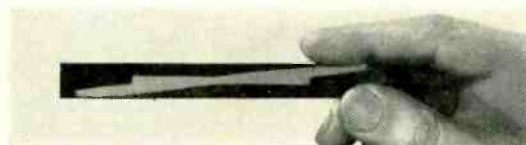This is another example of how Bell Telephone Laboratories research works to improve American telephony and telecommunications throughout the world.



**BELL TELEPHONE LABORATORIES**

WORLD CENTER OF COMMUNICATIONS RESEARCH AND DEVELOPMENT



**NEW! COLOR and Black-&-White  
LAB & TV 5" OSCILLOSCOPE #460  
KIT \$79.95. Wired \$129.50**

The **FINEST** professional 5 mc wide-band scope value. Ideal for research, h-f & complex waves, plus Color & Monochrome TV servicing. Flat from DC to 3.58 mc  $\pm 1$  db (color burst freq.), flat DC to 4.5 mc  $+1, -3$  db. Vert. sens. 25 rms mv/in. Vert. Z 3 megs. Has the following outstanding features not found in scopes up to several times its price, kit or wired:

**VERTICAL AMPLIFIER:** direct-coupled (DC) thruout to eliminate l-f phase shift; push-pull thruout for negligible distortion; K-follower coupling between push-pull pentode stages for extended h-f resp. (minimizes h-f phase shift, extends useful resp. to 10 mc); full-screen undistorted vert. defl; 4-step freq-compensated decade step attenuator up to 1000:1. **SWEEP CIRCUIT:** perfectly linear sweeps, 10 cps - 100 kc (ext. cap. for down to 1 cps); pre-set TV vert. & hor. positions (30 & 7875 cps); automatic sync. ampl. & limiter eliminates sync amplitude adj. **PLUS:** direct or cap. coupling; bal. or unbal. inputs; edge-lit engraved lucite graph screen; dimmer; anti-glare filter; bezel fits std photo equip. **OTHER IMPORTANT FEATURES:** High intensity trace CRT. Finest sq. wave resp. (.06 usec rise time). Push-pull hor. ampl., flat to 400 kc, sens. 0.6 rms mv/in. Built-in voltage calibration. Intensity mod. Sawtooth & 60 cps outputs. Astigmatism control. Retrace blanking.

Instant, drift-free full-screen vert. positioning & 2X full-screen hor. positioning. Bal., cal., astig. adj. externally accessible. 5U1 CRT, 2-6AU8, 2-6CB6, 1-12AU7A, 2-6J6, 1-6AX5, 1-1V2. Deep-etched satin aluminum panel, rugged grey wrinkle steel cabinet. Designed for easy building at home with no special equipment. 13" x 8 1/2" x 16". 30 lbs.

**SCOPE DIRECT PROBE\* #PD:** KIT \$2.75. Wired \$3.95. Eliminates stray-pick-up & signal re-radiation.

**SCOPE DEMODULATOR PROBE\* #PSD:** KIT \$3.75. Wired \$5.75. Demodulates AM carriers between 150 kc and 250 mc.

**SCOPE LOW CAPACITY PROBE\* #PLC:** KIT \$3.75. Wired \$5.75. For signal tracing in high frequency, high impedance & wide-band circuits (as in TV) without distortion from overloading or frequency discrimination.

for **COLOR** and Monochrome TV servicing

**New! PEAK-to-PEAK VTVM #232  
& UNI-PROBE (pat. pend.)  
KIT \$29.95. Wired \$49.95**

**UNI-PROBE:** exclusive with EICO! Terrific time-saver! Only 1 probe performs all functions—a half-turn of probe-tip selects DC or AC-Ohms.

The new leader in professional peak-to-peak VTVMs. Latest circuitry, high sensitivity & precision, wide ranges & versatility. Calibration without removing from cabinet. New balanced bridge circuit. High Z input for negligible loading. 4 1/2" meter, can't-burn-out circuit. 7 non-skip ranges on every function. 4 functions: +DC Volts, -DC Volts, AC Volts, Ohms.

Uniform 3 to 1 scale ratio for extreme wide-range accuracy. Zero center. One zero-adj. for all functions & ranges. 1% precision ceramic multiplier resistors. Measure directly peak-to-peak voltage of complex & sine waves: 0-1, 14, 42, 140, 420, 1400, 4200. DC/RMS sine volts: 0-1.5, 5, 15, 50, 150, 500, 1500 (up to 30,000 v. with HVP probe, & 250 mc with PRF probe). Ohms: 0.2 ohms to 1000 megs. 12AU7, 6AL5, selenium rectifier; xfmr-operated. 8 1/2" x 5" x 5". Deep-etched satin aluminum panel, rugged grey wrinkle steel cabinet. 7 lbs.

**New! DELUXE PEAK-to-PEAK VTVM #249  
with 7 1/2" METER & UNI-PROBE (pat. pend.)  
KIT \$39.95. Wired \$59.95**

All the advanced & exclusive features of #232—PLUS the extra convenience and readability of its big 7 1/2" meter. Your ideal bench instrument.

**VTVM RF PROBES\* #PRF-11 or PRF-25:** KIT \$3.75. Wired \$4.95. Accuracy  $\pm 10\%$ . Use with any 11 or 25 megohm VTVM.

**VTVM HV PROBE #HVP-2:** Wired \$4.95. Complete with multiplier resistor. Measures up to 30 kv with any VTVM or 20,000 ohms/volt VOM.



Calibration without removing from cabinet.

\*Only EICO Probes have all these features: fully shielded; rugged terminal board parts mounting; shock-mounted floating construction; swivel-action; color-coding; easy parts accessibility.



150 kc to 435 mc  
with ONE generator!

**New! RF SIGNAL GENERATOR #324  
KIT \$26.95. Wired \$39.95**

for **COLOR** and Monochrome TV servicing

New wide-range, stable generator — better value than generators selling at 2 or 3 times its cost! Ideal for: IF-RF alignment, signal tracing & trouble-shooting of TV, FM & AM sets; marker gen.; 400 cps audio testing; lab. work. 6 fund. ranges: 150-400 kc, 400-1200 kc, 1.2-3.5 mc, 3.5-11 mc, 11-37 mc, 37-145 mc; 1 harmonic band 111-435 mc. Freq. accurate to  $\pm 1.5\%$ ; 6:1 vernier tuning & excellent spread at most important alignment freqs. Etched tuning dial, plexiglass windows, edge-lit hairlines. Colpitts RF osc., directly plate-modulated by K-follower for improved mod. Variable depth of int. mod. 0-50% by 400 cps Colpitts osc. Variable gain ext. mod. amplifier: only 3.0 volts needed for 30% mod. Turret-mounted coils slug-tuned for max. accuracy. Fine & Coarse (3-step) RF attenuators. RF output 100,000 uv; AF sine wave output to 10 volts. 50-ohm output Z. 5-way jack-top binding posts for AF in/out; coaxial connector & shielded cable for RF out. Tubes: 12AU7, 12AV7, selenium rectifier; xfmr-operated. Deep-etched satin aluminum panel, rugged grey wrinkle steel cabinet. 8" x 10" x 4 3/4". 10 lbs.

The specs are the proof...

**4 NEW BEST BUYS  
by EICO**

**COMPLETE  
with Pre-amplifier, Equalizer and Control Section  
New! 20-WATT Ultra-Linear Williamson-  
type HIGH FIDELITY AMPLIFIER #HF20  
KIT \$49.95. Wired \$79.95**

A low-cost, complete-facility amplifier of the highest quality that sets a new standard of performance at the price, kit or wired. Every detail, down to the etched, brushed solid brass control plate, is of the fine quality EICO is famous for.

Rated power output: 20 watts (34 w peak). IM distortion (60 cps): 6 kc/4:1 at rated power: 1.3%. Mid-band harmonic distortion at rated power: 0.3%. Maximum harmonic distortion between 20 and 20,000 cps at 1 db under rated power: approx. 1%. Power response (20w):  $\pm 0.5$  db 20-20,000 cps;  $\pm 1.5$  db 10-40,000 cps. Frequency response (1/4w):  $\pm 0.5$  db 13-35,000 cps;  $\pm 1.5$  db 7-50,000 cps.

5 feedback equalizations for LP's & 78's including RIAA. Variable turnover feedback tone controls do not affect volume & permit large boosts or cuts at either end of audio spectrum with mid-freqs. unaffected. Loudness control & separate level set control on front panel. Low Z output to tape recorder. 4 hi-level switched inputs: tuner, tv, tape, auxiliary (xtal/ceramic phono or 2nd tuner); 2 low-level inputs for proper loading with all leading magnetic, FM & quality xtal cartridges. Hum bal. control. Extremely fine output transformer has interleaved windings, tight coupling, careful balancing & grain-oriented steel. 8 1/2" x 15" x 10". 24 lbs.

These amazing EICO values are **NOW IN STOCK** at your nearest distributor. Examine them side-by-side with ANY competitor. You'll see for yourself why indeed EICO is your **BEST BUY**. Fill out coupon on reverse page.


TURN PAGE FOR MORE EICO VALUES...

84 Withers Street, Brooklyn 11, New York

\*Prices 5% higher on West Coast.



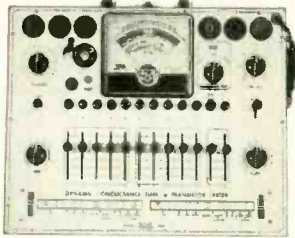
**the specs are  
the test that tells  
who's best!**



for COLOR & Monochrome  
TV servicing

**NEW! DYNAMIC  
CONDUCTANCE TUBE &  
TRANSISTOR TESTER #666**  
KIT \$69.95 WIRED \$109.95

Unexcelled testing thoroughness & accuracy. Checks transistor collector current & Beta using internal dc power supply. Tests all receiving tubes including subminiatures (& Color & Monochrome tv pic tubes with accessory adapter). Composite indication of mutual conductance, plate conductance, & peak emission. Simultaneous sel. of any 1 of 4 combinations of 3 plate, 3 screen, & 3 ranges of control grid voltage. Grid voltage variable over 3 ranges with 5% accurate pot. New series-string voltages for 600, 450 & 300 ma types. 5 ranges meter sens. with 1% precision shunts & 5% accurate pot. 10 SIX-position lever switches for free-point connection of every tube pin or cap. 10 pushbuttons for rapid insert of any tube element in leakage circuit & speedy sel. of individual tube sections. Direct reading of inter-element leakage in ohms. New gear-driven rollchart. Steel case with cover & handle. Sensitive 200  $\mu$ a meter.

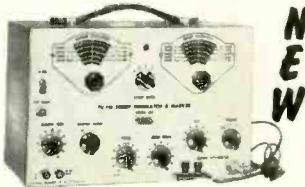

**NEW**

for COLOR & Monochrome  
TV servicing  
**TV-FM SWEEP GENERATOR  
& MARKER #368**

KIT \$69.95 WIRED \$119.95

The FINEST service instrument of this type ever offered in either kit or wired form at ANY price! Outstanding ease & accuracy in FM & TV (including Color) alignment. Entirely electronic sweep circuit with accurately biased Incredulor: superb linearity on both sides of selected center freq. Newly-designed AGC circuit automatically adjusts osc. for max. output on each band with min. amplitude variations. Sweep gen. range 3-216 mc in 5 OVERLAPPING FUND. BANDS. Sweep width continuously variable from 0-3 mc lowest max. deviation to 0-30 mc highest max. deviation. Variable marker gen. range from 5-75 mc in 2 FUND. BANDS plus a calibrated harmonic band (54-225 mc). Variable marker calibrated with int. xtal marker gen. 4.5 mc xtal included. Ext. marker provision. Double pi line filter. Edge-lit hairlines eliminate parallax.

Turn page for other EICO ad



**FREE 1956  
EICO CATALOG!**

Tells you how to **SAVE 50%** on  
your test equipment costs!

 <p><b>TUBE TESTER #625</b> KIT \$34.95 Wired \$49.95</p> <ul style="list-style-type: none"> <li>• tests 600 mil series string type tubes</li> <li>• illuminated roll-chart</li> </ul> <p>Pix Tube Test Adapter ..... \$4.50</p>	<p><b>New! GEIGER COUNTER #803</b> KIT \$19.95      Wired \$29.95</p>  <p>(less batteries) Professional, all-electronic, sensitive, rugged—at lowest cost! Indicates by neon lamp &amp; headphone clicks.</p>	 <p><b>5" PUSH-PULL OSCILLOSCOPE #425</b> KIT \$44.95 Wired \$79.95</p>  <p><b>7" PUSH-PULL OSCILLOSCOPE #470</b> KIT \$79.95 Wired \$129.50</p>																					
 <p><b>VACUUM TUBE VOLTMETER #221</b> KIT \$25.95 Wired \$39.95</p> <p><b>DELUXE VTVM #214 (7 1/2" METER)</b> KIT \$34.95 Wired \$54.95</p>	 <p><b>RF SIGNAL GENERATOR #320</b> KIT \$19.95 Wired \$29.95</p> <p>150 kc-34 mc, calibrated harmonics to 102 mc. Pure or mod. RF, &amp; Colpitts osc. 400 cps sine outputs.</p>	<p><b>NEW! UTILITY TESTER #540</b> KIT \$12.95 Wired \$15.95</p>  <p>Multi-range ac/dc voltmeter, ammeter, ohmmeter, wattmeter, leakage checker for home &amp; auto repairs.</p>																					
 <p><b>#944 FLYBACK TRANSFORMER &amp; YOKE TESTER</b> KIT \$23.95 Wired \$34.95</p> <ul style="list-style-type: none"> <li>• fast check all flybacks &amp; yokes in or out of set.</li> <li>• spots even 1 shorted turn!</li> </ul>	 <p><b>TV/FM SWEEP GENERATOR #360</b> 5MC-4.5MC CRYSTAL ..... \$3.95 ea.</p> <p>Range 500 kc-228 mc on fund. Cont. sweep width control, 0-30 mc.</p> <p>KIT \$34.95 Wired \$49.95</p>	 <p><b>DELUXE RF SIGNAL GENERATOR #315</b></p> <p>1% accuracy on all 7 ranges. Range 75 kc-150 mc. Volt reg.</p> <p>KIT \$39.95 Wired \$59.95</p>																					
 <p>Sep. volt-meter &amp; ammeter KIT \$29.95 Wired \$38.95</p>	 <p><b>DELUXE MULTI-SIGNAL TRACER #147</b></p> <p>Sep. hi-gain RF &amp; lo-gain audio inputs. Special noise locator. Calibrated wattmeter.</p> <p>KIT \$24.95 Wired \$39.95</p>	 <p><b>R-C BRIDGE &amp; R-C-L COMPARATOR #950B</b></p> <p>Reads 0.5 ohms -500 megohms, 10 mfd-5000 mfd power factor.</p> <p>KIT \$19.95 Wired \$29.95</p>																					
 <p><b>HI-FI PREAMPLIFIER #HF-6</b> KIT \$24.95. Wired \$37.95. With Power Supply: KIT \$29.95. Wired \$44.95</p> <p>Feedback circuitry thruout! Preamplifier, tone controls, scratch &amp; rumble filters, K-follower output.</p>	 <p><b>20,000 Ohms/Volt MULTIMETER #565</b> KIT \$24.95 Wired \$29.95</p>  <p><b>1000 Ohms/Volt MULTIMETER #536</b> KIT \$12.90 Wired \$14.90</p>	<p><b>VTVM PROBES</b></p> <table border="0"> <tr> <td>Peak-to-Peak</td> <td>KIT \$4.95</td> <td>Wired \$6.95</td> </tr> <tr> <td>RF</td> <td>\$3.75</td> <td>\$4.95</td> </tr> <tr> <td>High Voltage Probe-1</td> <td></td> <td>\$6.95</td> </tr> <tr> <td>High Voltage Probe-2</td> <td></td> <td>\$4.95</td> </tr> </table> <p><b>SCOPE PROBES</b></p> <table border="0"> <tr> <td>Demodulator</td> <td>\$3.75</td> <td>\$5.75</td> </tr> <tr> <td>Direct</td> <td>\$2.75</td> <td>\$3.95</td> </tr> <tr> <td>Low Capacity</td> <td>\$3.75</td> <td>\$5.75</td> </tr> </table>	Peak-to-Peak	KIT \$4.95	Wired \$6.95	RF	\$3.75	\$4.95	High Voltage Probe-1		\$6.95	High Voltage Probe-2		\$4.95	Demodulator	\$3.75	\$5.75	Direct	\$2.75	\$3.95	Low Capacity	\$3.75	\$5.75
Peak-to-Peak	KIT \$4.95	Wired \$6.95																					
RF	\$3.75	\$4.95																					
High Voltage Probe-1		\$6.95																					
High Voltage Probe-2		\$4.95																					
Demodulator	\$3.75	\$5.75																					
Direct	\$2.75	\$3.95																					
Low Capacity	\$3.75	\$5.75																					

For FREE 1956 catalog, mail coupon NOW!



84 Withers St. • Brooklyn 11, N. Y.

Prices 5% higher on West coast ©56  
and subject to change without notice.

EICO, 84 Withers Street  
Brooklyn 11, New York

C-6

Send FREE 1956 Catalog and name of neighborhood EICO jobber.

Name.....

Home Address.....

City.....Zone.....State.....

Occupation.....

1945 to 1955: a decade of Know-How & Value Leadership in Kits & Instruments—over 1/2 million sold to date!



## ELECTRONICS IN SPACE FLIGHT

... *Without electronics, space exploration is impossible* ...

THE *International Geophysical Year* of 1958 will witness the first major effort in the field of true space flight. The United States Government will launch between 6 and 10 space satellites, now in the building stage. They will gravitate around the Earth at altitudes from 200 to 1,500 miles above sea level. Unmanned, they will be in constant touch with Earth scientists through a variety of telemetering electronic instruments while the 20-odd-inch-diameter satellites completely circle our planet in about 2 hours.

The main purpose of these tiny experimental space globes is purely exploratory — spatial probes to investigate the great outer void of the interplanetary vacuum — and enrich our knowledge of the physical universe.

Mankind, from the beginning of its billion-year existence, has always lived at the bottom of a dense — and protective — sea, the atmosphere. So far he has never ventured above it into outer space. Therefore our knowledge of the airless world is mostly theoretical. If we are to conquer it, we must know it thoroughly, lest we run afoul of its unknown dangers.

Our manless spaceships of the immediate future will probe free space with great efficiency. Soon we will have actual physical knowledge of a number of outer-space radiations from which we have always been shielded by our thick atmospheric blanket. These radiations comprise some from the sun: X-Rays, infrared and ultraviolet, corpuscular and electromagnetic. Others, the so-called cosmic radiation, come from the depths of space.

There are also radio waves originating from our Milky Way and other galaxies, though some come from our sun and from the planet Jupiter. In addition to these there may be as yet undiscovered varieties of stellar radiation hitherto unsuspected.

One thing we have learned during the past century — space is by no means empty, as we once thought. It is crowded with electrons, radiation, gravitational flux, hydrogen gas, solid particles such as cosmic clouds and meteoric dust.\* Yet, curiously enough, all these names in the final analysis mean one and the same thing — the building blocks of the universe. It was Einstein who first proved that mass and energy were the same — they are interchangeable.

It is more than likely that our space laboratories will greatly assist man in unraveling many of the universe's secrets. The time is coming when we can demonstrate at will that *everything* in our physical world is one — interchangeable into solids, waveforms, radiations, gravitation and now-unknown forces. It may be known in the future under an all-inclusive name such as *Ultimatter* or *Ultiemele* (ultimate + *ele*, Greek for matter.)

The intimate knowledge gained from our experimental satellites will, within a few short years, make it possible for us to proceed to the next stage of space exploration: unmanned spaceships to the moon. This will be a much

more ambitious project, a pilot flight by an atomic-powered rocket to be guided by radio and television\*.

This pioneer interplanetary flight, as foreseen by the writer, may take place about 1970 or before. From a technical standpoint it could take place much sooner, but its high building cost, running into the tens of millions of dollars, will prove an obstacle.

Such a television-controlled spaceship to circumnavigate the Moon and return to make a safe landing on the Earth after its 250-hour trip is unthinkable without the most intricate array of electronic instrumentation, both on shipboard and on Earth. Scientists on Earth track the ship by radar during its entire flight (except for the short time when it disappears behind the moon). Television cameras on board continuously scan the test animals in their cages, so we can see how they fare and behave in their weightless state throughout the trip. TV cameras attached to a number of special telescopes continuously scan the heavens so the watching astronomers on Earth can see the planets, stars and nebulae as they really are, without the interference of a thick, obscuring atmosphere. A vast array of telemetering instruments report the temperatures from minute to minute in outerspace or inside the ship, radiations of every kind, frequency of meteoric dust impact on the ship's outer skin, gravitational flux and solar corona phenomena.

Microphones in various strategic parts of the ship report a constant stream of important information to the listening Earthpost scientists. Sounds from the animal quarters, sounds from the atomic engines, the hail-like bombardment sounds from the outer skin of the ship, from the impinging meteoric dust traveling at 5 to 15 miles *a second*, the stress sounds of the ship's metallic skin as it expands and contracts under the enormous temperature differences in outer space, from the 300°F heat on the sunny side to the -200°F cold on the dark side of the ship.

If the rocket ship gets off course, this can be automatically corrected by an electronic navigator on board, which then fires corrective rocket blasts. If the ship's automatic navigator should fail, a standby electronic navigator on Earth takes over via microwave. Nothing is left to chance. Likewise, on its return to Earth, the spaceship is landed at a specially selected and prepared landing field by scientists via radio impulse. In addition, for future study and research, *all* telemetered signals are recorded on tape on board ship and on Earth.

After a few such remote-control unmanned lunar flights, sufficient scientific experience and knowledge will have accumulated to make possible the third and final stage of man's conquest of the great universal void: *manned outer-space flight*, to the Moon, the planets and beyond.

—H. G.

\* See also "How Empty Is Space" by H. Gernsback, March 1923 *Science & Invention*.

\* See the *Television Guided Spaceship*, by H. Gernsback, *Forecast* 1954 (Christmas, 1953)



# HIGH-GAIN

# TRANSISTOR AUDIO AMPLIFIER

By JOSEPH BRAUNBECK

*Using six transistors, unit solves impedance mismatch problems*

**T**RANSISTORIZED audio amplifiers having low and medium gain and using one to four junction transistors are common. But how many transistor stages may be added without risking instability and excessive noise? This amplifier shows that up to six stages may be combined without these troubles.

Excellent results are obtained using grounded-collector and grounded-emitter stages together. Such a high-gain transistorized amplifier has many applications. Besides all purposes for which you need an audio amplifier with high gain and low output, it may be converted to an acoustic burglar alarm, a receiver for low-frequency wireless communication, a "speech-on-light" receiver, etc.

A junction transistor may be connected three ways: you can ground either base, emitter or collector. The grounded-base circuit, which is most important for the point-contact transis-

tor, is not very common in junction-transistor circuitry. Grounded-emitter stages have to be matched to a low-impedance input and a high-impedance output. A grounded-collector stage, however, has much different matching impedances: its input impedance is high, output impedance low.

If, as usual, several grounded-emitter stages are combined by transformerless R-C coupling, there is considerable mismatch between any two succeeding stages (Fig. 1-a), reducing gain. This may be avoided by combining grounded-emitter and grounded-collector stages (Fig. 1-b), providing better interstage matching. It is still not quite correct from the theoretical point of view, but the horrible mismatch between two grounded-emitter stages is avoided.

The complete amplifier circuit is shown in Fig. 2. The grounded-emitter stages use 2N38 junction transistors, the 2N36's are used with their collectors grounded. The 100,000-ohm resistors between the transistor bases and negative supply provide the necessary bias. The internal resistance of the single flashlight cell (which is the whole power supply) is low enough to prevent motorboating.

Every grounded-collector stage is thermally stabilized by itself, thanks to the load resistor in the emitter lead. All load resistors are 3,300 ohms. Coupling capacitors are 3  $\mu$ f for the grounded-collector inputs and 25  $\mu$ f for the grounded-emitter inputs. These values are not at all critical. The output is designed for use with a low-impedance miniature earphone. A 3,300-ohm load resistor shunts the output terminals to permit an oscilloscope or similar test gear to be connected to the amplifier.

The input is designed for low-impedance matching, too. A dynamic or magnetic microphone may be connected directly to it.

### Circuit applications

What is this elaborate amplifier good for? One possible application is shown in Fig. 3. Take a single headphone with an impedance of between 50 and 100 ohms. Connect it as a magnetic microphone to the input of the amplifier. Listen with a hearing-aid type miniature earphone—you will hear a faint hiss. This is the noise which prevents you from adding further stages. The amplifier now serves as a supersensitive listening device, but it is not a hearing aid! *For this purpose amplification is too great.* But you can use it to hear many things which you never heard before. For example, put the microphone on your chest and listen to your heartbeat. Do not speak while you do so; it would be painful for your ears.

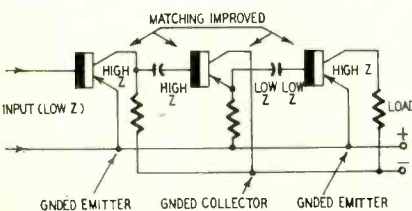
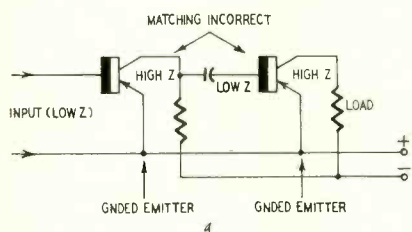


Fig. 1—Improving interstage mismatch.

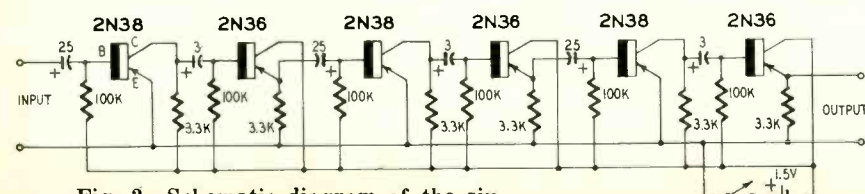


Fig. 2—Schematic diagram of the six-transistor high-gain audio amplifier.

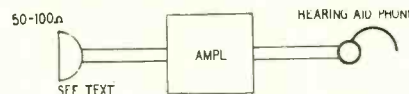


Fig. 3—A supersensitive amplifier.

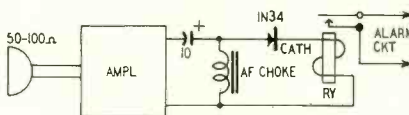


Fig. 4—An acoustic burglar alarm.


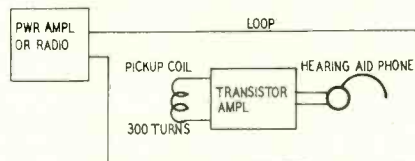


Fig. 5—Speech-on-loop diagram.

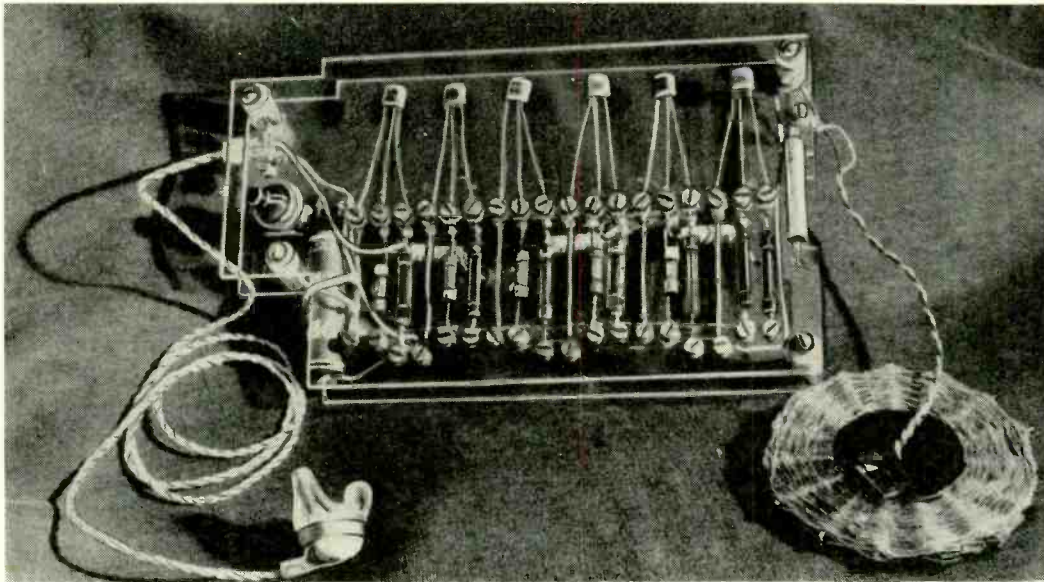

The high-gain amplifier connected to pickup coil for speech on loop.

**Acoustic burglar alarm** Disconnect the listening earphone from the amplifier. Add a coupling capacitor, an af choke, a crystal diode and a sensitive relay (Fig. 4). This changes the listening amplifier into an electronic burglar alarm. Any noise picked up by the microphone generates a voltage across the output terminals of the amplifier. This is rectified by the crystal diode, and rectified current actuates a sensitive relay.

For best results use a highly sensitive relay like the Weston Sensitrol or the Siemens polarized relay. They hold the contacts closed after their coil has been energized. Thus, noise starts the alarm which remains on until it is reset. Polarized telegraph relays are much quicker acting than the moving-coil types.

This alarm is very sensitive. It responds to speech at a distance of 30 feet. Nobody can break through a door fitted with the microphone. The relay

amplifier instead of a conventional hearing-aid circuit, real "dx" may be obtained. I installed one loop around a small room in the second floor of an apartment house and fed into it the output of a small phono amplifier (about 4 watts). Reception was perfectly clear and loud all over the street in front of the house. A coil of 300 turns on a 2-inch-diameter form served as a pickup coil.

**Phototransistor amplifier** The first transistor may be replaced by a phototransistor such as the X-25 (made by Transistor Products, Inc.). Fig. 6 shows the modified circuit. This transistor needs no bias. It has to be connected "upside down" with the emitter negative and the collector positive, as it is an n-p-n transistor. This circuit is that of a sensitive modulated light receiver.

Circuits for obtaining modulated light have been described very often.

the audio to be transmitted. Old hams will recognize this good old Heising modulator circuit. Though it works well indoors, you will have trouble when you want to focus the light beam over greater distances. In that case a conventional light modulator must be used.

As phototransistors are very sensitive to infra-red radiation, this device may also be used to detect infra-red radiation from devices such as hot stoves and soldering irons. In that case the radiation has to be chopped mechanically to give an ac signal. Chopping can be done with a small cardboard fan rotating in front of the transistor.

**Construction**

Thanks to the low input impedances of transistor stages as compared to vacuum-tube stages, capacitive hum cannot occur in a transistor amplifier. Therefore there is no need for a

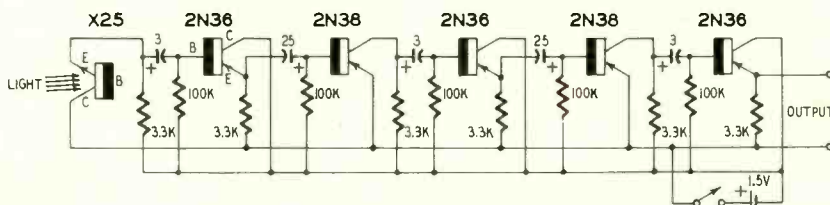


Fig. 6—A phototransistor amplifier. The X-25 does not require any bias.

will snap on if you rub the door with your fingertip.

**Speech on loop** Wireless communication within a certain area—a garden, house or room—is often established with a "speech-on-loop" system. A loop of wire surrounds the area. The loop is connected to the low-impedance output of a power amplifier (Fig. 5). The receiver consists of a small pickup coil connected to an earphone via the amplifier. The receiver picks up messages or music transmitted by the big loop everywhere inside as well as for some distance outside of it.

If you use the six-stage transistor

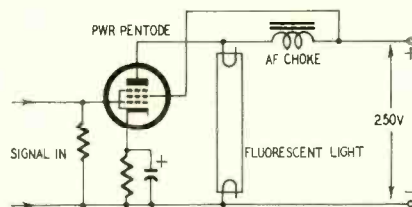


Fig. 7—Obtaining modulated light.

A very good one is shown in Fig. 7. A fluorescent light is connected in parallel with a power pentode. B plus is fed to both the pentode and the light through an audio-frequency choke. The control grid of the pentode is fed with

**Parts for transistor audio amplifier**

- 6—3,300-ohm 1/2-watt resistors; 6—100,000-ohm 1/2-watt resistors; 3—3- $\mu$ f, 3—25- $\mu$ f, 6-volt filter capacitors; 3—2N36, 3—2N38 transistors; 1—1.5-volt cell; 1—spst switch; 1—chassis (could be constructed on a plastic subchassis); 2—sets of terminals (input and output).

metallic chassis. The experimental model of the amplifier has been built on a sheet of polystyrene. Every soldering connection is supported by a soldering tag held by a screw. To keep the transistors from vibrating they are held in place by cellulose tape. Another polystyrene sheet of the same size and form is used as a cover to protect the transistor from curious fingers when the unit is used for demonstration. This way of construction might be called a sandwich layout, as the whole circuitry is enclosed between the polystyrene sheets. However, every point in the circuit is electrically accessible, as every soldering tag is held by one of the screws visible in the photograph of the amplifier. This unit is stable and should find many applications. END



# Servicing Home Tape Recorders

*Part II—Locating the source of weak or no sound, distortion, hum and noise*

By HERMAN BURSTEIN

**W**HERE the sound is weak or nonexistent, a preliminary check would consist of playing back a test tape (or other previously recorded tape). If the recorder functions in playback, the fault is in the record section. If not, the trouble lies in playback or in both record and playback.

Before signal tracing, test tubes and check for B-plus voltage and high resistance to ground (50,000 ohms or more) at the rectifier cathode. B plus at the rectifier is generally about 250 volts; at the plates of the various tubes it may range from as low as 50 in the early stages to 180 volts or more in later stages.

If playing back the test tape indicates trouble in the playback function and if the machine contains a built-in power amplifier and speaker as most home recorders do, it is advisable first to check the speaker by applying a signal to the power amplifier.

If it appears that the difficulty is in the record or playback preamplifier, signal tracing similar to that used for radio, TV, amplifiers, etc., may be applied. Commonly, an audio signal is fed to the grid of the output stage and output is observed on an oscilloscope or vtvm. Signals of lower amplitude are then fed to earlier stages. If the output signal disappears, the stage at which the signal was applied should be checked for defective components.

Tape recorders have relatively com-

plex arrangements for switching from record to playback. Some of the complexity is in the equalization circuits. In tape recording, the practice is to supply all or most of the treble boost in record and all or most of the bass boost in playback. Consequently, some tape recorders which use the same preamplifier for record and playback switch in different equalizing circuits for each function. When dealing with an elusive difficulty, do not overlook the possibility that it may lie in a switch or one of the circuit components controlled by it. Trouble is sometimes due to a dirty switch contact, easily remedied by applying volume-control cleaning fluid. However, more serious defects may call for a new switch, often a special item available only from the factory or a repair specialist.

Failure in record or playback may be due to a head with an open or shorted coil. To check for a shorted record head, feed an audio signal of about 1 volt

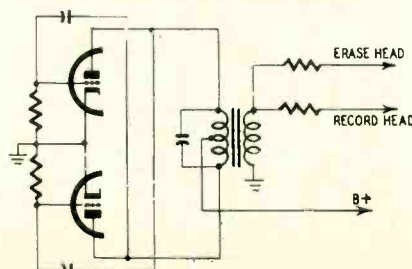


Fig. 1—Typical bias oscillator circuit.

into the record preamplifier and observe with an oscilloscope whether this signal is present across the record head—a shorted head shows no signal. The bias oscillator must be disabled before this test to prevent it from interfering with the pattern on the oscilloscope. This may best be done by removing the oscillator tube. To check for an open coil in the record head, connect a 100-ohm resistor between ground and the ground lead of the head. Then observe whether there is a signal across the resistor—no signal appears if the coil is open. If neither the short nor open test shows a signal at the head, then the record preamplifier should be checked.

To check for a defective playback head, disconnect the head and substitute an audio signal of about 10 millivolts at the grid of the first playback tube. The output of the playback preamplifier should produce a signal of about 0.5 volt or more. If not, the preamplifier rather than the head should be suspected.

Another means of checking for defective heads, if a tape recorder of the same or similar brand in good condition is available, is to bridge the transport mechanism and heads of the second machine across the recorder being checked and then make a tape recording. Leads from the heads being checked should be disconnected from the preamplifiers and leads from the other heads connected in their place. If sound, after recording and playback, appears reasonably normal, the heads of the machine under test are apparently defective.

A dead bias oscillator can account for very low, as well as distorted, output.

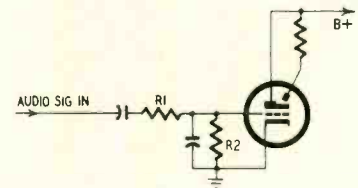


Fig. 2.—Electron-ray indicator circuit.

Fig. 1 shows a typical oscillator. With the recorder in record position, the presence of bias current may be determined by measuring the voltage across a 1,000-ohm resistor placed between ground and the ground lead of the record head. Since the bias current may be less than 1 ma, the voltage reading will be from a fraction of a volt to a few volts. Working farther back into the oscillator circuit, test at the grids of the oscillator tube for a high negative voltage which should be present if oscillation is taking place. If there is no oscillation, the circuit components should be checked.

### Distortion

This can result from too low a bias current that in turn may be due to a defect in the oscillator or to a resistor or capacitor which couples the bias current to the record head.



A frequent source of distortion is excessive recording level. Home tape recorders contain an electron-ray tube, neon bulb or VU meter to indicate when the recording level is such as to produce the maximum tolerable distortion. At this point the ray tube closes fully, the neon bulb lights or the VU pointer swings to a designated point. However, change in value of a circuit component may cause the indicator to read low, thus encouraging too high a recording level. Fig. 2 shows a typical electron-ray tube circuit. If R1 of the voltage divider to which the grid is connected increases considerably in value, the user is apt to be led into overrecording, with consequent distortion, because the audio signal required to close the "eye" is greater than it should be. The relationship between recording level and distortion is far from a linear one. Beyond the point where about 2% or 3% harmonic distortion occurs, a few db increase in recording level produces a vast increase in distortion. Thus the increase in distortion through slight overrecording is of far greater consequences than the reduction in signal-to-noise ratio through moderate underrecording.

To measure the point at which distortion begins to be discernible, use a scope. However, the human eye begins to detect harmonic distortion in a sine wave only when it reaches about 5%. Therefore, it is advisable to calibrate the indicator so that it registers maximum level at about one-half the recording level which produces visible distortion on the oscilloscope; in the case of a VU meter, however, about 8 db additional allowance may be made for the fact that the pointer cannot move rapidly enough to follow transients fully. If a harmonic or intermodulation distortion meter is available, more accurate calibration is possible. The intermodulation test is the better of the two and the level indicator should be calibrated to read maximum when IM distortion is about 5%, using a 4-to-1 ratio between a low frequency and a high one. If the harmonic distortion meter is used, calibration should be based on a level of about 2% distortion. More satisfactory calibration is obtained by the IM test because overrecording causes intermodulation to rise much more rapidly than harmonic distortion.

Faulty components in the preamplifier may cause distortion. Waveform checking with an oscilloscope is useful. Also, a harmonic or intermodulation distortion meter can be helpful in checking for distortion stage by stage, using the signal-tracing technique. Tracing should be done with the heads disconnected. When working back in the circuit, the signal should of course be reduced. By the time the first stage is reached, the signal input should be reduced to about 1 volt if the record preamplifier is being checked and 10 millivolts if the playback preamplifier is being checked. Otherwise overloading

of one or more stages may be the result.

#### Hum and noise

The listening satisfaction provided by a tape recorder depends not only upon low distortion and good frequency response, but also upon a satisfactory ratio between the desired audio signal and the undesired hum and noise generated by the recorder. Although it is not ordinarily the service technician's task to make changes in design, in the interest of cutting hum and noise there are some simple, rapid expedients he can try.

Hum may be of three kinds: principally fundamental (60-cycle) pickup from the power transformer or from power and heater leads; principally second-harmonic pickup (120 cycles) from the B supply; principally third-harmonic pickup from a motor or the power-transformer primary. Pickup may be inductive (hum fields) or capacitive (lead dress or insufficient B filtering).

Hum pickup can result from improper dress of heater and low-level grid leads. Special care must be observed in the lead dress from the playback head to the grid of the first playback tube. A filter capacitor may be at fault. Even though the existing filter capacitors check out good, adding a large capacitor—40 $\mu$ f or more—sometimes brings a significant improvement. Measures such as tightening the laminations of the power transformer or reversing the heater lead connections can reduce hum. In two instances that have come to my attention, an annoying hum which no other measures could alleviate was reduced to insignificance by removing the power transformer from the preamplifier chassis and mounting it elsewhere in the housing for the transport mechanism and preamplifier.

Some tape recorders have a hum balancing control which may not be properly adjusted. Usually the center arm of the control goes to ground. Occasionally, better results can be had by disconnecting the arm from ground and connecting it to between 10 and 75 volts. This voltage can sometimes be found at the cathode of the output tube of the internal power amplifier. If no such voltage is available, it can be obtained by putting two resistors of suitable value in series between B plus and ground and adding a filter capacitor of 20  $\mu$ f at the junction of the resistors. Total value of the two resistors should be about 200,000 ohms.

Considerable hum reduction can sometimes be obtained by trying several tubes of the required type in the first stage of the record or playback preamplifier. Even tubes like the 5879, specially designed for high-gain audio applications, vary with respect to heater-cathode leakage, which results in hum when heaters are operated on ac. Such variations may be even greater for other tubes, such as the 12AX7 or 6AU6, used in the first stage of con-

ventional tape recorder preamplifiers.

As with hum, noise also varies among tubes of a given type. If noise rather than hum is the predominant offender, a first-stage tube may be selected on the basis of its noise characteristic, bearing in mind that it should also have the necessary gain.

Although tube hum and noise most commonly originate in the first stage, it is possible for later stages to be at fault. This may be quickly checked by removing the first-stage tubes from the record and playback preamplifiers, then making a tape with no signal input and volume control all the way up. This tape should then be compared with a similar tape made when the first-stage tubes are in the circuit.

Thermal agitation in resistors in the first stage of a preamplifier is sometimes an important cause of noise. Replacement of plate, screen and cathode resistors in this stage with low-noise types often brings substantial benefits. The use of oversize, standard resistors, for example, a 2-watt instead of a  $\frac{1}{2}$ -watt size, can accomplish the same results. Avoid overheating a replacement resistor during soldering for this can increase its noise characteristic.

Another important source of noise is distortion in the bias waveform. A clean sine wave produces least noise in recording. A dc component in either record or playback produces noise and an asymmetrical bias waveform in effect contains such a component. The bias frequency should be observed on an oscilloscope. If distortion is noticeable, components in the oscillator circuit should be checked.

Any dc component produces noise and such a component may originate in a magnetized record or playback head. A head can be readily demagnetized by carrying a magnetic eraser slowly to and away from it. If the technician does not already have such an eraser, he can make one from a discarded power transformer. The I plates are removed, all the E plates are faced the same way, all leads except to the primary winding are cut off, a line cord and plug are attached to the primary and the service technician has a powerful electromagnet. This can also be used for quick erasure of an entire reel of tape by bringing the reel to the magnet and withdrawing it slowly, meanwhile describing a circular motion. END



A recorder for home entertainment.



# FOR GOLDEN EARS ONLY



The Fentone B & O ribbon microphone

*Browning L-500 broadcast and shortwave tuner; Crestwood 404 tape recorder, and amplifier-speaker; Robins tape splicer; two ribbon microphones*

By MONITOR

**E**VEN under the best circumstances and with the best tuners AM reception is inferior to FM. However, there is a great deal to interest listeners on both the broadcast and shortwave bands between 5.8 and 18 mc. Moreover, in some places FM reception is too poor or programs do not provide adequate fare and one is dependent on AM broadcasts. There has, therefore, been a need for an accessory tuner capable of delivering the best possible quality from broadcast stations and of receiving the shortwave as well. The Browning L-500 fills this bill nicely.

Though it is extremely compact and can be squeezed into just about any odd corner in the hi-fi layout, the Browning is self-powered and delivers very fine performance. The sensitivity is specified to be 2  $\mu$ v or better. I could not measure it absolutely but it is comparable with my old SX-32 which is still in excellent condition. There is a built-in ferrite-rod antenna which will give adequate broadcast reception in most localities and a hank of antenna wire hidden around the room will provide excellent shortwave reception in most parts of the country. The receiver is commendably stable and free of drift, the AVC action is excellent and the noise figure very fine.

With no bandspread dial or knob, tuning shortwave stations is a somewhat delicate operation and exact logging is not possible. But with very little experience it is not at all difficult to find and

tune in the stations one wants. It is even possible to do a pretty good job of tuning through the 20-meter ham band. It has a hot rf stage and two if stages—which accounts for the fine sensitivity.

The fidelity, too, is about as good as is usable on the broadcast and shortwave bands. A broad-tuning position provides a passband of about 15 kc at 3 db down and a tuned-T whistle filter provides nearly complete attenuation of the 10-kc adjacent-channel beat note and of monkey chatter. Fig. 1 gives the overall response as measured at 1600 kc with an audio generator modulating an rf generator at about 40%. The listening quality is good. A cathode follower in the output permits the use of long cables and an extra jack is paralleled with the output jack for a tape recorder.

Personally I would have preferred to have the variable-bandwidth feature available also on the shortwave bands. Granting that there are few occasions when it is possible to use a wide bandwidth for shortwave reception, the opportunity does arise sometimes when stations are receivable above 16 mc and the broadcasts of the BBC especially meet high-fidelity standards. However, I suppose the arrangement leads to more foolproof operation. The Browning comes either in chassis form or in a small cabinet with a timer clock for automatic on-off operation optional.


### Crestwood 404 tape recorder

Priced at \$230, this unit is meant to fill the gap between the home type recorders selling in the region of \$100 and the semiprofessionals costing \$400 or more. It does better than meet the minimum standards for high fidelity, and is in many respects comparable to the semipro types.

The electronic portions of the recorder are not completely flat, having a -4-db slope at 15 kc and a -2-db slope at 20 cycles. The high-frequency slope can be compensated with the tone control and the curve of Fig. 2 was taken with the tone control adjusted to provide

a flat response to 10 kc. The output level amplifier and indicator circuits have an even greater slope at both ends, hence the response was measured at the output jack rather than the monitor-headphone jack.

Many other recorders, even those of professional quality, are guilty of the same sin but it is not an important one provided that one remembers not to adjust the recording level for extremely low tones. Adjusting for full closing of the eye on a 50- or 60-cycle or lower input would overload the tape in the normal peak region between 200 and 1,000 cycles, and probably also lead to saturation on the very high frequencies. This is unlikely to happen when recording music or voice. The curve was taken through the mike channel at the usual

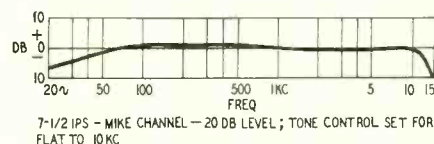

7-1/2 IPS - MIKE CHANNEL - 20 DB LEVEL; TONE CONTROL SET FOR FLAT TO 10KC

Fig. 2—Response of Crestwood 404.

-20-db level. The response through the radio channel is very little different. Beat notes appeared above 14,000 cycles and no attempt was made to measure above that point. Response at 3 3/4 ips was adequate for all voice use and good enough for AM recording.

The 404 tested was inferior to semipro and pro models (and below minimum high-fidelity standards) in distortion which amounted to nearly 4% harmonic at the peak input level (eye fully closed). Most of this was ascribable to the amplifiers which registered more than 2% when used as a PA pre-amp; it is possible the excessive reading was the result of a poor tube. The distortion is lower with the radio input. Distortion falls off fast as recording level is decreased and at a level of -10 db (eye about half closed) is quite acceptable.

Hum is more troublesome than with

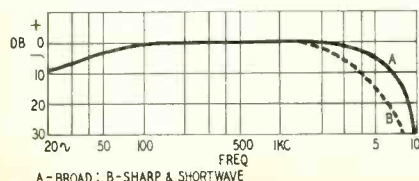


Fig. 1—Response of Browning L-500.

most semipro recorders but not a factor unless used with mikes of very low sensitivity. The wow and flutter were acceptable for nonprofessional and even for routine broadcast use and the lightness and compactness of the 404 lends itself nicely for portable applications.

Operation is simpler and more convenient than with most semipro types and incomparably better than with home types. Editing and cuing of adequate accuracy for routine broadcast use is possible. There is no provision for adjusting bias and the adjustment of recording and monitoring levels requires a service manual, instruments and some care. (Better leave it alone.) Head alignment is not too easy either but the mounting is such that loss of alignment should not occur under ordinary use. The heads, incidentally, are Brush.

A single motor is used for all operations through a well-thought-out and constructed mechanism which should give long service without trouble. The 404 can be used as a preamplifier to feed a power amplifier. Beside the mike and radio inputs it also has an input equalized for the G-E phono cartridge. With the Crestwood amplifier described below and a record player it will comprise a complete portable hi-fi or small PA system and deliver acceptable performance, considering its small size.

#### Crestwood amplifier-speaker


In a mere 1.5 cubic feet, this unit succeeds in delivering a response from 60-12,000 cycles highly acceptable for musical appreciation and above minimum high-fidelity standards.

The frequency response is little short of amazing, though the peak above 50 kc is excessive and, as the square waves indicate, results in a poorer transient response than one would like. However, the amplifier is completely stable under all normal operating conditions. The power output curve is excellent for small 6V6 amplifiers and the distortion (3% IM at 5 watts) is about average.

The listening quality is equal to that of average amplifiers with larger speakers. The fundamental response goes down to 60 cycles. The doubling below that impairs the definition but produces a bass which is sometimes awesome. The overall quality will permit a good evaluation of tape quality which is what it is principally intended to do. All in all, the system delivers notable quality for the space occupied.
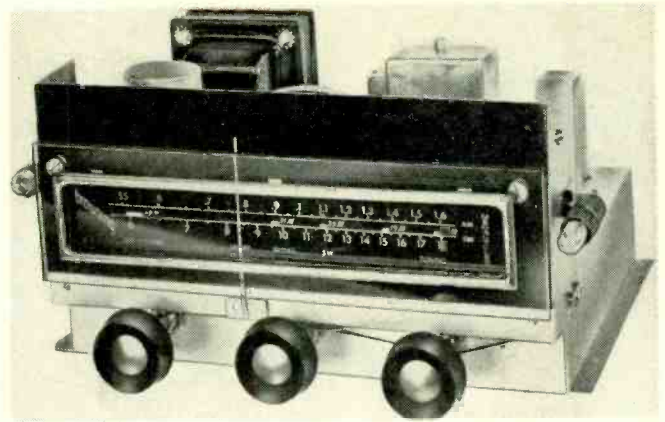
#### Robins Gibson-Girl tape splicer

More often than not the really big difference between amateur and professional or semiprofessional tapes is merely the editing. Many amateurs own recorders and mikes as fine as those used by recording studios; many also have considerable skill in mike placement, control of dynamic range, proper tone balance, etc. The professional, however, ends up with a better tape because he has more skill in taking out faults, synthesizing several versions into one, excerpting, etc. Tape editing is an art but



The Browning L-500 AM tuner.

as in all arts good tools help. The essential tool is a good tape splicer but it is amazing how few amateurs own one.

I have been using the Robins Gibson-Girl splicer many months and recommend it heartily. It is both effective and easy to use and the Gibson-Girl splice it makes is corrective for the error which produces most trouble with splices: letting the adhesive tape stick out even a few thousands of an inch beyond the edge of the tape which, when the tape is wound on the reel, results in adhesion to the adjacent layer and often breaks the tape.

The Gibson-Girl splicer has a track and clamps for fastening the two ends of tape in place. When they are properly positioned, they are cut with a diagonal slash. A piece of splicing tape can now be applied across the cut and another made—the Gibson-Girl cut which scallops out two shallow arcs on each side of the tape to make sure there is no overlap whatever. If the proper tape is used, there is practically no risk of adhesions. For that matter, even cellophane tape can be used in an emergency without undue risk. Those who want even more complete simplicity can get the deluxe model with a built-in tape dispenser so there is no need for separate cutting of bits of tape.

#### Two ribbon microphones

Microphones reasonably flat to 15,000 cycles or higher are scarce and expensive. Two imported ribbon mikes which claim a response within 2 db to 15,000 and indeed a relatively shallow slope to 20,000 cycles are now available. One is the B & O, made in Denmark; the other the Reslo, made in Britain. Aside from their specifications, which are apparently accurate, the remarkable thing about them is the price of under \$50, less than half the cost of previously available mikes with this response.

The B & O (see photo) is available only in the low (50-ohm) impedance and therefore requires an additional transformer to match the high-impedance mike input of semipro tape recorders. It has a switch which provides two characteristics—one for remotely (6 feet or more) miked music, the other for close talking. The pickup pattern is the normal figure-8 bidirectional one of velocity mikes but the nulls are not

as broad as is usual. Thus, no special placement is necessary to obtain good sound. Yet there is enough control to provide, in skilled hands, correction for some of the acoustic conditions one is likely to meet in portable or studio recording. The sensitivity is surprisingly high for a ribbon mike and no preamp should be necessary with any of the standard semipro recorders. It is very compact—about the same as the “slim type” dynamics—and it comes with a fine ball and socket mount which permits easy angle adjustment. The protection against blasting is unusually fine, though the mike is not suitable for outdoor use.

The British Reslo, also a ribbon job, comes in several combinations of impedances. The Celeste can be used to match either a 30-50-ohm or a high-impedance input and has a switch for muting. The impedance is changed by plugging in different cables (both cables come with the mike) which has the advantage of maintaining proper balance and match. The Symphony is for either 250-ohm balanced or 600-ohm unbalanced input. The frequency response is similar to that of the B & O but the high-end response is sharper and more evident to the ear, although I did not notice any particular coloration.



The Reslo provides a very high degree of versatility in changing pickup patterns and response. The normal pattern is the figure-8 bidirectional. However, the back has a sloping response at high frequencies, being down 2 db at 1 kc and 20 db at 10 kc. This is valuable for live pickups of bands which can be arranged so the bass section is picked up by the rear of the mike while the other instruments are picked up by the front. It also produces interesting results with remote miking since the room reverberation tends to be held down at high frequencies. Each Reslo comes with felt pads and cloth reflector which can be inserted in the back of the mike to change characteristics to semicardoid or to cardoid for close-talking. In this respect it is one of the most versatile of all microphones. Incidentally, it can also be used outdoors with good results. The sensitivity is a little higher than that of the B & O and should be adequate to saturate a semipro tape recorder. END


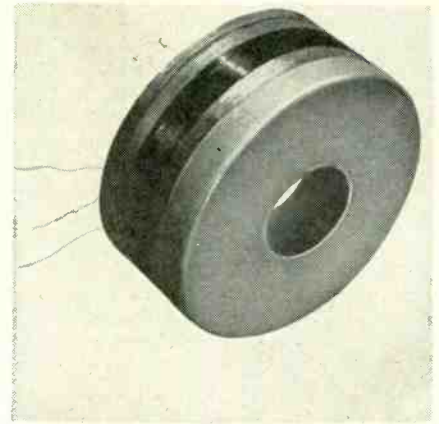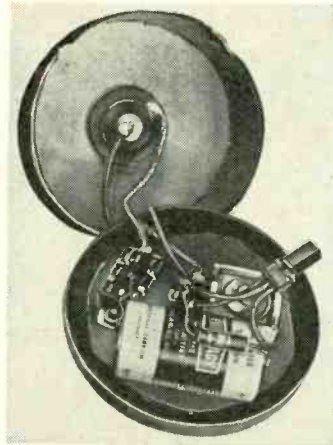
## AUDIO—HIGH FIDELITY



Extreme right—antenna coil wound around the case. Microphone is not as yet installed. Right—View of the completed microphone. Below—the microphone is put through its paces.



# TRANSISTORIZED WIRELESS MIKE

By ELLIOTT A. McCREADY

**A**BOUT the most widely available and certainly the least expensive transistor on the market today is Raytheon's CK722. Although designed primarily for audio and low radio-frequency applications, most of these units will oscillate at frequencies as high as 1 or 2 mc.

The wireless mike described here makes use of these attractive features of the CK722 and has proven a source of much enjoyment for my small daughter and her friends. Incidentally, this little gadget should make an excellent companion piece for the "Radio for Junior's Car" described in the December, 1954, issue of RADIO-ELECTRONICS.

A slightly modified Hartley oscillator (see diagram), modulated by an ordinary carbon telephone mike inserted in the collector lead of the transistor, puts out a respectable signal. The tap on L1 was experimentally placed for greatest output. Coil L1 is wound on the outside of the microphone case and serves as a loop antenna. The position of the tap on L1 has me puzzled. Theoretically, it should be closer to the base end of the coil to maintain the proper input-output impedance ratio for the CK722. But in this position the circuit won't oscillate at all.

With the L-C ratio shown, the oscil-

lator will tune from about 500-800 kc, a fairly blank spot in my part of the country. Reducing the size of C1 will, of course, raise this frequency range. The unit should be operated at as low a frequency as possible, however, to insure strong oscillation of the CK722.

### Construction

The unit is entirely self-contained and housed in a 1½-inch slice from the bottom of a 3¼-inch cardboard Morton salt container. Coil L1 is close-wound on the outside of the salt box with 36 turns of No. 30 enameled wire, tapped at 9 turns. After winding L1, give the entire outside of the carton a coat of service cement and allow it to dry thoroughly. Cut a 1-inch hole in the bottom of the salt box and insert an ordinary carbon telephone mike. A little service cement under the edge of the mike holds it in place.

The other components of the wireless mike are mounted on the cardboard re-enforced lid from a similar salt carton. The hearing-aid battery is held in place with a spot of service cement.

When all the components are mounted, proceed with the wiring, which is strictly noncritical. The CK722 can be soldered directly into the circuit or a Cinch five-prong hearing-aid socket can be used. I prefer the socket as the transistor is easily damaged by heat from the soldering iron. If a socket is

used, remove both of its alternate pins.

When the unit is completely wired, put the lid in place and glue on the base, being careful not to glue the lid to the salt box in the process. A coat of flat blackboard enamel completes the project. I used a cardboard base but a sturdier unit could be made of wood or sheet metal.

### Operation

When the paint is thoroughly dry, turn the unit on and place it near an operating receiver tuned to a blank spot within the operating range of the wireless mike. Adjust C1 until a carrier is heard and the unit is ready for the kids to use.

As this gadget was designed as a toy, its 10-15-foot operating range was considered adequate for room-to-room use. In some cases, however, it may be desirable to increase this range. This can most easily be done by increasing the size of the container and thus increasing the size of the loop antenna. If this is done, L1 will have to be redesigned to cover the desired frequency range. Output of the oscillator can also be increased slightly by reducing the value of R1, which was selected to limit collector current to about 2 ma. (Be careful not to exceed the transistor current rating.) In any event battery life will shorten considerably and hence this maneuver is not recommended.

The new G-E 2N76 transistor, designed to operate at higher frequencies, would also probably increase oscillator output. As yet I haven't been able to get my hands on one of them, but it will undoubtedly be an interesting experiment when they become a little more widely available.

END


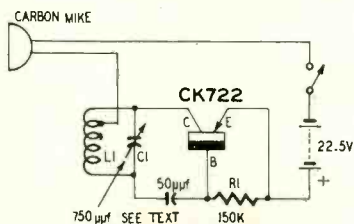


Diagram of transistorized wireless mike.
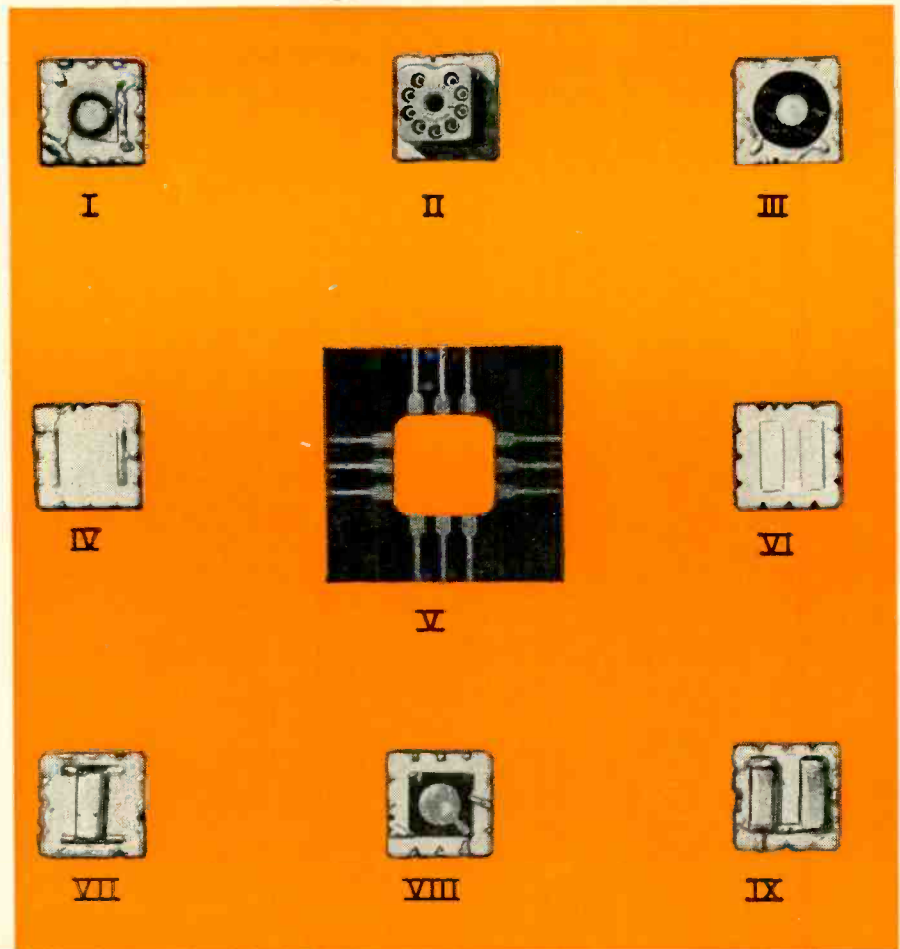
### Parts for wireless mike

1—150,000-ohm ½-watt resistor; 1—50-µF ceramic capacitor; 1—750-µF mica padder capacitor; 1—sps switch; 1—22.5-volt hearing-aid battery; 1—carbon telephone microphone; 1—CK722 transistor; 1—coil, 36 turns of No. 30 enameled wire on a 3¼-inch form, tapped at 9 turns (see text); 1—chassis (see text); 1—socket for CK722 (see text).

Typical module components: I—small inductor; II—tube socket; III—large inductor; IV—blank wafer with plated strip for attaching components; V—square hole in circuit board into which module is connected; VI—two adhesive resistors; VII—small plastic capacitor; VIII—ceramic capacitor; IX—two flat capacitors having one common terminal.



*A new type of electronic circuitry is on the way*

## NOW—A MODULAR TV RECEIVER

By FRED SHUNAMAN

MANAGING EDITOR

TELEVISION engineers—and radio engineers before them—have continually been on the search for more economical and simpler methods of wiring components into receivers. This search for economy and simplicity has taken two main paths: one in the direction of easier wiring methods; the other toward packaged circuitry. The first probably began when Western Electric started using harnesses and has now been pretty well solved with printed circuitry. Printed circuits (and even some earlier wiring methods) often include some components in the circuitry itself.

One of the earliest of these combination systems, in which flat conductors also acted as capacitor plates, was described in a patent issued to Flewelling in the mid-Thirties and later assigned to RCA. The Sargrove receiver, made in Britain in 1947, printed capacitors, resistors and conductors on the chassis by a fully automatic method ("Robot Makes Radios," RADIO-CRAFT,

September, 1947). The Compo radio, described in this magazine in December, 1947, combined components and wiring into cylinders resembling shield cans, which were plugged into sockets on the chassis. This was not so much an attempt at wiring simplification as to make servicing easier by simply replacing units containing a defective component.

Other types of packaging and unitization have been proposed and a few actually manufactured. Of them all, only etched ("printed") circuitry has survived and prevailed. It has also been combined with printed or appliqued resistors and capacitors which form part of the circuitry.

Yet printed circuits have their drawbacks. One of these is the crossover. Old-fashioned wiring is three-dimensional, and crossovers can be made very easily. Printed wiring is two-dimensional, and all conductors are directly in contact with the chassis or circuit board. To cross over, one of the "wires"


must be run through the circuit board, past the crossing conductor on the other side, and back again. This is often taken care of by running one lead on each side of the board. But in some cases actual hairpin tunnels through the board have been made to get past a crossing conductor.

Etched or printed circuits are not any easier to service than the conventional sort. Capacitors and resistors are often special printed-circuit types, and when they have to be replaced the job of removal and resoldering takes more time and care than with wired-in components.

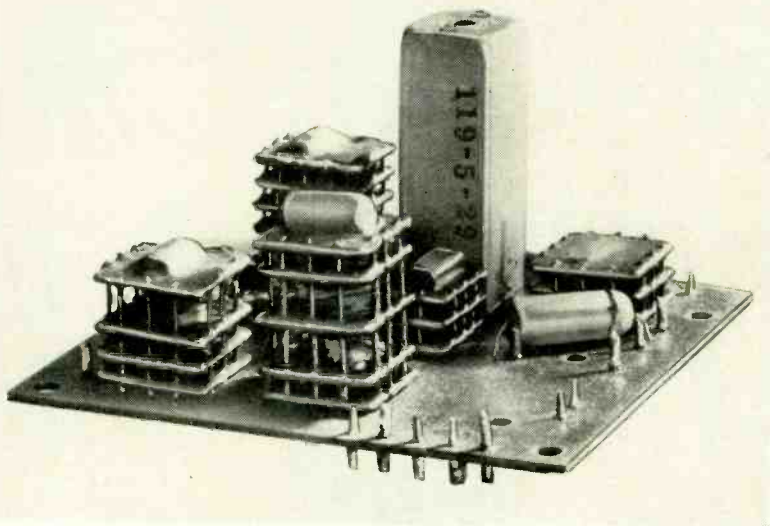
### A different approach

The modular concept combines some of the best features of printed wiring techniques with the idea of combining groups of components into a single package which can be replaced as a unit. The package typically contains the components associated with a single- or double-section tube, though it





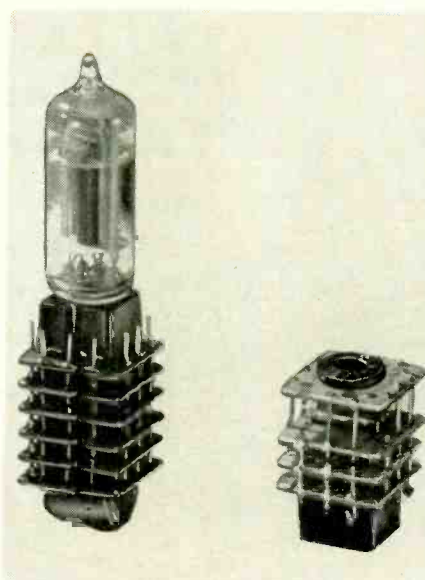A circuit board in the modular TV receiver. Note the variation in modules.



Complete modules—unit at left contains socket for miniature tube.

may contain less than one stage or more than two, and of course does not necessarily contain a tube. The tube is mounted in a socket that forms the module's top section. The rest of the unit is a series of ceramic plates or wafers, commonly about  $\frac{7}{8}$  inch square, spaced  $\frac{3}{16}$  inch apart.<sup>1</sup> The wafers are held together by 12 wire risers—3 on each side—which also serve as connectors. Each wafer may carry from 1 to 4 capacitors or resistors or an inductor or some other circuit component.

The module is inserted into a square hole in the circuit board, connecting to 12 printed leads which radiate from the 4 sides of the hole. Each module is therefore an independent package which may be conveniently replaced in minutes.

The module's greatest advantage is its adaptability to mass production. Components are applied and wafers assembled by automatic machinery. A second advantage is that it solves the crossover problem. If a lead is attached to a given riser, another lead that would cross it in printed circuitry can if expedient be attached to another riser. Then the wafer immediately above or below may possibly contain nothing but the crossing conductor. The module puts the third dimension back into wiring while retaining the advantages of printed circuitry. By adding depth, it makes great compactness possible. In some cases all the parts for two stages are contained in a module  $\frac{7}{8}$  inch square and not even an inch high.

### The components

Obviously, components of special

<sup>1</sup> These specifications describe the ACF modules, made by ACF Electronics, Alexandria, Va. They appear in the photographs and are used in the new Emerson TV receiver which forms the subject of our cover and this article.

form are needed for such compactness. The resistors are a type developed by the Bureau of Standards. They are processed in the form of adhesive tape and can be used singly or in parallel to dissipate from  $\frac{1}{2}$  to 2 watts. Capacitors are ceramic types similar to those used in ordinary printed circuitry or—for the larger sizes—special rolled plastic units. The ceramics go down to 10  $\mu\text{f}$  and the plastic types up to 0.5  $\mu\text{f}$ .

Inductors may be small, simple windings or larger flat universal-wound coils running up to 10 mh. Larger coils and capacitors are positioned on the chassis, external to the modules. This is seldom necessary in actual practice. The various types of components that can be wafer-mounted are shown in the photograph.

Since a tube is usually part of the unit, each module is likely to carry the circuitry of one or two stages, depending on whether it carries a single- or double-section tube. The double triode of Fig. 1, for example, acts as sync phase inverter and vertical oscillator.

The seven resistors and the four capacitors which comprise the circuitry are distributed among four wafers of a six-wafer module. The large number of wafers and risers reduce crowding to the vanishing point and the vertical construction permits greater compactness than has heretofore been achieved.

The Emerson 120306 chassis TV receiver pictured on the cover uses 13 modules. Tuner and power supply are conventional. It was also found convenient to mount tubes closely associated with transformers, such as if amplifiers, separately though parts of their circuitry may be module-mounted. Other tubes and most of the other components are mounted in modules. (Incidentally, Emerson has simultaneously

engineered this model for manufacture in printed-circuit form using conventional individual component parts, thus permitting comparisons as to cost, adaptability to servicing and other features.) The complete schematic of the receiver is on pages 46-47. (Its rather unfamiliar appearance may be typical of TV receiver diagrams in the foreseeable future.)

### Servicing the modular set

The ideal and ultimate method of servicing a modular receiver is simply to locate the module in which the defect is lurking and replace it. If modular construction becomes universal, no doubt soldering guns with heads in the form of a hollow square to unsolder the 12 contacts simultaneously will form part of every technician's tool kit. Another tool will be a swage with which the 12 risers on the replacement module will be bent outward and clinched against the 12 contacts on the chassis board. The same square-headed soldering tool can then be used to solder the new module into place.

While modules are new, it may be found advisable to replace individual components. Indeed, it is by no means certain that it will not always be more practical to replace certain parts than to substitute a complete new module. Troubleshooting will not be as simple as with open wiring, because it is not always possible to see the connections of a component. But since they are connected to given risers—which are indicated on the schematic—they can be located readily. No voltage at the plate of the sync amplifier in Fig. 1, for example, would almost certainly indicate an open R47 or R46, if plate voltage was found on riser 6 (riser numbers are circled in the diagram). A voltage check from riser 6 to riser 10 would indicate which of the resistors



was open and a new resistor could be soldered to the two risers between which the defective one was connected.

An open capacitor could be handled like an open resistor. A shorted capacitor would give more trouble but could in many cases be removed from the circuit by snipping one of the risers to which it was connected. It is likely that the plans of each module, like Fig. 2, will eventually be included in service data so the problem of locating a shorted capacitor would be simplified.

It is likely that modules will give rise to their own conventions and traditions, which may make life easier for the repairman. In traditional circuitry he is greatly aided by customs and habits. The great majority of tubes, for instance, follow one of three or four patterns as to placement of grid, ground and cathode terminals. In spite of the numerous exceptions, this uniformity helps the service technician. There is no reason to suppose that it may not become traditional to look to one riser (or one of four risers) for ground, another for B plus, etc. However, no pointers in that direction have yet been observed, and designers will be quick to point out that such strait-jacketing would reduce wiring flexibility.

To the technician, the module offers promise of a receiver that can be

serviced quickly and efficiently in the home and that should yield service charges large enough—due to the re-

placement of the fairly consequential-looking modules—to pay adequately for the work. END

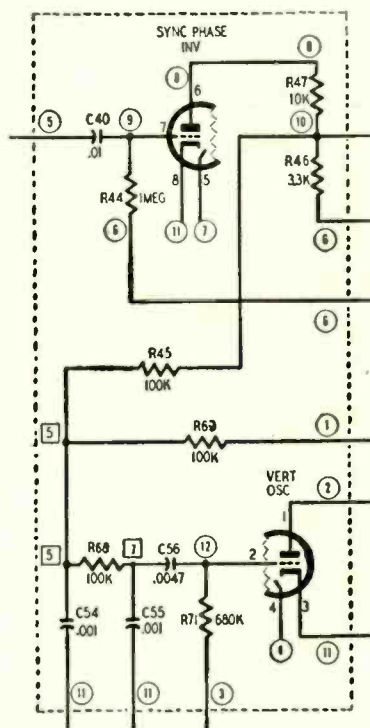


Fig. 1—Sync phase inverter and vertical oscillator as wired in a typical module.

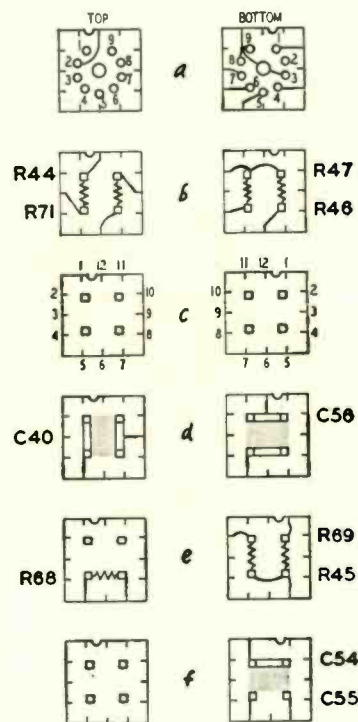


Fig. 2—How the Fig. 1 module is wired. Parts values are the same as in Fig. 1.

### Government TV-Set Certification Program

UNCLE SAM has set new and specific limits on permissible radiation from TV, FM and some communication receivers and has ordered receiver manufacturers to certify that their products meet these limits, beginning this spring. It has prescribed that "a distinctive seal or label" be affixed to each certified receiver for the protection of the customer.

While each manufacturer will design his own seal or label, they will all carry the same wording, approved by the Radio-Electronics-Television Manufacturers Association (although RETMA will not be identified with the certification program). The purpose of the label will be to indicate that the receiver doesn't generate radiations which can spoil neighbors' enjoyment of TV or interfere with communications services.

Use of the label will be required under the Federal Communications Commission's new receiver certification rule—the first Government attempt to regulate the manufacture of TV and FM receivers. The rule was prepared after 5 years of Government-industry conferences and has the approval of the vast majority of the receiver industry.

While the rule is aimed at manufacturers, the regulated party actually is the operator—the viewer or listener—since the FCC is permitted by law to regulate only users of communications equipment. The regulation stipulates

limits on the amount of radiation a receiver may legally transmit at various frequencies and provides for certification of each model or type of set offered for sale so the purchaser may know he will be complying with the FCC law when he operates the receiver.

The certification label is to be affixed to all sets which comply with the new FCC standards. It can be attached only to receiver models certified by the manufacturer or a private testing laboratory to meet the radiation specifications established by Government and industry engineers as being noninterfering.

It's estimated that 90% of television sets now being made comply with the radiation limits but the certification program is being relied upon to curb

those few manufacturers who have been putting out receivers which are also "transmitters."

The new regulations (see table) apply to all receivers which tune anywhere from 30-890 mc—and this includes not only TV and FM sets but many communications receivers.

The certification and labeling rules go into effect May 1 for vhf TV sets, FM sets and all other receivers, with these exceptions:

Uhf receivers are given later deadlines—new models put in production after Dec. 31, 1956, must comply with the rules. By July 1, 1957, all TV sets—uhf or vhf only—must meet the requirements and carry the seal. Pocket type superregenerative receivers used in one-way signaling service must be produced in conformance with the new radiation rules after the end of this year.

Some manufacturers haven't waited for the rules to go into effect, and are already telling prospective customers that their sets are noninterfering. One leading manufacturer attaches a tag to its new receivers stating that the television set "... has been carefully designed and heavily shielded to virtually eliminate oscillator radiation. This means that undesirable radiations from its circuits will not interfere with picture reception on your neighbors' TV sets. The elimination of excess radiation also results in a better picture for you."—David Lachenbruch

FCC RADIATION LIMITS	
Frequency of Radiation (mc)	Field Strength (μv/m)
0.45-25	See Note
Over 25-70	32
70-130	50
130-174	50-150*
174-260	150
260-470	150-500*
470-1000	500

\* Linear interpolation

NOTE: Pending the development of suitable techniques for measuring the actual radiation in this band, the interference capabilities of a receiver in this band will be determined by the measurement of rf voltage between each power line and ground at the power terminals of the receiver. The voltage so measured shall not exceed 100 μv at any frequency between 450 kc and 25 mc, inclusive.



# Troubleshooting AGC Circuits

By CYRUS GLICKSTEIN

Part II—Isolating agc defects; manufacturer's service notes

**A** LARGE group of agc troubles originates in the agc filter, the R-C network connected to the agc bus. Faulty agc filtering can cause buzz in the sound, hum pickup in the picture and unstable sync. Faulty filtering leaves in the agc voltage a ripple which is fed back to the controlled rf and if stages and modulates the incoming signal. Defective filtering is generally caused by an open capacitor in the agc filter, a capacitor or resistor which has changed value or incorrect values in the original filter-network design.

Another large group of agc symptoms arises from a complete or almost complete loss of agc voltage. This may be caused by a defect in the agc bus (shorted capacitor, open resistor, etc.), a failure in or loss of input to the agc stage. The loss of agc results in a confusing variety of symptoms. For example, it may cause either a very strong, contrasty video signal or exactly the opposite—a very weak video signal or possibly a blank screen.

The key to understanding the reasons for these symptoms is found not in the agc system but in the video detector-video amplifier circuitry found in many current models (Fig. 1). The video detector is direct-coupled to the video amplifier which in turn connects direct-

ly to the picture tube. The rectified video signal across the detector load is negative (Fig. 2).

When agc bias is lost, the controlled stages operate at maximum amplification. An unusually large detected video signal (Fig. 2-b) is developed across the diode load and applied to the video amplifier grid. Since this video signal is pulsating dc, it not only provides the signal input to the video amplifier but also biases the stage in accordance with signal amplitude.

Thus, a stronger than normal video signal may not only cause a contrasty picture but may drive the video amplifier to cutoff on the negative signal peaks. This in turn would cause sync pulse clipping and defective horizontal and vertical sync. An even stronger video signal may produce enough bias to shift the operating point of the video amplifier sufficiently to cause extremely low amplification. This produces weak video output and poor sync.

A very strong video signal may even drive the video amplifier stage to cutoff. This may also cause picture-tube cutoff since the higher video amplifier plate voltage is applied to the cathode, thereby increasing the bias on the picture tube. In this event, the picture tube may be cut off only when the set is tuned to an active channel. Sound

would come in at or above normal levels in split-sound sets. In intercarrier sets, sound would come through (though some buzz might be present) in sets with the sound takeoff point at the video detector. If the sound takeoff point is at the video amplifier plate, a signal strong enough to cut off the video amplifier results in no sound as well as a blank screen.

Varying the contrast control setting does very little to remedy an overload due to a loss of agc bias. The contrast control is generally in the video amplifier cathode circuit. Even with the control set for minimum bias, the abnormally large signal at the video amplifier grid would still overdrive it.

Most of these effects are also possible in models with two stages of video amplification. In these sets the video detector is still connected as shown in Fig. 1. There is usually R-C coupling between the two video amplifier stages and the plate of the second stage is connected to the grid of the picture tube to obtain the correct picture phase. The only effect not produced in such sets by a loss of agc would be picture-tube cutoff.

We have discussed symptoms caused by defects in the agc system proper. However, a substantial number of agc troubles can be caused by a defective component not actually a part of the agc network but merely connected to it. For example, a leaky coupling capacitor between the mixer plate and grid of the first if stage can place a small positive voltage on the agc bus, thereby producing the usual symptoms associated with the loss of agc bias.

The same effect on the agc bus can be caused by a gassy or partially shorted (high-resistance) rf or if tube, by a leaky coupling capacitor between the plate of an if stage and the grid of a following controlled if stage, by a leaky capacitor between plate and grid of the first stage in a cascade rf amplifier (C105, Fig. 3).

Excessive agc bias can be developed by a fault in the video amplifier stage in Fig. 4. The video amplifier is direct-coupled to the grid of the keyer tube. An open heater or low emission in the video amplifier causes a higher than normal plate voltage in the video amplifier stage. This higher plate voltage is also applied to the keyer tube grid which then conducts continuously. An excess agc bias, which may be sufficient to cut off the rf amplifier and other controlled stages, is developed. In sets with this kind of circuit there will be a loss of both video and sound.

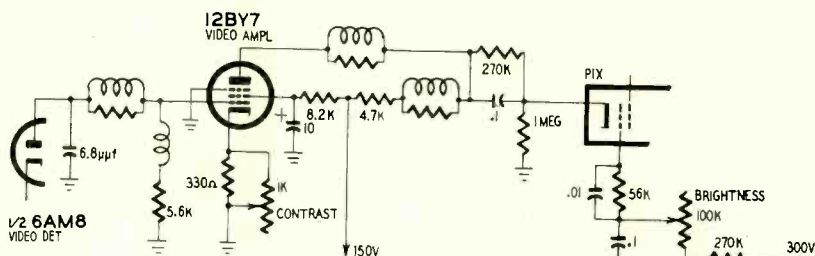


Fig. 1—Schematic diagram of direct-coupled video detector-video amplifier.

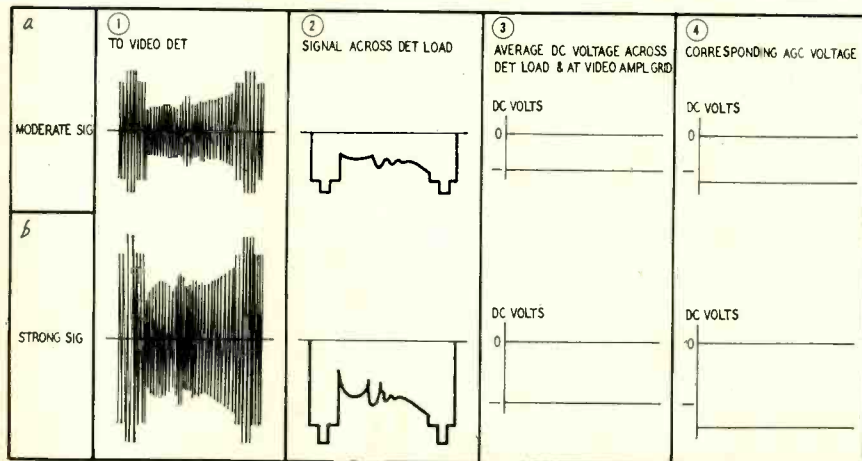


Fig. 2—Diagram shows various voltages related to agc circuitry.



As usual, the first step in troubleshooting is to check tubes. When symptoms point to video trouble, video and sound trouble or poor sync, change some or all of the following, depending on the symptoms: front end, video (common if), video detector, video amplifier, sync, horizontal afc and sweep oscillator tubes. In addition, the age tube(s) should be changed, including any tube used as an age clamping diode. This tube is easy to overlook since it usually is a diode section of the audio detector—first audio tube. Changes in tubes are usually made immediately after checking control settings (see step 1, below).

The following steps should be taken to determine whether the fault is in the age system:

1. Vary the contrast and, if present, the age and noise limiter controls. Incorrect setting of the age threshold control can cause bend, contrasty or weak picture, buzz in the sound or a complete loss of picture and sound. Vary the contrast control to determine if there is the normal range of control. Resetting these controls may clear up the trouble. If not, rotating each control on either side of the setting usually indicates whether they are operating normally.

2. The most important quick check is to measure the negative (dc) voltage across the video detector load resistor and then from the age bus to ground with an active channel tuned in. The voltages should be approximately equal (Fig. 2). (They may vary somewhat depending on the type of age system).

If little or no age voltage can be measured while several volts appear across the diode load, this indicates a loss of age and further checks should be made in the age system for shorts or an open age bus, a defect in the age diode or gated age stage or loss of signal input to the age system. If the age bus has a positive voltage, checks should be made for a faulty component which may be connected to the age line. A defective clamping diode or threshold-control voltage-divider may also be responsible.

If the negative age voltage is considerably higher than the voltage across the detector load, this indicates a continuously conducting keyer tube so check this stage and the video amplifier connected to it.

3. If age voltage is normal and the symptoms indicate the possibility of hum pickup in the age bus or defective filtering, bridge the age line with a 0.1- $\mu$ f capacitor and note the effect on the output. Because of the susceptibility of the age bus to hum pickup, the capacitor should be tacked in rather than held when making the test. If some improvement is noted, the various capacitors in the age filter should be bridged with units of equal value to determine which one of them may be defective.

4. If the above checks have no effect,

make the usual checks for trouble in other circuits which can cause similar symptoms.

Once trouble is localized to the age system, voltage and resistance checks around the age tube(s) and bus will usually uncover the defective part.

Signal tracing with an oscilloscope is an additional method for localizing video—sync—age troubles. Peak-to-peak voltage and waveform checks should be made at the diode load resistor, video amplifier grid and plate, picture-tube input and the keyed age tube grid and plate. A loss of signal or a noticeably incorrect signal as compared to the manufacturer's specifications indicates trouble at or immediately preceding the point under observation. The scope quickly reveals hum or ripple on the age line.

### Troubleshooting notes

A good deal of helpful information has been compiled by manufacturers on the basis of field service reports. In addition, various manufacturers have recommended field modifications to improve age operation. Some typical reports and recommended modifications are listed below for reference since they are useful in indicating possible faults in most other models.

#### 1. Sync instability

a. *Horizontal instability (jitter).* May be caused by a partially filtered horizontal signal fed to the grids of the first two if stages with the age voltage. This signal, which has shifted in phase with respect to the horizontal oscillator, modulates the video signal and causes horizontal instability when fed back to the sync circuits. Correct this by adding additional age decoupling capacitance.

b. *Tearing at top of pix.* Insufficient age. Check control setting.

c. *Distortion or pix tearing in strong signal areas; erratic horizontal hold.* Remove the resistor from the age bus to ground. This provides higher age voltage for pix if tubes. Weak or gassy if tubes will cause similar trouble.

d. *Loss of horizontal sync.* Open in age pulse coil (connected across a section of the flyback transformer). Disconnect one side of this coil from flyback transformer before checking continuity.

e. *Horizontal pulling or jittering.* Horizontal wavering regardless of the contrast control settings can be corrected in most cases by inserting a 0.47- $\mu$ f capacitor across the filter capacitor that bypasses the age line to ground. The electrolytic capacitor does not have adequate high-frequency bypassing action, which is provided by the 0.47- $\mu$ f unit. The pulling effect is more pronounced with strong signal reception and in many cases might be mistaken for overload. However, addition of the 0.47- $\mu$ f capacitor corrects the condition.

f. *Picture pulling.* Caused by either hum pickup in the age bus or from a

leaky age tube. If replacing the tube does not cure the trouble, place a 0.5- $\mu$ f paper capacitor from the age bus to chassis.

#### 2. Video defects

a. *Weak pix, very snowy; weak sound.* Defective age clamp. If this tube is nonconducting, the effect may not be immediately apparent but may cause the rf amplifier or mixer to become defective.

b. *Overloading with normal contrast—near station.* Insufficient age voltage is overdriving receiver. Check setting of age control.

c. *Pix overloads on strong signal.* If pix is unstable and age control has little effect, test capacitor in the age filter network. It may be leaky.

#### 3. Miscellaneous troubles

a. *Raster, no sound, no pix.* Trouble was found to be an open heater in the first video amplifier (one section of tube). Failure of this section of the tube causes the bias on the age line to cut off the common audio—video if amplifier stages, killing the sound as well as the picture although this is a split-sound receiver.

b. *Age drift (change in sensitivity as set is operating).* Defective age amplifier. When this tube is replaced, the age control setting should be re-adjusted.

c. *Age control adjustment.* In medium- and strong-signal areas the age threshold control adjustment should be made on the strongest signal to avoid receiver overload. In weak-signal areas the adjustment which gives the best signal-to-noise ratio (minimum snow) may be preferred. The position of the fine-tuning control is important. It should be set so the pix carrier is well up the if slope when making final adjustment of the age control. END

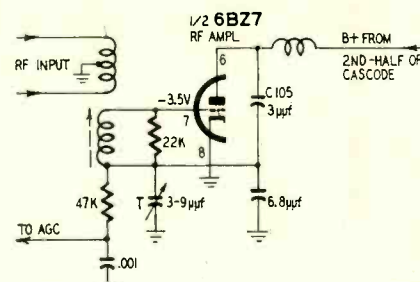


Fig. 3—Du Mont RA-312 rf input.

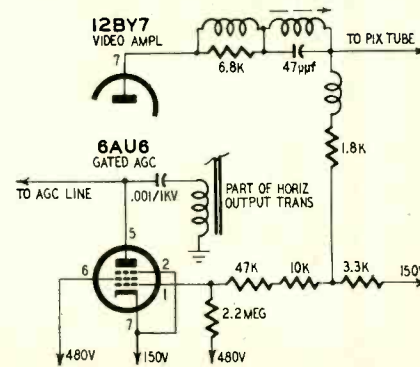


Fig. 4—Sparton 23U214 gated age.



# SERVICING INTERCARRIER BU-Z-Z-Z-Z

By JAMES A. McROBERTS

*Servicing procedures  
for locating  
trouble sources*

**T**ELEVISION sound and picture carriers are transmitted separately, independent except for a frequency interlock holding them 4.5 mc apart. The receiver's local oscillator heterodynes with the two carriers and produces two intermediate frequencies each containing its original modulation. Fig. 1 shows a block diagram of the signal paths.

The if amplifier delivers these two carriers to the video detector. The picture signal is sent through the video amplifier to the picture tube and we lose interest in it, as far as this article is concerned.

A new frequency is produced in the video detector as the result of mixing the sound and picture carriers—this is the 4.5-mc intercarrier signal, or the sound if as it is often called.

If the picture amplitude is about five times that of the sound, the picture carrier will act almost like a local oscillator. There will be some amplitude modulation in the 4.5-mc signal but very little in comparison with the frequency modulation which is retained in its entirety.

The 4.5-mc if may be taken directly off the pix detector, or at the output of the video amplifier, and amplified in one or more 4.5-mc if stages. An FM detector—almost universally a ratio detector—removes amplitude variations and demodulates the signal which is then fed to an audio amplifier. This completes the sound signal path.

Keep in mind that the picture if acts as a local oscillator at the pix if de-

detector. It must be present or there cannot be a 4.5-mc carrier!

### Overloading

If a tube is driven to cutoff by an excessively large negative voltage—its plate current does not change so long as it remains at cutoff. Or if a tube is driven to saturation as by a high positive signal on its grid, the plate current does not vary while the tube is in saturation.

Thus, if a sync pulse drives any tube into either saturation or cutoff, it cannot transmit the variations of either the picture or the sound carrier during the time it remains in that condition. Hence the 4.5-mc carrier will vanish and so will the sound! Although the horizontal pulses may produce such overloading if their amplitude is excessive, they are relatively inaudible. The vertical pulse group is audible since it has a 60-cycle repetition rate. If the sound is cut off 60 times a second, intercarrier buzz is produced due to carrier interruption rather than amplitude modulation. The picture is relatively unaffected since the blanking pulse cuts off the picture tube and no video information is being transmitted.

The cure is to remove the overload. The most frequent troublemakers are the last pix if stages; they may have their B plus feed from higher voltages to permit handling larger signals. In sets—the economical ones—where the sound takeoff is from the video amplifier output, the video amplifier is generally the offender. It must pass the

4.5-mc intercarrier variations which it cannot do if cutoff or saturated. Here, too, the remedy is to remove the overload. (Some overloading may occur due to overmodulation of the station.)

In sets using the video amplifier as a 4.5-mc amplifier, varying the contrast control will indicate the trouble. Applying a higher negative voltage from a bias box on the agc bus will lower the gain and cut out the overload on the last picture if stages, localizing the trouble.

### Excessive amplitude modulation

Another cause of intercarrier buzz is excessive amplitude modulation of the 4.5-mc intercarrier signal by the picture-carrier modulation. At a ratio of about 1 to 5 (sound to picture) practically no amplitude modulation exists in the 4.5-mc carrier but this is not true for lower ratios. The amplitude-limiting device—the ratio detector circuit or a separate limiter in the few discriminator sets—cannot handle excessive amplitude modulation. The vertical pulse group becomes audible as a result (note this in varying the fine tuning control on most sets).

Intercarrier sets have an if response approximately like that shown in Fig. 2. The sound carrier is at 10% of maximum and the pix carrier at 50%, resulting in the 1-to-5 ratio. Lowering the picture carrier to 20% will definitely result in intercarrier buzz. Fig. 2 is the output of the video if amplifier. Make a sweep alignment check or test with a signal generator and a voltmeter across the pix-detector load. Preferably feed a signal into the antenna input at both carrier frequencies to overly strong response of either carrier. The ratio must be about 1 to 5 at the detector!

Closely allied with the above is failure of the amplitude limiter in the sound system. This is simply an electrolytic capacitor in the typical ratio detector as shown in Fig. 3. The test is simple. Shunt the capacitor with another as in ordinary power-supply tests except that the value should be the same as that required for the set.

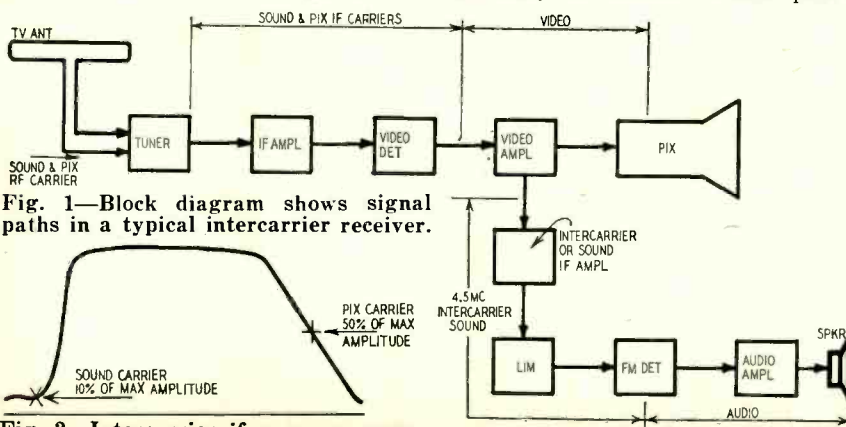


Fig. 1—Block diagram shows signal paths in a typical intercarrier receiver.

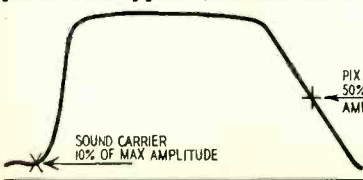


Fig. 2—Intercarrier if response curve.

A useful test is the sound agc voltage developed at the negative terminal of the ratio detector electrolytic capacitor whether actually used to control the sound if tubes or not. (See Fig. 3.) Use a high-resistance (20,000–100,000-ohms-per-volt) voltmeter or a vtvm between its negative terminal and ground.

Increasing the sound (4.5-mc) if

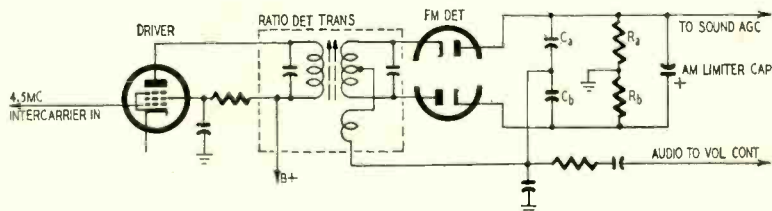


Fig. 3—A typical ratio detector. The sound agc is an important test point.

amplitude by increasing the contrast control should result in an increase in this agc voltage as should a stronger station signal. Any decrease taking place under such circumstances means that something is wrong with the signal paths. The contrast control will tell if the trouble is in the video amplifier or thereafter for such takeoffs of this type. Otherwise, the trouble is in the circuits ahead of the video detector, such as improper alignment, etc.

#### Sound alignment

Sound alignment requires centering the sound if stages on 4.5 mc so that even amounts of any residual amplitude modulation will be applied equally to the ratio detector and cancel out in it. Although instrument alignment is preferred, screwdriver alignment is most practical. Make a mark on the chassis with a pencil and count any half-turns made so that the adjustment can be turned back. Particularly important is the secondary of the ratio detector transformer. Do not neglect the sound take-off trap or other 4.5-mc alignment adjustments.

The balance of the ratio detector may be upset by variation in its components, particularly the load capacitors and resistors. The dual-diode tube should be substituted early in the testing procedure.

#### Test sequence

A logical sequence of testing is necessary to localize intercarrier buzz. A

suggested procedure follows:

1. Substitute tubes in sound if section, particularly the FM detector tube.
2. Balance secondary of FM detector transformer for minimum buzz.
3. Touch up remainder of 4.5-mc adjustments.
4. Shunt amplitude-limiting capacitor.

5. Make the bias box test on main agc and the test on the sound agc as described previously.
6. Inspect alignment by sweep or signal generator-voltmeter method.
7. Check ratio detector load components.


If the contrast control reduces the buzz rather sharply at some setting, look for overloading immediately.

If the fine tuning reduces the buzz, but cannot reach a good minimum on some station, the local oscillator slug needs adjustment or the strips of the turret may have to be replaced. In line type tuners, the rf and oscillator adjustments may be faulty so attention is immediately directed to them.

Worthy of mention are relatively obscure causes of intercarrier buzz.

Nonlinear action in any part of the receiver that acts as an amplifier in the signal path of the two independent carriers may result in a spurious modulation producing excessive buzz. Particularly offensive in a few localities is the cross-modulation of the FM carrier in the mixer stage. A strong local signal is the offender. The remedy is attenuation of that signal, even though it is the desired station, by wavetraps in the transmission line.

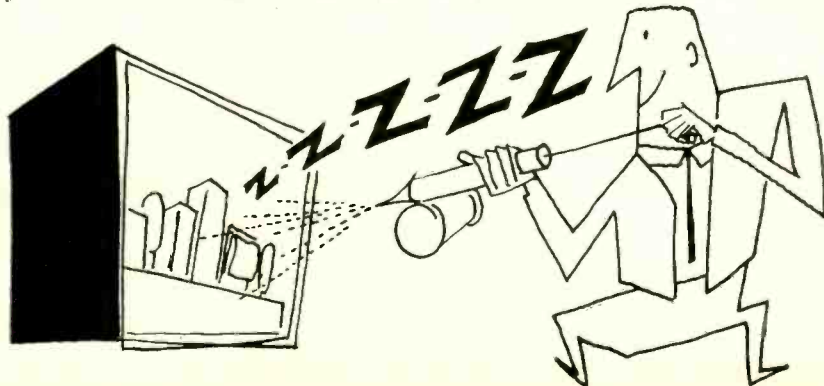Ghosts with their vertical buzz pulse groups can cause similar trouble which will also be evident as a false picture or ghost on the picture-tube screen. The problem is getting rid of the ghost in this case. Traps, antenna orientation, etc., are the methods. END



## DRAMATIC HIGH-VOLTAGE DEMONSTRATOR

By L. H. WILSON

**M**OST television technicians know that their repair work would be much easier if TV owners and their well-meaning but untrained friends would leave the set alone after a defect has occurred. Of course, there is nothing greatly wrong with a set owner applying a little first-aid to a set if he goes only as far as he really knows what he is doing. But 99% of TV owners are out of their class and just asking for more trouble once they take the back panel off. Besides the hazard to themselves they can make a really tough repair job out of a simple one. And the average technician cannot make money on the tough ones.

Thus, the technician should educate his customers to leave the set alone when it breaks down and to call him immediately. This is not an easy job, particularly with all the "Save Money—Fix Your Own TV" books on the newsstands these days, but it is worth a try. Many service organizations and set manufacturers have spent much time and money in an attempt to educate set owners against the advisability of tinkering. However it is no easy task stopping the home tinkerer.


I have found the best way to impress a customer with the fact that he would be foolish to tinker with his set is to demonstrate the high voltage and let him see for himself the hazard that he might be exposed to.

The most dramatic way to do this is to hold the base of an incandescent lamp bulb near the cap of the high-voltage rectifier tube. Since an incandescent lamp is not a vacuum tube, but contains an inert gas at just a little below atmospheric pressure, a brilliant display of lightning-like sparks can be obtained inside the bulb as the gas ionizes and lights up by capacitive coupling through your body to ground. A 200-watt clear glass bulb makes the most effective display, giving 2- or 3-inch purple sparks which crackle to each of your fingertips as you hold the glass bulb.

This trick has never failed to impress my customers, and once they see this demonstration we do not have much "people trouble" any more. There is no hazard to yourself in making this demonstration, and you cannot even feel it. But a little facial grimacing while the sparks are licking your fingertips might leave the impression that you are supernaturally qualified for such hazardous work. At the very least, this demonstration has an advertising value that will help the customer remember you the next time the set needs a repair.

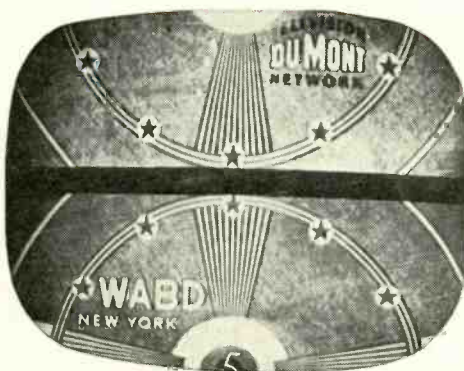(But don't do it if junior is present; he might get ideas.—Editor) END





The vertical blanking bar as it appears between frames of a TV picture.

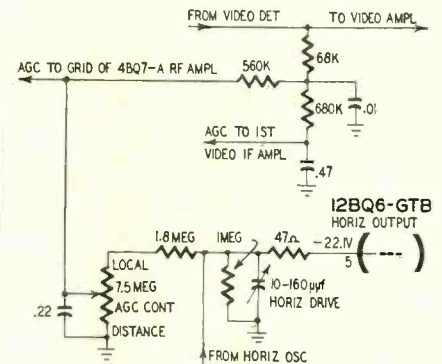


Fig. 1.—The agc divider circuit in some versions of RCA KCS95 chassis.

BY observing the sound and picture of a television receiver as its many controls are varied, the service technician can obtain a pattern or profile of a defect that will pinpoint the trouble to a particular stage and sometimes even to a particular component. A TV set is composed of many interdependent circuits—low- and high-voltage power supplies, keyed age, etc. Thus, some knob-twisting and straight thinking will usually dovetail the individual symptoms and produce a dependable generalization even before the back cover is removed. At the very least, much wasted servicing time will be eliminated.

Knob turning is of little value if it is practiced on defective sets only. The technician must get the "feel" of the controls on properly operating sets of different makes and models. This is especially true of the independent technician who may be called upon to repair any set from an Admiral to a Zenith.

Almost regardless of the defect, the channel selector provides the first significant clue. Observe the picture and sound as you turn to inactive and both weak and strong active channels. On each channel, vary the fine-tuning control through its entire range, generally about a 2-mc oscillator variation. The various channels will help isolate interference and intermittent effects, smearing, sync instability due to signal overload or insufficient signal strength, age action, sound bars in the picture, raster troubles, hum, buzz and many other effects. In conjunction with these controls, the oscillator slug of an individual channel can be varied where a defect appears due to improper oscillator adjustment on that channel.

Thus, the channel selector and fine tuning offer an important clue—not necessarily as to what is wrong but as to what is not wrong. Circuits as remote from the front end as the high-voltage power supply have been affected by signal strength (through the effect of sync amplitude on the horizontal afc and oscillator circuits).

The picture or contrast control is probably the next most important one on the front panel. Here, knowledge of

where it is located in the set is important. It is commonly found in the cathode circuit of the video amplifier, with some sets having it in the video amplifier plate circuit. Older receivers made great use of the contrast control in age circuitry. The location of this control is important in terms of the takeoff points for the intercarrier sound and the sync signals. Varying the contrast control should produce a wide range in shading between the blacks and whites in the picture.

Generally fed from the video amplifier output, the sync pulses pass through the sync circuits and control the timing of the horizontal and vertical sweep circuits. Here two other front-panel controls come into play. Normally, slightly varying the vertical hold control should not cause loss of vertical sync. When the vertical hold is critical or unstable, roll the picture and hold it so you can study the vertical blanking bar (see photo). This is the blacker-than-black region and it should appear as such; observe the strength of the vertical sync and equalizing pulses. Vary the contrast control and observe the change in sync strength. Letting this bar roll also gives a quick check of vertical linearity.

The effect of varying the horizontal hold control will differ greatly with the type of horizontal afc circuit used. However, in normal operation the pull-in and hold-in effects should be strong.

Thus, for example, where the contrast is normal and vertical and horizontal sync poor, the suspected area falls between the sync takeoff and the input to the sweep circuits. Also, where horizontal hold is poor and vertical hold good, the technician may initially assume the sync circuits are operating properly.

The brightness control varies the dc bias on the picture tube from cutoff to maximum brightness (often producing blooming). Observe its effect on sync stability and picture contrast. Experience with the contrast and brightness controls will often permit the technician to appraise the condition of a picture tube.

One other important front-panel control is that of volume (and sometimes tone). Since this controls the amplitude of the audio output, varying it offers a clue in cases of audio coupling to the video circuit. Sound bars often develop at high volume levels. Also, in a no-picture no-sound condition, the technician can often detect a difference in the sound of hiss produced by trouble in the tuner or in the if amplifier.

On the rear apron of a TV set the number and type of controls vary considerably. Observe which portion of the picture is affected by the height and vertical linearity controls and to what extent. Certain particular components will be found to exert a great influence over picture height and linearity.

Check the width control, especially in cases of insufficient high voltage. It appears in several forms, most popular being a variable inductive load on the flyback transformer or a variable screen-grid resistor for the horizontal output tube. A defective width coil not only causes horizontal trouble but could affect any stage fed from the boost circuit. In many cases a defective width coil can load down the low-voltage power supply, producing many strange symptoms. Varying it often brings out an intermittent condition that might otherwise be overlooked.

In the same general circuit is the horizontal linearity control. Check this out where it produces no noticeable effect.

The horizontal drive control should be checked wherever ringing or drive lines appear and in cases of insufficient high voltage. It could affect width, keyed age action and circuits fed with bootstrap voltage.

Many sets have noise controls. For example, the Capehart CX-43 has a noise-rejection control in the cathode circuit of the 3BN6 sound detector (some manufacturers call this the AM rejection or the buzz control). In many sets the sensitive sync circuits are protected by noise-rejection networks; recent Admiral sets have a noise gate control in the 6CS6 sync separator circuit. Thus, where there appears insufficient AM limiting or general sync



instability, study the effect of the noise-rejection controls.

One last common control is the agc potentiometer (Fig. 1) or local-distance switch. This control determines the amount of agc applied to rf and if circuits and affects the gain of the receiver. It has an important effect in very weak and very strong signal areas.

Thus, we see, although somewhat superficially, how the various circuits "lean" on each other. The technician who varies the many controls and applies logical thought to the effect each produces will be considerably informed before even a single component is tested or measurement made.

**Picture overload**

*A DuMont RA-164 came in with a complaint of insufficient brightness. It turned out that the picture appeared dark as a result of picture overload caused by improper agc action. Varying the agc potentiometer had little or no effect on the picture. I checked the alignment of the receiver and, except for certain settings of the agc control, the response was fine. At these settings the response seemed to peak. A check at the agc test point showed less than 1 volt, indicating that the trouble is picture overload.*

*The only other symptoms are poor horizontal lock-in and critical horizontal sync. A thorough check of the set indicates everything is in order except for the agc.—I. S., Chicago, Ill.*

Your symptoms leave little doubt that insufficient agc action is the cause of the trouble. The peaking you observed during alignment was most likely the result of regeneration in the if's caused by the large-amplitude signal. The poor sync stability is most likely the result of sync compression.

Fig. 2 shows the agc amplifier circuit and the normal dc pin voltages. You state that you measured less than 1 volt at the agc test point. For a moderately strong signal, you should measure about -6 volts or so. If replacing the 6AU6 does not help, replace C212, a 1- $\mu$ f capacitor with a notorious reputation for becoming defective. Closely allied with this unit is C215, a .001- $\mu$ f 2-kv capacitor that also opens far more than might be expected. One other good possibility is C296, a 4- $\mu$ f 200-volt cathode bypass capacitor. However, this capacitor opening produces cathode degeneration which brings on sync instability rather than picture overload. But as so often, happens, two or more of these components might be defective. Thus, check the above components and dc voltages.

**Installing uhf strip**

*I recently was called on to install uhf strips in an Emerson model 1106D. This is ordinarily a simple job, but I have been unable to get anything but the faintest of pictures and a great deal of snow. I used R type uhf strips recommended by a local distributor and*

*now wonder if perhaps some other type might perform better.*

*I have other technicians in on this but no one has improved the picture. My uhf antenna installation is known to be good. Some attempts have been made to measure voltages and check signals in the uhf strips but my test equipment could not cope with it.—M. P., Lexington, Ky.*

There is nothing wrong with using R-type uhf strips. They operate by double conversion in which the incoming signal beats with a chosen harmonic of the vhf oscillator and converts it to a vhf signal.

Make sure the oscillator slug and spring are properly positioned. Check to see that the male contact pin is not bent. Look for a corroded ground strap or drum detent disc and make a mechanical check for shorted leads, open connections and cold solder joints. If possible, try using one or more additional crystals, keeping the exact dress.

The trouble is often due to misalignment. Alignment can be done with the aid of a station signal. Remove about three sets of strips directly opposite the uhf strips. After the set is warmed up, adjust the oscillator slug for best picture and sound. Then, using a nonmetallic tool, adjust the uhf preselectors, through the opening made by removing the strips. Adjust the antenna input and uhf preselector for maximum contrast. During these adjustments use very loose antenna coupling. Then adjust the harmonic selector and if coil for minimum snow.

Adjusting the harmonic selector is very critical, so tune slowly. The if transformer tunes rather broad. When adjusting the above slugs, work carefully. Turning them out too far will permit the slug tension spring to snap out and it is difficult to reposition it.

**High-voltage failure**

*I have a peculiar trouble in a Philco model 50-T1600. There is no high voltage but every component in the high-voltage circuit checks good. With -18 volts on the grids of the horizontal output tubes, the drive is sufficient.*

*When the set came in, R104, a 4,700-ohm 1-watt resistor in the cathode circuit of the damper (Fig. 3), was burned out. I replaced this resistor but it immediately began to smoke. I don't want to replace it with a higher-wattage unit because I have seen it operate in other sets. The 5V4-G damper is running very hot. I have checked the damper circuit components but all check out good. I am passing this along for any suggestions you might have.—W. S., Portland, Ore.*

The key to this problem is the overheating of the 4,700-ohm resistor. In almost every case where there is no high voltage and this resistor overheats, replace C86, a 40- $\mu$ f capacitor connected to one side of the filter choke in the low-voltage power supply. This capacitor provides a bypass to ground for signals in the damper circuit. When

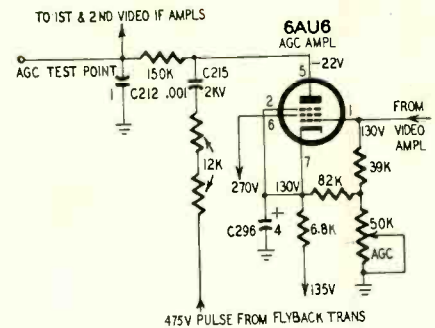


Fig. 2—Du Mont RA-164 agc amplifier.

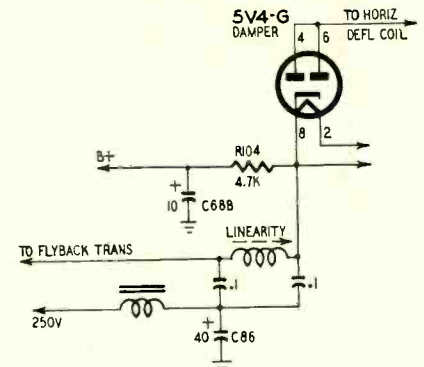


Fig. 3—Horizontal linearity and low-voltage filter circuit in Philco set.

it decreases in capacitance or—more likely—opens the current flow is through R104, causing it to overheat. If you check, you will notice that the boost voltage is considerably higher than normal. When replacing C86, also replace R104 and C68B.

**5AXP4 ion burns**

*I have recently purchased a 5AXP4 universal replacement picture tube. After only a few weeks' operation a small brown spot appeared on its face. It looks like an ion burn. Recently it has been getting larger and I have stopped using it. While in operation it worked very well and came in handy.*

*I have checked with service technicians and many of them have had a similar experience. My guess is that I am using the tube in circuits where it was not intended. However, RADIO-ELECTRONICS stated that it could replace any tube. What is causing the ion burns?—P. L., Baltimore, Md.*


This letter is one of several on the same subject. The spot may be a true ion burn, caused by negative undeflected ions in the beam striking the screen. In making a universal type picture tube the ion-trap magnet was intentionally omitted to make setup easier. Thus, the trouble is not so much in the tube design as it is in operation.

At all times, keep brightness as low as possible. This reduces the beam current. In some cases the spot is not actually a burn, but a darkened area caused by vaporized metal from around the anode aperture. In any case, this does not indicate a defective tube or one nearly so. It is merely a warning to keep the beam current (brightness) to as low a level as is suitable. END





# New Set Features Modular Construction

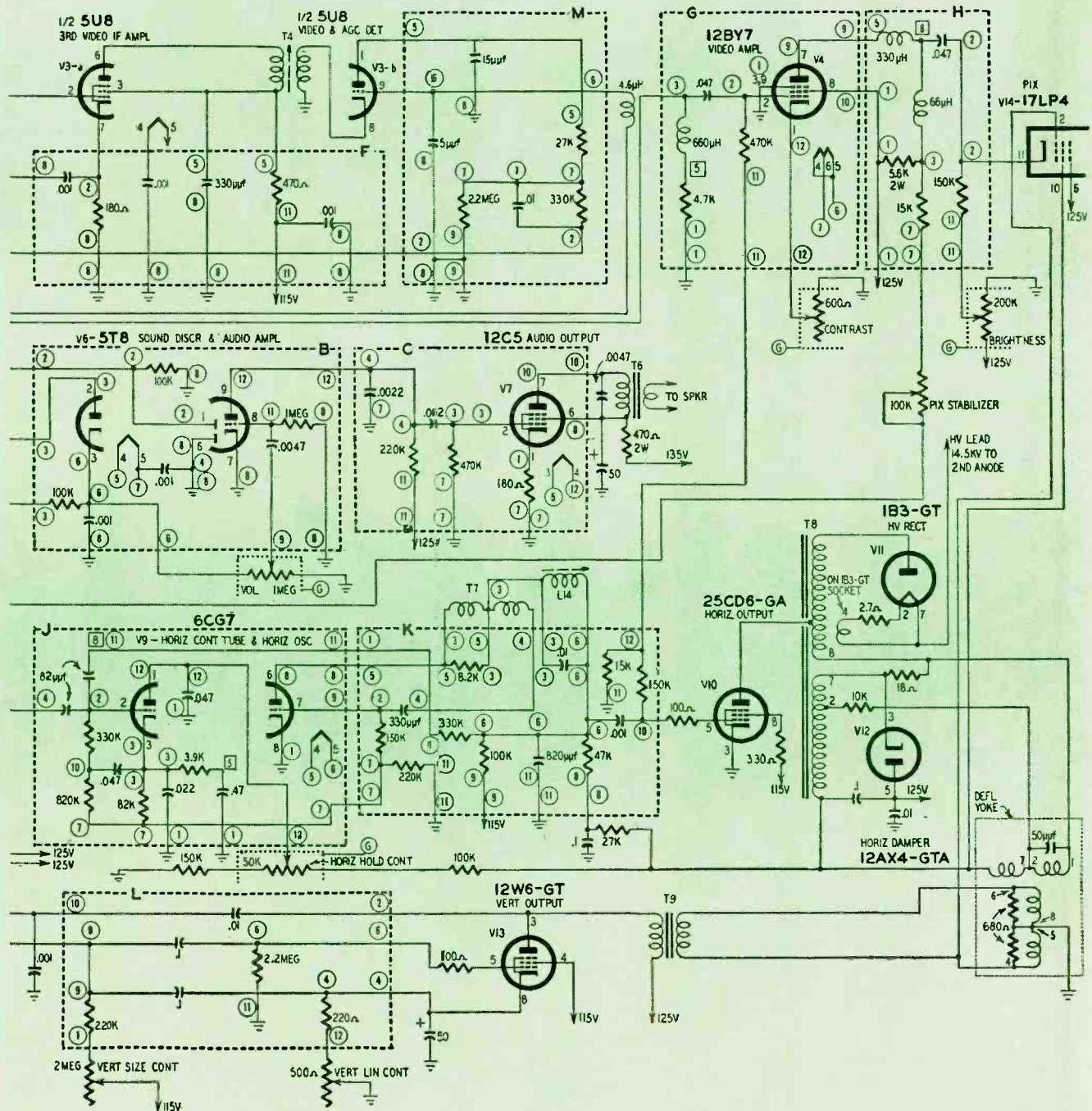

A reflex circuit combines the second video and first sound if amplifiers in one single-purpose tube. The video output containing the sound if (risers 6, module M) goes to the video amplifier through the 4.6- $\mu$ h rf choke and L8. L8 is coupled to L4 in the grid return of V2. This combination acts as a 4.5-me


sound trap in series with the input to the video amplifier and as a sound take-off transformer for V2. T2 and T3 are tuned to around 45 mc and L4 and L6 are tuned to 4.5 mc, the intercarrier sound intermediate frequency. The signals developed across T2 and T3 and across L4 and L6 do not interact with

each other. All controls sensitive to hum pickup or whose shafts would be hot if connected directly to chassis have their shields and shafts connected to a common grounding strip (G) connected to the chassis and B-minus bus through 220,000 ohms bypassed by a .001- $\mu$ f capacitor.


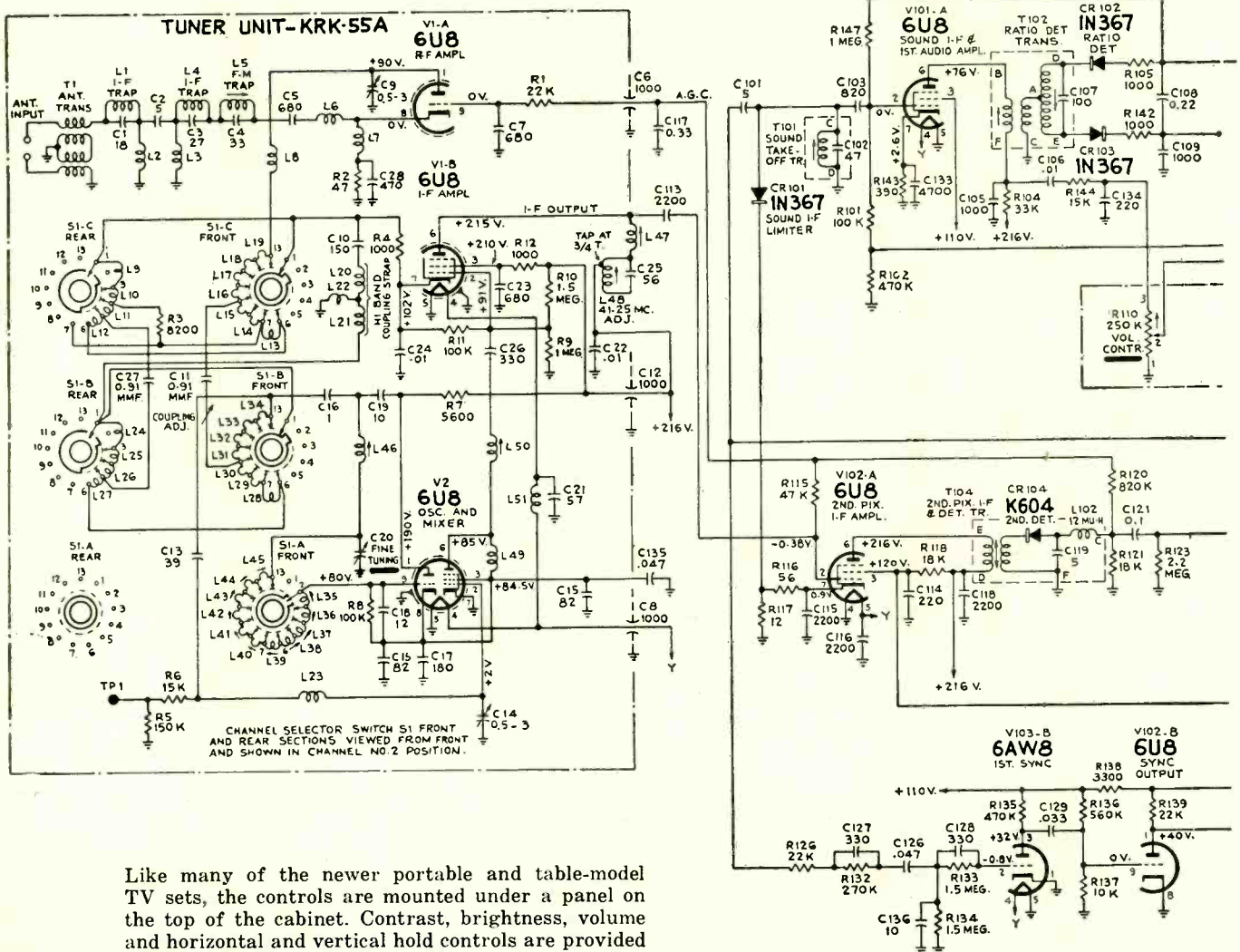
# RCA PERSONAL TV RECEIVERS


All models are vhf receivers identical except for cabinet color. A removable stand can be used to support the set and hold it at an angle convenient for viewing. An adjustable rod type antenna attached to the cabinet is adequate for use in many locations. Connections for an external antenna are provided for use in areas where one is required. These sets are easy to remove from the cabinet for servicing. The front and rear chassis can be separated so all components are readily available while the set is still in operation.



Like many of the newer portable and table-model TV sets, the controls are mounted under a panel on the top of the cabinet. Contrast, brightness, volume and horizontal and vertical hold controls are provided along with the fine-tuning and channel selector. The 45-mc if circuit is combined with a well-trapped front end to minimize interference from FM and adjacent-channel TV stations. The FM trap is slug-tuned and is adjusted to the frequency of the interfering station. The if trap coils (L1 and L4) are tuned for minimum response to 41.25- and 47.0-mc signals, respectively. L1 and L4 are adjusted by spreading or crowding the turns.
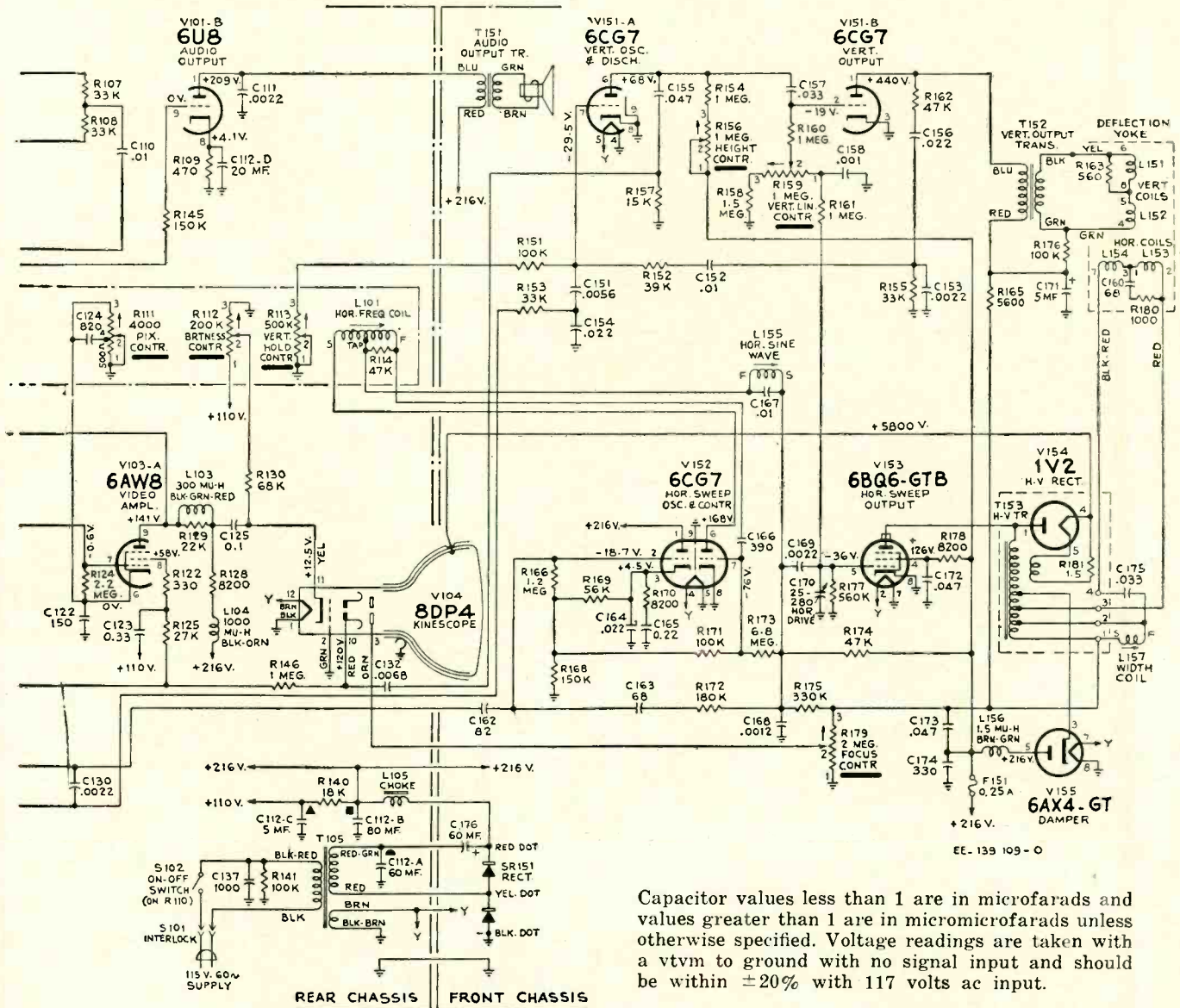
# Models 8-PT-7030, 8-PT-7031, 8-PT-7034


These models are only slightly larger than the average table-model radio. They are only 10½ inches wide, 9½ inches high and slightly less than 13 inches deep. The 8DP4 picture tube has a diagonal of 8½ inches and a viewing area of approximately 36 square inches. The 8DP4 has magnetic deflection with a 90° deflection angle and electrostatic focusing. The chassis has 11 tubes (including the 8DP4), 4 crystal diodes and a voltage-doubler type selenium rectifier to provide performance comparable to a standard 24-tube circuit.



Capacitor values less than 1 are in microfarads and values greater than 1 are in micromicrofarads unless otherwise specified. Voltage readings are taken with a vtvm to ground with no signal input and should be within ±20% with 117 volts ac input.



# HOFFMAN MARK 5

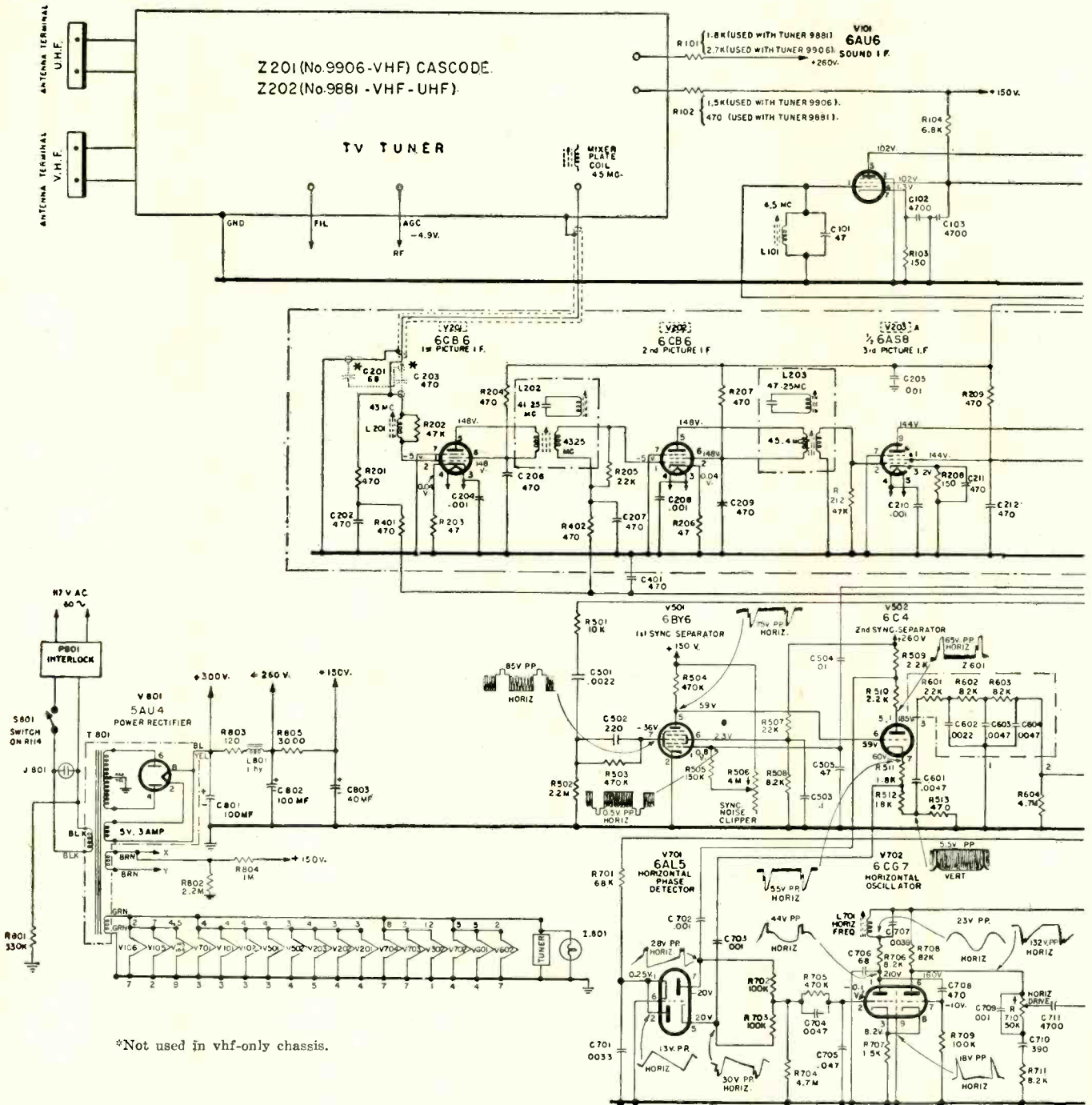


The Mark 5 models are available with the 419 chassis with a vhf tuner or the 419U chassis with a vhf-uhf tuner. It features a 10-watt push-pull of amplifier with three speakers. Cascode tuners are used in both chassis. The vhf tuner has a 6BQ7-A rf amplifier and 6AT8 mixer-oscillator. The tuner in the all-

channel chassis has a 6BZ7 rf amplifier, 6U8 mixer-oscillator, 6AF4 uhf oscillator and a crystal uhf mixer.

A three-stage if amplifier with delayed agc provides optimum performance under varying signal levels. Sync stability is insured by cascaded sync separators and a noise-clipper circuit. A

control sets the operating point of the noise clipper. In some models, this control is a potentiometer on the secondary control panel. In others, it is a push-pull switch combined with the contrast control. It should be pushed in for normal reception and pulled out in fringe areas.

# Chassis 419, 419U

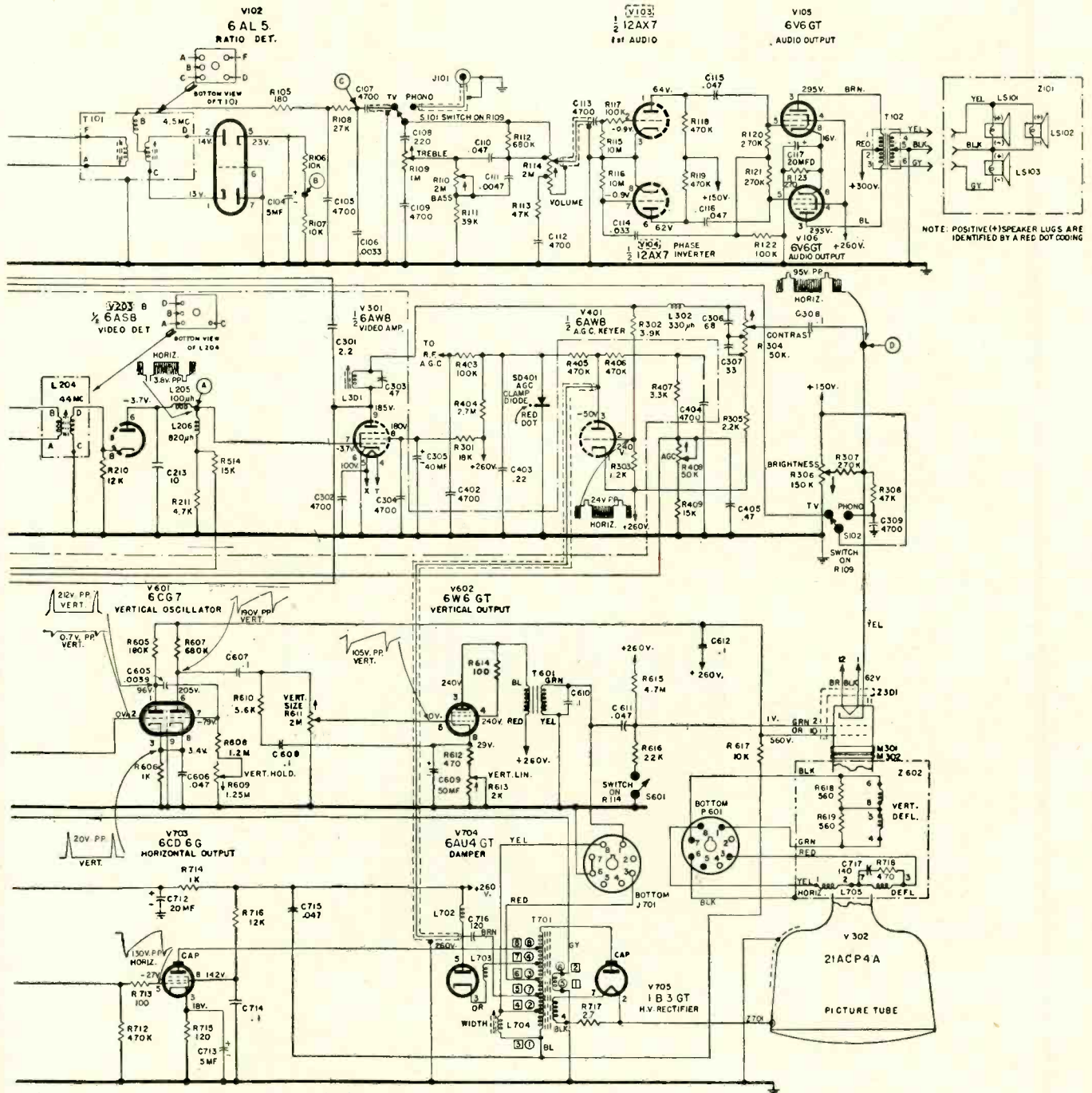

A switch between the CRT grid and ground eliminates the spot of light that often remains on the screen when the set is first turned off. This switch is ganged to the on-off control. Opening it reduces the grid bias, accelerates the residual electron beam and quickly discharges the high-voltage

filter capacitor, thus killing the spot. **Service notes:** Waveforms and socket voltages are taken with the set receiving an average signal and controls at normal settings. Socket voltages are measured with vtvm to ground and are positive unless otherwise specified. They

many vary within a  $\pm 20\%$  tolerance. Capacitor values shown as decimals are in  $\mu\text{f}$  and whole numbers are  $\mu\text{mf}$  unless specified. Boxed terminal numbers on flyback transformer are for part 5177A-2 used in later production. Circled terminal numbers are for part 5177A used in early production.



# UNDERSTAND YOUR COLOR BAR GENERATOR

*Analyzing the NTSC color signal*

By ROBERT G. MIDDLETON\*

**T**HE NTSC color bar generator is so named because it provides an NTSC color bar signal. This means that a properly adjusted color TV receiver will produce bars of saturated color on the screen of the color picture tube when energized by the output from the generator. Color bar generators other than the NTSC type are also available, usually at lower cost, but do not provide the standard NTSC signal and most of the color bars will not be pure or saturated.

To understand the NTSC color bar generator, let us refer first to the bar display in Fig. 1. Eight bars are shown, comprising the three primaries: red, green and blue; the three complementaries: cyan, magenta and yellow; the

two principal luminance signals: black and white. In addition to these bars, an NTSC color bar generator usually provides the color-difference signals: I, Q, R - Y, B - Y and G - Y. An instrument of this type may also provide a (G - Y)/90° signal, another useful test signal, discussed at a later point.

Let us review the appearance of the color bar signal on the screen of a wide-band scope. Sync and burst are provided, as shown in Fig. 2, to lock the horizontal and color sync sections of the color TV receiver properly. The sync and burst supplied by the color bar generator are in all respects similar to the sync and burst seen at the second detector (Fig. 3) of a color receiver tuned to a color TV program. The burst is somewhat contaminated by

noise and crosstalk with the picture and sound signals. However, the technician will soon become familiar with these imperfections.

Note carefully in Fig. 2 that the red bar appears as a 3.58-mc sine-wave signal superimposed upon a square wave. However, the white, gray and black signals have no 3.58-mc voltage component and consist solely of a square-wave voltage. This square-wave voltage is termed the Y or luminance voltage. The various colors reproduced on the screen of the color picture tube are not pure and saturated unless the color bar signal contains the proper Y voltage. This is the chief distinction between an NTSC type of color bar generator and a rainbow type of generator. The rainbow generator provides a 3.58-mc signal only, with the

\*Chief field engineer, Simpson Electric Co.

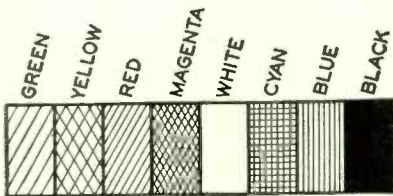


Fig. 1—Display from NTSC color bar generator. White signal is a reference white, as used in color TV transmitters.

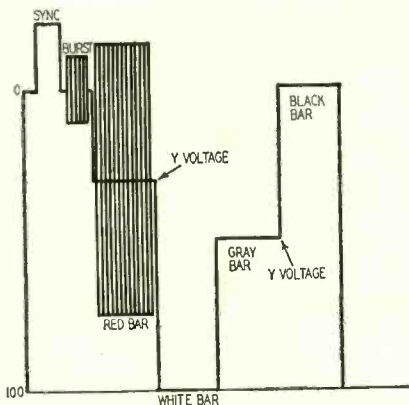


Fig. 2—Red bar appears on wide-band scope as a Y component upon which is superimposed a 3.58-mc chrominance signal.

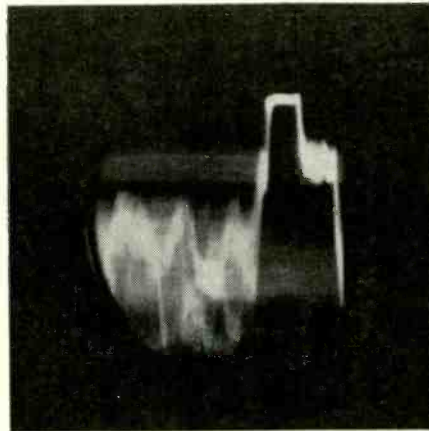


Fig. 3—Horizontal sync and burst at output of video detector of color set.

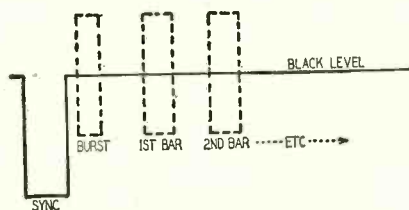


Fig. 4—Output from rainbow color bar generator—a succession of 3.58-mc signals centered on the black level.

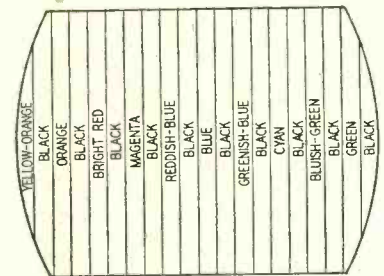


Fig. 5—Succession of hues from typical rainbow type color bar generator.

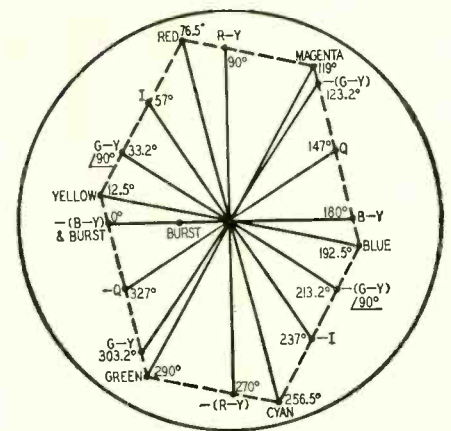


Fig. 6—Vectorscope type display shows the various colors and color-difference signals as seen on a scope screen.

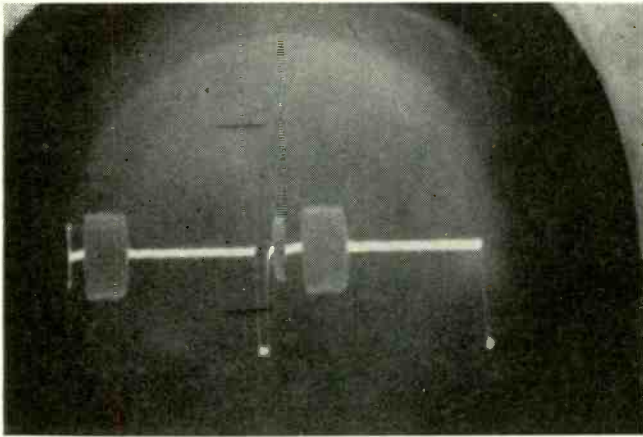


Fig. 7—Output from an NTSC color bar generator with sync, burst and a single color-difference bar.

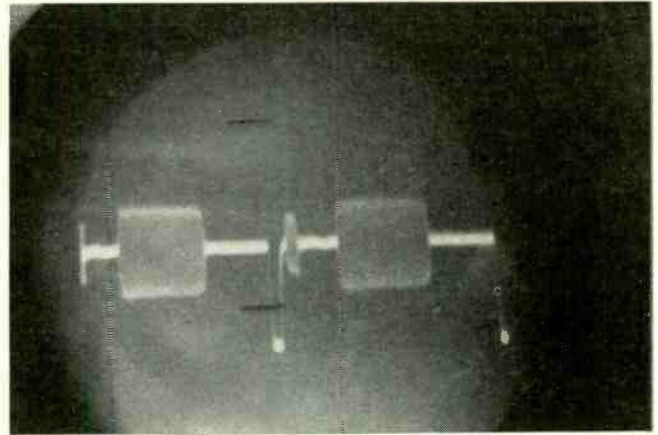


Fig. 8—Output from Fig. 7 generator with different-hue color-difference bar.

Y component. This distinction is shown in Fig. 4, which should be compared with Fig. 2.

The successive bars differ in hue because the 3.58-mc voltage varies in phase from one bar to the next. Fig. 5 shows the variation in hues obtained from a typical keyed-rainbow type of generator. The phases of the principal colors and color-difference signals are shown in Fig. 6. This is obtained by applying the output of the R - Y detector to the vertical amplifier and the output of the B - Y detector to the horizontal amplifier of the scope.

Fig. 7 shows the output from an NTSC color bar generator when a single color-difference bar is present in the output. Fig. 8 shows the output when a different color-difference bar is present. Fig. 9 illustrates the output form when the two color-difference bars are present simultaneously. The only difference between the two color-difference signals is a difference in phase, as indicated in Fig. 6.

When we proceed from the color-difference bars, such as R - Y, B - Y, etc., to the saturated color bars such as red, green and blue, it is required that the 3.58-mc signal not only vary

in phase, but also in relative voltage for each color, as seen in Fig. 10. The spaces for white and black have zero 3.58-mc voltage. When the proper Y voltage is added to these 3.58-mc signals, the full color signal is obtained. Fig. 11 shows the Y component which corresponds to each of these color bars.

#### Readjusted values

To deliver an NTSC signal, the color bar generator is adjusted to provide the *readjusted chrominance values* shown in Fig. 6. These require a bit of careful explanation. When the readjusted chrominance values are used to produce a bar pattern, the output from the generator appears as shown in Fig. 12 (as seen on the screen of a wide-band scope). The complete NTSC color signal is based on transmission of 75% saturated colors. A 100% saturated color is rarely transmitted, since it rarely occurs. Thus, the output from a color bar generator is adjusted to provide a 75% saturated signal.

Note that the black level is 10% below the porch level of the sync pulse. Green extends up to the black level; red, magenta, blue and cyan extend into the blacker-than-black region. The

lower excursions of the yellow and cyan signals are on the same level as the white signal. This is termed the *reference white level* and is used in this manner to adjust the level of the chrominance signal properly with respect to the level of the Y signal. There is a 20% whiter-than-white region between the reference-white and the zero carrier levels. This residual is provided in the NTSC transmission to avoid sync buzz in intercarrier receivers.

The setup interval is the region from 0% to 100% as shown along the ordinate. In terms of setup units, the sync pulse occupies an excursion of 40% and extends 50% above the black level. The black level is 10 setup units below the level of the back porch of the sync pulse. The burst has the same excursion as the sync pulse (40%); the when a different color-difference bar

The color bar signals in Fig. 12 are NTSC signals and are a modified signal in which R - Y is reduced to 0.877 of its original value and B - Y to 0.493 of its original value. The reason for this reduction of chrominance voltages with respect to Y voltage is to avoid overmodulation on

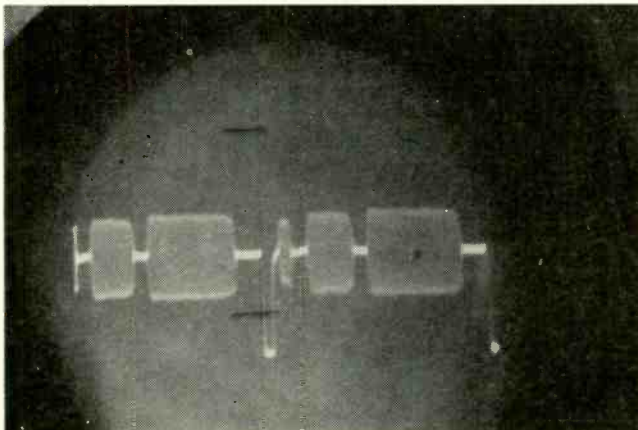


Fig. 9—Outputs of Figs. 7 and 8 produced simultaneously by generator.

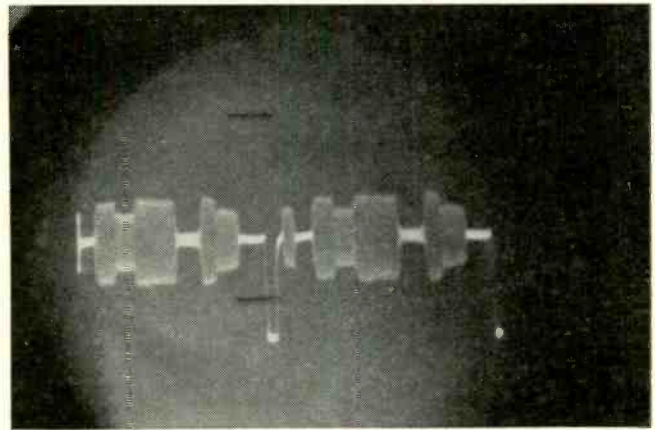


Fig. 10—The 3.58-mc color components. Black and white are at zero voltage.



## TEST INSTRUMENTS

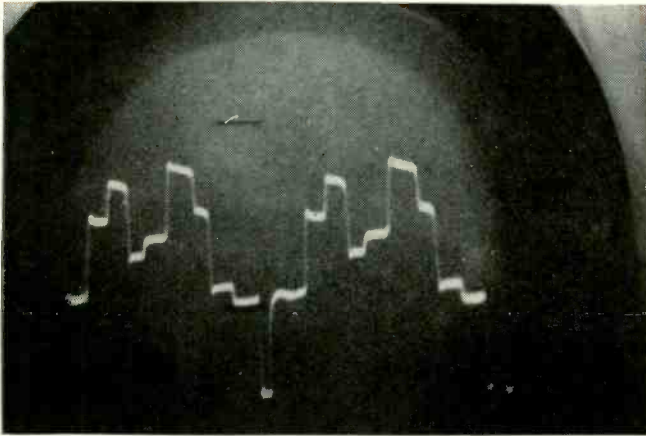


Fig. 11—This Y signal is added to 3.58-mc signal for complete color signal.

highly saturated colors (such as color bars), as illustrated in Fig. 13. The excursions of the Y signal and wave envelopes are shown with respect to the black level. When 100% saturated colors are transmitted without modifying the signal in accordance with NTSC specifications, overmodulation of as much as 79% can occur. But when the NTSC signal is used, overmodulation on 100% saturated colors is re-

duced to 33%. In practice, overmodulation does not actually occur since program material rarely reaches saturations greater than 75%, and 75% of 1.33 = 100%. A 75% saturated color transmitted by the NTSC signal reaches but does not exceed the white level.

In the NTSC system the Y signal is unmodified to permit normal operation of monochrome receivers. The R - Y and B - Y detectors (Fig. 14) receive the same drive from the bandpass amplifier. Since R - Y is reduced to 87.7% of its original value and B - Y to 49.3% to avoid overmodulation at the transmitter, the B - Y detector is adjusted to develop 1.78 times the output of the R - Y detector. The R - Y and B - Y outputs then represent correct chrominance balance and G - Y is obtained in correct proportions by mixing  $-0.51(R - Y)$  with  $-0.19(B - Y)$ . The B - Y level must first be set correctly with respect to the

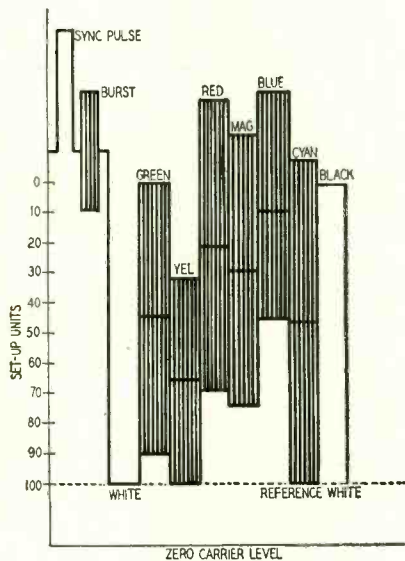


Fig. 12—NTSC complete color signal.

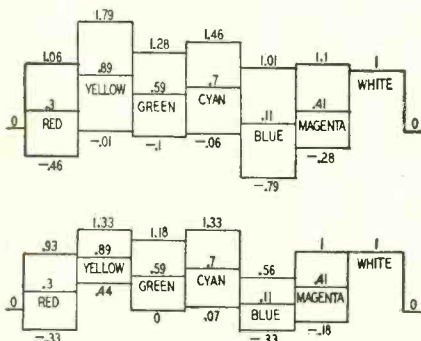


Fig. 13—Top, waveforms for bar generator providing 100% saturated color signals. Bottom, generator waveforms provide standard NTSC color signals.

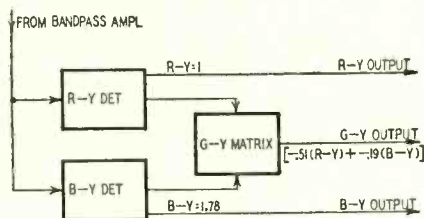


Fig. 14—The detector and matrix layout for obtaining correct color balance.

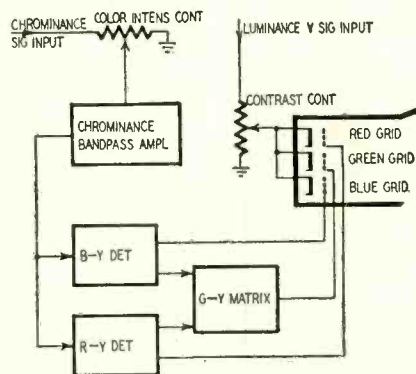


Fig. 15—Chrominance and luminance signals processed in separate channels.

R - Y level before the G - Y matrix is checked. The relative settings of the chrominance and luminance controls are made so that approximately 12% more gain is applied to the color signal than to the Y signal. In this manner, complete signal balance is restored, as shown in Fig. 15.

The chrominance and luminance signals are processed in separate signal channels, hence the operator has control of each signal level. The contrast control is set to provide a normal black-and-white picture of satisfactory contrast. The color-intensity control is then set to obtain the most satisfactory flesh tones, since the viewer is most critical of this aspect of color reproduction. If any color distortion is present, it is preferable to relegate the distortion to hues and saturations other than flesh tones. Since an NTSC signal is processed by the signal circuits, the output from the B - Y detector is made proportionally greater than the output from the R - Y detector, to restore color balance. Under these circumstances, the G - Y matrix then develops a green-signal output with proper color balance. The saturation of the NTSC signal is less than the theoretical value, which requires that the color-intensity control be advanced proportionally to restore color saturation.

We now proceed to a closer inspection of the mechanics of color bar generation. Bear in mind that a color bar generator produces the same end result as the transmission of a test pattern from the color TV station. In an R - Y B - Y transmitter Y is obtained by adding 0.3 red voltage to 0.59 green voltage and 0.11 blue voltage in the Y matrix. The -Y signal is obtained by passing Y through a phase inverter. R - Y is obtained by adding the red voltage and the -Y voltage in the R - Y adder. B - Y is obtained by adding the blue voltage to the -Y voltage in the B - Y adder. The output voltages from the R - Y and B - Y adders are used to modulate the output from the 3.58-mc color-subcarrier oscillator. The modulated 3.58-mc voltage is then added to the

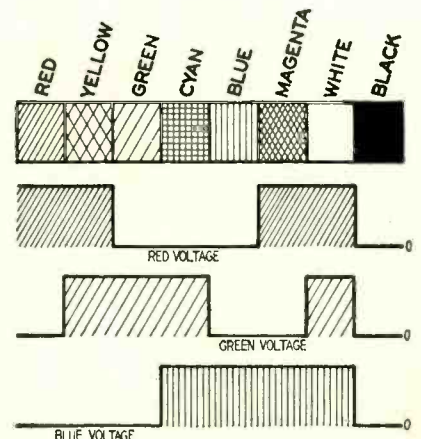


Fig. 16—Producing color range by keying red, green and blue multivibrators.

Y voltage in the complete-color-signal adder. The output from this adder is the complete color signal.

This same general arrangement can be used (and often is) in the design of color bar generators of the quadrature encoder type. However, in the color bar generator, the red camera is replaced by a multivibrator which provides a square-wave signal; likewise, the blue and green cameras are in their turn replaced by similar multivibrators.

We know that suitable mixtures of red, green and blue can produce any visible color. Fig. 16 shows how the red, green and blue multivibrators are timed to produce the hues of yellow, cyan and magenta, in addition to black and white. The square-wave outputs from the red, green and blue multivibrators shown in Fig. 16 are applied to the Y matrix and to the R - Y and B - Y adders. From the Y matrix is obtained the luminance signal +Y. This signal is passed through a phase inverter to obtain -Y for the formation of the R - Y and B - Y signals. The G - Y signal is recovered at the receiver from R - Y and B - Y, hence G - Y is not formed as such at the transmitter (bar generator). Instead, the green bar is transmitted as  $-0.59(R - Y) - 0.59(B - Y)$ . The result is that the G - Y signal phase appears as seen in Fig. 6. It might be supposed offhand that G - Y would appear at an angle of  $45^\circ$  with respect to  $-(R - Y)$  and  $-(B - Y)$ , but remember these are NTSC signals in which R - Y is 1.78 times B - Y.

The end result of applying this NTSC signal to a properly adjusted color receiver is as if the red camera (red multivibrator) were connected to the red gun in the color picture tube, the blue camera to the blue gun, the green camera to the green gun. The only reason for the seeming complication of the signal system is to achieve compatibility and to compress the color signal within the existing black-and-white TV channel space.

The reader will perceive that the various chrominance signals depicted in Fig. 6 are the *resultant* of R - Y and B - Y voltages and could be generated by direct switching of chrominance phases instead of using a quadrature encoding process. This direct-switching approach leads to important simplifications and makes possible a more stable instrument for service use. END

In the July  
**RADIO-ELECTRONICS**

**QUESTIONS ABOUT CROSSOVERS**

by Norman Crowhurst

## EISENHOWER HAILS INVENTOR

**T**HE magnitude of American contribution to world-wide better living was illustrated March 16, in a letter from President Eisenhower to Dr. Lee de Forest heralding the 50th anniversary of the radio tube.

Dr. de Forest, through his invention of the grid vacuum tube in 1906, endowed the world with electronics—the industry which provides the most breathtaking constellation of human conveniences ever to stem from a single discovery.

The fruits of the De Forest basic invention include such long-accepted wonders as radio and television, long-distance telephony, talking movies, hearing aids, radio therapy and radio aids to air navigation.

The President's letter stated: "You must also feel great satisfaction in remembering your past decades of service and in anticipating future achievements that your handiwork has made possible." The great scientist, with over 300 patents granted to him, is approaching his 83d birthday, his way lighted by the endless panorama of miracles born of his genius.



Among the more recent "spin-offs" from the 1906 De Forest invention are electronic computers, radar, guided missiles and a veritable chain effect in new industrial electronic controls and automation.

A man of great personal warmth and vigor, Dr. de Forest, in his Los Angeles laboratory, holds indomitably to his research with a keen, youthful interest in the future.

THE WHITE HOUSE  
WASHINGTON

March 16, 1956

Dear Dr. de Forest:

In this fiftieth anniversary year of a great invention, I congratulate you on your many contributions to scientific progress. Through your long and distinguished career you must have experienced many moments of pride that your imagination and talent furthered the development of modern radio, television and radar. You must also feel great satisfaction in remembering your past decades of service and in anticipating future achievements that your handiwork has made possible.

May you enjoy many more years in which to witness the fruit of your labors.

Sincerely,

*Dwight D. Eisenhower*



Dr. Lee de Forest  
c/o Rear Admiral Ellery W. Stone, USNR  
American Cable & Radio Corporation  
67 Broad Street  
New York 4, N. Y.



# PRESET AF CALIBRATOR

*Unit provides check frequencies  
from 100 to 15,000 cycles*

By I. QUEEN  
EDITORIAL ASSOCIATE

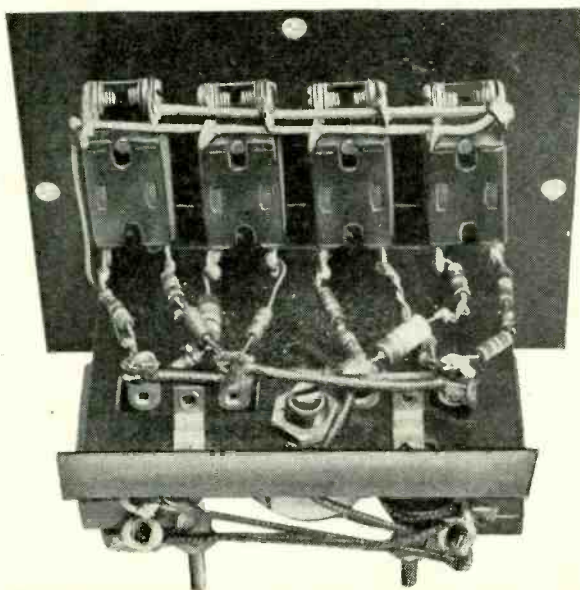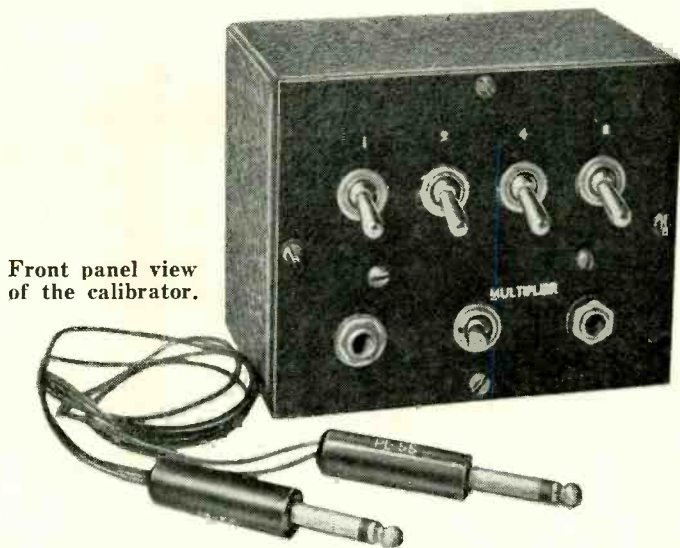

MANY constructors have built some form of variable af oscillator. Completion of the instrument still leaves a big problem, *frequency calibration*. Many technicians do not have an oscilloscope or standard frequency source for checking with Lissajous figures. Line frequency is not satisfactory because its multiples are inconvenient; the sub-multiples cannot be used because they are so low.

This preset calibrator provides check frequencies from 100-15,000 cycles. Instruments can be calibrated far more quickly and accurately than with any dial-set method. Calibrator frequency is determined from values of resistance and capacitance.

The calibrator is a Wien bridge with fixed elements as shown in the basic circuit in Fig. 1. There are four arms.

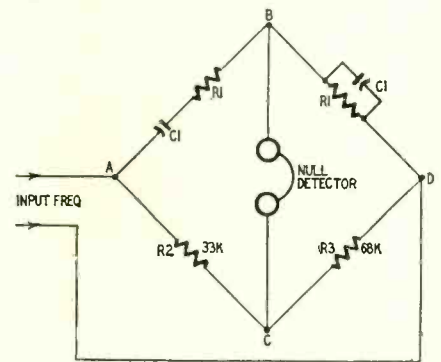


Fig. 1—A basic Wien-bridge circuit.

A-C and C-D are resistive with C-D twice the value of A-C. A-B and B-D are resistance-capacitance combinations. The bridge is balanced and produces a null at a frequency in *cycles* given by the formula

$$\frac{1}{2\pi RC}$$

where R is the resistance of R1 in megohms and C the capacitance of C1 in  $\mu f$ .

The complete circuit of the calibrator is shown in Fig. 2. A potentiometer has been added to compensate for minor deviations in the resistances from those required for balance. Resistors and capacitors corresponding to R1 and C1 (in Fig. 1) are fixed and are switched in pairs to vary the frequency. Changing the resistance varies the frequency

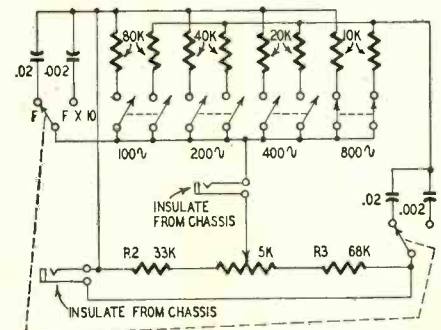


Fig. 2—A null type frequency calibrator using the Wien-bridge circuit.

## HAZARD on the BENCH

By B. W. WELZ

If you haven't yet seen the kind of guy Sam was, you will some day if you stick around television long enough. The trade is full of them. Sam pooh-poohed all danger. He laughed at high voltage and turned his back on picture-tube implosions.

He used to work at the same bench with me and got a big kick out of the gingerly way I probed for high voltage. He would laugh if I put one hand in a pocket. "High voltage gets only those who are afraid of it," he would say.

(It got me once. Not bad, just across a finger. I heard it sort of hiss and pulled away, but not before it arced to the finger. From then on I've been very careful around high voltage in TV, no matter what Sam said.)

Sam got big laughs when I put on shatterproof goggles to work around big picture tubes. At first I wore an apron and gloves when I did any kind of work on those babies, but Sam laughed so hard that I gave up the apron and gloves. But I wouldn't give up the goggles.

The boss took a dim view of Sam's easy attitude toward the dangers in TV servicing. He never laughed when Sam laughed at me. He warned Sam what could happen if he wasn't careful but Sam shrugged and went ahead doing things his way.

Sometimes Sam would shove the chassis haphazardly around on the bench with the picture tube in place, often banging it against instruments. I've seen him put a big tube against his chest and tap a tight yoke on the neck with a screwdriver to loosen it. I shake a little inside even now when I think about it. When anyone warned him of implosion, he'd laugh. "They make these bottles harder than people think," he would say.

And then one day his luck ran out! He had a 17-inch job on the bench and was pushing it around with his customary nonchalance when the tube let go.

Luckily, Sam had the tube away from him when it burst. If he had been over it or had it against his chest like he sometimes did, he would be worse off now—maybe even dead.

As it was, they spent half that first day taking glass out of him in the hospital. They say they will be probing him for about a week and then they might not have it all out. One of his eyes is pretty bad and they are not sure they can save it.

It's pretty tough for Sam and it's tough on his wife and two kids now that he won't be working for a while. You'd think a guy like Sam would think about his wife and kids even if he didn't think about himself when he worked around things as dangerous as television sets.—Aesop

in steps and changing the capacitance provides a multiplication factor to extend the range.

Four toggle switches select basic frequencies. These are 100, 200, 400 and 800 cycles in the low (F) range; the  $F \times 10$  range multiplies by 10. Ranges are marked 1, 2, 4 and 8 above the row of switches. In this case the switch between the jacks is thrown in one direction for *hundreds* and in the other for *thousands*. The instrument is not limited to these eight frequencies however. Actually, 29 frequencies are available by flipping one or more switches.

In a Wien bridge frequency is inversely proportional to resistance. When two resistors are connected in parallel, the new frequency is the sum of the first two. The same law applies when three or more resistors are paralleled. In each case the new frequency is the *sum of the frequencies* corresponding to individual resistors. The same theory holds when capacitors instead of resistors are switched.

With the basic frequencies listed above this calibrator (see diagram) can be tuned from 100–1,500 cycles in 100's and from 1,000–15,000 cycles in 1,000's. For example, if the switches corresponding to 100, 200 and 800 cycles are closed, the bridge is tuned to 1,100 cycles.

Resistors R2 and R3 are not critical because the potentiometer can be adjusted for balance. These may be 1-watt units. All other resistors should be carefully selected for close tolerance, about 1 or 2%. The values listed in the schematic are about 0.6% higher than the theoretically correct values. Therefore it is better to select resistors slightly lower than those called for. If a precision bridge is not available, use the values listed in the diagram. Time can be saved by pairing resistors; two may be connected in series or parallel to give needed values. For example, 40,000 ohms can be obtained by checking the resistance of several 39,000-ohm units or trying 18,000- and 22,000-ohm resistors in series. 80,000 ohms may be obtained from an 82,000-ohm unit or by connecting 33,000 and 47,000 ohms in series.

The instrument has two phone jacks, either of which may be used for input and the other for output. Headphones are plugged into the output jacks; the output from an af oscillator is plugged into the other jack. As the oscillator is tuned to the bridge frequency, minimum sound will be heard. Then the potentiometer is adjusted for a better minimum.

I found that the same null point held for all frequencies in either range. However, there was a slight difference between ranges. This indicated a slight error in one of the capacitors. It was corrected by adding a 250- $\mu\text{f}$  trimmer across one of the .002- $\mu\text{f}$  capacitors. The procedure was:

1. Set potentiometer for null on the low range.

2. Switch to some frequency on the high range. Do not touch the potentiometer again but add the trimmer across the .002- $\mu\text{f}$  capacitor which minimizes the sound further.


3. Adjust the trimmer for best null.

This bridge tunes out a narrow range on either side of the tuned frequency. Therefore only a pure sine wave can be entirely eliminated. A distorted signal can be only partially tuned out, because the harmonics will pass through the bridge into the phones. In this case minimum sound will be heard. The bridge can be used to measure distortion, reduce high-frequency noise or filter out an undesirable signal.
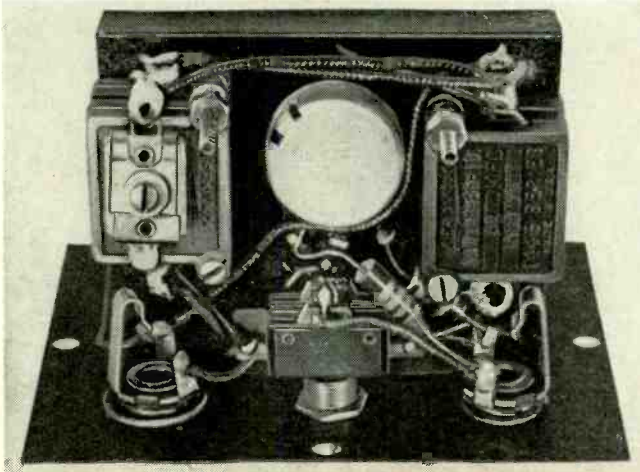
## Parts list for preset of calibrator

2—10,000, 2—20,000, 2—40,000, 2—80,000 ohms,  $\frac{1}{2}$  watt, 1 or 2% (see text); resistors: 1—33,000, 1—68,000 ohms, 1 watt; resistors: 1—5,000-ohm potentiometer; 2—.002, 2—.02  $\mu\text{f}$ , capacitors; 1—250- $\mu\text{f}$  trimmer capacitor (see text); 2—phone jacks; 1—metal box, approximately 3 x 4 x 5 inches with metal shelf for supporting resistors; 4—dpst, 1—dpsdt switch.

Although this bridge has been described as a rejection filter, it can be used in Wien-bridge type oscillators. The preset circuit has important advantages over conventional bridges with variable elements. It eliminates the bulky variable capacitor. Also it makes quickly available a large number of convenient frequencies. Switch tuning is always more accurate than dial tuning. If desired, the fixed resistors may be replaced with potentiometers. END



Bottom view of shelf — large capacitors may be replaced with smaller units.



# *ELECTRONICS in the* **AIR FORCE\***

*A survey of some of the opportunities for personnel and some of the equipment in use*

By RONALD A. LANE

**T**WO results of the enormous dependence of the Air Force on electronics are an extensive training program and a remarkable series of opportunities for trained technicians, both uniformed and civilian.

In general, three classifications of personnel handle Air Force electronics operation and maintenance: uniformed personnel, employees of the U. S. Civil Service and employes of private contractors (such as RCA, G-E, Westinghouse, etc.).

A typical case is that of an Air Force sergeant who entered the service totally ignorant of electronics, was trained while in uniform at Government expense and eventually specialized in the operation and maintenance of a highly intricate digital computer. In the whole United States there are not many persons who understand that computer. So when the sergeant was discharged he went on a little vacation with his accumulated service pay and then capitalized on his training by returning to operate the identical computer at a very attractive civilian salary. Some airmen prefer to serve out their 20 years and then retire in early middle age with a pension plus the training that can earn them an excellent civilian income in addition to it.

Another type of change in individual status takes place when the Air Force contracts with a private company to perform some functions previously handled by Civil Service personnel. In that case the Civil Service jobs disappear but the same work remains to be done and the private company needs experienced hands to do it. Numbers of people resign from Civil Service but remain in the same jobs as employes of a private company and sometimes (if the individual is badly needed) at a higher salary.


Stability and flexibility are provided

\*This article has been cleared with the Air Force for security and accuracy. Such clearance does not mean that the Air Force in any way sponsors its presentation.



Long-range Morse code communications.

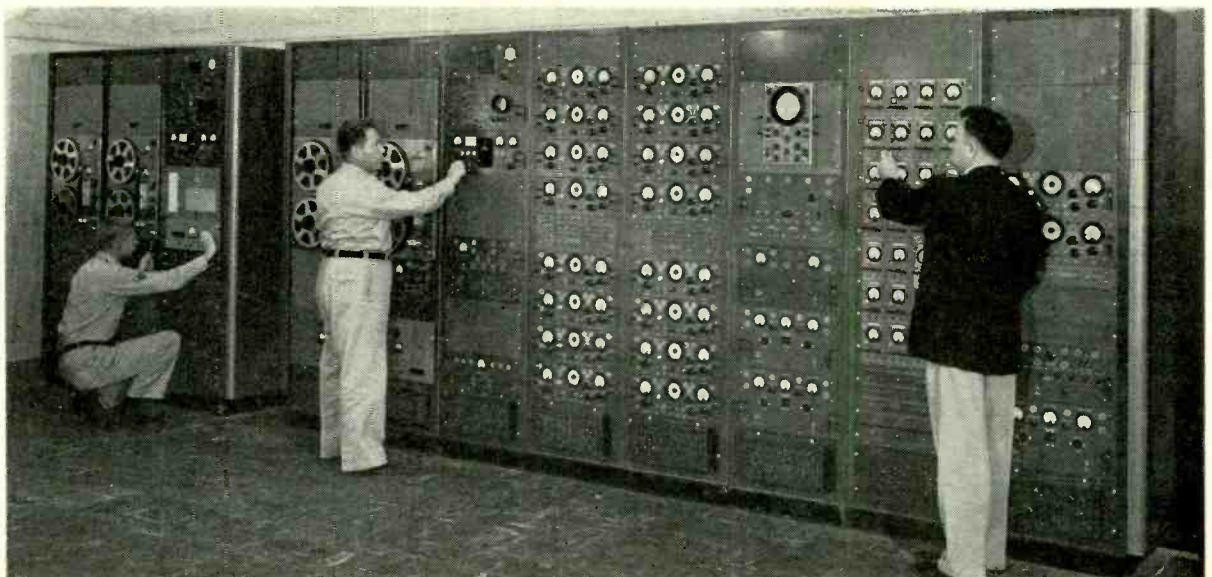**Uniformed and civilian personnel cooperate in operating Air Force equipment.**





by these arrangements. An electronics staff composed of uniformed airmen alone would be unstable because individuals reach the end of their term of service and are discharged. The Air Force cannot reap the full benefit of their training except by rehiring them as civilians. This is usually done indirectly, as explained, through the Civil Service or through private contractors.

A Civil Service staff provides stability since a substantial percentage of the personnel prefers to remain with the work for a long period of years for the sake of the pension at the end. But Civil Service regulations are legally rigid. Employees of a private contractor can be used more flexibly. The triplex organization, therefore, combines military discipline, relative permanence and adaptability—and it offers a triple opportunity to anyone interested in doing electronics work for the Air Force.

### Training and advancement

Those who choose to enlist in the Air Force can obtain very sound preliminary instruction in the Air Technical Training Command Schools at Scott Field, Ill., or Keesler Field, Miss. The course takes 6 months. Graduates emerge with the rating Airman Third

Class (equivalent to Pfc in the Army). Then they specialize in definite types of electronic equipment. They obtain further instruction either on the job or through additional courses at the Air Technical Training Command Schools. They can also obtain correspondence courses in electronics from the Air University.


Advancement in pay and status up to and including the rating of master sergeant depends on the individual's ability and interest. During his first 4 months in service the airman is paid \$83.20 per month plus maintenance, quarters, uniform allowances, allowances for dependents if any, the privilege of buying standard merchandise at reduced prices through the Post Exchange and other GI benefits. The pay of a master sergeant is \$206.39 per month plus the same allowances, privileges and benefits. If, after his discharge, he wants to work for the Air Force as a member of the U. S. Civil Service or as employee of a private contractor, he may find himself assigned to do the work of a commissioned officer but with civilian pay and status.

Civil Service personnel used by the Air Force may have been uniformed airmen. As a rule such personnel are in the GS (general service) category and classified from GS-5 to GS-11 or higher. The GS-5 classification corresponds more or less to a general electronics technician or "engineering aid" with a salary beginning at \$3,410 a year and advancing automatically to \$4,160 after 7 years—but much more rapidly if the incumbent takes and passes promotion examinations. An electronics technician who rates GS-7 is exceptionally qualified and more or less a "junior engineer." The 1953-54 GS-7 salary range was \$4,200 to \$4,955 per year. Ratings from GS-9 and up require engineering training and qualifications.


Civil Service employees stationed at Air Force bases may enjoy subsidiary advantages such as Post Exchange shopping privileges, Officers Club facilities, low-rent Government housing on the base, low-cost lunches in a GI mess hall, etc., the details varying greatly according to the individual, the location of the base, local conditions there and the current policy of its commanding officer or of the Air Force. They also enjoy relative employment security, vacation and sick leave privileges, automatic promotions within each grade and pensions.

Employees of a private company that works for the Air Force under contract are simply hired hands. Their pay, privileges and job conditions are those customary in the electronics industry for the type of work and competence involved, with two exceptions: the loyalty clearance required if the work brings the individual into contact with any hush-hush military matters, the location of the work. Sometimes this may be on a remote base, on an island or in a desert, where the civilian employe lives substantially under military conditions because there are no other facilities. In such cases the company employe may be able to collect, in addition to his salary, a bonus or expense account or travel allowance, depending on how badly he is needed and how easy or difficult it may be to hire someone else for so remote an assignment.

All three types of personnel—military, Civil Service and civilian—work on an enormous range of electronics equipment: communications, navigation devices, radar to track both friendly and hostile targets, etc. Communications alone includes five kinds of operation: plane to plane, plane to ground, point to point on the ground, intercommunication in the plane, intercommunication on the ground. Many frequencies are used for such communi-

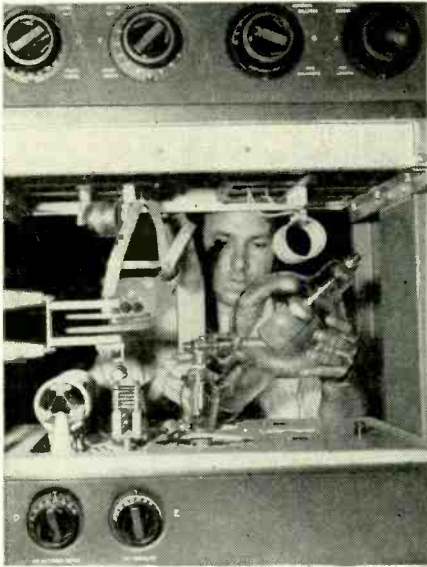

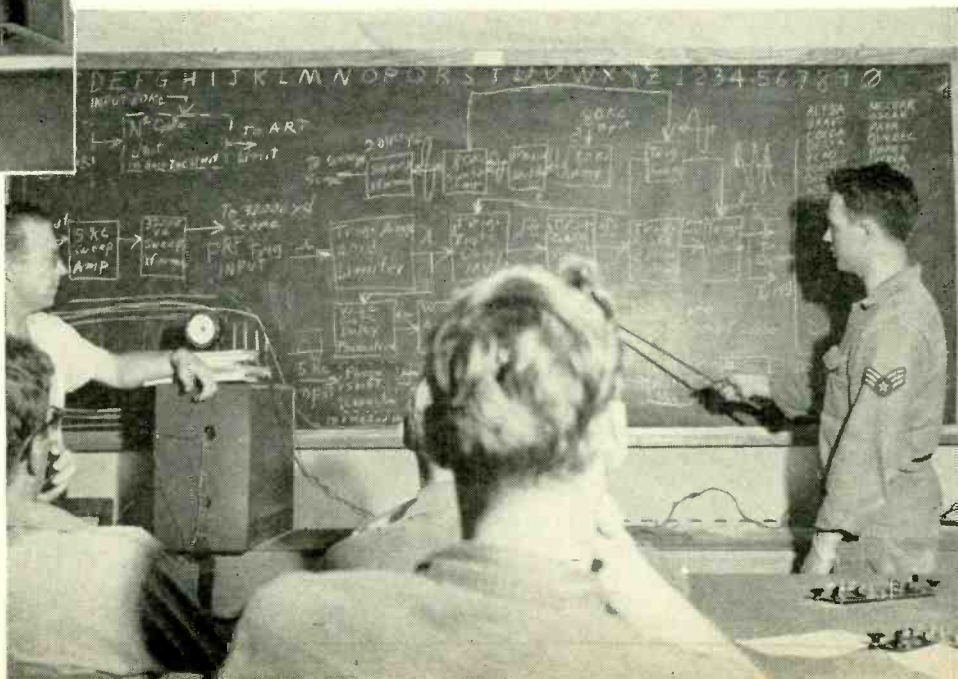Technician changing "bottle" in a 5-kw high-frequency transmitter.



Instructor explains electronic equipment.

All photos by U. S. Air Force



## ELECTRONICS

cations, ranging from audio on the intercom to vhf and uhf. Voice, Morse code and teletypewriter all have their place in this communications empire.

But the meat that lovers of electronics will find really juicy (and about which least can be said) belongs to the Air Research and Development Command of the Air Force. The mission of this command is to seek new basic knowledge; investigate the fundamental laws of nature; develop new and improved devices, processes and techniques and maintain the qualitative superiority of Air Force equipment. The ARDC has eight centers located in every part of the United States from Massachusetts to California. It defines its functions as follows:

"Basic research—fundamental, theoretical or experimental investigation to increase man's knowledge and understanding of the natural world. Immediate application is not a direct objective . . .

"Applied research—and application of the results of basic research to accomplish specific objectives . . .

"Development— . . . practical application, including the construction and testing of prototype models or devices . . ."

This is some of the work to which persons who serve the Air Force in or out of uniform may be assigned, and this is where the science of electronics finds a job as big as itself and is able to show what electronics can really do!

### One type of work

One highly complex ARDC program involving massive and elaborate application of the electronic sciences may be described briefly, with many omissions necessary for reasons of national security, as follows:

One of ARDC's eight centers, Patrick Air Force Base in Florida, is the headquarters of the Missile Test Center. The German V-1 and V-2 of World War II opened a new dimension of warfare—and perhaps ultimately of transporta-

tion. Laboratory models of improved guided missiles are now being developed. They need to be tested and evaluated. Some of these missiles are launched over a long-range proving ground. The present length of the range is 1,000 miles. Observation posts in the Bahamas and West Indies are strategically located to observe and record the flight and behavior of the passing missile.

(It is a curious aside, not exactly pertinent to the general subject of this article, yet most interesting and curious, that in the preparation of the Air Force Missile Test Center the Atomic Age and the Stone Age met face to face. The population of some of the remoter islands is extremely primitive in culture, substantially neolithic. To enlist their cooperation and goodwill—and to avoid scaring them half to death with passing missiles—teams of American technicians toured the island and gave the troglodyte inhabitants elementary lectures on jet propulsion, radar and aerodynamics!)

The science of electronics launches these missiles, reports and records their behavior in flight, destroys them in flight if necessary and times everything that happens to a millisecond. From the records thus created the science of electronics computes the data the engineers need in order to built better missiles.

Electronics also provides the communications that knit together all the bases, posts and stations of a thousand-mile long range, linking the whole into a single integrated unit as taut and controlled as a regiment on dress parade.

Timing begins with an electronic clock. Millisecond pulses are communicated by uhf radio to every post and operative position along the range. The range is radar-scanned for safety and ships in dangerous locations are warned by low-flying planes equipped

with loudspeakers. All posts are alerted to each step in the sequence of operations by voice and report by voice to the central control.

When all is ready, the missile is electronically launched from a control center located a mile distant from the launching pad. High-speed motion-picture cameras, some of them automatically controlled by electronic devices, photograph missile behavior in flight. Simultaneously these cameras record the millisecond timing signals along one edge of the film so that every aspect and phenomenon of the missile's behavior can be timed to 1/1,000 second from zero time.

As the missile proceeds down range its subsequent behavior is recorded in three ways—motion-picture cameras, radar and telemetering. A telemetering transmitter in the nose of the missile sends coded flight data. This information is in the form of a frequency-modulated subcarrier which is frequency-modulated upon a uhf carrier. This double modulation is called commutation; stripping the information from the double carriers is called decommutation. Electronic equipment currently used for telemetering at the Air Force Missile Test Center permits simultaneous transmission of 12-15 channels, some of which may be commutated with as many as 27 data channels each.

The data received by telemetered transmission are recorded on both oscillographs and magnetic tape. The data recorded by the motion-picture cameras (some of them operating as rapidly as 600 frames per second as against the ordinary rate of 24) exist on the developed film in the form of photographic images and lines of timing dots. Telemetered data, film data and data derived from radar tracking, all need to be mathematically evaluated.

Human beings could not handle the job; an army of mathematicians would be needed. The work is done by electronic mathematicians—digital computers, telereaders, automatic printing calculators—thousand-tube electronic circuits that remember and think.

The appearance of some of this incredible mathematical equipment resembles fantastic illustrations out of science-fiction magazines. Yet the personnel, uniformed and civilian, who operate and maintain it, are not necessarily mathematically trained. Most of them are trained only in electronics in general and the specific machine they operate in particular. They use standard electronics procedures and facilities. Their multimeters, oscilloscopes, signal generators, tube testers and the like are much the same—sometimes the same make and model—as in any crossroads radio repair shop. Their basic techniques of maintenance and testing are much the same. Buck Rogers obeys Ohm's law. The electronic skills that are taught in the Air Force may later be applied to repair a television portable. END



Air Force mobile radar installation.

# Heathkits

FOR THE ENTIRE ELECTRONICS INDUSTRY

more than 65 top-quality models to choose from, including such outstanding kit designs as . . . .

AMATEUR RADIO



RADIO & TV SERVICEMEN



THE  
WORLD'S LEADING  
MANUFACTURER  
OF ELECTRONIC  
KITS . . .



INDUSTRIAL LABORATORIES

TRAINING SCHOOLS

HI-FI ENTHUSIASTS



**V-7A VACUUM TUBE VOLTMETER:** Easily the world's largest selling VTVM. Features peak-to-peak scales—etched metal circuit board—1% precision resistors—full wave rectifier and AC input circuit—reads rms and peak-to-peak AC, DC, and ohms.

**O-10 LABORATORY TYPE OSCILLOSCOPE:** The world's largest selling oscilloscope kit, and the most successful oscilloscope in history. Designed especially for color and black-and-white TV service work. Its 5 megacycle bandwidth and new 500 Kc sweep generator readily qualify it for laboratory applications. Features easy-to-assemble etched metal circuit board construction.

**WA-P2 HIGH FIDELITY PREAMPLIFIER:** This is the world's largest selling hi fi preamplifier kit. Features complete equalization, 5 separate switch-selected inputs with individual pre-set level controls, beautiful modern appearance, high-quality components.

**HIGH FIDELITY AMPLIFIERS:** Five Heathkit Models to choose from at prices ranging from \$16.95 to \$59.75. Power output range from 7 to 25 watts.

**DX-100 TRANSMITTER:** A 100 watt phone and CW ham transmitter, offering the greatest dollar value available in the ham radio field today.

*Greatest Dollar Value Through Factory-To-You Selling!*

# Heathkits

**ONLY HEATHKITS CAN GIVE YOU ALL OF THESE DISTINCTIVE ADVANTAGES!**


- *The Most Complete Construction Manuals for Easy Assembly.*
- *Originality of Design—Developed Through Pioneering in the Kit Instrument Field.*
- *Greatest Dollar Value—Finest Quality with Real Economy.*
- *Direct Contact with Manufacturer—Lower Price, Guaranteed Performance.*
- *Etched Metal, Prewired Circuit Boards—Save Construction Time, Improve Performance.*
- *High Quality Standard Components for Long-Life Service,*

**HEATH COMPANY**

*A Subsidiary  
of Daystrom, Inc.*

**BENTON HARBOR 20, MICHIGAN**



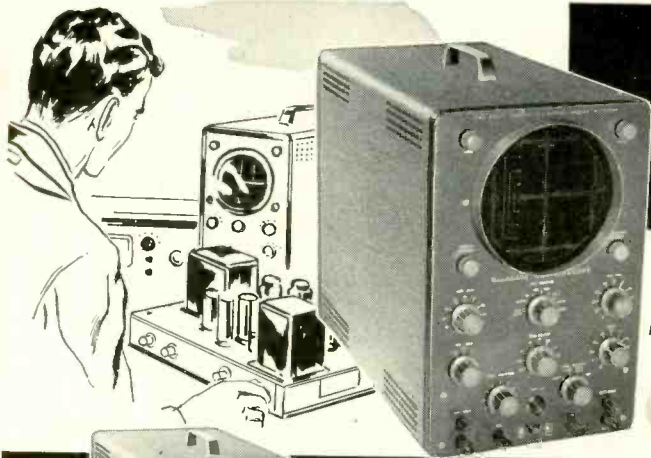

there is no substitute for  
**HEATHKIT QUALITY**


**YOU GET MORE:** All first-run, top quality parts —the latest in electronic design—complete and comprehensive step-by-step assembly instructions with large pictorial diagrams and assembly drawings. Proven performance through the production of thousands of kits.

MODEL O-10

1



2

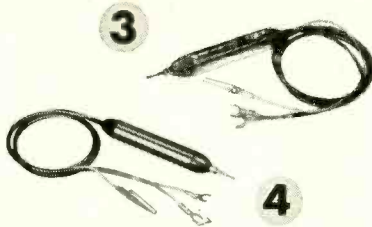

3

4



5

**1** *Heathkit* ETCHED CIRCUIT  
COLOR-TV  
**5" OSCILLOSCOPE KIT**

This deluxe quality oscilloscope has proven itself through thousands of operating hours in service shops and laboratories. Features the best in components—and the best in circuit design.

Features amplifier response to 5 Mc for color TV work, and employs the radically new sweep circuit to provide stable operation up to 500,000 cps. In addition, etched metal, pre-wired circuit boards cut assembly time almost in half, and permit a level of circuit stability never before achieved in an oscilloscope of this type.

Vertical amplifiers flat within +2 db -5 db from 2 cps to 5 Mc, down only 1½ db at 3.58 Mc. Vertical sensitivity is 0.025 volts, (rms) per inch at 1 Kc. 11 tube circuit employs a 5U1 CRT.

Plastic molded capacitors used for coupling and bypass—preformed and cabled wiring harness provided.

Features built-in peak-to-peak calibrating source—retrace blanking amplifier—push-pull amplifiers and step-attenuated input.

MODEL O-10

**\$6950**

Shpg. Wt. 21 lbs.

**2** *Heathkit* ETCHED CIRCUIT  
**5" OSCILLOSCOPE KIT**

This is a general purpose oscilloscope for the more usual applications in the service shop or lab, yet is comparable to scopes costing many dollars more.

Features full size 5" CRT (5BP1), built-in peak-to-peak voltage calibration—3 step input attenuator—phasing control—push-pull deflection amplifiers—and etched metal pre-wired circuit boards.

Vertical channel flat within ±3 db from 2 cps to 200 Kc, with 0.09 V. rms/inch, peak-to-peak sensitivity at 1 Kc. Sweep circuit from 20 cps to 100,000 cps. A scope you will be proud to own and use.

MODEL OM-1

**\$4950**

Shpg. Wt. 21 lbs.

**3** *Heathkit* LOW CAPACITY  
**PROBE KIT**

Scope investigation of circuits encountered in TV requires the use of special low capacity probe to prevent loss of gain, circuit loading, or distortion. This probe features a variable capacitor to provide correct instrument impedance matching. Also the ratio of attenuation can be controlled.

NO. 342

**\$350**

Shpg. Wt. 1 lb.

**4** *Heathkit* ETCHED CIRCUIT  
**SCOPE DEMODULATOR PROBE KIT**

Extend the usefulness of your Oscilloscope by observing modulation envelope of R.F. or I.F. carriers found in TV and radio receivers. Functions like AM detector to pass only modulation of signal and not signal itself. Applied voltage limits are 30 V. RMS and 500 V. DC.

NO. 337-C

**\$350**

Shpg. Wt. 1 lb.

**5** *Heathkit* ETCHED CIRCUIT  
**3" OSCILLOSCOPE KIT**

This compact little oscilloscope measures only 9½" H. x 6½" W. x 11¾" D., and weighs only 11 lbs! Easily employed for home service calls, for work in the field or is just the ticket for use in the ham shack or home workshop. Incorporates many of the features of the Model OM-1, but yet is smaller in physical size for portability.

Employing etched circuit boards, the Model OL-1 features vertical response within ± 3 db from 2 cps to 200 Kc. Vertical sensitivity is 0.25 V. RMS/inch peak-to-peak, and sweep generator operates from 20 cps to 100,000 cps. Provision for r.f. connection to deflection plates for modulation monitoring, and incorporates many features not expected at this price level. 8-tube circuit features a type 3GP1 Cathode Ray Tube.

MODEL OL-1


**\$2950**

Shpg. Wt. 14 lbs.

**HEATH COMPANY** A Subsidiary of Daystrom, Inc. **BENTON HARBOR 20, MICHIGAN**

# fill your test requirements WITH HEATHKITS


DESIGNED FOR YOU: Heath Company test equipment is designed for the maximum in convenience. Besides being functional, Heathkits represent the very latest in modern physical appearance, and incorporate all the latest circuit design features for comprehensive test coverage.

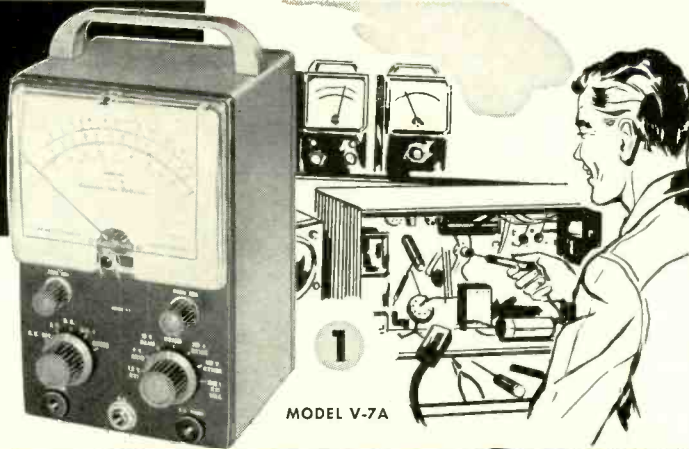

MODEL V-7A



2

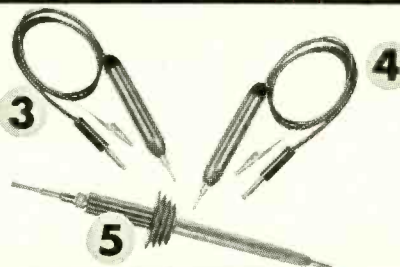

3

4

5

6



## 1 Heathkit ETCHED CIRCUIT VACUUM TUBE VOLT METER KIT

Besides measuring AC (rms), DC and resistance, the modern-design V-7A incorporates peak-to-peak measurement for FM and television servicing.

AC (rms) and DC voltage ranges are 1.5, 5, 15, 50, 150, 500, and 1500. Peak-to-peak AC voltage ranges are 4, 14, 40, 140, 400, 1400, and 4000. Ohmmeter ranges are X1, X10, X100, X1000, X10K, X100K, and X1 megohm. Also a db scale is provided. A polarity reversing switch provided for DC measurements, and zero center operation within range of front panel controls. Employs a 200  $\mu$ a meter for indication. Input impedance is 11 megohms.

Etched metal, pre-wired circuit board for fast, easy assembly and reliable operation is 50% thicker for more rugged physical construction. 1% precision resistors for utmost accuracy.

MODEL V-7A  
**\$24.50**  
Shpg. Wt. 7 lbs.

## 3 Heathkit ETCHED CIRCUIT RF PROBE KIT

The Heathkit RF Probe used in conjunction with any 11 megohm VTVM will permit RF measurements up to 250 Mc with  $\pm 10\%$  accuracy. Uses etched circuits for increased circuit stability and ease of assembly.

NO. 309-C  
**\$3.50**

Shpg. Wt. 1 lb.

## 4 Heathkit ETCHED CIRCUIT PEAK-TO-PEAK PROBE KIT

Now read peak-to-peak voltages on the DC scale of any 11 megohm VTVM with this new probe, employing etched circuit for stability and low loss. Readings made directly from VTVM scales, from 5 Kc to 5 Mc. Not required for Heathkit Model V-7A VTVM.

NO. 338-C  
**\$5.50**

Shpg. Wt. 2 lbs.

## 5 Heathkit 30,000 VOLT D.C. HIGH VOLTAGE PROBE KIT

For TV service work or similar application for measurement of high DC voltage. Precision multiplier resistor mounted inside plastic probe. Multiplication factor of 100 on the ranges of Heathkit 11 megohm VTVM.

NO. 336  
**\$4.50**

Shpg. Wt. 2 lbs.

## 6 Heathkit HANDITESTER KIT

The Model M-1 measures AC or DC voltage at 0-10, 30, 300, 1000, and 5000 volts. Measures direct current at 0-10 ma. and 0-100 ma. Provides ohmmeter ranges of 0-3000 (30 ohm center scale) and 0-300,000 ohms (3000 ohms center scale). Features a 400  $\mu$ a. meter for sensitivity of 1000 ohms/volt. Because of its size, the M-1 is a very handy portable instrument that will fit in your coat pocket, tool box, glove compartment, or desk drawer. Makes a fine standby unit in the service shop when the main instruments are in use, or is ideal for the hobbyist or beginner. An unusual dollar value.

MODEL M-1  
**\$14.50**

Shpg. Wt. 3 lbs.

## 2 Heathkit 20,000 OHMS/VOLT MULTIMETER KIT

The MM-1 is a portable instrument for outside servicing, for field testing, or for quick portability in the service shop. Combines attractive physical appearance with functional design. 20,000 ohms/v. DC, and 5000 ohms/v. AC. AC and DC voltage ranges are 0-1.5, 5, 50, 150, 500, 1500 and 5000 volts. Direct current ranges are 0-150  $\mu$ a., 15 ma., 150 ma., 500 ma., and 15 amperes. Resistance ranges are X1, X100, X10,000 providing center scale readings of 15, 1500 and 150,000 ohms. DB ranges cover -10 db to +65 db.

Features a  $4\frac{1}{2}''$  50  $\mu$ a. meter. Provides polarity reversal on DC measurements. 1% precision resistors used in multiplier circuits. Not affected by RF fields.

MODEL MM-1  
**\$29.50**  
Shpg. Wt. 6 lbs.

**HEATH COMPANY**

A Subsidiary  
of Daystrom, Inc.


**BENTON HARBOR 20, MICHIGAN**



*Heathkit*  
TV ALIGNMENT  
**GENERATOR  
KIT**



1

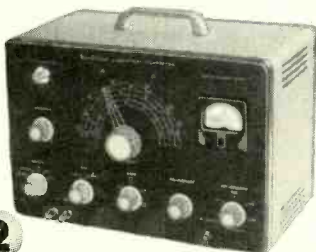

2



3



4

**HEATH  
COMPANY**

A SUBSIDIARY OF DAYSTROM INC.

The Model TS-4 features a controllable inductor for all-electronic sweep, improved oscillator and automatic gain circuitry, high RF output, center sweep operation, and improved linearity. It sets a new high standard for sweep generator operation, and is absolutely essential for the up-to-date service shop doing FM, black-and-white TV, and color TV work.

Voltage regulation and effective AGC action insure flat output over a wide frequency range. Electronic sweep insures complete absence of mechanical vibration. Sweep deviation controllable from 0 up to 40 Mc, depending upon base frequency. Effective two-way blanking.

Fundamental output from 3.6 Mc to 220 Mc in 4 bands. Crystal marker provides markers at 4.5 Mc and multiples thereof. Crystal included with kit. Variable marker covers from 19 Mc to 60 Mc on fundamentals, and up to 180 Mc on harmonics. Provision for external marker.



MODEL TS-4  
**\$49.50**  
Shpg. Wt. 16 lbs.

1

*Heathkit* LINEARITY PATTERN  
**GENERATOR KIT**

The new-design Model LP-1 produces vertical or horizontal bar patterns, a cross-hatch pattern, or white dots on the screen of the TV set under test. No internal connections required. Special clip is attached to the TV antenna terminals. Instant selection of the pattern desired for adjustment of vertical and horizontal linearity, picture size, aspect ratio, and focus. Dot pattern presentation is a *must* for color convergence adjustments on color TV sets.

Extended operating range covers all television channels from 2 to 13. Produces 6 to 12 vertical bars or 4 to 7 horizontal bars.

MODEL LP-1  
**\$22.50**  
Shpg. Wt. 7 lbs.

2

*Heathkit* LABORATORY  
**GENERATOR KIT**

The Heathkit Model LG-1 Laboratory Generator is a high-accuracy signal source for applications where metered performance is essential. It covers from 100 Kc to 30 Mc on fundamentals in 5 bands. Modulation is at 400 cycles, and modulation is variable from 0-50%. RF output from 100,000  $\mu$ v. to 1  $\mu$ v. 200  $\mu$ a. meter reads the RF output in microvolts, or percentage of modulation. Fixed step and variable output attenuation provided.

Features voltage regulation, and double copper plated shielding for stability. Provision for external modulation. Coaxial output cable (50 ohms).

MODEL LG-1  
**\$39.50**  
Shpg. Wt. 16 lbs.

3

*Heathkit* CATHODE RAY  
**TUBE CHECKER KIT**

This new-design instrument holds the key to rapid and complete picture tube testing, either in the set, on the work-bench, or in the carton. Tests for shorts, leakage, and emission. Features Shadow-graph test (a spot of light on the screen) to indicate whether the tube is capable of functioning.

The Model CC-1 tests all electromagnetic deflection picture tubes normally encountered in television servicing. Supplies all operating voltages to the tube under test, and indicates the condition of the tube on a large "GOOD-BAD" scale. Features spring loaded test switches for operator protection.

The CC-1 is housed in an attractive portable case and is light in weight - ideal for outside service calls.

MODEL CC-1  
**\$22.50**  
Shpg. Wt. 10 lbs.

4

*Heathkit* DIRECT READING  
**CAPACITY METER KIT**

Not only is this instrument popular in the service shop, but it has found extensive application in industrial situations. Ideal for quality control work, production line checking, or for matching pairs.

Features direct reading linear scales from 100 mmf to .1 mfd full scale. Necessary only to connect a capacitor of unknown value to the insulated binding posts, select the correct range, and read the meter. The CM-1 is not susceptible to hand capacity, and has a residual capacity of less than 1 mmf.

MODEL CM-1  
**\$29.50**  
Shpg. Wt. 7 lbs.

**BENTON HARBOR 20, MICHIGAN**

RADIO-ELECTRONICS



MODEL SG-8 **\$1950**  
Shpg. Wt. 8 Lbs.

This is one of the biggest signal generator bargains available today. The tried and proven Model SG-8 offers all of the outstanding features required for a basic service instrument. High quality components and outstanding performance.

The SG-8 covers 160 Kc to 110 Mc on fundamentals in 5 bands, and calibrated harmonics extend its usefulness up to 220 Mc. The output signal is modulated at 400 cps, and the RF output is in excess of 100,000 uv. Output controlled by both a continuously variable and a fixed step attenuator. Also, audio output may be obtained for amplifier testing. Don't let the

low price deceive you. This is a professional type service instrument to fulfill the signal source requirements in the service lab.

### 1 *Heathkit* . . . IMPEDANCE BRIDGE KIT

The IB-2 features built-in adjustable phase shift oscillator and amplifier, and has panel provisions for external generator. Measures resistance, capacitance, inductance, dissipation factors of condensers, and storage factor of inductance.

D, Q, and DQ functions combined in one control. 1/2% resistors and 1/2% silver-mica capacitors especially selected for this instrument. A 100-0-100 microammeter provides null indications. Two-section CRL dial provides 10 separate "units" with an accuracy of .5%. Fractions of units read on variable control.

MODEL IB-2 **\$5950**  
Shpg. Wt. 12 Lbs.

### 2 *Heathkit* "Q" METER KIT

The Heathkit Model QM-1 will measure the Q of inductances and the RF resistance and distributed capacity of coils. Employs a 4 1/2" 50 microampere meter for direct indication. Will test at frequencies of 150 Kc to 18 Mc in 4 ranges. Measures capacity from 40 mmf to 450 mmf within ± 3 mmf. Indispensable for coil winding and determining unknown condenser values. A worthwhile addition to your laboratory at an outstandingly low price. Useful for checking wave traps, chokes, peaking coils, etc. Laboratory facilities are now available to the service shop and home lab.

MODEL QM-1 **\$4450**  
Shpg. Wt. 14 Lbs.

### 3 *Heathkit* 6-12 VOLT BATTERY ELIMINATOR KIT

This modern battery eliminator will supply 6 or 12 volt output for ordinary automobile radios as well as 12 volts for the new models in the latest model cars. Output voltage is variable from 0-8 volts DC, or 0-16 volts DC. Will deliver up to 15 amperes at 6 volts, or up to 7 amperes at 12 volts. Two 10,000 microfarad filter capacitors insure smooth DC output. Two panel meters monitor output voltage and current. Will double as a battery charger. Definitely required for automobile radio service work.

MODEL BE-4 **\$3150**  
Shpg. Wt. 17 Lbs.

### 4 *Heathkit* DECADE RESISTANCE KIT

Twenty 1% precision resistors provide resistance from 1 to 99,999 ohms in 1 ohm steps. Indispensable around service shop laboratory, ham shack, or home workshop. Well worth the extremely low Heathkit price.

MODEL DR-1 **\$1950**  
Shpg. Wt. 4 Lbs.

### 5 *Heathkit* VIBRATOR TESTER KIT

Tests vibrators for proper starting and indicates the quality of the output on a large "GOOD-BAD" scale. Checks both interrupter and self-rectifier types in 5 different sockets. Operates from any battery eliminator delivering variable voltage from 4 to 6 volts DC at 4 amps. Ideal companion to the Model BE-4.

MODEL VT-1 **\$1450**  
Shpg. Wt. 6 Lbs.

### 6 *Heathkit* DECADE CONDENSER KIT

Provides capacity values from 100 mmf to 0.111 mfd in steps of 100 mmf. ± 1% precision silver-mica condensers used. High quality ceramic switches for reduced leakage. Polished birch cabinet. Extremely valuable in all electronic activity.

MODEL DC-1 **\$1650**  
Shpg. Wt. 3 Lbs.

# Heathkit SIGNAL GENERATOR KIT



1



2



3



5



4



6


# HEATH COMPANY

A SUBSIDIARY OF DAYSTROM INC.

BENTON HARBOR 20, MICHIGAN



# Heathkit TUBE CHECKER KIT

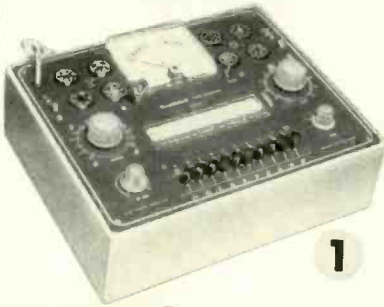

1

1 The Heathkit Model TC-2 is an emission type tube tester that represents a tremendous saving over the price of a comparable unit from any other source. At only \$29.50, you can have a tube tester of your own, even if you are an experimenter, or only do part time service work. Extremely popular with radio servicemen, it uses a 4½" meter with 3-color meter face for simple "GOOD-BAD" indications that the customer can understand. Will test all tubes commonly encountered in radio and TV service work.

Ten 3-position lever switches for "open" or "short" tests on each tube element. Neon bulb indicates filament continuity or short between tube elements. Line adjust control provided. The roll chart is illuminated.

Sockets provided for 4, 5, 6, and 7-pin, octal, and loctal tubes, 7 and 9 pin miniature tubes, and the 5 pin Hytron tubes. Blank space provided for future socket addition. Tests tubes for opens, and shorts, and for quality on the basis of total emission. 14 different filament voltage values provided.

MODEL TC-2  
**\$29.50**  
Shpg. Wt. 12 Lbs.

## 2 Heathkit PORTABLE TUBE CHECKER KIT

The Model TC-2P is identical to the Model TC-2 except that it is housed in a rugged carrying case. This strikingly attractive and practical two-tone case is finished in proxylin impregnated fabric. The cover is detachable, and the hardware is brass plated. This case imparts a real professional appearance to the instrument. Ideal for home service calls, or any portable application.

MODEL TC-2P  
**\$34.50**  
Shpg. Wt. 15 Lbs.



3

2

## 3 Heathkit TV PICTURE TUBE TEST ADAPTER

The Heathkit TV picture tube test adapter is designed for use with the Model TC-2 Tube Checker. Test picture tubes for emission, shorts, and thereby determine tube quality. Consists of 12-pin TV tube socket, 4 ft. cable, octal connector, and necessary technical data. (Not a kit.)

MODEL 355  
**\$4.50**  
Shpg. Wt. 1 Lb.

## 4 Heathkit . . . CONDENSER CHECKER KIT

Use this Condenser Checker to quickly and accurately measure those unknown condenser and resistor values. All readings taken directly from the calibrated panel scales without any involved calculation. Capacity measurements in four ranges from .0001 to 1000 mfd. Checks paper, mica, ceramic and electrolytic condensers. A power factor control is available for accurate indication of electrolytic condenser efficiency. Leakage test switch—selection of five polarizing voltages, 25 volts to 450 volts DC to indicate condenser operating quality under actual load conditions. Spring-return test switch automatically discharges condenser under test and eliminates shock hazard to the operator.

Resistance measurements can be made in the range from 100 ohms to 5 megohms. Here again, all values are read directly on the calibrated scales. Increased sensitivity coupled with an electron beam null indicator increases overall instrument usefulness.

For safety of operation, the circuit is entirely transformer operated. An outstanding low kit price for this surprisingly accurate instrument.

MODEL C-3  
**\$19.50**  
Shpg. Wt. 7 Lbs.



4

## 5 Heathkit VISUAL-AURAL SIGNAL TRACER KIT

This signal tracer is extremely valuable in servicing AM, FM, and TV receivers, especially when it comes to isolating trouble to a particular stage of the circuit under test.

This visual-aural tracer features a high gain RF input channel to permit signal tracing from the receiver antenna input clear through all RF, IF, detector, and audio stages to the speaker. Separate low-gain channel provided for audio circuit exploration. Both visual and aural indication by means of a speaker or headphone, and electron beam "eye" tube as a level indicator. Also incorporates a noise locator circuit for DC noise checks, and a built-in calibrated wattmeter (30-500 watts). Panel terminals provided for "patching" output transformer or speaker into external circuit for test purposes. Designed especially for the radio and TV serviceman. Cabinet size: 9½" wide x 6½" high x 5" deep. A real test equipment bargain.

MODEL T-3  
**\$23.50**  
Shpg. Wt. 9 Lbs.



5

**HEATH  
COMPANY**  
A SUBSIDIARY OF DAYSTROM INC.

BENTON HARBOR 20, MICHIGAN

RADIO-ELECTRONICS



MODEL HD-1

Shpg. Wt. 13 Lbs. **\$4950**

Used with a sine wave generator, the Model HD-1 will check the harmonic distortion output of audio amplifiers under a variety of conditions. Reads distortion directly on the meter as a percentage of the input signal. Operates between 20 and 20,000 cps. High impedance VTVM circuit for initial reference settings and final distortion readings. Ranges are 0-1, 3, 10, and 30 volts full scale. 1% precision resistors. Distortion scales are 0-1, 3, 10, 30 and 100% full scale. Requires only 3 volt input for distortion test.

# Heathkit HARMONIC DISTORTION METER KIT

## 1 Heathkit AUDIO ANALYZER KIT

This instrument consists of an audio wattmeter, an AC VTVM, and a complete IM analyzer, all in one compact unit.

Use the VTVM to measure noise, frequency response, output gain, power supply ripple, etc. Use the wattmeter for measurement of power output. Internal loads provided for 4, 8, 16, or 600 ohms. VTVM also calibrated for DBM units. High or low impedance IM measurements made with built-in 6KC and 60 cps generators. VTVM ranges are .01, to 300 volts in 10 steps. Wattmeter ranges are .15 mw. to 150 w. in 7 steps. IM scales are 1% to 100% in 5 steps.

MODEL AA-1

**\$5950**

Shpg. Wt. 13 Lbs.



1

## 2 Heathkit AUDIO GENERATOR KIT

This new Heathkit Model features step-tuning from 10 cps to 100 Kc with three rotary switches that provide two significant figures and multiplier. Less than .1% distortion. Frequency accurate to within  $\pm 5\%$ .

Output monitored on a large  $4\frac{1}{2}$ " meter that reads voltage or db. Both variable and step-type attenuation provided. Meter reads zero-to-maximum at each attenuator position. Output ranges (and therefore meter ranges) are 0-.003, .01, .03, .1, .3, 1, 3, 10 volts. Step-tuning provides rapid positive selection of the desired frequency, and allows accurate return to any given frequency.

MODEL AG-9

**\$3450**

Shpg. Wt. 8 Lbs.



2

## 3 Heathkit AUDIO OSCILLATOR KIT


(SINE WAVE — SQUARE WAVE)

The Model AO-1 features sine wave or square wave coverage from 20-20,000 cps in 3 ranges. It is an instrument specifically designed to completely fulfill the needs of the serviceman and high fidelity enthusiast. Offers high level output across the entire frequency range, low distortion and low impedance output. Features a thermistor in the second amplifier stage to maintain essentially flat output through the entire frequency range. Produces an excellent sine wave for audio testing, or will produce good, clean, square waves with a rise time of only 2 microseconds.

MODEL AO-1

**\$2450**

Shpg. Wt. 10 Lbs.

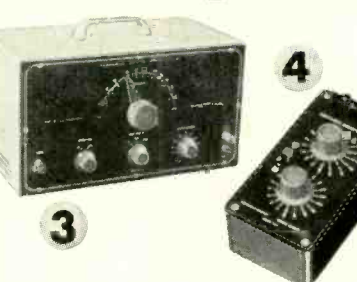

4


## 4 Heathkit RESISTANCE SUBSTITUTION BOX KIT...

Provides switch selection of 36 RTMA 1 watt standard 1% resistors ranging from 15 ohms to 10 megohms. Numerous applications in radio and TV work, and essential in the developmental laboratory.

MODEL RS-1

**\$550**

Shpg. Wt. 2 Lbs.

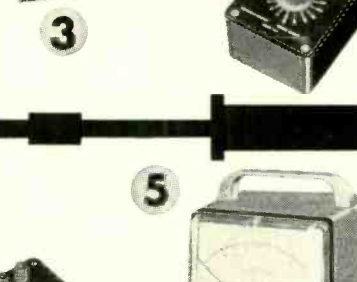

3

## 5 Heathkit AC VACUUM TUBE VOLTMETER KIT...

The Heathkit AC VTVM features high impedance, wide frequency range, very high sensitivity, and extremely wide voltage range. Will accurately measure a voltage as small as 1 mv. at high impedance. Excellent for sensitive AC measurements required by laboratories, audio enthusiasts and experimenters. Frequency response is substantially flat from 10 cps to 50 Kc. Ranges are .01, .03, .1, .3, 1, 3, 10, 30, 100, and 300 v. RMS. Total db range -52 to + 52 db. Input impedance 1 megohm at 1 Kc.

MODEL AV-2

**\$2950**

Shpg. Wt. 5 Lbs.



5


## 6 Heathkit CONDENSER SUBSTITUTION BOX KIT...

Very popular companion to Heathkit RS-1. Individual selection of 18 RTMA standard condenser values from .0001 mfd to .22 mfd. Includes 18" flexible leads with alligator clips.

MODEL CS-1

**\$550**

Shpg. Wt. 2 Lbs.

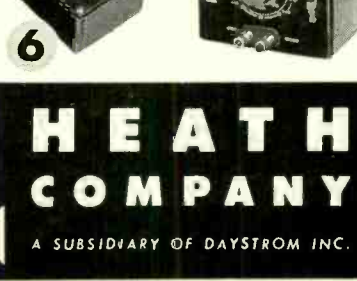


6

# HEATH COMPANY

A SUBSIDIARY OF DAYSTROM INC.

BENTON HARBOR 20, MICHIGAN



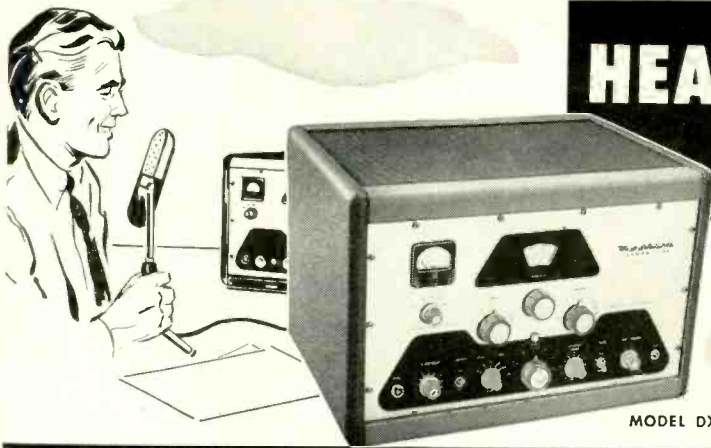

# HEATHKIT HAM GEAR

for high quality at moderate cost

**DOLLAR VALUE:** You get more for your Heathkit dollar because your labor is used to build the kit instead of paying for someone else's. Also, the middleman's margin of profit is eliminated when you deal directly with the manufacturer.

MODEL DX-100



2



3



4

## 1 Heathkit DX-100 PHONE & CW TRANSMITTER KIT

The reception given this amateur transmitter has been tremendous. Reports from radio amateurs using the DX-100 are enthusiastic in praising its performance and the high quality of the components used in its assembly. Actual "on the air" results reflect the careful design that went into its development.

The DX-100 features a built-in VFO, modulator, and power supplies, and is completely bandswitching for phone or CW operation on 160, 80, 40, 20, 15, 11, and 10 meters. All parts necessary for construction are supplied in the kit, including tubes, cabinet, and detailed step-by-step instructions. Easy to build, and a genuine pleasure to operate.

Employs push-pull 1625's modulating parallel 6146's for RF output in excess of 100 watts on phone and 120 watts on CW. May be excited from the built-in VFO or from crystals (crystals not included with kit). Features five-point TVI suppression: (1) pi network interstage coupling to reduce harmonic transfer to the final stage; (2) pi network output coupling; (3) extensive shielding; (4) all incoming and outgoing circuits filtered; (5) inter-locking cabinet seams to eliminate radiation except through the coaxial output connector. Pi network output coupling will match 50 to 600 ohm non-reactive load. Illuminated VFO dial and meter face. Remote control socket provided.

The chassis is made of extra-strong #16 gauge copper-plated steel. It employs potted transformers, ceramic switch and variable capacitor insulation, solid silver loading switch terminals, and high-grade well-rated components throughout. Features a pre-formed wiring harness, and all coils are pre-wound.

High-gain speech amplifier for dynamic or crystal microphones, and restricted speech range for increased intelligence. Plenty of audio power reserve. Measures 20 7/8" W. x 13 3/4" H. x 16" D. Schematic diagram and complete technical specifications on request.

MODEL DX-100  
**\$189<sup>50</sup>**

Shpg. Wt. 120 Lbs.

Shipped Motoc Freight Unless Otherwise Specified  
\$50.00 Deposit Required on C.O.D. Orders

## 2 Heathkit VFO KIT

The Model VF-1 covers 160-80-40-20-15-11 and 10 meters with three basic oscillator frequencies. Better than 10-volt average RF output on fundamentals. Features illuminated and pre-calibrated dial scale. Cable and plug provided to fit crystal socket of any modern transmitter.

Enjoy the convenience and flexibility of VFO operation at no more than the price of crystals. May be powered from plug on the Heathkit Model AT-1 transmitter, or supplied with power from most transmitters. Measures: 7" H. x 6 1/2" W. x 7" D.

MODEL VF-1  
**\$19<sup>50</sup>**

Shpg. Wt. 7 Lbs.

## 3 Heathkit CW AMATEUR TRANSMITTER KIT

The Model AT-1 is an ideal novice transmitter, and may be used to excite a higher power rig later on.

This CW transmitter is complete with its own power supply, and covers 80, 40, 20, 15, 11, and 10 meters. Features single-knob bandswitching, and panel meter indicates grid or plate current for the final amplifier. Designed for crystal operation or external VFO. Crystal not included in kit. Incorporates such features as key click filter, line filter, copper-plated chassis, pre-wound coils, 52 ohm coaxial output, and high quality components throughout. Instruction book simplifies assembly. Employs a 6AG7 oscillator, 6L6 final amplifier. Operates up to 35 watts plate power input.

MODEL AT-1  
**\$29<sup>50</sup>**

Shpg. Wt. 15 Lbs.

## 4 Heathkit . . . ANTENNA COUPLER KIT

The Model AC-1 will properly match your low power transmitter to an end-fed long wire antenna. Also attenuates signals above 36 Mc, reducing TVI. 52 ohm coax. input—power up to 75 watts—10 through 80 meters—tapped inductor and variable condenser—neon RF indicator—copper plated chassis and high quality components. Ideal for use with Heathkit AT-1 Transmitter.

MODEL AC-1  
**\$14<sup>50</sup>**

Shpg. Wt. 4 Lbs.

**HEATH COMPANY**

A Subsidiary  
of Daystrom, Inc.

**BENTON HARBOR 20, MICHIGAN**

# "AMATEUR-ENGINEERED"

## Equipment For The Ham

MODERN DESIGN: You can be sure of getting all the latest and most desirable design features when you buy Heathkits. Advanced-design is a minimum standard for new Heathkit models.



1

MODEL AR-3



2



3



4



5

### 1 Heathkit COMMUNICATIONS-TYPE ALL BAND RECEIVER KIT

The new Model AR-3 features improved IF and RF performance, along with better image rejection on all bands. Completely new chassis layout for easier assembly, even for the beginner.

Covers 550 Kc to 30 Mc in four bands. Provides sharp tuning and good sensitivity over the entire range. Features a transformer-type power supply—electrical bandspread—separate RF and AF gain controls—antenna trimmer—noise limiter—AGC—BFO—headphone jacks—5½" PM speaker and illuminated tuning dial.

CABINET: Fabric covered cabinet with aluminum panel as shown. Part No. 91-15, shipping weight 5 lbs. \$4.50.

MODEL AR-3  
**\$27<sup>95</sup>**

Shpg. Wt. 12 Lbs.  
(Less Cabinet)

### 2 Heathkit "Q" MULTIPLIER KIT

Here is the Heathkit Q Multiplier you hams have been asking for. A tremendous help on the phone and CW bands when the QRM is heavy. Provides an effective Q of approximately 4,000 for extremely sharp "peak" or "null." Use it to "peak" the desired signal or to "null" an undesired signal, or heterodyne. Tunes to any signal within the IF band-pass of your receiver. Also provides "broad peak" for conditions where extreme selectivity is not required.

Operates with any receiver having an IF frequency between 450 and 460 Kc. Will not function with AC-DC type receivers. Requires 6.3 volts AC at 300 ma. and 150 to 250 VDC at 2 ma. Derives operating power from your receiver. Uses a 12AX7 tube, and special High-Q shielded coils. Simple to connect with the cable and plugs supplied. Measures only 4-11/16"H.x7¾"W.x4½"D. A really valuable addition to the receiving equipment in your ham shack.

MODEL QF-1  
**\$9<sup>95</sup>**

Shpg. Wt. 3 Lbs.

### 3 Heathkit VARIABLE VOLTAGE REGULATED POWER SUPPLY KIT

Provides well filtered DC output, variable from zero to 500 volts at no load and regulated for stability. Will supply up to 10 ma. at 450 VDC, and up to 130 ma. at 200 VDC. Voltage or current monitored on front panel meter. Also provides 6.3 VAC at 4A. for filament. Filament voltage isolated from B+, and both isolated from ground. Invaluable around the ham shack for supplying operating potentials to experimental circuits. Use in all types of research and development laboratories as a temporary power supply, and to determine design requirements for ultimate power supply.

MODEL PS-3  
**\$35<sup>50</sup>**

Shpg. Wt. 17 lbs.

### 4 Heathkit ANTENNA IMPEDANCE METER KIT

Use in conjunction with a signal source for measuring antenna impedance, line matching, adjustment of beam and mobile antennas, etc. Will double as a phone monitor or relative field strength indicator. 100 µa. meter employed. Covers the range from 0-600 ohms. An instrument of many uses for the amateur.

MODEL AM-1  
**\$14<sup>50</sup>**

Shpg. Wt. 2 lb.

### 5 Heathkit GRID DIP METER KIT

This is an extremely valuable tool for accomplishing literally hundreds of jobs on all types of equipment. Covering from 2 Mc to 250 Mc, the GD-1B is compact and can be operated with one hand. Uses a 500 µa. meter for indication, with a sensitivity control and headphone jack. Includes prewound coils and rack. Indispensable instrument for hams, engineers, or servicemen.

MODEL GD-1B  
**\$19<sup>50</sup>**

Shpg. Wt. 4 lbs.

**HEATH COMPANY** A Subsidiary of Daystrom, Inc. **BENTON HARBOR 20, MICHIGAN**



*Heathkits*  
 PROVIDE THE  
 "CONSTRUCTIVE"  
 APPROACH TO  
**HIGH-FIDELITY**



**EASY TO BUILD:** *The assembly instructions supplied with Heathkits are so complete and detailed that anyone can assemble the kits without difficulty. Plenty of pictorial diagrams and step-by-step instructions. Information on resistor color codes, soldering, use of tools, etc. Build-it-yourself with confidence!*



**1** *Heathkit* **ADVANCED-DESIGN  
 HIGH FIDELITY AMPLIFIER KIT**

The 25 Watt Model W-5 is one of the most outstanding high fidelity amplifiers available today—at any price. Incorporates the very latest design features to achieve true "presence" for the super-critical listener.

Features a new-design Peerless output transformer, and KT66 output tubes handle power peaks up to 42 watts. The unique "tweeter-saver" suppresses high frequency oscillation. A new type balancing circuit results in closer "dynamic" balance between output tubes. Features improved phase shift characteristics and frequency response, with reduced IM and harmonic distortion. Color styling harmonizes with the Heathkit WA-P2 Preamplifier and the FM-3 Tuner.

Frequency response—within  $\pm 1$  db from 5 cps to 160 Kc at 1 watt. Harmonic distortion only 1% at 25 watts, 20-20,000 cps. IM distortion only 1% at 20 watts, using 60 and 3,000 cps. Output impedance 4, 8, or 16 ohms. Hum and noise—99 db below rated output. Uses two 12L.U7's, two KT66's and a 5R4GY.


**KIT COMBINATIONS:**

W-5M Amplifier Kit: Consists of main amplifier and power supply, all on one chassis. Complete with all necessary parts, tubes, and comprehensive manual. Shpg. Wt. 31 lbs. Express only.

**\$59<sup>75</sup>**

W-5 Combination Amplifier Kit: Consists of W-5M Amplifier Kit listed above plus Heathkit Model WA-P2 Preamplifier Kit. Complete with all necessary parts, tubes, and construction manuals. Shpg. Wt. 38 lbs. Express only.

**\$79<sup>50</sup>**

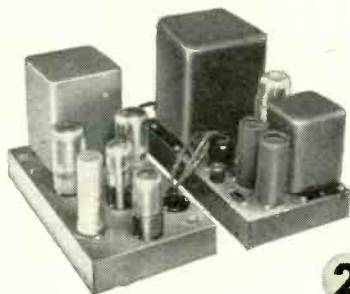

**2** *Heathkit* **DUAL-CHASSIS WILLIAMSON TYPE  
 HIGH FIDELITY AMPLIFIER KIT**

This is a very popular high fidelity amplifier kit that features dual-chassis type construction. The resulting physical dimensions offer an additional margin of flexibility in installation. It features the famous Acrosound TO-300 "ultra-linear" output transformer, and has a frequency response within  $\pm 1$  db from 6 cps to 150 Kc at 1 watt. Harmonic distortion only 1% at 21 watts. IM distortion at 20 watts only 1.3% at 60 and 3,000 cps. Rated power output is 20 watts. Output impedance 4, 8, or 16 ohms. Hum and noise—88 db below 20 watts. Uses two 6SN7's, two 5881's, and a 5V4G.

**KIT COMBINATIONS:**

W-3M: Consists of main amplifier and power supply for separate chassis construction. Includes all tubes and components necessary for assembly. Shpg. Wt. 29 lbs., Express only.

**\$49<sup>75</sup>**

W-3: Consists of W-3M Kit listed above plus Heathkit Model WA-P2 Preamplifier described on opposite page. Shpg. Wt. 37 lbs., Express only.

**\$69<sup>50</sup>**



**3** *Heathkit* **SINGLE-CHASSIS WILLIAMSON TYPE  
 HIGH FIDELITY AMPLIFIER KIT**

This is the lowest priced Williamson type amplifier ever offered in kit form, and yet it retains all the usual features of the Williamson type circuit. Main amplifier and power supply combined on one chassis, and uses a new-design Chicago output transformer. Frequency response—within  $\pm 1$  db from 10 cps to 100 Kc at 1 watt. Harmonic distortion only 1.5% at 20 watts. IM distortion at rated output, 2.7% at 60 and 3,000 cps. Rated power output is 20 watts. Output impedance 4, 8, or 16 ohms. Hum and noise—95 db below 20 watts. Uses two 6SN7's, two 5881's, and one 5V4G.

Instructions are so complete that the kit may be assembled successfully even by a beginner in electronics.

**KIT COMBINATIONS:**

W-4AM: Consists of main amplifier and power supply for single chassis construction. Includes all tubes and components necessary for assembly. Shpg. Wt. 28 lbs. Express only.

**\$39<sup>75</sup>**

W-4A: Consists of W-4AM Kit listed above plus Heathkit Model WA-P2 Preamplifier described on opposite page. Shpg. Wt. 35 lbs. Express only.

**\$59<sup>50</sup>**

**HEATH  
 COMPANY**

A SUBSIDIARY OF DAYSTROM INC.

**BENTON HARBOR 20, MICHIGAN**

RADIO-ELECTRONICS

**ATTRACTIVELY STYLED:** *Heathkit high fidelity instruments are not only functional, but are most attractive in physical design. Such units as the preamplifier and the W-5 main amplifier are designed for beauty as well as performance. They blend with any room decor and are the kind of instruments you will be proud to own.*



*enjoy...*  
**THE VERY BEST  
 IN AUDIO WITH  
 "BUILD-IT-YOURSELF"  
 HEATHKITS**

**1** *Heathkit* HIGH FIDELITY  
**PREAMPLIFIER KIT**


This outstanding preamplifier is designed specifically for use with the Heathkit Williamson type amplifiers. It completely fulfills the requirements for remote control, compensation and preamplification, and exceeds even the most rigorous specifications for high fidelity performance.

Features five separate switch-selected input channels (2 low level and 3 high level), each with its own input control. Full record equalization with four-position turnover control and four-position rolloff control.

Output jack for tape recorder — separate bass control with 18 db boost and 12 db cut at 50 cps. — treble control offering 15 db boost and 20 db cut at 15,000 cps — special hum control to insure minimum hum level — and many other desirable features. Overall frequency response (with controls set to "flat" position) is within 1 db from 25 cps to 30,000 cps. Will do justice to the finest available program sources. Beautiful satin-gold finish.

Power requirements from the Heathkit Williamson type high fidelity amplifier — 6.3 VAC at 1 amp., and 300 VDC at 10 Ma. Uses two 12AX7's and one 12AU7.

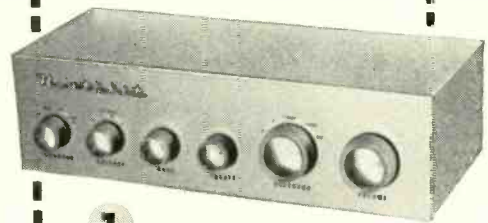MODEL WA-P1  
**\$1975**  
 Shpg. Wt. 7 Lbs.




**1**

**2** *Heathkit* 20-WATT HIGH FIDELITY  
**AMPLIFIER KIT**

This Heathkit Model offers you the least expensive route to high fidelity performance. Frequency response is  $\pm 1$  db from 20-20,000 cps. Features full 20 watt output using push-pull 6L6's, and incorporates separate bass and treble tone controls. Preamplifier and main amplifier are built on the same chassis. Four switch-selected compensated inputs and separate bass and treble tone controls provide all necessary functions at minimum investment. Features miniature tube types for low hum and noise.

Uses 12AX7, two 12AU7's, two 6L6G's and a 5V4G. A most interesting "build-it-yourself" project, and an excellent hi-fi amplifier for home use. Well suited, also, for public address applications because of its high power output and high quality audio reproduction. Another Heathkit "best-buy" for you!

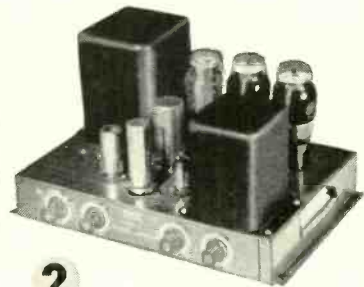MODEL A-9B  
**\$3550**  
 Shpg. Wt. 23 Lbs.



**2**

**3** *Heathkit* 7 - WATT  
**AMPLIFIER KIT**

The redesigned Model A-7D features a new type output transformer for tapped screen operation, and provides improved sensitivity, reduced distortion, and increased power output.

The full 7-watt output of the Model A-7D is more than adequate for normal home installations. Frequency characteristics are  $\pm 1\frac{1}{2}$  db from 20 to 20,000 cps. Potted output and power transformers employed. Push-pull output — detailed construction manual — top quality parts — high quality audio without great expense. Output transformer tapped at 4, 8, and 16 ohms. Bass and treble tone controls provided on the front chassis apron.

MODEL A-7D  
**\$1695**  
 Shpg. Wt. 10 Lbs.

Model A-7E: Provides a preamplifier stage with two switch-selected inputs and RIAA compensation for variable reluctance or low level cartridges. Preamplifier built on same chassis as main amplifier. Model A-7E. Shipping weight 10 lbs. \$18.50.



**3**

**BENTON HARBOR 20, MICHIGAN**

JUNE, 1956

**HEATH  
 COMPANY**  
 A SUBSIDIARY OF DAYSTROM INC.





# CIVIL DEFENSE RADIATION METER

*Compact instrument measures heavy radioactivity*

By EDWIN N. KAUFMAN

In the event an atomic bomb bursts over your city it would be a good idea for you to know the extent of radiation remaining after the blast to protect your family and self. We will assume that your location is far enough from "ground zero" to prevent serious injury but that insufficient personnel and radiation instruments will be available to advise you of rescue, staying put or evacuation hazards.

Emergency wartime exposure to nuclear radiation is permitted at a whole body dose of 25 roentgens per day (*one day a week*) for eight total exposures. In an extreme emergency a 100-roentgen dose either in 1 day or over a period of 1 week can be tolerated but the individual should not expose himself further and should seek medical supervision. These emergency exposure rates are high compared to normal government-regulated exposure of not more than 0.3 roentgen per week for nuclear workers. A 100% lethal dosage is estimated to be 600 roentgens while 400 roentgens will kill approximately 50% of those exposed; 200 roentgens will produce grave effects and in a few cases death.

The radiation from an air burst at fairly high levels will cause many deaths from radiation emitted at the time of the bomb detonation, but little residual radioactivity will remain. Still, great care should be used to test all bomb-damaged areas for radioactivity. The low air or underwater burst will cause very dangerous surface radioactivity. A typical example is the blast at Alamogordo where the bomb was set off 100 feet above the ground. *One hour after the bomb had exploded* the radiation had decayed to 600 roentgens 650 feet from ground zero. At 1,000 feet the radiation was 150 roentgens per hour. Large areas will be affected in the event hydrogen bombs are used, up to 10,000 square miles for one bomb. Fallout may occur in areas far removed from the bombed area, causing just as serious radioactive levels. *Now is the time to join Civil Defense.*

Alpha and beta radiation can be guarded against by wearing gloves when picking up objects in a dangerous area, but the gamma radiation must be detected to avoid body damage. In any event use great care.

If a conventional Geiger type instrument (such as used for prospecting) is carried into a radioactive area and the radiation level is over 20 milliroentgens per hour the instrument will be overloaded and the indicating meter will show a low radiation rate. Because of this great danger with conventional Geiger counters and their low range, I do not recommend them for general Civil Defense use. The ionization chamber type of instrument will always go off scale on high radiation rates above its range. These instruments also cover an immense range, typical being 5 to 50,000 milliroentgens (50 roentgens). These instruments, however, are too expensive for general use and difficult to construct.

There are, however, special Geiger tubes made by Raytheon which cover ranges of 0 to 5 and 0 to 500 roentgens. These ranges are approximately logarithmic, which permits low radiation rates to be read easily down to about 20 milliroentgens on the lower-range tube. These special tubes make up a very simple, relatively inexpensive and foolproof unit for Civil Defense radiation safety.

The simplest circuit (Fig. 1) consists of a Geiger tube, several resistors, a 50-microampere meter and batteries. The battery life is shelf life of 1-2 years. Two standard 300-volt and two Burgess K-45 67.5-volt batteries can be

used or any other arrangement which will supply about 700 volts dc such as 10 or 11 of the small 67.5-volt Burgess K-45's.

The second circuit (Fig. 2) is used in the illustrated instrument which contains two size-D flashlight cells that can operate the instrument for about three 8-hour days. High voltage is generated by a vibrator and stepup transformer (a standard 4,000-ohm-primary output transformer should work) and rectified by a high-voltage selenium rectifier and filtered. The voltage is stabilized at 700 by a Victoreen 5950 or Raytheon CK1037 voltage regulator tube. As an alternate for the voltage regulator, you can use 13 NE-2 neon lamps in series. If the microammeter deflects with no radioactive material present the voltage is too high. Reduce the number of NE-2's one by one until the meter does not deflect in the absence of radioactivity.

The test switch in both instruments indicates full-scale current is available and when the batteries or high-voltage generator will no longer supply full-scale meter current this is shown on the meter. Even when the high voltage is down (a low test meter reading), as



This Civil Defense radiation detector can be fastened to the wearer's belt.

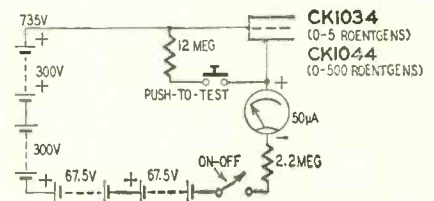


Fig. 1—Simple radiation meter.


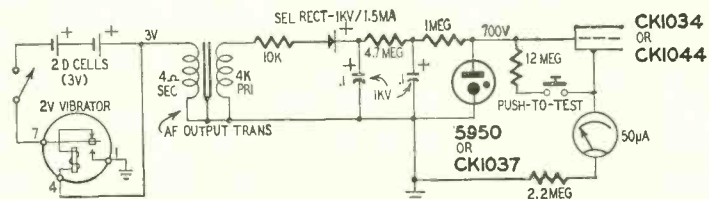


Fig. 2—With minor modifications, the Goldak CD-10 Civil Defense instrument.

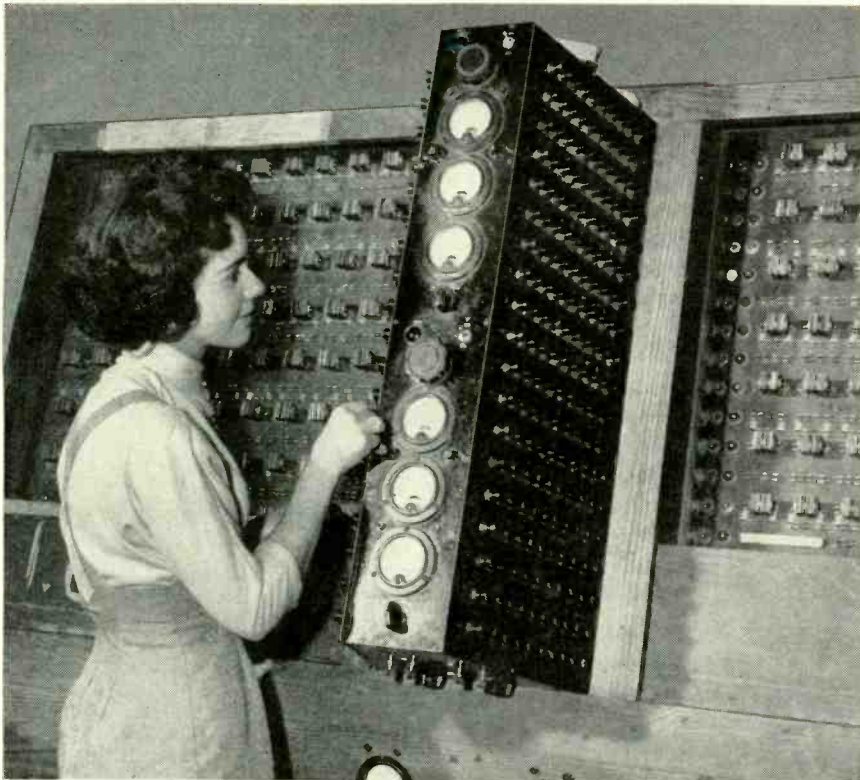



## ELECTRONICS

long as the indicated radiation is less than the test meter reading, the correct radiation rate is shown. This extends the usable life of the batteries.

A calibration table for the CK1034 and CK1044 is shown. Although some variation in Geiger tubes exists, this

### CALIBRATION TABLE

CK1034 Rated 0 - 5 r/hr

Meter Reading ( $\mu$ amps)	Radiation (mr/hr)
1	15
5	70
10	210
15	330
25	670
40	2300

CK1044 Rated 0-500 r/hr

2.5	1.3 r/hr
10	5.2 r/hr

should not prove serious if the emergency radiation dosages indicated in the article are not exceeded. Exact calibration can be obtained by varying the value of the 2.2-megohm resistor in series with the Geiger tube. The tubes are rated for operation at  $-55^{\circ}$  to  $+70^{\circ}$  Centigrade. The life is rated as "unlimited by counting rate."

The builder should select the range he feels most appropriate. Using both tubes with a switch is an excellent idea and would cost only the price of the extra Geiger tube and switch (use a rotary wafer type). The CK1044 can be obtained easier than the CK1034 and for my personal instrument I am using the CK1044. As the radiation from fallout dies off rapidly, the first indicated (highest) rate can be divided by half and multiplied by 36 hours to arrive at the *approximate* total dosage in roentgens that can be expected. This is a very rough approximation and should err on the safe side.

## Every RADIO RECEPTOR

# Safe Center

## selenium rectifier


passes this "final exam"  
before going to work for you!


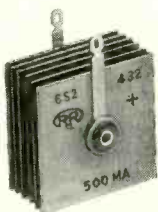
### 100% inspection means top performance

Our special test panel which simulates actual circuits, measures performance of each rectifier for a full half hour. Failures hit the reject bin—You get only the units that graduate with full honors.

100% factory testing is one more reason so many servicemen prefer Radio Receptor rectifiers. They're dependable, last longer... And there's a standard replacement for sets of every radio and TV manufacturer. Your parts distributor can supply you... Demand RRco. "Safe Centers" next time you order.



Semiconductor Division

## Radio Receptor Company, Inc.

Radio and Electronic Products Since 1922

240 Wythe Ave., Brooklyn 11, N. Y. • EVERGREEN 8-6000



### Parts for Fig. 2 radiation meter

1—10,000 ohms, 1—1, 1—2.2, 1—4.7, 1—12 megohms, 1/2-watt resistors; 2—0.1- $\mu$ f 1,000-volt capacitors; 1—output transformer, primary 4,000 ohms, secondary 4 ohms; 2—1.5-volt size-D flashlight cells; 1—spst switch; 1—spst pushbutton switch; 1—2-volt vibrator (Radiart 5469-2 or equivalent); 1—50- $\mu$ a meter; 1—selenium rectifier, 1,000 volts (International Rectifier Corp. U50HP or equivalent); 1—CK1034 or CK1044 Geiger tube; 1—Victoreen 5950 or Raytheon CK1037 voltage regulator (see text); 1—chassis.

I must add an important note. If an instrument is being carried waist high and reading *spot* contamination, such as from a pool of radioactive oil, the indication is low by a square-root factor. Radiation from point sources decreases as the square of the distance. For example, if the midpoint of the instrument is 26 inches above the ground and indicating 10 milliroentgens per hour—which is very safe—the contaminated spot on the ground by your feet would be 43.5 roentgens per hour. Great care must be used to avoid "hot spots."

Much Civil Defense literature is available, such as "Emergency Exposure to Nuclear Radiation." Pub. TB 11-1-1952, 5 cents, Superintendent of Documents, Washington 25, D. C. END

# ALLIED knight-kits

**FINEST ELECTRONIC EQUIPMENT  
IN LOWEST-COST KIT FORM**

- ★ Latest Advanced Design ★ Quality Components
- ★ Easiest to Assemble ★ Save Up To 50%

**BUY DIRECT...YOU SAVE MORE**

**free 1956 CATALOG**

Send for it! Describes the famous KNIGHT-KITS in detail—shows you how you can easily assemble your own instruments and get performance and appearance equal to equipment selling for several times the KNIGHT-KIT price. The 324-page ALLIED Catalog is the leading buying guide to *everything* in Electronics—write for your copy.




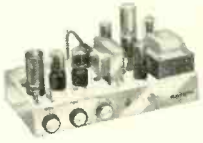
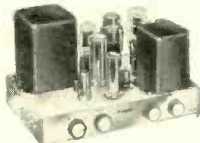
**SAVE ON THESE QUALITY knight-kit TEST INSTRUMENTS**

 5" Wide-Band Oscilloscope Kit F-144 69.00	 Printed Circuit VTVM Kit F-125 24.95	 Tube Tester Kit F-143 counter type 29.75 F-142 portable type 34.75	 VOM Kit 1000 Ohms/Volt F-128 15.95	 VOM Kit 20,000 Ohms/Volt F-140 28.50	 In-Circuit Capacitor Checker Kit F-119 11.65
 Audio Generator Kit F-137 31.50	 Resistance-Capacitance Tester Kit F-124 18.75	 High-Gain Signal Tracer Kit F-135 23.75	 RF Signal Generator Kit F-145 19.75	 Resistance Substitution Box Kit F-139 5.95	 Capacitance Substitution Box Kit F-138 5.50

**FAMOUS knight-kits FOR THE HOBBYIST**

 "Space Spanner" 2-Band Receiver Kit S-243 13.95 S-247 cabinet, 2.85	 "10-in-1" Lab Kit S-265 12.45	 "Ranger" Superhet Receiver Kit S-735 14.85
--	---	--

**TOP QUALITY HIGH FIDELITY knight-kits**

 Basic 25-Watt Deluxe Amplifier Kit S-755 41.50	 10-Watt Hi-Fi Amplifier Kit S-234 22.95	 20-Watt Hi-Fi Amplifier Kit S-750 35.75
---	---	---

**LOW-COST knight-kits FOR THE AMATEUR**

 "Ocean Hopper" Receiver Kit S-740 10.75	 Transistor Radio Kit S-765 3.95	 Geiger Counter Kit S-242 15.95
 3-Way Portable Radio Kit S-730 19.95	 Photoflash Kit S-244 28.50 S-246 AC supply, 3.40	 Wireless Broadcaster Kit S-705 8.75

 50-Watt CW Transmitter Kit S-255 42.50	 Self-Powered VFO Kit S-725 27.50	 Code Practice Oscillator Kit S-239 3.95
---	--	---

**FREE** Send for the 324-page ALLIED Catalog describing all KNIGHT-KITS—and your buying guide to everything in Electronics.

ALLIED RADIO CORP., Dept. 2-F-6  
100 N. Western Ave., Chicago 80, Ill.

Send FREE 1956 ALLIED Catalog.

Ship the following KNIGHT-KITS: \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

All Prices Net F.O.B. Chicago  
ORDER FROM

**ALLIED RADIO**


100 N. Western Ave., Chicago 80, Ill.



# what's

# new

# ?

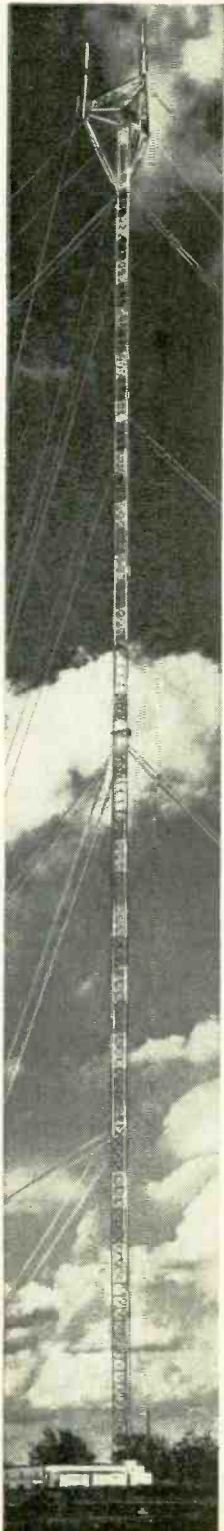

## FRENCH SPEAKER SPREADS HIGHS

This acoustic column speaker, made by Ge-Co (France), has three speakers in a vertical line, with their rear faces toward the auditorium. Used in this way, the cones disperse high notes perfectly instead of beaming them. The sound from the front of the speakers is absorbed in an acoustic labyrinth. The photo shows the speaker system resting on top of the case it occupies normally.



## TWO-ANTENNA TOWER

The antennas of WFAA-TV and KRLD-TV, Dallas, Tex., are on a single tower—the world's second highest structure. Unlike most installations, the two antennas are on the same level, on two of the corners of a triangular platform 80 feet on a side and 1,435 feet from the ground. This gives it the appearance that has earned it the name of "candelabra" antenna. The tower proper is three-sided—12 feet to a side—and is guyed in 5 places, at the 290-, 650-, 1,010-, 1,310- and 1,419-foot levels.



## ALL-TRANSISTOR PLANE RECEIVER

Designed for use on military aircraft, commercial and private planes, this little RCA marker-beacon receiver is the first of its type to be entirely transistorized. The smallest and lightest instrument of its type ever developed, it operates on less power than an ordinary flashlight and weighs only 15 ounces. Space occupied is 2 x 4 x 5 inches.

## NEXT MONTH


SHIRT POCKET TRANSISTOR RADIO

By I. Queen


WATCH FOR IT!
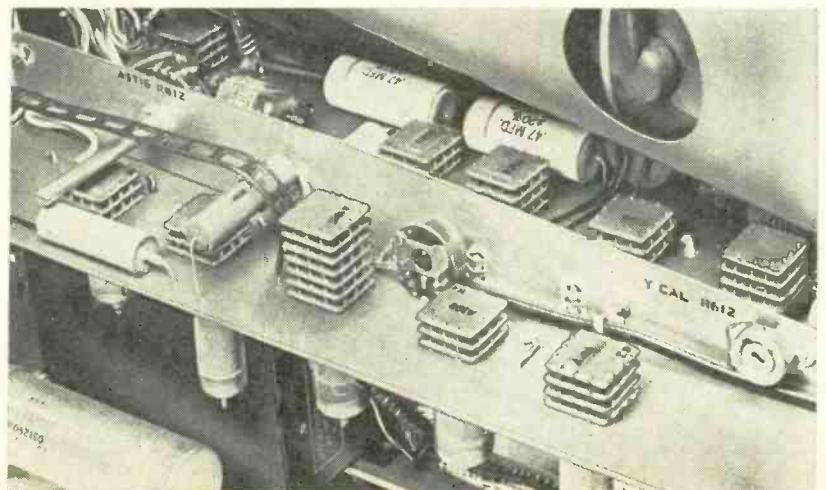
## MODULAR SCOPE

Modular construction is not confined to TV. The Du Mont oscillograph in the photograph below is said to be the first electronic test instrument using ceramic wafer unit construction. Each module is a complete circuit unit and instruments can be repaired very easily by discarding a faulty module and replacing it with a new one.



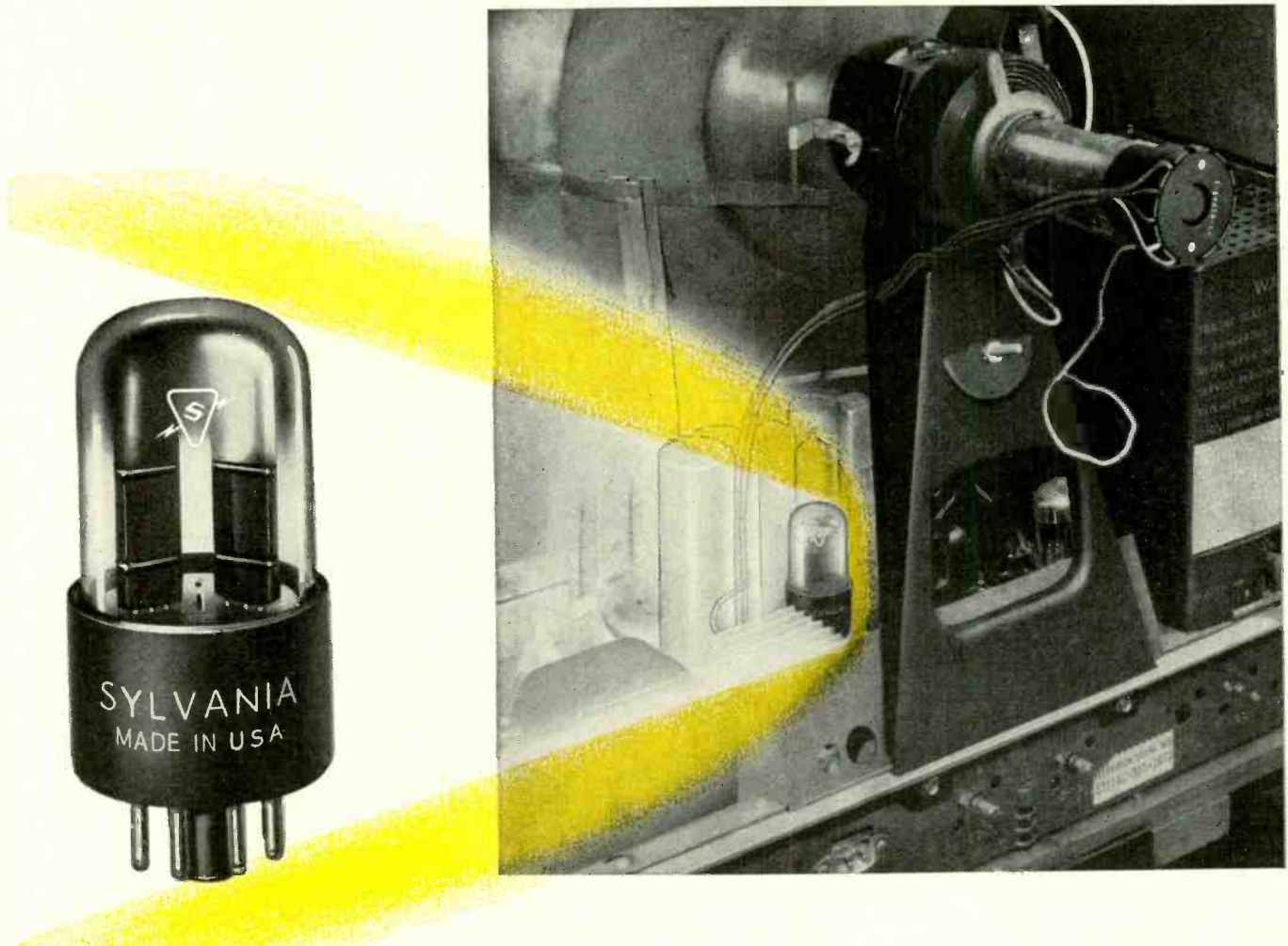A report on Sylvania's **6-Million-Hour Field Test** in receiving tubes



## "Circuit tested" in 139 stock TV sets for universal protection against callbacks

FOR UNIVERSAL PROTECTION against callbacks, use the tube that's tested for top performance under actual operating conditions in the sets you service. Sylvania tubes in the familiar yellow and black carton are backed by more than 6 million hours of field testing in TV sets of leading manufacturers.

The 139 stock models selected for the *6-million-hour field test* represent a cross section of the industry and their tube complements include every important replacement tube type. The 6-million-hour field test stacks up as the most extensive program ever under-

taken on the servicemen's behalf to insure universally dependable tubes.

Every set-testing cycle is based on one year of set use, assuring you maximum dependability during the period of your responsibility. That's why we say Sylvania tubes are "time-tested" for trouble-free service and the maximum profits which go along with it.

**Look for the yellow and black carton—it represents a new kind of dependability backed by the 6-million-hour field test.**



 **SYLVANIA**<sup>®</sup>

SYLVANIA ELECTRIC PRODUCTS INC.  
1740 Broadway, New York 19, N. Y.  
In Canada: Sylvania Electric (Canada) Ltd.,  
University Tower Bldg., Montreal



# TRANSISTOR RADIOS

## Part I—crystal detectors—transistor-amplifier circuitry

By I. QUEEN  
EDITORIAL ASSOCIATE

**T**RANSISTORS have supplanted tubes in many circuits and instruments and are now well established in the broadcast radio field. Many simple receivers designed by experimenters and hobbyists have been described in various magazines. Kits to build them are available. Transistor *superhets* are only a little more than a year old but already half a dozen manufacturers have put them on the market.

Semiconductor theory is difficult but fortunately very little is required to build and understand transistorized radio circuits. A transistor acts like a tube in many respects, especially when connected in grounded-emitter fashion (Fig. 1). The emitter is the source of

drawn by it to flow through the external load.

As a convenient short cut (but not short circuit) for our thinking, we may assume that the positive charges are emitted into the transistor and flow directly to the collector. This element, being negative, attracts them. The base element is between the emitter and collector so it controls the flow. When the base is more *negative* (or the emitter more positive) more charges can flow.

In a p-n-p semiconductor, both power supplies (for the base and the collector) must be negative; in an n-p-n type, these are both reversed.

The input circuit of a transistor has a low impedance, for example, 600 ohms. This differs considerably from a tube where the input is an open circuit (between grid and filament). This low impedance is due to the fact that the emitter-base junction (which acts as a diode) is biased in the *forward* (conducting) direction (emitter is more positive than the base). The transistor output has relatively high impedance, ordinarily about 1 megohm, since it is biased in the *reverse* direction (collector is more negative than base).

Fig. 1 shows two separate battery supplies to bias the elements. For convenience, it is customary to use one battery; Fig. 2 shows a simple arrangement. Resistor R is returned to the negative battery terminal to provide forward bias to the emitter-base circuit. The resistor may be determined by trial and error or may be chosen for a particular need. For example, if the battery is 3 volts and the required bias is 100 microamperes (.0001 amp) R must be 3/.0001 or 30,000 ohms. Normally this bias would support any signal varying from nearly zero to 200

microamperes if the transistor characteristic is linear at and near that point.

Better regulation is provided by the circuit of Fig. 3 where bias is provided by voltage divider R1, R2 across the battery. With the usual low voltages (3 to 6 volts) applied to transistors, their ratio should equal 4 or 5 to 1 for class-A operation. For example, R1, 10,000 ohms; R2, 2,000 ohms. This does not mean, however, that the base voltage will be one-fifth of the collector supply. Current also flows from the base into R1 so that the bias will be smaller than indicated by the ratio of R1 to R2.

The voltage-divider method is often used to bias high-frequency and class-B amplifiers, as we shall see later.

Certain precautions should be observed when handling transistors. They are very sensitive to temperature. Don't keep them in a warm place or put a soldering iron near them. When soldering directly to a transistor lead, hold it with a pair of pliers to prevent the heat from passing into the semiconductor. Many experimenters prefer to use sockets rather than solder directly to the transistor. This permits quick insertion and removal. A five-pin subminiature in-line socket should be used.

Before connecting the power supply make sure it is correctly polarized, that is, negative toward the collector of a p-n-p, positive toward the collector of an n-p-n. Also check the voltage—many types are limited to 20 or 22.5 volts on the collector. Some of the newer high-frequency types require 6 volts or less.

### Crystal detectors

In regions where broadcast stations are well separated frequency-wise, selectivity is not a problem. Here, a

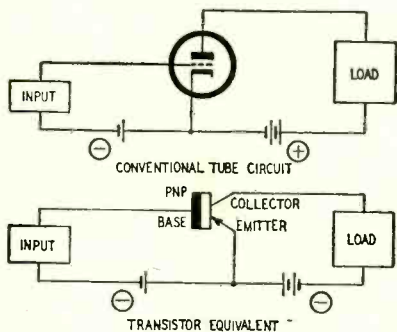


Fig. 1—Diagram shows comparison of vacuum tube and transistor circuits.

charged particles so it is equivalent to a filament or cathode; in a p-n-p transistor (shown with arrow pointing toward the base) it emits positive "holes." The base corresponds to a grid because its bias controls the flow of charges through the transistor. In an efficient semiconductor only a small fraction of the total current flows through the base. The collector is the plate; that is, the output current is

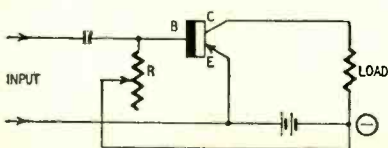


Fig. 2—A simple method of biasing.

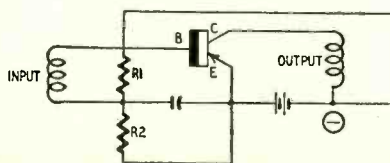


Fig. 3—Biasing with voltage divider.

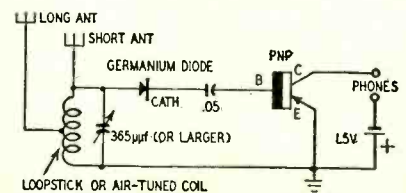


Fig. 4—Crystal set with audio stage.

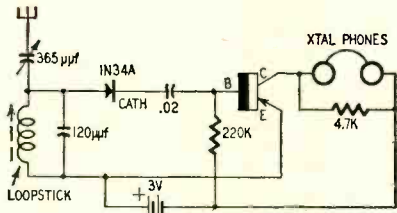


Fig. 5—Variation of Fig. 4 circuit.

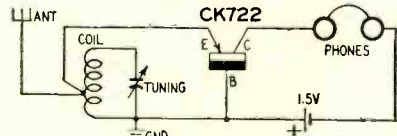


Fig. 6—Circuit uses printed wiring.

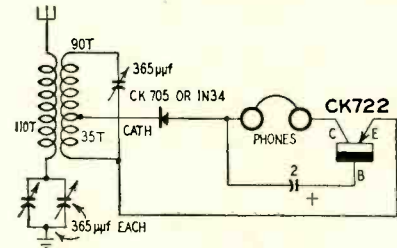


Fig. 7—Schematic shows crystal set using no apparent power supply.

crystal set with an amplifier may provide very satisfactory reception. The antenna should be at least 50 feet long and preferably longer since a crystal detector has low gain. However, its selectivity is not too great so there can be no sideband cutting. This means higher fidelity and low noise pickup.

Fig. 4 shows a simple yet practical crystal set with one stage of audio. It contains a ferrite-rod or equivalent antenna coil. The tap is not necessary but is advantageous in that it permits a good match to a long antenna if one is available. If the antenna is short—40 feet or less—connect it to the end of the coil.

The diode may be any rectifier type such as the CK705, 1N34, etc. The transistor is a p-n-p type such as the CK722. Modulated rf from the antenna is rectified by the diode. The capacitor is large enough so that it does not impede the rf. However, there is considerable impedance to the audio modulation. Therefore, the capacitor charges and discharges in accordance with the audio component of the signal, thereby varying the bias applied to the transistor.

Note that the diode polarity is such that the base is always more negative than the emitter. The audio output is amplified by the transistor and then fed to an earpiece or headphone set. Carefully check diode and battery polarities. The unit in Fig. 4 may be purchased in kit form (Philmore No. TR101).

A somewhat similar circuit is shown in Fig. 5. This is also available as a kit (Lafayette KT-80), and is designed to fit a small plastic pocket-size box measuring about 1 x 2 x 3 inches. This circuit contains a flat variable capaci-

tor to peak the antenna circuit. Ordinarily, the variable is the most bulky item in a radio and would hardly be expected to fit into a pocket-size box. The earpiece is shown as a crystal type and a resistor is added to shunt the dc component around it. When a signal arrives, it charges the .02-uf capacitor and combines with the bias already established by the resistor.

The circuit of Fig. 5, like that of Fig. 4, is a combination crystal diode and transistor amplifier which can provide excellent reception of stations within a radius of 50 miles. In favorable locations stations up to 500 miles can be received. The current drain on the batteries is so low that an on-off switch is not necessary—the radio will operate for the approximate shelf life of the batteries.

An interesting feature of this circuit is the double-tuned antenna stage—a high-Q loopstick to select the station and the flat 365- $\mu$ f variable capacitor to peak the response curve of the station selected.

The Lafayette kit version of this crystal-grounded-emitter amplifier unit is connected and operated through six holes drilled in the plastic case—two small ones on one side for the antenna and ground wires, three medium-sized holes on the opposite side to permit mounting of the earphone jacks and the loopstick, one on top for the shaft of the variable capacitor.

Allied makes a printed transistor circuit as shown in Fig. 6. Copper stripes, bonded on a plastic board, are the conductors between components. This simplifies the wiring to some extent. A 50-foot antenna should be used in metropolitan areas. In rural areas where most of the stations may be distant, a 75–100-foot antenna may be required. The ground lead may be connected to a cold water pipe or a rod buried in the ground. The ground lead should make a good electrical connection.


No switch is shown in the diagram. When the phone tips of the headset are removed from their jacks, the battery is automatically switched off. The first transistor acts as a detector and amplifier in this circuit, and the designer found no advantage in adding a crystal diode.

One rather unusual crystal set, designed by William H. Grace, Jr., consists of a crystal detector (Fig. 7) followed by a transistor with no apparent power supply. The collector returns through phones to one terminal of a large capacitor. The diode is connected opposite in polarity to those of Figs. 4 and 5. Thus the large capacitor charges with its left terminal negative so it can bias the collector properly. This offsets what was said previously about having it charge with its right terminal negative. However, the convenience of a battery-less receiver is the big feature in this case and it does have reasonable gain. TO BE CONTINUED
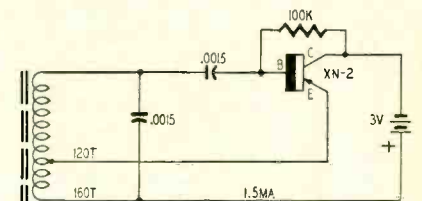
## TRANSISTORIZED GOLF BALL


Divot diggers take heart, a non-losable golf ball has been invented. Lost balls resulting from those hooks and slices into the rough may become a thing of the past with the development of a transistorized golf ball that transmits a sufficiently strong r.f. signal to be picked up by a portable pocket-size receiver (see photo). By merely rotating the receiver as a direction finder, a golfer can "home" on the elusive spheroid. The diagram shows circuitry of the transistorized golf ball.

An experimental p-n-p type transistor is used in a simple Hartley oscillator circuit, with the number of turns on the oscillator coil as indicated in the schematic. The unit is powered by a small 3-volt battery. Of greater importance than this application is the fact that the extreme ruggedness of transistors is demonstrated—on teeing off, a golf ball is figuratively "shot from a gun."



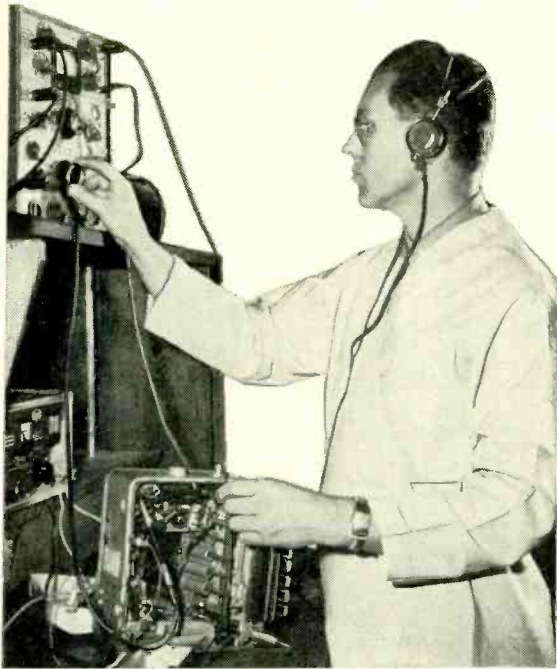Motorola, developer of the electronic golf ball, stressed the fact that this is still a gadget and cannot be found in any sporting goods stores at the present time.





Author aligning automobile receiver.

# ALIGNING BROADCAST RECEIVERS

*Speed and accuracy are  
features of this  
tuned-signal-tracer method*

By JAMES E. DALLEY

**T**HE alignment method described here has been used for many years with good success. It is very popular with technicians who have learned to use it because of its simplicity, speed and accuracy. It is easier on the nerves than the standard method using a tone-modulated signal generator and output meter.

It is faster because only one probe need be connected to the receiver and it must be moved only once (no ground connection is needed); the low-frequency padder can be tuned in directly without "rocking" the tuning capacitor and because the set can be aligned as a normal routine while tracing the signal through to hunt for other troubles.

It is more accurate because it uses the signal directly from the broadcast station which is crystal-controlled. The local oscillator cannot interfere and give false indications. And since only the normally received signals are used, the circuits are not apt to be overloaded.

It is pleasant because you can usually listen to music while you are working. Even soap operas are easier to listen to than a monotonous 400-cycle tone.

The only piece of equipment necessary is a tuned signal tracer. The calibration does not have to be too accurate because broadcast signals are used and their frequency is accurately controlled. Frequencies of all local stations should be memorized. The setting of the intermediate frequency will depend on the calibration of the signal tracer, but it isn't serious if the intermediate frequency is changed a few kilocycles.

The signal tracer must be sensitive enough to pick up local stations with just an alligator clip or a few inches of wire on the end of the probe. The probe, cable and entire instrument must be well shielded from stray pickup. Selectivity should be fairly good and the signal tracer must have some form of an output indicator such as an electron-ray tube or a meter.

Commercial tuned tracers are not too common today, though a number of the beacon receivers sold on the surplus market are excellent for the purpose, being accurately calibrated already. Or one can be constructed from an old broadcast receiver without much trouble, replacing the if trimmers with large variable capacitors and supplying an extra input direct to the if stages, bypassing the front end.


A permanent unit for the shop can be built without too much trouble. If made specially for the purpose, it should be designed to have a frequency range which would run from below the lowest if (there are still a few sets operating on a 175-kc if) to above the highest frequency you need. Ideally the range should be from 100 kc to 2 mc.

(Fig. 1 is a simple signal tracer covering from approximately 150 to 1600 kc in two bands. One like it can be built from an old trf receiver or from standard parts. The two-band coils are rf transformers for the aircraft-beacon and standard broadcast bands. Trimmers on the long-wave coils should be loosened or removed entirely so the circuits tune to at least 480 kc. An af output stage can be added if desired.—*Editor*)

In a superheterodyne receiver the intermediate frequency is produced by mixing and detecting the signals from the radio station and the local oscillator. In broadcast receivers the oscillator frequency is always above the station frequency by an amount equal to the intermediate frequency. For example, if a radio is tuned to a station on 600 kc and the local oscillator is tuned to 1055 kc, the intermediate frequency will be 455 kc. The intermediate frequency is found by subtracting the station frequency from the oscillator frequency. If the station and intermediate frequencies are known, the oscillator frequency can be found by adding them together. As different stations are tuned in, the difference between the oscillator and the station frequency must always equal the intermediate frequency. The adjustments to be made in aligning a receiver are: the dial pointer, the oscillator trimmer, the rf and mixer trimmers, the oscillator padder or coil slug, the if transformers. Most receivers do not have a low-frequency adjustment for the oscillator (padder or coil slug) or an rf stage. We will discuss the procedure to be used when both of these adjustments are included and they can merely be omitted when the set does not have them.

The radio and the signal tracer should be turned on and warmed up for 10-15 minutes before starting the adjustments. During this warmup period the radio dial can be "indexed" by turning the tuning capacitor to the low-frequency stop and adjusting the dial pointer to coincide with the lowest

Fig. 1—Diagram of simple signal tracer—covers 150-1600 kc in two bands.

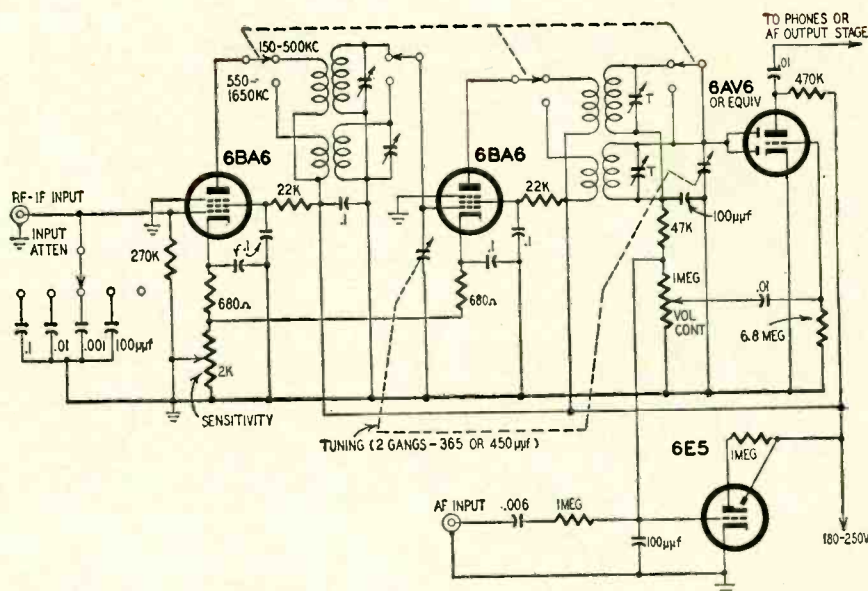

mark on the dial. If the pointer is cemented to a dial cord, it may be necessary to use cement thinner to loosen it. The pointer should be cemented in place again after it has been adjusted. Turn the volume control of the receiver all the way down.

**Front end—high-frequency adjustments**

1. Connect the if probe of the signal tracer to the plate of the mixer (point 1) in the receiver (see Fig. 2.)
2. Adjust the dial on the signal tracer to the intermediate frequency of the receiver.
3. Set the dial of the receiver to the frequency of a local station near 1400 kc. The receiver dial should be set to the correct frequency whether the station is heard there or not.
4. Adjust the oscillator trimmer (B) until the station is heard through the signal tracer. Make sure you have the right station by listening on another radio, or by tuning the signal tracer

to the station frequency and identifying the program material. Be sure to return the dial of the signal tracer to the intermediate frequency if it is changed.

5. Continue to adjust oscillator trimmer B until a peak reading is obtained on the visual indicator of the signal tracer.

6. Adjust rf trimmer A (if used) and the mixer trimmer for peak reading on the signal tracer.

7. If the receiver has a low-frequency adjustment, proceed to the if; if not, tune across the dial and check the sensitivity of the stations especially at the low frequencies. If the sensitivity is good on the low end of the dial, proceed to the if adjustments. If it is not, the outside rotor plates of the oscillator and rf tuning capacitor can be bent to improve response.

**Front end—low-frequency adjustments**

There are usually no rf adjustments for the low frequencies. This means

that we must find where the low-frequency stations come in best through the rf circuits and adjust the oscillator for the proper difference frequency. In the signal generator-output meter method we make adjustments and check the results while rocking the tuning dial of the receiver until the proper combination of adjustments is found. With this method we can go directly to the proper adjustment. The procedure is as follows:

8. Tune the signal tracer to a local station near 600 kc.
9. Leave the signal tracer connected to the plate of the mixer. Enough signal should get through for this adjustment even though the signal tracer is connected across a circuit tuned to another frequency—the intermediate frequency.
10. Tune the radio to the same station. The radio dial will probably not indicate the exact frequency of the station but this should be disregarded and the radio tuned until maximum

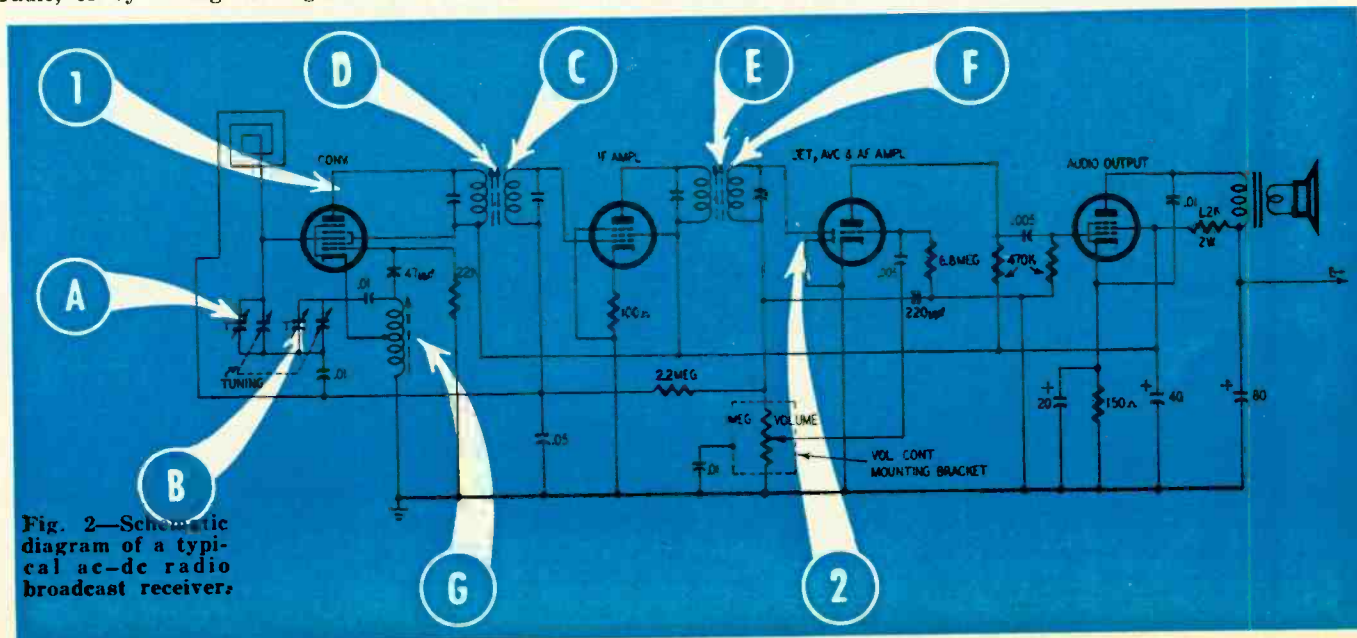


Fig. 2—Schematic diagram of a typical ac-dc radio broadcast receiver.





Superior's New  
Model TC-55

# FOR TUBE TESTER

The Experimenter or Part-time Serviceman, who has delayed purchasing a higher priced Tube Tester. The Professional Serviceman, who needs an extra Tube Tester for outside calls. The busy TV Service Organization, which needs extra Tube Testers for its field men.

Speedy, yet efficient operation is accomplished by:

1. Simplification of all switching and controls.
2. Elimination of old style sockets used for testing obsolete tubes (26, 27, 57, 59, etc.) and providing sockets and circuits for efficiently testing the new Noval and Sub-Minar types.

### You can't insert a tube in wrong socket

It is impossible to insert the tube in the wrong socket when using the new Model TC-55. Separate sockets are used, one for each type of tube base. If the tube fits in the socket it can be tested.

### "Free-point" element switching system

The Model TC-55 incorporates a newly designed element selector switch system which reduces the possibility of obsolescence to an absolute minimum. Any pin may be used as a filament pin and the voltage applied between that pin and any other pin, or even the "top-cap".

### Checks for shorts and leakages between all elements

The Model TC-55 provides a super sensitive method of checking for shorts and leakages up to 5 Megohms between any and all of the terminals. Continuity between various sections is individually indicated. This is important, especially in the case of an element terminating at more than one pin. In such cases the element or internal connection often completes a circuit.

Elemental switches are numbered in strict accordance with R.M.A. specification.

One of the most important improvements, we believe, is the fact that the 4 position fast-action snap switches are all numbered in exact accordance with the standard R.M.A. numbering system. Thus, if the element terminating in pin No. 7 of a tube is under test, button No. 7 is used for that test.

The Model TC-55 comes complete with operating instructions and charts. Housed in rugged steel cabinet. Use it on the bench—use it for field calls. A streamlined carrying case, included at no extra charge, accommodates the tester and book of instructions.

**\$26<sup>95</sup>**  
NET



Superior's new  
Model TV-11

# TUBE TESTER

★ Tests all tubes including 4, 5, 6, 7, Octal, Lock-in, Peanut, Bantam, Hearing Aid, Thyatron Miniatures, Sub-miniatures, Novals, Sub-minars, Proximity fuse types, etc.

★ Uses the new self-cleaning Lever Action Switches for individual element testing. Because all elements are numbered according to pin-number in the RMA base numbering system, the user can instantly identify which element is under test. Tubes having tapped filaments and tubes with filaments terminating in more than one pin are truly tested with the Model TV-11 as any of the pins may be placed in the neutral position when necessary.

EXTRA SERVICE—The Model TV-11 may be used as an extremely sensitive Condenser Leakage Checker. A relaxation type oscillator incorporated in this model will detect leakages even when the frequency is one per minute.

★ The Model TV-11 does not use any combination type sockets. Instead individual sockets are used for each type of tube. Thus it is impossible to damage a tube by inserting it in the wrong socket.

★ Free-moving built-in roll chart provides complete data for all tubes.

★ Newly designed Line Voltage Control compensates for variation of any Line Voltage between 105 Volts and 130 Volts.

★ NOISE TEST: Phono-jack on front panel for plugging in either phones or external amplifier will detect microphonic tubes or noise due to faulty elements and loose internal connections.

The model TV-11 operates on 105-130 Volt 60 Cycles A.C. Comes housed in a beautiful hand-rubbed oak cabinet complete with portable cover.

**\$47<sup>50</sup>**  
NET



Superior's  
New Model TV-12

# TRANS-CONDUCTANCE TUBE TESTER

### TESTING TUBES

★ Employs improved TRANS-CONDUCTANCE circuit. An in-phase signal is impressed on the input section of a tube and the resultant plate current change is measured. This provides the most suitable method of simulating the manner in which tubes actually operate in Radio & TV receivers, amplifiers and other circuits. Amplification factor, plate resistance and cathode emission are all correlated in one meter reading.

★ NEW LINE VOLTAGE ADJUSTING SYSTEM. A tapped transformer makes it possible to compensate for line voltage variations to a tolerance of better than 2%.

★ SAFETY BUTTON—protects both the tube under test and the instrument meter against damage due to overload or other form of improper switching.

★ NEWLY DESIGNED FIVE POSITION LEVER SWITCH ASSEMBLY. Permits application of separate voltages as required for both plate and grid of tube under test, resulting in improved Trans-Conductance circuit.

### TESTING TRANSISTORS

A transistor can be safely and adequately tested only under dynamic conditions. The Model TV-12 will test all transistors in that approved manner, and quality is read directly on a special "transistor only" meter scale.

The Model TV-12 will accommodate all transistors including NPN's, PNP's, Photo and Tetrodes, whether made of Germanium or Silicon, either point contact or junction contact types.

Model TV-12 housed in handsome rugged portable cabinet sells for only

**\$72<sup>50</sup>**  
NET

ALSO TESTS TRANSISTORS!

## ABOUT TESTING PICTURE-TUBES...

Of course you can buy an "adapter" which theoretically will convert your standard Tube Tester into a picture-tube tester. Sounds fine—but it simply doesn't work out that way!

We do not make nor do we recommend use of C.R.T. adapters because a Cathode Ray Tube is a very complex device and to properly test it, you need an instrument designed exclusively to test C. R. Tubes and nothing else. As compared to a makeshift adapter, which sells for about five dollars, our Model TV-40 C.R.T. Tube Tester sells for \$15.85. But, if you believe

that Television is here to stay, then you must agree that the difference in price is more than justified by the many years of valuable service you will get out of this indispensable instrument.

Incidentally, the Model TV-40 is the ONLY low-priced C.R.T. Tube Tester, which includes a real meter. Neons are fine for gadgets and electro-line testers, but there is no substitute for a meter with an honest-to-goodness emission reading scale.



Superior's New  
Model TV-40

# C. R. T. TUBE TESTER

Tests ALL magnetically deflected tubes... in the set... out of the set... in the carton!!

- Tests all magnetically deflected picture tubes from 7 inch to 30 inch types.
- Tests for quality by the well established emission method. All readings on "Good-Bad" scale.
- Tests for inter-element shorts and leakages up to 5 megohms.
- Test for open elements.

EASY TO USE: Simply insert line cord into any 110 volt A.C. outlet, then attach tester socket to tube base (Ion trap need not be on tube). Throw switch up for quality test... read direct on Good-Bad scale. Throw switch down for all leakage tests.

Model TV-40 C.R.T. Tube Tester comes absolutely complete—nothing else to buy. Housed in round cornered, molded bakelite case. Only

**\$15<sup>85</sup>**  
NET

**EXAMINE BEFORE YOU BUY!**


**USE APPROVAL FORM ON NEXT PAGE**



Superior's new  
Model 670-A
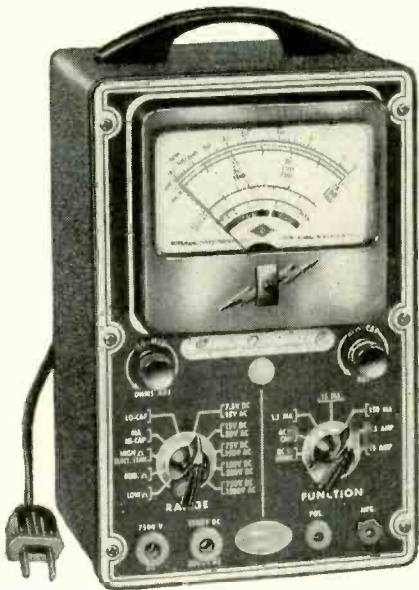
# SUPER METER

A COMBINATION VOLT-OHM MILLIAMMETER PLUS  
CAPACITY REACTANCE INDUCTANCE  
AND DECIBEL MEASUREMENTS



**SPECIFICATIONS:**

- D.C. VOLTS: 0 to 7.5/15/75/150/750/1,500/7,500 Volts
- A.C. VOLTS: 0 to 15/30/150/300/1,500/3,000 Volts
- OUTPUT VOLTS: 0 to 15/30/150/300/1,500/3,000 Volts
- D.C. CURRENT: 0 to 1.5/15/150 Ma. 0 to 1.5/15 Amperes
- RESISTANCE: 0 to 1,000/100,000 Ohms 0 to 10 Megohms
- CAPACITY: .001 to 1 Mfd. 1 to 50 Mfd. (Good-Bad scale for checking quality of electrolytic condensers)
- REACTANCE: 50 to 2,500 Ohms, 2,500 Ohms to 2.5 Megohms
- INDUCTANCE: .15 to 7 Henries 7 to 7,000 Henries
- DECIBELS: -6 to +18, +14 to +38, +34 to +58

**ADDED FEATURE:**

Built-in ISOLATION TRANSFORMER reduces possibility of burning out meter through misuse.


The Model 670-A comes housed in a rugged crackle-finished steel cabinet complete with test leads and operating instructions.

**\$28<sup>40</sup>**  
NET

Superior's New  
Model TV-50
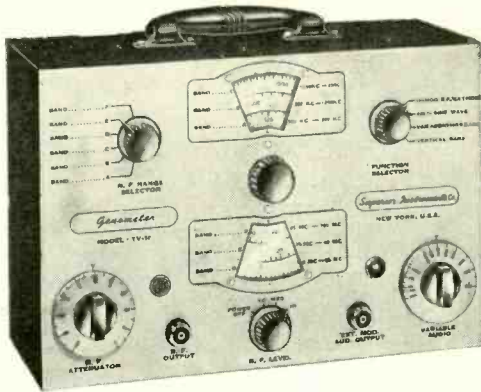
# GENOMETER

A versatile all-inclusive GENERATOR which provides ALL the outputs for servicing:  
A.M. Radio • F.M. Radio • Amplifiers • Black and White TV • Color TV  
**7 Signal Generators in One!**



- ✓ R.F. Signal Generator for A.M.
- ✓ R.F. Signal Generator for F.M.
- ✓ Audio Frequency Generator
- ✓ Bar Generator
- ✓ Cross Hatch Generator
- ✓ Color Dot Pattern Generator
- ✓ Marker Generator

**R. F. SIGNAL GENERATOR:** The Model TV-50 Genometer provides complete coverage for A.M. and F.M. alignment. Generates Radio Frequencies from 100 Kilocycles to 60 Megacycles on fundamentals and from 60 Megacycles to 180 Megacycles on powerful harmonics.

**VARIABLE AUDIO FREQUENCY GENERATOR:** In addition to a fixed 400 cycle sine-wave audio, the Model TV-50 Genometer provides a variable 300 cycle to 20,000 cycle peaked wave audio signal.

**BAR GENERATOR:** The Model TV-50 projects an actual Bar Pattern on any TV Receiver Screen. Pattern will consist of 4 to 16 horizontal bars or 7 to 20 vertical bars.

**CROSS HATCH GENERATOR:** The Model TV-50 Genometer will project a cross-hatch pattern on any TV picture tube. The pattern will consist of non-shifting horizontal and vertical lines interlaced to provide a stable cross-hatch effect.

**DOT PATTERN GENERATOR (FOR COLOR TV):** Although you will be able to use most of your regular standard equipment for servicing Color TV, the one addition which is a "must" is a Dot Pattern Generator. The Dot Pattern projected on any color TV Receiver tube by the Model TV-50 will enable you to adjust for proper color convergence.

**MARKER GENERATOR:** The Model TV-50 includes all the most frequently needed marker points. The following markers are provided: 189 Kc., 282.5 Kc., 456 Kc., 600 Kc., 1000 Kc., 1400 Kc., 1600 Kc., 2000 Kc., 2500 Kc., 3579 Kc., 4.5 Mc., 5 Mc., 10.7 Mc., (3579 Kc. is the color burst frequency.)

**THE MODEL TV-50** comes absolutely complete with shielded leads and operating instructions.

**\$47<sup>50</sup>**  
NET

Only \_\_\_\_\_

**SHIPPED ON APPROVAL  
NO MONEY WITH ORDER — NO C.O.D.**

Try any of the instruments on this or on the facing page for 10 days before you buy. If completely satisfied then send down payment and pay balance as indicated on coupon. No Interest or Finance Charges Added! If not completely satisfied return unit to us, no explanation necessary. All prices net, F.O.B., N.Y.C.

MOSS ELECTRONIC DISTRIBUTING CO., INC.  
Dept. D-237, 3849 Tenth Ave., New York 34, N. Y.

Please send me the units checked. I agree to pay down payment within 10 days and to pay the monthly balance as shown. It is understood there will be no finance or interest charges added. It is further understood that should I fail to make payment when due, the full unpaid balance shall become immediately due and payable.

- Model TV-40..... Total Price \$15.85  
\$3.85 within 10 days. Balance \$4.00  
monthly for 3 months.
- Model TV-11..... Total Price \$47.50  
\$11.50 within 10 days. Balance \$6.00  
monthly for 6 months.

- Model 670-A..... Total Price \$28.40  
\$7.40 within 10 days. Balance \$3.50  
monthly for 6 months.
- Model TV-50..... Total Price \$47.50  
\$11.50 within 10 days. Balance \$6.00  
monthly for 6 months.

- Model TC-55..... Total Price \$26.95  
\$6.95 within 10 days. Balance \$5.00  
monthly for 4 months.
- Model TV-12..... Total Price \$72.50  
\$22.50 within 10 days. Balance \$10.00  
monthly for 5 months.

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_



indication is obtained on the signal tracer. This step tunes the rf stages to the exact frequency of the station.

11. Set the dial on the signal tracer to the intermediate frequency. Be sure not to disturb the radio dial setting.

12. Turn the oscillator padder (or slug) G for maximum reading on the same station used in step 8.

13. Steps 1, 3, 4 and 5 will now have to be repeated. If the oscillator trimmer is very far out, the low-frequency adjustments will have to be repeated and the high-frequency adjustments done a third time.

Remember to start and end with the high-frequency adjustments and keep going until very little change is needed for the oscillator trimmer adjustment. If the radio dial cannot be read accurately, step 6 will have to be repeated in the high-frequency adjustments too.

**Intermediate-frequency adjustments**

The intermediate-frequency transformer trimmers are next adjusted as follows:

14. Move the signal tracer probe to the diode detector plate (point 2). Unless the if transformers are too far out of alignment, enough signal can be picked up by clipping the probe to the insulation of the plate lead rather than making direct connection. This gives better isolation which prevents detuning the circuit with the probe capacitance.

15. Leave the signal tracer tuned to the intermediate frequency.

16. Leave the radio tuned accurately to the local station near 1400 kc.

17. Adjust the if trimmers C, D, E and F for maximum indication on the signal tracer. Do not take too much time on this adjustment as only an approximate setting is required. The order of adjusting the trimmers is not important.

18. After all of the if trimmers have been adjusted to their approximate settings, repeat the adjustments for exact maximum readings. It is necessary to make the adjustments twice because the settings of the primary and secondary trimmers (or slugs) affect each other. If the set starts to oscillate during the if adjustments, it usually indicates that the if transformers cannot be operated exactly on maximum settings and the trimmers should be stagger-tuned slightly until maximum gain with good audio quality is obtained without oscillation.


Disconnect the signal tracer and turn up the volume control. Tune across the entire dial and check the number, strength and quality of the stations received against comparable sets.

This alignment method follows the natural signal through the set in a logical manner. After a little practice this outline can be discarded and no notes of any kind will be needed on most receivers. Variations for peculiar conditions can easily be worked out after the basic method of alignment is understood. END
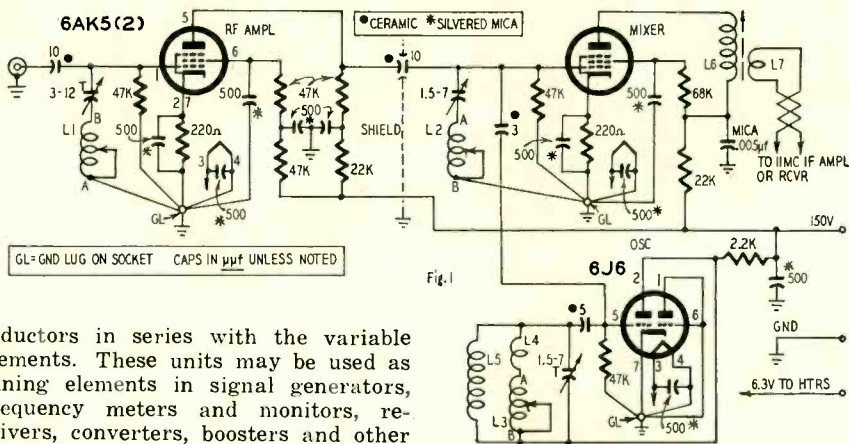
# 50-240-mc Converter-Receiver Using Helical Type Inductuner

**M**ANY readers have expressed interest in circuit applications for helical type Inductuners that they have purchased through the bargain or surplus pages of mail-order radio supply catalogs or salvaged from old TV receivers. The basic tuning range of these Inductuners is 50 to 240 mc but it may be shifted higher by using shunt inductors or lowered by inserting fixed

inductors in series with the variable elements. These units may be used as tuning elements in signal generators, frequency meters and monitors, receivers, converters, boosters and other devices.



inductors in series with the variable elements. These units may be used as tuning elements in signal generators, frequency meters and monitors, receivers, converters, boosters and other devices.

Fig. 1 is the diagram of a 50-240-mc converter that was described in a Mallory technical bulletin on the helical type Inductuner. The 11-mc if output of the converter can be fed to a receiver tuned to this range or to an 11-mc if strip designed for either AM or FM reception.

L1, L2 and L3 are the rear, center and front sections, respectively, of the Inductuner. L4 and L5 are end and shunt inductors required to shift the oscillator tuning range to 61 to 251 mc—assuming an 11-mc if L4 consists of 1/2 turn of No. 18 copper wire, with a radius of about 3/4 inch, soldered between terminal A on the front section of the Inductuner (see Fig. 2) and a ceramic standoff insulator installed next to the 6J6 oscillator socket. This insulator serves as the tie point for the junction of the 5-μμf 6J6 grid capacitor, end inductor L4, the 1.5-7-μμf oscillator trimmer and shunt inductor L5.

L5 consists of 28 turns of No. 30 enameled wire closewound on a 1/4-inch diameter polystyrene rod. Converter output coil L6 may be the primary of a 10.7-mc if transformer or approximately 49 turns of No. 28 enameled wire closewound on a National XR-50 form. L7 is a three-turn link of hookup wire wound around the ground end of L6.


Hum is minimized by bypassing the heater supply lead and running it above the chassis to isolate it from the hum-sensitive grid circuits.

An absorption type wavemeter or grid-dip oscillator is used for align-

ment. Connect a 25-ma meter between the B plus end of the oscillator plate resistor and the 150-volt line. Tightly couple the wavemeter to L5 and tune the Inductuner to the maximum counter-clockwise position. Tune the wavemeter through the range of about 40 to 80 mc and note the wavemeter frequency setting when oscillator plate current rises sharply. Vary the oscillator

trimmer capacitor so the meter reading peaks at 61 mc (60.7 mc for 10.7-mc if's). Now, tune the Inductuner to the extreme clockwise end of the range and check the oscillator frequency at around 251 mc. If the wavemeter shows the oscillator frequency to be higher than 251 mc, spread the 1/2-turn inductor (L4) to increase its inductance and lower the frequency. Squeeze the sides together if the oscillator frequency is low.

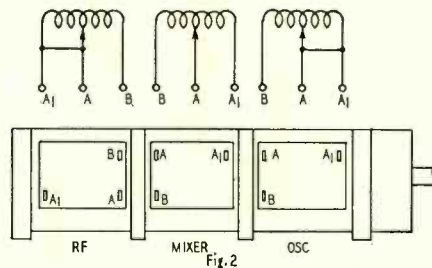Return to the low end of the dial and touch up the trimmer capacitor and



then check the high end again. Repeat the high- and low-end adjustments until the oscillator tuning range is exactly 61 to 251 mc.

Connect the converter output to a receiver tuned to 11 mc and peak L6 for maximum tube hiss. Set the Inductuner three full turns from the low-frequency end. Connect an antenna to the converter and feed in a signal from a signal or marker generator set in the range between 63 and 65.7 mc. Adjust

the capacitor you DREAMED about is HERE!



## this ONE new ceramic capacitor does the work of FIFTEEN

NOW . . . you can handle a big percentage of special value and standard value ceramic replacements with a few Sprague "Universals". Just four of these remarkable new capacitors take the place of forty-two regular capacitors, with capacitance values from 400  $\mu\text{F}$  to .015  $\mu\text{F}$ . You can also use them to replace molded mica, ceramic tubular, and paper tubular capacitors in many bypass and coupling applications.

Sprague "Universals" are easy to use! No complex arithmetic involved. One look at the handy reference card packed with each capacitor tells the complete story . . . which "Universal" to use . . . how to wire the leads for the capacitance required.

Type UHK-1, with seven needed values from .001 to .004  $\mu\text{F}$ , is a High-K capacitor for use where rated capacitance is the lowest value permissible. Type UGA-1, with twelve values from .0004 to .0013  $\mu\text{F}$ , is a general application unit with a capacitance tolerance of  $\pm 20\%$ . UHK-2, covering eight values from .0025 to .015  $\mu\text{F}$ , is a High-K capacitor like UHK-1. Type UGA-2 covers fifteen values from .0006 to .0027  $\mu\text{F}$ , and is a general application unit with a  $\pm 20\%$  capacitance tolerance.

Put Sprague "Universal" ceramic capacitors on your "want" list now. Your customers won't ever have to spend another night without television for lack of a simple ceramic replacement.

**don't be vague . . . insist on**

Sprague Products Company • Distributors' Division of the Sprague Electric Company • North Adams, Massachusetts.

JUNE, 1956

A FEW EXAMPLES OF HOW FOUR "UNIVERSAL" CAPACITORS MEET 90% OF ALL CERAMIC REPLACEMENT NEEDS

For .0004  $\mu\text{F}$

Cut leads 2 and 3 from a UGA-1 "Universal". Use leads 1 and 4 as terminals.

For .005  $\mu\text{F}$

Cut leads 2 and 4 from a UGA-1 "Universal". Use leads 1 and 3 as terminals.

For .001  $\mu\text{F}$

Cut lead 2 from a UGA-2 "Universal". Solder lead 3 to lead 4. Use leads 1 and 4 as terminals.

For .002  $\mu\text{F}$

Cut lead 4 from a UGA-2 "Universal". Solder lead 2 to lead 1. Use leads 1 and 3 as terminals.

For .0033  $\mu\text{F}$


Cut lead 4 from a UHK-1 "Universal". Solder lead 3 to lead 1. Use leads 1 and 2 as terminals.

For .01  $\mu\text{F}$

Cut lead 1 from a UHK-2 "Universal". Solder lead 4 to lead 2. Use leads 2 and 3 as terminals.

For .015  $\mu\text{F}$

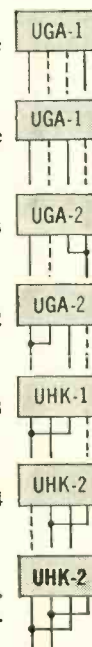Solder lead 3 to lead 1 on a UHK-2 "Universal". Solder lead 4 to lead 2. Use leads 1 and 2 as terminals.



# SPRAGUE®

world's largest capacitor manufacturer





Belden 8411

**If it's worth Engineers' time . . .**

Belden 8422

**. . . It's worth Engineered Cable**

Belden 8412

**Belden  
microphone  
cables**

Whatever the installation,  
whatever the requirements,  
there is an accurately  
rated Belden Microphone  
Cable built for the job.



**Belden**

WIREMAKER FOR INDUSTRY  
SINCE 1902  
CHICAGO


4-8

1001 WIRES FOR EVERY ELECTRONIC NEED



# PHAOSTRON

# 666 VOM

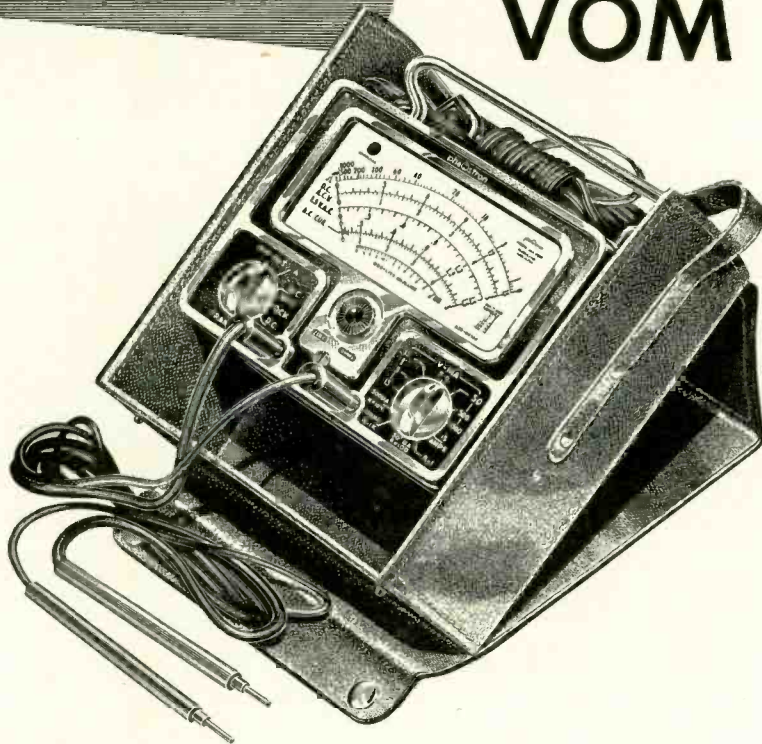

**METER OVERLOAD PROTECTION AND OVERLOAD SIGNAL LIGHT.** It is fused to prevent most common burn-outs and instrument damage. The 666 has complete meter movement overload protection. An overload signal light warns the operator of overloads, or incorrect polarity.

#### RAPID, RELIABLE AND ACCURATE MEASUREMENTS

43 Unduplicated Ranges.  
Long (4  $\frac{7}{8}$ " ) Scales are Color-Coded for clarity.  
Illuminated Dial for easier reading.

**AC CURRENT RANGES (from 1.5 MA to 15 Amps) MEAN FEWER INSTRUMENTS TO CARRY**

#### RELIABLE PERFORMANCE

Doubly Shielded 45 UA movement assures continuous accuracy.  
Permanent Accuracy 3% DC, 4% AC.  
Sensitivity: 20,000 Ohms/Volt DC, 2,000 Ohms/Volt AC.

#### CONVENIENT TO CARRY

This instrument, with its unbreakable steel case, fits into the provided handsome leather carrying case which has space for all accessories.  
Lightweight: 4 lbs. 4 oz.  
Compact: 3  $\frac{3}{4}$ " x 6  $\frac{5}{8}$ " x 7  $\frac{1}{2}$ ".

Complete with Probes, Power Cord, Batteries and Leather Carrying Case at your Parts Distributor. **\$59.50**

## PHAOSTRON INSTRUMENT AND ELECTRONIC COMPANY

151 Pasadena Avenue, South Pasadena, California

EXPORT: Ad. Caricoma, Inc., 89 Broad St., New York, N.Y.

## RADIO

# IDENTIFYING TRANSISTORS

By HENRY A. KAMPF\*

**T**HERE are more than 15 transistor manufacturers in the United States today and the total number of transistors manufactured has been estimated in excess of 50 million. The industry has grown rapidly with new processes developed daily and new types of transistors being put on the market every few weeks. However, very little energy has been directed at standardizing transistor type or lead designation with the result that almost every manufacturer has a different way of identifying his transistors. This necessitates having a complete manufacturers' data sheet for each type of transistor before it can be used.


In many instances the transistors have been available while their data sheets were, for some reason or another, not to be had for any price. This usually happens if the manufacturer decides to discontinue the transistor type and it becomes obsolete. These transistors can still be used by applying the method described here to determine the lead connection and transistor type. This will provide the starting point for measuring the other transistor characteristics should they be required.

The following information may be obtained:

1. The base lead
2. Polarity (p-n-p or n-p-n)
3. The emitter and collector leads
4. Type (point contact or junction)


The procedure listed below requires 10 simple resistance measurements made using an ohmmeter similar to the Simpson model 260 VOM (20,000 ohms per volt). Any given pair of leads of the transistor will show diode action; the resistance measured with the ohmmeter connected one way will be much lower than with the leads reversed. The low resistance is called the forward resistance, the high the back or reverse-bias resistance. The resistance measurements should be made with an ohmmeter whose lead polarity is known. If the ohmmeter leads are not marked, they can be determined by using another voltmeter.

\* Engineering Div., Link Aviation, Inc.

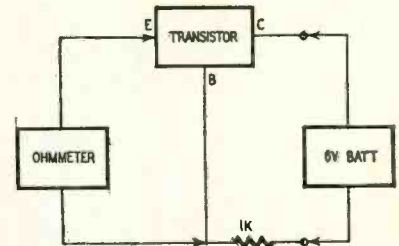

Determining type of transistor.

**MOST ACCEPTABLE**

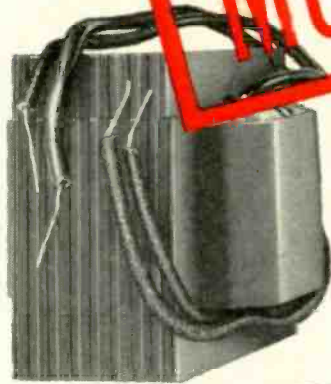

FROM DELCO RADIO

come the **transformers**  
with high acceptability.

You trust them...  
so do your customers!



Universal vibrator transformers, produced through the combined electronic skills of Delco Radio and General Motors, meet the requirements of nearly every model of auto radio. Each is designed for easy installation and complete customer satisfaction. Laminated core inserts are stamped out of low-loss silicon steel and heat treated to maintain correct magnetic properties. Coils are precision-wound on special machines. All models have ample leads. Your UMS-Delco Electronic Parts Distributor can supply you with all models. Call him today. Remember, the Delco Wonder Bar Radio is being nationally advertised in leading consumer publications... so you are tuned in on a constantly increasing service.

Uncased Models 6055, 6065, 6067  
do not include filter network

Cased Models 6060, 6064 and 6066 are made with "A" line filter network consisting of an "A" choke and .5 mfd. capacitor. Easy-mount drilling template, plus three self-tapping screws are included for your convenience.

**DELCO**



**RADIO**


DIVISION OF GENERAL MOTORS, KOKOMO, INDIANA



A GENERAL MOTORS PRODUCT—A UNITED MOTORS LINE  
Distributed by Delco Electronics Parts Distributors

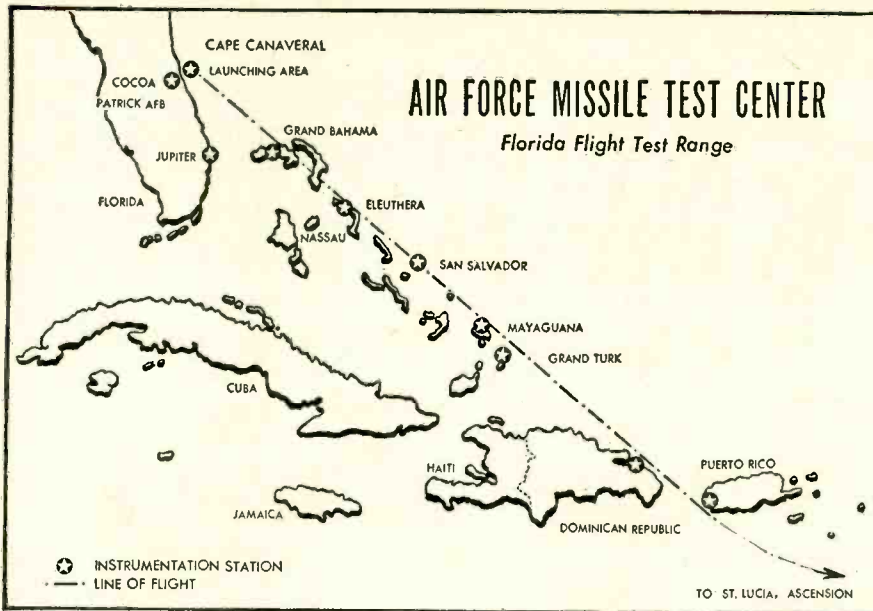A complete line of original equipment service parts from the  
**WORLD LEADER IN AUTO RADIO**





# RCA

ANNOUNCES OPPORTUNITIES

## In Guided Missile Test Instrumentation For Electronic Technicians

At the following locations

### PATRICK AIR FORCE BASE, FLORIDA

Engineering development technicians  
Radar  
Communications  
Test Equipment

### CAPE CANAVERAL

Radar  
Radio  
Telemetry  
Timing  
Telephone  
Optics

Enjoy pleasant Florida living and working at these locations.  
Liberal company benefits. Relocation assistance.

### INTERESTING DOWN-RANGE ASSIGNMENTS

Radar	Telemetry	Telephone
Radio	Timing	Optics

These positions are located on the Islands shown on the map above. Salary, 30% incentive, meals and lodging furnished. Return to U.S. every 3 months.



For information and arrangements for personal interview, send complete resume to:

Mr. H. C. Laur  
Technical Employment, Dept. N-15F  
Missile Test Project  
RCA Service Co., Inc.  
P.O. Box 1226, Melbourne, Florida



RADIO CORPORATION of AMERICA

## RADIO

**CAUTION:** Do not permit a current larger than 1 ma to flow through the transistor. If the current delivered by the ohmmeter is not known, it should be checked with a milliammeter. Some ohmmeters use currents as high as 100 ma. The Simpson model 260 is usable if only the two highest resistance ranges are used.

1. The first lead determined is the base lead of the transistor, found by measuring the three forward resistances of the transistor from lead to lead. The highest forward resistance is that between the emitter and collector. Therefore, the unused lead is the base lead of the transistor.

2. The transistor may now be classified as to polarity, p-n-p or n-p-n. With the negative lead of the ohmmeter connected to the base, connect the positive terminal of the ohmmeter alternately to the other two transistor leads. If forward-resistance measurements are obtained, the transistor has a p-n-p polarity. Note that the real positive lead of an ohmmeter may be the nominal negative (common). Check the leads with a dc voltmeter.

3. The emitter and collector leads have been identified as a pair and can now be individually identified. Connect the ohmmeter to them to read the forward resistance and note the position of the positive lead. If the polarity of the transistor is p-n-p, the positive lead will be at the emitter; if the transistor is an n-p-n type, the positive ohmmeter lead will be at the collector.

4. A point-contact transistor can easily be distinguished from a junction transistor by its negative emitter-base resistance. Connect the ohmmeter as shown in the diagram to measure the emitter-base forward resistance. (The positive lead is connected to the emitter for p-n-p polarity.) Momentarily connect the 6-volt battery so that it will give a reverse bias to the collector. The emitter-base forward resistance for a junction transistor will drop to about one-half its value when the reverse bias is connected to the collector. However, if the transistor is a point-contact type, the resistance indication will go past the zero point and indicate a negative resistance when this reverse bias is applied. END



# new Records



MONITOR

Note: Records below are 12-inch LP and play back with RIAA curve unless otherwise indicated.

**SCHUBERT: Sonata in A minor**

*Sonata in A major*

Friedrich Wuhrer, pianist

Vox PL-9130

A really faithful reproduction of the piano is still the hardest thing to find on records. Because Mr. Wuhrer does not believe in wasting delicacy where he feels the composer calls for brawn, he does a particularly good job in bringing out that very difficult bass end of the keyboard with some resemblance to the genuine in-the-flesh article. He is one pianist who can make the piano sound forte and bring out the characteristic sympathetic resonances and beat notes. This is one of the best and should please both lovers of the piano and high fidelity. It is played in a live room and when played back in a moderately dead one sounds as if the loud pedal were held down continuously—proof that hanxover and room resonance are fraternal twins.

**HAYDN: The Creation**

Soloists, Chorus and Vienna State Opera Orchestra, Mogens Woldike, conducting

Vanguard VRS-471/2

If, like myself, you have never cared much for oratorios, cantatas and the like, here is a version of one of the greatest of all of them which may well convert you if you give it a chance. As usual it is sung in the original German, but the commentary includes text in German and immediately beside it a literal English translation making it easy to follow the sense, particularly since the diction is much clearer than usual. With an understanding of the words the music acquires meaning and delightfulness and it is easy to see why it has been for so long one of the classics. But whether one understands the words or not, the overall effect of the sound is notable for the excellent balance of voices and orchestra and the fine definition. If you want to demonstrate to a choral conductor or teacher, this is superb fare.

**MILLOECKER, Karl: The Beggar**

*Student*

Soloists, Chorus and Vienna State Opera Orchestra, Paulik conducting.

Vanguard VRS-474/5

Miloecker was a contemporary of the Viennese Strausses and *The Beggar Student* was a highly popular comic operetta of the day; it is still popular on the continent. It is sung in German but English and German texts side-by-side make the plot easy to follow. The music has the authentic lilt and the recording is highly exceptional.

**Flamenco**

Solo guitar played by Mario Escudero  
Folkways FP-920 (10-inch LP)

Virtuosos of the Spanish guitar are almost incredible in their agility and provide some exceptional demonstration and test material, particularly the various transients which accompany picking, slapping and plucking the instrument. This is not as good in this latter respect as the Almeida disc (Capitol P-8295) but evidences a more effortless mastery of the instrument. The machine-gunlike bursts of tran-

# Simpson...the most Complete Line of VOM's

Select the one that fits your needs!

MODEL


## 260

world's most popular!

Over half a million Model 260's have been sold to date! 20,000 Ohms per volt. You'll find it wherever quick, accurate, electrical checks are needed. It's so handy, so dependable, so sensibly priced! Ask your jobber. Price, including Adjust-A-Vue Handle, only


**\$38.95**

Carrying Cases from **\$6.75**

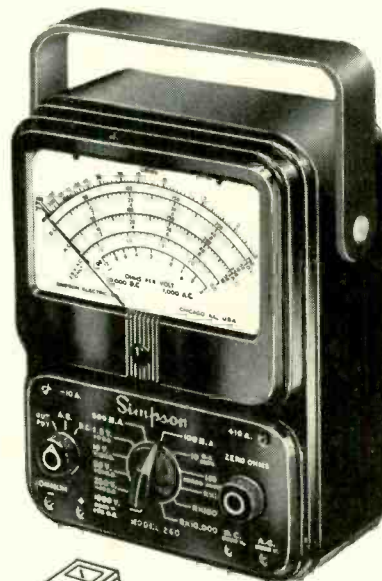

MODEL 262

Deluxe!

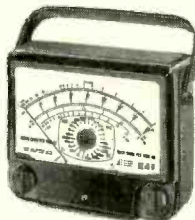

the new VOM with a 7" meter


20,000 Ohms per volt DC and 5,000 Ohms per volt AC sensitivity... 33 ranges... compact 7" case with Adjust-A-Vue Handle

**\$59.50**

Carrying Case **\$ 9.95**

MODEL 269

100,000 Ohms per volt!

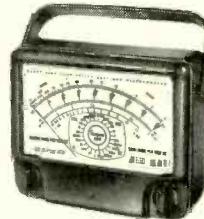

Most sensitive VOM

available! A Volt-Ohm-Microammeter with a big 7" meter in a compact 7" case... 33 ranges... Adjust-A-Vue Handle

**\$88.00**

price complete... **\$ 9.95**

**NEW!**

- ➔ MIDGETESTER Model 355—New shirt-pocket size Volt-Ohmmeter **\$29.95**
- MODEL 240—Small VOM; 14 ranges; up to 3000 volts AC or DC **\$26.35**
- MODEL 230—Small VOM; 12 ranges; up to 1000 volts AC or DC **\$24.95**
- ROTO RANGER Model 221—25 Separate meters at turn of a switch **\$75.00**
- LABORATORY STANDARD—For instrument calibration. Price on application.

# Simpson ELECTRIC COMPANY

World's Largest Manufacturer of Electronic Test Equipment

5200 W. Kinzie St., Chicago 44, Ill.

• Estebrook 9-1121

In Canada: Bach-Simpson, Ltd., London, Ontario



# WIN-TRONIX

## Makes Sweep and Sync Circuit Trouble-Shooting Easy! LOW-COST DYNAMIC SWEEP CIRCUIT ANALYZER

for  
Black-and-White TV  
and color too!  
only

**\$69<sup>95</sup>**

dealer net



Model 820

TWO  
INSTRUMENTS  
IN ONE

1. Horizontal and vertical sawtooth-square wave and sync pulse generator.
2. Complete compatible flyback and yoke tester.

### ISOLATE SWEEP/SYNC TROUBLES RAPIDLY IN FIVE EASY STEPS!!!

#### 1. VERTICAL TROUBLESHOOTING

Inject 60 cps on vertical output grid from "vertical grid drive" jack.



#### 2. HORIZONTAL TROUBLESHOOTING

Inject 15,734 cps on horizontal output grid from "horizontal grid drive" jack.



#### 3. HORIZONTAL TROUBLESHOOTING

Drive horizontal output xfmr directly from "xfrm drive" jack.



#### 4. COMPONENT TESTING

Test flyback transformer and deflection yoke in receiver with Model 820.

#### 5. SYNC CIRCUIT TROUBLESHOOTING

Inject vertical and horizontal sync pulses, stage by stage, in sync amplifiers, with accessory probes.

#### SPECIFICATIONS

Signal Outputs  
15,734 cps sawtooth and pulse adjustable.  
15,734 square wave adjustable.  
60 cps sawtooth locked to line.  
Overload indicator for safety and test.  
Oscillating neon indicator with D.C. amplifier for flyback/yoke test. Calibrated for color and black-and-white.  
Test leads supplied.  
Operates on 105-125 VAC.

### OTHER WIN-TRONIX LOW-COST TV TEST INSTRUMENTS—

Buy Now for Bl. & Wh. Service—be ready for color!

WHITE DOT—Linearity  
Generator

Model  
160



**\$79.95**

RAINBOW GENERATOR

Model  
150



Patent Pending **\$49.95**

COMPATIBLE FIELD  
STRENGTH METER

Model  
330



**\$129.95**

FLYBACK AND YOKE  
TESTER

Model  
810



**\$29.95**

- Compatible advanced design prevents obsolescence!
- Low cost with high quality!
- Portability!
- Standard warranty on all instruments!

SEE YOUR PARTS JOBBER!

WRITE FOR FREE LITERATURE!

COMPATIBLE CRYSTAL  
CALIBRATOR

Model  
120



**\$59.95**

## WINSTON ELECTRONICS, INC.

RE-656

4312 Main St., Philadelphia 27, Pa.

### NEW RECORDS

(Continued)

sients in spots, are, however, most demanding and provide a good measure of transient response. The disc comes with a booklet which tells the story of the flamenco and the guitar's part in them in detail.

#### SIBELIUS: *Symphony No. 4*

*Pohjola's Daughter*

Anthony Collins and London Symphony Orchestra

London LL-1059

Since this year celebrates the 90th birthday of Sibelius there will, no doubt, be a flood of Sibelius recordings and a brilliant Sibelius record such as this London recording would make an appropriate gift. Like most of Sibelius' music this is somber stuff with not too memorable melodies. But from a hi-fi point of view it gives the double basses a nice workout and with a horn or other large speaker should vibrate the floor nicely. Also notable are the typically snarling Sibelius brass chords, especially in the *Pohjola's Daughter*. The strings have the characteristic *ffrr* sharpness.

#### Erin o Erin

A Thomas Moore Suite, Richard Ellsasser at the Baldwin Organ

MGME 3205

The Irish especially will enjoy this potpourri of classic Irish songs but the Baldwin organ will sound impressive on any fair to middlin' hi-fi outfit, particularly because the bass is well furnished with harmonics to energize small speaker systems and provide the illusion that they are radiating a real pedal fundamental.

#### Vocals

Voices provide fine tests for naturalness because all of us are more familiar with their natural sound than we are with that of musical instruments. Unfortunately, in operatic and recital vocals the voice is too artificial in style to be familiar and popular vocals are so gimmicked up with miking tricks, echo boxes, etc., that any resemblance to the genuine human voice is coincidental. Here, however, are a few late records which do provide excellent examples of un-gimmicked human voices and therefore good test material for naturalness, presence, etc.

#### Paris After Midnight

Liane with Boheme Trio

Vanguard VRS-7025

#### Night and Day (Cole Porter Songs)

Liane with Boheme Trio

Vanguard VRS-7029

If you like your music as background to romancing, this over a fine hi-fi outfit can be as good an ally as you can find. The music is of the romantic mood type. The piano is very nice, the guitar is delicate, the double bass is unobtrusive but deep and well defined. As for Liane, her voice is so natural in its husky continental intimacy and emotional shading you may think it is being softly sung in your ear by your companion.

#### The Mitchell Boys Choir

Hifirecord R-301

The featured solo voices especially are presented with tremendous presence and naturalness—assuming you can picture yourself in the conductor's position—and the nuances of each youthful voice are wonderfully defined. The organ accompaniment has a fine pedal bass. The music consists of an even dozen favorites like *Come Back to Sorrento*, *The Happy Wanderer*, *Oh What a Beautiful Morning*, *El Rancho Grande*.

#### Dick Stewart Sings

Hifirecord R-401

Stewart is a crooner but this recording is free of the usual crooner effects with the result that the voice is so natural that its inadequacies of tone, pitch and volume are all too clearly defined. The accompanying Wurlitzer, electric guitar, drums, harp, bass and sax provide some listenable and impressive high-highs, bass, percussive, etc. The organ high-highs on the 1-inch pipes are especially sharp. END

Name and address of any manufacturer of records mentioned in this column may be obtained by writing Records, RADIO-ELECTRONICS, 154 West 14th St., New York 11, N.Y.

MISCELLANY



THE FUND REACHES  
\$12,019.36

**HELP -  
FREDDIE-WALK  
FUND**

THE Help-Freddie-Walk Fund has just received a very encouraging letter from Herschel Thomason, service technician of Magnolia, Ark., and father of 8-year-old Freddie, who, as most of our readers know, was born without arms or legs.

Freddie was fitted with legs some time ago and has learned to use them almost as well as any normal child. A short while ago he was fitted with his first arm, and it has opened up a new world of experience for him. As the accompanying photo shows, Freddie is learning to feed himself.

His father writes: "He is still doing very well with his arm and uses it all the time. He can wear it all day long without tiring and, as far as the basic movements are concerned, he has mastered it completely.

"He also walks very well on the new legs he received on his last trip. They are about 3 inches longer and quite a lot bigger than the previous ones. When he has his arms and legs on now, he really looks grown up."

Freddie has received some wonderful letters in the last 3 months. Bobby Hoffman, of Richmond, Va., writes:

"I was born the same day and the same year that you were (March 31, 1948). I hope that you are being taken good care of. I hope that you receive much greater help than my dollar from many, many more friends."

And another friend of Freddie's, who prefers to remain anonymous, has written to the Fund: "I am indeed happy to read of the good progress little Freddie is making. Glad to see that the Fund is growing and that you are still promoting this wonderful endeavor—it is a brilliant ray of light, shining through this age which tends toward overcommercialism."

Mr. W. H. Nicholson, of Voiture 370 of the 40 and 8 Society, sent the following along with their donation: "The primary purpose of our organization is child welfare and we are always interested in giving our help so that it will benefit some child.

"We feel that your Fund is an excellent cause and by unanimous vote the membership of Voiture 370 expressed its desire to assist in some small way. Please accept this donation with our best wishes."

We would also like to make special note of contributions received from the Philadelphia-Camden Chapter of the National Radio Institute Alumni Assn. and from the Newport County Radio Club, Newport, R. I., whose members are making their second donation to the Fund.

The Fund has now topped \$12,000,

but thousands more will be needed before Freddie's growth is complete. The mechanical limbs, upon which he will be dependent all his life, must grow as he does. Therefore we again ask our readers to be as generous as they can in support of this worthy cause.

Any contribution you might be able to make will be acknowledged and sincerely appreciated, no matter how large or small it may be. *Make out all checks, money orders, etc., to Herschel Thomason.* Send all contributions to:

Help-Freddie-Walk Fund  
% RADIO-ELECTRONICS  
154 West 14 Street  
New York 11, New York



Freddie Using His New Arm


RADIO-ELECTRONICS Contributions as of Jan. 10, 1956	\$11,272.23
FAMILY CIRCLE Contributions	602.50
Anonymous, Ontario, Canada	2.00
Anonymous, APO 858, New York, N.Y.	10.00
Anonymous, Aberdeen, Wash.	50.00
Joe Apathy, Sacramento, Calif.	2.50
"Beets," Buffalo, N.Y.	5.00
Corner Drug Store, Lawrence, Mass.	5.00
Dyna Company, Philadelphia, Pa.	10.00
Thomas B. Harvey, St. Louis, Mo.	10.00
Bobby Hoffmann, Richmond, Va.	1.00
Clyde Hudson, Cloverdale, Ore.	2.00
R. Kelly, Richmond, Va.	10.00
La Societe des 40 Hommes et 8 Chevaux, Voiture No. 370, New Britain, Conn.	10.00
H. C. Matzinger, Wyandotte, Mich.	2.00
Howard Merrylees and Family, La Mesa, Calif.	2.00
Newport County Radio Club, Newport, R.I.	5.00
Philadelphia-Camden Chapter of the National Radio Institute Alumni Assn., Philadelphia, Pa.	5.00
Robert Price, Chicago, Ill.	2.00
T. P. Roche, Rock Island, Ill.	1.00
Mr. and Mrs. Luis M Ruiz, Camden, N.J.	2.00
Fred K. Unick, Rockford, Ill.	2.00
Robert G. Watson, Xenia, Ohio	4.13
Herbert J. West, New York, N.Y.	2.00
<b>TOTAL CONTRIBUTIONS as of April 10, 1956</b>	<b>\$12,019.36</b>

The New  
**GOODMANS**



plus  
**YOUR LOUDSPEAKER**

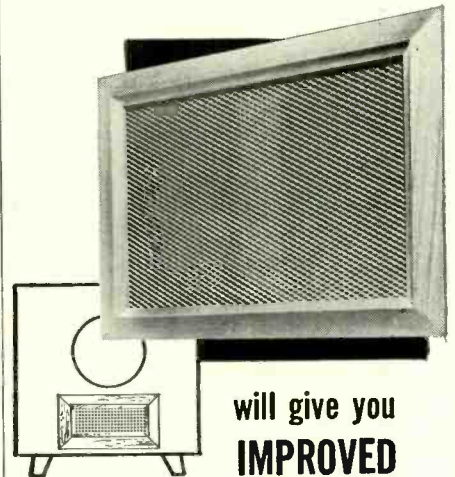plus  
**A SIMPLE ENCLOSURE**  
only two-thirds the size required  
for a bass reflex



will give you  
**IMPROVED  
SPEAKER SYSTEM  
PERFORMANCE...**  
through 'Friction Loading'

- Extended bass response to 20 cycles
- Virtually no peaks above this frequency
- Effective air-loading to zero cycles — greatly reducing distortion due to excessive cone displacement

See your hi-fi dealer, or write for complete details to Dept. RF-9

**ROCKBAR CORPORATION**  
650 Halstead Avenue, Mamaroneck, N. Y.

In Canada: A. C. Simmonds & Sons, Ltd., Toronto, Can.



# RADIO & ELECTRONICS TRAINING AT HOME

Only \$19.95

## BUILD 16 RADIO

CIRCUITS WITH THE DELUX 1956 PROGRESSIVE RADIO "EDU-KIT"

### A Practical Home Radio Course

- ★ No Knowledge of Radio Necessary
- ★ No Additional Parts Needed
- ★ Excellent Background for TV

FREE SET OF TOOLS, TESTER, SOLDERING IRON, HIGH FIDELITY, SIGNAL TRACER, CODE OSCILLATOR, PRINTED CIRCUIT SIGNAL INJECTOR



FREE HI-FI, RADIO & TV SERVICING LITERATURE (See Coupon)

### WHAT THE "EDU-KIT" OFFERS YOU

The "Edu-Kit" offers you an outstanding PRACTICAL HOME RADIO COURSE at a rock-bottom price. Our Kit is designed to train Radio & Electronics Technicians, making use of the most modern methods of home training. You will learn radio theory, construction practice and servicing.

You will learn how to build radios, using regular schematics; how to wire and solder in a professional manner; how to service and trouble-shoot radios. You will work with the standard type of punched metal chassis as well as the latest development of Printed Circuit chassis.

You will learn the basic principles of radio. You will construct, study and work with RF and AF amplifiers and oscillators, detectors, rectifiers, test equipment. You will learn and practice code, using the Progressive Code Oscillator. You will learn and practice trouble-shooting, using the Progressive Signal Tracer, the Progressive Signal Injector, the Progressive Dynamic Radio & Electronics Tester and the accompanying instructional material.

You will receive training for the Novice, Technician and General Classes of F.C.C. Radio Amateur Licenses. You will build 16 Receiver, Transmitter, Code Oscillator, Signal Tracer and Signal Injector circuits, and learn how to operate them. You will receive an excellent background for Television.

Absolutely no previous knowledge of radio or science is required. The "Edu-Kit" is the product of many years of teaching and engineering experience. The "Edu-Kit" will provide you with a basic education in Electronics and Radio, worth many times the complete price of \$19.95.

### THE KIT FOR EVERYONE

You do not need the slightest background in radio or science. Whether you are interested in Radio & Electronics because you want to enter a well-paying business or a job with a future, you will find the "Edu-Kit" a worth-while investment.

Here is an excerpt from a letter that we received from Loren DePriest, 1496 4th St., Manhattan, Ohio: "I have spent many pleasant hours in constructing the radios from the schematics in your book and have learned a great deal from them. Being as I am interested in Radio, I consider the money spent for your course as a wise investment. I have learned more from your course by actually doing, than I did from an expensive course."

Many thousands of individuals of all ages and backgrounds have successfully used the "Edu-Kit" in more than 79 countries of the world. The "Edu-Kit" has been carefully designed, step by step, so that you cannot make a mis-

take. The "Edu-Kit" allows you to teach yourself at your own rate. No instructor is necessary. The "Edu-Kit" is also used for courses of study, extra-curricular activities, industrial personnel training and rehabilitation. The "Edu-Kit" is used by Jr. High Schools, High Schools, Technical Schools, Jr. Colleges, Colleges, Universities, Industrial firms, Rehabilitation Hospitals, Boards of Education, U.S. Govt. agencies, United Nations Educational, Scientific and Cultural Organizations (UNESCO), and numerous adult, radio and young peoples' groups and clubs. The "Edu-Kit" is also popular with servicemen and veterans throughout this country and abroad.

Designed for universal use, the "Edu-Kit" operates on any voltage from 105 to 125 volts, AC and DC. For use in countries employing higher line voltages, a 210-250 Volt AC/DC model is available.

### PROGRESSIVE TEACHING METHOD

The Progressive Radio "Edu-Kit" is the foremost educational radio kit in the world, and is universally accepted as the standard in the field of electronics training. The "Edu-Kit" uses the modern educational principle of "Learn by Doing." Therefore you construct, learn schematics, study theory, practice trouble-shooting, all in a closely integrated program designed to provide an easily-learned, thorough and interesting background in radio.

You begin by examining the various radio parts of the "Edu-Kit." You then learn the function, theory and wiring of these parts. Then you build a simple radio. With this first step, you will enjoy listening to regular broadcast stations, learn theory, practice testing and trouble-shooting. Then you build a more advanced radio, learn more advanced theory and techniques. Gradually, in a progressive manner, and at your own rate, you will find yourself constructing more advanced multi-tube radio circuits, and doing work like a professional Radio Technician.

### THE "EDU-KIT" IS COMPLETE

You will receive all parts and instructions necessary to build 16 different radio and electronic circuits. Each is guaranteed to operate. Our Kits contain tubes, tube sockets, variable, electrolytic and paper dielectric condensers, resistors, tie strips, coils, hardware, tubing, punched metal chassis, Instruction Manuals, etc.

In addition, you receive Printed Circuit materials, including Printed Circuit chassis, special tube sockets, hardware and instructions. You also receive a useful set of tools, a professional electric soldering iron, and a self-powered Dynamic Radio & Electronics Tester. The "Edu-Kit" also includes Code Instructions and the Progressive Code Oscillator, in addition to F.C.C. type Questions and Answers for Radio Amateur License training. You will also receive lessons for servicing with the Progressive Signal Tracer and the Progressive Signal Injector, a High Fidelity Guide and a Quiz Book.

### TROUBLE-SHOOTING LESSONS

You will learn trouble-shooting and servicing in a progressive manner. You will practice repairs on the sets that you construct. You will learn symptoms and causes of troubles in home, portable and car radios. You will learn how to use the professional Signal Tracer, the unique Signal Injector and the Dynamic Radio & Electronics Tester. While you are learning in this practical way, you will be able to do many a repair job for your friends and neighbors, and charge fees which will far exceed the price of the "Edu-Kit." Our Consultation Service will help you with any technical problems you may have.

J. Stataitis, of 25 Poplar Pl., Waterbury, Conn., writes: "I have repaired several sets for my friends and made money. The "Edu-Kit" paid for itself. I was ready to spend \$240 for a Course, but I found your ad and sent for your Kit."

### FREE EXTRAS

- SET OF TOOLS • RADIO & ELECTRONICS TESTER
- ELECTRIC SOLDERING IRON • TESTER INSTRUCTION MANUAL • MEMBERSHIP IN RADIO-TV CLUB • CONSULTATION SERVICE • HI-FI GUIDE • QUIZZES • TV BOOK

UNCONDITIONAL MONEY-BACK GUARANTEE  
MAIL TODAY—ORDER SHIPPED SAME DAY RECEIVED

Order from ad—receive free bonus resistor kit worth \$5.00

Send "Edu-Kit" Postpaid. I enclose full payment of \$19.95.  
Send "Edu-Kit" C.O.D. I will pay \$19.95 plus postage.  
Send me FREE additional information describing "Edu-Kit." Include FREE valuable Hi-Fi, Radio and TV Servicing Literature. No obligation.  
(Outside U.S.A.—No C.O.D.'s. Send check on U.S. bank or Intern'l M.O. "Edu-Kit" for 105-125 V. AC/DC \$20.95; 210-250V. AC/DC \$23.45.)

Name: \_\_\_\_\_  
Address: \_\_\_\_\_


PROGRESSIVE "EDU-KITS" INC. 497 Union Ave., Room 1176, Brooklyn 11, N.Y.
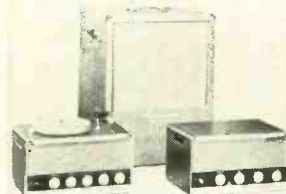
# new Devices



TV ANTENNA KITS, do-it-yourself jobs in display box include instructions. 26 hardware kits labeled from A to Z make up over 150 antenna packages. 6 basic Tescon conical antenna types used: 3 single-bay antennas and stacked versions of each single-bay unit. Hot-dipped galvanized masts complete pre-

paring 10-watt ac amplifier and speaker; 20-watt ac amplifier; 33-watt ac amplifier; two 6-volt




20-watt mobile amplifiers, with single- and 3-speed phono tops. 10-watt models have peak of 18, 30-watt models peak of 28 and 33-watt amplifier peaks at 48.—Bell Sound Systems, Inc., 555 Marion Rd., Columbus 7, Ohio.

assembled all-aluminum antenna construction. Every kit contains all hardware, lead-in wire, mast and other items necessary for complete installation.—Tescon TV Products Co., Inc., Springfield Gardens 13, N. Y.

DUAL AUTOMOBILE RADIO AERIAL for rear-deck installation. Each handy, compact green and yellow display carton contains 2 chrome-plated aerials,

HI-FI EQUIPMENT, PK-100 transcription turntable. PK-90 viscous-damped transcription tone arm and SK-58 12-inch coaxial speaker.

Main spindle and rubber drive

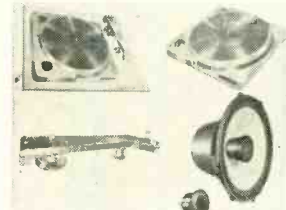

mounts, extension leads, clips and all fasteners. Compact base assembly for top mounting permits simple, speedy installation in restricted space. Sturdy, 3-section aerial masts extend to 30 inches. Built-in antirattlers.—Delco Radio, Div. of General Motors, Kokomo, Ind.

wheel of transcription turntable ball-bearing mounted. Four-pole shaded motor. Variable speed within  $\pm 7\%$  for 33 $\frac{1}{3}$ , 45 and 78 rpm. Wow less than 2%, flutter less than .05%.

PK-90 viscous-damped tone arm has plug-in solderless cartridge holder accommodating all standard cartridges including turnover G-E. Accepts records up to 16 inches; arm height fully adjustable.


SK-58 12-inch coaxial speaker's frequency range 30 to 15,000 cycles; rated at 20 watts maximum input. Cone of specially processed fiber suppresses circular and radial nodal vibrations. Crossover network built in. Voice-coil impedance 8 ohms.—Lafayette Radio, 100 Sixth Avenue, New York 13, N. Y.

CERAMIC CARTRIDGE weighs 4 $\frac{1}{2}$  grams. Uses osmium stylus for 33 $\frac{1}{3}$ - and 45-rpm and sapphire for standard 78-rpm recordings. Turnaround throw-away cartridge snaps in without use of tools.—Elgin National Watch Co., Elgin, Ill.



microphones than were available for earlier enclosure. Few slight changes in internal dimension gave considerable improvement. Available in kit and finished

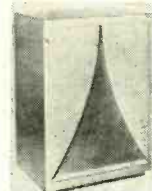IMPROVED SPEAKER ENCLOSURE, Karlson 15. Tested with better test equipment and



microphones than were available for earlier enclosure. Few slight changes in internal dimension gave considerable improvement. Available in kit and finished

COMMERCIAL AMPLIFIERS. Pacemaker line of 8 models and various accessories: 10-watt ac amplifier; 10-watt system com-



# TEST 5 TUBES in 4 SECONDS EACH...ACCURATELY!

WITH THE NEW ADVANCED ENGINEERED

**precise** MODEL 116

**Gm. & Em. ULTRAFAST  
TUBE & TRANSISTOR TESTER**



**Completely  
NEW!**

PRECISE MODEL 116K in kit form. .... **\$69.95**  
PRECISE MODEL 116W factory wired ..... **\$119.95**

Servicemen know the Precise Model 111 (the winner in an independent survey) easily rates "the finest tube tester in the field" at any price, BUT FOR AN ON THE JOB QUICK-TEST . . . the fastest, most accurate is the PRECISE Model 116. What's more you test tubes the foolproof method inherent in the famous Precise Model 111.


Did you ever wish you could plug in 5 of the same type tubes at once and check each one individually by rotating a switch? YOU CAN WITH THE PRECISE MODEL 116—Plug in 5 IF tubes and let them heat up at once and then check each one separately by rotating the TUBE BANK switch. ACTUALLY CHECK 5 TUBES IN 20 SECONDS, 4 SECONDS PER TUBE.

The Precise Model 111 taught the lesson that IF amplifier tubes (like the 6BC5 or 6AU6) should be tested for Gm (mutual transconductance) while the power amplifiers (like the 6L6) should be tested for Em (emission)—that's ULTRAFAST Model 116 test! It checks each section of each tube separately . . . by rotating the FUNCTION SWITCH . . . each triode of a dual triode is checked individually . . . each diode and the triode of a duo-diode-triode is separately tested and not lumped as in other testers . . . and a pentode is tested as a pentode—not a diode. TRANSISTORS, SHORTS, GAS, LIFE, Em, Gm etcetera can be tested with the PRECISE Model 116.


You can inexpensively extend the Precise Model 116 to test filament current, etc. The Model 116 gives an accurate, ultra-fast (3 basic knobs for testing) check of television tubes!

No Surplus—An etched panel—beautiful Moleskin covered wood carrying case and cover and specially simplified instructions makes the PRECISE MODEL 116 THE FINEST FAST-CHECK TUBE TESTER AND DOLLAR EARNING TRAVELING COMPANION A TV SERVICEMAN EVER HAD.

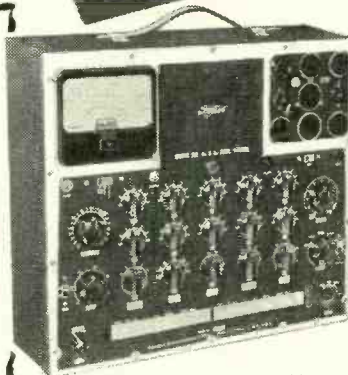Not yet at your distributor. Order NOW to insure early delivery.  
SEE YOUR LOCAL DISTRIBUTOR FOR PROOF OF WHAT WE OFFER — OR WRITE US FOR DOCUMENTARY RESULTS OF AN INDEPENDENT SCIENTIFIC SURVEY.



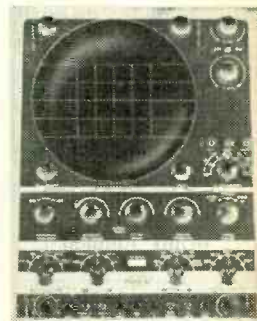
THE FAMOUS MODEL #111  
111K ..... **\$79.95**  
111W ..... **\$139.95**  
Incl. Carrying Case & Cover



THE FIRST LOW PRICED  
7" COLOR SCOPE  
300K ..... **\$99.95**  
300W ..... **\$199.50**



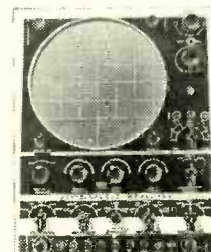LOW PRICED 5" SCOPE  
315K ..... **\$49.95**  
315W ..... **\$84.95**




THE FIRST AND ONLY  
8 1/2" COLOR SCOPE  
308K ..... **\$129.50**  
308W ..... **\$229.50**



LOWEST PRICED  
WIRED 4 1/2" VTVM  
909K ..... **\$25.98**  
909W ..... **\$37.50**



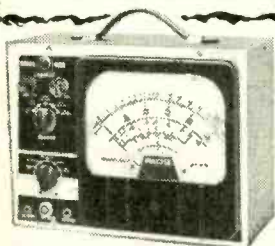RF-AF-BAR GENERATOR  
with pre-assembled\* head  
630K ..... **\$33.95**  
630KA\* ..... **\$38.95**  
630W ..... **\$53.95**



THE FINEST VOLT, REG,  
7" VTVM KIT  
9071K ..... **\$35.95**  
9071W ..... **\$49.95**



LOW PRICED RF SIGNAL GENERATOR  
"BEST BUY" IN GEN. FIELD  
610K ..... **\$23.95**  
610KA pre-assembled head ..... **\$28.95**  
610W ..... **\$39.95**



UNIV. AF, SINE, SQ, & PULSE GEN.  
635K ..... **\$33.50**  
635W ..... **\$52.50**

Prices slightly higher in the West. Prices and specifications subject to change without notice.

PTAK .. **\$2.95**  
PTAW .. **\$4.25**

WRITE FOR CATALOG RE 6-6


SEE THE MANY MORE PRECISE INSTRUMENTS AND PROBES AT YOUR DISTRIBUTOR TODAY!

**precise** DEVELOPMENT CORP. OCEANSIDE, NEW YORK, U.S.A.





Pyramid Electronic / New York

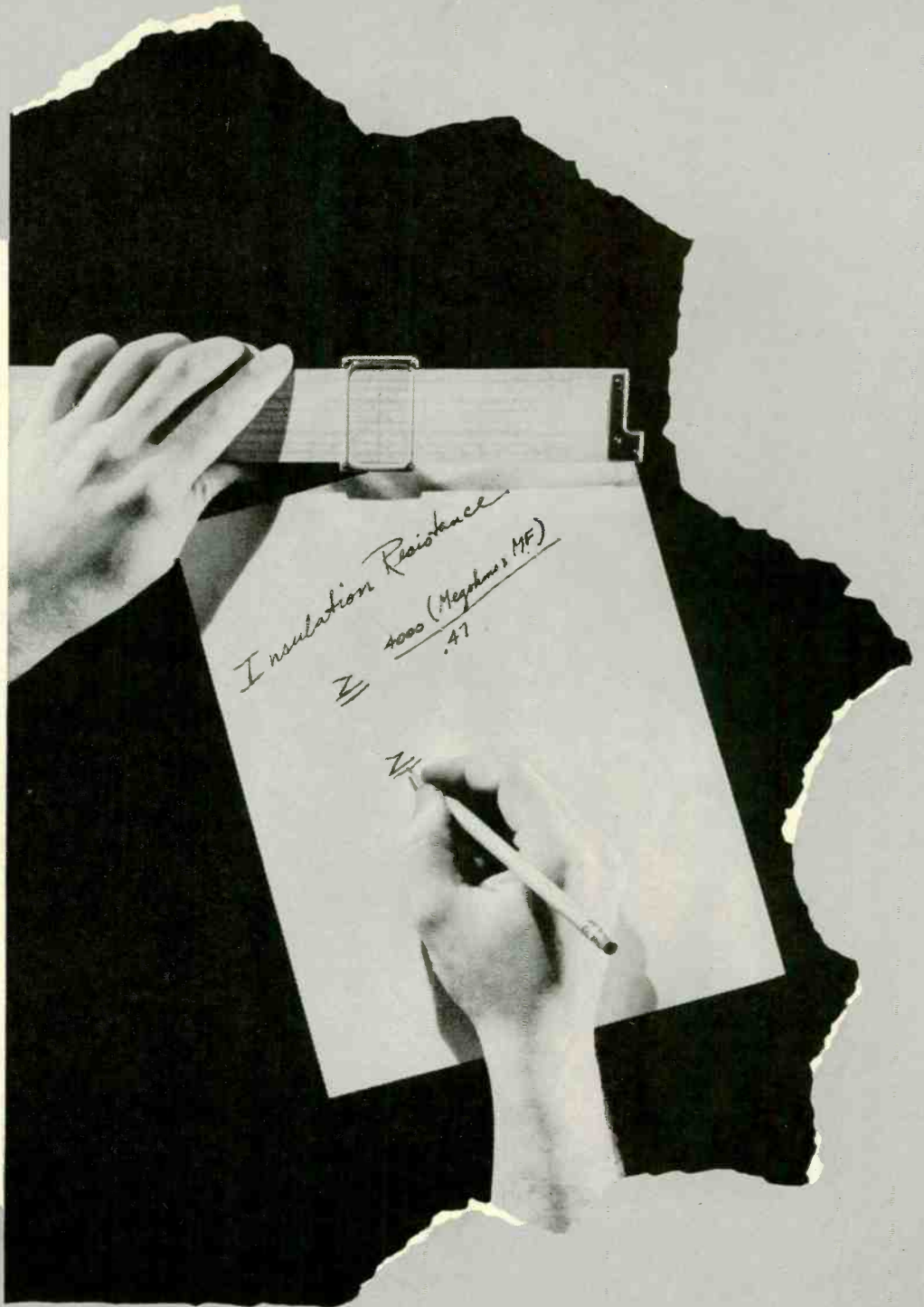

## HE PROVED IT FOR HIMSELF!

The new Pyramid Imp is smaller, yet better than any other molded paper tubular capacitor; Operates at full rating of 100°C (212°F—boiling point); Exceeds moisture resistance requirements of U. S. Government specifications MIL-C-91A; Copperweld leads are securely imbedded to withstand 4 360° bends without breaking.

These features, plus an almost indestructible thermo-setting plastic encasement make Pyramid Imps your best molded paper tubular capacitor.

*For full information on Pyramid capacitors and rectifiers, see your local distributor or write to*



DISTRIBUTOR DIVISION

**PYRAMID** ELECTRIC COMPANY

1445 Hudson Blvd., North Bergen, N. J.

NEW DEVICES

form.—Karlson Associates, Inc., 1610 Neck Rd., Brooklyn 29, N. Y.

**RANGE EXTENDING KIT, SS-1B**, forms 4-way speaker system when used with model SS-1, 2-speaker kit. Super tweeter and 10-inch woofer. Functions between 35-600 cycles and 4,000-16,000 cycles. Combined frequency response of SS-1 and



SS-1B  $\pm 5$  db from 35 to 16,000 cycles. Exposed panels furniture-grade plywood suitable for light or dark finish. Precut and ready for assembly. Instruction manual. Speakers ready for installation and crossover circuit with balance control included.—Heath Co., Benton Harbor 20, Mich.


**SELENIUM RECTIFIERS**, high-current density type, almost 50% smaller and lighter than



conventional selenium stacks. New process enables current


density in forward direction to be considerably increased while maintaining same voltage drop as conventional cells. Cell size for given output can be reduced. Operate safely at higher voltages and temperatures than before. Mechanical ruggedness of conventional cells while permitting miniaturization.—Component Div., Federal Telephone & Radio Co., 100 Kingsland Rd., Clifton, N. J.

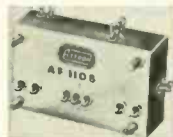**NOISE-SUPPRESSION FILTER, AF1108**, miniaturized rf type. Surpasses requirements of specification MIL-1-11748. 14 toroids and 8 capacitor sections, suppression range of 0.15 to 1,000 mc. Withstands great



amounts of shock and vibration as well as high temperatures. Hermetically sealed, extremely small size and lightweight. Can be custom-engineered without shape limitations. For portable field equipment.—Astron Corp., 255 Grant Ave. E. Newark N. J.

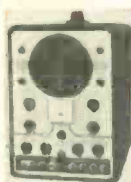**OSCILLOSCOPE, model 3441-A**, 5-inch instrument featuring multivibrator type sweep generator with rates to 60 kc, retrace blanking, meter for 0-3 and 0-10-volt peak-to-peak calibrations, Z-axis modulation, trace inversion and a 4-position compensated vertical attenuator. Narrow-band vertical response



10 cycles to 200 kc, wide-band response  $\pm 3$  db from 10 cycles to 4.5 mc in 3 positions of the input attenuator. Vertical input impedance: 2.2 megohms shunted by 20  $\mu$ f with low-capacitance probe and 2.2 megohms shunted by 45  $\mu$ f at input terminals. Horizontal response 20 cycles to 150 kc with sensitivity of 0.15 volt rms per inch.—Triplett Electrical Instrument Co., Bluffton, Ohio

**HORIZONTAL TRANSFORMER, HVO-53** high-voltage output, exact replacement for Zenith parts Nos.: S-15015, S-15709, S-15911, S-15912, S-16191, S-



16204, S-16566, S-17130, S-17140, S-17233, S-17244, S-17245, S-17265, S-17435, S-17646, S-17669, S-17767, S-17812, S-17925, S-17939, S-18125, S-18487, S-18537, S-18930, S-20908.—Merit Coil &

(Continued)  
Transformer Corp., 4427 N. Clark St., Chicago 40, Ill.

**PICTURE TEST TUBE AND YOKE ASSEMBLY** permits quick positive checks without removing parts from set. 5AXP4 tube, universal yoke and 6-foot extension leads for extending C-R tube socket, anode and yoke



connections. Lightweight leatherette case. Each part can be used as separate unit or in combination. Self-focusing and works with electrostatic or electromagnetic designs and with 52, 70, 72 and 90° yokes. Requires no ion trap. Complete unit or as assembly without tube.—Telematic Industries Inc., 16 Howard Ave., Brooklyn, N. Y.

**3 1/2-INCH RECTANGULAR CUSTOM METER**, features die-cast bezel finished in either pol-



ished chrome and black or solid black. Obtainable in colors to

Get This Valuable Book

**FREE**



Yes, you get this big, brand new book, "150 Radio-Television Picture Patterns and Diagrams Explained", absolutely FREE! Just off the press. Gives complete 11 x 22" Schematic Diagrams on leading models Radio and TV Sets. Easy-to-read, large 8 1/2 x 11" pages, with full instructions on how to use the diagrams. A "must" in every repair kit. You get this book as a FREE Gift for asking to see Coyne's new 7-book set, "Applied Practical Radio-Television"!

At Last! Money-Making "Know-How" on Transistors, Color TV and Servicing

Coyne's great 7-volume set gives you all the answers to servicing problems—quickly! For basic "know-how" that's easy to understand you'll find everything you want in Volumes 1 to 5 on over 5000 practical facts and data. Every step from fundamentals to installing, servicing and trouble-shooting all types of radio and TV sets. So up-to-date it covers COLOR TV, UHF and the latest on TRANSISTORS. All this plus Volume 6—NEW Coyne TECHNICAL DICTIONARY with over 4000 definitions of the latest terms, symbols and abbreviations in radio-TV, electronics and electricity.


EXTRA! 900-Page Television Cyclopeda Included

And then, for speedy on-the-job use, you get volume 7—the famous Coyne TELEVISION CYCLOPEDIA. It answers today's television problems on servicing, alignment, installation, etc. In easy-to-find ABC order, cross-indexed. Use this 7-volume TV-RADIO LIBRARY FREE for 7 days; get the Servicing Book ABSOLUTELY FREE!

Just For Examining COYNE'S New Set

"Applied Practical Radio-Television" on 7 DAY FREE TRIAL!

NOW!  
7 BIG BOOKS IN ONE GREAT SET!

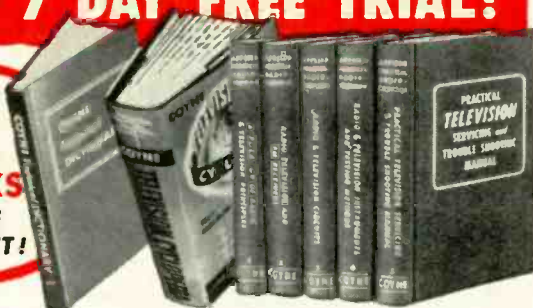

SEND NO MONEY! Just mail coupon for 7-volume set on 7 days free trial. We'll include book of 150 TV-Radio Patterns & Diagrams. If you keep the set, pay \$2 in 7 days and \$2 per month until \$24.50 plus postage is paid. (Cash price, only \$22.95). Or you can return the library at our expense in 7 days and owe nothing. YOU BE THE JUDGE. Either way, the book of TV-Radio Patterns is yours FREE to keep! Offer is limited. Act NOW!

FREE BOOK—FREE TRIAL COUPON!

Educational Book Publishing Division  
COYNE ELECTRICAL SCHOOL, Dept. 66-T1  
500 S. Paulina St., Chicago 12, Ill.

YES! Send 7-Volume "Applied Practical Radio-Television" for 7 days FREE TRIAL per your offer. Include TV-Radio Patterns & Diagram Book FREE.

Name..... Age.....  
Address.....  
City..... Zone..... State.....

Where Employed  
 Check here if you want library sent C.O.D. You pay postman \$22.95 plus C.O.D. postage on delivery. 7-day money-back guarantee.

Educational Book Publishing Division  
**COYNE** ELECTRICAL SCHOOL  
500 S. Paulina St., Dept. 66-T1, Chicago 12, Ill.



# 1<sup>st</sup> COMPLETE LINE of ELECTRONIC TOOLS


ever offered the industry

**HUNTER** Tools, originators of the TV Slug Retriever, now offer the only *complete* line of Electronic Hand Tools available.

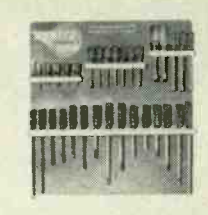**Famous Hunter Tools . . .**

- \* SLUG RETRIEVERS
- \* SCREWOLDING SCREWDRIVERS
- \* NUT DRIVERS
- \* DURA TIP SCREWDRIVERS
- \* SPIN DRIVERS
- \* INSULATED DRIVERS
- \* BELT TOOL KITS
- \* HEX DRIVERS
- \* DRIVE ALL JUNIOR
- \* SMITTY (Allen Type) DRIVERS
- \* TENSION TWEETIE
- \* HOT TUBE PULLERS
- \* ALIGNMENT TOOLS
- \* SEPARATELY OR COMPLETE KITS

**jobbers . . .**  
Order your matched displays, today!  
**DISPLAYS THAT COMPLIMENT YOUR STORE**



**SERVICE MASTER #100**



**SERVICE MASTER #500**

Write for a free copy of our new complete catalog, today!

**HUNTER TOOLS**  
Box 564  
Whittier, California

ALL TOOLS IN SIZES TO FIT YOUR SPECIFIC NEEDS! TOOLS DESIGNED FOR THE ELECTRONIC INDUSTRY.



**Converts Battery Radio to Electric Operation!**



**At All Distributors**

manufactured by  
**Perma-Power COMPANY**  
4727 N. Damen Ave., Chicago 25, Ill.  
manufacturers of electronic equipment since 1928  
Export: SCHEEL INT., Chicago

Watch for the July RADIO-ELECTRONICS

On Sale June 26

Always mention RADIO-ELECTRONICS

when you answer advertisers.

NEW DEVICES (Continued)

match or blend with panels. Self-illuminated if desired. Metal case will not chip, shatter or warp, and gives antimagnetic shielding. Available in all standard ranges and may be ordered with special ranges.—**Phaotron Instrument & Electronic Co.**, 151 Pasadena Ave., S. Pasadena, Calif.

**4 1/4-INCH RECTANGULAR METERS**, models 68 and 69, ac and dc models for semiflush panel-mount applications, sup-



plied with or without illumination. External zero adjust provided in all cases. Wide variety of ranges.—**Hickok Electrical Instrument Co.**, 10531 Dupont Ave., Cleveland 8, Ohio


**SELENIUM RECTIFIER TESTER**, *Win-Tronix* model 610. Gives complete test by continuously pulsing rectifier under actual load conditions. Flashing red light acts as monitor to show pulsing action. Rectifier quality as well as shorts, leakage and



open-circuit conditions indicated on multicolor good-bad meter scale. 5 fixed resistor loads calibrated to test rectifiers from 20 to 1,000 ma. Fixed resistor loads avoid instrument burnouts and give increased accuracy.—**Winston Electronics, Inc.**, 4312 Main St., Philadelphia 27, Pa.

**8 NEW REPLACEMENT FLYBACKS** for Admiral, Emerson, Motorola, Philco, Wells-Gardner, Westinghouse, Airline, Firestone, Raytheon, Truetone, Bendix TV receivers. Electrically and mechanically interchangeable with original equipment.—**Triad Transformer Corp.**, 4055 Redwood Ave., Venice, Calif.

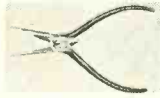**KLEIN SPRING PLIERS**. Coil spring keeps pliers open. Available for pliers offered in past



with leaf or volute springs.—**Mathias Klein & Sons**, 7200 McCormick Rd., Chicago 45, Ill.

**CONNECTOR**, rack and panel type, 40 contacts. Narrow for crowded installations. Flashover rated at 1,700 volts, 60 cycles




at sea level. Weight of mated connector 0.381 pound.—**Cannon Electric Co.**, 3209 Humboldt St., Los Angeles 31, Calif.

**LIGHTNING ARRESTER**, G-C No. 8642, intended for use with



every type of vhf and uhf TV lead-in lines. Universal type. Can be used either indoors or outdoors.—**General Cement Mfg. Co.**, 919 Taylor Ave., Rockford, Ill.

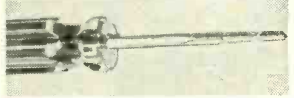**TRI-TAP** cleans or cuts any of 3 most common thread sizes in



conventional electrical boxes, fixtures, gutters, etc., without changing taps. Contains 6/32, 8/32, 10/32 taps.—**Hunter Tool**, Box 564, Whittier, Calif.

**UNUSUAL TEST ADAPTER**, *Rotoprobe*, facilitates measuring socket voltages, resistances and waveforms from above chassis. Adapter inserts between tube and socket. Built-in test lead



connects to measuring equipment. Outer shell of adapter rotated to switch to desired tube element or pin connection. Available in 7-pin miniature, octal and 9-pin noval types.—**Vector Electronic Co.**, 3352 San Fernando Rd., Los Angeles 65, Calif.

**WAVEGUIDE SWITCH**, model G14H2AX, vswr 1.05 maximum in position, 1.15 maximum during switching; crosstalk 45 db minimum; actuator, 28 volts dc;



actuation time, 0.5 second maximum; power-handling ability approximately 0.35 megawatts CW.—**Electronics Div., Thompson Products, Inc.**, 2196 Clarkwood Rd., Cleveland 3, Ohio

**7 ALIGNMENT TOOLS** for quicker servicing of color and late-model b-w TV sets: Walsco catalog Nos. 2541-2547; double-



ended; have hex-end diameters varying from .075 to 0.125 inch for fitting all currently used slug openings. Ends undercut on one side. No. 2541 for TV sets using if cans with smaller than standard openings. No. 2544-2547 11 inches long to minimize hand capacitance.—**Walsco Electronics Corp.**, 3602 Crenshaw Blvd., Los Angeles 16, Calif. END

All specifications given on these pages are from manufacturers' data.



new

# Tubes

# Transistors



This month has proved especially fruitful with the unveiling of some highly interesting items. Of special interest is a picture tube having a one-piece funnel and faceplate assembly, a lightweight 14-inch 90° picture tube, an improved cadmium-sulphide photo-cell and a miniature twin-pentode.

### 9-inch picture tube

Representing a radical departure from standard cathode-ray design a 9-inch rectangular picture tube (see photo), used in G-E's personal TV receiver, has a one-piece funnel and faceplate assembly made with high-speed glass-blowing machinery. The tube was described as offering minimum weight



and maximum viewing area for any given diagonal.

An electrical-grade lead glass is used in the neck and yoke region of the tube with the anode lead coming through the base—a procedure made possible by the relatively low design-center second-anode voltage of 6,800.

Data on the yet unregistered tube are: screen size, 6 x 7½ inches; screen area, approximately 45 square inches; overall length, 13 1/16 inches; magnetic deflection, electrostatic focus; recommended second-anode voltage, 5,500; 7-pin base.

### 14RP4

Intended primarily for low-cost, lightweight, portable TV receivers, RCA's 14RP4 is a short, directly viewed, rectangular, glass picture tube. It is a low-voltage electrostatic-focus and magnetic-deflection type. Its spherical faceplate has a screen of 12½ x 9½ inches (about 108 square inches).

A deflection angle of 90° permits an overall length of only 14 9/16 inches. An external conductive bulb coating



NOW...there's a

# GARRARD

**Auto-Manual  
Record Changer**  
for every  
hi-fi system



*World's Finest*  
**RECORD PLAYING EQUIPMENT**  
from Manual Players to  
Professional Transcription  
Turntables

New  
**RC 88**  
*Deluxe Changer*  
**\$54.50**  
net

Full manual and automatic positions. True-turret drive...uses no belts. 4-pole "Induction Surge" motor. Fool-proof Garrard Pusher Platform.



New  
**RC 121**  
*Mixer Changer*  
**\$42.50**  
net

Garrard's most compact, economical changer—fits any cabinet. Simpli-Mix Operation permits stacking all record sizes together. 4-pole motor. Manual position.



New  
**RC 98**  
*Super Changer*  
**\$67.50**  
net

All RC 88 features, including full manual position and true-turret drive, PLUS continuous + or - variable speed control on all 3 speeds.



**301**  
*Turntable*  
**\$89.00**  
net

Supreme in its class. Individual card gives performance measurements for each unit. Dynamically balanced cast aluminum turntable. Heavy-duty 4-pole shaded motor.



**Model T**  
*Manual Player*  
**\$32.50**  
net

This is the answer for a quality budget system. Incorporates all record playing features of the famed RC 80 record changer. 4-pole motor; automatic stop.

### MAIL THIS COUPON TODAY

All Garrard and other B.I.C. components are illustrated and described fully in the B.I.C. High Fidelity Plan Book, a useful guide in planning any hi-fi system.  
A quality-endorsed product of the B.I.C. Group



To: British Industries Corporation Dept. GF-386  
Port Washington, N. Y.  
Please send B.I.C. High Fidelity Plan Book.

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

IF YOU'RE MOVING, PLEASE DON'T FORGET TO SEND US YOUR OLD ADDRESS AS IT APPEARS ON THE ADDRESS LABEL OF YOUR CURRENT COPY OF THE MAGAZINE, INCLUDING THE NUMBERS SHOWN OPPOSITE YOUR NAME, AS WELL AS YOUR NEW ADDRESS. IF WE RECEIVE THIS INFORMATION BEFORE THE 20TH OF THE MONTH, YOU WILL CONTINUE GETTING THE MAGAZINE WITHOUT INTERRUPTION. YOUR COOPERATION WILL BE MOST HELPFUL AND GREATLY APPRECIATED.

### SPECIAL "HI-FI" OFFER!

Amazing woven saran Hi-Fi Grille Fabrics now available direct to every Hi-Fi enthusiast. Special yarns and constructions mean least distortion. In Mahogany, Walnut, or Blond at the special **INTRODUCTORY PRICE** of \$3.19 Ppd., per Sq. Yd.; or send 50c for 12 new sample swatches. HI-FI FABRICS INST., P. O. Box 15, Huntington Station, N. Y.

### DeRO All Purpose DeRO-Juvenator



One rejuvenator replaces all! Model RU-5—universal 6 wire, for use on all series or parallel filament TV sets, both electrostatic and electromagnet. Restores brilliance and contrast \$3.95 to pix tube.....LIST

AT ALL LEADING JOBBERS • FREE FOLDER  
DeRO • 134 Nassau Rd., Roosevelt, L. I., N. Y.



forms, with the internal conductive coating, a supplementary filter capacitor. Maximum ultor voltage is 14,000 and a single field ion-trap magnet is needed. The 14RP4 weighs only 8½ pounds.

**6694-A**

A tiny cadmium-sulphide photoconductive cell of the head-on type, the 6694-A, announced by RCA, features high luminous sensitivity, very low dark current, extremely low background noise and signal output approximately proportional to the incident light intensity. The cell is useful where a single, tiny photosensitive device is desired—light-controlled relay applications and light



meters for measuring the brightness of small luminous spots.

The 6694-A (see photo) has a radiant sensitivity at 5,000 angstroms of 415 microamperes per microwatt, a luminous sensitivity of 1 ampere per lumen and a luminous intensity sensitivity of 4 µa per foot-candle. Sensitivity is directly proportional to the applied voltage between terminals within the cell's rating. Dynamic sensitivity falls off with increase in frequency. Its upper limit is about 500 cycles.

**6DQ6-A, 12DQ6-A**


Glass octal types, the 6DQ6-A and

12DQ6-A are high-perveance beam power tubes. Announced by RCA, they are intended especially for use as horizontal deflection amplifiers in television receivers.

These tubes have maximum ratings substantially higher than those of the 6DQ6 and 12DQ6: maximum dc plate voltage (including boost), 700; dc grid-2 voltage, 200; average cathode current, 140 ma; grid-2 input, 3 watts. These higher ratings together with a high operating ratio of plate current to grid-2 current adapt these tubes into circuits providing deflection for 90° picture tubes. The 12DQ6-A is like the 6DQ6-A except that it has a 12.6-volt 600-ma heater for use in series-string circuits. The 6DQ6-A draws 1.2 amps at 6.3 volts.

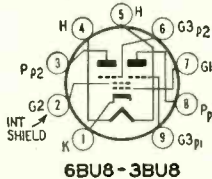**6BU8, 3BU8**

Miniature 9-pin twin pentodes, the 6BU8 and 3BU8 have separate plates and suppressor grids (see base diagram) for the two sections, and a common screen grid, control grid and




cathode. Combining the function of the 6BE6 and 6AU6, they are intended for use as a combined sync-agc tube in TV receivers; one section as a sync separ-

ator and clipper, the other to generate the agc voltage. By using a common control grid, noise pulses can be suppressed from both sync and agc circuits. Except for heater ratings, the 3BU8 is identical to the 6.3-volt 300-ma 6BU6. The 3BU8 draws 600 ma at 3.15 volts.

Maximum ratings as released by General Electric include: plate voltage, 300; screen grid voltage, 150; dc cathode current, 12 ma; plate dissipation, 1.1 watts; screen dissipation, 0.75 watt; negative control-grid dc voltage, 50.

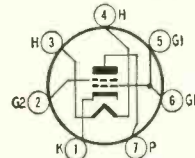**12K5**

A seven-pin miniature tetrode has been developed by Tung Sol. It is intended for use as a power amplifier



driver where the heater, plate and space-charge grid potentials are obtained directly from an auto battery. Typical operating conditions (see diagram) are: heater voltage, 12.6; plate voltage, 12.6; control-grid voltage, -2; space-charge grid voltage, 12.6; plate current 8 ma; space-charge grid current, 85 ma; plate resistance, 800 ohms; amplification factor, 5.6; transconductance, 7,000 micromhos; peak ac control grid voltage, 2.5; power output, 35 milliwatts.

*When signal conditions demand a TOWER... choose one built by AERMOTOR*

AERMOTOR TOWERS have proven their excellence in thousands of installations . . . installations exposed to the most severe weather and wind loading conditions.

AERMOTOR steel antenna towers are self supporting . . . require no cumbersome guy wires. Each part is heavily galvanized after fabrication to insure complete protection from exposure.

Towers are shipped knocked down in convenient bundles; well designed parts make section-by-section assembly easy.

AERMOTOR 3-post antenna towers are available in heights of 33, 47, 60, 73, 87 and 100 feet.

**WRITE FOR ADDITIONAL INFORMATION ABOUT THE AERMOTOR TOWERS AND A DEALER FRANCHISE IN YOUR TERRITORY.**

SINCE 1888, MANUFACTURERS OF QUALITY BUILT TOWERS

**• AERMOTOR COMPANY •**

2500 W. ROOSEVELT RD.—CHICAGO 8, ILLINOIS U.S.A. DEPT. 12 U 6

always buy

**RAD-TEL**

for HIGHEST QUALITY TUBES at lowest prices

SAME DAY SERVICE. FULL 1 YEAR GUARANTEE. ALL TUBES INDIVIDUALLY BOXED. FOR QUALITY, PERFORMANCE, DEPENDABILITY.

---

**Another Rad-Tel Super-Special!**

**5FP7 CATHODE RAY TUBE**

Magnetic focus and deflection. 53° deflection angle. Neck diameter: 1 3/8 inch. Base shell octal 8-pin. Special features: long persistence for either low speed non-recurring signals or high speed recurring signals; two or more signals can be observed with suitable switching.

Lots of 3 **79c**  
single 95c ea. each

---

Famous Make **TIMER CLOCK SPECIAL!**

Single, \$1.75 ea.  
lots of 3—\$1.50 ea.

Complete 24-hour famous make clock. Can be set to turn on radio and similar electrical appliances. Gold face, black numbers, sweep second hand. Mechanism only. No mounting hardware, knobs or bezel. 3 1/2" x 3 3/4".

---

Famous Make **TUNERS** 7FB and 6AG5 or 6BC5. Lots of 3 \$4.50 ea. 12 channels. 20 mc IF. single, \$4.95 ea.

---

FREE Tube & Parts Catalog Listing Over 400 High Quality Tube Types. Write Dept. RE-6.

---

**EXPORT INQUIRIES INVITED**

TERMS: 25% deposit must accompany all orders—balance C.O.D. All shipments F.O.B. Irvington warehouse.

**Rad Tel TUBE CO.**

Orders Under \$5.00—50c Handling Charge.  
PLEASE: Send full remittance. Allow for postage and save C.O.D. charges. Unused money refunded. Subject to prior sale.

Not Affil. With Any Other Tube Mail Order Co.

**115 COIT ST., IRVINGTON II, N. J.**

RADIO-ELECTRONICS

# Technicians' News



## GUILD SEES COLOR TV

A color TV receiver using the one-gun Lawrence tube was demonstrated to a large meeting of the Long Island Radio & Television Guild at a meeting in Garden City, N. Y., as a part of a lecture on simplified color TV.

Ray Popkin-Clurman, who heads Telechrome, Inc., builders of a number of receivers using the Lawrence tube, stated that the tube could be produced for \$75 or possibly \$50 if manufactured in lots of 100,000 or more.

The set demonstrated had 22 tubes, although Popkin-Clurman stated that the circuit could be designed to use only 18. It was one of a group of receivers produced on contract for Chromatic Television Laboratories, maker of the experimental Lawrence tubes used in the receivers.

## MARTS HAS NEW LAWS

The Milwaukee Association of Radio & Television Services made several important changes in their bylaws at the recent annual meeting. The most important was to provide a period of probation for new members. During the "tryout" period the provisional member is observed as to whether he obeys the MARTS Code of Ethics. A clean record with distributors was also made a requirement of membership as a part of the cooperation between MARTS and the local distributors. Two new classes of membership, patron and associate, were introduced. The patron membership is designed to accommodate distributors, manufacturers, TV stations and others, while the associate membership is for employes of member firms who want to attend MARTS functions as more than mere guests. The new slate of officers includes:

Walter Gregg, president; Gerald Hall, vice president; Mrs. Perry P. Cody, executive secretary and manager of the complaint bureau; Larry Zechel, secretary, and Ned Alpert, treasurer.

## KANS. GROUP INCORPORATES

The Television Electronic Association of Kansas has been incorporated as a nonprofit organization under the laws of Kansas, we are informed by E. A. Redman, secretary of the organization. At present TESA-Kansas has three chapters at Wichita, Salina and Great Bend.

The Salina chapter has appointed a committee to investigate the possibility of setting up a plan for self-licensing and investigation. The Great Bend group (Midwest chapter) was still in the formative stage when Mr. Redman

Why  
use  
ordinary  
tape...

...now that  
**FERRO-SHEEN**  
costs you no more?

# irish BRAND GREEN BAND

is now made by the exclusive  
**FERRO-SHEEN**  
process!



**FERRO-SHEEN** is the exclusive **irish** tape manufacturing process which astounded the audio world when it was introduced 18 months ago and has rendered ordinary tape old-fashioned, if not obsolete. **irish FERRO-SHEEN** process tape has by far the smoothest and most homogeneously bonded magnetic oxide surface of any recording tape ever made. It ends your worries about wearing or gumming up your recorder heads with the abrasive, easily shed oxide coating of ordinary coated tape. It gives you unprecedented fidelity because the mirror-smooth **FERRO-SHEEN** surface makes for vastly improved head-to-tape contact. It is simply the best-engineered tape in the world.

Write for **FREE irish Comparator Card**, a sampler of mounted strips of top-brand tapes, showing at a glance "Which Tape Has the Smoothest Surface."

If not available  
at your favorite  
dealer, write  
directly to:

- **ORRADIO INDUSTRIES, INC.,** OPELIKA 1, ALABAMA
- *World's Largest Exclusive Magnetic Tape Manufacturer*
- Export Division: Morhan Exporting Corp., N. Y. C.
- In Canada: Atlas Radio Corp., Toronto



**irish  
GREEN BAND**  
1200 feet..... \$3.50  
**THE ONLY  
PREMIUM QUALITY TAPE  
AT THE  
STANDARD PRICE**



COMPLETELY

SOLDERLESS



NO SOLDER—  
braid or contact

NO CRIMP—  
braid or contact

**AMPHENOL**

## NEW COAXIAL CABLE CONNECTORS

Two new time-saving, reusable, field-workable coaxial connectors are now available. The 83-850 is a *completely solderless* connector that can be assembled to RG-11/U or RG-59/U cable with a screwdriver and a pair of pliers! The 83-851 is *semi-solderless*, may be used wherever an 83-1SP has been used. Only the contact is soldered—the braid is locked mechanically by a positive-action cable clamp as in the 83-850. Both plugs are plated with corrosion-resistant cadmium.

### features

**COMPLETELY SOLDERLESS**  
83-850—no solder, no crimp  
83-851—semi-solderless

**FULLY RE-USABLE**  
attach and detach, use again and again


**EASY ASSEMBLY**  
even in field use

### applications

**MASTER TV INSTALLATIONS**  
hotels, motels, apartment houses

**LABORATORY & SERVICE  
TECHNICIAN USE**  
speeds work, saves money

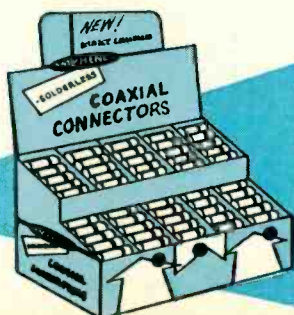**COMMUNITY TV INSTALLATIONS**  
for every field application



special  
Watch for this solderless  
connector dispenser at your Distributors!

**AMPHENOL**

AMERICAN PHENOLIC CORPORATION

chicago 50, illinois

www.americanradiohistory.com

### TECHNICIANS' NEWS

(Continued)

wrote. It expects to have more than 50 charter members at the conclusion of the membership drive.

TESA-Kansas was formerly RSDA of Kansas and has inherited its records and traditions. The new organization is affiliated with NATESA.

### FTC ACTS

The Federal Trade Commission (which has local jurisdiction in the District of Columbia) has taken action against Credit TV Service, Washington, D. C., charging it with misrepresenting that its charge for servicing and repairing a TV set in the home is 99 cents and that shop estimates are free.

Typical advertising, the complaint alleges, states:

Mr. and Mrs. TV Owner  
**ATTENTION**  
99c House Call 99c  
All makes serviced in your home  
or in our shop. Free shop estimates.

In fact, the complaint alleges, the charge for servicing or repairing a set in the home is "greatly in excess" of 99 cents. If sets are not left for repair, a charge is made for shop estimates.

Claims to the contrary, the complaint concludes, deceive the public and violate the FTC Act.

### LICENSE IN DETROIT

A law requiring a license for all who operate a business of installing and servicing television equipment has been enacted in Detroit by unanimous vote of the City Council. To be licensed as a service dealer, one must be a certified technician or employ a full-time certified technician. Fees for a service dealer are \$25 and for a certified technician \$10 annually.

According to the present law, a dealer must employ one certified technician. Other employees under the direction of the certified man would not require licenses. The situation on outside jobs is not as clear but the ordinance states that students or apprentices accompanied and supervised by a certified technician are not required to have licenses but must carry identification cards. This implies that—as understood at the present moment at least—the law would prevent sending uncertified men alone on the outside repair or installation jobs.

A board of examiners is to be appointed to test applicants for the technician license. The board is to consist of three service dealers, a TV instructor and an engineer from a local TV station. Candidates for certification must be over 21 years of age, have 4 or more years' experience in servicing or have technical training equivalent to 2 years, plus 1 year's practical experience. The requirements for a dealer license were not stated in any news report available at the time of writing.

Detroit service technicians and companies were reported as being "interested" in the new law, and some expressed the opinion that its usefulness or otherwise would be determined by the way it is administered. **END**

RADIO-ELECTRONICS



# Patents




## SECRET TRANSMITTER

Patent No. 2,710,345

Robert Lee Stephens, Los Angeles, Calif.

Actors and others can use this tiny transmitter which radiates effectively for about 100 feet. It is a low-power FM circuit that easily fits a pocket so that the user may move about without losing contact with a nearby radio

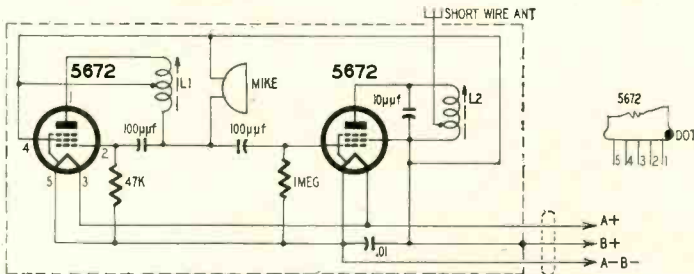turns (No. 24 enameled) on a 1/4-inch form, tapped at 1 turn. Both coils may be slug-tuned. The tubes' heaters require 1.25 volts at 50 ma. Maximum plate potential is 67.5 volts. The transmitter may be less than 2 inches



receiver. Both may be tuned to about 50 mc.

The figure shows the two-tube transmitter. The first pentode stage is a Colpitts oscillator. It is frequency-modulated by a capacitor microphone across the lower portion of L1. This coil may have 24 turns (No. 31 enameled) on a 1/4-inch form, tapped at 11 turns, and is tuned to 25 mc. Output is coupled to the grid of the second tube, a frequency doubler. L2 may be wound with 8 1/2

high, and is normally installed in a small case that can be carried in the vest pocket of a coat. The batteries, in a slightly larger case, can be carried in a side pocket. The transmitter is highly stable because of the frequency-doubling feature. Tests show that it can deliver a signal-to-noise ratio of better than 57 db. Response is flat from 20-15,000 cycles. The output of a 5672 tube is about 65 mw.

## REACTANCE-TUBE MODULATION


Patent No. 2,716,218

Alvan Donald Arsen, Liverpool, N. Y. (Assigned to RCA)

A reactance-tube modulator has limited frequency swing because it is truly reactive over only a narrow band of frequencies. Any large deviation results in a resistive as well as reactive component and the oscillations become damped. This new circuit uses control tubes to maintain pure reactance over a wide band.

Reactance tube V2 shunts an oscillator tank as usual. Plate voltage is fed back to the grid through an R-C phase network including control

center tap provides bias for all tubes. Now let the modulating signal drive the grid of V2 positive, increasing its Gm and its effective capacitance. This lowers the oscillator frequency. At this reduced frequency, the C component of the phase network has higher reactance. This must be matched by proportionally higher R if the same 90° lag is to be maintained. This is done automatically, when the grid of V1 goes positive, the control-tube grids go negative. This raises

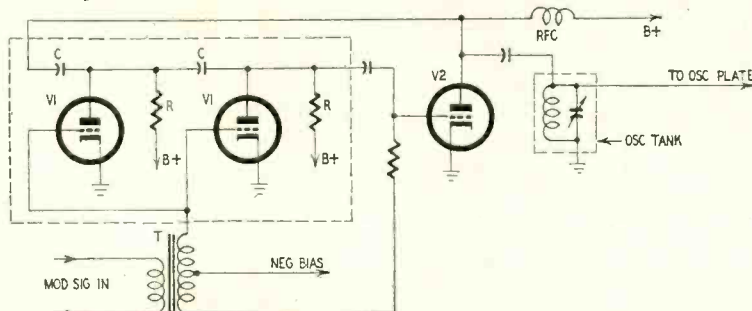

tubes V1. The network is designed for an overall lag of 90° at the center or carrier frequency. Under this condition Ip leads Ep by 90° and V2 behaves like a pure capacitance across the tank. This capacitance can be increased by raising tube amplification and decreased by reducing gain.

Modulation transformer T drives the grid of V2 in opposite phase to the grids of V1. Its

the resistance of the tubes shunting the phase-shift network.

It easily follows that when the modulating signal reverses its polarity the oscillator frequency goes higher. During this time both control tubes (V1) have lower shunting resistance as required to maintain the desired 90° lag. If the modulating signal is audio this circuit forms the basis of an FM transmitter.

## PHOTOGRAPHIC FLASHTUBE

Patent No. 2,722,631

James Normal Bowtell, Wembley, England. (Assigned to General Electric Co.)

This circuit can trigger a two-element flashtube through as much as 15 feet of cable. Furthermore, the trigger power is not hazardous since

it is supplied by a capacitor, not a battery or power supply.

The flash tube may be one that fires at 2,500

# COMPLETE TRAINING FOR BETTER RADIO-TV SERVICE JOBS



Let these two great new Ghirardi training books teach you to handle all types of AM, FM and TV service jobs by approved professional methods—and watch your efficiency and earnings soar!

Completely modern, profusely illustrated and written so you can easily understand every word, these books pave the way to fast, accurate service on any type of home radio-TV electronic equipment ever made. Each book is brand new. Each contains the latest data on the latest methods and equipment—NOT a rehash of old, out-of-date material. Each is co-authored by A. A. Ghirardi whose famous RADIO PHYSICS COURSE and MODERN RADIO SERVICE were, for 20 years, more widely used for military, school and home study training than any other books of their type!

## THE NEW Ghirardi

RADIO-TV SERVICE LIBRARY

Almost 1500 pages and over 800 clear illustrations show step-by-step how to handle every phase of modern troubleshooting and servicing.

### 1—Radio and Television Receiver TROUBLESHOOTING & REPAIR

A complete guide to profitable professional methods. For the novice, it is a comprehensive training course. For the experienced serviceman, it is a quick way to "brush up" on specific jobs, to develop improved techniques or to find fast answers to puzzling service problems. Includes invaluable "step-by-step" service charts. 820 pages, 417 illus., price \$6.75 separately.

### 2—Radio and Television Receiver CIRCUITRY AND OPERATION

This 669-page volume is the ideal guide for servicemen who realize it pays to know what really makes modern radio-TV receivers "tick" and why. Gives a complete understanding of basic circuits and circuit variations; how to recognize them at a glance; how to eliminate guesswork and useless testing in servicing them. 417 illus. Price separately \$6.50.

### New low price... You Save \$1.25!

If broken into lesson form and sent to you as a "course," you'd regard these two great books as a bargain at \$50 or more! Together, they form a complete modern servicing library to help you work faster, more efficiently and more profitably.

Under this offer you buy them both for only \$12.00. You save \$1.25 on the price of the two books—and have the privilege of paying in easy installments while you use them.

### 10-DAY FREE TRIAL

Dept. RE-66, RINEHART & CO., Inc., 232 Madison Ave., New York 16, N. Y.

Send books below for 10-day PREP EXAMINATION. In 10 days, I will either remit price, (plus postage) or return books postpaid and owe you nothing.

Radio & TV Receiver TROUBLESHOOTING & REPAIR (Price \$6.75 separately)

Radio & TV Receiver CIRCUITRY & OPERATION (Price \$6.50 separately)

Check here for MONEY-SAVING COMBINATION OFFER... Save \$1.25. Send both of above big books at special rate of only \$12.00 for the two (Regular price \$13.25... you save \$1.25.) Payable at rate of \$3 (plus postage) after 10 days if you decide to keep books and \$3 a month for 3 months until \$12 has been paid.

Name .....

Address .....

City, Zone, State .....

Outside U.S.A.—\$7.25 for TROUBLESHOOTING & REPAIR; \$7.00 for CIRCUITRY & OPERATION; \$13.00 for both books. Cash with order, but money refunded if you return books in 10 days.



... another  
**MALLORY**  
service-engineered  
product



# New Mallory "Gems" pace setters in paper capacitors

Next time you replace paper tubulars, make sure you use these new Mallory capacitors. They give you a lot of extra value features—without extra cost.

**Soldering iron heat can't loosen leads.** Wires are permanently attached in the plastic end seal... can't work loose from heating or vibration.

**Moistureproof construction,** using a protective case of high grade mica-filled bakelite, ends worries about premature shorts due to high humidity.

**True center construction** protects the foil element from deformation during assembly... assures uniform quality in each capacitor.

Get your stock now, from your local Mallory distributor. Ask for Mallory "Gems"—you'll agree they're a gem of a capacitor!

P. R. MALLORY & CO. Inc.  
**MALLORY**

P. R. MALLORY & CO. Inc., INDIANAPOLIS 6, INDIANA


- Capacitors
- Vibrators
- Resistors
- Power Supplies
- Controls
- Switches
- Rectifiers
- Filters
- Mercury Batteries

## PATENTS

(Continued)

volts or more. The main capacitor C1 is charged to about 2,000 volts prior to the flashing instant. It may be charged from the line through a high-voltage rectifier. A low-voltage dc source is connected across the primary of the transformer through the switch. The switch is normally closed and current flows in this circuit while C1 is being charged.

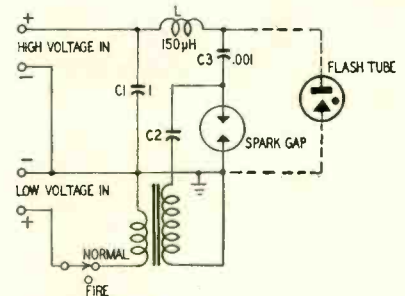It is opened to fire the flashtube. This inter-



rupts the steady current and induces a high potential across transformer secondary, C2, and the gap tube. A spark flies across the elements of this tube and shock-excites L and C3, which resonate at about 1 mc. The rf across C3 flows into the cable (dotted lines) and adds to the voltage on capacitor C1 to initiate the discharge.

## LONG-STORAGE VOLTMETER


Patent No. 2,721,978

Elihu Craig Thomson, Wellesley, Mass. (Assigned to Electronics Corp. of America, Cambridge, Mass.)

This circuit has a long memory. It deposits a charge on a storage capacitor which has polystyrene dielectric, which leaks only about 1/2% in an hour. The diagram shows the circuit for measuring the output of a photocell. The stored voltage corresponds to the peak value of the photocell. Whether this illumination arrives in pulse, square-wave or other form, the stored voltage corresponds to the peak value of the illumination.

The photocell is polarized to deliver positive output. This charges C1 and C2 (through the conducting diode consisting of the 5803 grid-filament circuit). When output falls off or disappears, C1 discharges through R1 but storage capacitor C2 is isolated. The charge is trapped because C2 acts through R1 to block the grid-filament diode.

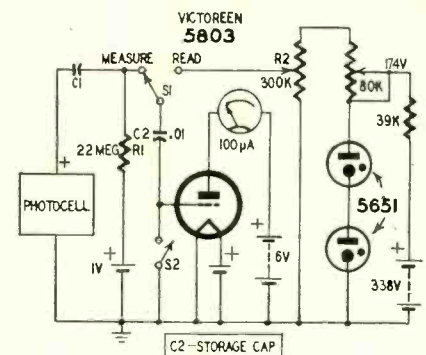To measure the voltage across C2, S1 is thrown to READ. It connects C2 in series with a part of R2 and both are now between grid and ground.



R2 is adjusted, starting with its contact at the ground end, until it delivers a voltage equal and opposite to that stored on C2. (Potentiometer output comes from a well-regulated dc source.) When the potentials of R2 and C2 are equal and opposite, they cancel. Grid bias at the 5803 is then zero and current begins to flow through the meter.

R2 should be calibrated. Thus, as soon as the meter deflection reaches some standard or predetermined value, the voltage across C2 may be read off directly, without loss of charge from the capacitor.

After completing the measurement, C2 is discharged by closing S2, automatically charging C2 (through R1) to 1 volt. This remains as bias for the tube when S1 is again thrown to MEASURE and S2 opened.

END


# Technotes



## RCA KCS84

Weak picture, poor definition and smear in this chassis often result from a partial short in peaking coil L1 (see diagram). This 250- $\mu$ H coil has black-black as identifying marks.

Resistance checks show no appreci-

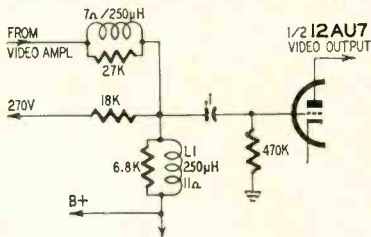

able difference from normal. However, a scope check at the plate of the first video amplifier indicated considerable distortion. Replacing the coil completely cleared the trouble.—*James A. McRoberts*

## OPTICAL SOUND TRACK

A Kodak Pageant movie projector with optical and magnetic sound-track facilities was sent to our shop with a complaint of distortion when played on the optical sound track at high output levels. An oscilloscope revealed sharp spikes in the output when a pure 250-cycle sine wave was applied to the input terminals (not directly to the first grid). These spikes were traced to the ionization of the neon record level indicator despite the fact that one side is disconnected when on optical playback. One of the neon leads is about 4 inches from the grid of the first stage where the pickup was taking place. Relocating and shielding the lead removed the trouble. The ultrasonic oscillator tube, which supplies voltage to the optical sound-track lamp, was removed during these measurements since pickup from it is normal.

One thing learned from this trouble is that neon level indicators may cause distortion in any high-gain audio amplifier. Ionization of these lamps sounds like speaker rattle.—*Joseph Stephany*

## TVI RADIATION

Recently a customer complained that when his TV set was operating, all radios in the house were blanked out. All that could be heard on the radios was a whistle.

Checking showed the TV set was putting out a beautiful blanket radiation. Without bothering to analyze the interference, we used a sure-fire remedy for whatever the trouble might be. With 30 cents' worth of copper window

... another  
**MALLORY**  
service-engineered  
product



## Servicemen's favorites in wire-wound controls

You're sure of giving your customers the best when you use Mallory wire-wound controls. The choice of servicemen and manufacturers everywhere, they have set the standards of the industry for value and performance.

**They're conservatively rated**—to assure you of cool operation without need for using over-sized units.

**They're compact**—fit readily into crowded chassis locations.

**They're long lasting**—give years of stable, dependable service.

**They're uniform**—made to strict specifications to meet or exceed original equipment requirements.

Mallory 2-watt and 4-watt controls are available in resistance values and tapers to match every replacement need. Your local Mallory distributor has a complete stock—see him today!

P. R. MALLORY & CO. Inc.  
**MALLORY**

P. R. MALLORY & CO. Inc., INDIANAPOLIS 6, INDIANA

- Capacitors
- Controls
- Vibrators
- Switches
- Resistors
- Rectifiers
- Power Supplies
- Filters
- Mercury Batteries





# "COLOR TV TRAINING MANUAL"

## THE NEW BOOK THAT PREPARES YOU FOR SUCCESSFUL COLOR TV SERVICING

Written by C. P. Oliphant and Verne M. Ray, of the Howard W. Sams editorial staff, in practical, down-to-earth language you can understand. Presented in 3 comprehensive sections. SECTION I: Principles of the Color TV System (includes chapters on Colorimetry; Requirements of the Composite Signal; Make-Up of the Color Picture Signal). SECTION II: Color Receiver Circuits (chapters on RF and IF Circuits; Video, Sync and Voltage Supply Circuits; Bandpass-Amplifier, Color-Sync and Color-Killer Circuits; Color Demodulation; Matrix and Output Circuits). SECTION III: Servicing the Color Receiver (chapters on Setting Up the Color Picture Tube; Aligning the Color Receiver; Trouble-Shooting; Test Equipment Required). Appendices include Equations, Vectors, Color-blocks, Colorplates, Glossary. A comprehensive training course that helps you qualify for Color TV servicing. 260 pages, 8½ x 11"; profusely illustrated.

Postpaid, only... \$695

HELPS YOU MASTER  
COLOR TV PRINCIPLES  
AND PRACTICES

only \$695

ORDER BELOW

**SAMS BOOKS**  
keep you ahead in  
**ELECTRONICS**

Sams books cover every phase of Electronics for the service technician, engineer, student or experimenter. Listed below are a few of the many valuable Sams books available at electronic parts distributors and leading book stores.

### USE THIS ORDER FORM

#### COLOR TELEVISION TRAINING MANUAL ..... \$695

- Analyzing and Tracing TV Circuits. Presents a new approach to TV servicing. 168 pages, 8½ x 11".....\$3.00
- TV Service Data Handbook. Most frequently needed charts, tables and formulas required in TV servicing and installation. 112 pages, 5½ x 8½".....\$1.50
- Principles & Practices of Telecasting Operations. Discusses equipment and techniques. Covers such subjects as: TV Cameras; Control Rooms; Fundamentals of Studio Lighting; Relay Systems; Maintenance Practices; Technical Production; etc. 600 pages; 6 x 9"; illustrated.....\$7.95
- Radio Receiver Servicing. Covers the basic receiver types—gives time-saving hints for solving basic troubles, such as dead set, weak set, noisy set, etc. 192 pages; 5½ x 8½".....\$2.50
- So You Want to Be a Ham. Tells you what you need to know about getting your license and acquiring equipment. Covers such subjects as: Conquering the Code; Getting Your Ticket; Going on the Air; Electronics as a Career; etc. 196 pages; 5½ x 8½"; illustrated.....\$2.50
- Servicing TV Sweep Systems. Describes the operation, circuit function and circuit variations of vertical and horizontal sweep systems common to most TV receivers. Tells how to analyze circuits; trouble-shoots for you. 212 pages; 5½ x 8½"; illustrated.....\$2.75
- The Recording and Reproduction of Sound. Widely used by Audio engineers, Hi-Fi enthusiasts, broadcasting stations and recording studios. Authoritative chapters cover: behavior of sound waves; basic recording methods; lateral disc recording; micro-groove recording; phono reproducers; microphones; home music systems; P.A. systems; amplifiers; tuners; etc. 810 pages; 6 x 9"; illustrated.....\$7.95

#### HOW TO UNDERSTAND AND USE TV TEST INSTRUMENTS

- Completely revised and enlarged to include latest data on instruments used for Color TV Servicing. Covers use of VTVM's Signal Generators, Sweep Signal Generators, Scopes, Video Signal Generators, Field Intensity Meters and Voltage Calibrators. 208 pages, 8½ x 11".....\$3.50
- Photofact Television Course. Gives a clear complete understanding of TV principles, operation, practice. Used by thousands of students. 208 pages, 8½ x 11".....\$3.00
- Atomic Radiation, Detection and Measurement. Provides basic understanding of nuclear science and its applications. Thoroughly covers and illustrates circuitry and operation of the many types of detection devices. 200 pages; 5½ x 8½".....\$3.00
- Basic Radio Manual. Provides all the basic facts on theory, definitions, components. Includes section devoted to actual projects that translate theory into practice. 248 pages; 8½ x 11"; illustrated.....\$5.00

#### Auto Radio Service Manuals

- Vol. 5. Presents complete, accurate service data, schematics, parts lists and photos based on actual laboratory analysis of 87 auto radio models produced during 1954-55. 288 pages; 8½ x 11".....\$3.50
- Vol. 4. 48 models; 1953; 288 pages.....\$3.00
- Vol. 3. 80 models; 1950-52; 288 pages.....\$3.00
- Vol. 2. 90 models; 1948-50; 288 pages.....\$3.00
- Vol. 1. 100 models; 1946-49; 396 p. \$4.95

There is an authoritative Sams book on virtually any Electronic subject in which you're interested. Check below for FREE Book List describing all Sams books.

Send Book List



Look for  
**SAMS BOOKS**  
on the  
"Book Tree"  
at your Parts  
Distributor

### HOWARD W. SAMS & CO., INC.

Order from your Parts Jobber today, or mail to Howard W. Sams & Co., Inc., Dept. 2-F6, 2205 East 46th St., Indianapolis 5, Indiana.

Send books checked above. My (check) (money order) for \$..... is enclosed.

Name.....

Address.....

City..... Zone..... State.....

(outside U.S.A. priced slightly higher)

### TECHNOTES

(Continued)


screen, using the shop staple gun, we covered the inside of the TV cabinet, grounding it to the chassis with copper braid. The shielding removed the radiation completely.

Coming across a similar case later, we asked the lady of the house for her box of household aluminum foil, and did the same job then and there (leaving some holes for ventilation), with the same results.

Old-timers may remember that some early TV sets came with shielding inside the cabinet. Some even had bottom plates for the chassis to harness radiation.—Ben Crisses and David Gnessin
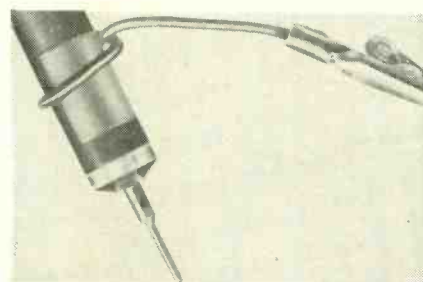
### GROUND-LEAD INDUCTANCE


At the high frequencies used in the front ends and intermediate-frequency amplifiers of television receivers, the inductance of ground leads used with probes will often produce misleading patterns and readings. The ground lead should be short and direct to the point



under test. A particularly glaring fault can be seen in the photo showing a crystal probe with its ground lead looped around the tube. The inductance formed by this arrangement may often be greater than the inductance of the circuit under test and could considerably distort its waveform.—L. A. Williams
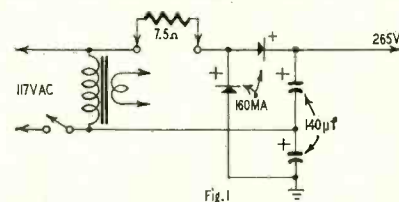
### MOTOROLA TS 292

This set had a defective selenium rectifier after replacement 3 months earlier. The voltage-doubler arrangement of the low-voltage power supply is shown in Fig. 1. The 265-volt output will drop to 200 or less if the back current from the rectifiers becomes excessive




sive and will modulate the B-plus line with a hum component which will cause a weave in the picture and a hum bar (60-cycle type) on picture and raster.

The brute-force method of preventing future trouble is to use higher-current-rating selenium rectifiers.

One cause of this trouble is excessive current drain in the horizontal output tube whose circuit is not "tuned" properly by a linearity coil—absent in this chassis. The substitute for this linearity coil is L1 and C1 (Fig. 2). The



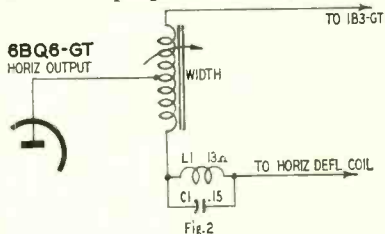value of C1 may be raised or lowered by shunting or adding series capacitance. The proper value is the lowest



current reading to the horizontal output tube which can be metered by opening the lead to the damper plate or to terminal 3 of the flyback transformer. A 200-ma meter is needed—a panel lamp drawing 0.25 ampere can be used instead of a meter.—*Lucian Palmer*

**PHILCO 51-1730 RADIO**

When the complaint on this set is fading and a check reveals no B plus when the sound disappears, the trouble is usually an open 20- $\mu$ f 150-volt electrolytic capacitor. This component is part of a voltage-doubler circuit and is in series with the ac line to the plate and cathode of the 7X6 rectifier.—*Miguel Vega*

**CONDENSATION**

After repairing an RCA KCS47B I called the customer to pick up his chassis as he had brought it into my shop. He put it in his car on this particularly cold night and went visiting. Returning to his steam-heated apartment he put the chassis in the cabinet and turned it on. After a few minutes he heard a hissing and the picture started to act up.

By the time he got to the back of the set to see what the trouble was, the high-voltage transformer had arced across the windings and started to burn. He pulled the plug but the damage was done.

The condensation caused by bringing the cold chassis into the heated room was too much for the flyback transformer and it broke down. The insulation had burned through so I was not able to repair it. Thus, one new horizontal output transformer because I forgot a word of caution to someone who could know no better. Thus, under similar conditions it may often pay you to let the set rest for several hours or overnight before turning it on.—*Fred W. Rodey*

**WARPED RECTIFIER MOUNT**

The high-voltage rectifier mounted underneath the chassis of a Motorola TS 118B is a source of trouble. The plasticlike insulation supporting the rectifier socket often warps and makes the already-small clearance between the cap end of the rectifier tube and the remainder of the chassis and components still less. The result was corona on humid days. Repair was made by replacing the socket mounting support with Bakelite instead of the rubber tape used by the amateur on the job previously.—*A. P. Monroe* END



**Here's why . . . sturdy steel PERMA-TUBE is stronger than any other television mast**

1. Its resistance to bending is *five times stronger* than structural aluminum.
2. Its resistance to deflection is *three times stronger* than structural aluminum.
3. Its resistance to destruction by wind-force is *twice as strong* as structural aluminum.

**ADDITIONAL REASONS FOR USING PERMA-TUBE EVERY TIME**

PERMA-TUBE IS CORROSION PROOF . . . it's treated with vinsynite—then coated *inside and outside* with a metallic vinyl resin base.

PERMA-TUBE IS EASILY INSTALLED . . . it's the *only mast* with *both ends* of the joint machine fitted.


ONLY GENUINE PERMA-TUBE GIVES THIS PROTECTION AND SERVICE . . . *look for this brand mark . . . accept no claims from substitute materials.*



For complete information and scientific data write to: Jones & Laughlin Steel Corporation, Department 496, 3 Gateway Center, Pittsburgh 30, Pa.

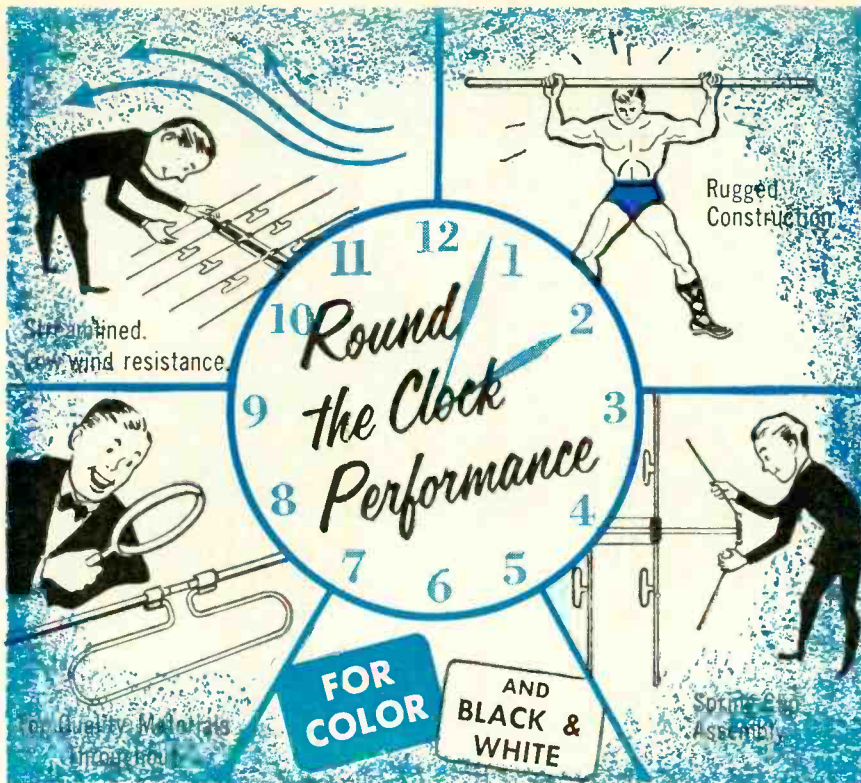**Jones & Laughlin**  
STEEL CORPORATION · PITTSBURGH





# TACO TRAPPERS®

Taco Trappers are **DEPENDABLE**—day in, day out through all the seasons. You can count on the Trapper design to provide outstanding performance. We call it “staying power”. Performance is our most important feature. However, this is only part of the story, for starting with the materials used and ending with the streamlined appearance when installed, the Trapper has no equal. For better pictures and satisfied customers, insist on the Taco Trapper design. You'll eliminate call-backs.




**SUPER TRAPPER**  
for extreme fringe area installations.



**TRAPPER**  
for fringe and near-fringe installations.



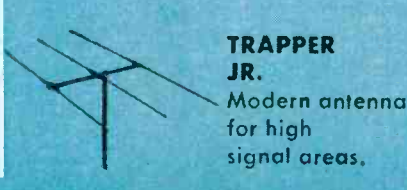**TRAPPER ROYAL**  
for improved low-band performance.



**TRAPPER JR.**  
Modern antenna for high signal areas.

**TACO TECHNICAL APPLIANCE CORPORATION**  
SHERBURNE, N. Y.


In Canada: Hackbusch Electronics, Ltd., Toronto 4, Ont.


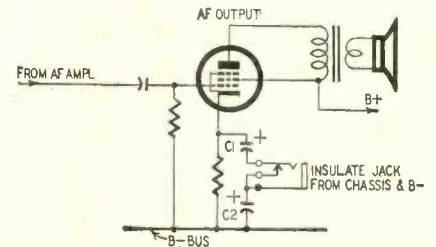
## AC-DC SET AS TUNER

The diagram shows how I convert ac-dc table-model radios for use with external power amplifiers. Cathode bypass capacitor C1 is connected to the leaf of a closed-circuit phone jack. A second capacitor (C2) is connected between the jack frame and B minus as shown.

When a phone plug is inserted in the jack, the stage is converted to a partial cathode follower with C1 serving as a blocking capacitor while C2 isolates the other side of the output line from B minus or ground. With this connection, ordinary unshielded line can be used to feed the amplifier without loss



of highs, but shielding may be needed in some cases to minimize hum pickup.

When using the receiver as a tuner for a wide-range system, you will probably have to increase the filtering in its plate supply to reduce hum and take steps to improve the frequency response of its audio system. (See “Table Radios Into Hi-Fi Tuners” and “Improving Your TV Audio” in the January, 1956 issue.)

If the receiver does not have a cathode bypass on the output stage, C1 and C2 should be about 40-50  $\mu\text{f}$  each. C1 may be rated at around 25 volts and C2 at 150 or higher.

A switch may be connected in the secondary circuit of the output transformer to cut out the speaker and cut in a 5-ohm 5-watt resistor when using the receiver as a tuner. Or, you can use the receiver as a tweeter. In this case, you can reduce the values of C1 and C2 to around 10  $\mu\text{f}$ .—Frank Bodine


## DRIVING GROUND RODS

Hard or rocky ground makes it difficult to drive the conventional Copper-weld TV ground rod without bending it. We overcome this by first forcing a short length of  $\frac{3}{4}$ -inch pipe into the ground and then inserting the rod into it. When the rod has been driven down several feet, the pipe can be removed and the rod driven home readily.—Harry J. Miller


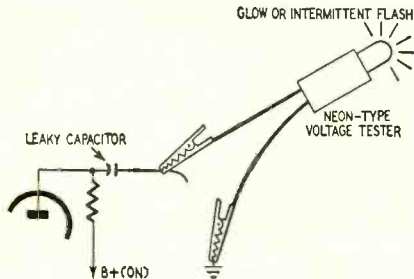
### QUICK CAPACITOR CHECK

A quick test for dc leakage in capacitors, especially coupling capacitors, can be made with an ordinary neon test lamp. Disconnect the cold end of the capacitor and connect the tester from the cold end to ground or B minus. With the B-plus power on the light will glow or flash intermittently on leaky capac-




itors. This test will detect leakages of several megohms. Though not as sensitive a test, on voltages lower than the ionizing voltage of the lamp a dc voltmeter can be used. Be careful to set it on a scale high enough to avoid pinning the needle on the initial charging "kick."  
—Paul Harwood
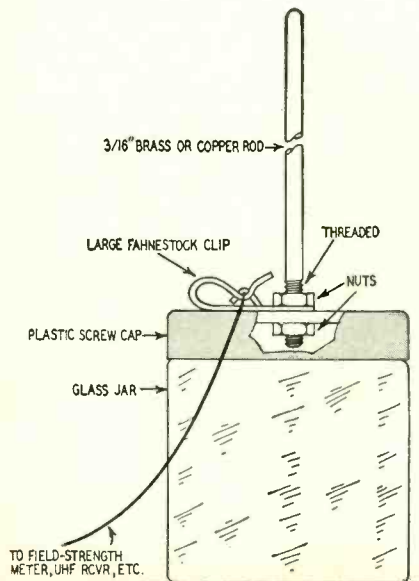
### SIMPLE UHF ANTENNA

Short vertical antennas are often used for field-strength meters and for various uhf experiments. Since supporting clamps and insulators are often inconvenient and cumbersome, I use glass jars with plastic caps to support and insulate the antenna rods.

Brass or copper rods 3/16 inch in diameter and up to 4 feet long can be supported by a 3-inch diameter jar without tipping. The rod is threaded at the bottom so it can be fastened to the jar cap with two hexagon nuts as shown in the illustration. A Fahnestock clip or soldering lug can be clamped between the top nut and cap for connecting to the antenna. The jar can be held in the hand and moved around without serious body-capacitance effects.




If a jar with a metal cap is used, scrape the enamel off the top of the cap and solder the rod directly to it. Before soldering, make a small loop in the end of the rod and bend it at right angles to the rod. This provides a broader base for the rod and a greater area for soldering.—Arthur Trauffer
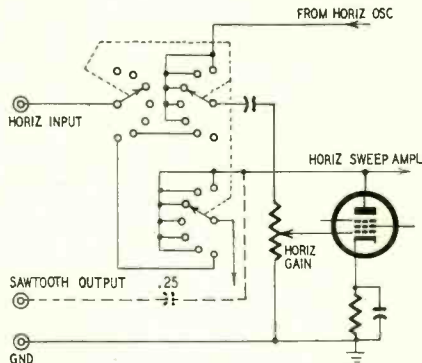
### SAWTOOTH GENERATOR

Most electronic technicians and experimenters have had, at one time or another, a need for a sawtooth-wave source variable in frequency and amplitude. It usually is needed when there is neither time nor inclination to construct one "from the ground up." However, if the experimenter owns an oscilloscope, there is a very easy and inexpensive way to provide just such a source.


The diagram shows a partial circuit of a typical oscilloscope with the modification shown in dashed lines. The only parts necessary are an insulated pin or banana jack and a 0.25- $\mu$ f 600-volt capacitor. The jack is mounted in the front panel near the ground post on the horizontal amplifier side of the panel. Insulate the jack from the panel. The capacitor connects the jack to the plate of the horizontal amplifier tube. The frequency is controlled by the coarse and fine frequency scope controls and the amplitude by the horizontal gain control.



A cable can be made up by using a length of coaxial line long enough to suit the needs of the user with appropriate lugs, clips and plug attached.

In use, there has been no discernible depreciation in the performance of the scope by making this modification, provided the cable is disconnected from the scope when it is not being used as a sawtooth source.

A very practical use for this modified equipment is in determining whether the trouble in the horizontal sweep section of a TV receiver lies in the oscillator or output stage. By disconnecting the horizontal drive trimmer and the coupling capacitor from the grid of the output tube (be sure the grid resistor is left connected) and feeding the sawtooth wave into the grid, a few voltage checks on the output and damper tubes will reveal if the output stage is functioning normally. If it is, then it can be assumed that the trouble lies in the horizontal oscillator section.—Frank D. Mowery

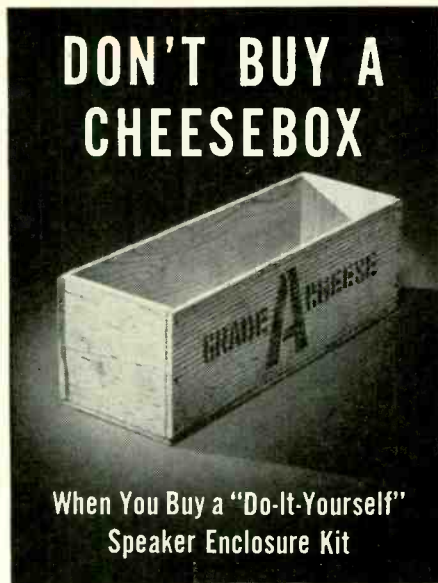

Your speaker enclosure is not just a box. It's an important component of your Hi-Fi system. A "build-it-yourself" enclosure should be as good as the finest factory-assembled enclosure. When you "build your own" don't end up with a cheesebox... make sure that the kit you buy has all these features:

- 1. Select 3/4" Hardwood Cabinet Plywood**  
Heavy 3/4" thick wood used throughout. Principal sections of enclosure are of Select Grade Birch. Same quality as used in finest furniture.
- 2. All Wood Pre-Shaped**  
Providing locked and mitred joints for extreme rigidity and buzz-free performance. Almost all assembly done with a screwdriver.
- 3. Speaker Mounting Board Flexibility**  
Interchangeable adapter boards for countless P.S.E. combinations of multispeaker systems with provision for future speaker expansion.
- 4. "Decor-Coustic" Design**  
A perfect union of the most advanced principles of acoustic baffling and interior decoration. No screws or other hardware visible on surface of enclosure. Self-contained... functions independently of walls and floors. Truly... a cornerless-corner enclosure.

Only University "KwiKits" have all these important features. Don't forget, the difference between mediocre kits and the finest is only a matter of a few dollars. Don't jeopardize the quality of your whole system by a false economy.



KEN-15



KEN-12

**Model KEN-15**—Similar to EN enclosure series in every respect except that "Kwi-Kit" employs simplified front frame design. Unique mounting board is pre-cut for 15" speakers and supplied with adapter for 12" speakers. Also for most of the popular 2 or 3 way P.S.E. Speaker Systems. Enclosure complete: 37" H, 28" W, 19 1/4" D. Model KEN-15—Net Price \$49.75.

**Model KEN-12**—Similar to Model KEN-15 except that mounting board is pre-cut for all 12" speakers. Also for most of the popular 2 or 3 way P.S.E. combinations. Completed enclosure measures 30" H x 21 1/2" W x 15 3/4" D. Model KEN-12—Net Price \$39.75.

(Instruction manual supplied free with each kit)

If you're interested in a lifetime of musical enjoyment, learn more about magnificent University "KwiKits."

**University**  
**LOUDSPEAKERS, INC.**

80 So. Kensico Ave. White Plains, N.Y. Desk B8  
Please send me valuable "KwiKit" information.

Name.....

Address.....

City..... Zone..... State.....



to  
be  
**SURE!**

buy  
**VOKAR**

the original-  
equipment  
**VIBRATOR**



Leading manufacturers of original-equipment auto-radios specify Vokar vibrators as components for installation on the production-line. Why? They're **sure** Vokar quality never varies—will always contribute to top performance demanded of today's radios.

You too can depend on Vokar vibrators—for sure starts, longer life, silent operation. For all replacement jobs, buy Vokar Imperial or Quality Brand vibrators to be **sure** of satisfied customers.

Now is the time to stock up on 12-volt vibrators—**ONLY TWO VOKAR IMPERIALS ARE NEEDED TO FILL ALL REPLACEMENTS!**



VOKAR—preferred by leading manufacturers of auto-radios.

**VOKAR**

VOKAR CORPORATION  
DEXTER 2, MICHIGAN


# Question Box


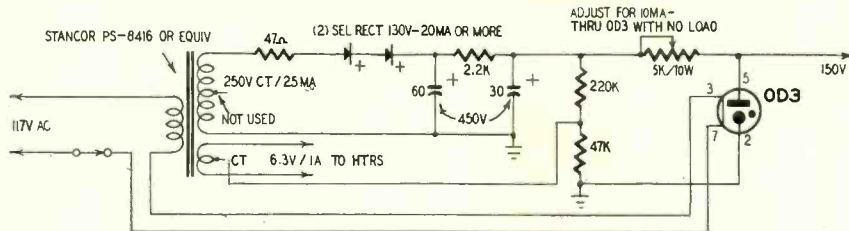
## CONTROL UNIT POWER SUPPLY

I plan to construct the Golden Ear control unit and would like to include a built-in power supply so it can be used with almost any power amplifier. Please show the circuit of a suit-

able supply.—R. G. A., Chicago, Ill. The power transformer is a Stancor PS-8416 or equivalent. The unit is wired so the primary of the power transformer is opened when the OD3 voltage regulator tube is removed from the socket. Set



This circuit will serve nicely when constructed as a separate unit or when built into the control unit. The power

able supply.—R. G. A., Chicago, Ill. This circuit will serve nicely when constructed as a separate unit or when built into the control unit. The power

## 155-MC CONVERTER

Please print or tell me where I can find a diagram of a converter for receiving 155.3-mc signals on an automobile radio. This frequency is used by our local volunteer fire department.—J. C. H., Kenmore, N. Y.


This converter will work into any receiver tuned to 1500 kc. A cascode rf amplifier and triode mixer are used for low-noise performance. The crystal-controlled oscillator minimizes drift and simplifies operation. Coils L1 and L3 are J. W. Miller types 1471 and 1472, respectively. L2 is 6 turns of No. 18 enameled wire on a ¼-inch form. The turns are spaced for minimum noise output. L4 is a CTC (Cambridge Thermionic Corp.) LS3 30-mc coil and L5 is a National type AR-2.

The rf chokes in the heater leads may be Miller type 4602 or equivalent

1-μh coils or 28 turns of No. 24 enameled wire closewound on a ½-watt 68,000-ohm resistor and connected in parallel with it.

This circuit can be used for almost any spot frequency between about 50 and 250 mc. The mixer injection frequency—the output of the multiplier following the oscillator—is 1500 kc above or below the desired signal. The oscillator operates on the fundamental of the crystal so the injection frequency is divided by 2, 3, 4, 5 or 6 to obtain a frequency in the range of readily available crystals.

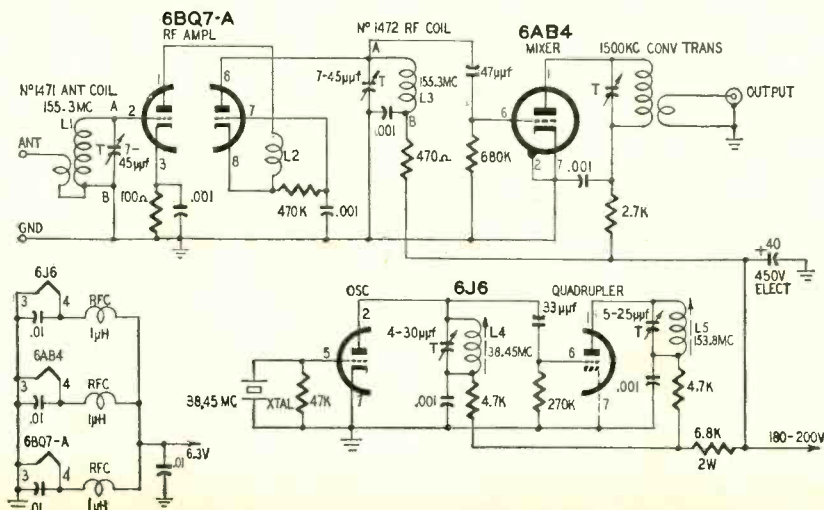The coils specified for L1 and L3 cover a range of from 110 to around 235 mc. The upper limit is determined by wiring and tube capacitances and the lower limit by the size of the tuning capacitor. For L4 you can use the CTC



30-mc coil to tune from around 18 mc with 100  $\mu\mu\text{f}$  to around 70 mc with 15  $\mu\mu\text{f}$ . The National AR-2 coil tunes from 70 mc with 100  $\mu\mu\text{f}$  to 220 mc with 10  $\mu\mu\text{f}$ .

A grid dip meter will be useful for prealigning the rf and oscillator circuits. In many instances, stray wiring capacitance and the proximity of the multiplier and mixer circuits will provide sufficient injection voltage to the mixer. In other cases a 2- $\mu\mu\text{f}$  capacitor or a twisted wire gimmick may be used between the mixer grid and the multiplier plate.

**RESISTOR TYPES**


*Resistors with ratings to about 2 watts are available in carbon-filament, deposited-carbon, boron-carbon, carbon-film, wirewound and noninductive wirewound types. In most instances parts lists do not specify the type. How can I determine the type to use for different circuits?—J. H. U., Youngstown, Ohio.*

The most commonly used resistor is the general-purpose carbon-filament type. It consists of a thin rod or slug of carbon encased in a composition or ceramic case for insulation and protection against humidity and mechanical damage. These are generally available in RETMA preferred values ranging from 2.7 ohms to 22 megohms in 1/2-, 1- and 2-watt sizes with tolerances of 10 and 5%. They are used where there is no need for exceptional stability or special low-noise characteristics.

Carbon-film, deposited-carbon and boron-carbon types are usually made by depositing a thin film of carbon or carbon compound on a ceramic body and then covering the whole with an insulator that seals the unit against moisture. These types are available in values ranging from around 10 ohms to 100 megohms with tolerances of 5, 2 and 1% and wattages ranging from 1/2 to 2. The full range of resistances may not be available from one manufacturer or in all wattages. These are used in low-noise preamplifiers and in applications where high stability and precision are required.

This type is ideally suited for use in the Williamson amplifier and similar circuits where high-quality and matched components are recommended. They are widely used in attenuators, bridges, test instruments and as meter multipliers and shunts. Generally, deposited-carbon resistors are much less expensive than wirewound types of the same tolerance, wattage and resistance.

Small wirewound resistors like the IRC BTW types are available in a much smaller range of values than are carbon-filament types. Generally, the values range from 0.24 to 820 ohms at 1/2 watt, 0.47 to 5,100 ohms at 1 watt and 1 to 8,200 ohms at 2 watts. Tolerances: 5 and 10%. This type is almost mandatory for values below about 10 ohms and is used—within its range of values—when the circuit requires re-

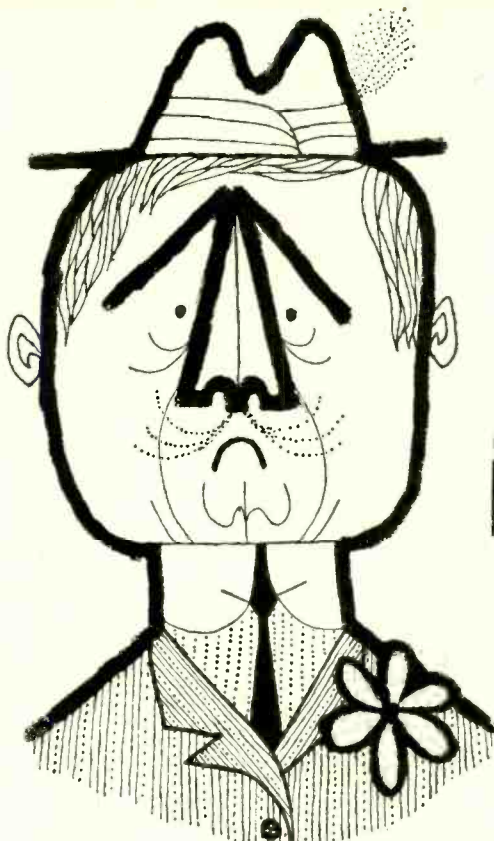

**SAD?**

because you weren't able to get your

**1956 *Radio Electronic* MASTER**

Sorry you were disappointed. In many areas, there just weren't enough MASTERS to meet the demand.

But — cheer up. If you act fast, we can help you get your industry-wide buying guide. We've located several distributors with extras on hand.


And what's more . . . you'll only pay the \$2.95 distributor price instead of the regular \$7.50.

- 100,000 items
- Complete descriptions
- Specifications—Prices
- 11,000 illustrations
- 8 x 11", 6 lbs.
- 350 mfrs.

*So send your coupon now . . . first-come — first-served.*

**1450-Page Buying Guide . . .**  
helps you shop before you buy The supermarket pages of The MASTER enable you to compare specs and prices first — then buy and save.

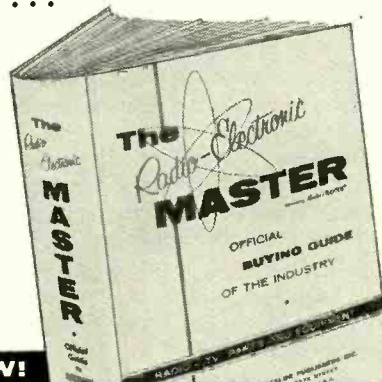**A Gold Mine of Facts . . .**  
on all the latest products and models . . . with changes in specs. It's all in The MASTER catalog file of the electronic parts industry.



**MAIL COUPON NOW!**

UNITED CATALOG PUBLISHERS, INC., 110 LAFAYETTE ST., NEW YORK 13, N. Y.  
*Here's my \$2.95. Please rush me the 1956 MASTER, Official Buying Guide of the Electronic Parts and Equipment Industry.*

Name.....

Address.....

City..... Zone..... State.....

RE-6



ELECTRICAL  
ENGINEERS  
or  
PHYSICS  
GRADUATES

with experience in  
RADAR  
or  
ELECTRONICS  
or those desiring to enter  
these areas...

The time was never  
more opportune than  
now for becoming  
associated with the field  
of advanced electronics.  
Because of military  
emphasis this is the most  
rapidly growing and  
promising sphere  
of endeavor for the  
young electrical  
engineer or physicist.

Since 1948 Hughes Research and Development Laboratories have been engaged in an expanding program for design, development and manufacture of highly complex radar fire control systems for fighter and interceptor aircraft. This requires Hughes technical advisors in the field to serve companies and military agencies employing the equipment.

As one of these field engineers you will become familiar with the entire systems involved, including the most advanced electronic computers. With this advantage you will be ideally situated to broaden your experience and learning more quickly for future application to advanced electronics activity.

Positions are available in the continental United States for married and single men under 35 years of age. Overseas assignments are open to single men only.

Scientific and Engineering Staff

RESEARCH AND  
DEVELOPMENT  
LABORATORIES

Culver City,  
Los Angeles County,  
California

Assurance is required that relocation of the applicant will not cause disruption of an urgent military project.

HUGHES

QUESTION BOX

(Continued)

sistors with greater stability and lower noise than carbon-filament types. Applications are the same as deposited-carbon types with the same ratings. However, they should not be used in rf and video circuits.

Noninductive wirewound resistors below 5 watts are usually precision types with tolerances around 1%. They are available in values between 0.1 and 500,000 ohms and are often used as meter shunts and multipliers.

Noninductive power resistors of 5 watts and higher, such as the Sprague NIT types, are often used as plate, screen and cathode resistors in high-powered video amplifiers, as grid leaks in high-powered class-C amplifiers and in other circuits where the inductance of a standard wirewound resistor cannot be tolerated.


In RADIO-ELECTRONICS parts lists we consider that resistors will be a carbon-filament type with 10% tolerance unless otherwise specified. When the make or type is not specified, precision resistors may be either wirewound or carbon types and power resistors will be the standard (inductive) type.

UNMARKED INDUCTORS

I have a number of surplus audio and filter chokes whose inductance is unknown. I have a scope, signal generator and vtvm. Is there any way that I can use these instruments to measure the inductance of the chokes?—W. M. C., Elizabeth City, N. C.

If an audio signal generator is available, connect the test circuit as shown with the vtvm across the unknown inductor. Vary the frequency of the generator between about 30 and 1,000 cycles and use different values of C until you get a peak deflection on the meter. Calculate the inductance from the formula

$$L = 25,000 / f^2 C$$

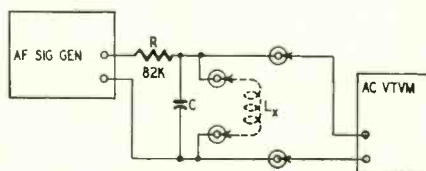

where f is the frequency in cycles, C the capacitance in microfarads and L the inductance in henries.

If a variable-frequency audio generator is not available, you can use the 400-cycle output of the signal generator or 10 volts or so from the 60-cycle line. The L-C circuit must now be tuned to resonance by varying the capacitance in the circuit. You can use a capacitance decade or a number of known capacitors in parallel. The inductance of iron-cored coils varies somewhat with frequency so filter chokes should be checked in the range of 60-120 cycles and audio chokes at 400 or 1,000 cycles. The value of R should be adjusted for a good sharp deflection on the meter. If too low, it loads the tuned circuit and the resonance curve is low and broad; if too high, deflection will be small. END

THE BOOK YOU NEED  
TO PRICE WITH SPEED...  
for profit

quick check for 60,000 prices  
Profit-making time-money-phone call-saver. 200 pocket-sized pages. Replacement parts listed by manufacturer, product and part number. up-to-date charging information  
Completely revised 4 times a year.



"Very useful to me" — Conway, Penna.  
"Need to have all prices" — Kincaid, Va.  
"Been able to find every item" — Frankfort, Ky.  
"It's a perfect book" — Truesel, Ont.

and the perfect partner...  
DAVE RICE'S OFFICIAL TV-RADIO SERVICE ORDER BOOK

For TV, Radio, Phono or Hi-Fi service, provides separate listings for:

Picture tubes, receiving tubes, parts and components, serial numbers, labor and state and local taxes. 5 1/2" X 8 1/2" — 50 sets of triplicate orders—carbons bound in.

at parts distributors or send check to

ELECTRONIC PUBLISHING CO., INC.  
180 NORTH WACKER DRIVE • CHICAGO 6, ILLINOIS

DIGEST: \$2.50 per copy.

ORDER BOOK: \$7.50 each or \$6.50 per dustproof box of 10.


# radio-electronic Circuits


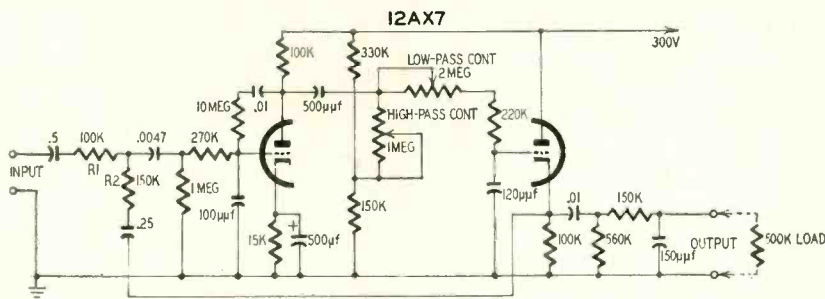
## VARIABLE BANDPASS FILTER

Bandpass filters with variable high- and low-frequency cutoffs are widely used in communications networks as sound-effects filters for recording and broadcast applications and may be used as combined rumble and scratch filters in phonograph amplifiers. The unusual bandpass filter shown in the diagram

18 db per octave. The cutoff (3-db point) of the high-pass filter is variable from 35 to 100 cycles and the low-pass element has a cutoff variable from 5,000 to 14,000 cycles. This results in a bandpass circuit with a minimum bandwidth of 100 to 5,000 cycles and maximum of 35 to 14,000 cycles. Bandpass is widest



was used as an example in the article "The Design of Filters Using Only R-C Sections and Gain Stages" in *Electronic Engineering* (London, England).


In this circuit, the bandpass effect is obtained by inserting variable-frequency high- and low-pass filters in the feedback loop around a two-stage amplifier. The filters have slopes of approximately

when the low-pass control is set to minimum and the high-pass control to maximum resistance. Circuit gain is unity and response is flat to within 0.5 db with the controls set for widest response. The circuit can be fed from any source of approximately 100,000 ohms and is designed to work into a load of around 500,000 ohms.
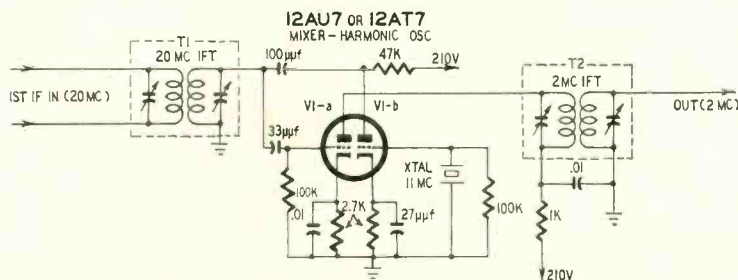
## NOVEL MIXER CIRCUIT

Double-superheterodyne type receivers are widely used for vhf and uhf reception. The first if is high to provide good image rejection; the second, much lower, one provides greater amplification and selectivity per stage than the first. In most double superhets, the

In this arrangement, the first if is 20 mc and the second is 2 mc. V1-b is a crystal oscillator with a shunt-fed plate circuit. The secondary of the 20-mc if transformer (T1) serves as the oscillator plate tank. Its resonant frequency is sufficiently close to the second



second converter or mixer stage uses a pentagrid converter tube in a circuit very much like that used in broadcast sets. This novel mixer circuit is the invention of Roy A. Beers, Jr. and Wm. L. Gensel and is described in patent No. 2,713,634. It is designed to reduce the number of components normally used in second-converter circuits and to use a frequency-doubling crystal oscillator without extra tuned circuits.

harmonic of the crystal (22 mc) to provide sufficient impedance for frequency doubling.

The incoming 20-mc if signal and the second harmonic of the crystal appear across the secondary of T1 and are capacitance-coupled to the grid of mixer V1-a. These two signals beat in the mixer and the difference frequency (2 megacycles) appears across the primary of T2.

# BEST BUY IN SCOPES



new!  
**Simpson**  
**COLORSCOPE**  
MODEL 458

Compare the new Simpson Colorscope Model 458 with any oscilloscope on the market. It is an advanced, seven-inch, high-gain, wide-band scope especially designed for color-TV service. Ideal for black and white, too.

**100% RESPONSE** at 3.58 mc color-burst!

**DUAL bandwidth**—narrow or wide!  
**FLAT FREQUENCY RESPONSE**, within 1 db to 4.5 mc!

**RISE TIME** less than 0.05 microsecond (wide band)!

**FULL RANGE** compensated vertical attenuator!

Price with shielded input cable, **\$229.95** manual...

Four accessory probes available for extra utility!

See your distributor for details or write—



## SIMPSON Electric Company

WORLD'S LARGEST MANUFACTURER  
OF ELECTRONIC TEST EQUIPMENT


5200 W. Kinzie St., Chicago 44, Illinois

Phone: EStebrook 9-1121

In Canada: Bach-Simpson Ltd., London, Ont.



# Time for Replacement?

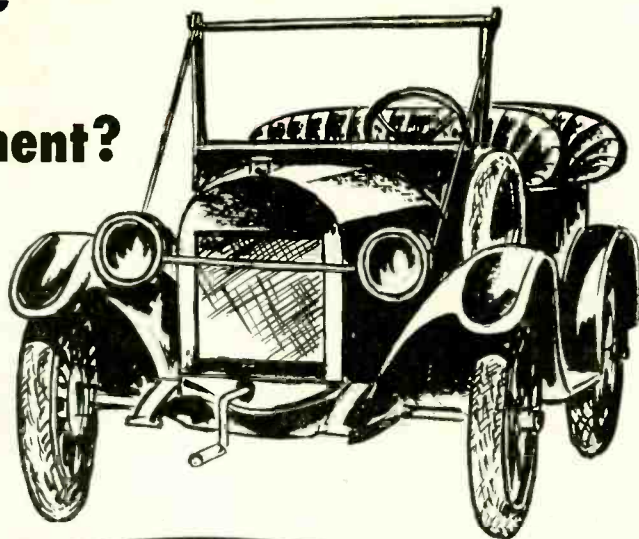

We **GUARANTEE** you speakers that are built to be the finest exact replacement speakers. We stand behind each and every speaker with a 100% guarantee against any mechanical or electrical defects for one full year.

**OXFORD** Replacement Speakers undergo a rigid inspection to make certain that they are as good or better than the original speaker. That's why more servicemen are switching to **OXFORD** . . . when it's time for replacement.

*Illustrated literature is available without obligation. . . . at better jobbers!*

## OXFORD ELECTRIC CORPORATION

Distributor Sales Division

556 West Monroe Street, Chicago 6, Ill.

In Canada: Atlas Radio Corp., Ltd., Toronto

Export: Roburn Agencies, New York City



The interesting July issue of  
**RADIO-ELECTRONICS**  
On Sale June 26

## ENGINEERING

B. S. DEGREE  
IN 27 MONTHS

Prepare for unlimited opportunities of the Electronic Age! Earn your B.S. degree in 27 months at Indiana Technical College. Intensive, specialized course. Comprehensive training in math and electrical engineering, advanced radio theory and design, television, electronics. Modern laboratories. Low rate. Also B.S. DEGREE IN 27 MONTHS in Aeronautical, Chemical, Civil, Electrical and Mechanical Engineering. G.I. approved. Enter June, September, December, March. Earn part of your expenses in Fort Wayne while studying. Write for catalog.

**INDIANA TECHNICAL COLLEGE**  
1766 E. Washington Blvd., Fort Wayne 2, Ind.

Please send me free information on B.S. ENGINEERING DEGREE IN 27 MONTHS as checked.

Electronics  Chemical  Aeronautical  
 Civil  Mechanical  Electrical

Name \_\_\_\_\_  
Address \_\_\_\_\_

## NORDIC

CUSTOM RADIOS FOR  
1952 TO 56 FORDS

SUPERHETERODYNE • BIG 6 x 9  
INCH SPEAKER • LOW BATTERY  
DRAIN • EASY INSTALLATION  
PERMEABILITY TUNER



\$38<sup>90</sup>

WRITE FOR LITERATURE

NORDIC RADIO COMPANY • BOX 582 • EVANSTON, ILL.

## LMB BOX CHASSIS OFFERS FREE

inside LMB boxes

10 tested kit diagram projects for the builder. Each one of these kit diagrams built by a recognized expert. Kit projects are complete in every detail. Circuit diagram, photo of project both front and rear photo. Rear photo shows wiring and parts. Detailed instructions for building, complete parts list and approximate cost. Complete to build except parts and your distributor can supply the parts. Ask your distributor for the list of LMB kit Diagram Projects. If he does not have them, write to


**LMB** 1011 Venice Blvd.  
Los Angeles 15, Calif.

## FLYBACK CHECKER

Shorted turns in a TV flyback transformer or horizontal deflection coils are difficult to detect without special equipment, especially when the defect does not cause complete loss of brightness or raster. This simple flyback tester, described in *Radio Constructor* (London, England), can be constructed readily from parts taken from the junkbox or for around \$15 or so with new parts.

The circuit is basically an L-C audio oscillator operating around 1 kc with a 500- $\mu$ a meter to indicate grid current. When a flyback transformer with a shorted turn is connected across the test prods, it loads the tuned circuit and produces a sharp dip in grid current.

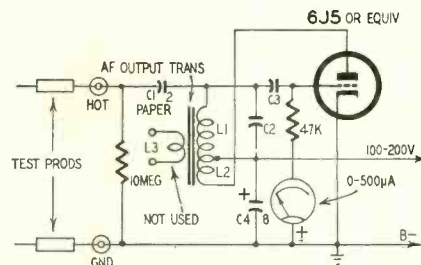The oscillator is designed around an audio output transformer with a tap one-quarter to one-third the distance



from one end. The inductance of the transformer primary should be low so a miniature or small output transformer is recommended. (An ac-dc type transformer with a hum-bucking tap or a type designed for three-way portables with separate output tubes for battery and line operation will probably work nicely.—*Editor*)

In the circuit, L1 is the part of the primary with the greater number of turns. L2 is used as the feedback winding and L3 is the secondary. This winding is not used when testing transformers.

To set up the checker, temporarily use a 500- $\mu$ f capacitor for C3 and connect a pair of high-impedance phones or an amplifier with high-impedance input across L3. Adjust the value of C2 for a pure note of about 1,000 cycles—a scope will be handy here. Remove the 500- $\mu$ f capacitor used for C3. Starting with around 100  $\mu$ f, increase the value of C3 to find one that gives a reading of about three-quarters of full scale before squegging starts. Disconnect the phones or amplifier and tape the leads to L3.

Connect the test prods across all or nearly all of the primary of a good flyback transformer. This will cause a slight drop in grid current. Now, temporarily connect a jumper between two adjacent taps on the transformer to simulate a shorted turn. The meter reading should drop sharply. As a final test, remove the jumper from the taps and wind a single turn of wire around the core close to the primary and short the ends together. The grid current should drop sharply.


If connecting the test leads across the plate winding of a good flyback transformer causes a large dip in grid current, the inductance of L1 is too high and must be reduced by removing laminations from the transformer used in the oscillator circuit or the core gap must be increased. In any case, re-adjust the value of C2.

C1 is a blocking capacitor. The 10-megohm resistor eliminates the static charge that would appear on the hot test lead when the tester is turned on.
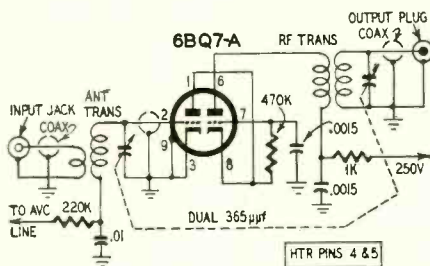
### BROADCAST BOOSTER

In an effort to increase the sensitivity of a 1936 superhet, I tried half of a twin triode as an rf amplifier. This helped but left much to be desired so I tried a cascode. After some experiment to get maximum gain I arrived at the circuit and values shown in the diagram.

Construction is simple and is not critical but I recommend that the layout be as compact as possible. Ground pin 9 of the tube socket and shield the lead to the grid (pin 2) of the input stage to prevent oscillations. Standard broadcast antenna and rf coils are used with a two-gang 365- $\mu$ f capacitor. My



unit uses unshielded coils and is quite stable but shielded coils will provide added insurance against oscillation. Use coax or low-loss cable where shielding is indicated. Regular shielded cable attenuates the signal too much.

The unit requires 250 volts dc at about 20 ma and 6.3 volts at 600 ma. This can be taken from most sets or you can use a small power supply. I have not measured the gain but it does bring the weak stations up out of the noise.—John M. Rhodes END



"Are you still on TV, Miss La Veri?"

**NO HUNTING**  
for the right dual-control replacement

... not if you have a

## Centralab Fastatch<sup>®</sup> FR-22A Kit

- Always handy, right at your fingertips — the dual-concentric replacements you need 80% of the time, for all popular TV, radio, and auto sets.
- Each control is factory assembled, tested, and guaranteed.
- Kit contains 22 control units, 4 Fastatch switches, 2 auto adapter bushings.
- Ask your Centralab distributor to tell you more. Or send coupon for bulletin 42-223.

**Centralab**  
A DIVISION OF GLOBE-UNION INC.  
922F East Keefe Avenue, Milwaukee 1, Wisconsin  
Send me Fastatch bulletin 42-223

Name.....  
Company.....  
Address.....  
City..... Zone..... State.....

**CRL**

B-5614

**\$23.50**  
including sturdy metal cabinet  
Suggested net price




Now Available! NEW...


# VACO®
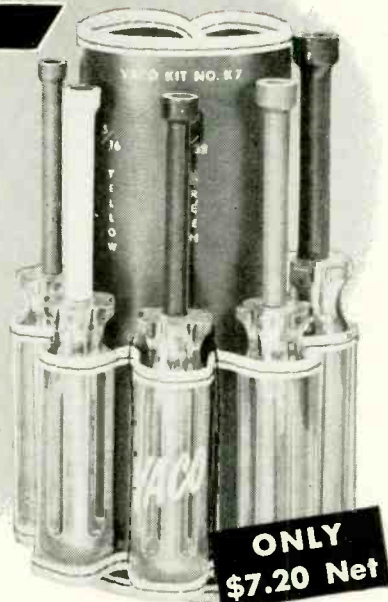
## Hollow Shaft NUT DRIVERS in Color

Nothing else like them anywhere! Choice of 28 types and sizes! New plastic kit at right contains 7 most popular drivers in self-standing bag for service work or bench use.



**ONLY \$7.20 Net**

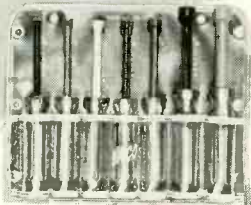

**No. K7 Self-Standing Service Kit  
Stands Up! Hangs Up! Folds Up!**

Stands upright for easy accessibility. May be hung flat on wall or may be folded. Each driver fits in individual holder marked for size, color.

### Check These 6 Important VACO Features

NEW! Each size color-keyed!

NEW! All-hollow shafts

NEW! Extra large VACO Comfordome Handles!



NEW! Extra hard long wearing sockets!

NEW! Shafts insulated from handle to tip!

NEW! Available in 4 shaft lengths and 7 Hex sizes!

**THIS COUPON WORTH \$1.20**

Coupon only valid for use as stated below. Not valid in states where prohibited.

Name..... R. E.  
Street.....  
City..... Zone..... State.....

**VACO PRODUCTS COMPANY**  
317 E. Ontario St., Chicago 11, Ill.  
In Canada: Vaco-Lynn Products Co., Ltd., Montreal 1, Que.

Take this coupon to your jobber. It is worth \$1.20 when filled in and used to purchase one VACO K7 Kit. If your jobber cannot supply you, write direct.

You can SAVE up to \$5.05 when you SUBSCRIBE to  
**RADIO-ELECTRONICS**

154 West 14 St.,

New York 11, N.Y.

## TAPE RECORDERS

Tapes—Accessories  
Nationally Advertised Brands  
**UNUSUAL VALUES**  
Send for Free Catalog  
**DRESSNER**  
69-02 RE 174 St.  
Flushing 65, N. Y.



## EASY TO LEARN CODE

It is easy to learn or increase speed with an Instructograph Code Teacher. Affords the quickest and most practical method yet developed. For beginners or advanced students. Available tapes from beginner's alphabet to typical messages on all subjects. Speed range 5 to 40 WPM. Always ready—no QRM.



**ENDORSED BY THOUSANDS!**

The Instructograph Code Teacher literally takes the place of an operator-instructor and enables anyone to learn and master code without further assistance. Thousands of successful operators have "acquired the code" with the Instructograph System. Write today for convenient rental and purchase plans.

**INSTRUCTOGRAPH COMPANY**

4701 Sheridan Rd., Dept. RC, Chicago 40, Ill.

## INVENTORS

Send for  
**PATENT INFORMATION**  
Book and  
**INVENTORS RECORD**  
without obligation  
**GUSTAVE MILLER**  
RE-66 WARNER BUILDING  
WASHINGTON 4, D. C.

**REGISTERED PATENT  
ATTORNEY**  
**ASSOCIATE EXAMINER**  
U.S. PAT. OFF. 1922-1929  
Patent Attorney & Advisor  
U.S. Navy Dept. 1930-1947  
**PATENT LAWYER**

# Business



## Merchandising and Promotion

Sprague Products Co., North Adams, Mass., has made window-sized blowups of its recent advertisement "Sprague Salutes the Independent Service Dealer." These will be made available to service technicians through parts distributors throughout the country.

RCA Tube Division, Harrison, N. J., has designed a colorful new carton for its Silverama aluminized TV picture



tubes. Tube numbers are printed in large type on the labels.

Clarostat Manufacturing Co., Dover, N. H., is now packaging the several different sizes of its RTV matched-replacement controls in standard cartons which have been designed to provide for easier stocking.

Tescon TV Products, Springfield Gardens, N. Y., is marketing its "Do-It-Yourself" outdoor antenna kits in brilliantly colored new display containers.

Gray Research & Development Co., Manchester, Conn., has planned a high-fidelity demonstration system to promote record sales. The systems are available to dealers on a liberal long-term rental plan.

General Cement Manufacturing Co., Rockford, Ill., designed a new merchandising display for its Spra-Koat power spray chemicals for TV-radio service technicians.



## Production and Sales

RETMA reported the production of 588,347 TV sets and 1,078,624 radios in

RADIO-ELECTRONICS



**NEW** BE QUALITY WISE...  
BUY QUAL-KITS!

**Hi-Fi AM-FM Tuner**  
Advanced 7 tube circuit provides full sensitivity and selectivity giving this AM-FM tuner exceptional hi-fi reception. Armstrong FM circuit with limiter, Foster-Seeley Discriminator. 20-20,000 cps response. Full AFC control—no drift.



**Hi-Fi Amp.**  
Complete 6 tube-10 watt amplifier. Push-pull beam power output, built-in pre-amp. 5 position selector switch, 3 position record equalization, LP, RIAA, Eur. Response 1/2 db. 20-20,000 cps. Output 10 watts at less than 2% IM. Low noise level and harmonic distortion.



\$23.95

\$28.50

Cover and legs optional

Every kit complete with step-by-step fully illustrated 28 page instruction and assembly manual. Write today for FREE catalogue and name of nearest dealer carrying these remarkable units.

**Quality-Electronics** Dept. E-4  
319 Church Street New York 13, N. Y.

## TV TUNER REPAIRS

### 48-HOUR SERVICE

Defective tuners rebuilt to factory standards. New tuner guarantee. Ship prepaid.

### RADIO PRODUCTS CO.

College Point 56 • New York

We carry a full stock of Replacement Tuners for all makes of T.V.

**EXAMINE** Profit NOW with the latest on successful transistor design, application, operation

—in ONE COMPLETE VOLUME!

# TRANSISTOR ELECTRONICS

by Arthur W. Lo, Richard O. Endres, Jakob Zawels, Fred D. Waldhauer, Chung-Chih Cheng; all RCA engineers.



At last, here's an authoritative, practical book which rounds up all available information, ideas and techniques on transistors and presents this useful data to you in 520 illustrated, easy-to-follow pages! These RCA experts cover the whole field, from design and operation of transistors to their application. Much material is just released, printed here for the first time. Whether you're a beginner or seasoned vet... working in radar, TV, radio, computing, or allied fields... this complete, new book will give you mastery of transistors and show you how to use this knowledge profitably and successfully!

### Gives Complete Coverage. Including:

Physical concepts (36 pages) . . . characteristics, parameters, equiv. circuits (44 pages) . . . basic amplifier configurations (50 pages) . . . low freq. amplifiers (42 pages) . . . hi-freq. amplifiers (39 pages) . . . power amplifiers (28 pages) . . . hi-freq. operation (47 pages) . . . physical interpretation of transistor parameters (38 pages) . . . oscillators (38 pages) . . . modulation & demod. (43 pages) . . . pulse circuits (76 pages) . . . tabular analyses of fundamental transistor networks & circuits . . . shows parallels, contrasts between transistor and vac. tube circuits . . . features practical circuits . . . plus much more valuable material and workable, useful techniques.

### MAIL NOW—FREE TRIAL OFFER

Prentice-Hall, Inc., Dept. 5744-H1  
Englewood Cliffs, New Jersey

Please send me a copy of TRANSISTOR ELECTRONICS for 10 days' FREE use. Within 10 days I'll either return book and owe nothing, or will keep it and remit \$4 down (plus small postage charge) and then \$4 a month for two months in full payment.

Name .....

Address .....

City..... Zone..... State.....

Save! Send \$12.00 with this coupon and we pay postage. Same return and refund guarantee.

## BUSINESS

(Continued)

January, 1956. This compares with 654,582 TV sets and 1,068,146 radios in January, 1955.

### New Plants and Expansions

Shure Brothers is now located in its own newly constructed plant in Evanston, Ill., which provides greatly expanded facilities for the manufacture of Shure's varied line of microphones, pickup cartridges, etc.

Sylvania Electric Products Parts Division, Warren, Pa., has purchased Formatic Machine Co., Naugatuck, Conn. The division also announced plans for a 110,000-square-foot plastics plant in Warren. The new building is scheduled to be completed and ready for occupancy by the end of this year.

United Catalog Publishers, Inc., New York, established a West Coast sales office in Beverly Hills, Calif., under the direction of Charles H. Mitchell.

Federal Telecommunication Laboratories, Nutley, N. J., established a California branch in Los Angeles. Paul R. Adams, director of the Electronics Systems Laboratory, was named manager of the new branch.

RCA established an Advanced Development Laboratory in Needham, Mass. for work on ferrites. It will be under the direction of Dr. Francis E. Vinal.

Mueller Electric Co., Cleveland, Ohio, broke ground for a 6,000-square-foot addition to its production floor space.

Ebcor Electronics Co., Baldwin, N. Y., was established by Edward Berliant, formerly head of Ed-Berl Products, Inc. The company will package and distribute Dow-Corning silicone products as well as manufacturing antennas, test equipment, etc.

Supreme Publications closed its Chicago office and consolidated operations at its Chicago warehouse, 416 W. Huron Street, and Highland Park, Ill. facilities.

Esco Electronics, Inc., Chicago, purchased the Electronics Division of Mitchell Manufacturing Co. of the same city. Esco will manufacture phonographs, radios and hi-fi equipment under the Mitchell brand name.

### Business Briefs

... Raytheon Manufacturing Co., Waltham, Mass., has begun production on an 8½-inch TV picture tube designed for portables. Photo shows C. F. Adams, Jr. (center), Raytheon president, discussing the tube with Curt Hammond—



(right), manager of Raytheon's equipment tube sales, and F. E. Anderson, manager of distributor tube sales. END

# HERSHEL SPECIALS

## All New MYSTERY PACKAGE of ELECTRONIC PARTS



Worth \$40.00

Our Price \$3.95

Ship. Wt. 20 lbs.

It's the surprise of your life! 20 pounds of BRAND NEW usable GOVT. surplus. The ideal gift for hams, etc.



TYPE A 4¼" Dia.  
TYPE A-106 330 MC-  
Average Type

## BUTTERFLY CONDENSERS YOUR CHOICE

\$4.95



TYPE B 4¾" Dia.  
TYPE B-122 485 MC



TYPE C  
TYPE C-300 1000 MC  
Type 30885 Vbr.

These units make the finest tuners for Ultra-high frequency transmitters, receivers, frequency meters, and oscillators.



TYPE D  
TYPE D-300 1000 MC  
C16 for 300 Vbr.

## RELAYS

3VDC 11-OHMS D.P.D.T.

3A. CONTACTS \$1.29

6VDC 24-OHMS D.P.S.T.

8A. CONTACTS \$1.95

110VAC 15A CONTACTS S.P.S.T. \$1.75

TELEPHONE TYPE 7500-OHMS S.P.D.T. 2A. CONTACTS \$2.49

## OIL CONDENSER

\$1.65

2 MFD. 3000 VDC. Pyranol Oil W/Mounting Brackets.

3-1 MFD. 3000 VDC. New, removed from equip. 4¾"x4¼"x 2½"

GE Pyranol Oil CONDENSER

12 MFD. 330 VAC. \$6.00

Removed from equip. NEW. 95¢

## PHOTO ELECTRIC CELL

95¢

CE Vacuum Cell, used in A. M. P. R. O. Sound Projector. Also useful for opening garage doors and Alarm Systems.

BRAND NEW \$4.95

## ALL-PURPOSE FIL. TRANSFORMER

PRI. 117 v. 60 cyc. sec.

8.4 v. ....12A

6.2 v. ....10A

5 v. ....7.5A

3.5 v. ....3A

2.5 v. ....1.75A

BRAND NEW \$4.95

## RCA Output Transformer

P.P. 6L6's 28 WATTS

Pri. 5000 ohms output SEC. ±1 500 ohms ±2 600 ohms bidstone 18 to 15,000 cy. Rat.

\$1.95

Hi Gain Dynamic Mike Kit

Uses UTC Transformer & Western Electric Mike. Ideal for Hams, PA., CAP, Recording Mobile Equip. —50 DB 80 to 7500 CPS. Diagram Furnished.

\$1.95

## SWING CHOKE

2H-7H 550 MA. Thordarson T48003. \$5.95

## AUDIO CHOKE

60H-1MA. 4,500 ohms. 15,000 turns of 44 wire. Size: 1½" x ¾" x ¾" Ideal for radio control, planes, boats, etc. 95¢

## 100 ASSORTED CRYSTALS

FT-243 FT-241A FT-171B Type Holders FREQ. RANGE 2015 KC to 38.1 MC.

\$50.00 Value \$7.95

HOTTEST BUY IN THE U.S.A.

## ALLIGATOR CLIP

Piercing type with 5 Ft. cord and spade lub. Ideal test clip. TL-137. 2 for 25¢

TERMS: Cash with order or 25% DOWN—BALANCE C.O.D. ALL PRICES NET F.O.B. DETROIT MINIMUM ORDER \$2.00

# HERSHEL RADIO CO.

5249 GRAND RIVER Detroit 8, Michigan

Si vous lisez le français technique, vous devez lire  
**ELECTRONIQUE INDUSTRIELLE**  
la grande revue française de technique moderne  
Specimen gratuit sur demande  
**EDITIONS RADIO**  
9, rue Jacob — Paris 6 — France



new!

twins by **ARKAY**

Arkay Model

**HFT-7 Hi-Fi AM FM Tuner Kit**

Matching tuner which offers less than 1% distortion and a -70db hum level. Sensitivity is 6 uv for 20 db quieting on FM and 20 uv on AM. FM selectivity is 200kc . . . bandwidth 8db down; AM, 8kc bandwidth 5db down. A unit to suit the discriminating tastes.

With AFC control and defeat **\$29.95**

Available in FM only **\$23.95**

Less Cover



Arkay Model

**FL-10 Hi-Fi Amp-Pre Amp Kit**

Williamson type super-linear amplifier with built-in pre-amp. Pushpull 12 watt output frequency response ± 1 db, 10 to 40,000 cps with extremely low IM and harmonic distortion. An amplifier to be proud of. **\$28.95**

Arkay Miniature Radio

Superheterodyne circuit and hearing aid type ear piece. 5 1/4" x 3 1/4" x 1". **\$12.95**



Arkay Model A-12

**Hi-Fi Amplifier Kit**

12 watt output . . . 5 inputs. Master controlled at front panel. **\$22.95**



Testing Kits



Television Kits



Radio Kits

Visit your local distributor for these wonderful kits and write today for the special FREE Radio Kits Catalogue and list of dealers. Your copy will be sent by return mail with no obligation. Write to . . .

**Radio Kits Inc., Dept. 8 120 Cedar Street, New York City**

**OPPORTUNITY ADLETS**

Rates—15c per word (including name, address and initials) Minimum ad 10 words. Cash must accompany all ads except those placed by accredited agencies. Discount, 10% for 12 consecutive issues. Misleading or objectionable ads not accepted. Copy for August issue must reach us before June 15, 1956.

**RADIO-ELECTRONICS,**  
154 West 14 St., New York 11, N. Y.

**HIGH-FIDELITY SPEAKERS REPAIRED.** Amprite Speaker Service, 70 Vesey St., New York 7, N.Y. BA 7-2580.

**SPEAKER RECONING:** Guaranteed workmanship. C&M Recone Co., 255 Tloza St., Trenton 9, N.J.

**CHASSIS & panels cut and punched to your specifications, panels engraved.** Send sketch for estimate. Chicago Electronics, 1214 West Madison Street, Chicago, Illinois.

**NEW. Build pocket radios, 5 selected plans, 50c.** COOK, 4003-R Roosevelt, Midland, Texas.

**DIAGRAMS FOR REPAIRING RADIOS \$1.00.** Television \$2.00. Give Make, Model. Diagram Service, Box 672-RE, Hartford 1, Conn.

**NEW! Versatile "No-Disturb" TV extension SPEAKER 4"x4"x2".** Three-way remote control. Details. ELECTRONIC, Box 1142, Lancaster, Pa.

**FREE PLASTIC CARD CASE!**  
**WITH YOUR ORDER FOR 1000 PROCESS EMBOSSED BUSINESS CARDS. AS YOU LIKE! ONE OR TWO COLORS!**

Every business man—and professional man as well—knows the impression created by his appearance. Most important is the card you present. A "Showmanship" Business Card is an important factor. You know the right impression is created when you proudly present—an Exclusive, Distinctive, Expensive-Looking EMBOSSED Card. Raised printing—done by Mastercraftsmen—with "know how." A card with Raised Letters—with the "feel" and Character of Fine Engraving. Leading Executives use Showmanship Cards, creating the impression of Position, Prestige and SUCCESS! Yet—our cards cost you less than the ordinary cheaply printed cards. It's easy to order cards from us. Simply PRINT or TYPE whatever you want to appear on the card—on any handy slip of paper. Pin to a money order or check for just \$4.95—and rush it to us —by fast mail. You'll get prompt service. Cards will be rushed to you prepaid. With your FREE Plastic Card Case. Get your order in the mail—NOW! FAULTLESS ORGANIZATION, 684 N. Sangamon St., Chicago 22, Ill.

**TUBES—TV, RADIO, TRANSMITTING, AND SPECIAL PURPOSE TYPES BOUGHT, SOLD AND EXCHANGED.** Send details to R. E. Gensler W2LNI, 512 Broadway, N.Y. 12, N.Y.

**ALL MAKES OF ELECTRICAL INSTRUMENTS AND TESTING equipment repaired.** Write for free catalogue on new and used instruments at a savings. Hazelton Instrument Co., 128 Liberty Street, New York, N.Y.

**TRADE IN TV SETS \$14 up.** JONES RADIO, 1115 Rambler, Pottstown, Pa.

**TAPE RECORDERS, tapes:** Wholesale prices. KARSTAN, 215 E. 88 St., New York 28, N.Y.

**WANTED: AN/APR 4, other, "APR", "TS-", "IE-", ARC-1, ARC-3, ART-13, BC-348, etc.** Microwave Equipment. Everything Surplus. Special tubes, Tec Manuals, Lab Quality Equipment, Meters, Fast Action, Fair Treatment. Top Dollar! Littell, Fairhills Box 26, Dayton 9, Ohio.

**JAPAN DIRECTORY.** 100 Japan exporters, plus opportunity mail. Just \$1.00 today. NIPPON ANNAL, 920-3rd Ave. Seattle 4, Wash.

**WANTED—Tech Manual or alignment instructions for R-28/ARC-5 VHF recvr.** A. M. NOHE, 246 W. 6 Ave., Huntington, W. Va.

**DIAGRAMS: Professional Model Timers, Counters, Intercoms, Organs, etc.** \$1.00 each. List free. Parks, 101 S.E. 57th, Portland 15, Oregon.

**RADIO, RADAR, TELEVISION instruction leading to Licenses.** Port Arthur (Texas) College.

**FOREIGN jobs list. Technicians needed.** \$1. RATHE, Box 173, New Orleans 3, La.

**WANTED—All types of electronic tubes:** broadcast, transmitting, receiving, Magnetrans. Klystrons, also all varieties airborne equipment: ADF-70; ARC-1, -3, -4, -12, -15, -27, -33; ARN-6, -7, -12, -14, -18; BC-312, -342, -610E, -788C, -2121; I-152, ID-18; MN-24C, -31C, -36, -42, -53, -58, -61, -85, -97F, -100A; RA-18; TA-18; 17-L3; 51-R, -R3; 51-V1, etc. TOP DOLLAR PAID. Write to ROBERT E. SANNET, W6REX, 1524 S. Edris Dr., Los Angeles 35, Calif.

**FOR ALL YOUR HI-FI REQUIREMENTS:** Speakers, Amplifiers, Tuners, Turntables, etc. COMPLETE STOCK. Shipments Prepaid. Write us your requirements TODAY. SOUND MATE UNLIMITED, INC., 63-03 39th Ave., WOODSIDE 77, N.Y.

**1,000 BUSINESS CARDS, CASE.** \$3.50. STUART PRINTING SERVICE, BOX 115-RE-1, PHILADELPHIA 5, PENNA.

**DIAGRAMS—Repair Information!** Radios, Amplifiers, Recorders \$1.00. Televisions \$1.50. Send Make, Model, Chassis (Air-Mail ? + 20c) TV MILTIE, Box 101-E, Hicksville, New York.

**GET INDUSTRIAL ELECTRONICS in Questions and Answers** by Edward Bukstein, RADIO-ELECTRONICS writer, for complete knowledge without systematic studies. Just published, \$3.95. FREDERICK UNGAR PUBLISHING CO., 105 E. 24 St., New York 10, N. Y.

**TV FM ANTENNAS, ALL TYPES.** Mounts, accessories. Lowest prices. Wholesale Supply Co., Lunenburg 2, Mass.

**CHICAGO PERSONAL MAIL ADDRESS \$1 MONTHLY.** Business Address for small concerns \$2. Confidential. Receiving, Forwarding. Write—F. ORGANIZATION—684 N. Sangamon St., Chicago 22, Ill.

**JUST OFF THE PRESS!**

There's money in servicing record changers, and this new Gernsback Library book shows you how to get it! Discusses each functional assembly as a unit, so that even if you're a rank beginner as far as changers go, in no time at all you'll be able to tackle any and all types. Many special line drawings illustrate all the details of automatic record-changer mechanisms. A basic book, it is nevertheless an excellent reference for those familiar with changers. Put in your bid for that extra servicing money now—order your copy today.

**Servicing Record Changers—Partial list of contents**

- Sequence of operation • Motors • Drive assemblies • Turntables • Pickup arm, cartridges • Trip Mechanisms • The Cycle Drive • Arm Lift and Pull-Back
- Record Release • Record Indexing and Arm • Set-Down • Automatic Shutoff • Care and Handling • Trouble Shooting Charts.

**THE COMPLETE GERNSBACK LIBRARY—PAPER-COVERED EDITIONS**

Basic Audio Course, No. 66.....\$2.75	Transistors—Theory and Practice, No. 51.....\$2.00
Hard cover ed.....\$5.00	TV Repair Techniques, No. 50.....\$1.50
Maintaining Hi-Fi Equipment, No. 58.....\$2.90	Radio & TV Test Instruments, No. 49.....\$1.50
Hard cover ed.....\$5.00	High-Fidelity—Design Construction, Measurements, No. 48.....\$1.50
The V.T.V.M. No. 57.....\$2.50	Radio & TV Hints, No. 47.....\$1.00
Hard cover ed.....\$4.60	Television Technotes, No. 46.....\$1.50
High-Fidelity Circuit Design, No. 56, Deluxe hard cover ed. only.....\$5.95	Radio Tube Fundamentals, No. 45.....\$1.00
Sweep and Marker Generators, No. 55.....\$2.50	Basic Radio Course, No. 44.....\$2.25
Hard cover ed.....\$4.60	Model Control By Radio, No. 43.....\$1.00
Probes, No. 54.....\$2.50	High-Fidelity Techniques, No. 42.....\$1.00
Hard cover ed.....\$4.60	Practical Disc Recording, No. 39......75
Radio-Control Handbook, No. 53.....\$2.25	
The Oscilloscope, No. 52.....\$2.25	
Hard cover ed.....\$4.60	

**NOW—MAKE EXTRA MONEY SERVICING RECORD CHANGERS**



Servicing Record Changers

By Harry Mileaf

Gernsback Library Book No. 59. 224 pages. Illustrated.

Paper cover ed. \$2.90

Hard cover ed. \$4.60

**GERNSBACK LIBRARY, INC.**

154 West 14th Street, New York 11, N. Y.

- 39  42  43  44
- 45  46  47  48
- 49  50  51  52
- 53  54  55  56
- 57  58  59  66

Hard cover editions By mail only

- 52H  54H  55H
- 57H  58H  59H
- 66H

Enclosed is my remittance of \$..... 66

Please send me the books checked postpaid. Prices 10% higher in Canada.

Name..... please print

Street.....

City..... State.....



# People



Maurice V. Odquist joined Sylvania Electric Products, New York, as director of new product sales. A well known marketing and advertising executive, he

was formerly associated with C & C Super Corp., Newell Emmett Co., Kenyon & Eckhardt, and Biow Co.

Russell D. Gawne, promoted to general sales manager of General Cement Manufacturing Co., Rockford, Ill., had been sales manager of the G-C Electronics



Manufacturing Co.

Richard A. Kleine was appointed sales manager of Rohn Manufacturing Co., Peoria, Ill., tower and mast manufacturer. He comes to Rohn from Baker



Manufacturing Co.

Jay Carver (left), former advertising manager of Cabinart, joined Electro-Voice, Inc., Buchanan, Mich., to handle wood product sales, including hi-fi loudspeaker enclosures and do-it-yourself enclosure kits. Frank Stroemple, formerly with Radiart, joined Electro Voice as assistant manager of the Dis-



tributor Sales Division. Jim Johnson (left), former Electro-Voice sales engineer, was appointed assistant manager of Manufacturers Sales Division.



Douglas A. Batin joined Turner Co., Cedar Rapids, Iowa, as its assistant sales manager. He had formerly been in the Sales Department of the Collins Radio Co.



## TELCO SELF-SUPPORTING tripod MAST TOWERS

FOR FAST, EASY INSTALLATION

ALL ASSEMBLED—NO GUY WIRES

Real profits on any antenna installation—Bolt the tower to the roof and that's it! No bothersome, time consuming screw eyes, guy wires and rings or turn-buckles. Get sturdy, dependable, weatherproof installations. Telco Tripod Towers are a whole roof installation in one! All assembled—ready to install. Get them at your Telco distributor now.

AVAILABLE IN 3 MODELS FOR ANY SIZE INSTALLATION

- Model No. 9063  
2 foot heavy steel gauge, plated tower
- Model No. 9144  
3 foot electro-galvanized tubing tower
- Model No. 9145  
5 foot electro-galvanized tubing tower

REMEMBER


THE NAME



3 Ft. Model No. 9144

5 Ft. Model No. 9143

2 Ft. Model No. 9063

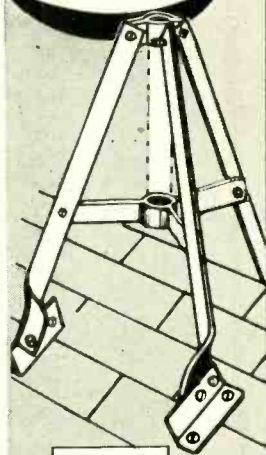

### TELEVISION HARDWARE MFG. CO.

Division of General Cement-Textron American, Inc.  
ROCKFORD, ILLINOIS

SEE YOUR TELCO DISTRIBUTOR NOW!

Stand-offs, mounts, arrestors . . . everything you need for every kind of TV installation . . . all at your Telco distributor.

FREE CATALOG  
Send a postcard for your big free Television Hardware catalog

Quality,  
Style and  
Beauty




### COMMUNICATIONS RECEIVER

- Six bands; .54 to 31 mc., AM, CW, MCW (FS with convert.)
- Accurate main tuning with full elect. bandspread
- Ferrite transformer, 75 ohm unbal. to bal. input
- One microvolt sensitivity on hf bands
- Image ratio; better than 60 db
- New Audio Selectivity design with variable bandwidth.
- 110 VAC 50/60 cy. appr. 90 Watts

Complete Receiver \$395 net  
Matching spkr \$16.00

WRITE FOR BULLETIN N-179

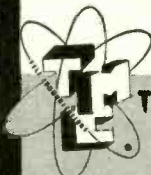

The TECHNICAL MATERIEL CORPORATION

IN CANADA: TMC Canada, LTD. OTTAWA, ONTARIO  
MAMARONECK, NEW YORK

LEARN

Television  
RADIO-COLOR-TV  
Electricity  
ELECTRONICS  
IN THE GREAT SHOPS OF COYNE

TRAIN QUICKLY! OLDEST, BEST EQUIPPED SCHOOL of ITS KIND in U.S.

Veterans and Non-Veterans—Get practical training in top opportunity fields. Prepare now for a better job and a real future. Advanced education or previous experience not needed. Employment service to graduates.

Enroll NOW—Pay Later

Finance Plan and Easy Payment Plan. Also Part Time Employment help for students. Training in Refrigeration and Electric Appliances can be included.

FREE BOOK Clip coupon for Big Free Illustrated Book. No obligation and No Salesman Will Call. Act NOW.

B. W. Cooke, President

COYNE ELECTRICAL SCHOOL

A TECHNICAL TRADE INSTITUTE OPERATED NOT FOR PROFIT Established 1899 500 S. Paulina, Chicago

B. W. COOKE, Pres.  
COYNE Electrical School  
500 S. Paulina St., Chicago 12, Ill. Dept. A6-81H

Send FREE BOOK and full details on:

- TELEVISION-RADIO
- ELECTRICITY-ELECTRONICS

NAME .....

ADDRESS .....

CITY ..... STATE .....



“... the hand of the princess in marriage, and half of all the JENSEN NEEDLES in my kingdom.”

**NOW!** INSTANT  
**SOLDER GUN**  
and COMPLETE  
“DO-IT-YOURSELF”  
KIT

FOR HUNDREDS OF RADIO, TV AND HOME-CRAFT JOBS

SOLDER GUN ONLY — MODEL G14 \$7.95  
BEST KIT VALUE! MODEL G14K \$8.95

- Includes:**
- ✓ 150-Watt Instant Solder Gun Model G14
  - ✓ Cutting Tip for plastic tile, old putty, toys, etc.
  - ✓ Smoothing Tip for furniture scratches, sealing, etc.
  - ✓ Famous Kester TV-Radio Resin Core Solder
  - ✓ Sandpaper for cleaning parts

“You’ll like the way it HANDLES!”

COMBINES ALL THE ADVANTAGES OF THE SOLDER GUN AND THE CONVENTIONAL SOLDERING IRON. No waiting — press trigger and solder at once. Ideal tool for shop or home use. Takes only half the space of transformer guns in tool boxes.

120 Volts AC-DC ¼" Tip (also available ⅜" Tip)

**COMPARE THESE FEATURES WITH ORDINARY SOLDER GUNS!**

POWER PACKED—150 Watts  
NO HEAVY TRANSFORMER —weighs only 8 oz.  
STURDY LIFETIME TIP —no soft fragile wire  
HEAT RIGHT IN TIP —new unique element design  
LONGER, THINNER REACH —EFFECTIVE SPOTLIGHT

**HEXACON ELECTRIC COMPANY**  
186 WEST CLAY AVENUE, ROSELLE PARK, NEW JERSEY

Serving Craftsmen for a Quarter-of-a Century

PEOPLE

(Continued)



Donald E. Smith (left), Midwestern district sales manager for CBS-Hytron, was promoted to Central district manager of CBS-Hytron Sales Corp. with headquarters in Chicago. Walter J. Fitzpatrick (right), Southern California district manager, was appointed West Coast regional manager, with headquarters in Los Angeles.

**Obituaries**

Dr. Eugene Casson Crittenden, internationally known scientist and expert on standards of physical measurement, in Washington, D. C., at the age of 75. Chief of the National Bureau of Standards' Electrical Division from 1921 to 1946, he retired as its associate director in 1950 and served as a consultant up to the time of his illness.

Lloyd L. Spencer, a retired vice president of Stromberg-Carlson Co. and associated with the phonograph and radio industries for over 30 years, recently at his home in Hudson, Ohio.

Rudolph F. Blash, founder and chairman of the board of Webster-Chicago Corp., Chicago, at the age of 70, in Fort Lauderdale, Fla.

**Personnel Notes**

... Emanuel Sacks, vice president of RCA and NBC and vice president and general manager of the RCA Victor Record Division, will now devote full time to NBC and RCA. Lawrence W. Kanaga, vice president and operations manager of the record division, succeeds Sacks as vice president and general manager.

... K. L. (Ken) Bishop joined the Electronics Division of Thompson Products, Cleveland, as president and general manager of Bell Sound Systems, Columbus, Ohio, a subsidiary. He had been general sales manager of V-M Corp. Other members of the Bell management team are W. H. Bunce, operations manager; H. H. (Pete) Seay, sales manager, and Floyd W. Bell, in charge of engineering.

... Paul V. Galvin, president of Motorola, will be awarded the 1956 Medal of Honor by RETMA during its Convention in Chicago June 12-14. END

**CORRECTION**

The text describes the Daystrom “Tiny Tim” miniature wirewound potentiometer (“What’s New?,” page 48, April, 1956) as a trimming capacitor. As readers have no doubt guessed, the unit is used as a trimming resistor—usually in connection with a fixed or semi-adjustable resistor.

We thank Mr. Philip Dempster of Sedona, Ariz., for this correction.

Hi-Fi record reproduction requires a **PRECISION** turntable...

THE NEW PRESTO

*Pirouette*  
T-18

MADE BY THE WORLD'S LARGEST MAKER OF PRECISION RECORDING EQUIPMENT

- Improves record performance tremendously...delivers professional broadcast quality!
- Simple operation—a sideways flick of the control lever selects 3 speeds—33⅓, 45, 78 rpm.
- Quiet insured! Precision deep-well turntable bearing.
- Quality plus! Extra heavy weight, cast aluminum 12-inch turntable covered with non-slip cork.
- Beautiful design—smart telephone black and brushed chrome finish.
- Easy to install...only rectangular cut-out needed. Easy to buy at only



**Revolutionary 3-Speed Mechanism**  
The Pirouette embodies the exclusive PRESTO “flick shift” speed mechanism, with 3 idler wheels mounted on a single movable plate. Insures professional speed accuracy and trouble-free performance.

**The New PRESTO K-11 Disc Recorder**

...A professional version of PRESTO's all-time favorite K-10 — incorporating the revolutionary T-18 turntable—for only \$396.00\*




For use as an on-location recorder. It's featherweight with a completely new pick-up arm, fully enclosed hi-fi speaker system, new panel design, push button controls and famous PRESTO cutting head. Three-speed operation.

Turntable mechanism including recording head and playback assembly available, separately, to fit into your sound system.

\*with hysteresis motor \$445.00

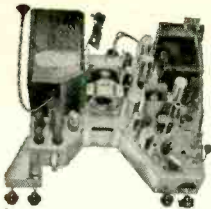Write for latest technical data  
**PRESTO RECORDING CORPORATION • PARAMUS, NEW JERSEY**  
Export Division: 25 Warren Street, New York 7, N.Y.  
Canadian Div.: Instantaneous Recording Service, 47 Lombard St., Toronto





*Build your own*  
**SUPER DE LUXE  
31-TUBE  
#630 TV CHASSIS**


**#630 SUPER DE LUXE 31-TUBE TV KIT**  
OPERATES 16" to 21" PICTURE TUBES. • Engineered in strict adherence to the genuine RCA #630 plus added features • FULL AMC BANDWIDTH • CASCODE TUNER • COSINE DEFLECTION YOKE • LARGE POWER TRANSFORMER • KEYED AGC • 12" SPEAKER • CONDENSERS and RESISTORS at rated capacities and tolerances. You receive a COMPLETE SET of PARTS and TUBES, everything needed is included (less CRT & wire). All I.F. Coils and Transformers are factory pre-aligned and tuned. You will enjoy building it with "LIFE-SIZE" easy to follow step-by-step ASSEMBLING INSTRUCTIONS" included with each KIT.

Slashed to **\$99.99**


Similar KIT for 24" or 27" CRT \$ **110.39** slashed to

**CUSTOM-BUILT CABINETS FROM FACTORY TO YOU**

MANHATTAN \$53.43 WESTCHESTER \$88.70

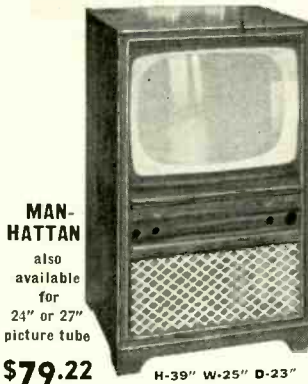

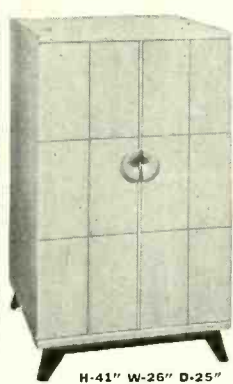MANHATTAN also available for 24" or 27" picture tube **\$79.22**



H-41" W-26" D-25"

**3 LEADING 1956 STYLES** in either Mahogany or walnut (blond 10% extra)  
• Ready drilled for any #630 TV chassis and cutout for any 16", 17", 19", 20" or 21" picture tube at no extra in price • Also supplied with undrilled knob panel for any other TV set • EVERYTHING NECESSARY for an easy perfect chassis and CRT assembly is included • Each cabinet is delivered complete as pictured with mask, safety glass, mounting brackets, backboard, backcup, hardware and assembling instructions • Each cabinet is shipped in an air cushioned carton from **FACTORY TO YOU!**

**GEM \$35.91**



**GEM** also available for 24" or 27" picture tube **\$59.54**

**DUMONT OR THOMAS PICTURE TUBES**

BRAND NEW in Factory Sealed Cartons — With a Full Year Guarantee

17" #17BP4A \$22.66 | 21" #21EP4B Aluminized \$32.21 | 24" #24CP4A Aluminized \$48.99 | 27" #27EP4A Aluminized \$74.31

**PM SPEAKERS (ALNICO #5)**

Brand New Factory Guaranteed Stock 1 oz. mag. on 3" to 6", heavier mag. on 8" & 12"

3" ..... \$ .98 | 6" ..... \$1.58  
4" ..... 1.17 | 8" ..... 2.64  
5" ..... 1.29 | 12" ..... 4.67

**SELENIUM RECTIFIERS**

65 ma. ... \$ .46 | 250 ma. ... \$1.08  
75 ma. ... .49 | 300 ma. ... 1.19  
100 ma. ... .62 | 350 ma. ... 1.26  
150 ma. ... .74 | 450 ma. ... 1.42

**TUBULAR CONDENSERS—85°C**

TOP QUALITY—Equally as Good for TV or Radio Work. Example of Value we offer .047—600v lists at 36c

.005—400v ..... 4c	.047—600v ..... 9c
.01—400v ..... 5c	.1—600v ..... 12c
.02—400v ..... 5c	.25—600v ..... 14c
.047—400v ..... 7c	.001—1000v ..... 11c
.1—400v ..... 9c	.01—1000v ..... 14c
.25—400v ..... 12c	.035—1000v ..... 16c
.005—600v ..... 7c	.05—1000v ..... 18c
.01—600v ..... 9c	.1—1000v ..... 22c
.02—600v ..... 8c	.5—400v ..... 28c
20 mfd—150v ..... 27c	8 mfd—150v ..... 26c
40/40 mfd—150v ..... 38c	40 mfd—450v ..... 49c
50/30 mfd—150v ..... 39c	80 mfd—450v ..... 56c

**CARBON RESISTORS**

Regular factory stock in. Stackpole, I.R.C. Speer. Order any ohmage from 2.2 ohms to 10 meg in the desired tolerance. Deduct 10% on lots of 100 or over.

1/2 WATT, 5%... .5c 10%... .4c 20%... .3c  
1 WATT, 5%... .6c 10%... .5c 20%... .4c  
2 WATT, 5%... .9c 10%... .7c 20%... .5c

**MICA & CERAMIC CONDENSERS**

Values up to 85c each  
5, 10, 51, 56, 82, 100, 120, 150, 220, 270, 330, 390, 470, 510, 680, 1000, 1200, 1500, 3900, 6800 MMF ..... Your choice **5c** each

**PULSE KEYED AGC KIT**

Finest, most accurate and the easiest Kit to install in any make TV RECEIVER including the No. 630. Improves performance and insures a steady picture on all channels.

COMPLETE SET OF PARTS **\$2.99** Including 6AU6 tube & Instructions

**#630 SUPER DE LUXE TV CHASSIS**

LICENSED UNDER RCA PATENTS  
COMPLETE READY TO PLUG IN AND PLAY  
Similar in features to the 16" to 21" TV KIT above.  
Slashed to **\$142.27** (less CRT)

**#630 B Y TECHMASTER**

COMPLETE LINE AT SPECIAL PRICES  
Catalog mailed on request

**STANDARD CASCODE TUNER**

For better all around performance  
Complete with tubes and Brooks CASCODE MANUAL with step-by-step instructions and all extra parts needed. **\$15.97**

**FLYBACK TRANSFORMER**

Latest single 1B3 type, for the 21" and all 70° Picture Tubes. It is similar to the popular No. X-093 and goes up as high as 16KV. With it you receive easy-to-follow instructions and schematic diagrams that apply to build, convert or improve practically all makes of TV Receivers. **\$4.86**

**COSINE DEFLECTION YOKE**

The latest achievement in the 70° type, with complete wired network. Will add new life to any TV Set, in brilliance, clarity and sweep. This is the same type we supply with our Kits, with it you receive easy-to-follow instructions and diagrams. **\$4.92**


**18KV FLYBACK TRANSF.**

This new Flyback Transformer now makes 90° conversions easy on any make TV Set. Customers report excellence on 24" and 27" TV sets built or converted with this Transformer. Instructions and schematic diagrams included. **\$5.24**

**COSINE DEFLECTION YOKE**

NEW 90° TYPE with complete wired network. It solves all problems formerly sought for, in 90° Yokes, for undistorted clear pictures and ease of overall sweep. Instructions and schematic diagrams included for building, replacing and converting. **\$5.98**

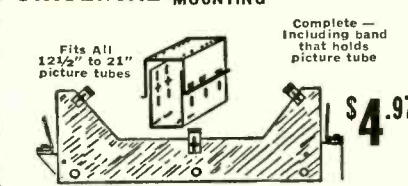**UNIVERSAL Picture Tube MOUNTING BRACKETS**



**GEM TV CABINET FRONT**

Similar to front of GEM TV Cabinet (above) and complete with mask, safety glass and undrilled knob panel for any TV fit. Beautifully finished in mahogany or blond.

Save money by building a TV Cabinet with it, simply by adding sides, top and bottom. Use it for mounting Receiver flush with wall.

Mahogany ... **\$19.44** Blond ... **\$21.38**

**21" TV CONVERSION KIT**

NOW ... Anyone with even a limited knowledge of TV—can Convert any Size, any Make TV RECEIVER to operate 21" or any 70° Picture Tube.

COMPLETE SET OF ESSENTIAL PARTS includes matched set of Todd 70° COSINE DEFLECTION YOKE and TODD HV FLYBACK TRANSFORMER, FOCALIZER, 20KV FILTER, DRIVE TRIMMER, LINEARITY COIL, CONDENSERS, RESISTORS.

Your price... **\$13.97** List Price \$33.50  
Incl. CONVERSION MANUAL with Step-by-Step Instructions & Diagrams.

Similar Kit for 24", 27" or any 90° CRT **\$15.98**

**27" TV CONVERSION KIT**

Convert any Size any Make TV RECEIVER to operate the 27", 24" or any 90° Picture Tube.

COMPLETE SET OF ESSENTIAL PARTS includes matched set of Todd 90° COSINE DEFLECTION YOKE and TODD 18KV FLYBACK TRANSFORMER, 30KV FILTER, 6AX4 TUBE, YOKE BRACKETS, WIDTH CONTROL, CONDENSERS, RESISTORS.

Your Price... **\$15.98** List Price \$39.75  
Incl. CONVERSION MANUAL with Step-by-Step Instructions & Diagrams.

Illustrations for mounting TV Sets flush with wall extending into garage, closet or wall recess included.

**Why Gamble With Picture Tubes**

Write us which type you need and let us show you that Brand New factory sealed

**DUMONT PICTURE TUBES**

are your best bet, yet inexpensive.

**SPECIAL TV PUBLICATIONS**

- Brooks LIFE-SIZE TV INSTRUCTIONS for building any #630 TV Receiver from the original 10" to the latest 27" **\$1.25** postpaid
- 90° TV CONVERSION MANUAL, how to convert any TV SET to 24", 27", etc. **50c** postpaid
- 70° TV CONVERSION MANUAL, how to convert any TV SET to 17", 21", etc. **50c** postpaid
- HINTS FOR BETTER PERFORMANCE on your #630 TV receiver. **50c** postpaid
- Brooks CASCODE MANUAL, how to install Cascode Tuner in any make TV set. **25c** postpaid
- A.G.C. STEP-BY-STEP INSTRUCTIONS, how to add A.G.C. to any make TV Receiver. **25c** postpaid

**FREE CATALOG** mailed on request

**BROOKS RADIO & TV CORP., 84 Vesey St., Dept. A, New York 7, N.Y.** TELEPHONE: Cortland 7-2359



# PRE-VACATION BARGAINS!

Get Ready for Summer Fun!  
DUAL-POWERED RADIO KIT



**\$7.88**  
COMPLETE

Phones for sun radio kit **\$1.95**

Ultra-modern, dual-powered transistor radio kit using famous sun battery for daylight operation and 1 1/2 V penlite for night. Stations loud and clear. Includes loopstick, diode det., transistor amp., variable cond., sun battery, 1 1/2 V cell, switch, cabinet, simple instructions.

## FAMOUS "KIT KING" KITS

- 12 AC-DC LINE CORDS.** for all electrical equipment. Molded plugs. Stock up now! Wt. 1 lb. **\$1**  
Reg. \$3
- 7 ROLLS OF WIRE.** Seven 25-ft. rolls. #18 to #24. Ass'd. stranding. Insulation, colors. Wt. 1/2 lb. Reg. \$4 **\$1**
- 8 TUBULAR ELECTROLYTICS.** Assortment of popular values: 5 to 100 mf., up to 450 volts. **\$1**  
Reg. \$9
- 20 INSTRUMENT KNOBS.** Knurled, skirting, precision instrument and equipment types. 10 styles, brass insert w/set screws. Reg. \$9 **\$1**
- 20 PRECISION RESISTORS.** Carbo-film, Ass'd. standard values, 1 watt 10%. Pre-cut leads. Wt. 1/2 lb. Reg. \$17 **\$1**
- 10 PANEL SWITCHES.** Micro, car, momentary, bush and rotary. Wide variety. Wt. 1 lb. Reg. \$12 **\$1**
- 60 TERMINAL STRIPS.** Ass'd. solder terminal strips and clips, 1 to 7 lugs. Wt. 1/2 lb. **\$1**  
Reg. \$4
- 2000 PCS. HARDWARE.** Woodwork, radio-TV, shop screws, springs, grommets, etc. Hundreds of items. Wt. 2 1/2 lbs. Reg. \$13 **\$1**
- DIODE KIT #1.** Four of the most used types: 1N21, 1N22, 1N23, 1N34. Shop. lab. must! **\$1**  
Reg. \$11
- DIODE KIT #2.** Three batt. 1N34, 1N48, 1N51. Reg. \$4.16 **\$1**
- 60 TUBULAR CONDENSERS.** ERS. 25 values. .00035 to 1 mf., up to 6000 v. oil. too! Wt. 2 lbs. **\$1**  
Reg. \$10
- 50 RF COILS & CHOKES.** 20 types RF coils, chokes & slug-tuned coils for radio. TV. lab. Wt. 1 lb. Reg. \$15 **\$1**
- 30 DISC CONDENSERS.** ceramic. 4.7 mmf. to .01 mf. up to 1000 V. Assorted values, duals. 1/2 too! Reg. \$12 **\$1**
- 20 WIREWOUND RESISTORS.** 20 values. 5 ohms to 12,000; 5 to 50 watts. Candohm & tubular types. Wt. 2 lbs. **\$1**
- 50 CERAMIC CONDENSERS.** ERS. Tubular, disc, button, standoff types. 5 mmf. to .01 mf. up to 1000 V. Wt. 1/2 lb. **\$1**  
Reg. \$14
- 25 TUBE SOCKETS.** Subminiatures, 7-9 Pin. 4 to 8-pins. Mica filled and ceramic. Some shield base. Wt. 1 lb. **\$1**  
Reg. \$9
- 60 CARBON RESISTORS.** Insulated. 35 values! 15 ohms to 10 megs. 1/2, 1 & Wt. 1/2 lb. Reg. \$18. **\$1**
- 10 ELECTROLYTICS.** EP twist-lock & tubular types. Ass'd. values up to 450 V. Wt. 2 lbs. **\$1**  
Reg. \$6.50
- 60 MICA CONDENSERS.** Postage stamp types. 25 values! .00001 to .01 mf. to 1200 WDC. Silver. 5% too! Wt. 1/2 lb. **\$1**  
Reg. \$21
- 150 RADIO PARTS.** Larke ass't. wire, mold-ed, paper, disc, ceramic, mica, resistors. Pre-cut leads. Wt. 3 lbs. **\$1**  
Reg. \$17
- PRE-AMP KIT.** Chassis condensers, resistors, wire, socket, schematic & ferrite equalizer (less 6SC7 tube) Wt. **\$1**  
1 lb. Reg. \$4.50
- 12 VOLUME CONTROLS.** Handy shop assortment of radio TV. lab. units. W.V. too! Wt. 1 lb. **\$1**  
Reg. \$9
- 15 ASSORTED KNOBS.** radio & TV types: push-on & set screw. Some worth 35¢ ea. Wt. **\$1**  
1 lb. Reg. \$9
- 30 ASSORTED BULBS.** Special! Wide variety of standard, miniature, screw & bayonet types. 1 thru 6 volts. **\$1**  
\$4 value
- 15 ERIE TRIMMERS.** TS2A ceramic type. 10 different values; sinless & duals. Wt. 1/2 lb. **\$1**  
Reg. \$14
- 8-PC. NUTDRIVER KIT.** Plastic handle; 3/16, 7/32, 1/4, 5/16, 11/32, 3/8, 7/16" steel socket wrenches in plastic case. Wt. 1/2 lb. **\$1**  
\$3.50 value
- PRINTED CIRCUITS KIT.** Ass'd. printed circuit boards with 1% precision A-B resistors, Transistor diodes and H-sealed oils. Wt. 1/2 lb. **\$1**  
Reg. \$15

## NEW & UNUSED JAN & COMMERCIAL TUBES 6 for \$1

TOP MAKERS! FULLY GUARANTEED! NO REJECTS!

- 2C26  39/44  34  46
- 7E5  956  35/51  9006
- 33

Simply enter number of tubes wanted beside tube number.

### OTHER HOT BUYS!

- ELECTRIC FAN SCOOP!** Get ready for summer heat! 115 VAC motor. 3000 RPM. 1/250 HP. **\$2.19**  
Fan blade, AC cord included. Reg. \$9
- 10 ELMENCO TRIMMERS.** 3-30 mmf., Panel mfg. 1" shaft. Reg. **\$5.** only \$ **\$1.**
- NAVY J-38 HAND KEY.** Ensign's! Genuine USN J-38 key w/solid bakelite base. Reg. \$3 only **\$1.**
- 3 MICROSWITCHES** w/sensitive spring leaf. Normally closed. 115V 15A. Reg. \$4.50 only **\$1.**
- 22M SUN BATTERY.** Direct sunlight generator. 0.5V @ .25ma. W/bracket. **\$1.50**

ANY \$1 ITEM FREE WITH EACH \$10 ORDER!  
**FREE! GIANT BARGAIN FLYER!**

HOW TO ORDER: Check items wanted. Return entire ad with check or M.O. Include sufficient postage, excess returns. C.O.D. orders 25% down. Rated, net 30 days. RE-6


Name .....  
Street .....  
City ..... Zone ..... State .....

Enclosed \$..... for items; \$..... for postage.

**Lektron Specialties**

28 Gardener Street Chelsea 50, Mass.  
Visit our Salesroom at 131 Everett Ave., Chelsea

## technical Literature

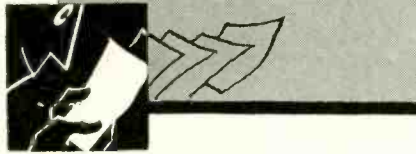

### BROCHURE ON MANUAL

A 4-page circular describes the newly published 1956 *Television Manual*, Vol. TV-11 of the TV series.

Supreme Publications, 1760 Balsam Rd., Highland Park, Ill.

Any or all of these catalogs, bulletins or periodicals are available to you on request direct to the manufacturers, whose addresses are listed at the end of each item. Use your letterhead—do not use postcards. To facilitate identification, mention the issue and page of RADIO-ELECTRONICS on which the item appears. UNLESS OTHERWISE STATED, ALL ITEMS ARE GRATIS. ALL LITERATURE OFFERS ARE VOID AFTER SIX MONTHS.

### TRANSFORMER LAMINATIONS

Detailed information and drawings on 100 standard lamination shapes are given in the seventh edition of *Transformer Laminations* in a revised and expanded edition of 120 pages. Such items as direction of grain, count and weight of laminations, magnetic and mechanical dimensions, lamination die layout as well as other important data are included in the book.

Sales Dept., Allegheny Ludlum Steel Corp., 2020 Oliver Bldg., Pittsburgh 22, Pa.

### REPLACEMENT GUIDE

An automobile radio replacement guide AR-56 lists recommended Triad replacement transformers for nearly 500 models of automobile radios including several 12-volt models.

Triad Transformer Corp., 4055 Redwood Ave., Venice, Calif.

### TIPS FOR SERVICE TECHNICIANS

A new publication *Tips* which is published "occasionally" contains articles of interest to the radio and TV service technician. International Rectifier Corp. offers a \$25 defense bond to anyone submitting an article that is subsequently published in it.

International Rectifier Corp., 1521 E. Grand Ave., El Segundo, Calif.

### SPEAKER LITERATURE

The *Progressive Speaker Expansion Guide* contains detailed information for step-by-step expansion of speaker systems illustrated with simple color-coded charts. It includes data on the use of adjustable networks, dual-impedance woofers, adjustable-response woofers, mid-range speakers and tweeters. The complete line of University speaker and network components is illustrated with all important specifications included.

Brochure 78A1 describes the Decor-

Improves  
phono  
quality...

## Ronette

new replacement  
cartridges


A new Ronette Fonofluid cartridge to enhance the sound of your present record player—regardless of make or model.

The Ronette high compliance, low intermodulation distortion and full frequency response assures peak performance from your equipment. Yet the cost is unbelievably low.

Acclaimed by critics and used by leading original equipment manufacturers, Ronette new replacement cartridges are available in high or low output, turnover or single needle models, and in a new universal mounting bracket that will fit your tone arm.

Replace your present cartridge with a RONETTE and you will immediately hear the difference that has made quality manufacturers switch to—better sounding RONETTE.

AT YOUR PARTS DISTRIBUTOR

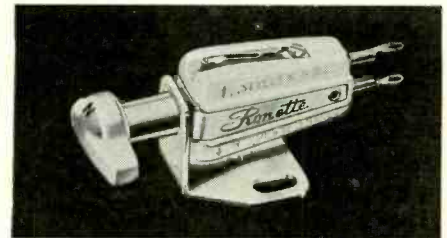

Diamond styli available at extra cost.

Hear all the music you are paying for... use a Ronette.





# STAN-BURN E-D-A-R-K-E

## CATHODE RAY TUBE SPECIALS ONE YEAR GUARANTEE

G.E. Type	STAN-BURN	G.E. Type	STAN-BURN
\$13.25...10BP4	\$10.20	\$31.25...17GP4	\$20.75
18.00...10FP4	14.00	32.25...19AP4A	22.50
16.25...12LP4A	13.95	27.40...20CP4	18.95
12QP4	10.50	33.00...21AP4	22.25
28.95...12UP4	14.50	27.40...21EP4	20.15
18.15...14CP4	13.40	33.25...21MP4	23.50
15DP4	14.50	90.75...24AP4	49.00
31.25...16AP4A	18.50	<b>DUMONT TUBES</b>	
26.25...16KP4	15.75	12QP4A	\$23.75
31.25...16GP4	18.50	15DP4	26.55
29.00...16LP4	15.05	18AP4A	31.00
29.00...16WP4	15.25	16FP4	26.00
22.50...17BP4	15.75	17KP4	25.00
28.15...17CP4	19.50	19AP4A/B	33.25
		21KP4	38.50

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

520 WORTH OF ELECTRONIC PARTS IN GRAB-BAG consisting of: porcelain sockets, coils, speaker, transformers, resistors, condensers, etc. ONLY \$1.98 (plus 50c postage)

**TAPE RECORDERS—Famous Brand**  
List Pr. \$249.95 \$169.00 List Pr. \$129.95 \$79.95  
Last Pr. 199.95 129.00 List Pr. 79.95 59.95  
Write for complete illustrated details.

**WINDOW FANS**  
VORNADO—18" Blade—Reversible—List \$89.95.....  
SPECIAL \$47.95 net  
FRIGID—20" Blade—6 speed—Reversible with Thermostat control—List \$89.95.....SPECIAL \$47.95 net  
WESTINGHOUSE in stock. Write for full details and prices.

**AIR CONDITIONERS—Famous Brand**  
3/4 TON 110V.....\$199.95  
G.E. Fedders, Mitchell, Westinghouse in stock.  
Write for full details and prices.

**KITS:** We stock the following manufacturers complete line of kits—see reference pages.  
EICO—see page 27-28. ARCAV—see page 118  
QUALITY—see page 117. PRECISE—see page 95  
All domestic orders will be shipped prepaid for a limited time. Send us your list. Order by Manufacturer and Model Number of item.

**AM-FM-SW AUTO RADIO**  
Drift Free FM—World's Finest—Becker-LoMans For PUSH BUTTON—\$179.95. For SIGNAL SEEKER—\$239.95 includes: GE SPEAKER with GILLE and AUTOMATIC ELECTRIC ANTENNA. Simple installation for all cars. Specify 8 or 12 Volt system.

VM 3 SPEED HI-FI CHANGER—Model 950 with Ronette Sonotone or Astatic flip-over cartridge—\$21.49  
NEW ORIGINAL CARTONS.....\$21.49  
VM 4 SPEED HI-FI CHANGER—Model 1210 with Ronette, Sonotone or Astatic flip-over cartridge—\$22.95

WEBSTER Model 140—3-SPEED Automatic with Ronette Sonotone or Astatic flip-over cartridge—\$22.49  
MONARCH 3 SPEED AUTO. INTERMIX CHANGER with crystal cartridge.....\$21.95  
Same with British reliable rubber roller.....24.95  
45 RPM SPINDLE.....1.88  
TU-8 MONARCH 3 Speed MOTOR & TURNTABLE UNIT (less arm).....5 4.95

3 SPEED PORTABLE RECORD PLAYER with MONARCH CHANGER—Ronette cartridge—Portable Two Tone Carrying Case.....\$32.95  
FEELERLESS PORTABLE BATTERY OPERATED RADIO—Colors: Green, White, Red or Blue—5 TUBE IMPORT.....\$14.95 less batteries  
BATTERY KIT for above.....\$ 2.00

JEWEL—Model 5200—5 TUBE \$12.50  
AC DC RADIO.....  
RECORDING TAPE—Top quality 1200 Feet Famous brand BOXED—1 to 5—\$1.69 ea. 6 to 11 \$1.59 ea. 12 or more \$1.49 ea.

**HALLICRAFTERS TV**  
17" Portable TV Dealers net \$103.95  
Model 17T5700M—Table Model—Dealers net.....\$91.95  
Model 21TS460M—Table Model—Dealers net.....\$129.46

**HI-FI PACKAGE DEAL**  
Includes: JENSEN K210 SPEAKER, MONARCH AUTOMATIC CHANGER with GE RPK-050, 12" SPEAKER ENCLOSURE in BLOOD or MAHOGANY WOOD (Specify color) MATCHING BASE FOR CHANGER, 10 WATT HF 10 BOGEN AMPLIFIER. Complete, ready to play. A \$99.50 net  
\$135.00 Value for Only  
or Your choice of similar units at relative Package price. Write for Prices.

**DEALERS:** Write for low cost prices and catalogs on 56 models—HALLICRAFTERS, CRESCENT, FANON, SONORA, WILSON, MASTER, WESTINGHOUSE, TUNG-SOL, DeWALD, MAJESTIC, GRUNDIG, ARKAY KITS, DELCO, GEN. MOTORS. Address all inquiries to Dept. RE-6.

**COMPLETE HIGH FIDELITY DEPARTMENT. SEND US YOUR LIST FOR LOWEST QUOTATIONS ON ANY ITEM.**  
We invite export inquiries and offers. Our export department will give special attention to expediting foreign orders at minimum commissions. We are authorized distributors for United Motors, all Delco and Gen. Motors Auto Radio parts in stock.  
We also carry a complete line of popular makes of Radio Tubes at 50/10 discount. Also many other special purpose and transmitting types, and all electronic parts and equipment at lowest prices. Send us a list of your requirements for prompt quotations. Terms: 20% with order. Balance C.O.D. All prices F.O.B., NEW YORK Warehouse. Minimum order \$5.00. Write for our latest price list and Hi-Fi Catalog RE-6.

**STAN-BURN RADIO and ELECTRONICS CO.**  
558 CONEY ISLAND AVE. • B'KLYN 18, N. Y.

## TECHNICAL LITERATURE (Continued)

Acoustic three-way speaker systems, including the new Master, Senior and Tiny-Mite cornerless-corner setups, and a feature story of the acoustic Baton. The deluxe Dean and Classic systems are also described.

University Loudspeakers Inc., 80 So. Kensico Ave., White Plains, N. Y.

### SELECTION CHART

A quick-selection chart ETD-1163-A lists G-E's 600-milliamperere series-string receiving type tubes—all of controlled heater warmup design. It classifies the 48 tube types according to elements; lists typical service, heater voltages, maximum plate and screen dissipation ratings; gives average characteristics.

General Electric Tube Dept., Schenectady, N. Y.

### SPEAKER

The Tempo series of high-fidelity speakers is described in a four-page catalog. Among the speakers are the model F8J408, an 8-inch, single-cone unit; model F12J408, a 12-inch full-range single-cone speaker, and the 12-inch single-cone model F12L608.

Oxford Electric Corp., 556 W. Monroe St., Chicago 6, Ill.

### TAPE RECORDERS

A 4-page folder describes the VU Magnemite series of tape recorders. A variety of single-, two-, three- and four-speed models are listed and their respective recording characteristics are tabulated. A full description of the various mechanical and electrical components is given, with individual illustrations. The recorders' operations are explained clearly and concisely. Complete technical specifications and recommended accessories as well as direct factory prices are included.

Amplifier Corp. of America, 398 Broadway, New York 13, N. Y. END

## Thirty-Five Years Ago In Gernsback Publications

### HUGO GERNSBACK, Founder

Modern Electric	1908
Wireless Association of America	1908
Electrical Experimenter	1913
Radio News	1919
Science & Invention	1920
Television	1927
Radio-Craft	1929
Short-Wave Craft	1930
Television News	1931

Some larger libraries still have copies of ELECTRICAL EXPERIMENTER on file for interested readers.

### In June 1922 Science and Invention (formerly Electrical Experimenter)

The Odor Organ, by Joseph H. Kraus.  
The Radio Science, by H. Gernsback.  
Secret Phone Aids Public Speakers.  
Building a Color Organ, by Manuel Comulada.  
Church Broadcasts Own Sermons, by Archie Richardson.  
Vacation-Time Radio Receiver, by Robert E. Lacault.  
Radio for the Beginner, No. 4, by Armstrong Perry.  
Radio-Frequency Amplification, by Arthur H. Lynch.  
The Radio Oracle.

# Futuramic VOM PROBES



now endorsed by

R. G. Middleton


Type 261 V-O-M High-Ohms Probe. Lets you read resistance much higher than ever before. Find those leakage troubles quickly and easily... with your V-O-M.....Net \$9.95

Type 262 V-O-M Signal Tracer Probe. Now you can read signal voltages with your favorite equipment... your V-O-M. Solve tough sweep circuit problems with speed and ease. Trace signals through I.F. and video, check oscillators... all without removing the chassis from the cabinet.....Net \$9.95

Type 263 Polarity Reversing Probe. No more lead changing, just a flick of the finger and the meter reads the right direction.....Net \$6.95

Type 264 V-O-M Range Splitter Probe. How many times have you wished your V-O-M had a range between 250 and 1000 volts? Now it can be yours, and at the flip of a switch.....Net \$9.95

How's YOUR batting average?

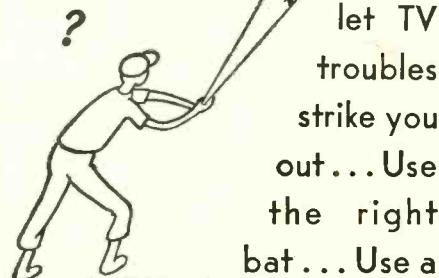

Don't let TV troubles strike you out... Use the right bat... Use a

## Futuramic

All Futuramic products are completely guaranteed. You must be satisfied, or you may return the probe and we will refund your money. Stocked by leading jobbers. Send for literature.


## Futuramic

2500 West 23rd Street  
Chicago 8, Illinois

Representative Inquiries Invited



don't do it  
the hard way!

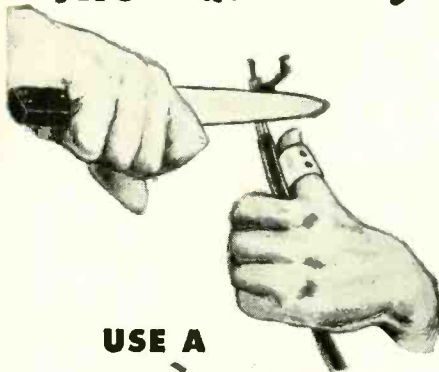

### ROTARY CABLE STRIPPER Model S-1



*As Easy  
as Sharpening  
a Pencil*

**FAST  
ACCURATE • CLEAN**

and Practically **AUTOMATIC**

- Cuts and strips the outer covering of coax cable without injuring the shielding.
- Cuts the shielding without pulling, fraying or unbraiding.
- Cuts and strips the inner insulation and...
- Measures just the right length of lead desired.
- Ideal for stripping all insulated wire and cable — as well as non-metallic tubing.

— and its **ONLY \$375**  
LIST


**A Must For Your Kit —  
Get One Today  
at your Parts Distributor.**

**BLONDER-TONGUE LABORATORIES, INC.**  
Dept. JF-3, Westfield, New Jersey



Manufacturers of TV Cameras,  
TV Amplifiers, Boosters,  
UHF Converters, TV Accessories  
and Originators of the Masterline  
and 'Add-A-Unit'  
Master TV Systems.

## Books

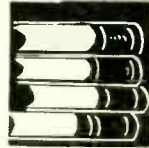

**TELEVISION FOR RADIOMEN** (revised), by Edward M. Noll. MacMillan Co., New York, N. Y. 6 x 9 inches, 662 pages (black and white) and 116 pages (color). \$10.

This new edition adds material on transistors, uhf and color. It presumes that the reader understands radio and wishes to learn TV.

The major portion of the book (16 chapters) is devoted to black-and-white TV. There are four chapters on color. The author gives clear and complete discussions on the functions of parts and circuits and his topics are well-planned. Many illustrations show typical circuits and block diagrams.

Installation, adjustment and troubleshooting receive two full chapters. They are all fully detailed with step-by-step procedures for the technician. There is also a step-by-step list for the viewer to guide him in turning on the set and adjusting for the best picture. Sweep oscillators, oscilloscopes and generators are also discussed.

One chapter shows the reader how to apply math in his work. The uhf chapter is comprehensive and includes basic information on antennas, tuners and test procedures.

The section on color provides a good groundwork of information on tubes and the NTSC system.

**ELECTRONICS: THE SCIENCE OF ELECTRONS IN ACTION**, by A. W. Keen. Philosophical Library, Inc., 15 E. 40th St., New York 16, N. Y. 5½ x 8¼ inches, 256 pages. \$4.75.

In their frenzied race toward extending electronics into new and hitherto improbable uses, a few engineers do worry about the increasing complexity of their work and its relationship to the lay public (for whom, after all, the research and work are being done).

There is no question that the fruits of electronics research are accepted. But this is not enough. What the author wants is acceptance with understanding. And so we have a book that describes how this new technology came into being and how it brings us many strange, wonderful and awe-inspiring new devices. Yet there is something missing. The developments are marvelous—the writing less so. The background history of electronics is made into a factual recital when it should be a mad rush of excited reporting. The author cannot leave his engineering training for any length of time so he brings his circuits, his waveforms and graphs along for a reader-

## Completely New! DYNAKIT MARK II



An amplifier kit which provides the finest sound at low cost. The listening quality of the Dynakit is unequalled by any amplifier, regardless of price; and this kit can be readily assembled in about three hours.

The Dynakit uses a new bug-free circuit, designed by David Hafler. Complete reproducibility of operating characteristics is guaranteed by the use of a factory-wired printed circuit board. The Dynakit comes complete with all components including the super-fidelity Dynaco A-430 transformer.

#### Specifications:

Power Output: 50 watts continuous rating, 100 watts peak. Distortion: under 1% at 50 watts, less than 1% harmonic distortion at any frequency 20 cps to 20 kc within 1 db of maximum. Response: Plus or minus .5 db 6 cps to 60 kc. Plus or minus .1 db 20 cps to 20 kc. Square Wave Response: Essentially undistorted 20 cps to 20 kc. Sensitivity: .5 volts in for 50 watts out. Damping Factor: 15. Output Impedances: 8 and 16ohms. Tubes: 6CA7/EL-34 (2) (6550's can also be used) 6AN8, 5U4GB. Size: 9" x 9" 6½" high.

**69.75**  
net

## Dynaco Output Transformers



Featuring para-coupled windings, a new design principle (patents pending). These transformers use advanced pulse techniques to insure superior square wave performance and undistorted reproduction of transients. Dynaco transformers handle full rated power over the entire audio spectrum from 20 cps to 20 kc, without sharp rise in distortion at the ends of the band which characterizes most transformers. Conservatively rated and guaranteed to handle double nominal power from 30 cps to 15 kc without loss of performance capabilities.

#### Specifications:

Response: Plus or minus 1 db 6 cps to 60 kc. Power Curve: Within 1 db 20 cps to 20 kc. Square Wave Response: No ringing or distortion from 20 cps to 20 kc. Permissible Feedback: 30 db.

#### MODELS

A-410	10 watts	6V6, EL-84	14.95
A-420	25 watts	KT-66, 5881, EL-34	19.95
A-430	50 watts	6550, EL-34 (6CA7)	29.95
A-440	100 watts	6550	39.95

(all with tapped primaries except A-440 which has tertiary for screen or cathode feedback)

Additional data on Dynakit and Dynaco components available on request including circuit data for modernization of Williamson-type amplifiers to 50 watts of output and other applications of Dynaco transformers.

**DYNA COMPANY**

5142 Master St.  
Phila. 31, Pa.

RADIO-ELECTRONICS



ship that will regard them as electronic abracadabra.

The author has written an excellent survey book on electronics—one that would be suitable for a freshman class in engineering. But the general public will have to wait. The Paul de Kruif of electronics has not yet appeared.—MC

**BASIC AUDIO COURSE**, by Donald Carl Hoeffler. Gernsback Library, Inc., 25 W. Broadway, New York, N. Y. (Book No. 66). 5½ x 8½ inches, 223 pages. \$2.75.

This is a complete and clear audio course on circuits, components and design procedure. Nonmathematical, it will be found useful by technicians and hi-fi fans.

The book discusses sound itself, amplifiers and power supplies, distortion, attenuators and filters, speakers and microphones and sound recording. The author shows how to work with logarithms and db, how to design amplifiers and how to understand and avoid distortion. The important subject of filters is covered in a large chapter. Another chapter gives adequate coverage to speaker enclosures and how to construct them. Placement and use of mikes and speakers are described. Recording information is given on tracking error, how to interpret the light patterns and faults revealed through a microscope. Tape head alignment and bias adjustment are also discussed.

Many useful charts, diagrams and tables are included. The chapter on pads and filters is especially rich in such data.

This is a happy combination—the author knows his subject very well and is adept at passing his knowledge along to the reader.—IQ

**HI-FI SPEAKERS AND ENCLOSURES**, by Abraham B. Cohen. John F. Rider Publisher, Inc., 480 Canal Street, New York 13, N. Y. 5½ x 8¾, 368 pages. \$4.60.

This comprehensive work will round out the library of any hi-fi fan for it deals with the least understood of all audio subjects. The author, who is engineering manager for University Loudspeakers, Inc., uses no "engineers' talk" in his book. The language is clear and the diagrams are many. The only mathematics are detailed dimensions for enclosure design, numerical data for crossover networks, correct horn lengths, etc.

The book has three parts: speakers, enclosures and the room. The first covers in much detail the construction and characteristics of dynamic, electrostatic, crystal and ionic speakers. The next part shows the effect of baffles, horns, speaker resonance, etc. and how to determine their optimum value. The last shows how the room plays a definite and important part in hi fi. Speaker placement, reverberation and correct volume level are among the topics.


The appendix includes 20 pages of

from the VOICE OF AUTHORITY IN SWEEPS...

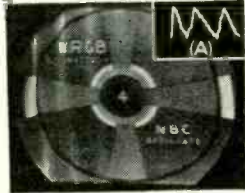
# SPOT and FIX TV FAULTS FAST!

FREE RAM BOOK SHOWS HOW!

Typical latest field-proven servicing data you'll find in your RAM book:



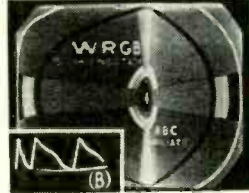**FAULT:** "Ringing."  
**CAUSE:** Incorrect value of balancing R-C network across one-half of H. Yoke winding.  
**(A):** H. Yoke current wave-form. Obtained by connecting scope across 10-ohm resistor inserted in series.



**FAULT:** Picture compression and stretching.  
**CAUSE:** Capacitance value of boost capacitor (connected to linearity coil) too low.  
**(B):** H. Yoke current wave-form. Leaky boost capacitor could cause similar effect.



**FAULT:** Picture stretching at left and compression at right.  
**CAUSE:** 0.02 mf boost capacitor (connected to linearity coil) used instead of 0.1 mf capacitor.  
**(D):** H. Yoke current wave-form.

For over 10 years, RAM has specialized and pioneered in sweeps exclusively. RAM designs them, makes them, counsels TV set manufacturers on them, field-services them, educates Servicemen on them — leads the industry.

No one but RAM can bring you such proven data — as shown here and in the RAM Manual. In manufacturing know-how and field experience, you can depend on RAM for . . .

**THE VOICE OF AUTHORITY IN SWEEPS**

Send coupon today — get the BEST information from the FOREMOST manufacturer now!



**RAM ELECTRONICS SALES CO.** · Irvington, N. Y.

Canadian Sales Division: Telequipment Mfg. Co., Ltd., Ontario  
Export Dept: Dage Corp., 219 E. 44 St., New York, N. Y.

## Fen-tone

### "INDUCT-O-PHONE"

The latest electronic marvel

No wires, works on fully magnetic induction. Ideal for hospitals, large assemblies, museums, beauty salons and a thousand and one other uses, or simply for fun at parties. Installed in many hospitals — and even in the British Parliament and House of Commons.....List \$15.65



**FREE!** 1956 Fen-tone Catalog. See the many terrific values in the new 1956 Fen-tone Hi-Fi catalog including mikes, tape decks, cartridges, record changers, silent listening devices, etc.

## FENTON COMPANY

15 Moore Street, New York 4, N. Y.

Sold through better Audio Distributors. See yours today!

West of Rockies, prices slightly higher.



**COYNE**  
TRAINS YOU  
IN SPARE TIME  
AT HOME

**COYNE QUALITY TRAINING AT LOWEST COST**

# TELEVISION

## RADIO-COLOR TV

Only from famous COYNE do you get this modern up-to-the minute TV Home Training. Easy to follow instructions—fully illustrated with 2150 photos and diagrams. Not an old Radio Course with Television tacked on. Includes UHF and COLOR TV. Personal guidance by Coyne Staff. *Practical Job Guides* to help you **EARN MONEY QUICKLY IN A TV-RADIO SALES AND SERVICE BUSINESS—part time or full time. COSTS MUCH LESS—pay only for training—no costly "put together kits."**

**SEND COUPON FOR FREE BOOK**

SEND COUPON BELOW for Free Book and full details including EASY PAYMENT PLAN. NO COST OR OBLIGATION—NO SALESMAN WILL CALL.



B. W. COOKE, Pres. **COYNE** FOUNDED 1899  
**ELECTRICAL SCHOOL**


A TECHNICAL TRADE INSTITUTE OPERATED NOT FOR PROFIT  
500 S. Paulina Dept. A6-HT4 Chicago 12, Illinois

**COYNE ELECTRICAL SCHOOL**  
Television Home Training Div.  
500 S. Paulina St., Chicago 12, Ill., Dept. A6-HT4

Send FREE BOOK and details of your Television Home Training offer.

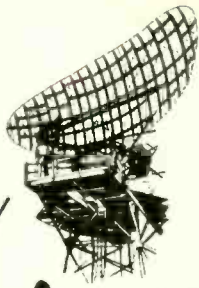Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_





# FIELD TECHNICIANS

*Broaden the scope of your career with Bendix Radio!*

Get these BIG ADVANTAGES!

- Professional status
- The prestige of representing the leader in its field.
- Top salaries
- Liberal field allowances

If you have 5 or more years of electronics experience, you benefit many ways as a Bendix Radio Field Engineer. You will receive full pay while you go to our company-sponsored school in Baltimore. Then, you will be given a key assignment in the United States or overseas with responsibility of maintaining search and surveillance radar equipment made by Bendix Radio.

Write, call or wire EMPLOYMENT SUPERVISOR Dept. R

## Bendix Radio

DIVISION OF BENDIX AVIATION CORP  
Towson 4, Maryland  
(Phone VAlley 3-2200)



Quickly locates "TOUGH DOGS"

### Senco Tube and Capacitor Leakage Checker Model LC-2

Dealer Net **\$19.95** Kit  
Complete with test leads. Simple to operate. \$24.95 wired

**"Two Testers in One"**  
Now—checks 70 critical tube types

- Quickly locates tubes with gas, grid to cathode or heater to cathode leakage, and grid emission in RF, IF and AGC Circuits.
- Only type tester that finds all tubes causing picture overload, low sensitivity, poor sync, etc.
- Checks all capacitors for leakage with voltage applied.

At Leading Distributors!  
Mfg by **SERVICE COMPANY**  
171 OFFICIAL ROAD • ADDISON, ILL.

## AUDEL'S TV TELLS HOW TO ANSWER RADIO T.V. QUESTIONS

### SERVICE LIBRARY

HERE IS LATE INFORMATION IN A HANDY FORM FOR TELEVISION AND RADIO REPAIRMEN, SERVICEMEN AND STUDENTS

**AUDEL'S T.V. RADIO SERVICE LIBRARY**—Highly Endorsed—Over 1500 Pages—1048 Illustrations & Diagrams. 1001 Important Facts & Figures on Modern Television, Radio, Electronic Devices at your finger ends.

**INCLUDES TRANSISTORS & Transistor Circuits, Record Changers, Rectifiers, P.A. Systems, Tape Recorders, Phonograph Pick-ups, F.M., Auto Radio; Radio Compass, Short Wave, Radar, etc.**

**ASK TO SEE IT! IT WILL PAY TO KNOW—**  
The Basic Principles—Construction—Installation—Operation—Repairs—Troubleshooting. Shows How to get Sharp, Clear T.V. Pictures. Install Aerials—How to Test. Explains Color Systems, Methods of Conversion, Terms, etc. Includes Ultra High Frequency—Valuable for Quick Ready Reference and Home Study.

**6 COMPLETE 2 VOLUMES** Get this Information for Yourself.  
**7 DAY TEST—PAY ONLY \$1 A Month**  
MAIL ORDER

**AUDEL Publishers, 49 W. 23 St., N.Y. 10, N.Y.**  
Mail AUDEL'S T.V. RADIO SERVICE LIBRARY (2 Volumes) \$6 on 7 days free trial. If O. K. I will remit \$1 in 7 days and \$1 monthly until \$6 is paid. Otherwise I will return them.

Name \_\_\_\_\_  
Address \_\_\_\_\_  
Occupation \_\_\_\_\_  
Employed by \_\_\_\_\_

diagrams with data for constructing enclosures for speakers from 8 to 15 inches.

**THE USE OF SELENIUM PHOTOCELLS AND SUN BATTERIES**, by John Sasuga. International Rectifier Corp., 1521 E. Grand Ave., El Segundo, Calif. 6 x 9 inches, 58 pages, \$1.50.

Hard on the heels of the recent publicity flare-up on sun batteries, is this first modest catabook \* on the subject. A small, though very definite step in the right direction, it is well written and contains a surprising amount of useful data.

Following a brief bit of introductory theory, the author supplies circuits and construction data for a variety of projects—light-powered motors, oscillators, a batteryless radio powered by light, a light meter and others. It takes no Nostradamus to foresee that sun batteries, plus transistors, miniaturized components and printed circuits will open entirely new avenues of approach for the electronic hobbyist.—MC

\* A coined word, extracted from catalog and book.

**SONICS**, by Theodor F. Hueter and Richard H. Bolt. John Wiley & Sons, Inc., 440 Fourth Ave., New York 16, N. Y. 5½ x 9 inches, 456 pages. \$10.

Many radio technicians may not be aware that sonics (and this includes ultra sonics as well) means more than a sound wave in front of a microphone. Sonic vibrations are used in soldering, drilling, medical diagnosis, metal testing, locating fish and other objects under water, siren generators, etc. This college-grade text covers the entire field from a theoretical and practical standpoint.

After discussing the basic principles of vibration and radiation, the author describes piezoelectric and magnetostrictive transducers and receivers. These chapters are lengthy and include many diagrams and tables, also references for the aid of students.

A chapter on testing and analysis discusses standing waves and pulse techniques. Photographs include a sonic washing machine, therapy applicators, a siren and drill.—IQ

**MASTER GUIDE TO THEATRE MAINTENANCE**, by Aaron Nadell. Aaron Nadell, 130-57 Lefferts Park Blvd., South Ozone Park, N. Y. 5¼ x 7¼ inches, 240 pages. \$5.

The author—known to readers of this magazine for some decades as a writer on electronics, with special emphasis on motion-picture applications—is an experienced motion-picture man. This book covers the range from financing and insuring theatres to "The Mechanics of Candy Selling." Four of the chapters are devoted to theater sound and acoustics; one to public address in the theater. Electronics and sound get into other chapters, specially the one on drive-ins and that on new developments. The glossary (which contains such terms as "color wheel" and Kerr cell) will interest electronics men.—FS END



# SCHOOL DIRECTORY

## LEARN TV

'At the most practical school in the west'

Work on late model sets—using modern equipment and service techniques; under qualified technician instructors. Short resident and correspondence courses—no unnecessary math or theory—also UHF and Color TV.

APPROVED FOR VETERANS . . . day and nite classes.

Write for free literature, Dept. IA for residence—Dept. IAC for correspondence.

**V.S.I. TELEVISION SCHOOL**

4570 Firestone Blvd.  
South Gate, California

Your choice of school  
is highly important  
to your career in



**INDUSTRIAL  
ELECTRONICS**



**RADIO**



**TELEVISION**

Become an  
**ELECTRICAL  
ENGINEER**

or an  
**ENGINEERING  
TECHNICIAN**

at  
**MSOE in Milwaukee**

Choose from courses in:

**ELECTRICAL ENGINEERING**  
Bachelor of Science degree in 36 to 42 months with a major in electronics or electrical power.

**ELECTRICAL TECHNOLOGY**  
Engineering Technician certificate in 12 months in electronics, radio, or electrical power;

Associate in Applied Science degree in 18 months in radio and television.

**TECHNICAL SERVICE**  
Service certificate in 6 months in electricity; in 12 months in radio and television.

MSOE — located in Milwaukee, one of America's largest industrial centers — is a national leader in electronics instruction — with complete facilities, including the latest laboratory equipment, visual aid theater, amateur radio transmitter — offers 93 subjects in electrical engineering, electronics, radio, television, electrical power, and electricity.

Advisory committee of leading industrialists. Courses approved for veterans. Over 50,000 former students. Excellent placement record.

TERMS OPEN JULY, SEPTEMBER, JANUARY, APRIL

Choose wisely — your future depends on it. Write for more information today!



**MILWAUKEE**

**SCHOOL OF ENGINEERING**  
Dept. RE-656, 1025 N. Milwaukee St.  
Milwaukee 1, Wisconsin

Send FREE career booklets on:

Electrical Engineering  Radio-Television

I am interested in \_\_\_\_\_ (Name of course)

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

If veteran, give discharge date \_\_\_\_\_

MS-31

## ENGINEERING

Prepare for unlimited opportunities in electronics! B.S. degree in 27 months. Intensive, specialized courses. Math, electrical engineering, TV, advanced radio theory & design. Modern labs. Low rate. Earn board. Also Aero, Chemical, Civil, Elec., Mech. Eng. G.I. appr. Spacious campus. 20 bldgs.; dorms, gym. Enter June, Sept., Dec. Mar. Catalog.

**INDIANA TECHNICAL COLLEGE**  
1566 E. Washington Blvd., Fort Wayne 2, Indiana



## wanted career men

Train for a career instead of a job. Demand for our graduates exceeds supply. Effective placement. Modest costs. Small classes. Well-equipped labs. Beautiful campus. Approved for Vets. Enter June, Sept., Jan., March.

**BACH. SCI. DEGREE IN 27 MONTHS**  
Complete Radio Eng. courses . . . TV, UHF, FM, Electronics. Also Mech., Civil, Elec., Chem., Aero. Eng. 36-month B.S. in Bus. Adm. (Gen. Bus., Acctg., Motor Transport Mgt.) . . . capable students faster. Prep courses. Write Jean McCarthy, Dir. Adm., for catalog and "Your Career in Engineering & Commerce."



## TRI-STATE COLLEGE

2466 College Avenue, Angola, Indiana



## TV REPAIRMEN EARN TOP MONEY!

IN JUST 12 MONTHS, COMPLETE TV SERVICE TRAINING, INCLUDING COLOR TV. Streamlined course gives you all essentials for a good job as service technician. Graduates in great demand; jobs are plentiful in this growing field. Other electronic courses in radio operation and maintenance. Day or evening classes. Opportunity for employment in local industry. Approved for Korean veterans.

Write for Catalog 111 Today

**INDIANAPOLIS ELECTRONIC SCHOOL**  
312 E. Washington, Indianapolis 4, Indiana

## EARN MORE MONEY— BE A PROFESSIONAL TELEVISION SERVICE TECHNICIAN

GET DOWN-TO-EARTH PRACTICAL TV TRAINING WITH WTI EXPERTS FOR THE TOP PAYING \$5,000-\$10,000 PER YEAR JOBS.

UHF—COLOR—VHF

Master the latest, up-to-the-minute TV and Color TV developments QUICKLY.

SEND FOR FREE BOOK TODAY!

WESTERN TV offers real experience on live equipment in our BIG SHOPS AND LABORATORIES in the shortest practical time under expert instructors. Graduates are in big demand because they have the "field experience" necessary for immediate "bench" or supervisory positions. You learn every phase of Radio and TV servicing (AM, FM, VHF, UHF). WTI men win fast promotion . . . can demand better pay . . . develop highly profitable businesses of their own with the latest and most PRACTICAL PERSONALIZED TRAINING BEHIND THEM. You concentrate all your time on being a PROFESSIONAL TV SERVICE TECHNICIAN — non-essential math and engineering theory omitted. YOU CAN EARN WHILE YOU LEARN. Special Finance Plan.

APPROVED FOR VETERANS. Find out how you can get into the TOP PAY GROUP — Send for this fact-packed book NOW!

**WESTERN TELEVISION INSTITUTE**

America's Leading  
Television  
Servicing School

Western Television Institute Dept. E-656  
341 W. 18th St., Los Angeles 15, Calif.  
Without obligation, please send FREE fully illustrated booklet. (No salesman will call.)

NAME \_\_\_\_\_ AGE \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_ ZONE \_\_\_\_\_ STATE \_\_\_\_\_

## TELEVISION

PREPARE FOR A GOOD JOB!

BROADCAST ENGINEER  
ELECTRONICS  
RADIO SERVICING

Television Servicing

(Approved for Veterans)  
BUILDING AIRCONDITIONED  
SEND FOR FREE LITERATURE  
**BALTIMORE TECHNICAL INSTITUTE**  
1425 EUTAW PLACE, BALTIMORE 17, MD.



## RCA INSTITUTES, INC.

A service of Radio Corporation of America  
350 West 4th St., New York 14, N. Y.

OFFERS COURSES IN  
ALL TECHNICAL PHASES OF  
RADIO, TELEVISION, ELECTRONICS

Approved for Veterans  
Write Dept. RE-66 for Catalog



## FINISH HIGH SCHOOL AT HOME!

No classes to attend. Easy spare-time training covers big choice of subjects. Friendly instructors; standard texts. Full credit for previous schooling. Diploma awarded. Write now for FREE catalog!

**WAYNE SCHOOL** Catalog HKE-4  
2527 Sheffield Ave., Chicago 14, Illinois

## Get Your F.C.C. LICENSE Quickly!

Guaranteed preparation in a MINIMUM OF TIME for F.C.C. commercial operator examinations. Our highly specialized training is available by correspondence, or in resident classes in

WASHINGTON, D. C. and HOLLYWOOD, CALIF.

Write for our free booklet with complete details.

**GRANTHAM School of Electronics**  
Desk 4-C, 821 19th Street N.W., Washington 6, D.C.

## CODE SENDING RECEIVING SPEED


Be a "key" man. Learn how to send and receive messages in code by telegraph and radio. Commerce needs thousands of men for jobs. Good pay, adventure, interesting work. Learn at home quickly through famous Candler System. Qualify for Amateur or Commercial License. Write for FREE BOOK.

**CANDLER SYSTEM CO.**  
Dept. 9-G, Box 928, Denver 1, Colo., U.S.A.
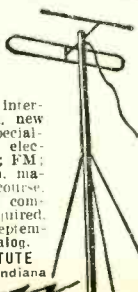
## GET INTO ELECTRONICS

You can enter this uncrowded, interesting field. Defense expansion, new developments demand trained specialists. Study all phases: radio & electronics theory and practice; TV; FM; broadcasting; servicing; aviation, marine, police radio. 18-month course. Graduates in demand by major companies. H.S. or equivalent required. Begin January, March, June, September. Campus life. Write for catalog.

**VALPARAISO TECHNICAL INSTITUTE**  
Dept. C Valparaiso, Indiana





Only the 5 TOP QUALITY brands of

# STANDARD BRAND TUBES

## AT SENSIBLE PRICES!

- Individually boxed ● First quality only
- Brand New ● 90-DAY RETMA guarantee
- No private brands ● No rejects
- No rebrands or rewashed bargains

Write for complete price list.  
Over 1000 tube types in stock.

### TRANSMITTING TUBE SPECIALS

(Brand New Surplus)

4PR60A	.....\$50.00	803	.....\$ 2.00
304TH	.....10.75	807	.....1.20
307A	......80	807W/5933	.....2.85
450TH	.....47.00	866A (RCA)	.....1.25
750TL	.....50.00	872A	.....1.25

### 2 COLOR TUBE CARTONS

Keeps your tube stock neat. New safety partition prevents tube breakage. Distinctive lithographed in glossy red and black. The most distinctive tube carton available today. Minimum quantity: 100 of any one size. Write for case lot prices.

SIZE	FOR TUBE	PER 100
Miniature	6AU6, etc.	\$1.00
GT	6SN7, etc.	1.25
Large GT	1B3, etc.	1.50
Large G	5U4G, etc.	2.00

**WHITE GLOSSY BOXES**  
Completely blank, no printing or color. Otherwise same as above. Same high quality, same low prices. Specify "WHITE" when ordering. When color is not stated, 2 color cartons will be shipped.

**TUBE STACKERS**  
White glossy only. Ministacker holds 10 Mini. tube cartons; "GT" stacker holds 10 "GT" cartons.

SIZE	PER 100
Ministacker	.....\$1.50
GT	.....2.00

SAVE ON STACKERS. Either size only \$10.00 per case of 1,000. F.O.B., New York!



### DIRECTRON SELENIUM RECTIFIERS

#### Full Wave Bridge Type

Max. Amps.	18VAC 14VDC	36VAC 28VDC	54VAC 42VDC	72VAC 56VDC	130VAC 100VDC
1	\$1.35	\$2.30	\$3.70	\$4.50	\$7.40
2	2.00	2.75	5.30	5.90	9.15
2 1/2	2.90	4.10	5.75	7.85	12.70
3	3.50	6.40	11.25	14.35	21.70
4	3.95	7.70	12.75	17.30	29.65
10	5.85	11.35	19.40	24.80	41.25
12	7.20	14.25	22.00	27.75	43.85
20	13.05	25.05	37.25	48.75	78.50
24	14.25	28.75	44.50	57.65	81.00

Complete line of new rectifier transformers, chokes and filter capacitors in stock at all times. May be ordered at same time as selenium rectifiers above for immediate delivery. Write for complete price list.

We build other Selenium Rectifiers, Transformers and Chokes to your specifications.

### NEW RECTIFIER TRANSFORMERS

Continuous Ratings	1 Amp.	\$ 5.75
PRI: 115V, 60 cycles input	2 Amps.	6.75
SEC: 9, 12, 16, 24 and 36 volts.	4 Amps.	8.75
	12 Amps.	16.65
	24 Amps.	35.65

### NEW RECTIFIER CHOKES

Continuous Ratings	1.5 ohm	\$ 4.95
1 Amp.	.04 Hy.	5.95
2 Amps.	.07 Hy.	7.95
4 Amps.	.01 Hy.	14.95
12 Amps.	.025 ohm	29.95

### FILTER CAPACITORS

Capacity	W. Voltage	Each
400 MFD	25 V.	\$1.00
500 MFD	200 V.	1.95
500 MFD	50 V.	1.95
1000 MFD	15 V.	.85
1000 MFD	35 V.	1.50
2000 MFD	50 V.	2.25
6000 MFD	15 V.	2.50

### GET A U. S. NAVY

## SNOOPERSCOPE

The Infra-red device that

LETS YOU SEE IN TOTAL DARKNESS!!



BRAND \$160.00 NEW

Write for details

WRITE FOR "BARRY'S GREEN SHEET" ISSUED MONTHLY. FREE!

TERMS: 25% deposit with order, balance C.O.D. All merchandise guaranteed. F.O.B. N.Y.C.

## BARRY ELECTRONICS CORP.

512 Broadway, Dept. RE, N.Y. 12, N.Y.

Call Us Day or Night  
24-Hour Phone Service  
Phone: Walker 5-7000

## ADVERTISING INDEX

Radio-Electronics does not assume responsibility for any errors appearing in the index below.

Aeromotor Co.	.....100	North American Philips Co., Inc.	.....86
Allied Radio Corp.	.....11,75	Opportunity Adlets	.....118
Almo Radio Co.	.....10	ORRadio Industries	.....101
American Phenolic Corp.	.....102	Oxford Electric	.....114
Arkay Radio Kits, Inc.	.....118	Perma-Power Co.	.....98
Audel Publishers	.....126	Phaotron Co.	.....88
Barjay Co.	.....128	Precise Development Corp.	.....95
Barry Electronics	.....128	Prentice-Hall, Inc.	.....117
Belden Manufacturing Co.	.....87	Presto Recording Corp.	.....120
Bell Telephone Labs.	.....26	Progressive Edu-Kits, Inc.	.....94
Bendix Radio	.....126	Pyramid Electric Co.	.....96
Blonder-Tongue Labs.	.....124	Quality Electronics	.....117
British Industries Corp.	.....99	RCA Institutes, Inc.	.....17
Brooks Radio & Television	.....121	RCA Service Co.	.....90
CBS-Hytron	.....20	RCA Tube Dept.	.....Back Cover
Capitol Radio Engineering Institute	.....25	Radiart	.....18
Centralab Div. of Globe Union	.....115	Radio Products Co.	.....117
Cleveland Institute of Radio Engineers	.....9	Radio Receptor, Inc.	.....74
Cornell-Dubilier	.....18	Radio Television Training Association	.....21
Coyne Electrical School	.....97, 119, 125	Rad-Tel Tube Co.	.....100
Delco Div. of General Motors	.....89	Ram Electronic Sales Co.	.....125
DeRo Electronics	.....99	Raytheon Manufacturing Co.	.....Inside Front Cover
DeVry Technical Institute	.....7	Rek-O-Kut	.....13
Dressner	.....116	Remington-Rand Univac	.....22
Dyna Co.	.....124	Rinehart Books, Inc.	.....103
Editions Radio	.....117	Rockbar Corp.	.....16, 93
Electro-Voice Inc.	.....6	Ronette Acoustical Corp.	.....122
Electronic Instrument Co. (EICO)	.....27, 28	Sams (Howard W.) & Co., Inc.	.....19, 106
Electronic Publishing Co.	.....112	Service Instruments Co.	.....126
Elgin National Watch Co.	.....14	Simpson Electric Co.	.....91, 113
Fenton Co.	.....125	Sonotone Corp.	.....12
Futurmatic	.....123	Sprague Products Co.	.....85
Garrard	.....99	Stan-Burn Radio & Electronics Co.	.....123
General Cement Manufacturing Co.	.....119	Sylvania Electric Products	.....77
General Industries Co.	.....10	Technical Appliance Co.	.....108
Gernsback Library, Inc.	.....118	Technical Materiel Corp.	.....119
Heath Co.	.....61-72	Television Hardware Mfg. Co.	.....119
Herschel Radio	.....117	Triplett Electrical Instrument Co.	.....Inside Back Cover
Hexacon Electric Co.	.....120	Tung Sol Electric Co.	.....8
Hi-Fi Fabrics Institute	.....99	United Catalog Publishers, Inc.	.....111
Hughes Research & Development Labs.	.....112	University Loudspeakers	.....109
Hunter Tool Co.	.....98	Vaco Products Co.	.....116
IBM	.....130	Vokar Corp.	.....110
Indiana Technical College	.....114	Wen Products Co.	.....15
Instructograph Co.	.....116	Winston Electronics, Inc.	.....92
Jensen Industries	.....120	SCHOOL DIRECTORY PAGE 127	
Jensen Manufacturing Co.	.....24	Baltimore Technical Institute	.....
Jones & Laughlin Steel Corp.	.....107	Candler System Co.	.....
LMB	.....114	Grantham School	.....
Lafayette Radio	.....129	Indiana Technical College	.....
Lektron Specialties	.....122	Indianapolis Electronic School	.....
Littelfuse, Inc.	.....23	Milwaukee School of Engineering	.....
Mallory (P. R.) & Co., Inc.	.....104, 105	RCA Institutes, Inc.	.....
Merit Coil & Transformer Corp.	.....14	Tri-State College	.....
Miller (Gustave)	.....116	Valparaiso Technical Institute	.....
Moss Electronics Distributing	.....82-83	V.S.I. Television School	.....
National Radio Institute	.....3	Wayne School	.....
National Schools	.....5	Western Television Institute	.....
Nordic Radio Co.	.....114		

NEW! For the First Time!

CHECK CAPACITORS UNDER WORKING CONDITIONS!



SATISFACTION GUARANTEED OR RETURN WITHIN TEN DAYS FOR REFUND

## CAPACITEST

Quickly, Accurately checks:

- PAPER, MICA, CERAMIC CAPACITORS
- ELECTROLYTICS
- CONTINUITY
- AC/DC VOLTAGES
- FLASHBULBS

\$9.95 postpaid Dir. Net complete, ready for operation

NOT A KIT

FREE Special Introductory Offer for limited time only: Set of test leads Free with each CAPACITEST.

Order direct from manufacturer - include \$3 deposit with C.O.D.'s. Save PP & COD fees, send \$9.95 & we'll pay postage.

### CAPACITEST, the result of months in development

It will check condensers at 150 Volts, which is approximately the working voltage in a radio or TV set. Meters will not give this type of check since the applied voltage is 20 Volts or less. Avoid call backs by using CAPACITEST. Accurately, quickly, it shows open, shorted, or intermittent capacitors and leaky electrolytics. Compact: 4"x4"x2"-lightweight, for bench or tool kit.

**BARJAY The Barjay Co.** 145 West 40 Street New York 18, N.Y.



# Just a few of **LAFAYETTES** Values

## PROFESSIONAL TRANSCRIPTION TURNTABLE AND VISCOUS-DAMPED TONE ARM THE FINEST TRANSCRIPTION TURNTABLE AND TONE ARM FOR THE PROFESSIONAL USER AND THE AUDIOPHILE



**COMBINATION DEAL**  
PK-100 TURNTABLE AND TONE ARM ..... **59.50**  
The above with G.E. 8PX, 057A, 14 MOND and S.F. PHIRE Cartridge ..... **72.50**

### PK-100 TRANSCRIPTION TURNTABLE

New 3-speed instrument to delight the connoisseur, is precision engineered to provide dynamic balance and "wow-free" operation. A heavy-duty, constant speed 4-pole induction motor has a variable speed control to permit instant adjustment of the individual speeds to within  $\pm 7\%$  to compensate for power source voltage variations. The motor is freely suspended and isolated by shock-mountings to eliminate vibration transfer. The heavy, cast aluminum turntable is rim-driven and has an extra-heavy rim for smooth, effective flywheel action. Idler disengaged in "off" position. Meets professional standards for wow, flutter content, etc. Size:  $13\frac{1}{2}'' \times 14''$  and requires  $2\frac{3}{4}''$  clearance above and  $3\frac{3}{4}''$  below motorboard. For 110-130V 60/50 cycle AC. Supplied with removable 3-speed stroboscopic disc and 45 rpm adapter. Handsome hammertone gray finish. Shpg. wt., 20 lbs. **Net 49.50**

### PK-90 VISCOUS-DAMPED TONE ARM

This transcription arm assures dependable and stable operation, utilizing the "floating action" principle of "viscous-damping." The arm is supported at a single point by a pivot and jewel bearing having negligible friction. Damping is accomplished by a silicone fluid occupying the gap between a ball and socket. This damping control permits high compliance and negligible tracking error, and prevents damage to either record or stylus should the tone arm be accidentally dropped. Low frequency resonance, skidding and groove-jumping are likewise minimized. The tone arm accepts all records up to  $16''$  and accommodates virtually all hi-fi cartridges by means of precisely engineered adapters which simplify installation and provide proper stylus pressure. This tone arm is a quality companion to the PK-100 with matching finish. Shpg. wt.,  $2\frac{1}{2}$  lbs. **Net 19.50**

### 2 TRANSISTOR POCKET RADIO KIT




Packed into a  $2\frac{1}{2}'' \times 3\frac{1}{2}'' \times 1\frac{1}{4}''$  plastic case. This Two Transistor plus crystal diode radio kit offers many surprises, utilizing a regenerative detector circuit with transformer coupled audio stage, gives you high gain and excellent selectivity. Pulls in distant stations with ease with more than ample earphone volume. Kit comes complete with two transistors, crystal diode, loopstick, Arzonne transistor audio transformer, resistors, condensers, plastic case, etc., including schematic and instructions.  
KT-68A Complete Kit less earphones. **11.80**  
MS-260 New Super Power Dynamic Earphone, ideal for Transistor Circuit imp. 8000 ohm, D.C. 2000 ohm ..... **3.95**

### HIGH SENSITIVITY 20,000 OHM PER VOLT DC 10,000 OHM PER VOLT AC MULTITESTER



35 up 3" METER SILVER CONTACT SELECTOR SWITCH 1% PRECISION RESISTOR  
LOOK AT THESE FULL SCALE RANGES!  
D.C. VOLTS: 0-6; 0-30; 0-120; 0-600; 0-1200; 0-6000 Volts—A.C. VOLTS: 0-6; 0-30; 0-120; 0-600; 0-1200 Volts—RESISTANCE: 0-10K; 0-100K; 0-1 Meg; 0-10 Megohms—D.C. CURRENT: 0-60 Microamp; 0-6; 0-60; 0-600 MILLIamps—DECIBEL: —20 to +17 db (0 db = 0.774V)—CAPACITY: .0001-.01; .005-.15 mfd—INDUCTANCE: 20-2000 millihenry—OUTPUT RANGES: 0-6; 0-30; 0-120; 0-600; 0-1200 Volts  
The new Lafayette high sensitivity Multitester is a complete instrument (not a kit). In addition to its unusual sensitivity of 20,000 OHMS PER VOLT ON D.C. AND 10,000 OHMS PER VOLT ON A.C., and the extraordinary number and scope of its ranges, it is packed with features that would make it cost at least twice as much if made in this country. Uses 1% precision resistors, silver contacts on selector switch, 35 up meter. Size:  $6\frac{1}{4}'' \times 4\frac{1}{4}'' \times 2\frac{1}{2}''$ . Complete with batteries and leads. Shipping weight  $4\frac{1}{2}$  lbs. **Net 19.95**  
Singly, Each **19.95**  
In lots of 3, each **12.25**

### HIGH-FIDELITY TURNOVER CARTRIDGE

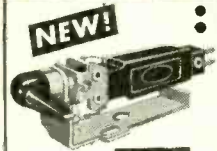

**NEW!**  
● 40-14000 CYCLE  
● NEVER BEFORE AT SUCH A PRICE!  
Lafayette brings you one of the finest high-fidelity turnover cartridges, AT UNBELIEVABLE PRICE!  
Frequency response from 40-14000 cycles + 2 db. Has 2 sapphire styli to play all speeds. Needle pressure only 5 grams on LP cond 12-15 grams on 78, output is 5 volts. Complete with turnover mechanism and knob, fits Webster, Garrard, VM, Collaro and tone arms of leading manufacturers of record changers and players.  
PK-79 ..... Singly, Each **2.75**  
In lots of 3, Each **2.50**

### NEW! POWERFUL SUPERHET POCKET RADIO SENSITIVE SELECTIVE BUILT IN ANTENNAS

● TRULY PORTABLE: Only  $5\frac{1}{2}'' \times 3\frac{1}{4}'' \times 1\frac{3}{8}''$  Weighs only 14 oz. with batteries  
● TRULY PERSONAL: Has built-in private earpiece so only you can hear  
● POWERFUL-SELECTIVE: Power, sensitivity and selectivity that only a vacuum tube superhet circuit can give




A personal portable radio with unmatched performance, featuring a superhet circuit with extreme sensitivity and selectivity and a power output still common only to vacuum tube circuits. It is entirely self-contained in a beautiful plastic case with lucite control knob. Available in Ivory or Red. Specify color. Shpg. wt., 2 lbs. Supplied with earpiece but less batteries.  
F5-101 (less batteries) ..... **Net 11.95**  
**BATTERIES**  
1 — Burgess U30 ..... **Net 1.75**  
1 — Burgess #1 ..... **Net .10**

### TRANSISTOR CHECKER KIT



● Checks Shorts, Leakage, and Gain  
A "must" for servicemen, experimenters and engineers. Tests both PNP and NPN type transistors. Gives 2 separate checks; first GOOD-BAD check for shorts and leakage, and second for GAIN. Gray hammertone case  $5\frac{1}{4}'' \times 3'' \times 2\frac{1}{4}''$ . Kit includes case, meter, all parts with full assembly and operating instructions. Simple to build. Fast, accurate. Shpg. wt. 3 lbs.  
KT-86 Kit ..... **7.95**

### NEW POCKET AC-DC VOM MULTITESTER

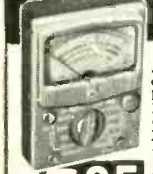

2,000 ohm per Volt on AC & DC  
● Completely wired — Not a kit  
Accurate VOM with a sensitivity of 2000 ohms per volt on both AC and DC. Single selector switch. 3-160 amp. meter. Scales: DC Volts: 0-10; 0-100; AC Volts: 0-10; 0-50; 0-100; Ohms: 0-10K; 0-1 Meg; DC Current: 500 ua and 500 ma; Decibel: —20 to +22, +20 to 36; Capacity: 250 mfd to 2 mfd and .005 to 1 mfd. Heavy plastic panel, metal bottom.  $4\frac{1}{4}'' \times 3\frac{1}{2}'' \times 1\frac{3}{8}''$ . With batteries and test leads. Shpg. wt. 4 lbs.  
RW-27A ..... **7.95**

### LAFAYETTE TIME + 1/2 TAPE 1800 FT. - 7 INCH REEL

\$2.59 Each, Singly  
\$2.45 Each, Lots of 10

### AN ENTIRE SYMPHONY ON ONE REEL OF TAPE! NO MORE ANNOYING INTERRUPTIONS!

Lafayette did it again! New plastic base. TIME + 1/2 High Fidelity Recording Tape at an amazingly low price! Over  $1\frac{1}{2}$  hrs. of playing time on one reel at  $7\frac{1}{2}''$  per second on dual track recording. At  $3\frac{3}{4}''$  per second you get 3 hours and 12 minutes. The same quality that has made the Lafayette Standard Tape the nation's outstanding value. 40-15,000 cycle response at  $7\frac{1}{2}''$  per second assures you of the finest professional quality high fidelity recordings. A true Lafayette value backed up with our Money Back Guarantee. You be the judge—try it!  
LAFAYETTE TIME + 1/2 TAPE } Lots of 10. Each **\$2.45**  
1800 FT. - 7 INCH REEL } Singly. Each **\$2.59**

### NEW! ALL-PURPOSE DYNAMIC EARPHONE



● FOR RADIO AND TV LISTENING  
● FOR SUBMINIATURE, MINIATURE AND TRANSISTOR RECEIVERS

A sensitive all-purpose earphone designed for your listening pleasure. Combines the range of a dynamic earphone with the performance of its special magnet to give you excellent reproduction. Lightweight and equipped with ear support that slips comfortably over your ear. You can relax! The support is practically invisible — the earphone can't slip out — it can't fall off. Ideal for use with TV and radio sets, amplifiers, miniature and transistor receivers etc. Complete with 3 ft. cord. A super value for the price!  
MS-278 — 3000 ohm impedance, 1000 ohm DC resistance, with phone tip plugs. **Net 1.95**  
MS-277 — 6 ohm impedance, with phone tip plugs. For Silent Radio and TV Listening or Viewing **Net 1.95**  
MS-273 — 3000 ohm impedance, 1000 ohm DC resistance, with subminiature phone plug and matching phone jack. **Net 2.39**  
MS-279 — 6 ohm impedance, with subminiature phone plug and matching phone jack. For Silent Radio and TV Listening or Viewing **Net 2.39**

### CRYSTAL MICROPHONE

COMPARE IT WITH ANY MIKE AT 2 TO 3 TIMES THE PRICE  
A quality crystal Microphone for PA systems, house recorders, etc. Frequency response 30 to 10,000 cycles. Output level — 52 db. Provides ample output for use with low gain amplifiers. Complete with 5 ft. of shielded cable. Shpg. wt.,  $3\frac{1}{2}$  lbs.  
PK-24 — in lots of 3, each .. **3.95**  
singly, each ..... **4.25**

### IMPORTED BINOCULARS

All have coated lenses — clamped in prism — light weight all metal bodies. Complete with case and straps.  
F-182 — 8x.15 I.F. .... **NET 10.75**  
F-103 — 8x.30 I.F. .... **NET 14.95**  
F-115 — 7x.35 I.F. .... **NET 17.95**  
F-183 — 7x.35 C.F. .... **NET 20.95**  
F-103 — 7x.50 I.F. .... **NET 21.50**  
F-164 — 7x.50 C.F. .... **NET 24.95**  
F-114 — 10x.35 I.F. .... **NET 23.95**  
F-104 — 12x.50 I.F. .... **NET 27.95**  
F-118 — 16x.60 C.F. .... **NET 31.50**  
F-185 — 20x.50 C.F. .... **NET 37.50**


### REMOTE CONTROL FOR SILENT TV VIEWING

● For Hard-of-Hearing  
● For Late Listening  
One or two people can both see or hear the program with the loud speaker cut-off. The hard-of-hearing can listen to radio or TV without turning the volume so high that others can't stand the noise. Comes complete with miniature phone and 20 ft. of cable. Shpg. wt. 3 lbs. **Net 6.50**

Add 10% Fed. Tax to Above Prices  
**Lafayette Radio** DEPT. JF  
BRONX, N.Y. 542 E. Fordham Rd.  
NEWARK, N.J. 24 Central Ave.  
NEW YORK, N.Y. 100 SIXTH AVE.  
PLAINFIELD, N.J. 179 West 2nd St.  
BOSTON, MASS. 110 Federal St.  
Include postage with order.

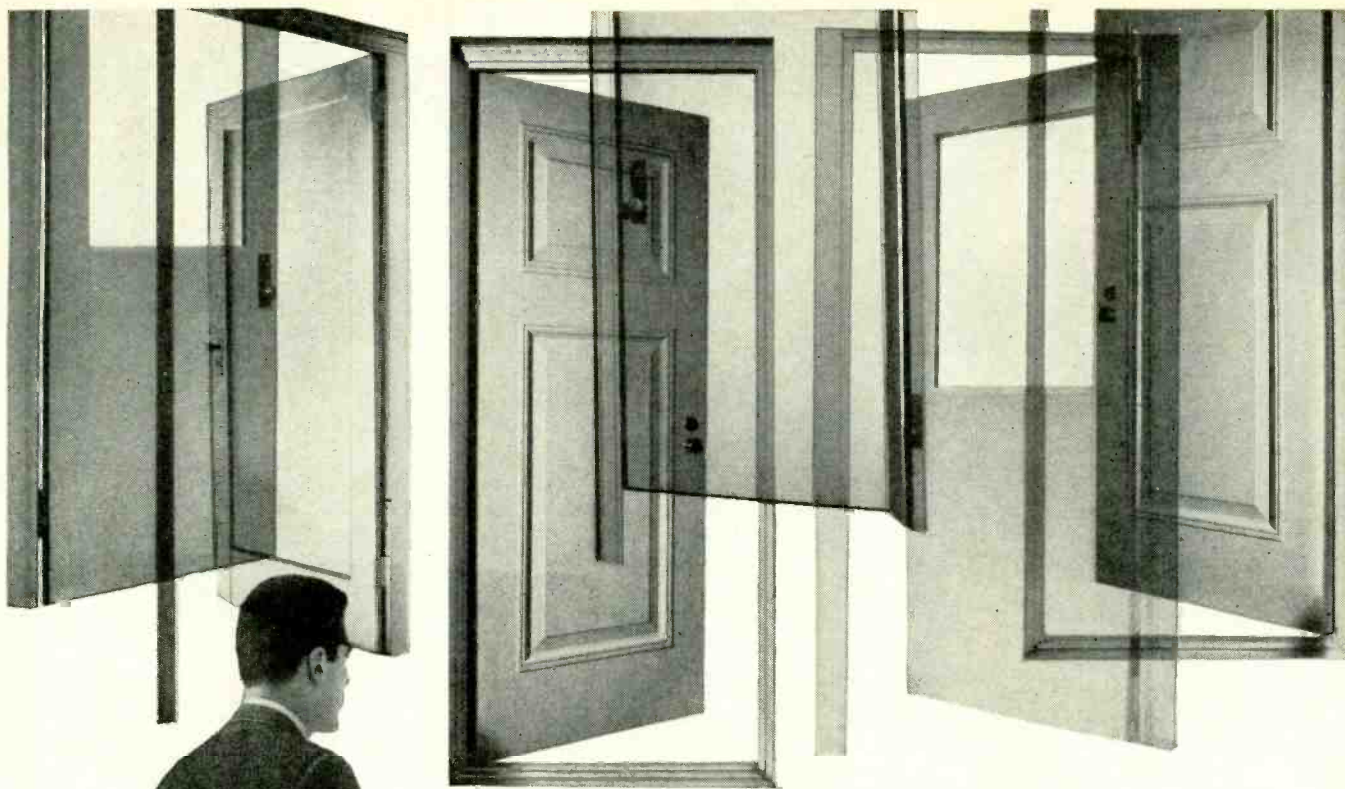Send **FREE 132-Page Lafayette Catalog**  
Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_





## DO TECHNICIANS GET JOBS TOO EASILY?

Never before has it been so easy for a technician to get a job. Just because jobs are so abundant—it's harder than ever to choose the right one.

At IBM, a leader in the rapidly expanding electronic computer field, you can *actually assume engineering responsibility working on the world's largest computer!*

After advanced computer training (up to 9 months with pay) at IBM's Kingston, N. Y. school, you'll take an active part in the fastest-growing program in the electronics industry. You'll learn the latest computing techniques, use the finest test equipment, and work with the largest computer in the world. The future never looked better at IBM, long a leader in its field

*If you possess at least a 2-year technical school background emphasizing electronics, you're eligible for experience money can't buy. Write now to N. O. Heyer, Room 3106, International Business Machines, Kingston, N. Y. We can arrange a personal interview to discuss your career objectives.*

**IBM**

*Producer of electronic data processing machines, electric typewriters, and electronic time equipment.*


**Customer Engineers:** opportunities are also available, locally, for technicians to service IBM machines, after training with pay. Contact your nearest IBM office

# ACTUAL SIZE

complete with selector switch...
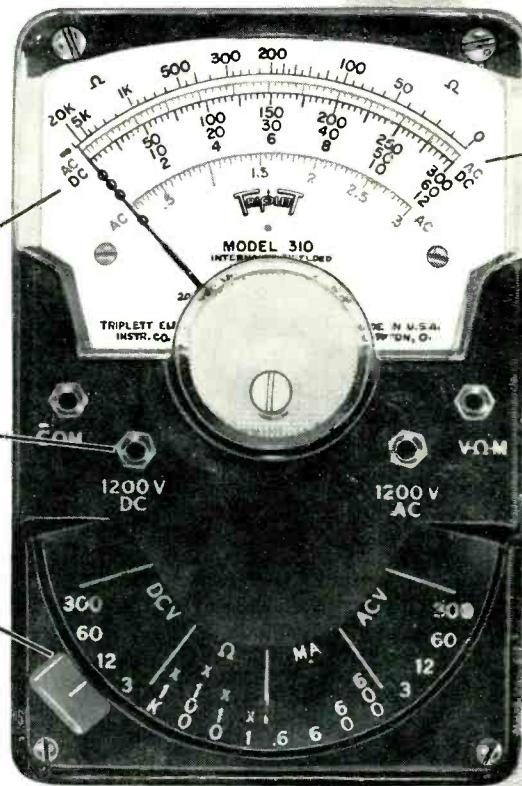
## TRIPLETT

ELECTRICAL INSTRUMENT CO.  
Bluffton, Ohio



• 5,000 ohms per volt. A.C.

• 20,000 ohms per volt. D.C.

• BANANA-TYPE JACKS—positive connection and long life.

• EXCLUSIVE SELECTOR SWITCH speeds circuit and range settings. The first and only miniature VOM with this exclusive feature for quick, fool-proof selection of all ranges.



### CARRYING CASE

Handsome leather carrying case with adequate space for Model 310 tester and accessories. Trousers belt slips through loop on back of the case for out-of-the-way carrying. MODEL 369 CASE—U.S.A. Dealer Net..... \$2.90

Model **310** MIGHTY MITE

the only complete miniature  
**V-O-M (AC-DC)**

### LOOK AT ALL THESE RANGES

DC VOLTS: 0-3-12-60-300-1200 at 20,000 Ohms/Volt.  
AC VOLTS: 0-3-12-60-300-1200 at 5,000 Ohms/Volt.  
DC MICROAMPERES: 0-600 at 250 Millivolts.  
DC MILLIAMPERES: 0-6-60-600 at 250 Millivolts.  
OHMS: 0-20,000-200,000 (200-2000 at center scale).  
MEGOHMS: 0-2-20 (20,000-200,000 Ohms at center scale).  
OUTPUT: Convenient chart in instruction book.

SEE IT AT YOUR JOBBER  
AND IT'S ONLY ONE OF TRIPLETT'S MIGHTY NINE VOM LINE!

ONLY **\$29<sup>50</sup>** Dealer Net



**631**  
Combination  
V-O-M—VTVM



**630-NA**  
For Best Testing  
Around The Lab,  
Production Line  
or Bench



**630**  
The Popular  
All-Purpose  
V-O-M



**630-A**  
A Good Lab and  
Production Line  
V-O-M



**630-T**  
For Telephone  
Service



**666-HH**  
Medium Size  
For  
Field Testing



**625-NA**  
The First V-O-M  
With 10,000  
Ohms/Volt AC




**666-R**  
Medium Size  
With  
630 Features

BURTON BROWNE ADVERTISING


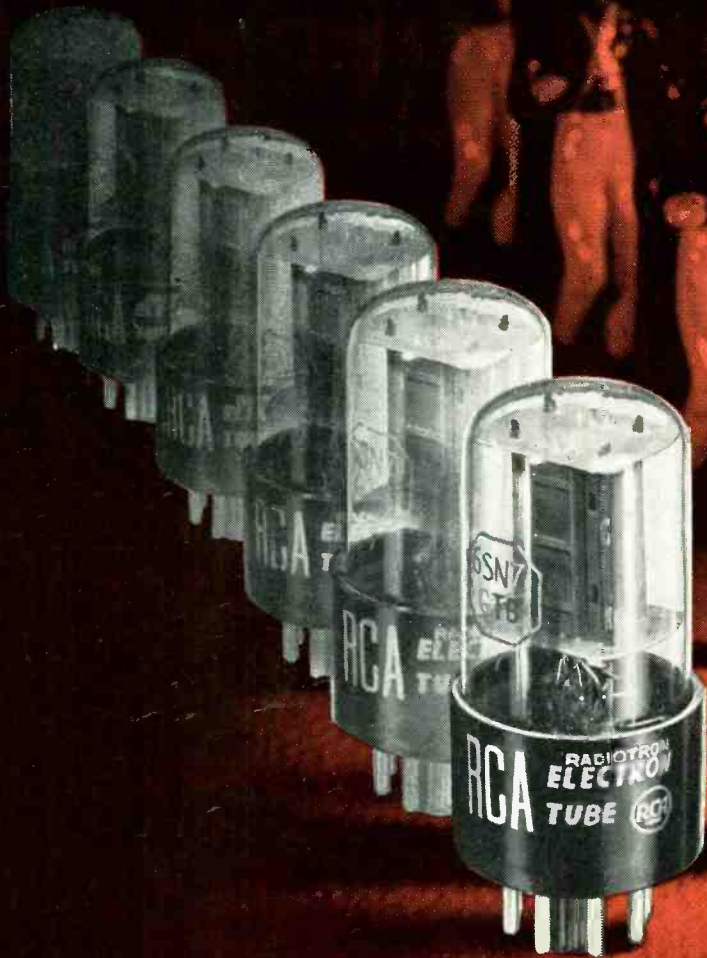
# ELECTRICAL UNIFORMITY

*for dependable  
replacement in  
critical circuits*



A BASIC ENGINEERING FEATURE OF RCA RECEIVING TUBES

To cut down on "tube juggling" and circuit realigning, RCA controls the quality of your tubes for you—at the factory.

Take the RCA-6SN7-GTB, for example. Every single tube—not just one out of a batch—is subjected to no less than 11 tests for individual electrical characteristics. Before and during manufacturing, RCA closely controls such things as: (1) Cathode material to insure uniform cathode emission and minimize interface resistance, (2) Heater wire to assure even cathode temperature. (3) Grid dimensions and inside plate diameter to insure uniform transconductance, (4) Mica hole size and hole spacing to reduce microphonics.

Yes, you can rely on the electrical uniformity of RCA Receiving Tubes! Tell *your* distributor to fill *your* tube order with *RCA Tubes only!*



**RECEIVING TUBES**

RADIO CORPORATION OF AMERICA, HARRISON, N. J.



Just released: 28-page booklet, "RCA Receiving Tubes for AM, FM and TV." Up-to-date. Gives characteristics and socket connections for more than 600 types. See your RCA distributor for Form 1275-G, or write RCA, Commercial Engineering, Sec. E-39X, Harrison, N. J.