

**THIS MONTH
156 Pages**

\$100 COMPUTER BOARDS—WHO MAKES WHAT

\$1.00 ■ APRIL 1978

34140

Radio-^{IND}Electronics

THE MAGAZINE FOR NEW IDEAS IN ELECTRONICS

pendulums, chimes, displays

UNUSUAL CLOCKS

for your wall and shelf

build for your car

DIGITAL TACHOMETER

with LED display

all about the

\$100 BUS

and your microcomputer

for the hobbyist


MODIFY HARDWARE

to suit your needs

how to select a

NEW DMM

more for your money

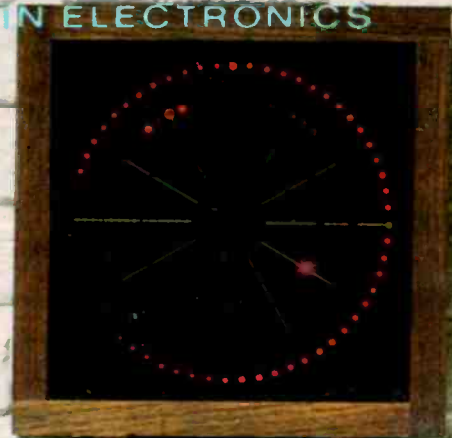

**Video-Tape Recorder Update
New RIAA Equalization Curves
Two Hi-Fi Lab Test Reports
Z-80 Computer Corner
Hobby Corner
State-Of-Solid-State
Service Clinic
XR-2208 Application Note**



**GERNSBACK
PUBLICATION**

THE SUPERLATIVE SONY.

THE NEW TC-766-2 HAS THE LOWEST WOW AND FLUTTER OF ANY DECK SONY EVER BUILT.



TC-766-2

AN INCREDIBLE 0.018% (WRMS) AT 15 IPS, AND 0.04% (WRMS) AT 7½ IPS. Closed Loop Dual Capstan Tape Drive System. One capstan extends from the motor shaft itself, eliminating intervening gears that can hamper speed accuracy. The other tape drive capstan connects through an extremely steady belt-drive inertia flywheel.

PHASE COMPENSATOR CIRCUIT. The goal of any recording is a "mirror image" of the original signal. Sony's exclusive Phase Compensator Circuit comes closest to achieving this by rectifying phase distortion and producing sound quality virtually identical to the original source.

PROFESSIONAL STUDIO STANDARD VU METERS. Illuminated, calibrated and ultra-clear for the best monitoring possible, are identical in size, shape, color and sensitivity to those on professional consoles.

SYMPHASE RECORDING. Because of Sony's outstanding

Ferrite & Ferrite Heads, plus the remarkably precise fabrication and alignment of the head gap, recordings retain exact positioning of signal throughout the stereo field. The "location" of individual sounds won't wander. There's no annoying phase shift.

MORE PROFESSIONAL FEATURES. The TC-766-2 has 4 incredibly durable Ferrite & Ferrite heads for 2-track recording and playback, 4-track playback and erase, direct-coupled playback FET amplifier, flashing Standby Signal, Punch-In Record and solenoid-operated Logic-Controlled Transport Functions to let you move instantly to and from any mode without stopping. Standard equipment: RM-30 full-function remote control unit with record mute and hinged head cover.

SONY®

Brought to you by
SUPERSCOPE

Printer Break- through



A new 10-digit display calculator with the world's first dual-element integrated printing head will revolutionize the printing calculator.

The full-featured \$89.95 Canon P10-D with its one-year parts and labor limited warranty is the greatest printer value ever offered by JS&A.

Hats off to IBM. Their single-element typing system did away with typewriter keys and started a new technology.

The new Canon P10-D printing calculator starts another new technology. Their dual-element printing system does away with the standard printing head which required a separate disc for each column. The Canon has only two discs—one with digits and the other with symbols.

The P10-D head weighs only 1/2 ounce compared to 31 ounces in a typical printing head. Its motor weighs only nine ounces—again much less than the heavier conventional motors required to drive larger heads. The Canon motor is smaller, lighter and more efficient because it moves less weight.

THE MOST EFFICIENT SYSTEM

The printing head is controlled by an LSI (large scale integrated circuit). As you press a key, a pulse is generated from this circuit and sent to the motor which does two things: 1) positions the two discs to print the numbers or symbols and 2) glides the numeric disc across the ten column width of the paper.

Conventional printers print from metal discs through thick fabric ribbon onto paper. The Canon system prints directly on paper so each impression is sharp, clear and easy to read. The synthetic polymer disc is first inked by a special cartridge before it prints. Each ink cartridge is easily replaceable. The cartridge lasts for more than 15 rolls of paper at a cost of 17¢ per roll—far less than any other system.

PLAIN PAPER PLUS

Using standard paper tape is only one of several advantages that make the Canon a truly spectacular value. Here are some other exciting new features:

Dual Power Operate the Canon from either your AC outlet or its built-in rechargeable batteries. It's totally portable, yet it also makes a handsome desk calculator.

Dual Display Just flip a switch and the 10-digit large green fluorescent display can be used with or without the printer.

Space-Age Styling Compare the sleek appearance of the Canon with any other printer. It's small enough to fit in your briefcase and large enough to use as a space-saving desk unit. It measures only 1 3/4" x 4 1/4" x 8 1/2", weighs only 24 ounces and the paper tucks into the body of the unit—perfect for travel.

Buffered Keyboard If you enter your prob-

lems faster than the printer can print them out, don't worry. The unit's memory stores your keystrokes and prints them out in rapid succession.

We have always looked at small printers as gimmicks—calculators that lack many important features. We were surprised with the Canon. It has features that far exceed most printers costing hundreds of dollars more.

The following is a list of those features: 10 digit capacity • full four-key memory • addition, subtraction, multiplication and division • percentage key • add-on and discount calculations • power and reciprocal calculations • repeat calculations • add-mode • switch for full-floating or second and third fixed decimal positions • round off or round down switch • paper tape advance.

There are other convenient features that make it perfect for people who spend hours at their calculators. There's a three-digit item counter that counts and prints out the number of entries while printing your total. The symbols on the right side of the tape tell you the nature of each entry. Even in its battery

operated position, you could print out more than half a roll of tape before the unit signals you that its batteries are low.

A NEW WAY TO BUY


JS&A offers you a new way to buy your 10-digit Canon P10-D. First we give you the opportunity to use one for 30 days. Carry it in your briefcase. Put it on your desk and see how handy it becomes and how little space it takes up. Check the paper tape and see how clear and easy-to-read it is. Bring it home and let the whole family use it.

Then, within 30 days, decide. If the Canon is not perfect for you, return it for a prompt and courteous refund. And if you do return it, not only will we still consider you one of our good customers, but we will also refund your \$2.50 postage, let you keep the paper tape, and thank you for giving us the opportunity of showing it to you. We couldn't be more positive about the quality and value of this incredible new product.

JS&A is America's largest single source of space-age products. We have been in business for over a decade—further assurance that your modest investment is well protected. Canon is one of the world's largest manufacturers of cameras and precision quality instruments and is highly respected as a quality manufacturer of electronic products.

The Canon costs only \$89.95 plus \$2.50 for postage and handling and includes a free roll of tape, one ink cartridge, rechargeable batteries and a power cord/charger. It's an incredible value thanks to its new technology. To order, send your check to the address below (Illinois residents add 5% sales tax) or credit card buyers may call our toll-free number.

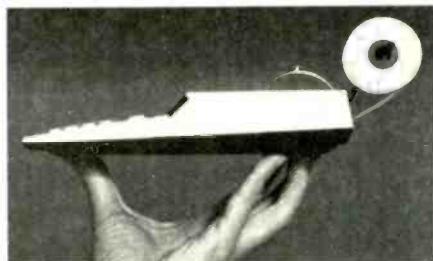Space-age technology has produced another major product breakthrough. Order your Canon P10-D at no obligation today.



The sleek appearance of the Canon P10-D makes it a handsome addition to any desk.



The direct-impression dual discs print cleaner and sharper on conventional paper tape.

JS&A NATIONAL SALES GROUP

Dept. RA One JS&A Plaza
Northbrook, Ill. 60062 (312) 564-9000
Call TOLL-FREE 800 323-6400
In Illinois Call (312) 498-6900

© JS&A Group, Inc., 1978

CIRCLE 29 ON FREE INFORMATION CARD

new design... new features...unique, time-tested principle!


Weller® controlled output soldering station

Model WTCPN. New convenience-features. Striking contemporary appearance. Completely new design. Now more than ever in a class by itself. Only Weller's advanced engineering could have improved on its own predecessor WTCPL Station, popular standard of the electronics industry.

- new heat shield for cool operator comfort
- new plug-in Iron design for zero down-time
- new integral tip-storage tray
- new larger sponge for easier tip cleaning
- improved, unitized rocker switch and neon indicator light
- new impact-resistant case

And add to these new features Weller's unique, proven, closed-loop, low-voltage circuit, with its "Interchangeable brains" in the tip . . . a ferromagnetic sensor that controls the temperature at 600, 700, or 800°F., protecting sensitive workpieces. To change temperatures, simply change tips with knurled thumb-screw. More than 50 options in configuration, tip size, reach, and temperature! Exclusive-process triple-plating prevents tip oxidation and "freezing".

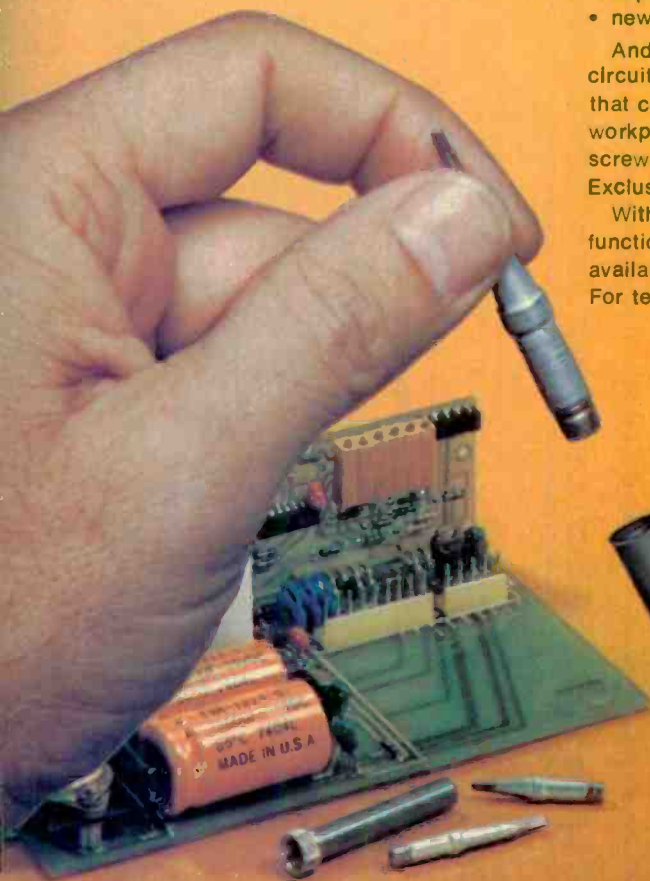With all these new features and exclusive principles, Model WTCPN is still all function . . . no frills! It's UL-listed and OSHA-compliant, of course. And now it's available at leading electronic distributors . . . coast-to-coast. See it there. For technical information, write on your letterhead.



The Cooper Group
Electronics Division

WELLER® • WISS® • XCELITE®

P.O. BOX 728, APEX, NORTH CAROLINA 27502, 919/362-7511

CIRCLE 5 ON FREE INFORMATION CARD

Radio-Electronics®

THE MAGAZINE FOR NEW IDEAS IN ELECTRONICS

Electronics publishers since 1908

APRIL 1978 Vol. 49 No. 4

BUILD ONE OF THESE

- 37 **Digital Tachometer For Car Or Boat**
2-digit LED display. Works with 2- or 4-cycle; 4-, 6- or 8-cylinder engines.
- 46 **Tuner Frequency Display**
Part II: Add on 4-digit display for easy reading of AM or FM tuned frequency.

JUST FOR EXPERIMENTERS

- 67 **Modifying Electronics Hardware**
Make your own low-cost custom hardware to suit your own needs—it's easy.
- 82 **Hobby Corner**
Part I of a special 2-part story on breadboarding and prototype systems.

COMPUTERS

- 45 **All About The S-100 Bus**
Identification, voltages and signals to interface a microcomputer.
- 51 **S-100 Directory**
Plug-ins for the bus.
- 80 **Z-80 Computer Corner**
Part VI: Completes our coverage of the Z-80.

IC DATA SHEET

- 74 **XR-2208 Operational Multiplier**
Specs and applications for nifty things you can build.

STEREO HIGH-FIDELITY

- 52 **New RIAA Equalization For Records**
Delivers more dynamic range, requires preamp changes you can do yourself.
- 59 **R-E Lab Tests Toshiba ST-910 FM Tuner**
It gets a "Perfect" for dial tuning accuracy.
- 61 **R-E Lab Tests U.S. Pioneer RT-707 Tape Deck**
It earns a "Superb" for 3¼-IPS wow and flutter.

GENERAL ELECTRONICS

- 4 **Looking Ahead**
Preview of tomorrow.
- 40 **Unusual Digital Clocks**
They tick, they chime, they swing—see how they work.
- 63 **Selecting DMM's**
What to look for when buying a digital multimeter. Get the most for your money.
- 72 **All About Audio Oscillators**
Everything you ever wanted to know about this valuable piece of test equipment.
- 79 **VTR Update**
Latest data on video tape recorders. Updates our February 1978 report.
- 84 **State Of Solid State**
Delta modulation IC decodes and encodes.

TELEVISION

- 86 **Jack Darr's Service Clinic**
Troubleshooting horizontal sweep circuits.
- 87 **Service Questions**
Jack Darr solves technician problems.

EQUIPMENT REPORTS


- 26 **Wilson Frequency Counter**
- 26 **Huntron Circuit Tester**
- 34 **Kager Soldering Pistol**
- 119 **Hickok CB Signal Generator**

DEPARTMENTS


- | | |
|-------------------------------------|----------------------------------|
| 156 Advertising Index | 113 New Books |
| 14 Advertising Sales Offices | 112 New Literature |
| 14 Editorial | 104 New Products |
| 16 Letters | 117 Next Month |
| 123 Market Center | 157 Readers' Service Card |
| 6 New & Timely | |

ON THE COVER

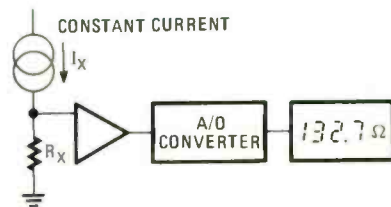Ever see electronic clocks with digital readouts equipped with pendulums and tick-tock sound and chimes? We did! And here's a story on how they operate. It's an exploration into interesting circuitry you may not have seen before. The story starts on page 40.



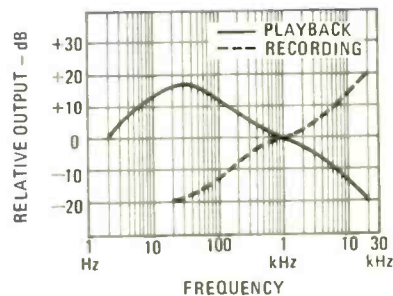OHMS CONVERTER IS A VITAL section of a digital multimeter. It's only one of many items to be considered when selecting a unit. For full selection data turn to page 83.



NEW RIAA EQUALIZATION CURVES. Note the rolloff in playback response in the low-frequency region. For full details turn to page 52.

Radio-Electronics, Published monthly by Gernsback Publications, Inc., 200 Park Avenue South, New York, NY 10003. Phone: 212-777-6400. Second-class postage paid at New York, NY and additional mailing offices. One-year subscription rate: U.S.A. and U.S. possessions, \$9.98, Canada, \$12.98. Other countries, \$14.98. Single copies \$1.00. © 1978 by Gernsback Publications, Inc. All rights reserved. Printed in U.S.A.

Subscription Service: Mail all subscription orders, changes, correspondence and Postmaster Notices of undelivered copies (Form 3579) to Radio-Electronics Subscription Service, Box 2520, Boulder, CO 80322.

A stamped self-addressed envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

As a service to readers, Radio-Electronics publishes available plans or information relating to newsworthy products, techniques and scientific and technological developments. Because of possible variances in the quality and condition of materials and workmanship used by readers, Radio-Electronics disclaims any responsibility for the safe and proper functioning of reader-built projects based upon or from plans or information published in this magazine.

looking ahead

Hi-fi TV: Or perhaps I should say higher-fi TV. Anyway, it's good news for people who are always complaining about television sound. The American Telephone & Telegraph Company announced it has converted its entire intercity network-television relay system to an audio bandwidth of 15,000 kHz from the former AM-type bandwidth of 5,000 kHz. AT&T did this by diplexing the audio signal within the television signal, eliminating the former practice of separating television picture from audio and carrying the latter on a standard telephone line. The diplex operation, in addition to producing better sound, is expected to save television networks considerable money by eliminating the need for extra audio lines for TV sound.

Late this year, the AT&T says it will be able to offer stereo sound. Whether it does so or not presumably will depend upon the outcome of an FCC proceeding on stereo sound for TV. Interestingly, the Public Broadcasting System was one of the prime movers originally in working with the AT&T through industry committees on improved TV sound—but it won't share in the new development. PBS will be doing its networking via space satellite, which already provides full 15-kHz sound bandwidth.

CCD color camera: The first complete solid-state tubeless color camera to be demonstrated and announced for production has been developed by RCA Electro-Optics & Devices. The camera uses three tiny silicon charge-coupled devices smaller than a postage stamp with a matrix of 512×320 elements, for a total of 163,840 elements. RCA claims it provides sensitivity and other characteristics comparable to those of a high-quality silicon vidicon camera. RCA said it would begin taking commercial orders for the camera in 1979. Initially, it will be offered as an industrial-institutional closed-circuit camera, but eventually it will be offered as a consumer-product accessory for home video recorders. The camera demonstrated weighed 3.6 pounds and measured $4 \times 5 \times 6$ inches, about the same size as its accessory zoom lens. Many companies have been developing CCD cameras, including Bell Telephone Laboratories, Fairchild Camera, General Electric, Eastman Kodak, Nippon Electric, Matsushita (Panasonic) and Sony, and you can expect many more announcements in the near future.

Longer-play videodisc: There's furious competition—at least in the press releases—among the various videodisc systems before the first player hits the market, and this competition recently has centered on playing time. First, RCA announced it had doubled the playing time of its capacitance disc to two hours. Then Matsushita announced in Japan a mechanical disc system which will play for two hours. Now, Philips and MCA Inc., sponsors of the optical system, have announced that they have developed a method to quadruple the playing time of their disc from the original 30 minutes to two hours. The original single-sided disc now has become a two-sided record. But to double the playing time per side, Philips and MCA use a principle which they call "variable angular velocity."

The original optical videodisc spun at a constant 1,800 rpm (for the American television system), storing a single TV frame per revolution. The new longer-play disc varies in playing time depending on the position of the stylus at any given time—so that the speed of the track being played is constant in relation to the laser-beam pickup. The disc, which plays from the inside out, starts at 1,800 RPM, but steadily decreases in speed until it's playing at about 600 RPM by the time the beam reaches the outside track at the end of the selection. Philips says its players will be able to accommodate both the variable-velocity discs and standard 1,800-RPM discs. The former will be known as continuous-play records and designed for such long programs as movies. Because the speed of turntable rotation isn't synchronous with the frame rate, these LP discs will lack some of the specific advantages of the optical system, such as freeze-frame, continually variable forwards and backwards motion, and precise location of a specific frame.

New video products: As the home TV set begins its metamorphosis from a single-purpose appliance to the multi-use home video center, new video products now are coming along rapidly. Projection TV, which in the past has generally been an area left to non-brandname assemblers, is now gaining adherents among major-brand manufacturers. Panasonic and Quasar, both subsidiaries of Matsushita, the world's largest TV maker, plan to market extremely bright and clear single-piece folding three-tube projection sets later this year. Mitsubishi will have a two-piece unit, strongly resembling Advent's projector, with shipments scheduled to start this spring. All three of these are expected to be quite high-priced. At the same time, a nationwide chain of retail stores specializing in projection TV is being formed, starting in California and moving east. It will offer the Projecto-Beam, which is like many other projectors using a single cathode-ray tube as a light source—except that it will be priced at \$750, in other words, about the same as a 25-inch color console—and the company's officials think this price break will be what propels giant-screen TV into the bigtime.

With the development of ultra-long-playing home video recorders (a six-hour cassette could come this year), the standard on-off VTR timer is no longer enough. Matsushita has developed an accessory programmer which will turn the recorder on and off and change channels, and is capable of being programmed for an entire week. Another such programmer, this one built into a television set, has been demonstrated by Sharp.

A few television sets, principally those made by GE, automatically adjust themselves to the vertical interval reference (VIR) used by broadcasters to keep color consistent. The GE circuit, which is discrete, uses 180 components and requires adjustment. Now Panasonic has announced development of VIR circuitry on an IC that is being offered to all TV set makers, and this could spread the idea of automatic VIR adjustment.

DAVID LACHENBRUCH
CONTRIBUTING EDITOR

New SIMPSON 5" Dual-Trace 15-MHz Scope

with triggered sweep. Reliable, versatile
and easy to use. It's your best scope buy.



MODEL 452 \$675

- For design, development and service of digital circuitry, communications, audio, TV equipment . . . in lab, shop or field.
- Differential vertical amplifier stages provide wide DC to 15 MHz bandwidth with smooth rolloff useable thru 27 MHz.
- Reliable integrated circuitry, all-solid-state (except CRT)
- Triggering — internal, external, TVV, TVH, VITS
- Automatically shifts between CHOP and ALTERNATE as you change sweep time.
- 24 nanosecond rise time
- Front-panel X-Y operation, dual matched vertical amplifiers.
- Displays CH A, B, A&B, A + B, A-B
- 0.5V peak-to-peak 1kHz square wave calibrator
- Voltage-calibrated vertical and horizontal inputs (eleven steps in 1-2-5 sequence)
- X5 magnification
- Human-engineered front panel controls

See Your Local Electronics Distributor or Write for Bulletin T-837.



SIMPSON ELECTRIC COMPANY


853 Dundee Avenue, Elgin, Illinois 60120
(312) 697-2260 • Cable SIMELCO • Telex 72-2416

CIRCLE 26 ON FREE INFORMATION CARD


KATY INDUSTRIES




Check logic including countdowns and PLL

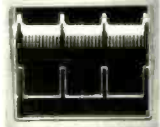


Display composite video and AGC pulse

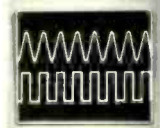

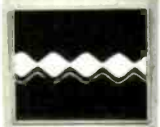Display op-amp input/output, A/D converter



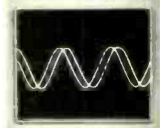27 MHz "CB" envelope and modulating signal



Check phase shift and distortion in amplifiers

CRT display terminals contribute to eye problems

Add "computer fatigue" to the list of eye complaints some observers feel are becoming more prevalent here and abroad as a result of the increased use of computer display terminals.

Dr. Jeryl Sparks, a Dallas, TX, optometrist, has a number of patients who work at local electronics firms. Even while conceding that soreness and swelling and blurred vision can result from any close-work situation, on-site observations at the firms in question have led him to the conclusion that CRT terminals are the main culprits.

Dot-matrix printouts are particularly hard on the eyes; they require a continual focusing adjustment. A better choice of printout would be light-(illuminated) characters on a dark screen. Other factors contributing to eye problems are glare and the lack of contrast between normal room brightness and the brightness of the screens.

Although these and similar observations are by no means conclusive and opinions vary among eye experts as to the validity of the diagnosis, some commonsense precautions can be taken to guard against potential hazards caused by CRT displays: look up from the work occasionally, take more breaks and blink—full blinking allows oxygen to reach the eyes, thus reducing swelling and soreness.

Cosmic rays believed to cause lightning zigzags

For some time, scientists have questioned the possible link between cosmic radiation and certain kinds of lightning behavior. At a recent meeting of the American Geophysical Union in San Francisco, Dr. James W. Follin of the Applied Physics Laboratory of Johns Hopkins University, presented a paper that bears out the conclusion that without cosmic rays there would be no lightning at all, since there is not enough electrical potential in a thundercloud to generate it.

Dr. Bernard Vonnegut, an authority on atmospheric electricity, and other scientists have theorized that the connection between cosmic radiation and lightning could be one of the ways in which sunspots affect the earth's weather. Cosmic rays are composed of highly charged particles, chiefly protons, that are released by the sun and travel at almost the speed of light. When there are many sunspots, the magnetic fields released from the sun's surface protect the earth from the majority of the cosmic rays; but the sun simultaneously increases its output of similar radiation at much lower energy levels.


Those cosmic rays with very high energy, when they strike the upper atmosphere,

create cascades of atomic fragments that are then released into our atmosphere as a "cosmic shower." This shower, when it connects with a thunderhead, knocks free electrons from nitrogen and oxygen atoms in the process known as ionization. The electrical charge already present in the cloud is sufficient to accelerate the released nitrogen and oxygen electrons to create a lightning stroke, known as a "step leader." This stroke then travels the path of least resistance to earth, following a series of steps, through segments of air ionized by secondary atomic ray atoms known as muons. Approximately 50 yards from the ground, an electrical discharge jumps up to join the leader stroke, creating a zigzag pattern. The circuit is complete and the return stroke follows the same zigzag path to the sky. This is the first lightning stroke one observes during a storm; the other strokes follow in such quick succession they appear as one.

Computer-operated disc-mastering system improves LP quality

A new disc-mastering system developed by CBS Records called *DISComputer* uses computer technology to improve both the sound and running time of LP records. The system cuts down on distortion and mistracking and contributes significantly to improving the signal-to-noise ratio. The records cut by the new system are also actually louder—by some 2-dB to 5-dB—than those cut by conventional methods.

The computer directs the lathe (with the

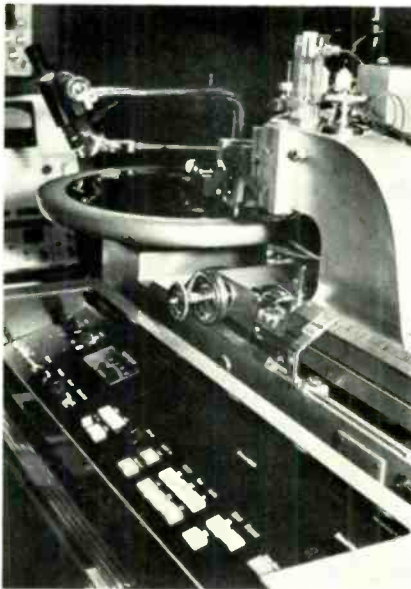


CBS DISCOMPUTER DISC-MASTERING SYSTEM combines computer technology with conventional lathes to cut LP's with improved sound quality and longer playing levels.

stylus) to cut grooves according to prerecorded tape sounds and automatically adjusts the size of the groove to accommodate as much sound as possible. It also controls each groove's relationship to the adjacent grooves by providing the correct amount of space. And because more grooves can be fitted into the same space, the record side can be extended up to five minutes longer in some instances.

The system cost CBS more than \$500,000 to develop, and it is at present estimated at \$250,000 per unit. The *DIS-Computer* mastering systems are currently being used at CBS studios in New York, Nashville, and in some studios abroad.

Bell microwave-beam technique could increase satellite capacity

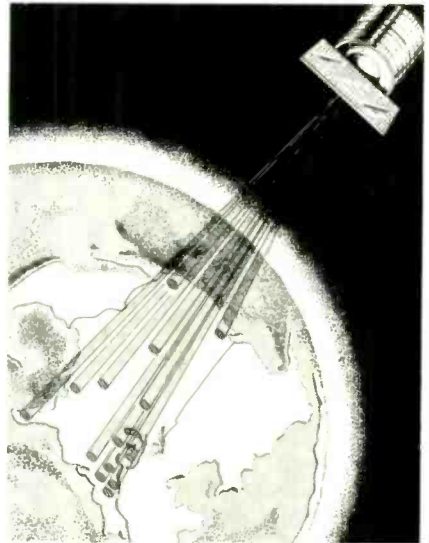Researchers at Bell Laboratories have advanced a totally new concept in satellite




BELL LABS' SCANNING/SPOT BEAM CONCEPT uses about a dozen fixed beams and a narrow, focused microwave beam that would sweep across the U.S., thus increasing satellites' transmission capacity.

telecommunications that is expected to more than double the satellites' present transmission capacity. The scanning/spot beam technique uses narrow microwave beams that are broken into pulses lasting only minute fractions of a second to sweep the U.S. in much the same way as an electron beam sweeps a TV screen. Some fixed beams would be reserved for more densely populated urban areas.

The smaller beam size would raise the transmission capacity of each satellite from 15,000 to 50,000 phone calls. This substantial increase in the number of transmissions would be partly effected by transmission frequency reuse, at present feasible only in

continued on page 12

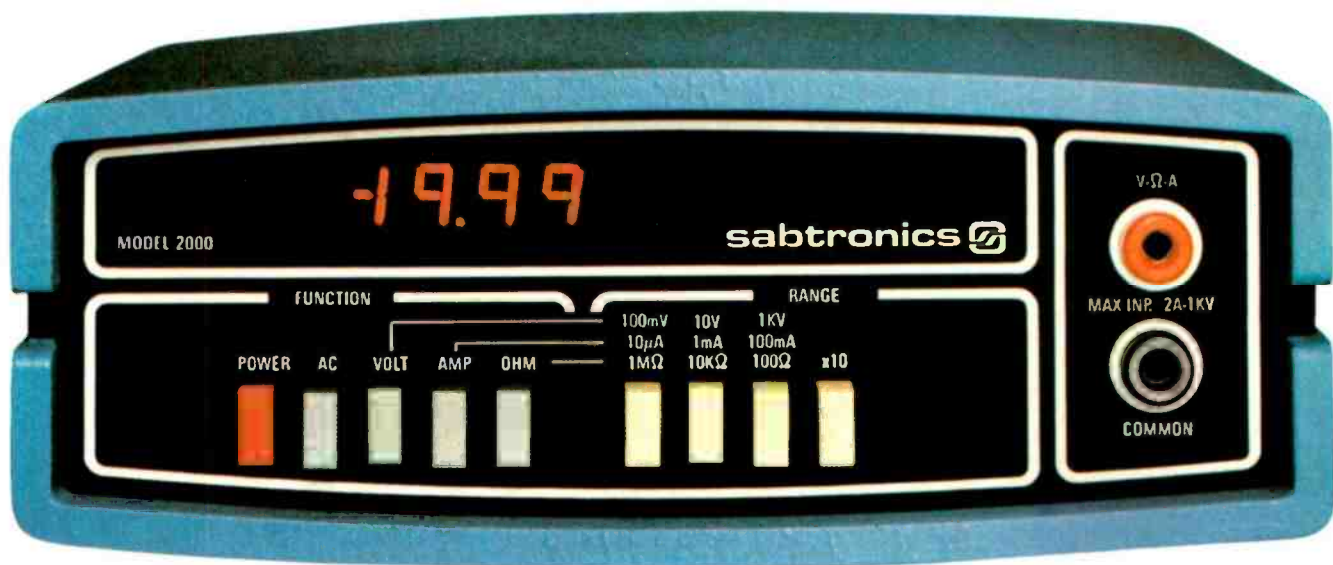Uncompromising performance. Incredible price. A professional 3½ digit DMM Kit for less than \$70.



Incredible? True! Professionals and hobbyists alike are believers in this Sabtronics 2000, the only portable/bench DMM which offers such uncompromising performance at the astonishingly low price of \$69.95.

Uncompromising performance you'd expect only from a specialist in digital technology such as Sabtronics: Basic DCV accuracy of 0.1% ± 1 digit; 5 functions giving 28 ranges; readings to ±1999 with 100% overrange; overrange indication; input overload protection; automatic polarity; and automatic zeroing.

The low price of \$69.95? Simple: The Model 2000 is all solid-state, incorporating a single LSI circuit and high-quality components. You assemble it yourself, using our clear, easy-to-follow, step-by-step assembly manual. Kit is complete, including a high-impact case.

Now you too can have it! A professional-quality, 3½ digit Sabtronics Model 2000 DMM kit for only \$69.95. If you don't have one in your lab, use the coupon below to order NOW.

BRIEF SPECIFICATIONS:

DC volts in 5 ranges: 100 µV to 1 kV · AC volts in 5 ranges: 100 µV to 1 kV · DC current in 6 ranges: 100 nA to 2 A · AC current in 6 ranges: 100 nA to 2 A · Resistance: 0.1 Ω to 20 MΩ in 6 ranges · AC frequency response: 40 Hz to 50 kHz · Display: 0.36" (9.1 mm) 7-segment LED · Input impedance: 10 MΩ · Size: 8" W x 6.5" D x 3" H (203 x 165 x 76 mm) · Power requirement: 4 "C" cells (not included).

GUARANTEE:

Examine the 2000 DMM kit for 10 days. If not completely satisfied, return unassembled for full refund of purchase price. (Less shipping and handling)

Use your Master Charge or Visa.
To order by phone call: (214) 783-0994



Made in U.S.A.

To: Sabtronics International, Inc.
13426 Floyd Circle, Dallas, TX 75243

RE 4

Please send me _____ Sabtronics Model 2000 DMM kit(s)
at \$69.95 each..... \$ _____
Shipping and handling, \$5.00 per unit* \$ _____
Texas Residents Add Sales Tax \$ _____
TOTAL enclosed \$ _____

Name _____

Street _____

City _____

State _____ Zip _____

*USA only. Canada \$6.50. All other countries, \$10.00 (surface mail)

sabtronics 
INTERNATIONAL INC.

13426 Floyd Circle • Dallas, Texas 75243

25 million reasons into NRI training in CB and

The CB boom means big opportunities for qualified technicians... learn at home in your spare time.


There are more than 25 million CB radios out there, millions more two-way radios, walkie-talkies, and other communications apparatus in use by business and industry, government, police and fire departments. And all of this equipment demands qualified technicians to maintain and repair it. In addition to knowing what you're doing, you must have an FCC Radiotelephone License to service most of it. NRI can help you get both... the training and the license.

Learn on your own 2-meter, digitally synthesized VHF transceiver or 40-channel CB.

With NRI, you learn by doing. You use the NRI Discovery Lab™ to build and test a whole series of typical communications circuits, even assemble



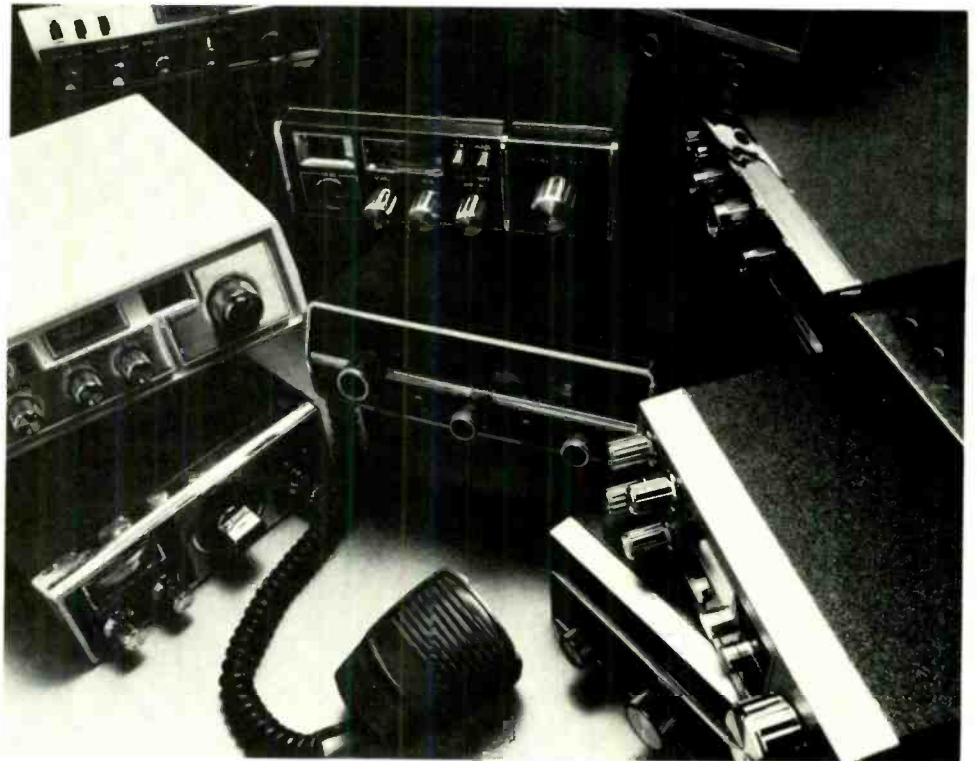Some designed-for-learning equipment you get



your own professional transistorized volt-ohm meter and a CMOS digital frequency counter. You test various types of antennas to gain a firm understanding of broadcasting principles. And finally, you assemble your own 2-meter transceiver for experiments in troubleshooting and servicing. Then, if you want to go on the air, we'll help you get your amateur license. As an alternate choice, you may elect to receive and experiment with a 40-channel CB to get more experience in this booming area.

™Trademark McGraw-Hill

You learn in your own home, in your spare time, at your convenience. NRI's bite-size lessons and carefully matched practical experiments combine theory and bench work to give you the most effective training for your money. No need to quit your job or take night classes, you move ahead at the pace that suits you best.

NRI guarantees your FCC license.

The law requires that technicians hold an FCC Radiotelephone License to work on broadcast equipment. NRI training in Complete Communications Electronics or our CB Radio Specialist course is carefully designed to give you the special coaching so helpful in passing FCC license exams. If you fail to pass the FCC examination for radiotelephone license after graduating, *NRI will refund your tuition in full.* The money-back agreement is valid for six months after completion of your course.

Send for free catalog. No salesman will call.

Find out all the facts about NRI's Communications or CB course. Or look into other areas of opportunity like TV and audio servicing, digital computer electronics, mobile communications, and more. Mail the postage-paid card today... there are more than 25 million good reasons why.

why you should look Communications Servicing.

Or get into TV and audio servicing

NRI can train you at home to service TV equipment and audio systems. Choose from five courses that go up to our 48-lesson Master Color TV/Audio Course. With it you get 14 kits for practical bench training and demonstrations, including NRI's exclusive, designed-for-learning, 25" diagonal solid state color TV, 4-channel audio system complete with speakers, and professional instruments you build and use for learning and earning. It's proven, effective training that's helped thousands of pros already. And it's the best value offered in the field. NRI's bite-size lessons speed learning, exclusive




"Power-On" training makes it real. Send card for free catalog.

Learn computer electronics

NRI trains you at home on a real digital computer.

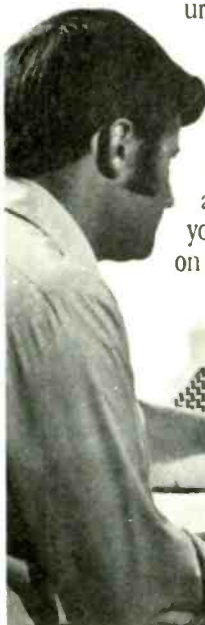Qualified technicians are urgently needed for careers in the new field of computer and digital electronics... and NRI trains you at home on the real thing.



As part of your training, you actually assemble a working digital computer with expanded memory, define and flow chart programs, code your program, store it along with data in the memory bank. It's just one of the 10 hands-on training kits you receive. You also build and use your own TVOM; experiment with NRI's exclusive electronics lab. It's the quickest and best way to learn and start a new career in troubleshooting digital computers. Send the card today.

NRI instructor/engineers

Each NRI student is assigned his own course instructor. He's there to help you over any rough spots, explain problems, and give you the advice you need as you progress toward your future. And he knows what he's talking about, because he was more than likely involved in the design of your course or some of the NRI equipment you use. NRI instructors are practical, experienced people who really know their field and do their best to pass their knowledge on to you.

You get more for your money from NRI.

NRI employs no salesmen, pays no commissions. We pass the savings on to you in reduced tuition, top-quality professional equipment, and reliable testing instruments necessary for a successful career. You can pay hundreds of dollars more at other schools, but you can't get better training.

Free catalog, no salesman will call.

Get your free catalog and discover why NRI is the leader in home technical training with over a million students, over 60 years experience in helping people build new careers. Mail the card today and get started on your new future. If card has been removed, write to:



NRI SCHOOLS

McGraw Hill Center
for Continuing Education
3939 Wisconsin Avenue
Washington, D.C. 20016

widely separated geographic areas. Raising the number of frequencies would also mean there would be less interference from other microwave transmissions. For instance, at present both terrestrial and satellite communications use 4- and 5-gigahertz channels; the scanning/spot beam satellite would transmit over 11- and 14-gigahertz channels.

Smaller (about 10 feet in diameter), less costly antennas could be used in urban areas, rather than in less developed regions as is present practice. The antennas could be installed on rooftops, thus permitting convenient access by businesses.

The concept, if developed, could go far in reducing the cost of multiple video conferencing and in increasing high-speed data transmission, while also lessening the cost of tie-lines and private communications networks extensively used by corporations.

Magnuson-Moss Warranty Act offers less consumer protection

A survey conducted for the FTC by the National Association of Service Managers (NASM) and sent to 83 manufacturers indicates that the 1975 Magnuson-Moss Warranty Act has delivered less than was expected in terms of consumer warranty protection. Originally intended to simplify matters for the consumer by outlining minimum warranty standards and improving warranty protection, the Act has served only to confuse manufacturers (who are not sure what they must do to comply with its provisions) and to limit the amount of protection consumers can expect.


The NASM survey showed that two-thirds of the manufacturers who have over \$1 million in gross sales (producing such items as appliances, furnaces, automotive parts, stereos, TV's, CB's, etc.) have switched from full to limited warranties. This means that consumers are now deprived of full warranty protection on their major purchases. Before the Act was passed, these companies tended to be the main providers of full warranties. Thirty-six of the 83 companies indicated they had changed over from full to limited warranties as a *direct result* of the Magnuson-Moss Act.

Announcing the result of the survey, NASM executive director Marvin Lurie said, "We now have solid evidence that the Act has reduced warranty coverage in major sectors of the consumer marketplace . . . We hope that the data NASM has provided to the FTC will permit rapid correction of the situation."

Decoder system for traffic information broadcasts

When you are driving, especially long distances, it is a great convenience to be

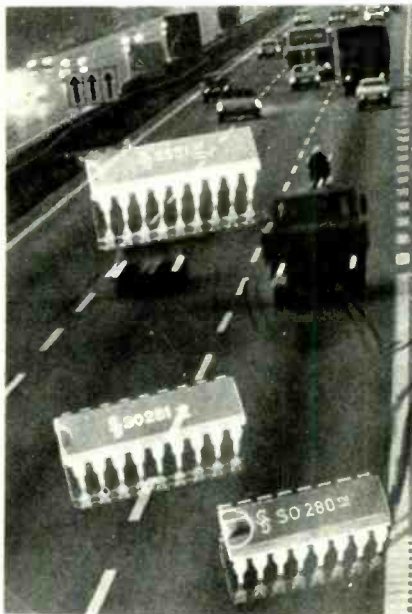able to receive periodic traffic information on your car radio. However, when you drive at high speed, the broadcast frequencies change and reception may not always be at optimum.



SIEMENS DECODER SYSTEM uses three IC's to automatically select and tune to traffic information stations.

Siemens AG of Germany has designed a decoder system containing three different IC's that can automatically select and tune to a traffic information station. The ARI decoder system (presently being used in Germany) is based on two special broadcast frequencies that are used by every traffic information station but cannot be heard on any other station: A 57-kHz pilot tone that lets you know you are tuned to a traffic information station and a 125-Hz frequency that is used for the actual broadcast.

The two bipolar S280 and S281 IC's of the ARI decoder respond to the 57-kHz and 125-Hz frequencies; IC S280 and IC S551 recognize the traffic service station by the pilot frequency; and IC S551 also controls the visual indicator, a green LED that tells you you have tuned in correctly. In operation, the system makes sure that the traffic announcements that interrupt regular programming are audible even if a cassette tape recorder is playing simultaneously. And even if the station volume has been lowered, the circuit assures the traffic announcement will come through loud and clear.

The system also warns you when you leave the area so that you can tune into a new station. The decoder drives an automatic station-seeking device until the traf-

fic information program is restored. An optional IC (S552) is also available to identify different travel regions.

Microcomputers to improve U.S. Postal Service

Whenever the U.S. Postal Service must determine when, where and how to shift personnel to take care of special workload requirements, it must generally rely on on-line analyses, which generally arrive too late to be much use, or else keep a perpetual sharp eye out for potential bottlenecks in the system.

To alleviate this problem and, hopefully, maximize the efficiency of Postal Service operations, a pilot data-gathering system built by Applied Computer Research Company has been installed in a Sacramento, CA, facility. This monitoring system uses microprocessors to interface with conventional electromechanical equipment such as letter sorters and postage-cancelling machines. The microcomputers used in the system are Intel's SBC 80/04 and Zilog's Z-80. The Intel microcomputer board interfaces with the actual equipment, while the Z-80's handle system control. The Z-80, with its 4-MHz clock, hooks up to an on-site minicomputer and interfaces with the Postal Service Data System, a nationwide communications link, which contains all time and attendance records of the Postal System's entire workforce.

It is hoped that the monitoring system will provide postal supervisors with enough information to be able to handle personnel shifts quickly and efficiently. While the Sacramento office is about the smallest postal facility that could expect to receive such a system, larger urban areas, such as Los Angeles and New York, that handle large amounts of mail could benefit from its installation.

FCC proposes eliminating Third Class Operator's license

The Federal Communications Commission's proposed reorganization of radio-telephone operator licensing procedures advises eliminating the Third Class Operator's license. The National Radio Broadcasters Association supports this proposal, citing the fact that in the past the Third Class Operator's exam was not really necessary for a broadcaster to function effectively . . . all that was needed was for the FCC to grant a one-year provisional permit.

The new rules would only require that technicians engaged in installing, repairing or servicing broadcast equipment be *certified* by the FCC—no exam would be needed. If any of the equipment does not fulfill the specifications required by the license, the technician must inform the licensee.

R-E



NLS LEADS AGAIN!!

THE NEW MS-15 MINISCOPE

PORTABLE
BATTERY OPERATED
15 MEGAHERTZ
OSCILLOSCOPE



FEATURES

- Automatic and line sync modes.
- Power consumption less than 15W.
- Vertical Gain — 0.01 to 50 volts/div — 12 settings.
- Weight is only 3 pounds.

- 15 megahertz bandwidth.
- External and internal trigger.
- Time Base — 0.1 microseconds to 0.5 Sec/div — 21 settings.
- Battery or line operation.

From the originator of the Digital Voltmeter, Non-Linear Systems comes the MS-15 Miniscope. It is a fine electronic instrument with a great deal of measuring capability and excellent accuracy. Its design is modern, utilizing the latest in low-powered integrated circuits, and it is packaged into the smallest practical size. The instrument fits into many briefcases and tool boxes with room to spare. Operating characteristics have been chosen so that the MS-15 will make all of the measurements needed in servicing most electronic equipment. It is field-portable so its use is not restricted to the bench.

SPECIFICATIONS:

Y Axis
Vertical Input: x1-10mV/div to 10V/div in four ranges, each continuously variable.
x2-20mV/div to 20V/div in four ranges, each continuously variable.
x5-50mV/div to 50V/div in four ranges, each continuously variable.
Accuracy is 3%.

Input Impedance: 1M ohm shunted by 50 pF

Input Voltage: 350 volts peak

Bandwidth (3 db points): DC/DC to 15 MHz; AC 5 Hz to 15 MHz

Internal Calibrator: 1.0V (±5%) peak-to-peak square wave at 10-20 kHz
4 div Y by 5 div X; 1 div = 0.25 inch. Viewing area: 1.1" H x 1.35" W.

Graticule:

X Axis
Horizontal Input: DC to 200 kHz
Bandwidth (3 db points): 1M ohm shunted by 50 pF
1V/div, 100V peak maximum input.

Input Impedance: x1-0.5uS/div to 500 uS/div, x2-0.5-0.1mS/div to 200 uS/div
x5-0.5-0.5mS/div to 500 mS/div, x5, mS-0.5mS/div to 100 mS/div

Sensitivity: x2, mS-0.2mS/div to 200 mS/div

Time Base: all in four ranges, each continuously variable. (Range increments are 1, 1, 10, 100.) With vernier in full clockwise position, calibrated time measurements are possible. Accuracy is 3%.

Triggering
Internal: Sweep triggered from internal trigger source.
Automatic: Trigger source is internal calibrator frequency. To be used if there is no other trigger source available to synchronize the sweep.
Trigger is derived from line frequency when using the battery charger.
Selects sync to positive- or negative-going wavetform.
Less than one division.
Controls function as for internal triggering.

Line: Three self-contained lead acid "D" cells.
Slope: Will run indefinitely but not reach full
Sensitivity: Typically 4 hours.
External: Charge.

Power
Batteries: Three self-contained lead acid "D" cells.
Operating Time: Typically 4 hours.
Charging Time: Scope Operating: Will run indefinitely but not reach full charge.

Non-operating: Sixteen hours
External Power: Battery charger 115 vac (220 vac on request), 50-60MHz, less than 15 watts.
3 1/2" H x 6 1/4" W x 8 0" D.
Three pounds.

Dimensions: Tilt stand, battery charger, input cable and miniature banana plugs (4).
Weight: Leather carrying case and 10-1 attenuating probe, 10M ohm input.
Accessories: One year parts and labor.

Options: One year parts and labor.

Warranty: MS-15 with Rechargeable Batteries and Charger \$289.00

Leather Carrying Case

The leather case has 2 separate compartments. One to hold the scope, the other to hold the charger, probe, shoulder strap, etc. The case can be worn on the belt, or over the neck. The snaps used on the case are "one way", thus accidental striking of the case against an object will not undo the snaps or let it be pulled off your belt.

41-140 \$30.00

Probe

10 to 1 probe with 10 megohm input. Probe uses spring hook tip for sure connection. Compensation network is located at the connector rather than at the probe, so as to keep size and weight to a minimum.

41-141 \$24.50

FREE PROBE
Just send or mention this COUPON and RADIO ELECTRONICS MAGAZINE and receive 41-141 PROBE FREE with purchase of MS-15 MINISCOPE.

CIRCLE 28 ON FREE INFORMATION CARD

PRIORITY ONE ELECTRONICS
10031 Woodley Ave. Sepulveda CA. 91343
Terms: VISA, MC, BAC checks. Money Order. C.O.D. U.S. Funds only. CA residents add 6% sales tax. Minimum order \$10.00. Orders less than \$15.00 include 10% shipping and handling, excess refunded. Just in case please include your phone no. "Sorry, no over the counter sales!" phone orders welcome (213) 893-8202
Send for our latest brochure.

PRIORITY ONE ELECTRONICS is a division of...
OSM and Institutional inquiries invited
Good thru June 1978

The Real Energy Crisis

Low-cost energy is the problem . . . not a shortage of energy itself.

Sure, at some point in time we will run out of oil, we will run out of natural gas, we will run out of coal. But there are plenty of other energy sources around. They include nuclear, solar, water power, wind, and who knows how many other sources that haven't been discovered yet.

The rising cost of fuel of all kinds is placing quite a hardship on most of us, but it does have a silver lining. It will result in the development of *practical* alternate supplies of energy; because it will pay, be profitable, to develop other sources.

You can buy solar cells today that have an efficiency of 18%, but we've got to get that up to 50%. We have solar hot-water heating systems today that work, but are expensive. What we need is a ruling requiring the installation of such a system in every new home. That would accomplish two aims—get a lot of energy-saving systems into use; and raise the volume of production so the cost of each system is reduced, making it more economical for people with older homes to add one.

Radio-Electronics is interested in our readers' ideas for alternate energy sources. Send me your thoughts. Include diagrams; photos if you have them. We'll publish the more interesting ones . . . remember, if it's built around electronic circuitry, it has an edge.


LARRY STECKLER
Editor

Radio-Electronics®

Hugo Gernsback (1884-1967) founder

M. Harvey Gernsback, editor-in-chief and publisher

Larry Steckler, KTX-3644, CET, editor

Arthur Kleiman, KTZ-3288,
managing editor

Robert F. Scott, CET, W2PWG,
KXX-8533, technical editor

Sonia Greenbaum, copy editor

Jack Darr, CET service editor

Leonard Feldman
contributing high-fidelity editor

Karl Savon, semiconductor editor

David Lachenbruch, contributing editor

Earl "Doc" Savage, K4SDS, hobby editor

Vincent P. Ciconia, production manager

Harriet I. Matysko, circulation director

Sheila Wertling, circulation assistant

Arline R. Bailey, advertising coordinator

Cover design by Louis G. Rubsamen

Cover photo by Michael Wilson

Radio Electronics is a member of the *Institute of High Fidelity* and is indexed in *Applied Science & Technology Index* and *Readers Guide to Periodical Literature*.

Gernsback Publications, Inc.
200 Park Ave. S., New York, NY 10003

(212) 777-6400

President: M. Harvey Gernsback

Vice President: Larry Steckler

Treasurer: Carol A. Gernsback

Secretary: Bertina Baer

ADVERTISING SALES

Paul McGinnis

Director of Marketing

EAST

Stanley Levitan

Radio-Electronics

200 Park Ave. South

New York, NY 10003

(212) 777-6400

MIDWEST/Texas/Arkansas/Okla.

Ralph Bergen

The Ralph Bergen Co.

6319 N. Central Ave.

Chicago, IL 60646

(312) 792-3646

PACIFIC COAST

Mountain States

Jay Eisenberg

J.E. Publishers Representative Co.,

8732 Sunset Blvd.,

4th Floor,

Los Angeles, CA 90069

(213) 659-3810

Sales Mart Building

1485 Bayshore Blvd., Box 140

San Francisco, CA 94124

(415) 467-0125

SOUTHEAST

J.E. Publishers Representative Co.,

214-387-2424



VERSATILITY - UNMATCHED

*by any other
micro-computer
system*



COMPUTERS
TERMINALS
PRINTERS
SOFTWARE

TAPE SYSTEMS
DISK SYSTEMS
GRAPHICS
PROM PROGRAMMER

MEMORY - 4K, 8K, 16K & 32K
PROGRAMMABLE REAL TIME CLOCK
CALCULATOR INTERFACE
A - D CONVERTER

Write, or circle our reader reply number for a catalog describing our complete line of computer hardware and software.

NOW AVAILABLE IN BOTH KIT AND ASSEMBLED FORM.



SOUTHWEST TECHNICAL PRODUCTS CORPORATION
219 W. RHAPSODY
SAN ANTONIO, TEXAS 78216

CIRCLE 36 ON FREE INFORMATION CARD

letters

AN OPEN LETTER TO THE PRESIDENT

Dear Mr. President:

We of the Maryland Electronics and Television Association feel it has become imperative at this time to denounce the foreign import practices allowed for too long by our government. We strongly urge that immediate steps be taken to cause a reversal in this trend of "overseas extortion."

The television industry, from the manufacturers to the technicians, has been feeling the impact of excessively low-price electronic equipment. In 1977, color TV retail prices are no higher, and in many cases lower, than in 1963, this being the only product that comes to mind that has not increased with the inflationary trend of these same years. The price of automobiles, for example, has increased 40% in the last five years alone.

True, prices on television sets may be increased by strong governmental action against importing foreign sets, but it would be more costly for consumers to pay higher

unemployment and welfare benefits to more unemployed, while ours decreases.

In recent years, Motorola sold its TV division to foreign interests, as did Magnavox. More and more, foreign countries' employment rates increase, while ours decreases.

We feel that if the government does nothing to combat this serious problem, organizations such as ours (and there are many) must take the initiative in refusing to sell or service foreign-made products. Of course, this would create a hardship on consumers who own such equipment, but we may be left with no alternative.

We appeal to you, Mr. President, to give this subject your earnest attention, and move to restore faith in our industry and system before we reach a point of no return.

We await your written response to this matter, which is of grave importance both to the Maryland Electronics and Television Association and the entire electronics industry.

EARL REDMAN, President
META Board of Directors

CB TEST GEAR

I am very appreciative of the special feature "What You Need to Know About CB Test Gear" by Forest Belt in your November 1977 issue.

I was especially impressed with Mr. Belt's treatment of the test bench in the last section entitled "Test Systems," in which he gave a very well-defined method of setting up our own comprehensive test bench for servicing radio transceivers.

Please include more articles of this type in future issues as I am sure that I, along with the majority of other readers, will receive great benefit from them.

BYRON McCABE
Tucson, AZ

PARTS HARD TO FIND

I have noted recently some editorial comment in electronics magazines with respect to the trouble people have in construction projects due often to substituting other than specified parts. I would like to point out some problems in this regard.

continued on page 22

A P BROUGHT YOU SOLDERLESS BREADBOARDING. NOW WE'VE ADDED POWER.

Introducing POWERACE, the new line of ACE All Circuit Evaluators.

POWERACE—for fast, solderless circuit building and testing. All models will accept all DIP sizes—plus TO-5's and discretes with leads to .032" diameter. POWERACE 101 has a variable 5-15 VDC 600 ma Power supply. POWERACE 102 features a fixed 5VDC 1 amp power supply; and POWERACE 103 has a fixed 5VDC 750 ma power supply, a fixed +15VDC 250 ma power supply, and a fixed -15VDC power supply at 250 ma.

Order from your A P distributor today. For the name of the distributor nearest you call Toll-Free 800-321-966E.

Faster and Easier is what we're all about.



AP PRODUCTS INCORPORATED

Box 110 • 72 Corwin Drive, Painesville OH 44077
(216) 354-2101 TWX: 810-425-2250



MODEL #103
\$124.95

MODEL #101 \$84.95

MODEL #102
\$114.95

CIRCLE 16 ON FREE INFORMATION CARD

Compare features. Compare prices. Philips is the logical choice.



Feature for feature, dollar for dollar, you get more for your money in a Philips scope. These four oscilloscopes, designed for use in service, production or education, are made by Philips to the same quality standards as more sophisticated Philips scopes used in laboratories all over the world. They are light and easy to carry with all controls carefully placed for ease and minimum human errors in operation. Their design and quality of components are your assurance of minimum down time and repair costs.

25MHz/2mV Dual Trace oscilloscope-PM3212

Triggering includes AC, DC, auto and composite mode. Double insulated power supply eliminates ground loop problems and measurement inaccuracies caused by hum or other spurious signals. The most versatile instrument in its price range. Size, weight and function capability make it ideal for field or lab use.

PM 3212-25MHz Dual Trace Scope-\$1155.00*

New, compact 15MHz/2mV oscilloscope-PM3211

Lightweight, compact dimensions, big 8 x 10 cm screen. Comprehensive triggering and display facilities not available in competitively-priced scopes.



Test & Measuring
Instruments

Same double insulated power supply as PM 3212.
PM 3211-15MHz Compact Dual Trace Scope-
only \$875.00*

15MHz/2mV Single and Dual Trace oscilloscopes

PM 3225 and PM 3225 Automatic triggering provides stable displays under almost any signal condition.

PM 3225-15 MHz Single Trace Scope-\$625.00*

PM 3226-Dual Trace 15 MHz Scope-\$820.00*

*U.S. Domestic Price only. All prices include probes and protective front cover.

For immediate information, use our toll-free Hotline number: (800) 631-7172. New Jersey residents, please call collect (201) 529-3800. Or contact Philips Test & Measuring Instruments, Inc.

In the U.S.:
85 McKee Drive
Mahwah, New Jersey 07430
Tel. (201) 529-3800

In Canada:
5 Leswyn Road
Toronto, Canada M6A 1K2
Tel. (416) 789-7188

PHILIPS

At CIE, you get electronics career training from specialists.

If you're interested in learning how to fix air conditioners, service cars or install heating systems – talk to some other school. But if you're serious about electronics, come to CIE – The Electronics Specialists.

John E. Cunningham

**Special Projects Director
Cleveland Institute of Electronics**



My father always told me that there were certain advantages to putting all your eggs in one basket. "John," he said, "learn to do one important thing better than anyone else, and you'll always be in demand."

I believe he was right. Today is the age of specialization. And I think that's a very good thing.

Consider doctors. You wouldn't expect your family doctor to perform open heart surgery or your dentist to set a broken bone, either. Would you?

For these things, you'd want a specialist. And you'd trust him. Because you'd know if he weren't any good, he'd be out of business.

Why trust your education and career future to anything less than a specialist?

You shouldn't. And you certainly don't have to.

FACT: CIE is the largest independent home study school in the world that specializes exclusively in electronics.

We have to be good at it because we put all our eggs in one basket: electronics. If we hadn't done a good job, we'd have closed our doors long ago.

Specialists aren't for everyone.

I'll tell it to you straight. If you think electronics would make a nice hobby, check with other schools.

But if you think you have the cool — and want the training it takes — to make sure that a sound blackout during a prime time TV show will be corrected in seconds — then answer this ad. You'll probably find CIE has a course that's just right for you!

At CIE, we combine theory and practice. You learn the best of both.

Learning electronics is a lot more than memorizing a laundry list of facts about circuits and transistors. Electronics is interesting because it's based on some fairly recent scientific discoveries. It's built on ideas. So, look for a program that starts with ideas — and builds on them.

That's what happens with CIE's Auto-Programmed® Lessons. Each lesson uses world-famous "programmed learning" methods to teach you important principles. You explore them, master them completely... before you start to apply them!

But beyond theory, some of our courses come fully equipped with the electronics gear to actually let you perform hundreds of checking, testing and analyzing projects.

In fact, depending on the course you take, you'll do most of the basic things professionals do every day — things like servicing a beauty of a Zenith color TV set... or studying a variety of screen display patterns with the help of a color bar generator.

Plus there's a professional quality oscilloscope you build and use to "see" and "read" the characteristic waveform patterns of electronic equipment.

You work with experienced specialists.

When you send us a completed lesson, you can be sure it will be reviewed and graded by a trained electronics instructor, backed by a team of technical specialists. If you need specialized help, you get it fast... in writing from the faculty specialists best qualified to handle your question.

People who have known us a long time, think of us as the "FCC License School."

We don't mind. We have a fine record of preparing people to take... and pass... the government-administered FCC License exams. In fact, in continuing surveys nearly 4 out of 5 of our graduates who take

the exams get their Licenses. You may already know that an FCC License is needed for some careers in electronics — and it can be a valuable credential anytime.

Find out more! Mail this card for your FREE CATALOG today!

If the card is gone, cut out and mail the coupon.

I'll send you a copy of CIE's FREE school catalog, along with a complete package of independent home study information.

For your convenience, I'll try to arrange for a CIE representative to contact you to answer any questions you may have.

Remember, if you are serious about learning electronics... or building upon your present skills, your best bet is to go with the electronics specialists — CIE. Mail the card or coupon today or write CIE (and mention the name and date of this magazine), 1776 East 17th Street, Cleveland, Ohio 44114.



Patterns shown on TV and oscilloscope screens are simulated.

CIE Cleveland Institute of Electronics, Inc.
1776 East 17th Street, Cleveland, Ohio 44114

Accredited Member National Home Study Council

YES... John, I want to learn from the specialists in electronics — CIE. Send me my FREE CIE school catalog — including details about troubleshooting courses — plus my FREE package of home study information.

RE-32

Print Name _____

Address _____ Apt. _____

City _____

State _____ Zip _____

Age _____ Phone (area code) _____

Check box for G.I. Bill information: Veteran Active Duty

Mail today!

LETTERS

continued from page 16

1. Have you ever made up a list of exactly what is required and then gone out to the local dealers to try to get these items? Even if I limit my list to Radio Shack parts and catalog numbers, I can visit (and have visited) 10 New York stores without finding 75% of what I need. I now order by mail.

2. You have not provided any help in at least one area where it is badly needed—capacitors. I do not remember any article in your magazine (or any other) discussing what capacitors are suitable substitutions or what cannot be changed to any other type. I refer particularly to ceramic, silver mica, mica, Mylar, tantalum, etc.—also to

electrolytics. Why was each type emphasized and what is it really required for?

3. Resistors offer a somewhat simpler problem. So can you point out when you can substitute 5% resistors for 1% resistors, on wire-wound vs. carbon, etc.?

4. How about an update on what items now on the market really require heat-sink protection in soldering.

5. How about some practical specifications for handling static-sensitive AC-field-sensitive solid-state items, MOS, etc.?

R. M. SANFORD
White Plains, NY

DIGITAL CAR CLOCKS

I read with great interest your October and November 1977 articles on "Digital

Car Clocks," as I had just recently built James Electronics' Quartz Digital Auto Clock.

It is working very well, but I still want to either convert it or get a similar clock to count in decimal minutes (hundredths) instead of seconds for use in road rally timing. This appears to require a special IC with a divide-by-100 in place of one divide-by-60 and a 100-Hz frequency. Perhaps you may have discovered such an item during research for your article . . . any ideas? A "split action" timing feature would also be of benefit.

In the October 1977 article you also referred to a Radio Shack WWV Converter Kit (No. 28-133 for \$5.95). I have inquired at several local Radio Shack outlets, and none of them knows about this kit.

JOHN R. GINGRICH
Massillon, OH

In answer to your first question, if you look in the latest Radio Shack catalog (1978, No. 289) on page 148 at the top, you'll find a super-duper "Quartz Computer Timepiece" for \$49.95. I have this identical item, under the Casio brand name, and have had it since it was introduced by Casio about five months ago.

It's terrific! The picture shown in the catalog is just slightly smaller than actual size. In the stopwatch functions it reads decimal seconds, but not decimal minutes or hours. Real-time is retained when using the elapsed-time function. The AA battery for the display should last for 10 hours or so in regular use as a stopwatch, since the display is always on in that function. It's difficult to adapt this to external power except with the special AC adapter, because the jack is nonstandard (it uses a larger-than-standard center prong). If you could find a mating plug, you could drop the car 12 volts through a resistor (220 ohms, 1 watt should do it nicely, since the display draws about 50 mA). I don't know of any clock that counts minutes in hundredths, although it certainly could be done as you describe.

Regarding the Radio Shack No. 28-133 WWV Converter Kit, it has apparently been discontinued. It's not shown in their current catalog.

FRED BLECHMAN

MAGNETIC SEMICONDUCTOR

During an energy crisis, in desperation, we are apt to seek such far-out solutions as a "magnetic semiconductor" as described by Andrew Fraser in the October 1977 issue.

Even if we should find such a material, Marc Scharf (same issue) also wrote of a basic law of science that has never been violated. If the material is ever found, it will be impossible to improve it or any permanent magnets beyond a certain efficiency. By scientific law the screen must always use more power than the iron block can generate.

It is hoped none of your readers waste their time pursuing John Ecklin's scheme as it is a complete flop unless we can find a "magic semiconductor." Perpetual motion is impossible even with all the many wonders of today's electronics.

A. G. HOLT
Silver Spring, MD



PHILIPS
BK PRECISION
HICKOK
LEADER
NLS Non-Linear Systems
FLUKE
DATA PRECISION
TRIPLETT VIZ formerly RCA

Simpson **ECD**
CONTINENTAL SPECIALTIES CORPORATION
CSC

SUPER SPECIAL
BK PRECISION
New 3-1/2 Digit Portable DMM
REG. \$99.95
\$79.95
OFFER EXPIRES APRIL 30, 1978
MODEL 2800

Compu model 710
FREQUENCY COUNTER

MEASURE

Advances

We give you immediate off the shelf delivery on Oscilloscopes, Power Supplies, Audio & R.F. Generators, Digital Multimeters, Frequency Counters, Logic Probes, Tube & Transistor Testers, Wow & Flutter Meters, Distortion Analyzers, Bridges, and Accessories. For more information call us Toll Free: 800-223-0474.

212-687-2224
THE TEST EQUIPMENT SPECIALISTS
TOLL FREE HOT LINE
800-223-0474
54 West 45 Street New York, N.Y. 10036

ADVANCE ELECTRONICS

**From blisters to
boxes to bags.**

**Mallory's got the
winning team
for your solderless
terminal needs.**

Mallory solderless terminals are available now — packaged to suit your needs. These crimp-type terminals and connectors fit virtually all popular applications and come in a complete range of sizes from 26 through 4/0 AWG.

Buy the winning team for convenience and reliability. See your Mallory Distributor. Or contact Mallory Distributor Products Company, a division of P. R. Mallory & Co. Inc., Box 1284, Indianapolis, Indiana 46206. (317) 856-3731.




MALLORY

Capacitors • Controls • Fastening Devices • Resistors • Security Products • Semiconductors • Solderless Terminals • Sonalert® Signals • Switches
CIRCLE 46 ON FREE INFORMATION CARD



wire wrapping center

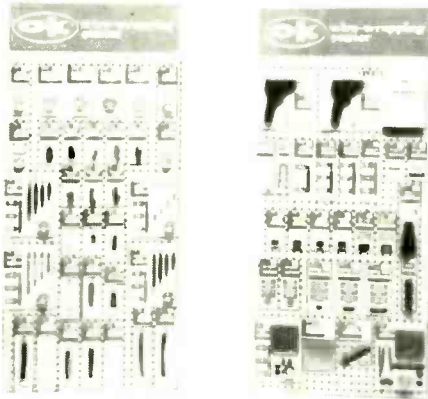

for quality electronic parts and tools.

WIRE-WRAPPING KITS

Contains: Hobby Wrap Tool WSU-30, (50 ft.) Roll of wire Prestripped wire 1" to 4" lengths (50 wires per package) stripped 1" both ends.

Wire Wrapping Kit (Blue)	WK 2 B	\$12.95
Wire Wrapping Kit (Yellow)	WK 2 Y	\$12.95
Wire Wrapping Kit (White)	WK 2 W	\$12.95
Wire Wrapping Kit (Red)	WK 2 R	\$12.95

WIRE-WRAPPING KIT


Contains: Hobby Wrap Tool WSU-30, Roll of wire R-30B-0050, (2) 14 DIP's, (2) 16 DIP's and Hobby Board H-PCB-1.

Wire-Wrapping Kit	WK-3B (Blue)	\$16.95
-------------------	--------------	---------

WIRE-WRAPPING KIT

Contains: Hobby Wrap Tool WSU-30 M, Wire Dispenser WD-30-B, (2) 14 DIP's, (2) 16 DIP's, Hobby Board H-PCB-1, DIP/IC Insertion Tool INS-1416 and DIP/IC Extractor Tool EX-1

Wire-Wrapping Kit	WK-4B (Blue)	\$25.99
-------------------	--------------	---------

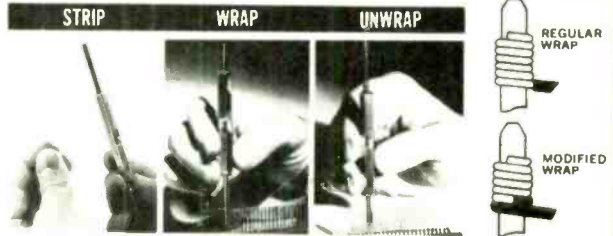


HOBBY WRAP TOOL

Wire-wrapping, stripping, unwrapping tool for AWG 30 on .025 (0.63mm) Square Post.

Regular Wrap	WSU-30	\$6.95
Modified Wrap	WSU-30M	\$7.95

NEW HOBBY WRAP Model BW-630

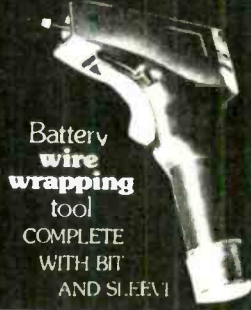

Battery wire wrapping tool COMPLETE WITH BIT AND SLIVER

WIRE-WRAPPING TOOL

For .025" (0.63mm) sq. post "MODIFIED" wrap, positive indexing, anti-overwrapping device.

For AWG 30	BW-630	\$34.95*
For AWG 26-28	BW-2628	\$39.95*

Bit for AWG 30	BT-30	\$3.95
Bit for AWG 26-28	BT-2628	\$7.95

*USE "C" SIZE NI-CAD BATTERIES (NOT INCLUDED)

ROLLS OF WIRE

Wire for wire-wrapping AWG-30 (0.25mm) KYNAR® wire, 50 ft. roll, silver plated, solid conductor, easy stripping.

30 AWG Blue Wire 50ft Roll	R 30B 0050	\$1.98
30 AWG Yellow Wire 50ft Roll	R 30Y 0050	\$1.98
30 AWG White Wire 50ft Roll	R 30W 0050	\$1.98
30 AWG Red Wire 50ft Roll	R 30R 0050	\$1.98

WIRE DISPENSER

- With 50 ft. Roll of AWG 30 KYNAR® wire-wrapping wire.
- Cuts the wire to length.
- Strips 1" of insulation.
- Refillable (For refills, see above)

Blue Wire	WD-30-B	\$3.95
Yellow Wire	WD-30-Y	\$3.95
White Wire	WD-30-W	\$3.95
Red Wire	WD-30-R	\$3.95

PRE CUT PRE STRIPPED WIRE

Wire for wire-wrapping AWG 30 (0.25mm) KYNAR® wire. 50 wires per package stripped 1" both ends.



30 AWG Blue Wire 1' Long	30 B 50 010	\$.99
30 AWG Yellow Wire 1' Long	30 Y 50 010	\$.99
30 AWG White Wire 1' Long	30 W 50 010	\$.99
30 AWG Red Wire 1' Long	30 R 50 010	\$.99
30 AWG Blue Wire 2' Long	30 B 50 020	\$ 1.07
30 AWG Yellow Wire 2' Long	30 Y 50 020	\$ 1.07
30 AWG White Wire 2' Long	30 W 50 020	\$ 1.07
30 AWG Red Wire 2' Long	30 R 50 020	\$ 1.07
30 AWG Blue Wire 3' Long	30 B 50 030	\$ 1.16
30 AWG Yellow Wire 3' Long	30 Y 50 030	\$ 1.16
30 AWG White Wire 3' Long	30 W 50 030	\$ 1.16
30 AWG Red Wire 3' Long	30 R 50 030	\$ 1.16
30 AWG Blue Wire 4' Long	30 B 50 040	\$ 1.23
30 AWG Yellow Wire 4' Long	30 Y 50 040	\$ 1.23
30 AWG White Wire 4' Long	30 W 50 040	\$ 1.23
30 AWG Red Wire 4' Long	30 R 50 040	\$ 1.23
30 AWG Blue Wire 5' Long	30 B 50 050	\$ 1.30
30 AWG Yellow Wire 5' Long	30 Y 50 050	\$ 1.30
30 AWG White Wire 5' Long	30 W 50 050	\$ 1.30
30 AWG Red Wire 5' Long	30 R 50 050	\$ 1.30
30 AWG Blue Wire 6' Long	30 B 50 060	\$ 1.38
30 AWG Yellow Wire 6' Long	30 Y 50 060	\$ 1.38
30 AWG White Wire 6' Long	30 W 50 060	\$ 1.38
30 AWG Red Wire 6' Long	30 R 50 060	\$ 1.38

© KYNAR PENNVALT

MINIMUM ORDER \$25.00. SHIPPING CHARGE \$1.00. N.Y. CITY AND STATE RESIDENTS ADD TAX


OK MACHINE & TOOL CORPORATION

3455 Conner St. Bronx, N.Y. 10475 (212) 994-6600 Telex 125091

CIRCLE 15 ON FREE INFORMATION CARD



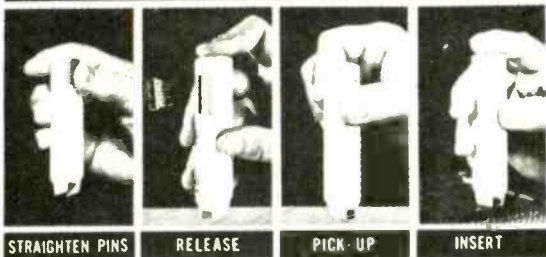DIP/IC INSERTION TOOL WITH PIN STRAIGHTENER



14-16 Pin Dip IC Inserter INS-1416 \$3.49

DIP/IC EXTRACTOR TOOL



The EX-1 Extractor is ideally suited for hobbyist or lab engineer. Featuring one piece spring steel construction. It will extract all LSI, MSI and SSI devices of from 8 to 24 pins.

Extractor Tool EX-1 \$1.49

P.C. BOARD




The 4 x 4.5 x 1/16 inch board is made of glass coated EPOXY Laminate and features solder coated 1 oz. copper pads. The board has provision for a 22/44 two sided edge connector, with contacts on standard .156 spacing. Edge contacts are non-dedicated for maximum flexibility.

The board contains a matrix of .040 in. diameter holes on .100 inch centers. The component side contains 76 two-hole pads that can accommodate any DIP size from 6-40 pins, as well as discrete components. Typical density is 18 of 14-Pin or 16-Pin DIP's. Components may be soldered directly to the board or intermediate sockets may be used for soldering or wire-wrapping.

Two independent bus systems are provided for voltage and ground on both sides of the board. In addition, the component side contains 14 individual busses running the full length of the board for complete wiring flexibility. These busses enable access from edge contacts to distant components. These busses can also serve to augment the voltage or ground busses, and may be cut to length for particular applications.

Hobby Board H-PCB-1 \$4.99

PC CARD GUIDES

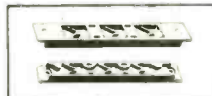


TR-1 consists of 2 guides precision molded with unique spring finger action that dampens shock and vibration, yet permits smooth insertion or extraction. Guides accommodate any card thickness from .040-.100 inches.

QUANTITY - ONE PAIR (2 pcs.)

Card Guides TR-1 \$1.89

PC CARD GUIDES & BRACKETS

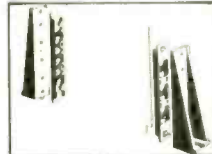


TRS-2 kit Includes 2 TR-1 guides plus 2 mounting brackets. Support brackets feature unique stabilizing post that permits secure mounting with only 1 screw.

QUANTITY - ONE SET (4 pcs.)

Guides & Brackets TRS-2 \$3.79


PC EDGE CONNECTOR

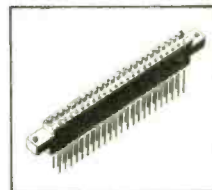

44 Pin, dual read out, .156" (3.96 mm) Contact Spacing, .025" (0.63 mm) square wire-wrapping pins.

P.C. Edge Connector CON-1 \$3.49


P.C.B. TERMINAL STRIPS

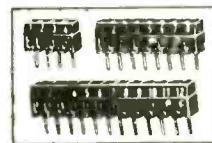

The TS strips provide positive screw activated clamping action, accommodate wire sizes 14-30 AWG (1.8-0.25mm). Pins are solder plated copper, .042 inch (1mm) diameter, on .200 inch (5mm) centers.

4-Pole	TS-4	\$1.39
8-Pole	TS-8	\$1.89
12-Pole	TS-12	\$2.59


DIP SOCKET

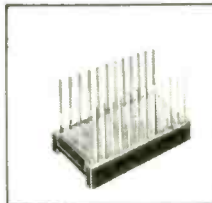

Dual-in-line package, 3 level wire-wrapping, phosphor bronze contact, gold plated pins .025 (0.63mm) sq., .100 (2.54mm) center spacing.


14 Pin Dip Socket	14 Dip	\$0.79
16 Pin Dip Socket	16 Dip	\$0.89

RIBBON CABLE ASSEMBLY SINGLE ENDED

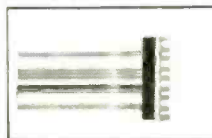

With 14 Pin Dip Plug 24" Long (609mm)	SE14-24	\$3.55
With 16 Pin Dip Plug 24" Long (609mm)	SE16-24	\$3.75

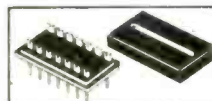
DIP PLUG WITH COVER FOR USE WITH RIBBON CABLE



14 Pin Plug & Cover	14-PLG	\$1.45
16 Pin Plug & Cover	16-PLG	\$1.59


QUANTITY: 2 PLUGS, 2 COVERS

RIBBON CABLE ASSEMBLY DOUBLE ENDED

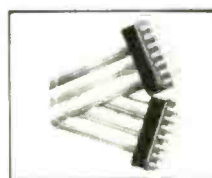

With 14 Pin Dip Plug -2" Long	DE 14-2	\$3.75
With 14 Pin Dip Plug -4" Long	DE 14-4	\$3.85
With 14 Pin Dip Plug -8" Long	DE 14-8	\$3.95
With 16 Pin Dip Plug -2" Long	DE 16-2	\$4.15
With 16 Pin Dip Plug -4" Long	DE 16-4	\$4.25
With 16 Pin Dip Plug -8" Long	DE 16-8	\$4.35

TERMINALS

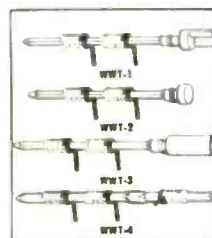

- .025 (0.63mm) Square Post
- 3 Level Wire-Wrapping
- Gold Plated

Slotted Terminal	WWT-1	\$2.98
Single Sided Terminal	WWT-2	\$2.98
IC Socket Terminal	WWT-3	\$3.98
Double Sided Terminal	WWT-4	\$1.98

25 PER PACKAGE

TERMINAL INSERTING TOOL



For inserting WWT-1, WWT-2, WWT-3, and WWT-4 Terminals into .040 (1.01 mm) Dia. Holes.

INS-1 \$2.49

WIRE CUT AND STRIP TOOL



Easy to operate... place wires (up to 4) in stripping slot with ends extending beyond cutter blades... press tool and pull... wire is cut and stripped to proper "wire-wrapping" length. The hardened steel cutting blades and sturdy construction of the tool insure long life.

Strip length easily adjustable for your applications.

DESCRIPTION	MODEL NUMBER	ADJUSTABLE "SHIMMER" LENGTH OF STRIPPED WIRE		Price
		INCHES	TO INCHES	
24 ga. Wire Cut and Strip Tool	ST-100-24	1 1/4"	1 3/4"	\$ 8.75
26 ga. Wire Cut and Strip Tool	ST-100-26	1 1/4"	1 3/4"	\$ 8.75
26 ga. Wire Cut and Strip Tool	ST-100-26-875	3/8"	1 1/4"	\$ 8.75
28 ga. Wire Cut and Strip Tool	ST-100-28	3/8"	1 1/4"	\$11.50
30 ga. Wire Cut and Strip Tool	ST-100-30	3/8"	1 1/4"	\$11.50

THE ABOVE LIST OF CUT AND STRIP TOOLS ARE NOT APPLICABLE FOR WILENE OR TEFLON INSULATION

MINIMUM ORDER \$25.00 SHIPPING CHARGE \$1.00. N.Y. CITY AND STATE RESIDENTS ADD TAX

OK MACHINE & TOOL CORPORATION


3455 Conner St. Bronx, N.Y. 10475 (212) 994-6600 Telex 125091

CIRCLE 15 ON FREE INFORMATION CARD

Got Gas Guzzler Gloom?

Try AUTOCOMP for quick relief from high fuel costs.

AUTOCOMP is a continuously updating micro-computer which reads TRUE MPG while you drive. Additional pushbutton controls also give automatic readouts of Time, Distance, and Fuel Consumption. You can monitor your engine's performance and your vehicle's efficiency. AUTOCOMP will help you save fuel, improve your driving habits, and provide you with valuable time and trip data. Install AUTOCOMP before your next trip and beat high fuel costs!

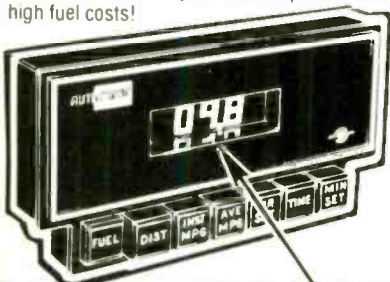

AUTOMATICALLY DISPLAYS:

- **FUEL USED** — When the FUEL button is depressed, the display indicates the amount of fuel the vehicle has used since last fill-up, beginning of trip, or last reset (up to 1000 gallons).
- **DISTANCE TRAVELED** — When the DIST button is depressed, the display indicates the distance the vehicle has traveled since the last reset (up to 1000 miles).
- **INSTANT MILES/GALLON** — When the INST MPG button is depressed, the display indicates how many miles per gallon the vehicle is attaining at each moment (up to 200 mpg).
- **AVERAGE MILES/GALLON** — When the AVE MPG button is depressed, the display indicates the average miles per gallon the vehicle has attained since the last reset (up to 200 mpg).
- **CORRECT TIME (clock)** — When the TIME button is depressed, the display indicates the correct time (in hours and minutes). The clock may also be used to display ELAPSED TIME.

EXAMPLE

09.8

187.2

21.3

19.1

3:45

AUTOCOMP comes with clear, illustrated instructions that make it easy for a do-it-yourselfer to install. Equipment supplied includes the Speedsensor which simply screws onto the speedometer cable, and the digital Flowsensor which easily installs onto the fuel line.



SAVE \$10 OFF REGULAR PRICE

Order now using the coupon below and save \$10 off the regular list price of \$129.50. A one year limited warranty is provided.



SpaceKom, Inc.
212 E. Gutierrez St.
Santa Barbara,
CA 93101

Please send AUTOCOMP Model 1000 (MSRP \$119.50 each) Master Charge

Vehicle Make/Year _____ CB # _____ Exp. Date _____

Card No. _____

Signature _____ Print Name _____ Address _____ City _____ State _____ Zip _____

CIRCLE 39 ON FREE INFORMATION CARD

equipment reports

Wilson Electronics Model WFC-500-S, Model WFC-500-E Frequency Counters



CIRCLE 147 ON FREE INFORMATION CARD

THE WILSON ELECTRONICS CORPORATION (4288 South Polaris Avenue, Box 19000, Las Vegas, NV 89119) has introduced two versions of a new frequency counter, the models WFC-500-S and WFC-500-E. Both instruments are 6-digit types, with a dual range giving an 8-digit resolution. The frequency range covered by the counters is from 10 Hz up to 500 MHz. The model WFC-500-S (shown) has a rated accuracy of 0.0001%, and the model WFC-500-E has an accuracy of 0.000002%, or 0.02 PPM. The model WFC-500-E uses a TCXO (temperature compensated crystal oscillator) clock.

Both versions can be AC-powered, and have a selector switch that can operate on AC lines of 100, 110, 117, 200, 220 or 234 volts. They can also be powered by 12 volts DC, for mobile use, and both models come with AC and DC input cables, plus an input cable with clips. There are two BNC input jacks on the front panel. Input A is used for frequencies from 10 Hz up to 10 MHz, and it can be switched from a 1.0-megohm impedance to a 50-ohm input. The sensitivity is 25 mV in both switch positions. Input B is used for frequencies from 10 MHz up to 500 MHz, at 50 ohms, with a 100-mV sensitivity at about 20 MHz; this sensitivity reading goes to 25 mV at about 100 to 120 MHz, then gradually rises to about 100 mV at 500 MHz.

The 7-segment red LED readout is plainly visible. An overrange LED on the left-hand side of the readout shows when the input frequency is above the normal readout. Two LED's on the right-hand side show whether the reading is in kHz or MHz. For greater resolution, the initial reading can be displayed in MHz, with the decimal point placed three digits from the left. Incidentally, the counter has lead zero blanking that makes the display simpler to read. For example, if you read 45.75 MHz in the MHz position, all you see is "45.750." When you move this reading to the kHz position, the "45" scoots out of sight to

the left, and you then read "750.000" in kHz. The three digits on the right-hand side give you the reading in Hz!

In our bench test, we connected the counter to the color oscillator of a TV set during a network program. The reading was "3.580." Switching to kHz gave a reading of "575.545." The last digit rocked at times, first to "6" and then back, which is normal. We were glad to see that the network's atomic clock was still right on the button. We left the counter and went out for coffee; when we returned it was still reading exactly the same.


When you use the model WFC-500-E, which contains the TCXO, a standby LED on the panel lights up as soon as the unit is plugged in. This shows that the crystal oven is operating. The manufacturer recommends leaving the counter on for an hour for greater stability. We didn't warm it up nearly that long, but found it was quite stable within no more than 15 minutes, in the bench test described above and on other frequency standards.

The circuitry of the model WFC-500-S and WFC-500-E is thoroughly integrated. Standard IC's are used for flip-flops, counter, dividers, etc. The DC power supply is tightly regulated on both AC and DC inputs.

The layout of the front panel is neatly arranged. The input jacks are at the lower right-hand corner, with the selector switches in the middle. All controls are push-push types, with the switch positions plainly marked on the panel. The rear panel contains the 4-pin power-input jack, a line fuse, and a BNC jack for access to the internal 1.0-MHz clock oscillator. The cabinet is made of sturdy metal and comes in two sections for easy access to the counter circuitry.

R-E

Huntron Tracker Circuit Tester

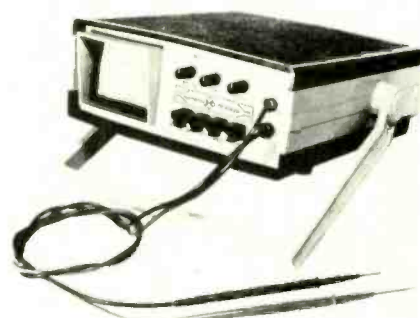

CIRCLE 148 ON FREE INFORMATION CARD

THE HUNTRON TRACKER IS A NEW VERSION OF an old circuit. This circuit is what some call an

continued on page 32

THE
ELECTRICAL
TERMINAL
&
CONNECTOR
SHOP™

Just about every bit
of electrical hardware
you'll ever need . . .
over 1,000 pieces (that's 7 gross!
over 84 dozen!)
all organized & labeled
in a heavy-duty,
bin-cabinet!


FREE

A \$2.50-value, wall-size
(17 1/2" x 24") Specifications
Chart Shows how to select
the right terminal or con-
nector . . . how to identify
wire and stud sizes . . . and
explains coding . . . and
much, much more.
Yours absolutely FREE!!

You'll wonder how you ever did
without it . . . truly one of the most
important "tools" you could own!

All for just
\$24.95
plus \$3.90
shipping &
handling

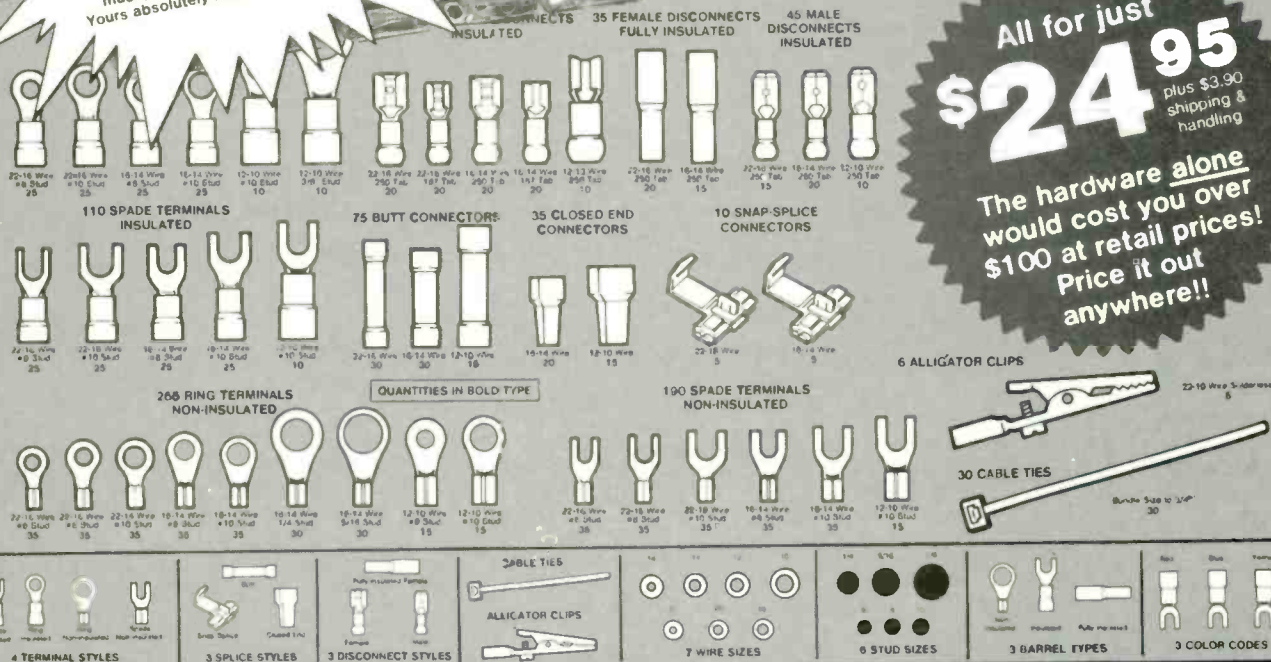The hardware alone
would cost you over
\$100 at retail prices!
Price it out
anywhere!!



LOOK AT ALL YOU GET! Every type, size and style of terminal and connector you'll probably ever need! Full size ranges!

- No more "making do" with just anything you have on hand!
- No more "drugstore quality" terminals and connectors!
- No more high prices!
- No more less-than-professional repair jobs!
- No more frustrating searches for the right piece of electrical hardware!
- No more time-consuming soldering!
- No more Saturday-morning trips to the hardware or electrical supply store!

BONUS BUY!

A Stanley, industrial-quality "Jobmaster" crimper at our wholesale cost!

REGULAR \$6.05 CRIMPER JUST \$2.99 (plus \$ 1.10 shipping and handling)

Limit: One crimper per shop. Crimpers not sold separately.

To Order — 24-hour Phone Service: Send check, money order, or company purchase order for full amount. Or charge it to any one of 5 major credit cards (see Order Coupon). Credit card buyers can also call our 24-hour, toll-free number: 800-331-1000 (from Oklahoma, call 918-664-8300 collect).



Not Available
in Retail
Stores!

UNCONDITIONAL 30-DAY GUARANTEE

Mail to and make remittance payable to:
D.R.I. Industries, Inc., Dept. RE-48
6864 Washington Avenue South, Eden Prairie, MN 55344

Indicate _____ Electrical Terminal & Connector Shop(s) @ \$24.95
Order: How many? plus \$3.90 shipping and handling each.
_____ Stanley Crimper(s) @ \$2.99 plus 75¢ shipping and
How many? handling each. (Limit: one per Shop purchased.)

Check (✓) Method Check, money order, or company purchase order enclosed (MN residents add 4% sales tax).
of Payment: Charge it to: VISA/BankAmericard
 American Express Carte Blanche
 Diners Club Master Charge

CARD NO. _____
SIGNATURE _____

NAME _____
ADDRESS _____
CITY _____ STATE _____ ZIP _____

All high-quality, 99% conductivity, plated copper terminals and connectors. Meet or exceed UL, CSA, and (where applicable) OEM standards. Not inexpensive "stamped-out-til" hardware. No "seconds" or "rejects." All high-quality! Truly over \$100 worth of hardware alone! Check out prices yourself . . . you'll be amazed!

Unconditional 30-Day Guarantee: If you're dissatisfied in any way or for any reason, just return your Shop(s) within 30 days for an immediate, full refund. No questions asked!

Exactly what you receive: One 25-tray, polystyrene bin-cabinet (tray dividers form 45 bins), 1,011 terminals, connectors, and electrical accessories. 25 preprinted, color-coded I.D. labels. One FREE Specifications Chart.

©1977 D.R.I. Industries, Inc., Eden Prairie, MN 55344

"The Electrical Terminal & Connector Shop" is a trademark of D.R.I. Industries, Inc.

D.R.I. Industries, Inc., 6864 Washington Ave. So., Eden Prairie, MN 55344

Whatever you're looking for you'll find it with a price/performance



Put Computer versatility and convenience in your home with the H8 Personal Computer System

Get into personal computing the right way with a powerful computer system from Heath. Start with the H8. It features 8-bit operation, fully expandable memory, a versatile 8080A CPU, and is the only machine in its price class that, due to its "intelligent" front panel and built in monitor program, can function without peripherals.

Next, add our 12" CRT video terminal. The H9 operates in three different modes, has a 67-key ASCII keyboard, and features a built in interfacing board to make hook-up a breeze.

Add "mass storage" with the ECP-3801 cassette recorder/player and cassette I/O and you've got a system that's ready to go wherever your programming skills take you.

Our low-cost, effective Microprocessor Course teaches you all about Computers

Using our challenging self-instruction techniques and the optional ET-3400 Trainer, the EE-3401 Microprocessor Course takes you step-by-step through hardware, I/O interfacing, machine language programming, number systems, microprocessor operation, and much more. You'll complete experiments, gain hands-on experience and work directly with the devices that are "taking over" in today's electronics.



Weigh yourself with electronic precision with our Digital Electronic "Weighing Machine"


Uses solid-state electronics and a strain-gauge transducer element like expensive laboratory scales. The GD-1186 features 300-lb. capacity, can be wired to give weight in pounds or kilograms, and has a bright, easy-to-read 4-digit LED display.

It's battery operated so it's safe to use even after a shower. And for extra convenience, the GD-1186 comes with additional cable so you can mount the read-out most anywhere you desire.



This Low-cost Multimeter gives you digital accuracy at analog prices

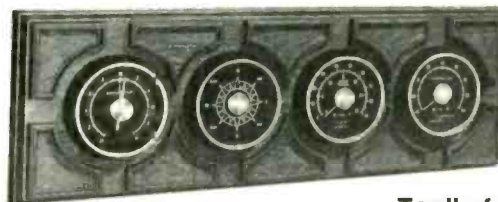The IM-1210 is an economical performer that hobbyists and service techs have been waiting for. Capabilities include AC voltage measurement to 700 volts, DC to 1000 volts, current measurement, and 5-ranges for resistance checks. Accuracy is excellent and the bright digital display gives you readings at a glance.



Stay "On Top" of the Weather with this Five-function Weather Station

The ID-1290 Weather Station monitors indoor and outdoor temperatures, barometric pressure, wind speed and direction — all with electronic accuracy and reliability. Ideal for home or office or anywhere accurate, instant weather information is needed.

in the way of electronics... advantage in the new Heathkit Catalog!



**Smartly-styled
Low-Cost
Digital
Alarm Clock**

Unobtrusive and elegant, the GC-1107 is styled in handsome wood grained vinyl, and features an easy-to-read 4-digit blue-green display, 12 or 24 hour format, and automatic dimming to adjust for ambient light conditions. Its "snooze" feature lets you take 9-minute "catnaps" for as long as an hour. And for extra convenience — there's even a handy power failure indicator. A perfect kit for the beginner.

This SSB/CW Receiver is the one the Hams are enthused about!



An excellent, low-cost choice for your first receiver is the HR-1680. With it you'll find total solid-state construction, no-instrument alignment, and a sensitivity figure of less than 0.5 μ V. It covers 80, 40, 20, 15 and the lower 1 MHz of 10 meters. And with a MOSFET "front end" and preselector tuning — you'll be digging out the "rare" ones in no time!


Send the coupon or visit the Heathkit Electronic Center nearest you today!



Units of Schlumberger Products Corporation. Retail prices on some products may be slightly higher.

ARIZONA — Phoenix, 2727 W. Indian School Rd. (602) 279-6247.
CALIFORNIA — Anaheim, 330 E. Ball Rd. (714) 776-9420; El Cerrito, 6000 Potrero Ave. (415) 236-8870; Los Angeles, 2309 S. Flower St. (213) 749-0261; Pomona, 1555 Orange Grove Ave. N. (714) 623-3543; Redwood City, 2001 Middlefield Rd. (415) 365-8155; Sacramento, 1860 Fulton Ave. (916) 486-1575; San Diego (La Mesa), 8363 Center Dr. (714) 461-0110; San Jose (Campbell), 2350 S. Bascom Ave. (408) 377-8920; Woodland Hills, 22504 Ventura Blvd. (213) 863-0531.
COLORADO — Denver, 5940 W. 38th Ave. (303) 422-3408.
CONNECTICUT — Hartford (Avon), 395 W. Main St. (Rte. 44) (203) 678-0323.
FLORIDA — Miami (Hialeah), 4705 W. 16th Ave. (305) 823-2280; Tampa, 4019 West Hillsborough Ave. (813) 386-2541.
GEORGIA — Atlanta, 5285 Roswell Rd. (404) 252-4341.
ILLINOIS — Chicago, 3462-66 W. Devon Ave. (312) 583-3920; Chicago (Downers Grove), 224 Ogden Ave. (312) 852-1304.
INDIANA — Indianapolis, 2112 E. 62nd St. (317) 257-4321.
KANSAS — Kansas City (Mission), 5960 Lamar Ave. (913) 362-4486.
KENTUCKY — Louisville, 12401 Shelbyville Rd. (502) 245-7811.
LOUISIANA — New Orleans (Kenner), 1900 Veterans Memorial Hwy. (504) 722-6321.
MARYLAND — Baltimore, 1713 E. Joppa Rd. (301) 661-4446; Rockville, 5542 Nicholson Lane (301) 881-5420.
MASSACHUSETTS — Boston (Peabody), 242 Andover St. (617) 531-9330; Boston (Wellesley), 165 Worcester Ave. (Rt. 9 just west of Rt. 128) (617) 237-1510.

MICHIGAN — Detroit, 18645 W. Eight Mile Rd. (313) 535-6480; E. Detroit, 16149 E. Eight Mile Rd. (313) 772-0416.
MINNESOTA — Minneapolis (Hopkins), 101 Shady Oak Rd. (612) 938-6371.
MISSOURI — St. Louis (Bridgton), 3794 McKelvey Rd. (314) 291-1850.
NEBRASKA — Omaha, 9207 Maple St. (402) 391-2071.
NEW JERSEY — Fair Lawn, 35-07 Broadway (Rte. 4) (201) 791-6935; Ocean, 1013 State Hwy. 35 (201) 775-1231.
NEW YORK — Buffalo (Amherst), 3476 Sheridan Dr. (716) 835-3090; Jericho, Long Island, 15 Jericho Turnpike (516) 334-8181; Rochester, 937 Jefferson Rd. (716) 244-5470; White Plains (North White Plains), 7 Reservoir Rd. (914) 761-7690.
OHIO — Cincinnati (Woodlawn), 10133 Springfield Pike (513) 771-8650; Cleveland, 5444 Pearl Rd. (216) 866-2590; Columbus, 2500 Morse Rd. (614) 475-7200; Toledo, 48 S. Byrne Rd. (419) 537-1887.
PENNSYLVANIA — Philadelphia, 6318 Roosevelt Blvd. (215) 288-0190; Frazer (Chester Co.), 630 Lancaster Pike (Rt. 30) (215) 647-5555; Pittsburgh, 3482 Wm. Penn Hwy. (412) 824-3564.
RHODE ISLAND — Providence (Warwick), 558 Greenwich Ave. (401) 738-5150.
TEXAS — Dallas, 2715 Ross Ave. (214) 826-4053; Houston, 3705 Westheimer (713) 623-2090.
VIRGINIA — Alexandria, 6201 Richmond Hwy. (703) 765-5515; Norfolk (Virginia Beach), 1055 Independence Blvd. (804) 480-0997.
WASHINGTON — Seattle, 2221 Third Ave. (206) 682-2172.
WISCONSIN — Milwaukee, 5215 W. Fond du Lac (414) 873-8250.

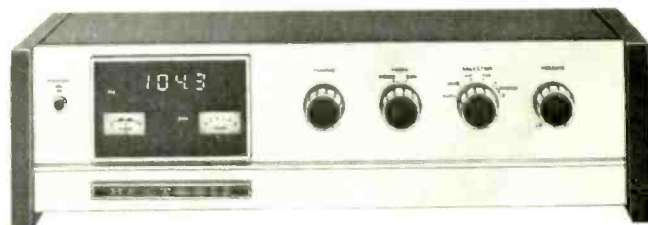

Our AR-1515 Stereo Receiver sets new standards in performance, price and features

Undoubtedly the finest AM/FM stereo receiver we've ever designed, the AR-1515 combines distinctive functional styling with excellent tuner performance, and a clean, powerful, amplifier section to give you a home entertainment center of unsurpassed quality. Power output is 70 watts, minimum RMS, per channel into 8 ohms with less than 0.08% total harmonic distortion from 20-20,000 Hz. FM sensitivity is an outstanding 1.8 μ V for really clean and clear reception. And the AR-1515 is the only stereo receiver in its price range that provides digital frequency readout!



HEATHKIT CATALOG

Send coupon today for your mail order catalog or redeem coupon at the Heathkit Electronic Center nearest you for a retail catalog.

HEATH
Schlumberger

Heath Company, Dept. 020-400
Benton Harbor, Michigan 49022

Please send me your new Heathkit Catalog.
I am not on your mailing list.

Name _____

Address _____

City _____ State _____

GX-346 _____ Zip _____

EQUIPMENT REPORTS

continued from page 26

"angle tracer." This simple device displays a sharp angle on a scope pattern by feeding an AC voltage across the scope. Huntron Instruments, Inc., 15123 Pacific Highway North, Lynnwood, WA 98036, has really refined and perfected this device, which sells for a suggested retail price of \$695.00. State-of-the-art circuitry gives it much more versatility than the original angle tracers.

The *Tracker* has its own scope—a 2 × 3-inch rectangular CRT. The scope controls are at the top of the front panel. Three pushbutton switches at the bottom of the front panel select HIGH, LOW or MEDIUM impedance for matching the circuitry to be tested. A fourth pushbutton is the ON-OFF switch. Also included are two test-lead jacks, and that's all. The test leads used are Huntron *Micro-Probes*. These probes have telescoping points and can be extended to almost 8 inches. The probe tips are quite sharp and are insulated almost to the very end for maximum safety in testing tightly packed circuit boards. You can check practically all parts from their side of PC boards; just push the sharp probe tips down into the holes.

The *Tracker* uses a low AC voltage for tests. This is both voltage- and current-limited by the circuitry. The tests will not damage any solid-state device; even MOSFET's can be safely checked, in-circuit. You can make quick tests on any kind of transistor, from bipolars to FET's, and even Darlingtons, which are hard to check on many transistor testers.

In addition, the *Tracker* can check capacitors of any size, from .0025 μF to 4 μF on the

High-Z range, and from 2.0 μF to 5000 μF on the Low-Z range. The display for a good capacitor is a circle or an ellipse; if you see a closed loop, the capacitor is OK. The instrument also checks inductors such as power transformers, vertical output transformers, etc., for shorted windings. If you see a definite loop, the winding is OK. If the winding is shorted, you will not see a loop. For a shorted winding, the display will be a vertical line.

Diodes of all types are easy to check. Just touch the test leads to the diode. If you see an angle, the diode is good. You do *not* have to reverse the test leads as in other testing methods. Reversing the leads reverses the angle. If you see the angle, OK. The same thing applies to transistor junctions: If you see the angle, there you are.

The so-called good pattern for all junctions is a sharp angle with straight legs. The angle varies, from being quite acute in low-impedance circuits to quite wide in high-impedance circuits; but the key clues will be the same—the sharpness of the angle and the straightness of the legs of the trace. Leakage causes one or more of the legs to bend, and the corner will be rounded, and not sharp.

It is also possible to catch intermittent devices with the *Tracker*. The display flickers at the ends of the trace, or the whole pattern may be erratic and unstable. By monitoring the trace while heating or cooling the device, this test can be speeded up.

All the preceding tests can be made either in-circuit or out-of-circuit. Because you do not have to reverse the test leads, the *Tracker* is ideal for speedy testing! You can use the special test probes to test all discrete transistors, diodes, resistors and capacitors on a

typical PC board in only a very short time.

You can make accurate tests on TV modules; all you need is one unit that's known to be good. Just check the same parts (test points, etc.) between the two units, and the defective part will soon be pinned down.


You can even test IC's in the same way. You do *not* have to know the pinout. If you have another IC of the same type, just take readings between the same pins of each IC and the pattern should be the same. These tests can also be made either in- or out-of-circuit, which can save a lot of time taking an IC out and putting it back in.

In some more complex circuits, such as control boards, memories, etc., there are often quite a few identical IC's on the board. You can use the *Tracker* to quickly compare key points between several of these IC's. If the same pattern is repeated on three of them, and an entirely different pattern shows up on the fourth, then the fourth IC should be suspected!

In all cases, the tests can be made with no power applied to the device, PC board, module, etc. The *Tracker*, in effect, feeds its own signal into the device and displays the results on the scope. In-circuit tests show slightly different patterns due to the presence of shunt loading on the junction. However, the key clues still apply: The angles must be sharp and the legs straight. The presence of a closed loop in a test shows there is capacitance in the circuit. However, the key angle will still be sharp. A coil in the circuit may show ringing on the horizontal trace, but, again, the key angle is sharp.

We connected the *Tracker* to a known
continued on page 34

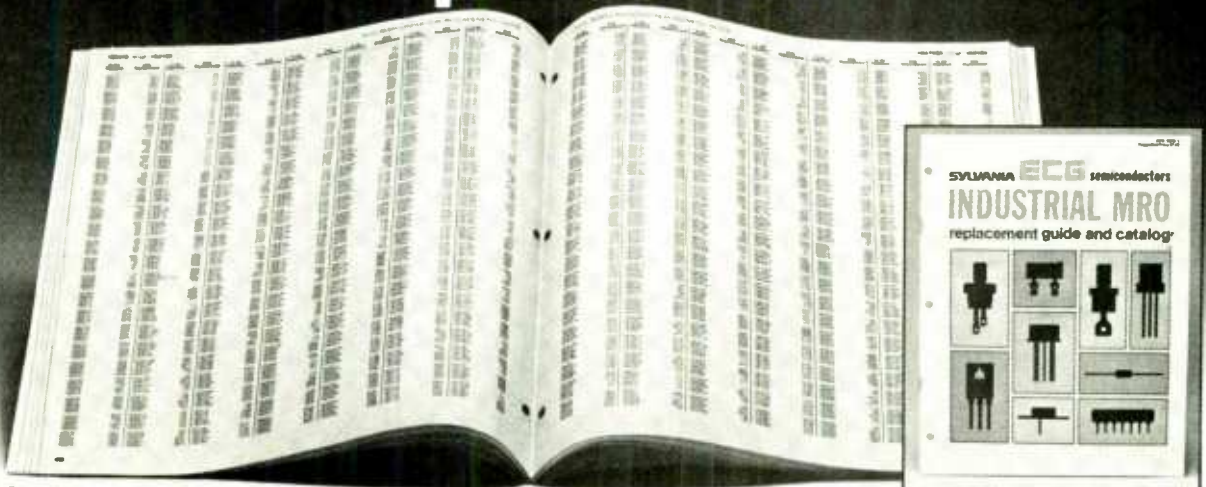We've made replacement parts an open book.



Our MRO replacement guide is required reading for people involved in maintenance, repair and operation of industrial electronic equipment.

It can solve your replacement parts problem at a single glance because it cross-references over 35,000 type numbers of OEM parts. Linear and digital ICs, triacs, SCRs and Zeners, plus a lot more.

Get your copy from the man who stocks the parts for off-the-shelf delivery—your local Sylvania distributor, or write to GTE Sylvania, Distributor and Special Markets Div., 1025 Westminister Dr., Williamsport, Pa. 17701.

SYLVANIA

“At last... a digital VOM I can trust.”



“I repair electronic equipment from TVs to computers. So I need dependable test equipment. That’s why I was unhappy with the first digital VOM I bought — it never worked right and I couldn’t trust it.

“Then I bought a VIZ WD-751A for \$150. The first thing I noticed was its speed; even on AC (the “problem” scale for most DMMs) the readings come fast — in a second at most. And this DMM is fully protected against overload. Even if I set it on OHMS and put in AC, I can’t damage it.

“I like how easy it is to read. Even in the bright sun, it doesn’t wash out. And this DMM changed my thinking about LCDs in low light; if there’s enough light to plug in the leads, there’s enough light to read the display.

“With its LCD readout and low-power CMOS circuits, this meter draws less than 50mA, so its batteries last a long time. And its CMOS large-scale ICs assure me that it’ll stay accurate over the long haul.

“I find this same quality built into all VIZ VOMs. Their WD-750A bench-type digital VOM has extra

features like an analog reference meter which is center-settable for nulling and peaking; a floating ground; a detachable power cord for complete AC isolation; low-power ohms; and an extra 20 Megohm resistance range. Its metal case provides great rf shielding, and it has the same overload protection as the smaller WD-751A DMM. One service magazine I read just rated it excellent in performance — and I agree; in fact, in their test it even gave very accurate readings on DC having high ripple or pulses, where some DMMs are off by as much as 40%.

“For years I’ve known that analog VOMs aren’t all the same, so why did I ever think that all 3½-digit DMMs would be the same? As my distributor told me, VIZ test instruments work right and they don’t come back for repairs.


“These VOMs have convinced me that if VIZ makes it, it’s made right.”

VIZ Test
Instruments Group

335 East Price Street Philadelphia, PA 19144 (215) VI-4-2626



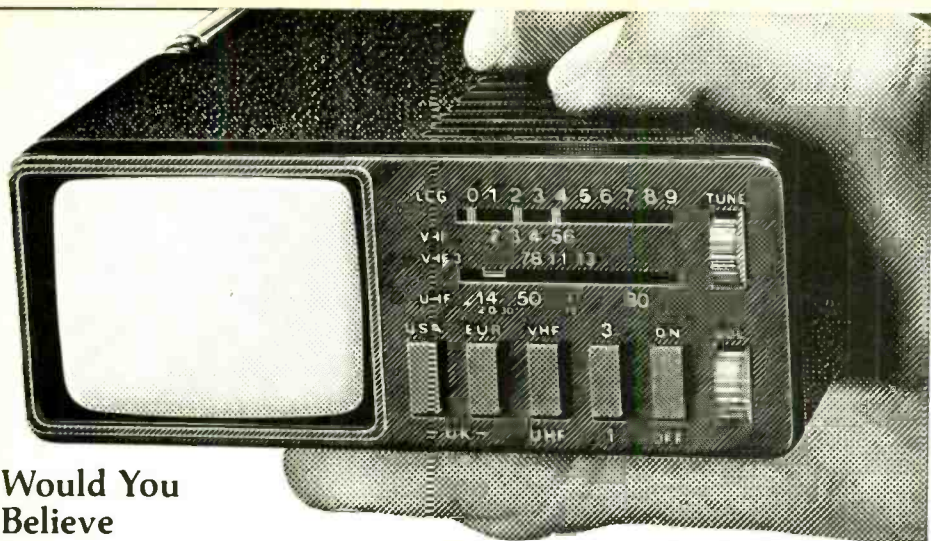The Circuit Tester line
Accuracy and stability assured



Would You Believe

The World's First Pocket T.V.

Pictured In Actual Size: 4" x 6 3/4" x 1 3/4"
Wt.: 26 1/2 oz. Fits In The Palm Of Your Hand!

Ideal For An Office, Home, In Bed, On Vacation & Business Trips, In Your Car, Boat, Camper, Plane Overseas Trips. Looks & Carries Like a Calculator.

• Designed and Manufactured In England by Sinclair • "Multiple Standard Reception" Works In USA, UK, and Europe! • Exceptionally Brilliant, High Resolution Reception • Completely Self-Contained: Built-In Antenna, RECHARGEABLE BATTERIES, AC ADAPTOR, AND Cigarette Lighter AUTO PLUG

Even these Photographs Can't Fully Emphasize The Unique "Hand-Held" Pocket-Size Format of the Sinclair "MicroVisions". You simply have to experience the amazement of watching the news on a 26 1/2 oz. TV resting in the palm of your hand! Yet it is a High-Precision black and white T.V. Receiver (made 100% in England by Conscientious Professionals), and more . . .

This T.V. Works Anywhere In The World. Wherever you go, if there's a TV Signal, *Only* the "MicroVision" Will Almost Certainly Pick It Up. Due to Its Sophisticated, Multiple-Standard Reception System. Its High-Performance, Miniature 2" diagonal screen gives you an exceptionally sharp, brilliant picture of incredible detail. At a distance of 1 foot, the picture is of equivalent size and brilliance to that of compact portables at a distance of 6 feet, or to that of 25" models at 12 feet! The Built-In Loudspeaker gives superb sound also.



As In The Finest Cameras and Watches, Quality Performance Is As Important As Size. The "MicroVision" has a uniquely high specification. VHF and UHF Tuners are as sensitive as they can be . . . Delayed Automatic Gain Control . . . Continuous Tuning . . . Automatic Frequency Control . . . Features Seldom Found in the most expensive b/w sets!

Important Technical Specifications (Please Read): • Rugged Construction Includes Tough, Steel Case, Solid-State Circuitry Throughout • Picture Tube is Carefully Protected and Snugly Embedded—Safe & Strong (Perfectly Safe In The Mail or Packed In A Suitcase) • 12 Month Manufacturer's Replacement or Repair Warranty — Fast, Efficient U.S. Service Facility • Push-Button Selection For US, UK, or European Transmissions • Push-Button UHF/VHF • Separate Brightness, Contrast, Line-Hold and Frame-Hold Controls • Vision is High Linearity • Delayed AGC, AFC • Built-In, Powerful Signal Aerials (telescopic for VHF, Loop for UHF) • Power: Includes 4 Standard Batteries, Rechargeable Batteries, 12V Car Battery Converter Plug, AC Adaptor/Recharger • Carrying Case & Ear-Phone.

Call Toll-Free: 1-800-528-6050 Ext. 1041. Ariz. Res. Call Collect 602-955-9710.

Two Week Trial Order Form (Please allow 4 weeks for deliveries) Please ship _____ Sinclair Micro-Vision Television Receiver(s) plus all accessories @ \$395 (plus \$5 shipping and insurance) each. If not Satisfied I may return it within two weeks of receipt for an immediate refund.

- Check or M.O. Enclosed (Calif. Res. Add 6% Sales Tax)
 Charge My Credit Card Number: _____
 BankAmericard/Visa Master Charge (Interbank # _____)
 American Express Diners Club
 Carte Blanche

Credit Card # _____ Exp. _____

Name _____

Address _____

City/State/Zip _____

Signature _____

Starshine Group.

Dept. 239, 924 Anacapa Street, Santa Barbara, CA 93101

Starshine, Inc. 1977

"bad" throw-away TV module (which, of course, I couldn't bring myself to throw out!). This one had two identical IC's. A cross-check between the two showed distinctly different patterns between the same test points on the IC. So, we knew that one of the IC's was bad.

The instruction manual shows all the good and bad traces that can be expected for any type of part—bipolars, FET's, diodes of all kinds, even SCR's and many four-layer devices.

A handy supplementary brochure entitled the "Prober" comes with the *Tracker*. It contains quite a few specialized tests and hints on how to identify patterns, etc. This supplement is expected to be a continuing service; as new *Tracker* applications are discovered, they will be sent out to the users.

If it is properly used, the *Tracker* should be a useful instrument for all kinds of solid-state circuitry. The long *Micro-Probe* test leads make it very easy to get down into tight places, and the sharp probe tips also make it simple to test IC's from the top.

If you do repair your own modules, this instrument should be a big help by making fast cross-checking and comparison tests possible. Another good trick: the *Tracker* should make it a lot faster to service those jam-packed, no-schematic little FM/AM radio receivers. You can check all transistors from the top in only a short time. **R-E**

Kager Model KL 3000 Auto-Feed Soldering Pistol



CIRCLE 149 ON FREE INFORMATION CARD

ALL MY WORKING LIFE I'VE KEPT A SHARP EYE out for time-saver tools, those small but useful items that will do only one thing but do it faster or easier.

I've just run into a new one: the Kager model KL 3000 One-Handed Soldering Pistol manufactured by Kager International, Suite 710, 1180 South Beverly Dr., Los Angeles, CA 90035. The basic model retails for \$38. This gun is not a soldering gun, but a solder-feeding "pistol" that weighs less than half a pound, in the box!

It has a good-sized plastic pistol grip. The heating element is mounted in the upper part of the pistol. A guide tube feeds the solder directly onto the joint. The flow is controlled by a trigger that does *not* control the heat, which is on continually.

This tool should be useful for any kind of PC-board work. It should also be a whizz at assembling all kinds of kits, especially those with many closely spaced joints, such as IC's, etc. Normally, you have to hold the board with one hand, hold the part in place with the other,

continued on page 119

322 WAYS TO INCREASE YOUR ELECTRONICS KNOW-HOW!

SEND NO MONEY! We'll invoice you on 10-DAY FREE TRIAL. ALL BOOKS 100% GUARANTEED. You must be satisfied or return the books and we'll cancel the invoice.

COMPUTERS, CALCULATORS & MICROPROCESSORS

- 995—Beginner's Guide to Microprocessors 182 p. 106 il. \$5.95
- 1000—57 Practical Programs & Games in BASIC 210 p. 64 il. \$7.95
- 985—Programming Microprocessors 280 p. 102 il. \$6.95
- 971—Microprocessors from Calculators to Computers 196 p. \$5.95
- 874—Master Handbook of Digital Logic Appls. 392 p. 287 il. \$7.95
- 952—Microprocessor Programming for Computer Hobbyists 387p. \$8.95
- 955—Modern Digital Communications 308 p. 122 il. \$6.95
- 975—The "Computer" Book—Build Super Calculators & Minicomputer Home with Calculator Chips 322 p. 227 il. \$7.95
- 752—Computer Programming Handbook 518 p. 114 il. \$9.95
- 554—Computer Technician's Handbook 480 p. 428 il. \$9.95
- 824—Advanced Applications for Pocket Calculators 304 p. 275 il. \$5.95
- 538—Computer Circuits & How They Work 192 p. 109 il. \$5.95
- 574—Beginner's Guide to Computer Programming 460 p. 364 il. \$9.95
- 785—Microprocessor/Microprogramming Hdbk. 294 p. 176 il. \$6.95
- 709—Modern Guide to Digital Logic 294 p. 222 il. \$6.95
- 724—Get the Most Out of Electronic Calculators 204 p. 28 il. \$4.95
- 546—Beginner's Guide to Computer Logic 192 p. 175 il. \$5.95

COMMUNICATIONS & AMATEUR RADIO

- 801—Master Handbook of Ham Radio Circuits 392 p. 301 il. \$8.95
- 1005—Hdbk of Solar Flare Monitoring & Prop. Forecasting 196 p. \$6.95
- 963—Home-Brew HF/VHF Antenna Handbook 210 p. 143 il. \$5.95
- 959—Cber's Handy Manual of SSB 80 p. 42 il. \$2.25
- 685—The Complete Shortwave Listener's Handbook 192 p. 36 p. \$6.95
- 683—Pictorial Guide to CB Radio Installation 304 p. 169 il. \$3.95
- 673—How to Be a Ham Radio Technician 200 p. 25 il. \$3.95
- 950—111 Dict. of Broadcast—CATV—Telecomms. 420 p. 104 il. \$8.95
- 799—CB Radio Operator's Guide—2nd Edition 256 p. 139 il. \$5.95
- 655—Modern Electronics Math 686 p. 424 il. \$9.95
- 899—Cber's Handy Manual 48 p. \$1.50
- 735—The Complete FM 2-Way Radio Handbook 294 p. 111 il. \$6.95
- 859—The Complete Handbook of Ground Wave 304 p. 169 il. \$3.95
- 645—Practical CB Radio Troubleshooting & Repair 406 p. 169 il. \$7.95
- 608—VHF Projects for Amateur & Experimenter 224 p. 262 il. \$4.95
- 597—RTTY Handbook 320 p. 230 il. \$6.95
- 933—Cber's Handy Atlas Dictionary 64 p. \$1.95
- 722—Amateur FM Conversion & Const. Projects 256 p. 187 il. \$5.95
- 678—Modern Communications Switching Systems 276 p. 171 il. \$7.95
- 581—Citizens Band Radio Service Manual 288 p. 64 il. \$5.95
- 621—The 2-Way Radio Operator's Handbook 312 p. 194 il. \$6.95
- 468—104 Ham Radio Projects for Novice & Tech. 192 p. 104 il. \$4.95

HOBBY ELECTRONICS & PROJECTS

- 841—Build Your Own Working Robot 238 p. 83 il. \$5.95
- 958—Beginner's Guide to Making Elec. Gadgets 140 p. 113 il. \$4.95
- 921—The ABC Book of Hi-Fi/Audio Projects 168 p. 131 il. \$4.95
- 909—How to Build Metal/Treasure Locators 140 p. 60 il. \$3.95
- 935—Build-It Book of Optoelectronic Projects 238 p. 175 il. \$5.95
- 964—Modern Crystal Radios (Make and Use Senses) 94 p. 101 il. \$2.50
- 637—Fun with Electronics 140 p. 50 il. \$3.95
- 836—Optoelectronic Guidebook with Projects 196 p. 115 il. \$5.95
- 905—Build-It Book of Guided Electronic Timepieces 294 p. 209 il. \$6.95
- 926—Model Railroad Electronics 308 p. 218 il. \$5.95
- 912—88 Practical Op Amp Circuits You Can Build 140 p. 120 il. \$4.95
- 868—Cber's Handybook of Simple Hobby Projects 168 p. 114 il. \$3.95
- 897—106 Easy Elec. Projects (Make and Use) 224 p. \$5.95
- 790—21 Simple Transistor Radios You Can Build 140 p. 122 il. \$3.95
- 726—Practical Circuit Design for the Experimenter 196 p. 119 il. \$4.95
- 861—Display Electronics 252 p. 195 il. \$5.95
- 679—Electronics for Shutterbugs 204 p. 109 il. \$5.95
- 771—Integrated Circuits Guidebook 196 p. 119 il. \$5.95
- 667—Miniature Projects for Electronic Hobbyists 168 p. 77 il. \$3.95
- 787—OP AMP Circuit Projects & Applications 280 p. 239 il. \$6.95
- 796—MOSFET Circuits Guidebook with 100 Projects 322 p. 196 il. \$4.95
- 714—Radio Astronomy for the Amateur 252 p. 88 il. \$5.95
- 730—Effective Troubleshooting with EVM & Scope 238 p. 185 il. \$5.95
- 571—Radio-Electronics Hobby Projects 192 p. 214 il. \$4.95
- 591—Solid-State Projects for the Experimenter 224 p. 228 il. \$4.95
- 780—111 Digital Logic Projects & Applications 280 p. 241 il. \$5.95
- 699—Solid-State Circuits Guidebook 252 p. 227 il. \$5.95
- 524—104 Easy Projects for Electronics Gadgets 160 p. 105 il. \$4.95
- 553—Electronics Self-Taught with Exp. & Projects 288 p. 191 il. \$5.95
- 695—Practical Trac-SCR Proj. for Experimenters 192 p. 146 il. \$4.95
- 486—104 Simple One Tube Projects 192 p. 104 il. \$3.95
- 628—Handbook of IC Circuit Projects 224 p. 136 il. \$4.95
- 487—64 Channel Stereo From Home & Car 192 p. 159 il. \$4.95
- 537—125 One-Transistor Projects 192 p. 125 il. \$4.95
- 83—Fun with Electricity 128 p. 94 il. \$3.95
- 647—Stereo/Quad Hi-Fi Principles & Projects 192 p. 100 il. \$4.95
- 540—Electronic Experimenter's Guidebook 182 p. 86 il. \$4.95
- 614—Electronic Hobbyist's IC Project Handbook 154 p. 86 il. \$4.95
- 464—New IC FET Principles & Projects 154 p. 86 il. \$4.95
- 462—104 Electronic Projects You Can Build 224 p. 105 il. \$5.95
- 590—Practical Solid-State Principles & Projects 176 p. 127 il. \$3.95
- 129—New Skill-Building Transistor Projects & Exp. 192 p. 129 il. \$4.95
- 568—IC Projects for Amateur & Experimenter 192 p. 252 il. \$5.95
- 424—Transistor Projects for Hobbyists & Students 192 p. 153 il. \$4.95
- 189—Transistor Projects 160 p. 123 il. \$2.95
- 70—Electronic Puzzles & Games 128 p. 75 il. \$3.95
- 112—Learn Electronics by Building 208 p. 214 il. \$4.95

AUDIO, RECORDING, HI-FI & STEREO

- 875—Microphones—How Work & How to Use Them 224 p. 97 il. \$5.95
- 646—Acoustic Techniques for Home & Studio 224 p. 168 il. \$5.95
- 781—Handbook of Multichannel Recording 322 p. 196 il. \$7.95
- 934—Photo Guide to AM/FM Stereo Repair 288 p. 261 il. \$6.95
- 632—Pictorial Guide to Tape Recorder Repairs 256 p. 320 il. \$4.95
- 756—4 Channel Stereo From Home & Car 192 p. 159 il. \$4.95
- 634—Basic Audio Systems 240 p. 302 il. \$4.95
- 689—Cassette Tape Recorders—How Work/Care/Repair 204 p. \$5.95
- 497—Tape Recording for Fun & Profit 224 p. 171 il. \$5.95
- 484—Audio Systems Handbook 192 p. 125 il. \$4.95
- 611—Questions & Answers About Tape Recording 264 p. 102 il. \$5.95
- 716—Servicing Cassette & Cartridge Tape Players 294 p. \$5.95
- 505—Installing & Repairing Home Audio Systems 224 p. 136 il. \$5.95
- 67—Elements of Tape Recorder Circuits 224 p. 145 il. \$4.95
- 642—Jap Radio, Record & Tape Player Service Manual 228p. \$6.95
- 86—Installing Hi-Fi Systems 224 p. 152 il. \$5.95
- 59—Servicing Record Changers 224 p. 173 il. \$5.95
- 529—Handbook of Magnetic Recording 224 p. over 90 il. \$4.95

APPLIANCES, ELECTRICITY & ENERGY

- 967—Heating Aid Handbook 336 p. 224 il. \$8.95
- 913—Complete Hi-Fi Electrical Use Wiring 476 p. 196 il. \$6.95
- 900—Homeowner's Guide to Solar Heating/Cooling 196 p. 113 il. \$4.95
- 962—Microwave Oven Service & Repair 420 p. 210 il. \$9.95
- 903—Guide to Modern Energy-Efficient Heating/Cooling Sys. \$5.95
- 1030—How to Completely Secure Your Home 224 p. 162 il. \$5.95
- 758—101 Practical Uses for Propane Torches 140 p. 83 il. \$3.95
- 1006—Build-It Book of Solar Heating Projects 196 p. 111 il. \$4.95
- 826—Central Heating/Air Cond. Repair Guide 320 p. 285 il. \$6.95

- T-97—Electric Motor Test & Repair 160 p. 102 il. \$6.95
- 515—Small Appliance Repair Guide-Vol. 1 224 p. 100 il. \$5.95
- 917—How to Repair Small Gasoline Engines 392 p. 251 il. \$6.95
- 904—Homeowner's Guide to Saving Energy 288 p. 169 il. \$5.95
- 745—The Home Appliance Clinic 195 p. 61 il. \$4.95
- 885—How to Repair Home Kitchen Appliances 294 p. 205 il. \$5.95
- 920—Complete Repair of Locks & Locksmithing 392 p. 348 il. \$5.95
- 855—How to Repair Home Appliances 260 p. 137 il. \$5.95
- 715—Small Appliance Repair Guide-Vol. 2 210 p. 119 il. \$4.95
- 555—Major Appliance Repair Guide 288 p. 278 il. \$5.95
- 671—Electrical Wiring & Lighting for Home & Office 204 p. 155 il. \$4.95
- 520—How to Repair Home & Auto Air Conditioners 208 p. 100 il. \$5.95
- 296—Refrigerator 160 p. 53 il. \$3.95

FCC LICENSE STUDY GUIDES

- 582—General FCC License Handbook 444 p. 150 il. \$6.95
- 595—2nd Class FCC Encyclopedia Study Guide 602 p. 445 il. \$7.95
- 630—Third Class FCC License Study Guide 308 p. 88 il. \$6.95
- 873—Ham Radio Novice Class License Study Guide 224 p. 57 il. \$5.95
- 851—Ham Radio General Class License Study Guide 448 p. \$7.95
- 827—Ham Radio Advanced Class License Study Guide 252 p. \$5.95
- 434—Ham Radio Extra Class License Study Guide 224 p. 162 il. \$5.95
- 969—Ham Radio Incentive Licensing Guide 154 p. 70 il. \$4.95

SEMICONDUCTORS, TUBES & TRANSISTORS

- 856—Master OP Amp Applications Handbook 476 p. 320 il. \$9.95
- 1016—Towers' International FET Selector 140 p. \$4.95
- 960—IC Function Locator 224 p. \$5.95
- 984—CMOS Databook 280 p. 270 il. \$6.95
- 870—Master Tube Substitution Handbook 548 p. 322 il. \$4.95
- 1010—Towers' Inter Transistor Selector 200 p. 179 il. \$6.95
- 970—Master Transistor/IC Substitution Handbook 518 p. 165 il. \$7.95
- 717—Transistor Theory for Technicians 488 p. 224 p. 116 il. \$4.95
- 638—Linear IC Applications Handbook 280 p. 183 il. \$6.95
- 470—Transistor Circuit Guidebook 224 p. 118 il. \$5.95
- 794—Microelectronics 266 p. 228 il. \$5.95
- 708—Modern Applications of Linear IC's 276 p. 301 il. \$9.95
- 501—Working with Semiconductors 224 p. 185 il. \$4.95
- 75—Transistors—Theory & Practice 160 p. 138 il. \$4.95
- 613—Understanding Solid-State Circuits 192 p. 104 il. \$4.95
- 63—Transistor Circuits 160 p. 144 il. \$4.95
- 116—Getting Started with Transistors 160 p. 90 il. \$3.95
- 493—Semiconductors from A to Z 272 p. 300 il. \$5.95
- 61—Transistor Techniques 96 p. 76 il. \$3.95

BASIC & GENERAL ELECTRONICS TECHNOLOGY

- 510—How to Read Electronic Circuit Diagrams 192 p. 140 il. \$4.95
- 588—Basic Electronics Course 384 p. 275 il. \$6.95
- 891—Practical Solid-State IC Power Supplies 196 p. 151 il. \$6.95
- 628—Basic Electricity & Beginning Electronics 252 p. 191 il. \$5.95
- 830—Introduction to Medical Electronics 320 p. 126 il. \$7.95
- 655—Modern Electronics Math 686 p. 424 il. \$9.95
- 728—Basic Digital Electronics 210 p. 117 il. \$4.95
- 691—Electronics Unraveled 228 p. 96 il. \$5.95
- 828—Switching Regulators & Power Supplies 252 p. 128 il. \$6.95
- 683—Practical IC Applications Handbook 280 p. 380 il. \$8.95
- 930—Servicing Medical & Biomedical Equipment 350 p. 165 il. \$8.95
- 300—Dictionary of Electronics 420 p. 487 il. \$4.95
- 601—Basic Color Television Course 420 p. over 300 il. \$9.95
- 575—Modern Radar—Theory, Oper. & Maint. 480 p. 253 il. \$7.95
- 104—Basic Radio Course—224 p. 128 il. \$5.95
- 638—Marine Solid-State IC Power Supplies 192 p. 106 il. \$4.95
- 628—Pulse & Switching Circuits 256 p. 184 il. \$5.95
- 585—Digital Electronics. Principles & Practice 292 p. 191 il. \$5.95
- 105—Basic TV Course 224 p. 128 il. \$5.95
- 111—Basic Transistor Course 224 p. 179 il. \$5.95

ELECTRONIC MUSIC

- 743—Electronic Music: Circuit Guidebook 224 p. 180 il. \$6.95
- 843—Sourcebook of Electronic Organ Circuits 168 p. 101 il. \$3.95
- 910—How to Repair Solid-State Hi-Fi Instrument Amplifiers 288 p. 50 il. \$5.95
- 718—Electronic Music: Production 156 p. 79 il. \$3.95
- 666—Experimenting with Electronic Music 180 p. 103 il. \$4.95
- 546—Electronic Musical Instrument 192 p. 121 il. \$5.95
- 832—Electronic Musical Instr. Manual 210 p. 7x10" 385 il. \$6.95
- 503—Servicing Electronic Organs 196 p. 8x11" 145 il. \$9.95

ELECTRONIC TEST EQUIPMENT

- 792—Build-It Book of Miniature Test & Msm. Instr. 238 p. 151 il. \$4.95
- 474—Working with the Oscilloscope 104 p. 183 il. \$4.95
- 672—Understanding & Using the VOM & EVM 192 p. 187 il. \$5.95
- 927—How to Use AF & RF Signal Generators 238 p. 162 il. \$5.95
- 702—Electronic Measurements Simplified 240 p. 217 il. \$4.95
- 729—RF & Digital Test Equipment You Can Build 252 p. 217 il. \$5.95
- 877—Under & Using Modern Signal Generators 294 p. 120 il. \$6.95
- 664—Understanding & Using the Oscilloscope 272 p. 170 il. \$5.95
- 577—How to Use Color TV Test Instruments 256 p. 234 il. \$4.95
- 669—Practical Test Instruments You Can Build 204 p. 157 il. \$4.95
- 131—Test Instruments for Electronics 192 p. 155 il. \$4.95
- 680—How to Test & Repair Electr. Test Equip. 252 p. 143 il. \$6.95
- 777—Under Using Modern Electr. Svngng. Test Equip. 252 p. \$5.95
- 498—The Oscilloscope—Third Edition 264 p. 169 il. \$5.95
- 483—99 Ways to Use Your Oscilloscope 252 p. 327 il. \$5.95
- 895—How to Use Test Instruments 256 p. 234 il. \$4.95
- 627—Basic Electronic Test Procedures 416 p. 178 il. \$6.95
- 550—Vectorscopes Scopes Sweep-Marker Generators 256 p. \$5.95

ENGINEERING & REFERENCE

- 800—Master Hdbk of 1001 Practical Electronic Circuits 602 p. \$9.95
- 742—Pro. Electrical/Electr. Engr's License Study Guide 476 p. \$7.95
- 750—Electronic Conversions, Symbols & Formulas 224 p. 46 il. \$4.95
- 782—Reference 196 p. 90 il. \$3.95
- 774—Digital Logic Electronics Handbook 308 p. 226 il. \$5.95
- 118—Electronics Data Handbook 256 p. 149 il. \$5.95
- 101—Electronic Circuit Design Hdbk.—4th Ed. 416 p. 966 il. \$17.95
- 30—Handbook of Semiconductor Circuits 444 p. 317 il. \$5.95
- 288—Circuit Consultant's Gasebook 224 p. 144 il. \$5.95
- 125—Handbook of Electronic Tables 224 p. 16 il. \$4.95
- 513—Electronic Engineering Tables 178 p. 8x11" 124 il. \$9.95
- 110—Electronic Design Charts 128 p. \$8.95
- 121—Charts & Nomographs for Techs & Engrs. 96 p. 8x11" 75.95

TV, RADIO & ELECTRONIC SERVICING

- 901—CET License Handbook—2nd Edition 448 p. 169 il. \$8.95
- 919—Color TV Trouble Factbook 612 p. 612 il. \$5.95
- 821—TV Troubleshooter's Handbook—3rd Ed. 448 p. over 300 il. \$4.95
- 563—Beginner's Guide to TV Repair 176 p. 90 il. \$4.95
- 956—Fire & Theft Security Systems—2nd Ed. 192 p. 108 il. \$5.95
- 715—Color TV Case Histories Illustrated—Vol. 2 252 p. 243 il. \$7.95
- 746—Color TV Case Histories Illustrated—Vol. 3 219 il. \$5.95
- 809—PhotoGuide: Solid-State Color TV Troubles 224 p. 169 il. \$5.95
- 730—Effective Troubleshooting with EVM & Scope 238 p. 185 il. \$5.95
- 772—Troubleshooting with the Dual-Trace Scope 224 p. 252 il. \$5.95
- 738—TV Schematics: Reading Between the Lines 252 p. 188 il. \$5.95
- 132—How to Test Almost Everything! Electronic 160 p. 144 il. \$3.95
- 604—How to Use Electronic Test Instruments 256 p. 160 il. \$5.95
- 696—TV Tuner Schematic/Servicing Manual-Vol. 1 224 p. 287 il. \$6.95
- 979—TV Tuner Schematic/Servicing Manual-Vol. 2 200 p. 374 il. \$6.95
- 633—Simplified TV Trouble Diagnosis 320 p. 292 il. \$5.95
- 690—Logical Color TV Troubleshooting 240 p. 151 il. \$5.95
- 595—199 TV Tough-Dog Problems Solved 252 p. 199 il. \$5.95
- 580—Modern Radio Repair Techniques 260 p. 201 il. \$5.95
- 616—How to Interf. TV Protective Systems 252 p. 250 il. \$4.95
- 532—How to Repair Solid-State Imports 192 p. 8 1/2" x 11" 122 il. \$7.95

- 644—Pictorial Guide to Color TV Circuit Troubles 256 p. 262 il. \$4.95
- 484—TV Servicing Guidebook 176 p. 110 il. \$4.95
- 761—Jack Darr's Service Clinic No. 3 252 p. 122 il. \$4.95
- 133—Jack Darr's Service Clinic No. 1 192 p. 125 il. \$4.95
- 428—Pinpoint TV Troubles in 10 Minutes 327 p. 394 il. \$5.95
- 682—TV Bench Servicing Techniques 228 p. 77 il. \$4.95
- 598—All-in-One TV Alignment Handbook 304 p. 145 il. \$5.95
- 517—Home-Call TV Repair Guide 144 p. 20 il. \$3.95
- 430—Pinpoint Transistor Troubles in 12 Minutes 492 p. 243 il. \$6.95
- 595—199 Color TV Troubles & Solutions 224 p. 178 il. \$5.95
- 70—Electronic Puzzles & Games 128 p. 75 il. \$3.95
- 507—101 TV Troubles: From Symptom to Repair 224 p. 170 il. \$5.95
- 619—T-Shooting Solid-State Electr. Power Supplies 192 p. 85 il. \$4.95
- 778—All-in-One TV Servicing Manual 240 p. 367 il. \$6.95
- 653—T-Shooting Solid-State Wave Gen. & Shaping Circuits \$4.95
- 636—Installing TV & FM Antennas 168 p. 158 il. \$4.95
- 593—199 Electronic Test & Alignment Techniques 224 p. 130 il. \$4.95
- 835—VHF/UHF Fire, Police, Ham Scanners Serv. Manual 250p. \$6.95
- 660—FM Stereo-Quad Receiver Servicing Manual 192 p. 130 il. \$4.95
- 706—Indexed Guide to Modern Electronic Circuits 216 p. 92 il. \$4.95
- 504—How to Fix Transistor Radios & Printed Circs. 256 p. 150 il. \$4.95
- 625—Troubleshooting Solid-State Amplifiers 256 p. 95 il. \$4.95
- 429—Easy Way to Service Radio Receivers 176 p. 100 il. \$3.95
- 732—Jap Consumer Electr. Serv. Manual 196 p. 36 p. 8x11" \$5.95
- 694—Auto Stereo Service & Installation 252 p. 245 il. \$5.95

MODEL RADIO CONTROL

- 825—Flying Model Airplanes/Helicopters by RC 192 p. 140 il. \$4.95
- 747—RC Modeler's Handbook of Gliders & Sailplanes 196 p. 90 il. \$4.95
- 812—Radio Control for Models 350 p. 417 il. \$6.95
- 693—Model Sail & Power Boating by Remote Cont. 192 p. 125 il. \$4.95
- 135—Radio Control Manual—2nd Edition 192 p. 158 il. \$4.95
- 122—Advanced Radio Control 192 p. 181 il. \$4.95
- 592—Model Car Racing, by Remote Control 224 p. 250 il. \$3.95
- 83—Fun with Electricity 128 p. 94 il. \$3.95
- 74—Model Radio Control 192 p. 192 il. \$4.95

BROADCAST, CATV, CCTV & VIDEOTAPE

- 811—Complete Hdbk of Videocassette Recorders 280 p. 160 il. \$5.95
- 852—B-Cast Eng. & Maintenance Hdbk 532 p. 235 il. \$19.95
- 815—Design/Maintain CATV/Small TV Studio 288 p. 100 il. \$12.95
- 1009—CCTV Installation, Maintenance & Repair 294 p. \$8.95
- 773—Talk-Back TV—Two-Way Cable Television 238 p. 64 il. \$5.95
- 833—Complete Broadcast Antenna Handbook 448 p. 308 il. \$9.95
- 657—Antenna Systems Handbook \$5.95
- 623—Guide to Radio TV Base Engng. Pract. 288 p. 140 il. \$12.95
- 298—CATV Systems Engineering—3rd Ed. 256 p. 141 il. \$12.95
- 733—Directional Broadcast Antennas 210 p. 60 il. \$12.95
- 557—How To Become A Radio Disc Jockey 256 p. 36 il. \$12.95
- 845—How to Prepare a Production Budget, Film & Videotape \$12.95
- 511—Videotape Prod. & Comm. Techniques 256 p. 100 il. \$12.95
- 793—TV Lighting Handbook 228 p. 230 il. \$12.95

COLOR TV SCHEMATIC/SERVICING MANUALS

- Each vol has complete service data, parts lists, full-size schematic layout section, and all other info needed. Each 8 1/2" x 11", only \$5.95 unless otherwise marked.
- 662—Svngng. New Modular Color TV Recvr's Vol. 1 176 p. \$6.95
 - 663—Svngng. New Modular Color TV Recvr's Vol. 2 178 p. \$4.95
 - 545—Admiral Vol. 1 196 p. 12 schematics \$6.95
 - 641—Admiral Vol. 2 196 p. 11 schematics \$5.95
 - 741—Arlime (Montgomery Ward) 196 p. 12 schematics \$5.95
 - 536—General Electric Vol. 1 196 p. 12 schematics \$5.95
 - 609—General Electric Vol. 2 212 p. 10 schematics \$5.95
 - 560—Japanese Vol. 1—Sony, Sharp, Midland 212 p. \$5.95
 - 576—Jap Vol. 2—Delmonico, Hitachi, Panasonic, etc. 212 p. \$5.95
 - 684—Japanese Vol. 3—Hitachi, Sanyo, Coronado 228 p. \$4.95
 - 740—Jap Vol. 4—Sharp, Midland, MGA 236 p. 36 p. layout \$5.95
 - 706—Japanese Vol. 5—Sony 196 p. 36 p. layout \$5.95
 - 520—Magnavox Vol. 1 196 p. 12 schematics \$7.95
 - 589—Magnavox Vol. 2 196 p. 9 schematics \$5.95
 - 770—Magnavox Vol. 3 196 p. 36 p. schematic layout \$5.95
 - 509—Motorola Vol. 1 178 p. 6 schematics \$4.95
 - 544—Motorola Vol. 2 196 p. 9 schematics \$7.95
 - 522—Phico 196 p. 12 schematics \$5.95
 - 496—RCA Vol. 1 212 p. 12 schematics \$5.95
 - 478—RCA Vol. 2 212 p. 12 schematics \$5.95
 - 720—RCA Vol. 3 196 p. 12 schematics \$5.95
 - 721—RCA Vol. 4 196 p. 12 schematics \$5.95
 - 822—RCA Vol. 5 196 p. 36 p. schematic section \$5.95
 - 740—Sears 228 p. 12 schematics \$5.95
 - 539—Sylvania Vol. 1 196 p. 12 schematics \$5.95
 - 618—Sylvania Vol. 2 212 p. 8 schematics \$5.95
 - 760—Toshiba 160 p. 12 schematics \$5.95
 - 502—Zenith Vol. 1 196 p. 12 schematics \$7.95
 - 562—Zenith Vol. 2 196 p. 12 schematics \$5.95
 - 606—Zenith Vol. 3

Measure resistance to $.01\Omega$ at a price that has no resistance at all.



The new B&K-PRECISION Model 2810 may well be the highest resolution $3\frac{1}{2}$ -digit DMM available. It is certainly the lowest cost DMM to provide $.01\Omega$ resolution. With ohms resolution ten times greater than most DMM's, the 2810 allows you to detect shorted windings in coils, transformers or motors.

You'll also be able to accurately check the low contact resistance of switches, relays, breaker points or connectors. Many poor solder connections or PC board imperfections can also be located.

The 2810 is a full-feature DMM providing selectable high-/low-power ohms, auto-zeroing and 100% overrange reading. Twenty-nine ranges provide maximum readings to 1500 volts DC, 2

amps, and 20 megohms. All ranges are fully overload protected. Typical DC accuracy is 0.5% with resolution to $100\mu\text{V}$. And unlike many electronic voltmeters, the 2810 is RFI shielded and can be accurately used in high R-F energy fields.

B&K-PRECISION also has a full complement of optional accessories for the 2810. Accessories include a carrying case, wire tilt stand, AC adapter/charger, high-voltage probe, direct/isolation probe, NiCad batteries and 10-amp current shunt.

At \$119.95, the 2810 is a standout value in today's DMM jungle. Don't resist the temptation...contact your local distributor for immediate delivery.

BK PRECISION DYNASCAN
CORPORATION

6460 West Cortland Avenue, Chicago, Illinois 60635 • 312 / 889-9087

In Canada: Atlas Electronics, Ontario

International Sales: Empire Exporters, 270 Newtown Rd., Plainville, LI. N.Y. 11803

CIRCLE 106 ON FREE INFORMATION CARD

BUILD

Automotive/Marine Digital Tachometer



Operate your car or boat at maximum efficiency by monitoring engine speed. This easy-to-build tach lets you keep a finger on your engine's pulse

MICHAEL H. KUHN

A CONSTANT AND ACCURATE CHECK ON engine RPM's is essential to the motor-boatsman for the following reasons:

1. It is vital if the boat is to be operated at top efficiency and maximum fuel economy. By running a measured course at a constant engine speed, it is possible for the operator to determine fuel consumption per mile and per hour under average conditions.
2. Engine speed can be a valuable navigation aid. Knowing the dis-

tance between two buoys or other points, an experienced boatsman can determine the engine speed needed to traverse the two points in a given time.

3. Similarly, knowing the craft's most economical cruising speed, the pilot will be able to estimate the sailing time between two known points.
4. Perhaps the most important reason for knowing the speed of a marine engine is the relationship


between RPM's and cruising range. Safety afloat demands that the pilot know how much fuel he must have on board to reach his destination or an intermediate fueling point with an adequate reserve.

An accurate engine-speed indicator is an important instrument for an aware automobile driver. For only by knowing engine RPM's can he obtain most efficient performance with minimum strain on the engine.

This digital tachometer overcomes the ambiguous swing of the analog-meter instrument. It can be used to measure the speed of 2- or 4-cycle automobile and marine engines having from two to sixteen cylinders. It works on any 12 to 24 volt DC electrical system that has a negative ground. Its 7-segment display is visible in darkness and shaded or dim sunlight and is not bright enough to affect the night-vision of a driver or pilot.

How it works

Digital and analog electronic tachometers operate by processing the voltage pulses developed by the make-and-break of the breaker points of an internal combustion engine. These tachometers are basically frequency counters modified to indicate revolutions per minute. Before going further, let's look at the operation of a 4-cycle internal combustion engine. (1) The points open and close once per crankshaft revolution per cylinder. (2) For all cylinders to fire (regardless of the number of cylinders) the crankshaft makes *two* revolutions. (3) The distrib-

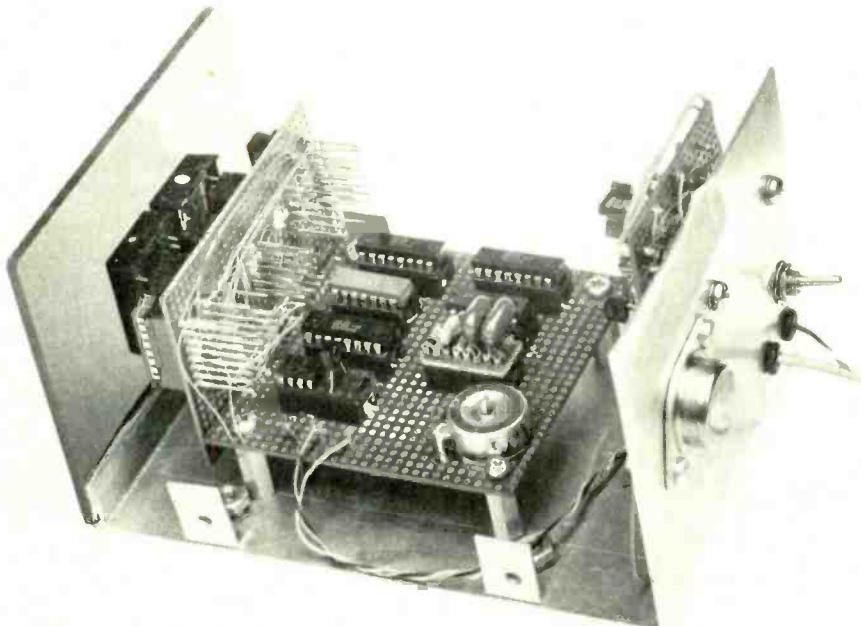

PERF-BOARD AND WIRE-WRAP was used exclusively to build the prototype. A total of three separate perf-boards was used.

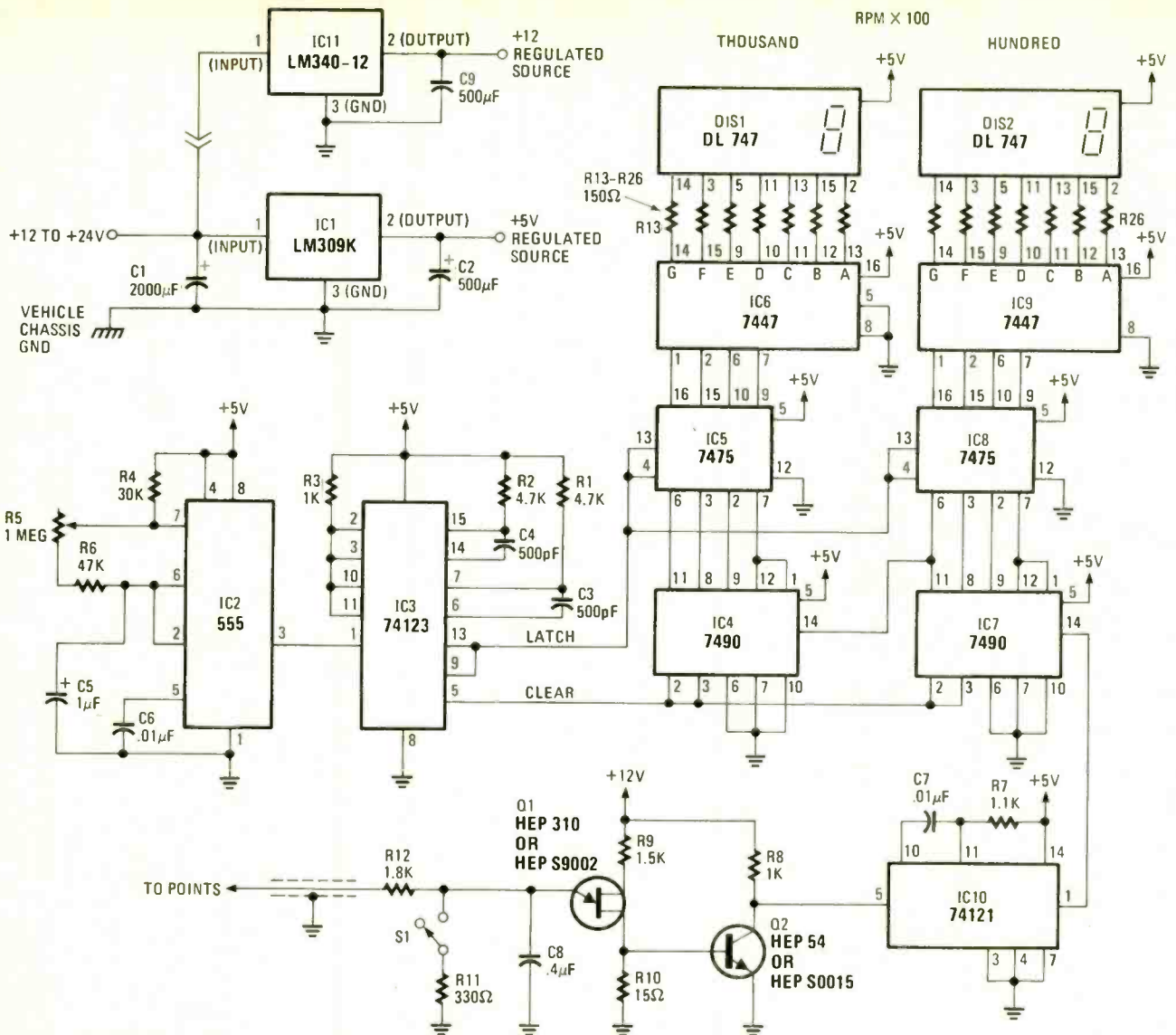


FIG. 1—TACHOMETER provides a direct readout of RPM \times 100 on a 2-digit 7-segment LED display.

C1—200 μ F, 50V, electrolytic
 C2, C9—500 μ F, 50V, electrolytic
 C3, C4—500 μ F, 50V, tantalum
 C5—1 μ F, 50V, electrolytic
 C6, C7—.01 μ F, 50V, disc
 C8—.4 μ F, 50V, disc
All resistors are 1/4 watt, 5%.
 R1, R2—4700 ohms
 R3, R8—1000 ohms
 R4—30,000 ohms
 R5—1 megohm potentiometer

PARTS LIST

R6—47,000 ohms
 R7—1100 ohms
 R9—1500 ohms
 R10—15 ohms
 R11—330 ohms
 R12—1800 ohms
 R13—R26—150 ohms
 Q1—HEP310
 Q2—HEP54

IC1—LM309K
 IC2—555
 IC3—74123
 IC4, IC7—7490
 IC5, IC8—7475
 IC6, IC9—7447
 IC10—74121
 IC11—LM340-12
 S1—SPST toggle
 DIS1, DIS2—DL747 common-anode 7-segment LED display

utor makes one-half revolution during each revolution of the crankshaft.

Since the distributor makes one revolution for every two revolutions of the crankshaft (No. 3 above) and since the crankshaft must make two revolutions for all cylinders to fire; the distributor points make-and-break—during each crankshaft revolution—only one-half as many times as the number of cylinders. Thus, in a 6-cylinder engine, the points make-and-break only three times for each engine revolution. Therefore, the tachometer

divides the number of pulses picked up from the distributor by half the number of cylinders.

Since a tachometer is calibrated in *revolutions per minute*, it would seem that we would count pulses for a full 60 seconds and then divide by half the number of cylinders to get a RPM reading. However, this is not the case. The tachometer electronics counts pulses for a second or fraction thereof and then multiplies that number by a factor that yields the number of revolutions per minute.

Consider an 8-cylinder engine running at 900 RPM. The breaker points operate 3600 times (900×4) per minute. If we divide this by 60 (seconds), we arrive at 60 as the number of pulses developed *per second*. Thus, at 900 RPM, the points generate 60-Hz pulses. Then, for the tachometer to display a "9" (for 900 RPM) we divide 9 by 60 and arrive at 0.15 second or 150 ms. This is the update time. If we want to display ten's, we divide 90 by 60 and arrive at a 1.5-second update time. Similarly, should we want

to display the full 900, we would divide 900 by 60 and come up with 15 seconds as the up-date time. The last two examples are of up-date times that are far too slow to provide accurate instantaneous readings.

The digital tachometer is shown in the schematic in Fig. 1 and block diagram in Fig. 2. Only two decades are used; indi-

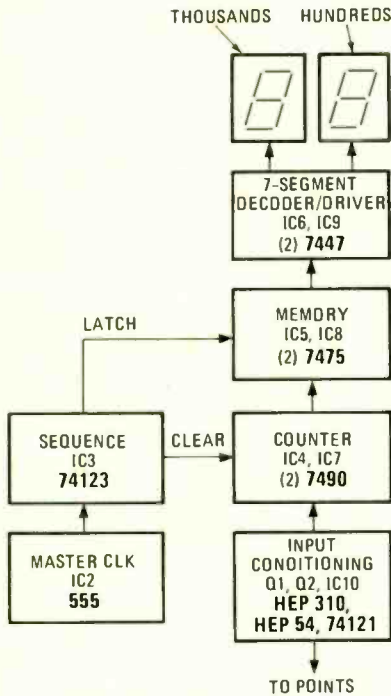



FIG. 2—BLOCK DIAGRAM of tachometer circuit. Master clock signals are provided by a 555-timer IC.

cating thousands and hundreds. Tens and units are not displayed as they would wander so much that the distraction would be greater than that of an erratically bouncing needle of an analog instrument. Also, by displaying only thousands and hundreds, we can take advantage of a faster up-date time. For a 4-cycle, 8-cylinder engine, we up-date at 150 ms. This provides a new reading approximately seven times a second.

To convert breaker-point openings and closings to engine RPM, the tachometer electronics performs all the math necessary for a direct read-out. The 555 timer, IC2, is the master clock. Its frequency must be adjusted, by R5, to suit the type of engine being monitored. Once set, this adjustment need not be touched unless the tachometer is switched to an engine of another type.

A dual retriggerable one-shot, IC3, provides the clear pulses for IC4 and IC7 and the latch pulses for IC5 and IC8. Transistors Q1 and Q2 and IC10 condition the input pulses from the distributor to produce a TTL-compatible signal. Switch S1 is used to adapt the tachometer to either standard or electronic ignition systems. Close the switch when the tach is used with electronic ignition.

The TTL devices and the displays

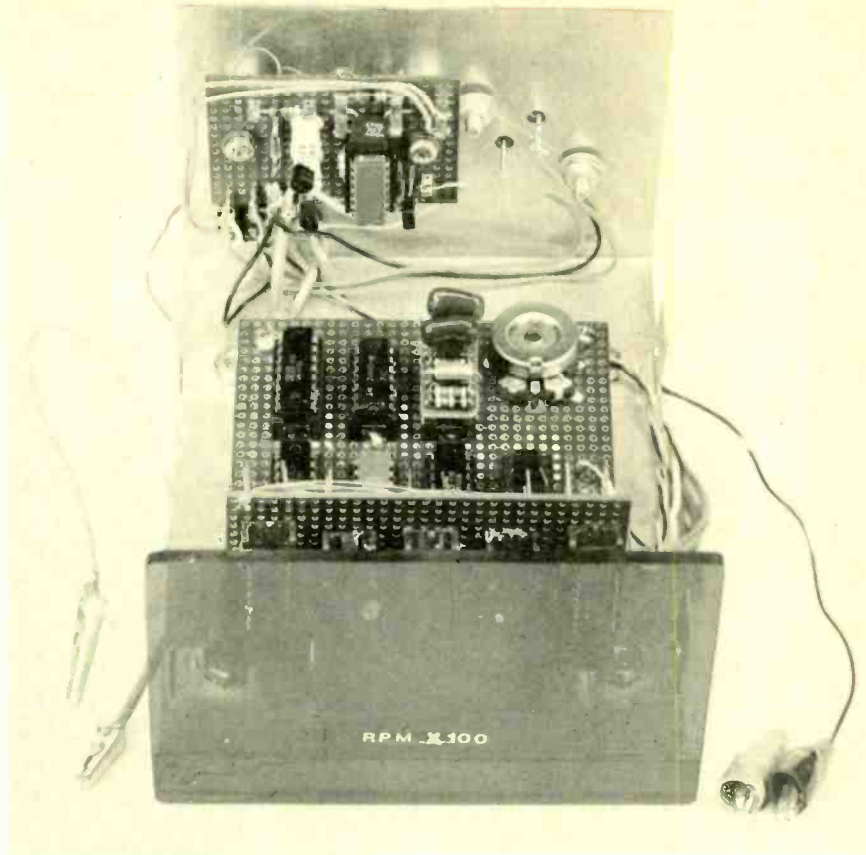

FRONT-PANEL OF TACHOMETER is made of red translucent plastic. Seven-segment LED display is mounted directly behind this.

operate from a regulated 5-volt DC line fed from regulator IC1. The regulator input is 12 to 24 volts DC. Transistors Q1 and Q2 operate from a 12-volt source so 12-volt regulator IC11 should be installed if you plan to use the tach in a vehicle that has an electrical system supplying more than 12 volts DC. By the same token, do not use IC11 if the tachometer is going in a vehicle with a 12-volt electrical system. Add a switch to bypass IC11 if the tach is to be used in both 12- and 24-volt vehicles.

Construction

I assembled the digital tachometer on perforated board using the wire-wrap method. Sockets were used for the IC's, transistors and most other components. Be sure to use heat sinks on the regulator IC's. Use shielded cable or coax for the hook-up between the tachometer and breaker points.

Calibration and use

Calibrate the tachometer before in-

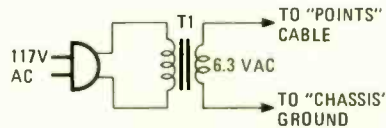


FIG. 3—CALIBRATION of the tachometer requires a low-level 60-Hz AC signal. An inexpensive filament transformer will do nicely.

stalling it in the vehicle. For this, you need a low-level 60-Hz signal—6.3 volts AC from a filament transformer (Fig. 3) will do nicely. Connect one lead to the shielded lead marked "to points" and

CALIBRATION TABLE

Engine Type (Stroke/Cylinder)	Display Readout at 60 Hz (X 100)
2/2 4/4	18
2/3 4/6	12
2/4 4/8	9
2/6 4/12	6
2/8 4/16	4*
* Halfway between 4 and 5	

connect the other lead to the shield. Connect the tach to a +12 to +24 volt DC source capable of delivering at least 1 ampere.

Refer to the calibration table and adjust trimmer R5 until the read-out displays the number corresponding to the type of engine in your car or boat. For example, when properly calibrated, the tachometer reads "18" for a 4-cycle, 4-cylinder or 2-cycle, 2-cylinder engine.

Now, install the tachometer in your boat or car, hook up the cable and you are set to go.

ROUNDUP

Unusual Electronic Clocks

Most of the clocks in earlier articles were table models. Here are details on full-featured wall and mantle models.

FRED BLECHMAN, K6UGT

DIGITAL ELECTRONIC CLOCKS FOR THE home have been available both ready-made and in kit form for several years. More recently, digital clocks for cars have been appearing. Initially these clocks were mechanical, but electronic clocks have been making gains. The latest in sophisticated digital electronic timekeepers, however, are mantel clocks and wall clocks with simulated pendulums and sound. This article discusses three of the more recent designs in detail. An explanation of the circuitry of these timekeepers can teach you a lot about the uses of digital IC's.

Comparison chart

The comparison chart shows the features of each of the clocks covered in this article. The do-it-yourself model is a miniature wall clock 4 inches high and 2 inches wide, using an LCD (Liquid Crystal Display) wrist watch.

Some of the terms used in the chart require some explanation. The "pendulums" are electronic and appear to swing as a result of the lighting of the LED's (Light-Emitting Diodes) in sequence. (Three different ways of doing this will be covered farther on in specific detail.) The "tick-tock" electronic sound simulates the sound of a typical mechanical pendulum clock. The "bongs" are bell-like sounds, produced electronically, that count the hours—two for two o'clock, three for three o'clock and so on. The "chimes" are musical notes arranged in the tune called "Westminster Chimes" that is used by the Big Ben clock in London. The alarms (on those clocks that

have them) are 24-hour repeating alarms, so that they can be turned off when they sound and turned back on the next day at the same time.

Grandfather-style clocks


Strictly speaking, none of the clocks described are true "Grandfather" clocks. This is a term that generally describes large hall-type timepieces with chimes, bongs and pendulums. These clocks are all much smaller, and two are wall clocks. However, we call them Grandfather clocks because several have pendulums, sound and early-American-style cases.

All the clocks have electronic digital displays and use digital circuitry except the Sankyo clock. It is a sort of hybrid instrument and is included because it plays the Westminster Chimes tune. All the clocks have wooden cases except for the Heath *Electronic Clock Chimes* unit, which fits into the case of the *Heath Super-Clock*. All operate from the 117-VAC power line, using the closely regulated 60-Hz frequency for accurate time-keeping, except for the "do-it-yourself" *Micro-Regulator*. It is battery-powered.

When you investigate how these clocks work you will see that no two are alike. Many different approaches have been taken to accomplish essentially the same goal—an accurate digital-display clock in a unique case with unusual conversation-piece features. Since each clock illustrates a different design approach, we'll cover each one in alphabetical order.

Amelect, Inc.

The model CL7402 *Electronic Eye*

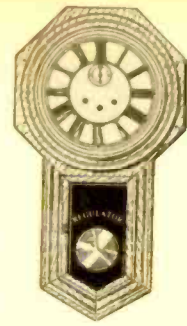


Pendulums



Displays Chimes

wall clock has some unique pendulum and timekeeping display circuits; chimes, a tick-tock sound and bongs will soon be added.

The time is read from three concentric circles, with 60 LED's in each of the outer circles and 12 LED's in the inner circle simulating the tips of hour, minute and second hands. The lighted LED in the outer circle shows the seconds, the center circle shows the minutes and the inner circle shows the hours. The black front panel has white lines inscribed 30 degrees apart to represent five minutes, or one hour, as might appear on a conventional clock face. The pendulum at the bottom of the case consists of 10 LED's arranged in arc form. It's fascinating to

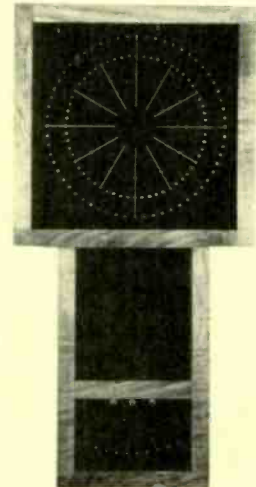

AMELECT, INC. CL7402 Grandfather wall-mount clock.

UNUSUAL CLOCKS—COMPARISON CHART

MANUFACTURER OR SOURCE	MODEL * = BUILT BY AUTHOR	KIT (\$)	ASSEMBLED (\$)	DIGITS	SECONDS	PENDULUM	TICK-TOCK	BONG	CHIMES	ALARM	ASSEMBLY INSTRUCTIONS	REMARKS
AMELECT, INC. BOX 367 GOODLAND, IN 47948	CL 7402 GRANDPA WALL MOUNT CLOCK	71.50	95.00	132	✓	✓	—	—	—	—	GOOD	"ELECTRONIC-EYE" PATENTED READOUT. CHIMES, BONGS AND TICK-TOCK TO BE ADDED. KIT WITHOUT CABINET: \$56.25.
BULLET ELECTRONICS BOX 19442E DALLAS, TX 75219	*MG-01 MINI- GRANDFATHER CLOCK	39.95	59.95	4	—	✓	✓	✓	—	—	GOOD	CASE: ADD \$14.95 UNFINISHED, \$19.50 FINISHED. ASH OR WALNUT.
HEATH COMPANY BENTON HARBOR, MI 49022	GCA-1195-1 ELECTRONIC CLOCK CHIMES	69.95	—	—	—	—	✓	✓	✓	—	EXCELLENT	USE ONLY WITH HEATH MODEL GC-1195 OR GC-1197 "SUPER CLOCKS".
SANKYO SEIKI (AMERICA) INC. 149 FIFTH AVE. NEW YORK, NY 10010	803AL DIGITAL CHIME ALARM	—	59.95	4	✓	—	—	—	✓	✓	—	MECHANICAL-DIGITAL, USING NUMBERED GEARED DRUM. SOUNDS WESTMINSTER CHIMES ON THE HOUR OR ALARM TIME, USING MUSIC BOX.
SOLID STATE TIME BOX 2159 DUBLIN, CA 94566	*ELECTRONIC PENDULUM CLOCK	59.95	69.95	4	✓	✓	—	—	—	✓	FAIR	KIT CASE IS UNASSEMBLED AND UNFINISHED. ASSEMBLED UNIT INCLUDES WALNUT-STAINED CASE. USES PROM FOR REALISTIC PENDULUM ACTION. EASY ASSEMBLY.
"DO-IT-YOURSELF"	*MICRO- REGULATOR	—	—	4	—	—	—	—	—	—	—	BUILD IT FROM BALSALOOD, LCD DIGITAL WATCH AND INSTRUCTIONS IN THIS ARTICLE.

watch the "seconds" march around the outer circle while the pendulum swings back and forth in exact synchronization—1 second in each direction.

The beautifully made wooden cabinet (available in natural walnut, mahogany, maple or cherry) is shaped like a tall wall clock (the top part is 9½ inches square, and the total height is 19¼ inches); and there is a knick-knack shelf between the clock and pendulum sections. A diagonal version of this clock, model CL7401A, without the pendulum is available from Amelect, with or without a base.

Figure 1 is the complete schematic of the model CL7402 wall clock. Although there are 16 IC's, 142 LED's (132 for the time indication, 10 for the pendulum) and many other parts, assembly is not

difficult, just time-consuming. The detailed manual takes you through the assembly step-by-step. Normal assembly precautions should be taken in building this kit and all the others described in this article: Use a small-tip soldering iron, check the solder connections with a magnifier to be sure there are no solder bridges and work slowly and carefully.

The instructions assume you are building this clock with the optional case. Unless you are a professional cabinet-maker, I recommend ordering the kit with Amelect's preassembled cabinet.


This clock circuitry uses many CMOS (Complimentary Metal-Oxide Semiconductor) 4001 Quad 2-input NOR gates. Just to refresh your memory, the positive logic action of a NOR gate can be described thus: The output is logic high *only* when *all* inputs are logic low; if *any* or *all* inputs are logic high, the output is logic low. If you can remember this as you read the circuit explanation, you'll be able to follow the operation of the rather

ingenious pendulum and hours-counter circuitry.


Circuit description

A transformer and full-wave bridge rectifier provide DC voltage. A 60-Hz supply is tapped off the transformer secondary and conditioned to a 60-Hz squarewave by AND gate IC1-b and IC2-a. This conditioned 60-Hz supply is fed to the clock input of divide-by-6 counter IC12. Therefore, the carry output of IC12 is a 10-Hz squarewave (60 ÷ 6 = 10). This 10-Hz output is wired to the clock input of IC14-b, a flip-flop that divides by 2 at output Q, providing a 5-Hz supply for time-setting the minutes and hours counters.

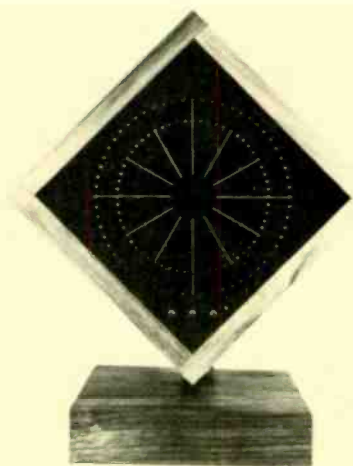The pendulum: The 10-Hz output from IC12 is also connected to divide-by-



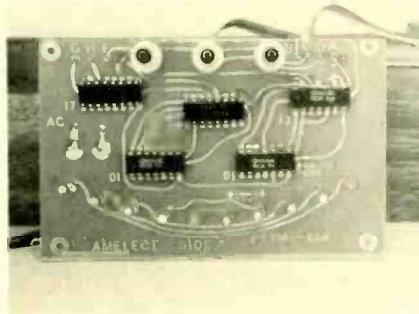AMELECT, INC. CL7401A, diagonal version with/without base.



AMELECT CL-7402 pendulum circuit board, front view.



AMELECT CL-7402 time-display circuit board.

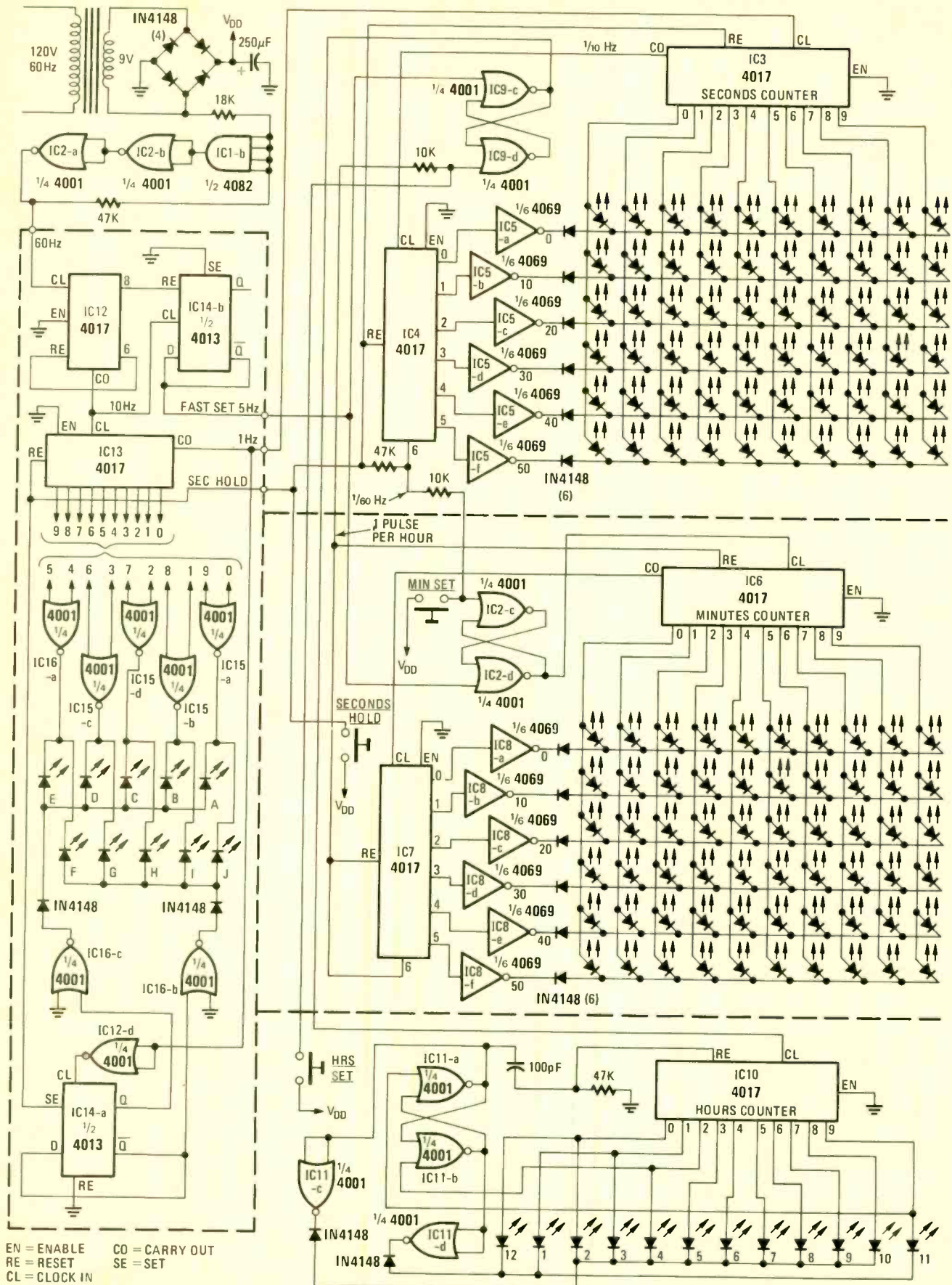


FIG. 1—SCHEMATIC DIAGRAM of the Amelec model CL7402 electronic wall clock. One hundred and thirty-two LED's are for time display and ten simulate the movement of a pendulum.

10 counter IC13. The 0-to-9 counting outputs of IC13 are wired directly to five 4001 2-input NOR gates so that they control 10 LED's one at a time. These LED's form the pendulum (see Fig. 2) that must swing back and forth. To describe this action, assume that IC13's output has just completed a 10-count cycle, so the 0 output is at a logic high. All the other outputs are at logic low, therefore, NOR gates IC15-b, IC15-c and IC15-d and IC16-a all have a logic-high output, thus keeping pendulum LED's B through I off. However, since IC15-a has one logic-high input (from IC13, count 0), its output is at logic low, and this

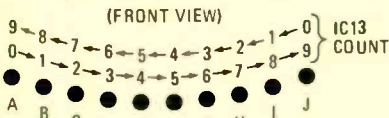


FIG. 2—THE PENDULUM, simulated by twelve LED's, appears to pause at the top of each swing.

enables LED's A and J to light, if they were receiving power from some other source. However, only LED A lights, and here's the reason why:

Referring to IC13, note that the carry output goes to IC12-d. This carry-output pin is at logic high for counts 0 to 4, and at logic low for counts 5 to 9. This polarity is inverted by IC12-d, which clocks flip-flop IC14-a. Because output Q is at logic low at this point, the output of IC16-c is at logic high, providing the current to light LED A. At the next count (1) of IC13, a tenth of a second later, LED B is enabled, then C at count 2, D at count 3 and E at count 4. On count 5, the carry output of IC13 goes to logic low and this is inverted to a *positive-going* edge by IC12-d, thus clocking IC14-a. Instantly, Q goes to logic high and \bar{Q} goes to logic low, which cuts off all the LED's that are connected to IC16-c and enables those that are connected to IC16-b. Therefore, at counts 5 through 9, LED's F, G, H, I and J light in that order.

Here's how to get the pendulum to swing *back* (or have the LED's light in reverse order). Counter IC13 is back to 0, but the IC16-b output remains at logic high. Why? Although the carry output of the counter has gone to logic high, IC12-d has inverted this output to a *negative-going* signal—and IC14-a responds only to *positive-going* signals. So the count progresses, lighting LED's J, I, H, G and F in order on counts 0 through 4. At count 5, however, flip-flop IC14-a sees a *positive-going* signal and changes state, with Q going to logic low and \bar{Q} going to logic high. This then allows LED's E, D, C, B and A to light in that order on counts 5 through 9, and a complete back-and-forth swing of the pendulum has been completed in 2 seconds. Note that conditions are now exactly as before, so the sequence repeats. Also, LED's A and

J each stay lighted for counts 0 and 9, pausing realistically at the top of the swing.

Seconds and minutes counters:

The 1-Hz output pulse of IC13 in the pendulum circuitry goes to divide-by-10 counter IC3. Each 0-to-9 output is at logic high for 1 second. These outputs are fed to 60 LED's that are arranged in a 6 X 10 matrix with 6 LED's wired to each of the 10 outputs. However, counter IC4, wired to divide-by-6, is used to ground each LED in the proper sequence. This takes the 0.1-Hz output of IC3 (one pulse every 10 seconds) to operate outputs 0 through 5 of IC4 for 10 seconds each. Whenever any output of IC4 is at logic high, the associated IC5 inverter grounds all 10 LED's in that line—but only the LED that is driven by IC3 for that specific second actually lights.

The output of IC4 in the seconds counter is one pulse every 60 seconds. This supply is fed through NOR gates IC2-c and IC2-d that are arranged as a flip-flop to the minutes counter, which then counts the minutes exactly the same way the seconds are counted.

Hours counter: The output of minutes counter IC7 is 1 pulse-per-hour and is fed through flip-flop IC9-c and IC9-d to hours counter IC10. In this case, however, counter outputs 0 through 9 are wired to four NOR gates (IC11) so that 12 LED's light up in sequence to indicate the hours. Figure 3 shows how this is

HOUR	12	1	2	3	4	5	6	7	8	9	10	11
IC10 COUNT HI OUTPUT	0	1	0	1	2	3	4	5	6	7	8	9
IC11-a OUTPUT	L	L	H	H	H	H	H	H	H	H	L	L
IC11-b OUTPUT	H	H	L	L	L	L	L	L	L	L	L	H
IC11-c OUTPUT	H	H	L	L	L	L	L	L	L	L	L	H
IC11-d OUTPUT	L	L	H	H	H	H	H	H	H	H	L	L

FIG. 3—HOURS ARE INDICATED by LED's lighting sequentially. This is the logic truth table.

accomplished. At midnight or noon, on the count of 0 at IC10, the IC11-a output is at logic low, making the IC11-c output at logic high, disabling LED's 2 through 10. At the same time, the output of IC11-b is at logic high (both inputs are at logic low), making the output of IC11-d low, thus enabling LED 12, which lights, driven by output 0 of IC10. On count 1, LED 1 lights, since the logic gates have not changed state. On count 2, the IC10 output drives IC11-b low at its output (since one input is now low), and this drives the IC11-a output high. The IC11-d output goes high and the IC11-c output goes low. Simultaneously, a *positive-going* pulse through a 100-pF capacitor resets IC10 to 0 and LED 2 lights. However, LED 12 does *not* light since the low at the IC11-b output makes the IC11-d output high.

Counter IC10 continues counting upward. At the third hour, the count is at output 1 of IC10 and LED 3 lights. The counter output is 2 at the next hour, but reset does *not* occur at this time, since the IC11-a output is already high and LED 4 lights. The count continues up through output 9 which triggers gate IC11-a to a low output, the IC11-b output to high, the IC11-c output to high, thus enabling LED 11 with a low output at IC11-d. This procedure also sets all the logic for hours 12 and 1 until reset by hour 2.

Time setting: A second-hold switch returns the second count to 0 and stops counting at pendulum IC13 by holding the reset at positive voltage. Releasing this switch starts the seconds counting from 0.

Separate switches set the minutes and hours. Both switches use NOR gates for switch debouncing. The "fast-set" 5-Hz signal from the pendulum (IC14-b) advances the LED's around their circle at 5 minutes or 5 hours-per-second when the switch is pressed. Time-setting is thus easy and fast. Amelect, Inc., Box 367, Goodland, IN 47948.

Bullet

Almost all the features one could ask for have been included in this inexpensive Mini-Grandfather Clock. The optional clock case, designed for table or mantel use, is really a necessity for proper packaging of this relatively complex unit. Two large 4½-inch X 6½-inch PC boards are used, interconnected with 17 wires, a special four-position slide switch and a small speaker. The case comes pre-grooved and predrilled; you simply screw it together. No glue is required. A back panel is used to mount the transformer, switch and speaker. You use one large ruby front lens, and the finished clock is 10 inches high, 8 inches wide and 5 inches deep.

The 2-inch-long pendulum is composed of 21 LED's that are arranged in

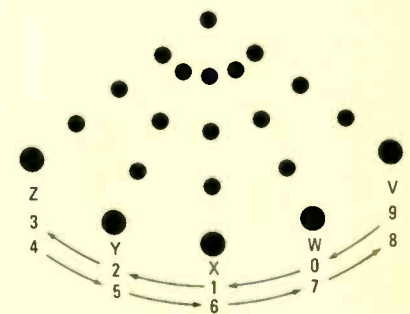


FIG. 4—THE BULLET CLOCK has pendulum simulated by five strings of LED's as radii of the arc.

five "strings" (see Fig. 4). The display has four 0.5-inch-high digits, with a flashing colon and AM-PM indicators. The seconds are not shown but can be set. One PC board contains a conventional-design clock circuit that uses a direct-drive FCM 7010 clock calendar IC. No


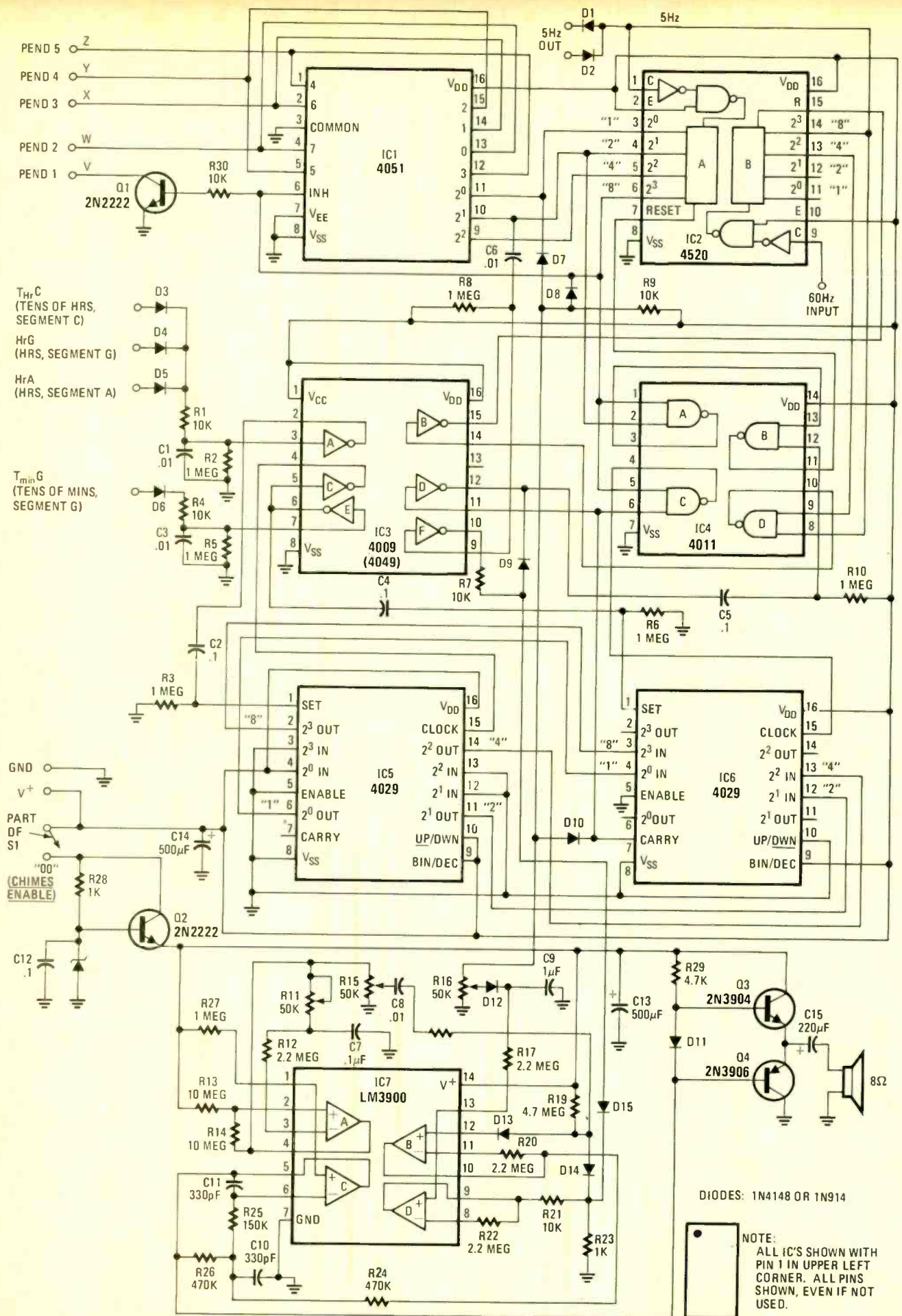


FIG. 5—THREE-DIGIT, SEVEN-SEGMENT READOUT displays time. Twenty-one LED's form the "pendulum". Logic circuitry shown runs the clock, ticks the seconds and chimes the hours.


DIODES: 1N4148 OR 1N914

NOTE: ALL IC'S SHOWN WITH PIN 1 IN UPPER LEFT CORNER. ALL PINS SHOWN, EVEN IF NOT USED.

calendar and alarm functions are provided, however, because they would interfere with the "bong" circuit operation. Resistors are used to connect individual segment outputs of the FCM 7010 to the 4-digit display. The pendulum LED's also mount on this board. To assemble this board is tedious but not difficult. Various points on this board are then connected through wires (ribbon cable) to the logic board, that contains the pendulum, bong and tick-tock circuitry. No chimes are provided. However, a Heath Westminster Chimes is connected to one of these clocks, but this voids Heath's warranty!

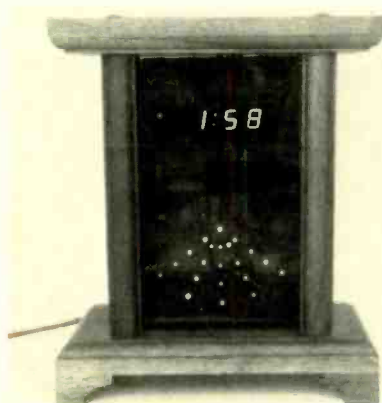

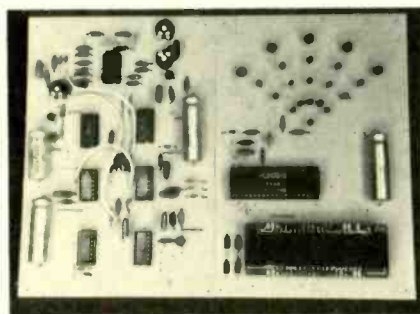BULLET MG-01, completely assembled. Time exposure shows all five pendulum positions.



BULLET MG-01 clock and logic boards side by side before interwiring. The clock board is on the left.

Logic circuitry

If you take time and effort to follow the logic-board circuitry shown in Fig. 5 closely, you will find that it illustrates many basic and inventive uses for IC's.

The logic circuitry shown in Fig. 5 performs three main functions:

1. It "swings" the electronic pendulum;
2. It bongs the hours and counts;
3. It tick-tock's the seconds.

All these functions are performed using the 60-Hz power line, using selected clock-display segment changes to set the bong count and enable function.

The pendulum: The pendulum "strings" shown in Fig. 4 are listed as V, W, X, Y and Z. The object of the pendulum circuitry is to light these strings in sequence so that the pendulum appears to swing back and forth every 2 seconds. The pendulum circuit (Fig. 5)

comprises IC1, IC2, and parts of IC3 and IC4. The 60-Hz power supply is received from the clock board, where it has been shaped and has had all negative portions removed. This 60-Hz power supply is fed to pin 9 of IC 2, a dual binary counter. Pin 9 is the input to counter B. Since enable input (pin 10) to this counter is held high, 60 counts-per-second are entered into B which counts up in BCD (*Binary-Coded Decimal*). When outputs 4 and 8 of this counter are both high, they trigger gate D (pins 8 and 9) of IC4, a quad 2-input NAND gate. Remember, for a NAND gate the output is low *only* when *both* inputs are high. So, the gate D output is low (pin 10). This low output is fed to inverter B (pin 14) of IC3, a hex-inverting buffer. The inverter B output is therefore high (pin 15), which resets counter B of IC2 through pin 15. Thus, counter B resets on every twelfth pulse (4 + 8), making this a divide-by-12 counter. The 8 output (pin 14) of counter B goes low on every twelfth count. Since 60 counts-per-second are entering, then the counter B output at pin 14 is $60 \div 12$, or 5 counts-per-second (5 Hz). Through diodes D1 and D2, these high and low states set the clock-display-time hours and minutes, advancing 5 digits-per-second.

The 5-Hz signal is also fed to clock input pin 1 of enabled counter A. It counts up and is reset through NAND gates A and B of IC4 when the count reaches 8 and 2, making this a divide-by-10 counter. Since 5 pulses-per-second enter counter A, it goes through a complete count of 10 in 2 seconds.

The BCD outputs of counter A go directly to IC1, a 1-of-8 decoder, which cycles through eight low outputs—0 through 7. Note that outputs 0 and 7 are connected together and to pendulum string W; outputs 1, 6 and X are also joined, as are outputs 2, 5 and Y and 3, 4, and Z. This makes the corresponding pendulum line low when *either* of the two pins in common goes low as long as inhibit pin 6 is also low. So, for counts 0 through 7, the pendulum LED strings each light for 0.2 seconds in the following sequence: W, X, Y, Z, Z, Y, X, W. But, what about string V? Since IC1 can only count to 8, the next two counts from IC2 counter A light up string V in this manner: On counts 8 and 9, the high on pin 6 (the binary 8 line) drives IC1 inhibit pin 6 high. This stops IC1 from counting. This same high signal simultaneously drives transistor Q1 into conduction, thus grounding pendulum string V. On IC2 count 0, IC1 inhibit pin 6 is released, Q1 is turned off and the sequence repeats, starting with string W again. Note that at each end of the pendulum swing (Z and V), the line stays low for two counts to simulate the pause effect of a real pendulum at the top of its swing.

Now that you're getting confidence in

your ability to follow all this logic stuff, let's dive into the bong circuit. Hold on tight and be ready for a rough ride.

Bong circuit: IC7 is a quad op-amp, with sections A, B, C and D. Section A is a squarewave oscillator whose tone is controlled by potentiometer R11. The squarewave is fed to section B through volume control R15. Section B is an AC amplifier whose gain is controlled by a DC voltage supply from section D. Section C is used as a low-pass filter to round off the corners of the squarewave, providing a smoother sinewave-like tone. Transistors Q3 and Q4 amplify the output of section C to drive the speaker. Section D is a DC amplifier, used with potentiometer R16 and capacitor C9 to control the duration of the bong through section B. The four-position switch turns on power to this entire section, so the bong sound may be disabled. Zener diode Z1 and transistor Q2 regulate the voltage. The bong sound is created by IC7 and its associated circuitry, but the digital circuitry controls *when* the bong should sound and how many times it should sound each hour. This is done primarily by IC5 and IC6, with the help of IC3, IC4 and IC2.

Up-down presettable counters IC5 and IC6 do the hours counting, along with IC3 inverters A, C and E, by sensing the time. The tens-of-hours segment C, and hours segments A and G of the clock display are connected through diodes D3, D4 and D5 to inverter A of IC3. When *any* of these segments are high (i.e., lighted), the inverter A input is high and its output is low. When *all three* monitored segments are low (only at 1:00 AM or 1:00 PM), the inverter output goes high. This charges C2, generating a short pulse to set input pin 1 of IC5. Since a positive voltage is permanently wired to the 2° input (pin 4), the counter clears and presets to 1 (2°) each time the set input receives a positive pulse at 1:00 AM or 1:00 PM. At 20 minutes past the hour, the tens-of-minutes G segment goes high, remaining that way until the beginning of the next hour when it goes low. The high tension at 20 minutes past the hour is detected by D6; changed to a pulse by C3, R4 and R5; double-inverted by inverters E and C; and applies as a positive pulse to clock input pin 15 of IC5. This advances IC5 by one count, since it is wired as an up-counter (pin 10 high). Therefore, at 20 minutes after the hour, an additional count is loaded into IC5. At 1:20, the total count held by IC5 is 2, at 2:20 the count is 3 and so on, until the count resets to 1 at 1:00 AM or 1:00 PM. When segment G of the tens-of-minutes digit goes low at the beginning of each hour, the inverter E output goes high, creating a positive pulse through C4 to set input pin 1 of IC6. Two things happen almost simultaneously: (1) IC6 is loaded with the count existing at the output pins of IC5; and (2) the IC6 carry output of IC6 (pin 7) goes high. Output IC6 is wired to

continued on page 100

BUILD

AM/FM Frequency Display

Part II. Update your hi-fi with this digital frequency and time display that you can add on or build into a modified AM/FM set. The construction is simple and inexpensive.

GARY McCLELLAN

IN THE JANUARY 1978 ISSUE, WE WENT step-by-step through the theory of operation and the basic wiring and construction of this time/frequency display that you can add to your AM/FM radio. In effect, it is a 12-hour clock that doubles as a radio frequency indicator.

Now that you have completed the modules, you have two choices in the final packaging. You can build the entire project inside the receiver as I did in a Sansui model 331 or build the display section as an add-on in an attractive cabinet that sits on top of the radio.

To build everything inside the radio takes a lot of courage. But, if you are an experienced electronics experimenter and constructor and don't mind tearing into a receiver, you should be successful. The advantages are that the finished modification looks very professional. The first thing you must do is to be sure you have room for all the parts. This includes a metal box or enclosure 7 inches high, 4 inches wide and 6 1/4 inches deep for the display and a box 3 1/4 inches high, 2 1/4 inches wide and 1 1/4 inch deep for the interface board. Then, there must be room for transformer T1 and space on the back panel for switches S1 and S2.

Figure 11 shows the additional parts and circuitry needed in the built-in version. The additional parts are mounted using point-to-point wiring on a small piece of perforated board. There are several points of interest in Fig. 11. Display switching is done by taking voltages from the radio function selector switch which selects time, AM or FM. This switch must include a section that switches a positive supply voltage between the AM and FM sections.

The first step is to get the display working properly outside the receiver. Then you connect the switching and modify the receiver mechanically. The switching voltage for the time, AM and FM functions is not critical; it can range from

+6 to +24 volts. Interface connections are shown in Fig. 12. This is covered in detail later in this article.

The second, and easier, method is to build the add-on version. This is because you don't have to make extensive mechanical modifications on the receiver. Also, if you have any doubts about your electronic skills, play it safe and build this version. Refer to Fig. 13 for the related wiring on the display board and then to Fig. 12 for the interface connections. Mount the interface board in a type 772 LMB box, or similar enclosure, after punching holes for the RF input and output cables. Then build the display section into a type 463N LMB box or

other suitable cabinet.

Connecting to the receiver

Connecting the interface board to the receiver is the toughest part of the project but it's not too hard—you just have to know where to connect several wires. Figure 12 shows the local oscillator sections of a typical radio receiver. Dig out the schematic of your set and locate the local oscillators. In the less expensive sets you may find a single converter section—the same transistor is used for AM and FM. Interfacing is much the same.

Note that you will be working around the tuning capacitor and it is imperative that the interface board be mounted as

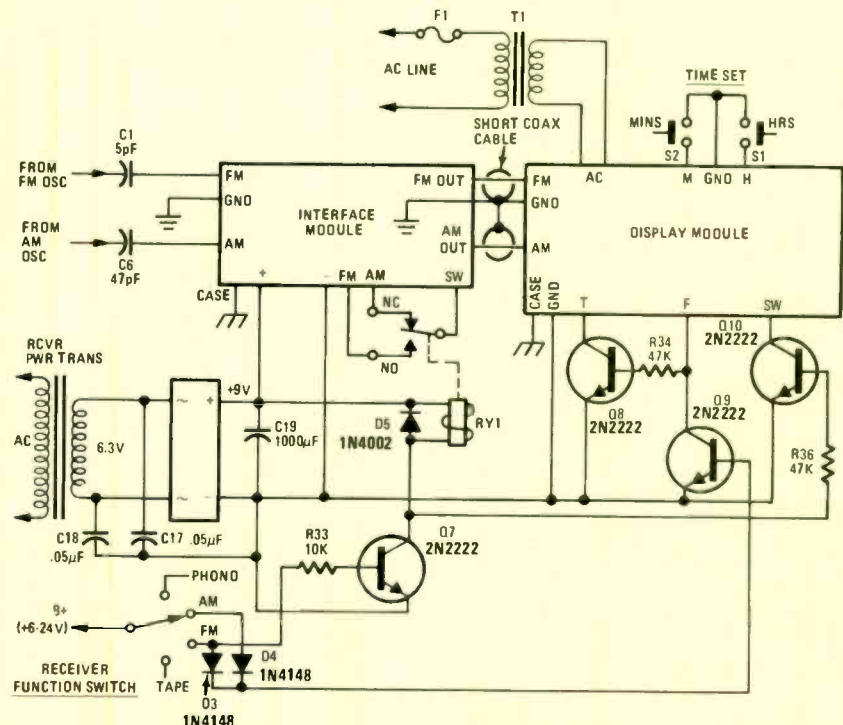


FIG. 11—HOW TIME/FREQUENCY DISPLAY is wired in built-in version. All external parts are mounted on a small piece of perforated circuit board. This arrangement was used in the Sansui receiver.



close as possible to the FM local oscillator. The AM section is not critical—you can even use a short length of coax for the connections.

Back to the schematic, locate the emitter resistor of the FM local oscillator/converter and tie C1 between it and the interface board. Keep the leads under 1 inch in length. Also, be sure to enclose the board in an aluminum utility box as mentioned earlier. Tie a short piece of ground braid from the interface board ground to the radio ground. Repeat this procedure with the AM section. Note that short leads are not as important here.

(For those readers that are concerned about the possibility of detuning the RF circuits caused by the additions, we tried this project with the following results: A

slight detuning effect was noticeable only on FM. It was so slight that realignment proved to be a waste of time. In addition to the Sansui model 331, we tried the time/frequency display on an Arvin receiver, a Radio Shack portable, a Delco AM/FM car radio and a Panasonic table model. All installations worked fine.)

While you are inside the radio, find a source of 8 volts or more to power the interface board. Usually you can get this voltage by removing the ground from the 6.3-volt AC dial lamp supply and attaching a bridge rectifier and filter capacitor as shown in Fig. 12. This source of power is desirable because it goes off and on

with the receiver. If you prefer, substitute a 6.3-volt, 600 mA filament transformer. If you get hum on strong AM stations add capacitors C17 and C18. Route the output cables out of the back and attach a plug PL1 to match the 9-pin tube socket or connector (J1) on the back panel of the main module.

Let's try it out

If you used the built-in version, plug in the receiver. The clock colons will light and you will get a reading of 000. Press SET HRS and, after a delay of several seconds, the hours will advance. Do the same with SET MIN and adjust the display for the correct time. Your clock is now working. (Remember the delay whenever you set the clock. This is a built-in feature.)

Turn on the AM radio and you'll get readings such as 640, 1220, 1540 and so on. The last digit will always be 0 in this mode. You should now be able to look up a station, dial its frequency and hear it! Do the same with FM. Note that you get a smooth transition between odd numbers such as 97.3, 97.6 MHz, etc.

The add-on version works the same way, but you must manually change the switch (S3) to read time or radio frequency. You can select the time mode without disturbing the radio—a bonus feature over the built-in version.

There are a few advantages this display has that haven't been mentioned. First, the clock section can be operated as an elapsed-time indicator. When you plug it in—after allowing 5 minutes for the filter capacitor to discharge—the entire clock is zeroed and will begin counting elapsed time in hours and minutes until the interval you are timing has ended. Also, the add-on display will run without the receiver and the receiver can operate without the display so the clock can be handy around the house.

R-E

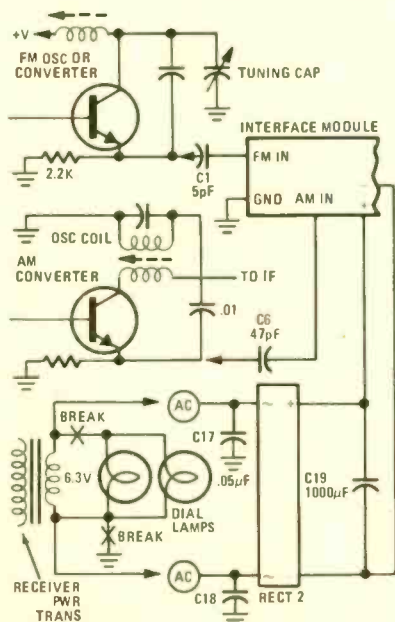


FIG. 12—HOW THE INTERFACE BOARD IS CONNECTED to the receiver. You can use set's dial-lamp supply or separate filament transformer to feed the rectifier.

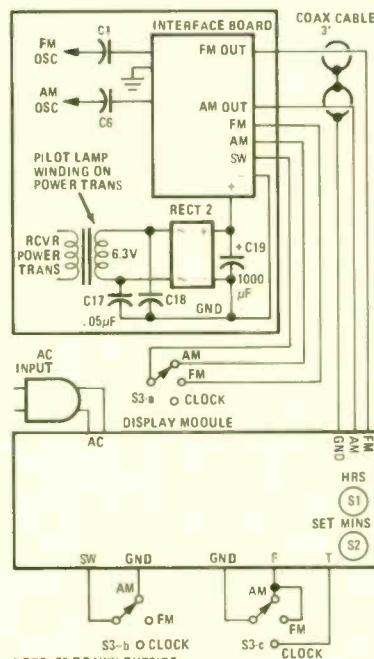


FIG. 13—AUXILIARY CIRCUITRY for the add-on version. Mode switch S3 is installed inside the display module box but is drawn outside for clarity.

All About The S-100 Bus

The 100-line bus that is almost standard equipment in 8080 computer systems. Here we look at the bus and how those 100 lines are used.

WILLIAM BARDEN, JR.

ONE OF THE MOST BENEFICIAL EVENTS IN the microcomputer explosion was the establishment of the S-100 microcomputer bus by MITS, Inc. MITS defined the S-100 bus by the design of the Altair 8800 in 1975. Although they did not intend it as a standard, it soon became one as IMSAI, Polymorphic Systems, Processor Technology, and others brought out microcomputers compatible with the S-100 bus structure. In addition to many microcomputers that use the S-100 bus, there are dozens of manufacturers producing memory boards, I/O boards, speech synthesizers, and other hardware compatible with the S-100 bus structure. This article will explain the basis for the S-100 structure in terms of the microprocessor for which it was designed, the 8080A, discuss the signals of the bus, and describe basic interfacing to the bus.

Physical characteristics

The S-100 bus is a collection of 100 logic and power signals developed from the microprocessor signals. Some signals are logically identical to the signals from the 8080, while others are related, and still others are signals defined by MITS. Physically the bus is represented by a printed-circuit board called a motherboard with 100 parallel foil strips and several 100-pin connectors that are soldered to the foil of the PC board. The typical PC boards that plug into the connectors on the motherboard have 100-pin edge connectors and are the approximate size shown in Fig. 1. A complete S-100 type microcomputer system could consist of the motherboard, power supplies, and a number of S-100 plug-in modules, such as a CPU (Central Processor Unit) module, memory modules, and I/O (Input/Output) modules.

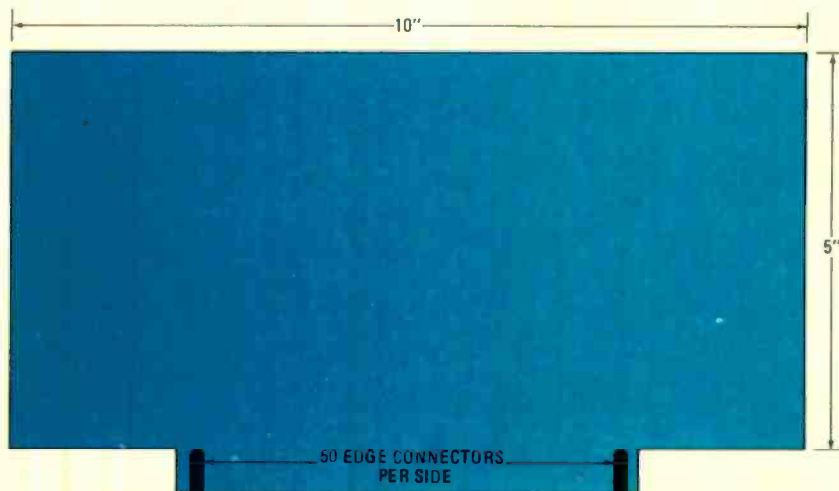


FIG. 1—TYPICAL S-100 BOARD has 100 edge connectors; 50 on each side of the board. These boards are intended to plug into the S-100 mother board.

8080 and the S-100

The 8080 microprocessor IC is the heart of most S-100 bus systems, although other microprocessors could be and are being used. Let's first describe the 8080 signals and then see how they relate to the S-100 bus. The pinout of the 8080 is shown in Fig. 2. Most signals are TTL compatible and most are active high.

The 8080 requires three voltages, +5V, -5V, and +12V as indicated. In addition, timing within the 8080 is controlled by a two-phase *non-overlapping* clock represented by $\phi 1$ and $\phi 2$.

Data is transferred bidirectionally between the 8080 and external devices by the data bus, shown as D7 through D0. Data may be instruction data, memory reference data, or input/output data. The 8080 addresses external memory to get the 8 bits of data by means of 16 address

lines A15 through A0. Since binary values from 0000000000000000 through 1111111111111111 may be contained on the lines, 65,536 different memory locations can be addressed.

When the 8080 *executes* an instruction, it goes through a predefined *instruction cycle* controlled by the internal logic of 8080. In the course of the cycle, the 8080 first outputs the address of the current instruction on the address bus. It knows the current address from the content of an internal register called a *program counter*. External memory decodes the 16-bit address from the bus and also detects another 8080 signal, DBIN, that indicates that an input (to the CPU) operation is to take place. External memory gates the 8 bits of the selected memory location onto the data bus and the CPU strobes in the data some time later in the cycle. During this *fetch* cycle, the

TABLE 1

Data Bus Bit	Symbol	Description
D0	INTA	Interrupt acknowledge
D1	\overline{WO}	Indicates a write to memory or output is about to occur
D2	STACK	Indicates the address bus holds stack address
D3	HLTA	Acknowledge for HALT Instruction
D4	OUT	Output device address on address bus; data bus will hold output data when WR active
D5	M1	CPU in fetch cycle for first byte of instruction
D6	INP	Input device address on address bus; data bus will accept input data when DBIN active
D7	MEMR	Data bus will be used for memory read data

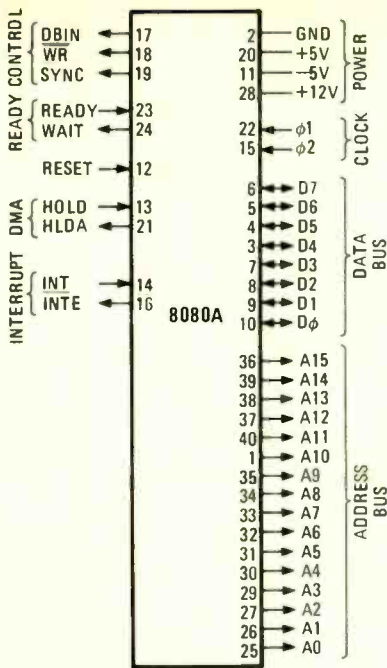


FIG. 2—THE 8080A MICROPROCESSOR IC has the pinout arrangement shown here. Most signals from the IC are TTL compatible.

first byte input represents the complete instruction if the instruction is a one-byte instruction. If the instruction is a two- or three-byte instruction, this first portion of the fetch cycle picks up on the first byte of the instruction. By decoding this first byte (the *operation code*), the CPU knows whether or not to make none, one or two more memory reads to obtain the remainder of the instruction.

When the CPU has the complete instruction, the fetch cycle is completed and the *execution cycle* begins. There are a wide variety of instructions the CPU may execute, but they essentially involve internal functions, reading (again) from memory, writing to memory, reading from an I/O device, or writing to an I/O device.

Reading from memory is similar to the fetch cycle. The address bus holds the memory address of the 8 bits of data to be read and signal DBIN is enabled. If data is to be written to memory, the address bus still holds the memory address of the data to be read, but signal DBIN remains low, and at the proper time signal WR is brought low to strobe the data into external memory. When the CPU executes a read or write (I/O) instruction, the sequence is similar to a memory read or write. The address bus contains the I/O address on lines A7 through A0, as there are only 8 bits available for an I/O address in an I/O instruction.

If data is to be input to the CPU from an external I/O device, signal DBIN is once again high and if an output operation is taking place, DBIN is low and WR is low. How does the I/O device know whether the input or output is from memory or from itself, though? For example, the CPU could read data from

memory location 55 and immediately follow that instruction with an input from I/O device 55! To differentiate between I/O addresses and memory addresses, additional signals called status signals are used. There are eight status signals and they are output on the data bus during the beginning of each machine cycle during the time when signal SYNC is high. The status bits and what they represent are shown in Table 1.

The READY signal of the 8080 is an input signal that enables the 8080 to interface with slow memory or I/O devices. If the memory cycle time is not fast enough to allow the memory to respond with data for the CPU, for example, the memory logic may bring down signal READY to a logic 0 level. This causes the CPU to insert an extra clock period in the instruction cycle for as long as READY is low. When in a "not ready" condition, the CPU responds with a WAIT signal that is output to external devices.

The RESET signal is an input that accomplishes what the name describes. It is used before program execution to reset the program counter to zero. Program execution then proceeds from memory location to zero, as previously described for the fetch operation.

The 8080 has the capability, as do most microprocessors, of temporarily suspending instruction execution for *direct-memory-access*, or DMA. DMA permits external memory to be accessed independently of the CPU for high-speed I/O that cannot afford the time required for the CPU to issue a simple byte at a time. When an external I/O device *controller* makes a HOLD request, the CPU responds with an HLDA (Hold Acknowledge), indicating that it has released the address and data buses to the external device. (This is important to avoid the conflict of use of the buses by both the CPU and the external device controller simultaneously.) Normal CPU operation resumes when the external device controller brings the HOLD signal to a logic 0 level.

The remaining two 8080 signals, INT and INTE, are associated with CPU *interrupts*. An interrupt is an external signal that forces the CPU to suspend program execution at the current instruc-

tion location and transfer control (or jump) to a predefined address that contains an interrupt program. An example of this might be a CPU dedicated to running a control program that is interrupted when a Teletype key is depressed. The external signal causing the interrupt is INT, which causes an interrupt only if the control program has enabled the interrupt condition by setting an internal interrupt enable flip-flop. The state of the interrupt enable flip-flop is brought out on line INTE.

The above description outlines the 8080 signals necessary to interface external devices to the microprocessor. Now let's see what MITS did with the microprocessor signals to construct a working microcomputer with a control panel, memory and I/O. What they did in the 8800 design defines the S-100 bus.

S-100 bus signals

Power signals: the +8V, +18V and -18V unregulated lines are provided on the S-100 bus. These voltages are regulated to +5 and other required voltages by on-board regulators for each S-100 module.

Data bus: The 8080 data bus is buffered in the S-100 configuration to provide a greater driving capacity. In addition, the data bus is converted from a bidirectional bus to two unidirectional buses. Lines DO7 through DO0 is the data bus coming out from an S-100 CPU while lines DI7 through DI0 is the data bus going into an S-100 CPU. The output lines are enabled by S-100 bus signals DO DBS that connects to tri-state buffers (see Fig. 3).

Address bus: Lines A15 through A0 of the 8080 are buffered in the S-100 bus system; the tri-state enable signal is ADDR DSBL (see Fig. 3).

The six command and control outputs described for the 8080—SYNC, DBIN, WAIT, WR, HLDA and INTE—are logically unchanged, but buffered in the S-100 bus system. Their tri-state buffer enable signal is C/C DBS. The six signals are renamed PSYNC, PDBIN, PWAIT, PWR, PHLDA and PINTE (see Fig. 4).

The eight status bits of the 8080 are latched into a status latch, as shown in Fig. 5. The status bits listed in Table 1

now become SINTA, SWO, SSTACK, SHLTA, SOUT, SM1, SINP and SMEMR. Status is disabled by signal STATUS DSBL. A memory write signal MWRITE is developed from SMEMR.

Four inputs to the 8080, READY, HOLD, INT and RESET are either buffered or latched from the S-100 bus signals PRDY/XRDY, PHOLD, PINT and PRESET.

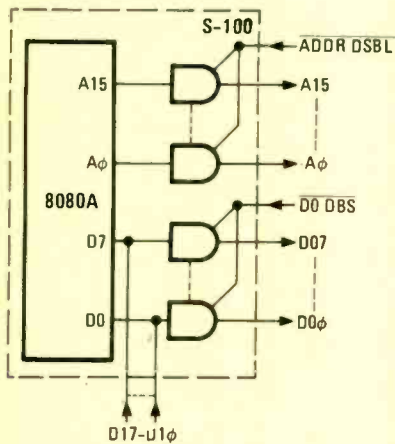


FIG. 3—IN THE S-100 BUS, the data lines from the 8080 are buffered by tri-state buffers as shown in this diagram.

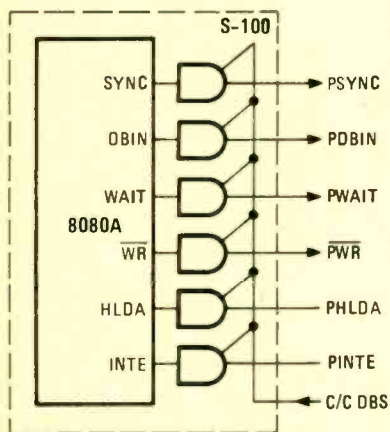


FIG. 4—SIX COMMAND AND CONTROL outputs are also buffered for the S-100 bus. These signals and the buffering can be seen here.

The $\phi 1$ and $\phi 2$ clocks are developed in the S-100 CPU circuitry and routed to the system via S-100 bus outputs $\phi 1$, $\phi 2$ and CLOCK. The latter is $\phi 2$ inverted. Signal POC, Power on Clear, is developed in the power supply logic and indicates when system power is on.

The above signals are S-100 bus signals intimately associated with the 8080, and together with unused pins cover about 80% of the S-100 lines. The remainder of the lines are for the most part associated with vectored interrupts and control panel functions in the microcomputer.

Signals V10 through V17 are eight vectored interrupt lines. The 8080 provides eight vectors or pointers to interrupt locations with proper external logic. Signals V10 through V17 are S-100 system signals fed to an interrupt board that would implement these functions.

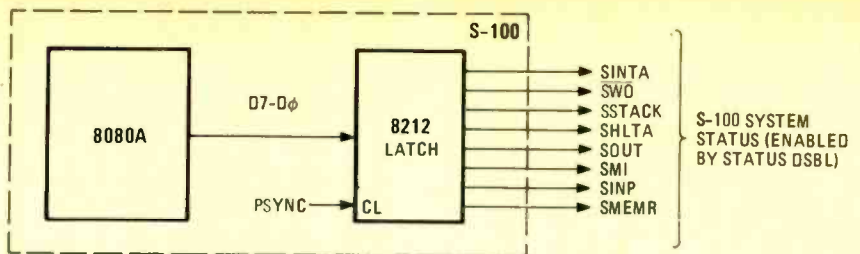


FIG. 5—EIGHT STATUS BITS of the 8080 are latched into a status latch as shown here. When desired, status is disabled by signal STATUS DSBL.

Control panel signals in an S-100 microcomputer system may be present on the S-100 motherboard that *does* have a control panel or they may be strapped to the proper logic level. Some control panel signals may be simply deprived from switch settings. Signals PROT and UNPROT would typically be derived from a switch on a front panel that controls alteration of data in memory. Signals PRESET or EXT CLR may be derived from a momentary switch for system reset and clear of external devices. Signals RUN and SS indicate that the system is running or that a single-step switch is being used to step through a program, respectively. Signal SSW1 indicates that a data transfer from the control panel sense switches is to take place, for example, altering memory contents.

Although most manufacturers that make S-100 motherboards have made their boards consistent with the above signals, some incompatibilities do exist, especially in cases where undefined pins have been used to carry required new signals. Boards of this kind are not completely compatible with the S-100 bus and may not be used without some modification.

An S-100 system

Now that we've seen the 8080 signals and their relation to S-100 bus signals, let's look at a typical S-100 bus system. We'll assume that the system uses an 8080 CPU card that contains only the 8080 microprocessor and related logic. This will probably consist of buffering and an 8212 status latch. Many of the S-100 bus signals are generated on this board, such as A15 through A0, the status signals and clock signals. Alternatively, the CPU board might contain a Z-80 or even a 6800 microprocessor. However, if a different microprocessor is used it must generate compatible S-100 signals. In many cases, additional logic will have to be added to the CPU board to create S-100 signals. See Fig. 6 for a look at the kinds of signals that may have to be added.

The memory boards in the system use the 16 address lines as inputs to select the memory location being accessed. If the board is an 8K (or 8192) byte board, 13 lines, A12 through A0, are used to select the specific memory location of the 8K while A15 through A13 are decoded to

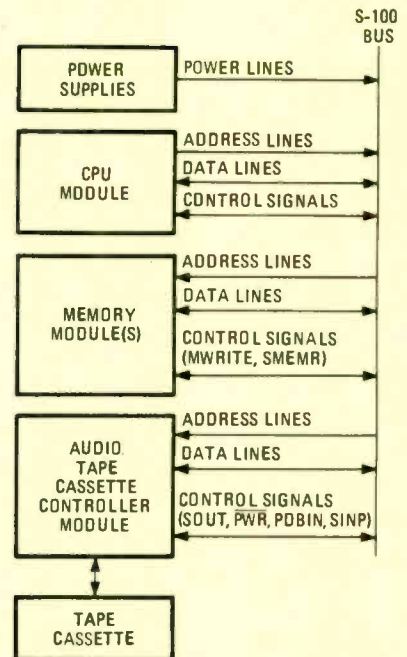


FIG. 6—IF AN 8080 IS NOT USED as the CPU, additional logic may have to be added to create S-100 signals.

select which of the 8K boards is being accessed. Signal MWRITE is used to select the read or write function for the memory IC's on the board, while SMEMR gates the data out to lines D17 through D10 on a memory read.

A typical I/O board in the system is an audio tape controller. The address of the controller is decoded from address lines A7 through A2. Address lines A1 and A0 are used to decode functions of the controller such as read and write. Data is output from the controller on lines D07 through D00 when the controller address is selected on lines A7 through A2, when a write function is specified by A1 and A0 and when SOUT and PWR are logic 1 levels. Signal SOUT indicates "output address available" and PWR indicates "data available." Data is input from the controller from lines D17 through D10 by decoding signals PDBIN, SINP and A7 through A0. Signal PDBIN is the 8080 DBIN (input address available).

The above describes some of the rudiments of S-100 bus operation. Although the S-100 bus has lately taken its share of abuse, it does *work*, it's adaptable, it's fairly efficient, and most importantly it is one of the few standards in an otherwise chaotic hobby.

R-E

ON THE S-100 BUS

This chart is a partial listing of manufacturers of hobby computer products that fit (plug into) the S-100 bus. To conserve space, we have not listed addresses or phone numbers here. **A complete list of addresses and phone numbers is available FREE.** Simply circle number 120 on the Readers Service Card inside the rear cover of this

issue. If we've left anyone out of this directory we'd like to know about it. Send us data on any missing entries so we can include them in the future. This is the first in a continuing series of directories that will cover all aspects of hobby computers. Look for more directories covering other bus systems later this year.

MANUFACTURER	MEMORY INTERFACE											OTHER	
	CPU	FRONT PANEL	RAM	PROM	SERIAL	PARALLEL	CASSETTE	VIDEO	FLOPPY CONTROLLER	MUSIC SYNTH	VOICE SYNTH		MATH
Artec Electronics			•										Prototype; Wirewrap
Canada Systems													Real Time Clock; AC Controller
Central Data	•		•										
CMC Marketing	•		•		•	•			•				A/D Converter; D/A Converter
Computalker Consultants											•		
Cromemco Inc.	•		•	•				•	•				A/D Converter; D/A Converter
Cybercom								•					
Dajen Electronics													2708 Programmer
Databyte													Logic Analyzer
DC Hayes Associates					•								
Digital Group, The						•							AC Controller; DC Controller
Digital Research Group			•	•									
Electronic Control Technology	•		•										Extender; Prototyping
Equinox Div.		•	•										
Extensyn Corp.			•						•				
Godbout			•										Mother, Extender, Control, Terminator Boards
Heurlistics											•		
Imsai	•		•		•	•	•	•	•				
International Data Systems													Clock; Data Access; Frequency Counter; Modem; Clock; D/A Converter
i.O.R.					•	•							
Ithica Audio	•		•	•									Prototype; Blank
Micropolis									•				
Micro Systems Development									•	•			
MITS	•	•	•		•	•	•	•					
Mountain Hardware													AC Controller
National Multiplex													System Controller
Peripheral Vision					•	•							
North Star Computers	•	•	•						•			•	
Priority One Electronics													Extender; Universal Plugboard
Processor Technology			•		•	•	•	•					
SD Sales	•		•										
Solid State Music										•			
Tarbell Electronics							•		•				
TDL	•		•				•	•					System Controller
Thinker Toys					•	•	•	•					
Trace Electronics			•										
Vector Graphics			•			•	•	•	•				
Vector													Universal Plugboards
Vista Computer									•				
Xitex Corp.													Video Terminal
Xybek				•									

HI-FI

New RIAA Equalization For Records

The playback curve of your hi-fi phono system must be the converse of the equalization curve used by the record maker. New equalization curves promise better overall performance

PERHAPS NOT MANY HI-FI ELECTRONICS manufacturers (or even audiophiles) are aware that the Record Industry Association of America (RIAA) has recently approved a brand-new recording and playback equalization curve. Before you panic and start taking your preamplifier, amplifier or receiver back to the manufacturer for modification, let's review some basic facts regarding record equalization, both at the recording and at the playback ends.

Back in the late 1940's and early 1950's, when long-playing records were first invented, almost every record manufacturer used his own form of record equalization. There were practically as many standards as there were record companies. Manufacturers of preamplifiers (separate hi-fi components were the rule in those days) prided themselves on the number of equalization-switch positions they offered on their products' front panels. Some preamplifiers featured as many as 36 different playback curves, and you had to change the setting every time you played a record from a different company.

Why equalization?

You will understand how equalization works during the recording process by considering how a magnetic cutting head works. Normally, such cutting heads operate as constant-velocity devices; that is, given a flat-frequency response input to the cutting head, the cutting stylus moves with constant velocity regardless of the frequency. However, the lower the fre-

LEN FELDMAN
CONTRIBUTING HI-FI EDITOR

quency to be recorded, the farther the cutting stylus must move to maintain its constant-velocity characteristic, as shown in Fig. 1.

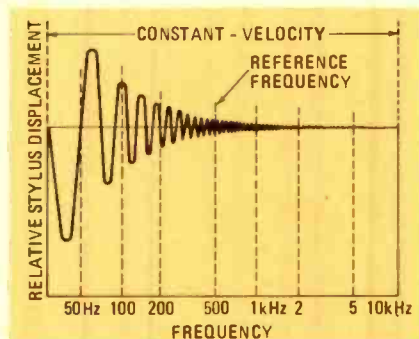


FIG. 1—CONSTANT-VELOCITY CUTTING HEAD requires greater stylus displacement for lower input frequencies.

In the case of a long-playing disc, allowing the cutting head to behave as a constant-velocity device all the way down to the lowest frequency would have meant that grooves would have had to be spaced quite far apart if those high-amplitude, low-frequency undulations were not to cut through from one groove to the next. Early on, it was decided to use a constant-velocity/constant-amplitude characteristic so that below a certain frequency, the cutting stylus moved the same amount from side to side regardless of frequency. Figure 2 shows an idealized constant-velocity/constant-amplitude characteris-

tic with a 500-Hz turnover frequency (the frequency at which stylus motion changes from constant velocity to constant amplitude).

In addition to permitting closer groove spacing by changing the cutting mode at the turnover frequency, recording companies also began to pre-emphasize high frequencies—but for quite another reason. In the high-frequency region, the cutting head again operates in the constant-velocity mode, which means that the amplitude of the wiggles in the groove becomes progressively smaller. At very high frequencies, the amplitude of the signal undulations may not be much

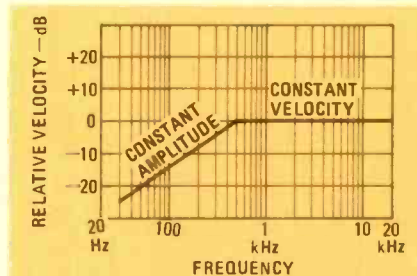


FIG. 2—CONSTANT AMPLITUDE/CONSTANT VELOCITY characteristic used in cutting records.

greater than the inherent surface noise irregularities in the vinyl disc itself. By boosting highs during the recording process, the recording company effectively spreads the distance between signals and noise, or, to put it simply, improves the high-frequency signal-to-noise ratio.

An idealized two-part recording equalization is shown in Fig. 3. Frequencies

below 500 Hz are attenuated, while frequencies above 1 kHz (for example) are boosted. From this basic idea came the

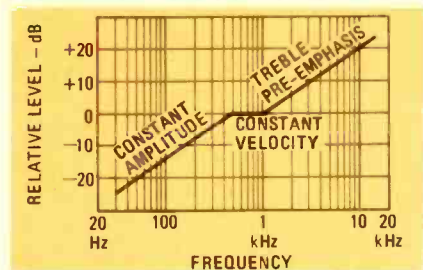


FIG. 3—S/N RATIO at high frequencies is improved by introducing treble pre-emphasis to the constant amplitude/constant velocity characteristic.

many variations of equalization curves that were introduced in early preamplifiers.

RIAA standardization

In June, 1953, the disc recording industry, concerned with the variety of equalization curves required to properly play back recordings from different manufacturers, adopted a standard recording and playback curve that was approved in March, 1964, by both the RIAA and the NAB (National Association of Broadcasters). In a very short time, all discs manufactured worldwide were using these standard curves. The official playback curve used at that time is shown in Fig. 4. This characteristic can be obtained by using a circuit consisting of a parallel L/R network having a 3180- μ s time constant, a series R/C network having a 318- μ s time constant and a parallel R/C network having a 75- μ s time constant. "Zero" reference level is taken at 1000 Hz. An actual frequency response plot taken at the output of a precision phono preamplifier shows how closely the playback curve corresponds to the point-by-

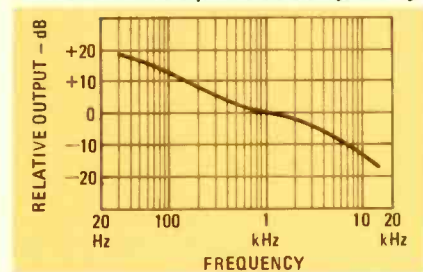


FIG. 4—OLD STANDARD RIAA playback equalization curve has been in use for many years.

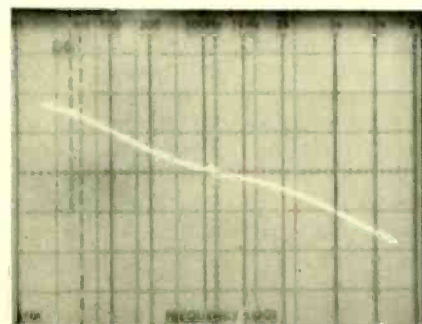


FIG. 5—ACTUAL PLAYBACK EQUALIZATION CURVE of old RIAA standard.

point plot shown in Fig. 4. This plot was stored on the scope face of a spectrum analyzer and is shown in Fig. 5.

In both Fig. 4 and Fig. 5, the frequencies are specified (and shown) only in the 30-Hz to 15,000-Hz range. At the time the RIAA curve was adopted, there were virtually no recordings that contained frequencies beyond those low and high extremes. Even if they did, the likelihood was that home equipment would not have faithfully reproduced such frequency extremes in any case.

However, consider the situation of a typical amplifier manufacturer of the time. Since the low-frequency time constant was set at 3180 μ s, in theory at least, if a manufacturer's amplifier (or preamplifier) had a response below 30 Hz, the bass boost continued to rise, as shown by the extended curve in Fig. 6. If the manu-

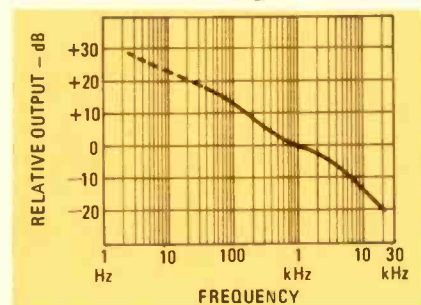


FIG. 6—MANY EQUALIZATION CIRCUITS provide bass boost below the low frequency limit of the old RIAA curve.

facturer did nothing to rolloff the bass response of his product, bass boost provided in the preamplifier-equalizer circuit would be around 20 dB at 20 Hz, 23.0 dB at 10 Hz and, if the amplifier response continued to be even lower (for instance, to 5 Hz) the bass boost would be around 26 dB at that ultra-low subsonic frequency.

Most early records did not contain frequencies below 30 Hz, and amplifiers and preamplifiers did not have uniform response much below 20 Hz either. Therefore, in most cases, there was a natural rolloff in response caused by the amplifier circuit itself rather than by any specific equalization circuitry built into the preamplifier section.

But now, consider what has been happening in amplifier and preamplifier technology in the past few years. Today, it is not uncommon to find amplifiers, preamplifiers and even receivers that have a flat response all the way down to 10 Hz or even lower. Some new so-called DC amplifiers can amplify signals as low as "0 Hertz," or DC! Such amplifiers, when combined with preamplifiers whose low-end equalization rises at a 6-dB-per-octave rate below the RIAA-specified 30-Hz point, can amplify subaudible tones at an increasing rate.

Rumble

Consider what this extreme bass boost does to turntable rumble. In the early

days, most turntables used 4-pole motors that were coupled to the turntable platter either via an idler wheel or via a belt. A 4-pole synchronous motor rotates at 1800 rpm. This translates to 30 revolutions-per-second, or a fundamental vibrational rate (based on the premise that the worst rumble occurs at a once-per-revolution rate of the motor shaft) of 30 Hz. This frequency is, of course, well within the audible range and there isn't much you can do about it.

Today, however, many turntables use motors that rotate at a slower speed. A 16-pole motor (commonly used in a popular line of turntables) has a 450-rpm speed, which translates to a fundamental rotational vibration of only 7.5 Hz. If there is significant vibration transmitted from the motor to the cartridge via the pickup arm, that frequency will be needlessly amplified by some 24 dB referenced to a 1000-Hz signal if the amplifier has flat response down to that low frequency.

Not surprisingly, many amplifier and preamplifier manufacturers have been aware of this problem for some time and have incorporated so-called subsonic cutoff filters that rolloff response beginning at some frequency at or below 20 Hz. While it is true that you cannot hear rumble that occurs at frequencies below 20 Hz, you have only to remove the front grill of one of your speakers while playing a silent groove of any record on your turntable with the volume turned up high to see what such low frequencies do to the woofer cone. You may find that it is wobbling wildly in and out at some subsonic rate that, although inaudible, places the speaker cone in its nonlinear operating range during much of the time that it is trying to reproduce the *music* that you *do* want to hear.

For these reasons, the RIAA has adopted a revised playback curve as well as a slightly revised recording curve. Both new curves are shown in Fig. 7. Note that

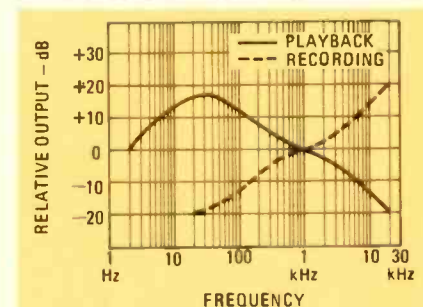


FIG. 7—NEW RIAA EQUALIZATION CURVES. Note the rolloff in playback response in the low frequency region.

the response peak for the bass section of the playback curve now occurs at 31.5 Hz and begins to rolloff below that frequency. The rolloff occurs by introducing a fourth R/C network with a 7950- μ s time constant to the three existing networks that make up the equalization circuit. The high end of the equalization curve is

Should your career in electronics go beyond TV repair?

**CREI prepares you at home
for broader and more advanced
opportunities in electronics —
plus offers you special arrangements
for engineering degrees**

There is no doubt television repair can be an interesting and profitable career field. TV repair, however, is only one of the many career areas in the fast growing field of electronics.

As an indication of how career areas compare, the consumer area of electronics (of which TV is a part) makes up less than one-fourth of all electronic equipment manufactured today. Nearly twice as much equipment is manufactured for the communications and industrial fields. Still another area larger than consumer electronics is the government area. That is the uses of electronics in such areas as research and development, the space program, and others.

Just as television is only one part of the consumer field, these other fields of electronics are made up of many career areas. For example, there are computer electronics, microwave and satellite communications, cable television, even the broadcast systems that bring programs to home television sets.

As you may realize, career opportunities in these other areas of electronics are mostly for advanced technical personnel. To qualify for these higher level positions, you need college-level training in electronics. Of course, while it takes extra preparation to qualify for these career areas, the rewards are greater both in the interesting nature of the work and in higher pay. Furthermore, there is a growing demand for personnel in these areas.

Unlike most other home study schools, CREI programs are devoted exclusively to preparing you for careers in advanced electronics. All of CREI programs are college level. And CREI gives you both theory and practical experience in advanced electronics.

Unique Design Lab

A unique feature of CREI training is its Electronic Design Laboratory Program, which trains you to actually design circuits. It also helps you understand the theories of advanced electronics and gives you extensive practical experience in such areas as tests and measurements, breadboarding, prototype construction, circuit operation and behavior, characteristics of electronic components and how to apply integrated circuits.

Career Training at Home

Only CREI offers this unique Lab Program. It is a complete college lab and, we believe, better than you will find in most colleges. The "Lab" is one of the factors that makes CREI training interesting and effective. And the professional equipment in this program becomes yours to keep and use throughout your professional career after you complete the training.

Engineering Degree

CREI offers you special arrangements for earning credit for engineering degrees at certain colleges and universities as part of your home study training program. An important advantage in these arrangements is that you can continue your full time job while "going to college" with CREI. This also means you can apply your CREI training in your work and get practical experience to qualify for career advancement.

Wide Choice of Programs

CREI gives you a choice of specialization in 14 areas of electronics. You can select exactly the area of electronics best for your career field. You can specialize in such areas as computer electronics, communications engineering, microwave, CATV, television (broadcast) engineering and many other areas of modern electronics.

FREE Book

In the brief space here, there isn't room to give you all of the facts about CREI college-level, home study programs in electronics. So we invite you to send for our free catalog (if you are qualified to take a CREI program). The catalog has over 80, fully illustrated pages describing your opportunities in advanced electronics and the details of CREI home study programs.

Qualifications

You may be eligible to take a CREI college-level program in electronics if you are a high school graduate (or the true equivalent) and have previous training or experience in electronics. Program arrangements are available depending upon whether you have extensive or minimum experience in electronics.

Send for this **FREE** Book describing your opportunities and CREI college-level programs in electronics



Mail card or write describing qualifications to

CREI **CAPITOL
RADIO
ENGINEERING
INSTITUTE**

McGraw-Hill Continuing Education Center
3939 Wisconsin Avenue Northwest
Washington, D.C. 20016

Accredited Member National Home Study Council

GI Bill

CREI programs are approved for training of veterans and servicemen under the G.I. Bill.



Frequency*	Relative level (dB referenced to 1 kHz)		
	"Old" RIAA	"New" RIAA	Net Difference
100	+13.11	+12.9	-0.21
80	—	+14.2	—
70	+15.31	—	—
50	+16.96	+16.3	-0.66
40	—	+16.8	—
30	+18.61	+17.0**	-1.60
20	—	+16.3	—
16	—	+15.4	—
8	—	+11.2	—
4	—	+5.7	—
2	—	-0.2	—

*For frequencies above 100 Hz, old and new curves are the same.

**Actually listed as 31.5 Hz in new RIAA curve.

TABLE I—COMPARING THE OLD AND NEW RIAA EQUALIZATION curves at specific frequencies.

extended to 20 kHz because recording at this frequency is not only practical but is, in fact, taking place on many current discs. At the high end of the playback curve, however, no change in preamplifier equalization circuitry is required, since the existing 75- μ s rolloff network does the job out to 20 kHz and beyond. The curve has simply been extended to recognize points out to 20 kHz.

With respect to the low end of the playback curve, adding the fixed rolloff network will make a difference. Table I shows the old and new RIAA bass-boost values from 100 Hz down. Next to these values are listed the difference (in dB) between the old and new equalization curves. Note, for example, that while at 100 Hz the difference is hardly significant (0.2 dB), at 50 Hz it amounts to 0.66 dB, and at 30 Hz (the previous end point of the old curve) it is more than 1.6 dB!


Such a difference in response may not seem significant, but when you compare the subsonic region of Fig. 6 with the now specified subsonic response of the new

RIAA curve, the importance of this change becomes apparent.

In a very real sense, the use of the new playback curve in preamplifiers, integrated amplifiers and receivers should significantly reduce turntable rumble quite audibly. Using the rumble frequency of 7.5 Hz cited earlier, we have already noted that an amplifier not equipped with any form of subsonic rolloff would provide about 24 dB of boost at that low frequency. Based upon the new RIAA curve, boost at the 7.5-Hz frequency will be down to only around 11.0 dB—an improvement of 13 dB at that particular rumble frequency.

Older equipment

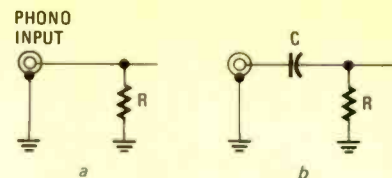Equalization circuit values differ from manufacturer to manufacturer and from product to product (usually, equalization constants are included in a negative-feedback network around the two or three amplification stages contained in the low-level preamplifying section of a preamplifier or amplifier). It would therefore



VALUES FOR 7950 TIME CONSTANT	
IF R IS NOW	CAPACITOR ADDED SHOULD BE
22K OHMS	0.36 μ F
47K OHMS	0.17 μ F
100K OHMS	0.08 μ F

FIG. 8—TYPICAL PHONO INPUT JACK arrangement in the preamplifier stages is shown in a. Simple modification to obtain new RIAA playback equalization is shown in b.

be impossible to advise what new resistor and capacitance values to add to your present preamplifier circuitry so that it conforms with the new RIAA curve. A simpler modification can be made, assuming that the manufacturer of your equipment has no other suggestions or recommendations. As you know, most phono input jacks are terminated with a 47,000-ohm resistor, which magnetic cartridge manufacturers recommend as the optimum load resistance. By adding a high-quality miniature Mylar capacitor of appropriate value, you can easily obtain the rolloff characteristic required by the new RIAA curve. Figure 8-a shows the typical phono input jack arrangement, with the load resistor wired directly across the phono input cartridge. In some instances, you may have to follow the shielded cable to its other end if no resistor is directly wired across these jacks. Figure 8-b shows a small capacitor added in series with the signal side of the load resistor, and the accompanying table in Fig. 8 shows values of capacitance to be used with commonly found load-resistor values.

It is to be hoped that designers and manufacturers of preamplifiers, amplifiers and receivers will quickly incorporate the new RIAA playback curve in their future products, since it will benefit record reproduction (regardless of turntable equipment). This is an improvement that has been a long time coming. **R-E**

CCD memories will replace MOS and core RAM's

Charge-coupled device (CCD) memories, while in some cases still being lab-tested, will be the next device adopted by the computer industry. CCD's will replace fixed-head disc storage, particularly low-end floppy discs. The CCD format of storing data is similar to that of mechanical discs, which will simplify its adaptation to present systems.

Texas Instruments and Fairchild are presently shipping samples of 65K-bit devices, while Intel Corporation and Motorola have devices that are still in the planning stage. Users will have a choice of three different CCD's, with the first size (65K) large enough to be a cost-effective replacement for mechanical storage units. Howev-

er, it is expected that the main use for the CCD's will be in auxiliary or main-storage applications, completely replacing MOS and core RAM's. Before this can happen, however, entire systems will have to be redesigned to incorporate the CCD's.


Texas Instruments introduced its 65K IC last March; Fairchild produced a scaled-up version on its earlier 16K devices; and Intel Corporation plans to introduce samples of its 65K device this spring. Motorola will produce a similar device, using Fairchild masks. The Fairchild and TI devices are organized in $16 \times 4K \times 1$ format (or 16 randomly accessible shift registers, each one 4,096-bits-long and arranged in an interleaved serial-parallel-serial structure that keeps power low and operating rate high). The Intel part looks like a RAM, with

256 loops of 256 bits each . . . to shorten latency time . . . and is also completely TTL compatible.

All manufacturers agreed that although CCD's will be harder to use than dynamic RAM's, the low-cost factor will dictate the success of the anticipated changeover to CCD's. It is estimated that the devices will have a minimum 4:1 cost advantage over RAM's.

The real key, however, to the final acceptance of CCD's, according to one spokesman, will be in standardization of design. At present, both Fairchild and TI use 16-pin devices and $16 \times 4K \times 1$ arrays; Fairchild's unit comes in the standard 0.3-inch-wide package, TI's in a 0.4-inch-wide configuration. And Intel uses an 18-pin device in a 0.3-inch-wide package.

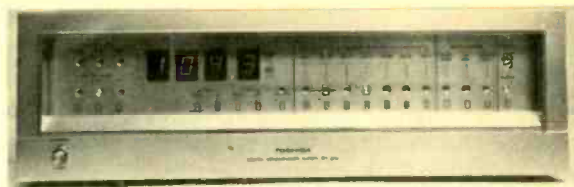Radio-Electronics Tests Toshiba ST-910 FM Tuner



CIRCLE 101 ON FREE INFORMATION CARD

LEN FELDMAN
CONTRIBUTING HI-FI EDITOR



THE TOSHIBA MODEL ST-910 IS THE MOST UNUSUALLY configured FM tuner we have ever seen or tested. The front panel (shown in Fig. 1) is completely devoid of knobs and conventional switches, except for a single mechanically operated power on-off pushbutton switch at the lower left of the front panel. Nor is the tuner equipped with a conventional type of frequency dial scale. So, to operate this handsome tuner, you simply touch appropriate points on the large screened glass surface that occupies about two-thirds of the front panel. Along the bottom edge of this glass area are no less than 19 small rectangular areas, each of which contains a touch switch composed of invisible, transparent electrodes. When you touch one of these areas, a small "hum" voltage is developed that signals the all-electronic switches to perform the various tuner functions.

The first three touch-switch areas determine the muting-threshold level. Touch one of these areas and a green light illuminates just above the area. Directly above these three green lights are three tiny red lights, each illuminating at a prescribed signal-strength input. If only the leftmost muting-level switch is touched, then any signals equal to or greater than the level needed to light the first signal-level light can overcome the muting circuitry. If the third muting-level switch is touched, then only those signals that are strong enough to light up all three red signal-level lights can overcome the muting-threshold level. When power is first applied, the first (lowest signal level) muting-level light comes on automatically, and, as we later learned, signals above around 7 μ V (22.1 dBf) will be received. All muting can be defeated (for ultra-weak signal reception) by touching the first already-illuminated muting-level switch area, at which time the green light goes out and the tuner is "wide open" regardless of incoming signal strength. However, interstation noise will also be heard when you tune up or down the frequency band.

The four darkened windows to the right of the signal-level indicators display tuned-to frequencies in bright red digits. The tuning range is from 87.5 MHz to 107.9 MHz in 100-kHz (0.1-MHz) increments. Increments of 100 kHz were chosen because even though FM stations in the U.S. are always assigned at 200-kHz intervals (i.e., 88.1, 88.3, etc.), this is not

the case in Europe and other foreign countries.

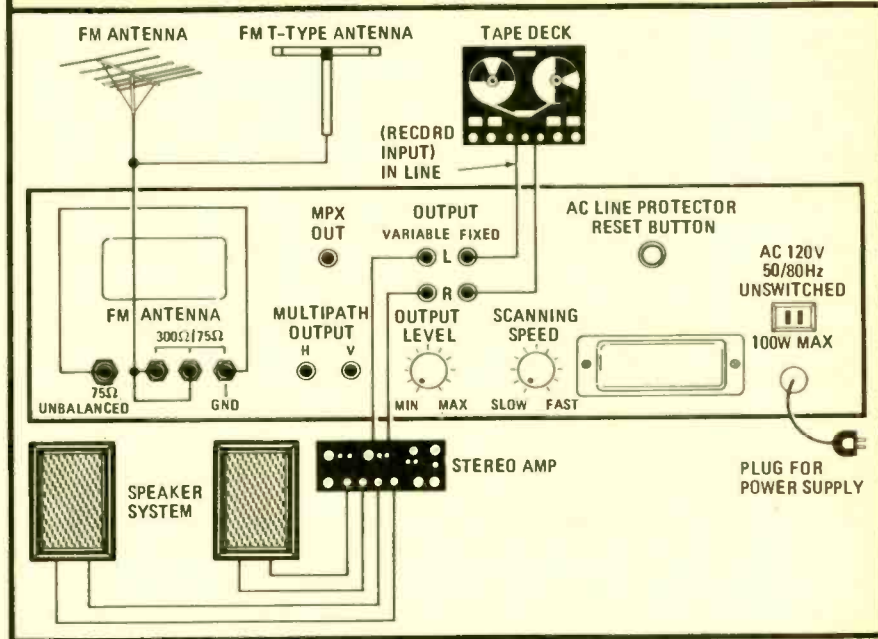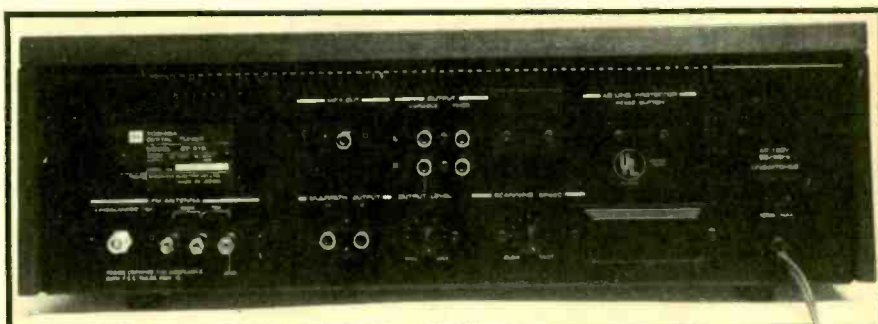Manual tuning is accomplished by means of four touch-switch areas located beneath the frequency readout windows. The first two switch areas are labeled UP and DOWN, and touching either of them shifts the receive frequency in 1-MHz increments (either up or



MANUFACTURER'S PUBLISHED SPECIFICATIONS:

Usable Sensitivity: mono, 1.8 μ V. **S/N Ratio:** mono, 75 dB. **Total Harmonic Distortion** (400 Hz, 100% modulation): mono, 0.15%; stereo, 0.2%. **Frequency Response:** 20 Hz to 15 kHz, \pm 0.5 dB. **Alternate Channel Selectivity:** 85 dB. **Image Rejection:** 100 dB. **IF Rejection:** 100 dB. **Spurious Rejection:** 100 dB. **AM Suppression:** 65 dB. **Capture Ratio:** 1.5 dB. **FM Stereo Separation:** 40 dB at 1 kHz. **Rated Output Level:** fixed, 650 mV (400 Hz, 100% modulation); variable, 0 to 2.0 V (400 Hz, 100% modulation). **Output Impedance:** 1000 ohms. **Power Requirements:** 120V, 60 Hz, AC. **Power Consumption:** 30 watts. **Dimensions:** 450 mm W \times 143 mm H \times 340 mm D. **Weight:** 8 kg (17.64 lbs.). **Suggested Retail Price:** \$1800.

down). The second pair of touch switches shifts the tuned-to frequency in 100-kHz increments, again either up or down, each time the appropriate switch is touched.

Next in line is a touch switch labeled MEMORY. Touching this switch turns on a red light above the switch. You then have approximately three seconds to enter the displayed frequency into one of the seven available "sensor" or memory channels by touching one of the available touch-switch areas numbered from 1 through 7. A green light above the selected

channel switch comes on, the red light above the MEMORY switch flashes brightly and is extinguished, and the selected frequency is permanently stored in the channel memory of your choice. In the future, to recall that frequency, just touch the appropriate touch switch again, and the frequency is recalled and appears in the readout. The frequency remains in memory even if the power is shut off and the set turned on at another time, just as long as the power plug remains connected to the wall outlet.

There is a third tuning method called AUTO TUNING. Two more touch-switch areas, labeled UP START and DOWN START are located to the right of the seven memory switches. When either the UP START or DOWN START switch is touched, the tuner starts scanning frequencies (either up or down) until a signal is received that is equal to or greater than the previously selected muting-level threshold. Another switch area next to these two areas labeled STEREO ONLY permits only stereo signals to overcome the muting circuitry. Activating this switch causes a light to come on just above it, to remind you that this mode has been selected. Finally, a touch-switch area labeled MONO, at the extreme lower right-hand corner of the panel, permits you to deliberately alter stereo reception to the monophonic mode, in case stereo signals are too weak and noisy. A stereo indicator above this last switch lights up when stereo signals are received. To return to stereo reception or to automatic mono/stereo switching, simply touch the MONO switch a second time and the light above it goes out.

The rear panel shown in Fig. 2 has screw-type antenna terminals for 300-ohm or 75-ohm transmission-line connection, along with a standard coaxial connector for using 75-ohm coaxial lead-in cable with an appropriate mating connector. Also provided are output jacks for connection to horizontal and vertical oscilloscope inputs for observing multipath reception (and properly orienting an antenna for least multipath interference), and an output jack that delivers a composite detector-output signal. (The latter might be needed if the FCC ever approves four-channel discrete FM broadcasting.) Next come output jacks that deliver fixed and variable audio levels, and below them

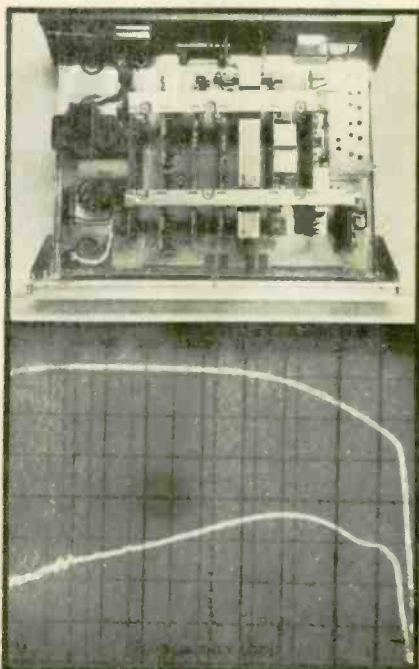


TABLE I
RADIO-ELECTRONICS PRODUCT TEST REPORT

Manufacturer: Toshiba

Model: ST-910

FM PERFORMANCE MEASUREMENTS

SENSITIVITY, NOISE AND FREEDOM FROM INTERFERENCE	R-E Measurement	R-E Evaluation
IHF sensitivity, mono (μ V) (dBf)	1.8 (10.3)	Good
Sensitivity, stereo (μ V) (dBf)	3.6 (16.3)	Very good
50-dB quieting signal, mono (μ V) (dBf)	2.8 (14.1)	Excellent
50-dB quieting signal, stereo (μ V) (dBf)	40.0 (37.3)	Fair
Maximum S/N ratio, mono (dB)	80	Excellent
Maximum S/N ratio, stereo (dB)	70	Very good
Capture ratio (dB)	1.6	Good
AM suppression (dB)	65	Excellent
Image rejection (dB)	100+	Superb
IF rejection (dB)	100	Excellent
Spurious rejection (dB)	100+	Superb
Alternate channel selectivity (dB)	85	Excellent
FIDELITY AND DISTORTION MEASUREMENTS		
Frequency response, 50 Hz to 15 kHz (\pm dB)	0.5	Excellent
Harmonic distortion, 1 kHz, mono (%)	0.08	Excellent
Harmonic distortion, 1 kHz, stereo (%)	0.085	Superb
Harmonic distortion, 100 Hz, mono (%)	0.18	Good
Harmonic distortion, 100 Hz, stereo (%)	0.17	Very good
Harmonic distortion, 6 kHz, mono (%)	0.17	Fair
Harmonic distortion, 6 kHz, stereo (%)	0.10	Excellent
Distortion at 50-dB quieting, mono (%)	1.4	Fair
Distortion at 50-dB quieting, stereo (%)	0.45	Good
STEREO PERFORMANCE MEASUREMENTS		
Stereo threshold (μ V) (dBf)	3.6 (16.3)	Very good
Separation, 1 kHz (dB)	39	Good
Separation, 100 Hz (dB)	48	Excellent
Separation, 10 kHz (dB)	29	Good
MISCELLANEOUS MEASUREMENTS		
Muting threshold (μ V) (dBf)	7, 60, 500 (22, 40.8, 59.2)	Excellent
Dial calibration accuracy (\pm kHz at MHz)	"Perfect"	Perfect
EVALUATION OF CONTROLS, DESIGN, CONSTRUCTION		
Control layout		Excellent
Ease of tuning		Superb
Accuracy of meters or other tuning aids		Perfect, see text
Usefulness of other controls		Excellent
Construction and internal layout		Excellent
Ease of servicing		Good
Evaluation of extra features, if any		Excellent
OVERALL FM PERFORMANCE RATING		Very good

TABLE II
RADIO-ELECTRONICS PRODUCT TEST REPORT

Manufacturer: Toshiba

Model: ST-910

OVERALL PRODUCT ANALYSIS

Retail price	\$1800
Price category	High
Price/performance ratio	Good
Styling and appearance	Excellent
Sound quality	Excellent
Mechanical performance	See text

Comments: There is no doubt that a good deal of the cost of this unusual FM tuner has been apportioned to its sophisticated touch-switch operation, its all-electronic operation and its seven-station memory capability. The audio purist may regard some or all of these features as pure "gimmickry," but at least one aspect of the novel design *does* contribute to audibly improved FM reception. That is the frequency-synthesized tuning. While it is true that other tuners we have measured can deliver as low distortion as this one (some do even better at the low- and high-frequency extremes), you must bear in mind that those ultra-low distortion results are obtained in our laboratory using a distortion analyzer hooked up to the tuner that enables us to tune to such minimum-distortion points. The home user rarely, if ever, has that advantage and must usually depend upon less-than-accurately calibrated center-tune meters. Even slight tuning errors create great increases in distortion. In the case of the *model ST-910*, no such tuning errors are possible. What you read on the digital readout is what you get—in frequency, that is. As for the novel touch-switch operation, it certainly does lend an air of elegance to the tuner and, as Toshiba points out, purely electronic switching of this type is not subject to wear or "dirty contacts" with extended use. On the other hand, such refinements do not, in and of themselves, contribute to better FM sound. At this price level, too, we would have expected to find some built-in means for indicating multipath distortion rather than having to use an externally connected oscilloscope.

is an output-level control. A second matching knob varies the scanning speed of the auto-tuning mode, as described previously. A line circuit-breaker pushbutton and an unswitched convenience AC outlet with 100-watt capacity complete the rear-panel layout. The dual pairs of output jacks permit you to connect a tape deck directly to the fixed output jacks, while the variable output jacks can be connected to the amplifier, as shown in Fig. 3.

Internal construction and circuitry

Figure 4 shows the internal layout of the *model ST-910* and, as might be expected, the parts density is extreme. To give you some idea of the complexity of the frequency-synthesis tuning system and its associated memory circuits, the *model ST-910* contains 32 transistors, 9 FET's, 100 diodes, 11 linear IC's, 85 digital IC's and 24 LED's!

The linear portions of the tuner include two RF stages using cascaded FET's and varicap diodes for front-end tuning. The IF section contains LC filtering (multipole) and a broad-band ratio detector. Phase-locked-loop circuitry is used in the multiplex decoder section.

Performance measurements

Table I summarizes major laboratory performance measurements, only a few of which can be compared with the manufacturer's specifications that are quite sparse for a tuner of this quality. Nevertheless, in absolute terms, the tuner's measured performance, although not quite as good as that of the highest-quality conventionally designed tuners we have measured, is more than adequate for good reception under most listening conditions. Distortion at midfrequencies was, in fact, excellent in both the mono and stereo modes, but tended to rise a bit too rapidly at the low- and high-frequency extremes. AM suppression and other rejection specifications were superb, however, and it is these lesser specifications that often make the difference between a very good tuner and an excellent one.

A plot of separation-versus-frequency is shown in Fig. 5, with the upper trace representing the response of the tuner to the "desired" channel (including 75- μ s de-emphasis) and the lower trace showing the output from the opposite stereo channel under the same modulating conditions.

Use and listening tests

The *model ST-910* is a joy to use. On occasion, we did note that touching certain touch-switch areas did not immediately activate the corresponding switching function. However, we found that this problem was immediately corrected by gripping the front panel with the other hand. In any case, it takes only a few minutes to become familiar with the unit's novel switching arrangement and memory capabilities. The transition from muting to receiving is completely without the accompanying noise, clicks or pops so often associated with some muting circuits.

A summary of this product will be found in Table II, together with our overall product evaluation. Certainly, the *model ST-910* is a great engineering accomplishment and we can easily understand why it is so costly. The well-heeled audio hobbyist may find this tuner hard to resist, especially after playing with its touch switches for a while. The less-affluent audiophile will have to settle for lower-cost tuners that receive FM broadcast signals as well (and sometimes better) than the *model ST-910*.

R-E

U.S. Pioneer RT-707 Tape Deck

CIRCLE 102 ON FREE INFORMATION CARD

LEN FELDMAN
CONTRIBUTING HI-FI EDITOR

THOSE READERS WHO ARE OLD ENOUGH TO remember some of the first open-reel tape decks designed for home use many years ago will experience a feeling of *déjà vu* when they see the new U.S. Pioneer Electronics *model RT-707* open-reel tape deck shown in Fig. 1. The wide, rack-mountable square shape resembles some of the old Magnecord decks popular some time back, and lends itself beautifully to home installation on a shelf or table top, unlike some tall, top-heavy open-reel units presently on the market. Don't be misled by appearances, however. The *model RT-707* is a modern and sophisticated open-reel machine, and, at its unusually low suggested price, may appeal to those serious home recordists who might otherwise purchase a cassette deck.


The tape deck's low profile does, of course, limit reel size to a 7-inch reel (even these reels project a bit above the top of the unit). But with the available speeds of 7½ ips and 3¾ ips, maximum recording time is as great as might be obtained with 10-inch reels at twice the

speed. With the excellent frequency response and high signal-to-noise ratio available at the 7½-ips speed, there is really no important loss in performance compared with the higher professional 15-ips speed machines—especially in view of the low wow-and-flutter figures obtainable at the 7½-ips speed.

Controls near the top of the deck (between the reels and surmounting the twin record-level meters) include a power ON-OFF pushbutton, a speed selector pushbutton, a TAPE/SOURCE monitor pushbutton, BIAS and EQ pushbuttons and individual left- and right-channel record pushbuttons. Wide-throw meters are calibrated from -20 dB to +3 dB. Between the meters are RECORD and PAUSE indicator lights; while below the meters are a four-digit counter, a RESET control, a REPEAT-play pushbutton and a pitch-control knob that varies playback speed by approximately $\pm 6\%$. Since this machine can be operated in either direction, it comes with four tape heads (record, erase and two playback heads). The playback heads and the record head are made of hard Permalloy, while the erase head is made of ferrite. The heads are protected by a metal cover, with screw holes provided for azimuth

adjustment of both playback heads and the single record head. Quarter-track configuration is supplied.

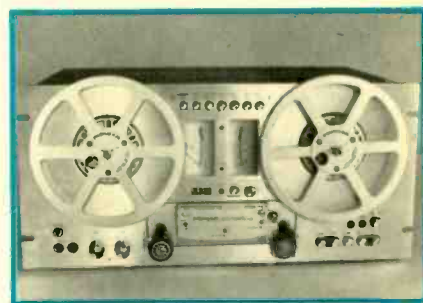Beneath the supply reel are two microphone input jacks, a stereo headphone output jack, a dual concentrically mounted microphone input and line input-level controls. Beneath the take-



up reel on the right are a PAUSE pushbutton, fast-forward and fast-rewind pushbuttons, STOP pushbutton, PLAY and RECORD pushbuttons, and a pair of pushbuttons with arrow lights indicating the direction of tape travel.

Drive system

The *model RT-707* uses three separate drive motors: A frequency-generating AC servomotor drives the single-capstan tape-drive system while two 6-pole inner-rotor induction motors handle reel rotation in both the play and fast-wind modes. A large flywheel is associated with the tape-drive motor. The motor is controlled by logic circuitry so that it is possible to switch from mode to mode without going through STOP. This same feature also permits you to rock the transport system between fast forward and fast rewind for locating specific points on a tape smoothly.

MANUFACTURER'S PUBLISHED SPECIFICATIONS:


Maximum Reel Size: 7 inches. **Speeds:** 7½ ips and 3¾ ips. **Speed Accuracy:** $\pm 0.5\%$. **Fast Rewind Time:** 1200 feet, approximately 100 seconds. **Wow and Flutter:** 7½ ips, 0.05% WRMS; 3¾ ips, 0.08% WRMS. **S/N Ratio:** better than 58 dB (referenced to a +6-dB record level). **Harmonic Distortion:** less than 1.0% at 7½ ips. **Frequency Response:** measured at -20-dB record level, 30 Hz to 24,000 Hz, ± 3 dB at 7½ ips; 30 Hz to 16,000, Hz ± 3 dB at 3¾ ips. **Crosstalk and Stereo Separation:** better than 50 dB. **Erase Coefficient:** 70 dB. **Bias Frequency:** 125 kHz. **Input Sensitivity:** mike, 0.25 mV (125 mV maximum); line, 50 mV (25 volts maximum); DIN, 16 mV. **Output:** at 0-dB reference: line, 450 mV; headphone, 70 mV into 8-ohm loads. **Power Requirements:** 120 volts, 50 to 60 Hz, 120 watts maximum. **Dimensions:** 18²⁹/₃₂ W X 9¹/₁₆ H X 14¹/₃₂ D. **Net Weight:** 43 lbs., 10 oz. **Suggested Retail Price:** \$575.

Laboratory measurements

We made all our measurements using 1200-foot reel lengths of *Scotch 206* recording tape because Pioneer's own published specifications are referenced to this tape. The results of our measurements are shown in Table I.

Figure 2 is a scope photo of the record/playback response at the 7½-ips speed, using record levels of 0-dB (upper trace) and -20-dB (lower trace). Note that even at the high 0-dB record level, response just begins to roll off at the 20-kHz extreme, while at the lower, -20-dB record level, the response is flat to beyond the 20-kHz sweep limit. Of course, this is one of the key advantages of an open-reel machine as compared with even the best tape cassettes. In the latter, any attempt to record a 20-kHz frequency sweep at 0-dB record level results in extreme tape saturation and extensive rolloff at the high end.

Figure 3 shows some evidence of this effect. In this test, the slower 3¾-ips speed was used, and three frequency sweeps were measured and displayed on the scope face. The upper trace shows the 0-dB sweep, -10 dB and -20 dB (in the bottom trace). When this slower speed is used, the greater amount of treble equalization during recording does result in tape saturation at the higher record levels, but at the -20-dB record level, the response extends to above 16 kHz.

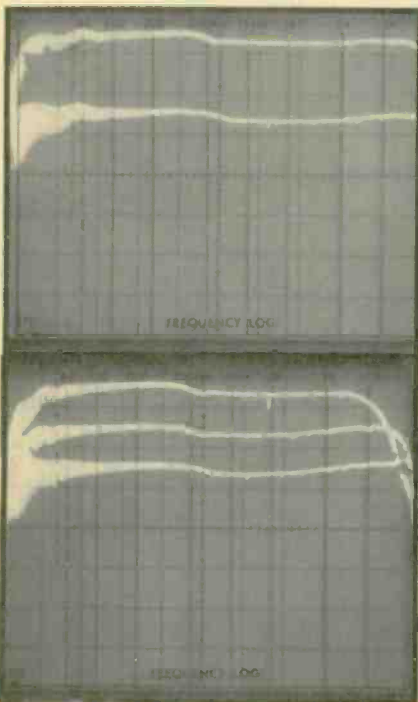

Harmonic distortion was generally much lower than would be obtained at equivalent record levels using a high-quality cassette deck. And, of course, the 64.5-dB signal-to-noise ratio (referenced to the 3% THD record level, or +10 dB) was observed *without* the aid of any separate noise-reduction system such as Dolby.

Summary

Our overall product evaluation together with comments are shown in Table II.

Pioneer has produced a fine open-reel machine at a relatively modest price that gives the serious home recordist on a limited budget a real choice between a cassette and an open-reel instrument. **R-E**

TABLE 1

RADIO-ELECTRONICS PRODUCT TEST REPORT

Manufacturer: U.S. Pioneer Electronics

Model: RT-707

OPEN-REEL TAPE DECK MEASUREMENTS

FREQUENCY RESPONSE MEASUREMENTS STANDARD TAPE	R-E Measurements	R-E Evaluation
Frequency response at 15 ips (Hz-kHz, ± dB)	N/A	N/A
Frequency response at 7½ ips (Hz-kHz ± dB)	21-21, 3	Excellent
Frequency Response at 3-3/4 ips (Hz-kHz ± dB)	29-16, 3	Very good
CrO₂ TAPE		
Frequency response at 15 ips (Hz-kHz, ± dB)	N/A	N/A
Frequency response at 7½ ips (Hz-kHz, ± dB)	N/A	N/A
Frequency response at 3¾ ips (Hz-kHz ± dB)	N/A	N/A
(See Figs. 2,3)		
DISTORTION MEASUREMENTS (RECORD/PLAY)		
Harmonic distortion at -3 VU (highest speed) (%)	0.6	Very good
Harmonic distortion at 0 VU (highest speed) (%)	0.7	Excellent
Harmonic distortion at +3 VU (highest speed) (%)	0.8	Excellent
Record level for 3% THD (dB)	+10.0	Excellent
SIGNAL-TO-NOISE RATIO MEASUREMENTS		
Best S/N ratio, standard tape (dB)	64.5	Excellent
Best S/N ratio, CrO ₂ tape (dB)	N/A	N/A
MECHANICAL PERFORMANCE MEASUREMENTS		
Wow and flutter at 15 ips (% WRMS)	N/A	N/A
Wow and flutter at 7½ ips (% WRMS)	0.045	Excellent
Wow and flutter at 3¾ ips (% WRMS)	0.06	Superb
Rewind time, 1200-foot tape (seconds)	65	Good
COMPONENT MATCHING CHARACTERISTICS		
Microphone input sensitivity (mV)	0.2	
Line input sensitivity (mV)	44	
Line output level (mV)	440	
Phone output level (mV or mW)	73 mV/8 ohms	
Bias frequency (kHz)	125	
TRANSPORT MECHANISM EVALUATION		
Action of transport controls		Superb
Tape guidance system		Very good
Absence of mechanical noise		Excellent
Tape head accessibility		Very good
Construction and internal layout		Excellent
Evaluation of extra features, if any		Excellent
OVERALL TAPE DECK PERFORMANCE RATING		Excellent

TABLE II

RADIO-ELECTRONICS PRODUCT TEST REPORT

Manufacturer: U.S. Pioneer Electronics

Model: RT-707


OVERALL PRODUCT ANALYSIS

Retail price	\$575
Price category	Low
Price/performance ratio	Excellent
Styling and appearance	Superb
Sound quality	Very good
Mechanical performance	Excellent

Comments: In recent years, most open-reel tape deck manufacturers have been catering to supposed needs of semiprofessional home recordists; those who simply want to record and listen to music on tape just for sheer listening pleasure have had to opt for better-quality cassette decks. High-priced open-reel decks of rather large proportions have generally been the rule. Pioneer has changed all that with this unusual open-reel machine. The *model RT-707* fits nicely on a shelf along with other components. All the advantages of an open-reel unit (easy editing, higher dynamic range and better signal-to-noise ratio compared with even the best cassettes) are retained, plus a few extra features that may be received with indifference by the "pro" recordist but will be much appreciated by the home user. These include the auto reverse playback feature, the repeat-play option (using sensing tape at one end of the tape and the 0000 setting of the tape counter as cues for the logic control system) and the pitch control, which insures in-tune playback of tapes made on other, less-than-perfect-speed recorders. Considering the going prices of competitive open-reel decks, we found it almost unbelievable that Pioneer was able to provide three-motor direct drive logic-actuated transport systems for the relatively low price indicated. Separate control of left- and right-channel recording provides even more flexibility and permits sound-on-sound recordings (by changing rear-panel amplifier patching). With response to well beyond 20,000 Hz in the high-speed mode, this open-reel machine outperforms cassette decks costing considerably more. Its mechanical and electrical performance, as well as its imaginative physical configuration, is likely to prompt many a prospective recordist to consider going back to open reel instead of settling for a cassette deck.

Selecting A DMM—

What you should look for

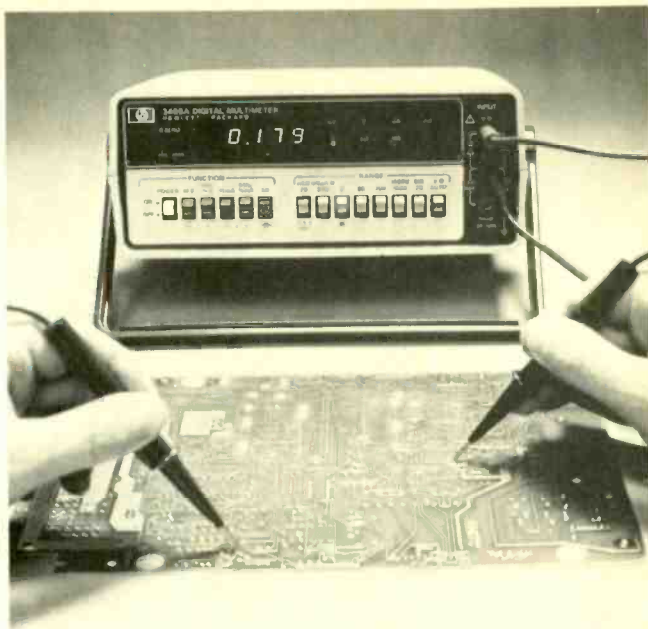

If you think you know everything about DMM's, you probably don't. So, let's follow the trials and tribulations of George Tinkerer after he's bought one.

MARSH FABER*

THE LOUD RING OF THE DOORBELL BREAKS the silence.

"I'll get it!"

George Tinkerer bounds down the stairs, throws open the door and greets the mailman like a long-lost brother.

"It's here, Blanche! It's here!"

"What's here, George?" his wife answers.

"My new DMM! My new Whoopee-tronics automatic dual-sensing, parametrically perambulating, 65-function, three-phase voltmeter."

"You mean you spent \$294.68 of Junior's future college fund for that?"

George ignores his wife's subtle prod as his trembling fingers unveil the prize. George savors every second with superhuman restraint. Ever so slowly, he uncoils the power cord and dramatically inserts the plug into the wall receptacle. The box responds with an impressive display of red zeros.

"Big deal, George. What does it do?"

"It measures volts, ohms and amperes."

"Fantastic. So what's a volt, George?"

"A volt is one of those things that comes out of the wall. I'll show you."

"Don't you think you better read the manual first, George?"

"Nah! Manuals are for amateurs. Look, you just take these probes and stick them in the wall socket, like this."

Of course, George Tinkerer's Whoop-

pee-tronics prestidigitator isn't ready to read 115 volts AC. In fact, it is eagerly looking forward to telling him what value resistor he might have in his hand.

As George applies his house current to the ohms input, the DMM responds predictably by smoking, arcing, hemorrhaging internally; it raises itself three inches off the bench and self-immolates. George is thrown to the floor. Blanche is scared out of three inches of baby fat and the new toy lies groaning and smoldering on George's blackened workbench.

Following the \$294.68 holocaust, George regains his wife's good graces by babysitting eight Saturdays in a row, dropping out of the bowling league and cleaning up the garage—not once, but twice. George's true cost of owning a DMM is more than any man should have to pay.

George's plight is less fantasy than fact. The initial purchase price of a DMM may be irrelevant compared to the cost and hassle resulting from the abuse of poorly designed protection circuitry.

George is a charter member in the most difficult customer group that a DMM manufacturer must cater to. As recently as ten years ago, DMM's were available only to a select few people supported by corporate research budgets. They were expensive and hardly portable; and they were designed for the sophisticated user who demanded the ultimate in accuracy.

Today, DMM manufacturers cater to

George. They produce small, portable instruments, at reasonable prices with the emphasis on durability. George may not have as much training and experience as a man in a standards lab, but he is much more demanding. When he makes a mistake in using his DMM, he expects the instrument to shrug off the overload and "keep on ticking."

In order to design a multimeter that is within George's price range, the manufacturer must make engineering trade-offs. The consumer must therefore beware of enticingly low price tags and consider the compromises that may have been made. The initial cost, usability, serviceability and dependability must all be considered.

Initial cost

The most obvious cost in owning a DMM is the purchase price, which is the amount that usually headlines the advertisement for the instrument. However, this amount may not include the cost of necessary options or attachments.

Always obtain a data sheet before ordering any piece of equipment. Often an accessory is listed on the data sheet that you must add to the instrument before it is capable of performing your desired measurement.

Such options and accessories include batteries, chargers, carrying cases, various probes and test leads. External accessories, such as probes, are easy to order at a later date, but some options may be

* Design Engineer, Hewlett-Packard

factory-installed in the main body of the instrument and should be considered carefully at the time of purchase. Field installation of certain options may not be possible.

Usability

George Tinkerer had a specific application in mind when he bought his multimeter. Had he not destroyed it upon receipt, he would have eventually judged its usefulness by how well it performed in his measurement application. George wanted a DMM that met his requirements, but he didn't want to pay extra money for capability that he would never use.

In order to receive the best return on his investment, George should have scrutinized and understood the data-sheet specifications. The most fundamental data-sheet specifications are often misinterpreted. Resolution, sensitivity and accuracy characterize the fundamental capability of any DMM.

The overrange capabilities of DMM's vary widely, and their labeling can often be ambiguous. Technically, the number of digits a DMM can display is the logarithm of the maximum reading (number of counts). For example:

Maximum reading	$\text{Log}_{10} \times$	Advertised resolution
1000	3	3 digits
1099	3.04	3½ digits
1999	3.30	3½ digits
2999	3.48	3½ or 3¾ digits

Some definitions take the \pm sign into account, which doubles the number of total counts and adds 0.3 digits to the $\text{Log}_{10} \times$ value. Thus, a ± 1999 -count DMM becomes a 3998-count DMM, and $\text{Log}_{10} 3998 = 3.6$ digits.

This is all delightfully confusing and of little interest until you attempt to measure a 15-volt supply with some accuracy and find that the reading is 15.0 on one DMM when it could be 15.00 on another DMM, the latter instrument having better accuracy.

The solution to the "number-of-digits" enigma is to look only at the total number of counts, or the overrange specification.

In a 3-digit DMM, 1000 counts is full scale and any count above that figure is considered to be overrange.

	Maximum reading	Overrange
3 digits	1000	0
3½ digits	1999	100%
3¾ digits	2999	200%

While the labels are not necessarily exact, the total maximum reading will always give the true resolution—the ability to detect a small incremental change in a signal. If a 3½-digit DMM displays 0 to 1999 counts, the resolution (one count) represents one part in 2000, or .05%.

Sensitivity is the quantity measured by the least-significant digit on the lowest

range. If the full-scale reading on the most sensitive range is 199.9 mV, the sensitivity is .1 mV, or 100 μ V. Similarly, if the lowest ohms range is 19.99 ohms, the sensitivity is .01 ohms, or 10 milliohms.

There are many cases where accuracy is not a prime consideration, but in those special instances where it is, it is useful to know the difference between full-scale accuracy and one-tenth-scale accuracy. Even a specification as fundamentally important as accuracy can be ambiguous. Here are two examples:

DMM (A)—Accuracy = 0.1% + 0.1% range

DMM (B)—Accuracy = 0.1% reading + 1 count

For a 1000-count DMM, both specifications are identical, but assume both are 2000-count instruments, and look at the error for a 15.0-volt input on the 200-volt range:

DMM (A)—Error = 150 counts \times 0.1% + 2000 counts \times 0.1%

$$= 0.15 \text{ counts} + 2 \text{ counts}$$

$$= 2.15 \text{ counts}$$

$$= 0.215 \text{ volt}$$

DMM (B)—Error = 150 \times 0.1% + 1 count

$$= 150 \times 0.1\% + 1 \text{ count}$$

$$= 0.115 \text{ volt}$$

Expressed as a percent of reading, which is the true measure of accuracy for any input, the errors are:

$$\text{DMM (A)—\% error} = \frac{0.215 \text{ volts}}{15.0 \text{ volts}}$$

$$= 1.43\% \text{ of reading}$$

$$\text{DMM (B)—\% error} = \frac{.115 \text{ volts}}{15.0 \text{ volts}}$$

$$= 0.77\% \text{ of reading}$$

Clearly, the percent-of-range error has a drastic effect upon the accuracy of a low-level measurement. Conversely, for best accuracy, the DMM range switch should be set to display the maximum number of counts. In the worst case shown above, DMM (A), which netted a 1.43%-of-reading error, assume the DMM is set to a lower range, from 200 volts to 20 volts.

$$\text{Range} = 20 \text{ volts}$$

$$\text{Reading} = 15.00 \text{ volts} = 1500 \text{ counts}$$

$$\text{Error} = 1500 \times 0.1\% + 2000 \times 0.1\%$$

$$= 1.5 + 2 = 3.5 \text{ counts} =$$

$$.035 \text{ volt}$$

As a percent of reading, this becomes:

$$\% \text{ reading error} = \frac{.035 \text{ volt}}{15.00 \text{ volts}}$$

$$= 0.233\%$$

This percent-of-reading error is a considerable improvement over 1.43%. It is interesting to note that the most accurate reading that can ever be made by either DMM (A) or DMM (B) is 0.2% of reading. At any voltage below full scale, the

effective accuracy decreases. This is particularly true for AC voltage measurements. The most common AC converters use either logging amplifiers or diode switches; both techniques exhibit poor performance near zero. Again, the most accurate measurements are made at full scale.

Features

Once decisions regarding resolution, sensitivity and basic accuracy were made, George Tinkerer was faced with a new set

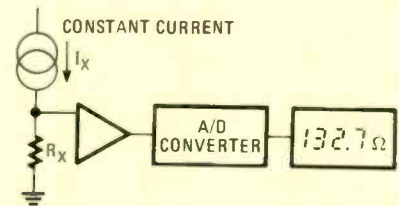


FIG. 1—OHMS CONVERTER consists of constant current source feeding the unknown resistor.

of choices labeled "convenience factors." He went over the list and checked off "current," "autoranging," "battery power" and "LCD." George mistakenly thought that "LCD" stood for "liquid crystal display" when, in fact, it meant "lizard crossing detector." (This option proved to be of marginal value to George who was a strict vegetarian!)

Preposterous? Yes, but some features appear better on paper than they do on the bench. Autoranging is an example. Some DMM's incorporate a switchable $\times 1$ or $\times 10$ amplifier that allows autoranging on only two ranges. This reduces the number of manual range-switch positions, but it does not offer full autorange capability.

Full autoranging almost guarantees input protection. Some manually ranged DMM's offer limited overvoltage protection on the lower voltage ranges, but an autoranged instrument, by the very nature of the design, must accept the full input voltage (for instance, 1000 volts) on the lowest range.

Fully autoranged current function, with a separate shunt for each range, is rarely found in low-cost instruments. The high currents, low-voltage drops and low-leakage currents do not lend themselves to inexpensive solid-state switching. For this reason, some DMM designs autorange all functions except current. Those that do autorange current usually use a 1-ohm or a 1000-ohm resistor across the input. Reading voltage on the 100-mV and 1-volt ranges then allows two ranges of current with voltage drops of 100 mV and 1 volt, respectively.

The ohms conversion offers more opportunity for confusion. The ohms converter is the circuit (see Fig. 1) that supplies a constant current to an unknown resistor. Its output is a voltage that is measured by the A/D converter and displayed as an ohms reading.

In an analog meter, the current source does not have to be constant because any arbitrary linearity function can be displayed by simply changing the markings on the meter scale. However, a DMM uses a linear A/D converter, so the current must be constant.

Sometimes an ohms converter will be specified as having a "5-volt maximum output." This does not mean that the ohms converter can send 5 volts across a low impedance. On the contrary, it simply means that the current-source output is limited to 5 volts. In no case will the current source supply more than its listed current on any given range.

The somewhat arbitrary 5-volt maximum specification was actually instituted when DMM's were manufactured for the armed forces. Because most active devices are damaged by current and not by voltage, the most important specification to consider is not the maximum output voltage, but the maximum output current that the ohmmeter can supply.

Display

When George checked off LCD on the data sheet, he really wanted a liquid crystal display. He was probably interested in long battery life. Liquid crystals offer exceptionally low current drain, and they can be manufactured with any number of different display characters. Some LCD's are very slow at cold temperatures, sometimes taking as long as half a second to change states completely, and certain other types encounter reliability problems in humidity at elevated temperatures. Since LCD's are slow, they are hard to multiplex, so the number of interconnections becomes quite high. They must be back-lighted to be seen in a dark room and certain types suffer from a narrow viewing angle.

Light-emitting diode displays (LED's) are fast enough to multiplex, and they offer more consistent temperature performance than liquid crystals. The LED is difficult to read in very bright sunlight, while the LCD is not. The LED is fast, but it also consumes more power. In order to reduce power requirements, LED's are sometimes made smaller and placed behind a lens, but this also restricts the viewing angle. LED displays are manufactured in predetermined sizes and shapes, and do not offer the display-character flexibility afforded LCD's. However, LED's are reliable under adverse environmental conditions.

In addition to obtaining accurate readings, George is also concerned with interpreting those readings. He wants full annunciation to lessen possible error. If an instrument is properly annunciated, the user should be able to glance at the display and know immediately that he has chosen the correct function and range, and that he has committed no error setting up the front-panel controls. A reading that exceeds the full-scale range

input should be displayed so distinctively that it cannot be interpreted as a valid reading. Smoke pouring from the front panel is generally considered an unsporting way of indicating overload.



TYPICAL LED DISPLAY is easier to read than LCD display but it consumes more power.

Service

The day is bleak . . . the wind is cold . . . the sky is overcast. George is overcast. He steps off the bus and pulls his collar high to fend off the freezing rain. Under his left arm, he carries the decimated remains of his DMM. Every slippery footstep on the rain-slicked sidewalk brings him closer to the Whoopee-tronics service center. He recalls the embarrassment of that infamous day when his DMM failed him. In his mind's eye, he can envision the Whoopee-tronics showroom full of ex-used car salesmen in checkered sport coats and polka-dot ties with big toothy grins that seem to say, "hello, sucker."

By the time he reaches his destination, George is livid. White knuckles squeeze the doorknob into submission as his wet shoes soil the polished tile floor. His temples start to pound and his already crimson neck starts turning purple as he approaches the service desk.

"Hi, pops. You look like a drowned rat." After making the remark, the service technician notices blue flames emanating from George's nostrils and decides to back off. Finally, George speaks.

"You turkeys sold me this blankety-blank instrument and it blew up, and I want to know what you're going to do about it!" The technician manages a weak smile as he extracts the DMM from George's midsection.

"Hmmm, looks like the ohms converter. I can tell because there's a little puddle of metal where the protection transistor used to be. Heh, heh." The levity goes unanswered. "Well, let's just try a new input module." As he applies power, the DMM returns like a phoenix to the living world. "Now, I'll calibrate it for you." The technician adjusts the controls, returning the instrument to its original condition. George is impressed, but still defensive.

"O.K., what's this gonna cost me?"

"Oh, nothing. We've corrected a design flaw in our ohms protection circuit, and we now list an ohms overload specifi-

cation in our data sheet. I'm glad you bought our DMM instead of an analog meter. An ordinary analog meter needle would have wound around like a pig's tail and it would have been cheaper to replace the whole instrument than to pay for the repair. Imagine how many pointers you could corkscrew around the stop in, say, five years. At \$70 apiece, you could easily justify buying a dandy self-protected, accurate autoranging DMM. Of course, we can't promise ours will never fail, but we are doing everything possible to make ours dependable. In any case, please try to be more careful in the future."

George feels like the guy who was under the bleachers ordering a hot dog when Hank Aaron hit his 714th homer. He came prepared for a fist fight and couldn't find an opponent. Suddenly, his opinion of Whoopee-tronics is reversed. He starts thinking about why the service is so good. He notices the quiet efficiency of the service center and recalls the service technician's skill. George realizes that the technician hardly looked at the manual when he calibrated the DMM because the order of adjustments and their relationship to each function had been clearly marked on a piece of sheet metal inside the DMM. The workmanship was excellent, and a drawing of the PC board in the manual allowed instantaneous component location. The manual contained detailed schematics and troubleshooting aids.

George is impressed with the service he obtained and appreciates the time and effort that go into making a product serviceable, but he wonders now how dependable his DMM will be in the future. He asks the service technician what steps Whoopee-tronics takes to guarantee reliability.

The technician first explains that George's mishap will be less likely to occur in the future due to some new abuse tests recently implemented by Whoopee-tronics. He proudly recites the company viewpoint on dependability:

Dependability

"Dependability is the characteristic that separates the quality instrument from the average instrument. It is a direct measure of design forethought.

"Even the most knowledgeable user will err at times in his application and unintentionally subject his multimeter to adverse conditions. A properly designed multimeter would have survived your debut into the rewarding world of electronics without so much as a whimper.

"There are some unavoidable adverse conditions, such as physical and electrical environments. Most 'expensive' multimeters undergo a strenuous series of environmental tests before designs are finalized, and the designs are often changed as a direct result of these tests.

"The more common environmental tests include operating temperatures like

-20°C and +55°C, 95% relative humidity (rain is 100%), shock and vibration tests to determine mechanical integrity, and operation in strong electrostatic and electromagnetic fields. Although these representative tests are difficult, they are by no means new, and they do not take into account the most difficult environment of all—your workshop and workbench.

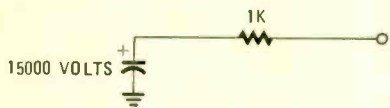


FIG. 2—STATIC DISCHARGE from the human body can be represented by this equivalent circuit.

"An entirely new set of tests has been devised to counteract the possible mishandling of a DMM. Every possible misuse of the product is simulated. Instruments are subjected to a current-limited static discharge of 15,000 volts to any exposed terminal. Voltages of over twice the input rating are applied to the input terminals, and extremely high currents are applied to ampere terminals to check for safety and fire hazards. A 230-volt supply is applied to the 115-volt line input as well as to the ohms input to see that no damage occurs. High voltage is applied to the input while selecting every conceivable combination of pushbutton or rotary-switch positions to insure that turning on a switch between positions or pushing buttons in illegal combinations will not cause damage to the instrument or to your circuit.

"High voltages are applied between circuit low and safety ground to check the transformer and all mechanical spacings for dielectric strength. If you wonder why we subject the voltmeter to inputs as extreme as 15,000 volts, this voltage simulates the static discharge from a human body.

Static discharge

"When MOS (Metal Oxide Semiconductor) devices first became available, it was found that they had a high failure rate with respect to other semiconductor technologies. Some clever detective work revealed that the failures were due to static discharge. Since the FET gates had extremely low leakage currents, they could accumulate charge to the point that internal breakdown occurred, destroying the device. Vast improvements have since been made in MOS circuit protection, but these devices are still susceptible to static discharge.

"Contrary to popular belief, MOS integrated circuits are not the only semiconductors that are susceptible. Junction FET's and even bipolar transistors are frequent victims of this phenomenon. This is especially true in voltmeter input circuitry. In order to provide good common mode rejection and minimum voltage drift with changing temperature,

DMM manufacturers use differential transistors in input amplifiers. Temperature tracking dictates a small junction area, which makes the device vulnerable to static discharge destruction.

"If you've ever lived in a dry climate, I'm sure you've experienced walking across a carpet and drawing an arc to the nearest grounded object. The potential static discharge from your body can reach 15,000 volts under such conditions. Many electrical models have been used to simulate the human body during static discharge. For example, here's one widely accepted model."

The technician draws the schematic shown in Fig. 2 for George.

"Theoretically, 15 amperes of instantaneous short-circuit current can be supplied by this circuit."

George breaks in: "Fifteen amperes? Hogwash! Why, you would die every time you touched a doorknob!"

"Certainly, 15 amperes of continuous current passing through your heart would cause instant fibrillation. However, the current is not continuous and it doesn't pass through your heart.

"The charge is stored on your body's surface and is discharged over that surface. The only place that the charge penetrates the skin to any extent is at the point of contact with the grounded object, where the increased current density causes pain. Since the time constant of the equivalent circuit is only 300 ns, the energy released is relatively small, but it is enough to damage a semiconductor.

"The design engineer must create an input amplifier that measures microvolts but not be damaged by tens of kilovolts. One method of controlling static is to intentionally design spark gaps around the input circuitry.

"A spark gap can be formed by the jagged ends of two hookup wires or by the blades of a switch wafer. A needle gap arcs at a voltage that is about one-tenth that of two equally spaced smooth surfaces. Because of the physical variations in designing spark gaps and the unpredictability of static discharge, circuit layouts must nearly always be modified empirically. In the early stages of designing to avoid static damage, this 'lightning bolt test' may destroy a large section of input circuitry. Troubleshooting and replacing the zapped circuit can involve considerable time and effort."

"Gosh," George comments. "I didn't know a static discharge could cause so much damage. But what about my multimeter? Why did it blow up?"


The technician casts a suspicious eye at George. "You probably applied the line voltage directly to the ohms terminals."

George's sheepish grin gives him away. "Yeah, I guess I wasn't very careful," he confesses.

The technician pats him reassuringly on the shoulder. "I wouldn't be too ashamed. All of us have done it at one

time or another. That's exactly what we try to avoid with our new testing program. Our new ohms converter can take the full-line voltage without being destroyed.

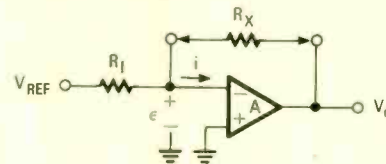"Let me show you a simple ohms converter." The technician draws the circuit shown in Fig. 3.



LET R_X REPRESENT THE UNKNOWN RESISTOR, AND R_I REPRESENT THE RANGE RESISTOR INSIDE THE DMM. FOR AN IDEAL OPERATIONAL AMPLIFIER,

$$i = 0$$

$$A = \infty$$

$$\text{THEN } \frac{V_{REF} - e}{R_I} = \frac{e - V_O}{R_X}$$

$$\text{BUT } e = \frac{V_O}{A} = \frac{V_O}{\infty} = 0$$

$$\text{SO } V_O = V_{REF} \left(\frac{-R_X}{R_I} \right)$$

FIG. 3—SIMPLE OHMS CONVERTER provides output voltage proportional to unknown resistance.

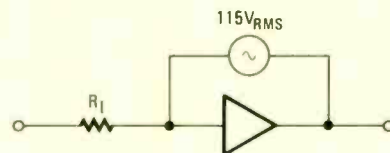


FIG. 4—APPLYING LINE VOLTAGE to input terminals of circuit in Fig. 3 will destroy amplifier.

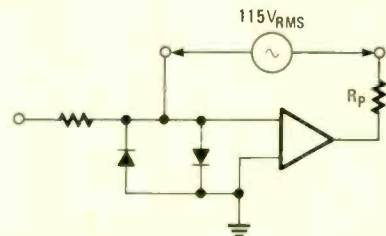


FIG. 5—DIODES PROTECT ohms converter circuit against application of line voltage.

"The voltage is proportional to the unknown resistor. Now, assume you apply 115 volts RMS across the ohms terminals. The circuit looks like this." (See Fig. 4.)

"An ordinary operational amplifier would be reduced to cinders, therefore, some protection circuitry is added." (See Fig. 5.)

"Resistor R_P protects the op-amp to some extent. However, R_P itself now becomes subject to burnout. The value of R_P must be small enough to allow the op-amp to supply high current on the lowest resistance range, but this small value means it will dissipate a lot of power if 115 volts AC is accidentally applied to the ohms input. High power usually means a metal-film resistor should be used, but in this case a carbon-composition resistor would probably perform

continued on page 118

Make Your Own CUSTOM HARDWARE

These days, it appears that the active electronics experimenter needs a greater variety of hardware just as sources seem to be drying up. Why not make the hardware you can't find or afford?

JAMES E. TEMPLE

LIKE MOST READERS OF RADIO-ELECTRONICS, I WANT TO build 50% of all construction projects described in each issue, within their specifications and with "hardware to suit." But, to suit what? Certainly not my pocket book. If I buy a minimum quantity, I have to pay a king's ransom to complete the project; if I purchase the standard quantities all that extra hardware sits in my parts boxes. Ah, then the idea lamp lights up: I'll modify the hardware to suit special purposes. So I'd like to share my experiences on how I successfully modify specialty hardware and make it twice as versatile.

Some necessary tools

The Dremel Motor tool and its many accessories is very versatile. The 1-inch-diameter cutoff wheel with its mandrel holder is a fantastic item. The wheel is no more than a $\frac{1}{16}$ -inch thick, made of a carbide material and a powerful cutter. It is somewhat brittle, especially with any side pressure. Yet it will cut through stainless steel as if it were butter. When it comes to cutting epoxy boards, the cutoff wheel again acts very smoothly. I am impressed with how quickly it cuts, and I try to grind each wheel down to the smallest possible size without breaking the disc. Wear safety glasses as a precaution. Since the tool travels at 24,000 rpm, a breaking disc can send particles all over the place, especially toward your face and eyes.

Jewelers' files also come in handy, as well as a miniature anvil along with a small vacuum vise, emery cloth, pliers, cutters, and any other time-saving tool.

Star No. one

(I refer to any item that cuts down on time and expense as a "star," and feel perhaps you might agree.) The miniature tubular terminal, *model 1236* by Keystone Electronics Corporation, 49 Bleeker St., New York, NY, is able to hold securely wires from 0.010 to 0.050 in diameter, discrete components that can be inserted from either side of the terminal. They mount in a $\frac{1}{16}$ -inch hole (0.062 to 0.067) with a special insertion tool for hand usage. The terminal comes in quantities of 100 and 1000 and is ideal for both printed circuits, rats'-nest-type of building and even Wire-Wrap setups. Figure 1 shows how it would normally be used when inserted into a board.

To modify this little gem, drill the hole and insert the terminal with the tool. Figure 2 shows what happens when you

cut it flush with the board, with the cutoff disc. The dotted lines indicate the material removed by cutting. There is no excessive material above the board and the top section has been hammered tightly down to the board (use a light tack hammer). The burrs have been cleaned out with a round jewelers' file, so the miniature tubing has been made even smaller.

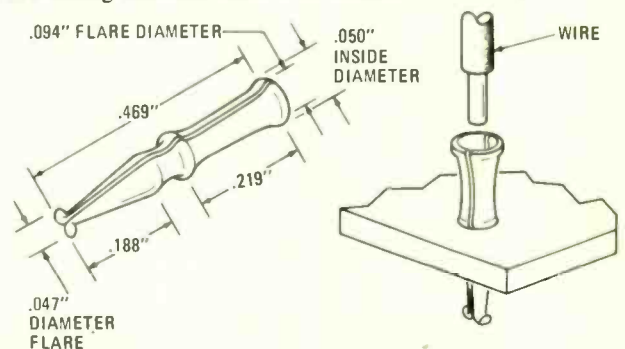


FIG. 1—MINIATURE TUBULAR TERMINAL fits snugly into $\frac{1}{16}$ -inch hole and can be used for component or wire connection.

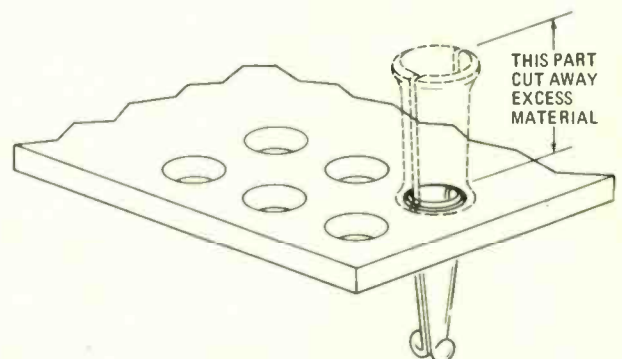


FIG. 2—HOW FLUSH-MOUNT SOCKET CAN BE MADE by removing the top part of a miniature tubular terminal and peening over.

What do you use this type of modified hardware for? Have you ever purchased large-size 0.0800 seven-segment LED's for a project, spent a small fortune for each, and just did not relish the idea of soldering them directly to boards or felt that socket mounting just did not fit the project? Well, next time try these tubular terminals, cut flush and matched up to the display leads;

each display is held firmly as if in a socket. With leads A to G, you can now use a minimum number of displays mounted without soldering to avoid possible damage. You can even remove them quite freely to use in another circuit without too much trouble.

Another use for this terminal (cut flush again) is to mount individual LED's without soldering the LED's directly to the board. You will need Vector's T-46 push-in pins, which are crimped to hold securely to the boards and sold in packs of 50. This pin has a rounded head, a crimped flange and fits a 0.042 drill hole. Remember the special tool to insert the tubular terminals? When you mount it in a vise upside down, it becomes a miniature setting tool supporting the PC board around the drill hole that will have a pin inserted into it. Merely place the board over the tool, line up the hole, insert the pin and, using a light hammer, hammer it home securely. Solder the round head to the circuit on either side to be sure of circuit continuity. Soldering is an easy way to set these pins. You can also try pushing the pins into the board holes with a pair of pliers. But the pins bend too easily this way.

With this type of LED mounting use the LED lens produced by James Electronics of 1021 Howard Ave., San Carlos, CA. This lens holds the LED securely, and the LED leads can be tied into the circuits. The holder fits a 1/4-inch hole, and does indeed hold the LED snugly. However, the LED leads must still be soldered to the circuit in which it will be used. Now we have the three parts that can be combined to make a neat and easily dismantled unit: the LED lens and holder, the Vector pins and the miniterminals.

Figure 3 shows a 1-inch long by 3/8-inch wide LED mounting

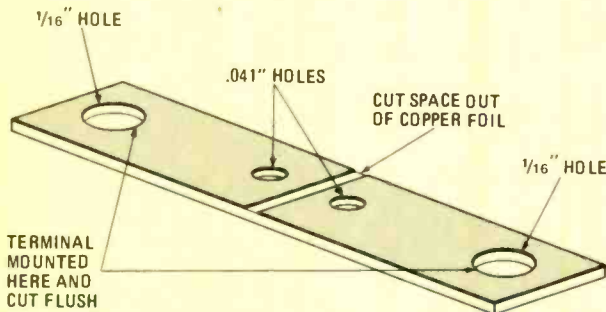


FIG. 3—LED MOUNTING STRIP made from a small piece of single-sided printed-circuit board. Mini-terminals fit the outer holes.

board made of copper foil. At the outermost points of the strip, drill two 1/16-inch holes, one on each end. In the direct center, drill two 0.041 holes spaced 0.100 apart. In between the holes, cut the copper foil in the center to make upper and lower sections that are electrically isolated from each other. Mount the miniterminals in the 1/16-inch holes. Use an anvil as a support to the board when you insert the terminals and push them all the way in. Cut off the excess tubing except for at least 1/16 of an inch, which can be spread apart with a nail and hammered flush with a tack hammer. Clean the holes for burrs with a jeweler's file and insert a wide needle to be sure the holes are open all the way. Where you want to mount a discrete LED, take the pattern strip and mark the centers of the 1/16-inch holes where the minitubes are. On the printed circuit board drill a 0.042 hole. At the dead center of these two holes, mark the board and drill a 1/4-inch hole (see Fig. 4). Leave room for the current-dropping resistor for the LED in the vicinity of the 0.042 holes, and be sure of the polarity of the line the resistor connects to; positive or negative. You can even install this resistor on the strip, but this will require an additional 1/4-inch length to accommodate it.

The Vector pins are placed into the 0.042 holes facing the same direction as the LED lens. Solder these pins on either the head side or the shaft side, or both sides, making the pin a part of the circuit. You even have enough space to wire-wrap and jump to another part of the circuit board, but it is best to keep the wrapping to only five turns. Mount the LED lens in the 1/4-inch hole, push the LED into the lens until it clicks into place;

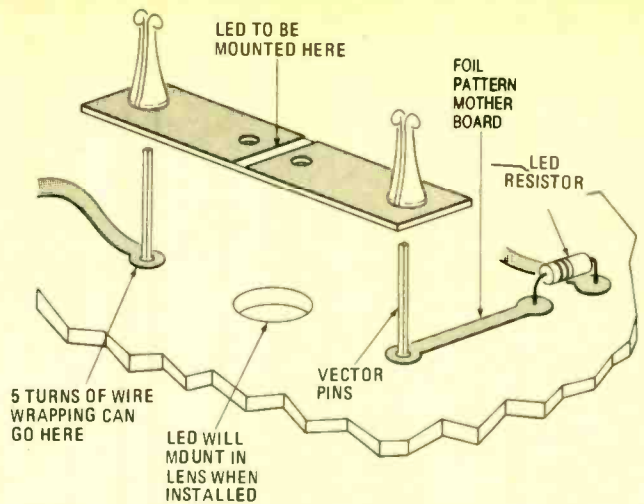


FIG. 4—HOW LED MOUNTING STRIP forms a plug-in connector when mated to suitable pins inserted into the PC board.

pass the LED leads through the holes in the mounting strip, making sure of the lead polarity; and push the strip down over the leads and the Vector pins until the strip fits snugly. To finish off, solder the LED leads to the mounting strip, and cut off the excess leads. You now have a removable LED from the lens that makes contact with the board circuit yet can be quickly replaced by another strip with a mounted LED of another color, a brighter output, etc. This system also lets you mount the LED lens on a front panel, not directly on the printed circuit board. Drill a 3/8-inch hole in the PC board behind the front panel. The lens will then pass through the PC board, and by using the LED

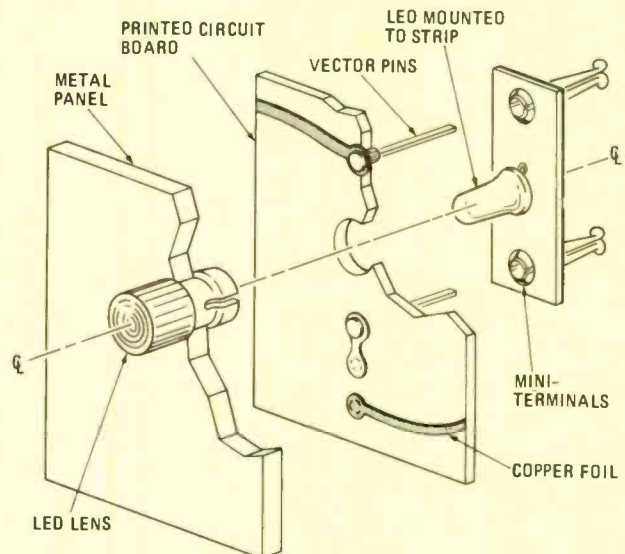


FIG. 5—LED LENS ON THE FRONT PANEL mates with the PC board and the LED on its mounting strip.

strips you can easily mount the removable LED's in the lens and show color through to the front panel. A front panel can now be serviced easily in case of trouble. Figure 5 shows the assembly.

Star No. two:

The No. K32 J-pin, marketed by Vector, is a perfect square wire used for wire-wrap connections or soldering into a printed circuit. It provides two points of contact, can be cut flush, bent at right angles, left as-is, can mount IC packages as if it were a socket, etc. (see Fig. 6).

To mount IC's directly without a socket, place J-pins one to each lead, and pass them through the mounting holes in the board; the pins will fit tightly against an IC lead in a 0.042 hole. The J-pin can face in either direction when it is installed next to the lead either up or down, depending where the lead will do the

most good for the circuit. Using the J-pin as a socket, you can remove the IC and place it back into the circuit if necessary.

A J-pin is used for terminal or tie points, in wire-wrap or PC systems and even in a rats' nest setup. This pin can be modified to take the place of many other hardware items, thereby saving money.

If you want a special IC socket, do the following: Take some Molex *Soldercon* IC pin connectors (another "star") and some J-pins; together they can be made into an IC socket of any pin size. Insert the Molex socket pins; push the J-pins next to the Molex lead; solder the Molex lead to the J-pin, top side and bottom; and you have a useful socket for wire-wrap circuits or

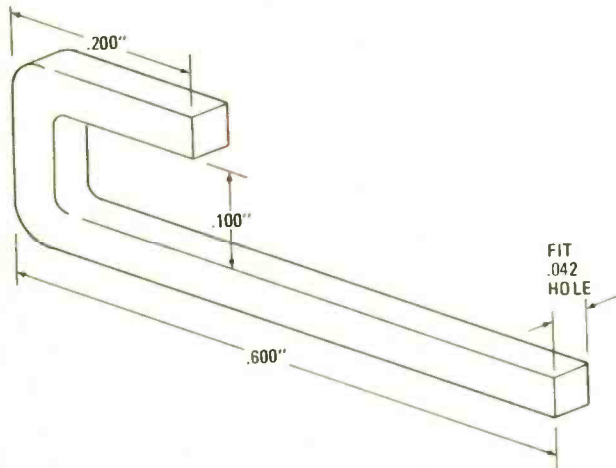


FIG. 6—THE VECTOR J-PIN is one of the more versatile of small hardware components. It's just over a half inch long.

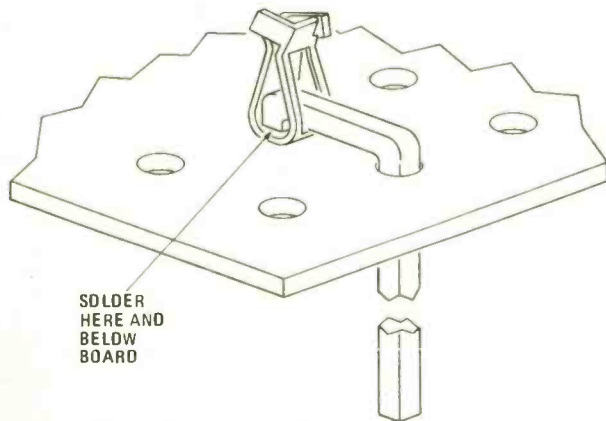


FIG. 7—HOW MOLEX SOLDERCON AND VECTOR J-PIN can be united to form one terminal of a socket for an IC.

rats' nests. Figure 7 shows J-pin and Molex *Soldercon* units used together to make a socket point. Using a miniature tubular terminal and a J-pin in pairs on a printed circuit board results in a mounting point for any discrete component. You have set up a specialty socket for wire-wrap circuits for the large seven-segment displays, which are now easily removed or replaced into the circuits.

Have you ever designed a PC board and found you needed to add several more IC's not provided for in the original layout, but you lack the room to add them directly to the board? Set some J-pins into the circuit board, trying to take off the power connections and the input or output connections of the original circuit. Try to keep the J-pin pattern as square as possible. Take a second copper board, make it match up to the square, mark off the J-pin points where they will come in contact with the second board, drill 0.042 holes, and check out the pin alignment. If it looks OK, either use these holes to mount the second board directly or set up your miniterminals to have a removable second board in case the original board needs servicing. The second PC

board will mount the needed IC's to the first circuit. Be sure to allow additional space for other possible circuits. For added security provide for some 2-56 nut-and-bolt holes to hold the two boards together securely in place. Duplex circuit boards are very neat and take little effort to produce.

Want to try a right-angle connection instead of a duplex set-up? If the original board has enough space for a second board mounted at a right angle, the J-pins can be modified to act as a push-in connector to the new board, which will have PC finger leads coming to the end of the board, similar to an edge connector (see Fig. 8.) If the original board has a blank area, you

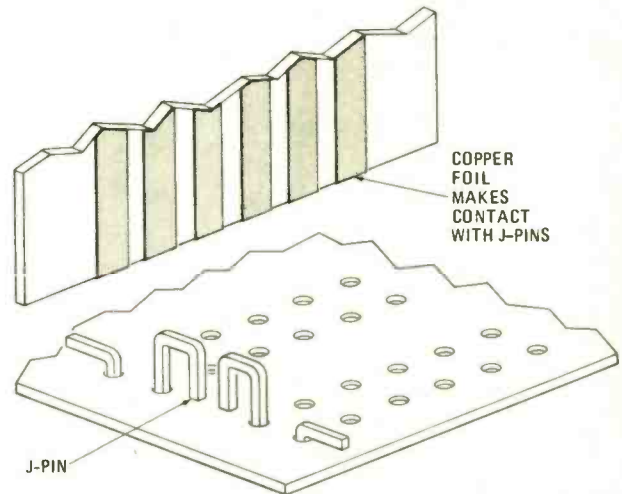


FIG. 8—HOW J-PINS CAN BE USED as edge-connector socket pins for a PC board.

can use a *Quik-Circuit* IC pattern to set up the pins. *Quik-Circuits* are copper foil, set up on a mounting strip with adhesive backing; they will stick securely to any clean portion of the board, have three holes for each contact point, and come in 36-lead strips. Note if only one IC is added to the original board, use the *Quik-Circuit* to make the connections.

If you decide to set up the right-angle second board to the first, then, using the *Quik-Circuit* pattern for the necessary number of contact points, press the pattern to the first board. Drill out three holes per lead for each lead. Place the J-pins as shown in Fig. 8; this will take up two holes. Then make the circuit connections to the third hole to the original board. You now have the edge connector for the second board match up to its outer copper leads. Also be sure to securely mount the right-angle board, using nuts and bolts. You can even twist some wire tightly to the two boards, but it will have to be cut if you have to separate the boards.

J-pins can be used as edge connectors in a motherboard setup. It is a little time-consuming to use them up in this manner, but they can save quite a bit of money. If you have time plan your next motherboard using J-pins. Then Star No. Four is a third type of edge connector you can use for these motherboard setups.

Star No. three

Figure 7 shows how the standard-size Molex *Soldercon* can be made into a wire-wrap type of connector using J-pins. Here are some other modifications you may want to try out:

Want to mount something to the end of a PC board that would require some form of right-angle connector? Merely set up the holes in the PC board, insert the Molex sockets, solder them securely to the board, and bend them to a right angle to the board. You don't have to mount them in a vertical position only. You can also use these sockets as edge connectors. Put a Molex socket on one board, and matching J-pins on the second board bent parallel with the board after soldering. The result is two boards that can be connected and taken apart from the ends without having to purchase special hardware.

Now for the best use. To add a piggyback IC, that is to mount a second IC directly to the first one, you can now mount two IC packages in the space of one by using the following method: This setup works nicely with memory IC's, since most of the leads are common to others in nature, except for the data lines or enable line if two circuits are separated. Start by drilling the IC holes for the base IC unit; then drill a second row of holes parallel to the base IC holes (see Fig. 9 for the pattern and spacing). Now


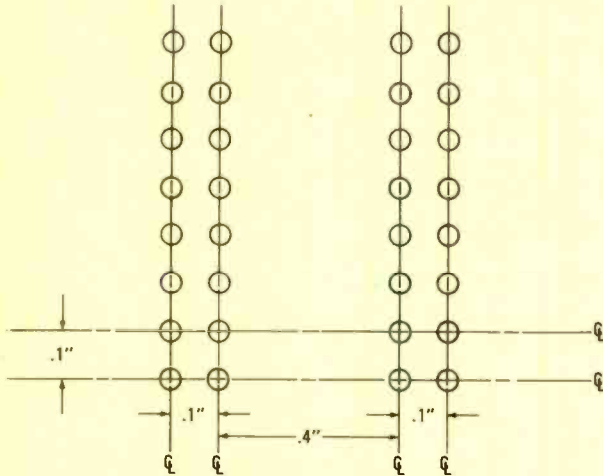


FIG. 9—THE STARTING POINT as you lay out PC board to take piggybacked dual-in-line integrated circuits.

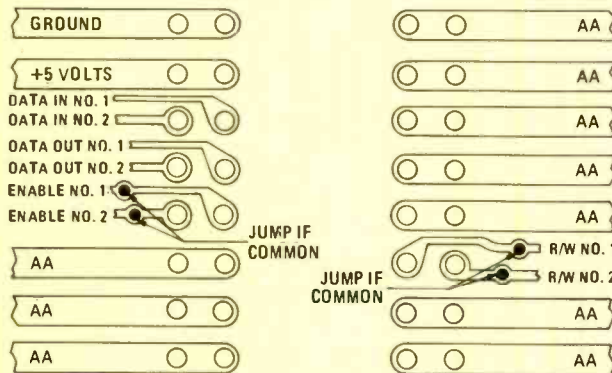set up the printed circuit pattern to accommodate the common lines, the separate input and output data lines, and others needed for the two IC's. Figure 10 shows a pattern for a 2102 duplex-mounted memory IC. After etching the circuit, mount the first memory IC by soldering directly to the board. Then take a piece



NOTE: AA = COMMON ADDRESS LINES

FIG. 10—HOW CONNECTIONS ARE MADE to the pins of piggybacked IC's. Leads can be etched or Quik Circuit types.

of masking tape cut just to the lead size and place over the outside of the uncommon leads (data or enable lines). This is done to be sure no accidental connections will be made after the next step. Then insert a row of Molex Soldercons, solder in to all points of the copper foil, and bend the row as close as possible to the mounted IC in the board. The second IC, with its leads slightly bent outward, is then inserted into the Molex connectors and pushed firmly in (see Fig. 11).

Inspect for possible uncommon-lead shorting because these leads must be kept separate from each other. Common-lead shorting is OK as the circuit does this anyway. Just be sure of those leads requiring separate data information lines. It would be a good idea to paint these particular leads on the first IC after mounting it for additional protection and lead identification.

You now have two IC packages in the space of almost one. Consider also directly soldering a third IC to the uppermost IC mounted to the Molex pins. What a space saver this can be if you are hard pressed for room. If stackable IC sockets were

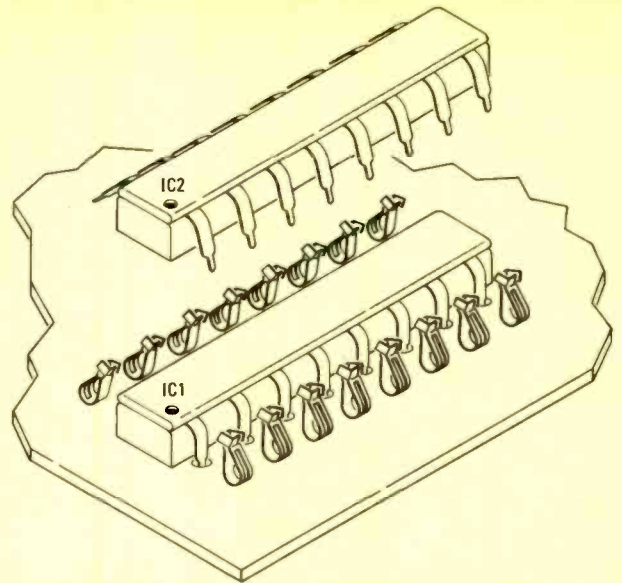


FIG. 11—HOW IC'S ARE PIGGY-BACKED. Pins on the top device are spread outward and then inserted into the Molex socket.

available you could avoid this type of modification. However, as yet they are not on the market, or if they are, a darn good secret has been kept from us "home-brew" users and builders.

Star No. four

This is a simple way to drill all those precision-spaced holes in the PC boards: Using predrilled perforated board with 0.100 X 0.100 spacing, place some double-sided Scotch-brand tape onto the perforated board section you will use as a drill guide. Press the perforated board over the PC board area, mark the drill holes, and just drill them as straight as you can directly by using the guide, the motor tool and the right drill-bit size. Remove the guide and, using blade No. 17 of an X-acto knife, you can easily remove any burrs left by drilling the board. No need to use any clamps as the sticking action of the double-sided tape holds the guide securely when you are drilling.

Star No. five

Are you tired of buying expensive edge connectors and wiring them to the motherboard to provide a backplane circuit? Here is a better way: AP Products, Box 110-Q, Painesville, OH, and Robinson-Nugent, 800 E. Eighth St., New Albany, IN, make and market male and female headers, both straight and some right-angle male headers (the female headers are not right angle). These 36-connector-wide headers can be broken into lesser sizes if needed. They match up beautifully when properly mounted in the PC boards and provide continuity of circuits from one board to another, without separate use of cable and connectors.

To use these headers to make a backplane board, use a board (made by Vero Electronics) which has 36 lines running about 18 inches long. If the Vero board is used with the female headers, two additional holes will have to be drilled for each header installed into the board. Just insert the female header and solder in place all 36 tabs, or less if all 36 lines are not used. Use as many female headers in this backplane board as needed for the circuit cards that will be made using the right-angle male header to mate with the header on the motherboard. I use this system in place of the standard 22-pin edge connectors. All I do is set up the general pattern for the motherboard, consider how many individual cards will use this board, install the headers as I go and work on my individual cards with the idea of matching up the circuits to the backplane motherboard. I also provide additional space on the motherboard for possible revisions or additions. Figure 12 shows the headers set up to the Vero board and how the individual male-header cards are to be inserted so circuits on the card and motherboard are interconnected.

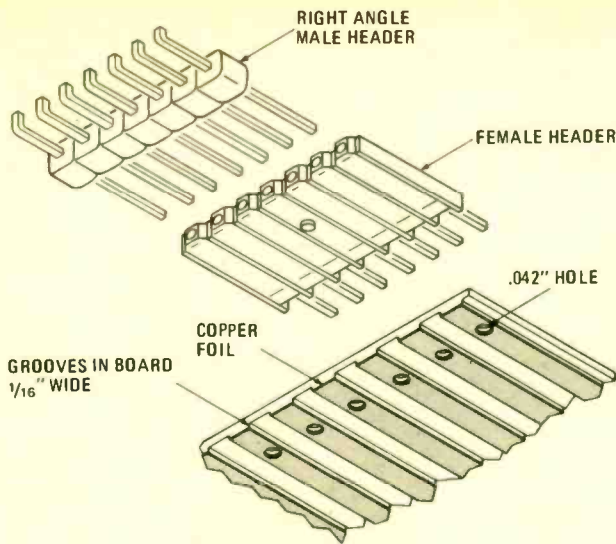


FIG. 12—HEADERS FORM CONNECTORS as auxiliary boards are plugged into the motherboard or main-frame.

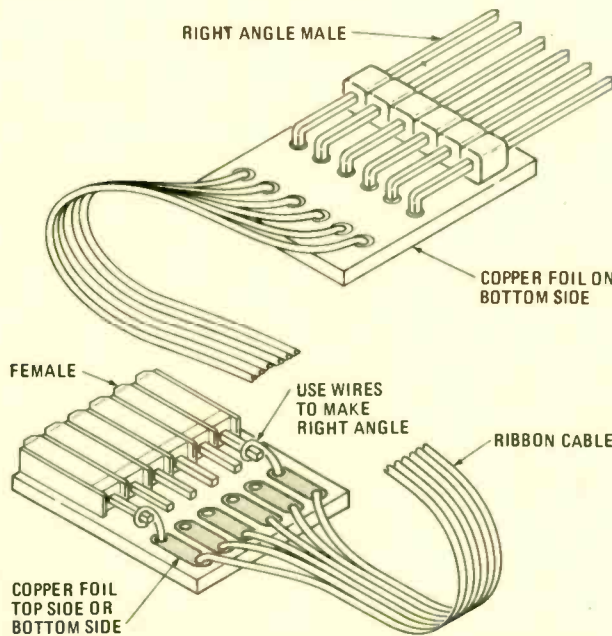


FIG. 13—RIBBON-CABLE CONNECTORS can be made from either male or female headers and small pieces of Veroboard.

Also I find I can make flat wire connectors with these headers. The female headers do require a slight modification, since they do not come with right-angle leads. Figure 13 demonstrates how to attach a female header at a right angle to a board using wires. All you need to build these cable assemblies is the Vero board (or equivalent); the necessary lines—8, 10, or up to 36; the flat ribbon cable; and male and female headers. Solder in the male or female header on one end of the strip, solder in the ribbon cable, and tape it securely; this completes one end of the cable assembly. Do the same at the opposite end of the wire cable or solder the wire directly to the circuit where it is to be attached. A matching male or female header will have to be provided in the circuit that has the cable connection attached to it. The foregoing method is an inexpensive way to use detachable cable assemblies in PC board layouts without buying special hardware. It is especially useful when you want to use cable between a main circuit board and a display panel.

Male and female headers can also be used as end board connectors, keeping in mind the right-angle modification for the females. The use for these headers is unlimited. Some readers who work with them will come up with other uses and modifications. From a simple motherboard and card connectors to cable

assembly, they can help to keep overall hardware costs down.

Star No. six

Vector's No. T-44 pins. Normal usage is to mount these pins in perforated board with a 0.042 hole, and use for mounting discrete components; the extra long lead can be wire-wrapped or soldered. Do you want to mount discrete devices to an IC socket? Consider this setup:

In the PC board install an IC socket or Molex pins. Then, take some perforated board with 0.100 × 0.100-hole spacing, cut it to fit the socket, and insert the T-44 pins where the IC leads would go. Now you can solder any device into the parallel pins, cut the T-44 pin lead to fit the socket snugly, and you have an inexpensive base to mount these discrete devices. A ready-made base for this purpose would cost a hundred times as much. Also you can modify the T-44 pin by cutting off the component mounting portion to make a T-pin (see Figs. 14 and 15). This modified T-44-pin to a T-pin can replace the Vector T-46 pin.

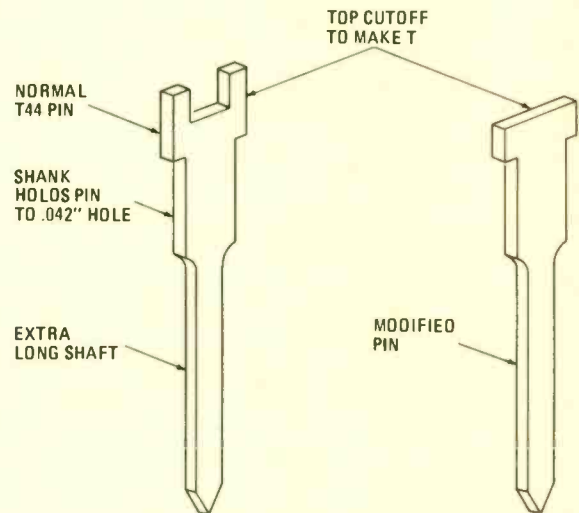


FIG. 14—MODIFIED T-44 PIN has notch section cut off forming a "T" pin substitute for the type T-46.

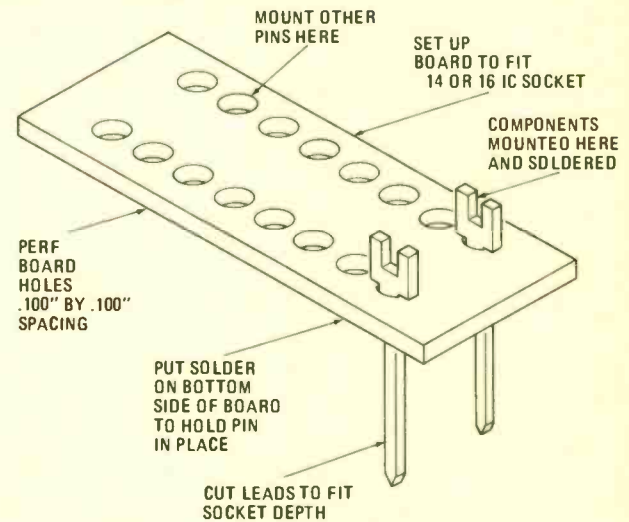


FIG. 15—VECTOR T-44 PINS AND PERFORATED BOARD can be used as a plug-in terminal strip for discrete components.

The T-section makes an excellent soldering base to hold the pin securely, and the extra long shaft length comes in handy.

A money-saving way to use IC test clips is to take the clip and carefully solder wires to each test terminal. After soldering and marking test lead No. 1, wrap up this end with electrical tape to strengthen the wire connections just made. Take a piece of perforated board, put in the T-44 pins, match up the wires to the

continued on page 121

TEST EQUIPMENT

All About Audio Oscillators

The audio oscillator of today ranges from the simplest audio source for signal tracing to the more precise and sophisticated lab-grade instruments. This story is about the latter type.

CHARLES M. GILMORE*

THE MODERN AUDIO OSCILLATOR ORIGINATED when electronic products were simple. It has since developed into a complex instrument with sophisticated specifications. The electronics world it serves has increased in sophistication so much that the original audio oscillator would no longer suffice in the areas of design, service or research.

The audio oscillator's low-distortion, low-noise signals are mainly used in the design and service of high-quality audio equipment. These are by no means the only uses. Design, service and research measurements in frequency response, attenuation, amplifier and system gain, distortion, noise and impedance are all made possible or simplified by using high-precision audio oscillators.

In the literature on the history of low-frequency signal sources, the terms "generator" and "oscillator" are used virtually interchangeably. A decade ago, these terms were truly interchangeable; generator or oscillator had little independent meaning. Today oscillator and generator indicate different technologies used to produce the fundamental signal. The term "oscillator" is applied to a circuit having a natural resonance and able to produce a pure sinusoidal signal. On the other hand, the term "generator" normally indicates some other form of electronic circuitry. For example, a constant-current source and a capacitor can be used to generate a triangle wave as the fundamental signal, and various electronic shaping networks process the triangle to produce the different waveforms.

A prime requirement for much audio work is a high-purity signal—a signal of extremely low harmonic content and low

noise. The oscillator is the logical circuit for a signal source meeting these needs.

Changes in the state of the art, especially in audio equipment, have resulted in a need for great improvements in audio oscillator specifications. Ten to fifteen years ago, the sine/square generator producing a sinusoidal signal with a 0.25% total harmonic distortion (THD) was entirely acceptable for audio equipment design and service. Today, to maintain increasingly sophisticated audio equipment, the audio oscillator must have THD specifications of less than 0.05%, and preferably less than 0.025%. This change has brought the audio oscillator to the forefront, and will soon make the sine/square generator obsolete.

Basic oscillators

Figure 1 is a block diagram of a typical audio oscillator. The major sections are: oscillator (the signal source), output amplifier and output attenuator. Occasionally, additional circuitry can be found to drive the oscillator to provide phase-locking or some form of frequency syn-

chronization. Squarewave shaping circuits are used if squarewave output is also furnished, and meeting circuits are added to some audio oscillators to display output amplitude. Of course, all these instruments have some form of electronically regulated power supply: either battery or line, depending upon the application for which the instrument was designed.

Oscillator circuits

A number of basic oscillator circuits are used to generate fundamental signals. Each has attributes that make it popular in particular situations. The Wien bridge is one of the most used audio oscillator circuits. Figure 2-a is a simplified schematic of a Wien-bridge oscillator. The twin-T oscillator (Figure 2-b) is a variation of the Wien bridge and has other derivatives known as the bridged-T oscillator (Figs. 2-c and 2-d).

The Wien bridge and the bridged-T (capacitive) are usually continuously tuned by a variable capacitor, and ranges are changed by changes in resistance. The


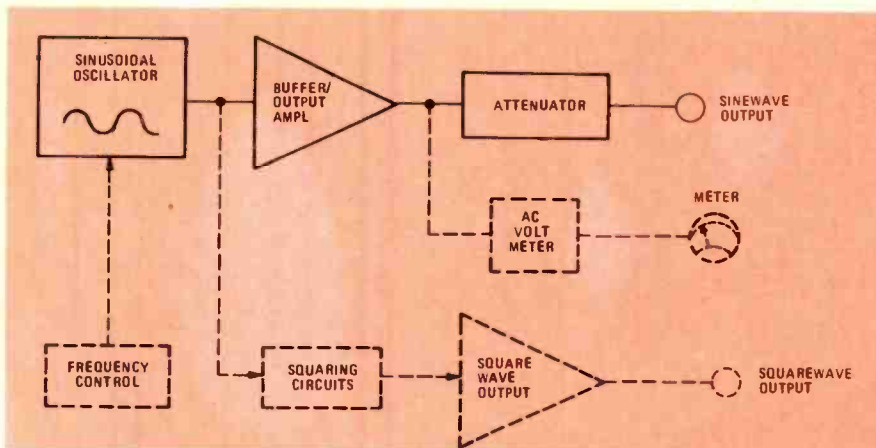


FIG. 1—BASIC AUDIO OSCILLATOR. The simplest type will include the sinusoidal wave generator, buffer amplifier and output attenuator. Other types may include meters, and squaring and electronic control circuits.

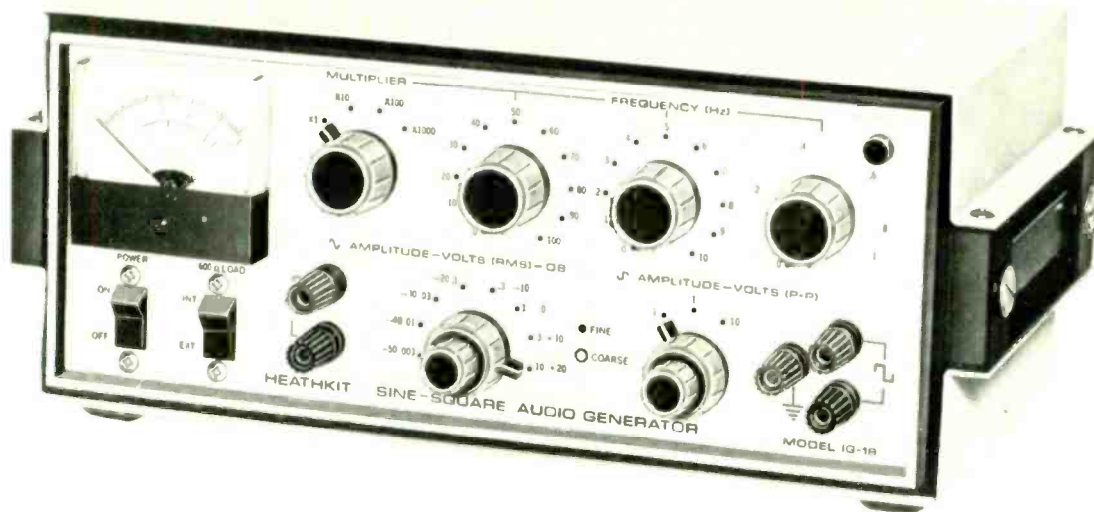* Manager, Design Engineering, Heath Co., Benton Harbor, MI.



bridged-T (resistive) is usually continuously tuned by varying one resistance (often by pushbuttons) and range-changed with fixed capacitance values. The twin-T circuit is not often used for continuously variable oscillators, since three elements must be changed to change the frequency. Such oscillator circuits typically operate over the span of a few hertz to 10 MHz.

The Wien-bridge oscillator operates when the net phase shift of the two R-C (resistance-capacitance) combinations is zero. Therefore, a two-stage amplifier that provides a 360° phase shift is neces-

sary for proper operation. Amplitude variations with changes in frequency are removed by a compensating element in one leg of the bridge. A thermistor, or more popularly, a tungsten lamp filament, is used for this amplitude compensation.

The phase-shift oscillator (Fig. 3) is another R-C circuit. Having approximately the same frequency range as the Wien-bridge oscillator series, the phase-shift oscillator derives its operation from successive 60° phase shifts at each of the R-C stages. This shift oscillator has two major disadvantages: The three R-C ele-

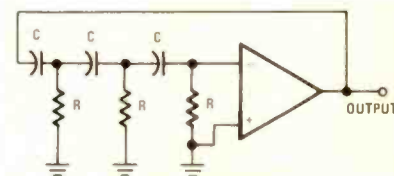


FIG. 3—PHASE-SHIFT OSCILLATOR. Each R-C section shifts the phase 60° .

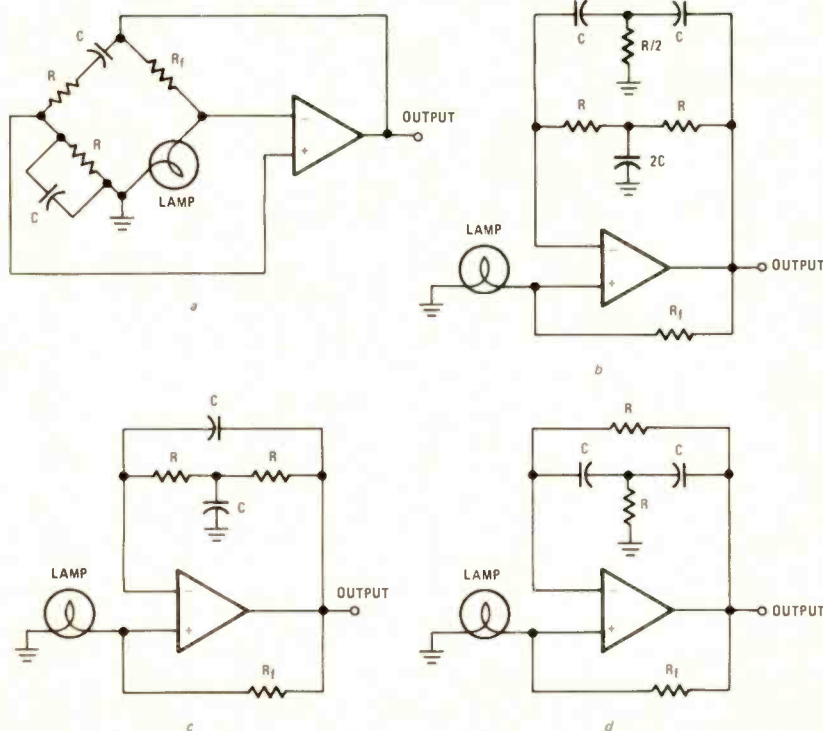


FIG. 2—COMMON AUDIO OSCILLATORS. a—Wien-bridge oscillator; b—twin-T; c—bridged-T (resistor); d—bridged-T (capacitor).

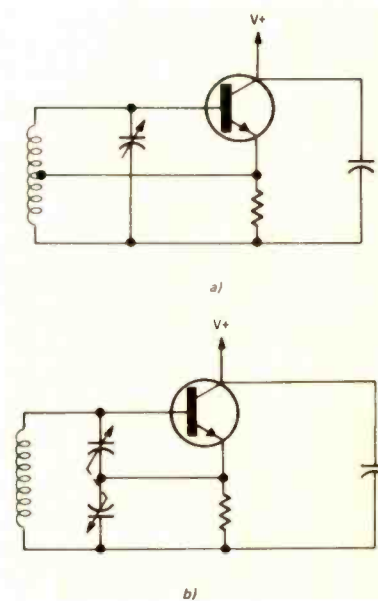


FIG. 4—COMMON L-C OSCILLATORS. a—Hartley circuit; b—Colpitts oscillator.

ments must be varied to change the frequency, and the oscillator output is amplitude-sensitive to the R-C ratio.

The frequency of both the phase-shift and Wien-bridge oscillators depends directly on the value of the capacitance. Therefore, a 10:1 change in the capacitance value produces a 10:1 change in the oscillator frequency. This characteristic of R-C oscillators makes them particularly popular.

continued on page 114

ic application of the month

XR-2208 Operational Multiplier

GENERAL DESCRIPTION

The XR-2208 operational multiplier combines a four-quadrant analog multiplier (or modulator), a high frequency buffer amplifier, and an operational amplifier in a monolithic circuit that is ideally suited for both analog computation and communications signal processing application. As shown in the functional block diagram, for maximum versatility the multiplier and operational amplifier sections are not internally connected. They can be interconnected, with a minimum number of external components, to perform arithmetic computation, such as multiplication, division, square root extraction. The operational amplifier can also function as a preamplifier for low-level input signals, or as a post detection amplifier for synchronous demodulator applications. For signal processing, the high frequency buffer amplifier output is available at pin 15. This multiplier/buffer amplifier combination extends the small signal 3-dB bandwidth to 8 MHz and the transconductance bandwidth to 100 MHz.

The XR-2208 operates over a wide range of supply voltages, $\pm 4.5V$ to $\pm 16V$. Current and voltage levels are internally regulated to provide excellent power supply rejection and temperature stability. The XR-2208 operates over a $0^{\circ}C$ to $75^{\circ}C$ temperature range. The XR-2208M is specified for operation over the military temperature range of $-55^{\circ}C$ to $+125^{\circ}C$.

FEATURES

- Maximum Versatility
 - Independent Multiplier, Op-Amp, and Buffer
- Excellent Linearity (0.3% typ.)
- Wide Bandwidth
 - 3 dB B.W. - 8 MHz typ.
 - 3° Phase Shift B.W. - 1.2 MHz typ.
 - Transconductance B.W. - 100 MHz typ.
- Simplified Offset Adjustments
- Wide Supply Voltage Range ($\pm 4.5V$ to $\pm 16V$)

ABSOLUTE MAXIMUM RATINGS


Power Dissipation	
Ceramic Package	750 mW
Derate above $+25^{\circ}C$	6 mW/ $^{\circ}C$
Plastic Package	625 mW
Derate above $+25^{\circ}C$	5.0 mW/ $^{\circ}C$

APPLICATIONS


- Analog Computation
 - Multiplication
 - Division
 - Squaring
 - Square Root
- Signal Processing
 - AM Generation
 - Frequency Doubling
 - Frequency Translation
 - Synchronous AM Detection
- Triangle-to-Sinewave Converter
- AGC Amplifier
- Phase Detector
- Phase-Locked Loop (PLL) Applications
 - Motor Speed Control
 - Precision PLL
 - Carrier Detection
 - Phase-Locked AM Demodulation

Power Supply V^{+}	+18 Volts
V^{-}	-18 Volts
Storage Temperature Range	$-65^{\circ}C$ to $+150^{\circ}C$

SIMPLIFIED SCHEMATIC DIAGRAM

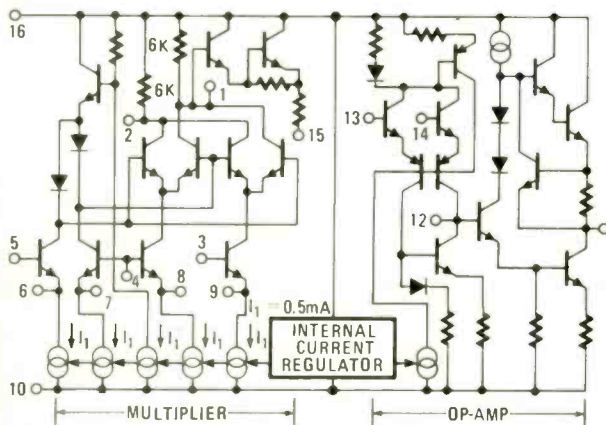

FUNCTIONAL BLOCK DIAGRAM

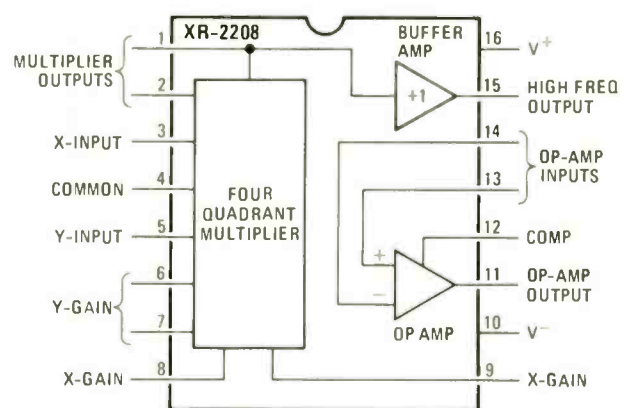

EXAR INTEGRATED SYSTEM, INC.
 750 Palomar Ave., P.O. Box 62229, Sunnyvale, CA 94088
 (408) 732-7970 TWX 910-339-9233

© EXAR INTEGRATED SYSTEMS, INC. 1976

AVAILABLE TYPES

Part Number	Package	Temperature Range
XR-2208M	Ceramic	-55°C to +125°C
XR-2208N	Ceramic	0°C to +75°C
XR-2208P	Plastic	0°C to +75°C
XR-2208CN	Ceramic	0°C to +75°C
XR-2208CP	Plastic	0°C to +75°C

DESCRIPTION OF CIRCUIT CONTROLS

MULTIPLIER INPUTS (PINS 3, 4, AND 5)

The X- and Y-inputs to the multiplier are applied to pins 3 and 5 respectively. The third input (pin 4) is common to both X- and Y-portions of the multiplier, and in most applications serves as a "reference" or ground terminal. The typical bias current at the multiplier inputs is 3 μ A for the X- and Y-inputs and 6 μ A for the "common" terminal. In circuit applications such as "synchronous AM detection" or "frequency doubling" where the same input signal is applied to both X- and Y-inputs, pin 4 can be used as the input terminal since it is common to both X- and Y-sections of the multiplier.

MULTIPLIER OUTPUTS (PINS 1 AND 2)

The differential output voltage, V_o , across these terminals is proportional to the linear product of voltages V_x and V_y applied to the inputs. V_o can be expressed as:

$$V_o \approx \left(\frac{25}{R_x R_y} \right) (V_x V_y)$$

where all voltages are in volts and the resistors are in $k\Omega$. R_x and R_y are the gain control resistors for X- and Y-sections of the multiplier.

The common-mode DC potential at the multiplier outputs is approximately 3 volts below the positive supply. One of the multiplier outputs (pin 1) is internally connected to the unity-gain buffer amplifier input for high frequency applications.

In most analog computation operations, such as multiplication, division, etc., pins 1 and 2 are DC coupled to the op-amp inputs (pins 13 and 14). The final output, V_z , is then obtained from the op-amp output at pin 11, as shown in Fig. 2.

X AND Y GAIN ADJUST (PINS 6, 7, 8, AND 9)

The gains of the X- and Y-sections of the multiplier are inversely proportional to resistors R_x and R_y connected across the respective gain terminals. The multiplier conversion gain, K_m , can be expressed as:

$$K_m \approx \frac{25}{R_x R_y} \text{ (volts)}^{-1}$$

where R_x and R_y are in $k\Omega$.

X- AND Y-OFFSET ADJUST (PINS 7 AND 8)

Two of the gain-control terminals, pins 7 and 8, are also used for adjusting X- and Y-offsets. Fig. 1 shows the typical adjustment circuitry which can be connected to these pins to null-out input offsets.

OP-AMP INPUTS (PINS 13 AND 14)

Pin 13 is the noninverting and pin 14 the inverting inputs

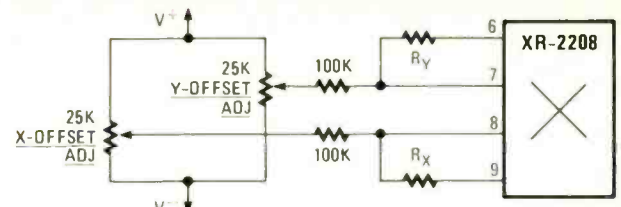


FIG. 1-OFFSET ADJUSTMENT

for the op-amp section. In most multiplier applications, these terminals are connected to the multiplier outputs (pins 1 and 2). Note: When the op-amp section is not used, these terminals should be grounded.

OP-AMP COMPENSATION (PIN 12)

The op-amp section can be compensated for unconditional stability with a 20 pF capacitor connected between pin 12 and pin 11. For op-amp voltage gains greater than unity, this compensation capacitance can be reduced to improve slew rate and small signal bandwidth.

OP-AMP OUTPUT (PIN 11)

This terminal serves as the output for the op-amp section. It is internally protected against accidental short circuit conditions, and can sink or source 10 mA of current into a resistive load. In most multiplier applications, pin 11 is the actual XR-2208 output, with the op-amp inputs being connected to the multiplier outputs.

BUFFER AMPLIFIER OUTPUT (PIN 15)

The buffer amp is internally connected to the multiplier section. The buffer amp has unity voltage gain, and provides a low-impedance output at pin 15 for the multiplier section. The buffer amp is particularly useful for high frequency operation since it minimizes the capacitive loading effects at the multiplier outputs.

The buffer amplifier is activated by connecting a load resistor, R_1 , from pin 15 to ground. When it is not used, pin 15 can be left open circuited. However, since the buffer amplifier output is a low-impedance point, reasonable care should be taken to avoid burnout due to accidental short circuits. The maximum DC current drawn from pin 15 should be limited to 10 mA. The DC voltage at pin 15 is typically 4.5 volts below V^+ .

APPLICATIONS INFORMATION

PART I: ARITHMETIC OPERATIONS

Multiplication

For most multiplication applications, the multiplier and op-amp sections are interconnected as shown in Fig. 3 to provide a single-ended analog output with a wide dynamic range. The circuit of Fig. 2 provides a linear output swing of 10V for maximum input signals of 10V, with a scale factor $K = 0.1$. The trimming procedure for the circuit is as follows:

1. Apply 0V to both inputs and adjust the output offset to 0V using the output offset control.
2. Apply 20V P-P at 50 Hz to the X-input and 0V to the Y-input. Trim the Y-offset adjust for minimum peak-to-peak output.
3. Apply 20V P-P to the Y-input and 0V to the X-input. Trim the X-offset adjust for minimum peak-to-peak output.

- Repeat step 1.
- Apply +10V to both inputs and adjust scale factor for $V_o = +10V$. This step may be repeated with different amplitudes and polarities of input voltages to optimize accuracy over the entire range of input voltages, or over any specific portion of input voltage range.

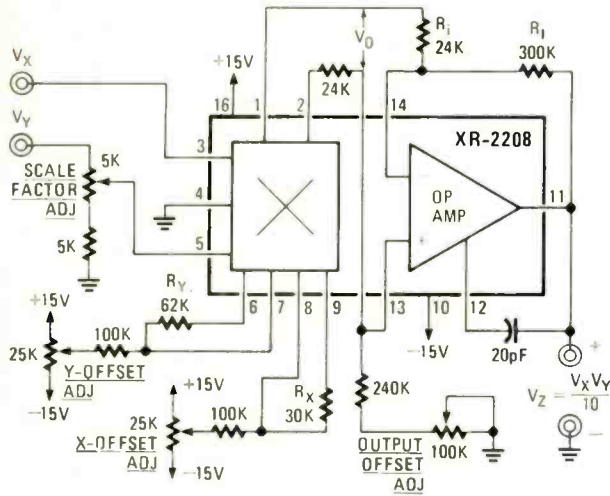


FIG. 2-MULTIPLICATION CIRCUIT

Squaring Circuit

The recommended circuit connection for squaring applications is shown in Fig. 3. This circuit is the same as the

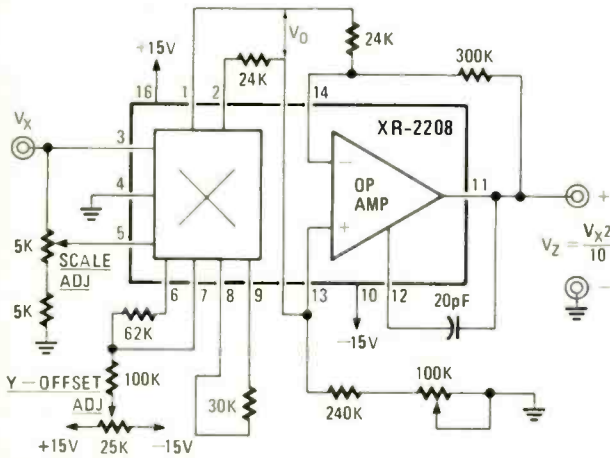


FIG. 3-SQUARING CIRCUIT

basic multiplier circuit with both inputs tied together, except only one input offset adjustment is necessary. Trimming procedure for the squaring circuit is as follows:

- Apply 0 volts to the input and adjust the output offset to zero.
- Apply 1.0V to the input and adjust the Y-offset until $V_o = 0.10V$.
- Apply 10V to the input and adjust the scale factor until $V_o = +10V$.
- Apply -10V to the input and check that $V_o = +10V$. If not, repeat steps 1 through 3. Some compromise may be necessary in scale factor adjustments given in steps 3 and 4.

Dividing Circuit

Recommended circuit connection for performing analog division is shown in Fig. 4. This circuit uses the multiplier

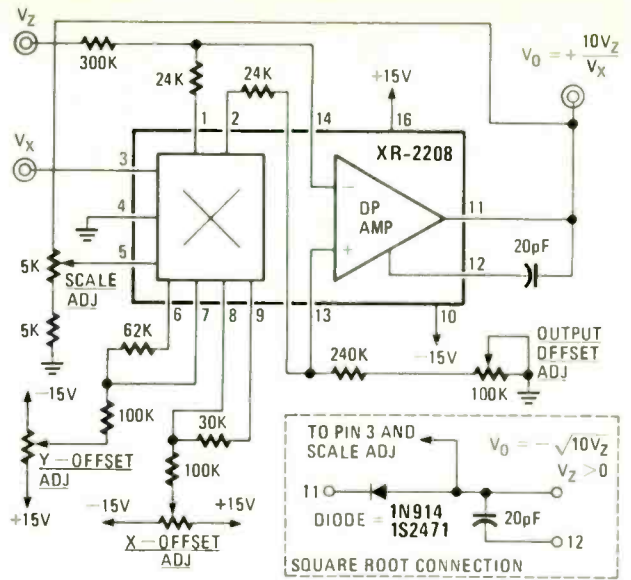


FIG. 4-DIVIDING CIRCUIT

in the feedback path of the op-amp. For the circuit shown, $V_o = +10 V_z/V_x$ where $V_x < 0$ and V_z can have either sign. Positive values of V_x are not allowed, causing positive feedback and latchup.

This latchup mode is nondestructive to the XR-2208, and is common to all analog division circuits. The divide circuit is trimmed as follows:

- Apply $V_z = 0$ and trim the output offset adjustment for constant output voltage as V_x is varied from -1V to -10V.
- Keeping $V_z = 0$, and applying $V_x = -10V$, trim the Y-offset adjust until $V_o = 0$.
- Let $V_z = V_x$ and/or $V_z = -V_x$ and trim the X-offset adjustment for constant output voltage as V_x is varied from -1V to -10V.
- Repeat steps 1 and 2 if step 3 required a large initial adjustment.
- Keeping $V_z = V_x$, adjust the scale factor trim for $V_o = -10V$ as V_x is varied from -1V to -10V.

Square Root Circuit

This is essentially the dividing circuit with the X-input tied to the output. Thus, the voltage on the Z-input is divided by the output voltage, i.e. the output is proportional to the square root of the input. A diode is included in series with the output to prevent a latchup condition which would result if V_z were allowed to go negative. The square root circuit may be trimmed as a divider by disconnecting the X-input from the output, keeping $V_z > 0$ and $V_x < 0$. The square root circuit may also be trimmed in the closed-loop mode by the following procedure:

- Apply $V_z = +0.10V$ and trim the output offset adjust for $V_o = -0.316V$.
- Apply $V_z = +0.9V$ and trim the X-offset adjust for $V_o = -3.0V$.
- Apply $V_z = +10V$ and trim the scale factor adjust for $V_o = -10V$.
- Repeat steps 1 through 3 until desired accuracy is achieved.

PART II: SIGNAL PROCESSING

AM GENERATION

Figure 5 is the recommended circuit connection for

generating double sideband (DSB) or suppressed carrier AM signals. Modulation and carrier inputs are applied to the X- and Y-inputs respectively. The carrier level at the output can be adjusted by the DC voltage applied to pin 3. For suppressed carrier operation, the carrier feedthrough can be further reduced by using the X- and Y-offset adjustments. In this application, the unity-gain buffer amplifier section will provide a low-impedance output if desired. If the buffer amp is not used, pin 15 should be open circuited to reduce power dissipation.

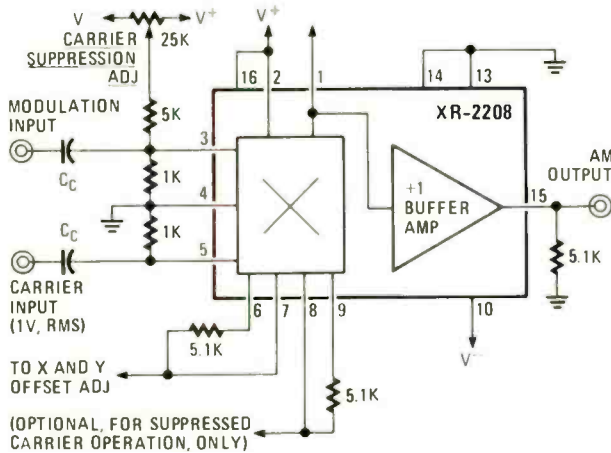


FIG. 5-AM GENERATION

Typical carrier suppression without offset adjustment is 40 dB for frequencies up to 1 MHz, and 30 dB for frequencies up to 10 MHz. For low frequency applications ($f < 10$ kHz), carrier suppression can be reduced to 60 dB by using the offset adjustment controls.

SYNCHRONOUS AM DETECTION

Figure 6 is a typical circuit connection for synchronous

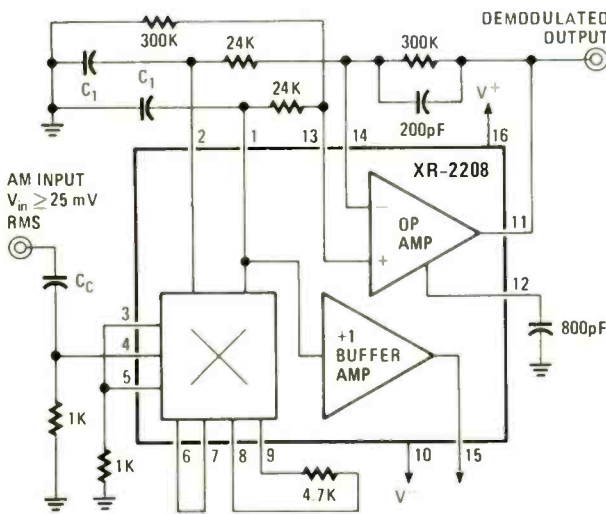


FIG. 6-SYNCHRONOUS AM DETECTOR

AM detection for carrier frequencies up to 100 MHz. The AM input signal is applied to the multiplier "common" terminal (pin 4). The Y-gain terminals are shorted, and this section of the multiplier serves as a "limiter" for input signals ≥ 50 mV RMS; the X-section of the multiplier operates in its linear mode. The low-pass filter capacitors, C_1 , at pins 1 and 2 are used to filter the carrier feedthrough. If desired, the op-amp section can be used as an audio pre-

amplifier to increase the demodulated output amplitude.

TRIANGLE-TO-SINEWAVE CONVERSION

A triangular input can be converted into a low distortion (THD $< 1\%$) sinusoidal output with the XR-2208. A recommended connection for this application is shown in Fig. 7.

The triangle input signal is applied to the X-input (pin 3). The multiplier section rounds off the peaks of this input and converts it to a low distortion sine wave. For the component values shown in Fig. 7, the recommended input signal level at pin 3 is ≈ 300 mV P-P in order to obtain a 2V P-P sine wave output at pin 15. This waveform can be further amplified using the op-amp section to provide high level (10V P-P), low distortion output at pin 11.

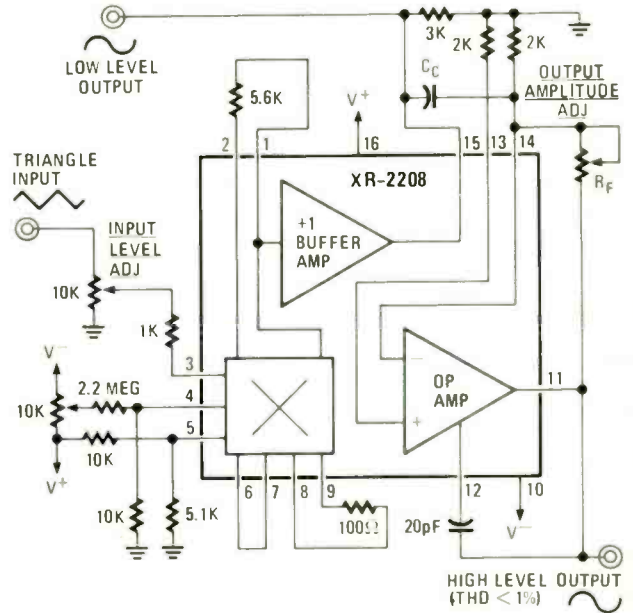


FIG. 7-TRIANGLE-TO-SINE CONVERTER

PHASE DETECTION

The multiplier section can be used as a phase detector. A recommended circuit connection is shown in Fig. 8. The

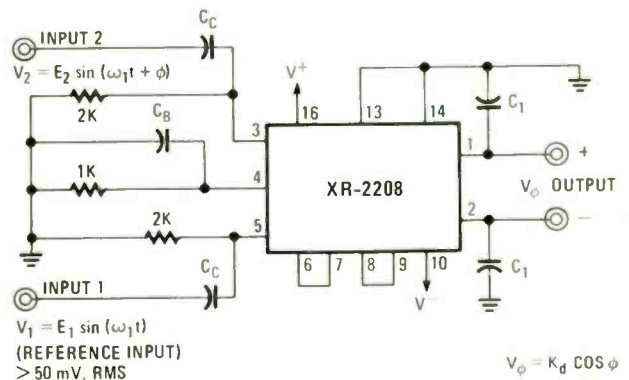


FIG. 8-PHASE-DETECTOR CIRCUIT

reference input is applied to pin 5, and the input signal whose phase is to be detected is applied to pin 3. The differential DC voltage, V_ϕ , at the multiplier outputs (pins 1 and 2) is related to the phase difference, ϕ , between the two input signals, V_1 and V_2 , as:

$$V_\phi = K_d \cos \phi$$

where K_d is the phase detector conversion gain. For input signals ≥ 50 mV RMS, K_d is $\approx 2\text{V/radian}$ and is independent of signal amplitude. For lower input amplitudes, K_d decreases linearly with the decreasing input level. The capacitors C_1 at pins 1 and 2 provide a low-pass filter with a time constant $T_1 = R_1 C_1$, where $R_1 = 6\text{ k}\Omega$ is the internal impedance level at these pins.

If needed, the phase conversion gain can be increased by using the op-amp section of the XR-2208 to further amplify the output voltage, V_ϕ . The XR-2208 operational multiplier is suitable for phase detection of input frequencies up to 100 MHz.

PART III: PHASE-LOCKED LOOP APPLICATION

MOTOR SPEED CONTROL

A motor speed control where the frequency of the motor is "phase-locked" to the input reference frequency, f_r , is shown in Fig. 9. The multiplier section of the XR-2208 is

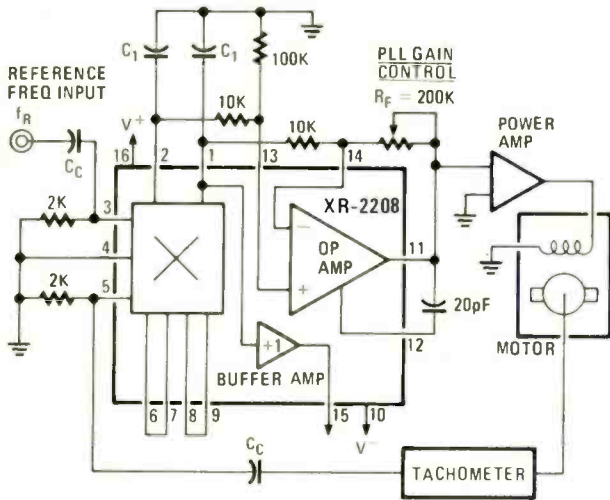


FIG. 9-MOTOR SPEED CONTROL CIRCUIT

used as a phase comparator, comparing the phase of the tachometer output signal with the phase of the reference input. The resulting error voltage across pins 1 and 2 is low-pass filtered by capacitors C_1 and amplified by the op-amp section. This error signal is then applied to the motor field-winding to phase-lock the motor speed to the input reference frequency.

PRECISION PLL

A precision phase-locked loop may be constructed using an XR-2207 voltage controlled oscillator and an XR-2208. (See Fig. 10.) Due to the excellent temperature stability and wide sweep range of the XR-2207 this PLL circuit exhibits especially good stability of center frequency and wide lock range. In this application the XR-2208 serves as a phase comparator and level shifter. Resistor R_L adjusts the loop gain of the PLL, thus varying the lock range. Tracking range may be varied from about 1.5:1 up to 12:1. For large values of R_L , temperature stability of center frequency is better than $-30\text{ ppm}/^\circ\text{C}$.

PHASE-LOCKED AM AND CARRIER DETECTION

The XR-2208 can be used as a "quadrature detector" in conjunction with monolithic PLL circuits to perform phase-

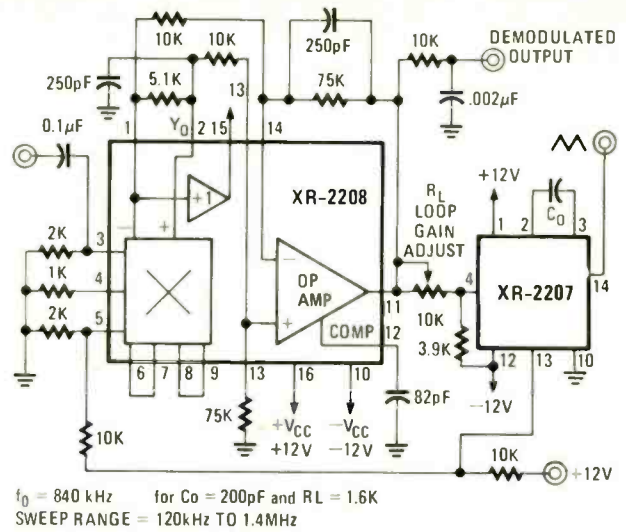


FIG. 10-PRECISION PLL

locked AM demodulation and for carrier-level detection. Fig. 11 shows a recommended circuit connection for such applications. The XR-210 or XR-215 monolithic PLL circuits can be adjusted to lock on the desired input AM signal and regenerate the unmodulated carrier. This carrier frequency appears across the timing capacitor, C_0 , of the PLL and is used as the "reference input" to the XR-2208 multiplier. The AM signal is applied simultaneously to the PLL input and to the XR-2208 multiplier input (pin 3), as shown in Fig. 11.

The demodulated signal is then low-pass filtered by capacitor C_1 at the multiplier output, and can be amplified further to the desired audio level by using the op-amp section of the XR-2208.

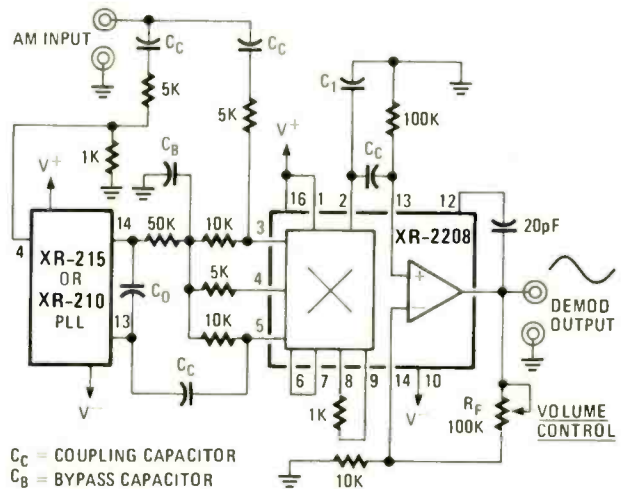


FIG. 11-PHASE-LOCKED AM DEMODULATION OR CARRIER DETECTION

In the carrier detector applications, the op-amp is used as a voltage comparator and produces a "high" or "low" level logic signal at the op-amp output when the input carrier level reaches a detection threshold level set by an external potentiometer. The output from the carrier detector can then be used to enable the "logic-output" stage of the XR-210 FSK modem.

The phase-locked AM or carrier detector system of Fig. 11 shows a high degree of frequency selectivity, as determined by the monolithic phase-locked-loop "capture" bandwidth.

VTR Update



A look at the latest equipment introduced since our February 1978 videotape recorder roundup

FRED PETRAS

ONE OF THE PERILS OF DOING A "WRAPUP" or "roundup" type of feature article in the fast-moving world of home electronics is that by the time it appears in print it is outdated to some degree. **Radio-Electronics** has run into this situation again, this time with our feature on Home Video Tape Recorders (HVTR's) that appeared in the February 1978 issue. Even as the presses were rolling, a half-dozen changes had taken place, and by the time the issue hit the newsstands and the Post Office mailing circuit, a lot more had happened. This article, then, is meant as an update piece, to bring you as close to the whole story as possible within the framework of press deadlines.

New HVTR entries

As noted, several companies were poised to enter the HVTR market. And some have done so. Among them is Akai, which revealed it will market VHS decks (two- or four-hour not specified at presstime). Aiwa and Pioneer, both strong in audio tape recorders, have announced plans to sell Beta 2 units in the United States. Quasar, marketer of the VX-2000 system, is branching out to additionally market a VHS-4 unit priced at \$995. And Montgomery Ward has gone the VHS-4 route with a Panasonic-brand-name unit at \$995. (That price will be dropped to \$947 in its spring-summer catalog, according to trade reports.) Competitor mass-merchant J.C. Penney is going with an RCA-brand-name VHS-4 at \$1000.

Another company, not mentioned in our feature article, announced that it is entering the U.S. HVTR market this year. It is Shin-Nippon Electric Company, home electronics arm of Nippon Electric Company, Tokyo. The firm will market two-hour Beta models "sometime this year" under the NEC brand name. Initially, Shin-Nippon will offer Sony-made units, but later will offer its own models.

And, just as we finished writing the above, word came that Philco is about to enter the HVTR field with a VHS-4 model in May.

At the same time we learned that

Magnavox is coming up with related HVTR products—25-inch color TV consoles with compartments to accommodate HVTR decks. A vertical armoire with *Star* tuning chassis is priced at \$1300; a horizontal console with *Touch-Tune* chassis at \$995; and a horizontal console with regular TV chassis at \$799.

As noted in our February article, HVTR pricing has been in a state of transition. Sony recently dropped its Beta 2 list price from \$1300 to a more competitively viable \$1095, as did Toshiba, both on the heels of Zenith, which triggered the drops by cutting its price from \$1300 to \$995. (This move by Zenith was reportedly done to be competitive with RCA, Zenith's arch-enemy in the color TV field.) JVC came up with a price cut on its two-hour VHS from \$1280 to \$1050.

Thus, manufacturer pricing of the three main contenders—Beta-2, VHS-2 and VHS-4—is in the \$995 to \$1095 range. This \$100 differential is usually smaller in terms of pricing at the retail level. With HVTR products still in a somewhat short-supply/heavy-demand state, retail pricing has stabilized to a notable degree. *At the moment*, no one is talking about or expecting any additional severe price cutting, either at the manufacturer level or at the retail level.

Relative to playing times, the battle continues. As noted, Sony, with two-hour capability, in an attempt to take the edge off the four-hour capability of competitors, came up with a "long-play" videotape that extends Beta running time to three hours, and a cassette changer to permit up to six hours of operation. Subsequently, JVC announced it would soon offer a three-hour cassette for its VHS-2 system.

This capability for long operation time poses a problem, namely, timers to enable its full use primarily in the area of automatic "absentee" recording. Manufacturers are reportedly at work on the matter and may possibly have LP timers in the marketplace by fall.

Heretofore, HVTR owners had three

basic, relatively low-priced color TV cameras to choose from—a JVC unit at \$1500, a GBC unit at \$1595 and a model from Toshiba at \$1700. Now Zenith is offering a two-tube Akai color camera at \$2895, and Sony is promoting a Tricon color camera at \$2995.

A source at Akai said the company expects to offer a high-performance color model at a "breakthrough price" sometime this year. Meanwhile, other companies have spurred their research and development departments to devise lower-priced color cameras for HVTR use. Among them is Sony, which recently entered a technical pact with NEC (Nippon Electric Company) with a view to developing low-cost color cameras.

Videotapes

At presstime, **Radio-Electronics** was still hearing reports that blank video tapes have been in short supply in many parts of the country, namely in VHS form. The word from tape suppliers is that this situation will ease off shortly. Key manufacturers are stepping up their efforts on behalf of HVTR users by increasing production in some cases, or by adding new tapes production facilities. An example of the latter is Sony, which built a \$50 million tape plant in Alabama to assure adequate supplies of Betamax cassettes.

As predicted in our February article, recorded HVTR tapes are growing in abundance as more and more companies get into the field. The latest development is the formation of Video Club of America, Farmington Hills, MI 48024, which sells (via mail-order) two-hour movies from 20th Century Fox Studios at \$39.95, and longer features at \$59.95, in the major HVTR formats. The club also offers a trade-in program under which consumers who bought a \$39.95 videotape can return it for a 50 percent credit on their next purchase.

R-E

computer corner

Z-80 How to interface the Z-80 to other devices and the associated timing

WILLIAM BARDEN, JR.

LAST MONTH, WE LOOKED AT THE THREE different ways the Z-80 can be interrupted. This month, we'll take a look at how the Z-80 can be interfaced to other devices.

Before discussing some real-world examples of interfacing, we'll look more closely at the interface timing diagrams and interfacing signals involved. The Computer Corner in the December 1977 issue briefly discussed CPU timing for the operation code-fetch portion of instruction execution. The timing for a memory read or memory write is similar except that the M1 cycle (operation code fetch) is not active during the read or write memory operation.

Figure 1 shows the timing diagram for a memory read and Fig. 2 shows the timing diagram for the memory write operation. They are usually three clock-

valid memory address is on address bus lines A0-A15. If a memory read is being performed, signal RD is brought down to a logic 0. If a memory write is being performed, RD is a logic 1 and signal WR is a logic 0. Data is strobed into the CPU register during read operations at the indicated time, or is available for a memory write during most of the three write cycles.

Provision is made in the Z-80 microprocessor for interfacing to slower memories by the WAIT signal input to the Z-80. Bringing this signal down to a logic 0 informs the Z-80 CPU that external memory is not ready to transfer data. Figure 3 shows the result: It simply stretches the memory read or write time as long as required by slow memory.

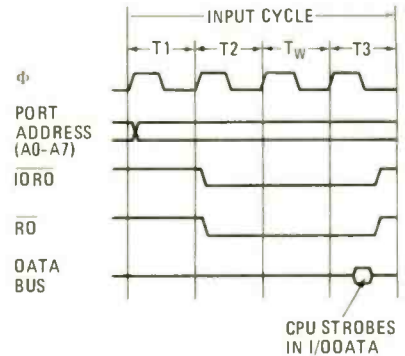


FIG. 4

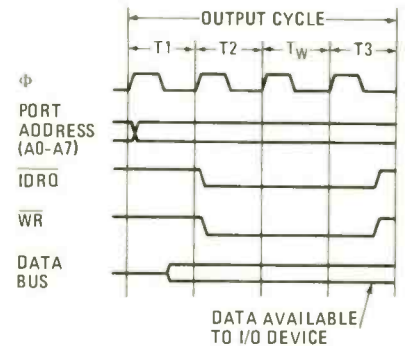


FIG. 5

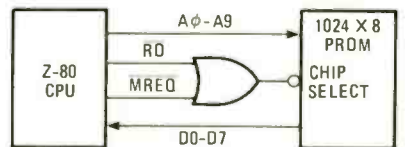


FIG. 6

to I/O device addresses, rather than to memory addresses alone.

Figure 4 shows the Input and Fig. 5 shows the Output cycles on the Z-80. Note that the major difference is in the IORQ signal that notifies the external I/O device that a valid I/O device address is present on address bus lines A0 through A7. The RD and WR signals are used in the same sense as in memory read and write operations. Note that input and output cycles are four clock cycles long, because the CPU automatically inserts an additional wait cycle to provide more time for the I/O device to respond. The I/O devices can also use the wait state capability provided by the wait input to synchronize slow-speed I/O devices with CPU execution of Input or Output instructions.

Figure 6 shows the operation of a Z-80

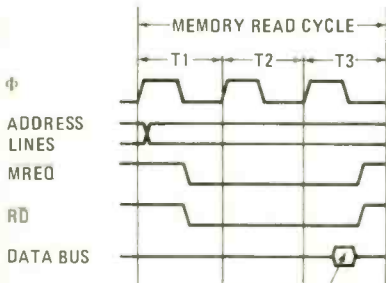


FIG. 1

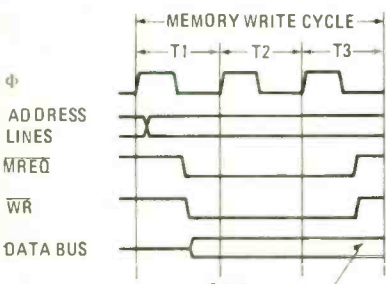


FIG. 2

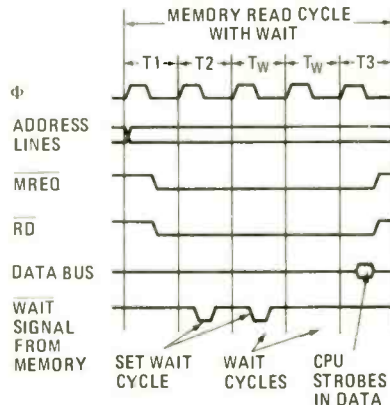


FIG. 3

I/O routines

Input and Output data transfers are initiated by unique I/O instructions. The CPU decodes these instructions and issues a special signal to indicate that data will be transferred to an I/O device, rather than a memory device. The Z-80 and the 8080 are different from most microprocessors in this respect since many microprocessors do not differentiate between memory addresses and I/O device addresses. Address decoding for many other microprocessors is done by the memory and I/O devices in a *memory-mapped* I/O scheme. The net effect is that some of the address range of this type of microprocessor must be dedicated

periods long, unless slow memories are being used, in which case additional wait clock cycles can be activated by the slow external memory. The MREQ signal is used to signal the external memory that a

CPU with a 1024-by-8 bit PROM. This simple example allows for no I/O device interfacing and is for demonstration purposes only. Address lines A0-A9 are brought into the PROM to provide 10 bits of address (0-1023). Since presumably no write operations to the PROM will be performed in the program, the signals \overline{RD} and \overline{MREQ} are OR'ed together to provide a chip select signal to the PROM. Signal \overline{RD} is not really necessary since every memory access is a memory read.

Figure 7 shows the same PROM stor-

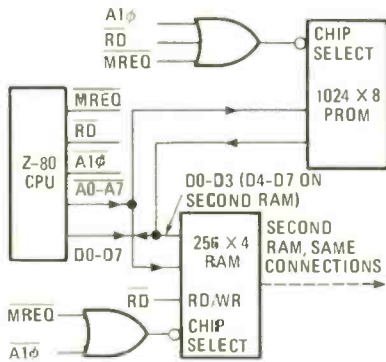


FIG. 7

age with additional RAM storage to supplement the somewhat limited RAM storage of the CPU registers in the first

example. Here, it is assumed that the RAM will not contain a program, and that it will provide storage for program variables computed in the course of program execution. In addition, the PROM memory is located at addresses 0000 through 03FF (ϕ through 1023₁₀), while the RAM addresses are 0400 through 04FF (1024-1279₁₀). Address-line 10 can therefore be used to decode whether PROM or RAM is being addressed. While \overline{RD} and \overline{WR} must both be provided to the RAM memory, only \overline{RD} is used for the PROM. As in the first example, \overline{RD} is a redundant signal for the PROM since a \overline{MREQ} with address line A10 = 0 will guarantee that only the PROM is being addressed.

In Fig. 8, an I/O device is added to the system. Since only one I/O device is used, signal \overline{IORQ} alone is sufficient to inform the I/O device that it is being addressed. A second simplification here is that the I/O device is a read-only device and that no decoding of read-versus-write is necessary. Anytime the I/O device is addressed, the \overline{IORQ} line is brought to a logic 0, and the device will output eight bits of data on the data bus. No address decoding is necessary either, since only one I/O device is used in this type of configuration.

The above examples are simple, workable interfacing examples for memory and I/O devices. Additional address de-

coding would be necessary in larger configurations, in addition to further gating and buffering of Z-80 outputs and inputs.

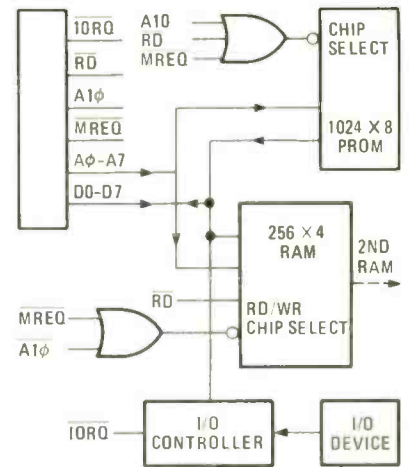


FIG. 8

While the 8080 microprocessor and updates to the 8080, such as the 8085, remain extremely popular and usable microprocessors, the Z-80 offers many advantages over the 8080. The Z-80 appears to be the microprocessor of the future, as short-lived as the future is in the world of microprocessors. We will be watching for up-dates and will keep you advised. **R-E**

Ungar Super-Wick™

the ultimate
desoldering braid...

SUPER-WICK desolders printed circuit boards, components, terminals and connectors by simply soaking up molten solder. It is quick and easy to use with nearly any soldering iron and its handy storage spool doubles as a holder during use. **SUPER-WICK** is made from clean, bright copper braid and a pure rosin flux. The copper color lets you actually see the solder being absorbed, and there is no need to remove the protective coating of rosin from the work after desoldering. **SUPER-WICK**'s convenience, ease of use and effectiveness makes it the perfect companion for any soldering iron, so ask your distributor for **UNGAR SUPER-WICK**.



Division of Eldon Ind., Inc.
Compton, CA 90220

hobby corner

A look at the various breadboarding and prototyping systems available (including a brand-new one) for building your own circuits from scratch. EARL "DOC" SAVAGE, K4SDS, HOBBY EDITOR

BACK IN THE OLD DAYS, THE HOBBYIST HAD two choices of procedure when he wanted to design or test a circuit. He could tack-solder the parts together on a breadboard (literally, a pine plank), or hard-wire it right on the chassis and hope for the best. Even so, that wasn't too bad—all the components were large and few were fragile, so it was no great problem to put them in and take them out.

Later on, things got better. At one time I was fortunate enough to have a small Vector breadboarding outfit for tubes. It was quite revolutionary because it provided for temporary circuit building and a relatively easy change of components.

Today, a hobbyist without a modern breadboarding and prototyping system is at a great disadvantage. With subminiature (sometimes even microminiature) parts that are often sensitive to heat and/or physical handling, how can he work at all? He must throw a lot of time *and* a lot of parts.

Happily, that struggle is not necessary. There are some good breadboarding and prototyping systems available that are effective and efficient. They are time-saving, component-saving, temper-saving and money-saving. Best of all, they are not costly—in fact, you can start inexpensively, then add on when and if you have the need and the means.

Before taking a look at these systems, let's make sure we are talking about the same things. The terms *breadboard*, *circuit board* and *prototype board* have been used so much lately they have become quite confusing. Right or wrong, here's how we'll use them.

A *breadboard* is any device that allows circuit elements to be electrically connected and disconnected by applying pressure on the component leads. Usually, these temporary connections are made by using spring clips embedded beneath the surface of a perforated block.

A *prototype board* allows circuit elements to be electrically connected in a physically stable manner. While components can be removed and exchanged, the connections are not considered temporary and are usually soldered or wire-wrapped. Furthermore, a prototype board accommodates a wide variety of circuits. One

kind of board is called a *universal* printed-circuit (PC) board, as opposed to a *dedicated* PC board.


The term *circuit board* encompasses several types of boards—in fact, all boards *except* breadboards. Therefore, to avoid confusion, we will not use this term.

A *dedicated* PC board is one that has been designed for one particular circuit only, and cannot normally be used for any other. It can be constructed by attaching stick-on pads to a nonconducting board, by etching a copper-clad board or by grinding a copper-clad board.


First, we'll look at the characteristics of each of the major breadboarding systems and then, we'll do the same for prototyping systems. Next, we'll examine how some of these systems match for combination use, particularly a new system just being introduced in this country. Finally, we will suggest ways to help you decide when and how to do what.

Breadboards

Table I shows five breadboarding systems along with the major characteristics of each. The prices indicated in the table and in this article are approximate suggested list prices.

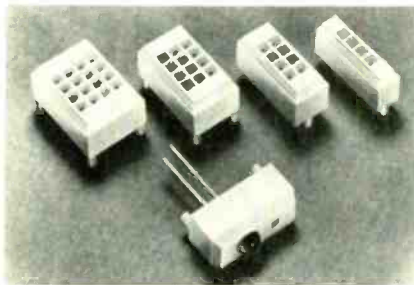


TIE-POINT BLOCKS by AP; one with an LED.

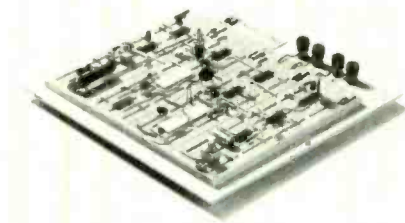

ALL-CIRCUIT EVALUATOR model ACE 236.

A breadboard is considered to be *indexed* if it is marked in such a way that each tie point can be identified by a number-letter (or any other) combination. (The full significance of indexing will become apparent later.) The wire size listed is not necessarily that claimed by the manufacturer but represents the maximum gauge that can be easily inserted into the tie points. Our breadboarding experience indicates that the maximum size of wire accepted is of greater significance than the minimum size.

The AP Products system features small *Tie-Point Blocks* that contain various tie-point configurations, and there is one block that holds an LED. These blocks are available in packages of 20. In addition, the *All-Circuit Evaluators*, available in kit form or assembled, contain different groups of terminal and distribution strips mounted on a metal plate with binding posts and bumper feet (\$19-\$80). AP Products also manufactures *Unicards*. These are breadboard strips mounted on cards for modular card-rack construction (\$32-\$56). Also available are various special boards, a jumper wire kit (\$10), as well as connectors, sockets and ribbons for interboard connections.

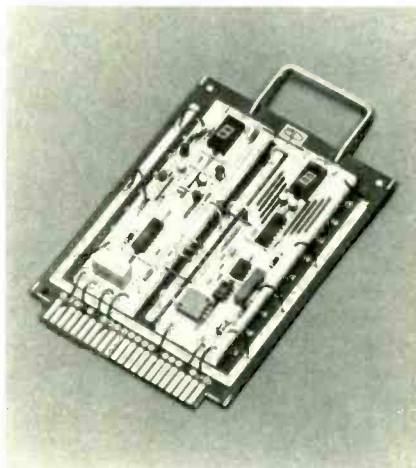

UNICARD by AP plugs into external circuitry.

The Continental Specialties breadboards interlock so that you can make larger layouts with ease. Continental Specialties QT sockets and strips are also available as various *Protoboards* on plates with binding posts and feet (\$16-\$80) and mounted on boxes with internal power supplies (\$55-\$120). Useful accessories include a function generator (\$70) and an R-C bridge (\$60).

TABLE I—BREADBOARDING SYSTEM CHARACTERISTICS

Manufacturer	Hole Pattern	Size	In-dexed	Component Sockets Re-quired	Bus	Wire Size	Other	Name(s)
AP Products, Inc. Box 110-Q Palmsville, OH 44077	Standard .1" X .1"	34 X 5TP* to 128 X 5	No	No	Attached and/or separate	to No. 20	Tie Point Blocks 1 X 4 to 4 X 4 and LED's 20 at \$4 to \$10	Terminal strips Distribution strips Unicards All-circuit evaluators
		15 to \$19**			12 X 4 to 36 X 4			
					\$2 to \$4**			
Continental Specialties Corp. Box t942 New Haven, CT 06509	Standard .1" X .1"	14 X 5 to 118 X 5	Some mod- els	No	Attached and/or separate	to No. 20	See text	QT sockets & bus strips Exper- imenter Protoboards
		\$3 to \$13**			12 X 5 to 40 X 4			
					\$2 to \$4**			
E & L Instru- ments, Inc. 61 First Street, Derby, CT 06418	Standard .1" X .1"	16 X 5 to 128 X 5	No	No	Attached	to No. 22	See text	SK sockets Mini-board Universal breadbox
Saxton Products, Inc. 215 N. Rte. 303 Congers, NY 10920	3 special types, see text	3 X 5-in. modules 70 to 208 TP	Yes	Yes/No, see text	Attached	to No. 18	Detach- able con- trol panels	S-DeC T-DeC U-DeC
		\$5 to \$20						
Vector Elec- tronic Co., Inc. 12460 Glad- stone Ave. Sylmar, CA 91342	Standard .1" X .1"	8 X 4 to 24 X 4 (for mounting on .1" X .1" board)	Yes	No	Separate 1 X 4 to 1 X 8	to No. 20	Can use both sides, see text	Klip-Blok Klip-Strip Klip-Bus Patchboard

* 34 units of five tie points each.
** Approximate suggested list prices.




E & L's model BB-IV Universal Breadbox.


Vector and Saxon approach breadboarding somewhat differently. Let's consider the two systems in reverse alphabetical order since the Vector system is based upon .1 X .1-inch hole spacing. That spacing, by the way, conforms to the pin spacing of practically all IC's. This is why it is not necessary to use IC sockets with these systems.

The Vector system differs from the others in two significant respects: First, the .1 X .1-inch patterned tie-point blocks (called *Klip-Blok's*) are designed to be mounted on .1 X .1-inch perforated boards. The *Klip-Blok's* and *Klip-Strip's* can then be shifted around at will and placed in almost any position on the perforated *Patchboard*.

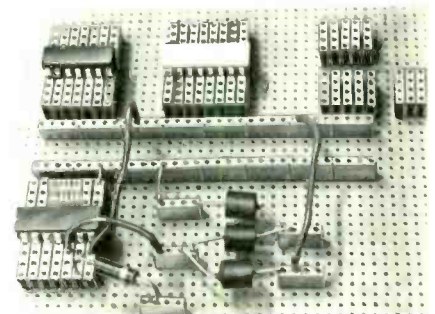The second big difference in the Vector system is that the tie points are




VECTOR's Klip Strips and Bus Strips.

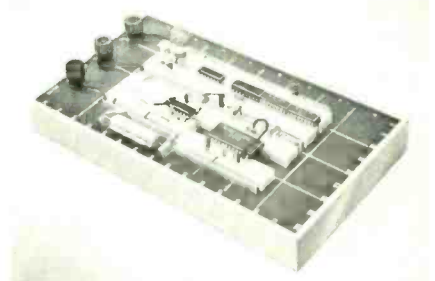

VECTOR 51X Klip-Blok DIP Patchboard.


constructed so that wires can be inserted from either side or even all the way through them. In fact, since the *Klip-Blok's*, *Klip-Strips* and *Patchboard* all have the same hole pattern, and since the *Patchboard* is mounted on an open-bottom frame, components can be placed on both sides of the system. Although not necessary, of course, you have the option of using this system in this manner

continued on page 103

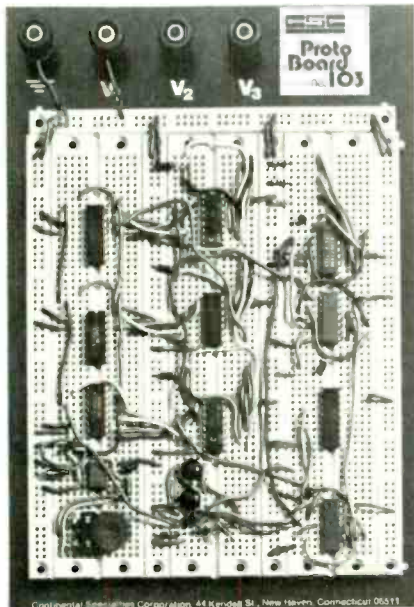

CONTINENTAL SPECIALTIES 103 ProtoBoard.

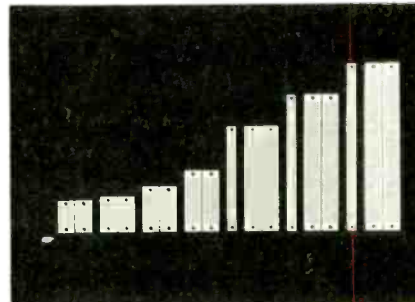The E & L Instruments system includes a *Mini-board* with binding posts and feet. Self-adhesive hook and loop fasteners hold the SK sockets and large components so that they can be mounted or removed with ease. The base of the *Mini-board* is somewhat more flexible



SERIES QT SOCKETS AND STRIPS by CSC.

than others we've seen. E & L also makes a *Universal Breadbox* consisting of SK sockets, binding posts and BNC connectors mounted on a sloping-top box. There's enough space inside the box to build such things as power supplies.



MINI-BOARD 101 by E & L Instruments.

state of solid state

Delta modulation is finding many useful applications. A new integrated circuit from Motorola performs both the decode and encode functions. **KARL SAVON**, SEMICONDUCTOR EDITOR

TRANSMITTING DIGITAL DATA OVER radio, telegraph or telephone channels is one of the most reliable methods of communication. Analog signals, whether audio, video or control waveforms, can be transmitted with similar reliability if they are first digitized into binary equivalents. If the instantaneous analog levels are first converted into a binary series of ones and zeros, they can then be routed through a digital communication channel and then decoded or reassembled into the original waveform.

Binary transmission is inherently reliable because it is simple to distinguish between only two different levels. The two levels can be represented by two DC voltages, two frequencies, two phases, or other more complicated schemes.

Motorola Semiconductors has developed the XC3417 and XC3418 IC's to perform the modulation and demodulation functions of a CVSD (Continuously Variable Slope Delta) modulation scheme.

Delta modulation, developed about 30 years ago, approximates an analog signal by using line segments. It is a digital coding system that performs well considering it requires relatively few components. The system is asynchronous and, therefore, does not require the transmission of sync signals. Delta modulation is somewhat less efficient in bandwidth than pulse-code-modulation (PCM) for speech and video. However, its characteristics are just about right for telephone-quality speech. For many telemetry and control applications, delta modulation uses less bandwidth than PCM.

How it works

Figure 1 shows the block diagram of a CVSD encoder. The analog input signal is compared against a waveform that is approximately the same as the one that will eventually be decoded at the receiver. Based on the result of this comparison, the system then reduces the error between the two comparator inputs. At specific clock-cycle intervals, the comparator output is sampled to determine the direction and magnitude of the slope of the next segment of the approximated waveform.

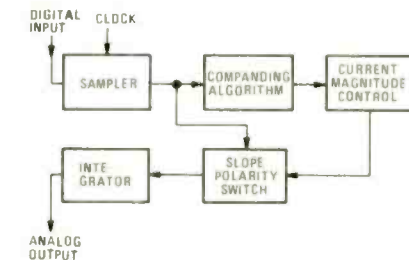


FIG. 1—CVSD ENCODER compares the input signal against a waveform that is approximately the same as the decoded signal and reduces the error between them.

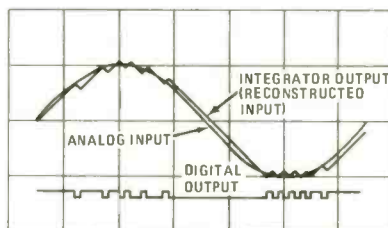


FIG. 2—WAVEFORMS showing how the CVSD encoder tracks the analog input.

Figure 2 shows that when the approximated signal exceeds the input waveform, the comparator changes the polarity of the slope. The sampler output operates the slope polarity switch, which directs current into an integrating capacitor. Since the integrated voltage is too great in this case, the current is switched so that the output discharges towards a lower voltage.

At each comparison interval, if the approximated signal still exceeds the input, the negative slope is maintained; or if the approximated signal is less than the input, the slope is switched to a positive value.

Some modified delta-modulation systems use a resistor to discharge the integration capacitor at a relatively high rate. This modification further simplifies the circuit but increases the channel bandwidth.

The digital output of the system, the same output that is transmitted over the communication channel, is the input to the slope polarity switch. By transmitting the slope polarity of the approximated signal, an integrator in the decoder, similar to the one used in the encoder, recon-

structs the same approximated signal. Approximate filtering smooths out the discontinuities to produce a close copy of the original analog input.

The companding algorithm and current-magnitude control blocks in Fig. 1 make the system even more interesting and useful. To optimize system performance, the integrator-output slope is changed to compensate for the range of input-signal slope variations. Constant-slope line segments may be too shallow to follow, or so steep that they overshoot the input waveform.

An algorithm to solve this problem was developed that was easy to implement in the circuit. A shift register keeps track of the slope polarity for a fixed number of clock pulses. If the slope polarity does not change for a number of clock pulses, it is possible that the output waveform is not keeping up. Under these conditions the slope is increased or decreased, accounting for the term, "continuously variable."

Figure 3 shows that the decoder has circuit blocks in common with the encoder. In fact, it is possible to switch a

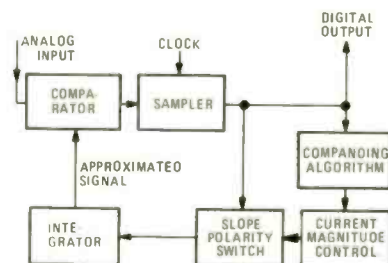


FIG. 3—CVSD DECODER contains the same functional blocks as the encoder.

couple of leads around on the IC to change the circuit from an encoder to a decoder. You can do this in simplex operation when only one station transmits at a time. Wherever full-duplex operation is required (simultaneous transmission and reception), separate modulators and demodulators are needed.

Figure 4 shows the schematic of a simplex voice CVSD using the XC3417 integrated circuit; all the functions discussed are included on the single IC.

The encode function is enabled by closing the push-to-talk switch, transfer-

ring the solid-state encode/decode switch to its upper encode position.

The analog input is shown AC-coupled to the inverting comparator input. The other input to the comparator is the reconstructed waveform reproduced at the receiver's demodulator. The comparator output continuously shows whether the input waveform is lower or higher than the reconstructed waveform.

The comparator output feeds the serial input of a three-stage shift register. Clocked by a 16-kHz signal, the shift register reads the comparator output on the falling edge of each pulse. The output of the first shift-register stage is the sampled output of the comparator and becomes the digital output.

The slope polarity switch sets the direction of the current that feeds integrator network R6-C2. The current integrated by capacitor C2 is equal to the voltage across R_X divided by the resistance of R_X (13K). Because the resistor connects to high-input impedance op-amp A2, essentially all the current in R_X flows into the polarity switch and then into integrator network R6-C2. The op-amp forces the voltage of the inverting and noninverting inputs to be equal. Controlling the voltage on pin 3 controls the voltage on pin 4 and also the value of the integrator current. Filter capacitor C_S is connected between pin 3 and V_{CC}, and R_S

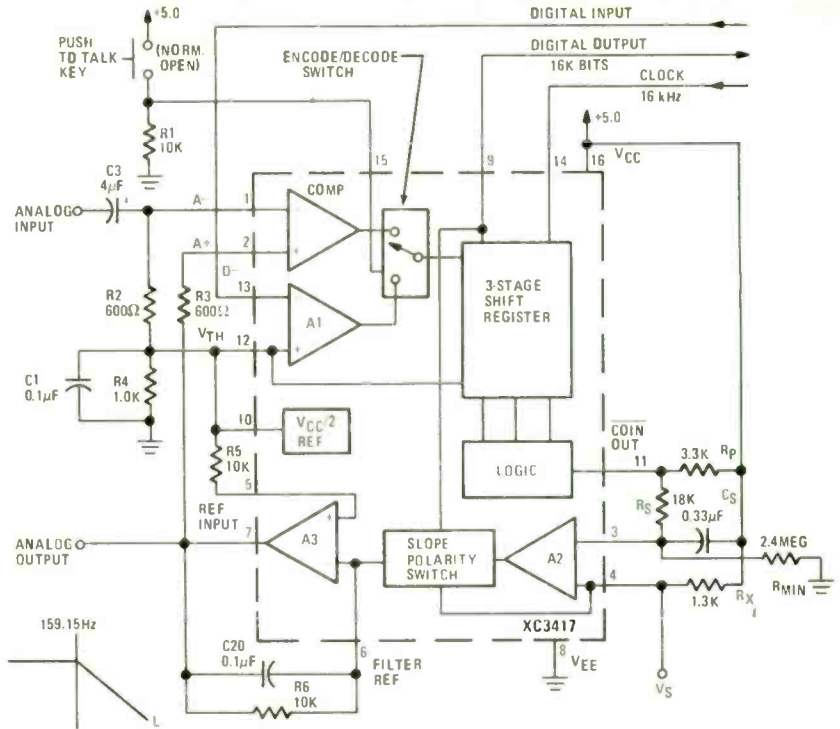



FIG. 4—SIMPLEX VOICE CVSD built around the XC3417. Encode and decode functions are controlled by the push-to-talk switch.

couples the inverted coincidence output to pin 3.

A logic circuit connected to the parallel outputs of the three shift-register stages

detects when the three outputs are either all ones or all zeros. If the output-signal polarity has been equal for three consecu-

continued on page 98

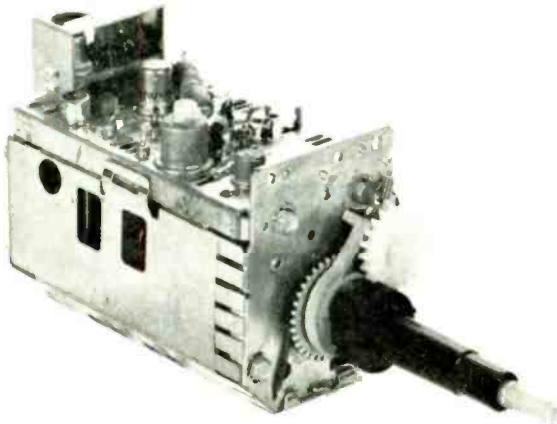

The Best of Everything Has Its Price

Even tuner service. From the beginning our goal has been to provide the best tuner service, not the cheapest. The extra dollar you might pay at PTS is peanuts when you consider the reliability and standards of excellence we apply to every job. Thousands of PTS customers must agree or we wouldn't be the world's largest tuner service company.

See The Yellow Pages For The PTS Servicenter Nearest You Or Contact:



PTS ELECTRONICS, INC.

P.O. BOX 272 BLOOMINGTON, IN 47401 812-824-9331

CIRCLE 76 ON FREE INFORMATION CARD

service clinic

Troubleshooting horizontal sweep circuits in solid-state television sets.

EVER SINCE TV BEGAN, WE HAVE SEEN one very familiar symptom: "Thin horizontal line across screen." This cause is easy: there's no vertical sweep. The problem is usually quite simple to find and fix. With the advent of solid-state TV, a new one has turned up: "Thin vertical line on screen." This shakes up us old tube-type technicians! I do not remember ever seeing this on a tube set—that is, for more than a few milliseconds when the damper blew up or something similar. This is because any problems in the horizontal deflection yoke killed the boost, which, in turn, killed the sweep, high voltage and the whole works in one fell swoop.

Most of the solid-state sets have an entirely different basic circuit. The horizontal deflection coil and the flyback are in shunt across the horizontal output transistor. If the horizontal deflection coil opens, the high voltage is often unaffected. There are also other differences in the deflection yoke circuitry as compared with the tube sets. Let's see how a couple of solid-state deflection circuits work, so that you'll know what to look for if this kind of symptom occurs.

Figure 1 shows a basic circuit, stripped to its bare essentials. The horizontal output transistor provides a current pulse that is fed to the flyback (which works just like other flybacks). This signal is also fed into the horizontal deflection coils, which are in parallel with the flyback. The current pulse flows through the yoke windings, then returns to ground through a yoke-return capacitor. The pulse actually charges and discharges this capacitor, thus completing the AC circuit for the horizontal deflection coils.

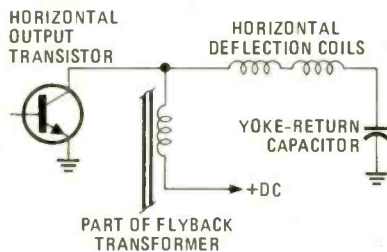


Fig. 1

What happens if this capacitor opens? A thin vertical line. There is a dandy quick check for this, just scope the yoke-return capacitor. If the yoke-drive pulse

JACK DARR, SERVICE EDITOR

appears on the hot side but there is obviously no horizontal sweep, there's your answer. Tack another capacitor across the original (with the power off) and check.

In actual sets, the circuits include a lot more components than the one in Fig. 1.

The complete horizontal-deflection-coil circuit for one popular chassis is shown in Fig. 2. Let's follow the signal through the circuit starting at the collector of Q401. The signal goes to the flyback and also to the deflection yoke socket,

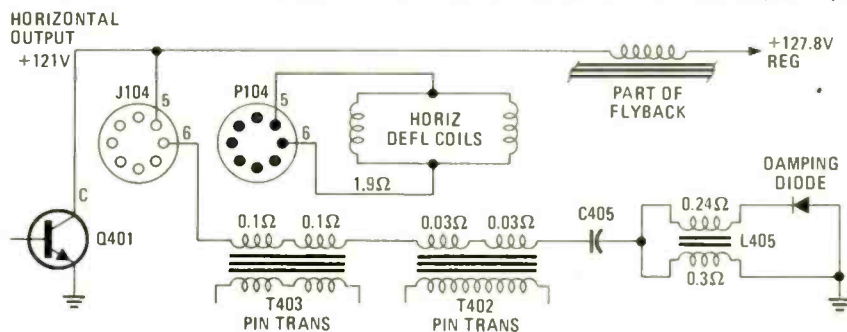


Fig. 2

J104 pin 5. From here it proceeds through the paralleled horizontal yoke windings (others are in series; it makes no difference) through the primary windings of T402 and T403 and two pincushion transformers. From T402, the signal goes through C405, a 0.55- μ F capacitor (there's the yoke-return capacitor; I knew we'd find it in here somewhere!); and on through L405 to ground.

This complete path for the horizontal deflection yoke currents is easy to check out with an ohmmeter. Start with one ohmmeter lead on pin 6 of the deflection yoke socket (J104). (You did check the yoke? Good.) You can check both pin transformers by reading the resistance from J104 pin 6 to the top of capacitor C405. Both of these windings measure only 0.26 ohm total. From the bottom end of C405, the other pin transformer measures only 0.3 ohm. If there is continuity at these points and still no horizontal sweep, the capacitor is apt to be open.

In a case at point, a Service Clinic reader wrote that he had no horizontal sweep in an RCA CTC-71J. I recommended checking the points as described above, and he found an open conductor on the PC board on the PW400 horizontal

deflection and pincushion board. All test points are easily accessible in this chassis, and capacitor C405 is right out in the open! In any other chassis, you might not be this lucky, but the troubleshooting principles will still be the same.

In another set, the circuit is basically similar. But instead of returning to DC ground, the horizontal deflection yoke returns to a horizontal-centering control with a pair of diodes. The horizontal-centering control is connected to the +145-volt line. However, it seems as though the AC return path is made at this point through a 30- μ F electrolytic capac-

itor that's connected to ground on the centering control. The +145-volt source in the DC power supply had better be at AC ground if the filter capacitors aren't open! This small difference in the circuit won't affect the basic diagnosis, of course.

So, if this symptom appears in a solid-state TV set, you can immediately eliminate a couple of things, namely the horizontal output stage, flyback, low voltage DC power supplies, and high-voltage rectifier. Also, you know the drive pulses are present or the other stages wouldn't be working either. If you follow the horizontal deflection coil circuit from the output transistor all the way to ground, the faulty part should show up pretty fast.

As I said, this can't happen in tube TV sets. I have never seen a genuine case like it. However, once I thought I did on an Admiral chassis that was brought in for service. Like most of the sets manufactured in those days, it had a large flat pantype chassis with the picture tube strapped to it. I set it up on the bench, with the picture tube on top, and applied power. Lo and behold, a thin vertical line *did* show up on the screen! I tested the horizontal sweep circuits, but this showed

absolutely nothing wrong. There was plenty of high voltage, the drive waveforms were all fine, etc. After some head scratching, the reason finally dawned on me. This was one of the rare sets with the chassis mounted *vertically* on the side of the cabinet so that the picture tube was not on the top but on the *side*! Placing the tube in this position made it look better; now I had a thin horizontal line. I fixed the problem in the vertical sweep, and took it home (blushing a little, but happy). The moral of this story is: "Don't get too much exercise by jumping to conclusions!" Make a complete analysis first.

R-E

service questions

MULTIPROBLEM TV

This is a tale of a tough dog—a Muntz AS-9015. This set had: a dim picture, poor focus, vertical shrinking. I checked the focus voltage; it didn't read right. Then I recalibrated the high-voltage probe, and now had 6 kV so that wasn't it! Checked the voltage-dependent resistor in the vertical circuit. The vertical-input grid resistor and the 150K resistor in the height-control circuit were off-value; changed them, but no help. Round and around!

Finally, I read the +1050 boost-boost voltage: I'd replaced the boost rectifier first—ZERO. I replaced it again . . . WHAM-O! Bright, full picture, no focus problem. The boost rectifier I used the first time around wasn't marked, and I guess I managed to get it in backward! (I've also run across some top hat diodes with markings reversed, so check these before installation.) Thank you for the help in solving this dog.

(Actually, about all I gave him was sympathy. Thanks to George Welker, George's TV, Spokane, WA, for this tale of woe.)

CROWBAR SHORT

I've really got a dead short in a Zenith 12CB12X. The fuse blows so fast that I can't find it! I've checked everything and found nothing. I'm pulling my hair out.—L. A., Franklin Furnace, OH.

Don't do that . . . when you get to my age, you'll need it!

Now, you have two loads on the AC line; one is the heater circuit, the other, the DC power supply. You say that a slow-blow fuse makes the heater rectifier blow out. This is a clue. Disconnect the heater rectifier and then turn it on, connecting a 25- to 50-watt lamp across the fuse holder. If the lamp lights up, there's a short in the DC power supply (diode, input-filter capacitor, etc.). If the lamp doesn't light up, the short is in the heater circuit. The likely suspects are: the

protective diode to the common ground or a wiring short in the input to the heater circuit. The trouble is not likely to be in the middle of the line, or some of the tubes would light very brightly.

"PUMPING" SPEAKERS

Here's a funny one: I've got a Harman-Kardon 930 receiver that has a very low-frequency pulsation, and the pilot light dims if the speakers are connected. After much searching, I found that this can be stopped by disconnecting the left preamp. The DC voltages at the preamp outputs are different. What have I overlooked?—D. B., San Jose, CA.


I think you've found it. Something in that left preamplifier is causing a feedback to make the speakers "pump" and take excessive current. Disconnect both preamplifiers and feed a signal into the power amplifiers; see if their output signals are equal. If so, connect the right-hand preamplifier, and feed a signal into it. If this works, take that left preamplifier apart and you'll find something in there that's way off.

SCREEN BLACKOUT

This problem on an RCA CTC-35 has me stumped! The screen goes dark, but it continued on page 92

NEW FROM LEADER

The Sensitive 80MHz 7-Digit Counter

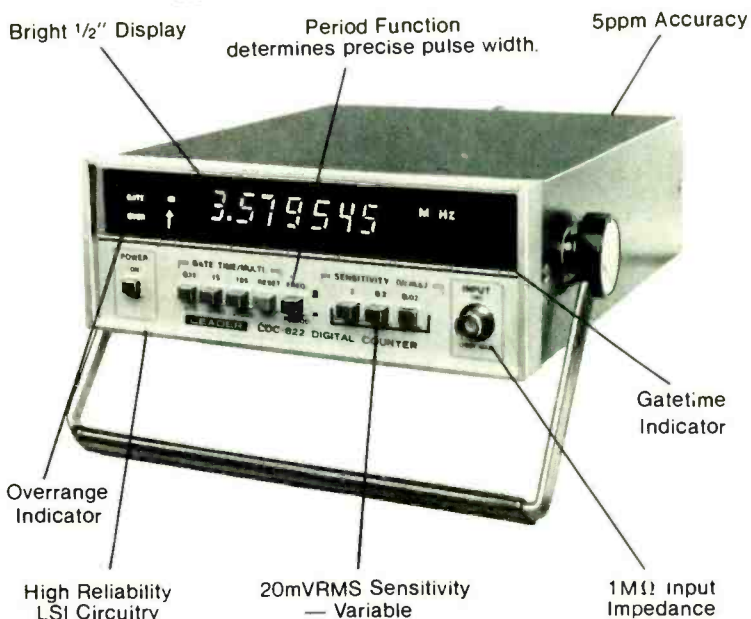

Compare Features, Accuracy, Sensitivity. We'll be Number 1.

Model LDC-822 \$ 299.⁹⁵ with accessories.

See your distributor or write direct for details.

151 Dupont Street, Plainview, N.Y. 11803
(516) 822-9300


In Canada: Omnironix Ltd., Montreal, Quebec

When Quality Counts . . .

LEADER
Instruments Corp.

CIRCLE 3 ON FREE INFORMATION CARD

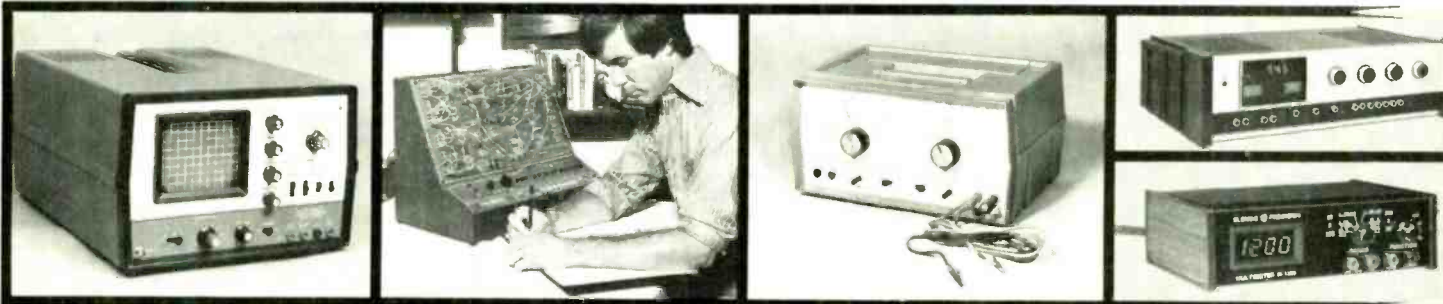Train with NTS for the MicroComputers, digital the first name



MicroComputers



The world of electronics is daily becoming more challenging. Technology is growing more specialized, and the importance of digital systems increases every day. Test instruments, home entertainment units and industrial control systems are all going digital. And now, NTS training programs include a wider choice of solid-state and digital equipment than ever before offered in any home study course: Advanced NTS/Heath digital color TV (25" diagonal with optional programming capability), NTS/Heath microcomputer, digital test equipment, digital stereo receiver (70 watts per channel), NTS compu-trainer, plus much more state-of-the-art equipment to make your training exciting and relevant.


The equipment you receive with NTS training programs is selected to provide you with a solid

background in electronic systems. Kits and lessons are designed to work together to demonstrate electronic principles and applications. The kit-building not only shows you how electronic hardware functions, but how various circuit designs accomplish different purposes. Your lessons guide you through any number of experiments associated with many projects. This is the Project-Method, and it works. Step-by-step, you learn how and why digital electronics has become a part of our world, and the even bigger role it is sure to play in the future.

Whether you are looking for training in Consumer, Commercial, or Industrial electronics, NTS offers fourteen courses, some basic, many advanced, in several areas of electronics. An all-new full-color NTS catalog shows you what each course covers,

electronics of the future.

systems and more...from
in home study.

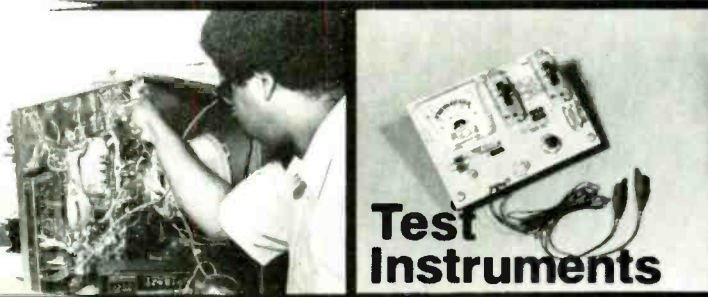

Test Instruments



Digital Color TV

Simulated TV Reception



Basic Electronics



NTS Training Programs in Consumer and Industrial Electronics

and every piece of equipment included.
Send for it today, and see for yourself what's really happening in electronics training technology at NTS. Find out how much has changed, and what new directions the field is taking. You'll probably want to be a part of it.
It's free. Just mail the card or coupon. Today.

**NO OBLIGATION. NO SALESMAN WILL CALL.
APPROVED FOR VETERAN TRAINING.**

NATIONAL TECHNICAL SCHOOLS

TECHNICAL-TRADE TRAINING SINCE 1905
Resident and Home-Study Schools
4000 South Figueroa St., Los Angeles, Calif. 90037

NATIONAL TECHNICAL SCHOOLS Dept. 206-048
4000 South Figueroa Street, Los Angeles, California 90037

Please send FREE Color Catalog and Sample Lesson.

- Color TV Servicing
- B & W TV and Radio Servicing
- FCC License Course
- Electronic Communications
- Electronics Technology
- Audio Electronics Servicing
- Digital Electronics
- MicroComputers/MicroProcessors

Name _____

Address _____

Apartment Number _____ Age _____

City _____

State _____ Zip _____

- Check if interested in G.I. Bill information
- Check if interested ONLY in classroom training in Los Angeles.



Revolutionary! Sound-shaping taping mike.

Never before — a single microphone that gives you the versatility of 16 microphones! Four tiny frequency filter switches built into the new Shure 516EQ E-Qualidyne Microphone let you tailor sound for studio effects in virtually any recording situation: flick a switch to add sizzle to vocals . . . flick another switch to highlight the sound of a bass drum. You can even compensate for the acoustic response of a room — *right from the microphone!* In all, the 516EQ creates 16 different response variations that can add a new, professional sound to every tape you make. Available singly or in pairs for stereo recording. Ask to hear a recorded demonstration at your participating Shure dealer.



Shure Brothers Inc.
222 Hartrey Ave., Evanston, IL 60204
In Canada: A. C. Simmonds & Sons Limited



Manufacturers of high fidelity components, microphones, sound systems and related circuitry.

CIRCLE 6 ON FREE INFORMATION CARD

SERVICE QUESTIONS

continued from page 87

does so only once every three or four weeks. When it does, the high voltage is still up. Then, I can turn it off for five minutes, turn it back on and it works for three to four weeks more. Something is biasing-off the picture tube, right?—R. D., Springfield, VA.

Right. There are a couple of things that cause this. One is a bad heater contact on the 12BY7 video output tube socket. If the heater contact is bad, this kills the tube, there's no plate current, the plate voltage rises to +405 supply voltage and out goes the screen. Similarly, it could also happen with the jumper on the PC board in the heater circuit to the two difference-amplifier tubes; if there's a bad solder joint here, these tubes go out and their plate voltage goes up, biasing the tube to heavy conduction and out goes the screen. It's more likely to be the video output tube in this case, since the difference amplifiers cause the high voltage to pull down just a little or, in some cases, a lot.

HIGH-VOLTAGE SHUTDOWN

I had a Quasar TS-938 with a peculiar symptom: If it was turned on in the evening, nothing came on. However, if it was turned on in the morning, it would play all day until turned off at night.

You gave me some hints from the Quasar Field Engineers, and they worked. When I reset the DC voltage to get +100 volts on pin 16 of the JA panel, everything worked fine. I didn't know that some of these voltage controls would shut down on *low* line voltage! When they write "sealed at the factory" on that high-voltage adjust control, they aren't kidding. The stuff they use could seal safes!

(Thanks to George Senn, Red Bank, NJ, for this feedback. Here's another way of resetting that voltage control: Quasar says to remove the original control, replace it, adjust it and then reseal it. A lot easier than trying to get that cement off!)

DEFLECTION YOKE

I need some help in getting a new deflection yoke for a Bradford TV, model WTG-61059. The original part number is 490V017C01. Do you have the company's address?—F. C., Victory, NY.

Sorry, Bradford isn't with us any more. However, here's one good clue: That part number is obviously a Westinghouse part number. Westinghouse is one of 15 firms that built Bradfords that are listed in my J. W. Miller Company *Catalog No. 175*. With a little head scratching and a lot of cross-checking, I found a substitute listed for this yoke: a Triad YT-103-1.

NO BRIGHTNESS CONTROL

There's a brightness problem in this Sharp C-922 that I can't find. The raster is
continued on page 94


Jim-pak[®]

electronic components

One-Stop Component Center

NEW!! EXPANDED PRODUCT LINE...

<p>TTL</p> <p>7400 7480 7402 7492 7404 7493 7408 74102 7410 74121 7420 74122 7430 74123 7432 74125 (DM8093) 7442 74154 7447 74161 (DM9318) 7473 74176 (DM9280) 7474 74177 (DM9281) 7475 74192 7476 74193 7485 74367 (DM8093)</p> <p>Low Power TTL Schottky</p> <p>74LS00 74LS73 74LS109 74LS02 74LS74 74LS123 74LS04 74LS75 74LS136 74LS08 74LS83 74LS139 74LS10 74LS85 74LS181 74LS20 74LS86 74LS175 74LS30 74LS90 74LS367 74LS32</p> <p>C/MOS</p> <p>4000 4020 4050 4001 4023 4051 4010 4024 4059 4011 4029 4071 4013 4084 4081 4016 4046 4051 4017 4049</p> <p>Display LEDs Discrete</p> <p>MAN2 KC556 Red DL704 KC558 Orange DL102 KC558 Yellow DL747 CLPL1 LED's Red, Green, Yellow</p>	<p>LINEAR</p> <p>LM301V LM963V LM303V LM723N LM309K LM739N LM311V LM761V LM320K-5 (7905) LM747N LM320T-5 (7905) LM1488V (555SV) LM320T-1 (7912) LM1488N LM320T-1 (7915) LM1488N LM339N LM1558V LM340T-5 (7805) XR2208 LM340T-12 (7812) CA3080 LM340T-10 (7815) CA3130 LM555V CA3140 LM558N LM5900N (CA3401)</p> <p>MICROPROCESSOR</p> <p>Z-80 2101 8080A 2102 8212 21102 8224 7489 8228 MM5262 6800 1702A 6810 8252Z 6830B 2708 M6801B DM8835N M6802B N897 M68014 (Clock Chip)</p> <p>SOCKETS</p> <p>8 pin low profile 16 pin wire wrap 14 pin low profile 16 pin wire wrap 16 pin low profile 24 pin wire wrap 24 pin low profile 40 pin wire wrap 40 pin low profile TO-3 Socket 14 pin plug TO-5 Socket 16 pin plug Molex Pins</p> <p>SWITCHES</p> <p>Slipswitches Slide Toggle Push Button Subminiature Push Button</p>	<p>CAPACITORS</p> <p>Aluminum Electrolytic</p> <p>1mfd 50V 100mfd 50V 4.7mfd 50V 220mfd 50V 10mfd 50V 470mfd 50V 22mfd 50V 1000mfd 25V 47mfd 50V 2200mfd 16V</p> <p>Ceramic Disc</p> <p>100p 50V .001mfd 50V 47p 50V .0047mfd 50V 1000p 50V .01mfd 50V 220p 50V .022mfd 50V 330p 50V .047mfd 50V 470p 50V 1mfd 50V</p> <p>Dipped Tantalum</p> <p>1mfd 35V 2.2mfd 25V 22mfd 35V 3.3mfd 25V 33mfd 35V 4.7mfd 25V 47mfd 35V 6.8mfd 25V 88mfd 35V 10mfd 25V 1mfd 35V 15mfd 25V 1.5mfd 35V 33mfd 25V</p> <p>Polyester Mylar</p> <p>.001mfd 100V .022mfd 100V .0015mfd 100V .047mfd 100V .0022mfd 100V 1mfd 100V .0047mfd 100V 22mfd 100V .01mfd 100V</p> <p>CRYSTALS</p> <p>CY1A CY2A CY12A</p> <p>TEST CLIPS</p> <p>14 pin clip 16 pin clip</p> <p>FUSE HOLDERS</p> <p>HKP 3AG</p>	<p>P.C. POTENTIOMETERS</p> <p>Single-Turn 15-Turn B40P-1K 830P-1K B40P-5K 830P-5K B40P-10K 830P-10K B40P-50K 830P-50K B40P-100K 830P-100K B40P-1Meg 830P-1Meg</p> <p>DIODES</p> <p>1N4148 (1N4148) 1N4333 1N4301 1N4734 1N4904 1N4742 1N4907 1N4744 MDA-980-3</p> <p>TRANSISTORS</p> <p>C10681 2N3055 2N2222A 2N3904 2N2007A 2N3906 MJE 2955 2N5129 MJE 3055 2N5129</p> <p>CONNECTORS</p> <p>DB25P Plug DB25S Socket</p> <p>DATA BOOKS*</p> <p>7400/74LS Data Book CMOS Linear Data Book Microprocessor LED Data Book *JIMPAK Products only</p> <p>HEAT SINKS</p> <p>1/4 W RESISTOR ASST. 3/8 Watt 5% 50 Pk. Assortments</p>
--	---	--	--

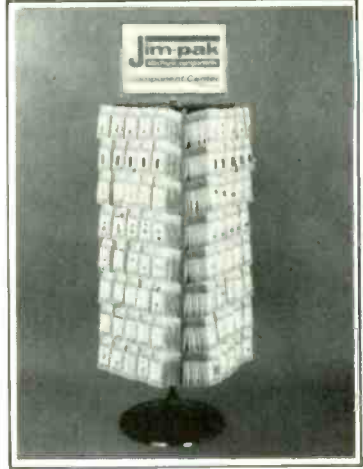

A new component product line of over 260 items developed for the independent dealer. Guaranteed, nationally advertised products. Complete JIM-PAK program includes national advertising, direct mail programs, store display racks, stock rotation plan and return policy. For dealer information, write or call JIM-PAK, 1021 Howard Avenue, San Carlos, CA 94070 (415) 592-8097.

SEE JIM-PAK AT NEWCOM '78—MAY 2, 3 and 4, 1978 AT THE LAS VEGAS HILTON



SEE YOUR LOCAL Jim-pak[®] DEALER TODAY...

<p>ALABAMA</p> <p>Mobile Lafayette Radio Electronics</p> <p>ARIZONA</p> <p>Fountain Hills P & C Communications Tucson Computerworld Inc. Yuma Yuma Electronics</p> <p>CALIFORNIA</p> <p>Bellflower Earl's Hobby Shop Berkeley Al Lasher Electronics Fontana Fontana Electronics Fullerton Orvis Electronics Inc. Long Beach Scott Radio Supply Los Angeles Electra Imports Inc. Mission Viejo Tower Electronics Corp. Monterey Zackit Oceanside Electronic Center Palo Alto Zack Electronics Pasadena Dow Radio Inc. Sacramento The Radio Place Sacramento Zackit San Carlos J & H Outlet Store San Diego Radio Shack A.S.C. Mira Mesa San Francisco Zack Electronics San Jose Quipnet Electronics San Luis Obispo Mid State Electronics Sunnyvale Sunnysvale Electronics Vallejo Zackit Walnut Creek Byte Shop Computer Store</p> <p>CANADA</p> <p>Alberta (Calgary) The Computer Shop Ontario (Willowdale) Home Computer Centre</p> <p>COLORADO</p> <p>Aurora Com Co Electronics Steamboat Springs Norm's TV & Electronics</p> <p>CONNECTICUT</p> <p>Bridgeport Computer World</p> <p>FLORIDA</p> <p>Lakeland Lakeland Specialty Electronics Orlando Altair Computer Center of Orlando Tampa AMF Electronics Tampa Microcomputer Systems</p> <p>FRANCE</p> <p>Paris Computer Boutique</p> <p>GEORGIA</p> <p>Atlanta Atlanta Computer Mart</p> <p>HAWAII</p> <p>Aiea Delcoms Hawaii Honolulu Integrated Circuit Supply</p> <p>IDAHO</p> <p>Idaho Falls Audiotronics</p> <p>ILLINOIS</p> <p>Evanston Tri-State Electronics Evanston Ity Bitry Machine Co. Groveland Mayer Electronics</p>	<p>ILLINOIS (Cont'd)</p> <p>Mount Prospect Tri-State Electronics Oak Park Suetronics Schmensburg Data Domain</p> <p>INDIANA</p> <p>East Chicago Acro Electronics Hammond Quantum Computer Works</p> <p>IOWA</p> <p>Indianola Electronics Limited</p> <p>KENTUCKY</p> <p>Lexington Radio-Electronic Equipment Co.</p> <p>LOUISIANA</p> <p>Baton Rouge Davis Electronics Supply</p> <p>MARYLAND</p> <p>Baltimore Computer Workshop of Baltimore Baltimore Everything Electronic Levale J & M Electronics Rockville Computer Workshop Towson Computers, Etc.</p> <p>MASSACHUSETTS</p> <p>Medford Tufts Electronics North Adams Electronics Supply Center Waltham Computer Mart Inc.</p> <p>MICHIGAN</p> <p>Grand Rapids Micro Computer World Lansing Fulton Radio Supply Mt. Clemens The Computer Store</p> <p>MINNESOTA</p> <p>Duluth Northwest Radio of Duluth Eagan Computer Room Inc.</p> <p>MISSOURI</p> <p>El Dorado Springs Beckman Electronics Parkville Computer Workshop of Kansas City</p> <p>MONTANA</p> <p>Billings Conley Radio Supply</p> <p>NEBRASKA</p> <p>Lincoln Altair Computer Center Omaha Omaha Computer Store</p> <p>NEVADA</p> <p>Las Vegas Century 23</p> <p>NEW JERSEY</p> <p>Bayville A.R.S. Communications Services Cherry Hill Computer Systems Unlimited Hoboken Hoboken Computer Works Pompton Lakes Computer Corner of New Jersey Ramsey Typetronic Computer Store</p> <p>NEW YORK</p> <p>Albany Fort Orange Electronics New York The Computer Stores Inc. New York Computer Mart of New York Troy Trojan Electronics White Plains The Computer Corner</p>	<p>NORTH CAROLINA</p> <p>Durham Futureworld Greensboro Byte Shop Raleigh Byte Shop of Raleigh</p> <p>OHIO</p> <p>Bucyrus Meed Electronics Cincinnati Digital Design Dayton Altair Computer Center Reynoldsburg Universal Amateur Radio Steubenville Hostfelt Electronics</p> <p>OKLAHOMA</p> <p>Gaymon Sound Service Oklahoma City Bits, Bytes & Micros</p> <p>OREGON</p> <p>Beaverton Altair Computer Center Coos Bay Herrick Electronics Ontario Miller Electronics</p> <p>PANAMA</p> <p>Panama City Sonitel, S.A.</p> <p>PENNSYLVANIA</p> <p>Hershey Microcomputer Systems Inc. Murrysville Computer Workshop of Pittsburgh</p> <p>RHODE ISLAND</p> <p>Cranston Jabour Electronics City Pawtucket Jabour Electronics City Inten-Trade (PTE) Ltd</p> <p>SINGAPORE</p> <p>SOUTH CAROLINA</p> <p>No. Charleston Technical Services Inc.</p> <p>TENNESSEE</p> <p>Knoxville Byte Shop Memphis Sere-Rose & Spencer Electronics Oak Ridge Computer Denn</p> <p>TEXAS</p> <p>Dallas Computer Shops Inc. Houston Altair Computer Center Houston Interactive Computers San Antonio Sherman Electronics Supply</p> <p>VIRGINIA</p> <p>Alexandria Computer Hardware Store Alexandria Computers Plus Charlottesville Layaltee Electronics Richmond Computers To-Go Springfield Computer Workshop of North Virginia Virginia Beach Heathkit Electronics Center</p> <p>WASHINGTON</p> <p>Bellevue Altair Computer Center Langview Progress Electronics Pasco Riverview Electronics Seattle Empire Electronics Spokane Personal Computers</p> <p>WEST VIRGINIA</p> <p>Morgantown The Computer Corner Morgantown Electro Distributing Co.</p>
---	---	---

SERVICE QUESTIONS

continued from page 92

too bright, there are retrace lines, etc., and the brightness control has no effect. I found +55 volts on the common control grids of the picture tube. This should be only -1.5 volt. When I shunt this to ground with a resistor to give zero volts, the brightness control works! Where does this small negative voltage come from?—E. F., Baltimore, MD.

The picture-tube grid circuit is a bit complicated. Apparently the bottom end of the high-voltage multiplier goes to the grids and then (somehow) to ground,

possibly through the DC power supply.

This is some kind of beam-current control circuit. The small amount of voltage that is developed from the high-voltage multiplier return would be positive. However, there's a diode in the circuit marked "Isolation": this current flows in pulses that may develop enough negative voltage to cancel the positive voltage fed through those resistors. Since the problem seems to be somewhere in this area, check all resistors and the diode.

HIGH-VOLTAGE SHUTDOWN

I need an idea on this Magnavox T989-

THE BEST EQ KIT VALUE ANYWHERE!

A Quiet* Announcement, Based
On The Undistorted* Truth
About Equalizers

Popular Electronics September '76 —

Chosen as cover project for "Special Focus on Audio" issue.

Modern Recording August '77 —

"The EQ-10 met or exceeded its published specifications" . . . excellent performance of a caliber that lends itself to professional as well as home audiophile applications"

Hundreds Currently in Use at major
Broadcast Stations, Recording Studios
and Universities worldwide.



*QUIET . . . 90dB below 1 volt input, 20 to 20K, set flat or fully boosted *UNDISTORTED . . . Below 0.1% THD & 0.05% IM at any EQ setting . . . below 0.05% THD and 0.0075% IM set flat.

Does the equalizer you're considering offer full ten band control with symmetrical "mirror-image" boost and cut responses centered on ISO preferred octave bands? Does it have permanently-lubricated 60mm metal-cased sliders with metal shafts and center click detents? Do the specs tell you what to expect at all settings . . . or only at the "flat" setting, where the critical tuned networks are bypassed? Does it employ advanced hum & saturation-free "gyrator" simulated inductors on all low and mid-frequency bands? How about truly differential balanced and unbalanced inputs and outputs for use in any audio system, amateur or pro? And "fit anywhere" packaging designed for 19" rack, in-wall, in-console or optional wood cabinet mounting? What about truly flat response (both amplitude and phase angle) at the center reference setting?

WE BELIEVE IN OUR PRODUCTS. We want you to see them . . . read our fully illustrated assembly and applications guide . . . inspect the quality of the components . . . at no risk to you! Simply use the coupon below to indicate the item(s) you want, your name and address and enclose a check or money order (no COD or bankcards) for the full amount. Upon receipt of your completed order, we'll rush your kit(s) to you, pre-paid shipping in the U.S.A.

After careful inspection of the kit(s), you may return any or all items in their original unassembled condition for a full immediate refund if you are not totally satisfied . . . (no questions asked). And, if you decide to keep and build the kit(s), our normal guarantee on the specs and parts still applies . . . if your properly assembled kit(s) fail to operate as stated, we will exchange any defective parts free for the first 90 days.

ORDER BLANK

QUAN.	ITEM	DESCRIPTION	PRICE
()	EQ-10M	Single EQ module kit (mono) less power supply	\$ 65.00
()	EQ-10SP	Two EQ module kits (stereo) plus PS-4 power supply kit	\$150.00
()	EQ-10QP	Four EQ module kits (quad) plus PS-4 power supply kit	\$275.00
()	EQ-1082P	Eight EQ module kits plus two PS-4 power supply kits	\$540.00
()	PS-4	Power supply kit (open frame) powers up to four modules	\$ 25.00
()	EQ-10WC	Walnut veneer (genuine wood) cabinet fits EQ-10SP kit	\$ 30.00
()	RA-2	Rack mount kit	\$ 6.50

Washington State residents add 5.4% state sales tax. Returns of unassembled kits for refund must be made within 10 days of receipt and returned items must be packed in original condition, using original packing materials. Prices and "trial offer" valid for orders postmarked on or before July 31, 1978. Outside U.S. check reader service card for ordering information.

NAME _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____

Delta-Graph Electronics Company

P.O. Box 247 Northgate Station • Seattle, WA. 98125 • (206)525-7196

CIRCLE 75 ON FREE INFORMATION CARD

01. The high-voltage shutdown works too fast. If I unhook the reference voltage, disabling the shutdown, everything works perfectly. The high-voltage is 29.5-kV, the +120-volt line regulates nicely, and so on. However, when I rehook the reference voltage, it works for quite a while, then away it goes again!—C. F., Iola, KS.

Since the high voltage and everything else seem to be normal, I agree that the problem is in the high-voltage shutdown. I looked through my Magnavox file and found a Service Note on "Nuisance Tripping of High-Voltage Shutdown"! The note says: Try setting the high-voltage to 28.0 kV at zero beam current. If this does not clear up the problem, then install Magnavox Kit No. 18138-2. This kit contains a new high-voltage bleeder resistor, a new Z301 and a new high-voltage limiter adjust control, along with instructions.

OPEN CEILING HEATER WIRING

Lloyd F. Bazant, Design Engineer with Western Instruments, 4714 S. W. Willetta St., Albany, OR 97321, writes that his company makes a special "locator" device for finding open circuits in built-in ceiling heating wires. [A reader in Rossville, GA, wrote (Radio-Electronics, November, 1977) asking about the subject.] Oddly enough, this instrument is called a "Ceil-Heat Fault-Finder," which is exactly what it does. Thanks for the data.

FAULTY REMOTE CONTROL

I have a problem in the remote control of a Philco 13J42 chassis. I can make it work on the channel selector or on the volume control, but they won't work together. It's either one or the other. What's happening?—M. B., Las Vegas, NV.

This sounds very much as if you have an alignment problem in the receiver. You have two tuned transformers on the limiter output. The 38-kHz transformer is the channel selector. Align each of these transformers and make sure the adjustment shows a definite peak. It is possible one of the ringer bars in the transmitter is broken, or something is damping it and throwing it off-frequency. Use the alignment procedure in Sams Photofact 650-2A that covers this receiver.

VIDEO PROBLEM

Recently, I wrote you for ideas on an AC problem in the video of this Zenith 8Y4B36. I got the schematic after I wrote you. As soon as I saw the schematic, I knew what was wrong. I had replaced a diode in the 24-volt source. This diode turned out to be a Zener and I had used an ordinary diode that wasn't well marked to replace the Zener. That cleared up the problem.—C. C., Chicago, IL

Good!

continued on page 96

Get a Voltswagon* for your VOLKSMETERS



VW-900A CASE: 20" x 15" x 6.5" **\$190.00**
Holds MS-15 Miniscope, FM-7 Counter, SC-5 Prescaler and any "LM" series DMM.

VW-800A CASE: 18" x 13" x 5.5" **\$175.00**
Holds MS-15 Miniscope, FM-7 Counter and any "LM" series DMM.


- Positive Protection For All NLS Instruments During Transport.
- All Instruments Are Instantly Ready For Use At A Convenient Viewing Angle.
- Battery Charger Motherboard—Accepts Up To Four NLS Chargers For Simultaneous Charging And Line Operation.
- Extremely Rugged Aluminized Cyclocac Case.
- Weighs Less Than 13 Pounds, Including Instruments And Chargers.
- Instant Instrument Removal—No Tools Needed.
- Optional Built-In Distortion Analyzer.
- Wired Remote Inputs And System Common Switching.

May be ordered built into VW series cases.

AN SERIES DISTORTION ANALYZERS



- **AN-4A DISTORTION ANALYZER** **\$195.00**
Direct digital display of THD to .01% when used with any DVM with four or more digits for readout. Exclusive "passive" dual tracking filters eliminates internal device errors. Ten turn balance control greatly simplifies balancing procedure. 15HZ-30KHZ: 350mv-20vrms: @ 8 ohms. 5.25" x 2.75" x 5.8"
- **AN-3A DISTORTION ANALYZER** **\$135.00**
Same specifications as AN-4A except measures THD to .1% when used with any DVM with three or more digits. Has single turn balance control.
- **AN-600 IMPEDANCE MATCHING NETWORK** **\$18.50**
Matches 600 ohm source to 8 ohm analyzer input impedance.

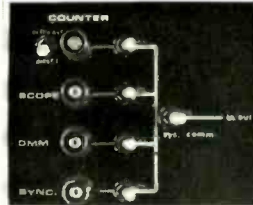

- Remote inputs provide one convenient location for all instrument input connections. Includes prewired instrument interface cabling.
- System common switching permits multiparameter measurement with one test lead connection and/or display input selection with multiple test leads.


NON-LINEAR SYSTEM INSTRUMENTS



SC-5 PRESCALER **\$89.00**
Includes input cable, FM-7 interface cable, NiCad batteries and charger.
• 20MHZ-512 MHZ
• 30 mv INPUT SENSITIVITY
• 1.9" H x 2.7" W x 4" D



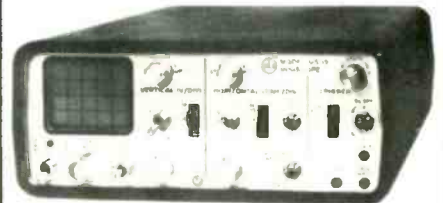"LM" MULTIMETERS, LED DISPLAY
Includes leads, NiCad batteries and charger.
LM-3A **\$125.00**
3 digit, 1% DC
LM-3.5A **\$147.00**
3½ digit, .5% DC
LM-40A **\$190.00**
4 digit, .1% DC
LM-4A **\$227.00**
4 digit, .03% DC
"LM" MULTIMETERS, LCD DISPLAY
Requires 3 "AA" batteries (not supplied).
LM-300 **\$99.50**
3 digit, 1% DC
LM-350 **\$125.00**
3½ digit, .5% DC
SIZE: 1.9" H x 2.7" W x 4" D



MS-15 MINISCOPE
\$289.00
Includes input leads, batteries, charger and 10 to 1 probe.
• 15 MHZ bandwidth
• Weighs only 3 lbs.
• Triggered internal and external sweep.
• Automatic and line sync.
• Vert. gain: .01-50v/div.
• .1 microsec. to .5 sec./div.
• Size: 2.7" H x 6.4" W x 7.5" D



FM-7 FREQUENCY METER **\$195.00**
Includes input leads, NiCad batteries and charger.
• 10HZ-60MHZ
• 7 DIGIT LED DISPLAY
• 1.9" H x 2.7" W x 4" D

MPM Labs

* **DEALER INQUIRIES INVITED**
VW series cases and AN series distortion analyzers are products of MPM Laboratories. Distributorships are available to qualified distributors.



MPM Laboratories
(406) 245-3296 1021 COOK AVE.
BILLINGS, MT. 59102

SERVICE QUESTIONS
continued from page 94

LOSS OF WIDTH

I can't get enough width on this Philco 18QT85A. It's shrunk in about 2 inches on each side of the screen. The high voltage is low too; it drops to about 14 kV if I turn up the brightness, and the raster blurs. The low brightness is about 22 kV. I've checked and changed a lot of things and can't find it.—M. D., Willimantic, CT.

Step one: Read the control grid voltage on the 6KD6 horizontal-output tube. The normal reading is -57 volts. If this reading is quite a bit more negative than it should be, try a new VDR. This resistor is the one that's used in the 6KD6 control grid and return circuit. It's apparently the only high-voltage regulation used in this chassis. If this resistor is bad it can develop too much negative bias and reduce the output of the 6KD6. Note that both sweep and high voltage are down. Just for luck, check the boost voltage. If this is low, you'll have these symptoms.

SYNC-AGC PROBLEMS

I'm having an odd problem in this CTC-36H RCA. When it's turned on, the horizontal sync goes. Then, the whole picture starts to fade after about 15 seconds, starting from the corners and working to the middle inside of 10 minutes, it goes

"click," and then works perfectly! What's the matter with this thing?—K. B., Brocklyn Park, MN.

There is one part that can, and does, cause weird symptoms like this—an intermittently open filter capacitor! If this capacitor is open or away down in capacitance at turn-on, it can cause a feedback signal through the B+ line that can give you almost any kind of symptom you want. Then, when the chassis has warmed up enough, the open joint heals, the set returns to normal and you sit there wondering what happened.

Clue: At turn-on, *scope* the B+ voltage lines, especially around the horizontal oscillator and/or the AGC stages. Look especially for pulses at horizontal frequency. If you see these pulses, that's probably what it is.

TRANSIENT SPIKES

You answered a reader's question in the July 1977 issue, saying that his trouble could be transients in the car's electrical system. I agree! I'm a Motorola two-way radio technician and the Motorola service bulletins state that in many cases, solenoids (and similar devices) in cars can cause spike transients of up to 400 volts peak when de-energized.

All Motorola's new equipment uses a dual Zener diode across the 12-volt input—i.e., 25-volt Zeners back to back. I

have seen these transient pulses hit hard enough to blow the diodes completely. The idea is to shunt off any pulse above 25 volts, and it does.

Thanks to Brian S. Hansen of Killingworth, CT for this information.

NO HORIZONTAL SWEEP


This RCA CTC-71J chassis has only a vertical line down the center of the screen. I've checked and changed the yoke; still no horizontal sweep. There's no yoke-return capacitor that I can see. Any help?—J. R., Detroit, MI.

I think you've done what I just finished doing—getting lost in that horizontal-yoke return circuit! The brown wire from the horizontal yoke is the return, and it goes all around the barn (through the pincushion circuitry), but it *does* go through a 0.55- μ F yoke-return capacitor C405. Capacitor C405 is on the right-hand side of the PW400 board, just below the toroid transformer. The capacitor is easy to get at, *after* you find it. Check all the connections and continuity through the pin circuits, as well as the capacitor.

WEAK COLOR

There's a color problem in this Admiral 4H12 chassis. The color signal is weak, and everything is all right up to the 6LE8 demodulator input, as far as the color signals are concerned. The colors are all

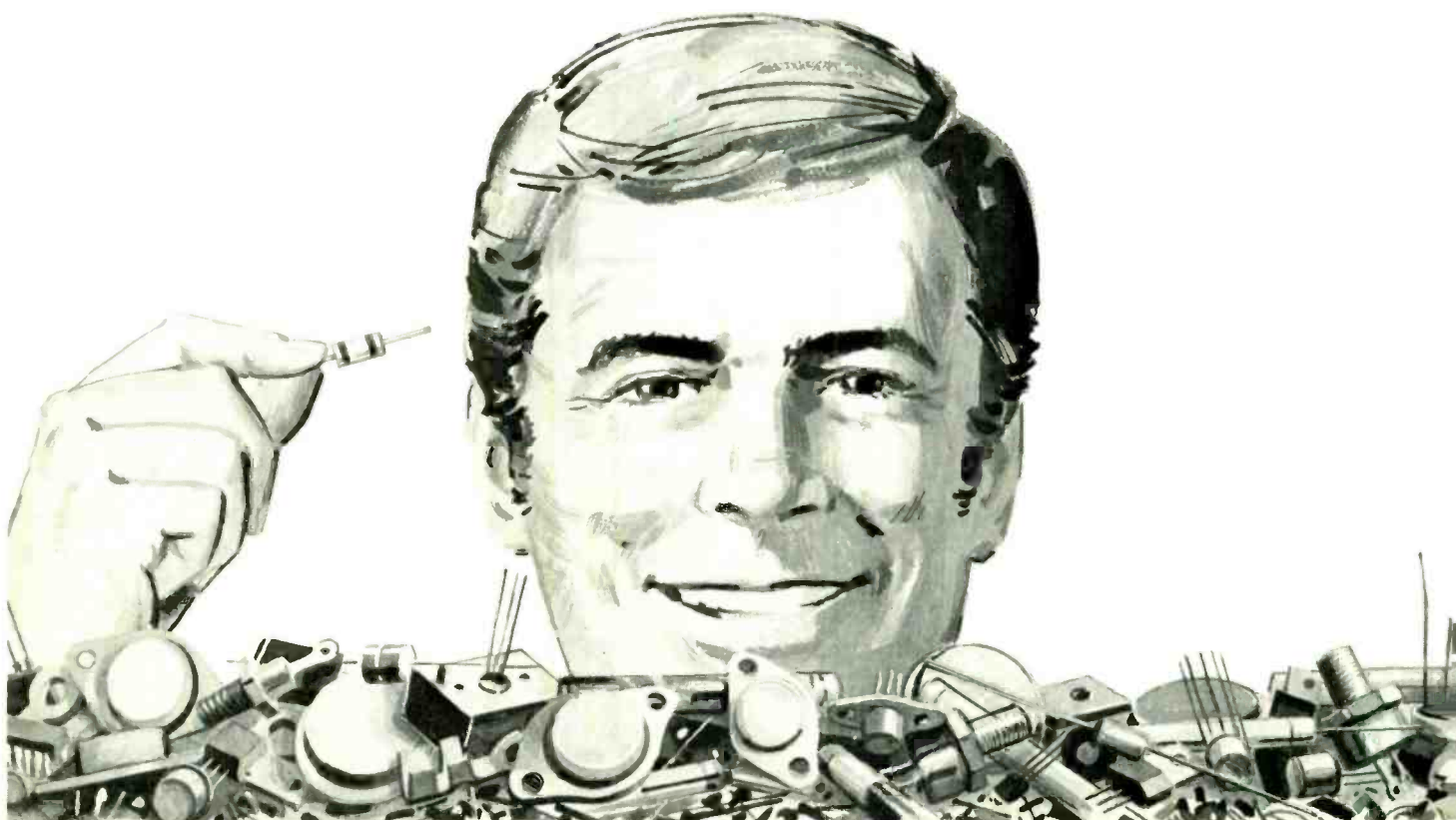Finding the right semiconductor replacement is easy with....



normal, they're just low in amplitude. Is there anything in your notes on this?—
R. C., Pacoima, CA.

We have found problems in sets using high-level demodulators, with tubes similar to the 6LE8 and others. The key clue is in the plate voltages; if these voltages are off, try a new tube. We've fixed several sets having this problem, using a new tube. Try a new 6GH8 in the 3.58-MHz oscillator socket just for luck. A low oscillator signal can also cause weak color.

HIGH-VOLTAGE DROP


I have no high voltage on a Webcor 4012 TV. (All parts are made by Toshiba.) If I unhook capacitor C411 from the flyback, I can read +250 volts on all its terminals. When C411 is connected, this voltage drops to less than +100. I hope you can help.—F. C., Seminole, FL.

So do I. Capacitor C411 is the boost capacitor, and the symptoms indicate it is very leaky. Note that your B+ voltage should be only -135, and you are reading +250 volts with the capacitor unhooked. Therefore, you are receiving a little "boost" from stray capacitance. Substitute a new capacitor for C411 (which is marked only for 400 volts). Try using at least a 600-volt capacitor here. The normal boost should be +350 volts. R-E

QUICK CHARGE IRON-QUICK CHANGE TIPS

ISO-TIP® Quick Charge Cordless Soldering Iron recharges in 3-4½ hours. Uses any of Wahl's 16 snap-in tips.

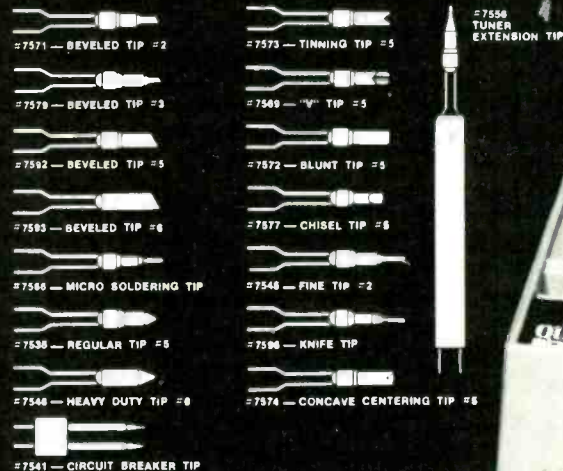Low voltage, battery powered, ground free isolated tip design.



WAHL CLIPPER CORPORATION
ORIGINATORS OF PRACTICAL CORDLESS SOLDERING.
Sterling, Illinois 61081 (815) 625-6525
"Manufacturing Excellence Since 1919"

CIRCLE 1 ON FREE INFORMATION CARD

RCA's all new 1978 Replacement Guide!

RCA's biggest and most complete Guide, ever. Our comprehensive line of replacement transistors, rectifiers, thyristors, integrated circuits, and high voltage triplers has now grown to over 750 SKs that replace 143,000 domestic or foreign semiconductors. And it's all under one cover.

It's an encyclopedia of solid state replacements. The new Guide includes 387 SKs which have been added to the line since February 1977. It contains 240 pages that represent thousands of hours of engineering know-how.

Everything you need to stay up-to-date. The new Guide covers consumer, TV, Hi-Fi, CB and industrial applications. And more importantly, they're available from your RCA SK distributor. And remember, too, that every RCA SK is backed up by RCA. They're Top-of-the-Line quality.

Ask your RCA Distributor for a copy of the 1978 SK Replacement Guide. Or write, enclosing \$1.50, (check or money order) to: RCA Distributor and Special Products Division, PO Box 85, Runnemede, NJ 07078.



RCA SK Replacement Solid State

CIRCLE 79 ON FREE INFORMATION CARD

tive clock edges, pin 11 switches low. Since one end of C_S is returned to the V_{CC} supply, the capacitor charges toward V_{CC} during periods of no coincidence. The voltage across the capacitor increases as does the voltage on pin 4 and the integrator current. This is how the companding algorithm is used to correct for insufficient or excessive slope. Time constants of the coincidence filter (also known as syllabic filter) are selected between 6 and 50 ms. In this particular

application, it is equal to $(R_P + R_S) \times C_S = 7$ ms.

For decoding, the push-to-talk switch is released so that the analog switch drops to its lower position and the shift register is fed from the digital sense amplifier instead of the modulator comparator. Other than that, everything works exactly as before. The same integrator circuitry and coincidence companding algorithm insure that the reconstructed signal is similar to the one approximated at the transmitter. Low-pass filtering removes the quantizing noise.

To design the circuit shown in Fig. 4

around the XC3417 or XC3418 integrated circuit, values must be assigned to a number of components to optimize the signal-to-noise ratio and distortion. As with all communication channels, bandwidth and amplitude limits require using filters and clock rates that are consistent with the limitations of the particular medium being used.

In conventional delta modulation systems, the clock rate is normally selected to be greater than the highest frequency to be sampled. Limited-integration delta modulation systems approach pulse-rate modulation (PRM) when the integration time actually becomes smaller than the period of the lowest signal frequency. Clock frequencies in the range of 9.6 to 64 kHz can be used to drive the circuit shown in Fig. 4. The higher the clock rate the greater the bandwidth needed for the channel, and the greater the signal-to-noise ratio. Voice channels are limited to a 9,600-Hz clock frequency, some radio systems can reach 12 kHz, and commercial telephone circuits will handle 37.7 kHz. Clock rates above 15 kHz work better with a longer shift register, which is how the four-bit XC3418 differs from the three-bit XC3417.

The value of R_x is selected so that the system can follow the input signal with companding ratios (the time the coincidence circuit is activated) that do not exceed about 25%.

With no analog input to the system, the digital output is an alternating sequence of ones and zeros. Although certain modified delta systems benefit from nonsymmetrical one-zero patterns, the one shown in Fig. 4 is designed for perfect balance. Because of circuit imperfections, the alternating ones and zeros should have a minimum step size of 20 mV (at 16 kHz) to guarantee the proper idle channel condition. The value of R_{min} determines the idle channel step size.

The XC3417 and XC3418 integrated circuits are available in ceramic or plastic 16-pin dual-in-line packages. The logic and analog functions are implemented with a combined P/L/Linear Bipolar processing technology. A data sheet is available from Motorola Semiconductor Products, Inc., Box 20912, Phoenix, AZ 85036.


AM/FM radio circuit

One of the primary design motivations for the Fairchild $\mu A721$ IC was the severe space limitations in automobile AM/FM radio/CB transceiver combinations. This IC along with a two- or three-transistor FM front end, a couple of diodes, some tuned circuits and an audio-output stage makes a complete AM/FM radio.

Figure 5 shows the AM/FM radio IC, which includes a bias circuit, two amplifiers, an IF limiter and detector and an oscillator mixer.

KITTATURE™

for the
computer
hobbyist

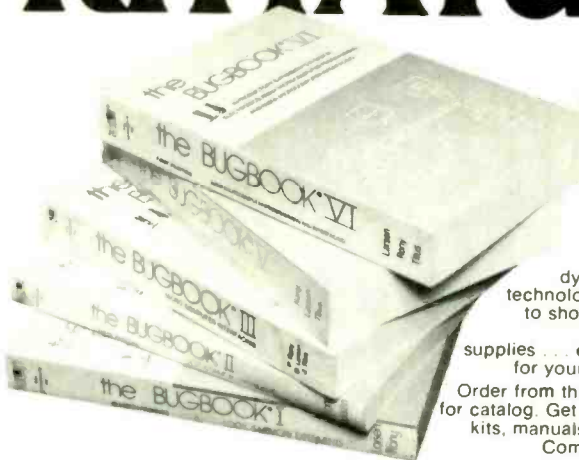

The Computer Depot is your single source for kits which teach the dynamics of computer technology... and manuals to show you how. We also carry tools and supplies... everything you need for your computer projects. Order from the list below. Or mail for catalog. Get your "Kittature"... kits, manuals and tools... from Computer Depot, today.

FAIRCHILD TECHNOLOGY KITS

<input type="checkbox"/> FTK 0001 0.5" Common Cathode Digit	\$ 1.75
<input type="checkbox"/> FTK 0002 .05" Common Anode Digit	1.75
<input type="checkbox"/> FTK 0003 .357 Common Cathode Digit	1.65
<input type="checkbox"/> FTK 0004 0.8 Common Cathode Digit	3.40
<input type="checkbox"/> FTK 0005 0.8 Common Cathode Digit	3.40
<input type="checkbox"/> FTK 0100 Clock Calendar with Radio Applications	35.00
<input type="checkbox"/> FTK 0101 6-Digit Wall Clock/Calendar	55.00
<input type="checkbox"/> FTK 0106 Auto Clock Calendar	40.00
10% OFF ALL TTL, including 7400 #s L, S, H and LS	
<input type="checkbox"/> E & L SK10 Breadboard Socket	SAVE \$1.50 15.00
<input type="checkbox"/> IMSAI 8080 Computer Kit	599.95
<input type="checkbox"/> Motorola MEK 6800 DII Computer Kit	235.00
<input type="checkbox"/> Vector Photo-resist Printed Circuit Kit	12.75


... THE BOOKS THAT SHOW YOU HOW!

<input type="checkbox"/> MicroComputer Primer	\$ 7.95
<input type="checkbox"/> E & L Bugbook Vol III	14.00
<input type="checkbox"/> E & L Bugbook Vol I & II	15.00
<input type="checkbox"/> E & L Bugbook Vol V & VI	19.00
<input type="checkbox"/> Understanding MicroComputers	9.95
<input type="checkbox"/> MicComputers at a Glance	9.95
<input type="checkbox"/> Osborne Vol I Basic Concepts	7.50
<input type="checkbox"/> How to Program MicroComputers	8.95
<input type="checkbox"/> TTL Cookbook	8.95
<input type="checkbox"/> Computer Technicians' Handbook	8.95
<input type="checkbox"/> Build Your Own Working Robot	5.95

computer depot, inc.

"Making Efficiency Economical"
3515 West 70th Street, Minneapolis, MN 55435
Phone: (612) 927-5601

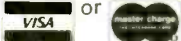RUSH me the items I have checked above. I have enclosed my check in the amount of \$ _____ (Or, credit my




or _____ account No.

I want to see more. Please SEND my FREE catalog.

NAME _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____

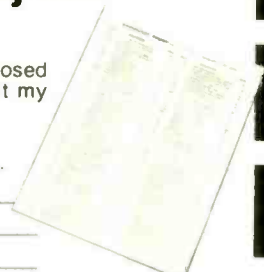

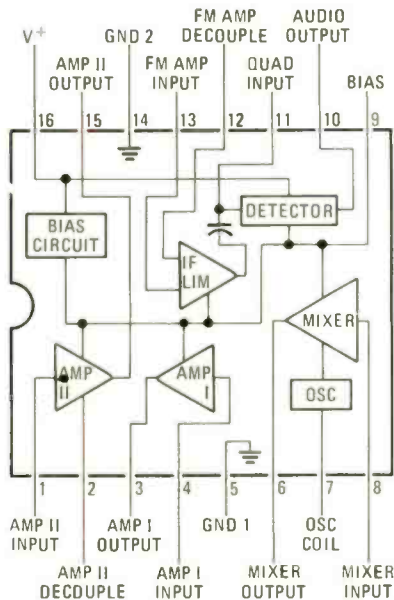


FIG. 5-- μ A721 PERFORMS most of the functions required for a complete AM/FM radio.

For additional details, write to Fairchild Camera and Instrument Corporation, 464 Ellis Street, Mountain View, CA 94042.

Another radio circuit

SGS-ATES Semiconductor Corp. also has AM/FM integrated circuits—the TDA1220 and TDA1230. The TDA1220 has an FM IF amplifier-limiter, an FM detector, and an AM RF amplifier, mixer, oscillator, IF amplifier and detector. The FM limiting sensitivity is 30 μ V, the amplitude modulation rejection (AMR) is 50 dB and the S/N ratio is better than 60 dB.

The TDA1230 goes further with an AF power amplifier that is driven from the on-chip FM detector or from an external audio source.

Voltage regulator

Silicon General's SG1532, SG2532 and SG3532 precision general-purpose regulators are substantially improved versions of the industry standard SG723. The SG1532 has a minimum required input voltage of 4.5 compared with the SG723's 9-volt specification. Lower voltages can be sustained across common 5-volt regulators, reducing the dissipation.

The SG1532 has thermal shutdown and current-limit protection. The IC is protected even if an external pass transistor fails. A sense voltage of only 89 mV is needed to current-limit the SG1532 compared with 650 mV for the SG723. A series-current sense resistor is inserted in the output current path to trigger the current-limit protection circuit. At 650 mV and, for example, 10 amps, the sense resistor dissipates 0.65×10 or 6.5 watts—a lot of wasted energy. Eighty mV reduces the number to 0.08×10 , or only 800 mW.

The older SG723 design uses a Zener
continued on page 101

Presenting
your
portable
automatic
solid state

“JOB
HOPPER”



Now, nobody likes to be called a Job Hopper, but the new, patented TF46 Portable Super Cricket can literally help you hop from job to job through solid state circuits faster than any other transistor tester on the market today. For the first time you can automatically analyze 162,000 different transistors and FETs, in or out of circuit at any job location in the world. Here are four reasons why.



It's 100% automatic.

Connect the test leads any way you want right in circuit and rotate the large permutator knob until the Cricket “chirps”. Read any transistor or FET as Good or Bad on the meter with the patented phase-inversion automatic Cricket test. It even identifies the transistor leads! It virtually thinks for you.



It takes no set-up information.

None at all. It tests over 162,000 transistors and FETs with the same, simple test, and can easily be used by a non-technical maintenance person.



It provides Leakage & Gain tests to completely analyze any transistor or FET.

The only portable tester that includes transistor Beta, FET Gm, and full leakage checks to totally check all parameters, and catch troubles other miss.



You can now test solid state circuits anywhere.

The TF46 is fully battery operated for the field, or AC operated for the bench with the optional 39G90 Power Adapter. You know what else? The TF46 automatically turns itself off after 10 minutes of testing in the field to save the batteries.

Hop to it. Call your local Sencore Full Line Promotional Distributor, or order your TF46 Job Hopper with the coupon below.

SENCORE 3200 Sencore Drive, Sioux Falls, So. Dak. 57107 (605) 339-0100
In Canada: Superior Electronics

I WANT TO BUY IT. Send _____ TF46s
to me at \$225 each.
 Check/MO enclosed. Send C.O.D.
Also send:
____ PA208 Power Adapter \$9.95
____ 39G85 Touch-Test Probe \$10.00

I WANT TO TRY IT. Have my nearest
Sencore distributor bring the TF46 to me.

SEND FULL SPECIFICATIONS.

NAME: _____
COMPANY: _____
STREET: _____
CITY: _____
STATE: _____ ZIP: _____
PHONE: _____

CIRCLE 8 ON FREE INFORMATION CARD

UNUSUAL CLOCKS

continued from page 45

count down (pin 10 low) from its loaded count each time the clock (pin 15) receives a positive-going signal.

The carry output of IC6 turns off D10 (which has been grounding the bong DC amplifier, section D of IC7) and puts a high input on NAND gate C (pin 6) of IC4. At the count of 8 of IC2 counter A, the other input to pin 5 of gate C goes high, its output goes low and D8 stops conducting. On the ninth count of counter A (8 and 1), diodes D7 and D8 are both reverse-biased and the bong generator is allowed to strike by enabling section D of IC7. On the very next count (0), diodes D7 and D8 are grounded, disabling the bong generator. Also, line 8 of counter goes low, so the gate C output goes high, clocking IC6. This subtracts one count from the preset total loaded in from IC5. Each time the pendulum swings into position V on count 8, the bong strikes once until the IC 6 count has gone down to 0. At this point, the carry line goes low, D10 conducts and the bong generator is disabled.

To achieve the bong sound, the bong DC amplifier (IC7-d) is enabled only when diodes D7, D8 and D10 are all turned off (with positive voltage on the cathode). When this happens, capacitor

C9 is allowed to charge through R9, a portion of R16 and D12 to a voltage level controlled by duration potentiometer R16. The charge on capacitor C9 controls the output of section D, which, in turn, controls the gain of section B through D14, R21 and R23. As the charge bleeds off capacitor C9, the section B output drops proportionally, giving a sustain effect and creating a bell-like sound through the speaker.

Tick-tock circuit

In regular operation, each time the pendulum swings to position Y on the count of 2 from counter A, capacitor C6 receives a positive charge. This charge remains on C6 during the count of 3, but on the count of 4 (the second count in position Z), C6 is suddenly grounded. This negative-going transition is inverted by IC3-f, and a short positive pulse is applied through D15, which turns on AC amplifier B of IC7, allowing a short toneburst to pass into the audio output section. The resulting sound resembles a tick. Similarly, on counts 6 and 7, the counter line 2 is high and capacitor C6 charges; on count 8 (the first count of pendulum position V) line 2 goes low, capacitor C6 discharges and causes another tick. There is actually no tock sound—just two ticks spaced 0.8 second and 1.2 seconds apart in the 2 seconds it

takes for the pendulum to swing back and forth.

The tick-tock is disabled when the bong is about to sound so that the bong sound is clean. The tens-of-minutes segment G transition on the hour triggers the set input of IC6 described earlier, and the carry output goes high. Since the 60-Hz count from the power line may result in the pendulum being anywhere in its swing at this instant, the carry-output high is inverted by section IC3-d and this negative-going transition is passed through C5 as a negative-going pulse to one input of NAND gate B of IC4. This results in a momentary high output of gate B, which resets counter A of IC2 to 0. Also, because inverter D now has a low output, diode D9 conducts, grounding the tick command from inverter F until IC6 completes the bong counting and the carry output goes to its normal low state.

Although the instructions are detailed and complete, this is not a kit for beginners, and it will take an experienced builder at least 10 hours to assemble it. But you really *have* something when you're finished—a large mantelpiece clock that displays the time digitally, has a swinging pendulum and tick-tock, and a bong that counts out the hours. *Bullet Electronics, Box 1944E, Dallas, TX 75219.* *(continued next month)*

OVERHEATING RESISTORS

I do get the weird ones! This Sanyo 51C51R came in with no picture and no sound. The voltage on collector Q931, the voltage-regulator pass transistor, is +131; on the emitter it is only -7.7. I checked, and nothing seemed wrong. With the set on, resistors R982 and R983 became hot enough to melt solder. (There are shunt resistors across the regulator transistor.) Error amplifier Q921 was bad. I replaced it, but now the circuit breaker cuts off! The rectifier diode is OK, etc. What's going on?—J. N., Houston, TX.

Everything is OK up to that regulator transistor. The shunt resistors overheat because collector Q931 obviously is not conducting at all. In normal operation, the transistor should carry most of the current. Disconnect the load on the +120-volt source. Remove the 1-amp fuse and connect a current meter across it. The normal current is 700 mA.

Check the error-amplifier circuit. It contains two transistors, and when that one went bad it could have damaged the bias resistors, etc. Also check the horizontal-output transistor to see if it has shorted.

AGC LOCKOUT

This Zenith 14N29Z showed an AGC lockout when the channels were changed. It stayed out for 3 to 5 seconds and then it came on. The AGC voltages read strangely. The AGC goes to +25 volts and then

slowly drops back. Checking the resistors in the AGC line gave no results. The AGC control showed hardly any range; the picture remained light. Checking the AGC keying pulse showed it was OK. The control grid voltage of the AGC tube showed far too much positive. Oh, oh! This voltage comes through a VDR.

When I freeze-sprayed the VDR the voltage jumped back to normal. I heated it, off we went again. Just for fun, I checked the resistance of the VDR—it varied (hot and cool) from 20 megohms to infinity. When I replaced the VDR, the set worked. This is Zenith part No. 63-5494, and you must be sure to get the right one! For a test, I replaced it with a 7.5-megohm resistor, and the set worked much better.

(This is a condensation of a page and a half of lab notes from my own bench!—Service Editor)

PROBLEMS GALORE

Here's an astonishing assortment of coincidences in a good old chassis:

In this Zenith 16Z25, cathode current in the 17DQ6 is 20 mA. The tube is good, the grid is very sensitive when touched with VTVM, and the 470,000-ohm grid resistor is open.

The raster shows a short, narrow, heavy shading from left to right. Is the filter open? Yes. This is a 10 μ F on B+ voltage. I replaced it. Result: a full blank raster but no sound.

The second IF voltages are all off.

Resistor R32 (120,000 ohms) to ground is open. The voltages are now OK. But there's no picture! I traced this to the radio-frequency AGC. Grounding the AGC on the tuner overloads the picture. Checking the RF amplifier shows that two 120,000-ohm resistors are up to more than 500,000 ohms each. The set works now, but warms up very slowly. I finally find that a 3CB6 tube was used instead of a 4CB6 tube in the IF. End of story!

BREAKER TRIPS, RESISTOR BURNS

When I turn on this Magnavox T-995-02, I get audio and the high voltage starts to come up. Then the breaker trips out and the 2200-ohm resistor R20 on the video board begins to burn up. I can't leave it on long enough to find out anything. Any ideas or tests?—J. S., Levittown, PA.


We've got one clue: Resistor R20 is burning up. This resistor is in the supply to the ABL (Auto Bright Limiter) circuit, and it comes from the return lead from the high-voltage tripler. Obviously, this voltage is far too high; it should be about +24 volts. Here's a check: connect the voltmeter to terminal 11 on the video board and turn the set on. If this voltage reads way above 24, this will confirm your guess.

It sounds very much as if the high-voltage tripler breaks down when the high voltage reaches a given value. Disconnect the black lead from the flyback to the tripler and recheck. If everything else works try a new tripler.

STATE OF SOLID STATE
continued from page 99

diode reference, while the SG1532 has a lower noise band-gap reference.

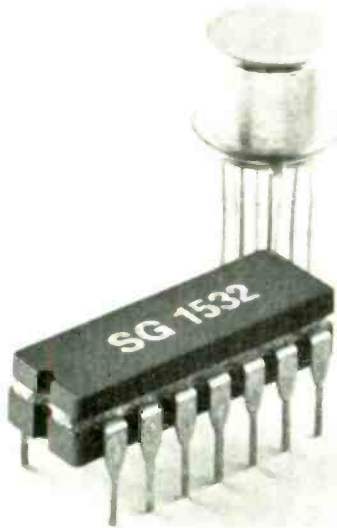Line regulation is 0.01%-per-volt maximum, and the output current capacity is




SILICON GENERAL'S SG1532 VOLTAGE REGULATOR

a minimum of 100 mA. The price is \$1.10 per unit in quantities of 100. Silicon General, Inc., 7382 Bolsa Avenue, Westminster, CA 92683.

Schottky rectifiers

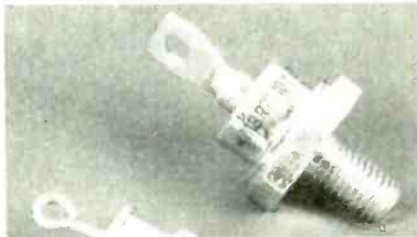Schottky rectifiers are ideal for power rectification because of their lower forward voltage and the resulting lower power dissipation. The 17-device MBR7520 family from Motorola has a greater trans-




SCHOTTKY RECTIFIERS FROM MOTOROLA

ient capacity than other rectifiers on the market. The diodes have a forward-current rating from 25 to 75 amp and have reverse voltage ratings up to 45 volts. Most devices in the series have dV/dt ratings of 100 volts-per- μs .

At a 100°C case temperature, 70-amp forward current and 45 volts, test units have been subjected to 8.3-ms, 1300-amp pulses once-per-minute, with no failures. The diodes recover from transients above the operating voltage specifications that drive them into temporary avalanche breakdown.

The rectifiers are mounted in DO-4 and DO-5 stud packages. Additional data is available from Motorola Semiconductor Products, Inc., Box 20912, Phoenix, AZ 85036. R-E

Probe the book for Probes.

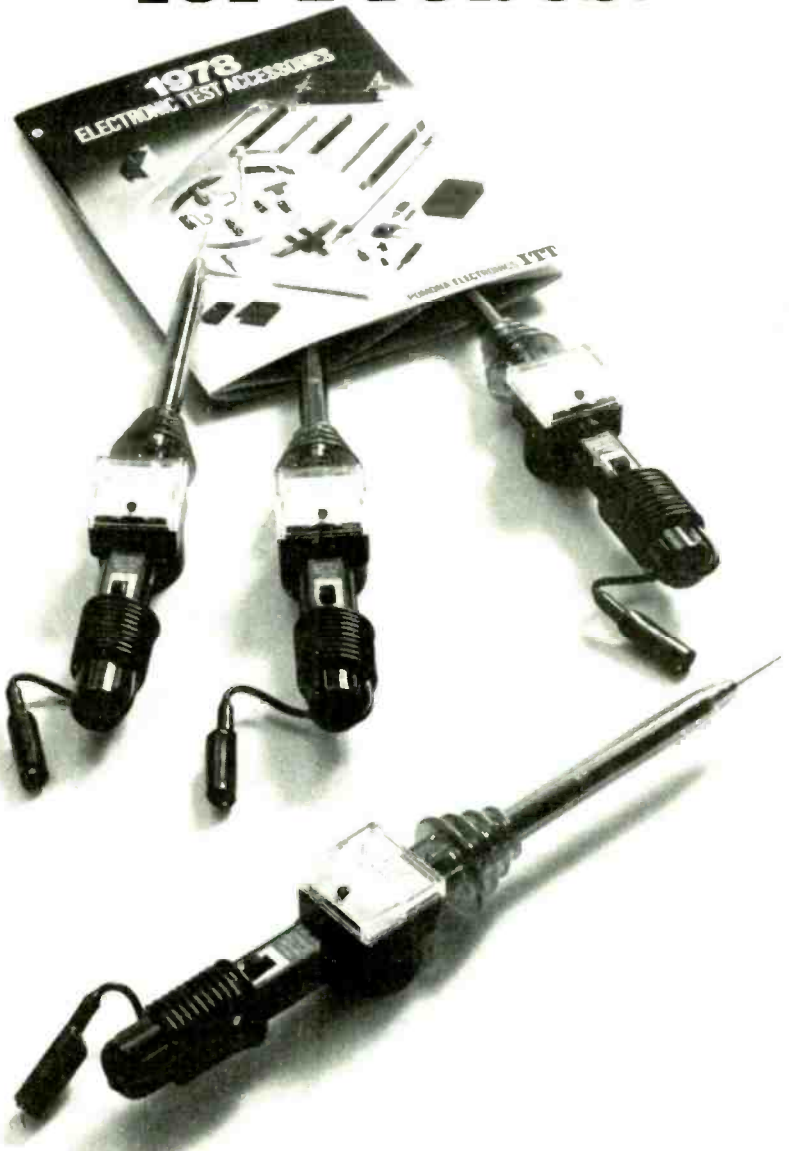

If high voltage testing is a problem, probe our 90-page catalog for the answers.

You'll find five different models of ITT Pomona Electronics high voltage test probes, along with complete applications information, illustrations and specifications.

They're designed for quick, convenient troubleshooting of a multitude of high voltage sources, including television, electronic air cleaner systems, microwave ovens, neon signs, and more.

And they're built to high quality standards, yet priced so low that every serviceman can carry one.

We perfected and introduced the first probe of this type more than a decade ago. And due to its popularity, we've been adding new models ever since.

Send for free catalog or see your favorite electronic parts distributor. See our pages in EEM.

AVAILABLE THROUGH YOUR FAVORITE ELECTRONIC PARTS DISTRIBUTOR

ITT POMONA ELECTRONICS

1500 East Ninth St., Pomona, Calif. 91766
Telephone (714) 623-3463 • TWX: 910-581-3822



CIRCLE 107 ON FREE INFORMATION CARD



FOR PROFESSIONALS . . . and those who want to be

Easy programs of service training you can pursue at home or shop. Unique. Broadly illustrated. Written in famous *Easi-Read*™ style. Practical, fast-paced, easy-to-learn upgrading for student and longtime technician, whatever your specialty. Expand and deepen your professional competence, and boost your personal and business earnings.

THE KEY: Forest Belt's Service Training MONOGRAPHS

Every MONOGRAPH deals thoroughly with its subject. No sketchy, glib abstracts of how things work; but deep, detailed explanations and illustrations that show you explicitly how to understand, analyze, troubleshoot, and repair—how to be a crackerjack technician. Fix just one extra set, faster and better, and it finances your entire MONOGRAPH subscription, in any category.

Introductory MONOGRAPH: "*Easi-Way*" Solutions for Electronics Math and Formulas." You won't believe this MONOGRAPH until you see it. Using an uncomplicated calculator, you can solve virtually any electronic problem in *minutes*, even in *seconds*. New insights to formula-handling; you DO NOT have to know algebra! Covers formulas in the FCC License exams, parallel resistance, frequency, resonance, decibels, dozens of others. All are easy with this unique method. Follow direct step-by-step rules. Even if you're good at math, this technique saves a world of time and effort.

SIX CATEGORIES TO CHOOSE FROM

A—ELECTRONIC BASICS—Applied fundamentals, more for experienced technicians than for beginners. Instead of expounding raw theory, these MONOGRAPHS guide you to everyday, practical understanding and application of vital electronic principles. Example: "*Easi-Way*" Solutions to Electronics Math and Formulas"—the slickest key you will ever find to worrisome formulas on the FCC Exam and for countless bench service problems.

B—SERVICE BUSINESS ADMINISTRATION—As experts know, you can generate as much profit by successful management as by expert servicing. This essential MONOGRAPH series reveals shortcuts to the ways professional managers assure profits. Step-by-step, up-to-date techniques. You need not be an accountant, nor spend all your time managing, to draw a healthy income from a modest-size servicing business.

C—CB RADIO SERVICING—Millions of CB radios out there need repairs. But low selling prices squeeze service profits . . . unless you really know the ropes. These MONOGRAPHS lead you to understand for sure how key CB stages work and exactly how to troubleshoot and repair even the tough ones. Phase-locked loops, single-sideband, digital ICs, keyboard entry, all the new stuff you can't afford not to know.

D—FM TWO-WAY RADIO SERVICING—To FM is where serious communications customers go: Business Radio, Land Mobile, soon even Personal Radio (CB). From this MONOGRAPH series, you learn the professional techniques that are peculiar to FM communications radio, how the stages operate, how to adjust and repair them, how to find defects promptly when they arise.

E—MODERN VIDEO SERVICING—The television servicing business has NOT gone downhill, except for technicians who fail to keep up with the advances. Transistors, integrated circuits, digital technology, automatic tuning and color correction, video games, home video players/recorders—all respond easily to modern methods in this group of MONOGRAPHS. You'll discover that many of today's best techniques are faster, simpler, and more easily understood than those used so long for older TV receivers.

F—KNOW YOUR TEST EQUIPMENT—Whatever kind of electronic gear you service, test instruments spell success—if you know how to use them well. This MONOGRAPH series shows you. Example: "Triggered Scopes: Eight Hours to Familiarity." Understand spectrum analyzers, logic testers, and other instruments you cannot do without if you plan to remain in consumer electronics servicing. Make test equipment work for you, and earn you money.

Satisfaction Guaranteed. You may cancel your subscription anytime you wish. We will rebill copies that have been sent to you, at the single-copy price plus \$1 per shipment, subtract that from your subscription payment, and refund the remainder.

Order this introductory MONOGRAPH separately if you want proof. It offers a fine example of the unique training approach awaiting you in all **Forest Belt's Service Training MONOGRAPHS**. They do not just rehash stuff you could find in old books and magazines. Every MONOGRAPH brings you original, carefully developed, thoroughly tested ways and means of servicing, of running your business, of utilizing new tools and equipment. You will find your MONOGRAPHS subscription an indispensable servicing tool, and a valuable training device for yourself and your technicians.

Two primary goals of any successful training program:

To keep you on top of electronics, so you cannot be edged out by competition or better technicians

To boost your ability to fix sets, which brings you more profits and better wages

All **Forest Belt's Service Training PROGRAMS**, including these MONOGRAPH series, stress these two goals. Our PROGRAMS bring you up-to-date training that is practical—training you can put to work immediately—training which fulfills our motto that

Learning and *Earning* BELONG TOGETHER!

Only By Subscription

Published approximately bimonthly (six per year) in each category. Save money by subscribing to all six categories (next 36 MONOGRAPHS).

- I don't want to miss any **Service Training MONOGRAPHS**. Enter my subscription immediately. Begin with No. 28A0101 "*Easi-Way*" Solutions for Electronics Math and Formulas." Send future MONOGRAPHS in categories checked, as they are published.
I enclose \$45 each for these categories:
A B C D E F
(next 6 MONOGRAPHS in each category checked)
 \$250 for all six categories (next 36 MONOGRAPHS)

- Let me see. Send only MONOGRAPH No. 28A0101 "*Easi-Way*" Solutions for Electronics Math and Formulas."
I enclose \$11 (\$8 single-issue price plus \$3 per-order handling/postage)

- Show me more. Send only the next MONOGRAPH in category indicated below
I enclose \$11 for each category checked:
A B C D E F

Send check or Money Order. No COD.
In Canada, add 20% to all prices.

Name _____ Age _____

Address _____ Phone _____

City _____ State _____ Zip Code _____


- Send bulk-subscription price sheet for school/association orders.

Name of School or Association _____

MAIL TO: Forest Belt's Service Training MONOGRAPHS
P.O. Box 88120 Indianapolis, IN 46268

increase board density and/or duplicate a double-sided PC board. This is the only system we have seen with this capability. Some of the possible Vector system variations are quite interesting, and among the available accessories are adapter pins for larger lead-wire sizes and a jumper wire kit.

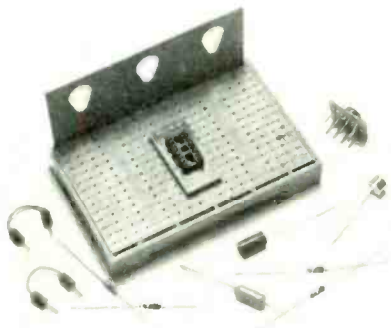The final breadboard system to be examined is new in the United States. Having been used for some time in England, it is being imported and distributed by Saxton Products. This system is based upon modules called DeC's, and does *not* follow the usual .1 X .1-inch tie-point spacing. Each DeC module mea-




T-DeC WITH IC SOCKET mounted on adapter.

sures about 3 X 5 inches, and is constructed so that two or more DeC's can be locked together to form a single unit of any size.

There are three types of DeC's in this system: The *S-DeC* is for discrete circuits and has 70 tie points. The *T-DeC*, with 208 tie points, is used for discrete circuits with some IC's and requires IC sockets mounted on a special adapter sockets that have the correct pin spacing to fit the *DeC* boards. The *Micro-* or *U-DeC* is used for IC circuits, and comes in Type A (requiring IC sockets) and Type B (built-in IC sockets).

The Saxton DeC's are sturdy and well constructed. They do not permit as high-density breadboarding as the other systems. However, their unusual tie-point pattern permits a somewhat simpler transition from schematic to breadboarded circuit. They also have another advantage, which we'll see when we get to the prototyping section in this article. Several accessories are also available.

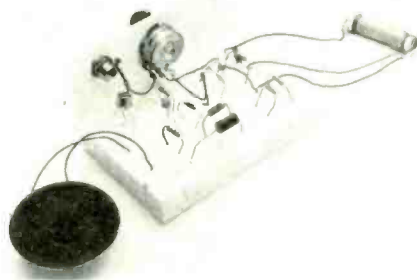Systems with indexed boards provide a facility that becomes more useful as the complexity of the circuit increases. For example, you can note on the schematic exactly where connections are made just by jotting in B3 or K48, etc. This can save time when you are modifying the circuit as you go along. It is also possible to code the index indicators on the schematic



S-DeC PROTOTYPING BOARD for discrete circuits.

before you assemble the circuit. In addition to this advantage, the indexing also

helps to eliminate wiring errors.

Finally, you should note especially the wire kits that are available. I had a little box of random length and color wires and thought this was as good as anything. More recently, however, I have been using one of the jumper-wire kits. These jumper wires come in various colors and lengths (in 0.1-inch multiples) and they can be used to connect one tie-point to another without wandering all over the board or arcing through the air.

Next month, we'll take a look at the various prototyping systems and wiring techniques. We will also discuss how to select the best method for building your own circuits. **R-E**

WE PUT THE WICK WHERE IT BELONGS


IN A UNIQUE, BUILT-IN DESOLDERING TOOL—YOURS FREE, AS A LIMITED-TIME INTRODUCTORY OFFER TO SD5.

Imagine having desoldering wick, right where you can get at it fastest, when you need it most... while you're soldering. It's our new patent-pending, refillable SD5 solder/desolder system with 2½ inch heat-resistant, telescoping Teflon* probe.

Snapped right into the center of a pound spool of our high quality 16, 18 or 21 gauge MIL-spec solder is D5—our easy-to-use desoldering tool. D5 contains 5 feet of pure copper wick that lets you see the absorption of solder... so you never overheat boards or components by working with a used portion of wick. Its non-activated, pure water-white rosin flux coating quickly removes all solder, without corrosive residue.

Nothing beats the D5 dispenser tool for easy desoldering without

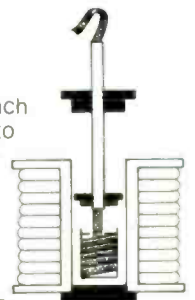burnt fingers. Its 2½ inch probe reaches right into tight areas. And by applying tension to the probe, you can shape or "web" the wick to provide a greater absorption surface. You also use less wick, dispensing the right amount as you need it.




Modular construction—D5 tool is removable. 2½" probe snaps into wick refill.

SD5 is the total system for maximum soldering/desoldering efficiency. Alone, the D5 tool is perfect for times when you want to pocket the wick and leave the solder behind. And D5 is also refillable... just snap out the Teflon* probe and plug in a D5 refill, available in two gauges—.10 inch and .06 inch.

The Chemtronics modular solder/desolder system can be purchased separately as half or one-pound spools of solder, D5 desoldering tool and D5 wick refill. Or as a complete SD5 unit with free D5 desoldering tool. Take advantage of this limited-time offer at your Chemtronics distributor now.



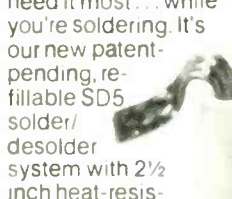Precision application even in high density circuits



Snap out, pocket D5



FREE!
\$2.45 VALUE!

*Reg. DuPont Trademark




CHEMTRONICS INC.

WHERE CHEMISTRY MAKES ELECTRONICS WORK BETTER

45 Hoffman Avenue, Hauppauge, N.Y. 11787 (516) 582-3322 / (212) 895-1930

CIRCLE 92 ON FREE INFORMATION CARD

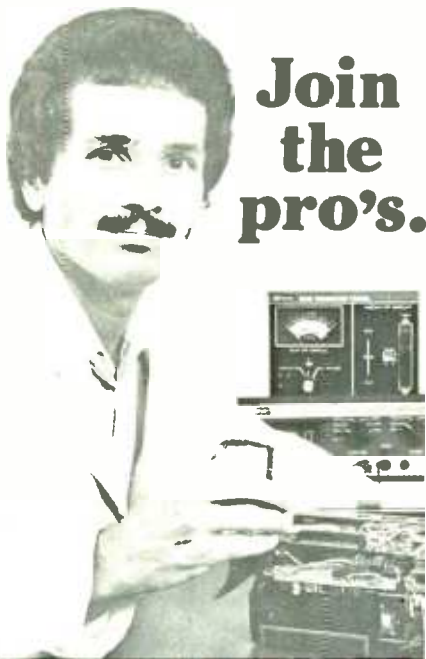

Join
the
pro's.

For technical specialists career prospects are good. Forecasts show that job openings in many technical areas are increasing.

In photography a high skill level as a camera repair technician commands a good salary and opens doors to advancement. As with other fields where the jobs are, good training is the key to success. National Camera has successfully trained photo equipment technicians for 25 years. And popular interest in new electronically controlled cameras is helping to create more opportunities than ever for you as a camera technician.

Expand your talents into a new area—work full time or part time, independently or for a wide variety of employers. Learn at home in spare time, or attend intensive training program in Colorado.

Founded 1952
Accredited member NHSC, NATTS.
Approved for Veterans' training.
Eligible institution,
Federal financial aid programs.
Resident training also available.

National Camera
Technical Training Division
2000 West Union Avenue Dept. GBC
Englewood, Colorado, 80170 U.S.A.

Return coupon today for free booklet. No salesman will call.

I am interested in Classroom
 home study Check here if veteran

Please print:

Name _____

Address _____

City _____

State _____ Zip _____

Send to: National Camera
2000 West Union Ave., Dept. GBC
Englewood, Colorado 80110

CIRCLE 35 ON FREE INFORMATION CARD

new products

More information on new products is available from manufacturers of items identified by a Free Information number. Free Information Card is inside back cover.

FUNCTION GENERATOR, model 301, is a versatile lab instrument for engineers, students and hobbyists. Unit provides three basic waveforms—sine, square, and triangular waveforms over a 1-Hz to 100-kHz range. Operates with



either a single 12-volt supply or ± 6 -volt supplies. A squarewave output is available at the sync output terminal for oscilloscope synchronization or for driving logic circuits. Price: \$119, post-paid.—Printronic, 1361 Flatbush Ave., Brooklyn, NY 11210.

CIRCLE 109 ON FREE INFORMATION CARD


WIRE TOOL, model 908-G, is five tools in one: wire stripper, bolt cutter, wire cutter; long-nose plier for pulling wire, loosening and tightening



small nuts; and wire crimper for solderless connections. Tool measures 8 1/4 inches long and has blue, plastic cushion-gripped handles. Price: \$8.90.—Channellock, Inc., Meadville, PA 16335.

CIRCLE 110 ON FREE INFORMATION CARD

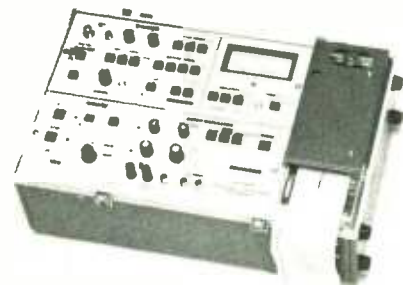FREQUENCY RESPONSE RECORDER, model LFR-5600, measures and plots frequency re-




sponse, wow & flutter, drift, voltage and temperature for a wide range of audio equipment. Unit

consists of two sections: an audio sweep oscillator (with 20-dB and 40-dB attenuation for high-sensitivity tests), and a pen recorder. Oscillator can also be used separately for direct-frequency-response readout on an oscilloscope. Chart section also serves as a DC reader to 10 mV-per-cm. The meter doubles as a sweep-frequency indicator. Unit contains standard 1-kHz and 333-Hz signal frequencies for reel-to-reel or cassette checks; selectable 25 dB, 50 dB or linear scales; external signals for response checks. The model LFR-5600, which comes in a sturdy built-in carrying case, costs \$2995.—Leader Instruments Corp., 151 Dupont St., Plainview, NY 11803.

CIRCLE 115 ON FREE INFORMATION CARD

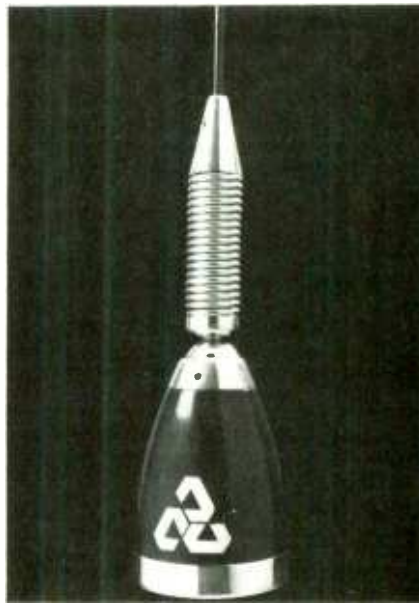BASE-LOADED ANTENNA is designed for flexibility, efficiency and long life. Quick-disconnect unit available with either trunk-clip, surface or magnetic mounts. Other features are: Uni-Axis ball joint, 500-watt pretuned coil, shielded coax




cable and in-line connector, and stainless steel whip. Suggested retail prices: trunk-clip mount, \$32.50; surface mount, \$28.50; magnetic mount, \$32.50.—Armstrong & Associates, 3635 First Ave., S.E., Cedar Rapids, IA 52402.

CIRCLE 111 ON FREE INFORMATION CARD

TEMPERATURE METER, Digitemp 100, is a lightweight instrument with easy-to-read 0.33-in. LED display and adaptable to both hand-held operations and bench work (using optional adapter/charger). With standard probes, unit measures a range of -55°C (-67°F) to $+150^{\circ}\text{C}$ ($+302^{\circ}\text{F}$) within ± 0.5 degrees accuracy. CMOS technology minimizes display drift to less than 0.1°C per 15-degree change. Meter operates on standard 9-

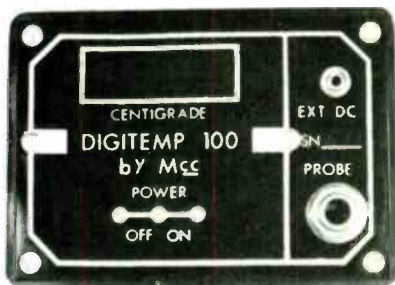volt battery; optional NiCad battery pack available. Other options include 3 standard probes—surface probe, for measuring semiconductor and heat-sink temperatures, etc.; bolt-down probe for monitoring chassis and heavy machinery; and submersible probe for measuring liquids. Also available are adapter/charger and two sizes of



cable. Unit measures $4 \times 2\frac{1}{4} \times 1\frac{1}{4}$ in. and weighs 8 oz. Prices: *Digitemp 100*, \$155 less probe; surface probe, \$25; bolt-down probe, \$27; submersible probe, \$25; adapter/charger, \$10; cables, \$16 and \$22; and battery pack, \$10.—**Mid-Continent Communications Co.**, 1103 Broadway, Oak Grove, MO 64075.

CIRCLE 114 ON FREE INFORMATION CARD


55-CHANNEL MARINE VHF-FM TRANSCEIVER, Key/Com 55, is totally synthesized to provide keyboard entry of any VHF channel (domestic and foreign) without crystals. Unit can receive 34 additional police, fire and ambulance monitoring



channels and four weather stations. Contains loudspeaker, LED readout, dimmer switch, battery meter, indicator light. *Key/Com 55* measures $3 \times 8 \times 9$ inches and costs \$659.95.—**SBE, Inc.**, 220 Alrport Blvd., Watsonville, CA 95076.

CIRCLE 112 ON FREE INFORMATION CARD

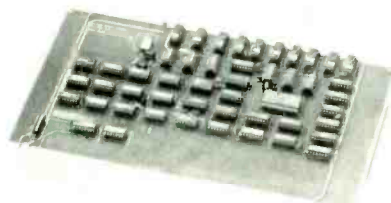HARDWARE FLOATING POINT BOARD, model FPB-B, is compatible with the Z-80 microprocessor and is specially designed for applications needing fast floating decimal calculations. Board is compatible with SBC-80 bus. The *model FPB-B* uses BCD enumeration to perform add, subtract,




multiply and divide with selectable precision up to 14 digits. Included is a paper tape version of extended BASIC. Prices: kit, \$299; assembled, \$399.—**North Star Computers, Inc.**, 2465 Fourth St., Berkeley, CA 94710.

CIRCLE 118 ON FREE INFORMATION CARD

MULTI-TESTER, model SP-170, comes in a rugged plastic case with convenient carrying handle. Multimeter ranges are: 2.5–1000 VAC; 0.25–1000 VDC; 0.05–500 mA DC; 10 amps DC; 2K–20 megohms and –20, +56 dB. Sensitivity is 20,000 ohms/VDC and 5000 ohms/VAC. Contains 21-

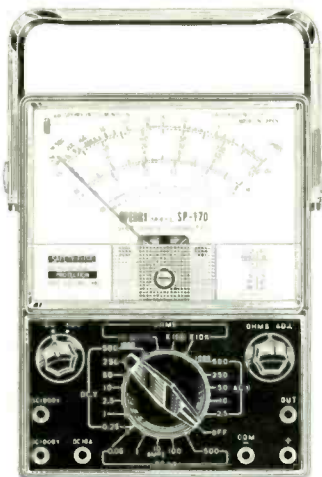
position selector switch, two-color scale, safety front panel, polarity selector switch. Unit is fuse-protected on all ranges except 10 amps DC. The *model SP-170* is battery-powered—uses one C-cell and one 9-volt transistor battery. Comes with



test leads, fuses, batteries, instructions. Weight: under 2 lbs. Prices: *model SP-170*, \$73.50; optional carrying case, *model C-11*, \$14.75.—**a.w. Sperry Instruments, Inc.**, 245 Marcus Blvd., Hauppauge, NY 11787.

CIRCLE 117 ON FREE INFORMATION CARD

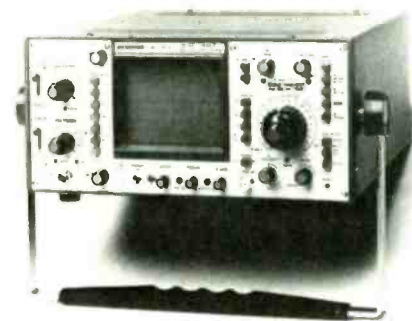DUAL-TRACE OSCILLOSCOPE, model LBO-515, is a dual-channel, 25-MHz instrument with a built-in variable delayed sweep of from $1 \mu\text{s}$ to 5 sec. Offers a 5 mV-per-division vertical sensitivity; rectangular CRT with internal graticule; selectable sync; auto, normal, single-trace and



reset modes with 20 Hz–10 kHz rejection. Features include beam rotator, Channel 1 & Channel 2 trigger with polarity inversion for Channel 2, front-panel astigmatism control, $\times 10$ magnification and 14-ns risetime. Finger-contoured handle doubles as locking bale. Priced at \$1395, the *model LBO-515* comes complete with probes and accessories.—**Leader Instruments Corp.**, 151 Dupont St., Plainview, NY 11803.

CIRCLE 116 ON FREE INFORMATION CARD

CB TRANSCEIVERS, Old Hickory, Adams (shown) and *Madison*, are 40-channel units all



providing 4-watt power output and 100% modulation capability plus standard controls. Budget—*continued on page 110*

Make Your Phone a Pushbutton Tone-Dial

Right From The Receiver



\$29⁹⁵

You simply will not believe how easy our Soft-Touch™ dial is to install. If you own your own telephone, you need only unscrew the mouthpiece and put on the Contemporary Soft-Touch™. In almost no time at all, you can be sitting in your own easy chair, at cord's length from your phone, dialing any number by just touching the number buttons.

With all controls right in the hand set, it's easy. Convenient. And best of all, it's so inexpensive. You pay one low price and the Soft-Touch™ is yours. No installation fee. No extra monthly charges—ever! Our Soft-Touch™ works on the very same tone dial principle used in all new telephones. It lets you dial a number in one tenth of the time it takes with those older spin back rotary dials.

Tone frequencies are crystal controlled, providing accuracy 6 times beyond actual requirements. The built-in microphone is similar to those found in the finest tape recorders. Clarity is better than the old carbon microphones currently used in most telephones.

Important: Soft-Touch™ is approved for you to put on your own phone. If you can unscrew a bottlecap, you can install your own Soft-Touch™ in less than a minute. But, if you lease your phone from the phone company, they may wish to install it. Regulations and telephone company charges for this service differ among local telephone companies.

It's A Portable Computer Terminal. The powerful tone generator is a perfect direct access communicator with traditional computer systems. Several banks have already begun to introduce their customers to direct computer services...right from a phone...using the Soft-Touch™ tone generating dialer.

Use It For 10 Days...At Our Expense. If not satisfied with the convenience of the extraordinary Soft-Touch™, return it within 10 days for a prompt and courteous refund of the purchase price. Soft-Touch™ is a registered trademark of 2001 Telephone Systems. Protected by U.S. Patent No. 4042793 with Manufacturer's Full Year Guarantee.

Please send me _____ Soft-Touch™ Tone Dials. My color choice is:

Black (Item 0036) \$29.95

Colors below at \$31.95 each:

Red (Item 0035)

Green (Item 0037)

Tan/Beige (Item 0038)

White (Item 0039)

Yellow (Item 0040)

Add \$2.00 each for shipping and handling

Ill. Res. add 5% sales tax

Check or M.O. Enclosed

Charge My Credit Card:

American Express

Mastercharge

Carte

Bank Amer./Visa

Diners Club

Bianche

Credit Card No. _____

Mastercharge Bank No. _____

Exp. Date _____

Name _____

Address _____

City _____

State _____

Zip _____

Signature _____

REMB-093

CREDIT CARD ORDERS

800-323-2272

Illinois: 312-595-0461

Telex Orders: 25-52568

CALL TOLL FREE

790 Maple Lane Bensenville, Ill. 60106

Contemporary Marketing, Inc.


5151781513

APRIL 1978

105


No easier, better way to learn electronics than with the HEATHKIT Self-Instruction Program!

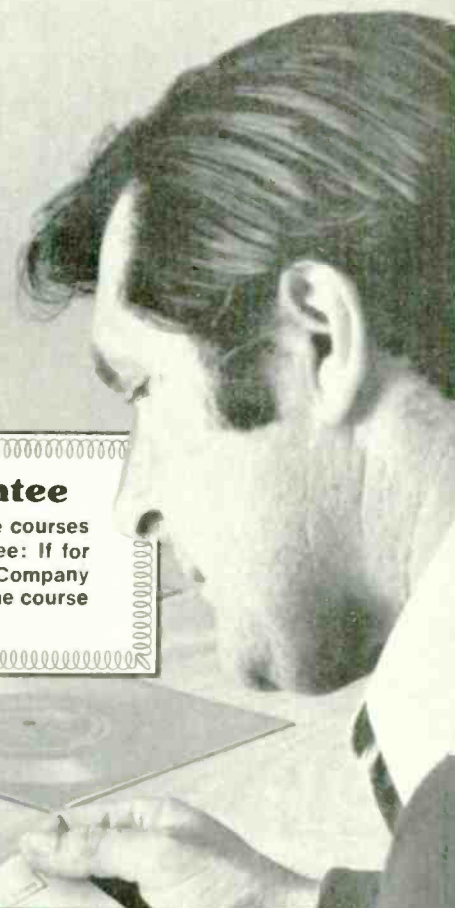It's true. Thousands of aspiring individuals just like you are moving ahead with the knowledge they've gained from these invaluable courses. Thousands more are updating what they already know. Start now on what could be a whole new world for you — the world of electronics. Learning has never been easier (or more thorough) than with Heathkit Self-Instruction Courses.



Money Back Guarantee

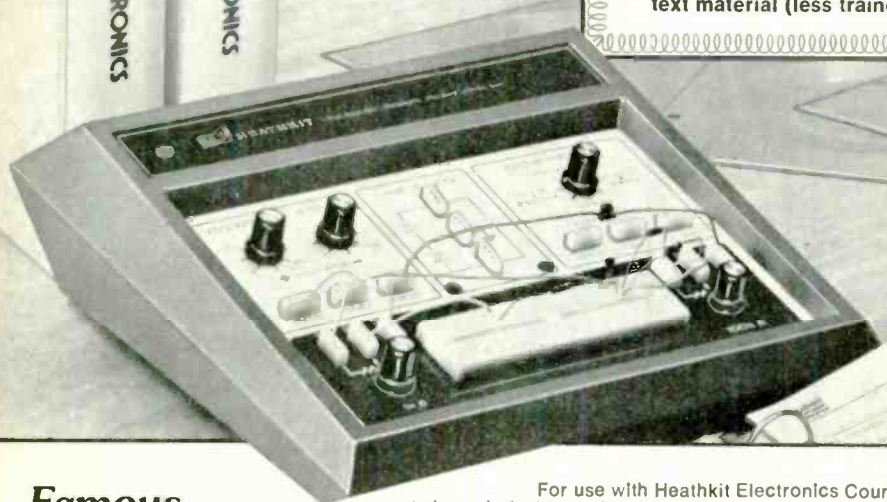The outstanding effectiveness of these courses is expressed in the Heathkit guarantee: If for any reason you're dissatisfied, Heath Company will refund the full purchase price of the course text material (less trainer).



Famous HEATHKIT EXPERIMENTER/TRAINER

For use with Heathkit Electronics Courses 1 through 4, this optional trainer helps you perform all the experiments that are supplied with the courses quickly and easily. Has solderless breadboarding sockets, dual variable power supply for positive and negative voltages, sine and square wave signal source, center-tapped line transformer. After you complete the course, the trainer is ideal for experimenting and breadboarding with your own circuit designs.

Kit ET-3100 \$59.95



What you should know about these courses

The courses and the optional trainers may qualify for a Federal Tax Deduction. Treasury Regulation 162-5 permits an income tax deduction for educational expenses undertaken to: (1) maintain or improve skills required in one's employment or other trade or business, or (2) meet express requirements of an employer or a law imposed as a condition to retention of employment, job status or rate of compensation. In many instances, your employer may re-imburse you in part or in total for taking these courses.

TRIPLE BONUS!

When you order promptly.

Buy Any Single Course with Trainer and —
SAVE \$9⁹⁵

Buy Courses 1 thru 4 with Trainer and —
SAVE \$29⁸⁰

Get This Pencil-Type Soldering Iron Worth \$7⁹⁵
FREE!
WITH YOUR ORDER

Learn electronics at your own pace – at the lowest cost.

COURSE 1: DC Electronics

The first step toward a complete understanding of a fascinating and rewarding field of endeavor. As you'd expect, Course 1 is simply and logically arranged and assumes no prior electronic knowledge. It begins at basic electron theory and goes on in detail with nothing omitted. Course 1 comes with everything you need for successful completion and, most importantly, a high degree of understanding. The only materials needed are a record player, a few basic hand tools and a VOM. Progressing at your own established pace, you learn in an unhurried environment free from pressure. Like all Heathkit courses, learning is easy with simple, step-by-step "programmed" instructions. Audio aids help emphasize the text material and an optional final exam lets you test your overall comprehension.

Essentially, Course 1 covers current, voltage, resistance, magnetism, Ohm's Law, electrical measurements, DC circuits, inductance and capacitance. In short, a complete foundation in basic electronics. Included are texts, records, and 56 electronic components for 20 different experiments. Also available is the ET-3100 Experimenter/Trainer that helps you perform projects and experiments quicker. The average completion time for Course 1 is 20 hours.

If you choose to take the optional final exam and score a grade of 70% or better, you will receive a Certificate of Completion and 2.0 Continuing Education Units (CEUs). CEUs are a nationally-recognized way of acknowledging participation in non-credit adult education.

Course EE-3101 39.95

COURSE 2: AC Electronics

The second of the Heathkit basic electronics courses which coupled with Course 1, forms the foundation for all the courses that follow. The same straightforward, simple format is utilized to teach you the theory of alternating current. Course 2 includes all the necessary material for best understanding and successful course completion. The only other materials required are a record player, a few basic hand tools and a VOM. Like the other Heathkit Self-Instruction Courses, AC Electronics is designed to let you progress at your own pace moving up when you're ready. Step-by-step, "programmed" instructions make it a rapid, easy process. Records reinforce the text material. An optional final exam lets you evaluate your understanding of the material.

Course 2 basically covers alternating current, AC measurements, capacitive and inductive circuits, transformers and tuned circuits. For best understanding, Course 2 requires the completion of Course 1 (or equivalent knowledge). Included are texts, records and 16 electronic components for 8 different experiments. The optional ET-3100 Experimenter/Trainer kit enables you to perform projects and experiments quicker. The average completion time for Course 2 is 15 hours.

If you choose to take the optional final exam and score a grade of 70% or better, you will receive a Certificate of Completion and 1.5 Continuing Education Units (CEUs). CEUs are a nationally-recognized way of acknowledging participation in non-credit adult education.

Course EE-3102 39.95

COURSE 3: Semiconductor Devices

One of the most important of the Heathkit Self-Instruction Courses and the one that reveals the technology you *must* know to stay ahead. What you'll learn in this course is absolutely necessary for understanding the solid-state devices prevalent in nearly everything electronic. Course 3 covers every aspect of a fascinating subject in simple, easily-understood terms. Everything is included except a few basic hand tools, a record player and a VOM. Progressing at a self-established pace, you move through the material as you are ready. Step-by-step "programmed" instructions make it a short, easy process. Records reinforce the text material. An optional final exam is available upon request if you wish to test your overall comprehension of the course material.

Course 3 covers semiconductor fundamentals, diodes, zeners, bipolar transistor operation and characteristics, FETs, thyristors, ICs and optoelectronics. Included are texts, records and 27 electronic components for 11 different experiments. Also available is the ET-3100 Experimenter/Trainer Kit that enables you to perform projects and experiments quicker. Prerequisites for the semiconductor course are Courses 1 and 2 or equivalent knowledge. The average completion time for Course 3 is 30 hours.

If you choose to take the optional final exam and score a grade of 70% or better, you will receive a Certificate of Completion and 3.0 Continuing Education Units (CEUs). CEUs are a nationally-recognized way of acknowledging participation in non-credit adult education.

Course EE-3103 39.95

COURSE 4: Electronic Circuits

This course lets you utilize what you've learned in Courses 1 through 3 to understand the operation of complex electronic circuitry. It's just as easy to follow as the first three courses and also includes all the materials you need except the small hand tools, VOM and record player. Like the other courses, you work at your own pace aided by the records (or optional tapes) and may test yourself with the optional final exam.

Course 4 covers basic amplifiers, typical amplifiers, operational amplifiers, power supplies, oscillators, pulse circuits, modulation and demodulation with emphasis on integrated circuits. Included are texts, records and more than 110 electronic components for 18 different experiments. The ET-3100 Experimenter/Trainer Kit is also available as an option. Course 4 requires the completion of Courses 1 through 3 or equivalent knowledge. The average completion time for Course 4 is 40 hours.

If you choose to take the optional final exam and score a grade of 70% or better, you will receive a Certificate of Completion and 4.0 Continuing Education Units (CEUs). CEUs are a nationally-recognized way of acknowledging participation in non-credit adult education.

Course EE-3104 49.95

Keep learning and growing – order today!

Prices are mail order net F.O.B. Benton Harbor, Michigan.
Prices and specifications subject to change without notice.

For advanced learning; DIGITAL TECHNIQUES

One of our most advanced courses in Digital Techniques prepares you for the world of computers and microprocessors, with particular emphasis on circuit design. Covers digital fundamentals, semiconductor devices for digital circuits, digital integrated circuits, Boolean algebra, flip-flops and registers, sequential logic circuits, combinational logic circuits, digital design and digital applications. Discusses TTL, ECL, CMOS, PMOS, NMOS; integrated circuits; SSI, MSI and LSI; ROM's, PLA's, microprocessors, computers and more. Assumes completion of Heathkit courses 1 through 4 above, or equivalent knowledge. The optional digital techniques experimenter/trainer helps you perform all the experiments in the course, and when you complete the course, build and design your own circuits. Course includes text, records and 44 parts for 24 different experiments. Average completion time, 40 hours. 4.0 Continuing Education Units and a certificate for passing final exam.

Course EE-3201 54.95
EEA-3201, Optional Cassettes 6.95
Kit ET-3200, Digital Trainer Kit 79.95

Recommended Test Equipment



You need a quality multimeter like the Heathkit IM-5284 to complete these courses. Tests and experiments are quicker and more precise with this solid-state VOM that measures AC and DC volts, ohms and DC current. The IM-5284 is easy to build and operate even for the first time kit builder and will continue to be very useful long after you've completed your Heath courses.

Kit IM-5284 37.95

NOTE:

Having completed the above courses, you will be ready to move up to our other advanced courses; Microprocessors and Computer Programming – the super technology of tomorrow.

HEATH
Schlumberger

Order Form/Agreement

Heath Company, Dept. 020-402
Benton Harbor, Michigan 49022

ED-114

Please send me items checked below and include FREE \$7.95-value Soldering Iron.

Send one course (checked below) with the Experimenter/Trainer (ET-3100) at the special price of only \$89.95 plus \$3.00 shipping and handling.

DC (EE-3101) AC (EE-3102) Semiconductors (EE-3103)

Send me the *Electronic Circuits Course* (EE-3104) with the *Experimenter/Trainer* (ET-3100) at the special price of only \$99.95 plus \$3.00 shipping and handling.

Send all four of the courses above (EE-3101, 3102, 3103, 3104) with the *Experimenter/Trainer* at the special price of just \$199.95 plus \$4.50 shipping and handling.

In addition, please send the following courses (less trainer):

DC (EE-3101) AC (EE-3102) Semiconductors (EE-3103) for just \$39.95 plus \$1.50 shipping and handling each.

Electronics Circuits (EE-3104) for just \$49.95 plus \$1.50 shipping and handling.

Send me the *Digital Techniques Course* (EE-3201) with its *Experimenter/Trainer* (ET-3200) for only \$124.95 plus \$3.00 shipping and handling.

Also send me the IM-5284 VOM kit for just \$37.95 plus \$1.50 shipping and handling.

Michigan residents add 4% sales tax.

I enclose check money order for \$_____; or, Charge to my:

BankAmericard Acct. Master Charge Acct.

No. _____ Exp. Date _____

If Master Charge, include Code No. _____

Signature: X _____
(necessary to send merchandise)

NAME (please print) _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____

Try this exciting new hobby!

Build your own electronic concert organ. It's easy. No technical knowledge required. Just follow the clearly pictured instructions of the famous Wersi do-it-yourself system. Choose from seven different models. Send \$2.00 (refundable) with coupon for colorful 104 page catalog.

WERSI



Wersi Electronics, Inc.
Dept. 24, Box 5318
1720 Hempstead Road
Lancaster, PA 17601

Enclosed is \$2.00 for my copy of your 104 page catalog.

Name _____
Address _____
City _____ State _____ Zip _____

CIRCLE 42 ON FREE INFORMATION CARD

ALDELCO ELECTRONICS COMPANY

NEW IMPROVED DIGITAL ALARM CLOCK KIT
0.5 LED Display 12 hour format
 Snooze Feature
 Elapsed Timer
 Simulated Wood Grain or Black Leather Cabinet \$24.95
 12 or 24 Hour Clock Kit. Similar to above but without Alarm or Timer features Only \$23.95
 Crystal Time Base Kit for 12 Volt DC use 4.95



COMBINATION FREQUENCY COUNTER & CLOCK. 0.4 LED Display. .00005% accuracy. 12 or 24 Hour Clock uses 8 AA Nicad batteries (not supplied). Assembled Unit \$99.95
 8 Size AA Nicad Batteries 17.50
 110 Volt AC Power Supply & Battery Charger 5.95

VOLTAGE REGULATORS

TO220 Package

Positive	Negative
7805 \$1.00	7905 \$1.25
7806 7906	7906 7906
7808 7912	7912 7912
7812 7915	7915 7915
7815 7918	7918 7918
LM309H \$1.10	
LM309K 1.10	
LM723 .55	

NEW—Interall DVM Kit 0-200 MV, expandable, PC Board part and instructions. Liquid crystal display \$39.95

LOGIC PROBE KIT DIGIPEAKE-A \$9.95

Kit of parts for power supply. Includes schematic. 5 Volt, 6 Amp \$17.95
 +15 and -15 2 Amp \$16.95

FETS 40673 1.55
 MPF102 .55

We have transistors. Send stamp for catalog.

MA 1003 National Car Clock Module
 With 3 push button switches and filters \$19.95
 New aluminum cabinet for MA 1003 \$6.95

WOW LOOK AT THIS JUMBO RED LEDS

11 for \$1.00
 Green, Yellow or Orange LEDS
 5 for \$1.00
 FND 70 CC 0.3 Display LED .49
 FND 500 CC 0.5 Display LED .89

AMATEUR TV CONVERTER
 Covers 420 to 450 AM TV BAND. Works on unused Commercial TV Channel KIT ONLY \$39.95
 ASSEMBLED \$49.95

BLINKY-FLASHER-TIMER KIT
 Includes 555, PC Board Parts & Instructions \$2.50

ACCUCYBER KIT. Uses TTL, includes IC's, sockets, Speaker, PC Board, instructions and all parts ONLY \$19.95
 MEMORY KIT. Matches above & other accucyber kits ONLY \$19.95

VARIABLE POWER SUPPLY KITs. 5 Amps 5-15 Volt DC \$6.95
 add \$1.00 per kit shipping 5 Amps 12-28 Volt DC 6.95

Visit Our Store Hours 9:00 AM to 6:00 PM Mon. to Fri. Sat. 9:00 AM to 2:00 P.M. Phone Orders accepted. Visa & Master Charge ADD 5% FOR SHIPPING. ORDERS UNDER \$10.00 add \$1.00. Foreign Orders add 15% shipping (Except Canada & Mexico) send Certified Check or Money Order in USA funds.

ALDELCO

2281R BABYLON TURNPIKE, MERRICK, N.Y. 11566
(516) 378 4555

CIRCLE 14 ON FREE INFORMATION CARD

NEW PRODUCTS

continued from page 105

priced model *Old Hickory* AM mobile radio features an S/Rf meter and ANL switch. The *Adams* AM/SSB unit (shown) has three-channel scan; S/Rf, modulation and SWR meters; RF noise blanker and gain control switches. The key features of the top-of-the-line *Madison* AM/SSB base station are: digital clock, S/Rf meter, noise blanker and RF gain control. Prices: *Old Hickory*, \$129.95; *Adams*, \$369.95; *Madison*, \$499.95.—**President Electronics, Inc.**, 16691 Hale Ave., Irvine, CA 92714.

CIRCLE 125 ON FREE INFORMATION CARD


AEROSOL BOOSTER, *Vibra-Jet*, attaches to any can of solvent/degreaser or cleaner to reach into tight areas. Rigid-construction 12-in. probe on 26-in. flexible tubing. Useful for TV servicing, and



large-scale industrial use as well as in the home. *Vibra-Jet* is available through electronics dealers, distributors and hardware outlets. Suggested retail price: \$1.98.—**Chemtronics, Inc.**, 45 Hoffman Ave., Hauppauge, NY 11787.

CIRCLE 119 ON FREE INFORMATION CARD

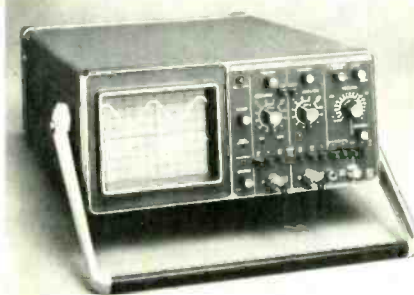PORTABLE OSCILLOSCOPE, model PM 3211, is a 15-MHz, 2-mV instrument designed for general lab, shop and field service applications. It features a comprehensive display on an 8 x 10-cm screen, measures 300 x 135 x 445 mm and weighs 7.5 kg. Contains a double-insulated pow-




er supply, automatic or level-set triggering, 18-speed timebase with vernier control. Channel B doubles as X-input and can also be inverted with ADD function to display $A \pm B$. Price: \$875, including two probes.—**Philips Test & Measuring Instruments, Inc.**, 85 McKee Dr., Mahwah, NJ 07403.

CIRCLE 122 ON FREE INFORMATION CARD

DIGITAL CASSETTE RECORDER, model STR-150, is designed for use with micro- and minicomputers, controllers and other devices requiring full remote-signal control of all tape-drive func-

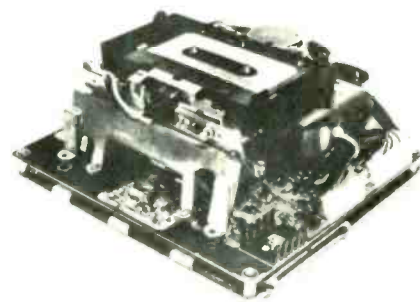tions. Unit includes read-write electronics, control and timing logic and motor control logic. Accepts any asynchronous 8-bit parallel data word. Speed Tolerate Technique (STR) assures



total unit-to-unit model *STR-150* tape compatibility as well as compatibility with all tapes recorded on STR-type recorders.—**Triple I**, 4605 N. Stiles, Oklahoma City, OK 73118.

CIRCLE 123 ON FREE INFORMATION CARD

LOGIC PROBE, *Catch-A-Pulse Experimentor*, has pulse accumulator; responds to single pulses up to 20 μ s and accumulates multiple pulse trains. Probe is compatible with RTL, DTL, TTL, CMOS, MOS and microprocessors using a 3.5- to



15-volt power supply. Thresholds are automatically programmed. LED readout displays hi, lo, bad or open-circuit logic and pulse levels. Probe comes with protective cap and detachable cord. Price: \$22.95.—**AVR Electronics**, Box 19299, San Diego, CA 92119.

CIRCLE 121 ON FREE INFORMATION CARD

DIP SOCKETS in 14- and 16-pin configurations for wire-wrapping SSI, MSI and LSI integrated circuits. Pins are three-level wire-wrap, gold-plated, .015 in. square on .100-in centers; spring



contacts are phosphor bronze leaf; and socket bodies are made of glass-filled thermoplastic.—**OK Machine & Tool Corp.**, 3455 Conner St., Bronx, NY 10475.

CIRCLE 124 ON FREE INFORMATION CARD

HI-FI SPEAKERS AND EQUIPMENT TABLES are designed like furniture—all units are constructed of solid cherry, oak or walnut, have carefully selected veneers, and are sanded, sealed and stained. Both speakers and tables come matched in four different styles (shown is Mediterranean). Tables have a wire-capturing feature that elimi-



nates unsightly wires. Speakers are available in 10-, 12- and 14-inch sizes. Tables measure 30 or 60 inches long; the larger size accommodates most color TV sets. Suggested retail prices: tables, \$125-\$180; speakers, \$180-\$360.—**Wrightwood Engineering, Div. Wrightwood Enterprises, Inc.,** 818 Evergreen Ave., Chicago, IL 60622.

CIRCLE 113 ON FREE INFORMATION CARD

TOOL DISPLAY, 90205, is designed to take the maximum advantage of floor space and minimizes set-up time. A wide variety of most-wanted tools can be displayed to full advantage; handy



out-of-stock and free catalog cards are included. Also available is separate nut/driver-screwdriver shelf (90206) with metal frame that holds drivers securely.—**Hunter Tools, 9674 Telstar Ave., El Monte, CA 91731.**

CIRCLE 126 ON FREE INFORMATION CARD


“Maybe it will go away.”
The five most dangerous words in the English language

American Cancer Society
100 Wood Avenue East, P.O. Box 5186, Metairie, LA 70002

HOBBYISTS! ENGINEERS! TECHNICIANS! STUDENTS!

Write and run machine language programs at home, display video graphics on your TV set and design microprocessor circuits — the very first night — even if you've never used a computer before!

RCA COSMAC microprocessor/mini-computer

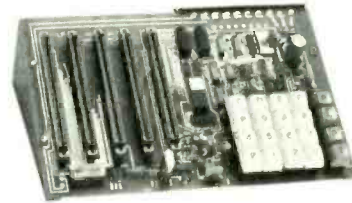

A THOUGHTFUL GIFT FOR ANYONE WHO MUST STAY UP TO DATE IN COMPUTERS AND ELECTRONICS!

ELF II \$99.95

SPECIFICATIONS
ELF II features an RCA COSMAC COS/MOS 8-bit microprocessor addressable to 64k bytes with DMA, interrupt, 16 registers, ALU, 256 byte RAM, full hex keyboard, two digit hex output display, 5 slot plug-in expansion bus, stable crystal clock for timing purposes and a double-sided plated-through PC board plus RCA 1861 video IC to display any segment of memory on a video monitor or TV screen.

Use ELF II to... **PLAY GAMES** using your TV for a video display... **CREATE GRAPHICS** pictures, alphanumeric, animated effects... learn how to **DESIGN CIRCUITS** using a microprocessor... the possibilities are infinite!

NOW AVAILABLE

- ELF II explodes into a giant when you plug the **GIANT BOARD™** into ELF's expansion bus. This powerful board includes cassette I/O, RS 232-C/TTY, 8-bit P I/O and system monitor/editor... meaning your ELF II is now the heart of a full-size system with unlimited computing power! \$39.95 kit. \$2 p&h.
- 4k Static RAM addressable to any 4k page to 64k. \$89.95 kit. \$3 p&h.
 - Prototype (Kluge) Board accepts up to 32 I.C.'s of various sizes. \$17.00 kit. \$1 p&h.
 - Expansion Power Supply. \$34.95 kit. \$2 p&h.
 - Gold plated 86-pin connector. \$5.70 postpaid.

Come Soon!
Tiny Basic
ASCII KEYBOARD* CONTROLLER BOARD* D-A, A-D CONVERTER* CABINET

SEND TODAY
NETRONICS R&D LTD., Dept. RE 4
333 Litchfield Road, New Milford, CT 06776 Phone (203) 354-9375

Yes! I want to run programs at home and have enclosed:
 \$99.95 plus \$3 p&h for **RCA COSMAC ELF II kit. Featured in POPULAR ELECTRONICS.** Includes all components plus everything you need to write and run machine language programs plus the new Pixie chip that lets you display video graphics on your TV screen. Designed to give engineers practice in computer programming and microprocessor circuit design. ELF II is also perfect for college and college-bound students (who must understand computers for any engineering, scientific or business career). Easy instructions get you started right away, even if you've never used a computer before!

As your need for computing power grows, five card expansion bus (less connectors) allows memory expansion, program debugger monitor, cassette I/O, A to D and D to A converters, PROM, ASCII keyboard inputs, controllers, etc. (soon to be available as kits). Manual includes instructions for assembly, testing, programming, video graphics and games plus how you can get ELF II User's Club bulletins. Kit can be assembled in a single evening and you'll still have time to run programs, including games, video graphics, controllers, etc., before going to bed! \$4.95 for 1.5 amp 6.3 VAC power supply, required for ELF II kit. \$5.00 for RCA 1802 User's Manual.

I want mine wired and tested with the power transformer and RCA 1802 User's Manual for \$149.95 plus \$3 p&h. Conn. res. add sales tax.

NAME _____
ADDRESS _____
CITY _____
STATE _____ ZIP _____
 Send info on other kits!
Dealer Inquiries Invited

CIRCLE 44 ON FREE INFORMATION CARD

You Can Count On DAVIS!

500 MHz & 1 GHz COUNTERS
If you need a reliable counter at an affordable price, the CTR 2 is the answer.

- 8 Digit .3" LED Display
- High Stability TCXO Time Base
- Built-in VHF-UHF Prescaler
- Automatic Dp Placement
- TCXO Std. ± 2 ppm
- Input Diode Protected
- 12V-DC Operation (Optional)
- Oven Controlled Crystal (Optional) ± .5 ppm
- Selectable Gate Times

CTR-2-500 (range: 10 Hz to 512 MHz)
CTR-2-1000 (range: 10 Hz to > 1000 MHz)

500 MHz Kit CTR-2-500K	\$249.95
500 MHz Assembled CTR-2-500A	349.95
1 GHz Kit CTR-2-1000K	399.95
1 GHz Assembled CTR-2-1000A	549.95

OPTIONS:

(02) Oven Crystal	\$49.95
(03) .43" LED	10.00
(04) 12V-DC	10.00
(05) 10 sec. Time Base	10.00

DAVIS SEE YOU AT THE DAYTON SHOW

DAVIS ELECTRONICS
636 Sheridan Drive
Tonawanda, NY 14150
716/874-5848

VISA

CIRCLE 69 ON FREE INFORMATION CARD

PAIA 8700 Computer/Controller

The Answer For... Student Hobbyist Manufacturer

8700 Processor: 6503 MPU. Wear free "Active Keyboard" Micro-Diagnostic. Extensive documentation. Fully Socketed.

Piebug Monitor: User Subroutines. Relative address calculator. Pointer High-low. Back-step key.

Cassette Interface: Load & Dump by file #. Positive indication of operation. Tape motion control.

Applications systems from \$90 (10 unit quantity)
Development systems from \$149 (single unit)

TELL ME MORE I want to see for myself that the 8700 is The Answer.

Please send documentation \$10 enclosed.
 send price lists & FREE Catalog of other PAIA kits.

name: _____
Address: _____
City: _____ State: _____ zip _____

PAIA DEPT. 4-R • 1020 W. Wilshire Blvd. ELECTRONICS • Oklahoma City, OK 73116 •

CIRCLE 20 ON FREE INFORMATION CARD

new lit

More information on new products is available from manufacturers of items identified by a Free Information number. Free Information Card is inside back cover.

TEST INSTRUMENTS, 42-page illustrated catalog includes CB testers, DMM's, frequency counters, multimeters, oscilloscopes, semiconductor and transistor testers, power supplies and many other test instruments. Specifications and features of each unit are included. Separate price schedule.—**B&K-Precision**, Dynascan Corp., 6460 W. Cortland Ave., Chicago, IL 60635.

CIRCLE 128 ON FREE INFORMATION CARD

MICROCOMPUTER SYSTEM CATALOG, *Byte Shopper*, features all kinds of microcomputer schemes, from the simplest home setup to large timesharing, multi-user systems. Each product described includes not only specifications but a complete discussion of how it works and its application. More than 50 manufacturers are represented, and almost all products are S-100 bus-compatible. Catalog is available for \$2.50.—**Byte Shopper**, Byte Shop of Arizona, Box 28106, Tempe, AZ 85282.

COMPONENTS CATALOG, 64 pages, contains a wide variety of more than 100 components and kits and features listings of surplus and replacement semiconductors. A transistor reference data listing is also included in the back of the catalog. Other items include bridge rectifiers, function generators, IC's, LED's, microprocessors, PC boards, switches, solar cells, Zeners. Also describes kits for radios, a signal injector, a timer, TV games, counters, and psychedelic lights. A handy order form is included in the back, and a separate catalog flyer with additional products is also available.—**J. & J. Electronics, Ltd.**, Box 1437, Winnipeg, Man. R3C 2Z4.

CIRCLE 129 ON FREE INFORMATION CARD

ELECTRONIC INSTRUMENT CATALOG contains 32 pages of test equipment, burglar/fire alarm systems, CB accessories and hobby projects. Test instruments include oscilloscopes, frequency counters, logic testers, DMM's,

VOM's, tube testers and an IC color generator. Also described are such devices as smoke detectors, heat/fire sensors, and a complete home-protection security system. Solid-state circuitry kits feature AM/FM radios, an electronic organ, an ESP tester, a stereo amplifier and many more.—**EICO Electronic Instrument Co.**, 108 New South Rd., Hicksville, NY 11801.

CIRCLE 130 ON FREE INFORMATION CARD

INSTRUCTIONAL BOOKLET, *A Brief Guide to Microphones*, 15 pages, uses a step-by-step approach to a basic understanding of different microphone types and features. Eight basic microphone terms are described, and an additional section deals with mike accessories.—**Audio-Technica U.S., Inc.**, 33 Shiawassee Ave., Fairlawn, OH 44313.

CIRCLE 131 ON FREE INFORMATION CARD

FREQUENCY COUNTERS, *Freq. Out.*, is a 4-page, full-color description of manufacturer's *Max-100*, a portable, 8-digit, 100-MHz frequency counter with a suggested resale price of \$134.95.—**Continental Specialties Corp.**, 70 Fulton Terrace, New Haven, CT 06509. **R-E**

CIRCLE 132 ON FREE INFORMATION CARD

THE END OF THE TOOLBOX.

The tool box is obsolete. It's being replaced by Platt's tool case. Here's why. In a tool box, tools and parts are hard to find. They get lost. Dirty.

With a Platt tool case, that doesn't happen. There's a patented one-piece pallet with pockets for each tool. Tools can be picked out and replaced without searching. Work can be done quickly and efficiently.


Platt's tool case also helps you look more professional. It comes in handsome, lightweight ABS Thermoplastic. Or rich looking vinyl reinforced by ABS Thermoplastic.

What's more, it has a 5 year guarantee. Contact us for complete information on Platt's full line of tool cases and your nearest distributor.

platt

Pat. No. 3,880,285

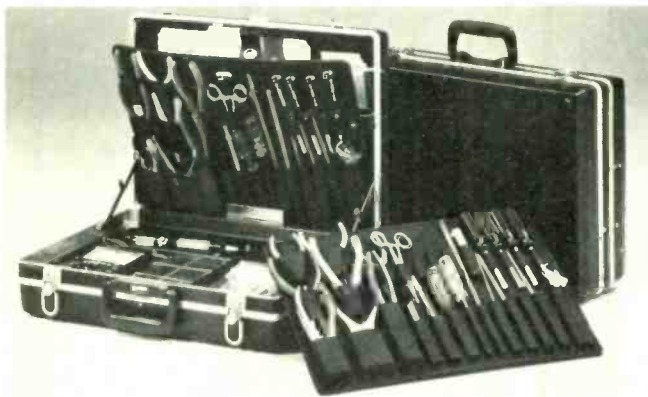Cases for business and industry.
2301 S. Prairie Ave., Chicago, Ill. 60616 (312) 225-6670



CIRCLE 98 ON FREE INFORMATION CARD

ALL TOGETHER NOW!

The acclaimed Equinox 100[™] mainframe kit (\$799) is now a complete S-100 system.

Because now there is an Equinox 100[™] I/O interface kit (\$122) that handles the hard work of interfacing all your peripherals.

And Equinox 100[™] 4K memory kits (\$109). Assembled 8K memory boards (\$188). EQU/ATE[™] editor/assembler and BASIC-EQ[™] software on cassettes.

It all goes together. It all works together. It's all together now at special system prices.

See The Equinox System[™] at your local computer shop. Call toll-free to 800-548-5311. BAC/MC accepted. Or write Equinox Division, Parasitic Engineering, P.O. Box 6314, Albany California 94706.



THE EQUINOX SYSTEM[™] When you put it together, it's really together.

CIRCLE 77 ON FREE INFORMATION CARD

books

BUGBOOKS V AND VI, by Peter R. Rony, David G. Larsen and Jonathan A. Titus. E&L Instruments, Inc., 61 First St., Derby, CT 06418. *Bugbook V*, 493 pp.; *Bugbook VI*, 490 pp. 6 × 9 in. Softcover \$9.50 each.

These two volumes combine a course in introductory digital electronics with programming and interfacing an 8080A-based microcomputer. Designed for study and guidance in performing "hands-on" experiments with a low-cost microcomputer, breadboards and available components.

Bugbook V covers programming and instruction basics, as well as digital codes, register, logic gates and truth tables. Instruction and experiments with the 7400-series TTL IC's, including flip-flops and latches, decoders, counters, digital signal gates and multivibrators.

Bugbook VI contains detailed instructions and lab experiments with instruction set, three-state busing techniques, and accumulator and memory-mapped I/O techniques. This volume also covers advanced I/O concepts and interrupt servicing. Complete appendices for both volumes are contained in the back of *Bugbook VI*.

GROUNDING AND SHIELDING TECHNIQUES IN INSTRUMENTATION, Second Edition, by Ralph Morrison. Wiley-Interscience, Div. of John Wiley & Sons, 605 Third Ave., New York, NY 10016. 146 pp. 6 × 9 in. Hardcover \$15.50.

This is a revised and updated version of an earlier popular book for engineers, technicians, designers, and anyone concerned with electronic equipment. Notice has been taken of more recent developments in electronics, such as digital circuits, and schematics have been revised to reflect these developments. Electrostatic concepts are outlined in simple fashion so that the reader can come away with a clear understanding of the common shielding errors and how to avoid them. The text is well illustrated with block diagrams and halftones.

LOGIC DESIGNER'S MANUAL, by John D. Lenk. Reston Publishing Co., Div. of Prentice-Hall Co., Reston, VA 22090. 504 pp. 6 × 9 in. Hardcover \$18.95.

This book introduces the reader to commercially available IC's that can be used for specific applications. The text and illustrations show how these IC's can be interconnected to form logic systems. Chapter 1 is an introduction to logic design; Chapter 2 describes how decoders, counters, etc., work; the remaining chapters cover such subjects as A/D and D/A converters, arithmetic units, memories, interface and other logic circuits.


SECURITY ELECTRONICS, Second Edition, by John Cunningham. Howard W. Sams & Co., Inc., 4300 W. 62nd St., Indianapolis, IN 46268. 192 pp. 5½ × 8½ in. Softcover \$5.95.

This book takes a look at how various electronic security devices and systems work, and suggests what type of system is best for specific applications.

Chapter 1 is an introduction to the various types of systems available. Modes of operation, antishooping devices, metal detectors, the use of computers in alarm systems and debugging devices are just some of the topics covered in other chapters. Included in the back of the book is a glossary of terms and definitions as approved by the U.S. National Bureau of Standards Law Enforcement Standards Lab. **R-E**

FREE catalog

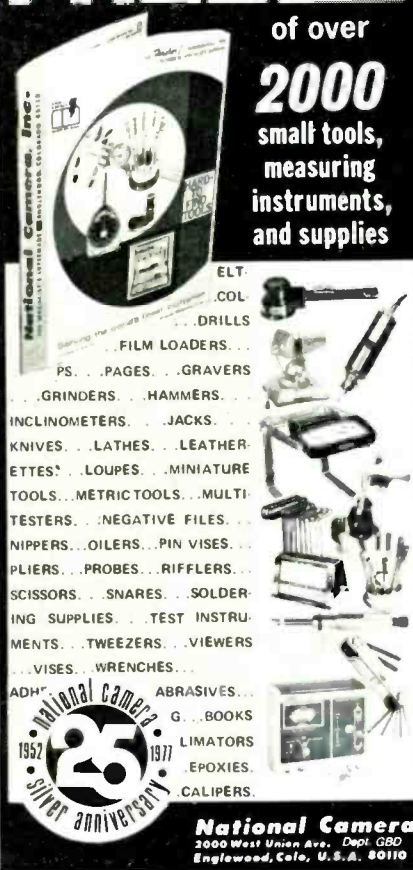of over
2000
small tools,
measuring
instruments,
and supplies



ELT.
COL.
DRILLS
FILM LOADERS...
PS...PAGES...GRAVERS
GRINDERS...HAMMERS...
INCLINOMETERS...JACKS...
KNIVES...LATHES...LEATHER-
ETTES...LOUPES...MINIATURE
TOOLS...METRIC TOOLS...MULTI-
TESTERS...NEGATIVE FILES...
NIPPERS...OILERS...PIN VISES...
PLIERS...PROBES...RIFFLERS...
SCISSORS...SNARES...SOLDER-
ING SUPPLIES...TEST INSTRU-
MENTS...TWEEZERS...VIEWERS
...VISES...WRENCHES...
ADH... ABRASIVES...
G...BOOKS
LIMATORS
EPOXIES
CALIPERS

National Camera
2000 West Union Ave., Dept. G30
Englewood, Colo., U.S.A. 80110

CIRCLE 9 ON FREE INFORMATION CARD

NEW EICO 480 TRIGGERED SWEEP 10 MHz SCOPE

100% Solid State • Includes 10:1 Probe

More Professional scope performance for your money! DC to 10 MHz bandwidth, AC and DC coupling, 11 position calibrated attenuator, 10 mV/cm sensitivity, push-button operation. Outstanding features: Built-in TV Sync Separator; Digitally controlled trigger circuits; reference baseline display; calibrated 21 step sweep speed; Fully regulated power supply; Custom Bezel for standard camera mounting. **Assembled \$425.00**

FREE '78 EICO CATALOG

Check reader service card or send 50¢ for first class mail. See your local EICO Dealer or call (516) 681-9300, 9:00 a.m.-5:00 p.m. EST. Major credit cards accepted.

EICO-108 New South Rd.
Hicksville, N.Y. 11801



CIRCLE 87 ON FREE INFORMATION CARD

**"Our whole family
helped assemble
this wonderful
Schober Organ...
now we all play it!"**



Talk about real family fun! We all worked together, for a few hours almost every day. Almost too soon, our Schober Organ was finished. Our keen-eyed daughter sorted resistors. Mom soldered transistor sockets, although she'd never soldered anything before. And it did our hearts good to see the care with which our son—he's only 12—installed the transistors. Me? I was the quality control inspector—they let me do the final wiring. And when it came time to finish the beautiful walnut cabinet the easy Schober way, we all worked at it!

Now, we gather around our Schober Organ every evening to play and sing together. Some of us play better than the others, but we're all learning—with the help of the easy Schober Organ playing courses. I might add that I'm especially pleased with all the money we saved. Our completed Schober Organ compares favorably with a "ready-made" one costing twice as much! (The five models range from \$650 to \$2850.) And we didn't even need to pay the whole amount all at once, because we were able

to buy Schober Kits a component at a time, to spread costs out. Or we could have had two-year time payments!

Families like ours have been building Schober Organs for 20 years. How about your family? You can have all the details, without cost or obligation. Just send the coupon for the fascinating Schober color catalog (or enclose \$1 for a 12-inch LP record that lets you hear as well as see Schober quality). Clip the coupon right now—and mail it TODAY!

The Schober Organ Corp., Dept. RE-173
43 West 61st Street, New York, N.Y. 10023

- Please send me Schober Organ Catalog
 Enclosed please find \$1.00 for 12-inch LP record of Schober Organ music

NAME _____
ADDRESS _____
CITY _____ STATE _____ ZIP _____

CIRCLE 72 ON FREE INFORMATION CARD

**MATHEMATICS
ELECTRONICS
ENGINEERING MATHEMATICS
ADVANCED MATHEMATICS**

These unusual courses are the result of many years of study and thought by the President of Indiana Home Study, who has personally lectured in the classroom to thousands of men, from all walks of life, on mathematics, and electrical and electronic engineering.

You will have to see the lessons to appreciate them!

NOW you can master mathematics and electronics and actually enjoy doing it!

WE ARE THIS SURE:—you order your lessons on a money-back guarantee.

In plain language, if you aren't satisfied you don't pay, and there are no strings attached.

Write today for more information and your outline of courses.

You have nothing to lose, and everything to gain!

**The INDIANA
HOME STUDY INSTITUTE**
P.O. BOX 1189
PANAMA CITY, FLA 32401

CIRCLE 11 ON FREE INFORMATION CARD

burglar—fire alarm catalog

FREE!



**MORE THAN
900 PRODUCTS**

**detectors,
controls,
sounders,
locks,
tools**

**EVERYTHING NEEDED
TO PROTECT HOME,
BUSINESS, INSTITUTION**

Huge selection of high quality professional alarm products. 64 fact-filled pages with detailed specs, diagrams, technical notes.

Products range from basic switches, controls, bells, sirens to most sophisticated detectors — radar, modulated or passive infrared, microwave, ultrasonics, ion, data links using pulse code multiplex, FSK radio, automatic phone dialers, leased line connections and display panels. Full selection of tools, relays, wire, foil, terminals, books.

WRITE FOR FREE CATALOG TODAY!

(Outside U.S., send \$1.00.)



mountain west alarm
box 10780 • phoenix, az 85064
(602) 263-8831

CIRCLE 12 ON FREE INFORMATION CARD

AUDIO OSCILLATORS

continued from page 73

Figure 4 shows another popular circuit—the L-C (inductance-capacitance) combination. Figure 4-a is the Hartley oscillator, which uses a tapped inductor and Fig. 4-b is the Colpitts oscillator, with a split capacitor. The natural frequency of either of these oscillators depends on the square root of $L \times C$. Therefore, for a 10:1 tuning range, the value of C (or L) must vary by 100:1. This is one of the major disadvantages of the L-C oscillator. Another major disadvantage lies in the size of the inductance and capacitance required to reach low frequencies. The advantage of the L-C oscillator lies in the ease with which a high-Q (high-selectivity) tuned circuit, which results in extremely pure sine-waves, can be obtained.

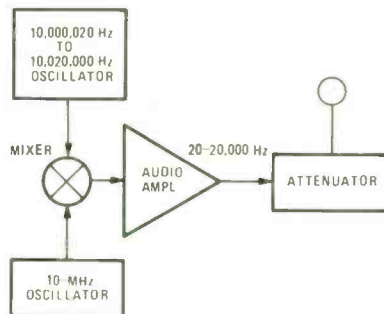


FIG. 5—THE BEAT-FREQUENCY TYPE. The audio signal is the difference—or beat—between two separate radio frequencies.

Today an L-C circuit is not often used. However, it was commonly used in heterodyning or beat-frequency oscillators, as shown in Fig. 5. This arrangement has an extremely wide frequency range. For instance, the oscillator in Fig. 5 can cover a 20-Hz to 20-kHz range, while the L-C 10-MHz oscillator frequency changes by only 2%. (Such oscillators often have frequency stability problems.)

Tuning

Two forms of frequency selection are common. One is switch-selectable decade ranges, with a continuously variable frequency adjustment within the selected decade. Such oscillators are continuously tunable and usually have a ganged variable capacitor that is adjusted to produce changes within each decade. Ranges are changed by changing sets of resistors. The L-C oscillator ranges can be changed by adjusting taps on the inductor or switching in new inductors.

Selection of discrete frequencies by switches is the other frequency selection method. Although not as common as continuous tuning, it has many operational advantages. When switched frequency selection is used, ranges are changed by selecting sets of fixed capacitors whose capacitance increases in decade steps.

Why buy a multi-capability counter for frequency-only measurements?



The 1911A multimeter makes accurate field transmitter frequency checks easy with the optional battery-pack and whip antenna.

For accurate readings in the presence of noise. Our new 1911/12A multi-counters have both trigger-level and attenuator controls.

For high resolution measurement of low frequency control tones in the period or period-average mode.

For economy. They're priced about the same as many frequency-only models, with totalize, autozero, autoranging, manual and automatic range selection, and more. Standard.

- 1911A for 250 MHz applications: \$495.*
- 1912A for measurements to 520 MHz: \$620.*

Call (800)426-0361, toll free, or write: John Fluke Mfg. Co., P.O. Box 43210, Mountlake Terrace, WA 98043.

*(U.S. price)



1912A 520 MHz model

Fluke Multimeters for Communications Service



2110-8001

CIRCLE 57 ON FREE INFORMATION CARD

CIRCLE 80 FOR DEMONSTRATION

Within a particular decade, frequency is adjusted by selecting appropriate resistors. In other words, the switched tuning technique usually inverts the role of capacitance and resistance as compared with continuous tuning.

Designing an oscillator suitable for generating fundamental audio oscillator signals involves many techniques for reducing distortion and noise to the lowest possible levels. The amplifier in the basic oscillator circuit must have extremely high gain over the entire frequency range used. The higher the gain, the greater the feedback and the lower the distortion. This amplifier must not introduce any appreciable phase shift over the oscillator's entire frequency range. Amplifier noise and hum must be reduced to the lowest possible levels. Frequency stability with component aging and temperature variations must be carefully considered. Any effect that would tend to modulate the basic oscillator signal in either amplitude or frequency must be removed, as all these effects contribute to total distortion.

Output amplifier

The output amplifier has three purposes. First, it supplies some gain to increase the oscillator output amplitude to the maximum level required. Second, the amplifier serves as a buffer, isolating the oscillator from load changes at the output. Third, it serves to reduce the output impedance of the oscillator stage to the required impedance (usually either 50 or 600 ohms). Most amplifiers used for this type of work consist of one or more Class A amplifier stages. The am-

output. A series resistor at the amplifier output yields the desired impedance. Although this limits the maximum power transfer capabilities of the amplifier, it does insure a reflectionless signal source.

Designing the output amplifier for the audio oscillator requires great care to avoid introducing hum, noise or amplitude modulation. Low noise techniques and careful shielding are routinely applied to such amplifiers. Other more advanced techniques, such as special isolating transformers, are not uncommon. Additional leveling techniques can be applied at the output amplifier, although they are more commonly applied at the oscillator.

Output attenuator

Output attenuators may vary in complexity from the very simple to the exotic. Figure 6 shows an extremely simple attenuator. The output impedance of the audio oscillator varies with the setting of the 400-ohm variable attenuator. The output impedance of this circuit may drop to nearly zero at the minimum setting.

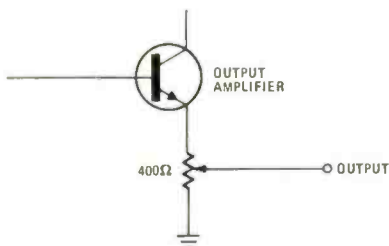


FIG. 6—AN OUTPUT ATTENUATOR that is commonly used on low-priced audio oscillators.

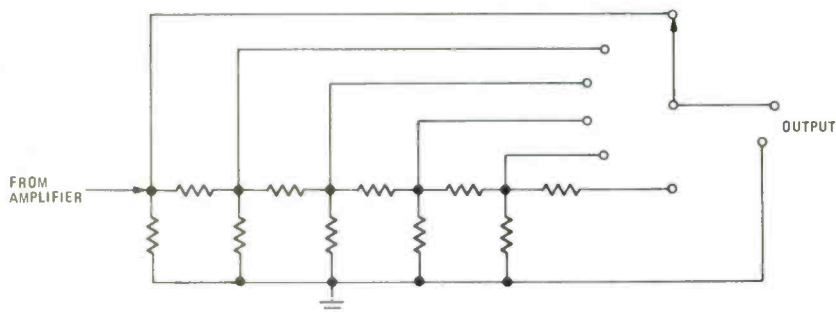


FIG. 7—THE LADDER ATTENUATOR operates in steps and maintains a constant impedance throughout its range.

plifier in common use consists of a number of stages connected to form a high-gain, wideband, low-noise circuit.

Normally, the gain of the output amplifier must be in the range of one to five. Large amounts of negative feedback are introduced to reduce the gain to this required range, which tends to improve amplifier frequency response, phase and distortion characteristics. Frequently, the amplifier output impedance, which has been reduced to an extremely low value by the large amount of feedback, is significantly lower than required at the

Attenuators like the one shown in Fig. 7 are common in more sophisticated oscillators. The continuous variable attenuation is inserted before the amplifier stages. Therefore, the output impedance does not vary as the continuously variable attenuator is adjusted. The step attenuator is of the constant-impedance type, with either 10-dB or 20-dB steps, and maintains either a 600-ohm or 50-ohm output impedance regardless of attenuator setting.

The design of the output attenuator

turn page

Now...learn computer programming faster & easier with HEATH'S BASIC PROGRAMMING COURSE!



Just **\$29.95**
plus \$1.69 shipping and handling

This self-instruction course uses proven programmed instruction methods to teach you BASIC... the most popular and widely used higher level programming language. With the help of this course, you'll learn all the formats, commands, statements and procedures... then go on to actually apply them with "hands on" experiments and program demonstrations on your own or any available computer. And unlike other courses or books on BASIC, we teach you problem solving as well as programming so you can apply what you learn. Self-evaluation quizzes and exams guarantee that you understand every detail and when you finish, you may take an optional examination to qualify for a Certificate of Achievement and 3.0 Continuing Education Units (CEU's), a widely recognized means of participating in non-credit adult education. **MONEY-BACK GUARANTEE:** If for any reason you are dissatisfied, Heath Company will refund the full purchase price of the course.

HEATH Schlumberger	HEATH CO., Dept. 020-401 Benton Harbor, MI 49022
YES Please send me your EC-1100 BASIC Programming Self-Instructional Course.	
My <input type="checkbox"/> check <input type="checkbox"/> Money order for \$_____ is enclosed. Or please charge to my <input type="checkbox"/> VISA/ <input type="checkbox"/> BankAmericard <input type="checkbox"/> Master Charge	
Account # _____	
Exp. Date _____ M.C. Code # _____	
Signature _____ (necessary to send merchandise)	
NAME _____ (please print)	
ADDRESS _____	
CITY _____	
STATE _____ ZIP _____	
ORDER TODAY — PRICE GUARANTEED THROUGH APRIL 25, 1978 ONLY!	
Price is mail order F.O.B. Benton Harbor, MI. Price subject to change without notice.	

THE COUNTERS YOU REALLY WANT



AT AFFORDABLE PRICES.

A Model for every need.

MODEL 380. 1 Hz to 80 MHz, 10 ppm	\$209
MODEL 380X. 1 Hz to 80 MHz, 1ppm	\$269
MODEL 385. 1 Hz to 512 MHz, 10ppm	\$419
MODEL 385X. 1 Hz to 512 MHz, 1ppm	\$499

Perfect for communications, CB, audio, TV and digital work, servicing and laboratory applications.

All 4 field-proven models feature full 7-digit display with automatic decimal and full autoranging. Our exclusive SPEED READ mode provides fast update (5/sec) time for easy tuning and adjusting.

Handsome, rugged metal case with brushed aluminum panel including all-angle tilt stand. (Low cost rack mounting kits for standard 19" rack also available.) All models come packaged in a plastic carrying case that protects the unit in shipment and in use.

Why settle for less than the best. See these hard-working counters at your distributor now

must insure identical performance at high and low frequencies. This becomes especially important if squarewaves are included; they contain components of much higher frequency than the sinusoidal waveforms of the same frequency. Equal attenuation of the high-frequency and low-frequency components is necessary to reproduce the squarewave faithfully.

Metering circuits

Many audio oscillators display the exact output signal amplitude on a meter. Normally, the metering circuit monitors the signal applied to the fixed attenuator, and the attenuation supplied by the fixed (step) attenuator is presumed to be constant and accurate. Metering circuits require a rectifier that is flat over the entire frequency range of the oscillator. The rectifier-circuit output drives the meter; a typical circuit is shown in Fig. 8.

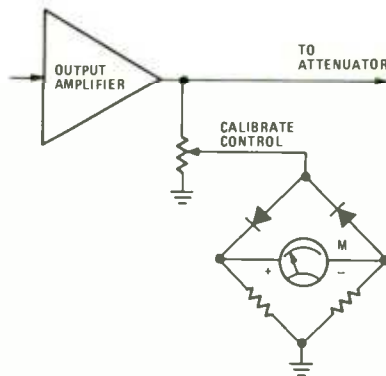


FIG. 8—TYPICAL OUTPUT METER. The audio frequency is rectified and measured.

Squaring circuits

The Schmitt trigger is the circuit most commonly used to generate a squarewave from the internal sinewave of the audio oscillator. The Schmitt trigger circuits are usually designed to avoid fast risetimes to keep noise from entering the sinewave output. The input to the squaring circuit must be buffered so it does not affect the sinewave characteristics by loading. The squarewave output of the Schmitt trigger is passed through a simple amplifier, reducing the output impedance to drive an attenuator.

Frequency control

Some audio oscillators offer auxiliary circuitry giving a few percent frequency variation. This feature permits locking to an external standard for more precise frequency control. Depending upon the basic oscillator circuit chosen, the external frequency control circuitry consists of an electronically variable capacitor to shunt the oscillator capacitance, or electronically variable resistors to shunt the oscillator resistance elements. Light-dependent resistors or Varicaps are used.

Specifications

The specifications of an electronic instrument are usually provided briefly in advertising, and in more detail in the operator's manual. Audio oscillator specifications, like those of most other instruments, vary from a simple listing covering less than a page to detailed listings covering a number of pages (generally found on more expensive units). Frequently, such specifications vary from manufacturer to manufacturer and at times even among instruments sold by the same manufacturer. It is therefore important that the user be able to organize the specifications in one common format to compare audio oscillators so he can decide on which one to buy.

Frequency range

The frequency range specification indicates the lowest frequency generated, as well as the highest frequency generated. This specification also indicates the number of ranges over which the oscillator must be tuned to cover its complete frequency range.

A note of caution: It is common to advertise only those performance specifications that lie within the classic audio frequency range (20 Hz to 20 kHz). Low-frequency limits for audio oscillators may run from a fraction of a hertz for the most sophisticated oscillators to 10 Hz for the lower-cost units. In higher-priced models, upper frequency limits of 1 MHz to 2 MHz are common. Lower-cost units may extend to an upper limit of only 100 kHz. All extend beyond the classic audio spectrum, and one cannot assume that a specification holds over this entire range. Read *all* the specifications to determine the capabilities of the audio oscillator at *any* particular frequency.

Frequency setting accuracy

Frequency accuracy, given as a percentage of the operating frequency, varies from a precise $\pm 0.5\%$ on switch-selected incremental oscillators to an error of $\pm 5\%$ on the less expensive units. For most work, a $\pm 5\%$ accuracy is entirely acceptable. Accuracy specifications for oscillators with switched incremental frequency tuning are given with any vernier frequency control in a fixed calibrate position. On oscillators with an exceptionally wide frequency range, a reduction in accuracy should be expected at the extreme ends of the range.

Audio oscillators are not intended to be used as frequency standards, and a high accuracy level is not generally necessary. Applications such as measuring the band-pass characteristics of extremely sharp filters, or measurements in such cases where legislation requires compliance to a frequency tolerance, may require an external frequency meter for ultimate accuracy.

to be continued

HICKOK

the value innovator

INSTRUMENTATION & CONTROLS DIVISION
THE HICKOK ELECTRICAL INSTRUMENT CO.
10514 Oupont Avenue • Cleveland, Ohio 44108
(216) 541-8060 • TWX: 810-421-8286

CIRCLE 31 ON FREE INFORMATION CARD

next month

MAY 1978

■ Build A Hi-Fi Graphic Equalizer

Two independent channels, 12 bands-per-channel and super specs make this a great add-on. Circuit highlights include inductorless bridged-T filters.

■ Build A Telephone Auto-Dialer And Cassette Interface

Telephone accessory automatically dials a predetermined number and plays a prerecorded message when triggered. Use it to upgrade an alarm system or as the basis for building your own system.

■ Digital Data Transmission

Ever wonder how a computer communicates with a peripheral device? Here's a look at serial and parallel transmission modes and the various industry standards.

■ Servicing With Oscilloscopes

A special Forest Belt section tells you what you need to know about using this most vital test instrument.

PLUS:

More Unusual Clocks

Getting Rid Of Noise In Mobile Radios

2 Hi-Fi Lab Test Reports


6502 Computer Corner

More Breadboarding And Prototyping Systems

State-Of-Solid State

Jack Darr's Service Clinic

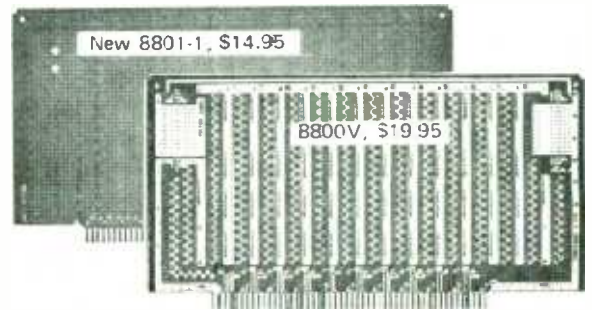
VECTOR PACKAGING MATERIALS SAVE TIME & MONEY




S100 CARDS—100 PLUG CONTACTS—Convenient universal tinned pads and bus lines. For interface, memory expansion, breadboarding. Mount almost anything anywhere on card.



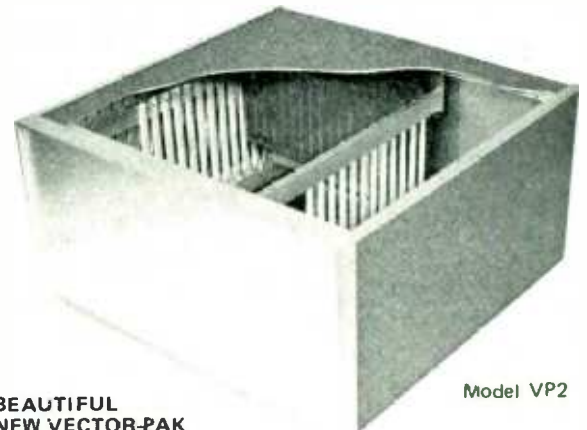S100 CONNECTORS for WIRE WRAPPING or SOLDERING



BEAUTIFUL NEW VECTOR-PAK CASES for micro-computer circuitry, assembled. Constructed of aluminum, finished in vinyl. Slide out covers for easy access. Includes card guides, heavy chassis plate, perforated bottom cover for cooler operation. Card guides perpendicular to front panel, Model VP1, \$128.30. Card guides parallel to front panel, Model VP2, \$134.30.

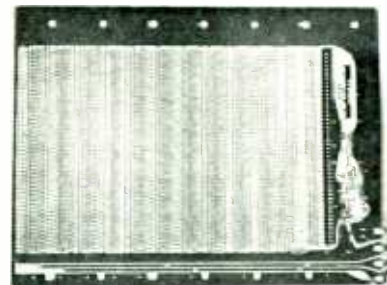

Model 8803

S100 MOTHERBOARD, \$29.50. 11 positions ready for connectors. Glass epoxy, etched circuitry for passive or active termination, 12 tantalum capacitors and instructions.

PLUS revolutionary Slit-N-Wrap wiring tools, Micro-Vector-board® printed circuit kits, I.C. sockets, extenders.


Send for new catalog.



VECTOR ELECTRONIC COMPANY, Inc.
12460 Gladstone Avenue, Sylmar, CA 91342
phone (213) 365-9661, twx 910-496-1539

540777

CIRCLE 89 ON FREE INFORMATION CARD

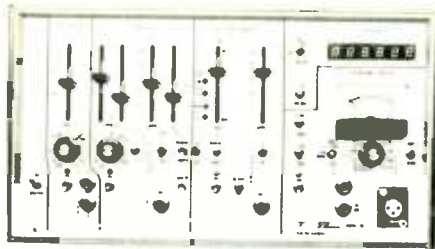

MODEL 101 AUDIO TEST SYSTEM consists of two sine/square/triangle function generators, pulse generator, frequency counter and AC voltmeter. As a system it will generate a frequency response plot on an X-Y recorder or scope.

Time base generator offers symmetrical or independent control of the positive and negative sides of the ramp providing a duty cycle of 1% to 99%. Frequency range is .002 Hz to 100k Hz. Amplitude is 16 Vpp into 500 ohms with ± 5 VDC offset. The time base output drives the X axis of an X-Y recorder. Manual mode provided for setup.

Audio sweep generator provides manual frequency adjustment or log or linear sweep of 20 Hz to 20k Hz. Blanking mode provides zero reference line on an X-Y recorder or tone burst. Amplitude is 16 Vpp into 500 ohms or 10 Vpp into 8 ohms.

Pulse generator frequency range is .002 Hz to 800k Hz. Pulse width is adjusted independent of frequency from 4 seconds to 40 nanoseconds. Outputs are complementary TTL.

AC voltmeter has full scale sensitivities from 1 mV to 250 V. Fast or slow, peak or true RMS and log or linear modes are provided. Output drives Y axis of X-Y recorder.

Frequency counter is 6 digit, 50 or 60 Hz line triggered, and reads either internal or external. Sensitivity is 10% of voltmeter full scale at 20k Hz 1 or 1/2 second update


Dimensions: 8 x 14 x 3. Shipping weight: 9 lbs. \$695. Stock to 30 days. Warranty: 1 year, 3 year \$70. Master Charge and Visa. Specs and operating information on request.

1894 Commercenter W. #106
San Bernardino, Ca 92408
(714) 889-7623

FIDELITY SOUND

Put Professional Knowledge and a
COLLEGE DEGREE
in your Electronics Career through

**HOME
STUDY**

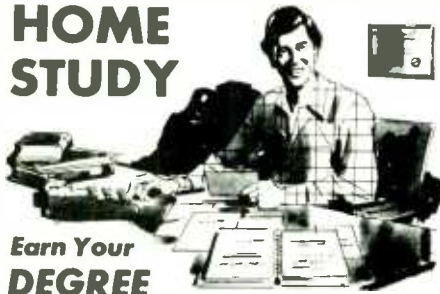

Earn Your
DEGREE

by correspondence, while continuing your present job. No commuting to class. Study at your own pace. Learn from complete and explicit lesson materials, with additional assistance from our home-study instructors. Advance as fast as you wish, but take all the time you need to master each topic. Profit from, and enjoy, the advantages of directed but self-paced home study.

The Grantham electronics degree program begins with basics, leads first to the A.S.E.T. degree, and then to the B.S.E.E. degree. Our free bulletin gives complete details of the program itself, the degrees awarded, the requirements for each degree, and how to enroll. Write for *Bulletin R-78*,

Grantham College of Engineering
2000 Stoner Avenue
P. O. Box 25992
Los Angeles, CA 90025

Worldwide Career Training thru Home Study

SELECTING A DMM

continued from page 66

best. The reason is that when high voltage is applied to a metal-film resistor, it typically fails by opening up until the metal film melts, then it shorts and finally opens. This, of course, defeats the desired protection. A carbon-composition resistor under the same conditions will typically open without the interim short.

"Another way to implement ohms protection is to use an active protection device. This is used in our new ohms circuit." (See Fig. 6.)

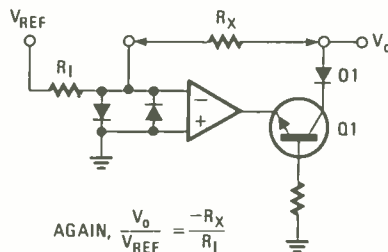


FIG. 6—ACTIVE PROTECTION CIRCUIT used in the ohms circuit of the digital multimeter.

"In normal operation, transistor Q1 is saturated and diode D1 is on. Consider the two opposite polarity cases (Fig. 7):

"The input to the op-amp is limited to -0.7 volts, causing the output to go positive -0.7 volts, causing the output to go positive which turns off Q1 (Fig. 7-a). Transistor Q1 is a 450-volt switching transistor, so nearly all the 163 volts appear at its collector. Since Q1 is off, virtually no collector current flows, and Q1 does not dissipate a large amount of power.

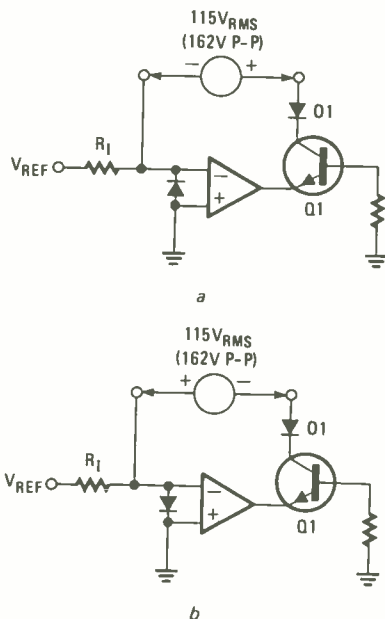


FIG. 7—ACTIVE CIRCUIT PREVENTS external voltage from damaging the DMM ohms circuit. Diode D1 and Q1 are the basic components.

"In Case 2 (Fig. 7-b), the op-amp output is negative, which forces transistor Q1 on. The input is limited to $+0.7$ volts, and diode D1 is off.

"So now we have an ohms converter that is protected, even if a 220-volt line is

connected to it. I think you'll agree that we make our product rugged."

George is visibly impressed. "I had no idea you people spent so much time with reliability and customer satisfaction. I wish I had known before I bought my first DMM. Of course, I probably would still have purchased your product."

George now realizes the forethought and extra testing effort that went into the design of his DMM. He will gladly pay more for a DMM whose usability he can verify from careful scrutiny of the data sheet. He wanted a "quality" DMM, and the service reputation of the manufacturer has already paid for itself. With renewed confidence in his DMM, he steps out of the Whoopee-tronics service center into the bright sunshine and hurries off to reenlist in the summer bowling league. **R-E**

**BETTER
THAN A
THIRD HAND!**



PANAVISE TILTS, TURNS, AND ROTATES TO ANY POSITION. IT HOLDS YOUR WORK EXACTLY WHERE YOU WANT IT.

PanaVise has great strength yet is gentle enough to firmly hold delicate objects.

Quite possibly the finest new tool you will buy this year, PanaVise is built to exacting professional standards. We guarantee it!

Illustrated is the Electronics Vise Model 396. Three other bases and a wide variety of heads are available. All interchangeable! Buy a basic unit, then add on to create your system.

Available through your dealer. Write for a free catalog.

PANAVISE

Dept. 5E

10107 Adella Ave., South Gate, CA 90280
In Canada: 25 Toro Rd., Downsview, Ont. M3J 2A6



A Division of Colbert Industries

CIRCLE 55 ON FREE INFORMATION CARD

EQUIPMENT REPORTS
continued from page 34

use the other hand to hold the soldering iron and feed solder with the fourth hand! With the model KL-3000, you can hold the board and part with one hand, and use the other hand to solder it.

The soldering pistol uses small-gauge solder, .031- and .050-inch in diameter. In the standard model KL 3000, the feed-reel is mounted on the top of the grip at the back, almost flush with the grip. Enough of the small solder can fit on this reel for quite a lot of joints. If a larger capacity is needed for production-line work, etc., you can mount a larger solder reel that holds three times as much as the standard reel. For making many joints without stopping, you can even obtain a bench-mounted reel that holds 2.2 lbs. of solder, or one kilogram!

The model KL 3000 comes in 20-, 30-, 40- and 60-watt sizes. The heating elements are interchangeable and can all be used in the same handle. The solder feed must match the size of the solder used, but this only requires changing the feed tube, which is not hard to do.

A great many soldering tips are available: 10 different 4-mm tips for the three lower heats, and 16 tips in the 6-mm size for the 60-watt unit. The tips are all specially coated so that you never file them. You just wipe them off with a wet sponge, and you're ready to go again. A bench stand is available that holds the pistol in the recommended upright position. And you can use any stock solder-gun holder.

The four stock pistol sizes are 115-volt AC-powered. A 24-volt unit, powered by a step-

down transformer, is rated at 40 watts. By changing taps, this unit can be used at 20 or 30 watts. An electronic temperature-controlled unit is also available for precision control of tip temperature.

We found a small junked PC board, put some parts in it and tried the pistol out. After only a little practice, we could make really smooth professional-looking joints with ease. A thumbscrew under the barrel can be used to adjust the amount of solder that is fed out when you press the trigger. The trigger also has click-stops that you can use. One squeeze delivers enough solder to make any average-sized joint, with one or two leads.

You can obtain the solder from Kager or use any stock solder. The sizes are standard.

For all IC work or for very closely spaced joints, this pistol is a very useful tool. **R-E**

**Hickok Model 266 CB
Signal Generator**

THE HICKOK ELECTRICAL INSTRUMENT COMPANY, 10514 Dupont Avenue, Cleveland, OH 44108, have been manufacturing RF signal generators for a long time. (Other things too, of course!) There's a model 188 generator on my bench that's been there since 1935! It works, too.

The company's latest entry is a real state-of-the-art instrument that can do many things accurately and make many tests easily. This instrument is the model 266 CB signal generator. It uses the latest technology to develop all
turn page

**Cramped
for Antenna
space?**



The McKay Dymek DA 100.

The DA 100 is a compact, wide dynamic range, broadband, untuned, omni-directional receiving antenna covering the frequency range of 50 kHz to 30 MHz.

The exterior module, a small weather-proof box with a 56 inch (142 cm) whip delivers the signal to the power supply unit through a supplied 50' coaxial cable.

The power supply locates near your general coverage receiver and attaches with a supplied patch cord.

The DA 100 antenna is small, but will equal or outperform a 100' long wire antenna, and is priced within reach of everyone!

Output Impedance - Attenuator Switch provided to match receiver input requirements and prevent overload.

Order factory Direct. Call toll free today! Money Back guarantee. Rent/Own Plan available. Specs and details on request.

Nationwide 800/854-7769
California 800/472-1783



MK McKay Dymek Co.
111 S. College Ave., PO Box 5000
Claremont CA 91711

CIRCLE 85 ON FREE INFORMATION CARD

**"POOR BOY" TUNER SUB
ONLY \$19.95**

Since all tuner subs that we know of are modified TV Tuners, we decided to market an excellent performing yet very low cost sub for the technician who has to get all he can for his money... a "Poor Boy's Sub" for only \$19.95.

This was not an easy task since cabinets, knobs and controls would push the price far above \$19.95... We searched for a tuner that needed no cabinet and no controls... one that the tech could scrounge the knobs from most any old TV...

It took over two years but we finally found it. The gain is excellent... Battery drain is very low (only 18 mils). It's self biasing so there is no R.F. gain control to fiddle with... It works equally well on tube or transistor sets... b/w or color... and is as easy to use as starting a fight with your wife (well, almost). All you need do is hook the set's IF cable to the "Poor Boy" and view the picture... That's it... no set up controls to confuse you.

We compared the "Poor Boy" with other subs costing over twice the price and found it to work just as well on all the comparison tests we made... and often a lot easier to use... Even though instructions aren't needed... you get those too.

The "Poor Boy" is small enough to easily hold in one hand... no wires or controls dangling around. It comes completely wired and tested including batteries and ready to use. Send a check for only \$19.95, and we even pay the shipping (how about that?) or we will ship COD. (\$1.85 C.O.D. Fee)

Try it for 10 days... If not completely satisfied... return for full refund.
Call us toll free 1-800-433-7124.

ALL ORDERS SHIPPED THE SAME DAY RECEIVED!!

TEXAS TUNER SERVICE

4210 N.E. 28TH STREET, FORT WORTH, TEXAS 76117
TEXAS CUSTOMERS PHONE (817) 834-8201

Please rush me the "Poor Boy" Substitute Tuner.
I understand that I can return it within 10 days for a full refund if I'm not completely satisfied... with no questions asked.

I am enclosing full amount of \$19.95 and will not be charged shipping.

Ship C.O.D. and I will pay an extra \$1.85 shipping and C.O.D.

RE-4/78

Name: _____

Street Address: _____

City: _____ State: _____ Zip: _____

CIRCLE 67 ON FREE INFORMATION CARD

**FREE! GTS-10 two-volume
owner's manual.**

Get all the facts on the new GTS-10 General Television Servicer - the concept that is changing the course of TV servicing!

Advanced yet sensibly priced at \$349.00 the GTS-10 is the ultimate instrument on the TV service equipment market.

In addition to free two-volume set of GTS-10 owner's manuals you will receive a comprehensive 6 page full color brochure - describing its profit making potential and its many unique patterns as well as information on our 30 day shop trial of GTS-10 General Television Servicer.



SEND TODAY!

Limited time offer on FREE manuals.

Telephone orders of GTS-10 General Television Servicer on VISA and MASTER CHARGE accepted for same day shipment. (303) 275-8991.

ATC AMERICAN TECHNOLOGY CORP.
225 Main Street
Canon City, CO 81212

Send \$1.00 if First Class delivery is desired.

Name _____ Phone _____

Company _____

Address _____

City _____ State _____ Zip _____

RE04

CIRCLE 108 ON FREE INFORMATION CARD

Get the Works, FREE.

"The Complete Bugworks"

From simple solderless breadboards to complete design stations, we have the products, instruments and educational materials (like the famous Bugbook® Volumes) that let you understand and design virtually any circuit system. "The Complete Bugworks" will show you the least expensive, most direct route to mastering the world of electronics. Send for your free copy today.

EI E&I INSTRUMENTS
61 First Street, Derby Conn 06418
(203) 735-8774 Telex No. 96 3536

Please shoot me "The Works."

NAME _____

ADDRESS _____

CITY _____

STATE _____

ZIP _____

TM

CIRCLE 83 ON FREE INFORMATION CARD

the different signals needed for present-day CB work. The suggested retail price is \$495.

The heart of the *model 266* is a digital phase-locked loop (PLL). A highly accurate reference oscillator together with the PLL generates an RF output signal exactly on-



CIRCLE 133 ON FREE INFORMATION CARD

frequency for all 40 CB channels. In our tests, the most deviation was about 20 Hz, which is far tighter than the average CB radio. The PLL uses an IC programmable divider to change CB channels. You just punch the two numbers in on the 12-button keyboard, and then press one of the two ENTER pushbuttons. The RF output locks tightly onto the reference, and a bright LED pilot labeled PHASE-LOCK lights! The channel number appears instantly on the two-digit LED readout. An IC memory remembers the correct divisor for the channel.

If you press the wrong pushbuttons, and the

LED readout gives you a number that is not one of the 40 channels (such as Channel 46 or Channel 95), this number shows up on the readout, but the PHASE-LOCK light stays out. You must press a 0 pushbutton for the first nine channels—i.e., "01," "06," etc. Hickok states that the PLL can be programmed for any extra channels in the 27-MHz band that may be added later.

The RF signal output is monitored by a panel meter, which reads directly in microvolts. The meter can be set in six steps, from $\times 1$ to $\times 100K$, and has a continuously variable level control. You can obtain any signal strength needed, from 100-mV RMS down to microvolt levels. The attenuator is also calibrated in dBm, and there is a dBm scale on the meter. (Example: 0 dBm = 1 mV, or 1000 μV .) This is especially useful for measuring adjacent sideband rejection, squelch setting, etc., that must be a certain dB below a reference level.

You can generate both AM and SSB signals. On AM, the RF signal can be unmodulated (or modulated) with an accurate 1.0-kHz signal. Pressing a button adjusts the modulation percentage from 0% to 100%; you can then read this on the meter.

For SSB tests, set the *model 266* to the CB channel desired without modulation. Set the CB rig to the same channel and to either upper sideband (USB) or lower (LSB). Now just press the USB or LSB pushbuttons on the front panel. The PLL moves exactly 1 kHz in either direction. The resulting RF signal is the same as a sideband signal with 1000-Hz modulation. The modulation percentage is also adjustable.

continued on page 122



Clever Kleps

Test probes designed by your needs—Push to seize, push to release (all Kleps spring loaded).

- Kleps 10.** Boathook clamp grips wires, lugs, terminals. Accepts banana plug or bare wire lead. 4¾" long. **\$1.39**
- Kleps 20.** Same, but 7" long. **\$1.49**
- Kleps 30.** Completely flexible. Forked-tongue gripper. Accepts banana plug or bare lead. 6" long. **\$1.79**
- Kleps 40.** Completely flexible. 3-segment automatic collet firmly grips wire ends, PC-board terminals, connector pins. Accepts banana plug or plain wire. 6¼" long. **\$2.59**
- Kleps 1.** Economy Kleps for light line work (not lab quality). Meshing claws. 4½" long. **\$.99**
- Prof 10.** Versatile test prod. Solder connection. Molded phenolic. Doubles as scribing tool. "Bunch" pin fits banana jack. Phone tip. 5½" long. **\$.89**

All in red or black - specify. (Add 50¢ postage and handling). Write for complete catalog of - test probes, plugs, sockets, connectors, earphones, headsets, miniature components.

Available through your local distributor, or write to:



RYE INDUSTRIES INC.
130 Spencer Place, Mamaroneck, N.Y. 10543
In Canada: Rye Industries (Canada) Ltd.

CIRCLE 45 ON FREE INFORMATION CARD



Kleps 10-20




Kleps 30



Kleps 40



Kleps 1

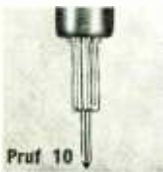

Prof 10

For
faster
service

USE
ZIP
CODE

on
all
mail

9 reasons why
the real pros
prefer Endeco
desoldering
irons

1. Operates at 120v. 40w. Idles at 20w for longer tip life
2. Flexible, burn resistant Neoprene cord set
3. Cool, unbreakable polycarbonate handle
4. Exclusive bracket insures alignment, prevents damage
5. Safety light in handle tells when it's on
6. Stainless steel construction
7. Temperature control Low, high or off
8. Eight tip sizes. Comes with .063 I.D.
9. Converts to soldering iron with ¼" shank type tip

See your distributor or write

Enterprise Development Corp.

5127 E. 65th St. • Indianapolis IN 46220
PHONE (317) 251-1231

CIRCLE 19 ON FREE INFORMATION CARD

MAKE YOUR OWN CUSTOM HARDWARE

continued from page 71

IC lead pin, solder the wire to the T-44 pins, put in a strain relief, and again mark pin No. 1 on this socket connector. The Glomper clip now can fit itself to an IC socket, yet still has testing points as handy as the original unmodified Glomper test

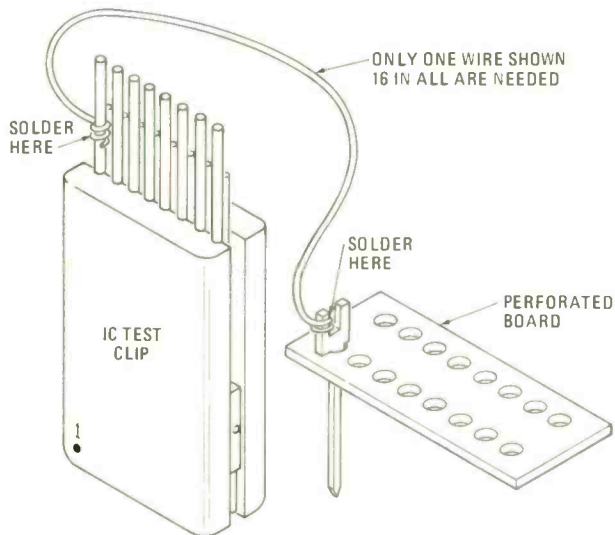


FIG. 16—IC TEST CLIP can be modified with a piece of cable and a homebrew jig to plug directly into an IC socket.

clip (see Fig. 16). The wire cable should be kept to under 36 inches, and 24 inches seems to work nicely. This same test clip prewired would cost a small fortune at the electronic shop, and for only pennies you have made the same unit.

Star No. seven

Just a helpful tip to those who use a great deal of solder wick to remove IC's and other components from boards. The cost of this wick is quite expensive. So, if you have some old zip cord, why not save some hard cash? Simply strip the cord to the braided wire, smear on some flux and use this in place of the solder wick.

Throughout this article I have given the names and addresses of makers of the special hardware stars I have introduced you too. Why not write them for their catalogs and try some of the ideas presented in the article next time you need a special situation device. Don't be afraid to try your hand at some modification of your own making, and let's hear from you through **Radio Electronics**; us home brewers have to stick together just to keep out of hot water. **R-E**

Everything we know about money-saving, time-saving, energy-saving ride sharing programs is yours for the asking.

Free. Our Double Up kit contains facts, figures, ideas, promotional help and other good things you and your company should know about.

Just write the U.S. Department of Transportation, P.O. Box 1813, Washington, D.C. 20013.

Name _____ Title _____
 Company _____
 Address _____
 City _____ State _____ Zip _____

A public service of this magazine, the U.S. Department of Transportation and the Advertising Council.

INTERNATIONAL FM-2400CH

FREQUENCY METER FOR TESTING MOBILE TRANSMITTERS AND RECEIVERS

• Portable • Solid State • Rechargeable Batteries

The **FM-2400CH** provides an accurate frequency standard for testing and adjustment of mobile transmitters and receivers at predetermined frequencies.

The FM-2400CH with its extended range covers 25 to 1000 MHz.

The frequencies can be those of the radio frequency channels of operation and/or the intermediate frequencies of the receiver between 5 MHz and 40 MHz.

Frequency stability: $\pm .0005\%$ from $+50^\circ$ to $+104^\circ\text{F}$.

Frequency stability with built-in thermometer and temperature corrected charts: $\pm .00025\%$ from $+25^\circ$ to $+125^\circ$ (.000125% special 450 MHz crystals available).

- Tests Predetermined Frequencies 25 to 1000 MHz
- Extended Range Covers 950 MHz Band
- Pin Diode Attenuator for Full Range Coverage as Signal Generator
- Measures FM Deviation

FM-2400CH (meter only) Cat. No. 035320	\$595.00
RF crystals (with temperature correction)	24.00 ea.
RF crystals (less temperature correction)	18.00 ea.
IF crystals	catalog price

Write for catalog



INTERNATIONAL CRYSTAL MFG. CO., INC.
 10 North Lee / Oklahoma City, Okla. 73102

CIRCLE 43 ON FREE INFORMATION CARD

APRIL 1978



Our new Bearcat® 250

has all the fantastic space age features of our super popular Bearcat® 210, but now we've added:

- 50 synthesized crystalless channels
- User selectable scanning speeds
- Priority channel
- Digital time clock—accurate to seconds
- Automatic or user controlled squelch
- Search Direction—Search "up" or "down" for quicker return to desired frequencies
- Transmission activity counter—tells you how busy each frequency has been
- Search & Store—Will find and "remember" up to 64 active frequencies for later recall
- Direct channel select—Advance directly to a channel without stepping through interim channels
- Non volatile memory—No batteries required to retain memory, even when scanner is unplugged
- Auxillary—On/Off control of equipment (tape deck, alarms, lights, etc.) when transmissions occur on programmed channels

To reserve your space-age Bearcat® 250 and receive your order priority number for spring-summer delivery, send \$389.00 plus \$5.00 for U.S. U.P.S. shipping. Foreign orders invited at slightly higher cost. Visa and Master Charge card holders may call toll free 800-521-4414 to order. Outside the U.S. and Michigan dial 313-994-4441. To order by mail or for a free catalog completely describing the fantastic crystalless Bearcat® 250 write: COMMUNICATIONS ELECTRONICS, Box 1002—Dept. 2, Ann Arbor, Michigan 48106 U.S.A.

©1978 Communications Electronics

CIRCLE 95 ON FREE INFORMATION CARD

EQUIPMENT REPORTS

continued from page 120

This test is a fast check for upper or lower sideband rejection, RF sensitivity and centering of any fine-tuning or clarifier controls on the CB transceiver.

A noise generator circuit is also included that produces a standard pulse-train noise, with a width of 1.0 μ s and a 100-PPS repetition rate. This noise is superimposed on the RF output signal. It can be used to check the receiver's noise blanking, noise limiter, etc., circuits on either AM or SSB.

For IF alignment and many other tests, the model 266 has a crystal-controlled 455-kHz signal that is 30% modulated and variable. For dual-conversion receivers, a crystal on the first IF frequency can be plugged into a crystal socket, and used to check this stage.

The IF test is also useful for checking a CB rig with a frequency synthesizer. Feed an unmodulated RF signal into the input of the CB rig and then press the 455-kHz IF signal output pushbutton. Couple the 455-kHz IF signal into the second IF stage. If the CB isn't exactly on-frequency, you'll hear an audible beat note in the speaker. Just tune the synthesizer for zero beat, and the job is done. A mistuned synthesizer can cause low sensitivity, etc. You can use the crystal function to check crystals for activity and frequency. Just plug the crystal into the model 266, select the crystal via the front-panel pushbutton and read the frequency on a counter connected to the IF output of the model 266. Crystals in the 1- to 20-MHz range can be checked out. Third

overtone crystals, used in many CB's, oscillate on the fundamental frequency, at one-third the RF frequency.

The model 266 has an RF signal output of up to 100,000 μ V, and an IF output signal of 150 mV. This output is sufficient to operate a frequency counter directly. The step attenuator on the RF signal output uses precision resistors and careful shielding, and the output signal can be adjusted down to a level of 1.0 μ V or a bit less. If fractional-microvolt signals are needed for an especially sensitive CB, you can construct a simple 20-dB attenuator that divides the RF output signal down by the necessary amount. The manual contains full construction details for this.

Amplitude-modulated CB's, as well as SSB's, can be easily checked for adjacent-channel rejection. Measure the sensitivity of the CB rig and then switch the PLL to the next channel in either direction. Increasing the RF output signal level until the output meter shows the same reading provides the adjacent-channel rejection ratio in dB instantly.

SSB tests are equally simple. For adjacent-sideband rejection, just measure the sensitivity on the USB, set the meter, then switch the model 266 to the LSB setting. Bring the signal level up until the meter shows the same reading, and read it off the RF meter in dBm.

Even the receiver's audio stages can be checked for maximum power output as well as for frequency response. For power tests, just read the RMS voltage across the speaker voice coil or a dummy load with a high signal input. Two charts in the instruction manual show the signal voltage for any power level—from 0.1

continued on page 148

Accuracy like a VTVM... Convenience like a VOM...


NEW BATTERY-OPERATED FET SOLID-STATE VOLT-OHMMETER #116

Easy-to-build KIT

\$41.85 =116K

Factory-Wired & Tested

\$56.12 =116W

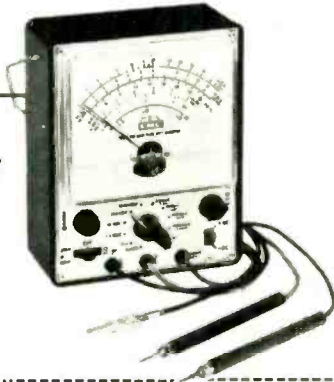

Now you can get all the benefits of a VTVM (laboratory accuracy, stability and wide range) but with its drawbacks gone: no plugging into an AC outlet, no waiting for warm-up, no bulkiness. New Field Effect Transistor (FET) design makes possible low loading, instant-on battery-operation and small size. Excellent for both bench and field work.

Compare these valuable features:

- High impedance low loading: 11 megohms input on DC, 1 megohm on AC
- 500-times more sensitive than a standard 20,000 ohms-per-volt VOM
- Wide-range versatility: 4 P-P AC voltage ranges: 0-3.3, 33, 330, 1200V; 4 RMS AC voltage ranges: 1-1.2, 12, 120, 1200V; 4 DC voltage ranges: 1-1.2, 12, 120, 1200V; 4 Resistance ranges: 1-K, 0-100K, 0-10 meg., 0-1000 meg.; 4DB ranges: -24 to +56DB.

Sensitive easy-to-read 4 1/2" 200 micro-amp meter. Zero center position available. Comprises FET transistor, 4 silicon transistors, 2 diodes. Meter and transistors protected against burnout. Etched panel for durability. High-impact bakelite case with handle useable as instrument stand. Kit has simplified step-by-step assembly instructions. Both kit and factory-wired versions shipped complete with batteries and test leads. 5 1/4" H x 6 3/4" W x 2 7/8" D. 3 lbs.

Send FREE catalog of complete EMC line and name of nearest distributor.

RE-4

Name _____

Address _____

City _____

State _____ Zip _____

EMC

ELECTRONIC MEASUREMENTS CORP.
625 Broadway, New York, N.Y. 10012

For
faster
service

USE
ZIP
CODE

on
all
mail



THERM I:

DIGITAL HEAT SENSOR

* THERM I kit: \$59.95 (assy. \$15 additional)

* Battery operated

* 3 digit .3" LED display

* Rugged handheld anodized aluminum case with 15' probe lead

* Range: 20 degrees to 158 degrees F (-7 to 70 C) \pm 1 degree F

* May calibrate in degrees F or C

Other members of the THERM family include:
* THERM II: LCD display for ultra-low power dissipation.

* MINI-THERM plugs directly into DVM for readout in mV/degree F or C.

Check, money order, Master Charge or Visa accepted (include expiration date with credit card orders).

Add \$1.25 for UPS shipping costs.

(415) 941-2764

P.O. Box 4477 Mtn. View CA 94040



CIRCLE 73 ON FREE INFORMATION CARD

market center

CLASSIFIED COMMERCIAL RATE (for firms or individuals offering commercial products or services). **\$1.50 per word** (no charge for zip code) . . . minimum 15 words.

NONCOMMERCIAL RATE (for individuals who want to buy or sell personal items) **85¢ per word** . . . no minimum.

ONLY FIRST WORD AND NAME set in bold caps. Additional bold face (not available as all caps) at 10¢ per word. Payment must accompany all ads except those placed by accredited advertising agencies. 5% discount for 6 issues, 10% for 12 issues within one year, if paid in advance. All copy subject to publisher's approval. Advertisements using P.O. Box address will not be accepted until advertiser supplies publisher with permanent address and phone number. Copy to be in our hands on the 26th of the third month preceding the date of the issue (i.e., August issue closes May 26). When normal closing date falls on Saturday, Sunday or a holiday, issue closes on preceding working day.

PLANS & KITS

CONSTRUCTION plans; over 100. From TV to telephone, from broadcasting to computers. Catalog air mailed \$1.00; includes year's subscription to Electronic Newsletter. **DON BRITTON ENTERPRISES**, PO Box G, Waikiki, HI 96815

MINI-laser plans \$1.00, science projects catalog 25¢. **MOTEN**, 323 S. Franklin, #804, Chicago, IL 60606

LINEAR Amplifier: Ham only 2—30 MHz, 100 watt, solid-state. **Frequency Counter:** 300 MHz, miniportable/mobile, memory! **VOX—Compressor:** Splatter free modulation booster. Construction plans \$3.00 each. All \$7.50! Kits, others, catalog available. **PANAXIS PRODUCTIONS**, Box 5516-F4, Walnut Creek, CA 94596

CB antenna construction manual: Build 16 dB gain beams plus quads, verticals, groundplanes, all from common hardware. Easy assembly/highest performance—complete \$4.00—**TENNA-FARM**, 1117 Dewitt Terrace, Linden, NJ 07036

THE most complete library of BASIC programs. Send \$1 for catalog to: **C.E.S.**, Box 1783, Waco, TX 76703

HOBBYIST give your project the professional look. Printed circuit boards from your sketch or artwork. Affordable prices. Rush free details. **DANOCINTHS**, Box 261, Westland, MI 48185

BUILD signal injector and tracer, under \$5.00, plan \$1.00 and stamped envelope. **Box 1041, Bellflower, CA 90706**

VIDEO cassette tape recorders RCA Selectavision. Free information. **HODAPP TV SALES**, 322 Main St., St. Clair, MN 56080

MULTIPROJECTOR tape-slide synchronizer, lap-dissolve plans, \$5.50. Free catalog. **MILLER**, 1896 Maywood, S. Euclid, OH 44121

67 kHz solid-state kits for reception of music-only, medical, special-interest programs not otherwise heard on FM. No crosstalk, excellent muting, with AC power supply. Quality product. \$47.50. Wired \$60.00. **MUSIC ASSOCIATED**, 65 Glenwood Road, Montclair, NJ 07043. 201-744-3387.

BUILD: T.V. Tuner Subber from junkbox parts. Plans and useful hints \$5.00. **SIMMS**, Dept RE, 38 East White Terrace, Nutley, NJ 07110

EDUCATION & INSTRUCTION

GRANTHAM's FCC License Study Guide—377 pages, 1465 questions with answers/discussions—covering third, second, first radiotelephone examinations. \$13.45 postpaid. **GSE PUBLICATIONS**, 2000 Stoner, Los Angeles, CA 90025

UNIVERSITY degrees by mail! Bachelors, Masters, Ph.D.'s . . . Free revealing details. **COUNSELING**, Box 317-RE4 Tustin, CA 92680

TELEPHONE bugged? Don't be Watergated! Countermeasures brochure \$1.00. **NEGEYE LABORATORIES**, Box 547-RE, Pennsboro, WV 26415

BUSINESS OPPORTUNITIES

CABLE FM STATION. No investment, excellent spare time income, others operate for you. Details free. **BROADCASTING**, Box 5516—F4, Walnut Creek, CA 94596

"RENT lease TV's anyone can! Easy to start and operate, even from your home." Send \$2.00 for basic information! **PERRY'S TV LEASING**, 308 N. McClelland St., Santa Maria, CA 93454

MECHANICALLY inclined individuals desiring ownership of Small Electronics Manufacturing Business—without investment. Write: **BUSINESSSES**, 92-R, Brighton 11th, Brooklyn, NY 11235

FOR SALE

FREE catalog. IC's, Semi's. **CORONET ELECTRONICS**, 649A Notre Dame W., Montreal, Que., Canada, H3C-1H8. US inquiries.

RECONDITIONED test equipment. \$0.50 for catalog. **WALTER'S TEST EQUIPMENT**, 2697 Nickel, San Pablo, CA 94806

BREATHE BETTER AIR WITH AMAZING NEGATIVE ION GENERATOR

Scientists have long known that negative ions can be beneficial to man's health. These tiny but potent, atmospheric particles abound in nature. Now, through the magic of science, you can duplicate this delightful phenomenon in the privacy and convenience of your own home or office.

Output: 9 x 10⁹ ions/sec
Size: 19" x 14" x 8"
Weight: 18 pounds

DEALERS
WANTED

GOLDEN ENTERPRISES
P.O. Box 1282-RE
Glendale, Arizona 85311

(Please send \$1.00 for fascinating details)

TELEPHONE recording equipment and other 'unusual' electronic devices. Free information. **GARRISON**, Box 128-B, Kew Gardens, NY 11415

BUILD YOUR OWN TV CAMERA!

— Ideal for home & business —
THE ECONOMICAL ANSWER TO HOME MONITORING OF BUSINESS, INDUSTRIAL SURVEILLANCE, TV AMATEUR TV PLUS HUNDREDS OF OTHER APPLICATIONS. MODEL ST-1A, SERIES D - KIT FORM SIBL ASSEMBLED \$215. SOLID-STATE WORKS ON ANY TV SET. OPTIONAL SOUND KIT \$25. PHONE OR WRITE for catalog. Dial 402-987-3771
BOX 453-RE ATV Research DAKOTA CITY, NE 68721

WARBLE ALARM CAR-VAN CLOCK WITH HEADLIGHT ALARM



COMPLETE KIT \$35.95
ASSEMBLED \$45.95

- ELAPSED TIMER
- SECONDS DISPLAY SWITCH
- 9 MINUTE SNOOZE ALARM
- SIMPLE 4 WIRE HOOK UP
- JUMBO LED DISPLAY
- 1 TO 59 MINUTE COUNTDOWN TIMER RUNS SIMULTANEOUSLY WITH CLOCK*
- RUGGED ABS CASE
- QUARTZ CRYSTAL ACCURACY

DIGITAL AUTO INSTRUMENTS

SEVEN MODELS!

- #1 TACHIMETER
- #2 WATER TEMP
- #3 FUEL LEVEL
- #4 SPEEDOMETER*
- #5 OIL PRESSURE
- #6 OIL TEMP
- #7 BATTERY MONITOR



*KIT INCLUDES: 255 A, 255 AAH, 255 AB, 255 AC, 255 AD, 255 AE, 255 AF, 255 AG, 255 AH, 255 AI, 255 AJ, 255 AK, 255 AL, 255 AM, 255 AN, 255 AO, 255 AP, 255 AQ, 255 AR, 255 AS, 255 AT, 255 AU, 255 AV, 255 AW, 255 AX, 255 AY, 255 AZ, 255 BA, 255 BB, 255 BC, 255 BD, 255 BE, 255 BF, 255 BG, 255 BH, 255 BI, 255 BJ, 255 BK, 255 BL, 255 BM, 255 BN, 255 BO, 255 BP, 255 BQ, 255 BR, 255 BS, 255 BT, 255 BU, 255 BV, 255 BW, 255 BX, 255 BY, 255 BZ, 255 CA, 255 CB, 255 CC, 255 CD, 255 CE, 255 CF, 255 CG, 255 CH, 255 CI, 255 CJ, 255 CK, 255 CL, 255 CM, 255 CN, 255 CO, 255 CP, 255 CQ, 255 CR, 255 CS, 255 CT, 255 CU, 255 CV, 255 CW, 255 CX, 255 CY, 255 CZ, 255 DA, 255 DB, 255 DC, 255 DD, 255 DE, 255 DF, 255 DG, 255 DH, 255 DI, 255 DJ, 255 DK, 255 DL, 255 DM, 255 DN, 255 DO, 255 DP, 255 DQ, 255 DR, 255 DS, 255 DT, 255 DU, 255 DV, 255 DW, 255 DX, 255 DY, 255 DZ, 255 EA, 255 EB, 255 EC, 255 ED, 255 EE, 255 EF, 255 EG, 255 EH, 255 EI, 255 EJ, 255 EK, 255 EL, 255 EM, 255 EN, 255 EO, 255 EP, 255 EQ, 255 ER, 255 ES, 255 ET, 255 EU, 255 EV, 255 EW, 255 EX, 255 EY, 255 EZ, 255 FA, 255 FB, 255 FC, 255 FD, 255 FE, 255 FF, 255 FG, 255 FH, 255 FI, 255 FJ, 255 FK, 255 FL, 255 FM, 255 FN, 255 FO, 255 FP, 255 FQ, 255 FR, 255 FS, 255 FT, 255 FU, 255 FV, 255 FW, 255 FX, 255 FY, 255 FZ, 255 GA, 255 GB, 255 GC, 255 GD, 255 GE, 255 GF, 255 GG, 255 GH, 255 GI, 255 GJ, 255 GK, 255 GL, 255 GM, 255 GN, 255 GO, 255 GP, 255 GQ, 255 GR, 255 GS, 255 GT, 255 GU, 255 GV, 255 GW, 255 GX, 255 GY, 255 GZ, 255 HA, 255 HB, 255 HC, 255 HD, 255 HE, 255 HF, 255 HG, 255 HH, 255 HI, 255 HJ, 255 HK, 255 HL, 255 HM, 255 HN, 255 HO, 255 HP, 255 HQ, 255 HR, 255 HS, 255 HT, 255 HU, 255 HV, 255 HW, 255 HX, 255 HY, 255 HZ, 255 IA, 255 IB, 255 IC, 255 ID, 255 IE, 255 IF, 255 IG, 255 IH, 255 II, 255 IJ, 255 IK, 255 IL, 255 IM, 255 IN, 255 IO, 255 IP, 255 IQ, 255 IR, 255 IS, 255 IT, 255 IU, 255 IV, 255 IW, 255 IX, 255 IY, 255 IZ, 255 JA, 255 JB, 255 JC, 255 JD, 255 JE, 255 JF, 255 JG, 255 JH, 255 JI, 255 JJ, 255 JK, 255 JL, 255 JM, 255 JN, 255 JO, 255 JP, 255 JQ, 255 JR, 255 JS, 255 JT, 255 JU, 255 JV, 255 JW, 255 JX, 255 JY, 255 JZ, 255 KA, 255 KB, 255 KC, 255 KD, 255 KE, 255 KF, 255 KG, 255 KH, 255 KI, 255 KJ, 255 KK, 255 KL, 255 KM, 255 KN, 255 KO, 255 KP, 255 KQ, 255 KR, 255 KS, 255 KT, 255 KU, 255 KV, 255 KW, 255 KX, 255 KY, 255 KZ, 255 LA, 255 LB, 255 LC, 255 LD, 255 LE, 255 LF, 255 LG, 255 LH, 255 LI, 255 LJ, 255 LK, 255 LL, 255 LM, 255 LN, 255 LO, 255 LP, 255 LQ, 255 LR, 255 LS, 255 LT, 255 LU, 255 LV, 255 LW, 255 LX, 255 LY, 255 LZ, 255 MA, 255 MB, 255 MC, 255 MD, 255 ME, 255 MF, 255 MG, 255 MH, 255 MI, 255 MJ, 255 MK, 255 ML, 255 MM, 255 MN, 255 MO, 255 MP, 255 MQ, 255 MR, 255 MS, 255 MT, 255 MU, 255 MV, 255 MW, 255 MX, 255 MY, 255 MZ, 255 NA, 255 NB, 255 NC, 255 ND, 255 NE, 255 NF, 255 NG, 255 NH, 255 NI, 255 NJ, 255 NK, 255 NL, 255 NM, 255 NN, 255 NO, 255 NP, 255 NQ, 255 NR, 255 NS, 255 NT, 255 NU, 255 NV, 255 NW, 255 NX, 255 NY, 255 NZ, 255 OA, 255 OB, 255 OC, 255 OD, 255 OE, 255 OF, 255 OG, 255 OH, 255 OI, 255 OJ, 255 OK, 255 OL, 255 OM, 255 ON, 255 OO, 255 OP, 255 OQ, 255 OR, 255 OS, 255 OT, 255 OU, 255 OV, 255 OW, 255 OX, 255 OY, 255 OZ, 255 PA, 255 PB, 255 PC, 255 PD, 255 PE, 255 PF, 255 PG, 255 PH, 255 PI, 255 PJ, 255 PK, 255 PL, 255 PM, 255 PN, 255 PO, 255 PP, 255 PQ, 255 PR, 255 PS, 255 PT, 255 PU, 255 PV, 255 PW, 255 PX, 255 PY, 255 PZ, 255 QA, 255 QB, 255 QC, 255 QD, 255 QE, 255 QF, 255 QG, 255 QH, 255 QI, 255 QJ, 255 QK, 255 QL, 255 QM, 255 QN, 255 QO, 255 QP, 255 QQ, 255 QR, 255 QS, 255 QT, 255 QU, 255 QV, 255 QW, 255 QX, 255 QY, 255 QZ, 255 RA, 255 RB, 255 RC, 255 RD, 255 RE, 255 RF, 255 RG, 255 RH, 255 RI, 255 RJ, 255 RK, 255 RL, 255 RM, 255 RN, 255 RO, 255 RP, 255 RQ, 255 RR, 255 RS, 255 RT, 255 RU, 255 RV, 255 RW, 255 RX, 255 RY, 255 RZ, 255 SA, 255 SB, 255 SC, 255 SD, 255 SE, 255 SF, 255 SG, 255 SH, 255 SI, 255 SJ, 255 SK, 255 SL, 255 SM, 255 SN, 255 SO, 255 SP, 255 SQ, 255 SR, 255 SS, 255 ST, 255 SU, 255 SV, 255 SW, 255 SX, 255 SY, 255 SZ, 255 TA, 255 TB, 255 TC, 255 TD, 255 TE, 255 TF, 255 TG, 255 TH, 255 TI, 255 TJ, 255 TK, 255 TL, 255 TM, 255 TN, 255 TO, 255 TP, 255 TQ, 255 TR, 255 TS, 255 TT, 255 TU, 255 TV, 255 TV, 255 TW, 255 TX, 255 TY, 255 TZ, 255 UA, 255 UB, 255 UC, 255 UD, 255 UE, 255 UF, 255 UG, 255 UH, 255 UI, 255 UJ, 255 UK, 255 UL, 255 UM, 255 UN, 255 UO, 255 UP, 255 UQ, 255 UR, 255 US, 255 UT, 255 UY, 255 UZ, 255 VA, 255 VB, 255 VC, 255 VD, 255 VE, 255 VF, 255 VG, 255 VH, 255 VI, 255 VJ, 255 VK, 255 VL, 255 VM, 255 VN, 255 VO, 255 VP, 255 VQ, 255 VR, 255 VS, 255 VT, 255 VU, 255 VV, 255 VW, 255 VX, 255 VY, 255 VZ, 255 WA, 255 WB, 255 WC, 255 WD, 255 WE, 255 WF, 255 WG, 255 WH, 255 WI, 255 WJ, 255 WK, 255 WL, 255 WM, 255 WN, 255 WO, 255 WP, 255 WQ, 255 WR, 255 WS, 255 WT, 255 WU, 255 WV, 255 WW, 255 WX, 255 WY, 255 WZ, 255 XA, 255 XB, 255 XC, 255 XD, 255 XE, 255 XF, 255 XG, 255 XH, 255 XI, 255 XJ, 255 XK, 255 XL, 255 XM, 255 XN, 255 XO, 255 XP, 255 XQ, 255 XR, 255 XS, 255 XT, 255 XU, 255 XV, 255 XW, 255 XX, 255 XY, 255 XZ, 255 YA, 255 YB, 255 YC, 255 YD, 255 YE, 255 YF, 255 YG, 255 YH, 255 YI, 255 YJ, 255 YK, 255 YL, 255 YM, 255 YN, 255 YO, 255 YP, 255 YQ, 255 YR, 255 YS, 255 YT, 255 YU, 255 YV, 255 YW, 255 YX, 255 YZ, 255 ZA, 255 ZB, 255 ZC, 255 ZD, 255 ZE, 255 ZF, 255 ZG, 255 ZH, 255 ZI, 255 ZJ, 255 ZK, 255 ZL, 255 ZM, 255 ZN, 255 ZO, 255 ZP, 255 ZQ, 255 ZR, 255 ZS, 255 ZT, 255 ZU, 255 ZV, 255 ZW, 255 ZX, 255 ZY, 255 ZZ

ELECTRONIC 'PENDULUM' CLOCK



- SWING PENDULUM
- 7 HOURS AND MINUTES DISPLAY
- TIME SET PUSH BUTTONS
- ALARM FEATURE

KIT UNFINISHED CASE \$59.95
ASSEMBLED STAINED CASE \$69.95

QUARTZ DIGITAL AUTO CLOCK OR ELAPSED TIMER*

ELAPSED TIMER: HRS, MINS & SECS
SIMPLE PUSHBUTTON RESET & HOLD TOGGLE SWITCH
12 OR 24 HR MODE



KIT: \$27.95 ASSEMBLED: \$37.95

NOW WITH ELAPSED TIME!



3 1/2 DIGITAL CLOCK

- 3 1/2 DIGIT \$49.95
- 4 1/2 DIGIT \$59.95
- 6 1/2 DIGIT \$79.95
- 117 VAC 12 OR 24 HR MODE
- 4 DIGIT HOURS 12, 24, 30
- 4 DIGIT MINS 12, 30, 45
- 4 DIGIT SECS 12, 30, 45
- 4 DIGIT SECS 12, 30, 45

TV-WALL CLOCK

- 25 VIEWING DISTANCE
- 6 HOURS & MINUTES
- 3 SECONDS
- COMPLETE WITH WOOD CASE



KIT: \$34.95 ASSEMBLED: \$39.95

ECONOMY CAR CLOCK

- LED MODULE*
- COMPLETE WITH CASE BRACKET & TIME SET PUSHBUTTONS
- ALARM OPTION



KIT: \$19.95 ASSEMBLED: \$26.95

PENDULUM



\$14.95 CASE WITH BRACKET **\$3.75**

MARK FOSKETS'
SOLID STATE TIME
P.O. BOX 2159
DUBLIN, CALIF. 94566
ORDERS (415) 828-1923



CALIFORNIA RESIDENTS ADD 6% SALES TAX

CIRCLE 24 ON FREE INFORMATION CARD

PET owner need information? Send SASE for details. TIS, Box 921, Los Alamos, NM 87544

F.C.C. EXAM MANUAL

PASS FCC EXAMS! Memorize, study—Test—Answers for FCC 1st and 2nd class Radio telephone licenses. Newly revised multiple choice questions and diagrams cover all areas tested in FCC exams, plus Self-Study Ability Test. \$9.95 postpaid. Money-back guarantee.

Tests: Answers for FCC 1st and 2nd class Commercial License

COMMAND PRODUCTIONS P.O. Box 76348 E
RADIO ENGINEERING DIV. SAN FRANCISCO, CALIF. 94176

RADIO & TV tubes 36¢ each. One year guaranteed. Plus many unusual electronic bargains. Free catalog. CORNELL, 4217-E University, San Diego, Calif. 92105

SERVICEMEN—Cleaners, lubricants, adhesives for all electronic repairs. Write for free catalog. PROJECTOR-RECORDER BELT CORP., Box 176, Whitewater, WI 53190 800-558-9572 ex. WI

PRINTED CIRCUIT

Positive Acting Photo Resist; Carbide bits; Bubble etchers; Artwork; Epoxy Glass Boards.

Send stamp & address label for flyer


TRUMBULL

833 Balra Dr., El Cerrito, CA 94530

CARBON film resistors—1/4W, 5% (1-4M7 ohms) 3.5¢ each. 50/value—\$0.85. Postage, handling \$1.00. Other components. Free catalog, resistor sample. COMPONENTS CENTER, Box 295R, West Islip, NY 11795

TUBES, receiving and Industrial, semiconductor, factory boxed, low prices, free price list. TRANSLETERONIC INC., 1365 — 39th Street, Brooklyn, NY 11218 212-633-2800

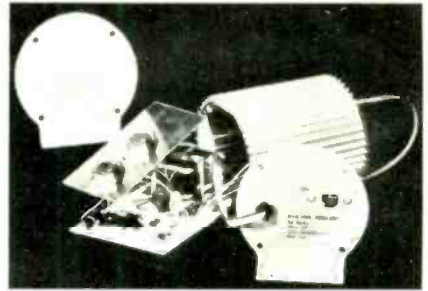TAPE head cleaner. 8 oz.—\$2.30. Includes postage and handling. Write: "CLEANER," Box 176, Whitewater, WI 53190



FROM KIT TO CAR IN 80 MINUTES!

Electronic ignition is "in." Update your car with the TOPS in power, efficiency and reliability — the TIGER SST capacitive discharge ignition (CD).

The TIGER delivers everything other CD's promise — and more: quicker starting, more power, more gas mileage, tune-ups eliminated, lifetime plugs and points, reduced repairs and pollution.

The TIGER can be built and installed in your car in 80 minutes. The TIGER is unique!

The TIGER comes with a switch for TIGER or standard ignition for 12V negative ground only.

Simpli-Kit \$21.95
POST PAID U.S.A.

WE ACCEPT:

Mastercharge or BankAmericard.
Send check or money order with order to:

Tri-Star Corporation

DEPT. FF, P.O. Box 1727
Grand Junction, Colorado 81501

CIRCLE 37 ON FREE INFORMATION CARD

INTERNATIONAL ELECTRONICS UNLIMITED

CLEARANCE SALE

PC BOARDS - for use with ELEKTOR MAGAZINE PROJECTS

MAGAZINE PROJECTS

ELEKTOR #32 Dec 77	\$1.50
music synthesizer (E25-31)	9724-1 7.45
CPU - SC/MP	9851a 18.80
UNO TV modulator	9864 2.95
microphone preamp	9866 1.30
ANALOG FREQ. METER	9869 2.40
heating controller	9877 7.05
Hi reflex receiver	9880 1.85
sensitive lightmeter	9886 1.30
stylus balance (E12)	9343 1.05
signal generator (E24)	9765 1.10
knotted handkerchief (E27/28)	9830 .45
ELEKTOR #31 Nov 77	1.50
music synthesizer	9723-1 18.35
CCIR TV pattern generator	9800-3 5.65
video bloffed back	9825-1 5.60
display generator	9825-2 4.60
alpha amplifier	9826-1 1.50
electrometer	9826-2 1.40
sensors for electrometer	9827 1.45
magnetiser	9827 1.45
CPU-SC/MP	
RAM-1/0	9846-1 12.70
SC/MP Board	9846-2 3.95
model car track (E24-E30)	
transmitter power supply	9218 2.20
chassis	9850 6.35
ELEKTOR #20 Oct 77	1.50
CCIR TV pattern generator (E29)	9800-2 7.35
Infrared transmitter	9822 5.55
ioniser	9823 6.60
Kirlian camera (set) 4523	9831 5.00
model car track (E24-26,29)	
infrared receiver	9848-1 1.80
multidex decoder	9848-2 1.90
ELEKTOR #19 Sept 77	1.50
FM intercom	9359 10.75
music synthesiser (E25,26)	
interface receiver	9721-2 2.80
power supply	9721-3 9.15
keyboard divider(1 octave)	9721-4 1.70
logarithmic timer	9767 3.35
CCIR TV test pattern generator	9800-1 13.10
model car track (E24-26)	
motor speed control	9829-1 1.20
prototester	9829-2 3.45
ELEKTOR #27/28 Jul-Aug 77	3.00
LED peak indicator	9525 2.70
knotted handkerchief	9830 .45
phasor	77001 2.50
distortion meter	77005 4.10
guitar preamp	77020 2.45
time switch	77021 3.50
0-10V supply	77059 2.10
11 - quilliser	77071 1.50
automatic Ni Cad charger	77075 1.45
TV games	77084 4.50
4w car radio amp	77101 1.40
3-1/2 digit DVM	77109 4.70
ELEKTOR #26 June 77	1.50
precision time base	9438 3.40
power supply for time base	9438-1 1.30
music synthesiser	
keyboard interface (E25)	9721-1 5.75
levitator	9763 5.20
loudspeaker cross-over filters (E25)	9768 4.30
model car track (E24,25)	
servo amp	9803 .80
ELEKTOR #25 May 77	1.50
music cleaner	9785 3.90
model car track (E24)	
multidex encoder	9796-1 6.85
infrared transmitter	9796-2 3.55
ultrasonic alarm (E19)	
single transducer/recvr	9815-1 2.80
transmitter	9815-2 1.85
ELEKTOR #24 April 77	1.50
display (E13)	9376 6.90
LED volume unit meter	
rectifier section	9419-1 5.15
display section	9419-2 9.95
FM tuner (E23)	
s.f. converter	9447-2 3.60
stereo decoder	9447-3 2.55
auto slide changer	9743 1.45
noise decoder	9759 16.25
signal injector	9765 1.10
ELEKTOR #23 March 77	1.50
running light	9203 2.30
FM tuner (E24)	
front end	9447-1 8.45
OTA-PLL	6029 3.10
scope calibrator	9455 .65
run rabbit run	9764 9.15

7400 series TTL
tested and passed logic test -
not full parametric specs
minimum 10 of item

7400	\$.05	7476	.12
7401	-.07	7483	.18
7402	-.05	7485	.25
7403	-.05	7486	.12
7404	-.06	7491	.20
7405	-.06	7493	.14
7406	-.09	7495	.20
7407	-.09	74100	.12
7409	-.07	74107	.12
7410	-.05	74123	.18
7412	-.06	74125	.22
7420	-.12	74126	.22
7423	-.12	74132	.22
7425	-.12	74145	.25
7426	-.09	74145	.25
7427	-.09	74150	.25
7430	-.07	74151	.20
7432	-.08	74153	.15
7437	-.07	74154	.40
7438	-.07	74155	.20
7440	-.05	74163	.35
7441	-.30	74163	.35
7442	-.20	74164	.35
7443	-.20	74170	.25
7444	-.20	74173	.45
7445	-.30	74174	.30
7446	-.30	74175	.25
7448	-.06	74176	.25
7450	-.06	74177	.25
7451	-.07	74180	.25
7453	-.06	74182	.25
7454	-.05	74191	.30
7460	-.05	74192	.28
7472	-.12	74194	.28
7473	-.12	74195	.18
7474	-.10		

SEE ADDITIONAL AD THIS SECTION

5 BACK ISSUES OF ELEKTOR MAGAZINE
containing a variety of electronic
projects, with schematics, PC lay-
outs, parts list. PC boards are
available. Regular \$1.50/copy
\$4.00/5 issues

25 26 29 30 31

8000 SERIES - NATIONAL

8000	\$.05	8553	\$.75
8002	-.05	8560	.75
8004	-.05	8561	.35
8041	-.25	8570	.35
8086	-.25	8588	.35
8090	-.25	8590	.35
8091	-.25	8597	.75
8092	-.25	8598	.45
8093	-.25	8599	.75
8094	-.40	8600	.35
8095	-.40	8612	.75
8096	-.40	8810	.25
8097	-.40	8811	.25
8102	-.45	8812	.05
8103	-.45	8822	.75
8122	-.45	8830	.25
8123	-.45	8831	.45
8200	-.45	8833	.45
8212	-.50	8835	.45
8214	-.45	8836	.20
8219	-.45	8838	.35
8220	-.45	8842	.45
8221	-.45	8845	.45
8230	-.45	8852	.45
8280	-.45	8866	.45
8281	-.45	8880	.45
8288	-.45	8884	.60
8551	-.50	8890	.25
8552	-.75		

CLOCK KIT - Mark I
6 digit clock kit with one PC
board. Accommodates MM5314
clock chip and 6 FND 359 displays
Contains all components except
transformer. Includes 3 switches.
Board has terminals for remote
displays. \$10.95

with 12V/300 ma transformer \$13.95

UNTESTED PROM - HI Yield
Same Pin-out as 8223
5600 4/\$1.00
5610 3/\$1.00

RESISTOR PACKAGE
Carbon Film - 5% 1/4 w or 1/2 w
15 ea. of 12 values:
100, 220, 470, 1K, 1.5K, 3.3K,
4.7K, 6.8K, 10K, 33K, 100K, 1M.

RESISTOR PACKAGE
Carbon Film - 5% 1/4w or 1/2w
Usage Evaluated Assortment
5 to 20 ea of 44 values. \$12.95
Supplied in 15 Drawer 60 Comp.
Cabinet. \$22.95 - \$2.00 SH.

EDGE CONNECTOR
Eico modular unit.
6 pin, 3 position, wirewrap
6/\$1.00

CLOCK KIT - Cx 6-3
6 digit clock kit with MM5314 clock
chip, 6 3" CA displays, 2 PC boards.
Contains all components except
transformer. Includes 3 switches.
with 12V/300 ma transformer \$15.95

LINEAR ASSORTMENT
each of following - all functional
301M, 302M, 307M, 311M, 340T-5,
340T-6, 340T-15, 380-S, 385K, 723N,
739K, 741M, 748M, 75453M \$4.75

ELECTRONIC DOOR CHIME KIT
WITH TI TMS 1000
MICROPROCESSOR CHIP
PROGRAMMED TO PLAY
24 DIFFERENT TUNES
\$39.50 SHIPPING \$1.00

Complete satisfaction guaranteed. Shipment to US and Canada prepaid
unless indicated otherwise. Other countries add 10% excess refunded.
Orders shipped in 3 working days from receipt. Minimum order \$10.00.
California residents add sales tax. Minimum CDD or charge order \$15.00

INTERNATIONAL ELECTRONICS UNLIMITED
VILLAGE SQUARE, P.O. BOX 449, CARMEL VALLEY, CA 93924 USA
TELEPHONE 408 659-3171

MESHNA SPECIALS

PHOTO FLASH complete on PC board w/flash
tube in reflector, 2 ni-cads & camera connecting
cable. Cycles in 3 seconds \$6.00

8 SWITCHES in MINI DIP 1.80

10 SWITCHES in MINI DIP 2.00

AA NI-CADS fast charge 1.25

5 WAY BINDING POST US made .35

U-FIX-EM TV games, w/power pack & video
Cube in original boxes (sold for \$50) 11.00

JUMBO LED .187 diam. long leads 6/1.00

TV CHEATER CORDS 6 ft .75

LIQUID CRYSTAL thermometer, reads 86 to 108
degrees F 4/1.00

MULTI USE xfmr puts out 140 volts, 12.6, 6,
33.5 volts Many home projects 1.50

SEISMIC DETECTOR radio transmitter, used in
Viet Nam for troop detection. 4.00

COPY LENS FROM ZEROX in mount. 8 1/4" focal
length Iris f4.5 to f8 10.50

U-FIX-EM hand calculator 4 function 3.00

LAMBDA solid state regulated 10.5 line power
supply 12 volts DC 8 amps 50.00

ULTRA SONIC transducer 37 or 40 Khz \$2.00

The above includes data on alarm system

PL 259 coax connector .75

SO-239 coax socket .60

TOUCH TONE ENCODER KIT, pad, chip &
Instructions 12.95

IR NIGHT VIEWER, new ready to use, see in the
dark 199.00

All above FOB LYNN MASS (you pay shipping)
Amazing 64 page catalog free

JOHN MESHNA JR, INC. PO Box 62, E. Lynn
Mass. 91904

CIRCLE 34 ON FREE INFORMATION CARD

CIRCLE 2 ON FREE INFORMATION CARD

INTERNATIONAL ELECTRONICS UNLIMITED

IC-LED INVENTORY CLEARANCE SALE

TTL			
7400	.09	7489	1.75
7404	.14	7493	.28
7406	.19	7490	.35
7407	.19	7495	.35
7416	.22	7496	.35
7430	.12	74121	.21
7432	.15	74123	.23
7437	.15	74141	.65
7438	.15	74145	.55
7440	.12	74151	.35
7445	.45	74153	.49
7446	.40	74154	.75
7450	.12	74157	.52
7454	.08	74161	.52
7460	.08	74165	.85
7475	.32	9601	.29
7480	.25	9602	.35
7486	.23		

CMOS	
4002	.19
4006	.95
4007	.19
4009	.39
4011	.16
4014	.79
4019	.25
4021	.85
4022	.89
4023	.18
4051	.89

MAN 1	.27	Red CA LHO	.99
MAN 2	.30	Red 5x7 LHO	3.95
MAN 5	.27	Green CA LHO	.99
MAN 7	.27	Yellow CA LHO	.49
MAN 54	.30	Green CC RHO	1.19
MAN 66	.60	Red CA LHO	1.19
MAN 72	.30	Red CA LHO	.59
MAN 82	.30	Red CA LHO	.99
MAN 3610	.30	Orange CA RHO	.69
MAN 3640	.30	Orange CC RHO	.69
MAN 4610	.40	Orange CC RHO	.59
MAN 6660	.56	Orange CA RHO	.59
DL 10A	.27	Red CA LHO	.99
DL 702	.30	Red CC LHO	.79
DL 707	.30	Red CA RHO	.79
DL 747	.60	Red CA LHO	1.19
FND 359	.375	Red CC RHO	.59
FND 500	.50	Red CC RHO	.69
FND 507/510	.50	Red CA RHO	.69
NSN 74R	.30	Red CC RHO	.69

MAN 6610	2 0ig .56"	Drng CA RHO	.69
MAN 6630	1-1/2 0ig .56"	Drng CA RHO	.59
MAN 6640	2 0ig .56"	Drng CC RHO	.69
MAN 6650	1-1/2 0ig .56"	Drng CC RHO	.59
MAN 6710	2 0ig .56"	Red CA RHO	.69
MAN 6730	1-1/2 0ig .56"	Red CA RHO	.59
MAN 6740	2 0ig .56"	Red CA RHO	.69
MAN 6750	1-1/2 0ig .56"	Red CC RHO	.59
DL 338	3 0ig .17"	Red CC	.29
DL 338	2 0ig .17"	Red CC	.49
NSN 33	3 0ig .17"	Red CC	.39
HP 5082	4 0ig .11"	Mag. RHO	.39
HP 5082	5 0ig .11"	Mag. RHO	.49
SPA25-09	9 0ig Gas	Discharge	.69
Calc Disp	9 MAN 3s	on board Red	.79
TI 434	9 Dig	Red	.49

LINEAR			
301M	.25	555M	.39
307M	.19	556M	.79
309H	.98	560M	1.95
311H	.59	565M	.99
311N	.59	567M	.99
324N	1.09	723N	.45
340T-5		733H	.49
(7805)	.59	739N	.69
340T-15		741M	.16
(7815)	.59	1414N	.99
370N	.79	1458M	.89
376M	.39	CA3046N	.49
380N	.59	75453	.19
380-BM	.99	75491N	.49
540H	1.59	75492N	.69

Jumbo Red LEDs	12/\$1.00	140/\$10.00
Jumbo Green LEDs	8/\$1.00	100/\$10.00
Jumbo Yellow LEDs	8/\$1.00	100/\$10.00
Jumbo Clear LEDs	12/\$1.00	140/\$10.00

EXAR	
320	1.19
2206	3.90
2207	1.49
2567	1.49
4136	.69
4202	.69
4212	.69
4739	.69

2513(caps)	Char. Gen.	2.95
2513(L.C.)	Char. Gen.	2.95
MM1101	256 bit RAM	.65
MM1103	1K RAM	.75
1702A	EROM	4.75
MM5261	1K RAM	.55
MM5262	1K RAM	.95
F93410	256 bit RAM	.95
2708	8K EROM	\$8.95

SIGNAL DIODES 400mw 100/\$1.00		
2510	Dual 50 bit Shift Reg.	.95
2511	Dual 100 bit Shift Reg.	.95
2518	Hex 32 bit Shift Reg.	1.25
2522	Dual 132 bit Shift Reg.	.95
MM5016	500/512 bit Shift Reg.	.95
SL-5-4025	Quad 25 bit Shift Reg.	.59

CT5002	Calc. Chp	.35
CT5005	Calc. Chp	.75
MM5725	Calc. Chp	.29
MM5736	Calc. Chp	.65
MM5738	Calc. Chp	.95
MM5739	Calc. Chp	.95
MM5314	Clock Chip	2.95
MM5316	Clock Chip	.95
MM5370	Clock Chip	3.95
MM5375AA	Clock Chip	2.95
CT7001	Clock Chip	4.95
8038	Funct. Generator	3.75

IC SOCKETS TT	
Low Profile Solder Tail	
8 pin	\$.16
24 pin	\$.36
14 pin	.19
28 pin	.44
16 pin	.21
40 pin	.61
18 pin	.28

KEYBOARD	
20 Keys - 2 slide switches	
3" x 3-3/4"	\$1.00/3

METAL FILM RESISTORS			
+ 1%, 1/4w, + 50 PPM/OC			
Standard Decade values 10.5 - 464K			
Qty.	Ea.	Min 10/value	Min 100/value
1-99	\$.20	\$.15	
100-999	.20	.10	\$9.00/100
1000-			8.00/100

CERAMIC DISC CAPACITORS - 50V			
1pf	22pf	56pf	120pf
270pf	820pf	820pf	.022uf
5pf	27pf	68pf	150pf
390pf	.001uf	.030uf	
7pf	33pf	82pf	180pf
470pf	.001uf	.030uf	
10pf	56pf	150pf	470pf
.0047uf	.050uf		
100pf	47pf	100pf	220pf
600pf	.01uf	.1uf	
0-10 per value, \$.10ea 10-up per value \$.05ea			
10-up per value \$.05ea			

REGULATED POWER SUPPLY

Plus & minus 5V, 12V and 15V. Uses 3 LM340T and 3 LM307 regulators, 115V/29V CT transformer plus PC board capacitors & diodes. All parts, schematic, instructions PS-29.....\$11.95 + \$1.00 Shppng.

WIRE WRAP	
8 pin	.45
14 pin	.49
16 pin	.55

Carbon Film Resistors ± 5% 1/4w, 1/2w			
Qty.	Ea.	Min 10/value	Min 100/value
1-99	\$.10	\$.05	
100-999	.10	.04	\$3.00/100
1000-			2.50/100

BEZELS - with red filters			
140-2	cut-out 1.125" x 2.375"	max .062" panel thickness	\$1.75
140-4	cut-out 1.160" x 4.375"	max .125" panel thickness	\$2.75

CAPACITOR KIT - ceramic disc			
50V, 24 values, 10 capacitors each			
1pf	33pf	82pf	220pf
820pf	.022uf		
5pf	47pf	100pf	270pf
.001uf	.030uf		
10pf	56pf	150pf	470pf
.0047uf	.050uf		
22pf	68pf	180pf	600pf
.01uf	.1uf		
capacitors only...\$11.95			
Packaged in 15 drawer, 60 compartment cabinet...\$19.95 plus \$2.00 shipping			

DIODES	
Silicon SW diode assorted	400 mw \$0.05ea
1N4148 (1N914)	Silicon diode 400 mw .10
1N3064	Silicon SW diode 400 mw .10
1N4006	Silicon rect. diode 600V 400mw .10
Zener diode 400 mw - 2.4V, 3.6V, 5.1V, 6.5V, 8.2V, 10V, 12V, 14.5V, 15V, 120V	.15
Germanium diode 400 mw	.08

UNIVERSAL BREADBOARD	
Silver plated copper circuits fits any IC and related components. 2 triple rows of 27 holes for DIP. 3-3/16"x5-1/16"	\$1.00

ELECTRONIC BUZZER	
Miniature, Solid State	
6V 15ma (4-9V oper.)	\$1.69 ea.
12V 15ma (8-20V oper.)	\$1.69 ea.

BUGBOOKS	
I & II - Logic, memory text & experiments	\$17.00 /set
Instructors Manual (for I & II)	\$3.00 ea.
III - Introduction, use of UART	\$5.00 ea.
V & VI - Experiments in Digital 8080A programming & interfacing	\$9.50 ea.
555 - Timer applications, experiments	\$19.00 /set
695 - Designers primer and handbook	\$6.95 ea.
CMOS - Designers primer and handbook	\$6.00 ea.
SK10 - E & L Solderless Breadboard	\$16.50 ea.

TANTALUM CAPACITORS - solid dipped			
.1u/35V	\$.20	6.8/16	\$.25
15/50	\$.40		
.22/35	\$.20	6.8/16	\$.25
22/16	\$.25	6.8/16	\$.30
33/16	\$.20	10/16	\$.30
47/16	\$.20	10/16	\$.30
68/16	\$.25	10/16	\$.35
10/25	\$.25	10/25	\$.35
15/20	\$.25	10/25	\$.35
22/16	\$.25	10/25	\$.35
33/16	\$.25	15/10	\$.35
150/15	\$.25	15/20	\$.35

ELEKTR MAGAZINE PROJECTS	
3 1/2 DIGIT DVM - parts pack	
LD101/111 chip set - 2V, 20V, 200V ranges auto zero, auto polarity, .3" LEDs. All components, PC boards, power supply for 115V use. Case not included.	\$44.90 + \$2.00 shipping
Inst. case (VERO 2760D) bezel & filter, cord & banana jacks.	\$11.90 + \$7.75 shipping
Instructions only (refundable with DVM purchase)	\$3.50

I C BREADBOARD	
Silver plated copper circuits holds 5 - 16 pin DIP IC's and interconnection holes. \$1.00	

ZENER DIODE HANDBOOK - Motorola	
Switching Transistor Handbook - Motorola	\$2.50 ea.
CMOS Data Book - Solid State Scientific	\$3.00 ea.
Micro Computer Application Hdbk. - TASIS-8080 microcomputer debugging, architecture and instruction set.	\$6.95 ea.

SOLDER	
60/40 w/rosin in dispenser	
13 fit of .040" dia.	\$1.95

TANTALUM CAPACITOR KIT			
solid dipped, 12 values, 5 each			
.1u/35V	2.2/35	10/25	33/10
.33/35	4.7/16	15/20	47/25
1/35	6.8/16	22/16	56/25
capacitors only...\$14.95			
supplied in styrene utility box...\$19.95			

SCOPE CALIBRATOR - parts pack	
Checks gain & band width of the Y amp & attenuators and freq. calibration of timebase. Build into any scope. All parts, PC board & instructions...\$3.80	

BIMBOARD - BREADBOARD KIT	
Solderless breadboard section has 94 breadboard strips of 5 sockets each. 2 bus strips of 40 sockets each. Component bracket for switches lamps etc., accepts leads .01" to .035" diameter.	\$11.95 ea.

SOLDER	
60/40 w/rosin in dispenser	
13 fit of .040" dia.	\$1.95

TRIMPOT - Single Turn	
Mepeco - Cermet 8014	
5w, ± 100 PPM/°C ± 20%	
500 ohm, 2K, 10K, 25K, 50K, 100K, 500K, 1M.	\$.75 ea.
.69/10-	

TRANSISTORS		
2N1132	PNP Gen Purp. Ampl TO-5	\$.69
2N218A	NPN Low Power Trans TO-5	.69
2N2222A	NPN Low Power Trans TO-18	.29
2N2223	NPN Low Power Trans TO-5	.69
2N2369	NPN Low Power Trans TO-5	.29
2N2904	PNP Low Power Trans TO-5	.49
2N2905A	PNP Low Power Trans TO-5	.76
2N3227	NPN Low Power Trans TO-18	.69
2N3904	PNP Low Power Trans TO-92	.17
2N3906	NPN Low Power Trans TO-92	.17
SCA 13572	NPN Pwr Trans - 200V TO-5	1.75

SIGNAL INJECTOR - parts pack	
Compact portable signal generator that produces 1 Khz square wave keyed at approx .2 Hz. PC board, instructions, plastic case and all components except 5.6V battery and probes...\$9.10	

VECTOR BOARD - Phenolic	
169P44-062 (.1" spacing .42" dia.)	
4-1/4" x 4-1/2" x .0625".....	\$1.15 ea.

SOLDER	
60/40 w/rosin in dispenser	
13 fit of .040" dia.	\$1.95

TRIMPOT - 25 Turn	
Bourns - Cermet 3299W	
PK Mount, vert. adj.	
2K, 10K, 20K	\$1.75 ea

COMPLETE SATISFACTION GUARANTEED.	
SHIPMENT TO US AND CANADA PREPAID UNLESS INDICATED OTHERWISE. OTHER COUNTRIES ADD 10% - EXCESS REFUNDED. ORDERS SHIPPED IN 3 WORKING DAYS FROM RECEIPT. MINIMUM ORDER \$10.00. CALIFORNIA RESIDENTS ADD SALES TAX. MINIMUM CDD OR CHARGE ORDER \$15.00	

MUSIC CLEANER - parts pack	
A treble and bass filter that eliminates snap, crackle & pop without eliminating half the music. May be connected virtually anywhere in an audio system. PC board (for stereo system) all components and instruction.....	\$16.50

INTERNATIONAL ELECTRONICS UNLIMITED
 VILLAGE SQUARE, P.O. BOX 449 | CARMEL VALLEY, CA 93924 USA
 TELEPHONE 408 659-3171



RADIO HUT

1-800-527-2304

Use Our Toll Free Watts Line
For Master Charge and BankAmericard Orders



VARIABLE POWER SUPPLY KIT NO. 1 ONLY \$10.95

- Continuously variable from 5V to 20V
- Excellent regulation up to 1/2 Amp
- Kit includes all components
- Drilled fiberglass P.C. Board
- Case included
- 4400 Mfd of filtering
- One hour assembly



VARIABLE POWER SUPPLY KIT NO. 2

Same as above but with a 1 Amp output, also with case
ONLY \$13.95

This model will power a 5 watt transistorized CB Radio

LOOK AT THIS SPECIAL FROM RADIO HUT

- Power Supply Kit 5V1 amp reg.
- Line regulation .005%
- Load regulation 50mV

Kit includes components, PC board, transformer, fuse and pilot light. Line cord not included

Only \$6.50

60 Hz. Crystal Time Base for Digital Clocks

\$4.50
Buy 2 for \$8.



- 60 Hz output with accuracy comparable to a digital watch
 - Directly interfaces with all MOS clock chips.
 - Super low power consumption (1.5 mA type)
 - Uses latest MOS 17 stage divider IC
 - Eliminates forever the problem of AC line glitches
 - Perfect for cars, boats, campers, or even for portable clocks at ham field days
 - Small size, can be used in existing enclosures
- KIT INCLUDES CRYSTAL, DIVIDER IC, P.C. BOARD PLUS ALL NECESSARY PARTS & SPECS

UNSCRAMBLER



\$19.95

Plugs into earphone or external speaker of any Scanner or Monitor. Guaranteed to unscramble any 1065 call

- Easily tuned
- Full Instruction Included
- Drilled fiberglass P.C. Board
- One Hour Assembly
- Punched Case

7400 TTL DIGITAL CIRCUITS

7400	11	7430	13	7480	31	74153	61
7401	13	7432	23	7481	55	74154	96
7402	13	7433	26	7482	57	74155	89
7403	13	7437	23	7483	67	74156	89
7404	15	7438	23	7485	89	74157	55
7404A	29	7440	13	7489	125	74160	55
7404A	44	7441	76	7490	61	74161	65
7405	13	7442	47	7491	65	74163	65
7406	16	7443	59	7492	43	74164	89
7407	16	7444	59	7493	43	74165	89
7408	19	7445	68	7494	67	74174	85
7409	19	7447	68	7495	67	74175	85
7410	13	7448	71	7496	67	74180	67
7411	18	7450	13	74100	30	74181	193
7412	26	7451	13	74104	49	74182	68
7413	37	7453	13	74107	26	74191	96
7416	15	7454	13	74109	31	74192	79
7420	13	7460	19	74121	29	74193	81
7421	13	7470	27	74123	48	74194	81
7423	25	7472	25	74132	99	74195	69
7425	29	7473	29	74136	99	9316	85
7426	24	7474	29	74138	195	9601	3151
7427	19	7475	47	74141	75	9L04	35
7428	26	7476	31	74151	61		

TTL SPECIAL!

- 9002/7400 10/1 00
 - 9003/7410 10/1 00
 - 9004/7420 10/1 00
 - 9005/7460 6/1 00
 - 9007/7430 10/1 00
 - 9009/7440 10/1 00
 - 9016/7404 8/1 00
 - 9024/74109 3/1 00
 - 9300/74195 3/1 00
- 9000 series parts
Prime from ITT
Pin for Pin
compatible with
7400 series

DTL

- 932 Dual 4 Input Buffer 8/51
- 934 Dual 5 Input NAND Gate 10/51
- 941 One Shot Multivibrator 5/51
- 945 JK F/F 8/51
- 946 Quad 11 Input Gate NAND/NOR 8/51
- 948 JK F/F 10/51
- 950 F/F 10/51
- 951 One Shot Multivibrator 5/51
- 1800 (see 534 above) 10/51
- 1806 Quad 2 Input NAND Gate 10/51
- 9093 Dual JK F/F 8/51
- 9094 Dual JK F/F 8/51
- 9097 Dual JK F/F 8/51
- 9099 Dual JK F/F 8/51
- 9109 Hex Inverter 7/51
- 9110 Hex Inverter 7/51
- 9112 Hex Inverter 7/51
- 9601 One Shot 3/51
- 9930 Dual 4 Input Ext. NAND 8/51
- 9932 Quad 2 Input NAND Buffer 8/51
- 9945 RS F/F 8/51
- 9946 Quad 2 Input NAND 8/51
- 9949 Quad 2 Input NAND 8/51
- 9951 Monostable Multivibrator 8/51
- 9962 Triple 3 Input NAND 8/51

DIODES

- IN 4004 1 Amp 100V PIV 40/\$1
- IN 4004 1 Amp 400V 15/\$1
- IN 4007 1 Amp 1000V 10/\$1

GERMANIUM DIODES

- IN 54A \$8/\$1
- IN 270 10/\$1

ZENER DIODES

- IN 746 3.3V 400M 4/\$1
- IN 752 5.6V 400M 4/\$1
- IN 1958 8.2V 400M 4/\$1
- IN 5259 35V 500M 10/\$1
- IN 5271 100V 500M 10/\$1
- IN 5280 180V 500M 10/\$1

HOUSE # ZENER

- 4.7V 500 MW 10/\$1
- 9. V 500 MW 10/\$1
- 10V 1 Watt 8/\$1
- 15V 500 MW 10/\$1
- 22V 5 Watt 6/\$1

SWITCHING DIODES

- IN 4148/IN914 Long Leads 20/\$1
- IN 4148/IN914 Cut Leads 40/\$1
- IN 4148/IN914 PC Leads 100/\$2

HOUSE # TTL IC's

- 7400 10/1 00
 - 7404 10/1 00
 - 7408 10/1 00
 - 7420 10/1 00
- Please specify 7437 6/1 00
that you 74161 3/1 00
are ordering 74153 3/1 00
- House Number TTL

CRYSTALS

- 300 KHZ \$1 50
- 3.57945 \$1 25

COUNTER AND CLOCK CHIPS

- MM5252 Clock Chip \$4.99
- MM5316 Clock Chip 3.75
- MM5250 Alarm Clock 3.75
- MM5380 Alarm Chip 2.95
- FCM7010 Direct Drive Clock Chip 4.95
- MM5005 4 Digit Counter w/Latch 6.50
- MM5002 4 Digit Counter 8.95
- MM5095 6 Digit LPI Down Counter 12.95
- MM50397 6 Digit Elapsed Timer 8.95
- CT5005 Calculator Chip w/Specs 1.25
- MM5021 Cal Chip w/Specs 2.50

SOCKET SPECIAL!
28 PIN IC SOCKET
3 FOR \$1
WHEN PURCHASED
W/ CLOCK IC

74LS00 LOW POWER SCHOTTKY

74LS00	21	74LS47	73	74LS136	37	74LS258	71
74LS02	21	74LS51	26	74LS137	37	74LS260	26
74LS03	21	74LS54	26	74LS139	71	74LS266	26
74LS04	28	74LS55	26	74LS145	100	74LS279	55
74LS05	28	74LS73	35	74LS151	70	74LS290	70
74LS08	21	74LS74	35	74LS153	70	74LS293	61
74LS09	28	74LS76	49	74LS155	69	74LS295	95
74LS10	21	74LS83	73	74LS156	70	74LS298	95
74LS11	21	74LS85	135	74LS157	75	74LS365	55
74LS13	45	74LS86	36	74LS158	71	74LS366	55
74LS14	99	74LS90	55	74LS160	85	74LS367	55
74LS15	26	74LS92	55	74LS161	85	74LS368	55
74LS20	24	74LS93	55	74LS162	85	74LS390	175
74LS21	26	74LS94	35	74LS163	85	74LS393	145
74LS22	28	74LS112	38	74LS164	149	74LS670	230
74LS26	32	74LS113	38	74LS168	85	74LS192	95
74LS27	32	74LS114	38	74LS169	85	74LS193	95
74LS30	26	74LS122	49	74LS170	169	74LS194	95
74LS32	32	74LS125	99	74LS173	110	74LS195	100
74LS37	32	74LS127	49	74LS174	100	74LS196	85
74LS38	32	74LS126	47	74LS175	81	74LS197	85
74LS40	26	74LS132	79	74LS190	95	74LS251	85
74LS42	65	74LS133	35	74LS191	95	74LS253	81
						74LS257	71

74H SERIES TTL

74H00	18	74H21	29	74H53	29	74H73	39
74H05	29	74H40	29	74H61	25	74H74	39
74H20	29	74H50	20	74H72	45		

CMOS

CD4004	19	CD4017	95	CD4040	100	CD4071	19
CD4001	19	CD4018	95	CD4041	69	CD4081	19
CD4002	19	CD4019	95	CD4042	69	CD4087	35
CD4006	19	CD4020	97	CD4043	60	CD4088	280
CD4007	19	CD4021	97	CD4044	60	CD4510	100
CD4009	47	CD4022	97	CD4046	139	CD4512	110
CD4010	39	CD4023	95	CD4047	150	CD4516	79
CD4011	19	CD4024	75	CD4048	39	CD4520	69
CD4012	29	CD4025	19	CD4050	35	CD4518	110
CD4013	32	CD4027	39	CD4051	19	CD4528	85
CD4014	78	CD4028	85	CD4053	119	74C02	32
CD4015	78	CD4029	99	CD4056	15	74C04	32
CD4016	32	CD4030	35	CD4065	78	74C107	79

VOLTAGE REGULATORS

7805 Pos	5V 1 Amp	99	7818 Pos	18V 1 Amp	99
7806 Pos	6V 1 Amp	99	7824 Pos	24V 1 Amp	99
7808 Pos	8V 1 Amp	99	7805 Neg	5V 1 Amp	110
7812 Pos	12V 1 Amp	99	7912 Neg	12V 1 Amp	110
7815 Pos	15V 1 Amp	99	7915 Neg	15V 1 Amp	110

723 VOLTAGE REGULATORS

Output voltages variable from 2 volts to 37 volts
A very versatile and popular device. — 14 PIN DIP

MOTOROLA VOLTAGE REGULATOR
MC1469R TO-66 9 lead package for 3 to 30V outputs. Provides 600 MA direct output or more by using an external power transistor. Regular catalog price — \$4.00 each! With specs \$1.95 each

ITT LED DRIVERS

- ITT 501 Quad Seg. Dr. 35
 - ITT 502 Hex Digit Dr. 49
 - ITT 503 Quad Seg. Dr. 49
 - ITT 506 Hex Digit Dr. 49
 - ITT 509 8 Seg. Dr. 49
 - ITT 511 Quad Seg. Dr. 55
 - ITT 514 8 Digit Dr. 59
- We have 100's of thousands of listed parts. These parts are 100% Prime.

BRIDGE RECTIFIERS

- 1 Amp 200V 6/\$1
- 6 Amp 50V 1.10
- 10 Amp 50V 1.25
- 25 Amp 50V 1.39

SOCKETS

- 8 Pin Low Profile 20
- 14 Pin Low Profile 22
- 16 Pin Low Profile 25
- 18 Pin Low Profile 30
- 28 Pin Low Profile 69
- 40 Pin Low Profile 89

MUSICAL HORN

One tune supplied with each kit. Additional tunes — \$6.95 each. Special tunes available. Standard tunes now available: — Dixie — Eyes of Texas — Oh Wisconsin — Yankee Doodle Dandy — Notre Dame — Pink Panther — Aggie War Song — Anchors Aweigh — Never on Sunday — Yellow Rose of Texas — Deep in the Heart of Texas — Boomer Sooner — Bridge over River Kwai

- CAR & BOAT KIT \$34.95
- HOME KIT \$26.90
- Special Design Case \$3.50

709	Operational Amplifier	25	LM 377	Dual 2W Amplifier	1.85
710	Differential Comparators	40	LM 3900	Quad Op. Amplifier	.40
711	Dual Differential Comp	35	LM 741	Operational Amplifier	.25
712	Half Adder	25	LM 748	Operational Amplifier	.25
749	Stereo Pre-Amp by Fairchild	2.51	NE 563	Quad Timer	1.95
LM 301	Operational Amplifier	30	NE 555	Timer	.40
LM 307	Operational Amplifier	30	NE 566	Dual Timer	.95
LM 308	Operational Amplifier	30	NE 567	1 one Decoder	1.25
LM 309K	5V Lamp Regulator	1.49	1498	Dual Op. Amplifier	.55
LM 710	Voltage Comparator	25	75491	Quad Segment Driver	.35
LM 311	Voltage Comparator	85	75492	Hex. Digit Driver	.75
LM 718	Operational Amplifier	15	3043	IF Amplifier	.35
LM 323	Voltage Comparator	69	8038	Voltage Cont. Osc	3.95
LM 324	Quad Operational Amplifier				

RTL's by FAIRCHILD

The most popular digital IC's ever produced. Very hard to find!

- UL DUAL 2 INPUT NOR 99
- UL923 JK FLIP FLOP \$1.19


LINEARS

UNMARKED 1702A EPROMS 3.50 Ea. or 10/\$32.00 LIMITED SUPPLY

12V 1 AMP POWER SUPPLY INPUT VOLTAGE 25V MAX. OUTPUT CURRENT 1 AMP. MAX. LOAD REGULATION 50mV. OUTPUT VOLTAGE 12V. LINE REGULATION 0.01%. KIT CONTAINS ALL PARTS EXCEPT FOR LINE CORD AND TRANSFORMER. ONLY \$4.50

TELEPHONE RELAY Assembled & Tested \$29.95

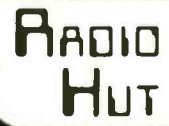SURREPTITIOUS INTERCEPTION OF TELEPHONE CONVERSATION IS A VIOLATION OF FEDERAL LAW AND THIS DEVICE IS NOT DESIGNED NOR INTENDED FOR SUCH USE.



(All prices subject to change without prior notice.)
P.O. BOX 38323
DALLAS, TEXAS 75238
AN EMPIRE IND. CO.

Money back guarantee. NO COD'S. Texas residents add 5% sales tax. Add 5% of order for postage and handling. Orders under \$15.00 add 75 cents. Foreign orders add 20% for postage. For your convenience, call your Bank Americard or Master Charge orders in on our Toll Free Watts Line: 1-800-527-2304. Texas residents call collect: 1-214-271-8423.

CIRCLE 65 ON FREE INFORMATION CARD



S.D. COMPUTER PRODUCTS

AN EMPIRE IND. CO.

P.O. BOX 28810C DALLAS, TEXAS 75228

64K FOR \$995.00


At last! The popular Expandoram is available in a 16k multiple version. Similar to our 32k Expandoram, the new Super Expandoram is offered in 16k, 32k; 48k and 64k. Low power devices mean the very lowest power consumption. Allow 3-4 weeks for delivery.

16K — \$281.00 48K — \$757.00
32K — \$519.00 64K — \$995.00

32K FOR \$475 EXPANDORAM KIT 24K FOR \$367.00

MEMORY CAPACITY
MEMORY ADDRESSING
MEMORY WRITE
PROTECTION

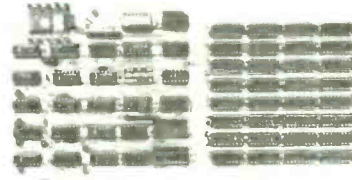8K, 16K, 24K, 32K using Mostek MK4115 with 8K boundaries and protection. Utilizes DIP switches. PC board comes with sockets for 32K operation. Orders now being accepted. Allow 6 to 8 weeks for delivery.



INTERFACE CAPABILITY
Control, data and address inputs utilizes low power Schottky devices

POWER REQUIREMENTS
+ 5VDC 400MA DC
- 18VDC 400MA DC
- 18VDC 30MA DC

on board regulation is provided. On board (invisible) refresh is provided with no wait states or cycle stealing required.

MEMORY ACCESS TIME
IS 375ns
Memory Cycle Time is 500ns

Buy an S100 compatible 8K Ram Board and upgrade the same board to a maximum of 32k in steps of 8K at your option by merely purchasing more ram chips from S.D. Sales! At a guaranteed price — Look at the features we have built into the board.

16K FOR \$259.00

8K FOR \$151.00

Z-80 CPU BOARD KIT — \$139.

CHECK THE ADVANCED FEATURES OF OUR Z-80 CPU BOARD. Expanded set of 158 instructions, 8080A software capability, operation from a single 5VDC power supply, always stops on an M1 state, true sync generated on card (a real plus feature!), dynamic refresh and NMI available, either 2MHz or 4MHz operation, quality double sided plated through PC board, parts plus sockets priced for all IC's. *Add \$10 extra for Z-80A chip which allows 4MHz operation. Z-80 chip with Manual — 29.95



S.D. SALES NEW EXPANDABLE EPROM BOARD

16K or 32K EPROM \$49.95 w/out EPROM
Allows you to use either 2708's for 16K of Eprom or 2716's for 32K of Eprom.

KIT FEATURES:

1. All address lines & data lines buffered.
2. Quality plated through P.C. Board, including solder mask and silk screen.
3. Selectable wait states.
4. On board regulation provided.
5. All sockets provided w/board.

WE CAN SUPPLY 450ns 2708's AT \$11.95 WHEN PURCHASED WITH BOARD.

4K LOW POWER RAM KIT

Fully Buffered — on board regulated — reduced power consumption utilizing low power 21L02 — 1 500ns RAMS — Sockets provided for all IC's. Quality plated through PC board. *Add \$10 for 250ns PAM operation



The Whole Works - \$79.95

8K LOW POWER RAM — \$159.95

Fully assembled and tested. Not a kit! Insa: — Altair — S-100 Buss compatible, uses low power static 21L02-500ns fully buffered on board regulated, quality plated through PC board. Including solder mask. 8 pos. dip switches for address select.



250 ns Operation
\$189.95

6 DIGIT ALARM CLOCK KIT

Features: Litronix dual 1/2" displays, Mostek 50250 super clock chip, single I.C. segment driver, SCR digit drivers. Kit includes all necessary parts (except case). Xfmr optional. Eliminate the hassle.

AC XFMR — \$1.50 Case \$3.50 \$12.95

Bowmar 4 Digit LED Readout Array Full 1/2" Litronix Jumbo Dual Digit LED Displays

4 JUMBO .50" DIGITS ON ONE STICK!
WITH COLONS & AM/PM INDICATOR

DL 722 - C.C. DL 728 - C.C.
DL 721 8 C.A. DL 727 - C.A.
99c \$1.29

NEW FROM S.D. "VERSAFLOPPY"™ KIT THE VERSATILE FLOPPY DISK CONTROLLER ONLY \$149.00

Features: IBM 3740 Soft Sectors Compatible. S-100 BHS Compatible for 280 or 8080. Controls up to 4 Drives (single or double sided). Directly controls the following drives:
1. Shugart SA800/450 Mini Floppy.
2. Shugart SA800/850 Standard Floppy.
3. PERSCI 70 and 277.
4. MFE 700/750.
5. CDC 940/9406

34 Pin Connector for Mini Floppy, 50 Pin Connector for Standard Floppy. Operates with modified CP/M operating system and Basic Compiler.
The new "Versafloppy" from S.D. Computer Products provides complete control for many of the available Floppy Disk Drives. Both Mini and Full Size. At the heart of "Versafloppy" is the powerful Western Digital FD1718-1 Single Density Controller Chip. This allows a great flexibility via Control Software. Listings for Control Software are included in the price.

FD 1718-1 CHIP ALONE \$39.95

Low Cost Cassette Interface Kit



Features: Play and record R.C. Standard 2400/1200 Hz tapes, 300 Baud, TTL I/O Compatible, Phase Lock Loop, Both 22 Pin Connector and 8 Pin Motes Connector. Comes partially assembled. Oscillator and phase lock loop pre-tuned to R.C. Standard. Selector switch sends cassette data or auxiliary input data to microprocessor. LED indicates logic level.

\$19.95

Jumbo LED Car Clock Kit

FEATURES:

- A. Bowmar Jumbo 5 inch LED array
- B. MOSTEK — 50250 — Super clock chip
- C. On board precision Crystal time base
- D. 12 or 24 hour Real Time format
- E. Perfect for cars, boats, vans, etc
- F. PC board and all parts (less case) Inc.

Alarm option — \$1.50
AC XFMR — \$1.50



\$16.95

RAMS

21L02 500NS	8 11 50
21L02 250NS	8 15 95
2114 — 4K	14 95
1101A — 256	8 54 00
1103 — 1K	35
MK 4115 8K	15 45
74S 200 256	3 95

CPU's

Z-80 includes manual	29 95
Z-80A includes manual	34 95
8080A CPU & BIT	11 95
8008 CPU & BIT	6 95

PROMS

1702A - 1K - 1.5us	3.95 or 10/35
2708 - 8K - 450ns	14.95
5204 - 4K	7.95
82S129 — 1K	2.50
2708U 8K signetics 650ns	9.95

COUNTER CHIPS

MK50397 6 Digit elapsed timer	8.95
MK50250 Alarm clock	4.99
MK50380 Alarm chip	2.95
MK50395 6 digit up/dn count	12.95
MK5002 4 digit counter	8.95
MK5021-Cal. chip sq. root	2.50

★ ★ ★ ★ SUPER FLOPPY SPECIAL ★ ★ ★ ★

S. D. SALES' VERSAFLOPPY S-100 CONTROLLER BOARD PLUS SHUGART SA 400 FLOPPY DISK DRIVE INCLUDING CABLE FOR ONLY \$479.00

MICRO-DIP \$1.95

New — Series 2300
The World's Smallest
Coded BCD Dual-In-Line
Switch! PC Mount
2300 02G BCD 1-2-4-8
2300 12G BCD 1-2-4-8
Compliment

★ ★ JOY STICKS ★ ★

FOUR 100 K-OHMS
POTS
Ideal for
electronic
games
\$3.95

Z-80

Programming Manual
IN DEPTH DETAIL OF
THE Z-80 CPU
MICRO-COMPUTER
S. D. SALES SPECIAL
\$9.95

* Silicon Rectifier Special 1N4007 *

Thermistors 1.5K ohm	5/\$1.00
Tantalum Caps 1 mfd. 20VDC	
P.C. Leads	15/\$1.00
Flat Pack IC Assort.	20/\$1.00
Electrical Coil	
13T Type C - 10T Type C	12/\$1.00
2 Transistor Audio	8/\$1.00
Trimmer Pots	
10K, 20K, 25K, Mini	10/\$1.00
Disc Caps For Bypass	
.01 mfg - 100 WUDC	
PC Leads	40/\$1.00
New Cambion Jacks	
Part #450-4352	
Gold Plated	50/\$1.00
1 amp 1000 PN.	10/\$1.00
Photocell Assortment	12/\$1.00
Plastic Readout Filters	
Amber	6/\$1.00
Disc Cap Assortment	60/\$1.00
P.C. Lead Diodes	
1N4148 1N 914	100/\$2.00
1N4002-1A-100 PN	40/\$1.00
MICA Trimmer	
PC402 Miniature	
1.5-20 P.C. P.C. Mount.	4/\$1.00
Resistor Special 22 ohm	
Carbon Comp.	25/\$1.00
Resistor Assortment 1/4 W 5% &	
10% PC leads	200/\$1.50

CHOOSE \$1. FREE MERCHANDISE FROM ASTERISK ITEMS ON EACH \$15 ORDER

MICROPROCESSOR CHIPS

8212 - I/O port	3.50
8214 — P.I.C.	12.95
8216 — Non Invert Bus	4.95
8224 — Clock Gen.	4.95
8226 — Invert Bus	3.95
PIO for Z-80	14.95
CTC for Z-80	14.95
8228 Sys. Controller	8.20
8251 Prog. comm. interface	10.95
8255 prog. prep. interface	13.50
8820 Dual Line Recv	1.75
8830 Dual Line Dr.	1.75
2513 Char. Gen.	7.50
8838 Quad Bus. Recvr.	2.00
74LS138N — 1/8 decoder	.99
8797-Hex Tri-State Buffer	1.25
1488/1489 RS232	1.50
TR 1602B Uart	3.95
TR 1863 Uart	8.50
FD 17718-1	39.95

CMOS

4001	19	4029	99
4002	19	4042	69
4011	19	4047	1.50
4013	32	4049	35
4016	32	4069	23
4017	95	4071	19
4020	97	4076	97
4022	97	14518	1.10
4024	75	14528	85
4027	39	14529	85

CALL IN YOUR BANKAMERICARD (VISA) OR MASTER CHARGE ORDER IN ON OUR CONTINENTAL TOLL FREE WATTS LINE:

1-800-527-3460

Texas Residents Call Collect:
214/271-0022


DEALER INQUIRIES INVITED!



NO COD'S. TEXAS RESIDENTS ADD 5% SALES TAX. ADD 5% OF ORDER FOR POSTAGE & HANDLING. ORDERS UNDER \$10. ADD 75c HANDLING FOREIGN ORDERS — U. S. FUNDS ONLY!

SUPER SALE!

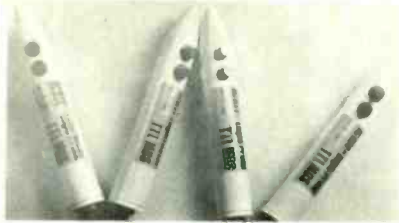Offer Expires May 18, 1978
LOW COST LOGIC PROBES



ORDER NOW SUPPLIES LIMITED

This Logic Probe is good for TTL and CMOS Integrated Circuits. The Probe can check high, low and pulsating levels in digital breadboarding and other electronic circuits.

The Logic Probe Kit comes complete with all parts and instructions and there is an assembled version also. The Logic Probe Kit includes 2 LED's, wire, case, and all other materials.

COMPLETE KIT.....\$13.25—Postpaid
ASSEMBLED ONLY.....\$17.50—Postpaid

Offer not valid In N.Y. State
No Foreign Orders

WOLF ELECTRONICS Mailing
1361 Flatbush Ave. Address
Bklyn, N.Y. 11210 Only

CIRCLE 68 ON FREE INFORMATION CARD

POWER booster, in car, 25 watts stereo, transformerless. Guitar amplifier, up to 250 watts. Schematic, parts list, \$5.00 each, \$7.50 both. BURMON, P.O. Box 2483, Dearborn, MI 48123



YES, YOU CAN BUILD AN ELECTRONIC ORGAN

That has a PIPE ORGAN SOUND

With **DEVTRONIX** easy to build assemblies. Own the ultimate in organ design & sound at 1/2 the cost of commercial organs.

Several models to choose from.

BROCHURE AND DEMO RECORD \$1.00



Dept. B
5872 Amapola Dr.
San Jose, CA 95129

RECORDS-TAPES! Discounts to 73%; all labels; no purchase obligations; newsletter; discount dividend certificates; 100% guarantees. Free details. **DISCOUNT MUSIC CLUB**, 650 Main St., Dept. 3-0478, New Rochelle, NY 10801

BETAMAX 2-Hour video Cassette Recorder. \$200 under list. Cassettes and prerecorded movies at discount prices. **A&D ELECTRONICS**, 5331 Thrasher Drive, Cincinnati, OH 45239

HIGHLY PROFITABLE ONE-MAN ELECTRONIC FACTORY

Investment unnecessary, knowledge not required. Sales handled by professionals. Ideal home business. Write today for facts! **Postcard will do. Barta-RE-D, Box 248, Walnut Creek, CA 94597.**

COMPUTER, peripheral, technical reports; project supplies; kits. Send \$1 for **THE CPU HOBBYIST**, Box 738-RE, College Park, MD 20740

IC's—100 assorted 7400 series—all marked \$12.50 ppd—send stamp for bargain list. **GULL ELECTRONICS**, 12690 Rte. 30, N. Huntingdon, PA 15642

SAVE UP TO 85% GOV'T SURPLUS and NEW EQUIP'T

Powerful Battery Motor
BUILD MOTORIZED BICYCLE, ELECTRIC CAR, ETC.
\$29.95
F.O.B. SOURCE
Normal Retail Over \$100.00

COMPACT 12 V. BATTERY FOR USE WITH ABOVE MOTOR
\$14.95
Normal Retail Over \$30.00

SURPLUS CENTER P.O. Box 122288 Lincoln, Nebraska Zip Code 68501

Send 25c Coin or Stamps
BIG, Equip. Catalog
LOWEST PRICES ON:
-TORQUE COMPRESSORS
-SURVEYING INSTRUMENTS
-WINCHES
-GEAR PUMPS
-CABLE SPEED REDUCERS
-WHEELS
-ELECTRONICS
-TELEVISIONS
-MANY OTHERS

RC-101 CURVE TRACER
STILL BY FAR THE LOWEST COST FULL FUNCTION CURVE TRACER ON THE MARKET. ATTACHES TO YOUR SCOPE IN SECONDS. USED BY EDUCATORS, PROFESSIONALS AND HOBBYISTS ALL OVER THE WORLD. 30 DAY MONEYBACK GUARANTEE.


Lab Science \$49.50
ADD \$2 PALM
COLO. RES. ADD 3% SALES TAX

PO BOX 1972, BOULDER, COLO. 80306

NEW, adjustable, three output, regulated power supply, plus 900 parts worth over \$400.00 in complete **cartrivision** television electronic assembly. Documentation included. Perfect for **microprocessor** and all electronic applications. \$17.95 plus \$3.50 S&H. Master Charge, BankAmericard. Free brochure. **MADISON ELECTRONICS**, 369, Madison, AL 35758. Satisfaction guaranteed

NAME brand test equipment. Up to 50% discount. Free catalog and price list. **SALEN ELECTRONICS**, P.O. Box 82, Skokie, IL 60076

MAKE YOUR OWN AUTOMATIC STROBE KIT

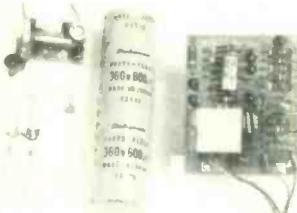

We have all the parts to custom design your own automatic photo graphic strobe. These individual modules may be put together in several different ways, depending on how powerful, or whether you want automatic shut off. We have a DC to DC power supply, that raises the output of 4 NICADs from 4.8 volts, to 320 volts. We have the trigger coil, to fire the flash tube. We have 2 flash tubes, a straight tube 2" long, and a horseshoe tube 1 1/2" long.

a small, high voltage, high capacity capacitor, rated at 360 V, 600 mfd. 38 watt seconds., an electronic cut off device that shuts off the flash tube when the exposure is correct. You may make up your own kit by choosing the parts you wish. We list the price of each part, but when 3 or more parts are chosen, you may deduct 10% from the total. We suggest that only one capacitor be used if the straight flash tube is used. With the horseshoe tube, 2 capacitors may be used for greater output. Use of the cut off module is optional. We provide circuitry for the entire system.

	STOCK NO.	
DC to DC power supply	5528R	\$4.95
Trigger coil	5565R	\$1.50
Capacitor	2675R	\$2.00
Horseshoe flash tube	9941R	\$3.00
Straight flash tube	9244R	\$2.50
Cut-off module	6423R	\$2.50

VIDEOCUBE -TV/COMPUTER INTERFACE

taind RF oscillator-modulator, allowing easy interface with any video output device to a standard TV set. We provide a reprint of article from **RADIO-ELECTRONICS**. Approved by FCC. **VIDEOCUBE** is a self con-
STOCK NO.5500R Complete kit of parts. \$13.95 2/26.00
STOCK NO.5500PR Partial kit. (Special parts) \$9.95 2/18.00

DELTA ELECTRONICS

7 OAKLAND ST., P.O. Box 2
AMESBURY, MASS. 01913

BOSTON, MASS.


DELTA ELECTRONICS WAREHOUSE OUTLET
590 Commonwealth Ave, Boston, Mass.

ATLANTA, GA.

DELTA ELECTRONICS HOBBIES
5151 Bufor Highway, Atlanta, Ga.



Why Wait?

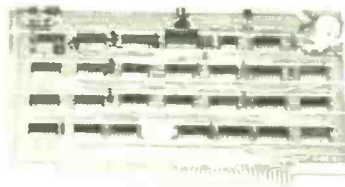

The Tarbell Cassette Interface

- Plugs directly into your IMSAI or ALTAIR*
- Fastest transfer rate: 187 (standard) to 540 bytes/second
- Extremely Reliable — Phase encoded (self-clocking)
- 4 Extra Status Lines, 4 Extra Control Lines
- 37-page manual included
- Device Code Selectable by DIP-switch
- Capable of Generating Kansas City tapes also
- No modification required on audio cassette recorder
- Complete kit \$120, Assembled \$175, Manual \$4

TARBELL ELECTRONICS

20620 S. Leapwood Ave., Suite P, Carson, Ca. 90746
(213) 538-4251

California residents please add 6% sales tax
*ALTAIR is a trademark/tradename of MITS, INC.


CIRCLE 40 ON FREE INFORMATION CARD

CIRCLE 18 ON FREE INFORMATION CARD

NEW LSI TECHNOLOGY
FREQUENCY COUNTER

TAKE ADVANTAGE OF THIS NEW STATE-OF-THE-ART COUNTER FEATURING THE MANY BENEFITS OF CUSTOM LSI CIRCUITRY. THIS NEW TECHNOLOGY APPROACH TO INSTRUMENTATION YIELDS ENHANCED PERFORMANCE, SMALLER PHYSICAL SIZE, DRASTICALLY REDUCED POWER CONSUMPTION [PORTABLE BATTERY OPERATION IS NOW PRACTICAL], DEPENDABILITY, EASY ASSEMBLY AND REVOLUTIONARY LOWER PRICING!

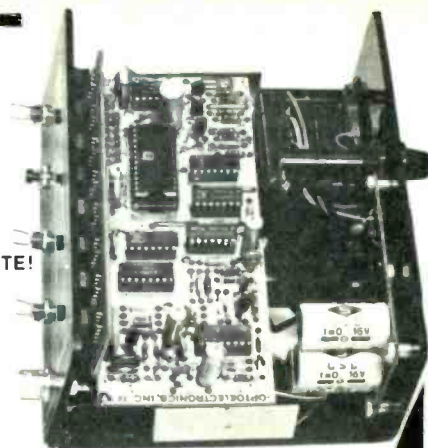- KIT #FC-50C 60 MHZ COUNTER WITH CABINET & P.S. **\$119⁹⁵** COMPLETE!
- KIT #PSL-650 650 MHZ PRESCALER [NOT SHOWN] 29.95
- MODEL #FC-50WT 60 MHZ COUNTER WIRED, TESTED & CAL. 165.95
- MODEL #FC-50/600 WT. 600 MHZ COUNTER WIRED, TESTED & CAL. 199.95



SIZE:
3" High
6" Wide
5 1/2" Deep

FEATURES AND SPECIFICATIONS:

DISPLAY: 8 RED LED DIGITS .4" CHARACTER HEIGHT
GATE TIMES: 1 SECOND AND 1/10 SECOND
PRESCALER WILL FIT INSIDE COUNTER CABINET
RESOLUTION: 1 HZ AT 1 SECOND, 10 HZ AT 1/10 SECOND.
FREQUENCY RANGE: 10 HZ TO 60MHZ. [65 MHZ TYPICAL].
SENSITIVITY: 10 MV RMS TO 50 MHZ, 20 MV RMS TO 60 MHZ TYP.
INPUT IMPEDANCE: 1 MEGOHM AND 20 PF.
[DIODE PROTECTED INPUT FOR OVER VOLTAGE PROTECTION.]
ACCURACY: ± 1 PPM [± .0001%]. AFTER CALIBRATION TYPICAL.
STABILITY: WITHIN 1 PPM PER HOUR AFTER WARM UP [0.001% XTAL]
IC PACKAGE COUNT: 8 [ALL SOCKETED]
INTERNAL POWER SUPPLY: 5 V DC REGULATED.
INPUT POWER REQUIRED: 8-12 VDC OR 115 VAC AT 50/60 HZ.
POWER CONSUMPTION: 4 WATTS



KIT #FC-50C IS COMPLETE WITH PREDRILLED CHASSIS ALL HARDWARE AND STEP-BY-STEP INSTRUCTIONS. WIRED & TESTED UNITS ARE CALIBRATED AND GUARANTEED.


PLEXIGLAS CABINETS

Great for Clocks or any LED Digital project Clear-Red Chassis serves as Bezel to increase contrast of digital displays.

- CABINET I**
3"H, 6 1/4"W, 5 1/2"D Black, White or Clear Cover
 - CABINET II**
2 1/2"H, 5"W, 4"D \$6.50 ea.
- RED OR GREY PLEXIGLAS FOR DIGITAL BEZELS
3"x6"x1/8" 95¢ ea. 4/93

SEE THE WORKS Clock Kit
Clear Plexiglas Stand

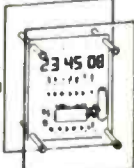- 6 Big .4" digits
- 12 or 24 hr. time
- 3 set switches
- Plug transformer
- all parts included



Plexiglas is Pre-cut & drilled
Kit #850-4CP
Size 6"H, 4 1/4"W, 3"D
Assembled \$29⁹⁵
\$23⁵⁰ ea. 2/45.

60 HZ.

XTAL TIME BASE:
Will enable Digital Clock Kits or Clock-Calendar Kits to operate from 12V DC.
1"x2" PC Board
Power Req: 5-15V (2.5 MA TYP.)
Easy 3 wire hookup
Accuracy ± 2PPM
#TB-1 (Adjustable)
Complete Kit \$4⁰⁵
Wir & Cal \$9.95

SPECIAL PRICING!
PRIME - HIGH SPEED RAM


21L02-3 400 NS
LOW POWER - FACTORY FRESH
1-24 \$1.75 ea. 100-199 \$1.45 ea.
25-99 1.60 ea. 200-999 1.39 ea.
1000 AND OVER \$1.29 ea.

6-DIGIT LED CLOCK CALENDAR KIT
DATE-TIME-SNOOZE ALARM & MORE... KIT 700L

FOR THE BUILDER THAT WANTS THE BEST. FEATURING 12 OR 24 HOUR TIME - 29-30-31 DAY CALENDAR. ALARM, SNOOZE AND AUX. TIMER CIRCUITS

Will alternate time (8 seconds) and date (2 seconds) or may be wired for time or date display only, with other functions on demand. Has built-in oscillator for battery back-up. A loud 24 hour alarm with a repeatable 10 minute snooze alarm, alarm set & timer set indicators. Includes 110 VAC/60Hz power pack with cord and top quality components through-out.

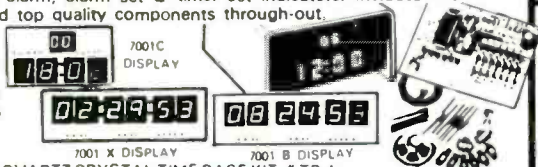- KIT - 7001B WITH 6 - 5" DIGITS \$39.95
- KIT - 7001C WITH 4 - 6" DIGITS & 2 - 3" DIGITS FOR SECONDS \$42.95
- KIT - 7001X WITH 6 - 6" DIGITS \$45.95



KITS ARE COMPLETE (LESS CABINET)


ALL 7001 KITS FIT CABINET I AND ACCEPT QUARTZ CRYSTAL TIME BASE KIT # TB 1

PRINTED CIRCUIT BOARDS for CT 7001 Kits sold separately with assembly info. PC Boards are drilled Fiberglass, solder plated and screened with component layout.

Specify for 7001
B, C or X - \$7.95

AUTO BURGLAR ALARM KIT

AN EASY TO ASSEMBLE AND EASY TO INSTALL ALARM PROVIDING MANY FEATURES NOT NORMALLY FOUND. KEYLESS ALARM HAS PROVISION FOR POS & GROUNDING SWITCHES OR SENSORS. WILL PULSE HORN RELAY AT THE RATE OR DRIVE SIREN. KIT PROVIDES PROGRAMMABLE TIME DELAYS FOR EXIT ENTRY & ALARM PERIOD. UNIT MOUNTS UNDER DASH - REMOTE SWITCH CAN BE MOUNTED WHERE DESIRED. CMOS RELIABILITY RESISTS FALSE ALARMS. & PROVIDES FOR ULTRA DEPENDABLE ALARM. DO NOT BE FOOLED BY LOW PRICES! THIS IS A TOP QUALITY COMPLETE KIT WITH ALL PARTS INCLUDING DETAILED DRAWINGS AND INSTRUCTIONS OR AVAILABLE WIRED AND TESTED.

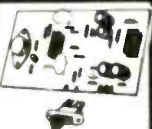

KIT #ALR-1 \$9.95
#ALR-1WT WIRED & TESTED \$19.95

VARIABLE REGULATED 1 AMP POWER SUPPLY KIT

- VARIABLE FROM 4 TO 14V
 - SHORT CIRCUIT PROOF
 - 723 IC REGULATOR
 - 2N3055 PASS TRANSISTOR
 - CURRENT LIMITING AT 1 Amp
- KIT IS COMPLETE INCLUDING DRILLED & SOLDER PLATED FIBERGLASS PC BOARD AND ALL PARTS (Less TRANS-FORMER) KIT#PS-01 \$8.95
TRANSFORMER 24V CT will provide 300MA at 12V and 1 Amp at 5V. \$3.50

MOBILE LED CLOCK

12/24 HR. 4" DIGITS!
MODEL 12 VOLT AC or #2001 DC POWERED



- 6 JUMBO .4" RED LED'S BEHIND RED FILTER LENS WITH CHROME RIM
 - SET TIME FROM FRONT VIA HIDDEN SWITCHES • 12/24-Hr. TIME FORMAT
 - STYLISH CHARCOAL GRAY CASE OF MOLDED HIGH TEMP. PLASTIC
 - BRIDGE POWER INPUT CIRCUITRY - TWO WIRE NO POLARITY HOOK-UP
 - OPTIONAL CONNECTION TO BLANK DISPLAY [Use When Key Off in Car. Etc.]
 - TOP QUALITY PC BOARDS & COMPONENTS - INSTRUCTIONS.
 - MOUNTING BRACKET INCLUDED
- KIT #20G1 \$27⁹⁵ 3 OR \$25⁹⁵ 115 VAC \$250
COMPLETE KIT EA. MORE EA. Power Pack #AC-1 EA.
- ASSEMBLED UNITS WIRED & TESTED ORDER #2001 WT [LESS 9V. BATTERY] \$37⁹⁵ 3 OR \$35⁹⁵
Wired for 12-Hr. Op. If not otherwise specified. EA. MORE EA.



OPTOELECTRONICS, INC.

5821 N.E. 14th AVENUE,
FORT LAUDERDALE, FLA. 33334
PHONE (305) 771-2050 / 771-2051

ORDER BY PHONE OR MAIL
COD ORDERS WELCOME

ORDERS TO USA & CANADA ADD 5% FOR SHIPPING, HANDLING & INSURANCE. ALL OTHERS ADD 10% ADDITIONAL \$1.00 CHARGE FOR ORDERS UNDER \$15.00 - COD FEE \$1.00. FLA. RES. ADD 4% STATE TAX.



CIRCLE 59 ON FREE INFORMATION CARD

SOCKET JUMPERS

Mates with two rows of .025" sq. or dia. posts on patterns of 100 centers and shielded receptacles. Probe access holes in back. Choice of 6" or 18" length.

Part No.	No. of Contacts	Length	Price
924003-18R	26	18"	\$ 5.38 ea.
924003-06R	26	6"	4.78 ea.
924005-18R	40	18"	8.27 ea.
924005-06R	40	6"	7.33 ea.
924006-18R	50	18"	10.31 ea.
924006-06R	50	6"	9.15 ea.

JUMPER HEADERS

Solder to PC boards for instant, plug-in access via socket-conductor jumpers. .025" sq. posts. Choice of straight or right angle.

Part No.	No. of Posts	Angle	Price
923863-R	26	straight	\$1.28 ea.
923873-R	26	right angle	1.52 ea.
923865-R	40	straight	1.94 ea.
923875-R	40	right angle	2.30 ea.
923866-R	50	straight	2.36 ea.
923876-R	50	right angle	2.82 ea.

INTRA-CONNECTOR

Provides both straight and right angle functions. Mates with standard 10" x 10" dual row connectors (i.e. 3M, Ansley, etc.) Permits quick testing of inaccessible lines.

Part No.	No. of contacts	Price
922576-26	26	\$6.90 ea.

INTRA-SWITCH

Permits instant line-by-line switching for diagnostic or QA testing. Switches actuated with pencil or probe tip. Mates with standard 10" x 10" dual-row connectors. Low profile design. Switch buttons recessed to eliminate accidental switching.

Part No.	No. of contacts	Price
IS-26	26	\$13.80 ea.

CRYSTALS

Part #	Frequency	Case Style	Price
CV1A	1.000 MHz	MC33 U	\$5.95
CV2A	2.000 MHz	MC33 U	\$5.95
CV2D	2.010 MHz	MC33 U	\$6.90
CV3A	4.000 MHz	MC18 U	\$4.95
CV7A	5.000 MHz	MC18 U	\$4.95
CV12A	10.000 MHz	MC18 U	\$4.95
CV14A	14.31818 MHz	MC18 U	\$4.95
CV19A	18.000 MHz	MC18 U	\$4.95
CV22A	20.000 MHz	MC18 U	\$4.95
CV30B	32.000 MHz	MC18 U	\$4.95

CONNECTORS

Part No.	Description	Price
15/30	155 Spacing - Tin Double Read-Out	\$1.95
18/36	Bifurcated Contacts — Fits .054 to .070 P.C. Cards	\$2.49
22/44	PINS (Solder Eyelet)	\$2.95
50/100A	PINS (Wire Wrap)	\$6.95
DB25P	25 PIN-D SUBMINATURE (RS232)	\$3.25
DB25S	SOCKET COVER FOR 25S/25P	\$4.95
DB25126-1	COVER FOR 25S/25P	\$1.75

LOTS OF POTS

Part No.	Description	Price
GB134	3 ea. of 10-20-25-50 100-200-250-500 ohm	\$2.95
GB135	3 ea. of 1K-2K-5K-50K 10K-20K-25K-50K	\$2.95
GB136	3 ea. of 1Meg-200K-250K-500K 1Meg-2Meg-2.5Meg-5Meg	\$2.95

SWITCHES

Part No.	Description	Price
JMT121	SPDT on-off-on	\$1.95
JMT123	SPDT on-none-on	1.65
JMT221	DPDT on-off-on	2.55
JMT223	DPDT on-none-on	2.15

MICROPROCESSOR COMPONENTS

Part No.	Description	Price	Part No.	Description	Price
8080A	CPU	\$10.95	CDP1802	CPU	\$19.95
8212	8 Bit Input/Output	4.95	MC6800	8 Bit MPU	19.95
8214	Priority Interrupt Control	7.95	MC6820	Periph. Interface Adapter	7.95
8216	Bi-Directional Bus Driver	4.95	MC6801A	128 x 8 Static RAM	5.95
8224	Clock Generator/Driver	5.95	MC6801B	1024 x 8 Bit ROM	15.00
8228	System Controller Bus Driver	5.95	Z80	CPU	24.95

Part No.	Description	Price	Part No.	Description	Price
8080A	Super 8080	\$10.95	2101	256 x 1 RAM's	\$ 1.49
2650	8 Bit MPU	28.50	1101	256 x 4 Static	5.95
2650B	CPU	28.50	2102	1024 x 1 Static	1.75
2504	1024 Dynamic SR'S	\$ 3.95	2107/2200	4096 x 1 Dynamic	4.95
2518	Hex 32 Bit	7.00	2111	256 x 4 Static	6.95
2519	Hex 40 Bit	4.00	1M5404-45N	4K Static	24.99
2522	Dual 132 Bit SSR	2.95	7469	16 x 4 Static	1.49
2524	512 Dynamic	9.95	8101	256 x 4 Static	5.95
2525	1024 Dynamic	3.00	8111	256 x 4 Static	6.95
2527	Dual 256 Bit	3.95	8599	16 x 4 Static	3.49
2529	Dual 512 Bit	4.00	2112/2110/2	1024 x 1 Static	2.26
2532	Quad 80 Bit	3.95	74200	256 x 1 Static	6.95
2533	1024 Static	5.95	93421	256 x 1 Static	7.95
3341	I/O	6.95	UPD41421041	4K Dynamic 16 Pin	5.95
7415670	16 x 4 Reg	3.95	UPD416	16K Dynamic	49.95

SPECIAL REQUESTED ITEMS

Part No.	Description	Price	Part No.	Description	Price	
FCM3817	11C30	19.95	7289	19.95	3.95	
AY-3-8500-1	7.50 AN33	3.95	ICM7405	24.95	L0110/111	25.00/100
AY-5-9100	17.50 8720	7.50	ICM7207	7.50	95980	11.95
AY-5-9200	14.95 8797	2.00	ICM7208	22.00	MC3061P	3.50
AY-5-9500	4.95 H00163	7.95	ICM7209	7.95	MC4018 (74416)	7.50
AY-5-2375	14.95 MCM5571	13.50	MCM5240	17.50	MC1408.1	9.95
9374	1.95 MCM6574	13.50	D500202H	3.75	MC1408.8	9.95
825115	25.00 MCM6575	13.50	TL308	10.50	74C922	9.95

PARATRONICS

Featured on February's Front Cover of Popular Electronics

Logic Analyzer Kit Model 100A \$229.00/kit

- Analyzes any type of digital system
- Checks data rates in excess of 8 million words per second
- Trouble shoot TTL, CMOS, DTL, RTL, Schottky and MOS families
- Displays 16 logic states up to 8 digits wide
- See ones and zeros displayed on your CRT, octal or hexadecimal format
- Tests circuits under actual operating conditions
- Easy to assemble — comes with step-by-step construction manual which includes 80 pages on logic analyzer operation.

PARATRONICS TRIGGER EXPANDER - Model 10

Adds 16 additional bits. Provides digital delay and qualification of input clock and 24-bit trigger word. — Connects direct to Model 100A for integrated unit.

3 1/2-Digit Portable DMM

- Overload Protected
- 3 1/2 High LED Display
- Battery or AC operation
- Auto Zeroing
- 10m 1Va, 0.1 ohm resolution
- Overrange reading
- 10 meg input impedance
- DC Accuracy 1% typical
- Ranges: DC Voltage - 0-1000V/ AC Voltage - 0-1000V/ Freq. Response 50-400 Hz/ DC/AC Current - 0-100mA/ Resistance - 0-10 meg ohm/ Size 8 1/2" x 4 1/2"

Model 2800 \$99.95

Comes with test leads, operating manual and spare fuse

Accessories:

- AC Adapter BC-28 \$9.00
- Rechargeable Batteries BP-26 20.00
- Carrying Case LC-28 7.50

CONTINENTAL SPECIALTIES

Part No.	Description	Price
PROTO BOARD 6	Other CS Proto Boards	\$15.95
PB100	4.5" x 6"	\$ 9.95
PB101	5.8" x 4.5"	29.95
PB102	7" x 4.5"	39.95
PB103	9" x 6"	59.95
PB104	9.5" x 8"	79.95
PB203	9.75 x 6 1/2 x 2 1/2	80.00
PB203A	9.75 x 6 1/2 x 2 1/2	129.95

LOGIC MONITOR for DTL, HTL, TTL or CMOS Devices \$84.95

QT PROTO STRIPS

Part No.	Description	Price
01-595	01-595	10.00
01-598	01-598	10.00
01-475	01-475	10.00
01-478	01-478	10.00
01-355	01-355	8.50
01-358	01-358	2.00
01-125	01-125	3.75
01-85	01-85	3.25
01-75	01-75	3.00

\$5.00 Minimum Order — U.S. Funds Only

Spec Sheets - 25¢ — Send 35¢ Stamp for 1978 Catalog

California Residents — Add 6% Sales Tax

Dealer Information Available

James ELECTRONICS

1021-A HOWARD AVE., SAN CARLOS, CA 94070

PHONE ORDERS WELCOME — (415) 592-8097

Advertised Prices Good Thru April

The Incredible "Pennywhistle 103"

\$129.95 Kit Only

The Pennywhistle 103 is capable of recording data to and from audio tape without critical speed requirements for the recorder and it is able to communicate directly with another modem and terminal for telephone "handing" and communications for the deaf. In addition, it is free of critical adjustments and is built with non-precision, readily available parts.

Data Transmission Method Frequency-Shift Keying, full-duplex (half duplex selectable)

Maximum Data Rate 300 Baud

Data Format Asynchronous Serial (return to mark level required between each character)

Receive Channel Frequencies 2025 Hz for space, 2225 Hz for mark

Transmit Channel Frequencies Switch selectable, Low (normal) = 1070 space, 1270 mark, High = 025 space, 2225 mark.

Receive Sensitivity -45 dbm acoustically coupled

Transmit Level -15 dbm nominal Adjustable from -6 dbm to -20 dbm

Receive Frequency Tolerance Frequency reference automatically adjusts to allow for operation between 1800 Hz and 2400 Hz

Digital Data Interface EIA RS-232C or 20 mA current loop (receiver is optoisolated and non-polar)

Power Requirements 120 VAC, single phase, 10 Watts

Physical All components mount on a single 5" x 9" printed circuit board. All components included.

Requires a VDM, Audio Oscillator, Frequency Counter and/or Oscilloscope to align.

The Original the 3rd Hand \$9.95 each

- Leaves two hands free for working
- Clamps on edge of bench, table or work bench
- Position board on angle or flat position for soldering or clipping
- Sturdy, aluminum construction for hobbyist, manufacturer or school rooms

DIGITAL STOPWATCH

- Bright 8-Digit LED Display
- Times to 99 minutes 59.99 seconds
- Crystal Controlled Time Base
- Three Stopwatches in One
- Times Single Event — Split & Taylor
- Size 4.5" x 2.15" x .90" (4 1/2 ounces)
- Uses 3 Penrite Cells

Kit — \$39.95

Assembled — \$49.95

Heavy Duty Carry Case \$5.95

Stop Watch Chip Only (7205) \$19.95

3 1/2-DIGIT DPM KIT

Model BK500 DPM Kit \$49.00

Model 3110-5C-5V Power Kit \$17.50

JE700 CLOCK

The JE700 is a low cost digital clock, but is a very high quality unit. The unit features a simulated walnut case with 6 x 2 1/2" x 1 1/2" dimensions. It uses a MAX72 high brightness readout, and the MMS314 clock chip.

115 VAC KIT ONLY \$16.95

HEXADECIMAL ENCODER 19-KEY PAD

- 10
- ABCDEF
- Shift Key
- 2 Optional Keys

\$10.95 each

New 63 KEY KEYBOARD \$29.95 IN STOCK

This keyboard features 63 unenclosed SPST keys, unattached to any kind of P.C.B. A very solid, molded plastic 13 x 4 base holds most applications.

Model 18 Encoder Chip (encodes 16 keys) \$7.95 ea.

Model 23 Encoder Chip (encodes 56 keys) \$14.95 ea.

JE803 PROBE

The Logic Probe is a unit which is for the most part independent in trouble shooting logic families. TTL, DTL, RTL, CMOS. It derives the power it needs to operate directly off of the circuit under test. Drawing a current 10 mA max., it uses a MAX27 readout to indicate any of the following states by these symbols: (H) 1 (LOW) 0 (PULSE) P. The Probe can detect high frequency pulses to 45 MHz. It can't be used at MOS levels or circuit damage will result.

\$9.95 Per Kit

printed circuit board

T-FL 5V 1A Supply

This is a standard TTL power supply using the well known LM309K regulator IC to provide a solid 1 AMP of current at 5 volts. We try to make things easy for you by providing everything you need in one package, including the hardware for only

\$9.95 Per Kit

DIODES/ZENERS

1N914	100v	10mA	.05
1N4005	600v	1A	.08
1N4007	1000v	1A	.15
1N4148	75v	10mA	.05
1N753A	6.2v	z	.25
1N758A	10v	z	.25
1N759A	12v	z	.25
1N4733	5.1v	z	.25
1N5243	13v	z	.25
1N5244B	14v	z	.25
1N5245B	15v	z	.25

SOCKETS/BRIDGES

8-pin pcb	.25	ww	.45
14-pin pcb	.25	ww	.40
16-pin pcb	.25	ww	.40
18-pin pcb	.25	ww	.75
22-pin pcb	.45	ww	1.25
24-pin pcb	.35	ww	1.10
28-pin pcb	.35	ww	1.45
40-pin pcb	.50	ww	1.25
Molex pins .01	To-3 Sockets		.45
2 Amp Bridge	100-prv		1.20
25 Amp Bridge	200-prv		1.95

TRANSISTORS, LEDS, etc.

2N2222A	NPN (2N2222 Plastic .10)	.15
2N2907A	PNP	.15
2N3906	PNP (Plastic)	.10
2N3904	NPN (Plastic)	.10
2N3054	NPN	.35
2N3055	NPN 15A 60v	.50
T1P125	PNP Darlington	.35
LED Green, Red, Clear, Yellow		.15
D.L.747	7 seg 5/8" High com-anode	1.95
XAN72	7 seg com-anode (Red)	1.25
MAN71	7 seg com-anode (Red)	1.25
MAN3610	7 seg com-anode (Orange)	1.25
MAN82A	7 seg com-anode (Yellow)	1.25
MAN74A	7 seg com-cathode (Red)	1.50
FND359	7 seg com-cathode (Red)	1.25

C MOS

4000	.15
4001	.15
4002	.20
4004	3.95
4006	.95
4007	.35
4008	.95
4009	.45
4010	.45
4011	.20
4012	.20
4013	.40
4014	.95
4015	.90
4016	.35
4017	1.10
4018	1.10
4019	.50
4020	.85
4021	1.00
4022	.85
4023	.25
4024	.75
4025	.30
4026	1.95
4027	.50
4028	.95
4030	.35
4033	1.50
4034	2.45
4035	1.25
4040	1.35
4041	.69
4042	.95
4043	.95
4044	.95
4046	1.75
4049	.45
4050	.45
4066	.95
4069	.40
4071	.35
4081	.70
4082	.45
MC 14409	14.50
MC 14419	4.85

7400	.15
7401	.15
7402	.20
7403	.20
7404	.15
7405	.25
7406	.35
7407	.55
7408	.25
7409	.15
7410	.10
7411	.25
7412	.30
7413	.35
7414	1.10
7416	.25
7417	.40
7420	.15
7426	.30
7427	.45
7430	.15
7432	.30
7437	.30
7438	.35
7440	.25
7441	1.15
7442	.45
7443	.65
7444	.45
7445	.65
7446	.95
7447	.95
7448	.65
7450	.25
7451	.25
7453	.20
7454	.25
7460	.40
7470	.45
7472	.40

7473	.25
7474	.30
7475	.35
7476	.40
7480	.55
7481	.75
7483	.95
7485	.75
7486	.25
7489	1.35
7490	.55
7491	.95
7492	.95
7493	.35
7494	.75
7495	.60
7496	.80
74100	1.15
74107	.35
74121	.35
74122	.55
74123	.55
74125	.45
74126	.35
74132	1.35
74141	.90
74150	.85
74151	.65
74153	.75
74154	.95
74156	.95
74157	.65
74161	.85
74163	.85
74164	.60
74165	1.50
74166	1.35
74175	.80

- T T L -

74176	1.25
74180	.75
74181	2.25
74182	.95
74190	1.75
74191	1.05
74192	.75
74193	.85
74194	1.25
74195	.95
74196	1.25
74197	1.25
74198	2.35
74221	1.00
74367	.85
75108A	.35
75110	.35
75491	.50
75492	.50
74H00	.15
74H01	.25
74H04	.20
74H05	.20
74H08	.35
74H10	.35
74H11	.35
74H15	.45
74H20	.30
74H21	.25
74H22	.40
74H30	.20
74H40	.25
74H50	.25
74H51	.25
74H52	.15
74H53J	.25
74H55	.20

74H72	.45
74H101	.75
74H103	.75
74H106	.95
74L00	.25
74L02	.25
74L03	.30
74L04	.30
74L10	.30
74L20	.35
74L30	.45
74L47	1.95
74L51	.45
74L55	.65
74L72	.45
74L73	.40
74L74	.45
74L75	.55
74L93	.55
74L123	.85
74S00	.35
74S02	.35
74S03	.30
74S04	.30
74S05	.35
74S08	.35
74S10	.35
74S11	.35
74S20	.35
74S40	.20
74S50	.20
74S51	.25
74S64	.20
74S74	.35
74S112	.60
74S114	.65

74S133	.40
74S140	.55
74S151	.30
74S153	.35
74S157	.75
74S158	.30
74S194	1.05
74S257 (8123)	1.05
74LS00	.25
74LS01	.35
74LS02	.35
74LS04	.30
74LS05	.45
74LS08	.25
74LS09	.35
74LS10	.35
74LS11	.35
74LS20	.25
74LS21	.25
74LS22	.25
74LS32	.40
74LS37	.35
74LS40	.45
74LS42	1.10
74LS51	.50
74LS74	.65
74LS86	.65
74LS90	.95
74LS93	.95
74LS107	.85
74LS123	1.00
74LS151	.95
74LS153	1.20
74LS157	.85
74LS164	1.90
74LS367	.75
74LS368	.75
74C04	.25
74C151	2.25

MCT2	.95
8038	3.95
LM201	.75
LM301	.45
LM308 (Mini)	.95
LM309H	.65
LM309K (340K-5)85	
LM310	1.15
LM311D (Mini)	.75
LM318 (Mini)	.95
LM320K5(7905)1.65	
LM320K12	1.65

LINEARS, REGULATORS, etc.

LM320T5	1.65
LM320T12	1.65
LM320T15	1.65
LM324N	.95
LM339	.95
7805 (340T5)	.95
LM340T12	1.00
LM340T15	1.00
LM340T18	1.00
LM340T24	.95
LM340K12	1.65

LM340K15	1.25
LM340K18	1.25
LM340K24	.95
78L05	.75
78L12	.75
78L15	.75
78M05	.75
LM373	2.95
LM380 (8-14 PIN)	.95
LM709 (8, 14 PIN)	.25
LM711	.45

LM723	.50
LM725N	2.50
LM739	1.50
LM741 (8-14)	.25
LM747	1.10
LM1307	1.25
LM1458	.95
LM3900	.50
LM75451	.65
NE555	.50
NE556	.95
NE565	.95
NE566	1.75
NE567	1.35

9000 SERIES

9301	.85	95H03	1.10
9309	.35	9601	.45
9322	.75	9602	.45

MICRO'S, RAMS, CPU'S, ETC.

74S188	3.00
1702A	4.50
MM5314	3.00
MM5316	3.50
2102-1	1.45
2102L-1	1.75
TR1602B	4.50
TMS 4044-45NL	14.50
8080AD	12.00
8T13	1.50
8T23	1.50
8T24	2.00
8T97	1.00
2107B-4, A	4.00
2708	11.50

INTEGRATED CIRCUITS UNLIMITED

7889 Clairemont Mesa Boulevard, San Diego, California 92111
(714) 278-4394 (Calif. Res.)

All orders shipped prepaid

No minimum

Open accounts invited

COD orders accepted

Discounts available at OEM Quantities California Residents add 6% Sales Tax

All IC's Prime/Guaranteed. All orders shipped same day received.

24 Hour Toll Free Phone 1-800-854-2211

American Express / BankAmericard / Visa / MasterCard

SPECIAL DISCOUNTS

Total Order	Deduct
\$35 - \$99	5%
\$100 - \$300	10%
\$301 - \$1000	15%
\$1000 - Up	20%

**TCXO
ACCURACY/PRICE BREAKTHROUGH!
± 0.1 PPM OR BETTER ACCURACY
GUARANTEED!!**

OPTO-8000.1



This new unit has taken a giant step in front of the multitude of inexpensive counters made recently available. The Opto-8000.1 boasts a combination of features and specifications found only in units costing several times its price. Accuracy of ± 0.1 PPM or better—*Guaranteed*—with a factory-adjusted, sealed TCXO (Temperature Compensated Xtal Oscillator). **Even kits require no adjustment for guaranteed accuracy!** Built-in, selectable-step attenuator, rugged and attractive, black anodized aluminum case (.090" thick aluminum) with tilt bail. 50 Ohm and 1 Megohm inputs, both with amplifier circuits for super sensitivity and both diode/overload protected. Front panel includes "Lead Zero Blanking Control" and a gate period indicator LED. AC and DC power cords with plugs included.

SPECIFICATIONS:

Time Base—TCXO ± 0.1 PPM GUARANTEED!
Frequency Range—10 Hz to 600 MHz
Resolution—1 Hz to 60 MHz; 10 Hz to 600 MHz



OPTOELECTRONICS, INC.

5821 NE 14 Avenue
Ft. Lauderdale, FL 33334
Phones: (305) 771-2050 771-2052 771-2051
Phone orders accepted 6 days, until 7 p.m.



All IC's socketed (kits and factory-wired)
Display—8 digit LED
Gate Times—1 second and 1/10 second
Selectable Input Attenuation—X1, X10, X100
Input Connectors Type—BNC
Approximate Size—3" h x 7½" w x 6½" d
Approximate Weight —2½ pounds
Cabinet—black anodized aluminum (.090" thickness)
Input Power Required—9-15 VDC, 115 VAC 50/60 Hz or internal batteries
OPTO-8000.1 Factory Wired **\$299.95**
OPTO-8000.1K Kit **\$249.95**

ACCESSORIES:

Battery-Pack Option—internal Ni-Cad Batteries and charging unit **\$19.95**
Probes: P-100—DC Probe may also be used with scope **\$13.95**
P-101—LO-Pass Probe, very useful at audio frequencies **\$16.95**
P-102—High Impedance Probe, ideal general purpose usage **\$16.95**
VHF RF Pick-Up Antenna-Rubber Duck w/BNC #Duck-4H **\$12.50**
Rt. Angle BNC adapter #RA-BNC **\$ 2.95**

FC-50—Opto-8000 Conversion Kits:

Owners of FC-50 counters with #PSL-650 Prescaler can use this kit to convert their units to the Opto-8000 style case, including most of the features.

FC-50 → Opto-8000	Kit \$59.95
*FC-50 → Opto-8000F	Factory Update \$99.95
FC-50 → Opto-8000.1 (w/TCXO)	Kit \$109.95
*FC-50 → Opto-8000.1F	Factory Update \$149.95


*Units returned for factory update must be completely assembled and operational

TERMS: Orders to U.S. and Canada, add 5% to maximum of \$10.00 per order for shipping, handling and insurance. To all other countries, add 10% of total order. Florida residents add 4% state tax. C.O.D. fee \$1.00. Personal checks must clear before merchandise is shipped.

CIRCLE 60 ON FREE INFORMATION CARD

ELECTRONIC SYSTEMS

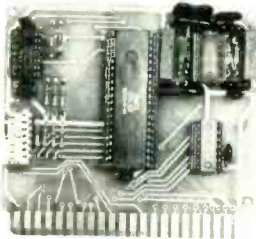p.o. box 212 Burlingame CA 94010
(408) 374-5984



UART & BAUD RATE GENERATOR

- Part no. 101
- Converts serial to parallel and parallel to serial
 - Low cost on board baud rate generator
 - Baud rates: 110, 150, 300, 600, 1200, and 2400
 - Low power drain +5 volts and -12 volts required
 - TTL compatible
 - All characters contain a start bit, 5 to 8 data bits, 1 or 2 stop bits, and either odd or even parity.
 - All connections go to a 44 pin gold plated edge connector
 - Board only \$12.00; with parts \$35.00

8K STATIC RAM

- Part no. 300
- 8K Altair bus memory
 - Uses 2102 Static memory chips
 - Memory protect
 - Gold contacts
 - Wait states
 - On board regulator
 - S-100 bus compatible
 - Vector input option
 - TRI state buffered
 - Board only \$22.50; with parts \$160.00



RS-232/TTL INTERFACE



- Part no. 232
- Converts TTL to RS-232, and converts RS-232 to TTL
 - Two separate circuits
 - Requires -12 and +12 volts
 - All connections go to a 10 pin gold plated edge connector
 - Board only \$4.50; with parts \$7.00

DC POWER SUPPLY

- Part no. 6085
- Board supplies a regulated +5 volts at 3 amps., +12, -12, and -5 volts at 1 amp.
 - Board has filters, rectifiers, and regulators
 - Power required is 8 volts AC at 3 amps., and 24 volts AC C.T. at 1.5 amps.
 - Board only \$12.50



TIDMA

- Part no. 112
- Tape Interface Direct Memory Access
 - Record and play programs without bootstrap loader (no prom) has FSK encoder/decoder for direct connections to low cost recorder at 625 baud rate, and direct connections for inputs and outputs to a digital recorder at any baud rate.
 - S-100 bus compatible
 - Comes assembled and tested for \$160.00


TAPE INTERFACE

- Part no. 111
- Play and record Kansas City Standard tapes
 - Converts a low cost tape recorder to a digital recorder
 - Works up to 1200 baud
 - Digital in and out are TTL-serial
 - Output of board connects to mic. in of recorder
 - Earphone of recorder connects to input on board
 - Requires +5 volts, low power drain
 - Board \$7.60; with parts \$27.50
 - No coils



RF MODULATOR

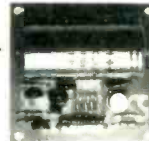- Part no. 107
- Converts video to AM modulated RF, Channels 2 or 3
 - Power required is 12 volts AC C.T., or +5 volts DC
 - Board \$4.50; with parts \$13.50




APPLE I MOTHER BOARD

- Part no. 102
- 10 slots - 44 pin (.156) connectors spaced 3/4" apart
 - Connects to edge connector of computer
 - Pin 20 and 22 connects to X & Z for power and ground
 - Board has provisions for by-pass capacitors
 - Board cost \$15.00



TELEVISION TYPEWRITER

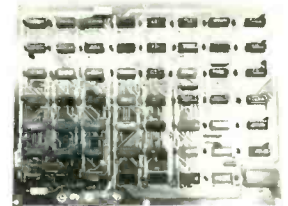

- Part no. 106
- Stand alone TVT
 - 32 char/line, 16 lines, modifications for 64 char/line included
 - Parallel ASCII (TTL) input
 - Video output
 - 1K on board memory
 - Output for computer controlled cursor
 - Auto scroll
 - Non-destructive cursor
 - Cursor inputs: up, down, left, right, home, EOL, EOS
 - Scroll up, down
 - Requires +5 volts at 1.5 amps, and -12 volts at 30 mA
 - Board only \$39.00; with parts \$145.00

MODEM

- Part no. 109
- Type 103
 - Full or half duplex
 - Works up to 300 baud
 - Originate or Answer
 - No coils, only low cost components
 - TTL input and output-serial
 - Connect 8 ohm speaker and crystal mic. directly to board
 - Uses XR FSK demodulator
 - Requires +5 volts
 - Board \$7.60; with parts \$27.50




To Order:

Mention part number and description. For parts kits add "A" to part number. Shipping paid for orders accompanied by check, money order, or Master Charge, BankAmericard, or VISA number, expiration date and signature. Shipping charges added to C.O.D. orders. California residents add 6.5% for tax. Parts kits include sockets for all ICs, components, and circuit board. Documentation is included with all products. Dealer inquiries invited. 24 Hour Order Line: (408) 374-5984.



E21

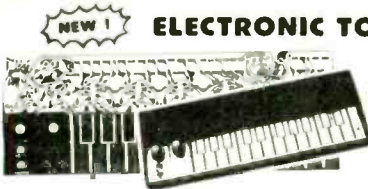

NEW 1

ELECTRONIC TOUCH ORGAN KIT

Fantastic new design uses CMOS I.C. and a total of 39 semi-conductors to give a touch control keyboard, all the electronic parts in one PC Board. This organ is easy to build, yet has features like a full two-octave range touch keyboard, variable tremolo; two voices; built-in I.C. amplifier with volume control, complete with speaker and a specially designed plexi-glass case.

BATTERIES NOT INCLUDED *Ideal kit for beginner or gift for children **\$24.50 ea.**

30MHZ FREQUENCY COUNTER KIT



Take advantage of this new state-of-the-art counter featuring the many benefits of custom LSI circuitry. This new technology approach to instrumentation yields enhanced performance, smaller physical size, drastically reduced power consumption (portable battery operation is now practical), dependability, easy assembly and revolutionary lower pricing!

Only **\$59.50**

Model 250-30A Includes all parts, PC Board and Transformer

- * 0.5" red LED 6 digits display
- * Resolution: 1 Hz at 1 sec. 10 Hz at 1/10 sec.
- * Sensitivity: 10 Mv RMS to 30 Hz
- * Internal power supply: 5.2V at 1 amp regulated
- * Input connector: BNC type
- * Input power required: 117V AC 50/60 Hz
- * Diode protected for over voltage input

DIGITAL CASSETTE TAPE C-60



COMPUTER RECORDING
All these tapes made in U.S.A. by a top cassette tape Co. Never Recorded—Reg. \$6.80 ea. **3 packs/\$5.00**
Can be used in Audio Recording as well.


- Type A - With Linear Tape
- Type B - Without Linear Tape
- * Without R.O.T.F.E.D.T.
- * 90 Minutes Recording Time
- * Silver Etched Tape
- * AMBI Noise
- * AMBI Single-Play Phone

SOUND ACTIVATED SWITCH



All parts completed on a PC Board SCR will turn on relay, buzzer or trigger other circuit for 2-10 sec. (adjustable) Ideal for use as door alarm, sound controlled toys and many other projects Supply voltage: 2.5V-9V D.C. \$1.75 ea./2 for \$3.00

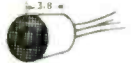Sub-Mini Size Condenser Microphone \$2.50 each
FET Transistor Built-In



SIGMA 78RE1, 12DC RELAY 400R COIL SPDT

\$1.30 ea. or 10 for \$10.00



ALL BRAND NEW UNITS

COMPUTER GRADE CAPACITORS



5,600 MFD 60V	\$2.20 ea
10,000 MFD 50V	\$3.25 ea
11,500 MFD 75V	\$3.95 ea
34,800 MFD 50V	\$4.25 ea
85,000 MFD 25V	\$4.10 ea
100,000 MFD 6V	\$3.50 ea

CALCULATOR with STOPWATCH

6 Functions with % and memory
8 Digits big green display
* Built-in X'tal controlled stop watch count to 1/10 of a second.

Special Price Only **\$16.50 Ea.**

BATTERIES NOT INCLUDED



MECHANICAL DIGITAL CLOCK



WITH DAY AND DATE OF THE WEEK

This clock is beautifully designed. Case is made from high quality die cast alloy. Movement is the popular flip type with a back up light.

Supply Voltage 110V AC. limited quantity **\$15.50 ea.**

QUARTZ CRYSTALS

1 MHz	\$4.95
2 MHz	\$5.25
4 MHz	\$5.25
10 MHz	\$5.25
3.579 MHz	\$1.25

Color TV Type



12V D.C. AUTO DIGITAL CLOCK

Complete Unit Not a Kit!

0.4" blue color 4 digits display. Turn off readouts when car is not running. X'tal controlled time base for time accuracy. Special designed case for easy mounting on top of your dashboard. Ideal for car, boat and campers.

ONLY **\$28.50 ea.**



HEAVY DUTY CLIP LEADS

10 pairs - 5 colors Alligator clips on a 22" long lead. Ideal for any testing.

\$1.85/pack

MINI-SIZED I.C. AM RADIO

Size smaller than a box of matches! Receives all AM stations Batteries and ear phone included

Only **\$8.50**



1Watt AUDIO AMP

All parts are pre assembled on a mini PC Board Supply Voltage 6-9V D.C. SPECIAL PRICE **\$1.95 ea.**



"FISHER" 30 WATT STEREO AMP (15W X 2)

Kit Includes: 2 pck. Fisher PA 301 Hybrid IC all electronic parts with PC Board. Power supply: 16V DC (not included). Power band with (KF = 1% ± 3dB). Voltage gain: 33dB, 20KHz - 20KHz.


Super Buy Only **\$22.50 each kit**



5W AUDIO AMP KIT

2 LM 380 with Volume Control Power Supply 6-18V DC

only **\$5.00 ea.**

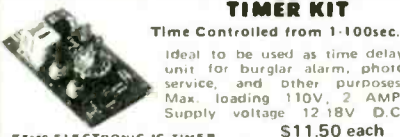

TIMER KIT

Time Controlled from 1-100sec.

Ideal to be used as time delay unit for burglar alarm, photo service, and other purposes. Max. loading 110V, 2 AMP. Supply voltage 12 18V D.C.

\$11.50 each



ELECTRONIC ALARM SIREN

COMPLETE UNIT

Ideal for use as an Alarm Unit, or hook up to your car back up to make a reverse Indicator Light Output up to 130 dB. Voltage Supply 6-12V

\$7.50



19 KEY HEXADECIMAL KEY PAD

- 1-0
- Homekey
- ABCDEF
- ← → Key

SPECIAL **\$10.50 ea.**

Low Cost Hexadecimal 16 Key Pad

Designed for Calculator. Can be used for Computer Data Entry Pad or Digital Lock. All key tops blank with super good touch feeling. \$0.95 ea.



DIGITAL ELECTRONIC LOCK KIT

for auto ignition, entry door, burglar, alarm, etc. CMOS I.C. 4 Digits Programmable in Circuit. Any Combination

\$6.50 ea.

400A RELAY AND KEY PAD NOT INCLUDED




POWER SUPPLY KIT

0-30V D.C. REGULATED Uses UA723 and ZN3055 Power TR output can be adjusted from 0.30V, 2 AMP. Complete with PC board and all electronic parts.

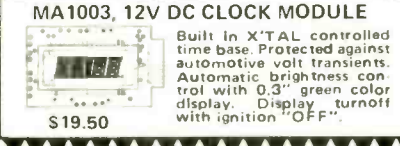0-30 POWER SUPPLY **\$9.50 each**

Transformer for Power Supply, 2 AMP 24V x 2 **\$4.50 ea.** 30V DC Panel Meter **\$4.20**



MA1003, 12V DC CLOCK MODULE

Built in X'TAL controlled time base. Protected against automotive volt transients. Automatic brightness control with 0.3" green color display. Display turnoff with ignition "OFF".

\$19.50



LED ALARM CLOCK

COMPLETE UNIT NOT A KIT

- 0.5" RED LED READ OUT
- 24 HRS. ALARM SET
- 10 MINS. SNOOZE SET
- AM/PM ALARM INDICATORS
- SECOND DISPLAY SWITCH
- AUTOMATIC BRIGHTNESS CONTROL
- COMPACT AND HANDSOME PACKING
- 110V AC 60HZ INPUT


\$17.50 EACH



5" MUFFIN FAN HEAVY DUTY

5 Blade Type 110V 50/60HZ Case made of Die-Cast metal used but almost brand new

SPECIAL PRICE **\$9.60 ea.**

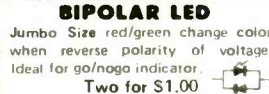


BIPOLAR LED

Jumbo Size red/green change color when reverse polarity of voltage. Ideal for go/nogo indicator. Two for \$1.00



I.C. TEST CLIPS

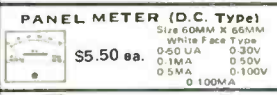
Same as the E Z clips With 20" Long Leads In Black and Red Colors **\$2.75 per pair**



PANEL METER (D.C. Type)

Size 60MM x 60MM White Face Type 0-60 U.A. 0-30V 0-1MA 0-50V 0-5MA 0-100V 0-100MA


\$5.50 ea.

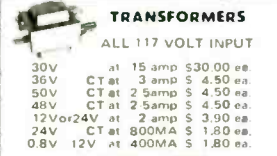

TRANSFORMERS

ALL 117 VOLT INPUT

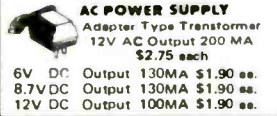- 30V at 15 amp \$30.00 ea.
- 36V CT at 3 amp \$ 4.50 ea.
- 50V CT at 2.5 amp \$ 4.50 ea.
- 48V CT at 2.5 amp \$ 4.50 ea.
- 12V or 24V at 2 amp \$ 3.90 ea.
- 24V CT at 800MA \$ 1.80 ea.
- 0.8V 12V at 400MA \$ 1.80 ea.



AC POWER SUPPLY

Adapter Type Transformer 12V AC Output 200 MA

\$2.75 each

- 6V DC Output 130MA **\$1.90 ea.**
- 8.7VDC Output 130MA **\$1.90 ea.**
- 12V DC Output 100MA **\$1.90 ea.**




150UA METER

only **\$1.50 ea.**



HOUR INDICATOR

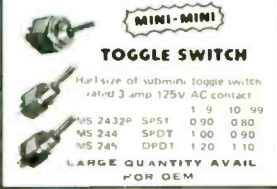This unit is 1 5/8" long operating voltage 4V D.C. will tell you how many hours your circuit or machine has been in service up to 100 hours. Limited Quantity ONLY **\$1.75 ea.**




MINI-MINI

TOGGLE SWITCH

Half size of submini. toggle switch rated 3 amp 125V AC contact

1 9 10 99	1 9 10 99
MS 2432P SPST	0 90 0 90
MS 244 SPDT	1 00 0 90
MS 245 OPDT	1 20 1 10


LARGE QUANTITY AVAIL FOR OEM

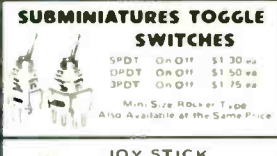

SUBMINIATURE TOGGLE SWITCHES

- SPDT On-Off **\$1.30 ea.**
- DPDT On-Off **\$1.50 ea.**
- 3PDT On-Off **\$1.75 ea.**

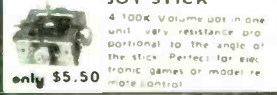Mini Size Rocker Type Also Available at the Same Price



JOY STICK


4 100K volume pot in one unit very resistance and proportional to the angle of the stick. Perfect for electronic games or model remote control.

only **\$5.50**



PUSH-BUTTON SWITCH

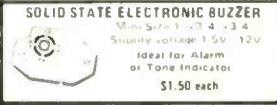N/Open Contact Color: Red, White, Blue, Green, Black. 4/\$1.00 N/Close also Available 50c ea. LARGE QTY AVAILABLE



SOLID STATE ELECTRONIC BUZZER

Mini Size 1/2" x 4-3/4" Square voltage 1.5V-12V Ideal for Alarm or Tone Indicator **\$1.50 each**

MINIMUM ORDER \$10.00 California residents add 6% sales tax. All orders add 10% postage for out of state. Overseas countries add 15% of total order for postage. SEND CHECK OR MONEY ORDER TO



FORMULA INTERNATIONAL INC.

12603 CRENSHAW BOULEVARD • HAWTHORNE CALIFORNIA 90250

For more information please call (213) 679-5167 STORE HOURS 10-7 Monday-Saturday



ACOUSTIC COUPLER

BY NOVATION OR LOGIC
This originate only coupler, was manufactured for use in 725 data terminal. It is compatible with Ball 103 and 113 data rates or the equivalent. The coupler operates asynchronously to a maximum speed of 300 baud in the half or full duplex mode. All signal outputs are compatible with TTL. Transmit freq. is 1270hz. for mark and 1070hz. for space. Receive freq. is 2225hz. for mark and 2025hz. for space. Unit requires ± 12 V and +5 V for operation. Complete with schematic and all pertinent information. Fully reconditioned, calibrated, and guaranteed... \$47.50
RS232 to TTL to RS232 converter kit. Complete with PC board components, and schematic \$6.50

LOOK! I.C. DUMP-OFF!

74100.....\$1.10	7480.....\$2.20
7402.....\$1.10	7483.....\$2.25
7403.....\$1.10	7493.....\$1.15
74104.....\$1.10	7495.....\$1.30
7404.....\$1.10	74198.....\$1.30
7405.....\$1.10	745112.....\$1.30
74110.....\$1.10	74121.....\$1.15
74111.....\$1.10	74145.....\$1.30
74120.....\$1.10	74153.....\$1.30
74121.....\$1.15	74156.....\$1.30
7423.....\$2.20	74165.....\$1.50
74130.....\$1.10	74193.....\$1.40
7450.....\$1.10	74298.....\$1.40
74S251.....\$1.50	75453.....\$1.30
7453.....\$1.10	DM8093.....\$1.20
74154.....\$1.10	DM8094.....\$1.20
74L73.....\$1.15	DMB123.....\$1.20
74L74.....\$1.15	

NE555V 10 FOR \$2.50
8 PIN MINI DIP BY INTERSIL.

EAGLE-PICHER BATTERY
CF6V5, 6 VOLT 5A.H. SPILL-PROOF, RECHARGEABLE BATTERY \$12.50EA. NEW-1 YEAR WARRANTY.

HIGH POWER RECTIFIER
VARO H407 6000V 750MA. \$2.50 EACH

TEFLON TUBING
Extremely high operating temperature range and chemical inertness. Will not crack or become brittle. Remains flexible throughout entire operating temp. range. CLEAR 18 GA. 100' roll \$4.95 1000' roll \$24.95

12VDC COOLING FAN
THAT'S RIGHT A 12VDC IDEAL FOR SMALL COOLING PROBLEMS. 2" BLADE DIA. MOTOR DIA. 1-3/8". ONLY \$4.95

THERMALLOY
60308 flat power device heat sink. 10/\$1.98

THERMALLOY
6111-B-66. To-6 heat sink. 10/\$5.00

TO-3 HEATSINK
680-1.25A. BLACK ANODIZED ALUM. 1.81" BASE X 1.25" HIGH. \$1.25 EACH 10 FOR \$9.95

DIPPED TANTALUMS

10	100
47MFD@35V \$20 \$15	15MFD@20V \$30 \$25
22MFD@16V \$20 \$15	33MFD@10V \$30 \$25
3.3MFD@35V \$20 \$15	47MFD@20V \$30 \$25
4.7MFD@25V \$20 \$15	100MFD@10V \$60 \$50
6.8MFD@16V \$25 \$20	220MFD@10V \$75 \$60
10MFD@25V \$25 \$20	PRICED PER EACH.

SPRAGUE 36D POWERLYTICS
LIKE NEW PARTS AT USED PRICES! PULLED FROM NEW EQUIPMENT AND OFFERED TO YOU AT SUBSTANTIAL SAVINGS. AVAILABLE IN:
5500MFD @ 40V 8200MFD @ 25V
YOUR CHOICE \$1.00 EA. 10 FOR \$7.95

PHOTO-FLASH CAP
600 MFD @ 360 VOLT 1" X 3/4". \$1.98 EACH 10 FOR \$15.00

SNAP-IN ROCKER SWITCH
"ON-OFF" 10A-120VAC. FITS 1/2" X 1-1/8" CUT-OUT. 10 FOR \$2.50

ROCKER SWITCH
2 pole-3 position. 4A-125VAC. 5A-125VDC. 1.5A-250VAC. Specify spring loaded center off or 3-pos. lock. 10 FOR \$2.50

LEAF SWITCH
Ideal for your synthesizer keyboard. 1 1/2" overall length x 3/16" thk. 2A rating. cast block, and nylon plunger. 10 FOR \$1.98

PRECISION POTS
5K OR 10K OHM 10-TURN POTS BY SPECTROL THIS MODEL 534 IS $\pm 2.5\%$ LIN. AND $\pm 5\%$ RES. (1.750" x .875" DIA.) \$2.50 EA. 10 FOR \$19.95

KYNAR WIRE WRAP WIRE. Solid silver plated 30AWG in Blue, Red, Yellow, Black, Green, or White. 100' Spool for \$2.50; 500' Spool for \$5.95; 1000' Spool for \$9.95
26AWG Red or Black 500' Spool for \$7.95; 1000' Spool for \$12.50.

HOOK UP WIRE. Stranded 22 GA. available in white, brown, red, orange, black, blue, purple, yellow, green, or gray. 200 FT. SPIOOL FOR \$3.50

BREADBOARD JUMPER WIRE KIT. Each kit contains 300 wires in various colors and sizes. Lengths range from 1.2" to 9". Each wire is stripped, both ends, solid tinned 24 gauge with PVC insulation. \$1.95 PER KIT

WHILE THEY LAST, SPECIAL!
\$3.50 EA. 10 FOR \$32.50
IBM-25S FEMALE CONNECTOR NEW! GREEN INSERT. SOLDER CUP PINS.

EDGE CONNECTOR
43/64 pin dual read-out. .156" spacing with solder cyclot pins. 1 wtd. but you will love them at \$1.00 each.

MOLEX I.C. PINS
100 FOR \$9.98 1000 FOR \$6.95
2N5449 NPN 50V 800MA 6/S1.00 100/\$9.95 1000/\$49.95

SOCKETS
14 pin (gold) WW 2 for \$1.00
16 pin (gold) WW 2 for \$1.00

IN914B SWITCHING DIODE
100/\$4.95 1000/\$39.95
1N752 5.6V ZENER @ 400MW 100/\$5.95 1000/\$49.95

G.E. SC51B TRIAC
15A 200V in press fit case. Ideal for color organs. \$1.00 10 FOR \$7.50

PC BOARD MATERIAL IS BACK!
WHITE POLYESTER FIBERGLASS 1/16" THK. UNETCHED COPPER CLAD 10Z. 2-SIDED.

10	100
6" X 12".....\$1.25ea.....\$1.00ea.	
9" X 12".....\$1.75ea.....\$1.50ea.	
12" X 12".....\$2.00ea.....\$1.75ea.	

G-10 1/16" THK. EPOXY UNETCHED COPPER CLAD 10Z. 2-SIDED.

10	100
9" X 10".....\$1.75ea.....\$1.50ea.	

ETCH MATERIAL
ACE MAKES IT EASY WITH ETCH POWDER. ETCH'EM TO YOUR OWN SPECIFICATIONS.
EP-1.....MAKES 10T.....\$1.50
EP-2.....MAKES 10AL.....\$3.50
(WITH INSTRUCTIONS)

SHOP ACE FOR THE REAL SURPLUS BARGAINS!

HEAT SHRINK TUBING 25-6" lengths in various sizes & colors. \$2.95 PER ASST.

TEFLON TUBING 25-6" lengths in various sizes and colors. \$1.95 PER ASST.

DISC CAPACITORS 100 FOR \$2.95
INCLUDES THESE VALUES: 75pf, 100pf, 220pf, 470pf, .0047mfd, .01mfd, .001mfd, .047mfd, .1mfd & .2mfd

ELECTROLYTICS 100 FOR \$9.95
Ministors alum. axial leads Includes values from 1mfd/50V to 1500mfd/16V

DIPPED POLYESTER FILM CAPS 100 FOR \$4.95

1% PRECISION RESISTORS 200 FOR \$4.95
assortment contains a balanced inventory.

POWER CORD ASSORTMENT 6 2 conductor w/ strain relief FOR plug and connector \$2.95 6-8 ft. UL LISTED

SLIDE SWITCHES 40 FOR \$5.00
STANDARD & MINIATURE

AC ADAPTERS 4 FOR \$9.95
INCLUDES: 3.1 VDC @ 100ma, 4.4VDC @ 50ma, 8VDC @ 60ma, & 8VAC @ 100ma.

SPEEDY BEND BEND 1/4W RESISTORS ON ONE SIDE, 1/2W ON THE FLIP SIDE TO PRECISE MEASUREMENTS. \$1.95 EA.

LED SPECIALS
200" DIA. RED-10/\$1.00, GREEN-4/\$1.00
200" DIA. RED-MV-10B 8/\$1.00
.125" DIA. RED-5/\$1.00, GREEN-4/\$1.00, YELLOW-4/\$1.00

PITTMAN 12VDC MOTOR
Runs on as low as 2 volts rated 12 volts, 250 ma, with 2.8 inches of torque at 5000 RPM. 1-1/8" dia. x 2" long with 0.118" shaft. NEW & GUARANTEED. 10 for \$15.00

12VDC SOLENOID
36 ohm, 10 oz. push with 1/8" stroke. Panel mount bushing. 3/4" dia. x 1-3/4" overall. \$1.98 ea. 10 for \$15.00

SLOTTED OPTICAL SWITCH (TYPE OPB 800)
The OPB800 consists of a gallium arsenide infrared LED coupled with an n-pn silicon photo-transistor in a plastic housing. The gap in the housing provides a means of sensing motion of opaque objects. 1/2" mounting centers. Manufactured by OPTRON INC. \$1.98 EA

BISMUTH ALLOY
MELTS IN BOILING WATER. 4 OUNCE INGOT FOR \$3.95. 1 POUND INGOT \$9.95. FUN TO PLAY WITH!

SCREW TYPE TERMINAL
Ideal for stereo or TV connector. H.M. Smith 872. Cinch 17-2. 1-3/8" mt. ctrs. 9/16" term. spacing 20/ST. 100/\$3.95

PERMA-FLEX TAPE
1/2" wide X 66" long. All wts. ther. 8000V, (.085" thk.) black. \$1.00/roll 10/\$7.95 UL APPROVED.

LITTLE VINYL FEET
We all know there are many uses for vinyl feet, so stock up with these self-sticking square or round feet. 1/2 x 3/16 high. Sheet of 50 for \$1.00 (For customers with vivid imaginations, feet are not shaped as shown.)

MILLER CHOKE
P/N 6310. 1392 TURNS. 50 mh 65 ma. 10 FOR \$2.95

AMP 10 POSITION DIP SWITCH. \$3.50 EA. 10/\$25.00

THIS DEAL!
Stacked Foil Caps
Metalized polycarbon with stack foil construction. Extremely low self-induction. 1000/\$12.50

ZERO CROSSING DETECTOR
SN16268 by T.I. detects when line current is at its minimum for switching devices at zero current. 14 pin package with specs. 10 for \$4.95

ARNOLD CORE
135 MH. PER 1000 TURNS. 1" ID x 1-7/8" OD x 3/4" THK. P/N A-759135-2 \$1.50 EA

PLASTIC TEST LEAD WIRE
18 GA. TIN COPPER WITH FLEX LIFE JACKET. 65 36 STRANDING AVAILABLE IN BOTH RED AND BLACK. 25 FOOT FOR \$ 98

PHOTO CELL
Type CL508. CDS material by Clairex. Dark resistance 15 meg. ohm. max. voltage 175V. \$1.00 100/\$17.50

VARIABLE CAP
JOHNSON P/N 167-3, 4-50PF. \$2.50 EACH 10 FOR \$19.95

WHAT? LINEAR POTS 4/\$1.00 WITH SWITCH

100K P/N 7750 PUSH-ON PUSH-OFF. 1/2"x1/2" shaft, 3/8" BUSHING MOUNT. 1/8" Dimmer knobs for above; specify black, brown, or ivory. \$1.00EA. 1/8" Instrument knob for 250K pot...\$2.50EA. \$1.00

SUBMINIATURE 250K P/N 1414, ON-OFF SWITCH. 1/8"x3/8" shaft, 1/4" BUSHING MT. 1/8" BUSHING MT. \$1.00EA

2N4991 SILICON BIDIRECTIONAL SWITCH. 4/\$1.00 100/\$19.95

TMS1030J. DYNAMIC RAM 4096-BIT LOW POWER (40mw). REMOVED FROM SOCKETS. TESTED AND GUARANTEED. WITH DATA AND 22 PIN SOCKET. \$9.95ea. 8/\$64.95

NEW! EVEREADY BATTERY
STOCK UP ON THIS SUPER SAVINGS 10/\$2.00 "AA" 100/\$15.00

SPECIAL PRICE OFFER!
NEW! OPTIMA ENCLOSURE ROYAL BLUE WITH WHITE FRONT BEZEL. 19" RACK, 7" PANEL SPACE, AND 16" DEPTH. ACE SPECIAL PRICE \$59.95 WHILE THEY LAST.

RECESSED RUBBER BUMPS
1" dia. x 1 1/4" h. w. 5/16" hole. 8/\$1.00 50/\$3.95

SCHOTTKY DIODE
1N5812 High efficiency rect. 20A 50VPI. low leakage. fast recovery. \$1.00EA. 10 for \$7.95


NATIONAL MM5013 1K SHIFT REGISTER. 8 PIN MINI DIP \$6.00 EACH 10 FOR \$4.95

*******WRITE FOR FREE CATALOG*******
ACE ELECTRONIC PARTS
5400 MITCHELLEDALE, B-8 HOUSTON, TEXAS 77092 (713) 688-8114
TERMS: MINIMUM ORDER \$10. Send check or money order. NO COD. Texas residents add 5% sales tax. Canada and Mexico add \$2.50. Overseas countries add \$5.00 for surface rates. We pay postage up to 10 pounds.

GOOD NEWS

ETCO SURPLUS BARGAIN BLITZ!

FREE-GIFT!

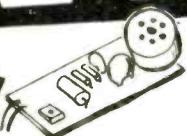

WITH EVERY ORDER OF \$10 OR MORE - SOUND ACTIVATED SWITCH!
Intriguing surplus assembly. Microphone picks up sound and drives SCR switch. Ask for H210SU or you may order these at \$1.29 each.

TeleMatic
469 CR200 COLOUR PIX-TUBE BOOSTER!
SPECIAL PRICE!

For 70° shell base tubes. Autotransformer type. Below regular price because we brought out a deal. Full warranty. H344MS.

MINIATURE BEAD-IN-GLASS THERMISTORS

PAK OF TEN, Philips No. 2322-634-2122A. Tiny thermistor with a 9-sec. thermal time constant and a dissipation capability of 60mw. Tiny glass case only 3/8" long. Use for experimental temperature sensing in timing, gain-control, test, medical and research circuitry. Brand new Factory Surplus at a fraction of regular price! H390MS.

2.99 PAK 10
REAL VALUE

"LESLIE" ROTATING TREMOLO ORGAN SPEAKER

49.95

Sold Out to ETCO

In original factory cartons. Brand new surplus rotating Leslie organ speaker units. Consists of a stationary heavy duty 8" speaker over which rotates a cleverly designed baffle with adjustable speed control that disperses the sound with a tremolo effect. Excellent basis for construction of experimental organ, hi-fi or musical instrument "special effects" speaker system. Motor operates on 110 VAC. Speaker is 8 ohms. H012SP.

SPDT MOMENTARY LEVER SWITCH

1.49 super buy

C & K No. 7108 high quality switch capable of 5A @ 110 vac. Snap fits in 10/16" x 7.16" hole. Spring return momentary action. H*233W.
H142SW - As above but SPDT regular action. 89c.

10 "FLY-SPECK" MICRO-THERMISTORS

INCREDIBLE! **3.99** PAK 10

Thermistors so small they could hide under a period on this page. Bear Philips No. 2322-634-01333. Suitable for temperature sensing in exceedingly small measurement probes for medical research, etc. Each with fine little axial wire leads. H391MS.

SO SMALL THEY COULD HIDE UNDER THIS PERIOD.

PHOTOCOPY MACHINE SHEET DETECTOR

2.95 NEW!

Clever gadget: this unique sheet detector consists of a CdS photocell, LED light source and amplifier with -ET input, 741 op-amp and gain control. A very interesting surplus assembly at a fraction of factory cost. H084MS.

SURPRISE RELAY BOARD!

SCOOP **2.95** 10/\$24.95

We bought this item "blind" - and it turns out to be a winner! Contains DPDT P.C. slide switch, 2 resistors, 2 rectifiers, 2 ceramic .01 caps, 3 valuable transistors and a beautiful Potter & Brumfield 12V DC relay (No. R505-E2-Y2-12V). The relay alone is worth the price! Brand new factory surplus - while they last. Exactly as pictured. H308SU.

44-PIN EDGE-CARD CONNECTOR!

1.99 SPECIAL PURCHASE

For 22 pin double sided boards. 44 solder-terminals. Insulated, non-corrosive contacts. Excellent value. Brand new Factory Surplus. H088MS.

5 AMP MULTIVOLTAGE TRANSFORMER

5.95 SURPLUS 10/\$49.95

SCHOTT Corp. No. 67063180. Excellent for low voltage projects. This transformer provides 13.8 volts @ 1 amp and a choice of 7.5, 6.5, 5.7 or 4.9 volts @ 5 amps. Input voltage, 110-117 vac. Size: 3-3/8" x 2-7/8" x 2 1/2" D. H021XF.

8-TRACK STEREO TAPE HEAD

Compare! Save!.. 2.89 10/\$24.95

Beautiful brand new production surplus. Ideal for service or experimental application. Bears part No. 1182, also A197421 (4E22A). 1/2" x 1/2". Made in Japan. Complete with rubber bootied plug-in connector cable. DC resistance 500 ohms. We don't have specs - but you'll find these fit popular stereo players. H604TR.

FASCINATING CAMERA SURPLUS!

FACTORY SURPLUS! **1.95** 3/\$4.95 10/\$13.95

Brand new factory surplus electronic apparatus. Photocell capable of up to 120V @ 4 ma. Drives sensitive d'Astonval relay type movement to close and open camera aperture; provide "flag" indicator. Ingenious device for inventors, builders and gadgeteers. Educational for schools. H303SU.

5 ASSORTED OPTICAL LENSES!

1.98 Government SURPLUS!

We just located an inventory of government surplus optical lenses. They were too mixed to catalog separately so we packed them up this way to bring you this great value. Ideal for schools! H263OP.

BEAU 33-PIN CONNECTOR!

SPECIAL! **1.95**

Beau No. P3333DB 33-pin male chassis connector. Each pin capable of 10A @ 125vac. Mounts in 1-3/8" x 3-7/8" cutout. Brand new factory surplus. Exactly as pictured. H185MS.

SURPLUS PLUG-IN RELAY MODULE!

BARGAIN SCOOP **2.95**

Exactly as pictured. Encased in 2" x 2" x 3" plastic case with 10 pin base plug. Contains a Potter & Brumfield relay No. KA-3091-7 (109P110) and assorted rectifier diodes. Only 90 in stock. H309SU.

TELEPHONE YOUR ORDERS Phone in your charge-card orders at low station-to-station rates. CAL: 1-518-561-8700.

SURPLUS WANTED - Contact our buying office at 1-514-695-0400 or send list and samples to Plattsburgh address below.

CANADIANS - Ordering from this ad is simple. Please remit in U.S. funds (just add 10% to total) - (Charge and Mastercharge welcome). We do the paperwork and ship to you direct from the U.S.A. at low American prices. You pay duty and tax to Canadian Customs. (Canadian schools are exempt) - We have stores in Canada, too! Write for Canadian catalogs. We invite you to visit our Plattsburgh store - just 50 minutes from Montreal on the throughway.



ETCO ELECTRONICS

Rush Your Order Today To . . . ETCO ELECTRONICS CORP. U.S.A.
North Country Shopping Center,
Route No. 9, Plattsburgh, N.Y. 12901.

Merchandise subject to prior sale. Prices subject to change without notice. Full remittance with each order please. Money Order, Certified check, BANKAMERICARD, VISA, MASTERCHARGE or CHARGEX. Add 15% for UPS (or postage) and handling (we refund excess). Please try to bring your order total to \$10 or more. Worldwide export orders solicited. Open account to Government agencies, schools, institutions and triple "A" rated industrial and commercial accounts. Special quotes for quantities N.Y. state residents add 7% sales tax.

CIRCLE 70 ON FREE INFORMATION CARD

APRIL 1978

WE'RE #1.

The DATA HANDLER is the #1 microcomputer endorsed by schools and Universities throughout the world because it is low in price, easy to assemble and program, and offers more than any other computer in its class. The Western Data Systems DATA HANDLER was the first microcomputer to couple the \$100 bus to the popular 6502 microprocessor and they remain the first and only \$100 bus computer for slightly more than \$1500. WITH THE DATA HANDLER YOU CAN START OUT A BEGINNER, AND END UP A COMPUTER PRO.

Complete easy Instructions get you started right away, even if you've never used a computer before. In no time at all you will be writing and running your own programs, or use the ones in the software section of the owner's manual. EDUCATE YOURSELF INTO THE FASCINATING WORLD OF COMPUTERS. At this price you owe it to yourself. As your need for computer power grows, you will be amazed how easily and inexpensively the DATA HANDLER is to expand. Simply plug any ALTAIR/5-100 compatible type peripheral board of your choice directly onto the DATA HANDLER mother board, or purchase our EX/PRO 1 board which adds memory, system software, and a complete display or video, coupled to your black and white T.V. set.

- SPECIFICATIONS**
- ON BOARD COMPLETE DATA & ADDRESS DISPLAY.
 - 6502 MICROPROCESSOR
 - CONTAINS 1K BYTES OF STATIC RAM
 - EASY TO USE KEYBOARD.
 - DUAL LATCHING I/O PORTS & ONE BIT DYNAMIC INPUT PORT.

ORDER NOW!

YES! I WANT TO ORDER NOW AND HAVE ENCLOSED.

- \$279.95 plus \$3.00 postage and handling for the DATA HANDLER BARE BONES KIT. (Includes P.C.B., P.C.B. case, 26 switch keyboard, and the complete instruction/owner's manual).
- \$189.95 DATA HANDLER COMPLETE KIT. (Includes P.C.B. and case, 26 switch keyboard, complete set of I.C.'s, one 6502 microprocessor, Sockets, LEDs, Resistors, Capacitors, 500ms Memory, and the complete instruction/owner's manual).
- \$224.95 THE COMPLETE DATA HANDLER ASSEMBLED AND TESTED.
- \$349.95 THE CASSETTE INTERFACE PACKAGE. This provides the DATA HANDLER with unlimited storage of user programs and requires only standard cassette tape recorder/player. It mounts on the P.C.B. and requires only the +5 volts available on the P.C.B. Reliably loads and recovers programs in 1/15 the time others take.
- \$315.95 THE DATA HANDLER EX/PRO 1 BOARD. (Memory expansion) enables the DATA HANDLER to expand into a professional system. Featuring 4K of static RAM, (expandable on board to 16K), 1K ePROM, (expandable to 4K), ePROM contains a resident cassette operating system which is especially designed for the D.H. along with the necessary video drivers, Video display, with R.F. modulator (64 character x 32 lines), and will interface the DATA HANDLER system to a standard black and white T.V. set.
- \$5.00 THE DATA HANDLER INSTRUCTION/OWNER'S MANUAL, which is refundable with future purchase of any of the DATA HANDLER products.


PLEASE PUSH ME THE FREE BROCHURE. PLEASE SEND ME COMPLETE DEALER INFORMATION

Name _____ Please send check or money order to:
 Address _____ WESTERN DATA SYSTEMS
 3650 Charles Street, Dept H
 Santa Clara, CA 95050
 City _____ State _____ Zip _____
 Bank of America or _____ or call:
 (408) 984-7804
 MasterCard # _____ Delivers time is 15 days from invoice.
 (All card charges, please add \$3.00 postage and handling) Total Amount Enclosed _____

CIRCLE 84 ON FREE INFORMATION CARD

WINNERS' CHOICE

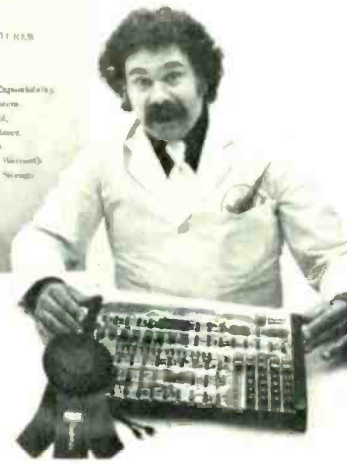- Low Cost
- Simple To Assemble/Program
- Complete One Board System
- Full Event Based Control
- Requires Only 4 Mhz. Power
- Kit Or Assembled Form
- Word Parts & Storage Memory
- Available With Camera Storage



SEE ONE OF OUR NEWEST DEALERS

QUEST ELECTRONICS
 1426-388 1660
 P.O. Box 4430
 Santa Clara, California
 BYTE SHOP SACRAMENTO
 (916) 961-2983
 6041 Glenhurst Lane
 Citrus Heights, California

TEK AIDS
 (312) 328-0110
 1513 Grant Street
 Evanston, Illinois

FUTURE ELECTRONICS
 (612) 822-2119
 3122 Hennepin Avenue
 Minneapolis, Minnesota
 ERIE COMPUTER CO
 (814) 454-8691
 1293 W. Eighth Street
 Erie, Pennsylvania

COMPUTER TERMINALS
 (415) 247-9884
 309 So. San Mateo Drive
 San Mateo, California

INTERNATIONAL SALES
 MICRO SERVICES INTERNATIONAL
 (415) 726-9197
 2 Sierra Road, #1
 Halfmoon Bay, California

Electronic Warning Flasher Kit

This battery operated device continuously emits bursts of intense light. Great safety device for bicycle riders, skiers, hikers, boaters & campers. Comes complete w/ all electronic parts, quality glass epoxy P-C board & easy to understand instructions. Uses high-output xenon flash tube which flashes 2 times per second when batteries are fresh. Operates continuously for 12 hours on 2 alkaline "C" batteries. You need only to supply the batteries and, if desired, a battery holder & case. C23207 \$6.95 (3 for \$18.00)

Strobe Light Kit
 C23207 \$6.95 (3 for \$18.00)

6 kV TRIGGER COILS 2 for \$1
 required to fire xenon flash tubes

Green Neon
 Same as NE2 but glows GREEN. Operates on 120V. 6 for \$1.00

LIQUID CRYSTAL WATCH DISPLAY
 WITH SPEAKERS \$1.25
 MOTOROLA (MILWAUKEE)

SLIDE SWITCH ASSORTMENT
 20 \$1.00

MV109 TUNING DIODE
 2 for \$1.00

LASCR
 200 VOLT .3 AMP. C23063 \$1.00

MICRO-MINIATURE ROTARY SWITCH
 1 POLE, 8 POSITION 79¢

HONEYWELL STROBE 14" SHUTTER CORD
 \$1.00

Electronic Flash Unit

Guide no. 28 ASA 25
 These were to be installed in cases but the final assembly was never completed. You get a complete working flash unit. Operates on 2 AA penlight batteries. You need only supply a shutter cord, battery holder & batteries, & if desired, some sort of case. Approx overall size of circuit board, reflector & capacitor 3" x 2 1/2" x 1 1/2". C22867 \$3.95

PHOTOFLR/M CAPS
 350 ml 330V 100
 720 ml 360V 150
 520 ml 500V 200

REFLECTOR
 Metal matte finish round reflector for electronic flash strobes, stage lights, etc. 3 1/4" Dia x 1 7/8" \$2.00

STROBE TUBE ASST.
 Brand new factory prime strobe tubes & assortment of strobe tubes. C23280 \$2.00

5V REED RELAY SPST \$1.00
5V REED RELAY SPDT 1.50
JUMBO YELLOW LL 5/51 00
7-05 5V REG. 5 \$1.00
400V 2A 1/2" SLR -GSE# 3/1 00



P.O. BOX 27038, DENVER, CO. 80227 Ph (303) 973-1052

Send for our FREE GIANT CATALOG of unique items!!!!

CIRCLE 58 ON FREE INFORMATION CARD

8K ECONORAM II™: kit \$135, 3 kits for \$375, assembled and tested \$155.

This is the board that thousands of owners sweat on, not at. There are lots of reasons, such as unique addressing options, reliability, full buffering, fast access time. A full set of sockets, but probably the most popular feature is the price, which is all the more remarkable because of the high level of quality. One owner reviewed this board in the 1/77 issue of KiloBaud, closing with the words "if you're not convinced by now that the Econoram II is one of the best memory buys on the market today, you really have to be one tough cookie—either that or you work for someone else who makes memory boards."



12K ECONORAM VI™: \$235

We proudly welcome our newest memory board family member, designed from the ground up for full compatibility with the Heath Company HB. Organized as two independent blocks, one 8K block and one 4K. Has the same basic features as our ECONORAM II™—all static design, switch selected protect and phantom sockets for all ICs, full buffering—plus the required hardware and edge connector to mate mechanically with the HB. You can have our 12K board for the price of the Heath Company's 8K with the performance you have come to expect from products carrying the ECONORAM trade mark.




A Message:

Now you can have the quality of Godbout products and the convenience of local shopping many computer stores and other electronic outlets stock a number of our items, from individual components to complete board kits.

We always welcome new dealers. If you have a store and want to know more about adding these popular products to your line, write or phone and ask for our dealer package.

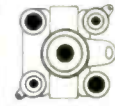Finally, we'd like to add that even inveterate optimists such as ourselves have been amazed and delighted at the response to our computer kits. We thank you very much for your support (and your patience during our period of heaviest expansion); it will enable us to keep you excited with more new goodies in the months ahead.



Send for our flyer

Terms: Cal res add tax. Allow 5% shipping, excess refunded. MasterCard® VISA® orders (\$15 min) call (415) 562-0636, 24 hrs. COD OK with street address.

GODBOUT
 BILL GODBOUT ELECTRONICS
 BOX 2355, OAKLAND AIRPORT, CA 94614

MORE COMPUTER ITEMS

"8K X 8 ECONORAM III™" Dynamic memories have a reputation for low power, economy — and difficulty of use. If you'd like to have the good without the bad, then this is the board for you. Not a kit, comes assembled, tested, and ready to run in any S-100 machine (Altair, IMSL, etc.) Configuration as two separate 4K blocks. Zero wait states with 8080 CPU. 1 year warranty. \$149.00

"Vector 8803 Bare 10 Slot Motherboard" This is a version of our 10 slot motherboard, but contains no edge connectors, active termination circuitry, or other components — just the board. Great for experimenters or people with small systems who don't need the full kit. \$29.50

10 SLOT MOTHERBOARD \$90
 18 SLOT MOTHERBOARD \$124
 These S-100 bus motherboards come with edge connectors and active termination circuitry

We got our start in this business selling components to fanatics, hobbyists who couldn't find the parts of their dreams anywhere else. What with all the attention being lavished on our computer kits, music kits, and hobby kits, we wanted to take this opportunity to remind you that we still sell parts at the same outrageously low prices that got us going in the first place.

Need some resistors? Capacitors? Or maybe some ICs, CMOS ladders, memories, Vector products (like the SMI-N-Wrap or wire pencil), or a really classy chassis to dress up your next project — we've got all that, and then some.

How about an American made, Switchcraft RCA phono jack? (Closed circuit too — that's a rare bird) Comes mounted on a little plastic carrier with screw holes for easy mounting. At 7 for \$1, here is a chance to stock up on some top quality connectors.

AUTO FM CONVERTER WITH WEATHER BAND
 Reg. 29.99 AU-560 **14.99** Converts AM Auto Radio to FM & Instant Weatherband

PUSHBUTTON AM AUTO RADIO
 • Mounts In Or Under-Dash
 • Volume & Tone Reg. 18.99 **8.49**

Cassette Tape, Pkg. of 3-30 Minute	TA-879	79¢
8-Track Tape, 40 Minute	TA-907	49¢
Earphones, 8 Ohm, Less Cord, Pkg. of 4	PH-405	49¢
Singer 12 Digit MOS Calculator Chip With Data	XM-635	1.79
UMF Varactor Tuner With Data Sheet	XM-676	1.49
Ceramic Capacitors, Pkg. of 100	CC-211	1.00
RED LED, 2 Volt, 10mA, Pkg. of 5	PL-233	59¢
LCD 3 1/2 Digit Display	XM-371	2.79
709 High Gain OP AMP	RE-131	79¢
Deluxe Stereo Headphones	PH-460	2.99
Ni-Cad Battery Pack (3 "AA" Size Cells)	BA-327	3.50
Cassette Lapel Mike, 3 5mm Pkg.	MM-174	1.00
3" Recording Tape, Pkg. of 5 (125' to 300')	TA-928	50¢
Sidemount For Auto Stereo or CB	AU-149	1.99
6 to 12 Volt DC Converter, 6V, Acc. On 12V, Batt.	AU-297	4.99
650 RPM Motor, 5 1/2" Shaft, 120V, AC	MO-265	1.00

OFFER GOOD ONLY IN THE CONTINENTAL U.S.

Olson electronics
 260 S. Forge St.
 Dept. L.A. Akron, Ohio 44327

NAME _____
 ADDRESS _____
 CITY _____ STATE _____ ZIP _____
 Qty. Stk. # Description Price Ea. Total _____

FREE Please Send Catalog Tax Postage TOTAL _____

CIRCLE 97 ON FREE INFORMATION CARD

RADIO-ELECTRONICS

CIRCLE 38 ON FREE INFORMATION CARD

THIS SPECIAL ONE CENT SALE IS FOR MAGAZINE ADS ONLY

POLY PAKS IS THE NEW WORLD'S 'CENT-ER' FOR DOUBLING YOUR MONEY

THIS NEW LIST OF "ONE-CENTERS" HELPS FIGHT INFLATION!

LEDS! YOUR CHOICE 5 for \$1.00 10 for \$1.01
1c SALE

Order by Cat. No.
 #R2135 JUMBO RED LEDS
 #R2137 MICRO RED LEDS
 #R2790 JUMBO RED CLEAR LEDS
 #R2792 JUMBO TAPE RED AMBER
 #R2140 MICRO GREEN LEDS

1.5 AMP BULLET RECTIFIERS!
Order by Cat. No. 4R60B84 and voltage

50V	10 for \$59	20 for \$60
100V	10 for 69	20 for 70
200V	10 for 79	20 for 80
400V	10 for 89	20 for 90
600V	10 for 109	20 for 110
800V	10 for 119	20 for 120

OP AMP 1c GIVEAWAYS

Type	2 for \$1.00	4 for \$1.01
LM308V	2 for 1.00	4 for 1.01
LM311V	2 for 1.00	4 for 1.01
LM558V	3 for 1.19	6 for 1.20
LM709N	10 for 1.19	20 for 1.20
LM741V	5 for 1.19	10 for 1.20
LM1800N	1 for .99	2 for 1.00
LM3900N	2 for 1.00	4 for 1.01

MICRO MINI TOGGLE SWITCHES!
3 Amps, 125 VAC contacts with chrome handles, complete with mounting hardware.

Cat. No.	Type	2 for \$1.29	4 for \$1.36
4R3936	SPDT	1.39	1.40
4R4037	DPDT	1.45	1.46
4R5087	4PDT	1.95	1.96

4 DIGIT FLUORESCENT CLOCK BASIC KIT

12 or 24 hours! 57" bright blue digits! Easy to breadboard, uses MM5316 clock chip and minimum of external components! AM-PM indicator, includes options for alarm, clock, snooze, and more! Basic kits include: readouts, ICs, sockets, transistors & all necessary components (case, PC board, transformer, line chord not included). Requires 12VCT transformer.

#R3791 Fluorescent Basic Kit \$9.95, 2 kits \$9.96
 #R3792 Components for optional alarm \$2.95 (No 1c sale)
 #R3796 12VCT "pluggable" transformer 1.95 (No 1c sale)

POLY PAKS® BIGGEST 1c GIVEAWAY SALE!

IT MAKES "CENTS" TO GIVE OUR CUSTOMERS THE BEST BARGAINS!

TTL'S, BUY ONE AT SALE PRICE, GET 2ND FOR ONLY 1c MORE

Honest Abe Penny Sale!

Type	Each	2 for
SN7483	.99	1.00
SN7484	.99	1.00
SN7486	.39	.40
SN7488	1.95	1.96
SN7490	.69	.70
SN7491	.79	.80
SN7492	.45	.46
SN7493	.49	.50
SN7494	.69	.70
SN7495	.69	.70
SN7496	.69	.70
SN7498	.69	.70
SN74100	1.49	1.50
SN74107	.39	.40
SN74111	.19	.20
SN74113	.19	.20
SN74114	.25	.26
SN74121	.45	.46
SN74123	.69	.70
SN74125	.59	.60
SN74126	.39	.40
SN74132	1.25	1.26
SN74140	.99	1.00
SN74141	1.49	1.50
SN74145	1.25	1.26
SN74148	1.75	1.76
SN74150	.99	1.00
SN74151	.99	1.00
SN74153	.99	1.00
SN74154	1.75	1.76
SN74155	.79	.80
SN74156	.69	.70
SN74157	.99	1.00
SN74158	.99	1.00
SN74160	1.25	1.26
SN74161	1.25	1.26
SN74163	1.19	1.20
SN74164	1.35	1.36
SN74165	1.25	1.26
SN74166	1.25	1.26
SN74173	1.25	1.26
SN74174	1.25	1.26
SN74175	.99	1.00
SN74177	.79	.80
SN74179	1.49	1.50
SN74180	.49	.50
SN74182	.69	.70
SN74190	1.49	1.50
SN74191	1.75	1.76
SN74192	.85	.86
SN74193	.85	.86
SN74194	1.25	1.26
SN74198	.49	.50
SN74197	.75	.76
SN74199	1.75	1.76
SN74200	5.50	5.51
SN74251	1.75	1.76
SN74284	4.50	4.51
SN74285	4.25	4.26

POP-AMPS AT "CENT-CIBLE" PRICES
Buy ONE At Sale Price, Get 2ND For Only 1c More - Order By Type No.

Type	Each	2 for
LM300H	\$4.49	\$5.50
LM301H-V	.45	.46
LM306H-V	.79	.80
LM309H	1.29	1.30
LM311H-V	.79	.80
LM318V	1.29	1.30
LM320H-5, 12, 15	1.29	1.30
LM320H-15	1.29	1.30
LM320T-5, 15	1.29	1.30
LM322N	1.19	1.20
LM324N	1.75	1.76
LM339N	1.09	1.10
LM340K-5, 6, 8, 12, 15, 18, 12.15, 18, 15, 6, 8	1.29	1.30
LM340T-5, 6, 8, 12, 15, 18, 24	1.29	1.30
LM350N	.59	.60

Type	Each	2 for
LM370H	1.79	1.80
LM376V	.29	.30
LM377N	2.25	2.26
LM381H	1.69	1.70
LM531H	1.49	1.50
LM532H-N	.29	.30
LM555V	.75	.76
LM588V	.49	.50
LM561N	1.00	1.01
LM565N	.99	1.00
LM703H	.49	.50
LM704H	.29	.30
LM709H-N	.25	.26
LM710N	.39	.40
LM733N	.79	.80
LM739N	.89	.90

Type	Each	2 for
LM1304	.80	.79
LM1310	1.00	.99
LM1312	2.00	1.99
LM1414V	.80	.79
LM1458V	.70	.69
LM1800V	1.00	.99
LM3028H	.66	.65
LM3900N	.50	.49
LM490V	1.75	1.74
LM491V	1.96	1.95
LM4250	1.20	1.19
LM75451	.40	.39
LM75453	.40	.39
LM75491	.80	.79
LM75492	.80	.79
LM75494	.70	.69
PA263	1.50	1.51

BUY 1 AT OUR SALE PRICE GET 2 FOR 1c MORE

Order by Cat. No.

Type	Each	2 for
LM308V	2 for \$1.00	4 for \$1.01
LM311V	2 for 1.00	4 for 1.01
LM558V	3 for 1.19	6 for 1.20
LM709N	10 for 1.19	20 for 1.20
LM741V	5 for 1.19	10 for 1.20
LM1800N	1 for .99	2 for 1.00
LM3900N	2 for 1.00	4 for 1.01

POP-AMPS AT "CENT-CIBLE" PRICES
Buy ONE At Sale Price, Get 2ND For Only 1c More - Order By Type No.

Type	Each	2 for
LM300H	\$4.49	\$5.50
LM301H-V	.45	.46
LM306H-V	.79	.80
LM309H	1.29	1.30
LM311H-V	.79	.80
LM318V	1.29	1.30
LM320H-5, 12, 15	1.29	1.30
LM320H-15	1.29	1.30
LM320T-5, 15	1.29	1.30
LM322N	1.19	1.20
LM324N	1.75	1.76
LM339N	1.09	1.10
LM340K-5, 6, 8, 12, 15, 18, 12.15, 18, 15, 6, 8	1.29	1.30
LM340T-5, 6, 8, 12, 15, 18, 24	1.29	1.30
LM350N	.59	.60

PENNY SALE PRICES LISTED ARE GOOD TILL MAY 15, 1978
WE RESERVE THE RIGHT TO LIMIT QUANTITIES!!!!!!
Mail your order in & save many dollars!

Qunt.	Description (Order by Cat. No. in parenthesis)	Sale	1c SALE
10	CALCULATOR KEYBOARDS, 20 keys and more (4R3524)	\$2.00	20 for \$2.01
15	SLIDE VOLUME CONTROLS, asstd values (4R3057)	2.00	30 for 2.01
10	CRYSTALS, may include CB, Ham & more (4R3250)	2.00	20 for 2.01
150	MOLEX IC SOCKETS, to 1 meg, 3 turn, 1W (4R3245)	2.00	300 for 2.01
100	TERMINAL STRIPS, rom 2 lugs up (4R3136)	2.00	200 for 2.01
30	NE-NEON LAMPS, all 100%, good (4R2613)	2.00	60 for 2.01
40	SHIELDED CABLE, 1 cond, mika, phono (4R3577)	2.00	80 for 2.01
50	TRANSISTOR ELECTROS, asstd values, nylon (4R2747)	2.00	100 for 2.01
3	SOUND TRIGGERS, sound triggers scr w/amp (4R3625)	2.00	6 for 2.01
15	6V TEST INDICATORS, leads, grain-o-wheat (4R3526)	2.00	30 for 2.01
100	CAPACITOR SPECIAL, discs, mylar, lytics, more (4R2738)	2.00	200 for 2.10
30	MINI TRIMPOTS, to 1 meg, 1 turn, 1W (4R3937)	2.00	60 for 2.01
10	VOLTAGE REGULATORS, hobby LM320, 340, TO-3 (4R2330)	2.00	20 for 2.10
30	PANEL SWITCHES, slides, rotaries, mod. etc (4R3268)	2.00	60 for 2.01
200	RESISTOR SPECIAL, 1/4 to 1W, carbon, metal (4R3054)	2.00	400 for 2.01
200	HALF WATTERS, resistors, carbon, metal (4R3046)	2.00	400 for 2.01
100	NATIONAL IC BONANZA, linear, 7400s ROMs (4R2860)	2.00	200 for 2.01
40	HOBBY LEDS, asstd types, mostly useable (4R2859)	2.00	80 for 2.01
15	LM340T VOLTAGE REGULATORS, 5 to 24V, TO-220 (4R2635)	2.00	30 for 2.01
100	TWO WATTERS, resistors, carbon-metal marked (4R2735)	2.00	200 for 2.01
100	POLYSTYRENE CAPS, asstd values, voltage, HQ (4R2729)	2.00	200 for 2.01
50	THERMISTORS, resistors that change with temp (4R4089)	2.00	100 for 2.01
20	BRIDGES, untested, 2, 4, 6, 10, amp, full wave (4R4022)	2.00	40 for 2.01
25	LAMP "SOCKET" SETS, micro, 1.5W, T2 (4R3937)	2.00	50 for 2.01
15	MIXED READOUTS, hobby, untested, 127, 3, 5, etc (4R3619)	2.00	30 for 2.01
150	QUARTER WATTERS, resistors, metal film, marked (4R3413)	2.00	300 for 2.01
100	PLASTIC TRANSISTORS, untested, RO-92 (4R2604)	2.00	200 for 2.01
200	PRECISION RESISTORS, 1/4, 1W, 1%, 2% marked (4R2608)	2.00	400 for 2.01
60	DIPPED MYLARS, shiny finish, asst values (4R2597)	2.00	120 for 2.01
30	VOLUME CONTROL DS, audio, linear, asst values (4R2421)	2.00	60 for 2.01
5	7.5 VOLT ZENER DIODES, 1 watt (4R1871)	1.00	2 for 1.01
5	9.1 VOLT ZENER DIODES, 1 watt (4R5188)	1.00	10 for 1.01
30-F	WIRE WRAP WIRE, 30 gauge (4R3830)	1.19	60-ft for 1.20
5	TANTALUM CAPS, 2.2uf, 25V (4R5189)	1.00	10 for 1.01
1	TV GAME SWITCH, choose TV or game, 75 pr 300 ohms (4R3970)	1.00	2 for 1.01
1	ALARM CLOCK CHIP, MM5316, 4 digits (4R1759)	2.95	2 for 2.96
5	PANCAKE PHOTOCELLS, 600 to 15K ohms (4R2939)	1.00	10 for 1.01
1	100MHZ MARKER CRYSTALS, approx for marker gen (4R3896)	1.95	2 for 1.96
1	MOTHERBOARD EDGE CONNECTOR, 106 pins, 125" (4R3967)	3.50	2 for 3.51
1	48-PIN EDGE CONNECTOR, .156" spacing (4R3963)	1.95	2 for 1.96
1	JOSTYCK, two 10K pots, for computers, TV games (4R5037)	2.95	2 for 2.96
1	CHARACTER GENERATOR, 5 x 7 Mosaic MK 202P (4R3898)	4.95	2 for 4.96

READOUTS!

3 1/2 DIGIT LCD WRISTWATCH DISPLAY, (#R3960)	3 for \$1.19	6 for \$1.20
GE FLUORESCENT NIXIES, 7-seg, blue (#R3684)	1 for 1.00	2 for 1.01
SPEERRY FLAT NIXIES, orange dual digit (#R5014)	2 for 1.19	4 for 1.20
SPEERRY FLAT NIXIES, orange, 3", 1 1/2-digit (#R4051)	2 for 1.19	4 for 1.20
MAN-3 BUBBLE READOUT, .19" red, com cath, (#R4338)	6 for 1.00	12 for 1.01
MAN-4 READOUT, bubble, red, com anode (#R4503)	2 for 1.00	4 for 1.01
FND-10 BLOCK READOUT, 122" com cathode (#R4802)	2 for 1.19	4 for 1.20
8-DIGIT READOUT, led, com cathode, (#R45190)	1 for 1.95	2 for 1.96

SPEAKERS!

6" TWIN CONE SPEAKER, hi-fi, for car's home (#R5059)	Each \$4.50	2 for \$4.51
2 1/2" x 5" OVAL SPEAKER, 8 ohms (#R2553)	1.49	1.50
2" x 6" OVAL SPEAKER, 8 ohms (#R3454)	1.49	1.50

MICROPHONES!

CONDENSOR MIKES, sensitive, 500 ohms, 1/2W (#R3178)	Each \$4.95	2 for \$4.96
COMMUNICATIONS MIKE, 500 ohms, CB-HAM (#R4074)	4.50	4.51
NOISE CANCELLING MIKE, Ham-CB, 500 ohms (#R3902)	6.95	6.96

RELAYS!

SPDT 12V BLOCK RELAY, 5A contacts (#R4032)	Each \$1.98	2 for \$1.99
SPDT 12V REED RELAY, 1A contacts (#R4094)	1.49	1.50
SPDT 12V SENSITIVE, 2000 ohm coil (#R3044A)	1.95	1.96

AMPLIFIERS!

8 WATTS ON A BOARD, with built-in preamp (#R5040)	Each \$5.95	2 for \$5.96
9 WATTS ON A CHIP, Toshiba TA7205 (#R5057)	4.95	4.96
3 WATTS ON A CHIP, G-E PA 263 (#R1522)	1.50	1.51

TRANSFORMERS!

12V TRANSFORMER, 300ma, pc leads, 110pri, (#R3412)	Each \$1.49	2 for \$1.51
12V TRANSFORMER, 1A, 110V ZIOP, open frame (#R4040)	2.95	2.96
24VCT TRANSFORMER, 300ma, open frame, 110pri, (#R3323)	1.95	1.96

DIP SWITCHES!

2 SWITCHES ON A DIP (#R3668)	Each \$1.77	2 for \$1.78
3 SWITCHES ON A DIP (#R3669)	.88	.89
6 SWITCHES ON A DIP (#R3671)	1.29	1.30

IC SOCKETS!

8-PIN MINI-DIP (#R2123)	4 for \$1.19	8 for \$1.20
14-PIN DIP (#R1308)	3 for 1.19	6 for 1.20
16-PIN DIP (#R1309)	3 for 1.19	6 for 1.20
18-PIN DIP (#R1376)	2 for 1.19	4 for 1.20
24-PIN MS/DIP (#R3886)	2 for 1.19	4 for 1.20
28-PIN MS/DIP (#R3887)	2 for 1.19	4 for 1.20
8-PIN TO-5 (#R1307)	4 for 1.19	8 for 1.20

2-Amp Epoxy BRIDGE RECTIFIERS!

PENNY SALE! BUY ONE AT SALE PRICE, GET 2ND FOR ONLY 1c MORE

PIV	Sale Each	2 for
100	\$5.59	\$6.60
200	.79	.80
400	.89	.90
600	.99	1.00
800	1.19	1.20
1000	1.29	1.30

Order by Cat. No. 4R2447 & voltage

PRV	Sale	2 for
50	\$1.29	\$1.30
100	1.49	1.50
200	1.19	1.20
400	1.99	2.00
600	2.25	2.26
800	2.50	2.51

10 AMP - POWER TABS! SCRS! TRIACS! QUADRACS!

Order by Cat. No. and voltage

PRV	Sale	2 for
50	\$1.55	\$1.56
100	.69	.70
200	.89	.90
300	1.19	1.20
600	1.59	1.60

POLY PAKS CATALOG FEATURING **BEST BARGAINS** IN ELECTRONICS

FREE!

Terms: Add postage. Rated: net 30
Phone: Wakefield, Mass. (617) 245-3829
Retail: 16-18 Del Carmine St., Wakefield.
MINIMUM ORDER — \$6.00

POLY PAKS
C.O.D.'s MAY BE PHONED
P.O. BOX 942E
LYNNFIELD, MA.

WIREWRAP

PRECUT WIRE

Why buy wire on rolls?

PRECUT & STRIPPED WIRE IS:

- Fast - No more cutting & stripping by hand
- Reliable - Good, clean, uniform strip
- Economical - Cheaper than using bulk wire

Precut Wire

100 pcs of 3' at \$1.82 - 3 1/4' ft. 50 ft. roll at \$1.99 - 42 ft. 100 pcs of 6' at \$1.06 - 24 ft. 100 ft. roll at 2.95 - 36 ft. Wire Kit 1 at \$6.95 - 2 1/2' ft.

Bulk Wire

100 pcs of 3' at \$1.82 - 3 1/4' ft. 50 ft. roll at \$1.99 - 42 ft. 100 pcs of 6' at \$1.06 - 24 ft. 100 ft. roll at 2.95 - 36 ft. Wire Kit 1 at \$6.95 - 2 1/2' ft.

* 30 Kynar stripped 1" on each end. Lengths are overall. Colors: Red, Blue, Green, Yellow, Black, Orange, White. Wire packaged in plastic bags. Add 25¢ length for tubes.

	100	500	1000	5000
2 1/2 in.	78	2.40	4.30/K	3.99/K
3 in.	82	2.60	4.71/K	4.22/K
3 1/2 in.	86	2.80	5.12/K	4.55/K
4 in.	90	3.00	5.53/K	4.88/K
4 1/2 in.	94	3.21	5.93/K	5.21/K
5 in.	98	3.42	6.34/K	5.52/K
5 1/2 in.	102	3.65	6.75/K	5.88/K
6 in.	106	3.85	7.16/K	6.19/K
6 1/2 in.	115	4.05	7.57/K	6.52/K
7 in.	120	4.25	7.98/K	6.89/K
7 1/2 in.	125	4.45	8.39/K	7.18/K
8 in.	129	4.65	8.80/K	7.53/K
8 1/2 in.	132	4.85	9.21/K	7.84/K
9 in.	136	5.05	9.62/K	8.17/K
9 1/2 in.	140	5.25	10.03/K	8.50/K
10 in.	145	5.51	10.44/K	8.83/K
Add in.	10	41	82/K	66/K

WIRE KITS

# 1	\$6.95	# 2	\$19.95
250 3' 100 4'		250 2' 250 4' 250 6'	
250 3' 100 5'		100 3' 250 5' 100 6'	
100 3' 100 6'		100 3' 100 5' 100 7'	
		500 3' 1,250 ft. Roll Bulk	

Choose One Color or Assortment

WIREWAP SOCKETS

	1-9	10-24	25-99	100-249	250-999	1K-5K
8 pin	41	38	35	31	29	27
14 pin	42	39	36	32	29	27
16 pin	46	43	39	35	32	30
18 pin	63	58	54	47	44	41
20 pin	84	75	71	63	59	54
22 pin	130	120	110	95	90	84
24 pin	91	84	78	68	64	59
28 pin	125	115	108	95	89	82
40 pin	165	155	142	125	115	106

Gold 3-level Closed Entry Sockets
End & Side Stackable All prices include gold
Tm sockets and 2-level sockets available

WIREWAP TOOLS



\$34.95

HOBBY WRAP
Model BW 630
With Free Wire Kit 1
(\$6.95 Value)

- Batteries & Charger \$11.00
- WSU 30 Hand Wrap-Unwrap Strip Tool 5.95
- WSU 30M, for Modified Wrap 6.95
- BT 30 Extra Bit 2.95

INTERCONNECT CABLES

Ribbon cable connectors for connecting boards to front panels or board to board

	SINGLE ENDED		DOUBLE ENDED	
	14 pin	24 pin	14 pin	24 pin
6"	1.24	1.34	2.05	2.24
12"	1.33	1.44	2.24	2.33
24"	1.52	1.65	2.63	2.52
48"	1.91	2.06	3.40	3.17

Ordering Information:

- Orders under \$25 and COD's, add \$2
- All others, shipped Ppd in U.S. via UPS
- For Blue Label (Air) or 1st Class, add \$1
- We accept Visa & MasterCard
- Most orders shipped same day

Dealer Inquiries Invited

PAGE DIGITAL ELECTRONICS

135 E. Chestnut Street 4A
Monrovia, California 91016
Phone (213) 357-5005

Reliable TV Antenna System Components

Connectors

- F-59 \$1.17
- RG59 Connector with Crimp Ring
- F-56 \$2.20
- RG6 Connector with Crimp Ring
- F-81 \$4.40
- Female Splice
- G-59P \$4.40
- Mates with "G" Type Fitting
- MP-1 \$4.40
- Motorola Plug with Ring

Splitters

- MS-2 Unique \$2.95
- MS-4 \$4.95
- BD-1 \$2.00
- 75 OHM Input PC Board

Transformer

- (75-300 OHMS - INDOOR)
- ACU-1 \$9.5
- Features: UHF, VHF, FM, AC/DC blocking, Shielded and balanced, Minimal direct back-up

Band Splitters

- BD-2 \$1.40
- 75 OHM Input PC Board

Wall Plate

- DUPEX TYPE-CONNECTOR BACK \$2.10
- FDP-8 \$4.60
- Flush mounted UHF/VHF/FM tapout. Single 75 ohm output from 75 ohm thru line. Dual isolations 12V F-80 on 17.25 ohm. 1 power isolation as supplied clip (1) wire for higher isolation. Supplied with mounting screws.

Specialty Items

- FAM \$2.10
- Available in 3, 6, 11 & 20 dB attenuation

- FM 10AP \$4.60
- 75 ohm FM band rejection tap. Top of 30 dB attenuation at access FM band with minimum insertion loss. Supplied with two tabs. Connects mounting, AC/DC, pass-4.
- MSJ \$4.60
- HIGH ISOLATION FILTER
- MSJ separates a basic 75 ohm 2 thru line and FM signal from high band channels. 11db 3 thru line. 11db 5 thru line. 11db 7 thru line. 11db 997 thru line. 11db 999 thru line.

FREE 32 PAGE CATALOG

MINIMUM \$10.00 PLEASE

TASCO TEXAS ANTENNA SUPPLY CO.
PO BOX 30143
HOUSTON, TEXAS 77009

- Distribution Amplifiers
- Wall Plates
- Jumper Cables
- Drop Taps - Two & Four Way
- Outdoor Baluns

SENCORE VALUE FROM FORDHAM

FOR PRICING AND TO ORDER

CALL TOLL FREE
(800) 645-9518

For N.Y. State call (516) 752-0050

FREE 164 page catalog of over 3000 items ... test equipment, CB, tools, tubes, components and electronic supplies

FORDHAM
YOUR ONE STOP DISCOUNT CENTER



RADIO SUPPLY CO., INC.
855R Conklin St
Farmingdale, N.Y. 11735

TRANSISTOR & FET TESTER Model TF 46 Portable Super Cricket

- Completely portable
- Automatic
- Simple to use
- Automatic power shut-off after 10 minutes



FREQUENCY COUNTER Model FC 45

- Frequency range coverage for every use from audio through VHF
- Better than FCC accuracy.
- High sensitivity for circuit testing
- Easy-to-use pushbuttons.
- Direct readout.




AUTOMATIC CB ANALYZER Model CB 42

- The total CB service bench ... simplified.
- Combines 5 units in one for complete testing:
 - 1) Frequency Counter;
 - 2) RF-IF Generator;
 - 3) Audio Generator;
 - 4) Digital RF Wattmeter; and
 - 5) Special CB Tester



TV-VTR-MATV & VIDEO ANALYZER Model VA 48

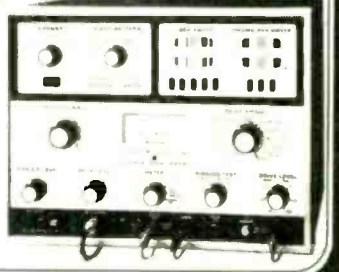- New patented Bar Sweep patterns for simplified speed alignment
- All RF & IF signals for injection before the detector from one cable
- All drive signals for every stage after the detector - tube and solid state
- Uses standard color bars and patterns
- 100% accurate Ringer yoke and flyback test
- Accurate drive signal monitoring
- Video sweep generator
- Bias and B+ substitute power supply.



hobbi house

Send for Free Hobbi House Catalog
969 BALL AVE., UNION, N.J. 07083
Retail Store Open Mon.—Sat., 9 to 6

lowest prices



**MA1003
MOBILE CLOCK
MODULE (National)**
\$18⁹⁵ complete

Attaches directly to 9-12V Battery. Automatic Nighttime Dimming. Fluorescent Display gives Color Choice (Red, Blue, Green or Yellow) when used w/corresponding Color Filter. Includes — Module, Switches, & Filter

ALUMINUM CASE WITH FILTER.

(switches included with clock kit). In Silver, Bronze, Black and Gold. Filter colors — red, blue, green, or yellow. **\$5.75**

Complete Clock Kit \$9.95
4 DIGIT 12 24 HOUR

Includes: PC Board, 5316 Clock Chip, all components and Power Supply.

Displays hours and minutes . . . Switch to minutes and seconds . . . AM-PM Indicator . . . Elapsed Timer . . . Fluorescent Display
Options: If alarm function desired add \$2.50 (includes speaker and all components)
Plexiglas Case Kit (red or blue) \$2.00

Transformer \$1.49
6.3 volts at 1.2 amps

Capacitors
500 MFD at 50V 4/\$1.00
500 MFD at 15V 6/\$1.00

Clock Chips
MM5314 or MM5316 \$3.50

Voltage Regulators.
Positive — To 220 Pkg \$1.00
7805, 7806, 7812, 7815, 7824
Negative — To 220 Pkg \$1.25
7905, 7912, 7915
To — 3 Pkg. — LM309K \$1.25

Dry Reed Switch Capsules 25/\$1.98
Glass Sealed, 5 amp 115 VAC

1C Sockets \$1.00
8, 14, 16, 18 Pin 5/\$1.00

Bridges
1.5 amp, 200v 3/\$1.00
3 amp, 200v 3/\$1.25

Bridges

VOLT	2 AMP	4 AMP	6 AMP	25 AMP
50	\$.60	\$.70	\$.80	\$1.30
100	.70	.80	.90	1.40
200	.80	.90	1.00	1.60
400	1.00	1.10	1.20	
600	1.25	1.35	1.40	

Your Home for Quality Kits, Projects and Components
Toll-Free Wats Line — 800-631-7485 • Open Saturdays
In New Jersey Call (201) 964-5206

250 K Slide Volume Controls . . 4/\$1.00
By Mallory

2 Amp Circuit Breaker 2/\$1.00
Front Panel Mount through 1/2 dia. hole.
120 VAC, 32 VDC. Trips at 2.7 amps.

Grain of Wheat type chic. min. Display
Lamp — red or white 10/\$1.00


60 Hz. Crystal Time Base Kit . . . \$4.95
Use with Digital Clocks for 12 VDC or
Portable Operation.
Kit includes: PC Board, 5369 Divider Chip,
3.5795 MHZ XTAL and all other parts plus
complete instructions.

70 Volt Line Transformer \$2.90
Power Rating — 10 watts, Model TR-1
Primary Volts: 70.7 — Primary Taps: 0.63,
1.25, 2.5, 5, and 10 W. Secondary Impedance:
4 & 8 ohms. Primary and Secondary Terminations:
8" color coded leads. 1% "H, 1" 1/16D, 2" W,
Base 2 3/8" W

6" Pioneer Pincushion Speakers
3.2 ohms, 7 1/2 watts \$3.95 pair

Heavy Duty Alligator Clip Test Lead
Set \$2.49
Set of 10 color coded leads with insulated
alligator clip on each end.

3-WAY AUTO SPEAKER STEREO SYSTEM

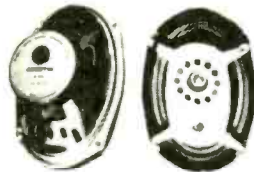

3-WAY Concert Hall Sound

Two 6"x9" 20 ounce 3-Way
Speakers complete with
chrome accents padded vinyl
grilles, mounting cables and
hardware. **Only \$49.95**

High Power Transistors 2/\$1.00
2N3055 NPN (ITT TO 3 Case)

1000 MFD 30 Volt Electrolytic
Capacitor Axial Leads 5 for \$1.00

AC/DC Wall Plug
Adaptor-Charger \$1.00
120 volt input/6VDC 130 MA output.

Sound Actuated Switch \$.85
6 Ft. Line Cords 6 for \$1.00

DL741 Jumbo Displays \$1.35
7 Segment-Common Anode

Diffused LED's, Jumbo Red LEDs 0.2",
and Factory Prime . . . 7/\$1.00, 100/\$11.00

7 SEG LED Displays \$.59 ea., 10/\$5.00
33" Type 707/MAN-1 14 Pin Dip, Com-
mon Anode or Cathode.

Jumbo Red LED's 10/\$1.00,
100/\$9.00

25 PK. LED's Asstd Sizes &
Colors \$2.50

WESTINGHOUSE TUBE SPECIAL BOXED AND BRANDED

6GH8A	\$1.60
6LQ6 6JE6C	4.00
6DW4B 6CL3	2.00
3A3C	2.50
6HM5 6HA5	2.00
6FQ7 6CG7	1.60
6LB6	4.00
6GF7A	2.50
6BK4C 6EL4A	4.00
8FQ7 8CG7	2.00
6JS6C	4.00
12GN7A 12HG7	3.00
6GJ7 ECF801	2.00
17JZ8	2.00
5GH8A	2.50

Plug-In Component Oven \$1.75
Used in housing crystals, I.C.'s etc. — for
stable operation. Temp.: 65 C-3 C. 1/2 C.
Regulation 24V. Bi Filar Winding. Cold
Resistance: 110 ohms 10%, 2.4 watts @
25 C 6.5 watt max.

6 Digit LED Alarm Clock Kit and
Elapsed Timer Indicator . . . \$13.95

Red Display
Complete kit includes: National 5375AB Clock
Chip, Transformer; PC Boards, Drilled and Silk
Screened; SLA-7 Red 33 High Brightness
Displays; All components; Instructions and
pictorials.
Features: Hrs., Min., and Sec. . . . 12 Hr.
format with 24 hr. Alarm . . . Snooz Fea-
ture . . . AM PM Indication . . . 60 min.
elapsed Timer . . . Freeze Capability . . .
Power Fail Indicator.
Options: Wood grain case \$4.00 when pur-
chased with kit.

Potentiometer Assortment . . 12/\$1.00
Includes 1K to 100K. Tab mounts, printed
circuit, duals, push-pulls, nylon and metal
shafts (long and short)

IN 4148 Switching Diodes . . . 50/\$1.00
Factory prime, taped and reeled

Mini-Audio Transformers . . . 10/\$1.99
Asst. of outputs 1" square

15 Trimmers & Sensitivity
Controls 5/\$1.00
2.5 meg central cermet trimmers and
miniature wire wound rheostats.

LM 555 Timers 3/\$.99
Vinyl Electrical Tape 2/\$1.00
8 mil x 3/4" x 66"

Screws \$1.99 lb.
1 pound, assorted sizes

C106 SCR to 202 Package \$.99
300 V, 4 amp

Terms and Conditions

\$7.00 Min. C.O.D. Order, Phone Orders
accepted.

\$15.00 Minimum Bank Americard/
MasterCharge order.

Add \$1.50 Postage and handling on all
orders.

Outside Continental U.S., U.S. Funds
only. — Add postage -

N.J. Residents — 5% Sales Tax.
Money Back Guarantee on all orders.

PLAYMASTER 40W + 40W PROFESSIONAL AMPLIFIER KIT

The PLAYMASTER 4040 is a sophisticated, advanced design incorporating the latest developments, yet uses reliable, rugged, easily available components. The 2N3055 power transistors, for example, are the most popular power transistors in the world. If disaster strikes and they need to be replaced, you'll have no trouble buying spares.



ONLY \$105.
each
kit

	MODEL 25W/40W	MODEL 75W/40W
POWER OUTPUT	One Channel	Both Channels
4 ohms	35W/54W	27W/43W
8 ohms	25W/40W	22W/34W
16 ohms	15W/24W	13W/21W
FREQUENCY RESPONSE	R.I.A.A. equalization within 1dB from 30 Hz to 20 kHz	
Phono inputs	20 Hz to 20 kHz - 1 dB	
High level inputs	10kHz -33dB	1kHz -46dB
CHANNEL SEPARATION (with respect to 25W)	100 Hz	-40dB

SPECIFICATIONS

HUM & NOISE	Phono (with respect to 10mV)	70dB unweighted with typical cartridge
Other inputs	70dB unweighted with inputs open circuit	
TOTAL HARMONIC DISTORTION	At full power with both channels operating from 20 to 20kHz less than 0.2% Typically less than 0.05% at normal listening levels	
INPUT SENSITIVITY	Phono at 1kHz	2mV
	Overload at 1kHz	120mV
	High level inputs	150mV 35µ (minimum)

DAMPING FACTOR	at 1kHz	> 60
	at 30kHz	> 30
STABILITY	operational	
TONE CONTROLS	Bass	+12 -13dB at 50Hz
	Treble	±10dB at 10kHz

SPECIALS OF THE MONTH

I.C. SOCKETS ON SALE !!

14 PIN S/T	10 FOR	\$2.00
16 PIN S/T	10 FOR	\$2.40
14 PIN W/W	10 FOR	\$3.50
16 PIN W/W	10 FOR	\$4.00
28 PIN S/T	5 FOR	\$3.50
28 PIN W/W	5 FOR	\$4.50

T.I. LED DISPLAY SPECIAL

TIL 305	5 X 7 Alphanumeric	\$3.50 ea.
TIL 311	Hexadecimal with Logic	\$4.50 ea.
TIL 306	7 Seg with Logic	\$6.70 ea.
<i>(Counter, Latch, Decoder, and Driver built-in)</i>		
TIL 308	7 Seg with Logic	\$4.75 ea.
<i>(Latch, Decoder, and Driver built-in)</i>		



SUPER 15 WATT AUDIO AMP KIT

Uses STK-015 Hybrid Power Amp

Kit includes: STK-015 Hybrid IC, power supply with power transformer, front Amp with tone control, all electronic parts as well as PC Board. Less than 0.5% harmonic distortion at full power 1/2dB response from 20-100,000 Hz. This amplifier has QUASI-Complimentary class B output. Output max is watt (10 watt RMS) at 4 Ω.

ONLY \$23.50 each

"FISHER" 30 WATTS STEREO AMP KIT (15W x 2)



Kit includes: 2 pcs. Fisher PA301 Hybrid IC all electronic parts with PC Board. Power supply: +16V DC (not included). Power band with (KF = 1% ± 3dB). Voltage gain: 33dB, 20Hz-20KHz.

ONLY \$22.50 each kit

MINIMUM ORDER \$10.00. California residents add 6% sales tax. All orders add 10% postage for out of state. Overseas countries add 15% of total order for postage. SEND CHECK OR MONEY ORDER TO:



FORMULA INTERNATIONAL INC.

12603 CRENSHAW BOULEVARD • HAWTHORNE, CALIFORNIA 90250
For more information please call (213) 679-5162
STORE HOURS 10-7 Monday - Saturday

CIRCLE 91 ON FREE INFORMATION CARD


JUMBO LED READOUT ARRAY



\$1.95 LIMITED STOCK

By Bowmar. .5 in. character common cathode. Designed for use with multiplexed clock chips 4 digits in 1 pack!

3W. AUDIO AMP

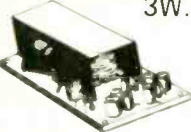

\$3.95
2 1/4 x 3"

Assembled & tested. Not a kit. Has tapped output for either 4, 8 or 16 OHMS. With schematic.

CMOS SPECIAL!

CD4001-5/\$1. CD4011-5/\$1.
CD4013-3/\$1. CD4040-1. each
CD4042-2/\$1. CD4049-3/\$1.

FILTER CAP

Mini Size. Axial. 1,000 MFD. 16 WVDC. 4/\$1.00

RED LED READOUT FILTER
Very handy. Can be used with our calculator displays. 2 1/4 x 1/2" 6/\$1.

2708 1KX8 EPROMS 2708

Prime new units from a major mfg. 450 N.S. access time. Equivalent to 4-1702 A's in 1 package! 450 ns \$15.75 each

MOTOROLA 7805R Voltage Regulator

Same as standard 7805 except 750 MA output. TO-220. 5VDC output. 44c each 10/\$3.95

4K STATIC RAM'S

2114. The new industry standard. Arranged as 1K x 4. Equivalent to 4-21 L02's in 1 package! 18 Pin DIP. 2 chips give 1Kx8. 2 for \$24. 8 for \$85.

OPCOA LED READOUT

SLA-1 Common Anode. .33 inch character size. The original high efficiency LED display.

75c ea. 4/\$2.50

TRANSFORMER

12 Vac. 60 MA. PRI-115 VAC 60 HZ. Perfect for clocks or power supplies!

Small Size. \$1.95

LED IC Counter Kit

You Get: 1-7490; 1-7475; 1-7447; 1- Led Readout. All this for \$1.99 (Led Readout is famous SLA-1. .33 in. By Opcoa.)

741C OP AMPS

Mini Dip. Prime new units. Has computer Mfg's house number. 12/\$2. 100 for \$15.

DISC CAPACITORS

.1 MFD 16V. P.C. leads. Most popular value! By Sprague. 20 for \$1.00

Full Wave Bridge
4 Amp 200 PIV
69c ea. 10/\$5.75

5V. NI-CAD Battery
4 cell Pack. Rated 500 MAH. NEW!
\$3.95 pack

2N3904-House No.
TO-92. NPN.
VCEO-45.
HFE 100 to 300
10 for \$1.00

Jumbo Red Leds
New by G.E. Like MV5024. Number SSL-22. 6/\$1. 25/\$3.75

Motorola PNP Power!
2N4905. TO-3 case. 90W. VCEO-60; HFE-100 max. at 2.5A. Good mate for the 2N3055. 75c each. 4/\$2.50 PRIME!

TI POWER TRANSISTORS
TO-220. VCEO-60V. 30W.
TIP29A-NPN 44c
TIP30A-PNP 44c

CMOS QUAD Bilateral Switch
CM4116. By Solitron. An improved CD4016. 3/\$1.

Motorola Quad Op-Amp MC3401. Pin for Pin Sub for popular LM3900. 3/\$1.00

Digital Research Corporation

(OF TEXAS)

P. O. BOX 401247 • GARLAND, TEXAS 75040 • (214) 271-2461

TERMS: Orders under \$15. add 75c. No COD's. We accept VISA, MasterCard and American Express Cards. Money Back Guarantee on all items! Texas Residents add 5% Sales Tax. WE PAY POSTAGE!

CIRCLE 96 ON FREE INFORMATION CARD

S-100 EXPANDABLE MOTHER BOARD

• 8-SLOT EXPANDABLE BACKPLANE—in line male and female connectors enable backplanes to be plugged together, or the female may be used in place of an extender board.

QUIET—ground plane decouples all signal lines.

RELIABLE—SAE 8100 phenolic body, gold contact connectors.

COMPLETE KIT **\$66.00** ASSEMBLED **\$89.00**

DEC® LSI-11 16K MEMORY BOARD

- Q-BUS—FULLY STATIC
- BUFFERED AND NOISE SUPPRESSED
- MODULAR
- PROM COMPATIBLE
- ADDRESSABLE TO 128K WORDS
- MAPPABLE IN 4K INCREMENTS

ASSEMBLED, TESTED & BURNED IN **\$124900** COMPLETE KIT **\$115900**

LARGEST & FASTEST STATIC MEMORY AVAILABLE

S-100 32K STATIC MEMORY BOARD

features:

1. FULLY STATIC - usable with all DMA devices
2. BUFFERED - with noise suppressed control inputs
3. MODULAR - populated in 1K increments
4. RELIABLE - single source +5V. regulator
5. PROM COMPATIBLE - monitors available on request

Available: COMPLETE KITS or ASSEMBLED UNITS which have been fully tested and burned in

BARE BOARD **\$39.00**

	KIT	ASSEMBLED
8K	\$278	\$320
16K	\$468	\$515
24K	\$648	\$695
32K	\$800	\$845

SHIFT REGISTERS	
C1402A 4x256 BIT	MM1403AH 2x512 BIT
\$195	\$195

U.V. PROMS

1702	2K	\$4.75	2101	\$2.45
2708	8K	\$13.95	2102	.99
2716	16K	\$31.95	2102-1	\$1.25


1K STATIC RAMS

BIPOLAR PROMS

8223	256 BIT	\$2.75
82S23	256 BIT	\$3.50
6306-1	2K TRISTATE	\$5.95
82S126	256x4	\$4.95

4K STATIC RAMS

2114	650ns	600mW	\$9.95
TMS4045-4	450ns	300mW	\$11.95
HM-472114	450ns	200mW	\$13.95

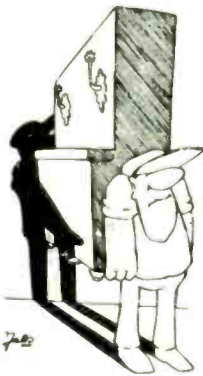

WE DELIVER

COMPUTER KEYBOARD

KEYTOPS

assorted styles & characters

100/\$6.95

CIRCUIT ASSEMBLY INTERCONNECT CABLE

single ended 16 pin header 18" Ribbon

\$1.49

OPERATIONAL AMPLIFIERS

PART	OFFSET	BIAS	DIFF IMP	3dB BW	VOLT GAIN	SLEW RATE	CMRR	\$
40J	adj. 0	25PA	50PA	100M	100kHz	94dB	6	80dB 3.95
1402	3mV	10PA	30PA	1000M	2.5MHz	80dB	3	76dB 8.95
1407	10mV	10PA	150PA	100M	30.0MHz	86dB	8	80dB 8.95
1324	10mV	30NA	300NA	3M	10MHz	100dB	35	100dB 8.95

MC1568D ±15V DUAL TRACKING VOLTAGE REGULATOR

100mA **\$1.95**

CDS PHOTO CELL

OFF 20MΩ ON 200Ω 2/99c

FOREIGN REPLACEMENTS

TA7092P \$3.95 AN214 \$4.25 uPc1025H \$4.95

AUDIO I.C.'s

LM387 PREAMP .99 LM380 2W PWR .99 MFC9020 2W PWR \$2.25

POWER OP AMP

uA 791P5S 1 AMP **\$4.95**

5W ZENERS 5%

PLASTIC-AXIAL LEADED

V	V	V
IN5338 5.1	IN5347 10	IN5356 19
IN5339 5.6	IN5348 11	IN5357 20
IN5340 6.0	IN5349 12	IN5358 22
IN5341 6.2	IN5350 13	IN5359 24
IN5342 6.8	IN5351 14	IN5360 25
IN5343 7.5	IN5352 15	IN5361 27
IN5344 8.2	IN5353 16	IN5362 28
IN5345 8.7	IN5354 17	IN5363 30
IN5346 9.1	IN5355 18	IN5364 33

99c ea. 10 MIX/ \$7.60 100 MIX/ \$59

YOUR CHOICE

CHEAP THRILLS LIMIT 10 OF EACH ITEM PER ORDER NO EXCEPTIONS, PLEASE!

7400 .09	7474 .20
7401 .09	7494 .25
7404 .10	74161 .40
74504 .12	DM8880 .50
7432 .10	uA709 .19
7442 .25	LM301 .18
74173 .20	MC1458 .39

DIODES & TRANSISTORS

MARKINGS STANDARD HOUSE & SOME UNMARKED BUT ALL MEET SPECS

IN 91	10	IN 4148	05	2N 2222	10
IN 270	09	IN 4001	05	2N 3904	10
IN 3600	10	IN 4007	10	2N 3906	10

NE-2 NEON BULB 08

SWITCHES

ROCKER 125V 6A 2/99c UL APPROVED
SLIDE 125V 3A 12/99c SPST

10 MEG POT

1/4 shaft 3/8" long

4/99c

DIACS

Specify TO-92 or axial DO-7 pkg 28V **3/99c**

D/A CONVERTER

SIGNETICS NE 500R

\$13.95

D/A CONVERTER

DAC-01/SH

\$12.95

16 CHANNEL MULTIPLEXER

ANALOG OR DIGITAL BREAK BEFORE MAKE SWITCHING SCHMITT TRIGGER INPUTS FAST SETTLING TIME HIGH TRANSFER ACCURACY OVERVOLTAGE PROTECTION EVEN WITH +Vcc = 0 LIST 40.00 NOW ONLY **\$13.95**

POWER DEVICES SCR'S

850 A 600 V PUK \$99.00
225 A 800 V STUD \$29.00

DIODES

400 A 400 V PUK \$19.95
300 A 300 V STUD \$14.95
250 A 1000 V STUD \$19.95

BRIDGES

500 A 200 V 3 PHASE \$99.00
25 A 500 V \$4.95
1.5 A 400 V \$1.25
1.5 A 100 V .75

HEWLETT PACKARD JUMBO RED HI EFFICIENCY LED

ON BOARD STATUS INDICATOR **6/99c**

HIGH INTENSITY RED LED LAMP

FROSTED WHITE CASE **3/99c 10/\$2.25**

PLASMA READOUT

0.75 4 digit **\$4.95**

ELECTROLYTIC 7500 MFD at 16VDC

99c

MAIL ORDER "GOOF PROOF" GUARANTEE

Because MAIL ORDER CUSTOMERS cannot inspect their parts before purchase, for them only, we guarantee an IMMEDIATE REFUND—NO QUESTIONS ASKED—should you be unhappy with the parts,* or should the parts fail for any reason.* Just ship parts to us in a protective carton with proof of purchase within 30 days of receipt of shipment. *MOS AND LED DEVICES EXCLUDED!

LOS ANGELES

(213) 967 4611

LMN ELECTRONICS

1042 E GARVEY AV W COVINA CA (VINCENT & SAN DIEGO FWY)

PORTLAND

(503) 646 4044

WIZARD OF PARTS

8725 SW CIRCUS DR BEAVERTON ORE (KOLL BUS CNTR WASHINGTON SQUARE)

SEATTLE

(206) 575 3709

SEMION OF SEATTLE

964 INDUSTRY DR TUNWILA WA (KOLL BUS CNTR/SOUTH CENTER)

DENVER

(303) 573 5714

ELECTRONIC LOLLIPOP

5643 N BROADWAY DENVER CO (125 & 58th AVE)

IF AT ALL POSSIBLE TRY TO DROP INTO ONE OF OUR LOCATIONS BUT IF YOU LIVE TOO FAR AWAY YOU MAY ORDER BY MAIL FROM

NO BACK ORDERS

YOUR PARTS OR IMMEDIATE REFUND

WE PAY POSTAGE & HANDLING

ON U.S. ORDERS ONLY \$20 MINIMUM CALIF. RES. ADD 6%

FOR UNDER 8 HOURS PROCESSING SEND MONEY ORDER, CERTIFIED OR CASHIERS CHECK. SORRY! WE CANNOT ACCEPT PURCHASE ORDERS, COO'S, PHONE ORDERS OR CREDIT CARDS. CANADA PUERTO RICO. U.S. POSSESSIONS ADD \$3.50. ALL OTHER FOREIGN ORDERS ADD \$7.00 IN U.S. FUNDS

F. Reichert Sales
1110 E. GARVEY AVE
W. COVINA, CA 91790

ALL ITEMS SUBJECT TO PRIOR SALE

PRICES GOOD UNTIL MAY 3, 1978

CIRCLE 74 ON FREE INFORMATION CARD

VARIABLE POWER SUPPLY KIT \$119⁹⁵

- Continuously Variable from 2V to over 15V
- Short-Circuit Proof
- Typical Regulation of 0.1%
- Electronic Current Limiting at 300mA
- Very Low Output Ripple
- Fiberglass PC Board Mounts All Components
- Assemble in about One Hour
- Makes a Great Bench or Lab Power Supply
- Includes All Components except Case and Meters

ADD \$1.25 FOR POSTAGE/HANDLING



FREE

IC or FET's WITH \$5 & \$10 ORDERS. + DATA SHEETS WITH MANY ITEMS.

SPECIALS - THIS MONTH ONLY

1N34A	Germanium Diode 60V 10mA	10/51	LW308H	Low Bias Current Op Amp. Super 709	50.84
1N270	Germanium Diode 80V 200mA	4/51	LM309K	5 Volt Regulator	10.3
1N914	Silicon Diode 100V 10mA	25/51	LM317K	Adjustable Voltage Regulator	2.37V 3.50
1N6263	Hot Carrier Diode (HP2200, etc.)	51/00	LM380N	2 Watt Audio Power Amplifier	DIP 94
FF Power Varactor 1-2W 0.4p @ 432MHz			NE555A	Phase Locked Loop	DIP 94
DIPDE GRAB BAG - Mixed transistors, rectifiers, etc.		50/51	LM223CN	Precision Voltage Regulator	DIP 3/51
2N706	NPN High Speed Switch 75mA	4/51	LM747	Dual 741 Compensated Op Amp	DIP 2/51
2N918	UPN Transistor - Osc Amp. up to 1GHz	4/51	2102	1024 Bit Static RAM (1K25 x 1)	DIP 81.75
2N2609	P-Channel FET Amplifier 2500uA, 500uA	4/51	27400E	FET Input Op Amp. IAK NE 536/LA740	1.95
2N2920	NPN Dual Transistor 3mV Match .025	2.95	CA3018A	4-Transistor Array/Darlington	99
2N2904	NPN Amp/Switch 100 uA/200mA	8/51	CA3028A	RF/IF Amplifier DC to 120MHz	1.45
2N4122	PNP RF Amplifier & Switch	3/51	CA1075E	FM IF Amp/Limiter/Detector	DIP 1.45
2N4889E	N-Channel Audio FET Super Low Noise	2/51	CA4558	Dual High Gain Op Amp	mDIP 3/51
2N4888	150 Vpn PNP Transistor for Keyer	2/51	MS555V	Precision Fast Op Amp	mDIP 3/51
E112	N-Channel FET VHF RF Amp	3/51	8038	Function Generator/VCO with Circuits	3.75
11574	N-Channel FET High Speed Switch 40p	3/51	8223	256 Bit PROM (32 x 8) 50ns	2.89
10-220	Mounting Kit/Mica insulator & bushing	10/51	LP-10	LOGIC PROBE kit-TTL, CMOS, etc.	57.85

SEND FOR ADVA'S NEW 1978 CATALOG OVER 700 SEMICONDUCTORS, KITS, CAPACITORS, ETC. - SEND 13¢ STAMP.

OTHER ADVA KITS:

LOGIC PROBE KIT - Use with CMOS, TTL, DTL, RTL, HTL, HMTL and most MOS ICs. Built-in protection against polarity reversal and overvoltage. Drawn only a few mA from circuit under test. Dual LED readout. Complete kit includes case and test leads. ONLY \$7.85

FIXED REGULATED POWER SUPPLY KIT Short-circuit proof with thermal current limiting. Compact size and typical regulation of 0.5%. Make three ideal for most electronic projects. Available for 5V @ 500mA, 12V @ 500mA, 12V @ 100mA, 12V @ 400mA, 15V @ 300mA. Specially voltage when ordering. \$8.95 ea.

These easy-to-assemble kits include all components, complete detailed instructions and tested fiberglass PC boards. Power supply kits do not include case or meters. Add \$1.25 per kit for postage and handling.

MAIL NOW! FREE DATA SHEETS supplied with many items from this ad. FREE ON REQUEST - 741 Op Amp with every order of \$5 or more - 749 Dual Op Amp or two E100 FET's with every order of \$10 or more, postmarked prior to 12/31/77. One free item per order. ORDER TODAY! All items subject to price sale and price/supply to change without notice. All items are new unless stated. 100% functionality tested.

WRITE FOR FREE CATALOG offering over 700 semiconductor devices or stock. Send 13¢ stamp.

TERMS: Send check or money order (U.S. funds) with order. Add \$10 postage for U.S. Canada and Mexico. \$10 handling charge on orders under \$10. Cash payments add 6% rate for foreign orders add 10% postage. COD orders add \$1.00 service charge.

MORE SPECIALS:

RC4195DN 15V @ 50mA VOLTAGE REGULATOR IC. Very easy to use. Makes a neat Highly Regulated 15V Supply for OP AMP's, etc. Requires only unregulated DC (18-30V) and 2 bypass capacitors. With Data Sheet and Schematics. 8-pin PDIP \$1.25

RC4135 Dual 741 Low Noise Op Amp mDIP 50.95

LM1304 FM Multiplex Stereo Demodulator DIP 0.99

LM1211 FM IF Subsystem (IF Amp, Det., Limiter) DIP 0.99

1N6263 Hot Carrier Diode 0.4V @ 1mA 0.1x 0.35 1.00

ZENERS: Specially Voltage 3.3, 3.9, 4.3, 5.1, 6.8, 8.2 400mW 4 \$1.00
9.1, 1.0, 12, 15, 16, 18, 20, 22, 24, 27, or 33V (10%) 1 Watt 3 \$1.00

- MONEY-BACK GUARANTEE
- ALL TESTED AND GUARANTEED

ADVA ELECTRONICS

BOX 4181 ER, WOODSIDE, CA 94062
Tel. (415) 851-0455

DIODES	TRANSISTORS	TRANSISTORS	TRANSISTORS	LINEAR IC's						
ZENERS & RECTIFIERS	2N706	50/24	2N4001	3/51	2N6368	2/51	LM1304	5	51.20	
	2N718	24	2N4092	50/75	2N6460	2/51	LM1340	5	1.20	
	1N456	6/51	2N720	48	2N6471	3/51	CP643	54.00	LM1340-T	1.20
	1N458	6/51	2N618	3/51	2N6472	3/51	CP650	55.00	LM1340-1	1.20
	1N483	1/51	1N613	50/75	2N6124	5/51	CP651	54.40	LM1340-15	1.20
	1N486	6/51	2N611	29	2N6260	5/51	E100	4/51	LM1340-24	1.20
	1N496	4/51	2N1910	38	2N6269	5/51	E101	3/51	LM1378M	.85
	1N756	4/51	2N1953	38	2N6250	6/51	E102	3/51	LM1377M	2.50
	1N914	15/51	2N2129	24	2N6274	5/51	1N757	3/51	LM1379M	1.20
	1N962	6/51	2N2222	6/51	2N6302	50/25	MPF102	10	NE555V	2/51
	1N974	6/51	2N2222A	5/51	2N6303	20	MPF104	3/51	NE556A	50.90
	1N984	6/51	2N2369	5/51	2N6351	5/51	MPF105	1/51	LM105CN	29
	1N3000	6/51	2N6306A	2/51	2N6352	5/51	MPF106	4/51	LM105CN	29
	1N4001	12/51	2N6308	5/51	2N6351	5/51	SE1001	4/51	LM123M	2/51
	1N4002	12/51	2N6305	50/24	2N6352	50/90	SE1002	4/51	LM123M	3/51
	1N4003	12/51	2N6306	24	2N6356	2/51	SE1003	4/51	LM123M	51.00
	1N4004	12/51	2N6307	5/51	2N4116A	50/40	SE2002	4/51	LM101CN	3/51
	1N4005	10/51	2N3553	1/50	2N6856	5/51	SE5001	3/51	LM101CN	4/51
	1N4007	10/51	2N3562	1/51	2N6861	2/51	SE5003	3/51	LM101CN	34
	1N4148	15/51	2N3563	6/51	2N6862	2/51	SE5020	53.00	LM101CN	65
	1N4154	25/51	2N3568	6/51	2N6861	2/51	TI573	10	74LS10	25
	1N4230	2/51	2N3568	6/51	2N6862	2/51	TI575	2/51	74LS10	80
	1N4372	2/51	2N3568	6/51	2N6861	2/51	DIGITAL IC's		74LS10	80
	1N4374	2/51	2N3568	6/51	2N6862	2/51	74LS13	25.95	74LS13	3/51
	1N4375	2/51	2N3568	6/51	2N6861	2/51	74LS14	25.95	74LS14	3/51
	1N4376	2/51	2N3568	6/51	2N6862	2/51	74LS15	25.95	74LS15	3/51
	1N4377	2/51	2N3568	6/51	2N6861	2/51	74LS16	25.95	74LS16	3/51
	1N4378	2/51	2N3568	6/51	2N6862	2/51	74LS17	25.95	74LS17	3/51
	1N4379	2/51	2N3568	6/51	2N6861	2/51	74LS18	25.95	74LS18	3/51
	1N4380	2/51	2N3568	6/51	2N6862	2/51	74LS19	25.95	74LS19	3/51
	1N4381	2/51	2N3568	6/51	2N6861	2/51	74LS20	25.95	74LS20	3/51
	1N4382	2/51	2N3568	6/51	2N6862	2/51	74LS21	25.95	74LS21	3/51
	1N4383	2/51	2N3568	6/51	2N6861	2/51	74LS22	25.95	74LS22	3/51
	1N4384	2/51	2N3568	6/51	2N6862	2/51	74LS23	25.95	74LS23	3/51
	1N4385	2/51	2N3568	6/51	2N6861	2/51	74LS24	25.95	74LS24	3/51
	1N4386	2/51	2N3568	6/51	2N6862	2/51	74LS25	25.95	74LS25	3/51
	1N4387	2/51	2N3568	6/51	2N6861	2/51	74LS26	25.95	74LS26	3/51
	1N4388	2/51	2N3568	6/51	2N6862	2/51	74LS27	25.95	74LS27	3/51
	1N4389	2/51	2N3568	6/51	2N6861	2/51	74LS28	25.95	74LS28	3/51
	1N4390	2/51	2N3568	6/51	2N6862	2/51	74LS29	25.95	74LS29	3/51
	1N4391	2/51	2N3568	6/51	2N6861	2/51	74LS30	25.95	74LS30	3/51
	1N4392	2/51	2N3568	6/51	2N6862	2/51	74LS31	25.95	74LS31	3/51
	1N4393	2/51	2N3568	6/51	2N6861	2/51	74LS32	25.95	74LS32	3/51
	1N4394	2/51	2N3568	6/51	2N6862	2/51	74LS33	25.95	74LS33	3/51
	1N4395	2/51	2N3568	6/51	2N6861	2/51	74LS34	25.95	74LS34	3/51
	1N4396	2/51	2N3568	6/51	2N6862	2/51	74LS35	25.95	74LS35	3/51
	1N4397	2/51	2N3568	6/51	2N6861	2/51	74LS36	25.95	74LS36	3/51
	1N4398	2/51	2N3568	6/51	2N6862	2/51	74LS37	25.95	74LS37	3/51
	1N4399	2/51	2N3568	6/51	2N6861	2/51	74LS38	25.95	74LS38	3/51
	1N4400	2/51	2N3568	6/51	2N6862	2/51	74LS39	25.95	74LS39	3/51
	1N4401	2/51	2N3568	6/51	2N6861	2/51	74LS40	25.95	74LS40	3/51
	1N4402	2/51	2N3568	6/51	2N6862	2/51	74LS41	25.95	74LS41	3/51
	1N4403	2/51	2N3568	6/51	2N6861	2/51	74LS42	25.95	74LS42	3/51
	1N4404	2/51	2N3568	6/51	2N6862	2/51	74LS43	25.95	74LS43	3/51
	1N4405	2/51	2N3568	6/51	2N6861	2/51	74LS44	25.95	74LS44	3/51
	1N4406	2/51	2N3568	6/51	2N6862	2/51	74LS45	25.95	74LS45	3/51
	1N4407	2/51	2N3568	6/51	2N6861	2/51	74LS46	25.95	74LS46	3/51
	1N4408	2/51	2N3568	6/51	2N6862	2/51	74LS47	25.95	74LS47	3/51
	1N4409	2/51	2N3568	6/51	2N6861	2/51	74LS48	25.95	74LS48	3/51
	1N4410	2/51	2N3568	6/51	2N6862	2/51	74LS49	25.95	74LS49	3/51
	1N4411	2/51	2N3568	6/51	2N6861	2/51	74LS50	25.95	74LS50	3/51
	1N4412	2/51	2N3568	6/51	2N6862	2/51	74LS51	25.95	74LS51	3/51
	1N4413	2/51	2N3568	6/51	2N6861	2/51	74LS52	25.95	74LS52	3/51
	1N4414	2/51	2N3568	6/51	2N6862	2/51	74LS53	25.95	74LS53	3/51
	1N4415	2/51	2N3568	6/51	2N6861	2/51	74LS54	25.95	74LS54	3/51
	1N4416	2/51	2N3568	6/51	2N6862	2/51	74LS55	25.95	74LS55	3/51
	1N4417	2/51	2N3568	6/51	2N6861	2/51	74LS56	25.95	74LS56	3/51
	1N4418	2/51	2N3568	6/51	2N6862	2/51	74LS57	25.95	74LS57	3/51
	1N4419	2/51	2N3568	6/51	2N6861	2/51	74LS58	25.95	74LS58	3/51
	1N4420	2/51	2N3568	6/51	2N6862	2/51	74LS59	25.95	74LS59	3/51
	1N4421	2/51	2N3568	6/51	2N6861	2/51	74LS60	25.95	74LS60	3/51
	1N4422	2/51	2N3568	6/51	2N6862	2/51	74LS61	25.95	74LS61	3/51
	1N4423	2/51	2N3568	6/51	2N6861	2/51	74LS62	25.95	74LS62	3/51
	1N4424	2/51	2N3568	6/51	2N6862	2/51	74LS63	25.95	74LS63	3/51
	1N4425	2/51	2N3568	6/51	2N6861	2/51	74LS64	25.95	74LS64	3/51
	1N4426	2/51	2N3568	6/51	2N6862	2/51	74LS65	25.95	74LS65	3/51
	1N4427	2/51	2N3568	6/51	2N6861	2/51				

DIGI-KEY CORPORATION

Quality Electronic Components

TOLL FREE 1-800-346-5144

MINNESOTA RESIDENTS 218-681-6674

DON'T FORGET OUR DISCOUNTS WHEN COMPARING PRICES

I.C.'S • RESISTORS • TRANSISTORS • CAPACITORS • DIODES • I.C. SOCKETS & PINS • SWITCHES
 CLOCK MODULES • OPTOELECTRONICS • BREADBOARDING & TESTING DEVICES • DRAFTING SUPPLIES
 DATA BOOKS • HEAT SINKS • WIRE • TOOLS... AND MORE... WRITE FOR FREE CATALOG

INTEGRATED CIRCUITS

TTL	74198	149	741561	2.00	LF352N	1.20
7400	21	74271	80	LF3741	.76	
7401	21	74574	1.28	LM301A	.44	
7402	21	74279	.55	LM302A	.64	
7403	21	74298	.94	LM309	1.00	
7404	21	74366	.67	LM309P	1.80	
7405	25	74367	.67	LM311	2.70	
7406	25	74368	.67	LM317	3.00	
7408	21	74100	.28	LM317P	3.00	
7409	21	74101	.28	LM317Z	3.00	
7411	21	74102	.28	LM317ZP	3.00	
7412	21	74103	.28	LM319	1.80	
7413	21	74104	.28	LM319P	1.80	
7414	89	74150	.29	LM320	1.30	
7415	25	74151	.28	LM320P	1.30	
7416	25	74152	.28	LM320P-24	1.30	
7417	25	74153	.28	LM323	7.50	
7418	21	74154	.28	LM323P	7.50	
7419	21	74155	.28	LM323Z	7.50	
7420	21	74156	.28	LM323ZP	7.50	
7421	25	74157	.28	LM324	2.70	
7422	25	74158	.28	LM324P	2.70	
7423	25	74159	.28	LM324Z	2.70	
7424	25	74160	.28	LM324ZP	2.70	
7425	25	74161	.28	LM325	2.70	
7426	25	74162	.28	LM325P	2.70	
7427	25	74163	.28	LM325Z	2.70	
7428	25	74164	.28	LM325ZP	2.70	
7429	25	74165	.28	LM326	2.70	
7430	21	74166	.28	LM326P	2.70	
7431	25	74167	.28	LM326Z	2.70	
7432	25	74168	.28	LM326ZP	2.70	
7433	25	74169	.28	LM327	2.70	
7434	25	74170	.28	LM327P	2.70	
7435	25	74171	.28	LM327Z	2.70	
7436	25	74172	.28	LM327ZP	2.70	
7437	25	74173	.28	LM328	2.70	
7438	25	74174	.28	LM328P	2.70	
7439	25	74175	.28	LM328Z	2.70	
7440	21	74176	.28	LM328ZP	2.70	
7441	25	74177	.28	LM329	2.70	
7442	25	74178	.28	LM329P	2.70	
7443	25	74179	.28	LM329Z	2.70	
7444	25	74180	.28	LM329ZP	2.70	
7445	25	74181	.28	LM330	2.70	
7446	25	74182	.28	LM330P	2.70	
7447	25	74183	.28	LM330Z	2.70	
7448	25	74184	.28	LM330ZP	2.70	
7449	21	74185	.28	LM331	2.70	
7450	21	74186	.28	LM331P	2.70	
7451	21	74187	.28	LM331Z	2.70	
7452	21	74188	.28	LM331ZP	2.70	
7453	21	74189	.28	LM332	2.70	
7454	21	74190	.28	LM332P	2.70	
7455	21	74191	.28	LM332Z	2.70	
7456	21	74192	.28	LM332ZP	2.70	
7457	21	74193	.28	LM333	2.70	
7458	21	74194	.28	LM333P	2.70	
7459	21	74195	.28	LM333Z	2.70	
7460	21	74196	.28	LM333ZP	2.70	
7461	21	74197	.28	LM334	2.70	
7462	21	74198	.28	LM334P	2.70	
7463	21	74199	.28	LM334Z	2.70	
7464	21	74200	.28	LM334ZP	2.70	
7465	21	74201	.28	LM335	2.70	
7466	21	74202	.28	LM335P	2.70	
7467	21	74203	.28	LM335Z	2.70	
7468	21	74204	.28	LM335ZP	2.70	
7469	21	74205	.28	LM336	2.70	
7470	21	74206	.28	LM336P	2.70	
7471	21	74207	.28	LM336Z	2.70	
7472	21	74208	.28	LM336ZP	2.70	
7473	21	74209	.28	LM337	2.70	
7474	21	74210	.28	LM337P	2.70	
7475	21	74211	.28	LM337Z	2.70	
7476	21	74212	.28	LM337ZP	2.70	
7477	21	74213	.28	LM338	2.70	
7478	21	74214	.28	LM338P	2.70	
7479	21	74215	.28	LM338Z	2.70	
7480	21	74216	.28	LM338ZP	2.70	
7481	21	74217	.28	LM339	2.70	
7482	21	74218	.28	LM339P	2.70	
7483	21	74219	.28	LM339Z	2.70	
7484	21	74220	.28	LM339ZP	2.70	
7485	21	74221	.28	LM340	2.70	
7486	21	74222	.28	LM340P	2.70	
7487	21	74223	.28	LM340Z	2.70	
7488	21	74224	.28	LM340ZP	2.70	
7489	21	74225	.28	LM341	2.70	
7490	21	74226	.28	LM341P	2.70	
7491	21	74227	.28	LM341Z	2.70	
7492	21	74228	.28	LM341ZP	2.70	
7493	21	74229	.28	LM342	2.70	
7494	21	74230	.28	LM342P	2.70	
7495	21	74231	.28	LM342Z	2.70	
7496	21	74232	.28	LM342ZP	2.70	
7497	21	74233	.28	LM343	2.70	
7498	21	74234	.28	LM343P	2.70	
7499	21	74235	.28	LM343Z	2.70	
7500	21	74236	.28	LM343ZP	2.70	

MICROPROCESSORS

8080A	8-BIT CPU 2 USE CYCLE	\$12.95
8212	8-BIT I/O PORT	\$3.95
8216	BI-DIRECTIONAL BUS DRIVER	\$4.25
8224	CLOCK GENERATOR	\$3.95
8228	SIGNAL CONDITIONER	\$3.95
8251	COMMUNICATIONS INTERFACE	\$12.95
8255	PERIPHERAL INTERFACE	\$11.95
1702A	2K EPROM (126x8)	\$6.95
2708	8K EPROM (1Kx8)	\$7.50
21021	1K RAM 512 M	\$1.79
5650	5 VOLT SC MP CPU	\$5.95
7815	MICROPROCESSOR 1.25 MM 2 CLOCK 40 DIL	\$24.95

I.C. SOCKET

8080A CHIP SET
 ONE EACH 8080A, 8212, 8224 AND 8228 PLUS SIXTEEN 2102-1's ALL FOR **\$49.95**

MOLEX I.C. SOCKET PINS

8202M 38-20/38 275.00/50M

PLESSEY SAMPLER

AN ASSORTMENT OF METALIZED POLYESTER CAPACITORS
 300 CAPS 18 VALUES \$26.00

MINIBOX METALIZED POLYESTER CAPACITORS

001	14	1.15/10	9.00/6	033	15	1.25/10	10.00/6
002	14	1.15/10	9.00/6	047	15	1.25/10	10.00/6
003	14	1.15/10	9.00/6	068	15	1.25/10	10.00/6
004	14	1.15/10	9.00/6	088	14	1.15/10	9.00/6
006	14	1.15/10	9.00/6	22	23	1.85/10	15.00/6
008	14	1.15/10	9.00/6	33	30	2.00/10	20.00/6
002	15	1.25/10	10.00/6	47	36	3.00/10	24.00/6


ELECTROLYTIC CAPACITORS

VALUE	RADIAL LEADS	AXIAL LEADS
47.50V	.08	65.10
100V	.08	65.10
2.2V	.08	65.10
3.3V	.08	65.10
4.7V	.08	65.10
6.8V	.08	65.10
10V	.08	65.10
15V	.08	65.10
22V	.08	65.10
33V	.08	65.10
47V	.08	65.10
68V	.08	65.10
100V	.08	65.10
150V	.08	65.10
220V	.08	65.10
330V	.08	65.10
470V	.08	65.10
680V	.08	65.10
1000V	.08	65.10
1500V	.08	65.10
2200V	.08	65.10
3300V	.08	65.10
4700V	.08	65.10
6800V	.08	65.10
10000V	.08	65.10
15000V	.08	65.10
22000V	.08	65.10
33000V	.08	65.10
47000V	.08	65.10
68000V	.08	65.10
100000V	.08	65.10
150000V	.08	65.10
220000V	.08	65.10
330000V	.08	65.10
470000V	.08	65.10
680000V	.08	65.10
1000000V	.08	65.10

LED DIGITS AND LAMPS


PN0535	3 1/2 Single Digit CC Red	\$1.35
PN0550	5 Single Digit CC Red	1.35
PN0555	5 Single Digit CC Red	1.35
PN0560	5 Single Digit CC Red	1.35
PN0565	5 Single Digit CC Red	1.35
PN0570	5 Single Digit CC Red	1.35
PN0575	5 Single Digit CC Red	1.35
PN0580	5 Single Digit CC Red	1.35
PN0585	5 Single Digit CC Red	1.35
PN0590	5 Single Digit CC Red	1.35
PN0595	5 Single Digit CC Red	1.35
PN0600	5 Single Digit CC Red	1.35
PN0605	5 Single Digit CC Red	1.35
PN0610	5 Single Digit CC Red	1.35
PN0615	5 Single Digit CC Red	1.35
PN0620	5 Single Digit CC Red	1.35
PN0625	5 Single Digit CC Red	1.35
PN0630	5 Single Digit CC Red	1.35
PN0635	5 Single Digit CC Red	1.35
PN0640	5 Single Digit CC Red	1.35
PN0645	5 Single Digit CC Red	1.35
PN0650	5 Single Digit CC Red	1.35
PN0655	5 Single Digit CC Red	1.35
PN0660	5 Single Digit CC Red	1.35
PN0665	5 Single Digit CC Red	1.35
PN0670	5 Single Digit CC Red	1.35
PN0675	5 Single Digit CC Red	1.35
PN0680	5 Single Digit CC Red	1.35
PN0685	5 Single Digit CC Red	1.35
PN0690	5 Single Digit CC Red	1.35
PN0695	5 Single Digit CC Red	1.35
PN0700	5 Single Digit CC Red	1.35
PN0705	5 Single Digit CC Red	1.35
PN0710	5 Single Digit CC Red	1.35
PN0715	5 Single Digit CC Red	1.35
PN0720	5 Single Digit CC Red	1.35
PN0725	5 Single Digit CC Red	1.35
PN0730	5 Single Digit CC Red	1.35
PN0735	5 Single Digit CC Red	1.35
PN0740	5 Single Digit CC Red	1.35
PN0745	5 Single Digit CC Red	1.35
PN0750	5 Single Digit CC Red	1.35
PN0755	5 Single Digit CC Red	1.35
PN0760	5 Single Digit CC Red	1.35
PN0765	5 Single Digit CC Red	1.35
PN0770	5 Single Digit CC Red	1.35
PN0775	5 Single Digit CC Red	1.35
PN0780	5 Single Digit CC Red	1.35
PN0785	5 Single Digit CC Red	1.35
PN0790	5 Single Digit CC Red	1.35
PN0795	5 Single Digit CC Red	1.35
PN0800	5 Single Digit CC Red	1.35
PN0805	5 Single Digit CC Red	1.35
PN0810	5 Single Digit CC Red	1.35
PN0815	5 Single Digit CC Red	1.35
PN0820	5 Single Digit CC Red	1.35
PN0825	5 Single Digit CC Red	1.35
PN0830	5 Single Digit CC Red	1.35

BLITZ ZONK ZATT: UNSCRAMBLE these fascinating police communications with our **CODE-BREAKER** and keep informed. Tunes all scramble frequencies, works with all scanners, and is factory built and guaranteed. **\$34.95PP. UNSCRAMBLER KIT:** Latest Technology, 2 1/2" X 2 1/2" inch, complete instructions, only \$19.95PP. Thousands of satisfied customers. Catalog 50c. Order from **KRYSTAL KITS, BOX 445, BENTONVILLE, ARK. 72712.** COD orders. 501-273-5340.



FLAT-RATE pricing for television repair. Complete manual \$3.50, information \$.50. **APPERT'S**, 1815 Sharon Avenue, Davis, CA 95616

PICTURE TUBE MACHINE
We buy and sell **NEW** and **USED CRT** rebuilding machinery. **COMPLETE TRAINING.** Buy with **CONFIDENCE** from the **ORIGINAL MFR.**
For complete details send name, address, zip to:
LAKESIDE INDUSTRIES
3520 W. Fullerton Ave.
Chicago, Ill. 60647
Phone: 312-342-3399



ELECTRONIC parts! Refundable \$1 gets you 1978 catalog. Send to: **B.C. ELECTRONICS, P. O. Box 226, West Lynn, MA 01905**

Govt. SURPLUS ELECTRONIC EQUIPMENT CATALOG

New ITEMS... New BARGAINS!
FREE UPON REQUEST!
If you haven't received our new Catalog, write for free copy today. Address: Dept. FE

FAIR RADIO SALES
1016 E. EUREKA • Box 1105 • LIMA, OHIO • 45802

FREE KIT Catalog
STOP! Take a minute & let us send your latest kit catalog. If you like, send us the name & address of a friend who may also be interested and we'll include to you our booklet "How to build electronic thermometer"
contains **TEST & EXPERIMENTER'S EQUIP.**
DAGE SCIENTIFIC INSTRUMENTS
BOX 1054R LIVERMORE CA 94550

MANUALS for Govt. surplus radios, test sets, scopes, List 50c (coin) **BOOKS**, 7218 Roanne Drive, Washington, D.C. 20021

MAKE PC boards. Step-by-step "how-to" manual with build-it-yourself equipment plans, charts and illustrations. For polyze and film-chemical processes. \$4.98 plus 50c p&h. **CENTURY AMERICAN INSTRUMENTS**, Dept. 416, Box 1014, Placentia, CA 92670

System Power Supplies
PS1: ±15 @ .5A, 5V @ 2.5A, and 0-35V with 24V @ .5A.
PS2: ±15V @ .3A, 5V @ 3.3A, and 0-15V with 12V @ 1A
Both have four excellently regulated voltages; (resistor programmable). From three winding; compare. Great for home computer, bench or hobby work. Just add AC cord and plug 'em in. Assembled: PS1 or PS2 \$27.95.
Kit (less transformer); PSK1 or PSK2 \$19.95.
\$2.00 postage & handling; in Calif. add 6% sales tax.
PLUS* Electronics, 1260 El Camino No.306
Millbrae Ca. 94030

NEW periodic table of chemical elements. Striking wall chart \$3.00. **CIRCLON**, Greenriver George, Enumclaw, WA 98022

PRINTED circuit chemicals, supplies, tools, equipment. Laminates, magazine copying, reversal film, plating, drill, punch, etc. Always detailed instructions. Send two stamps. **CIRCOLEX**, Box 198, Marcy, NY 13403

PINK NOISE GENERATOR
Uses latest digital MOS IC. See Radio-Electronics January, 1978 or write:
West Side Electronics P.O. Box 636, Chatsworth, CA 91311

FREQUENCY allocation chart 2 kHz-200 GHz. Send \$2.00. **COLLINS CHART CO.**, Box 1067, Coronado, CA 92118

CB xtals. Ch. 3 thru 23, A and D. Two for \$1.00. Limited qty. **R. DICKSON**, Box 1131, Melbourne, FL 32901

TAPE SYSTEMS model 1010 Volt. cont. d. active LOW PASS filter kit, 10 Hz-30kHz, 10V-P-P, 1 volt per octave, 15V 1 30kHz. Variable 'R' for only \$47. each
S. stat. Audio Delay Filter ST-4 DELAY IC 10 pin. made same as RETICON'S SAD 1024A. w/data etc. \$17. each
Voltage Controlled Oscillator Module; **TAPE SYSTEMS** model 1230. 1v/oct, 10 Hz-10kHz, 10 v-P-P output. sawtooth & pulse outs. ready to use w/data \$24.50
HYBRID STATE VARIABLE FILTER. Features: 1P, 1P, LP, 51 vlt. outs + extra opt. Same as Nat'l's AF-100. DC-10kHz, 2 resistors set Fc. with Data: \$7.30 each

CFR ASSOCIATES Box F
Newton NH 03858
TO ORDER: add \$1.75 for Shpg. & Hdlg. That's all it takes.
UPDT FOR OUR LIST OF PRODUCTS

FREE wire-wrap samples—30# cut and stripped Kynar included with list of our incredibly low prices. **SASE** to: **KAYRO**, Box 4335, Walnut Creek, CA 94596

SCOOP! 4 MEGABYTE TAPE RECORDER!
QUAD 5 CHANNEL TAPE TRANS PORT, ONE FURNISHED. LOGIC FOR AUTO SELECT, REWIND, TAPE BREAK, EOT, LOW LEVEL & LAST CARTRIDGE. POWER RECD 12 VOLTS 5 AMPS DC
STD. HIGH PANEL 2 1/2" HIGH 19" WIDE 20" DEEP. WT. 85 LBS. SHIPPED COD-USED-GOOD COND. LIMITED QTY.
J&E ELECTRONICS INC.
P.O. BOX 4504, FORT WORTH, TEXAS, 76106. OR PHONE 817-625-2961. BANK AMERICAN, MC OR VISA ACCEPTED. TEXAS RES. ADD 9% SALES TAX-NO CHECKS.

CASES: 6 1/2" X 2 1/2" X 5 1/2" D; Black, white, or smoked Plexiglas; Clear-red bezel; \$6.25 + 0.75 shipping. **D. K. RAUER CO.**, Box 638, Vienna, VA 22180

B&K test equipment. Free catalog. Free shipping. Dinosaur discounts. **SPACETRON-DD**, 948 Prospect, Elmhurst, IL 60126



Original Japanese Transistors, FET, IC, Diodes
CHECK OUR LOW PRICES!

TRANSISTORS	2SA 816	70	2SC 403	59	2SC 871	59	2SC 1448	1.10	2SD 358	1.30	
2SA 49	59	2SA 818	1.40	2SC 430	1.10	2SC 897	2.65	2SC 1449	1.00	2SD 360	1.20
2SA 70	1.10	2SA 839	2.15	2SC 454	.59	2SC 898	4.40	2SC 1451	1.60	2SD 382	1.40
2SA 101	59	2SA 841	.59	2SC 458	.59	2SC 900	.59	2SC 1475	1.40	2SD 388	3.40
2SA 102	59	2SA 847	.59	2SC 460	.59	2SC 929	.59	2SC 14785	70	2SD 424	8.50
2SA 234	59	2SA 850	70	2SC 461	.59	2SC 930	.59	2SC 1509	1.10	2SD 427	2.80
2SA 242	90	2SA 872A	59	2SC 481	1.60	2SC 943	1.20	2SC 1584	8.50	2SD 525	1.60
2SA 353	70	2SA 908	11.00	2SC 482	1.50	2SC 945	.59	2SC 1586	6.50	2SD 526	1.10
2SA 377	2.00	2SB 54	.59	2SC 485	1.60	2SC 959	1.50	2SC 1624	1.30	2SD 555A	6.60
2SA 440	90	2SB 55	1.10	2SC 486	1.60	2SC 971	1.00	2SC 1626	1.10	2SD 610	1.90
2SA 483	3.00	2SB 75	.59	2SC 493	3.90	2SC 983	1.00	2SC 1628	1.30		
2SA 484	2.50	2SB 77	.59	2SC 495	1.00	2SC 984	.90	2SC 1647	.59		
2SA 485	2.00	2SB 186	.59	2SC 497	1.60	2SC 1000BL	.59	2SC 1669	1.60	FET	
2SA 489	1.60	2SB 187	.59	2SC 509	.90	2SC 1014	1.20	2SC 1674	.59	2SK 19	1.60
2SA 495	.70	2SB 202	1.60	2SC 517	3.95	2SC 1017	1.40	2SC 1675	.59	2SK 30	1.10
2SA 496	1.10	2SB 220	.70	2SC 535	.70	2SC 1018	1.20	2SC 1678	2.25	2SK 34	1.10
2SA 497	1.60	2SB 203	.59	2SC 536	.59	2SC 1030C	2.80	2SC 1682	.45	2SK 40	.70
2SA 509	70	2SB 324	.70	2SC 537	.59	2SC 1047	.70	2SC 1684	.59	2SK 49	1.30
2SA 525	2.50	2SB 337	1.60	2SC 538A	70	2SC 1060	2.25	2SC 1708	.59	2SK 55	1.30
2SA 537	2.25	2SB 367	1.50	2SC 562	2.15	2SC 1078	1.40	2SC 1728	2.00	2SK 68	1.30
2SA 539	.70	2SB 368B	2.15	2SC 563	1.10	2SC 1080	4.40	2SC 1760	2.00	3SK 22	2.55
2SA 561	.59	2SB 379	1.10	2SC 619	.59	2SC 1096	1.00	2SC 1775	.45	3SK 35	2.25
2SA 562	.59	2SB 400	.59	2SC 620	.59	2SC 1111	3.40	2SC 1816	4.25	3SK 39	2.25
2SA 564A	.59	2SB 405	.70	2SC 632A	.70	2SC 1115	3.40	2SC 1885	.70	3SK 40	2.25
2SA 565	1.10	2SB 407	1.40	2SC 644	.59	2SC 1116	4.40	2SC 1908	.59	3SK 41	2.50
2SA 566	3.40	2SB 415	.70	2SC 645	.70	2SC 1116A	4.90	2SC 1909	4.40	3SK 45	2.50
2SA 606	1.90	2SB 434	1.20	2SC 650	1.30	2SC 1124	1.30	2SC 1951	1.10	MK 10	2.00
2SA 624	1.10	2SB 440	.70	2SC 668	.59	2SC 1162	1.10	2SC 1957	1.20		
2SA 627	3.60	2SB 463	1.50	2SC 680	2.80	2SC 1166	.59	2SC 1969	4.90	IC	
2SA 628	.59	2SB 471	1.60	2SC 684	1.40	2SC 1173	.90	2SC 1973	1.10	AN 2140	3.40
2SA 634	.90	2SB 472	2.90	2SC 693B	.59	2SC 1175	.90	2SC 1975	4.40	AN 315	3.70
2SA 640	.59	2SB 474	1.20	2SC 696	1.95	2SC 1177	14.00	2SC 2028	.90	BA 511	3.40
2SA 643	.70	2SB 492	1.00	2SC 708A	1.90	2SC 1189	1.40	2SC 2029	3.90	BA 521	3.70
2SA 659	.59	2SB 507	1.60	2SC 710	.59	2SC 1211D	.70	2SC 2091	3.60	HA 151	3.70
2SA 663	4.90	2SB 509	1.90	2SC 711	.59	2SC 1213	.70	2SC 2092	3.90	TA 7045M	3.00
2SA 666	.70	2SB 514	1.90	2SC 712	.59	2SC 1222	.45	2SC 2098	3.90	SN 7400	.19
2SA 672	.70	2SB 526C	1.30	2SC 717	.59	2SC 1226	1.00	2SD 28	2.80	SN 7490	.60
2SA 678	.70	2SB 527	1.70	2SC 730	4.40	2SC 1237	4.25	2SD 75	1.10	TA 7055P	3.00
2SA 682	.70	2SB 528D	1.60	2SC 732	.59	2SC 1239	3.50	2SD 90	1.60	TA 7056P	1.60
2SA 683	.70	2SB 536	1.60	2SC 733	.59	2SC 1279	.70	2SD 91	1.60	TA 7061P	1.90
2SA 684	.70	2SB 539	4.90	2SC 734	.59	2SC 1306	4.40	2SD 92	1.50	TA 7062	1.90
2SA 695	.70	2SB 541	4.40	2SC 735	.59	2SC 1307	4.90	2SD 118	3.00	TA 7205P	3.90
2SA 697	.70	2SB 554	10.00	2SC 738	.59	2SC 1312	.59	2SD 130	1.20	TA 7310P	3.95
2SA 706	1.60	2SB 561B	.90	2SC 756	2.80	2SC 1313G	1.40	2SD 142	2.00	UPC 592H2	1.60
2SA 715	1.40	2SB 564	.90	2SC 763	.59	2SC 1317	.59	2SD 143	2.80	PLL 02A	8.80
2SA 719	.70	2SB 595	1.90	2SC 773	.70	2SC 1318	.59	2SD 178	1.40		
2SA 720	.70	2SB 600A	7.00	2SC 774	1.60	2SC 1327	.59	2SD 180	2.50	DIODES	
2SA 721	.70	2SC 183	.59	2SC 776	2.65	2SC 1330	1.50	2SD 187	.59	IS 84	1.00
2SA 725	.59	2SC 184	.59	2SC 778	3.60	2SC 1342	.59	2SD 188	3.00	IS 168	.45
2SA 726	.59	2SC 211	.59	2SC 781	2.65	2SC 1344	.59	2SD 207	1.40	IS 332	.45
2SA 733	.59	2SC 284	1.40	2SC 783A	3.60	2SC 1345D	.59	2SD 217	1.40	IS 953	.45
2SA 740	2.85	2SC 367	.90	2SC 784	.59	2SC 1359	1.40	2SD 223	1.90	IS 1007	.45
2SA 744	3.70	2SC 369	.70	2SC 785	.70	2SC 1360	1.00	2SD 224	1.90	IS 1209	.45
2SA 745R	4.40	2SC 371	.59	2SC 789	1.00	2SC 1362	.59	2SD 227	.59	IS 1211	.45
2SA 747	5.80	2SC 372	.59	2SC 793	2.80	2SC 1364	1.40	2SD 234	1.00	IS 1555	.32
2SA 750	.59	2SC 373	.59	2SC 799	3.60	2SC 1377	4.90	2SD 235	1.00	IS 1585	.32
2SA 756	3.40	2SC 374	.59	2SC 815	.59	2SC 1383	.59	2SD 287	3.70	IS 1885	.45
2SA 758	5.80	2SC 380	.59	2SC 828	.59	2SC 1400	.59	2SD 313	1.10	IS 2076	.45
2SA 774	.59	2SC 381	.59	2SC 829	.59	2SC 1402	3.70	2SD 315	1.20	IS 2093	.45
2SA 777	1.10	2SC 382	.59	2SC 838	.59	2SC 1403	3.70	2SD 325	1.10	IS 2473	-.45
2SA 798	.70	2SC 387	.59	2SC 839	.59	2SC 1419	1.10	2SD 356D	1.10	IN 34	.25
2SA 814	1.90	2SC 394	.59	2SC 870	.59	2SC 1444	2.80	2SD 357D	1.00	IN 60	.25

PRICES MAY CHANGE WITHOUT NOTICE COD ORDERS WELCOMED

IMMEDIATE DELIVERY WITHIN 48 HOURS
ON ALL TRANSISTORS IN STOCK
Minimum order \$5.00 Ohio residents add 4% sales tax.
Add \$1.00 postage and handling. Quantity discount prices.
ASK FOR OUR COMPLETE PRICE LIST
MANUFACTURER INQUIRIES WELCOMED
All Parts Guaranteed Against Factory Defects

FUJI-SVEA ENTERPRISE
Dept. Radio Electronics
P.O. Box 40325
Cincinnati, OH 45240
(513)874-0220
874-0223

RADIO-ELECTRONICS

TTL LOW POWER SCHOTTKY PLASTIC DUAL-IN-LINE I.C.					
SN74LS00N	.17	SN74LS91N	.99	SN74LS191N	1.25
SN74LS01N	.17	SN74LS92N	.69	SN74LS192N	.95
SN74LS02N	.17	SN74LS93BN	.60	SN74LS193N	.95
SN74LS03N	.17	SN74LS95AN	.99	SN74LS194AN	.99
SN74LS04N	.17	SN74LS96N	1.45	SN74LS195AN	.75
SN74LS05N	.19	SN74LS107N	.39	SN74LS196N	1.25
SN74LS08N	.19	SN74LS109N	.39	SN74LS197N	1.25
SN74LS09N	.20	SN74LS112N	.39	SN74LS201N	18.00
SN74LS10N	.17	SN74LS113N	.44	SN74LS208N	18.00
SN74LS11N	.19	SN74LS114N	.44	SN74LS214N	13.95
SN74LS12N	.23	SN74LS122N	.79	SN74LS215N	15.95
SN74LS13N	.55	SN74LS107N	.89	SN74LS221N	1.25
SN74LS14N	.99	SN74LS124N	1.50	SN74LS240N	1.95
SN74LS15N	.21	SN74LS125N	.65	SN74LS241N	1.95
SN74LS20N	.19	SN74LS126N	.65	SN74LS242N	1.95
SN74LS21N	.21	SN74LS132N	.99	SN74LS243N	1.95
SN74LS22N	.21	SN74LS133N	.29	SN74LS244N	1.95
SN74LS23N	.29	SN74LS136N	.45	SN74LS247N	1.25
SN74LS27N	.25	SN74LS138N	.79	SN74LS248N	1.95
SN74LS28N	.27	SN74LS139N	.79	SN74LS249N	1.30
SN74LS30N	.21	SN74LS145N	.99	SN74LS251N	1.25
SN74LS32N	.25	SN74LS148N	2.65	SN74LS253N	1.25
SN74LS33N	.29	SN74LS151N	.65	SN74LS257N	1.40
SN74LS37N	.29	SN74LS153N	.65	SN74LS258N	.95
SN74LS38N	.29	SN74LS155N	1.25	SN74LS259N	1.45
SN74LS40N	.23	SN74LS156N	1.25	SN74LS260N	.29
SN74LS42N	.69	SN74LS157N	.65	SN74LS261N	2.50
SN74LS47N	.99	SN74LS158N	.99	SN74LS266N	.39
SN74LS48N	.99	SN74LS160N	.95	SN74LS273N	1.65
SN74LS49N	.99	SN74LS161N	.95	SN74LS279N	.69
SN74LS51N	.21	SN74LS162N	.95	SN74LS280N	1.75
SN74LS54N	.21	SN74LS163N	.95	SN74LS281N	5.50
SN74LS55N	.21	SN74LS164N	1.50	SN74LS283N	1.30
SN74LS63N	1.50	SN74LS165N	1.45	SN74LS290N	1.20
SN74LS73N	.39	SN74LS166N	1.45	SN74LS293N	1.20
SN74LS74N	.35	SN74LS168N	1.95	SN74LS295AN	1.70
SN74LS75N	.49	SN74LS169N	1.95	SN74LS298N	1.70
SN74LS78N	.39	SN74LS170N	1.50	SN74LS299N	4.70
SN74LS78N	.39	SN74LS173N	1.50	SN74LS314N	13.95
SN74LS83AN	1.25	SN74LS174N	.75	SN74LS315N	15.95
SN74LS85N	1.19	SN74LS175N	.75	SN74LS324N	1.50
SN74LS86N	.35	SN74LS181N	2.75	SN74LS325N	2.55
SN74LS90N	.65	SN74LS190N	1.25	SN74LS326N	2.55

CMOS		CMOS	
CD4010BE	.35	CD4060BE	.99
CD4011BE	.15	CD4066BE	.55
CD4012BE	.15	CD4068BE	.21
CD4013BE	.28	CE4069BE	.21
CD4014BE	.69	CD4070BE	.21
CD4015BE	.69	CD4071BE	.21
CD4016BE	.28	CD4072BE	.25
CD4017BE	.68	CD4073BE	.25
CD4018BE	.74	CD4075BE	.25
CD4019BE	.35	CD4076BE	.89
CD4020BE	.78	CD4078BE	.21
CD4021BE	.79	CD4081BE	.21
CD4022BE	.79	CD4082BE	.25
CD4023BE	.15	CD4085BE	.69
CD4024BE	.59	CD4086BE	.69
CD4025BE	.15	CE4502BE	.95
CD4026BE	1.29	CD4507BE	.38
CD4027BE	.37	CD4510BE	.95
CD4028BE	.64	CD4511BE	1.00
CD4029BE	.69	CD4512BE	.65
CD4030BE	.35	CD4514BE	1.95
CD4033BE	1.50	CD4515BE	1.95
CD4034BE	2.85	CD4516BE	.79
CD4035BE	.85	CD4518BE	.79
CD4040BE	.79	CD4519BE	.65
CD4041BE	.65	CD4520BE	.75
CD4042BE	.57	CD4522BE	.99
CD4043BE	.44	CD4526BE	.99
CD4044BE	.44	CD4527BE	1.50
CD4046BE	1.50	CD4528BE	.95
CD4047BE	2.50	CD4531BE	.95
CD4049BE	.33	CD4539BE	1.15
CD4050BE	.33	CD4555BE	.69
CD4051BE	.74	CD4556BE	.69
CD4052BE	.85	CD4581BE	1.98
CD4053BE	.74	CD4582BE	.89
CD4055BE	1.29	CD4585BE	1.25

TEXAS INSTRUMENTS I.C. SOCKETS (Low Profile Solder Tail)			
Description	Unit Price	Description	Unit Price
8 Pin DIL (C840802)	.15	22 Pin DIL (C842202)	.34
14 Pin DIL (C841402)	.18	24 Pin DIL (C842402)	.34
16 Pin DIL (C841602)	.19	28 Pin DIL (C842802)	.45
18 Pin DIL (C841802)	.29	40 Pin DIL (C844002)	.65
20 Pin DIL (C842002)	.35		

VOLTAGE REGULATORS			
78H05KC	6.35	5 Amp 5 Volt Positive Regulator T03	
7800 Series	.79	Positive Voltage Regulators (Plastic)	
		1 Amp	
T0-220 / LM340T		5, 6, 8, 12, 15, 18, 24 Volts	
78M00 Series	1.39	Positive Voltage Regulator 1/2 Amp	
T0-5 / LM340H		5, 6, 8, 12, 15, 18, 24 Volts	
7800 Series	1.49	Positive Voltage Regulator 1 Amp	
T0-3 / LM340K		5, 6, 8, 12, 15, 18, 24 Volts	
78L00 AWC Series	.29	Positive Voltage Regulator 100 MA	
T0-92		2.6, 5, 6.2, 8.2, 12, 15 Volts	
7900 Series	.99	Negative Voltage Regulator 1 Amp	
T0-220 / LM320T		5, 6, 8, 12, 15, 18, 24 Volts	
79M00 Series	1.35	Negative Voltage Regulator 1/2 Amp	
T0-5 / LM329H		5, 6, 8, 12, 15, 20, 24 Volts	
7900 Series	1.75	Negative Voltage Regulator 1 Amp	
T0-3 / LM320K		5, 6, 8, 12, 15, 18, 24 Volts	
78MGT2C	1.20	Dual In Line Adjustable 4 Terminal	
		Positive Voltage Regulator	
79MGT2C	1.20	Dual In Line Adjustable 4 Terminal	
		Negative Voltage Regulator	
78GU1 T0-220	1.45	1 Amp Adjustable Positive Voltage	
		Regulator	
79GU1 T0-220	1.25	1 Amp Adjustable Negative Voltage	
		Regulator	
78GKC T0-3	1.80	1 Amp Adjustable Positive Voltage	
		Regulator	
79GKC T0-3	2.10	1 Amp Adjustable Negative Voltage	
		Regulator	



Our new comprehensive 1978 Catalogue, listing complete descriptions, illustrations and special monolithic pricing on over 10,000 items, is now available on request.

Active Electronic Sales Corp.

P.O. BOX 1035 FRAMINGHAM, MASSACHUSETTS 01701
Telephone Orders & Enquiries (617) 879-0077

In Canada, 2 Locations. 5651 Ferrier St. 44 Fasken Dr-Unit 25
Foreign Customers: Please Remit Payment in U.S. Bank Draft or American Postal Money Order. Montreal, Quebec Rexdale, Ontario
Tel. (514) 735-6425 Tel. (416) 675-3311

MINIMUM ORDER \$10.00 * ADD \$2.00 TO COVER POSTAGE & HANDLING * Canadian customers add 30% for duty and handling. All federal and provincial taxes extra.

CIRCLE 81 ON FREE INFORMATION CARD

A
c
t
i
v
e


E
l
e
c
t
r
o
n
i
c

S
a
l
e
s

C
o
r
p

\$2 50 1978

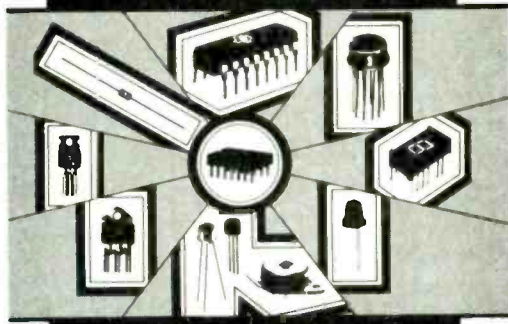THE WORLD'S LARGEST
INTERNATIONAL SEMICONDUCTOR
DISTRIBUTOR



Active Electronic Sales Corp.

P.O. BOX 1035
FRAMINGHAM, MASSACHUSETTS 01701
TELEPHONE ORDERS (617) 879-0077

Over The Counter Sales
12 Mercer Rd.
NATICK, MASS. 01760
(Behind Zayres on Route 9)

Our New and Expanded Comprehensive 1978 Catalogue (144 pages) is finally available.

Please write for your complimentary copy.

Active Electronic Sales Corp.

P.O. BOX 1035 FRAMINGHAM, MASSACHUSETTS 01701
OVER-THE-COUNTER SALES, 12 Mercer Rd., Natick, Mass. 01760 Behind Zayres on Rte. 9
Telephone Orders & Enquiries (617) 879-0077

IN CANADA 2 Locations	5651 Ferrier St. Montreal, Quebec Tel. (514) 735-6425	44 Fasken Dr-Unit 25 Rexdale, Ontario Tel. (416) 675-3311
--------------------------	---	---

MINIMUM ORDER \$10.00 * ADD \$2.00 TO COVER POSTAGE & HANDLING * Canadian customers add 15% for exchange and handling. All federal and provincial taxes extra. Foreign customers please remit payment on an international bank draft or international postal money order in American dollars.

CIRCLE 78 ON FREE INFORMATION CARD

APRIL 1978

EQUIPMENT REPORTS
continued from page 122

watt to 10 watts. You can even read the audio frequency response of the receiver. An AF signal generator can be connected to the external modulation jack on the front panel. Set up a reference level at 1000 Hz, then vary the frequency above and below this level.

You can use the variable RF signal output to check squelch threshold, control action, the signal needed to break squelch, etc. The same setup also checks out the automatic gain control on any CB receiver. Just inject the AM signal at 30% modulation into the input, then set the model 266 for a high RF signal, at 50,000 μ V. Connect an output meter across

the external speaker jack, and note the reading. Now reduce the RF output signal slowly to about 1.0 μ V. The audio output signal should drop slowly and smoothly without dips or peaks. The audio output at the lowest signal level should be no more than 30 dBm below the reference level set up with the high RF signal. This procedure will also check and calibrate the S-meter on the CB, if one is used; this should read maximum at the high signal output and then drop to zero at the lowest RF signal.

The model 266 CB signal generator is a versatile piece of test equipment that is surprisingly easy to set up and use. The RF test attenuator is a 6-position switch; the RF modulation and IF levels are variable controls, and everything else is done with pushbuttons.

The instruction manual contains full setup data (including all the control positions for both generator and CB) for every kind of test imaginable. The manual is actually like a good CB troubleshooting handbook. Full checking and recalibration instructions are given. There's even a complete list of CB channel frequencies, which is nice because I'm sure not going to ever remember 'em! **R-E**

Philips/MCA, Inc. announce two-hour videodisc format

A new two-hour playing format for optical videodiscs was announced recently by Philips and MCA, Inc., that will enable the viewer to enjoy full-length feature films and programs of up to hours in length on a single double-sided disc.

The optical videodisc player will not only accommodate the two hour format using variable angle velocity, but also play programs recorded at the present 1800 RPM format. Magnavox will market the player and the videodisc will be handled by MCA Disco-Vision.

Ion implantation improves FET's, optical couplers and solar cells

Several ion-implantation methods are presently being developed that are expected to improve the performance of microwave FET's, create new optoelectronic devices for use in telephone couplers and fiber-optic communications, and increase the efficiency of solar cells.

Hewlett-Packard has built an ion-implanted FET that, as a result of its planar construction, promises greater reliability than conventional crystalline devices. The company sees the potential application of these FET's in GaAs IC's. With a 5-dB gain, HP researchers have been able to obtain an output power of more than 1 watt at 6 GHz and a power-added efficiency of 34%. Avantek, Inc., has also been working with low-noise microwave FET's; silicon implanted into a GaAs semi-insulating substrate results in a shallow but steep profile.

On the optoelectronic front, Bell Labs has developed two semiconductors—one, a bilateral phototransistor to be used as an optical coupler in telephone switching, and an optically switched LED to interface between digital logic circuits and glass fibers. Bell researchers believe this LED has application in a tap and-repeater circuit.

With the possibility of having an effect on the national energy crisis, the efficiency of solar cells has been improved by a special chemical process developed by the Jet Propulsion Lab of the California Institute of Technology at Pasadena. The oxide surface layer of the gallium-arsenide MOS cell is formed by physical deposition, and pulsed-laser evaporation is used to improve the antireflecting coating of the solar cell surface. This has pushed the efficiency of the GaAs MOS solar cell to 17%.

Texas Instruments has also created a tandem-junction thin-film solar cell with collecting junctions on both the dark and illuminated sides of the cell. So far, experimental solar cells have yielded an open-circuit voltage of 600 mV, a short-circuit current of 50 mA per-square-centimeter and an 18% efficiency at 25°C.

P.O. Box 4430E Santa Clara, CA 95054
For will call only: (408) 988-1640
2996 Scott Blvd.



Same day shipment. First line parts only. Factory tested. Guaranteed money back. Quality IC's and other components at factory prices.

INTEGRATED CIRCUITS

74007TL	74LS208A	41	74LS017	12	10	CMOS	74LS017	12	10	CMOS
7400A	74LS10	10	74LS015	10	10	CMOS	74LS015	10	10	CMOS
7400B	74LS10A	10	74LS016	10	10	CMOS	74LS016	10	10	CMOS
7400C	74LS10B	10	74LS017	10	10	CMOS	74LS017	10	10	CMOS
7400D	74LS10C	10	74LS018	10	10	CMOS	74LS018	10	10	CMOS
7400E	74LS10D	10	74LS019	10	10	CMOS	74LS019	10	10	CMOS
7400F	74LS10E	10	74LS020	10	10	CMOS	74LS020	10	10	CMOS
7400G	74LS10F	10	74LS021	10	10	CMOS	74LS021	10	10	CMOS
7400H	74LS10G	10	74LS022	10	10	CMOS	74LS022	10	10	CMOS
7400I	74LS10H	10	74LS023	10	10	CMOS	74LS023	10	10	CMOS
7400J	74LS10I	10	74LS024	10	10	CMOS	74LS024	10	10	CMOS
7400K	74LS10J	10	74LS025	10	10	CMOS	74LS025	10	10	CMOS
7400L	74LS10K	10	74LS026	10	10	CMOS	74LS026	10	10	CMOS
7400M	74LS10L	10	74LS027	10	10	CMOS	74LS027	10	10	CMOS
7400N	74LS10M	10	74LS028	10	10	CMOS	74LS028	10	10	CMOS
7400O	74LS10N	10	74LS029	10	10	CMOS	74LS029	10	10	CMOS
7400P	74LS10O	10	74LS030	10	10	CMOS	74LS030	10	10	CMOS
7400Q	74LS10P	10	74LS031	10	10	CMOS	74LS031	10	10	CMOS
7400R	74LS10Q	10	74LS032	10	10	CMOS	74LS032	10	10	CMOS
7400S	74LS10R	10	74LS033	10	10	CMOS	74LS033	10	10	CMOS
7400T	74LS10S	10	74LS034	10	10	CMOS	74LS034	10	10	CMOS
7400U	74LS10T	10	74LS035	10	10	CMOS	74LS035	10	10	CMOS
7400V	74LS10V	10	74LS036	10	10	CMOS	74LS036	10	10	CMOS
7400W	74LS10W	10	74LS037	10	10	CMOS	74LS037	10	10	CMOS
7400X	74LS10X	10	74LS038	10	10	CMOS	74LS038	10	10	CMOS
7400Y	74LS10Y	10	74LS039	10	10	CMOS	74LS039	10	10	CMOS
7400Z	74LS10Z	10	74LS040	10	10	CMOS	74LS040	10	10	CMOS
7400AA	74LS10AA	10	74LS041	10	10	CMOS	74LS041	10	10	CMOS
7400AB	74LS10AB	10	74LS042	10	10	CMOS	74LS042	10	10	CMOS
7400AC	74LS10AC	10	74LS043	10	10	CMOS	74LS043	10	10	CMOS
7400AD	74LS10AD	10	74LS044	10	10	CMOS	74LS044	10	10	CMOS
7400AE	74LS10AE	10	74LS045	10	10	CMOS	74LS045	10	10	CMOS
7400AF	74LS10AF	10	74LS046	10	10	CMOS	74LS046	10	10	CMOS
7400AG	74LS10AG	10	74LS047	10	10	CMOS	74LS047	10	10	CMOS
7400AH	74LS10AH	10	74LS048	10	10	CMOS	74LS048	10	10	CMOS
7400AI	74LS10AI	10	74LS049	10	10	CMOS	74LS049	10	10	CMOS
7400AJ	74LS10AJ	10	74LS050	10	10	CMOS	74LS050	10	10	CMOS
7400AK	74LS10AK	10	74LS051	10	10	CMOS	74LS051	10	10	CMOS
7400AL	74LS10AL	10	74LS052	10	10	CMOS	74LS052	10	10	CMOS
7400AM	74LS10AM	10	74LS053	10	10	CMOS	74LS053	10	10	CMOS
7400AN	74LS10AN	10	74LS054	10	10	CMOS	74LS054	10	10	CMOS
7400AO	74LS10AO	10	74LS055	10	10	CMOS	74LS055	10	10	CMOS
7400AP	74LS10AP	10	74LS056	10	10	CMOS	74LS056	10	10	CMOS
7400AQ	74LS10AQ	10	74LS057	10	10	CMOS	74LS057	10	10	CMOS
7400AR	74LS10AR	10	74LS058	10	10	CMOS	74LS058	10	10	CMOS
7400AS	74LS10AS	10	74LS059	10	10	CMOS	74LS059	10	10	CMOS
7400AT	74LS10AT	10	74LS060	10	10	CMOS	74LS060	10	10	CMOS
7400AU	74LS10AU	10	74LS061	10	10	CMOS	74LS061	10	10	CMOS
7400AV	74LS10AV	10	74LS062	10	10	CMOS	74LS062	10	10	CMOS
7400AW	74LS10AW	10	74LS063	10	10	CMOS	74LS063	10	10	CMOS
7400AX	74LS10AX	10	74LS064	10	10	CMOS	74LS064	10	10	CMOS
7400AY	74LS10AY	10	74LS065	10	10	CMOS	74LS065	10	10	CMOS
7400AZ	74LS10AZ	10	74LS066	10	10	CMOS	74LS066	10	10	CMOS
7400BA	74LS10BA	10	74LS067	10	10	CMOS	74LS067	10	10	CMOS
7400BB	74LS10BB	10	74LS068	10	10	CMOS	74LS068	10	10	CMOS
7400BC	74LS10BC	10	74LS069	10	10	CMOS	74LS069	10	10	CMOS
7400BD	74LS10BD	10	74LS070	10	10	CMOS	74LS070	10	10	CMOS
7400BE	74LS10BE	10	74LS071	10	10	CMOS	74LS071	10	10	CMOS
7400BF	74LS10BF	10	74LS072	10	10	CMOS	74LS072	10	10	CMOS
7400BG	74LS10BG	10	74LS073	10	10	CMOS	74LS073	10	10	CMOS
7400BH	74LS10BH	10	74LS074	10	10	CMOS	74LS074	10	10	CMOS
7400BI	74LS10BI	10	74LS075	10	10	CMOS	74LS075	10	10	CMOS
7400BJ	74LS10BJ	10	74LS076	10	10	CMOS	74LS076	10	10	CMOS
7400BK	74LS10BK	10	74LS077	10	10	CMOS	74LS077	10	10	CMOS
7400BL	74LS10BL	10	74LS078	10	10	CMOS	74LS078	10	10	CMOS
7400BM	74LS10BM	10	74LS079	10	10	CMOS	74LS079	10	10	CMOS
7400BN	74LS10BN	10	74LS080	10	10	CMOS	74LS080	10	10	CMOS
7400BO	74LS10BO	10	74LS081	10	10	CMOS	74LS081	10	10	CMOS
7400BP	74LS10BP	10	74LS082	10	10	CMOS	74LS082	10	10	CMOS
7400BQ	74LS10BQ	10	74LS083	10	10	CMOS	74LS083	10	10	CMOS
7400BR	74LS10BR	10	74LS084	10	10	CMOS	74LS084	10	10	CMOS
7400BS	74LS10BS	10	74LS085	10	10	CMOS	74LS085	10	10	CMOS
7400BT	74LS10BT	10	74LS086	10	10	CMOS	74LS086	10	10	CMOS
7400BU	74LS10BU	10	74LS087	10	10	CMOS	74LS087	10	10	CMOS
7400BV	74LS10BV	10	74LS088	10	10	CMOS	74LS088	10	10	CMOS
7400BW	74LS10BW	10	74LS089	10	10	CMOS	74LS089	10	10	CMOS
7400BX	74LS10BX	10	74LS090	10	10	CMOS	74LS090	10	10	CMOS
7400BY	74LS10BY	10	74LS091	10	10	CMOS	74LS091	10	10	CMOS
7400BZ	74LS10BZ	10	74LS092	10	10	CMOS	74LS092	10	10	CMOS
7400CA	74LS10CA	10	74LS093	10	10	CMOS	74LS093	10	10	CMOS
7400CB	74LS10CB	10	74LS094	10	10	CMOS	74LS094	10	10	CMOS
7400CC	74LS10CC	10	74LS095	10	10	CMOS	74LS095	10	10	CMOS
7400CD	74LS10CD	10	74LS096	10	10	CMOS	74LS096	10	10	CMOS
7400CE	74LS10CE	10	74LS097	10	10	CMOS	74LS097	10	10	CMOS
7400CF	74LS10CF	10	74LS098	10	10	CMOS	74LS098	10	10	CMOS
7400CG	74LS10CG	10	74LS099	10	10	CMOS	74LS099	10	10	CMOS
7400CH	74LS10CH	10	74LS100	10	10	CMOS	74LS100	10	10	CMOS
7400CI	74LS10CI	10	74LS101	10	10	CMOS	74LS101	10	10	CMOS
7400CJ	74LS10CJ	10	74LS102	10	10	CMOS	74LS102	10	10	CMOS
7400CK	74LS10CK	10	74LS103	10	10	CMOS	74LS103	10	10	CMOS
7400CL	74LS10CL	10	74LS104	10	10	CMOS	74LS104	10	10	CMOS
7400CM	74LS10CM	10	74LS105	10	10	CMOS	74LS105	10	10	CMOS
7400CN	74LS10CN	10	74LS106	10	10	CMOS	74LS106	10	10	CMOS
7400CO	74LS10CO	10	74LS107	10	10	CMOS	74LS107	10	10	CMOS
7400CP	74LS10CP	10	74LS108	10	10	CMOS	74LS108	10	10	CMOS
7400CQ	74LS10CQ	10	74LS109	10	10	CMOS	74LS109	10	10	CMOS
7400CR										

J.B. Saunders Co.

**3050 VALMONT ROAD
BOULDER, COLORADO 80301
Ph: (303) 442-1212**

Terms

- Prices, specifications and availability subject to change without notice.
- U.S. & Canadian orders minimum \$10.00.
- All other foreign orders \$20.00 minimum.
- Please add \$1.00 postage and handling.
- Foreign orders (exc. Canada) add 15% of total order for postage and handling.
- Colorado residents add 3 1/2% sales tax.
- No C.O.D.'s please.
- Foreign orders send U.S. funds ONLY.

Elapsed Time Indicator



New, model ED71 001 Elapsed time indicator made by General Time Co. 120 volts, 60 cycles, 2.5 watts nominal current. 1 1/2" square face; 1 1/2" diameter by 2 1/2" deep housing. Sells retail for over \$30.00!!!

J-8000 **\$15.95**

Reed Relay



Ultra sensitive 5VDC, SPST reed relay. Ideal when transistors or SCR's are not suitable.

J-5000 **\$1.50**

Keyboard



With point closure (non matrix) switches. Data sheet tells how to combine 3 to make alphanumeric keyboard!

J-5001 **\$1.95 3/\$5.00**


Fan Motor



117VAC fan motor for a variety of applications: Equipment cooling, hobby devices, cooling yourself off, etc. Use your imagination!!!

J-5002 **\$2.25**

Logi-Case



The Logi-Case is a universal instrument enclosure designed to be attractive, as well as extremely durable and useful. The unique side-out interior assembly is designed to hold up to 6 - 1 1/2" x 4" PC boards (great for packing a lot of components into a very small space!!!). Made from 1/8" thick extruded, anodized aluminum. Choice of red or smoke grey front lenses (reversible). Now available in two popular sizes!!! Small: 4 1/2" L x 3 1/4" D x 1 3/8" H, Large: 6 L x 4 1/2" D x 2 H.

(Small) J-8001 **7.95**
(Large) J-8014 **9.95**


4N25 Opto Isolator



NPN phototransistor and PN infrared light emitting diode, 1500 volt isolation, 3ma coil output current. Excellent frequency response to 300 KHz. New Motorola 6 pin dip w/ full data and specs.

J-4000 **\$1.00** 10 for \$9.00


PC Board



Highest quality glass epoxy, .062" thick, 1 sided - 5 boards/pack

4" x 6"	5 for \$3.00
3" x 6"	5 for 2.25
6" x 6"	5 for 3.60
2" x 8"	5 for 2.00

PC Trimmer Pots



TYPE	PART NO.	PRICE
470 ohm, vertical	2000	.25
1K ohm, vertical	2001	.20
2.5K ohm, vertical	2002	.20
5K ohm, vertical	2003	.20
22K ohm, horizontal	2004	.25
50K ohm, vertical	2005	.20
470K ohm, horizontal	2006	.25


Speaker



High quality miniature 8-ohm, 0.1 watt PM-type speaker. Individually boxed. Cone diameter: 1 1/4".

J-6000 **75¢**

RO170 Diode



The famous Motorola RO170 universal replacement diode, rated 1000 PIV @ 2.5A.

J-1000 **20¢**
100 for \$14.50

Rubber Feet



Molded, adhesive-back rubber feet in peel-off sheets.

J-8002 (round) **75¢ - 12**
J-8003 (square) **55¢ - 12**


V.O.X.



Solid state Voice Operated Switch. Complete and assembled. With schematic.

J-5003 **\$1.50**

Ribbon Cable



Cond Part No 1' 10'

6	S-7000	25	2.00
12	S-7001	45	3.95
24	S-7002	85	7.95


Jumbo LED



.200" factory prime LED's for experimenters. Use with our LED clip shown below.

J-4004 5 for **1.**

Wire Special



22 ga. magnet wire with unique solder through insulation. Buy by the pound & save (500 feet.)

J-7003 **\$2.50**

Toggle Switch



Heavy duty, high quality SPST toggle. Rated 15A @ 125 Volts.

J-5004 **95¢**

Transformer



Mini transformer for clocks, etc. 8V @ 500 ma or 12/190 ma, w/ specs.

J-5005 **\$1.50**

Trimmer Cap



1-3 pf Miniature trimmer cap. Ideal for crystal circuits, etc. 3/16" diam.

J-3000 **75¢**

Snap Switch



Mini SPDT snap switch made by Cherry. Rated 5 amps/125VDC.

J-5006 **65¢**


.1uf, 6000V Cap



New units by Sprague. Great for those experimenting w/ high voltage

J-3001 **70¢**


2N3055



The king of the audio power-transistors. Now at an unbelievable price!!!

J-1001 **50¢**


Heat Shrink



Much easier and faster than electrical tape. Twelve 6" peices, ass'd.

J-7004 **\$1.45**

Telephone Wire



26 AWG telephone hook-up wire. Single cond. 100ft/90¢ Twisted pr. 100/\$1.40 25 pair 1 foot/20¢

J-7005

Power Relay



Heavy duty, 25 Amps @ 115V. New by Potter & Brumfield.

J-5007 **\$4.00**


Pot with Switch



New by Allen Bradley, 100K mini 1/8" slotted shaft, 1/2" mount With SPST switch.

J-2008 **65¢**

Glue Syringe



An extremely useful tool for anybody!!! Appx. 4" long x 3/4" diameter. High impact plastic; w/ cap.

J-8004 **35¢**

Unique Switch



A strange but perhaps a very useful reverse action snap switch w/ lever. NC & NO connections

J-5008 **75¢**

Micro Switch



Miniature SPDT momentary pushbutton, rated 5A @ 125VAC.

J-5009 **95¢**

Strobe Tube/ Trigger Transformer



An experimenter's delight!!! Brand new Xenon strobe tube and 4 kv trigger transformer. Dozens of uses in light shows, photography, special effects, etc.

J-4001 **1.75¢**

High Voltage Pot



5 megohm, insulated shaft high voltage pot. 1/2" shaft, 3/8" bushing.

J-2009 **75¢**


1N4148 Diode



Brand new, miniature glass type 1N4148 general purpose high-speed switching diode. Case AA.

J-1002 12 for **\$1.00**

AA Nicad Batteries



Brand new, prime quality AA nicad batteries, manufactured by Sanyo. These won't last long!!!

J-8005 **\$1.50**

AA Battery Holder



All metal, size AA battery holder, with solder mounting tabs.

J-8006 **40¢**

TO-3 Heat Sink



High-heat transfer, brushed aluminum TO-3 heat sink.

J-8007 **45¢**


Rubber Edging



Protection from unsightly and dangerous metal edges. Contours to any shape. For material up to 1/16" thick.

J-8008 10'/\$1.60 100'/\$12.00

Photoflash Cap



Brand new by Ruby-con, 600uf @ 360 V. Use with our strobe tube & transformer to make your own strobe light!!!

J-3002 **\$1.95**

Toggle Switch



SPDT momentary center off (on-off-on). Rated 15A @ 125VAC, 10A @ 250VAC.

J-5010 **55¢**

Computer Caps



High-quality capacitors that meet the rigid demands of computer use. Brand new, 2700 uf @ 25 volts DC.

J-5011 **\$1.75**


Transformer



Unique split primary. Wire in either series or parallel to get either 9 or 18 volts @ 1.5A. -With specs & data.

J-5012 **\$2.50**

.01uf Disc Cap



.01 uf disc ceramic capacitor. Buy while they last!

J-5013 **5¢**

.02 uf Disc Cap



.02 uf ceramic disc capacitor. Buy while they last!

J-5014 **5¢**

47pf Mini Cap



Ultra miniature ceramic capacitor for crystal circuits, etc

J-5015 **10¢**

Felt Feet



3/8" diameter. Peel off strips, 25 feet per strip.

J-8010 **25¢**

Comp. Clip



7/16" I.D. high impact plastic, center mount.

J-8011 10' **25¢**

Dixie Bell



Enclosed signal bell 6 BVAC or 36VDC.

J-6001 **\$2.00**

Barrier Strip



Black molded bakelite. 5 posit ion barrier strip.

J-7008 **25¢**

.1/50V Cap



dipped mylar cap. .1uf @ 50 VDC.

J-5016 **15¢**

.01uf Mini Cap



Ultra-miniature .01 uf ceramic chip capacitor, axial leads.

J-5017 **15¢**

.01 Type MKM



Very stable metalized polycarbonate. .01uf @ 150V

J-5018 **20¢**

Hex Nuts



Standard size hex nuts for pots, lamps & switches, 25 for

J-7006 **\$1.00**

LED Panel Clip



Black plastic clip for mounting LED in panels.

J-4002 12' **1.**

Epoxy - Patch



Resin, hardener, mixing sticks and instructions.

J-8013 **\$1.25**


Lamp Socket



Double contact automotive type, bayonet-base.

J-4003 **20¢**

8200uf Cap



8200 uf @ 15VDC. Brand new by Mallory. Axial leads.

J-5019 **75¢**

.5uf/5KV Cap



Hi-voltage cap for experimenting or special applications.

J-5020 **2.50**

PB Switch



PC mount SPST momentary contact.

J-5021 **45¢**

Stand-Off



Insulated stand-off terminal, 5/8" long w/ 1/4" mtng screw.

J-7007 10' **1.49**


PC Trimmer



3/8" square, top adjusting, single turn. 20K ohm.

J-2011 **90¢**

Reed Switch



Giant 1 amp magnetic reed switch. 2 1/8" long.

J-5023 **50¢**


10K Pot



New from CTS. mini 1/8" shaft. 1/2" mount dia.

J-2012 **65¢**

TO-3 Insulator



Teflon coated aluminum. Much better than mica

J-8009 12' **1.00**

PC Trimmer



3/8" square, adjust. 50K ohm.

J-2010 **90¢**


PB Switch



PC mount push-on, push-off. SPST.

J-5022 **65¢**

60 Amp

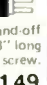

60 amp power terminator strip, 12 cont.

J-8012 **\$4.00**

Rocker Switch



PC mount 2 pole, 3 position. (used).

J-5024 **25¢**

Terminal



Single bakelite solder term. strip.

J-7009 6' **25¢**

more than
20,000 different
components

RECTIFIERS

	10	100
	For	For
1N4001	.60	5.00
1N4002	.70	6.00
1N4003	.80	7.00
1N4004	.90	8.00
1N4005	1.00	9.00
1N4006	1.10	10.00
1N4007	1.20	11.00

JAPANESE TRANSISTORS

2SA484	2.44	2SC482	1.40	2SC1226A	.85	2SD170	1.50
2SA495	.60	2SC495	.85	2SC1237	4.00	2SD180	2.50
2SA497	1.44	2SC517	3.60	2SC1239	3.50	2SD188	2.70
2SA634	1.00	2SC634A	.60	2SC1306	3.50	2SD234	.85
2SA636	1.25	2SC710	.49	2SC1307	4.75	2SD235	.85
2SA673	.70	2SC711	.49	2SC1377	4.00	2SD313	1.05
2SA678	.65	2SC735	.49	2SC1383	5.50	2SD314	1.50
2SA682	1.49	2SC756A	2.40	2SC1448	1.00	2SD315	1.20
2SA683	.60	2SC778	3.50	2SC1449	.85	2SD358	1.10
2SA699	1.30	2SC781	2.50	2SC1678	2.00	2SD360	1.05
2SA699A	1.45	2SC789	1.00	2SC1728	1.85	2SD427	2.55
2SA733	.49	2SC798	3.95	2SC1760	1.60	2SD525	1.50
2SA777	.99	2SC799	3.25	2SC1816	3.50	2SK19	1.25
2SB54	.49	2SC1000	.49	2SC1908	.49	2SK30A	.75
2SB56	.95	2SC1013	.95	2SC1909	3.75	2SK33	.90
2SB186	.49	2SC1014	.95	2SC1957	1.00	2SK55	1.00
2SB187	.55	2SC1017	1.20	2SC1973	.90		
2SB324	.60	2SC1018	1.00	2SC1975	3.50	3SK22Y	2.20
2SB370	.65	2SC1061	1.25	2SC2028	.80	3SK40	2.00
2SB405	.60	2SC1079	3.95	2SC2029	3.40	3SK45	2.20
2SB415	.65	2SC1096	.80	2SC2091	2.50	3SK49	2.20
2SB461	1.60	2SC1098	1.00	2SC2092	3.25		
2SB463	1.40	2SC1115	3.00				
2SB507	1.40	2SC1170B	4.95	2SD72	.80	4004	3.00
2SC371	.49	2SC1172	5.25	2SD77	1.50	4005	3.00
2SC372	.49	2SC1173	.75	2SD88	4.80	40081	1.50
2SC481	1.50	2SC1209	.75	2SD118	3.00	40082	3.00

JAPANESE CIRCUITS

AN136	2.90	LA4400FS	3.40	TA7055P	3.00	UPC20C	3.75
AN214	3.35	LA4400FR	3.40	TA7060P	1.40	UPC41C	2.80
AN239	6.50	LD3120	2.40	TA7061P	1.50	UPC563H2	8.00
AN241	2.40	M5115PR	7.80	TA7063P	1.50	UPC566H	1.25
AN315	3.50	PLL01A	13.50	TA7075P	3.75	UPC573C	2.60
BA511	3.00	PLL02A	8.50	TA7089P	2.90	UPC595C	2.95
BA521	3.40	PLL02A-G	8.50	TA7120P	1.50	UPC1001H2	3.50
HA1202	2.20	SG613	6.75	TA7150P	3.75	UPC1008C	5.75
HA1306	4.90	STK011	7.50	TA7153P	6.90	UPC1020H	3.25
HA1308	4.50	STK015	6.50	TA7203P	4.25	UPC1025H	3.50
HA1322	4.20	STK032	14.20	TA7204P	3.70	UPC1166H	4.50
LA1201	4.25	STK050	24.50	TA7205P	3.60	UPD277C	4.50
LA4031P	3.20	STK056	11.35	UH1C003	6.50	UPD857C	15.50
LA4032P	4.20	STK415	8.50	UH1C004	6.50	UPD858C	9.50
LA4051P	3.20	TA7045M	3.25	UPC16C	2.50	UPD861C	18.50

CHECK OUR NEW LOWER PRICES

VOLT. REG 5400 SERIES OEM SPECIALS

LM340K-5	1.70	5400	1.00	1N34	.25	2N2905A	.30	2N3903	.16
LM340K-6	1.70	5404	1.25	1N60	.25	2N2906	.25	2N3904	.16
LM340K-8	1.70	5410	1.00			2N2906A	.30	2N3905	.16
LM340K-12	1.70	5426	1.25					2N3906	.16
LM340K-15	1.70	5473	1.50	1N270	.25	2N2907	.25	2N3955A	2.45
LM340K-18	1.70	5475	1.50	1N914	.10	2N2907A	.30	2N3957	1.25
LM340K-24	1.70	5486	1.90	2N173	1.75	2N2913	.75	2N3958	1.20
LM340T-5	1.50	5493	2.00	2N404	.75	2N2914	1.20	2N4037	.60
LM340T-6	1.50	54100	1.80	2N443	2.50	2N3019	1.00	2N4037	.60
LM340T-8	1.50	54LS04	1.00	2N508A	.45	2N3053	.30	2N4037	.60
LM340T-12	1.50			2N718	.25	2N3054	.70	2N4037	.60
LM340T-15	1.50			2N930	.25	2N3055	.75	2N4124	.16
LM340T-18	1.50			2N956	.30	2N3227	1.00	2N4126	.16
LM340T-24	1.50			2N1302	1.25	2N3247	3.40	2N4141	.20
				2N1305	.75	2N3250	.50	2N4142	.20
				2N1540	.90	2N3393	.20	2N4143	.20
				2N1544	.80	2N3394	.17	2N4220A	.45
				2N1560	2.80	2N3414	.17	2N4234	.45
				2N1605	1.75	2N3415	.18	2N4400	.16
				2N1613	.50	2N3416	.19	2N4401	.16
				2N1711	.50	2N3417	.20	2N4402	.16
				2N2102	.70	2N3442	1.85	2N4403	.20
				2N2160	.70	2N3563	1.50	2N4409	.16
				2N2218	.25	2N3563	.20	2N4410	.16
				2N2218A	.30	2N3565	.20	2N4441	1.00
				2N2219	.25	2N3638	.20	2N4442	1.15
				2N2219A	.30	2N3642	.20	2N4443	.95
				2N2221	.25	2N3643	.20	2N4852	55
				2N2221A	.30	2N3645	.20	2N5061	.30
				2N2222	.25	2N3646	.14	2N5064	.50
				2N2222A	.30	2N3731	3.75	2N5130	.20
				2N2270	.40	2N3740	1.00	2N5138	.15
				2N2369	.25	2N3771	1.75	2N5296	.50
				2N2484	.32	2N3772	1.90	2N5306	.20
				2N2712	.18	2N3773	3.00	2N5400	.40
				2N2904	.25	2N3819	4.00	2N5401	.50
				2N2904A	.30	2N3823	3.00	2N5457	.35
				2N2905	.25	2N3866	1.25	2N5458	.30

7400 TTL

7400	.18	7442	1.08	74107	.49
7401	.21	7448	1.15	74121	.55
7402	.21	7450	.26	74122	.49
7404	.21	7451	.27	74123	1.05
7405	.24	7453	.27	74125	.80
7407	.45	7454	.41	74126	.81
7408	.25	7460	.22	74132	3.00
7409	.25	7472	.39	74141	1.15
7410	.20	7473	.45	74150	1.10
7411	.30	7474	.45	74151	1.25
7413	.85	7475	.80	74153	1.35
7416	.43	7482	.75	74154	1.54
7417	.43	7483	1.15	74157	1.30
7420	.21	7485	1.12	74161	1.45
7422	1.50	7486	.45	74164	1.65
7425	.43	7489	2.49	74165	1.65
7427	.37	7490	.69	74166	1.70
7428	.35	7491	1.20	74174	1.95
7430	.26	7492	.82	74175	1.95
7432	.31	7493	.82	74180	1.05
7437	.47	7494	.91	74181	3.55
7438	.40	7495	.91	74191	1.50
7440	.21	7496	.91	74195	1.00
7441	1.10	74100	1.25	74197	1.00

N.J. residents add 5% sales tax.
All orders add \$1.00 Postage \$1.50 Canada
minimum order \$5.00



**NEW-TONE
ELECTRONICS**

PO Box 1738A Bloomfield, N.J. 07003
Phone (201) 748-6171, 6172, 6173


PARTIAL LISTING - WRITE FOR FREE CATALOG

CIRCLE 47 ON FREE INFORMATION CARD

ELECTRONIC DISCOUNT SALES

Dept. R, 138 N. 81st Street, Mesa, Arizona 85207

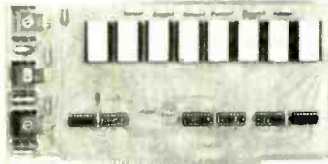- ★ ★ S-100 bus compatible
- ★ ★ Optional wait states: none, one or two (selectable with plug-in jumpers)
- ★ ★ Epoxy board with plated thru holes (double sided)
- ★ ★ Address any one of 8 different 8K blocks or any one of 16 different 4K blocks
- ★ ★ All sockets provided



2708 EPROM BOARD

AVAILABLE SOON: (S-100 BUS)

★ ★ Phase encoded cassette interface with programmable serial port: Dual recorder, tarbell or K-C method supported ★ ★ 2708 Programmer

- ★ ★ Gold plated connectors
- ★ ★ On board regulation (heat sinked)
- ★ ★ Convertible for use with 2716 EPROMS
- ★ ★ Complete instructions
- ★ ★ ASSEMBLED & TESTED (without EPROMS) \$59.95
- ★ ★ COMPLETE KIT (without EPROMS) \$49.95
- ★ ★ BARE BOARD WITH INSTRUCTIONS \$35.95

TVT-III (with 2K memory capability)
This system provides 16 lines of 32 characters each. It is composed of all TTL except for the 2513 and 2102's. Basic kit includes: Main board, 2K Memory board, six 2102's (1K of memory), plus other components. (Keyboard, case and power supply not included.)



All boards are double sided and plated thru. Small boards plug into main board at right angles.

	KITS	ASSEMBLED	BOARD ONLY
Basic TVT-III	\$99.95	\$135.45	\$32.50
Screen Read	12.65	17.30	8.10
Manual Cursor	9.95	13.95	6.50
U.A.R.T.	29.95	39.95	15.50

Construction packet sold separately: \$2.95
AVAILABLE NOW! 64 CHARACTER CONVERSION AND/OR SCROLLING OPTION FOR THE TVT-III. Complete documentation. Kit: \$6.95. Data only: \$1.00

PROGRAMMING SERVICE	
1702A: \$5. original program, copies \$2. (same order)	
2708: \$16. original program, copies \$4. (same order)	
2716: \$26. original program, copies \$8. (same order)	
WE REQUIRE A WRITTEN PROGRAM IN EITHER HEX OR SPLIT OCTAL or a CHIP ALREADY PROGRAMMED.	
CPU's	
Z-80A \$18.95	2716, 16K \$37.50
8080A 8.50	2708, 8K 10.50
6800 17.50	1702A, 2K 3.75
F-8 18.95	

RAMS	
2102A (450ns)	\$1.25
21102 (250ns)	1.60
21102 (450ns)	1.35
2107A, 4K DYN.	3.50
MISC. CHIPS	
2813, 32 word x 9 BIT FIFO	\$5.50
AY5-2376, kybd	\$12.95
MM5320 TV SYNC. GEN.	\$5.50
AY5-1013A UART	\$4.75
OK™ Wire Wrapping	
WSU-30 HAND TOOL	\$5.50
WSU-30M HAND TOOL (mod. wrap)	\$6.50

WD-30-(blu),(yel),(wh), (rd) wire & dispenser	\$3.25
50' ROLL #30 WIRE, ABOVE COLORS	\$1.50

SHOP YOUR NEARBY RADIO SHACK FOR QUALITY PARTS AT LOW PRICES!

Top quality devices, fully functional, carefully inspected. Guaranteed to meet all specifications, both electrically and mechanically. All are made by well known American manufacturers, and all have to pass

manufacturer's quality control procedures. These are not rejects, not fallouts, not seconds. In fact, there are none better on the market! Count on Radio Shack for the finest quality electronic parts.

TTL Digital ICs

First Quality

Made by National Semiconductor and Motorola



Type	Cat. No.	ONLY
7400	276-1801	35c
7402	276-1811	39c
7404	276-1802	35c
7406	276-1821	49c
7410	276-1807	39c
7413	276-1815	79c
7420	276-1809	39c
7427	276-1823	49c
7432	276-1824	49c
7441	276-1804	99c
7447	276-1805	99c
7448	276-1816	99c
7451	276-1825	39c
7473	276-1803	49c
7474	276-1818	49c
7475	276-1806	79c
7476	276-1813	59c
7485	276-1826	1.19
7486	276-1827	49c
7490	276-1808	79c
7492	276-1819	69c
74123	276-1817	99c
74145	276-1828	1.19
74150	276-1829	1.39
74154	276-1834	1.29
74192	276-1831	1.19
74193	276-1820	1.19
74194	276-1832	1.19
74196	276-1833	1.29

Resistor and Capacitor Packs



Resistor and capacitor kits in handy plastic storage boxes you can use over and over again. Stock up!

1/2 Watt, 10% Tolerance Resistors. 271-601 Pkg. of 350/9.95
 1/4 Watt, 5% Tolerance Resistors. 271-602 Pkg. of 350/9.95
 50WVDC Ceramic Disc Capacitors. 272-601 Pkg. of 175/9.95
 35WVDC Radial Lead Capacitors. 272-602 Pkg. of 35/9.95
 35WVDC Axial Lead Capacitors. 272-603 Pkg. of 36/9.95

Tantalum Capacitors

Maximum capacity in smallest size. Low ESR, highly stable electrical characteristics and low leakage. Radial leads.

Cat. No.	μF	Each	Cat. No.	μF	Each
272-1401	0.1	39c	272-1407	2.2	45c
272-1402	0.22	39c	272-1408	3.3	45c
272-1403	0.33	39c	272-1409	4.7	49c
272-1404	0.47	39c	272-1410	6.8	49c
272-1405	0.68	39c	272-1411	10.0	49c
272-1406	1.0	39c			

Nos. 1401-1408, 35WVDC. 1409-1411, 16WVDC.



PC Board Accessories



8-piece photographic PC board processing kit — fastest, easiest way to produce perfect printed circuit projects.

276-1560 12.95
 Etch-Resist Marking Pen. 276-1530 1.19
 Etchant Solution. 276-1535 1.89
 PC Board Assortment. 276-1573 1.98


Build an LED Digital Clock



12-HR LED Clock Module. Just add a transformer and switches for a complete clock with 0.5" LED display. 277-1001 14.95
 Transformer for above. 120VAC 60 Hz. 273-1520 3.99
 SPST Miniature Pushbutton Switch. 275-1547 5/1.99
 Display Case. 1 1/2"x6 3/4"x4 7/16". 270-285 3.95


CMOS ICs

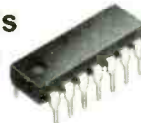100% guaranteed electrically and mechanically



Type	Cat. No.	ONLY
74C00	276-2301	49c
74C02	276-2302	49c
74C04	276-2303	49c
74C08	276-2305	49c
74C74	276-2310	89c
74C76	276-2312	89c
74C90	276-2315	1.49
74C192	276-2321	1.69
74C193	276-2322	1.69
4001	276-2401	49c
4011	276-2411	49c
4013	276-2413	89c
4017	276-2417	1.49
4020	276-2420	1.49
4027	276-2427	89c
4049	276-2449	69c
4050	276-2450	69c
4511	276-2447	1.69
4518	276-2490	1.49

LED Digital Displays

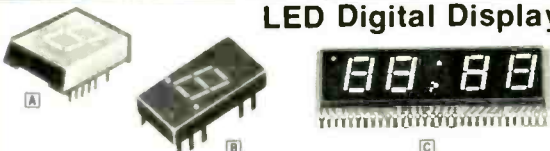

Digits	Size	Drive	Cat. No.	ONLY
1	0.6"	Anod.	276-056	2.99
1	0.6"	Cath.	276-066	2.99
1	0.3"	Anod.	276-053	1.99
1	0.3"	Cath.	276-062	1.99

Digits	Size	Drive	Cat. No.	ONLY
1	0.3"	Anod.	276-1210	4/6.99
1	0.3"	Cath.	276-1211	4/6.99
4	0.5"	Anod.	276-1201	6.95
4	0.5"	Cath.	276-1202	6.95


IC Accessories



- Ⓜ Bus Strip. 276-173 1.99
- Ⓜ Experiment. Socket. 276-172 9.95
- Ⓜ DIP Switch. 275-1301 1.99
- Ⓜ DIP Header. 276-1980 1.29
- Ⓜ Right Angle 16-Pin Socket. 276-1985 1.49

Pins	Cat. No.	Price
8	276-1995	2/59c
14	276-1999	2/89c
16	276-1998	2/89c
28	276-1997	Ea. 89c
40	276-1996	Ea. 99c

Power Supply Parts

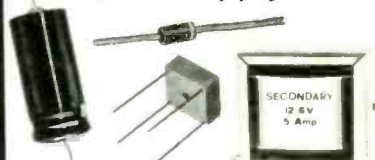

6-Amp Full-Wave Bridge Rectifier. 50 PIV. 276-1180 1.99
 50V 3-Amp Power Rectifier. 300-A surge. 276-1141 Pkg. 2/69c

Electrolytic Capacitors
 3300 μF at 35V. 272-1021 2.99
 5000 μF at 35V. 272-1022 3.49

Heavy-Duty Transformers. All for 120VAC, 60 Hz.


Cat. No.	Volts	Current	Size	Each
273-1512	25.2 CT	2A	2 1/2"x2 1/2"	4.99
273-1513	12	5A	4x2x2 1/2"	8.95
273-1514	18 CT	4A	4x2x2 1/2"	8.95

Linear ICs

By National Semiconductor and Motorola — first quality

Type	Cat. No.	ONLY
301CN	276-017	49c
324N	276-1711	1.49
339N	276-1712	1.49
386CN	276-1731	99c
555CN	276-1723	79c
556CN	276-1728	1.39
566CN	276-1724	1.69
567CN	276-1721	1.99
723CN	276-1740	69c
741CN	276-007	49c
741H	276-010	49c
3900N	276-1713	99c
3909N	276-1705	99c
3911N	276-1706	1.99
4558CN	276-038	79c
75481	276-1701	99c
75492	276-1702	99c
7805	276-1770	1.29
7812	276-1771	1.29
7815	276-1772	1.29


Computer Chips

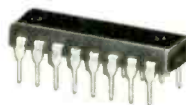

8080A Microprocessor. An 8-bit National Semiconductor chip in a 40-pin DIP. 100% Prime. 276-2510 17.95

2102 Static RAM. 1024-word by one bit read/write memory. Under 600 nS access time. 276-2501 2.49 Ea. or 8/14.95

Silicon Solar Cells

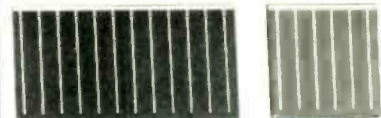

Produce Power from Light!

2cmx4cm. 0.5V at 100mA. 276-120 2.99
 2cmx2cm. 0.5V at 60mA. 276-128 1.99

Clock Chips



50252. 12-hour clock, 24-hour alarm chip. With full specifications. 276-1751 6.99
 7001. 12-hour calendar alarm clock IC. With all data. 276-1756 10.95

WHY WAIT FOR MAIL ORDER DELIVERY? IN STOCK NOW AT OUR STORE NEAR YOU!

Radio Shack

Prices may vary at individual stores and dealers

A TANDY COMPANY • FORT WORTH, TEXAS 76102
 OVER 6000 LOCATIONS IN NINE COUNTRIES

APRIL 1978

AMAZING ELECTRONIC PROJECTS and PRODUCTS:

Lasers Super Powered, Burning, Cutting, Rifle, Pistol Pocket. See in Dark—Shotgun Directional Mike—Unscramblers—Giant Tesla—Stunwand—TV Disrupter—Energy Producing, Surveillance, Detection, Electrifying, Ultrasonic, CB, Auto and Mech. Devices, Hundreds More—All New Plus INFO UNLTD PARTS SERVICE. Catalog \$1. Information Unlimited, Box 626, Lord Jeffery Court, Amherst, N.H. 03031.

PRE-RECORDED videocassettes: 1/2" Betamax and VHS formats. Send for free list. **TRI-STATE VIDEO PRODUCTIONS**, P.O. Box 1332, Portsmouth, OH 45662



HIGH BLOOD PRESSURE.
Treat it...and live.

We're Fighting for Your Life

Please give generously
American Heart Association

DON'T MISS ANY

Get every single issue of Radio-Electronics delivered right to your door, and before it appears on the newsstand. Use this coupon and subscribe now.

Mail to: Radio-Electronics
SUBSCRIPTION DEPT., P.O. BOX 2520,
BOULDER, COLO. 80322

name (please print) _____
address _____
city state zip code _____

check offer preferred

- 1 Year—12 issues ONLY \$9.98
- 2 Years—24 issues SAVE MORE \$19.00
(You save \$5.00 over newsstand)
- 3 Years—36 issues GREATER SAVINGS \$27.00
(You save \$9.00 over newsstand prices)
- Payment enclosed Bill Me
- Check here if this is a new subscription
- Check here if you are extending or renewing your subscription

Extra Shipping: Canada \$3.00 per year, all other countries \$5.00 per year.

40DB

Why is this the LARGEST SELLING low cost COUNTER KIT?

This counter is such a great seller because people like you have found that, feature for feature, the CT-50 gives you more for your money. Advanced LSI and CMOS circuitry has; lowered power consumption, increased performance, and reduced cost. Complete push button operation makes using the CT-50 a snap, and automatic decimal point positioning gives you quick, reliable readings. Battery operation is also possible because the CT-50 runs equally as well on 12VDC as it does on 110VAC. For ultra-accuracy we offer the CB-1 color burst adapter, it locks the CT-50's internal crystal to the television networks color standard for .001 ppm accuracy! Why sacrifice performance by using another counter when you can get professional quality at the unheard of price of \$79.95? Order yours today!



SPECIFICATIONS
Sensitivity: less than 10 mv.
Frequency range: 5 Hz to 60 MHz, typically 65 MHz
Gatetime: 1 second, 1/10 second, with automatic decimal point positioning on both direct and prescale
Display: 8 digit red LED, 4" height
Accuracy: 2 ppm, Internal TCXO standard.
Input: BNC, 1 megohm direct, 50 Ohm with prescale option
Power: 110 V ac @ 6 Watts or 12 V dc @ 300 400 ma
Size: Approx. 6" x 4" x 2", high quality aluminum case
CT 50,60 MHz Counter Kit, wired & tested \$79.95
CT-600, 600 MHz prescaler option for CT-50, add ... \$29.95

MINI-KITS

FM WIRELESS MIKE KIT
Transmit up to 300' to any FM broadcast radio, uses any type of mike. Runs on 3 to 9V. Type FM-2 has added super-sensitive mike preamp.
FM-1 - \$2.95 FM-2 - \$4.95

SUPER-SLEUTH AMPLIFIER
A super-sensitive amplifier which will pick up a pin drop at 15 feet! Great for monitoring baby's room or a general purpose test amplifier. Full 2 watts of output, runs on 6 to 12 volts, uses any type of mike. Requires 8-45 ohm speaker.
Complete Kit, BN-9 \$4.95

COLOR ORGAN/MUSIC LIGHTS
See music come alive! 3 different lights flicker with music or voice. One light for lows, one for the mid-range and one for the highs. Each channel individually adjustable, and drives up to 300 watts. Great for parties, band music, nite clubs and more.
Complete Kit, ML-1 \$7.95

TOPE DECODER KIT
A complete tone decoder on a single PC Board. Features: 400-5000 Hz adjustable frequency range, voltage regulation, 567 IC. Use: full for touch-tone decoding, tone burst detection, FSK demod, signaling, and many other uses. Use 7 for 12 button touchtone decoding. Runs on 5 to 12 volts.
Complete Kit, TD-1 \$4.95

LED BLINKY KIT
A great attention getter which alternately flashes 2 Jumbo LEDs. Use for name badges, buttons, or warning type panel lights. Runs on 3 to 9 volts.
Complete Kit, BL-1 \$2.95

POWER SUPPLY KIT
Complete triple regulated power supply provides variable +15 volts at 200 mA and +5 volts at 1 Amp. 50 mV load regulation good filtering and small size. Kit less transformers. Requires 6-8V at 1 Amp and 18 to 30 VCT.
Complete Kit, PS-3LT \$6.95

SIREN KIT
Produces upward and downward wail characteristic of police siren. 5 watts audio output, runs on 3-9 volts, uses 8-45 ohm speaker.
Complete Kit, SM-3 \$2.95

VIDEO MODULATOR KIT
Converts any TV to video Monitor, Super stable tunable over Ch. 4-6. Runs on 5-15V, accepts std video signal. Best unit on the market.
Complete Kit, VD-1 \$6.95

SIX DIGIT 12/24 HOUR CLOCK KIT

Here's a clock you can be proud of. The best looking, most complete kit on the market! Features include: time set push-buttons, jumbo 4" readouts, and extruded aluminum case available in 5 colors. All parts included. Colors: gold, silver, bronze, black, blue (specify)



Clock Kit, DC-5 \$22.95 Alarm Clock, 12 Hr., DC-8 24.95
Mobile Clock, DC-7 25.95 Clock with HAM ID timer DC-10 25.95
Assembled and tested clocks available, add \$10.00 to Kit price.

600 MHz PRESCALER

Extend the range of your counter to 600 MHz. Works with all counters. Less than 150 mv sensitivity. Specify -10 or -100. Wired, tested,
PS-1 B \$59.95
Kit, PS-1 B \$44.95

CALENDAR ALARM CLOCK

Has every feature one could ever ask for. Kit includes everything except case. Build it into wall, station or even car!

- FEATURES:**
- 6 Digits, 5" High LED
 - 12/24 Hour Format
 - Calendar shows mo., day
 - Snooze Button
 - True 24 Hour Alarm
 - 7001 chip does all!
 - Battery back up with built-in chip time base.

Complete Kit, less case DC-9 \$34.95

TV TYPEWRITER KIT

A compact 5 x 10 inch PC card that requires only an ASCII keyboard and a TV set to become a complete interactive terminal for connection to your microprocessor asynchronous interface. Its many features are: single 5-volt supply, crystal controlled sync and baud rates (up to 5600 baud), 2 pages of 32 characters by 16 lines, read to and from memory, computer and keyboard operated cursor and page control, power-on initialization, full 64-character ASCII display, block type, see-thru cursor, keyboard/computer backspaces, for word spaces, line feeds, rev. line feeds, home, returns cursor. Also clears page, clears to end of line, selects page 1 or 2, reads from or to memory. The card requires 5 volts at approx. 900 ma and outputs standard 75 ohm composite video.

TH3216 Kit \$149.95
TH3216, Assembled and Tested 239.95
VD 1 Video to RF Modulator Kit 6.95

CAR CLOCK KIT

12/24 Hour 12-Volt AC or DC
• High Accuracy (1 minute/month)
• 5 Jumbo 4" LED readouts
• Easy, no-polarity hookup
• Display blanks with ignition
• Case mounting bracket included
• Super instructions
Complete Kit, DC-11 \$27.95
Auto dimmer for OC-11 \$2.50

741 OP AMP SPECIAL Prime, Mini-dip 10/\$2.00

ICs	LINEAR	REGULATOR	TRANSISTORS	
5314 Clock	\$2.95	555 \$ 50	78MG \$1.49	MRF 238 30W VHF \$11.95
7001 Clock	6.95	556 \$ 75	309K \$.89	PNP 2N3904 type 10/\$1.00
5369 Cnos	1.95	566 1.49	309H \$.99	PNP 2N3906 type 10/\$1.00
7447	.79	567 .50	340K-12 \$.99	NPN Power Tab 40W 3/\$1.00
7473	.35	1458 .50	7805 \$.89	PNP Power Tab 40W 3/\$1.00
7475	.50	LED DRIVE R 7812 \$.89	FET MPF-102 type 3/\$2.00	UJT 2N2646 type 3/\$2.00
7490A	.85	75491 .50	7815 \$.89	2N3055 NPN Power
74143	3.50	75492 .50	7818 \$.89	

ORDER BY PHONE OR MAIL
Satisfaction guaranteed or money refunded. Add 8% for shipping and handling. COD add \$1.00. Orders under \$10.00 add \$3.75. NY residents add 7% sales tax. Minimum order \$6.00.

ramsey electronics

BOX 40728 ROCHESTER, NY 14610 (716) 271-4487

MOVING?

Don't miss a single copy of **Radio-Electronics**. Give us:

Six weeks' notice

Your old address and zip code

Your new address and zip code

ATTACH LABEL HERE

name (please print) _____
address _____
city state zip code _____

Mail to: Radio-Electronics
SUBSCRIPTION DEPT., P.O. BOX 2520,
BOULDER, COLO. 80322

service questions

HOPELESS PROBLEM

This Zenith D3720L is a hopeless problem! There's no high voltage and the horizontal output tube isn't conducting. The drive waveform checked good as did the DC supply voltage, deflection yoke, etc. I replaced the flyback—no change. I note that the DC voltage on pins 3 to 11 of the 20LF6 drops from +300 to only +60—A. H., New York, NY.

Nothing is hopeless if you attack the problem systematically. There are 17 different things you must eliminate in this kind of problem, and there may be more. You've already eliminated quite a few. Now, the one significant reaction is the high-voltage drop in the 20LF6 screen grid voltage when the set warms up. I've seen this before.

There are two possible causes for the voltage drop. One is that the top cap on the 20LF6 may not be making contact, so there is actually no plate voltage. The screen does have voltage, so it tries to act as the plate and the resulting high current causes the voltage to drop. Check the continuity between the 20LF6 plate cap lead and the damper cathode; this should read only a very few ohms. Also check the solder joint between the lead and cap.

The other cause is even rarer, but it has shown up lately. Try another 20LF6 tube. We've run into this before, and there is some weird defect in the tube itself, showing up even in new tubes. Open the 20LF6 cathode and read the current to find out whether the tube is taking excessive current or not enough.

Here's another rare cause for your problem. Place a DC voltmeter on the damper cathode and turn the set on. You should read the full B+265 volts here as soon as the damper tube warms up. If you do not, try a new damper tube; sometimes the cathode ribbon in some of these tubes opens up.

HORIZONTAL RADIATION

A reader recently wrote about some incorrect answers to Reader Questions in the November 1977 issue. His letter contained one remark that I'd like to correct. Referring to a question dealing with horizontal radiation from one TV set into another, he wrote "your answer is more theoretical than practical," etc. And claimed this radiation was due to co-channel interference!

Not so. This answer was the result of actual personal observations of real sets, as well as many letters from readers with the same problem. For instance, in the first case I ever saw years ago, an old Dumont 301 in a two-set home would tear up the picture on a portable in the next room! The cause: one of the 5U4 rectifiers was very gassy. Whenever possible, which is most of the time, the published answers in Reader Questions have been verified by reader feedback.

COLOR PROBLEM

I've got a lulu of a problem here. This set was vandalized by an angry husband who had to turn it over to his wife as a part of the settlement! I found and fixed all the missing and broken parts, and got it working. The set came back with a focus problem; I fixed that. Now I've got a fine sharp black and white picture, but no color at all! With the set working, all I can get in the color circuits is a big flattened horizontal pulse. If I open the cathode of the horizontal-output tube, the color waveforms come back, all the way to the picture tube grids! What the Sam Hill is this?—R. M., Kensington, MD.

From the symptoms you describe, this color problem is being caused by the presence of the horizontal blanking pulse! When you kill the horizontal output, you kill these pulses. Since the color-signal circuits are obviously working, something in the blanking circuitry is causing the color to be blanked out. **R-E**

MINI MINI TOGGLE

EXTRA SMALL DPDT.
3A 125VAC CONTACTS

each \$1.50

8 - 10.

100 - \$105.



actual size




ACTUAL SIZE

\$1.35 10-\$12

C & K #7103
Single pole double throw
center off (3 position)
toggle switch.....

BISTABLE RELAY

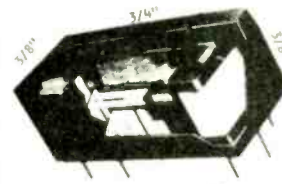

SPDT 6VDC 200 OHM COILS
1 AMP 20 WATT DC CONTACTS
LONG LIFE (1 X 10⁵) OPER.
HIGH SPEED (500 HZ)
HERMETICALLY SEALED

\$2.95 ea.

COUNTER DISPLAY KIT

Ideal module for home built counter projects. Includes 7490 decade counter 7475 latch, 7447 driver, and RCA .6" NUMITRON display. PCB with plated thru hole and instructions supplied..... KITS SUPPLIED FROM ONE TO TEN DIGITS PER BOARD (all interconnects plated)...

\$5.89 per digit

7490 7475 7447

ultra sensitive relay



\$2.95 ea.

Single pole normally open dry reed relay. Unbelievable sensitivity, 1800 ohm coil with 9 volt pull-in (voltage less than 3 ma.) A TTL gate will drive many of these. A CMOS buffer will directly actuate this nifty relay..... MFR. unknown, but I was told they came from IBM. 600 available

ELEC-TROL REED RELAY 12 vdc 440 Ω coil 4 dpst n.o.

PICTURE IS APPROXIMATION. RELAY HAS FOUR PINS ON ONE END AND TWO ON OTHER. PINS ARE SPACED .1" X 1". 1/2A CONTACTS.

\$1.75 ea. - ten \$15

POTTER BRUMFIELD

Type KHP Relay
4 PDT 3A Contacts

24VDC COIL
650 ohms
120VAC
10.5MA



\$1.60 ea.

DIP TRIMMER

12 TURN 1/4" x 1/4" x 1/4"
5K or 200K only
mfg. DALE
TEN FOR \$4



-SUPER SPECIALS-

- DIAC 27 TRIGGER DIODE20
- PULSE XFMR. 1/1 TOROID-ENCASED .25
- 600MFD. 360VDC PHOTO FLASH CAP. .90
- 1702A 2K, lus, EPROM7.95
- SP425 SPERRY 9 digit 1/2" HV multiplexed 7 seg.1.25
- MM5369 time base osc. chip1.75
- T.V. crystal for above..... 1.75
- 1101A 256 x 1 MOS RAM59
- 93410 256 x 1 45NS RAM85
- 75451 peripheral driver40
- 7402 TTL nor gate16
- 7430 TTL nand gate14
- CERAMIC FILTER 10.7 MHz.1.20
- MM5058 1024 bit static SR1.50
- UA715 60MHz. op-amp1.20
- 74S206 256 x 1 45NS RAM90
- 78L2.6 2.6V TO92 .1A +regul.29
- 78L05 5.0V " " " "29
- 78L6.2 6.2V " " " "29
- 78L12 12V " " " "29
- 78L15 15V " " " "29
- 78M05 5V tab .5A + regul.59
- 78MC 4 term. adj. .5A + reg.1.29
- 79NC " " " " - reg.1.39
- 7805T tab 1A 5v regul89
- 7812 to-3 1A +12V regul.59

FANTASTIC

RCA 40536

2A 400V TRIAC
FACTORY ASSEMBLED ON HEAT SINK READY TO PUT IN YOUR CIRCUIT RD.

SPERRY 9 DIGIT PLASMA DISPLAY, COMMON CATHODES, 1/4" HIGH DIGITS—
D#8880 IC DRIVER FOR "NIXIE" ABOVE DISPLAYS 0123456789ABCDEF WITH 0-15 BINARY INPUT.....

DISPLAY or IC \$1.50 BOTH \$2.75 \$.90 ea. 10 for \$7.50

TOLL-FREE TELEPHONE SERVICE

24 HOURS A DAY \$15 minimum order
7 DAYS A WEEK
NOTE: Operators can only handle orders to please orders of 1000 and questions @ 800 to our company.

To order by phone
DIAL: 800 423 2355 EXT 307
Any Time Day or Night (California Residents Please Dial 800 232 2175)

PHONE ORDERS CAN ONLY BE CHARGED TO MASTER CHARGE OR VISA/BANKAMERICARD

PO BOX 41778
Sacramento, Ca. 95841
916 334 2161
4811 MYRTLE AVE

Money back guarantee—\$5 minimum order. We pay post on orders for \$10 or more. All payment must be in U.S. funds. Foreign orders must include post. BAC & MC are not prepaid orders and shipping is added.

BABYLON ELECTRONICS
BANKAMERICARD

CIRCLE 51 ON FREE INFORMATION CARD

ADVANCED COMPUTER PRODUCTS

THE FIRST TO OFFER PRIME PRODUCTS TO THE HOBBYIST AT FAIR PRICES NOW LOWERS PRICES EVEN FURTHER!

1. Proven Quality Factory tested products only, no re-tests or fallouts. Guaranteed money back. We stand behind our products.

2. Same Day Shipment All prepaid orders with cashiers check, money order or charge card will be shipped same day as received.

MOTOROLA 6800 COMPATIBLE MODULES

- MEK 6800 D2 KIT \$235.00**
- 9600 6800 MPU 595.00
 - 9601 16 Slot Mother Bd. 175.00
 - 9602 16 Slot Card Cage 75.00
 - 9603 8 Slot Mother Bd. 100.00
 - 9610 Proto Board 35.00
 - 9615 4K EPROM Module (1702A) 26.00
 - 9620 16 Port Parallel I/O 375.00
 - 9626 8K Static RAM Module 295.00
 - 9626K 8K Static RAM Kit 225.00
 - 9630 Extender Card 60.00
 - 9650 8 Port Duplex Asyn Serial I/O 395.00
 - Connectors \$6.50 6/84.00

All assembled & tested not Kits
PLUS MOTOROLA TV MONITORS-PRIME
 Model M3560-155 L01 12" display 219.95
 Model M2000-155 9" display 199.95
 Add \$10.00 for shipping

LOGOS 8K STATIC MEMORY



\$125.99
Kit

Assembled & tested **\$179.95**
 250 ns. Kit 149.95
 Assembled & tested **199.95**

Features: Lowpower, Dip Switch Selectable memory protect down to 256 Bytes, addressing on 1K Boundaries, No wait states, fully buffered, battery back-up.

SPECIAL OFFER:
 Buy 4 Units Only \$117.00 ea.

BYTEUSER 8K EPROM \$64.95

Assembled & tested \$ 94.95
 Bare PC Board w/Data 21.95
 8K EPROM (8) 2708 \$112.00

Features: Power on Jump, Reset Jump, all socketed with top quality PC Board material.

SPECIAL OFFER:
 Buy 4 Units Only \$59.95 ea.

Z-80 CPU KIT \$129.95

Low Price (regular price 269.95) Kit
 Assembled & tested \$199.95

FEATURES:
 S-100 IMSA/Altair compatible, completely compatible to TDL hardware and software. Can be used at 4MHz with Z-80A. Add \$7.00 for sockets. Add \$5.00 for Z80 manual.

NOW IN STOCK FOR IMMEDIATE SHIPMENT.

DATA BOOKS

- NSC Digital \$ 3.95
- NSC Linear 4.95
- NSC Linear A/N Vol 1 7.95
- NSC Linear A/N Vol II 7.95
- NSC CMOS 2.95
- NSC Audio 2.95
- NSC Voltage Reg 2.95
- NSC Memory 3.95
- Intel Data Book 3.95
- Intel MCS 85 Manual 4.95
- Intel MCS 80 Manual 7.95
- Intel MCS 40 Manual 4.95
- AMD 8080 Microproc Handbook 7.95
- AMI MOS Catalogue 3.95
- Raytheon Linear 2.50
- Raytheon Quads/Duals 1.95
- GI MOS Catalogue 4.95
- Osborne Intro to Micro Vol I 4.95
- Osborne Intro to Micro Vol II 7.50
- Osborne Intro to Micro Vol III 15.00
- Osborne 8080 Programming 7.50
- Osborne 6800 Programming 7.50
- Osborne 8080 Programming 7.50

AMI 6800 KIT EVK 99



only **\$133.00**

Send for complete details

- EVK 99 Kit \$133.00
- EVK 100 Kit 269.95
- EVK 200 Kit 449.95
- EVK 300 Assembled 699.00
- Universal Kluge Board 95.00
- 16K Byte RAM Board 75.00
- 6 Slot Motherboard 35.00
- Extender Board 45.00
- Video Board (avail. future) 95.00
- Connectors \$6.50 12/59.95
- Solid Frame Chassis 120.00
- Frame Chassis 69.95
- Micro Assembler ROM 30.00
- Proto ROM 30.00
- Tiny Basic Paper tape 20.00
- Tiny Basic EPROM 125.00

Hardware or Programming Manuals 15.00 ea

8080A CPU KIT \$99.95

Assembled & tested \$129.95

FEATURES:

S-100 bus compatible, complete CPU with eight level vector interrupt. Includes sockets. Add \$5.00 for 8080 Manual

16K SUPERFAST RAM'S

µp D 416/4116 350ns. PRIME
 Buy 8 pcs. - Only **\$29.95 each**
 Buy 16 pcs. - Only **\$27.95 each**
 Larger quantity or group buys call for current price quote

TARBELL FLOPPY INTERFACE

Complete Kit Only **\$179.95**
 Assembled & tested **\$269.95**

FEATURES: S100/Altair/IMSAI compatible, compatible to most disc drives including Persci, Innovex, GSI, Shugart and others.

SOFTWARE: Uses CPM which is available for \$70.00 CPM documentation add \$20.00
Same Day Shipment

NAKED PC BOARD SALE S-100

- Z-80 CPU \$31.95
- 2708 EPROM 8K 21.95
- 8K Static RAM 21.95
- 32K Static RAM 59.95
- Floppy I/O \$39.95
- Cassette I/O 29.95
- Proto Bd. 27.95
- Extender 15.95

UV "EPROM" ERASER

Model UVS-11E only **\$59.95**
 Holds (4) chips at a time. Special holding tray with UV-A Absorber. Exclusive safety interlock system. Backed by 45 years UV experience.

WOW 1771 FLOPPY SPECIAL

While they last **\$32.95**
 regular price \$55.95
 Western digital P/N 1771A with App. Note & Data
 Only 100 units available

MICROPROCESSORS

- Z 80 \$21.95
- Z 80A 29.95
- 80C01 19.95
- 80C02 29.95
- 80C03 19.95
- 80C04 12.95
- 80C05 12.95
- 80C06 14.95
- 80C07 21.95
- 80C08 29.95
- 80C09 49.95
- 80C10 79.95
- 80C11 19.95
- 80C12 29.95
- 80C13 29.95
- 80C14 19.95
- 80C15 19.95

SUPPORT DEVICES

- 3881 (Z80 PIO) \$12.95
- 3882 (Z80 CTC) 12.95
- 3883 (Z80 Program) 14.95
- 3884 (Z80 Memory I/O) 14.95
- 8217 8 bit I/O 3.50
- 8218 Priority Interrupt 3.95
- 8219 Bus Driver 2.25
- 8224 Clock Gen. 4.85
- 8224 & 4MHz CLK Gen. 12.95
- 8255 PPI Bus Driver 14.95
- 8255 Bus Driver 3.95
- 8228 Sys Controller 9.95
- 8253 8255 Prog. I/O 11.95
- 8253 Internal Timer 11.95
- 8255 DMA Control 12.95
- 8259 Prog. Interrupt 32.95
- 68011 128 x 8 RAM 7.95
- 6820 PIA 7.95
- 6818 1 EPROM 4K 16.95
- 6819 8 EPROM 4K 16.95
- 6850 ACIA 9.95
- 6851 Serial Adapter 11.95
- 6852 8255 Bus Driver 11.95
- 6853 8255 Bus Driver 11.95
- 6817 1 MHz Clock OSC 26.95
- 6818 1 MHz Clock OSC 26.95
- 6819 1 MHz Clock OSC 26.95
- 6900 1 MHz Clock OSC 26.95

STATIC RAM HEADQUARTERS

Part No.	Capacity	Speed	Price
21102	1K	100ns	1.25
21104	2K	100ns	2.50
21106	4K	100ns	5.00
21108	8K	100ns	10.00
21110	16K	100ns	20.00
21112	32K	100ns	40.00
21114	64K	100ns	80.00
21116	128K	100ns	160.00
21118	256K	100ns	320.00
21120	512K	100ns	640.00
21122	1M	100ns	1280.00
21124	2M	100ns	2560.00
21126	4M	100ns	5120.00
21128	8M	100ns	10240.00
21130	16M	100ns	20480.00
21132	32M	100ns	40960.00
21134	64M	100ns	81920.00
21136	128M	100ns	163840.00
21138	256M	100ns	327680.00
21140	512M	100ns	655360.00
21142	1M	100ns	1310720.00
21144	2M	100ns	2621440.00
21146	4M	100ns	5242880.00
21148	8M	100ns	10485760.00
21150	16M	100ns	20971520.00
21152	32M	100ns	41943040.00
21154	64M	100ns	83886080.00
21156	128M	100ns	167772160.00
21158	256M	100ns	335544320.00
21160	512M	100ns	671088640.00
21162	1M	100ns	1342177280.00
21164	2M	100ns	2684354560.00
21166	4M	100ns	5368709120.00
21168	8M	100ns	10737418240.00
21170	16M	100ns	21474836480.00
21172	32M	100ns	42949672960.00
21174	64M	100ns	85899347840.00
21176	128M	100ns	171798695680.00
21178	256M	100ns	343597391360.00
21180	512M	100ns	687194782720.00
21182	1M	100ns	1374389565440.00
21184	2M	100ns	2748779130880.00
21186	4M	100ns	5497558261760.00
21188	8M	100ns	10995116523520.00
21190	16M	100ns	21990233047040.00
21192	32M	100ns	43980466094080.00
21194	64M	100ns	87960932188160.00
21196	128M	100ns	175921844376320.00
21198	256M	100ns	351843688752640.00
21200	512M	100ns	703687377505280.00
21202	1M	100ns	1407374755010560.00
21204	2M	100ns	2814749510021120.00
21206	4M	100ns	5629499020042240.00
21208	8M	100ns	11258998040084480.00
21210	16M	100ns	22517996080168960.00
21212	32M	100ns	45035992160337920.00
21214	64M	100ns	90071984320675840.00
21216	128M	100ns	180143968641351680.00
21218	256M	100ns	360287937282703360.00
21220	512M	100ns	720575874565406720.00
21222	1M	100ns	1441151749130813440.00
21224	2M	100ns	2882303498261626880.00
21226	4M	100ns	5764606996523253760.00
21228	8M	100ns	11529213993046507520.00
21230	16M	100ns	23058427986093015040.00
21232	32M	100ns	46116855972186030080.00
21234	64M	100ns	92233711944372060160.00
21236	128M	100ns	184467439888744120320.00
21238	256M	100ns	368934879777488240640.00
21240	512M	100ns	737869759554976481280.00
21242	1M	100ns	1475739519109952962560.00
21244	2M	100ns	2951479038219905925120.00
21246	4M	100ns	5902958076439811850240.00
21248	8M	100ns	11805916152879623700480.00
21250	16M	100ns	23611832305759247400960.00
21252	32M	100ns	47223664611518454801920.00
21254	64M	100ns	94447329223036909603840.00
21256	128M	100ns	188894658446073819207680.00
21258	256M	100ns	377789316892147638415360.00
21260	512M	100ns	755578633784295276830720.00
21262	1M	100ns	1511157267568590553661440.00
21264	2M	100ns	3022314535137181107222880.00
21266	4M	100ns	6044629070274362214445760.00
21268	8M	100ns	12089258140548724328891520.00
21270	16M	100ns	24178516281097446657783040.00
21272	32M	100ns	48357032562194893315566080.00
21274	64M	100ns	9671406512438978663113132160.00
21276	128M	100ns	19342813024877957326226264320.00
21278	256M	100ns	38685626049755914652452528640.00
21280	512M	100ns	77371252099511829304905057280.00
21282	1M	100ns	1547425041990236586098001045760.00
21284	2M	100ns	3094850083980473172196002091520.00
21286	4M	100ns	6189700167960946344392004183040.00
21288	8M	100ns	123794003359218926887840083

MOVING?

Don't miss a single copy of **Radio-Electronics**. Give us:

Six weeks' notice

Your old address and zip code

Your new address and zip code

ATTACH
LABEL
HERE

name (please print)

address

city state zip code

Mail to: Radio-Electronics
SUBSCRIPTION DEPT., P.O. BOX 2520,
BOULDER, COLO. 80322

DON'T MISS ANY

Get every single issue of Radio-Electronics delivered right to your door, and before it appears on the newsstand. Use this coupon and subscribe now.

Mail to: Radio-Electronics
SUBSCRIPTION DEPT., P.O. BOX 2520,
BOULDER, COLO. 80322

name (please print)

address

city state zip code

check offer preferred

1 Year—12 issues ONLY \$9.98

2 Years—24 issues SAVE MORE \$19.00
(You save \$5.00 over newsstand)

3 Years—36 issues GREATER SAVINGS \$27.00
(You save \$9.00 over newsstand prices)

Payment enclosed Bill Me

Check here if this is a new subscription

Check here if you are extending or renewing
your subscription

Extra Shipping: Canada \$3.00 per
year, all other countries \$5.00 per
year.

40D8


ADVERTISING INDEX

RADIO-ELECTRONICS does not assume any responsibility for errors that may appear in the index below.

Free Information Number Page

105	Ace Electronics	136
81.78	Active Electronics	147
61	ADVA Electronics	144
32	Advanced Computer Products	154
	Advance Electronics	22
14	Aidelco	110
108	American Technology	119
16	A P Products	16
	A T V Research	123
17	Avanti Research & Development...Cov IV	
51	Babylon Electronics	153
	Karel Barta	128
106	B & K Precision Dynascan	36
	C F R Associates	148
58	Chaney Electronics	138
92	Chemtronics	103
	C I E - Cleveland Institute of Electronics	18-21
	Command Productions	124
95	Communications Electronics	122
94	Computer Depot	98
	Contemporary Marketing	105
86	Continental Specialties	Cov.III
5	The Cooper Group Electronics Division	2
	C R E I - Div of McGraw Hill Continuing Education	54-57
	Dage Scientific Instruments	148
69	Davis Electronics	111
40	Delta Electronics	128
75	Delta Graph Electronics	94
	Devtronix Organ Products	128
64	Digi-Key	145
96	DRC Electronics	142
	DRI Industries	27
87	EICO	113
83	E & I Instruments	120
22	Electronic Discount Sales	150
73	Electronic Control Systems	122
56	Electronic Systems	134
	E M C - Electronic Measurements	122
19	Enterprise Development	120
70	Etco Electronics	137
	Fair Radio Sales	148
	Fidelity Sound	118
57,80	Fluke	114
88	Fordham Radio Supply	140
	Forest Belt	102
62,91	Formula International	135,142
7	Fuji-Svea	146
38	Godbout Electronics	138
82	GTE Sylvania-Consumer Renewal	32
21	Grantham College of Engineering	118
	Golden Enterprises	123
100	Heath	28-31,106-109,115
31	Hickok Electrical Instruments	116
71	Hobbi House	141
11	Indiana Home Study	114
	Information Unlimited	152
23	Integrated Circuits Unlimited	132
43	International Crystal	121
34,33	International Electronics	124,125
52,53,54	James Electronics	93,130,131
	J & E Electronics	148

29	J S & A National Sales Group	1
	Krystal Kits	148
	Lab Science	128
	Lakeside Industries	148
	Leader	87
	L M N Electronics	143
3		
74		
48	Mallory	23
85	Mckay Dymek	119
2	Meshna	124
12	Mountain West Alarm Supply	114
103	Montana Precision Measurements	95
35,9	National Camera	104,113
	National Technical Schools	88-91
47	New Tone Electronics	150
44	Netronics	111
	National Radio Institute (NRI)-Div. of McGraw Hill Continuing Education Center	8-11
15	O.K. Machine & Tool	24-25
97	Olson	138
59,60	Optoelectronics	129,133
4	Page Digital	140
20	PAIA	111
55	Panavise	118
77	Parasitic Engineering	112
30	Philips Test & Measuring Division	17
98	Platt Luggage	112
	Plus Electronics	148
49	Poly Paks	139
107	Pomona	101
27,28	Priority 1 Electronics	155,13
76	P T S Electronics	85
25	Quest	148
65	Radio Hut	126
	Radio Shack	151
46	Ramsey Electronics	152
79	RCA	96-97
45	Rye Industries	120
	Sabtronics	7
	J.B. Saunders	149
10	Schober Organ	113
72	SD Computer Products	127
66	Sencore	99
8	Shure Brothers	92
6	Simpson Electric	5
26	Solid State Sales	144
41	Solid State Time	123
24	Southwest Technical Products	15
36	Spacekom	26
39	Starshine	34
	Superscope	Cover 11
	Surplus Center	128
	Tab Books	35
13	Tarbell Electronics	128
18	Tasco	140
104	Texas Tuner Service	119
67	Trumbull	124
	Tri-Star	124
37		
90	Ungar - Div. of Eldon Industries	81
89	Vector	117
63	VIZ Mfg.	33
1	Wahl Clipper	97
42	Wersi Electronics	110
84	Western Data Systems	138
	West Side Electronics	148
68	Wolf Electronics	128

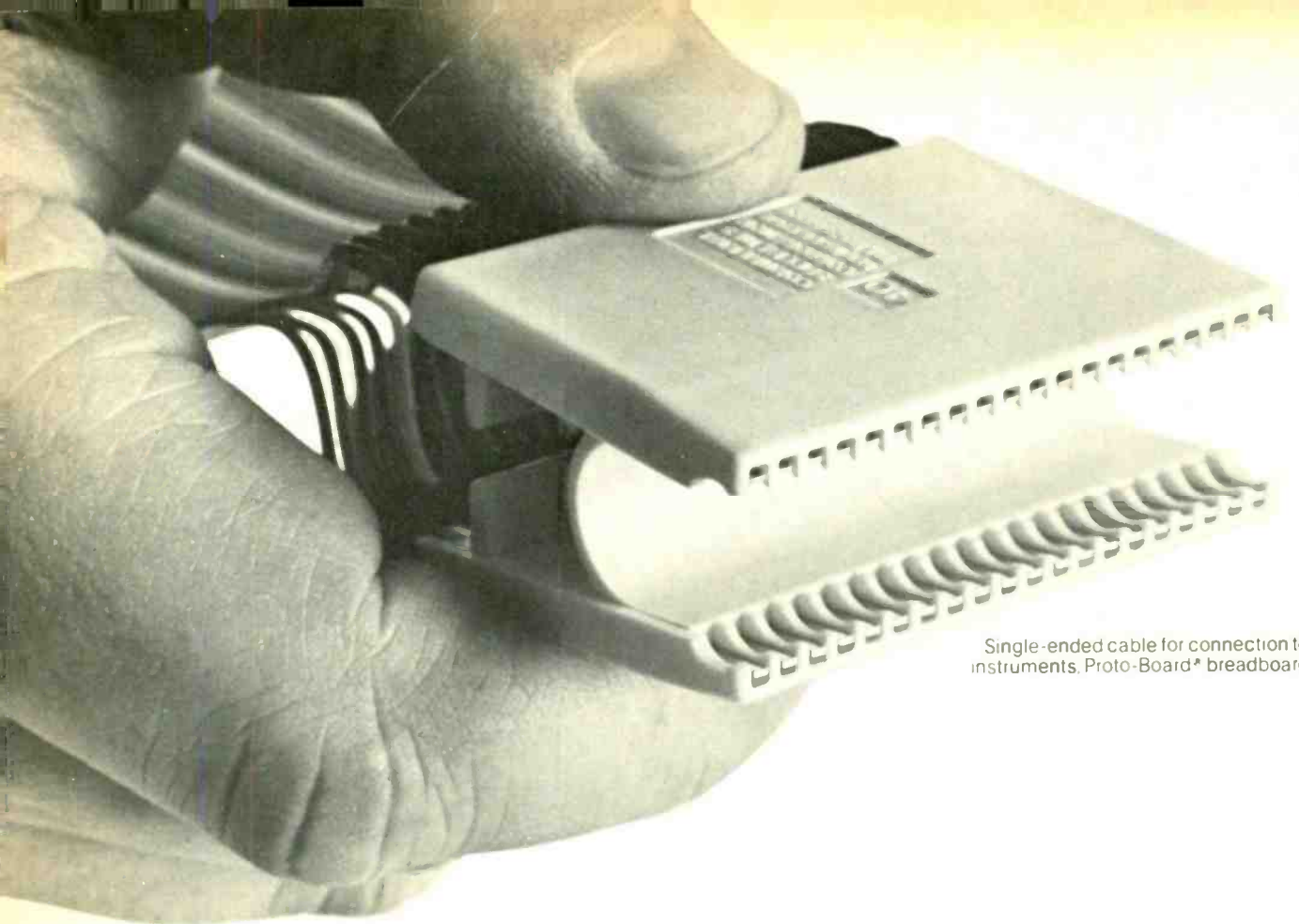

Single-ended cable for connection to test instruments, Proto-Board[®] breadboards, etc.

WHEN IT COMES TO DIP's, WE'VE GOT THE BEST CONNECTIONS.


With today's high-density packaging, one accidental short can wipe out an expensive IC, turning test procedures into painstaking manual labor. And minor problems into major repairs.

The answer? *DIP insurance*. Fast, fail-safe, short-proof access to DIP nodes. In other words, CSC's patented Proto-Clip[™] IC test connectors.

Proto-Clip IC test clips are available with easy-access top pins shaped to prevent hook-clip slip-off; or attached to one or both ends of color-coded cables. The double-ended cables make the job of patching-in



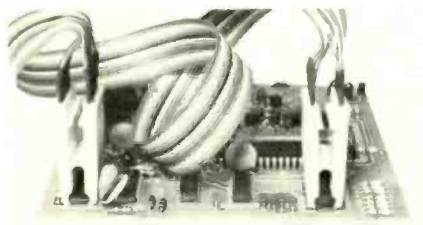Basic Proto-Clip[™] with no-slip terminals for use with hook clips or test probes.



Double-ended cable for convenient IC patching, bypassing, etc.

an IC, or getting to an unused logic block easier.

Order Proto-Clip connectors in 14, 16, 24, or 40-pin configurations, for all popular IC's. And single or double-ended connector/cable combinations in 18" and 36" lengths. Whatever sizes suit your needs, you'll find that in time and components saved, they'll pay for themselves the first time.

Order today. Call 203-624-3103 (East Coast) or 415-421-8872 (West Coast): 9 a.m.-5 p.m. local time. Major credit cards accepted. Or see your CSC dealer. Prices slightly higher outside USA."

CONTINENTAL SPECIALTIES CORPORATION



© 1978 Continental Specialties Corporation

70 Fulton Terrace, Box 1942, New Haven, CT. 06509, 203-624-3103 TWX 710-465-1227
WEST COAST: 351 California St., San Francisco, CA 94104, 415-421-8872 TWX 910-372-7992
GREAT BRITAIN: CSC UK LTD., Spur Road, North Feltham Trading Estate, Feltham, Middlesex, England, 01-890-8782 Int'l Telex. 851-881-3669
CANADA: Len Finkler Ltd., Ontario

CIRCLE 86 ON FREE INFORMATION CARD

AVANTI® ASTRO PLANE™ CB Base Antennas give you patented performance!

CO-INDUCTIVE design of this patented antenna gives long range, noise free performance.

The result of years of research & development, the ASTRO PLANE has top radiation which means that your signal gets out from the highest part of your antenna. Your signal radiates about 15 feet higher than with other antennas which radiate near the bottom.

The ASTRO PLANE has a lower angle of radiation which makes more efficient use of the radiated signal by allowing it to hug the curvature of the earth instead of shooting your power up into the sky.

The ASTRO PLANE has 4.46 db gain over isotropic which gives you a stronger signal and better, clearer reception.

You'll get long lasting, trouble free performance because it is compact in design — without long drooping radials, without coils to burn or short out, and with direct ground construction to help dissipate static charges and lightning.

- Stainless steel radials concentrate signal
- Rigid heavy-duty aluminum tubing
- No long drooping radials to ice up or break off
- So unique it's backed by a U.S. patent (Patent #3537109)
- No coils to burn out or detune
- Easy assembly
- Lightweight — easy to install on simple pipe mast



Ordinary collinear or ground plane antenna signals are blocked...they radiate from the bottom.



ASTRO PLANE gets its signal over obstacles...it radiates from the top.

SPECIFICATIONS

Total Length — 12 feet	Vertical Polarity
Weight — 4 lbs.	Aircraft Quality Aluminum
Power Gain — 4.46 db	SWR — Pre-tuned — Less
Impedance — 50-52 ohms	than 1.2:1
Omnidirectional — needs no rotor	band width — full 40 channels

high performance **CO-INDUCTIVE**™ antennas

Avanti makes a complete line of high performance mobile CB antennas and accessories. For free catalog, write:

N.A.S.A. PHOTO

avanti

creators of the
famous

MOONRAKER

AVANTI RESEARCH AND DEVELOPMENT, INC., 340 Stewart Avenue, Addison, IL 60101

CIRCLE 17 ON FREE INFORMATION CARD