

# BUILD THIS AUDIO EXPANDER




MARCH 1993

# Electronics NOW

Radio Combined with Electronics®
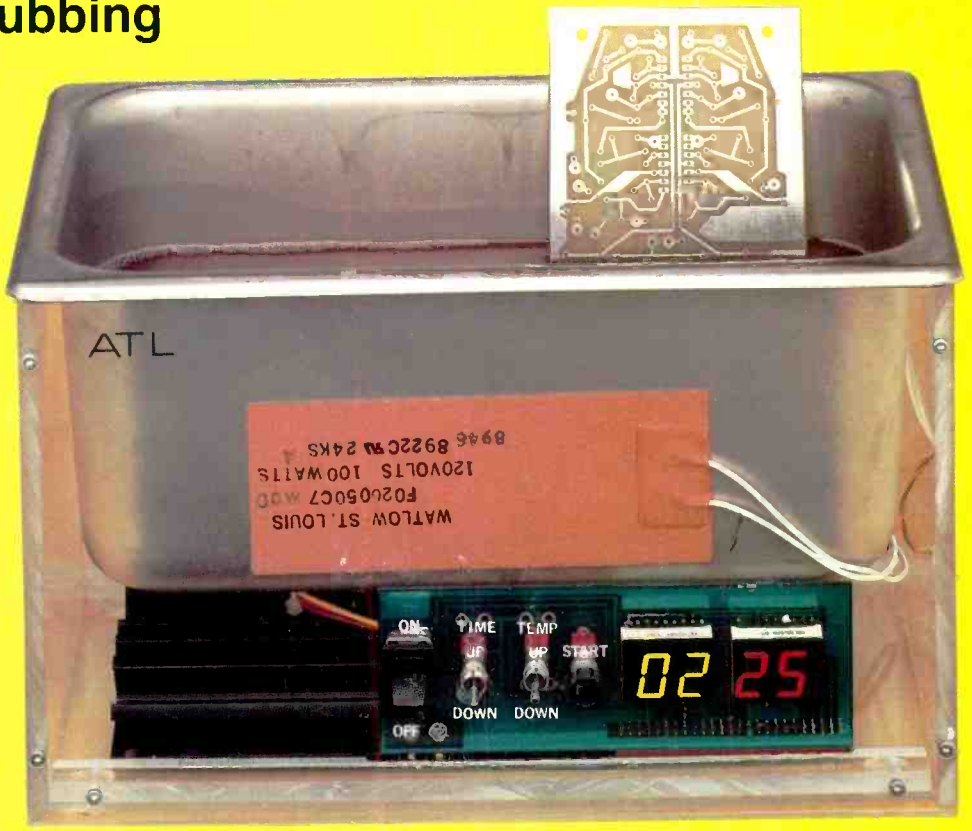
## BUILD THIS ULTRASONIC CLEANER

Put it to work scrubbing circuit boards, connectors, and even coins and jewelry!



## FIELD-EFFECT TRANSISTORS

FET principles, terminology, and circuits

## FORCE-SENSING RESISTORS

Learn how to put them to work!

## CAPACITORS

What they are, how they're made, and how they're used

- Plus: ★ Hardware Hacker
- ★ Audio Update
- ★ Video News
- ★ And Lots More!



\$3.50 U.S.  
\$3.95 CAN

A  
**GERNSBACK**  
PUBLICATION

# Multi-Choice.

Whether you're doing first-level troubleshooting or component-level diagnosis, Fluke meters offer you one of the widest choice of capabilities and price ranges in the industry. Choices ranging from the basic Fluke 12 with auto function V-Chek™ and Continuity Capture™. To the classic Fluke 77

with Auto Touch Hold® and current measurements. **Fluke 77**  
The classic  
Multimeter  
\$169.00

To the advanced Fluke 83 with Min/Max/Average recording,

Frequency, Duty Cycle and Input Alert™. Plus a full

line of quality accessories to extend those

capabilities even further. No matter which Fluke

meter you choose, you can count on precise, reliable, consistent performance year in and

year out. Plus, strong customer support and product warranties that measure up to any

in the industry. Make the choice

that gives you the most choices.

Look to Fluke

for the tools you need to get the job done right.

See your Fluke distributor, or call 1-800-87-FLUKE

for a catalog and the name of the

distributor nearest you.

**Fluke 12**  
Auto-function  
Multimeter  
\$89.95



**Fluke 83**  
Full-featured  
Multimeter  
\$255.00



**Fluke 77**  
The classic  
Multimeter  
\$169.00



**Fluke 12**  
Auto-function  
Multimeter  
\$89.95

FLUKE 12	FLUKE 77	FLUKE 83
The Fluke meters listed above feature DC/AC voltage, resistance, audible continuity and diode test.		
Capacitance measurements	Auto Touch Hold®	Auto Touch Hold® and Relative modes
V-Chek™ (auto function)	Current measurements	Current measurements
Min/Max Record with Relative Time Stamp	Analog/Digital display	Analog/Digital display
Two-year warranty	Three-year warranty	Three-year warranty
Continuity Capture™	Yellow holster with Flex Stand™	Yellow holster with Flex Stand™
Basic accuracy 0.9%	Basic accuracy 0.3%	Input Alert™
		Capacitance measurements
		Frequency and Duty Cycle
		Min/Max/Avg. Recording
		Basic Accuracy 0.3%

John Fluke Mfg. Co., Inc.  
P. O. Box 9090, Everett, WA 98206  
For more information call:  
(416) 890-7600 from Canada  
(206) 356-5500 from other countries

© Copyright 1992 John Fluke Mfg. Co., Inc. All rights reserved.  
Prices subject to change. Suggested U.S. list price.  
Ad No. 00276

**FLUKE**®  
CIRCLE 121 ON FREE INFORMATION CARD




## ON THE COVER



Delicate jewelry can be hard enough to clean. It's difficult to reach all the nooks and crannies using ordinary cleansers and cloths, and scrubbing with harsh abrasives can cause damage to fragile items. The same problems can be even worse when trying to clean tools, connectors, and parts. Ultrasonic cleaning has been a common solution in commercial and industrial applications, but factory-made ultrasonic

cleaners are beyond the budgets for small companies and hobbyists. Now you can build your own ultrasonic cleaner. It uses non-toxic, non-flammable cleaning solutions—and a bubbling action created by piezoelectric transducers—to get your jewelry, car and bicycle parts, card-edge connectors, circuit boards, tools and coins spic and span. Turn to page 33 for all the details on this professional-quality project.

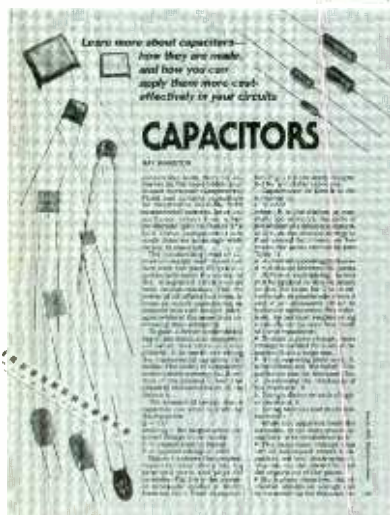

PAGE 57



PAGE 71



PAGE 65

As a service to readers, ELECTRONICS NOW publishes available plans or information relating to newsworthy products, techniques and scientific and technological developments. Because of possible variances in the quality and condition of materials and workmanship used by readers, ELECTRONICS NOW disclaims any responsibility for the safe and proper functioning of reader-built projects based upon or from plans or information published in this magazine.

Since some of the equipment and circuitry described in ELECTRONICS NOW may relate to or be covered by U.S. patents, ELECTRONICS NOW disclaims any liability for the infringement of such patents by the making, using, or selling of any such equipment or circuitry, and suggests that anyone interested in such projects consult a patent attorney.

ELECTRONICS NOW, (ISSN 0033-7862) March 1993. Published monthly by Gemsback Publications, Inc., 500-B Bi-County Boulevard, Farmingdale, NY 11735. Second-Class Postage paid at Farmingdale, NY and additional mailing offices. Second-Class mail registration No. R125166280, authorized at Toronto, Canada. One-year subscription rate U.S.A. and possessions \$19.97, Canada \$27.79 (includes G.S.T. Canadian Goods and Services Tax Registration No. R125166280), all other countries \$28.97. All subscription orders payable in U.S.A. funds only, via international postal money order or check drawn on a U.S.A. bank. Single copies \$3.50. © 1993 by Gemsback Publications, Inc. All rights reserved. Printed in U.S.A.

POSTMASTER: Please send address changes to ELECTRONICS NOW, Subscription Dept., Box 55115, Boulder, CO 80321-5115.

A stamped self-addressed envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

**PLEASE TURN PAGE FOR COMPLETE CONTENTS**

## BUILD THIS

- 33 ULTRASONIC CLEANER**  
Keep components, tools, and gadgets shiny clean!  
**Reinhard Metz**
- 69 TIME-DELAY RELAY**  
Turn off your appliances automatically and stop wasting power!  
**James Melton**
- 71 AUDIO EXPANDER**  
This inexpensive, one-chip device enhances stereo and mono audio.  
**Phill Hausman**
- 83 REMOTE-CONTROL TESTER**  
Make sure your remotes are working properly.  
**A. E. Plavcan**

## TECHNOLOGY

- 47 FIELD-EFFECT TRANSISTORS**  
Put JFET's, MOSFET's, and the rest to work in your designs.  
**Ray Marston**
- 57 CAPACITORS**  
Learn how they're made and how to apply them cost-effectively.  
**Ray Marston**
- 65 FORCE-SENSING RESISTORS**  
All about the "ultimate switch technology."  
**T. L. Petruzzelis**

## DEPARTMENTS

- |  |  |
|--|--|
| <b>6 VIDEO NEWS</b><br>What's new in this fast-changing field.<br><b>David Lachenbruch</b> | <b>85 AUDIO UPDATE</b><br>The Audio Answerman returns.<br><b>Larry Klein</b>               |
| <b>18 EQUIPMENT REPORT</b><br>B+K Precision Model 1686 Power Supply.                       | <b>87 DRAWING BOARD</b><br>Our descrambler is almost finished.<br><b>Robert Grossblatt</b> |
| <b>75 HARDWARE HACKER</b><br>Nichrome, resistance wire, and more.<br><b>Don Lancaster</b>  | <b>90 COMPUTER CONNECTIONS</b><br>The emerging PC.<br><b>Jeff Holtzman</b>                 |

## AND MORE

- |                                     |                        |
|-------------------------------------|------------------------|
| <b>98 Advertising Sales Offices</b> | <b>16 Letters</b>      |
| <b>98 Advertising Index</b>         | <b>22 New Lit</b>      |
| <b>93 Buyer's Mart</b>              | <b>24 New Products</b> |
|                                     | <b>12 Q&amp;A</b>      |
|                                     | <b>4 What's News</b>   |

# Electronics NOW®

Hugo Gernsback (1884-1967) founder

**Larry Steckler, EHF, CET,**  
editor-in-chief and publisher

### EDITORIAL DEPARTMENT

**Brian C. Fenton,** editor  
**Marc Splwak,** associate editor  
**Neil Sclater,** associate editor  
**Teri Scaduto,** assistant editor  
**Jeffrey K. Holtzman**  
computer editor  
**Robert Grossblatt,** circuits editor  
**Larry Klein,** audio editor  
**David Lachenbruch**  
contributing editor  
**Don Lancaster**  
contributing editor  
**Kathy Terenzi,** editorial assistant

### ART DEPARTMENT

**Andre Duzant,** art director  
**Injae Lee,** illustrator  
**Russell C. Truelson,** illustrator

### PRODUCTION DEPARTMENT

**Ruby M. Yee,** production director  
**Karen S. Brown**  
advertising production  
**Marcella Amoroso**  
production assistant  
**Lisa Rachowitz**  
editorial production

### CIRCULATION DEPARTMENT

**Jacqueline P. Cheeseboro**  
circulation director  
**Wendy Alanko**  
circulation analyst  
**Theresa Lombardo**  
circulation assistant  
**Michele Torrillo**  
reprint bookstore

Typography by Mates Graphics  
Cover photo by Diversified Photo Services.

Electronics Now is indexed in *Applied Science & Technology Index*, and *Readers Guide to Periodical Literature*, *Academic Abstracts*, and *Magazine Article Summaries*. Microfilm & Microfiche editions are available. Contact circulation department for details.

**Advertising Sales Offices listed on page 102.**

Electronics Now Executive and Administrative Offices  
**1-516-293-3000.**

Subscriber Customer Service:  
**1-800-288-0652.**

Order Entry for New Subscribers:  
**1-800-999-7139.**



Audit Bureau  
of Circulations  
Member





FFT and a scope for  
under \$3,000!

# Within budget. Without compromise.


The value of this 100 MHz scope is easy to see.

The HP 54600 gives you superior viewing of virtually any waveform, even at low rep rates and slow sweep speeds. It looks and feels like an analog scope, with dedicated knobs and a display that responds instantly to your control changes. And it has the digital power that analog can't give you — high accuracy, automatic measurements, hard copy output and programmability.

But what really stands out is that all this performance costs just **\$2,895** (4-channel) or **\$2,495** (2-channel)\*. What's more, now through April 30, 1993, you can add FFT by purchasing an HP 54657A or 54658A Measurement/Storage Module for only **\$375**.

**For more information, call HP DIRECT at 1-800-452-4844\*\* ext. TB28.** We'll be happy to send you literature or let you talk to an HP engineer.

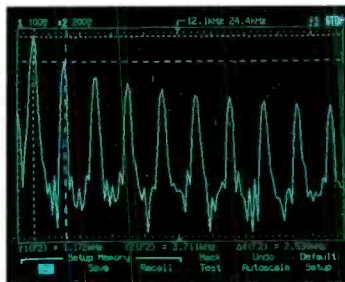\*U.S. list price  
\*\*In Canada call 1-800-387-3154, Dept. 435



*FFT is just one of the advanced waveform viewing tools you'll get with the HP 54657A/58A Measurement Storage Module.*

There is a better way.

©1992 Hewlett-Packard Co. TMCOL139/RE



**HEWLETT  
PACKARD**

CIRCLE 176 ON FREE INFORMATION CARD

# WHAT'S NEWS

*A review of the latest happenings in electronics.*

## **Personal communicator explosion seen**

Evidence from a number of sources points to the heating up of the handheld "personal communicator" market. As presently visualized, a personal communicator will be a box that includes the functions of a scratch pad, personal computer, electronic organizer, and, perhaps, a cellular telephone.

It is expected that the user will be able to write messages for storage on a screen with a pen, send those notes elsewhere, call up files of data and phone numbers, and even make phone calls—if the box has an integral cellular phone.

AT&T has been working hard to stake out a position in the communicator market. It has two axes to grind. It would like to sell its cellular communication services in that field, and it is seeking business for its own equipment manufacturing facilities. One way to assure that foothold is for AT&T to develop the standards that will be accepted by all other manufacturers and communications services providers.

So far, AT&T has forged alliances with several major electronics manufacturers, developed the "Hobbit" microprocessor chip for the units, and has stated its willingness to provide financial backing for suppliers and support software publishers.

Matsushita (Panasonic), NEC, and Toshiba have announced plans to build communicators based on AT&T's Hobbit microprocessor. AT&T is also negotiating a licensing agreement that would allow NEC to manufacture the Hobbit microprocessor. In addition, AT&T expects to sell its own brand of personal communicator, manufactured by Eo Computer, Inc. Mountain View, CA, a joint venture between AT&T, Matsushita, and Marubeni of Japan. It expects to sell the units through its national chain of AT&T Phone Centers.

AT&T is also working with Go Corp., whose PenPoint operating system is incorporated into the Eo-made products, to encourage the adoption of the operating system as an industry standard. Its plans include lining up more than a dozen software suppliers to write applications software that is compatible with the PenPoint software.

In another move, AT&T has designed the circuitry for a micro-miniature disk drive, and it is backing Sundisk, a company that makes a data-storage device for the communicators.

Apple has developed prototypes of a similar unit called the Newton, which it calls a "personal digital assistant" or PDA. Intel is reported to be working with VLSI Technology Inc. to develop a processor for the new units, and Motorola has signed investment and cross-technology agreements with both Apple and Sony.

## **Doubling digital video rate**

The possibility of doubling the amount of digital information that can be transmitted on cable TV channels, without additional video compression, is now a reality. Zenith Electronics of Glenview, IL, has developed vestigial sideband (VSB) digital modulation and transmission technology that makes it possible.

Zenith's 16-level digital transmission system can send two digital HDTV signals on a single 6-MHz cable channel. That doubles the number of digitally compressed standard TV signals on a cable channel, and permits the delivery of as many as 23 movie channels or nine live-video channels. An alternative mix of one HDTV and several standard TV programs is also a possibility.

According to Zenith, radio transmission of digital TV signals results in lower quality TV received signals than cable. Programs transmitted to

customers over cable are less likely to be distorted and suffer from interference. Signals in cables have better peak carrier-to-noise ratios and lower levels of interference.

Zenith took advantage of the greater noise-margin of cable transmissions to increase the information-carrying capacity, or data rate, of cable. To increase the amount of digital data delivered through a 6-MHz channel, a cable system must maintain a high signal-to-noise ratio, and must acquire and lock in the carrier, clock, and synchronization information. This is difficult to accomplish with the advanced digital modulation techniques such as 16- and 64-QAM (quadrature amplitude modulation).

By contrast, Zenith's VSB digital modulation and transmission technology, uses auxiliary signals for acquisition and synchronization. The pilot carrier, not feasible in QAM systems, and a data-segment synch signal are both independent of the data.

Zenith's 4-VSB technology obtains a data rate of 21.5 megabytes per second for its "Digital Spectrum Compatible" HDTV (DSC-HDTV) system. The company's newly developed, 16-VSB approach, an extension of the 4-VSB system, yields twice the channel data rate, or 43 megabits per second, with no increase in data compression requirements.

The 16-VSB system obtains signal acquisition even when ghosts and impedance mismatches are present. The system has simple analog-to-digital conversion needs, and it does not require the more complex adaptive equalizer of the QAM systems. Therefore, 16-VSB is said to offer cost-effective, noise-free TV pictures and digital audio. Moreover, it is said to be compatible with existing computer, telephone, and other digital communications systems.  $\Omega$



# Electronic Paperbacks at Special Prices

**BP325—A CONCISE USER'S GUIDE TO WINDOWS 3.1 . . . . \$7.95.** Come to grips with Windows 3.1 in the shortest and most effective way. Learn how to manipulate Windows screens and DOS by Windows graphics interface. Master its word processor, Paintbrush and data base along with Notepad, Macro Recorder, PIF Editor, and Calculator.



**BP311—AN INTRODUCTION TO SCANNERS AND SCANNING . . . . \$7.95.** Radio scanners have opened a realm of exciting radio listening. Understand radio wave propagation, types of transmissions, antennas, band assignments—the straight dope on what to hear and where to hear it! Comes complete with index, glossary of important terminology.



**BP287—A REFERENCE GUIDE TO PRACTICAL ELECTRONICS TERMS . . . . \$8.95.** More than just a dictionary of practical electronics terms, the book goes a step further in getting down to fundamentals. A reference volume that can be read casually by a reader seeking knowledge.



**BP248—TEST EQUIPMENT CONSTRUCTION . . . . \$5.95.** Details construction of simple, inexpensive, but extremely useful test equipment. AF Gen, Test Bench Ampl, Audio Millivoltmeter, Transistor Tester and six more.



**BP267—HOW TO USE OSCILLOSCOPES AND OTHER TEST EQUIPMENT . . . . \$6.95.** Mastering the oscilloscope is not really too difficult. This book explains all the standard controls and functions. Other equipment is also described.



**BP265—MORE ADVANCED USES OF THE MULTIMETER . . . . \$5.95.** Use these techniques to test and analyze the performance of a variety of components. Also see how to build add-ons to extend multi-meter capabilities.



**BP256—INTRO TO LOUDSPEAKERS AND ENCLOSURE DESIGN . . . . \$5.95.** We explore the variety of enclosure and speaker designs in use today, so the reader can understand the principles involved.

**CMOS1—CMOS POCKET GUIDE 1 . . . . \$18.95.** Works like the TTL Guides but covers all commonly used CMOS standard devices. Six major sections. The first shows the device schematic. Next is a brief description of the component and is followed by full operating details. The fourth section lists major applications, while the 5th and 6th sections present essential data for that device and a list of the relevant manufacturers. The final two sections are a valuable cross-reference.



**BP299—PRACTICAL ELECTRONIC FILTERS . . . . \$6.95.** Presents a dozen filter-based practical projects with applications in and around the home or in the constructor's workshop. Complete construction details are included.



**BP249—MORE ADVANCED TEST EQUIPMENT CONSTRUCTION . . . . \$6.95.** Eleven more test equipment construction projects. They include a digital voltmeter, capacitance meter, current tracer, etc.




**BP245—DIGITAL AUDIO PROJECTS . . . . \$5.95.** Practical circuits to build and experiment with. Includes A/D converter, input amplifier, digital delay line, compander, echo effect and more.



**BP247—MORE ADVANCED MIDI PROJECTS . . . . \$5.95.** Circuits included are a MIDI indicator, THRU box, merge unit, code generator, pedal, programmer, channelizer, and analyzer.



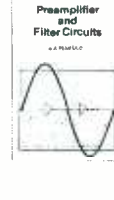**BP257—INTRO TO AMATEUR RADIO . . . . \$6.95.** Amateur Radio is a unique and fascinating hobby. This book gives the newcomer a comprehensive and easy to understand guide to the subject.



**BP309—PREAMPLIFIER AND FILTER CIRCUITS . . . . \$6.95.** Provides circuits and background info for a range of preamplifiers, plus tone controls, filters, mixers and more. All are high-performance circuits that can be built at a reasonable cost.

**BP303—UNDERSTANDING PC SOFTWARE . . . . \$6.95.** This book will help you understand the basics of various types of business software in common use. Types of software covered include word processors, spelling checkers, graphics programs, desktop publishing, databases, spreadsheets and utilities.



**BP251—COMPUTER HOBBYISTS HANDBOOK . . . . \$8.95.** A wrapup of everything the computer hobbyist needs to know in one easy to use volume. Provides a range of useful reference material in a single source.



**PCP115—ELECTRONIC PROJECTS FOR HOME SECURITY . . . . \$10.00.** 25 projects ranging from a single-door protection circuit that can be completed in an hour or two, to a sophisticated multi-channel security system. Each project is described in detail with circuit diagrams, explanations of how it works, instructions for building and testing, and how to adapt circuits to meet special requirements.



**BP190—ADVANCED ELECTRONIC SECURITY PROJECTS . . . . \$5.95.** Includes a passive infra-red detector, a fiber-optic loop alarm, computer-based alarms and an unusual form of ultrasonic intruder detector.

**BP235—POWER SELECTOR GUIDE . . . . \$10.00** Complete guide to semiconductor power devices. More than 1000 power handling devices are included. They are tabulated in alpha-numeric sequence, by technical specs Includes power diodes, Thyristors, Triacs, Power Transistors and FET's.

**BP234—TRANSISTOR SELECTOR GUIDE . . . . \$10.00.** Companion volume to BP235. Book covers more than 1400 JEDEC, JIS, and brand-specific devices. Also contains listing by case type, and electronic parameters. Includes Darlingtons transistors, high-voltage devices, high-current devices, high power devices.

**BP117—PRACTICAL ELECTRONIC BUILDING BLOCKS—Book 1 . . . . \$5.75.** Oscillators, Timers, Noise Generators, Rectifiers, Comparators, Triggers and more.

**BP195—INTRODUCTION TO SATELLITE TV . . . . \$9.95.** A definitive introduction to the subject written for the professional engineer, electronics enthusiast, or others who want to know more before they buy. 8 x 10 in.

**BP179—ELECTRONIC CIRCUITS FOR THE COMPUTER CONTROL OF ROBOTS . . . . \$7.50.** Data and circuits for interfacing the computer to the robot's motors and sensors

**BP239—GETTING THE MOST FROM YOUR MULTIMETER . . . . \$5.95.** Covers basics of analog and digital meters. Methods of component testing includes transistors, thyristors, resistors, capacitors and other active and passive devices.

**BP97—IC PROJECTS FOR BEGINNERS . . . . \$5.50.** Power supplies, radio and audio circuits, oscillators, timers, switches, and more. If you can use a soldering iron you can build these devices.

**RADIO—100 RADIO HOOKUPS . . . . \$3.00.** Reprint of 1924 booklet presents radio circuits of the era including regenerative, neutrodyne, reflex & more.

**BP42—SIMPLE LED CIRCUITS . . . . \$5.50.** A large selection of simple applications for this simple electronic component.

**BP122—AUDIO AMPLIFIER CONSTRUCTION . . . . \$5.75.** Construction details for preamps and power amplifiers up through a 100-watt DC-coupled FET amplifier.

**BP92—CRYSTAL SET CONSTRUCTION . . . . \$5.50.** Everything you need to know about building crystal radio receivers.

**BP255—INTERNATIONAL RADIO STATIONS GUIDE . . . . \$7.95.** Provides the casual listener, amateur radio DXer and the professional radio monitor with an essential reference work designed to guide him or her around the more than ever complex radio bands.

## CHECK OFF THE BOOKS YOU WANT

**ELECTRONIC TECHNOLOGY TODAY INC.**  
P.O. Box 240, Massapequa Park, NY 11762-0240

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

EN393

### SHIPPING CHARGES IN USA AND CANADA

\$0.01 to \$5.00 . . . . .	\$1.50
\$5.01 to \$10.00 . . . . .	\$2.50
\$10.01 to 20.00 . . . . .	\$3.50
\$20.01 to 30.00 . . . . .	\$4.50
\$30.01 to 40.00 . . . . .	\$5.50
\$40.01 to 50.00 . . . . .	\$6.50
\$50.01 and above . . . . .	\$8.00

**SORRY No orders accepted outside of USA & Canada**

Number of books ordered

Total price of merchandise . . . . .	\$ _____
Shipping (see chart at left) . . . . .	\$ _____
<b>Subtotal</b> . . . . .	\$ _____
Sales Tax (NY State only) . . . . .	\$ _____
<b>Total Enclosed</b> . . . . .	\$ _____

**All payments must be in U.S. funds**

# VIDEO NEWS

What's new in the fast-changing video industry.

DAVID LACHENBRUCH

● **HDTV costs.** No matter which of the five proposed HDTV systems is chosen, receiver costs are expected to be about the same. That's the conclusion of a report made to the FCC Advisory Committee on Advanced TV Service, detailing the most complete study of receiver costs made to date. The Specialist Group on Advanced TV Receiver Cost, consisting of representatives of all HDTV system proponents and engineers from receiver-manufacturing companies, found that by 1998 (which was assumed to be the first year of true mass production) the average HDTV receiver with a 34-inch widescreen (16:9) tube could retail for about \$2550 and a 56-inch projection set could sell at around \$3850.

These findings are interesting in view of the fact that the first two widescreen (non-HDTV) sets to be announced for the American market—a 34-inch tube set under the RCA brand and a 50-inch projector by Panasonic—both will carry suggested list prices of \$4999.

The HDTV cost study group found that no proposed HDTV system had a significant cost advantage as far as receivers are concerned. Electronics in 34-inch sets varied from \$216 to \$258 in cost, and for projectors from \$305 to \$374. Cabinet cost of all 34-inch sets was estimated at \$90, and for projectors at \$140. The tube price was put at \$700; projection optics, tubes, screen, and assembly at \$1050. Retail prices were estimated by adding the normal 2.5 multiplier for various markups.

The specialist group threw cold water on those counting on new giant picture-on-the-wall displays to replace CRT-based systems. "The cost of future displays with various flat panel technologies and light-valve projectors could not be estimated with any degree of accuracy, because no such displays appear

ready for consumer HDTV at this time," the report stated. "Therefore direct-view CRT and projector technology were assumed to be the most cost-effective displays for the time frame of this analysis."

● **8mm/VHS VCR.** Something that home videographers have been wishing for is on the way. In Japan, Sony has introduced a dual-deck VCR that can edit from 8mm to VHS and vice versa. Both decks have high-end features such as stereo audio and capability of accommodating high-band recordings (Hi8 and S-VHS), but in standard resolution only. Included are several editing features, including jog/shuttle controls. Presumably frightened by the blustering talk of movie-industry association figures, who claim that dual decks are designed to infringe copyrights, Sony says that it has no plans to export the deck to America, but demand could convince it to change its mind.

Competition could do that as well. Go-Video, which introduced the first VHS-to-VHS dual deck to America, says that it will introduce an 8mm/VHS deck here at midyear. So does Samsung, which makes the dual decks for Go-Video.

● **CD-ROM movies.** How do you sell a multimedia system when the public doesn't know what multimedia is? Call it a movie machine. That's the formula that will be followed by Denon America, according to its president, Robert Heiblim. People aren't interested in buying something for which they have demonstrated no need and don't understand, Heiblim reasons. Denon is developing a CD-based multimedia system using Intel's Digital Video-Interactive (DVI) system. The most important need is to put regular non-interactive movies on the ROM discs first, according to Heiblim. Consumers know what movies are

and will buy videodisc machines that use little five-inch discs, as long as they are superior to existing laserdiscs, he predicts. When many of these CD movie machines are in place, then interactive programming can be inaugurated.

Denon says that its DVI system soon will have laserdisc quality, which is considered a prerequisite for consumer acceptance. Heiblim says that early multimedia consumer products must be marketed as "VTR's," which stands for "videotape replacements," because consumers won't put their money into unknown devices. He prefers to call Denon's system "something that plays movies and is also interactive."

● **Video goggles.** Two companies have demonstrated ski-mask-like contraptions that provide personal video pictures using LCD's. Sony displayed its "Visortron" system in Japan, using two small LCD's that are viewed through built-in lens systems. Since each eye views a separate picture, it's possible to display images in true 3-D. Sony says that it's exploring commercial uses for the product.

But another system, "Virtual Vision sport," was about to go into production at our press time. That system is based on the "heads-up" displays used in aircraft, and uses a single LCD and lens-mirror to display a picture that appears to be as large as 60 inches, 8 to 15 feet in front of the viewer. The picture is off to one side, so the user can perform other tasks while watching it.

The five-ounce wrap-around glasses, with a belt-packed TV tuner, battery, and jacks to connect a VCR, camcorder, or TV cable, will go on sale this spring at less than \$900, says its producer, Virtual Vision. An accessory will permit it to pick up wireless signals from the television. Ω



# HOME-WORK For Electronics

MADE IN  
U.S.A.



Here's PB-503-C. It has every feature that our famous PB-503 offers, but we added one more, portability. Work on your projects at the office or school, take it home at night... it's for the engineer or student who wish to take their lab with them. **Instrumentation**, including a function generator with continuously variable sine, square, triangle wave forms and TTL pulses. **Breadboards** with 8 logic probe circuits. And a **Triple**

**Power Supply** with fixed 5VDC, plus two variable outputs (+5 to +15VDC). Throw-in 8 TTL compatible LED indicators, switches, pulsers, potentiometers, audio experimentation speaker... plus a life-time guarantee on all breadboarding sockets! And, because it's portable you will always have everything you need right in front of you! PB-503-C, one super test station for under \$350! Order yours today!!



**FOR MORE INFORMATION  
CALL 1-800-572-1028**



**GLOBAL  
SPECIALTIES®**

CIRCLE 184 ON FREE INFORMATION CARD

Global Specialties®, 70 Fulton Terrace, New Haven, CT 06512  
Tele: 203-624-3103/Fax: 203-468-0060 · ©1990, Interplex Electronics  
All Global Specialties® breadboarding products are made in the U.S.A.  
Proto-Board is a registered trademark of Global Specialties® A033 an Interplex Industries company

[www.americanradiohistory.com](http://www.americanradiohistory.com)

# Other Schools The Best Computer At NRI, We Graduates Do

## Train With The Leader—NRI


Train with NRI and prepare for a high-paying position as a computer service technician, even a computer service business of your own! Regardless of your previous electronics background, you can succeed with NRI, the leader in career-building at-home electronics training for over 78 years. You begin with the basics, rapidly building on the fundamentals of electronics to master today's advanced microcomputer concepts.

## Learn By Doing

NRI's highly acclaimed learn-by-doing approach gives you a complete understanding of the intricate electronics behind the 1 meg RAM, 32-bit CPU computer system included in your course.

You perform hands-on electronics experiments with your NRI Discovery Lab and digital multimeter, then build and test the powerful 486sx/25 MHz computer you train with and keep. You install the 1.2 meg, 5-1/4" floppy disk drive, learning disk drive operation and adjustment. Later, you dramatically improve your computer's data storage capacity by installing a powerful 80 meg IDE hard drive.

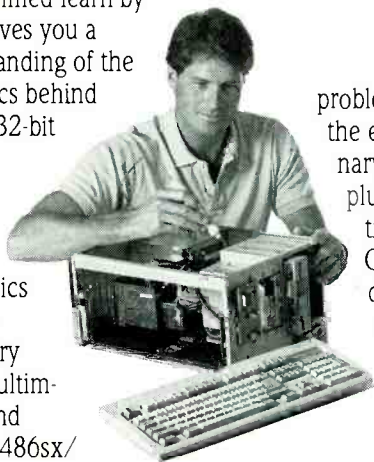You even learn to diagnose and service virtually any computer



R. Buda  
Tinley Park, IL

C. Bane  
Chicago, IL

problem with the extraordinary R.A.C.E.R. plug-in diagnostic card and QuickTech diagnostic software included in your course.

## Study At Your Own Pace

With NRI, you study in the privacy and convenience of your own home — with your personal instructor and NRI's team of technical professionals behind you every step of the way. You learn at your own pace — no classroom pressures, no night school, no need to quit your present job until you're ready to make your move. Step by step

V. Bender  
Calgary, Alberta

"I recommend NRI to anyone looking for a change, success, and REAL challenge. The Action Learning Kits allow you to build what you study — lessons — no better way exists to learn to troubleshoot and service computers!"

Just two years after finishing the NRI training in microcomputer servicing, I set up my own company. I contracted myself out to several computer retailers as their service technician. I have never regretted the NRI course and now have control and confidence in my business.

"A  
loo.  
rea.  
and  
the  
than  
know

"With four NRI courses under my belt, I've set up a workshop at home repairing everything from TVs to VCRs to appliances and now, computers! The computer I received in the micro course is a lifesaver in keeping track of my customers, invoicing, inventory of supplies, and personal finances. I have prospered financially as a result of my NRI training, owing to the income my small business generates — and to my regular salary increasing three times since completing the first NRI course!"

you're guided through the assembly of a powerful 486sx-based computer system — the centerpiece of your coursework — complete with monitor, floppy drive, 80 meg hard drive, operating and applications software. You get the hands-on experience you need to work with, troubleshoot, and service any IBM PC/AT-compatible computer, plus the confidence to tackle any service job you take on.





# Say They Offer Service Training... Let Our The Talking.

service business of your own — you'll be well prepared, continuously drawing on the real-world experience of your NRI training. Master electronics and computers the NRI way and master your future!

## Learn More About NRI Today

Let NRI hear from you next. Send today for NRI's free, full-color catalog which describes every aspect of NRI's innovative microcomputer training, as well as hands-on training in other growing high-tech fields. If the coupon is missing, write to NRI Schools, McGraw-Hill Continuing Education Center, 4401 Connecticut Avenue, NW, Washington, DC 20008.



N. Tenerelli, II  
Millington, IN

"No doubt, the excellent back-up of your staff was a significant factor in my swift completion of NRI's microcomputer servicing training. Their helpfulness, by phone or by letter, has been nothing short of amazing. I can see why you are so proud of your training. The thing I read in your catalog was

ough many technical training courses I've seen are almost 100% theory-oriented, NRI's hands-on approach is what a technician's ability to troubleshoot equipment is where 'the rubber meets the road.' As a result, NRI graduates are more prepared to handle any situation that may arise.

As a family man, a home study course was the only way to go. It has up to me to spend as much or as little time as I needed on course material — drawing down on the tough stuff and racing through the familiar. After completing NRI's microcomputer course, new doors began to open for me. I literally created the job I now hold and am considered 'the one to call' in the event someone needs help with computer hardware or programs.

J. Preusker  
Angston, SA Australia

D. Gattin  
Carrollton, GA

wide-open opportunity and become a high-paid computer service technician. Whether you choose a full- or part-time job — or start a computer

What's more, you work with today's most popular integrated software package, Microsoft Works, learning to use its word processing, spreadsheet, database, and communications utilities for your own personal and professional applications.

## Master Your Future

The Department of Labor forecasts over 220,000 jobs for computer service technicians by the year 2005 — a 38 percent increase over today's level. With the right training and skills, you can cash in on this

IBM is a registered trademark of International Business Machines Corp. R.A.C.E.R. and QuickTech are registered trademarks of Ultra-X, Inc.



## NRI Schools

McGraw-Hill Continuing Education Center  
4401 Connecticut Avenue, NW, Washington, DC 20008

For career courses approved under GI Bill,  check for details

- Check one FREE catalog only
- Microcomputer Servicing
  - TV/Video/Audio Servicing
  - Industrial Electronics & Robotics
  - Basic Electronics
  - Computer-Aided Drafting
  - Computer Programming
  - Desktop Publishing & Design
  - PC Applications Specialist
  - Programming in C++ with Windows

Name \_\_\_\_\_ (please print) Age \_\_\_\_\_

Address \_\_\_\_\_

City/State/Zip \_\_\_\_\_ Accredited Member, National Home Study Council 3-0393

Write to Q & A, Electronics Now, 500-B Bi-County Blvd., Farmingdale, NY 11735

## MONITOR BUG

**I have an IBM clone and use it with a monochrome monitor. The system has always been very reliable but recently I've been having trouble with the monitor. I'm not sure what's going on, but the symptoms are that the image flickers randomly. Sometimes it will be perfect for a while and then it will get brighter or darker in random spurts. If I turn the monitor off and then on again, the problem sometimes fixes itself for a while, but it's only a matter of time before the flickering returns. Any ideas?—B. Frish, Los Angeles, CA**

You may think of this as a computer problem but any experienced TV person will tell you that this is a simple problem with the clamping circuit on the video input. Most TV's use a combination of diodes and resistors to set the white and black levels to somewhere around a volt or so. Computer monitors do the same.

If you have access to the schematic for the monitor, it should be a fairly simple matter to fix it. All you have to do is locate the relevant part of the circuitry and then take a look at the DC levels with a white and black screen. You'll probably find that one of the diodes is intermittently failing. Changing the bad component is a quick job although it may take a bit of work—with a screwdriver—to get your hands on the component.

If you can't get the schematic for the monitor you can still snoop around with a scope or meter until you locate the clamping circuit. If this is the first time you've ever thought about doing something like this, my advice is to forget about it since there are some real knock-you-down voltages floating around the inside any TV or monitor.


Since the purpose of your letter

seems to be getting your computer working again, the best advice is to buy another monitor. You can get a monochrome monitor for under 80 bucks these days and they even come with warranties. If you don't want to scrap your old monitor, take the guts out of it and turn the case into a fish tank. That's what I did with mine!

## LIMITING LED CURRENT

**I'm building a circuit that has several LED's as indicators to let me know how the circuit is performing. Quite often more than one LED is on at a time, and since the circuit is battery powered, it causes a real power drain. All the LED's have one leg in common so I have no way to control individual brightness. Isn't there some simple circuit that will regulate and limit the current used by the LED's, no matter how many are lit?—W. Meredith, Elkins, WV**

I'm not really clear about why you can't use separate resistors on the LED's to individually limit the currents, but there is another way to solve the problem. The 78XX-series of voltage regulators have been around for a long time and are even available in special low-power configurations. If I had your problem I'd use whichever regulator was suitable and wire it as shown in Fig. 1.

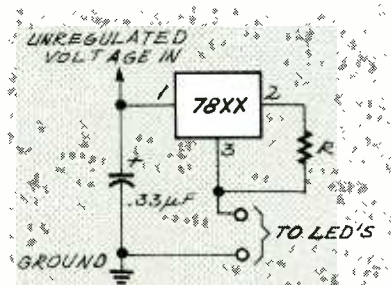

**FIG. 1—THE 78XX-SERIES of voltage regulators can be used in a configuration like this to limit current rather than voltage.**

You should tailor the value of the capacitor to the number of spikes on the line but, in general, the 0.33  $\mu$ F capacitor shown in the schematic should work well.

When you set up the regulator as shown, it works as a current regulator rather than a voltage regulator. The output current draw will be the regulated voltage divided by R. The only thing to watch out for is that you don't try to draw more current through the regulator than what it's rated for. But since you only want to drive a handful of LED's, I don't think you'll have any problems.

## ONLY HALF-WAY THERE

**I have a laser printer that I'm trying to use for printing graphics. The problem is that I can't seem to print more than half a page—the picture is incomplete and the bottom half of the paper is always blank. What's going on?—A. McChord, Ames, IO**

Laser printers produce terrific output, but it's amazing that, while so many people use them, so few really understand how they work. The major constraint in printing graphics with a laser printer is the amount of memory it has, and that seems to be your problem as well.

Copy machines and laser printers are very similar. The former uses an optical image as the source of its output and the latter uses an electronic image in memory for the source. If you want to print with 300-dpi (dot per inch) resolution, your printer will need enough memory to "take note" of the image. If there's not enough memory, the printer will print the page when it runs out of memory—which, in your case, is about halfway through the image.

You have two choices to solve the problem. The first is to add memory to the printer, and you'll need at least one and a half megabytes of RAM to do a 300-dpi full-page

*Continued on page 86*



# WHY CARRY ALL THESE?

# WHEN YOU CAN CARRY ALL-IN- ONE!



Meet the new **TEST BENCH®** DMMs, with more of what made the original a best seller.

B+K PRECISION's original TEST BENCH testers became overnight best sellers because they fused the power of many instruments in one compact meter. These new models also out-feature ordinary DMMs, and outperform them as well. All are ruggedized, offer long battery life and carry a three-year warranty.

With True RMS, 4½ digit, 20,000 counts and 0.05% DCV accuracy, the Model 391 is a **BEST BUY**.

Now you can have very high accuracy, extra resolution and True RMS reading at a very affordable price. The Model 391 Test Bench DMM also has frequency, logic, duty cycle and data hold. It's even water resistant.

There's a **TEST BENCH DMM** to fit every application and budget.

Choose from three, 3¾ digit TEST BENCH DMMs, starting with the Model 388A. All measure AC/DC voltage or current, ohms, frequency, logic levels and test components and continuity. The Models 389 and 390 add 41 segment bar graphs for smooth peak, null or level adjustments; Min/Max, memory and relative modes. The 390 also has a temperature probe.

So why carry an ordinary DMM, when you can grab a TEST BENCH! See your local distributor for immediate delivery.

MODEL	391	390	389	388A
% DCV ACCURACY	0.05	0.1	0.25	0.5
DISPLAY	4½ LCD	3¾ LCD	3¾ LCD	3¾ LCD
ANALOG BAR GRAPH		•	•	
CAPACITANCE		•	•	•
FREQUENCY	•	•	•	•
LOGIC LEVEL	•			•
TEMPERATURE		•		
RUGGEDIZED, RUBBER BOOT	•	•	•	•
PRICE	\$179	\$159	\$139	\$119



**BK PRECISION**

MAXTEC INTERNATIONAL CORP.  
Domestic and International Sales  
6470 W. Cortland St., Chicago, IL 60635  
312-889-1448 • FAX: 312-794-9740

CIRCLE 185 ON FREE INFORMATION CARD

[www.americanradiohistory.com](http://www.americanradiohistory.com)

Rest assured, no scope was injured in the making of this ad.

After all, the volunteer is a member of our new TAS 400 family of analog oscilloscopes. And every TAS has its entire acquisition system (including the vertical, horizontal and trigger functions for each input channel) housed on a proprietary hybrid circuit.



The result is a kind of scope on a chip.

One with 75% fewer parts and far greater reliability. In fact, the TAS is three times more reliable than previous scopes.

What's more,  
each and every  
TAS

**To demonstrate the value and durability of this amazing**



comes with smashing features like AutoSet, on-screen cursors and readout, dual timebases, and save and recall settings. Plus a unique user interface that makes the 60 MHz TAS 455 and 100 MHz TAS 465 easier to use and dramatically unlike any other analog scope.

A claim that is further backed up by their remarkably affordable price.

But then a lot of performance for not a lot of money is exactly what the TAS is all about.

Scopes that add to a long list of low-cost Tektronix products. Like our handheld 60 MHz 224



digitizing oscilloscope.



Our fully programmable,

analog/digital 2212 scope. And our family of affordable and



stackable basic test gear.

Now that's a lot to

drop on you in one ad. So to learn more

about these and other economical

Tektronix products, call your


authorized Tektronix distributor today.

Or call us at (800) 426-2200, ext. 140

to place your order or for the

name of the distributor

nearest you.

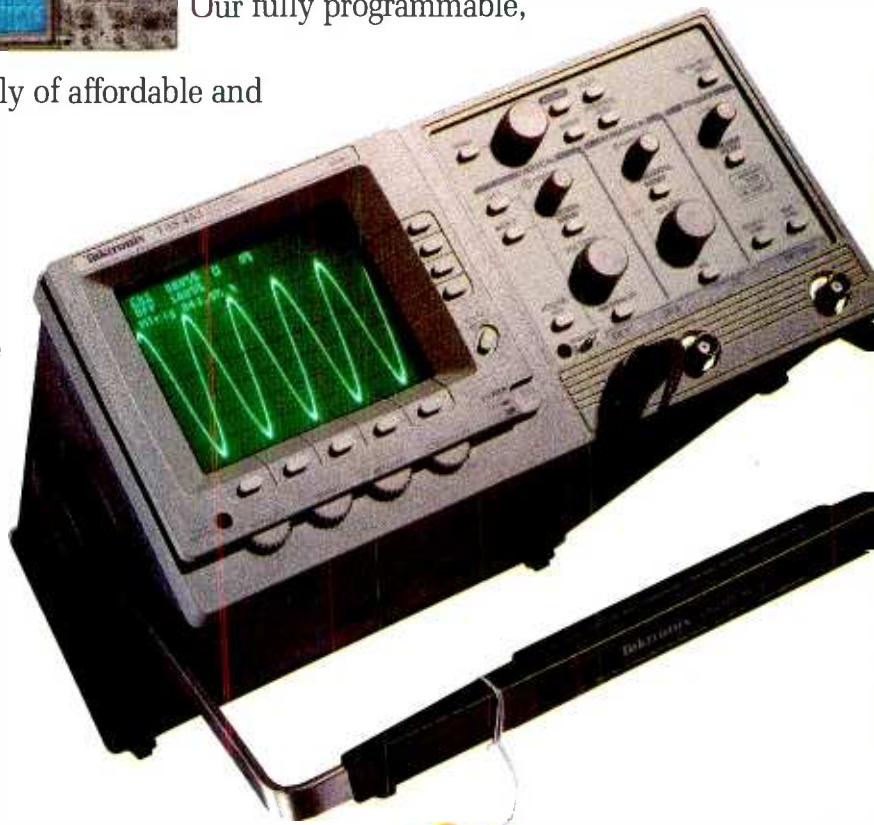

**new analog scope, we dropped it.**

**Tektronix**  
Test and Measurement

March 1993, Electronics Now

# LETTERS

Write to Letters, Electronics Now, 500-B Bi-County Blvd., Farmingdale, NY 11735

## INRUSH CURRENT LIMITER CORRECTIONS

There are two problems with the "Inrush Current Limiter" (*Electronics Now*, December 1992).

First, in Fig. 6 on page 49, the emitter of Q2 and the high end of R5 should be connected to the plus end of C2 (about 24 volts DC). As shown, the Darlington transistor, Q2, and possibly the relay, RY1 (24-volt DC coil) would burn out.

Second, the circuit is too complicated and oversized. I designed a much simpler circuit, shown here in Fig. 1 (a) and (b). The relay RY1 will not activate until the resistance of the NTC thermistor  $R_T$  drops low enough for the voltage across RY1 to reach about 80 volts (or whatever the activating voltage for the relay used might be). Resistor R1 might be added to slow down the action by effectively boosting the needed voltage.

Find the maximum resistance (of R1) with which the relay will activate when connected directly to 120 volts AC, and then use a resistor of about half that value. That resistor should be shorted out by another set of contacts of RY1. The effectiveness of the circuit can be seen by finding values of fuses at the just-blow threshold (or just not-blow) when the circuit is used and not used ( $R_T$  shorted out).

I cannot think of an instance when a delay of one second (or more), as stated in the article, would be needed. (If the capacitors in the power supplies need one second to recharge after a spike in the loading current, I would say that the circuit is in peril, and a major redesign of the power supply is needed.) Therefore, the circuit shown here should do the same job nicely.

PTER PESKA  
Taylor, MI

In addition to responding to Mr. Peska's comments, I would like to point out several errors that ap-

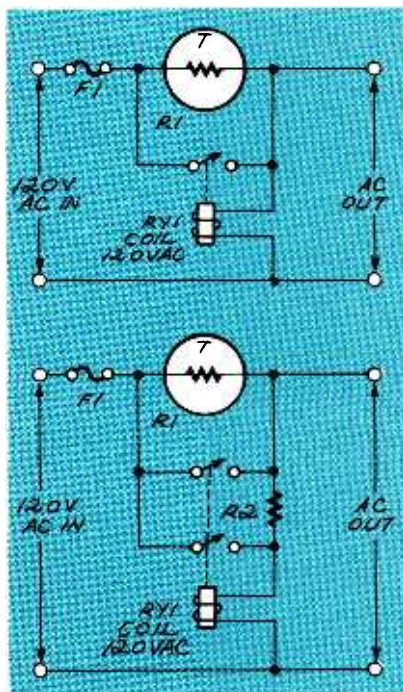


FIG. 1—TWO ALTERNATIVE INRUSH current-limiting circuits.

peared in the article. There is, indeed, an error in Fig. 6 on page 49. The emitter of Q2 and the high end of R5 should be connected to the positive end of C2 (i.e., the positive 24-volt supply). The parts placement diagram, Fig. 7, is correct.

In response to Mr. Peska's comment that the circuit is "too complicated," I'd like to point out that the circuit was designed with a line-derived regulated power supply for several reasons. The main reason to combine such a power supply and timer circuitry was to illustrate the concept of a transformerless line-derived, regulated power supply.

This circuit is popular in such commercial products as remote-controlled lamp/appliance controllers. Other advantages of the circuit are that it is independent of the load connected to it, and it features a predictable and easily adjustable time delay. Finally, the circuit is not that "complicated" in the first

place: It does not consist of many components, and it is easy to construct. I agree that Mr. Peska's circuit is much simpler and will work, but my project was designed for the reasons stated in the article.

My response to Mr. Peska's comment that a delay of more than one second is unnecessary is that the circuit allows for a wide range of delays by appropriate selection of a fixed resistor or by the use of a variable resistor. Delays of one second or less are easily obtained by choosing a suitable resistance (simply reduce the value of R4). Again, the wide range of time delays possible was given in Table 1 to illustrate the versatility of the circuit.

In the parts placement diagram (Fig. 7), resistor R8 should be labeled MOV1, R9 should be labeled R8, and R10 should be labeled R9 (there is no R10 in the circuit).

In the first sentence of the last paragraph on page 48, the sentence containing the phrase "shorts out thermistor R9" should read "shorts out thermistor R8."—Douglas Wirth

## AUDIO UPDATE COMPLAINT

Larry Klein's November *Audio Update* contains gross errors and unwarranted assumptions, and it is insulting to audiophiles and readers. For example: The "Hafler test" shown in Fig. 1 has a fatal error in that the amplifier is not evenly loaded. Changes in an amplifier's load usually alter the response of the system significantly, and this change would be included in the null speaker signal.

Klein assumes that a better amplifier will make a better system; this is not necessarily so. The equipment surrounding an amplifier will interact with the amplifier for better or worse, and this makes it difficult to judge an amplifier accurately without considering the related equipment. For this reason, respon-



sible reviewers list the equipment used with the unit under test.

Klein also ignores the fact that audiophiles have a wide range of music preferences that influence equipment purchasing decisions. I argue that one can objectively evaluate equipment, but must include other factors such as performance expectation and personal musical preference.

Klein fails to recognize that sophisticated listening skills take time and effort to develop into a useful tool for evaluating high-end audio equipment. I find his attitude typical of those whose hearing is undeveloped and whose experience seems to be the result of confiding in salesmen, listening to rumors, and "wannabe" experts. Klein's incompetence is so complete that he probably would even claim that CD's sound better than records, contrary to what is obvious. S.D.

Address withheld by request

Mr. Duncan's long letter (heavily condensed for space reasons) contains several technical and philosophical confusions—aside from being stupid and insulting. To start:

The Hafler circuit shown in Fig. 1 of my article connects the "null" speaker so it can compare only the input and output of the right channel, which is loaded with a conventional speaker. The resistance loading on the left channel output simply provides the input signal for the right channel.

If I understand Mr. Duncan correctly, he believes that it's more important to match the complementary defects of amplifiers and other equipment than to seek the best performance from each. Since well-designed power amplifiers—which were the subject of my article—are essentially audibly perfect within their power ratings, Mr. Duncan's mix-and-match approach is chasing a wild goose up a blind alley. Incidentally, the only "responsible" high-end reviewers that I know about write for *The Audio Critic*, mentioned last month.

As to my inexperience in critical listening, I became an avid audiophile in the early 1950's when hi-fi equipment first became available in the U.S. For five years I worked as

a technician for an electronics kit manufacturer, where I made tests, did repairs, and handled the technical correspondence on my employer's kits that included hi-fi kits. In the evenings and on weekends I "moonlighted" as a freelance hi-fi serviceman.

After being a technical editor at *Popular Electronics* for two years and a similar magazine for another two years, I became the technical editor of *Stereo Review*, where I was in charge of its equipment-testing program for about 20 years. During that time I auditioned countless products in my home and office listening room.

Moreover, I was invited to visit the test laboratories and factories of audio equipment manufacturers in England, Germany, Japan, Denmark, Hungary, Austria, Canada, and the U.S. during that 20-year period. At all those locations I was asked to evaluate the sound of their products (mostly loudspeakers), and I frequently was able to validate my responses against objective test data.

I do not "confide" in salesmen, rumor/mongers, and "wannabes." However, I know many product engineers and audio researchers—and guess what—most of them agree with me that, in general, CD's do sound better than LP's—if only for their superior signal-to-noise ratio.

It's always good to hear from a fan.—Larry Klein

#### AN AUDIO/VIDEO-PHILE

I recently discovered *Electronics Now*, checked out every back issue from my public library branch, and spent many rewarding hours reading each one from cover to cover. I can't follow everything yet, but I expect that will come with time.

On a general note, I enjoyed Larry Klein's debunking of some of those outrageous claims from audiophiles. I now have an authority to quote when I say that I cannot discern any significant difference between my \$5000 equipment and the \$20,000 worth of equipment that is supposedly being installed in average 18 × 15-foot American living rooms.

I haven't seen one subjective au-  
*continued on page 70*

## Earn Your B.S. Degree in ELECTRONICS or COMPUTERS



### By Studying at Home

Grantham College of Engineering, now in our 43rd year, is highly experienced in "distance education"—teaching by correspondence—through printed materials, computer materials, fax, and phone.

No commuting to class. Study at your own pace, while continuing on your present job. Learn from easy-to-understand but complete and thorough lesson materials, with additional help from our instructors.

Our Computer B.S. Degree Program includes courses in BASIC, PASCAL and C languages — as well as Assembly Language, MS DOS, CADD, Robotics, and much more.

Our Electronics B.S. Degree Program includes courses in Solid-State Circuit Analysis and Design, Control Systems, Analog/Digital Communications, Microwave Engr, and much more.

An important part of being prepared to *move up* is holding the right college degree, and the absolutely necessary part is knowing your field. Grantham can help you both ways—to learn more and to earn your degree in the process.

Write or phone for our free catalog. Toll free, 1-800-955-2527, or see mailing address below.

Accredited by  
the Accrediting Commission of the  
National Home Study Council

**GRANTHAM**  
**College of Engineering**  
Grantham College Road  
Slidell, LA 70460

# EQUIPMENT REPORTS

## B + K Precision Model 1686 DC Power Supply

Power your 12-volt equipment with this rugged supply.

CIRCLE 10 ON FREE INFORMATION CARD



**W**hether powering a prototype circuit or providing power for equipment being serviced, the bench-top DC power supply is an essential tool for anyone in the electronics industry. It's also essential for any anyone who plays an active role as an electronics hobbyist. B + K Precision (6470 W. Cortland St., Chicago, IL 60635) has recently introduced the *Model 1626*, a supply that is ideal for powering equipment rated at 12 volts.

The *1686* can deliver an output from 3 volts to 14 volts DC with a maximum current of 12 amperes. That high current rating is sufficient to power most car stereo systems, even those with high-power amplifiers. Most mobile amateur radio equipment, as well as CB transceivers, marine radios, and other high-current automotive accessories can be powered safely from the *1686*.

The maximum output current available from the power supply is proportional to the output voltage. When the supply is set to deliver 13.8 volts—which is the operating voltage for most equipment nominally rated at 12 volts—the *1686* can deliver 12 amperes continuously to the load. That drops to 10 amperes at 12 volts, 4.5 amperes at 5 volts, and 2.5 amperes at 3 volts.

At all voltage settings, the specified load regulation is less than 0.8%. That is, regardless of the load

at the output terminals, the supply's output voltage will deviate less than 0.8% from its initial setting. The line regulation of the supply is also rated at 0.8% from 108–132 volts AC. That means that regardless of the change in the line voltage to which the supply is connected, the output voltage will deviate less than 0.8%. The ripple and noise is specified at less than 10 millivolts rms. Overload current limiting provides protection against excessive overload or short-circuit output.

The *1686* is housed in a black metal cabinet that measures about 5½ × 6 × 12 inches; it weighs just over 12 pounds. The front panel features a pair of easy-to-read analog meters along the top edge, one for voltage and the other for current—that provide an indication of what the supply is doing at a glance. To the right of the meters is a rotary knob that controls the output voltage. The bottom half of the panel contains two sets of output connectors, a power switch, and two LED indicators.

The main voltage-output is provided on a set of binding posts. Two sets of spring-loaded terminals—much like the kind commonly found on audio speakers—are provided for connecting low-current loads. The tie points can supply a maximum of 2 amperes. Above the power toggle switch is an LED that serves as a power-on indicator. Above that is an LED that indicates

that the supply is in an overload condition and has reduced its output voltage.

The rear panel contains a fuse holder and a small fan. The fan, which helps to keep the supply compact by reducing the size of the heatsinks needed, does not run constantly. Rather, it is controlled by a thermostat, and comes on only when the internal temperature of the supply is too high for safe operation.

The outputs of the supply are isolated from the chassis and earth grounds, which is essential for flexibility in connections. If required, for example, the positive output can be connected to ground for powering positive-ground automotive equipment.

The isolated outputs also allow multiple supplies to be connected together in series or parallel for powering equipment that has higher voltage and current requirements. For example, connecting two supplies in parallel will provide a continuous source of 24 amperes, while connecting two supplies in series will provide an adjustable 6 to 28-volt power supply.

The model *1686* can operate from either 120-volt or 230-volt AC power lines with frequencies of 50 or 60 hertz. A slide switch on the bottom of the chassis permits easy selection.

We found the operation of the model *1686* to be quite straightforward. The manual supplied with the supply was more than adequate, and we were happy to find that calibration instructions were included there.

B + K Precision has priced its model *1686* at \$199. We think that the supply is ideal for service shops that regularly repair mobile equipment, as well as for retailers who need to power equipment on display. Of course, radio amateurs will also appreciate the 12-ampere continuous duty rating.  $\Omega$



# Graduate as a Fully Trained Electronics Professional!

If you want to learn about electronics, and earn a good income with that knowledge, then CIE is the best educational value you can receive.

CIE's reputation as the world leader in home study electronics is based solely on the success of our graduates. And we've earned our reputation with an unconditional commitment to provide our students with the very best electronics training.

Just ask any of the 150,000-plus graduates of the Cleveland Institute of Electronics who are working in high-paying positions with aerospace, computer, medical, automotive and communications firms throughout the world.

They'll tell you success didn't come easy...but it did come...thanks to their CIE training. And today, a career in electronics offers more rewards than ever before.

## CIE'S COMMITTED TO BEING THE BEST...IN ONE AREA...ELECTRONICS.

CIE isn't another be-everything-to-everyone school. CIE teaches only one subject and we believe we're the best at what we do. Also, CIE is accredited by the National Home Study Council. And with more than 1,000 graduates each year, we're the

largest home study school specializing exclusively in electronics. CIE has been training career-minded students like yourself for nearly sixty years and we're the best at our subject...ELECTRONICS...BECAUSE IT'S THE ONLY SUBJECT WE TEACH!

## CIE PROVIDES A LEARNING METHOD SO GOOD IT'S PATENTED.

CIE's AUTO-PROGRAMMED® lessons are a proven learning method for building valuable electronics career skills. Each lesson is designed to take you step-by-step and principle-by-principle. And while all of CIE lessons are designed for independent study, CIE's instructors are personally available to assist you with just a toll free call. The result is practical training...the kind of experience you can put to work in today's marketplace.

## LEARN BY DOING..WITH STATE-OF-THE-ART EQUIPMENT AND TRAINING.

CIE pioneered the first Electronics Laboratory Course and the first Microprocessor Course. Today, no other home study school can match CIE's state-of-the-art equipment and

training. And all your laboratory equipment, books and lessons are included in your tuition. It's all yours to use while you study and for on-the-job after you graduate.

## PERSONALIZED TRAINING...TO MATCH YOUR BACKGROUND.

While some of our students have a working knowledge of electronics others are just starting out. That's why CIE has developed twelve career courses and an A.A.S. Degree program to choose from. So, even if you're not sure which electronics career is best for you, CIE can get you started with core lessons applicable to all areas in electronics. And every CIE Course earns credit towards the completion of your Associate in Applied Science Degree. So you can work toward your degree in stages or as fast as you wish. In fact, CIE is the only school that actually rewards you for fast study, which can save you money.

## SEND FOR YOUR CIE COURSE CATALOG AND WE'LL SEND YOU A FREE 24-PAGE CIE ELECTRONIC SYMBOLS HANDBOOK.



electronics

# FREE!

SEND FOR YOUR CIE HOME STUDY COURSE CATALOG AND RECEIVE A FREE 24 PAGE CIE ELECTRONIC SYMBOLS HANDBOOK!

Includes hundreds of the most frequently used electronic symbols. Published exclusively by CIE for our students and alumni. Yours free when you request a CIE Course Catalog.



**YES!** I want to get started. Send me my CIE course catalog including details about the Associate Degree Program. (For your convenience, CIE will have a representative contact you - there is no obligation.)

AE48

Please print clearly

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_

Zip \_\_\_\_\_ Age \_\_\_\_\_

Phone No. (\_\_\_\_) \_\_\_\_\_

Check box for G.I. Bill Benefits

Veteran  Active Duty

**CIE** 1776 East 17th Street  
Cleveland, Ohio 44114

A School of Thousands.  
A Class of One. Since 1934.

# NEW LIT

Use The Free Information Card for fast response.

**Understanding Digital Troubleshooting: Third Edition;** by Don L. Cannon. Sams, Division of Macmillan Computer Publishing, 11711 North College, Carmel, IN 46032; Phone: 800-428-5331 or 317-573-2500; Fax: 800-448-3804 or 317-573-2655; \$24.95.

Digital systems must be effectively maintained if they are to operate reliably at peak performance levels. That is the central theme of Don Cannon's book on troubleshooting digital electronics. Mixing general tutorial information with "how to" instruction, the book is intended to help readers keep their digital circuits operating prop-


erly "in the pink."

Intended for readers with a wide range of experience and formal technical background from the novice hobbyist to the experienced professionals, Cannon's book includes comprehensive text on basic electronic engineering concepts and the fundamentals of digital circuitry. After readers have learned (or refreshed their knowledge) of the fundamentals, they will be ready to start troubleshooting.

Cannon explains how to locate faults in digital circuitry and make repairs of increasing complexity on everything from simple control circuits to computers. Chapters cover the tech-

niques for troubleshooting with advanced timing techniques, analysis of serial, parallel, synchronous, and asynchronous circuits, signal tracing, and the use of logic clips and probes, and other specialized digital test equipment.

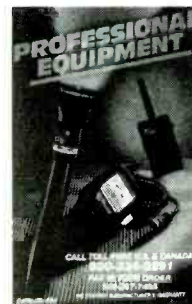The book also covers the solution of problems in sequential logic circuits, how to test complex digital devices, and how to select logic analyzers and computer test equipment appropriate to the maintenance task at hand. Each chapter includes a self-quiz to permit readers to evaluate their progress and understanding of the subjects to which they have been introduced.




CIRCLE 39 ON FREE INFORMATION CARD

and fire safety codes. Use Professional Equipment's toll-free phone number to learn what specialized tools are available for your specific maintenance and inspection tasks.


**Glossary of DC/DC Converter Terminology.** Conversion Devices, Inc., 15 Jonathan Drive, Brockton, MA 02401; Phone: 508-559-0880; Fax: 508-559-9288; free.

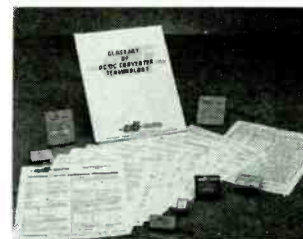This 10-page application note is the first in a planned series from Conversion



CIRCLE 38 ON FREE INFORMATION CARD

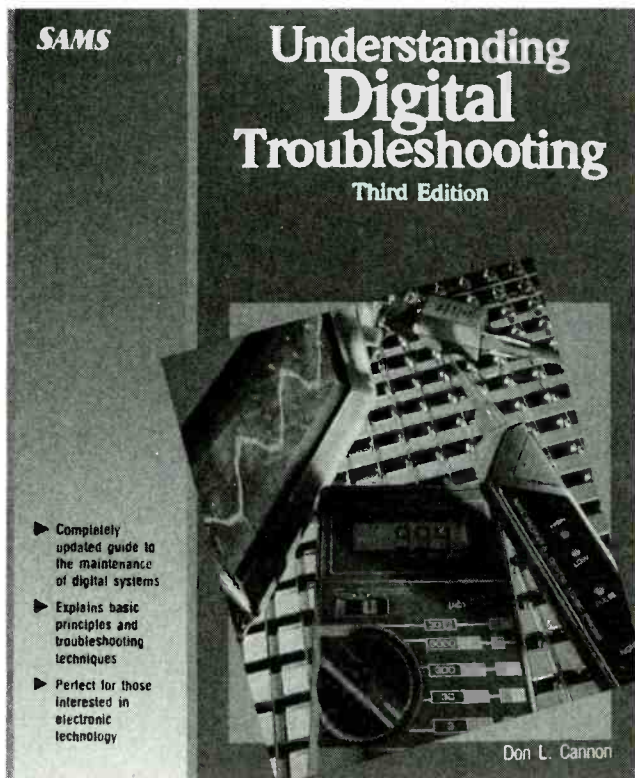Devices, a designer and manufacturer of DC/DC converters. It contains more than 180 definitions of terms commonly associated with DC/DC converters and power supplies. Arranged in alphabetical order, the technical terms are simply and completely explained. Ω



CIRCLE 40 ON FREE INFORMATION CARD


**Professional Equipment, Catalog No. 33.** Professional Equipment, 153 Plainview Road, Woodbury, NY 11797; Phone: 800-334-9291; Fax: 516-367-7405; free.

This 36-page catalog is a source book of information on specialty tools available for such tasks as maintaining air conditioning, heating and ventilating equipment, monitoring the environment, and inspecting industrial equipment. Pictures and information are provided in the catalog for the latest moisture meters, gas detectors, circuit analyzers, flow meters, and industrial electronic test equipment.

Catalog No. 33 will be of interest to maintenance engineers, architects, and inspectors, as well as those with responsibilities for the enforcement of electrical



# The DMM our customers designed.

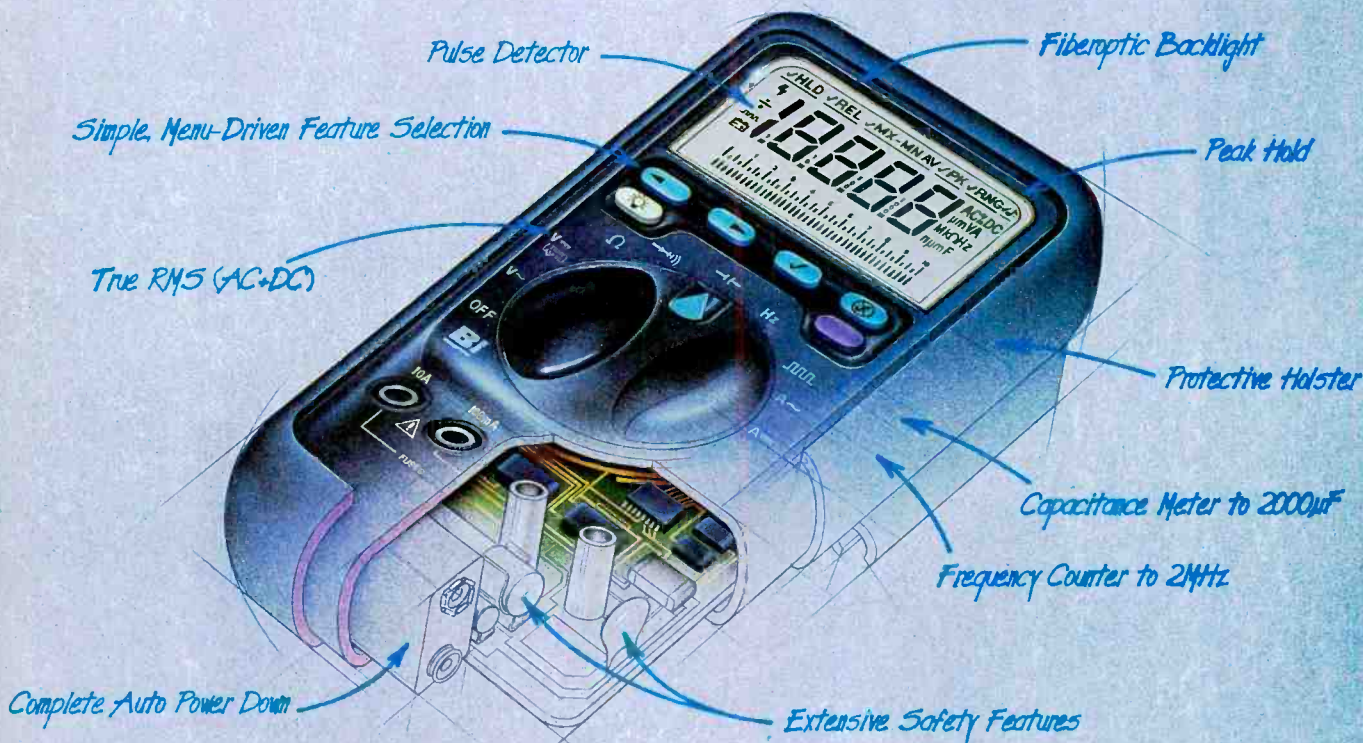

Before we built the new generation Beckman Industrial Series 2000 DMMs, we asked people like you what you *really* want.

You want more. More test and measurement capabilities. More troubleshooting features. All in an affordable hand-held DMM. The Series 2000 features the widest range Frequency Counter in any professional DMM, a full-range Capacitance Meter, True RMS measurements, Intermittent Detection, 50ns Pulse Detection, and Peak Measurement capabilities. Plus, the Series 2000 is the only meter to offer autoranging Min/Max recording and relative modes.

You want a DMM that's easier to use. The Series 2000's display is 25% larger, with bigger digits and backlighting for easier reading, even in the worst light. Plus the fast 4 digit display provides the high resolution needed for adjusting power supplies and generators down to 1mV. And only the Series 2000 features a menuing system for fast, simple feature access.



Made in the USA

The Beckman Industrial Series 2000, priced from \$209 to \$279 offers you the best performance for your dollar. Look again at these features:

- 4 Digit, 10,000 Count Resolution
- Basic Accuracy to 0.1%
- True RMS, AC or AC on DC
- 0.01Ω Resolution
- Automatic Reading Hold
- 1ms Peak Hold
- Fully Autoranging Relative and Min Max Modes
- Intermittent Detector
- UL1244, IEC1010 Design
- Three Year Warranty

The Series 2000 offers the most solutions for your everyday test and measurement needs. The only DMMs designed by the people who use them. You.

For more information on these new DMMs call (outside CA) 1-800-854-2708 or (inside CA) 1-800-227-9781.

WAVETEK INSTRUMENTS DIVISION  
9045 Balboa Ave., San Diego, CA 92123  
USA (619)279-2200 • UK (384)442394 • FRANCE (1) 4302 7606 • GERMANY (089) 960 94 90

\*BI (formerly Beckman Industrial Instrumentation Products Division) is now a part of Wavetek Corporation.

CIRCLE 98 ON FREE INFORMATION CARD

[www.americanradiohistory.com](http://www.americanradiohistory.com)

## WAVETEK




# NEW PRODUCTS

Use the Free Information Card for more details on these products.
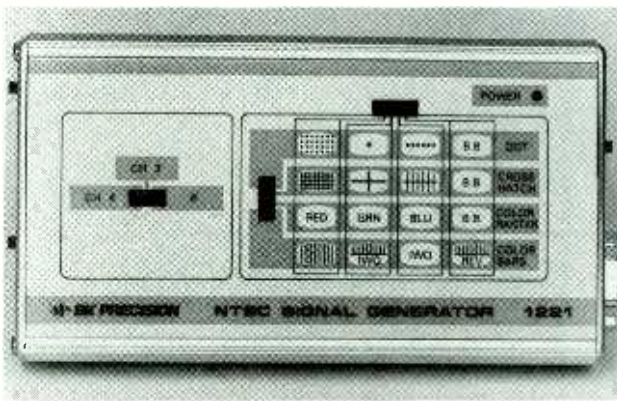
## HANDHELD NTSC COLOR GENERATOR.

A television/video signal generator small enough to fit into a field-service kit is now available from *B+K Precision*. The Model 1221, said to offer the same capabilities usually found only in bench models, generates 14 patterns of stable video signals for testing, servicing, and adjustment of TV's and other video equipment.

The generator's patterns include standard NTSC color bars (with and without IWQ), full-field IWQ, split-field color bars with reverse bars and red, green, blue, and black rasters. It also offers six convergence patterns. For monochrome tests, the chroma can be turned off to display the luminance level only. A 1-kHz subcarrier audio tone can also be switched on or off.



CIRCLE 16 ON FREE INFORMATION CARD

Generator outputs include composite video, IF (45.75 MHz, crystal-controlled), and CH3 and CH4 (crystal-controlled). For testing CGA computer monitors, a 9-pin D-type connector provides an RGB output. The user can select either interlaced or progressive scan, TTL or low-level (analog level) for RGB outputs.

The Model 1221 is

housed in a rugged, lightweight aluminum case that acts as an RF shield. It can be powered by the included AC adapter or an external 12-volt DC to 18-volt DC source.

The Model 1221 NTSC color signal generator is priced at \$369.

**B + K Precision**  
Chicago, IL 60635  
Phone: 312-889-1448  
Fax: 312-794-9740



CIRCLE 17 ON FREE INFORMATION CARD

printer interface, and display backlighting.

The price of the ScopeMeter Model 93 is \$1350, the Model 95 is \$1650, and Model 97 is \$1950. Upgrades of earlier ScopeMeter's are \$155.

**John Fluke Mfg. Co., Inc.**  
P.O. Box 9090  
Everett, WA 98206  
Phone: 800-44-FLUKE

## FOIL-SHIELDING TAPES KIT.

Foil-shielding tapes are now available from 3M in convenient kits. Each kit contains 3M's full line of shielding tapes organized in a compact dispenser box. The Scotch brand tapes are intended for reliable point-to-point electrical contact. Examples of applications include EMI/RFI shielding, grounding, and electrostatic-charge draining.

The eight 3/4-inch-wide,

## UPGRADED 90 SERIES

**SCOPEMETER.** Fluke's upgraded ScopeMeter combines a 50-MHz, 25-megasamples per second dual-channel digital storage oscilloscope with a digital multimeter. It has been given a Version 4 software upgrade.

This ScopeMeter includes a lot of new features intended to improve its flexibility and "user friendliness." They include percent duty-cycle measurements for pulse-width modulated signals in control circuits, 30-ohm range, and 0.01-ohm resolution

for tracing elusive shorts. Other new features include a "time stamp" to mark the occurrence of minimum and maximum values, waveform inversion on both channels for easier calculations, and increased frequency-counter resolution.



The upgrade also includes circuitry that returns the instrument to previous settings when changing between the meter mode and the scope mode. Additional record functions are included, and there is continuous meter-mode display of voltage, frequency, and duty cycle. A smart

trigger algorithm allows hands-off duty-cycle measurements of pulse-width modulated motor-control waveforms.

The three ScopeMeters (Models 93, 95, and 97) offer oscilloscope and digital multimeter functions. They all include such features as autoset, waveform and set-up memory, combined display of meter results and waveforms, and convenient menus. The Model 97 also features a built-in signal generator, a component tester, and remote control through an optically isolated RS-232 interface,


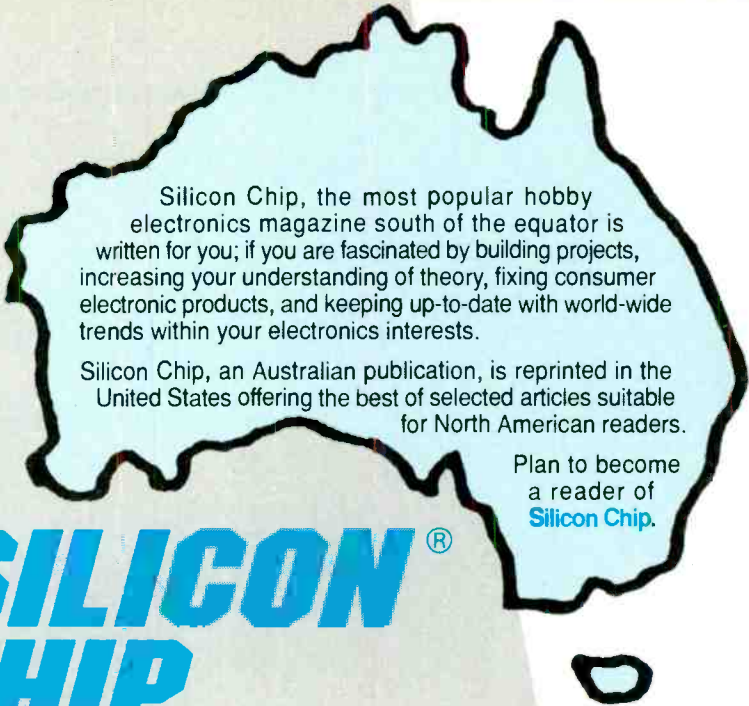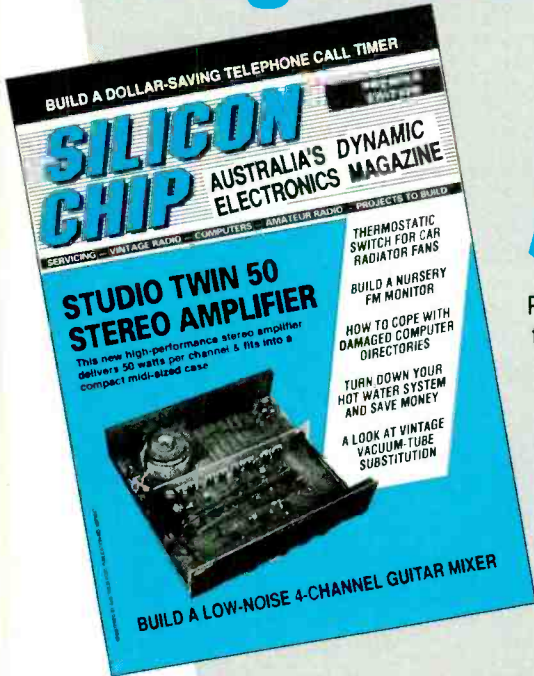
# Introducing Australia's Leading Electronics Magazine...



# SILICON CHIP®

Packaged in a specially prepared format guaranteed to excite the electronics hobbyist with new ideas, novel projects, extraordinary features and down-right good reading.

Inside **Silicon Chip** you will discover how the other side of our world—down under—approaches the same hobby interests as you do, with ramifications that will amaze you.

Detailed construction projects to appear in upcoming issues of Silicon Chip include:

- 4-Channel Guitar Mixer**
- Adjustable 0-45V, 8A Power Supply**
- Interphone Digital Telephone Exchange**
- 1.5V to 9V DC Converter**
- Multi-Sector Home Burglar Alarm**
- 1-Megabyte Printer Buffer**



*Exciting and imaginative Features like:*

- Understanding Computer Memory**
- How to Interlink Musical Instruments**
- What's New in Oscilloscopes**

If you are fascinated by electronics, especially the hobby aspects related to construction projects, theory, applications in home and shop, and latest developments, if you are compelled to experiment and "fix-it," then **Silicon Chip** is your kind of magazine.

**Silicon Chip** is available exclusively by subscription. So take advantage of this great opportunity and start your Charter Subscription today.

**SILICON CHIP**, 500-B Bi-County Boulevard, Farmingdale, New York 11735 EN393

I'm convinced! Enroll me as a Charter Subscriber. Enter my subscription as designated below.

<b>United States of America</b>		<b>Canada</b>	
<input type="checkbox"/> 12 issues for \$29.95	<input type="checkbox"/> 24 issues for \$49.95	<input type="checkbox"/> 12 issues for \$40.61	<input type="checkbox"/> 24 issues for \$70.57
		(Includes postage & G.S.T.)	
<input type="checkbox"/> Payment enclosed	Please charge my	<input type="checkbox"/> VISA	<input type="checkbox"/> Mastercard

For your convenience, if paying by credit card: To avoid any interruption in service, your subscription will be renewed automatically at 12-issue intervals, at the then prevailing introductory rate, until you advise us to cancel it.

Signature \_\_\_\_\_

Account No. \_\_\_\_\_ Expiration Date \_\_\_\_\_

Offer valid in the U.S.A. and Canada only. No foreign Orders.

Name \_\_\_\_\_

Address \_\_\_\_\_


City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

All orders payable in U.S.A. funds only. Allow 6-8 weeks for delivery.



**TROUBLESHOOTING AND REPAIRING AUDIO & VIDEO CASSETTE PLAYERS & RECORDERS**




3795-XX \$29.95  
Counts as 2

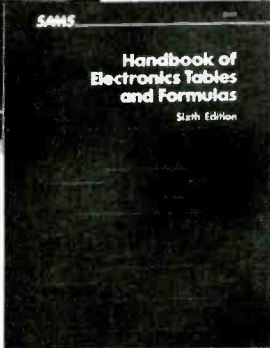

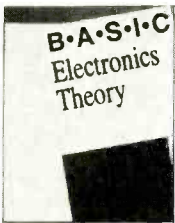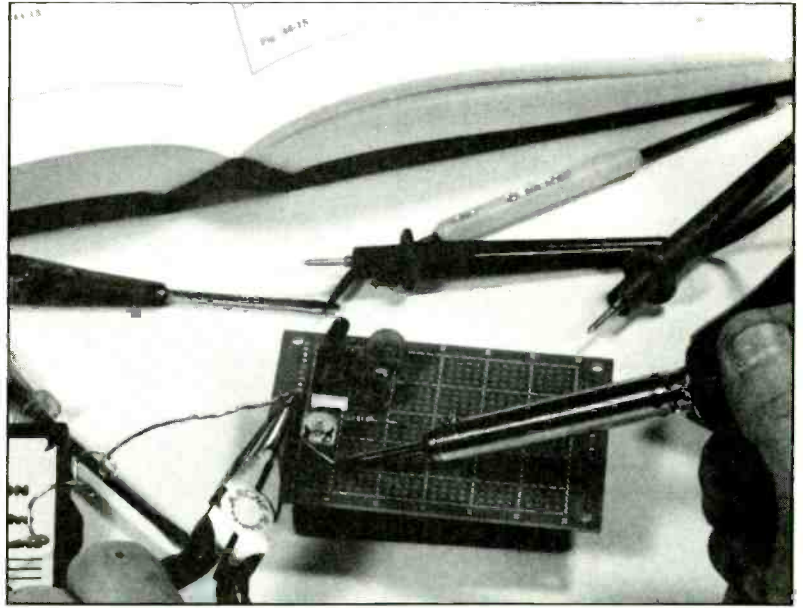583804-XX \$19.95  
Counts as 2/Softcover



3195P-XX \$22.95  
Counts as 2/Softcover

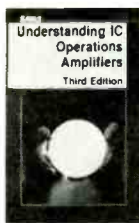

585120 \$12.95  
Softcover




4089P \$18.95  
Softcover



2883P \$18.95  
Softcover



804P-XX \$21.95  
Counts as 2/Softcover

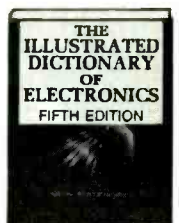


3345P-XX \$26.95  
Counts as 2/Softcover



2613P \$18.95  
Softcover




585107-XX \$24.95  
Counts as 2

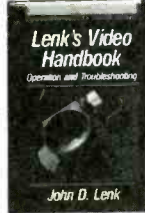

1001B \$39.95



1367P \$29.95  
Softcover

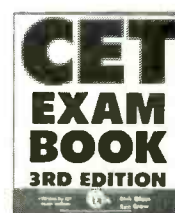

4199 \$27.95




3438-XX \$39.95  
Counts as 2




3677-XX \$34.95  
Counts as 2



3671P \$18.95  
Softcover

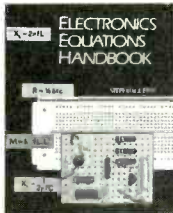

3241P \$16.95  
Softcover

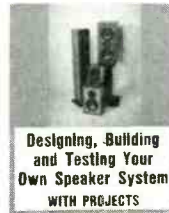

3374P \$16.95  
Softcover




3107P \$18.95  
Softcover



3700-XX \$36.95  
Counts as 2




1604P \$17.95  
Softcover

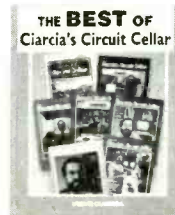


011019-XX \$39.95  
Counts as 2




4143 \$22.95

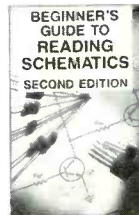

3632P \$10.95  
Softcover

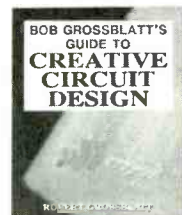

3610 \$28.95

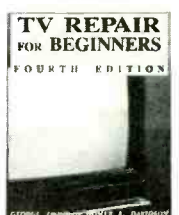

3627-XX \$29.95  
Counts as 2



# Select any 5 books for only \$4<sup>95</sup>

when you join the **ELECTRONICS BOOK CLUB**<sup>®</sup> (values up to \$161.75)




2724P \$17.95  
Softcover




2925P \$10.95  
Softcover




3765P \$18.95  
Softcover

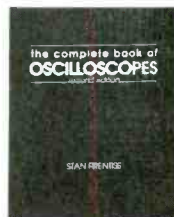


3825 \$26.95

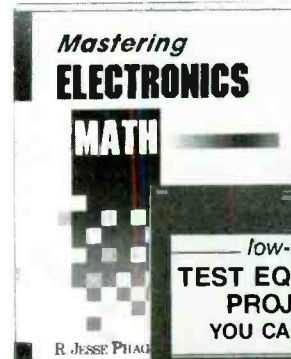


3589 \$27.95

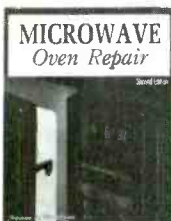


3457 \$29.95

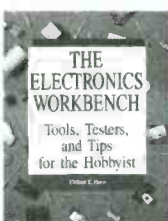


3672P \$18.95  
Softcover

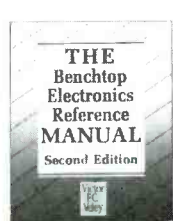


3414-XX \$39.95  
Counts as 2

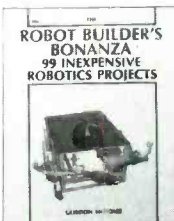


2800P \$16.95  
Softcover

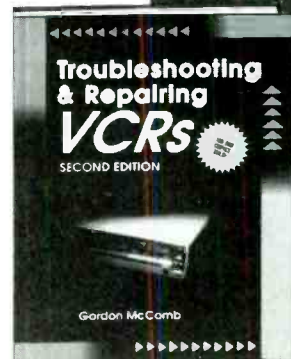


3886 \$22.95

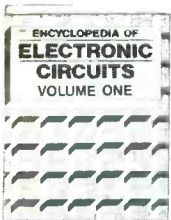

1938-XXX \$60.00  
Counts as 3

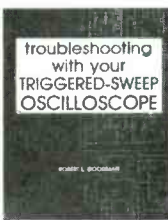

3669 \$27.95

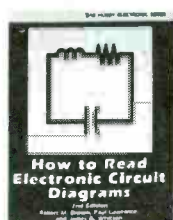

2880P \$14.95  
Softcover



3923 \$32.95

3777-XX \$32.95  
Counts as 2

If coupon is missing, write to: Electronics Book Club, Blue Ridge Summit, PA 17294-0810

## As a member of the Electronics Book Club . . .

. . . you'll enjoy receiving Club bulletins every 3-4 weeks containing exciting offers on the latest books in the field at savings of up to 50% off of regular publishers' prices. If you want the Main Selection do nothing and it will be shipped automatically. If you want another book, or no book at all, simply return the reply form to us by the date specified. You'll have at least 10 days to decide. And you'll be eligible for **FREE** books through the **NEW** Bonus Book Program. Your only obligation is to purchase 3 more books during the next 12 months, after which you may cancel your membership at any time.

(Publishers' Prices Shown)  
All books are hardcover unless otherwise noted. ©1993 EBC  
A shipping/handling charge & sales tax will be added to all orders.  
If you select a book that counts as 2 choices, write the book number in one box and XX in the next.  
If you select a Counts as 3 book, write the book number in one box and XXX in the next 2 boxes.

**Your most complete and comprehensive source for the finest electronics books**

## ELECTRONICS BOOK CLUB<sup>®</sup>

Blue Ridge Summit, PA 17294-0810

**YES!** Send the 5 volumes listed below, billing me just \$4.95 plus shipping/handling & tax. Enroll me as a member of the **Electronics Book Club** according to the terms outlined in this ad. If not satisfied, I may return the books within ten days and have my membership cancelled. A shipping/handling charge and sales tax will be added to all orders.


If you select a book that counts as 2 choices, write the book number in one box and XX in the next.  
If you select a Counts as 3 book, write the book number in one box and XXX in the next 2 boxes.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_

Zip \_\_\_\_\_ Phone \_\_\_\_\_

Valid for new members only, subject to acceptance by EBC. Canada must remit in U.S. funds drawn on U.S. banks. Applicants outside the U.S. and Canada will receive special ordering instructions. RE393C



**CIRCLE 18 ON FREE INFORMATION CARD**

four-yard-long rolls include one each of: 1170 (aluminum), 1181 (copper), 1182 (double-coated copper), 1183 (tin-alloy-coated copper), 1194 (copper), 1245 (embossed copper), 1267 (embossed aluminum), and 1345 (embossed tin-alloy-coated copper). Replacement rolls are available from the same source as the kits.

The kit simplifies the task of finding the right tape when it is needed. The 4 × 4 × 7.5-inch container is labeled with useful technical and applications information about the tapes: product number, backing, adhesive type and thickness, adhesion, resistance, and shielding effectiveness.


**3M Electrical Specialties Division**  
**Building 130-3N-56**  
**6801 River Place Blvd.**  
**Austin, TX 78726-9000**  
**Phone: 1-800-328-1368.**

**900-MHz RADIO POWER MODULE.** Motorola has introduced 7.5-volt RF power modules that operate in the 806–940-MHz frequency range with an input power of 1 milliwatt and an output power of 4 watts. The *MHW804 Series* is intended for cellular telephone, trunking, or other two-way radio systems.

The series includes two modules that differ only in operating frequency band. Both are packaged in cases less than 1/2-inch wide. According to

Motorola, the modules are exceptionally stable, rugged, low in harmonics, and have wide dynamic ranges.

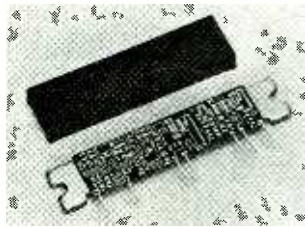The *MHW804-1* operates in the 800 to 870-MHz range, and the *MHW-*




**CIRCLE 19 ON FREE INFORMATION CARD**

*804-2* operates in the 896 to 940-MHz range. The *MHW804-1* is priced at \$50.82 and the *MHW-804-2* is priced at \$52.36 in 1 to 399 quantities.

**Motorola, Inc.—E114**  
**5005 East McDowell Road**  
**Phoenix, AZ 85008**  
**Phone: 602-244-4597**  
**Fax: 602-244-4597**

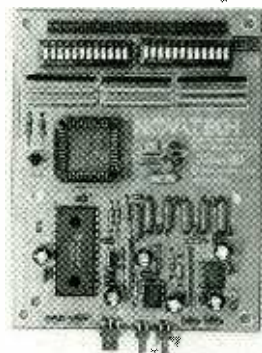**DIRECT DIGITAL SYNTHESIZER KIT.** This direct digital synthesizer from Novatech can produce output signals up to 12 MHz. The *DDS-3* direct digital synthesizer kit can be programmed to produce sine and TTL/CMOS-compatible signals from 2 Hz to 12 MHz in 2 Hz steps. Its output frequency is set with a 23-bit binary word introduced by DIP switch or ribbon cable.




**CIRCLE 20 ON FREE INFORMATION CARD**

The synthesizer's output amplitude is 1.4 volts peak-to-peak into an open circuit. Fast switching of the output frequencies can be obtained because the transition time for changing frequencies is less than 250 nanoseconds. Spectral purity is specified as better than -90-dBc phase noise at 1-kHz offset, -45-dBc spurious, and -40-dBc harmonic.

Stability is specified as better than 10 ppm. The *DDS-3* is powered by ± 5-volt DC power. The kit includes a 3.5 × 4.5-inch printed circuit board and all necessary parts.

The *DDS-3* kit is priced at \$119.95 plus \$5 for shipping and handling.  
**Novatech Instruments, Inc.**  
**1530 Eastlake Ave. E.,**  
**Suite 303**  
**Seattle, WA 98102**  
**Phone: 206-328-6902**  
**Fax: 206-328-6904**

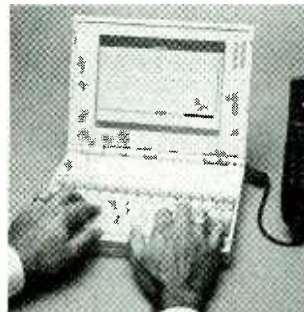**CELLULAR NOTEBOOK LINK.** A prominent Finnish electronics manufacturer has introduced its *Cellular Notebook Link*. Nokia designed the link for use with Compaq notebook computers equipped with the *SpeedPAQ 144* modem



**CIRCLE 21 ON FREE INFORMATION CARD**

and *Nokia 121* cellular phones. The link permits data and fax transmissions to be sent and received over a cellular network.

The interface is a coiled cable with a quick-release

data cradle that holds the phone while it is in the fax/data mode. That design eliminates the separate interface box required in most mobile data installations. The link needs no external battery because the interface is powered by the phone's battery and the computer's internal power source.

When used with the Compaq *SpeedPAQ 144* modem, the *Cellular Notebook Link* transmits data at 4800 bits per second. However, if the data is compressed, Nokia says the data throughput will exceed 11,000 bps. Fax transmissions are sent and received at 9600 bps.  
**Nokia Mobile Phones, Inc.**  
**2300 Tall Pines Drive**  
**P.O. Box 2930**  
**Largo, FL 34649-2930**  
**Phone: 813-536-5553**  
**Fax: 813-530-7245**

**STANDBY POWER SUPPLIES.** *Perma Power Electronics* is offering a series of standby power systems for backing up computers and peripherals if power fails. *WatchDOS* supplies can be used with any DOS-based computer or network, but cannot be used with Windows or memory-management software. Each system includes a "Hibernate" software utility program.



**CIRCLE 22 ON FREE INFORMATION CARD**

When AC-line power fails, the software detects a signal from the backup power supply, transfers conventional, expanded, and extended memory and



data to the hard drive, and then safely shuts down the computer. When AC power is restored, the software system restarts the computer, restores all memory, and resumes program execution at the point of power interruption.

The 400-VA Model DPS-400I is priced at \$299 and the 600-VA Model DPS-600L, for single personal-use 386 computers, has price of \$375. The 800-VA Model DPS-800L, for office 386 and 486 computer systems, has a price of \$489.

**Perma Power Electronics, Inc.**  
5601 West Howard Avenue  
Niles, IL 60714  
Phone: 708-647-9414  
Fax: 312-763-8330

**CW TRANSCEIVER.** This 5-watt, 20-meter CW transceiver covers the 14.000 to 14.075-MHz band. MFJ Enterprises' MFJ-9020



**CIRCLE 23 ON FREE INFORMATION CARD**

compact transceiver measures only 2.25 x 6 x 6.5 inches. It has a sharp, 8-pole crystal filter, 500-Hz bandwidth, and Vernier tuning. The transceiver has a 5-watt transmitter, a super-heterodyne receiver, audio-derived AGC, CW side-tone, and a built-in speaker with an earphone jack. The MFJ-9020 is powered from 12 to 15 volts DC, and it fits in a briefcase.

The price of the MFJ-9020 CW transceiver is \$179.95.

**MFJ Enterprises, Inc.**  
P.O. Box 494  
Mississippi State, MS 39762  
Phone: 1-800-647-1800  
Fax: 601-323-6551.

## Clean Without CFCs or 1,1,1-Trichloroethane With New HCFC Blend

Tech Spray has developed a fast-acting and highly effective cleaner called Envi-Ro-Tech™ 1677 (1677) that uses a formulation of HCFCs and other non-CFC chemicals.

This extremely pure product is non-corrosive, making it safe for use on most electronic equipment. Envi-Ro-Tech 1677 is effective in removing oils, greases, dirt, silicone, fluxes and similar soils.

Although Envi-Ro-Tech 1677 has universal cleaning power, its low surface tension makes it ideal for precision and microscopic cleaning.

For a sample of this, or any Tech Spray cleaner, defluxer, duster or freeze spray, contact our Technical Assistance Department toll free at 1-800-858-4043.



Envi-Ro-Tech™ 1677 (1677)

**TECH SPRAY, Inc.**  
P.O. Box 949  
Amarillo, TX 79105-0949  
(806) 372-8523

©1992 TS

**CIRCLE 180 ON FREE INFORMATION CARD**

# Train at HOME to be an Electronics Technician!

As the demand for computers and microprocessors in business, manufacturing and communications continues to grow, so does the need for qualified technicians. It's not unusual for experienced technicians to earn from \$30,000 to more than \$40,000 a year.\* Now through Peoples College of Independent Studies you can train for this exciting field without interrupting your job or home life.

### Choose From Five Programs of Study

- Electronics & Microprocessor Technology
- Industrial Electronics & Microprocessor Technology
- Communications Electronics with Microprocessor Technology
- Computer Servicing & Electronics Technology
- Specialized Associate Degree In Electronics Technology

### Professional Equipment Is Included

Depending on the program you select, you'll perfect your skills using this advanced equipment, included in the price of tuition:

- IBM-Compatible Personal Computer
- Digital Multimeter
- Digital Logic Probe
- Elenco Oscilloscope
- Portable Cellular Telephone

(\* Source: U.S. Bureau of Labor Statistics)



### Exclusive Extras That Enhance Your Training

Peoples College introduces some training firsts to make your learning experience more complete:

- Accelerated Learning System — a scientifically proven study system that helps you learn faster and easier than ever before.
- Video Tutor Training Tapes — give you a permanent, visual record of informative lectures and close-up demonstrations.
- Experience Labs — professionally designed experiments that give you hands-on "bench" experience.
- Industry Certification Training Guide — provided with four of our programs. Prepares you for examinations you may take for your professional license or certification.

### Easy Payment Plans — No Finance Charges

To help you get started on your education, Peoples College has reduced tuition rates and offers low monthly payment plans with no finance fees. So don't delay, call or write for more information today!

### For COLOR CATALOG Mail Coupon or Call TOLL FREE 1-800-765-7247

Programs offered only in United States, Canada, Puerto Rico and Virgin Islands. No Obligation. No sales person will call.

Our programs are accredited by the Accrediting Commission of the National Home Study Council

YES! I would like to know more about your training programs. Send a catalog to:

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

Phone # \_\_\_\_\_

**PEOPLES COLLEGE**  
OF INDEPENDENT STUDIES

233 Academy Drive • P.O. Box 421768  
Kissimmee, FL 34742-1768

Member, D.I. Peoples Group R-393

# THE PARTS PLACE

## Pocket LCD-digital multimeter value

Take it along! This UL listed, autoranging multimeter folds up, with its probes, to easily fit a shirt pocket. Continuity buzzer, diode-check mode. Measures to 400 volts AC or DC and 2 megohms resistance. #22-171 . . . . . 24.99



## TECHLINE™ Tools—The new standard in strength and precision!



- Precision-crafted with top-quality materials
- Designed for long life and ease of use
- Backed by Radio Shack's 1-Year Limited Warranty


New TECHLINE tools represent Radio Shack's uncompromising dedication to quality. Each is precision-crafted of long-lasting, hard-working materials and employs the latest design innovations for comfort and ease of use. And, each is backed by our full 1-year limited warranty.



**Portable Power Inverter.** For camping, fishing, emergencies. Converts car/boat 12VDC to 115VAC for powering a TV, VCR, light or tool. Compact and efficient. Rated 140W continuous. #22-132 . . . . . 99.99



**TECHLINE Swiss Army Knife.** Tool kit for your pocket! You'll be prepared with a large blade, Phillips and slot screwdrivers, wire stripper, cutters, pliers, opener, tweezers and toothpick. #64-2001 . . . . . 29.95

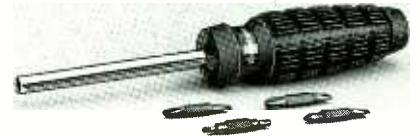

**TECHLINE 9-in-1 Screwdriver.** With eight steel tips in the most needed sizes—Phillips, slot and special purpose. Tips store in handle and shank doubles as 1/4" nutdriver. #64-1967 . . . . . 9.99



**Hi-Current Car DC Adapter.** Plugs into vehicle lighter socket. Provides 6, 9 or 12VDC. With four Adaptaplugs. #270-1562 . . . . . 15.95



**12VDC Brushless Micro Fan.** Use to cool hum-sensitive circuits and small car stereo amps. Provides 3.5 CFM. #273-0244 . . . . . 17.95



**Anti-Static Spray.** By STATX® brands. New high-tech cleaner and protector repels dust—cleans without scratching. #64-3310 . . . 3.99



**Mini Audio Amp With Built-in Speaker.** Many uses—test amp, signal tracer, phone amp and amplified PC speaker. #277-1008 . . . . . 11.95



**Desoldering Helper.** Handy solder remover is easy to use. Your nearby Radio Shack has everything in soldering needs. #64-2120 . . . . . 5.99

## Speedy service and low prices on thousands of parts and accessories!



- FREE delivery to Radio Shack on orders \$5 and up
- Semiconductors and ICs ■ Hard-to-find batteries
- CB and scanner crystals ■ Long-life vacuum tubes
- Phono cartridges/styli ■ SAMS® service books

Why pay more for mail-order? Your Radio Shack stocks 1000 electronic components, and another 15,000 are available fast from our special-order warehouse. Ordering is easy! Bring in the exact part number (or old part). We'll check availability and order by phone. Delivery time to your nearby Radio Shack for most items is a week.

**Radio Shack** SINCE 1921  
**AMERICA'S TECHNOLOGY STORE** SM

CIRCLE 78 ON FREE INFORMATION CARD

Prices apply at participating stores and dealers.



# BUILD THIS



# ULTRASONIC CLEANER

**Build a professional-quality ultrasonic cleaner and keep hard-to-clean connectors, parts, and tools spic and span.**

## REINHARD METZ

ULTRASONIC CLEANING HAS BEEN commonplace in commerce and industry for years, particularly for cleaning small, convoluted parts that would be a difficult or impossible to clean otherwise. Items that are routinely cleaned ultrasonically include machine parts, standard and micro-miniature tools and connectors.

Factory-made ultrasonic cleaners are still too expensive for the average consumer and hobbyist. But with the drawings, photos, and text in this article, you can build your own ultrasonic cleaner. You have options in building this ultrasonic cleaner. You can build the complete system with micro-processor-based time and temperature controls, or you can build only the basic model with on-off controls. You'll be surprised at the low-cost of the parts, regardless of the option you choose. The basic specifica-

tions for the ultrasonic cleaner are given in Table 1.

Only non-toxic, non-flammable solutions will be needed to do effective cleaning with this ultrasonic cleaner. You'll be able to clean many different kinds of household or shop objects that are hard to clean—or, in the past, have just been too much trouble to clean well with conventional methods. Those objects include jewelry, kitchen utensils, circuit boards, bicycle and auto parts, and tools. What is more, you can do all your ultrasonic cleaning indoors—you don't have to go into your garage or backyard to keep noxious fumes out of your house.

### Ultrasonic cleaning

The basis for ultrasonic cleaning is a bubbling action in a fluid called *cavitation*—millions of tiny bubbles forming and collapsing within the cleaning solution do the scouring. You have probably seen the cartoons of thousands of cleaning bubbles at work on the TV com-

mercials for bathroom cleaners. The big difference here is that with our cleaner, the bubbles are created ultrasonically by piezoelectric transducers, not by the solution itself.

The disk-shaped piezoelectric transducers are bonded to the underside of the cleaning pan. The dimensions of these barium-titanate ceramic disks change continuously in response to high-frequency signals applied across their sensitive surfaces. These transducers are similar to those used

**TABLE 1  
LEADING SPECIFICATIONS  
FOR THE ULTRASONIC CLEANER**

Transducers	piezoelectric
Operating frequency	40 to 60 kHz
Cleaning pan capacity	¾ gallon
Microcontroller	Intel 8751
Timing range*	1 to 99 min.
Solution temperature w/heater*	25 to 99°C
Power requirement	117-V AC, 60 Hz

\*Optional feature

in marine depth finders.

The compression and expansion of the crystalline transducers is coupled mechanically through the bottom of the pan to create the cavitation bubbles in any cleaning solution that you use. (For a complete description of the piezoelectric effect, refer to page 46 of the January 1993 *Electronics Now*).

If the cleaning solution that you select is a recognized solvent for the contaminants that you expect to find on the parts to be cleaned (for example, oil or grease), the ultrasonic cleaner will enhance the cleaning action of that solution.

### Description of the cleaner.

The ultrasonic cleaner has three main parts: a stainless steel pan with two transducers attached, a large circuit board containing the power oscillator and time- and temperature-control circuitry, and a small switch/display circuit board containing the control switches and LED displays.

The large circuit board (approximately 5 × 8 inches) is shown in Fig. 1. The left side of the board is occupied by the power transistor amplifier for the oscillator and its heat sink. The oscillator, made up of components on the board, supplies a 40- to 60-kHz, 1000-volt sine wave to the piezoelectric transducers. The large objects in the center of the board are the two transformers—one standard and one special. The microcontroller and other IC's are located on the right side of the board.

All of the switches are located on the smaller (approximately 2 × 5-inch) PC board shown in Fig. 2. They include, from the left, the ON-OFF power switch, the TIME UP-DOWN toggle switch, the TEMP UP-DOWN SWITCH and the START pushbutton. The green two-digit, seven-segment display on the left indicates time, and red one to its right indicates temperature.

Figure 3 shows the stainless steel cleaner pan upside down with the two piezoelectric ceramic transducers (white disks) bonded to a stainless steel plate

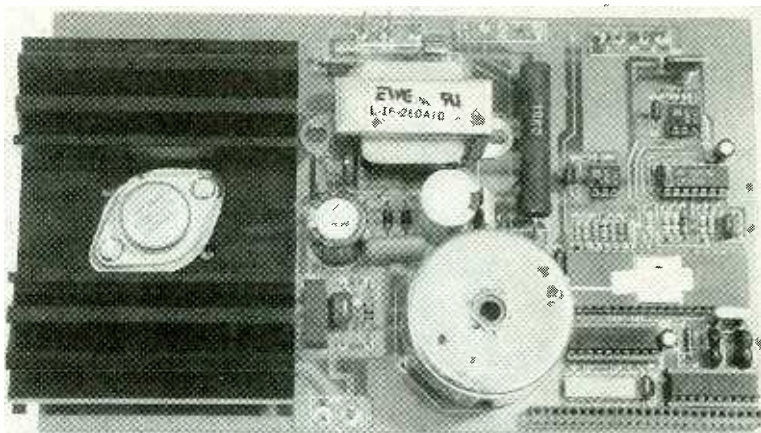


Fig. 1—CIRCUIT BOARD CONTAINING power oscillator and microcontroller-based time and temperature control circuitry.

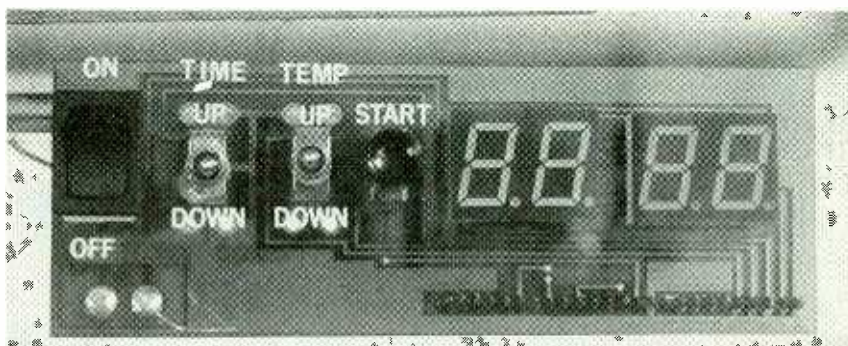


FIG. 2—CIRCUIT BOARD CONTAINING the manual operating control switches and LED time and temperature digital displays

which, in turn, is bonded to the pan bottom. The plate transmits the vibrations from the transducers more uniformly through the bottom of the pan to the cleaning solution, and it helps to protect the brittle transducers from damage that might be caused by objects accidentally dropped into the pan.

The ultrasonic cleaner will work very well without the time and temperature circuitry, but building them should be interesting, and they will add value to the cleaner. The controls will be especially useful if you plan to heat the cleaning fluid, and want to set time limits for the cleaning action on specific objects. Moreover, the controls will shut the unit off automatically.

Both time and temperature are programmable—time from from 1 to 99 minutes, and temperature from 25° to 99° C. The time and temperature functions are controlled by an Intel 8-bit CMOS 8751 microcontroller, which you can program or purchase already programmed.

### Driver circuit

Refer to the right side of the two-page schematic diagram Fig. 4. The amplifier in the transducer oscillator driver is a Hitachi 2SC1922 bipolar power transistor, Q1. The oscillator tank circuit is formed by the inductance the secondary winding of transformer T1 and the effective capacitance of transducers RES1 and RES2. Bridge rectifier BR1 and capacitor C1 form a 160-volt DC power supply operated from the 120-volt, 60-Hz line. Resistor R1 provides the base bias for Q1, through the feedback winding of T1.

As Q1 turns on, current flows through the primary of T1, which generates an opposing voltage in its feedback winding, tending to turn Q1 off again. At the parallel-resonant frequency of the tank circuit, made up of the secondary of T1, RES1 and RES2, the phase shift between the base and collector of Q1 is exactly 180°, which is necessary for circuit oscillation. The winding ratios of T1 determine the



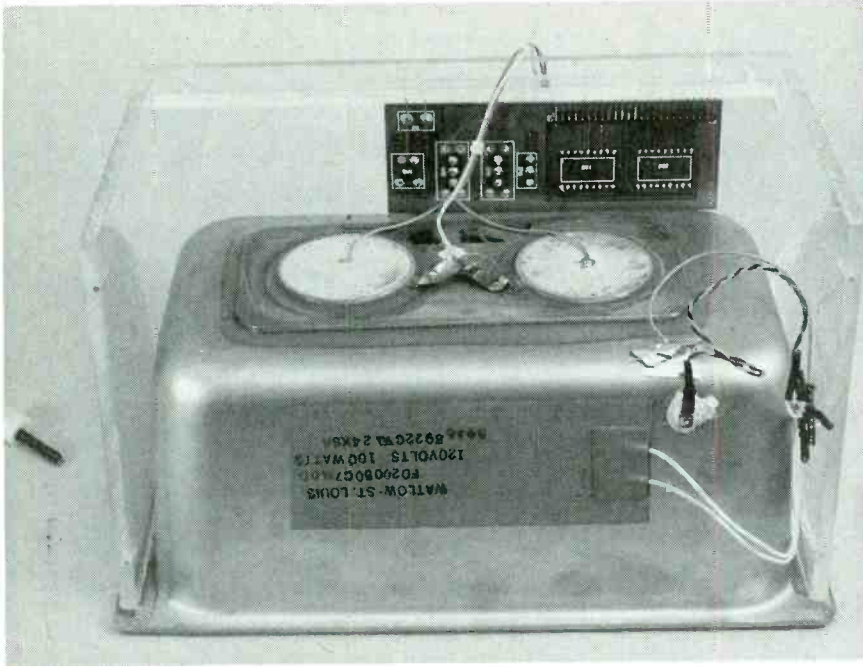


FIG. 3—VIEW OF INVERTED CLEANER PAN with two piezoelectric transducers mounted on it. The back of the control/display board is shown in the background.

put voltage is about 1000 volts peak-to-peak. In addition, the DC startup current provided by R1 and C2 is the AC drive current for Q1. Resistor R2 and capacitor C3 suppress spurious oscillations at frequencies other than the tank's primary resonant frequency.


As the drive voltage across the transducers swings through the 1000-volt peaks, the transducers expand and contract across their thickness dimensions, and their vibrations are coupled through the pan walls to the cleaning solution.

### Time and temperature control


The CMOS8751 microcontroller, IC1, is the key component of both time and temperature controls. It responds to input from the START button, TIME UP-DOWN switch, TEMP UP-DOWN switch, and the

temperature-sensor circuit. It provides the drive signals for the two-digit time and two-digit temperature LED displays, the transducer power Triac Q2, and the heater Triac Q3.

An assembly-code listing for the Intel 8751 firmware is available from the address given in the Parts List or from the R-E BBS (516-293-3000; 1200/2400 baud 8, N, 1). The program consists of a loop, whose time corresponds to the multiplex rate of the LED displays. Each time the loop is traversed, one of the four digits is enabled; the loop rate is sufficient to eliminate display flicker. Within the loop, inputs are checked and various time, temperature, and display variables are updated. The switches provide direct input through

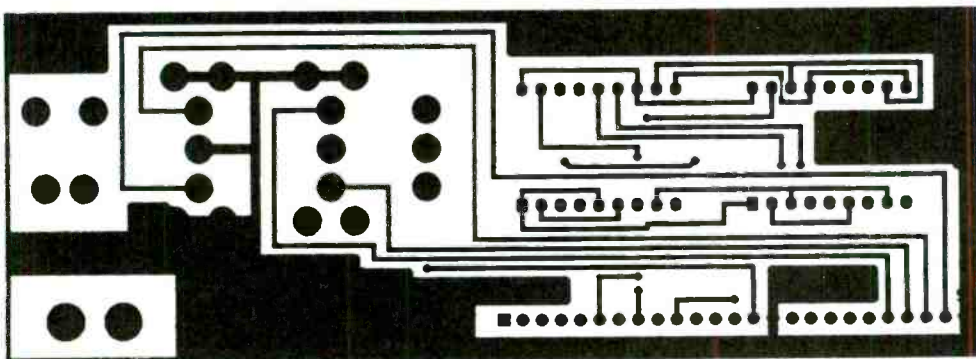

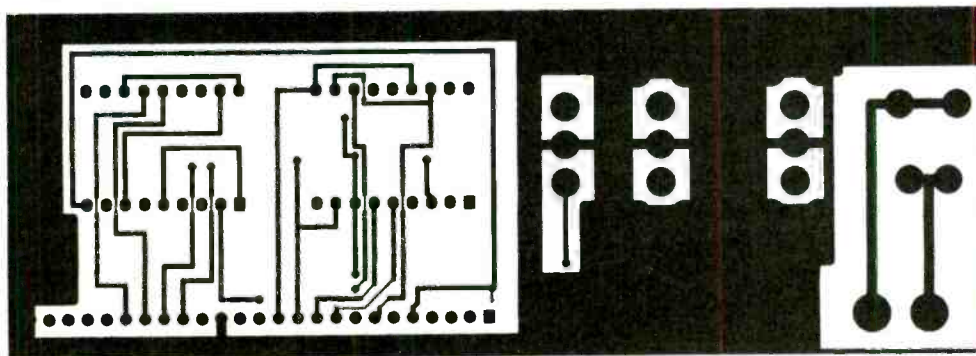THE FOIL PATTERN FOR THE FRONT (component) side of the switch/display circuit board



THE FOIL PATTERN FOR THE REVERSE (solder) side of the switch/display circuit board.

output voltage, and thus the voltage applied to the two transducers.

The input supply voltage is 160 volts DC, and the turns ratio is about 5 to 1, so the out-

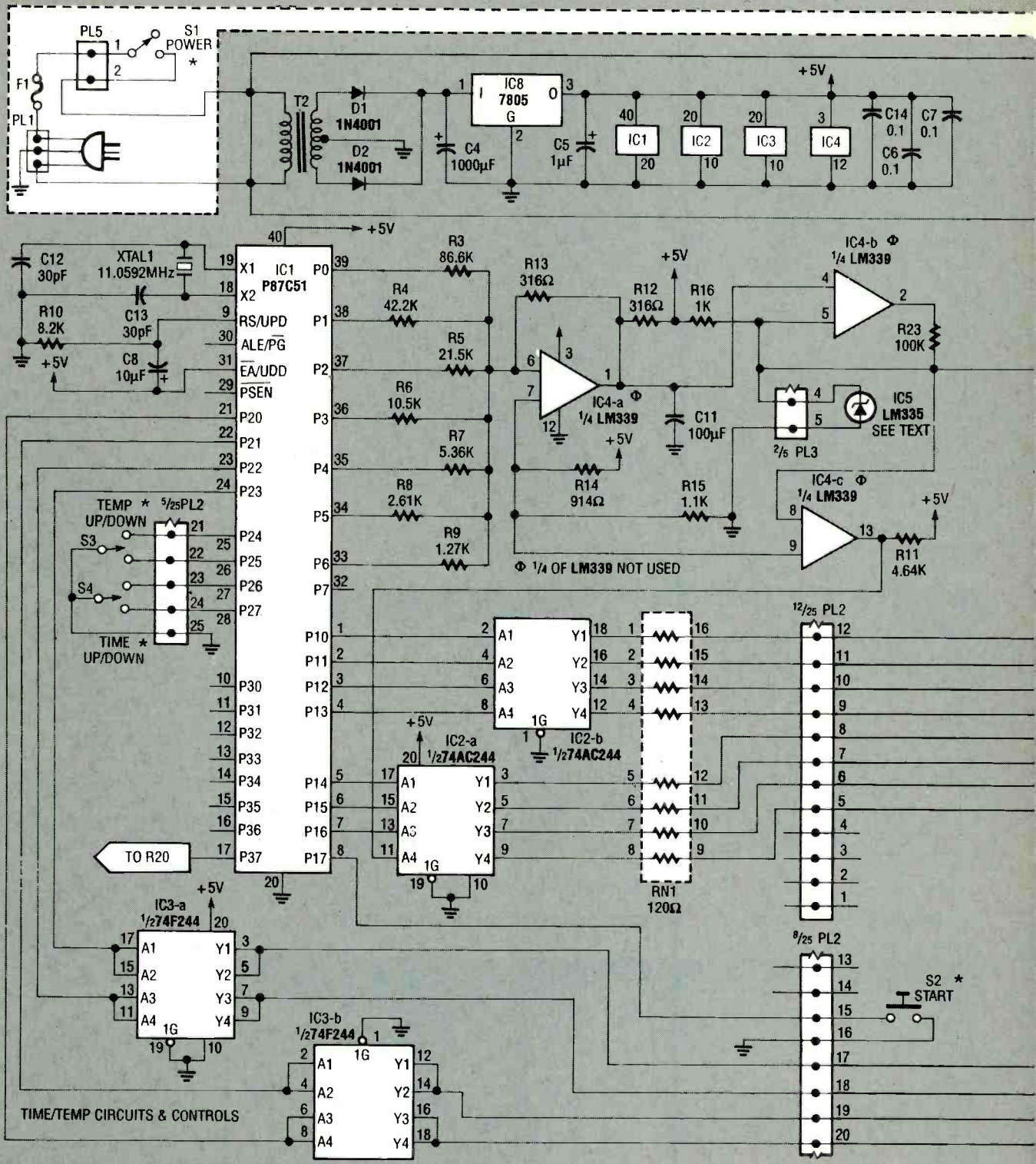


FIG. 4—SCHEMATIC FOR THE ULTRASONIC CLEANER is divided by dotted lines into the operating control section and the time-temperature control section

the I/O port.


Temperature is registered in binary format, and it is converted from a digital to an analog signal by resistor string R3 through R9 and IC4-a. This analog signal is then compared

with the pan temperature signal from IC5 by IC4-b. When solution temperature falls below the selected threshold, IC6 turns on to energize Q3, which provides current to pan heaters HTR1 and HTR2. When the

cleaner is first turned on, the temperature is automatically reset to 25 degrees C. Whenever heat is on, the decimal point of the temperature display LED is turned on.

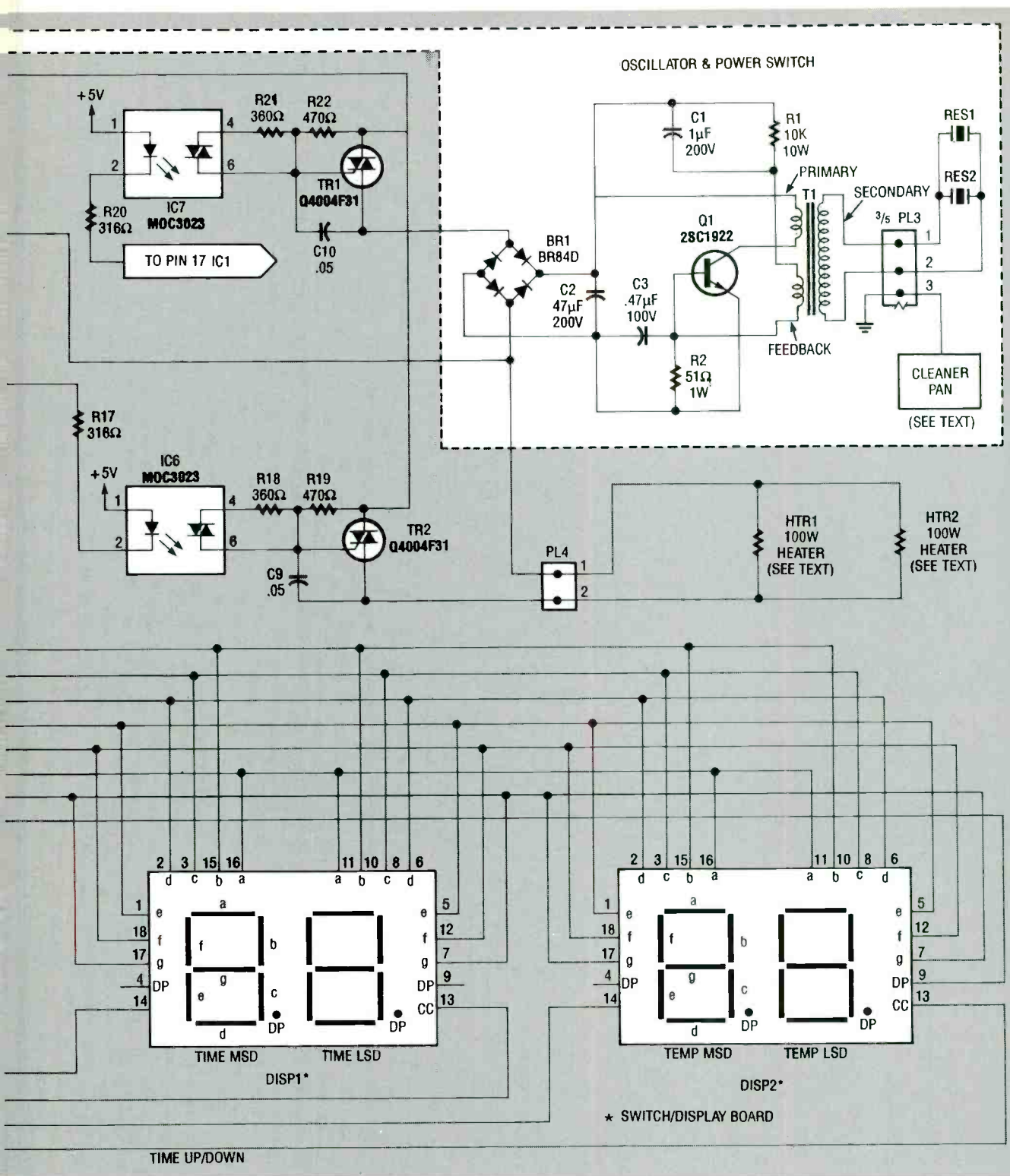The timer circuit or function depends on the internal timing capabilities of the '8751, IC1.





When the START button is pressed, Q2 is energized, powering the transducers. The internally registered time is decremented and displayed, and when zero time is reached, Q2 is turned off and the original time is reset. When the cleaner is turned on, the time is set auto-

matically to 5 minutes, but this setting can be adjusted up or down. Finally, multiplexed segment and digit drive is provided to the displays by IC2, IC3, and current is limited by the eight 120-ohm resistors in network RN1. Power for the control section is

provided by T2, D1, D2, and 5-volt regulator IC8. Further details of the firmware operation can be found by reading the code comments.

**Circuit board assembly**  
Refer to Fig. 4, the two-page schematic for the complete ul-

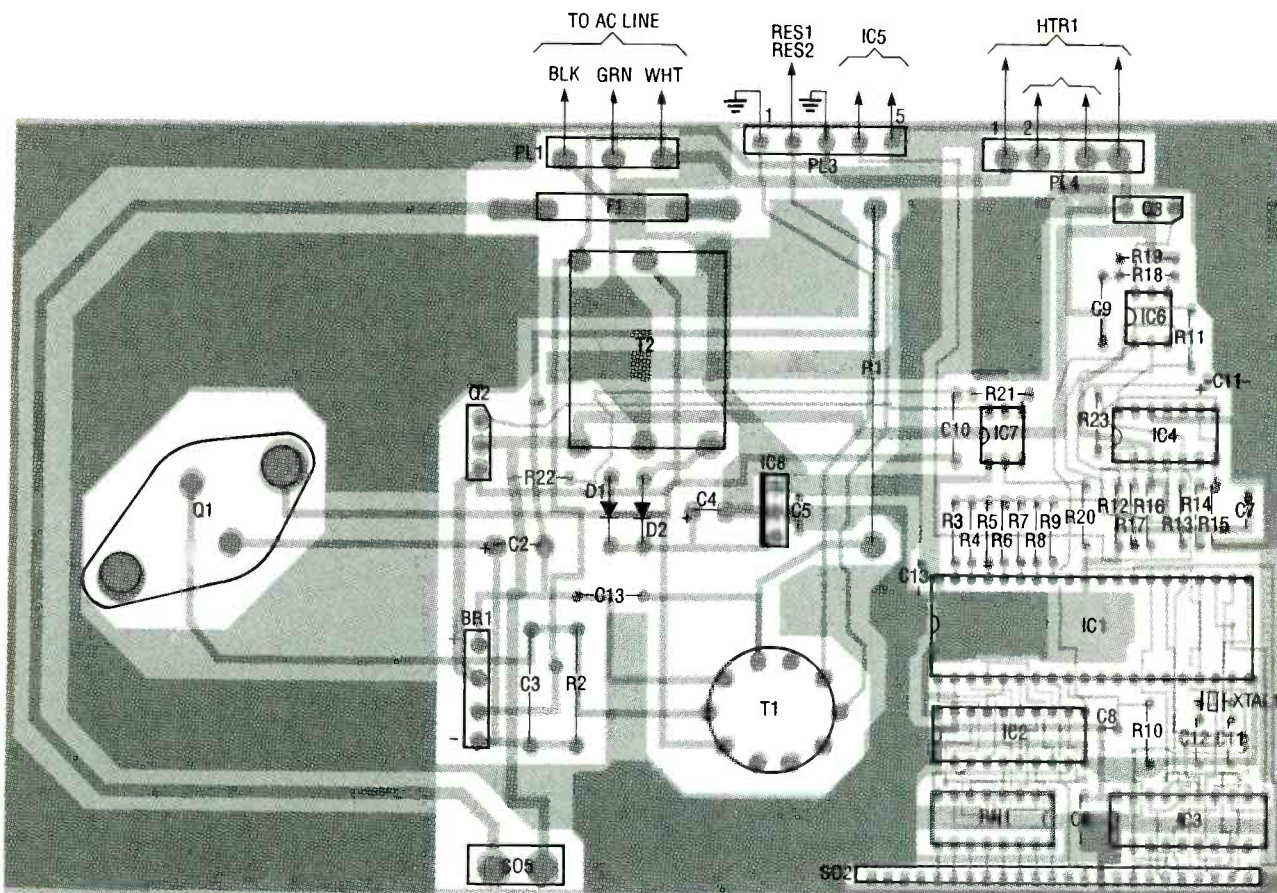


FIG. 5—PARTS PLACEMENT DIAGRAM for large circuit board.



FIG. 6—PARTS PLACEMENT DIAGRAM for switch/display circuit board.

trasonic cleaner. A boundary on the schematic separates the oscillator and power switch circuit from the time and temperature circuits and controls. This permits you to distinguish between the basic circuitry needed to operate the cleaner and the time and temperature control circuitry.

Note that both circuit boards are two-sided. Foils for the parts placement and solder sides of both boards are included here. Making these boards might prove to be a challenge if you have not had much experience fabricating printed circuit boards of this complexity. Therefore, both boards complete with solder masks and through-hole plating are offered in the Parts List.

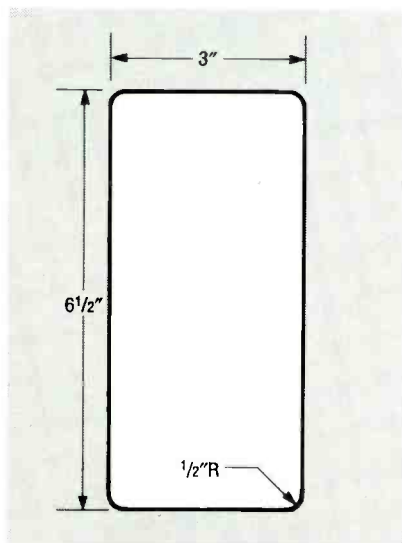


FIG. 7—OUTLINE FOR THE TRANS-DUCER MOUNTING PLATE to be cut from 0.063-inch stainless steel plate.

Refer to Fig. 5, the parts placement diagram for the large board circuit board. The order of component placement on this circuit board is not critical—whether or not you plan to include the time/temperature circuitry and control switches.

The only component on that board not available as a standard catalog item is transformer T1. You can purchase transformer T1 from the same source given in the Parts List or you can wind your own if you choose to do so.

If you choose to wind your own transformer T1, it will be necessary for you to obtain a ferrite core and Litz wire. The core in the prototype is a Ferroxcube 4229-PA275 ferrite core obtainable from Philips Components Discrete Products, Saugerties, NY 12477. The primary winding has 20 turns of 21 strand/36 AWG Litz wire and the secondary has 99 turns of the same wire. Feedback is obtained with 3½ turns of No. 22 AWG wire.

Be sure to double check the values of all the components as you insert them. Power transistor Q1 is positioned on top of the heatsink as shown in Fig. 1, and both parts are fastened to the board with screws at the same time. Insulate Q1 from the



More lessons!

More Services!

# A Shocking Offer!

Now you don't have to be enrolled at CIE to receive our introductory Electronic and Electricity Lesson Modules. This program is available for a limited time to non-students for the shockingly low price of only \$99.50.

With CIE's patented AUTO-PROGRAMMED method of learning you will quickly learn and then master the basics of electronics and electricity and then move on to... DC/AC circuit theories, fundamentals of bi-polar junction transistors (BJT), field effect transistors (FET), wiring, diagram and schematic readings, component identification, soldering techniques... and much, much, more. This introductory offer includes the first 39 lessons in CIE's Associate in Applied Science in Electronic Engineering Technology Degree.


Your commitment to CIE ends with your payment, but CIE's commitment to your success just begins when you receive your lessons, exams, binder and equipment. This special introduc-

tory price includes all the benefits and assistance CIE normally extends to its full time students. You'll be entitled to unlimited access to CIE's faculty and staff to assist you in your studies via a toll free 800 number six days a week, 24-hour turnaround on grading your submitted exams, CIE bookstore privileges, a patented learning method, reference library, access to CIE's electronic bulletin board and a free issue of CIE's school newspaper The Electron.

**And best of all, when you decide to continue your electronics education in any of CIE's programs you'll receive full academic credit for successful lessons**

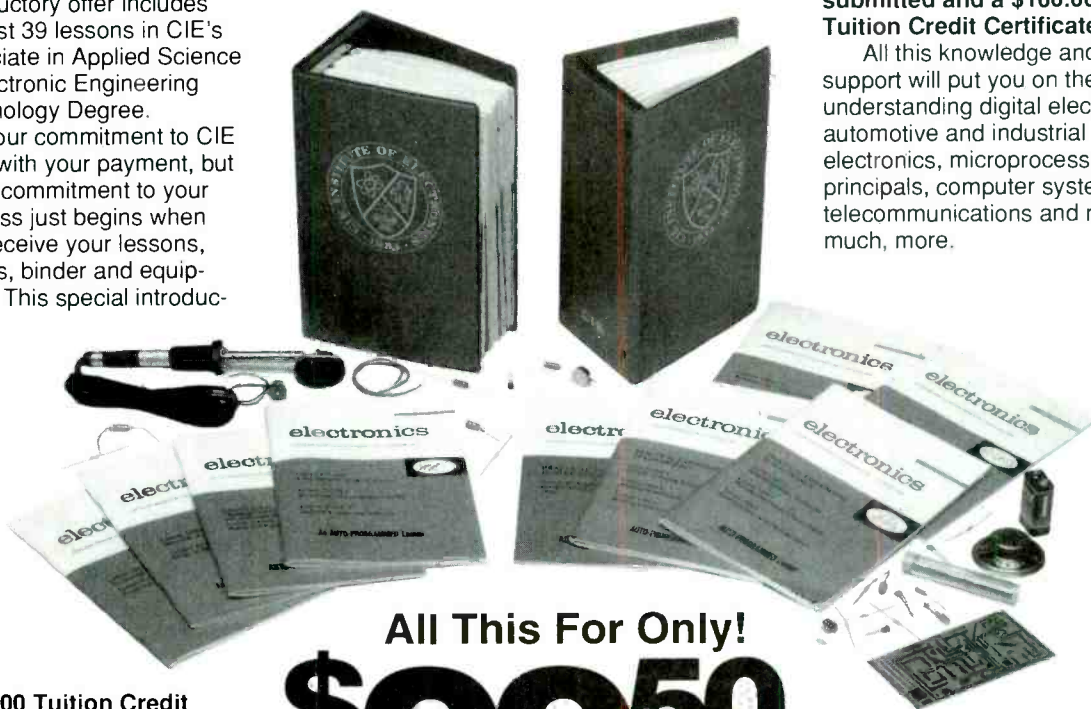**submitted and a \$100.00 Tuition Credit Certificate.**

All this knowledge and support will put you on the road to understanding digital electronics, automotive and industrial electronics, microprocessing principals, computer systems, telecommunications and much, much, more.



All This For Only!

# \$99.50

- \$100.00 Tuition Credit
- Academic Credit
- Free issue of The Electron
- Build your personal burglar alarm
- Toll Free Instructor Assistance
- 24-hour grading
- CIE bookstore privileges

- 39 theory and hands-on training lessons and exams.
- Patented learning method
- CIE electronic bulletin board privileges

**Yes! Send me CIE's Introductory Electronic and Electricity Lessons and Equipment.**

A7319

Name: \_\_\_\_\_

Street: \_\_\_\_\_ Apt#: \_\_\_\_\_

City: \_\_\_\_\_

State: \_\_\_\_\_ Zip: \_\_\_\_\_

Age: \_\_\_\_\_ Phone: (\_\_\_\_) \_\_\_\_\_

Total Merchandise: \_\_\_\_\_ \$99.50

Ohio Residents add 7% Sales Tax: \_\_\_\_\_

California Residents add 6 1/2% Sales Tax: \_\_\_\_\_

Total This Order: \_\_\_\_\_

Shipping and Handling Charge: \_\_\_\_\_ \$5.00

Method of Payment/Amount Enclosed: \_\_\_\_\_ \$

Personal Check or Money Order

Master Card     Visa     Discover

Card Expiration Date: \_\_\_\_\_

Signature: \_\_\_\_\_




**BOOKSTORE**  
1776 East 17th Street  
Cleveland, Ohio 44114



**CHARGE BY PHONE!**

9 AM to 4:30 PM Eastern Time:  
1-800-321-2155 ext. A7319

March 1993, Electronics Now

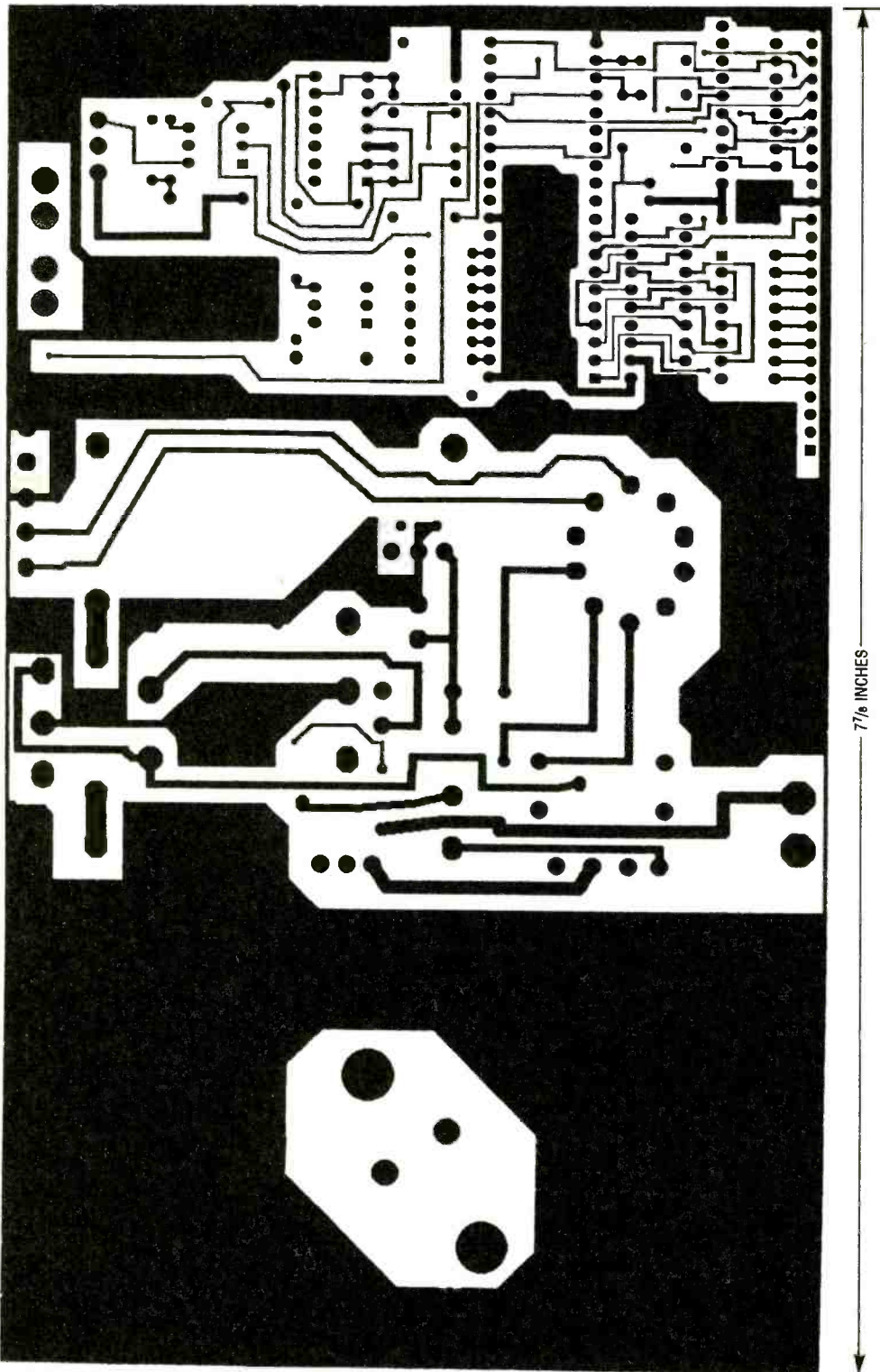

THE FOIL PATTERN FOR THE FRONT (component) side of the main circuit board

heatsink with a mica insulator coated liberally with heatsink grease. After mounting Q1, check its isolation with a meter to be sure that it really is insulated from the other components or conductors.

Mount transformer T1 by the lugs on its frame and connect

its wires individually as indicated in Fig. 4. If you plan to build the cleaner without the time and temperature controls, the positions for those components will remain open. The precision temperature sensor, LM355, (IC5) will be epoxied on the bottom of the stainless steel pan,

and be connected to the board by a twisted pair of wires at P3.

Sockets are recommended for all DIP-style IC's (IC1, IC2, IC3, IC4, IC6, IC7), particularly the microcontroller, IC1. Insert all resistors, capacitors, plugs (three-pin plug, PL1; five-pin plug, PL3; and four-pin plug, PL4), sockets (25-pin socket SO2 and two-pin socket SO5, resistor network, rectifier bridge, Triacs and diodes. Solder all leads and trim excess lead lengths. Examine the circuit board closely to be sure there are no accidental solder bridges or cold joints.

Refer to the parts positioning diagram, Fig. 6, and insert the three switches (S1-S3), the sockets for the two dual-digit, segmented LED displays, DISP1 and DISP2, and the right-angle, 25-pin header PL2. Solder all leads and trim excess. Again, check for inadvertent solder bridges or cold solder joints before inserting the displays.

### Transducer plate and tank

Start the assembly of the tank and transducers by cutting out a +3 x 6 1/2-inch rectangle from 0.062-inch stainless steel plate as shown in Fig. 7. Round the corners to 1/2-inch radiuses, deburr all edges, and sand or grind both sides so the plate will lie flush against the bottom of the stainless steel tray.

Next, prepare both trans-



ducers, RES1 and RES2, for wire attachment by cleaning their surfaces with alcohol or other suitable solvent. Strip about 1/4-inch of insulation from both ends of a pair of 24 to 26 AWG multistrand hook-up wires approximately 12 inches long for transducer connection. Flatten the wires by fanning out their stranded ends, and tin the strands with lead-tin solder.

Carefully solder the fanned out strands of one wire to the centers of each transducer as rapidly as possible to prevent overheating and damaging the ceramic transducer. Then solder a copper wire, approximately 3 inches long to connect the reverse sides of the transducers, observing the same precautions about soldering.


*Note: the transducers are polarized, and both must have the same polarity on top and on the bottom. If this is not observed, the opposing vibrations of each transducer will cancel the effect of the other one.*

After the wires are soldered to the transducers, the next step is to bond the transducers to the rectangular transducer mounting plate. Refer to Figs. 3 and 8 to see how the transducers are positioned on the plate. Mix the two parts of a high quality, slow-setting epoxy and apply a film of it to the plate. Position the transducers on the plate, and while applying slight pressure, rotate them slightly so that

some epoxy underneath the transducers is squeezed out to form a bead of epoxy around the edges of the transducers where they contact the plate.

When the epoxy holding the transducers has set, apply epoxy to the transducer plate assembly and cement it to the

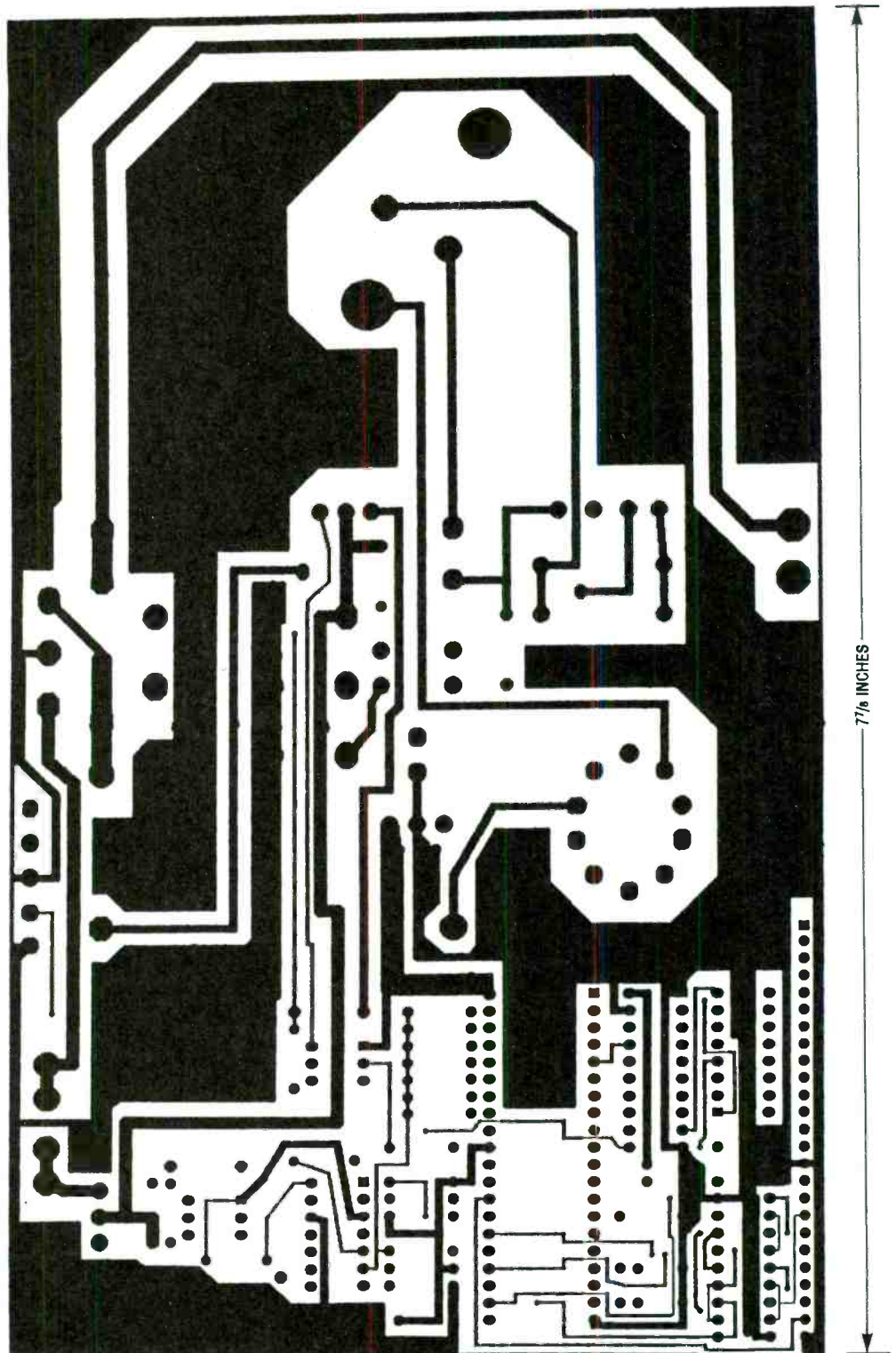bottom of the tank, also as shown in Figs. 3 and 8. If you intend to include the optional temperature control, adhere the two heating elements, HTR1 and HTR2, to the sides of the pan (one is shown in Fig. 3.) Solder or crimp sleeves to the ends of the heater wires. Solder a



THE FOIL PATTERN FOR THE REVERSE (solder) side of the main circuit board

twisted pair of hook-up wire approximately 12 inches long to the LM335 temperature transducer (IC5) and solder or crimp sleeves to the other ends of the four wires. Epoxy temperature sensor IC5 to the bottom of the pan as shown in Fig. 8. Mark the wires to identify their polarity.

### Final wiring and assembly

There are no requirements for the ultrasonic cleaner case. You can make one by assembling a box from 1/4-inch sheet plastic or you can purchase a small 6 × 6 × 9-inch plastic storage bin from your neighborhood hardware or houseware store. The bin will work very well as a protective case.

Pass the bare ends of the three-wire line cord terminated with a three-prong plug through the grommeted hole in the case. Strip the ends of the wires for soldered or crimped sleeves to connect them to three-pronged plug PL1, observing the ground wire. The ON-OFF switch on the switch-display board will perform the switching function when the small board is plugged into the large board through plug PL5.

Install fuse F1 in its holder, and place the large circuit board in the case. Connect the transducer, heater, and temperature transducer wires by pressing their terminating sleeves over the header pins as shown in Fig. 8. Plug the switch/display board into the sockets SO2 and SO5. Carefully check all component values and placement, and all wiring against the schematic, Fig. 4, before carrying out the test and checkout procedures. Make any corrections necessary.

Before operating the ultrasonic cleaner, check to be sure that the pan is grounded to the line cord ground and the primary of transformer T1 is isolated from its secondary and tank circuit.

### Test and checkout procedure

Temporarily support the tank next to the circuit board. Fill the pan at least half full with water. *Caution—Never operate the*

## PARTS LIST

All resistors are 1/4-watt, metalized film, 5 % unless otherwise stated.

- R1—10,000 ohms, wirewound, 10 watt
- R2—51 ohms, wirewound, 1 watt
- R3—86,600 ohms
- R4—42,200 ohms
- R5—21,500 ohms
- R6—10,500 ohms
- R7—5300 ohms
- R8—2610 ohms
- R9—1270 ohms
- R10—8200 ohms
- R11—4640 ohms
- R12, R13—316 ohms
- R14—914 ohms
- R15—1100 ohms
- R16—1000 ohms
- R17, R20—316 ohms
- R18, R21—360 ohms
- R19, R22—470 ohms

### Capacitors

- C1—1μF, 200 volt, polyester film
- C2—47μF, 200 volt, polyester film
- C3—0.47μF, 100 volt, polyester film
- C4—1000μF, 15 volt, aluminum electrolytic
- C5—1μF, 15 volts, aluminum electrolytic
- C6, C7, C14—0.1μF, polyester film
- C8—10μF, 15 volts, aluminum electrolytic
- C9, C10—0.05μF, polyester film
- C11—100μF, 15 volt, aluminum electrolytic
- C12, C13—30 pF

### Semiconductors

- IC1—87C51 CMOS microcontroller with EPROM, Intel or equiv.
- IC2—74AC244PC octal bus driver, non-inverting, National or equiv.
- IC3—74F244 octal bus driver, non-inverting, National or equiv.
- IC4—LM339 quad comparator, National or equiv.
- IC5—LM335 temperature transducer, National or equiv.
- IC6, IC7—GE3023 optoisolator, Harris or equiv.
- IC8—LM340TS (7805) voltage regulator, 1A, Motorola or equiv.
- Q1—2SC1922 power transistor, Hitachi or equiv.
- Q2, Q3—triac, Teccor Q4004F31 or equiv.
- D1, D2—1N4001 silicon diode
- DISP1—LN526GA 7-segment LED display, Panasonic or equiv.
- DISP2—LN526RA 7-segment LED display, Panasonic or equiv.
- BR1—BR840, full wave rectifier bridge, Diodes Inc. or equiv.
- RN1—eight 120 ohm resistor network, CTS9043 or equiv.

### Other component

- F1—fuse, 6 ampere, standard
- HTR1, HTR2—100 watts, 120 volts, Watlow FO20050C7 or equivalent
- S1—switch, rocker, panel-mounted
- S2—switch, miniature toggle, momentary SPST, panel-mounted
- S3, S4—switch, miniature toggle, momentary SPDT, panel-mounted
- XTAL1—11.0592 MHz crystal holder
- T1—transformer, custom wound (see text)
- T2—transformer, EWC Inc. EL-16-260A10 or equiv.
- P1—three-pin header
- P2—25-pin right-angle header
- P3—five-pin header
- P4—four-pin header
- P5—two-pin header
- SO2—25-pin socket
- SO2—2-pin socket
- RES1, RES2—piezoelectric transducers, ceramic, 2-inch, Vernitron 56786 PZT-4 or equiv.

**Miscellaneous:** large and small circuit boards, stainless steel tank (6 7/8 × 4 1/4 × 4 inches, Polarware No.E904 or equiv.), Anodized aluminum heat sink, (4 × 3 × 2 inches), transducer mounting plate (see text), mica insulator for a bipolar power transistor, thermal conductive grease, sockets for IC1, IC2, IC3, IC4, IC5, IC6, IC7, three-wire power cord with 3-prong plug, line cord grommet, fuse holder, case (see text), hookup wire, wire sockets, epoxy, solder.

**Note:** The following parts are available from A&T Labs, P.O. Box 4884, Wheaton, IL 60187:

- Kit of parts for the ultrasonic cleaner without time and temperature controls/displays or case, \$169.00.
  - Kit of all parts for the complete ultrasonic cleaner including programmed 8751 microcontroller except case, \$249.00
  - Double-sided printed circuit boards—large, \$25.00; small, \$9.00
  - Programmed Intel 8751 microcontroller, \$29.00
  - Custom-wound transformer T1, \$69.00
  - Ceramic piezoelectric transducers RES1 and RES2, \$32.00
  - Stainless steel cleaner pan, \$19.00
- Add 6% shipping and handling on all orders paid for by check or money order. Add 10% shipping and handling on all COD orders (U.S. only) via UPS. Illinois residents add 6.75% state sales tax. For all correspondence please include a stamped, self-addressed envelope.

*cleaner unless the pan is at least half full of liquid.* Apply power, and turn on the cleaner. You should hear a hissing sound from the pan and you should be able to feel the vibrations with your fingertips on

the edge of the pan. If you do not hear or feel these operating indications, check for the presence of the primary 160 volts at C1, and +5 volts at C5.

When testing, remember that the primary circuit is connected



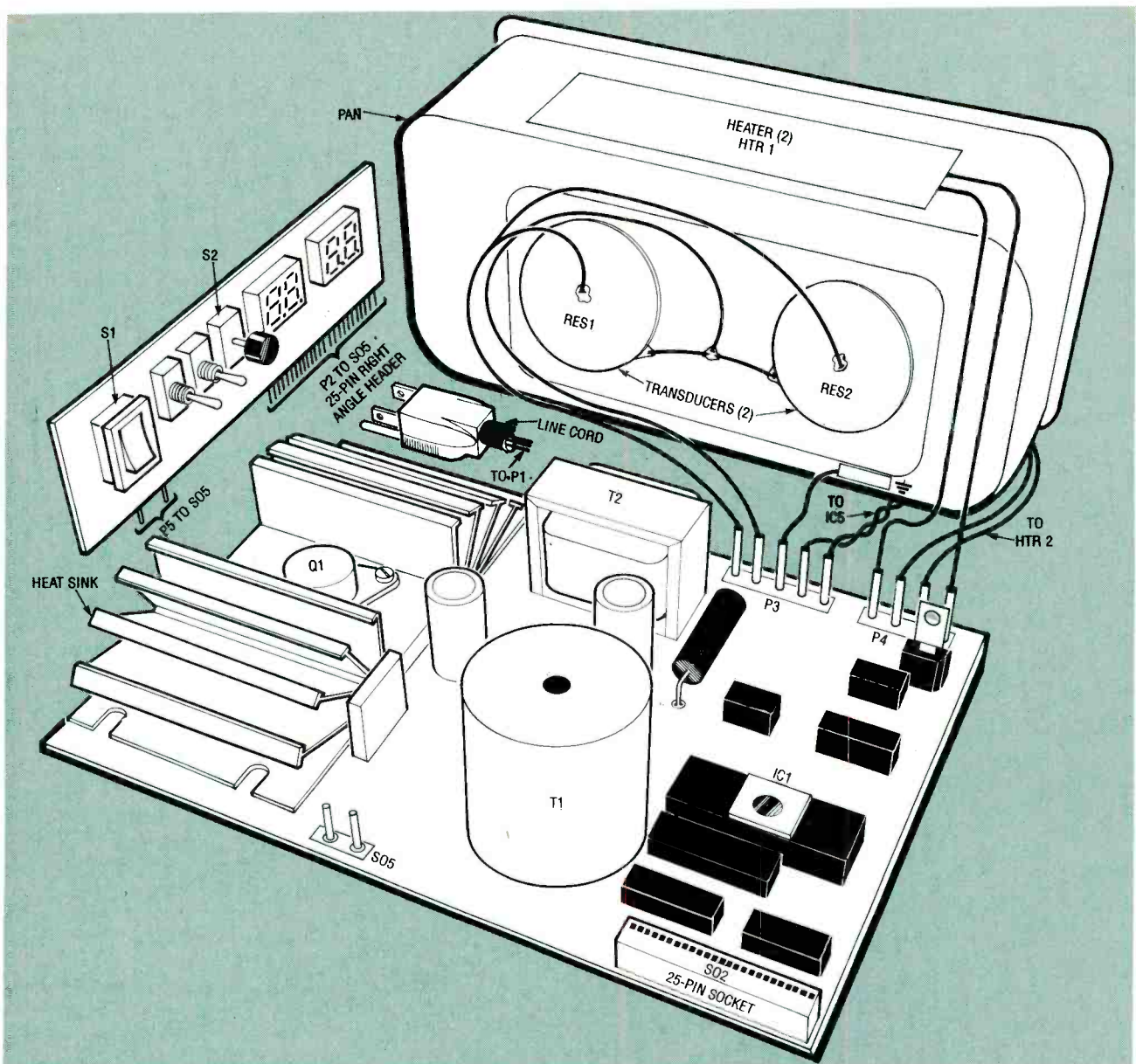


FIG. 8—EXPLODED VIEW showing wiring connections between the main circuit board to the piezoelectric transducers, pan heaters, and temperature sensors mounted on the pan.

to the 120-volt power line, so exercise caution to avoid electric shock. Also, the voltage applied to the transducers is about 1000 volts. If the unit fails to function at turn-on, check for the presence of 11 MHz at pin 18 of the microcontroller IC1, and look for changes in the time and temperature display LED's. At turn-on, those digital displays should readout 5 and 25, respectively.

Although the design frequency should be close to optimal, further adjustment could improve efficiency. Perform any additional tuning by turning the

slug core of transformer T1. Adjust it gradually until you are able to observe maximum turbulence in the cleaning fluid. One way to determine a maximum is by adding a drop of food coloring to the water, and adjusting for maximum dispersion rate of the color in solution.

#### Cleaner operation

You can purchase cleaning fluids from hardware, auto parts, and grocery stores, but you can also easily mix your own. You might want to experiment with cleaning mixtures. A general rule of thumb is that

any cleaning solution that works satisfactorily in cleaning objects by hand methods will also work in the ultrasonic cleaner. Liquid detergent in water, for example, is a good general cleaner, while ammonia in water works well for jewelry. Carburetor cleaner cleans carburetors and other automotive, bicycle or machine parts that are coated with oily or greasy contaminants.

Before cleaning any object in the ultrasonic cleaner, it is a good idea to remove as much surface dirt and grime as possible manually with paper towels, brushes, or cotton rags to minimize the contamination entering the cleaning solution. The

# For your Heart's sake get **PULSE STICK II**


**Y**our very own sophisticated pocket health monitor, PULSE STICK II, checks your pulse rate quickly and accurately anywhere. Regular monitoring of your pulse rate during exercise will enable you to plan an exercise regimen suitable for your stage of fitness. pulse stick II provides an early warning that you may be exceeding your own capabilities.

PULSE STICK II photoelectrically measures the changes

in the pulsed intensity of infrared radiation emitted by superficial blood vessels below the skin of the thumb. The time intervals between pulses are automatically measured and analogued by the micro-processor based circuitry and displayed in a liquid-crystal display (LCD).

Before attempting any exercise program, consult your doctor. Ask for guidance regarding the recommended safe pulse ranges for your exercise program. Follow your doctor's instructions carefully.

Only  
**\$39<sup>95</sup>**

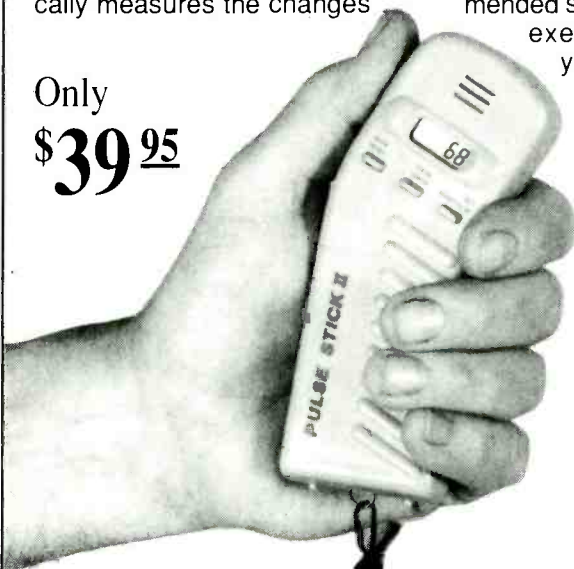

Uses three AA dry cells supplied with PULSE STICK II



Ideal for running, walking and aerobic training programs!

cleaner is most effective in cleaning hard-to-reach recessed areas. Place the parts to be cleaned in the pan filled with the cleaning solution, and turn on the cleaner. Experiment with various objects to determine their optimum cleaning time.

If the cleaning solution is to be heated, turn the main power on first to allow the solution to reach its set temperature. Time and temperature values are set by pushing the up/down buttons.

## Precautions

The cleaner operates from 120-volt line power and there are liquids present; together these pose an added electric shock hazard if proper grounding is not maintained. Moreover, some cleaning solutions and their vapors can be toxic. Other precautions are:

- *The use of flammable cleaning fluids is not recommended.* If they are used, exercise all reasonable precautions by moving the cleaner out of doors and never leave it unattended while the fluid is in the pan. Be sure to return all toxic fluids to a safe storage container when cleaning is complete. *Never use gasoline as a cleaning fluid!*
- Never put your hands into the cleaning solution when the cleaner is on. The intense vibrations can drive particulates into your skin, and the ultrasonic energy could damage body tissues.
- Minimize any time spent close to the operating cleaner because the high-frequency 40-kHz oscillations can cause headaches and might lead to hearing impairment although they are not audible.
- Be sure that the pan is at least half filled with solution during all cleaning operations.
- Place any objects to be cleaned carefully in the pan with tongs, and take care not to drop any heavy object in the pan that could damage the fragile transducers.
- The use of chlorofluorocarbon (CFC) solvents, commonly used to remove solder paste from circuit boards, is not recommended because of their threat to the environment.   Ω

PSII-2

**YES!** Please send me \_\_\_\_\_ PULSE STICK II at \$39.95 each. Price includes shipping and handling charges.

Total amount of order \$ \_\_\_\_\_

Check or Money Order enclosed. Make check payable to **CLAGGK Inc. PULSE STICK II Offer**

Charge my  Visa  MasterCard

Account No. \_\_\_\_\_

Exp. Date \_\_\_\_ / \_\_\_\_

Credit Card Signature \_\_\_\_\_

Print Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

No telephone orders or C.O.D. Signature required on credit card orders. All prices include postage and handling. Payments in U.S.A. funds only. New York residents must include local applicable sales taxes. No foreign orders.

**Mail orders** to CLAGGK Inc. Pulse Stick II Offer, P.O. Box 4099, Farmingdale, NY 11735.

**FAX orders** to 1-516-293-3115.



# Take this GIANT Handbook for only \$9.95


when you join the *Electronics Engineers' Book Club*®

## ELECTRONICS ENGINEERS' HANDBOOK, Third Edition

Edited by D.G. Fink  
and D. Christiansen

Completely revised, expanded, and updated, this third edition of the desktop reference is widely considered the definitive work in its field, covering all aspects of today's electronics engineering. Written and compiled by more than 170 experts, this giant handbook shows you how to use the latest design and cost-cutting solutions at work in the industry today. You'll find a wealth of new material on electronic systems design, computer systems and digital recording, telecommunications, process control, laser technology, and CAD of electronic circuits. It deals with the full range of theory and practice, covering essential principles, data, devices, components, assemblies, circuits, functions, and applications.

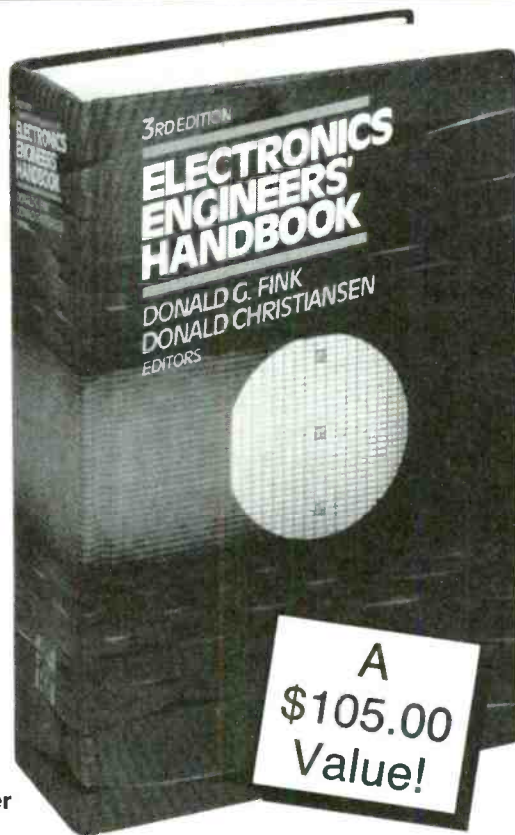2,624 pages 1,800 illustrations **Book No. 9255H Hardcover**



If coupon is missing, write to: Electronics Engineers' Book Club, Blue Ridge Summit, PA 17294-0860

### As a member of the Electronics Engineers' Book Club . . .

. . . you'll enjoy receiving Club bulletins every 3-4 weeks containing exciting offers on the latest books in the field at savings of up to 50% off of regular publishers' prices. If you want the Main Selection do nothing and it will be shipped automatically. If you want another book, or no book at all, simply return the reply form to us by the date specified. You'll have at least 10 days to decide. And you'll be eligible for *FREE BOOKS* through the *NEW Bonus Book Plan*. Your only obligation is to purchase 3 more books during the next 2 years, after which you may cancel your membership at any time.

Publisher's price shown. ©1993 EEBC

### **ELECTRONICS ENGINEERS'** BOOK CLUB

Blue Ridge Summit, PA 17294-0860

**YES!** Please send me *Electronics Engineers' Handbook, 3rd Ed.* (9255H), billing me \$9.95 plus shipping/handling & tax. Enroll me as a member of the **Electronics Engineers' Book Club** according to the terms outlined in this ad. If not satisfied, I may return the book within 10 days and have my membership cancelled. A shipping/handling charge & sales tax will be added to all orders.

Name \_\_\_\_\_

Address \_\_\_\_\_

City/State \_\_\_\_\_

Zip \_\_\_\_\_ Phone \_\_\_\_\_

Valid for new members only, subject to acceptance by EEBC. Canada *must* remit in U.S. funds drawn on U.S. banks. Applicants outside the U.S. and Canada will receive special ordering instructions. RPIF393

# Countersurveillance

**Never before has so much professional information on the art of detecting and eliminating electronic snooping devices—and how to defend against experienced information thieves—been placed in one VHS video. If you are a Fortune 500 CEO, an executive in any hi-tech industry, or a novice seeking entry into an honorable, rewarding field of work in countersurveillance, you must view this video presentation again and again.**

*Wake up!* You may be the victim of stolen words—precious ideas that would have made you very wealthy! Yes, professionals, even rank amateurs, may be listening to your most private conversations.

*Wake up!* If you are not the victim, then you are surrounded by countless victims who need your help if you know how to discover telephone taps, locate bugs, or “sweep” a room clean.

There is a thriving professional service steeped in high-tech techniques that you can become a part of! But first, you must know and understand Countersurveillance Technology. Your very first insight into this highly rewarding field is made possible by a video VHS presentation that you cannot view on broadcast television, satellite, or cable. It presents an informative program prepared by professionals in the field who know their industry, its techniques, kinks and loopholes. Men who can tell you more in 45 minutes in a straightforward, exclusive talk than was ever attempted before.

## Foiling Information Thieves

Discover the targets professional snoopers seek out! The prey are stock brokers, arbitrage firms, manufacturers, high-tech companies, any competitive industry, or even small businesses in the same community. The valuable information they filch may be marketing strategies, customer lists, product formulas, manufacturing techniques, even advertising plans. Information thieves eavesdrop on court decisions, bidding information, financial data. The list is unlimited in the mind of man—especially if he is a thief!

You know that the Russians secretly installed countless microphones in the concrete work of the American Embassy building in Moscow. They converted



**CALL NOW!**

**1-516-293-3751**

**HAVE YOUR VISA or MC CARD AVAILABLE**

what was to be an embassy and private residence into the most sophisticated recording studio the world had ever known. The building had to be torn down in order to remove all the bugs.

## Stolen Information

The open taps from where the information pours out may be from FAX's, computer communications, telephone calls, and everyday business meetings and lunchtime encounters. Businessmen need counselling on how to eliminate this information drain. Basic telephone use coupled with the user's understanding that someone may be listening or recording vital data and information greatly reduces the opportunity for others to purloin meaningful information.

The professional discussions seen on the TV screen in your home reveals how to detect and disable wiretaps, midget radio-frequency transmitters, and other bugs, plus when to use disinformation to confuse the unwanted listener, and the technique of voice scrambling telephone communications. In fact, do you know how to look for a bug, where to look for a bug, and what to do when you find it?

Bugs of a very small size are easy to build and they can be placed quickly in a matter of seconds, in any object or room. Today you may have used a telephone handset that was bugged. It probably contained three bugs. One was a phony bug to fool you into believing you found a bug and secured the telephone. The second bug placates the investigator when he finds the real thing! And the third bug is found only by the professional, who continued to search just in case there were more bugs.

The professional is not without his tools. Special equipment has been designed so that the professional can sweep a room so that he can detect voice-activated (VOX) and remote-activated bugs. Some of this equipment can be operated by novices, others require a trained countersurveillance professional.

The professionals viewed on your television screen reveal information on the latest technological advances like laser-beam snoopers that are installed hundreds of feet away from the room they snoop on. The professionals disclose that computers yield information too easily.

This advertisement was not written by a countersurveillance professional, but by a beginner whose only experience came from viewing the video tape in the privacy of his home. After you review the video carefully and understand its contents, you have taken the first important step in either acquiring professional help with your surveillance problems, or you may very well consider a career as a countersurveillance professional.

## The Dollars You Save

To obtain the information contained in the video VHS cassette, you would attend a professional seminar costing \$350-750 and possibly pay hundreds of dollars more if you had to travel to a distant city to attend. Now, for only \$49.95 (plus \$4.00 P&H) you can view *Countersurveillance Techniques* at home and take refresher views often. To obtain your copy, complete the coupon or call.

**EN**

**CLAGGK INC.**  
**P.O. Box 4099 • Farmingdale, NY 11735**

Please rush my copy of the Countersurveillance Techniques Video VHS Cassette for a total cost of \$53.95 each (which includes \$4.00 postage and handling).

No. of Cassettes ordered \_\_\_\_\_  
 Amount of payment \$ \_\_\_\_\_  
 Sales tax (N.Y.S. only) \_\_\_\_\_  
 Total enclosed \_\_\_\_\_  
 Bill my  VISA  MasterCard  
 Card No. \_\_\_\_\_  
 Expire Date \_\_\_\_ / \_\_\_\_  
 Signature \_\_\_\_\_  
 Name \_\_\_\_\_  
 Address \_\_\_\_\_  
 City \_\_\_\_\_ State \_\_\_\_\_ ZIP \_\_\_\_\_

All payments in U.S.A. funds. Canadians add \$4.00 per VHS cassette. No foreign orders.



## RAY MARSTON

FIELD-EFFECT TRANSISTORS (FET'S) are unipolar rather than bipolar devices, and this gives them certain properties that are superior to those of bipolar transistors. Unlike the bipolar transistor, whose current depends on the movement of both electrons and holes, FET operation depends on only one of those charge carriers. Freed from the time delays that occur when those charge carrier recombine, FET's offer faster switching speed and higher cutoff frequencies.


Other advantages of the FET include:

- Voltage rather than current operation.
- Extremely high input impedance in the OFF state.
- Virtually constant current with respect to voltage at specific bias levels.
- Current change that is inversely rather than directly proportional to temperature.

Despite these advantages, the FET has not replaced the bipolar the bipolar transistor in all applications, but it has encouraged new generations of small-signal and general purpose and RF MOSFET's as well as general purpose and RF MOSFET power transistors. Moreover, the latest digital logic families are based on FET technologies. The basic FET is a simple, three-terminal, voltage-controlled device with characteristics that are similar to those of vacuum-tube pentodes. Thus, the FET is considered to be the solid-state equivalent of a pentode.

The two major classes of FET's are the *junction* FET (JFET) and *metal-oxide-semiconductor* FET (MOSFET), formerly called an *insulated-gate* FET (IGFET). FET's are further divided into *N-channel*, *P-channel*, *depletion-mode* and *enhancement-mode* devices. MOSFET's with N-doped channels are called NMOS, and those with P-doped channels are referred to as PMOS.

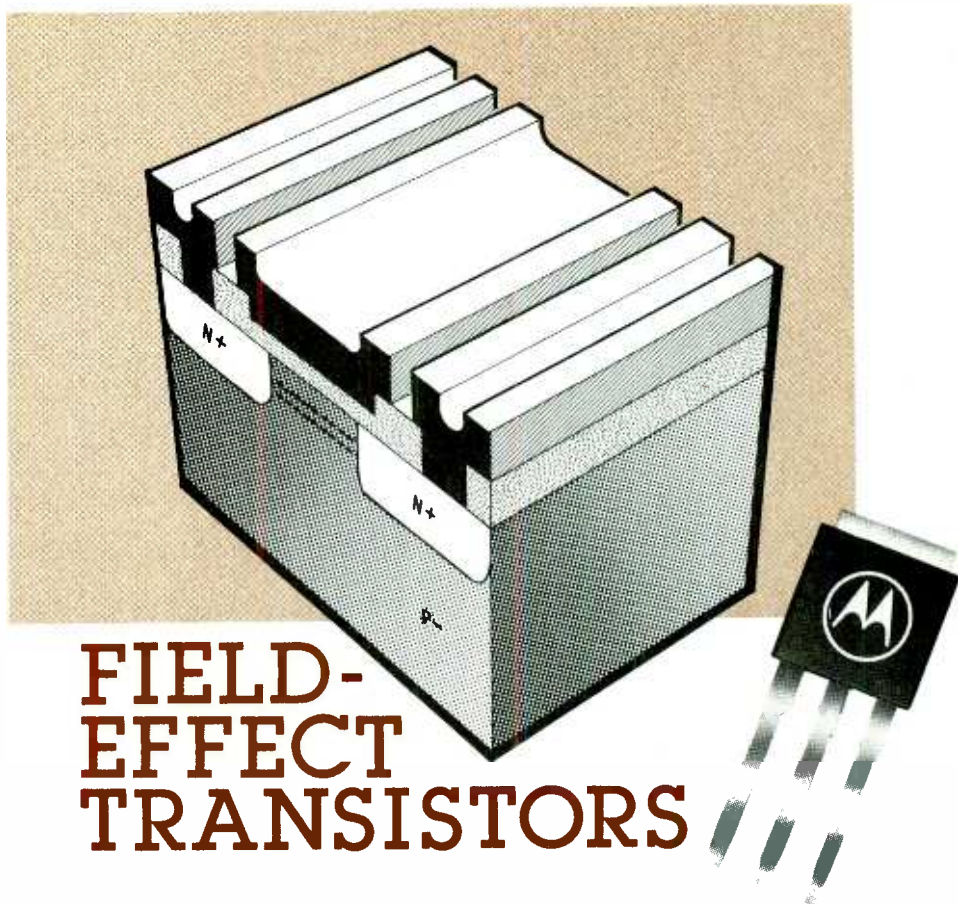The three electrodes in all FET's are the *source*, *drain*, and *gate*, analogous to the emitter,



# FIELD-EFFECT TRANSISTORS

**Learn about field-effect transistors: JFET's, MOSFET's, DMOS MOSFET's and CMOS—how they are made, how they work, and what to look for when selecting them for your designs.**

collector, and base of the bipolar transistor. Both JFET's and MOSFET's are available as discrete transistors. Some MOSFET's have dual gates and are intended for use as radio-frequency mixers.

This article explains how P-channel and N-channel MOSFET's are combined to form the popular complementary-MOS (CMOS) digital logic families. CMOS technology has made possible very large scale integrated (VLSI) memories, microprocessors and dedicated circuits that contain more than one million transistors and still have very low power requirements.

Most small-signal FET's today

are fabricated with *planar* geometry in which all electrodes are accessible from the top of the device. The active regions are defined on the wafer or substrate by successive masking, etching, and deposition or ion-implantation steps. But power MOSFET's now being fabricated with vertical structures are actually capable of handling much higher current in smaller areas of silicon.

### Junction FET's

The simplest FET, the JFET, is illustrated by the cross-section view of Fig. 1-a. It is made by selectively implanting or diffusing ions into the wafer or substrate. An N-type region is

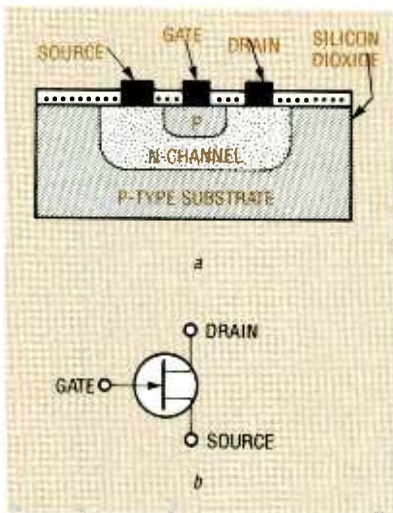


FIG. 1—N-CHANNEL PLANAR JFET showing diffused or implanted channel and gate regions (a), and schematic symbol (b).

defined on the P-type substrate by photolithographic methods, and N-type ions are implanted to form the N-channel. Later in the manufacturing process, following further masking, oxide-deposition and etching steps, P-type ions are implanted or diffused into the N-channel to form the P-type gate.

Aluminum source and drain terminals are formed directly on the N-channel and an aluminum gate terminal is formed on the P-type gate. The symmetrical construction of the JFET permits the drain and source to be interchanged, if necessary.

If a positive voltage is applied at the drain of the N-channel JFET shown in Fig. 1-a, and a negative voltage is applied at the source with the gate terminal open, a drain current flows. When the gate is biased negative with respect to the source, the PN junction is reverse biased, and a depletion region, devoid of current carriers, is formed.

Because the N-channel is more lightly doped than the P-type gate material, the depletion region penetrates into the N-channel. This region, depleted of charge carriers, behaves like an insulator. The depletion region narrows the N-channel and increases its resistance. If the gate bias is made even more negative, drain current is cut off

completely.

The gate-bias voltage that cuts off the drain current is called the *pinch-off* or *gate-cut-off* voltage. However, as the bias becomes positive, the depletion region recedes, the channel resistance is reduced, and drain current increases. Thus, the JFET gate actually controls JFET current.

The schematic symbol for the N-channel JFET is shown in Fig. 1-b. As in other schematic symbols for solid-state devices, the arrowhead (representing the direction of conventional

current flow) points from P-doped material to N-doped material. In the N-channel JFET symbol, the arrowhead points from the P-type gate toward the N-type channel.

A section view of a P-channel JFET is shown in Fig. 2-a. The channel of the device is P-type material, and the gate is N-type. If a positive voltage is applied to the source, conventional current flows from the source to the drain. To reverse bias the junction between the N-type gate and the P-type channel, the gate must be made positive with respect to the channel. The biasing voltages of a P-channel JFET are opposite to those of the N-channel JFET.

The schematic symbol for the P-channel JFET is shown in Fig. 2-b. The arrowhead also points from P-type material to N-type material. In this instance, it points from the P-type channel to the N-type gate region. The characteristics of the P-channel JFET are similar to those of the N-channel device, except that the voltage and current polarities are reversed.

Both N-type and P-type JFET's operate in the *depletion* mode; that is, they conduct with zero bias on their gates. Figure 3 shows a typical family of *drain characteristics* for an N-channel JFET. As the gate-to-

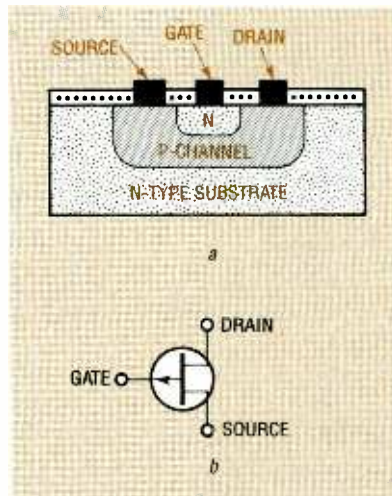


FIG. 2—P-CHANNEL PLANAR JFET showing diffused or implanted channel and gate regions (a), and schematic symbol (b).

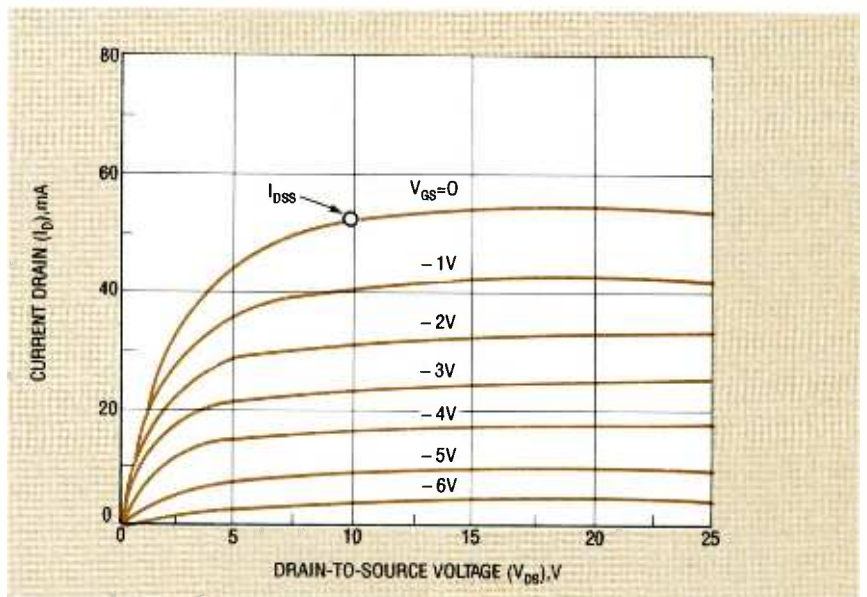


FIG. 3—DRAIN CHARACTERISTICS FOR AN N-CHANNEL JFET. The family of gate curves has its origin at zero drain-to-source volts, and the gate bias values show voltage control.



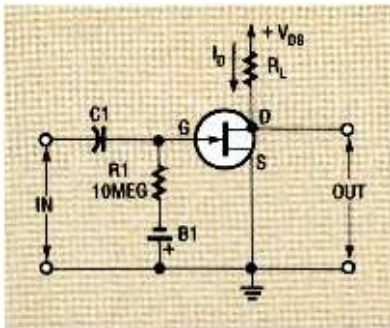


FIG. 4—N-CHANNEL JFET COMMON-source amplifier is analogous to a bipolar common-emitter amplifier.

source voltage is made increasingly negative, the depletion region is increased, and drain current decreases. As a result, pinchoff voltage occurs at a lower value of  $V_{DS}$ . Curves for different values of gate-to-source bias,  $V_{GS}$ , are plotted in the figure because the FET is a voltage-operated device.

#### JFET circuits

When an N-channel JFET is connected to a  $V_{DS}$  supply as shown in Fig. 4, a drain current,  $I_D$ , flows in the device. The magnitude of  $I_D$  can be controlled by a gate-to-source bias voltage,  $V_{GS}$ . Similarly, when a P-channel JFET is connected to a negative drain voltage, a drain current,  $I_D$ , flows in the device. The value of  $I_D$  is maximum when  $V_{GS}$  equals zero, and it is reduced (to bring the JFET into a linear operating region) by applying a reverse bias to the gate terminal of the device (negative bias in a N-channel device, positive bias in a P-type).

In Fig. 3, the value of  $V_{GS}$  to reduce  $I_D$  to zero, the gate-to-source pinchoff voltage  $V_P$ , is about -7 volts. The value of  $I_D$  when  $V_{GS}$  equals zero (called  $I_{DSS}$  or drain saturation current for zero bias) is about 52 milliamperes for the device shown in the figure.

The gate-to-source junction of the JFET has the characteristics of a silicon diode. When reverse biased (to bring it into its linear operating region), gate leakage currents ( $I_{GSS}$ ) are measured in thousandths of a microampere at room temperature. Actual gate signal currents are only a fraction of a

that, and the input impedance to the gate is typically 1000 megohms at low frequencies. The gate junction is effectively shunted by a capacitance of a few picofarads, so input impedance falls as input frequency is increased.

If the gate-to-source junction of the JFET is forward biased, it conducts like a normal silicon diode, and if it is severely reverse biased it avalanches like a Zener diode. Neither of those conditions will harm a JFET if its gate currents are limited to those specified.

Referring to the N-channel JFET drain characteristics in Fig. 3, it can be seen that, for each value of  $V_{GS}$ , drain current  $I_D$  rises linearly from zero as the

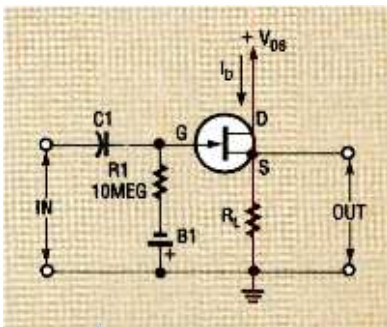


FIG. 5—N-CHANNEL JFET COMMON-drain (source-follower) amplifier is analogous to a bipolar emitter-follower amplifier.

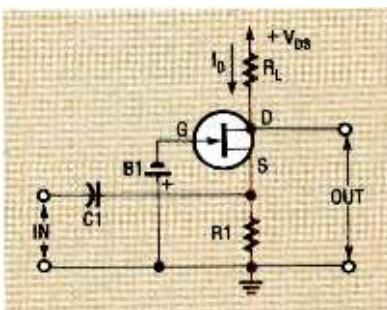


FIG. 6—N-CHANNEL JFET COMMON-gate amplifier is analogous to a bipolar common-base amplifier.

drain-to-source voltage ( $V_{DS}$ ) is increased from zero to a value at which a *knee* occurs on each curve. Moreover,  $I_D$  remains virtually constant as  $V_{DS}$  is increased beyond where the knee occurs.

Thus, when  $V_{DS}$  for any of the family of  $V_{GS}$  curves is below its knee value, the drain-to-source

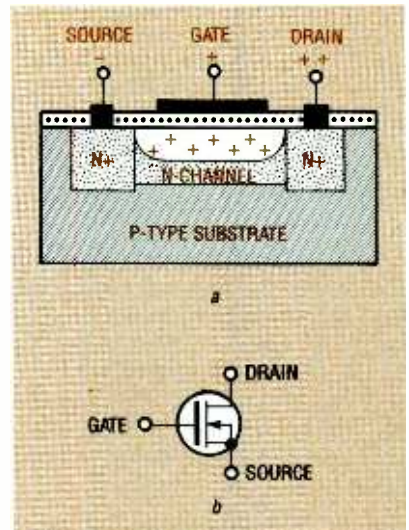


FIG. 7—N-CHANNEL, DEPLETION-mode MOSFET with negative gate bias (a), and schematic symbol (b).

pins of the JFET act like a voltage-variable resistor with its value determined by  $V_{GS}$ . The drain-to-source resistance,  $R_{DS}$ , can be varied from several hundred ohms at  $V_{GS} = \text{zero}$  to thousands of megohms at pinchoff. That characteristic permits the JFET to be used in a circuit as a voltage-controlled switch.

From the drain characteristic curve of Fig. 3, it can be seen that when  $V_{DS}$  is above the knee value, the  $I_D$  value is dictated primarily by the  $V_{GS}$  value, and is virtually independent of the  $V_{DS}$  value. This characteristic permits the JFET to function as a voltage-controlled current generator.

The *gain* of a JFET is specified as a *transconductance*,  $g_m$ , the rate of change of drain current with respect to gate voltage. A  $g_m$  of 5 milliamperes per volt indicates that a variation of one volt on the gate produces a change of 5 milliamperes  $I_D$ . The units of this measurement are in inverse ohms or *mhos*. You will find that JFET data sheets usually specify  $g_m$  in millimhos or micro-mhos.

The N-channel JFET in Fig. 4 is organized as a common-source amplifier, analogous to a bipolar NPN common-emitter amplifier. In typical applications, the JFET is biased into its linear region and organized

as a voltage-to-voltage converter or amplifier. As shown in Fig. 4, a load resistor of suitable value,  $R_L$ , should be placed in series with the JFET's drain-to-source current.

Another common JFET configuration is the *common drain* or *source-follower* configuration shown in Fig. 5. That configuration is analogous to the bipolar emitter-follower configuration. Yet another possible JFET configuration is the *common-gate* configuration shown in Figure 6. That configuration is analogous to a bipolar common-base configuration.

### MOSFET's explained

The metal-oxide FET or MOSFET was developed as an improvement on the JFET, and it has become the most important form of FET. Figure 7-a illustrates an N-channel depletion-mode MOSFET with a negative gate bias. The gate of this MOSFET is fully insulated from the adjacent channel. This is the most important distinction between an N-type depletion-mode MOSFET and an N-type JFET, which is manufactured with a doped gate region directly under and in contact with the gate.

The surface of the silicon P-type wafer is first coated with a layer of silicon dioxide ( $\text{SiO}_2$ ), and the source and drain windows are masked and etched to expose the P-type substrate. N-dopants are heavily diffused or implanted into those two regions. Another window is masked and etched over the channel, and it is given a lighter concentration of N dopant. In subsequent steps, the channel is recoated with an insulating oxide, and the metal source, drain, and gate terminals are deposited.

When the drain is positive with respect to the source, a drain current will flow, even with zero gate voltage. However, if the gate is made negative with respect to the substrate, positive charge carriers (holes) induced in the N-channel will combine with the electrons and cause channel resistance to increase. With increasing nega-

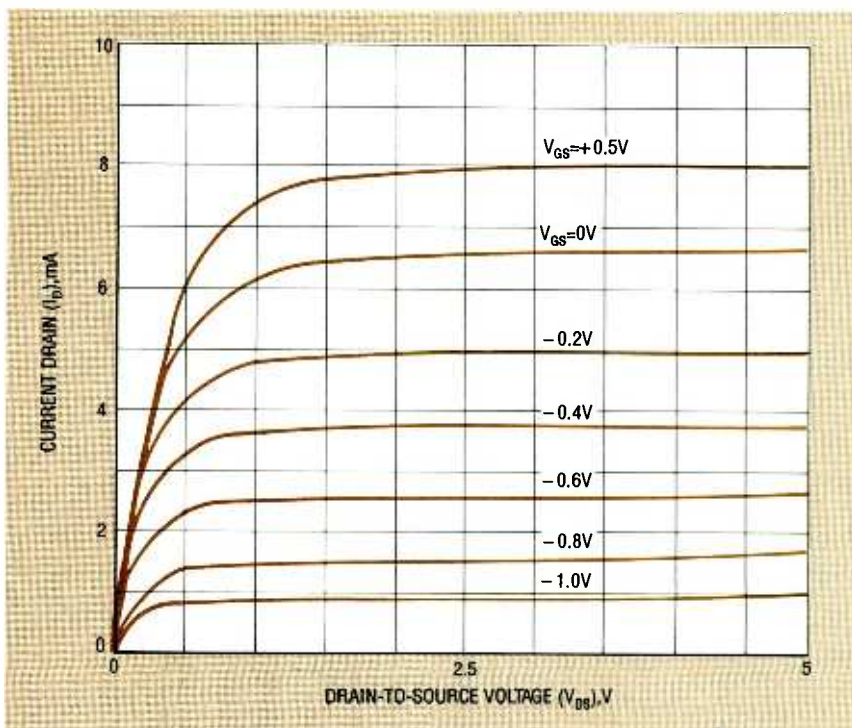


FIG. 8—DRAIN CURVES FOR N-CHANNEL DEPLETION-MODE MOSFET showing the effects of positive and negative bias

tive bias, the pinchoff voltage will be reached, and drain current will cease. However, if the gate is made positive with respect to the substrate, additional electrons are induced, and the channel current then increases.

The schematic symbol for the N-type depletion-mode MOSFET is shown in Fig. 7-b. The path or channel between the source and drain is shown as a solid bar. The symbol for the P-channel depletion-mode MOSFET is identical to the N-type, except that the arrow points outwards.

Figure 8 is a drain-to-source characteristic curve for an N-channel depletion-mode MOSFET. It can be seen that the current drain,  $I_D$ , is inversely proportional to the magnitude of the negative gate voltages,  $V_{GS}$ . Compare Fig. 8 with Fig. 3 for the N-channel JFET to see their similarities.

Planar *enhancement-mode* MOSFET's are made by the same methods as planar depletion-mode MOSFET's. However, the N-channel enhancement-mode MOSFET shown in Fig. 9 does not have the N-doped drain-to-source channel through the P-type substrate of

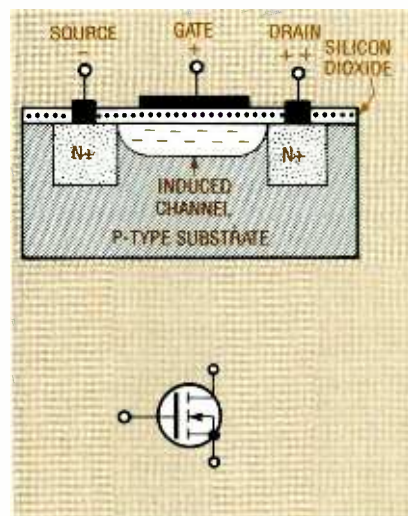


FIG. 9—N-CHANNEL ENHANCEMENT-mode MOSFET with positive grid bias (a), and schematic symbol (b).

the N-channel depletion-mode MOSFET. Therefore, there is no conduction between drain and source at zero gate bias.

To turn an enhancement-mode MOSFET on, positive gate bias is needed. As the gate voltage is increased, more electrons are induced into the channel. They cannot flow across the oxide layer to the gate, so they accumulate at the substrate surface below the gate oxide. When a sufficient number of



# Electronic SHOPPER™

## COLLINS 490T-1

490T-1 (CU-1669) AUTOMATIC ANTENNA COUPLER for 2-30 MHz range; 600 W PEP, 200 W average. Use with 20 ft whip or 25-100 ft long-wire antenna. Terminal for wire and "C" coax connection. Has 5-500 pf 10 KW vacuum capacitor and variable step-coil. Requires 115 V 400 Hz; 7.6x10.1x12.6, 24 lbs.

USED-NOT TESTED ..... \$300  
MANUAL for CU-1669 ..... \$15 w/set purchase



## BC-348R RECEIVER


BC-348R RECEIVER, late WW-2 & Korean War vintage receiver covers 200-500KHz & 1.5-18 MHz AM-CW in six bands. Has BFO, crystal filter, AVC, and DM-28 28 VDC dynamotor. No PL103 plug. 9.5x18x10.5, 44 lbs.

USED-REPARABLE ..... \$165  
MANUAL, partial repro ..... \$10


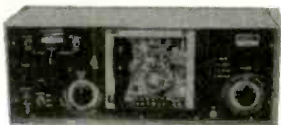
## COLLINS HF POWER AMP DECK

COLLINS HF POWER AMP DECK, AM 367A-3 amplifies 0.15 W input to 500 W output using two 4CX250B tubes over 2-30 MHz in four bands. Verniers for driver and PA tune. Requires +2000 V 500 ma, +400 V 80 ma, & +28 V. 7x19x7.8, 25 lbs sh. USED W/SCHEMATIC ... \$235



## HP-8640B opt 323 RF GENERATOR

Rugged military version of HEWLETT-PACKARD 8640B; covers 500 KHz to 512 MHz AM/FM/Pulse in 10 ranges using 6-digit LED readout. Output: 0.013 uv to 2 V (-144 to +19 DBM). Modulation 400, 1K and 5K Hz. Does NOT have phase-lock, X100 resolution expand or external input like standard HP-8640B. Mounted in transit case; w/manual

copy. Requires 103-127/207-242 VAC 48-440 Hz; 7.8x19.5x22.4, 70 lbs sh.

USED-CHECKED ..... \$1250

10 DB SMA ATTENUATOR, gold-plated; Elcom AT53-10, NEW ..... \$14.95

Prices F.O.B. Lima, O. • VISA, MASTERCARD Accepted.

Allow for Shipping • Write for latest Catalog Supplement

Address Dept. ES • Phone 419/227-6573 • Fax 419/227-1313

## FAIR RADIO SALES

1016 E. EUREKA • Box 1105 • LIMA, OHIO • 45802

## TECHNICAL SCHOOL CLOSED!

Selling hundreds of HEATH Co. test and training equipment at up to 70% off their catalog prices. Use Heath catalog for description. Condition: new to slightly used, many without manuals. All professionally wired & tested, or in kit form if noted. First come, first served. Check or major credit cards. Sorry, no COD or open accounts. Add \$4.50 Mailing & Handling, any quantity.

HEATH TEST EQUIPMENT		GENUINE KESTER 44 RESIN CORE SOLDER - 1LB.	
Stk #	Price	Stk #	Price
SM2420	Digital Frequency Counter	185.00	
4228(or equal)	Dual Trace 25 MHz Scope	295.00	
	Non-Operative Condition	180.00	
2" Project Speaker	Experimenter's Delight, 8 ohm, .1 Watt		
2" Spk 3 for 2.00	10 for 4.95		

HEATH EDUCATIONAL SYSTEMS		
Z-DOS	Software Documentation, Vol. 1 & II	39.50
Z-DOS	Microsoft Documentation, Vol I	19.75
EW100	Dual 5.5" Disk Drive (for Above)	49.00
ZVM133	Terminal for ET 100 Above	89.00
ET750	750 Hole Breadboard Block	6.95
ET340	340 Hole Breadboard Block	2.95
ET170	170 Hole Breadboard Block	1.95
ETB3300	2250 Hole Experiment Breadboard	19.95
ETB6201	Dig. Experiment Circuit Brd Module	34.50
EEA3104A	Electronic Kits Guide & 2 Audio Tapes	14.50
HCA3000	Univ. RF Connector Adaptor Kit	49.00

MISCELLANEOUS		
DSA654	DX Aut Satellite Receiver	485.00
HP-150BM	Owners Handbook Only	4.95
RS232-V2A	Datscom NW Breakout Box, RS232	29.50
DB2525-2V	RS232 AB Sw. Box, Metal	14.50
CN3825-2V	Centronic AB Sw. Box, Metal	18.50
B1060	*500 Insul. Lug Asst, AWG12-22 w/case	12.50
HT301	*Deluxe Ratchet Close Lug Crimp Tool	11.50
	*Combination Both Items	19.95

BNC Receptacle Assemblies		
BC60	BNC / Banana Plugs	
BC70	BNC / Test Clips	
BC80	BNC / Alligator Clips	
4.45	10 Mixed @ 3.95	

BNC Plug Assemblies		
BC30	BNC / Banana Plugs	
BC40	BNC / Test Clips	
BC50	BNC / Alligator Clips	
4.95	10 Mixed @ 4.45	

Stainless Pliers Set		
Designed for precision electronic work. Stainless, rustproof, washable and won't contaminate. Furthermore, they're non-magnetic. Features: box joint, precision ground cutting edges and plastic grips. Fits palm. Limited quantity available.		
H104A	5-1/4" Offset Needlenose	4.85
H104B	4-1/4" Diagonal Cutter	4.85
H104D	5" Long Needlenose	4.85
H104E	4-3/4" Short Needlenose	4.85
H104AE	One Set of 4	14.85, 5 sets ea. 12.85

Quick Guard Motion Alarm	
Instant attachment to car computer etc. by magnets. Emits 800hz pulsed alarm signal if disturbed. Simple arm & disarm w/remote key. 20 sec. entry & exit delay. Auto reset after 30 sec. of alarm. 9V battery operation. ST23 SPECIAL 12.85 ea 10 @ 10.50 ea.	
9V Battery Snap Clip	100 for 7.95 500 for 29.95

Round Telephone Cable, Solid AWG-26				
Stk #	# Wires	Lgt. Ft.	Price	Special
TDC4-25	4	25	1-96	.95
TDC8-25	6	25	2-96	.95
TDC6-50	6	50	6-96	1.75
TDC8-100	8	100	14-96	3.25
TDC8-50	8	50	8-96	2.95
TDC8-100	8	100	17-96	4.85

Round Telephone Cable, Solid AWG-24				
Stk #	# Wires	Lgt. Ft.	Price	Special
TDD4-250	4	250	21-46	9.25
TDD6-100	6	100	12-96	5.95
TDD6-250	6	250	29-46	14.95
TDD8-500	8	100	61-96	27.95
TDD8-100	8	100	49-96	7.95
TDD8-250	8	250	46-96	19.50
TDD8-500	8	500	87-96	38.75

**MODULAR-TELCO RJ11 & RJ45 CABLE TESTERS**  
These economical hand-held units test their respective cables for opens & miswiring. Identifies straight-thru or cross wired cables. Equipped with 9V alkaline battery.  
DX50 RJ11-12 Tester 29.95  
DX50-DEC MMJ-DEC Tester 32.95  
DX45 RJ45 Tester 36.95  
DX40A 10BaseT Tester 38.95

**1755 Osgood St., N. Andover, MA 01845**  
CALL: 508/682-6936 FAX: 508/689-9484  
ORDER TOLL FREE: 800/343-1455 RE11

March 1993, Electronics Now

**EKI**

Electronic Kits International Inc.

**FULL-COLOR PACKAGING!**

## OVER 100 Fun & Challenging KITS!

- \* Thief Catcher - Burglar Alarm
- \* Alien Zapper
- \* Fisherman's Secret
- \* Robot Blinker
- \* Mini Holiday Tree
- \* Space Age Metronome
- \* Hold-The-Phone Button
- \* Digital Roulette
- \* Mini Metal Detector
- \* Digital Slot Machine
- \* Dinosaur Bird Sound Generator
- \* FM Transmitter w/ Microphone
- \* Color Organs
- \* Power Supplies

.....AND MANY MORE!!!

**SEE THEM AT  
YOUR LOCAL  
HOBBY/CRAFT  
AND  
ELECTRONIC STORES!**

**1-800-453-1708**

16631 Noyes Ave., Irvine, CA 92714

CALL TOLL FREE FOR THE STORE NEAREST YOU

# ADVERTISERS INDEX

RS #	Page	RS #	Page
211	Accord .....	52A36	—
212	Ace Communications .....	52A67	250
—	Active Micro .....	52A73	291
213	Alfa Electronics .....	52A6	292
214	All Electronics .....	52A12	293
215	Alltronics .....	52A69	251
—	Alpha Lab .....	52A57	—
—	Amazing Concepts .....	52A31	—
282	American Science & Surplus .....	52A72	—
—	Amerix Corp. ....	52A43	—
—	Andromedia .....	52A57	254
217	B&S Sales .....	52A29	—
—	Barebonz Discount .....	52A36	—
218	Battery Tech .....	52A54	—
306	Beige Bag .....	52A37	256
283	Bel-Merit .....	52A23	—
219	BG Micro .....	52A30	257
284	Brigar Electronics .....	52A49	258
—	C&L Electronics .....	52A44	260
285	C&S Sales, Inc. ....	52A52	—
—	Cable Warehouse .....	52A73	259
—	Cable Warehouse .....	52A76	—
286	Caig Labs .....	52A9	262
302	Chase Scientific Co. ....	52A80	—
—	Chenesko Products .....	52A47	294
—	Command Productions .....	52A32	264
225	Computer Business Mart .....	52A62	265
287	Computronix .....	52A42	301
—	Consumtronics .....	52A57	—
227	Contact East .....	52A58	261
228	Cool Amp Conducto Lube .....	52A70	266
229	Crestwood Products .....	52A60	295
234	Dalbani Electronics .....	52A17	268
235	Danbar Sales .....	52A51	267
236	Davilyn Corp. ....	52A11	269
232	DC Electronics .....	52A21	270
230	Debeco Electronics .....	52A45	296
—	Design Computation .....	52A42	297
—	Dynaspek Corp. ....	52A46	298
—	E.S.F. ....	52A36	271
239	EKI .....	52A2	299
241	Electronic Goldmine .....	52A55	272
242	Electronic Rainbow .....	52A65	273
—	Emac Inc. ....	52A42	274
—	Fair Radio .....	52A1	303
243	Gateway Electronics .....	52A48	275
307	Graymark International .....	52A50	276
244	Halted Specialties Elec. Supply .....	52A63	277
289	Haltek Electronics .....	52A79	—
305	Index Publishing Group .....	52A43	—
—	Int'l Micropower Corp. ....	52A66	—
247	Interactive Image Technology .....	52A34	300
290	Jan Crystals .....	52A44	280
—	JDR Microdevices .....	52A40	281
249	Kelvin Electronics .....	52A39	—
—	L-Com Tech .....	52A1	—
—	Lake Sylvan Sales .....	52A24	—
—	M.D. Electronics (Everquest) .....	52A75	—
—	Mark V Electronics .....	52A50	—
—	MCM Electronics .....	52A19	—
—	Mendelson Electronics Surplus .....	52A15	—
—	Mental Automation .....	52A43	—
—	Merrimack Valley Systems .....	52A74	—
—	MicroTHinc .....	52A74	—
—	Midwest Laser Products .....	52A48	—
—	Ming Engineering .....	52A33	—
—	Mondotronics Inc. ....	52A68	—
—	Mouser Electronics .....	52A47	—
—	Movie View .....	52A3	—
—	MWK Industries .....	52A44	—
—	Nat'l Amateur Radio Assoc. ....	52A72	—
—	Needham Electronics .....	52A54	—
—	New Sensor Corp. ....	52A28	—
—	Ocean State Electronics .....	52A8	—
—	Ohio Automation .....	52A74	—
—	Optoelectronics .....	52A61	—
—	Paladin Electronics .....	52A72	—
—	Parts Express Inc. ....	52A26	—
—	PC Boards .....	52A75	—
—	Prairie Digital .....	52A76	—
—	Print (Pace) .....	52A56	—
—	Prizm Resources .....	52A14	—
—	Project Pro .....	52A46	—
—	Pyramid Electronic Products .....	52A66	—
—	Quad Energy .....	52A19	—
—	Ramsey Electronics .....	52A5	—
—	Resources Unltd. ....	52A56	—
—	RF Parts .....	52A4	—
—	Rogers Specialists .....	52A16	—
—	Sescom Inc. ....	52A38	—
—	Skyvision Inc. ....	52A10	—
—	Spy Supply .....	52A38	—
—	Startek .....	52A7	—
—	Statpower Technologies Corp. ....	52A18	—
—	Surplus Traders .....	52A20	—
—	Tanner Electronics .....	52A60	—
—	Tech Services .....	52A64	—
—	Tech Systems .....	52A32	—
—	TECI .....	52A66	—
—	Tektronix Inc. Corp. ....	52A47	—
—	Timeline .....	52A77	—
—	Ucando .....	52A62	—
—	United Electronic Supply .....	52A22	—
—	Universal Electronics, Inc. ....	52A48	—
—	Vanguard Electronic Labs .....	52A68	—
—	Vantage Point Technologies .....	52A46	—
—	Weka Publishing .....	52A25	—
—	WPT Publications .....	52A73	—
—	Xandi Electronics .....	52A37	—



# MIKE NELSON'S MOVIE VIEW SALES, INC.

**WHERE YOU'RE TREATED POLITE AND GIVEN INDIVIDUALIZED ATTENTION!**

**INFO (708) 250-8690/FAX (708) 250-8755**

P.O BOX 26 • WOOD DALE, IL 60191

Call C.S.T. Monday thru Friday 9:00 - 6:00 • Sat. 10:00 - 2:00

Friendly Courteous Service • 10 Yrs. Experience • 6 Mo. Warranty

<b>JERROLD</b>	1-3	4 or more	<b>PIONEER</b>	1-3	4 or more
NEW TRI/BI COMBO (FTB)	125.00	120.00	*NEW SA-PIO-COMBO	155.00	150.00
NEW TRI/BI PAN	75.00	55.00	NEW SA-PIO-PAN W/SWITCH	80.00	75.00
NEW SB-3 COMBO	110.00	105.00	NEW ORIG. BA-6100 PAN	CALL	MIKE
NEW SB-3 PAN	55.00	50.00	<b>SCIENTIFIC ATLANTA</b>	1-3	4 or more
DPV-7212	260.00	CALL	*NEW SA-3 COMBO (SA-3B)	125.00	120.00
STARCOM 6/7 (1 PC UNIT)	215.00	CALL	NEW SA-3 PAN	75.00	55.00
DPBB-7212	CALL	MIKE	8550:	175.00	165.00
CAMOUFLAGE TRI/MODE	CALL	MIKE	8580:	250.00	CALL
NEW FTB-2	75.00	55.00	8536:	195.00	CALL
NEW SB-2	55.00	50.00	<b>OAK</b>	1-3	4 or more
<b>HAMLIN</b>	1-3	4 or more	NEW OAK N-12 COMBO(Vari Sync)	115.00	110.00
NEW HAMLIN COMBO (CH 2 OR 3)	110.00	105.00	NEW OAK N-12 PAN(Vari Sync)	60.00	55.00
NEW HAMLIN MLD-1200	50.00	45.00	M-35-B	50.00	45.00
MLD-1200-2	50.00	45.00	<b>PANASONIC-VIEWSTAR</b>	20 LOT	100 LOT
				75.00	CALL
			<b>ZENITH: Z-TAK</b>	220.00	CALL
			<b>NOTCH FILTERS</b>	16.00	12.00

Price effective 7/1/92 (Subject to change without notice)

**MOST ORDERS SHIPPED SAME DAY!**

QTY.	ITEM	PRICE EA.	TOTAL PRICE

SUB TOTAL

SHIPPING Add \$4.00 per unit

\$4.00 PER COD TAG/CREDIT CARDS Add 5%

TOTAL

\* All Combos come with new Panasonic or Viewstar converter.

(Parental lockout units: No extra charge.)

Volume control units available

(WAIVER) - MUST BE SIGNED FOR OUR RECORD

Yes, I am paying for full service. This is only to be used as a second unit.

**DECLARATION OF AUTHORIZED USE** - I, the undersigned, do hereby declare, under penalties of perjury, that all products purchased, now and in the future, will only be used on cable TV systems with proper authorization from local officials or cable company officials in accordance with all applicable federal and state laws. FEDERAL AND VARIOUS STATE LAWS PROVIDE FOR SUBSTANTIAL CRIMINAL AND CIVIL PENALTIES FOR UNAUTHORIZED USE.

**ABSOLUTELY NO ILLINOIS SALES**

VISA-MASTER  C.O.D.   
CASHIER'S CHECK  MONEY ORDER

**ORDERS ONLY: 1-800 735-5912**

SIGNATURE

X \_\_\_\_\_

It is not the intent of MOVIE VIEW to defraud any television operator and we will not assist any company or individual in doing the same.

Card # \_\_\_\_\_ Exp. Date \_\_\_\_\_

Name \_\_\_\_\_


Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Phone ( ) \_\_\_\_\_

**If for any reason you are not satisfied with any item purchased, you may return it within 30 days of delivery for a full refund.**
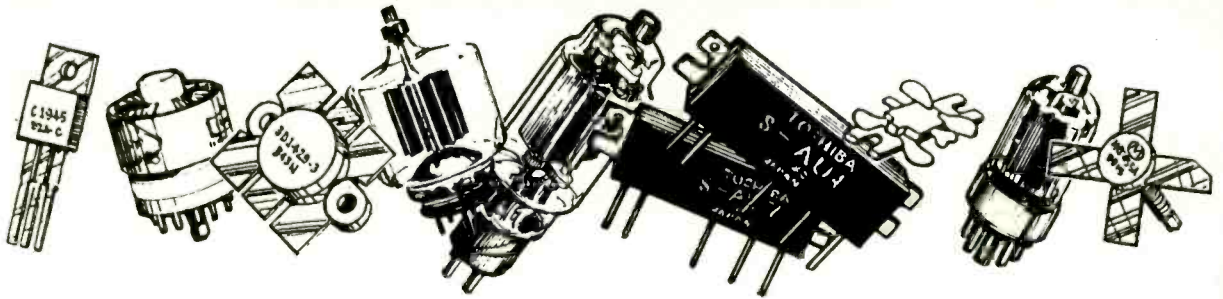
# RF POWER - TRANSISTORS - TUBES - MODULES



## PARTIAL LISTING OF POPULAR TUBES AND TRANSISTORS IN STOCK

TRANSISTORS		MRF433MP		SRF3749		CALL		2SC1955		\$9.00		2SC3101		\$7.95		MHW SERIES		CALL		30KD6 SYL		\$18.95		8560AS		\$149.95		
CD2664A	\$24.00	MRF450	13.50	2N3553	\$2.85	2SC1969	2.25	2SD235Y	2.25	2SD235Y	2.25	2SD235Y	2.25	6AN8A	\$13.95	RECEIVING TUBES	572B/5160L	54.95	8675 EI	339.95	8675 EI	339.95	8675 EI	339.95	8675 EI	339.95	8675 EI	339.95
ECG340	3.95	MRF454	14.50	2N3771	2.95	2SC1970	2.45	2SD613	1.40	2SD613	1.40	J310	1.50	6AZ8	14.95	Match Pr.	810 PL	119.95	8908 GE	26.95	8908 GE	26.95	8908 GE	26.95	8908 GE	26.95	8908 GE	26.95
MGF1302	7.95	MRF455	10.95	2N3866	1.25	2SC1971	4.80	J310	1.50	J310	1.50	M88719	6.35	6B8	11.95	Match Pr.	811 PL	13.95	8950 GE	20.75	8950 GE	20.75	8950 GE	20.75	8950 GE	20.75	8950 GE	20.75
MGF1402	17.95	MRF455A	11.95	2N4048	12.95	2SC2028	1.95	M88719	6.35	M88719	6.35	TA7205AP	2.25	6BZ6	7.95	Match Pr.	811 PL	13.95	9095 GE	45.90	9095 GE	45.90	9095 GE	45.90	9095 GE	45.90	9095 GE	45.90
MRF134	18.00	MRF458	17.95	2N4427	1.25	2SC2029	3.50	TA7205AP	2.25	TA7205AP	2.25	TA7222AP	3.00	6CA7-MP G.E.	49.95	Match Pr.	813 PL	31.90	2C39A/B	59.95	2C39A/B	59.95	2C39A/B	59.95	2C39A/B	59.95	2C39A/B	59.95
MRF136	21.00	MRF475	9.25	2N5179	1.25	2SC2053	1.20	TA7222AP	3.00	TA7222AP	3.00	UC1250	29.50	6C86	6.95	Match Pr.	813 PL	31.90	3-400Z (#)	CALL	3-400Z (#)	CALL	3-400Z (#)	CALL	3-400Z (#)	CALL	3-400Z (#)	CALL
MRF137	24.00	MRF476	4.00	2N5589	13.00	2SC2075	1.45	UC1250	29.50	UC1250	29.50	SAU4	46.70	6C86A	10.95	Match Pr.	833C PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95
MRF140	75.00	MRF477	11.95	2N5590	10.00	2SC2094	15.95	SAU4	46.70	SAU4	46.70	SAU16SH	49.50	6C86A	10.95	Match Pr.	833C PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95
MRF141	84.50	MRF485	CALL	2N5591	14.50	2SC2097	23.95	SAU16SH	49.50	SAU16SH	49.50	SAV6	32.95	6C86	6.95	Match Pr.	833C PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95
MRF141G	190.00	MRF492	15.95	2N5945	10.00	2SC2131	4.90	SAV6	32.95	SAV6	32.95	SAV7	32.95	6C86	6.95	Match Pr.	833C PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95
MRF150	68.75	MRF497	18.75	2N5946	15.00	2SC2166C	1.50	SAV7	32.95	SAV7	32.95	SAV12	17.25	6C86	6.95	Match Pr.	833C PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95
MRF150MP	148.75	MRF515	2.90	2N6080	9.75	2SC2221	8.25	SAV12	17.25	SAV12	17.25	SAV15	44.00	6C86	6.95	Match Pr.	833C PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95
MRF151G	168.50	MRF555	3.50	2N6081	11.35	2SC2237	8.40	SAV15	44.00	SAV15	44.00	SAV22A	44.00	6C86	6.95	Match Pr.	833C PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95
MRF224	17.75	MRF559	2.25	2N6082	14.35	2SC2289	15.15	SAV22A	44.00	SAV22A	44.00	SAV26	32.95	6C86	6.95	Match Pr.	833C PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95
MRF237	3.70	MRF629	4.25	2N6083	14.35	2SC2290	15.95	SAV26	32.95	SAV26	32.95	SAV27	32.95	6C86	6.95	Match Pr.	833C PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95
MRF238	14.95	MRF630	3.75	2N6084	14.35	2SC2290MP	37.95	SAV27	32.95	SAV27	32.95	SAV28	32.95	6C86	6.95	Match Pr.	833C PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95
MRF239	15.95	MRF641	19.95	2SA1012	1.30	2SC2312C	4.95	SAV28	32.95	SAV28	32.95	SAV29	32.95	6C86	6.95	Match Pr.	833C PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95
MRF240, A	16.50	MRF644	23.00	2SB754	2.50	2SC2395	23.90	SAV29	32.95	SAV29	32.95	SAV30	32.95	6C86	6.95	Match Pr.	833C PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95
MRF245	32.00	MRF646	24.75	2SC730	4.50	2SC2509	10.85	SAV30	32.95	SAV30	32.95	SAV31	32.95	6C86	6.95	Match Pr.	833C PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95
MRF247	23.35	MRF648	29.95	2SC741	5.90	2SC2538	1.85	SAV31	32.95	SAV31	32.95	SAV32	32.95	6C86	6.95	Match Pr.	833C PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95
MRF260	11.50	MRF901	1.50	2SC1306	CALL	2SC2630	22.95	SAV32	32.95	SAV32	32.95	SAV33	32.95	6C86	6.95	Match Pr.	833C PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95
MRF262	12.75	MRF966	4.35	2SC1307	CALL	2SC2640	17.00	SAV33	32.95	SAV33	32.95	SAV34	32.95	6C86	6.95	Match Pr.	833C PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95
MRF264	13.45	MRF1946	15.00	2SC1419	4.70	2SC2782	37.75	SAV34	32.95	SAV34	32.95	SAV35	32.95	6C86	6.95	Match Pr.	833C PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95
MRF327	62.00	RF120	CALL	2SC1729	13.25	2SC2783	59.85	SAV35	32.95	SAV35	32.95	SAV36	32.95	6C86	6.95	Match Pr.	833C PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95
MRF421	22.95	SD SERIES	CALL	2SC1945	4.95	2SC2879	19.95	SAV36	32.95	SAV36	32.95	SAV37	32.95	6C86	6.95	Match Pr.	833C PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95
MRF422	34.95	SRF2072	13.75	2SC1946A	15.65	2SC2904	30.50	SAV37	32.95	SAV37	32.95	SAV38	32.95	6C86	6.95	Match Pr.	833C PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95
MRF433	12.20	SRF3662	27.70	2SC1947	9.75	2SC2905	34.50	SAV38	32.95	SAV38	32.95	SAV39	32.95	6C86	6.95	Match Pr.	833C PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95	3-500Z PL	89.95

Migr: EI = Eimac, PL = Penta Labs Note: (#) = Industrial Boxed Eimac/Ampere

Limited Warranty: 12 month / 3,000 hours on Penta & Eimac transmitting tubes

Price & availability subject to change without notice • Quantity Pricing Available

### TECHNICAL BOOK

ARRL RADIO AMATEURS HANDBOOK, 1992 Edition, (The "Bible") 5-1/4 lb.	NET \$25.00
ARRL ANTENNA BOOK. HF/VHF/UHF-Wire Ant's/Beams. 16th Ed. 4 lb.	20.00
ARRL ANTENNA IMPEDANCE MATCHING 1.8 LB.	15.00
ARRL REFLECTIONS/TRANSMISSION LINES AND ANTENNAS 1.8 LB.	20.00
ARRL DATA BOOK. Formulas, schematics, tables, etc. 1.3 LB.	12.00
ARRL TRANSMISSION LINE TRANSFORMERS, 2nd ed. Baluns/etc. 1.4 LB.	20.00
ARRL NOW YOUR TALKING. NEW NO-CODE Novice/Tech License Study Guide 1.8 LB.	19.00
ARRL YOUR INTRODUCTION TO MORSE CODE. Novice & Tech 5 wpm Tapes	10.00
ARRL RADIO FREQUENCY INTERFERENCE, How to find it and fix it	15.00
ARRL LICENSE MANUAL, TECHNICIAN CLASS & Novice w/ code	6.00
ARRL LICENSE MANUAL, GENERAL CLASS	6.00
ARRL REPEATER DIRECTORY. Current Issue	6.00
ARRL YOUR GATEWAY TO PACKET RADIO 1.2 LB.	12.00
ARRL UHF/MICROWAVE EXPERIMENTERS MANUAL 2.5 LB.	20.00
ARRL SATELLITE EXPERIMENTERS HANDBOOK	20.00
ARRL THE COMPLETE DX'er. Techniques/Tips/OSL	12.00
PASSPORT TO WORLDO BANO RADIO. Short Wave Listening & freq. 1.8 LB.	14.95
MOTOROLA RF DEVICE MANUAL (incl. Appl. Notes & Cross Ref. 4.3 lbs)	14.95
ECG Semiconductor Master Replacement Guide/Specs. ECG-212Q 3 lbs	4.95

Monday - Friday 7:30 a.m. - 5 p.m. PST / 10:30 a.m. - 8 p.m. EST

• EXPORT • O.E.M. • SERVICE • R&D • AMATEUR • MARINE

SHIPPING METHOD & CHARGES: Minimum Order \$20.00

BEST WAY: UPS ORDERS RECEIVED BEFORE 4 p.m. PST (7 p.m. EST) SHIPPED SAME DAY.

Federal Express / Airborne / DHL / USPS are also available.

GROUND SERVICE: 3-7 working days (max.) depending on destination in contig. U.S.

\$4.00 minimum. Add \$.50 per pound above 2 pounds.

2-DAY AIR SERVICE: UPS BLUE, \$6.00 minimum. Add \$1.00 per pound above 2 pounds. Federal Express also available at same charge. No COD. Alaska / Hawaii / Puerto Rico. Canada: No COD. Please ask for charges.

NEXT DAY DELIVERY: UPS RED, \$13.50 minimum. Ask for shipping charges above 1 lb.

Saturday delivery available for additional \$10.00

PAYMENT METHOD: PREPAID with check or money order. Personal checks must have preprinted address and are limited to \$40.00. Checks returned for insufficient funds will be subject to a \$20.00 charge. Any over-payment will be returned. Prepaid orders are not subject to minimum.

VISA/MASTERCARD accepted

C.O.D.: Add \$4.00 UPS charge. Cash, Cashiers Check, Money Order, or Pre-approved Company Check only.

FOREIGN: Bank check drawn on U.S. Bank, or VISA/MASTERCARD.

WIRE TRANSFER: Contact us for account information.

OPEN ACCOUNT: Net 30 accounts to firms whose credit has been pre-approved.

CALIFORNIA: Residents add appropriate sales tax.

FOREIGN: Insurance/Registration is often available. Advise if desired.

SMALL PACKET: Ideal Air shipment for small orders of parts. \$8.00 up to 8 oz.; 4 lb. max. 8"x8"x8" box.

AIR PARCEL POST is available on larger items.

CANADA: \$5.50 minimum shipping/handling charge up to 1 lb. for postal.

### TECHNICAL BOOK

RADIO/TECH MODIFICATIONS Freq Exp. HF/VHF Icom/Kenwood/Yaesu/Scanners	NET \$19.95
U.S. REPEATER MAPBOOK Location/frequency geographically	9.95
SCANNER REPAIR & MODIFICATION MANUAL. Bearcat/Uniden. Vol. I	29.95
SERVICE MANUAL AR-3300 & AR-3500 Ranger 10M Xcvr.	20.00
SERVICE MANUAL FOR CYBERNET "Export" Radios	15.00
SERVICE MANUAL FOR UNIDEN "Export" Radios	15.00
SERVICE MANUAL RCI-2950 10M Xcvr.	NEW! 15.00
SERVICE MANUAL RCI-5500/6500/8500 VHF Marine Transceiver	17.50
UNDERSTANDING & REPAIRING CB RADIOS. Lou Franklin. 2 lb.	Special 34.95
ENGINEERS SECRETS OF RADIO. Tube Amps/Modulation tips/Schematics/TVI	16.95
CB PLL DATA BOOK, New International Edition, L. Franklin	19.95
CB TRICKS OF THE TRADE. Test/peaking/antennas/ & much more	15.95
CB TRICKS II. Schematics of popular linear amps & more	15.95
CB TUNE UP MANUAL, Master Edition, What to cutweek mods., etc.	24.95
CB TUNE UP MANUAL, Master Ed./Vol. II. More info on popular xcvs	29.95
CB TUNE UP MANUAL, Master Ed./Vol. III. Additional info on other equip.	Special 29.95
RADIO SECRETS. (Secret CB) Performance Improvements on Amateur & CB transmitters/amplifiers/mods/etc. Vol. 1-30 Reg. \$20.00/vol.	14.95
SECRET CB Index. Listing by model number and article	2.50



# RAMSEY ELECTRONICS

**COM-3**  
**\$2995.00**



## 2 WAY RADIO SERVICE MONITOR

COM-3, the world's most popular low-cost service monitor. For shops big or small, the COM-3 delivers advanced capabilities for a fantastic price—and our new lease program allows you to own a COM-3 for less than \$3.00 a day. Features: •Direct entry keypad with programmable memory •Audio & transmitter frequency counter •LED bar graph frequency/error deviation display •0.1-10,000 µV output levels •High receive sensitivity, less than 5 µV •100 kHz to 999.9995 MHz •Continuous frequency coverage •Transmit protection, up to 100 watts •CTS tone encoder, 1 kHz and external modulation.



**RSG-10**  
**\$2495.00**

## SYNTHESIZED SIGNAL GENERATOR

Finally, a low-cost lab quality signal generator—a true alternative to the \$7,000 generators. The RSG-10 is a hard working, but easy to use generator ideal for the lab as well as for production test. Lease for less than \$3.00 a day. Features: •100 kHz to 999 MHz •100 Hz resolution to 500 MHz, 200 Hz above •-130 to +10 dBm output range •0.1 dB output resolution •AM and FM modulation •20 programmable memories •Output selection in volts, dB, dBm with instant conversion between units •RF output reverse power protected •LED display of all parameters—no analog guesswork!

**•2 METERS**  
**•223 MHz**  
**•440 MHz**

# FANTASTIC FM TRANSCEIVERS

**SYNTHESIZED—NO CRYSTALS**

Ramsey breaks the price barrier on FM rigs! The FX is ideal for shack, portable or mobile. The wide frequency coverage and programmable repeater splits makes the FX the perfect rig for Amateur, CB or MARS applications. Packeteers really appreciate the dedicated packet port, "TRUE-FM" signal and almost instant TR switching. High speed packet? ... No problem. Twelve diode programmed channels, SW RF output, sensitive dual conversion receiver and proven EASY assembly. Why pay more for a used foreign rig when you can have one AMERICAN MADE (by you) for less. Comes complete less case and speaker mike. Order our matching case and knob set for that pro look.

- FX-146 kit (2 Meters) ..... \$149.95
- FX-223 kit (1 1/2 Meters) ..... \$149.95
- FX-440 kit (3/4 Meters) ..... \$169.95
- CFX matching case set ..... \$ 24.95

**\$149.95**

## 2 MTR & 220 BOOSTER AMP

Here's a great booster for any 2 meter or 220 MHz hand-held unit. These power boosters deliver over 30 watts of output, allowing you to hit the repeater's full quieting while the low noise preamp remarkably improves reception. Ramsey Electronics has sold thousands of 2 meter amp kits, but now we offer completely wired and tested 2 meter, as well as 220 MHz, units. Both have all the features of the high-priced boosters at a fraction of the cost.

- PA-10 2 MTR POWER BOOSTER (10 X power gain) ..... \$89.95
- Fully wired & tested
- PA-20 220 MHz POWER BOOSTER (8 X power gain) ..... \$89.95
- Fully wired & tested



# FREQUENCY COUNTERS

**CT-70 7 DIGIT 525 MHz**      **CT-90 9 DIGIT 600 MHz**      **CT-125 9 DIGIT 1.2 GHz**



Ramsey Electronics has been manufacturing electronic test gear for over 10 years and is recognized for its lab quality products at breakthrough prices. All of our counters carry a full one-year warranty on parts and labor. We take great pride in being the largest manufacturer of low-cost counters in the entire U.S.A. Compare specifications. Our counters are fully featured, from audio to UHF, with FET high impedance input, proper wave shaping circuitry, and durable high quality epoxy glass plated-through PCB board construction. All units are 100% manufactured in the U.S.A. All counters feature 1.0 ppm accuracy.

## NEW CT-250 2.5 GHz

- ACCESSORIES FOR COUNTERS**
- Telescopic whip antenna—BNC plug, WA-10 ..... \$11.95
  - High impedance probe, light loading, HP-1 ..... \$16.95
  - Low-pass probe, audio use, LP-1 ..... \$16.95
  - Direct probe, general purpose use, DC-1 ..... \$16.95
  - Tilt ball, elevates counter for easy viewing, TB-70 ..... \$9.95
  - Rechargeable internal battery pack, BP-4 ..... \$8.95
  - CT-90 oven timebase, 0.1 ppm accuracy, OV-1 ..... \$9.95

## ALL COUNTERS ARE FULLY WIRED & TESTED

MODEL	FREQ. RANGE	SENSITIVITY	DIGITS	RESOLUTION	PRICE
CT-50	20 Hz-600 MHz	<25 mV to 500 MHz	8	1 Hz, 10 Hz	\$189.95
CT-70	20 Hz-550 MHz	<50 mV to 150 MHz	7	1 Hz, 10 Hz, 100 Hz	\$139.95
CT-90	10 Hz-600 MHz	<10 mV to 150 MHz <150 mV to 600 MHz	9	0.1 Hz, 10 Hz, 100 Hz	\$189.95
CT-125	10 Hz-1.25 GHz	<25mV to 50 MHz <15 mV to 500 MHz <100 mV to 1 GHz	9	0.1 Hz, 1 Hz, 10 Hz	\$289.95
CT-250	10 Hz-2.5 GHz typically 3.0 GHz	<25 mV to 50 MHz <10 mV to 1 GHz <50 mV to 2.5 GHz	9	0.1 Hz, 1 Hz, 10 Hz	\$389.95
PS10B Prescaler	10 MHz-1.5 GHz, divide by 1000	<50 mV		Convert your existing counter to 1.5 GHz	\$89.95

## SPEED RADAR \$89.95 complete kit \$6-7

New low-cost microwave Doppler radar kit "clicks" cars, planes, boats, horses, bikes or any large moving object. Operates at 2.8 GHz with up to 1/4 mile range. 8 digit digital displays speed in miles per hour, kilometers per hour or feet per second! Earphone output allows for listening to actual doppler shift. Uses two 1-lb coffee cans for antenna (not included) and runs on 12 VDC. Easy to build—all microwave circuitry is PC striping. ABS plastic case with speed graphics for a professional look. A very useful and fun-of-fun kit.

## BROADBAND PREAMP

Boost those weak signals to your channel TV, shortwave radio or frequency counter. Flat 25 dB gain, 1 to 1000 MHz, 3 dB NF, BNC connectors. Runs on 12 VDC or 110 VAC. FR-2, wired, includes AC adapter. \$59.95

## FM WIRELESS MIKE KITS

Pick the unit that's right for you! These units transmit stable signal in 88-108 MHz FM band up to 300' except for hi power FM-4 that goes up to 1/2 mile.

- FM-1, basic unit ..... \$ 5.95
- FM-2, as above but with added mike preamp ..... \$ 7.95
- FM-4, long range, high power with very sensitive audio section, picks up voices 10' away ..... \$14.95

MC-1, miniature sensitive mike cartridge for FM-1, 2, 4 ..... \$ 2.95

## 2M POWER AMP

Easy to build power amp has 8 times power gain, 1W in, 8W out, 2W in, 16W out, 5W in for 40W out. Same amp as featured in many ham magazine articles. Complete with all parts, less case and T-R relay. PA-1, 40W per amp kit ..... \$34.95  
TR-1, RF sensed T-R relay kit ..... \$11.95

**MICROWAVE INTRUSION ALARM**  
A real microwave Doppler sensor that will detect a human as far as 10 feet away. Operates on 1.3 GHz, and is not affected by heat, light, or vibrations. Drives up to 100 mA output, normally open or closed, runs on 12 VDC. Complete kit MD-3 ..... \$19.95

**MUSIC MACHINE**  
Near kit that will produce 25 different classical and popular tunes, plus 3 doormat sounds. Lots of fun for doorbells, shop, or store entrances, car horn, music boxes, etc. Runs on 9V battery or wall transformer. Excellent speaker volume and adjustable tempo and pitch. Add a case set for a handsome finished look. Complete kit, MM-5 ..... \$24.95  
Case + knob set, CMM-5 ..... \$12.95

**PACKET RADIO**  
Two new versions are available for the Commodore 64 (P-64A) or the IBM-PC (P-IBM). Easy assembly "NO TUNING". Includes FREE disk software, PC Board and Full Documentation.  
KIT P-64A ..... \$59.95  
P-IBM ..... \$59.95  
CASE CPK ..... \$12.95

**LO NOISE PREAMPS**  
Make that receiver come alive! Small size for easy installation with HI-Q tuned input for peak performance. Excellent gain and noise figure—guaranteed to improve reception! Specify band: 2M—PR-10, 220 MHz—PR-20, 440 MHz—PR-40. Each kit ..... \$17.95

## VOICE ACTIVATED SWITCH

Voice activated switch kit provides switched output with current capability up to 100 mA. Can drive relays, lights, LED, or even a tape recorder motor. Runs on 9 VDC. Complete kit, VS-1 kit ..... \$6.95

## TELEPHONE TRANSMITTER

Minimized with professional performance. Self-powered from phone line, transmits in FM broadcast band up to 1/4 mile. Installs easily anywhere on phone line or inside phone! PB-1 kit ..... \$14.95

## NEW SPEAKER PHONE

Talk on the phone hands-free, great to put in shop or shack, press the button to answer—no actual phone needed. Works same as commercial units. Talk from anywhere in room, phone line powered—no battery needed. Super for family and conference calls or buy two for hands-free intercom! Add our case set for a pro look.  
SP-1 ..... \$29.95      Base-CSP ..... \$12.95

## TICKLE STIK

A shocking little Blinking LED attracts victims to pick up innocent-looking packages. You watch the fun! Ideal for office desks, parties, nossey know-it-alls! TS-4 kit ..... \$9.95

## LIGHT BEAM COMMUNICATORS

Transmits audio over infrared beam up to 300—use same eyes to see up to 1/4 mile! Hum free, uses 30 kHz carrier. Great for wireless earphones or undetectable "bug". Transmitter + receiver set, LB55 ..... \$19.95

## SUPER SLEUTH

A super sensitive amplifier which will pick up a pin drop at 15 feet! Great for monitoring baby's room or as general purpose amplifier. Full 2W rms output. Runs on 6 to 15 volts, uses 8-45 ohm speaker. BN-9 kit ..... \$6.95

# QRP TRANSMITTERS HAM RECEIVERS

## 20, 30, 40, 80M CW TRANSMITTERS

Join the fun on QRP! Thousands of these mini-rigs have been sold and lots of DX contacts have been made. Imagine working Eastern Europe with a \$30 transmitter—that's ham radio at its best! These CW rigs are ideal mates to the receivers at right. They have a position variable crystal control (one popular CW rig included), one watt output and built-in antenna switch, runs on 12VDC. Add our matching case and knob set for a handsome finished look. Your choice of bands ..... \$29.95  
(Specify band: CRP-20, 30, 40 or 80)  
Matching case & knob set, CORP ..... \$12.95

## 20, 30, 40, 80M All Mode RECEIVERS

Build your own ham station. Sensitive all-mode FM, CW, SSB receivers use direct conversion design with NE602 IC as featured in QST and ARRL handbooks. Very sensitive varactor tuned over entire band. Plenty of speaker volume. Runs on 9V battery. Very EASY to build, lots of fun and educational—ideal for beginner or old pro. New 30-page manual. Add the case set for well-fitted professional look. Your choice of bands ..... \$29.95  
(Specify band: HR-20, HR-30, HR-40, HR-80)  
Matching case & knob set, CHR ..... \$12.95

## E-Z KEY CMOS KEYS

Send perfect CW within an hour of receiving this kit! Easy-to-build kit has sidetone oscillator, speed control and keys most any transmitter. Runs for months on a 9V battery. 28-page manual gives ideas on making your own key for extra savings. Add our matching case set for complete station look. CW-7 kit ..... \$24.95  
Matching case knob set, CCW ..... \$12.95

## 2, 6, 10 MTR. 220 FM RECEIVERS

Keep an ear on the local repeater gang, monitor the cops, check out the weather or just plain listen around. These sensitive superhet receivers are just the ticket. They tune any 5 MHz portion of the band and have smooth varactor-tuning, dual conversion with ceramic IF filters, AFC, adjustable squeal and plenty of speaker volume. Runs on 9V battery and performance that rivals the big rigs! For a complete finished pro look, add our matching case and knob set with screened graphics. FM communications receiver kit ..... \$29.95  
Specify band: FR-146 (2m), FR-6 (6m), FR-10 (10m), FR-220 (220 MHz) ..... \$12.95  
Matching case & knob set, CFR ..... \$12.95

## ACTIVE ANTENNA

Cramped for space? Get longwire performance with this desktop antenna. Properly designed unit has dual HF and VHF circuitry and built-in whip antenna, as well as external jack. RF gain control and 9V operation makes unit ideal for SWLs, traveling hams or scanner buffs who need better reception. The matching case and knob set gives the unit a hundred dollar look! AA-7 kit ..... \$24.95  
Matching case & knob set, CAA ..... \$12.95

## SPEECH SCRAMBLER

Communicate in total privacy over phone or radio. Kit features full duplex operation using frequency inversion. Both mike and speaker or line input connections. Easy hookup to any radio, and telephone use requires no direct connection! Easy to build 2 IC circuit. Can also be used to descramble many 2-way radio signals. Finish your kit off with the handsome case & knob set. SS-7 kit ..... \$29.95  
Matching case & knob set, CSS ..... \$12.95

## SHORTWAVE RECEIVER

Fantastic receiver that captures the world with just a 12" antenna! Can receive any 2 MHz portion from 4-11 MHz. True superhet has smooth varactor tuning, AGC, RF gain control, plenty of speaker volume and runs on a 9V battery. Fascinating Scout, school or club project provides hours of fun for even the most serious DXer. For the car, consider our shortwave converter. Two switchable bands (in 3-22 MHz range), each 1 MHz wide—tunable on your car radio dial. Add some interest to your drive home! Shortwave receiver kit, SRI ..... \$29.95  
Shortwave converter kit, SCI ..... \$27.95  
Matching case set for SRI, CSR ..... \$12.95  
Matching case set for SCI, CSC ..... \$12.95

## FM STEREO TRANSMITTER

Run your own stereo FM station! Transmit a stable signal in the standard FM broadcast band throughout the house, dorm or neighborhood. Connects easily to line outputs on CD player, tape decks, etc. Runs on 9V battery, has internal whip antenna and external antenna jack. Add our case set for a "station" look! FM-10 kit ..... \$29.95  
Matching case set, CFM ..... \$12.95

## AIRCRAFT RCVR

Hear exciting aircraft communications—pick up planes up to 100 miles away! Receives 110-136 MHz AM air band, smooth varactor tuning superhet with AGC, ceramic filter, adjustable squeal, excellent sensitivity and lots of speaker volume. Runs on 9V Battery. Great for show or just hanging around the airport! New 30-page manual details pilot talk, too. Add case set for "pro" look. AR-1 kit ..... \$24.95  
Matching case set, CAR ..... \$12.95

**PHONE ORDERS CALL**  
**716-924-4560**  
FAX 716-924-4555

**RAMSEY ELECTRONICS, INC. 793 Canning Parkwy, Victor, NY 14564**



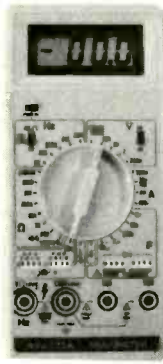
# ALFA ELECTRONICS

QUALITY TEST EQUIPMENT  
AFFORDABLE PRICE



**DMM 2360**  
**\$129.95**  
**DMM + LCR Meter**  
**Most Versatile DMM**  
Inductance: 1μH-40H  
Capacitance: 1pF-40μF  
Frequency: 1Hz - 4MHz  
Temperature: -40 - 302°F  
Logic Test: 20MHz  
Diode, Continuity  
Volt, Amp, Ohm  
3999 count display  
Peak Hold  
Auto power off



**DMM 175A \$67.95**  
**DMM with 20 MHz**  
**Frequency Counter**  
**Most popular DMM**  
Freq. Counter 1Hz-20MHz  
DCV .1mV-1000V  
ACV .1mV-750V  
ACADCA .1mA-10A  
R .1Ω-2000MΩ  
Cap 1pF-20μF  
TTL Logic test 20 MHz  
Transistor HFE test  
Diode test  
LED test  
3 1/2 digit display  
10 MΩ impedance



**Fluke Multimeter**  
Fluke 70 II \$62  
Fluke 73 II \$87  
Fluke 75 II \$125  
Fluke 77 II \$145  
Fluke 79 II \$165  
  
Fluke 83 \$215  
Fluke 85 \$255  
Fluke 87 True RMS \$285  
  
Fluke 86 Automotive \$359  
Fluke 88 \$419




**LCR Meter 814**  
**\$199.95**  
**The Best Handheld**  
**LCR**  
Inductance: 0.1μH-200H  
Capacitance: 0.1pF-20,000μF  
Resistance: 1mΩ-20MΩ  
1% basic accuracy  
Dissipation factor indicates leakage  
in capacitor and Q factor in inductor  
Zero adjustment to reduce parasitics  
from test fixture  
Very good for high frequency RF  
and surface mount components.



**LCR Meter 195**  
**\$119.95**  
**Very popular LCR**  
Inductance: 0.1μH-200H  
Capacitance: 0.1pF-200 μF  
Resistance: 0.01Ω-20MΩ  
Basic accuracy: R:1%, C:2%, L:3%  
Test frequency 1 kHz




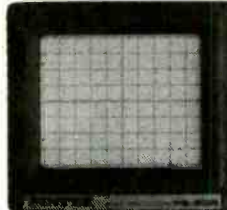**Capacitance Meter**  
**7705 \$57.95**  
0.1 pF-20,000μF in 9 ranges  
0.5% basic accuracy  
Zero adjustment ± 20pF to compensate parasitics from test fixture  
  
**Also Available:**  
Heavy duty DMM  
AC/DC clamp meter  
Thermometer, Lux meter  
pH meter, Logic probe  
High voltage probe  
RC oscillator  
Electronic scale  
Frequency counter



**20 MHz Oscilloscope with Delay**  
**Sweep PS-205 \$429.95**  
Dual Trace, Component test, 6" CRT, X-Y Operation, TV Sync, Z Modulation, CH2 Output, Graticule Illum, 2 probes x1, x10. Best price with delay sweep.  
**PS-200 20MHz DUAL TRACE \$339.95**  
**PS-405 40MHz DELAY \$569.95**  
**PS-605 60MHz DELAY \$769.95**

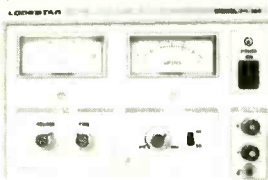
**20 MHz Digital Storage**  
**Oscilloscope DS-203 \$769.95**  
Switchable between digital and analog  
2 K word per channel storage  
Sampling rate: 10 M sample /sec  
8 bit vertical resolution (25 Levels/div)  
Expanded Timebase 10ms/div - 0.5 s/div  
Refresh, Roll, Save all, Save CH2, Pre-Trig  
Plotter Control



**Power Supply**  
**PS-303 \$169.95**  
**0-30 VDC , 0-3A output**  
0.02% + 2mV line regulation  
0.02% + 3mV load regulation  
1 mVrms noise and ripple  
Short circuit and overload protected



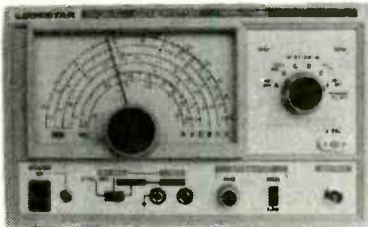**Power Supply**  
**PS-1610 \$299.95**  
**0-16 VDC , 0-10A output**  
Constant voltage & constant current mode  
0.2%+2mV line regulation  
0.04% +2mV load regulation  
1mVrms noise and ripple  
Short circuit and overload protected



**RF SIGNAL**  
**GENERATOR**  
**SG-4160B \$124.95**  
100 kHz-150MHz sinewave in 6 ranges  
Output 100mVrms to 35 MHz  
Internal 1kHz, External 50Hz-20kHz modulation

**AUDIO GENERATOR**  
**AG-2601A \$124.95**  
10Hz - 1MHz in 5 ranges  
Output: 8Vrms sine, 10Vp-p squarewave  
Synchronization: ±3% of oscillation frequency per Vrms  
Output distortion: 0.05% 500Hz - 50kHz  
0.5% 50Hz - 500kHz  
Output Impedance: 600 ohm

**FUNCTION GENERATOR**  
**FG-2100A \$169.95**  
0.2 Hz - 2 MHz in 7 ranges  
Sine, square, triangle, pulse and ramp  
Output: 5mV-20Vp-p  
1% distortion, DC offset ± 10V  
VCF: 0-10V control frequency to 1000:1

**FUNCTION GEN./COUNTER**  
**FG-2102AD \$234.95**  
Generates signal same as FG-2100A  
Frequency counter 4 digits  
Feature TTL and CMOS output



**RF SIGNAL**  
**GEN./COUNTER**  
**SG-4162AD \$234.95**  
Generates RF signal same as SG-4160B  
Frequency counter 1Hz -150MHz  
Sensitivity <50mV  
For internal and external sources

**AUDIO GEN./COUNTER**  
**AG-2603AD \$239.95**  
Generates audio signal same as AG-2601A  
Frequency counter 1Hz-150MHz  
Sensitivity <50mV  
For internal and external sources

**SWEEP FUNCTION**  
**GEN./COUNTER 329.95**  
0.5MHz to 5 MHz  
Sweep: Lin 10:1 Log 10:1 20ms to 2S  
AM Modulation  
Gated Burst, Voltage Control Generator,  
Generator Control Voltage & 6 digit Counter.

**ALFA ELECTRONICS**  
P.O. BOX 8089 Princeton, NJ 0854

(800) 526-ALFA/(609) 275-0220  
FAX:(609) 275-9536  
Visa, Master Card, American Express, COD, Purchase Order Welcome

15 DAY MONEY BACK GUARANTEE. 1 YEAR WARRANTY  
WRITE FOR FREE CATALOG. PRICES SUBJECT TO CHANGE





# STARTEK INTERNATIONAL INC

## ATH™ - BAR GRAPH FREQUENCY COUNTERS

Check out the **ALL NEW ATH-15 ... It's FAST!**

The **ATH-15** can ACCURATELY READ an input signal, DISPLAY the frequency and AUTOMATICALLY switch to HOLD status, in less than 8% of a second !!

- **ATH™ - AUTO TRIGGER & HOLD**
- ONE-SHOT ATH™ OPTION
- AUTOMATIC CLEAN DROPOUT
- 800% FASTER RESPONSE TIME
- ULTRA BRIGHT LED DIGITS
- MAXIMIZED SENSITIVITY <1mV typ
- 3 to 5 HOUR NI-CADs STANDARD
- BATTERY CHARGE INDICATOR
- 4 GHZ - 2 INCH LED BAR GRAPH
- 2 RANGES - 6 FAST GATE TIMES
- 1 PPM TCXO STANDARD
- HIGH STAB 0.2PPM TCXO OPTION
- MANUAL HOLD FUNCTION
- BLANK DISPLAY FUNCTION
- 9-12V AUTO-POLARITY PWR JACK
- **StarCab™** ALUMINUM CABINET
- 1 YEAR LIMITED WARRANTY

**ATH™** refers to our exclusive new **AUTOMATIC TRIGGER & HOLD** circuit with **AUTOMATIC CLEAN DROPOUT**. With **ATH™** you can say good-bye to almost all of that annoying random counting and the false readings we have become accustomed to when using portable counters. The model **ATH-15** is an **ULTRA HIGH SENSITIVITY**, 1 MHz to 1500 MHz frequency counter with an **INTEGRATED BAR GRAPH** circuit which **instantly** displays the signal strength of an input signal from < 1 MHz to over 4 GHz. When the **ATH™** feature is used, the counter displays the last readable signal received. It automatically triggers on a readable signal and automatically switches to the "hold" status when the signal disappears. Because of **AUTO TRIGGERING**, the first reading is correct. If the signal stops in the middle of a sample or gate time, the last complete accurate reading will be displayed and the unit switched back to "HOLD" status, hence the **AUTOMATIC CLEAN DROPOUT** prevents the display of erroneous data, all this is done automatically, with hands free operation - and it works great !!!

We are further responding to user requests by offering a **ONE-SHOT ATH™** option. This consists of a **ONE-SHOT** select switch, a push button **RESET** switch and two LED indicators all located on the top of the counter (not shown). When this function is used, the first readable signal that triggers the counter will be held on the display until manually reset. One push of the reset button will reset the display to zeros and enable the one-shot circuit again. The display can be blanked or turned off pending the auto triggering from an input signal, which also saves power under battery operation.

**RESPONSE TIME**, defined as the time from the beginning of the input signal to a stable, accurate, readable display, has been dramatically speeded up. The **RESPONSE TIME** is actually 800% faster than previous models and if you consider not having to manually throw the hold switch, at just the right time, the **ATH-15** is functionally the fastest counter you can buy !!



**MADE IN USA**

**SAY GOOD-BYE  
TO RANDOM  
COUNTING &  
FALSE READINGS**

**ATH-15**

SIZE: 4"H x 3.5"W x 1"D

<b>#ATH-15</b>	<b>FREQUENCY COUNTER</b>	
	WITH NI-CADs & 110VAC ADP	\$235.
<b>FACTORY INSTALLED OPTIONS:</b>		
#O/S-ATH-15	ONE-SHOT ATH™	40.
#HSTB-15	HIGH STAB TCXO 0.2ppm	100.
<b>ACCESSORIES:</b>		
#CC-90	BLACK VINYL ZIPPER CASE	12.
#TA-90	TELESCOPING BNC ANTENNA	12.
#P-110	PROBE, 200 MHZ, 1X-10X	39.
#M207IC	CABLE FOR MFJ-207/208	10.

**CHECK IT OUT. ... BEFORE YOU BUY A COUNTER**  
 Does Bar Graph give **INSTANT** readings or 3 gate times delayed?  
 Does Bar Graph work on every range? Over 2 GHz? With HOLD on?  
 Does HOLD switch **CHANGE** the GATE selection when turned off?  
 Does unit **SELF-OSCILLATE** - random count with no input signal?  
 How many switches needed to select range? Gate times per range?  
 How long does unit operate with batteries? One hour?  
**NO PROBLEM** with a **STARTEK POCKET COUNTER™ II**

**ALL MODELS  
IN STOCK  
WE SHIP  
SAME DAY!**

Orders & Information  
**305-561-2211**  
 Orders only  
**800-638-8050**  
 FAX 305-561-9133



**STARTEK INTERNATIONAL INC**  
 398 NE 38th St., Ft. Lauderdale, FL 33334

**TERMS:** Shipping-handling charges for Florida add \$4 + tax, US & Canada add 5% (\$4 min - \$10 max), others add 15% of total. COD fee \$4. VISA, MC or DISCOVER accepted. Prices & specifications subject to change without notice or obligation.

CIRCLE 297 ON FREE INFORMATION CARD



# OCEAN STATE ELECTRONICS

PROFESSIONAL, AMATEUR, OR COMMERCIAL — WE'RE YOUR ONE STOP ELECTRONIC SOURCE  
CALL OR WRITE FOR OUR FREE 112 PAGE CATALOG 1-401-596-3080



### DELUX CODE KEY

Adjustable, heavy duty brass base with ball bearing pivots  
Designed for hard usage  
3/16" plated contacts.

\$10.75

### MASTERING THE MORSE CODE

This book teaches the beginner how to learn the Morse Code. Some of topics covered are Rules for practicing the Morse Code, the code alphabet, how to send and receive code, how to build and hook up a code practice oscillator. 32 pages.

\$2.50

### CODE PRACTICE OSCILLATOR & MONITOR IN KIT FORM OR WIRED

A solid-state code practice oscillator and monitor that uses the latest IC circuitry. It contains a 3" built-in speaker, headphone terminals, a volume control and a tone control. It is attractively packaged with a two color panel. With the addition of a few parts, the unit can easily be converted into CW monitor. It can there fore be used as an operating aid after the code has been learned.



Kit ..... \$19.95

Wired ..... \$24.95

### LINEAR IC'S

NE555	.25
NE564	1.75
LM733N	.65
LM741	.30
UA7805	.39
UA7812	.39
UA7820	.49
UA7824	.49
UA7912	.75
LM317T	.69

### TRANSISTORS

PN2222A	.07
2N2222A	.35
2N3055	.69
2N3553	2.75
2N3563	.35
2N3866	1.00
2N3904	.10
2N3906	.10
2N4401	.15
MPP102	.29



### MAGNET WIRE

Plain enamel. Solid bare copper. For winding coils, transformers and toroids. Prices for 1/4 lb. spools.

#14	3.25	#24	3.70	#34	4.80
#16	3.30	#26	3.75	#36	4.90
#18	3.35	#28	3.85	#38	4.95
#20	3.55	#30	4.00	#40	5.10
#22	3.65	#32	4.40		

### TOROIDS

IRON		FERRITE	
T-25-2	.40	FT37-43	.60
T-25-6	.40	FT37-61	.60
T-37-6	.45	FT37-77	.60
T-37-12	.45	FT50-43	.75
T-50-2	.55	FT50-61	.75
T-50-3	.55	FT50-77	.75
T50-8	.55	FT82-43	1.00
T68-0	.75	FT82-67	1.00
T68-2	.75	FT82-68	1.00
T68-6	.75	FT114-61	2.15
T80-2	.85	FT140-43	4.10
T200-2	4.00	FT240-61	8.00

WE STOCK A COMPLETE LINE OF TOROIDS AND BEADS.



### Q-DOPE

Solution of pure polystyrene in solvents. Dries fast and leaves a clear, protective coating on toroids, coils and transformers, with no or minimal effect on inductive values. May also be used as a cement for molded or fabricated items made of polystyrene.  
(Bottle with Brush 2 fl. oz. 59 ml) ..... \$3.75

### CD22402E

CMOS LSI Sync Generator  
\$9.95



### MAKE CIRCUIT BOARDS THE NEW, EASY WAY WITH TEC-200 FILM

JUST 3 EASY STEPS:

- Copy circuit pattern on TEC-200 film using any plain paper copier
- Iron film on to copper clad board
- Peel off film and etch



Convenient 5 1/2 x 11 size  
With Complete Instructions

5 SHEETS ..... \$6.25

10 SHEETS ..... \$10.75

20 SHEETS ..... \$16.25

### REGULATED POWER SUPPLIES 13.8 VDC

Perfect for ham equipment, CB's, car stereos and other 13.8 VDC items. LED on indicator, short circuit protection. Binding post output. 2 year warranty.



3 AMP	\$29.50
4 AMP	\$39.50
6 AMP	\$46.50
10 AMP	\$79.50
20 AMP	\$119.50
30 AMP	\$139.95

### MINI-CIRCUITS SBL-1 DIODE RING MIXER

Double balance Mixer  
LO/RF - 1-500MHZ  
RF DC - 500 MHZ  
\$6.75

### MINIATURE TOGGLE SWITCHES 3A 125V Solder Terminals

SPDT ON-ON	\$1.25
DPDT ON-ON	\$1.50



### DIGITAL CAPACITANCE/ INDUCTANCE METER



DIGITAL LCR METER measures inductance, capacitance and resistance. At Last! An LCR meter that everyone can afford. Now you can measure coils, transformers, chokes from 1µH to 200H. Capacitors from 1 pfd to 200 mfd and resistors from 1 ohms to 20 meg ohms. All in one handheld instrument.  
MODEL LCR-1801 ..... \$119.95



### VERNIER DIALS

1-1/2" Diameter 0-10 Marking \$8.25  
1-1/2" Diameter 0-100 Marking \$9.25  
2" Diameter 0-100 Marking \$10.25



### SIGNETICS NE602AN

Balanced Mixer/OSC. Popular IC among experimenters for building DC and super-het receivers  
\$2.49 ..... BUY 3 OR MORE ..... \$2.25

### 200 WATT INVERTER

Plugs into your lighter and runs:




- Ham Equipment
- Lights
- Soldering Iron
- Computer
- Power Tools
- Shaver
- 13" TV with VCR
- MUCH MORE

Model: POW 200  
Input: 10 to 15 volts DC  
Output: 115 volts AC true RMS  
Power: 400 Watts peak  
200 Watts for 2 minutes  
140 Watts continuously  
5" x 2.6" x 1.7"  
Weight: 15 ounces  
Warranty: 3 year  
\$99.95
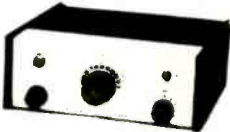
### QRP CW TRANSCEIVER KIT

- Covers 14.0 MHz to 14.1 MHz on 20 M or covers 7.0 MHz to 7.150 MHz on 40M
- Available on 20M or 40M band
- Superior Superhet
- Single signal receiver
- CW crystal ladder filter
- VFO tuning with vernier dial
- RIT w/center detent control
- Very effective AGC
- Selectable audio filter
- Side-tone Oscillator
- 2-3 watts of RF output
- Semi break-in
- 12VDC operation
- Custom pre-painted, punched & silkscreened cabinet
- 100% complete kit with instructions. Nothing else to buy!
- Measures (HWD): 2 1/4" x 6 1/4" x 6"
- Weight 24 oz.



QRP-20	20M VERSION	\$149.95
QRP-40	40M VERSION	\$149.95

### SIGNAL INJECTOR/ TRACER KIT

This handy tester is both a signal generator and receiver. As a generator use it to check out an amplifier, stage by stage. Also tests AM radio IF and RF stages. As a receiver you can pin point where a defective part exists. Will transmit and receive simultaneously.



\$18.95

### LOGIC PROBE KIT

Hand held Digital Logic Probe provides convenient and precise use in the measurement of logic circuits. It displays logic levels (high or low), pulses and voltage transients down to 300 nanoseconds. High intensity LED readouts provide instant response to the logic state.




\$18.95

### TRIMMER CAPACITOR ASSORTMENT

Top Quality. May contain some two and three gang as well  
10 pcs ..... \$1.50
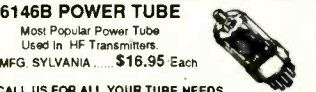
### VERNIER DRIVE

American made 6:1 vernier drive. Has dual plate mounting flange with two tapped holes (2-56) for dial mounting input & output mate with 1/4" shaft  
\$10.75



### 6146B POWER TUBE

Most Popular Power Tube Used in HF Transmitters.  
MFG. SYLVANIA ..... \$16.95 Each

CALL US FOR ALL YOUR TUBE NEEDS

### LEARN COMPUTER THEORY BY BUILDING THIS KIT DIGITAL TRAINER MODEL MM-8000

Starting from scratch you build a complete computer system. Our Micro-Master trainer teaches you to write into RAMs, ROMs and run a 8085 microprocessor. You will write the initial instructions to tell the 8085 processor to get started and store these instructions in permanent memory in a 2816 EPROM. Teaches you all about input and output ports, computer timers. Build your own keyboard and learn how to scan keyboard and display. No previous computer knowledge required. Simple easy to understand instruction teaches you to write in machine language. Upon completion of this course you will be proficient in computer technology.

- Uses the 8085 Microprocessor
- Uses the 2816 EPROM, electrically erasable programmable ROM
- Uses the 8156C, 2048 Bit static MOS RAM with I/O ports and timer
- Memory expandable option
- Built in 5V power supply
- 28 key keyboard
- Complete with lesson manual, instructions and experiments



\$119.95

### circuit™ works CONDUCTIVE PEN

### NEW MICRO TIP FOR THINNER TRACE

- Use where conductive electronic traces are needed
- For designing Prototype circuits
- Pen tip redesigned to draw more narrow traces
- Offers improved conductivity, better trace adhesion, and a reduced settling in the pen
- Dries in 3-5 minutes at room temperature
- Spring loaded tip for smooth flow



\$10.95

Call 1-800-866-6626  
(Catalog requests can not be taken on toll free number.)

8 a.m. - 5 p.m. EST  
Monday through Friday

OR WRITE TO:

Ocean State Electronics,  
P.O. Box 1458, Westerly, R.I. 02891

OR FAX TO: CATALOG REQUESTS  
(401) 596-3590 (401) 596-3080

If paying by CREDIT CARD include Card No. and Expiration Date

Mail in orders please include \$4.00 shipping  
CANADA \$7.00 - OVERSEAS \$12.00  
Minimum order \$10.00

R. I. Residents add 7% Sales Tax

ORDERS RECEIVED BY 1:00 PM EST—

SHIP SAME DAY!

FREE SHIPPING ON ALL MAIL IN ORDERS  
OVER \$25.00.

NOT VALID WHEN COMBINED W/CAT. ORDERS.  
Applies to UPS Ground in Continental U.S. Only.

PRICES SUBJECT TO CHANGE

### TO ORDER



### EDGEWISE MOUNT S-METER/SWR

200µA movement. Scale reads signal 0-60db. Has two ear flanges with holes for mounting.  
Measures approx. 1 1/2"W x 1 1/4"D x 7/8"H. \$4.00



200µA movement. Scale reads both signal (0-30db) and SWR. Same mounting as above  
Measures 1.38"W x 1 1/4"D x 3/4"H. \$4.00

### MULTIVOLTA AC ADAPTER

Rated 500MA  
Input 117VAC  
Output 3V, 4.5V, 6V,  
7.5V, 9V, 12V DC  
Polarity switch  
Universal plug



\$5.95

### RECTIFIER DIODES

1N4001	.09
1N4002	.09
1N4003	.10
1N4004	.10
1N4005	.12
1N4006	.15
1N4007	.17
1N5400	.20
1N5401	.20
1N5402	.20
1N5404	.25
1N5406	.25
1N5407	.25
1N5408	.25

### COPPER CLAD PC BOARDS

One oz. copper, phenolic base.  
Single sided

7" x 5"	\$1.50
8" x 7"	\$2.00





# CAIG Electronic Chemicals for Manufacturing, Maintenance & Service!

## ProGold™ Gold Conditioner & Protector

- Protects Gold Surfaces & Base Metals!
- Improves Conductivity!
- Forms Protective & Anti-tarnish Coating!
- Reduces Wear & Abrasion!
- Reduces Arcing & RFI!
- Reduces Intermittent Connection Failures!



**ProGold** is specifically formulated to improve conductivity and protect gold, base metals and other precious metal surfaces.

A common problem with gold plated surfaces is that the base metals migrate to the surface due to gold's soft and porous nature (dendrite corrosion). Once exposed, base metals oxidize, adding unwanted resistance that impedes electrical performance. Since gold plated surfaces are thinly coated, they are susceptible to scratching & abrasion, further exposing the base metals.

**ProGold**, a one step treatment, conditions gold connectors, contacts and other metal surfaces, enhancing the conductivity characteristics to efficiently transmit electrical signals. Non-abrasive/non-corrosive formula, non-flammable, non-toxic, ozone-safe.

## DeoxIT™ & PreservIT™ Improves Conductivity and Protects Electrical Connections

- Improves Conductivity
- Reduces Intermittent Connection Failures
- Reduces Arcing & RFI
- Reduces Wear & Abrasion
- Extended Temperature Range, -34°C to 200°C



**DeoxIT**, a one step treatment, is a fast-acting deoxidizing solution that cleans, preserves, lubricates and improves conductivity on all metal surfaces. Temperature range -34°C to 200°C. Non-flammable, non-toxic, non-corrosive, non-gumming, ozone-safe.

**PreservIT**, seals, lubricates and preserves metal surface for protection from oxidation and contamination. For use on clean surfaces or ones pre-cleaned with **DeoxIT**. Temperature range -34°C to 200°C. Non-flammable, non-toxic, non-corrosive, non-gumming, ozone-safe.

These new advanced formulas contain improved deoxidizers, preservatives, conductivity enhancers, anti-tarnishing compounds, arcing & RFI inhibitors and provide extended temperature range. **DeoxIT's** new formulation also prevents dissolved oxides/contaminants from re-attaching to metal surfaces, providing longer lasting protection.

*"We were having trouble with edge connectors in our manufacturing environment until we tried ProGold Wipes...great product."*  
J. P., General Electric

*"Static and dirt buildup on our CRT screens have always been an annoying problem. We have tested many products and find OpticALL to last considerably longer and work just as well on our plastic and metal enclosures."*

A. R., University of Maryland, College Park, Dept. of Physics & Astronomy

*"For many years we have been using CAIG's liquid and spray products in the lab for service and repair of connectors, switches and potentiometers. I also use their paste products on my boat to prevent corrosion from salt water and air ... fine products for a variety of applications"*

T. S., University of California, Lawrence Livermore National Laboratory

*"Corrosion problems on very sensitive connectors have been an annoying problem for us. We have tried many products without success until we tried CAIG's DeoxIT. DeoxIT is the only product that has worked perfectly. We highly recommend it!"*

R. V., Xerox Corporation

## OpticALL™

Effectively cleans, polishes and eliminates static electricity on optical viewing surfaces. OpticALL is also recommended as a general purpose antistatic cleaner on plastic, glass and metal surfaces.

## StaticALL™

Neutralizes static build-up caused by friction & low humidity conditions.

## DustALL™

Quickly & safely removes dust, lint & particles from sensitive electronic equipment, computers, lab equip., optical grade surfaces & other mechanisms & equipment.

## FreezALL™

Quickly and safely cools circuits to -54°C. Locates intermittent components due to heat failure and hairline cracks on PCBs.

## MechanicALL™

High Penetrating Anti-Corrosive Anti-Tarnishing Cleaner & Lubricant. Lubricates & Protects, Displaces Moisture, Stops Squeaks, Migrates & Coats Entire Surface.

## ElectricALL™

Rejuvenating Solution For All Electrical Applications. Cleans, Preserves, Improves & Protects Connections, Removes Corrosion & Oxidation, Reduces Wear, Abrasion, Arcing & RFI.

## DegreasALL™

For degreasing, cleaning & defluxing equipment and parts. Removes oil, grease, dirt and contaminants including rosin flux from PCBs, components and metal parts. Biodegradable.

## CAEON™ 27

For sensitive equipment applications. For removal of oil, grease & dirt from surfaces. (Freon® TF).

## CAEON™ 28

Degreaser and cleaning liquid removes organic contaminants including rosin flux from PCBs, components and metal parts. (Freon® TMC).

## X-10S Instrument Oil

Contains silicone. Finest quality instrument oil for use on rubber, plastics and metals. Non-gumming, rust inhibiting, long lasting lubrication.

## X-10 Instrument Oil

Lubricates precision instruments, fine parts & mechanisms. Use on all metals (gauges, gears, clocks, instruments, etc.). Non-gumming, rust inhibiting, long lasting lubrication.



## Caig Products ... used by those who demand the best!

Amplex	Hewlett Packard	RCA
Boeing	Honeywell	Switchcraft
Capitol Records	IBM	Tektronics
Diebold, Inc.	John Fluke Mfg.	Texas Instruments
Dolby Laboratories	McIntosh Labs	Wayne-Dresser
General Electric	Motorola	Xerox Corp.
Grumman Aerospace	Nakamichi	... and many more



16744 W. Bernardo Drive,  
San Diego, CA 92127-1904

Phone: (619) 451-1799,  
FAX: (619) 451-2799

CIRCLE 286 ON FREE INFORMATION CARD

www.americanradiohistory.com

# Satellite Television

Order Your **FREE** Catalog/Buyers Guide Today!



**Skyvision Inc.**®

The World Supplier of Satellite T.V. Products. . . "Down To Earth Prices"

**LOWEST PRICE EVER**  
On Complete Ku Band  
Satellite Systems

### STANDARD KU SYSTEM

Package **INCLUDES** all of this:

- Quality aluminum 3ft dish
- Pansat BR 1100 Receiver
- Polar tracking mount
- Polarity switching feed
- Low Temperature LNB
- 100ft All in one ribbon cable

**\*Complete System**  
**Only \$479**

### DELUXE KU SYSTEM

Package **INCLUDES** all of this:

- Quality aluminum 3ft dish
- Pansat BR 3000 programmable receiver with IR remote control
- Pansat AP 3000 Antenna positioner with 77 satellite programmability
- Polar tracking mount and motorized arm
- Polarity switching feed
- Low Temperature LNB
- 100ft All in one ribbon cable

**\*Complete System**  
**Only \$698**

\*All you need to supply is ground pole to mount dish on. (23/8" O.D.)



**Satellite Analysis and Antenna Aiming Software**

An extremely valuable tool for designing and installing TVRO's, tailored for ease of use by professionals and dealers as well as by technically orientated TVRO owners. Demonstrates how changing parameters such as dish size or LNB noise temperature affect picture quality. The program performs both TVRO system analysis and antenna aiming. The analysis subcomponent, is especially useful for predicting performance when viewing signals from a particularly weak satellite. The aiming subcomponent calculates azimuth and elevation angles and range to all satellites within "view" of a TVRO. The names and latitudes of all world-wide C and Ku-band broadcast satellites, presently in service or to be launched by 1995, are listed. The user simply enters TVRO site latitude and longitude.

5.25" disk S&H \$ 4.75 \$49.95  
3.5" disk S&H \$ 4.75 \$49.95



**SATELLITE SYSTEM DO-IT-YOURSELF INSTALLATION VIDEO**

**"Now You Can Watch It Being Done"**

Install or "Tune up" your satellite system in no time flat with this professional video.

VHS or Beta (45 Min.) S&H \$3 (U.S.) .....\$33.95



Pico dish Tuning Meter



Bulz-I-Tuning Meter Now with audio alert



**TUNE YOUR DISH TO IT'S MAXIMUM!**

Dish tuning meters are a must for the serious dealer or satellite system owner. Saves time, frustration and money. Use when installing a new system, moving your dish, re-alignment of a dish that has been moved by wind, frost heaves etc., gets you right on the satellite belt for the best possible pictures!


Pico meter (meter tuning) S&H \$6 \$89.95  
Bulz-I-IV meter (meter & audio alert) S&H \$6 \$149.95



**LNBs**  
Now Lower Temp's

**Hemt Technology Commercial Grade**

45° LNB C-band 4GHz	S&H \$6	\$99
35° LNB	"	99
25° LNB	"	139
1.2db LNB Ku 12GHz	S&H \$6	\$99
1.0db LNB	"	126
0.9db LNB	"	139
0.7db LNB	"	199
0.6db LNB	"	229

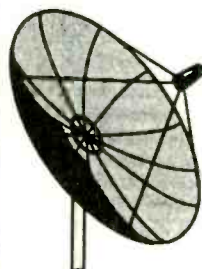

**MESH DISHES by ORBITRON**

*Quality Demonstrated by Performance*

Orbitron antennas ("size for size") are known the world over for their superior reception and picture quality.

7ft dish & polar tracking mount	\$239
8.5ft	299
10ft	349
10ft H D.	439
12ft	639

All Major Credit Cards Accepted

**Skyvision Inc.**®

1046 Frontier Drive, Fergus Falls, MN 56537 - Toll Free 800-334-6455

Mail in coupon or call today for the SKYVISION Satellite TV Product Catalog/Buyers Guide Delivered free to your mail box in U.S. and its possessions.

- Send Free Domestic Satellite TV Products Catalog
- Send International Satellite Catalog (For International Catalog add \$8.00 to cover S&H)

Name \_\_\_\_\_ Phone ( ) \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_



**Install A System, Upgrade & Repair Yourself And Save \$\$\$**

**Call Toll Free 800-334-6455 International 1-218-739-5231 Fax 218-739-4879**

CIRCLE 270 ON FREE INFORMATION CARD

www.americanradiohistory.com



# Davidyn CORP.

13406 Saticoy Street  
North Hollywood, CA 91605-3475

VISA

MasterCard

## R.F. WATTMETER ME-82/U (MFG M.C. JONES MODEL MM-625)



Contains built in power load—oil filled.  
Frequency Range: 50 to 600 MHz.  
Impedance: 52 OHMS.  
Power Level: 120 Watts.  
Size: 6"W x 7"H x 13" Deep.  
Weight: 10 lb.


Price: \$150.00



## TEKTRONIX 528 SOLID STATE N.T.S.C. WAVEFORM MONITOR

8 x 10 display, two composite video inputs  
75 ohms, selectable 1 volt or 4 volt full scale,  
(140 IRE units)  
YRGB and RGB input. Video output response  
25Hz to 5 MHz  $\leq$  3%.  
FOUR RESPONSE POSITIONS: 1) Flat, 2) IRE, 3) Chroma, 4)  
Differential gain.  
FOUR SWEEP MODES: 1) 2-V Sweep 1, 2) 2-V mag sweep,  
3) 2-H sweep, 4) 1 US sweep.  
SIZE: 5'4"H x 8'1/2"W x 18'1/2"D  
WEIGHT: 15 LBS  
POWER: 115V 60 HZ 48 watts

Price: \$495.00

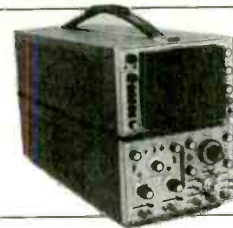

## MODEL HP 180A

Oscilloscope: Mil Spec AN/USM-281A,  
8 x 10 CM display, 100 MHz response  
which accepts standard 1800 series  
Plug-ins. Includes Vertical Plug In:  
1801A (PL-1186), frequency BV 50 MHz,  
maximum sensitivity 5mV/DIV. Horizontal  
Plug-In: 1821A (PL-1187), triggering  
to 100 MHz, minimum sweep time  
100 NS/DIV, has delayed sweep capacity.  
Price: \$250.00



## COLLINS 30L-1 LINEAR AMPLIFIER (S-LINE)

Frequency: 80, 40, 20, 15, 10 meters  
3.4 to 5.0 MHz, 6.5 to 9.5 MHz  
9.5 to 16 MHz, 16 to 22 MHz, 22-30 MHz  
Mode: SSD or CW  
Power Out: 1000 W PEP, 1000W CW  
Drive: 70-100 watts full output  
Harmonic Distortion: -40 dBc 2nd  
-30 dBc 3rd  
Output Impedance: 5052 VSWR <2:1  
Power Requirements: 1200 watts CW  
300 watts SSB no modulation  
550 watts SSB speech modulation  
Voltage 115V or 230V 50-60HZ  
Wt: 38 lbs. Size: 14'3/4" x 7'3/4" H x 14"D  
Price: \$895.00



## TEKTRONIX SOLID STATE PORTABLE 491 SPECTRUM ANALYZER

Frequency 10MHz—2 GHz with internal mixers. 1.5GH to  
40GHZ with plug-in mixers for use to 12.4GHZ. Dispersion  
1KHZ/div. to 10MHz/div. Coupled Resolution: 1KHZ to 100KHZ.  
Display Flatness: over 100MHz dispersion to 12.5GHZ  $\leq$  3dB  
above 12.5GHZ,  $\leq$  6dB. Incidental FM:  $\leq$  300HZ. Frequency Stability:  
(after warm up)  $\pm$  10KHZ with line variation.  
 $\pm$  5.0KHZ/°C with  $\pm$  100KHZ, KHZ dispersion.  $\pm$  20.0KHZ/°C  
with  $\pm$  200KHZ, MHz dispersion. Internal 1MHz phase lock.  
Input Impedance 5052. Max Input Power: -30dBm (linear  
range), +15dBm (mixer limit). I.F. Attenuator: 51dB in 1d steps.  
I.F. Gain: >50dB. Display: Log,  $\leq$  40dB, Linear,  $\leq$  26dB, Square  
Law,  $\leq$  13dB. Sweptime: 10 micro seconds to .5 Sec./div. CRT is  
8 x 10 divisions (.8cm/div). Power Requirements: 90K136 VAC or  
180 to 272VAC, 48 to 440HZ, 55 watts. Size:  
7'3/16"H x 12'7/16"W x 19'1/16"D. Weight: 30 lbs. Price: \$1400.00

## GENERAL MICROWAVE 476 THERMALELECTRIC POWER METER



With type 4240A power head.  
Power range: 30n watts to 10m W  
(-45 to +10 dBm).

Frequency Range: 0.01 to 18 GHz  
VSWR: 1.5 from 0.01 to 0.015 GHz  
1.35 from 0.015 to 10 GHz  
1.6 from 10 GHz to 18 GHz

Connector: Type N  
Meter Size: 4.5 inches  
Accuracy:  $\pm$  1% of full scale on all ranges  
Built in 10 KHZ calibration signal. Power  
Requirements: 115V/230V, 50-1000HZ @ 5 watts.  
Size: 6.1"H x 5.1"W x 11.3"D.  
Weight: 7 lbs.

Price: \$350.00




## ANRITSU ML422B

Anritsu ML422B Programmable Selective Level Meter. Has  
synthesized frequency tuning (rotary dial on keypad entry).  
Automatic tone search for unknown signals, swept frequency,  
keypad data entry for amplitude and frequency limits,  
IEEE488 computer control capability. Frequency range: 50HZ to  
30MHz (8 digit LED readout). Stability:  $\leq$   $5 \times 10^{-7}$  to 45°C,  
 $\leq$   $1 \times 10^{-6}$  year. Bandwidths: Wideband, 48khz, 3.1khz and  
20hz (-3dB). Amplitude Range: -120dBm to +30dBm  
depending on bandwidth setting (5 digit readout and meter).  
Amplitude Accuracy:  $\pm$  0.15dB to  $\pm$  1.5dB depending on level  
range and frequency setting. Input Impedance: 75 ohms terminated  
unbalanced or 10Kohm unbalanced, 75, 124,  
135, or 600 ohms terminated balanced. 1.5Kohm and 20Kohm  
unterminated balanced. Distortion: Input  $\leq$  10dBm, single  
tone, 2nd and 3rd order  $\leq$  -70dBc from 1khz to 12mhz. I.F.  
Rejection:  $\leq$  -70dBm @ 56.6mHz,  $\leq$  -80dB elsewhere. Image  
Rejection:  $\leq$  -80dB. Phase Jitter:  $\leq$  0.5° p-p, 0.1° resolution.  
Power: 115V, 3.15A, 60Hz AC. Size: 16'3/16"W x 7'3/8"H x 19'3/4"D.  
Wt: 45 lb. Price: \$56,500.00


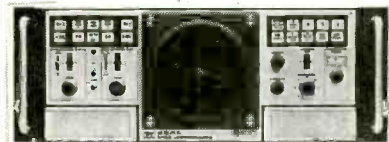
## COLLINS KWM—2A TRANSCEIVER

Frequency Range: 3.4 to 30 MHz except 5.0 to  
6.5MHz. Unit Cover: 80, 40, 20, 15 and 10 meter.  
Amature bands. Modes: SSB, CW or RRTY. Sensitivity:  
0.5 uv for 10 db S+N/N. Selectivity: 2.1 KHZ,  
6db down; 4.2 MHz, 60 db. Image Rejection:  
 $\leq$  40db. Power Output: 3.4 to 15 MHz 100 watts PEP,  
50 ohms; 15 to 25 MHz, 90 watts PEP, 50 ohms; 25 to  
30 MHz 80 watts PEP, 50 ohms. Plate Input: 175 watts  
PEP on SSB; 160 watts CW Size: 14.75" x 7.75"H x  
14"D. Weight: 18 lbs., 3 oz. Price: \$795.00



## TEKTRONIX 520A DUAL CHANNEL VECTORSCOPE

Measures: Luminance Amplitude, Chrominance  
Amplitude and Phase differential phase and gain  
(1% accuracy). CRT accuracy of 12.5" and 2.5 IRE  
units for vector and amplitude measurements. In-  
ternal calibrated phase shifter with a range of 30°,  
with accuracy of 0.5°. Color demodulation in I, Q or  
R-Y axis. Vertical internal test signal observation.  
Video inputs: 75 ohms, 2 each, >46dB, return loss to  
5MHz. Swept measurements of Y, R, G, B. Input  
power: 90 to 136 VAC or 180 to 272 VAC, 47 to 63HZ,  
95 watts. Size: 19"W x 7.0"H x 19.8"D. Weight: 33  
lbs. Price: \$1495.00

(818) 787-3334

(800) 235-6222

FAX (818) 787-4732

CIRCLE 236 ON FREE INFORMATION CARD

www.americanradiohistory.com




We Sell **QUALITY PARTS** • We Have **DISCOUNT PRICES** • We Ship **FAST**

# ALL ELECTRONICS CORP.
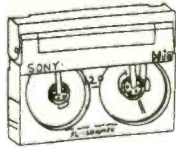
## 8 MM SONY VIDEO CASSETTES (USED)

Sony 120 minute, Hi8 metal particle video cassettes.



Used and bulk erased. In new condition these high quality cassettes would sell for considerably more. A great deal for 8mm camcorder users. **CAT# VCU-8** \$2.50 each • 5 for \$11.00

## Solid State RELAY For D.C. Loads

Opto 22 # DC60S3  
Control Voltage: 3-32 Vdc  
Load: 3 amps  
@ 4-60 Vdc



(5 amp surge). This Solid State relay is designed to switch D.C. loads. 2.25" X 1.75" X 0.91" high. Epoxy block with metal base. Screw terminals.

**CAT# SSRLY-12U** \$9.50 each

## General Use A.C. Switch

Leviton. Standard SPST, 15 amp AC switch. Brown. Screw terminals. Fits all standard wall switch boxes. **CAT# ETS-1** 2 for \$1.00



## 12 VDC 300 ma. Wall Transformer

New 12 Vdc, 300 ma wall transformers. Cord terminates to bare wire.



Large quantity available.

**CAT# DCTX-1231** \$2.25 each


100 for \$20.00 • 1000 for \$185.00
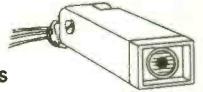
## PHOTOELECTRIC SWITCHES

Adalet model 57010. Turn lights, signs and other electrical devices on at dark and off at dusk. Built-in delay to prevent switching caused by sudden change in ambient light. 120 Vac, 300 watts. UL listed. 0.65" diameter threaded bushing for mounting. Threaded plastic nut. 9" long pigtail leads. **CAT# PES-1** \$3.00 each




Adalet model 57000. Operates the same as the unit left, but this one is built into an adjustable swivel mount to facilitate aiming the device. Base of swivel is threaded 3/4" threaded bushing designed to screw into standard electrical knock-out box. **CAT# PES-2** \$4.00 each


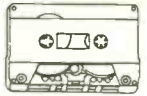
## HIGHEST QUALITY METAL CASSETTES (Erased)

Premium quality metal tape in C-60 cassettes (30 or more per side). One of the finest "brand-name" tapes on the market, in durable, clear plastic transport mechanisms. Recorded and bulk erased, the record-protect tabs have been removed and therefore, need to be taped over to re-record. Audiophiles will appreciate the wide dynamic range of this tape. If your cassette deck has a "metal" setting you will hear the difference. A real bargain!




**CAT# C-600M** \$1.25 each  
10 for \$10.00
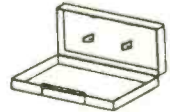
## CASSETTE STORAGE CASE

Black, unbreakable plastic audio cassette storage case.

**CAT# CBOX** 5 for \$1.00 • 100 for \$15.00



## CABLE TIES

Cat#	Approx. Length	Min. Tensile Strength	Color	Max. Bundle Dia.	10	100	1000
TR-400	4"	18 lbs	neutral	15/16"	.30	\$2.50	\$15.00
TR-400B	4"	18 lbs	black	15/16"	.35	\$3.00	\$17.50
TR-600	6"	30 lbs	neutral	1 1/2"	.50	\$4.00	\$30.00
TR-600B	6"	30 lbs	black	1 1/2"	.50	\$4.00	\$30.00
TR-800	8"	50 lbs	neutral	1 3/4"	.60	\$5.00	\$40.00
TR-800B	8"	50 lbs	black	1 3/4"	.70	\$6.00	\$50.00
TR-1100	11"	50 lbs	neutral	3"	.70	\$6.00	\$50.00
TR-1100B	11"	50 lbs	black	3"	.80	\$7.00	\$60.00
TR-1500	15"	50 lbs	neutral	4"	\$1.00	\$8.00	\$70.00
Heavy-duty 15" cable tie.							
TR-1500HD	15"	120 lbs	neutral	4 1/4"	\$1.50	\$12.00	\$100.00



## DYNAMIC MICROPHONE




Good quality dynamic mike. Brushed aluminum with black trim. 0.93" dia. X 4.42" long. 5' cord with 3.5mm mini-plug.

**CAT# MIKE-12** \$1.50 each

## 115 VAC COOLING FAN

Open frame cooling fan with 3.25" square plastic cage. Mounting holes on 2.75" centers.

**CAT# CF-16** \$4.00 each

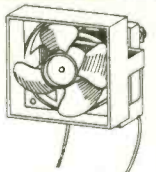

## 15" POWER CORD

15" Belden SVT 18/3 black detachable power cord. 3 prong right angle grounded AC plug one end, IEC socket other end

**CAT# LCAC-15** \$1.25 each 10 for \$1.00



CALL OR WRITE FOR OUR **FREE 60 PAGE CATALOG**

WITH OVER 4000 PARTS!  
OUTSIDE THE U.S.A. PLEASE SEND  
\$2.00 POSTAGE FOR A CATALOG

**TOLL FREE  
PHONE ORDERS  
1-800-826-5432**

MAIL ORDERS TO:  
**ALL ELECTRONICS CORP.**  
P.O. Box 567  
Van Nuys, CA 91408-0567



We Sell **QUALITY PARTS** • We Have **DISCOUNT PRICES** • We Ship **FAST**

# ALL ELECTRONICS CORP.

## LASER COMPONENTS

### WARNING!!!

**DO NOT BUY these products if you do not know the dangers of laser energy! We are selling components only. If assembled into a complete laser system, they must comply with all C.D.R.H. regulations.**



### Laser Tube



Siemens # LGR 7659  
1 mW helium-neon laser tube.  
22.5 mm diameter X 146 mm long. 1.7  
mrad beam divergence. 7 kV start voltage.  
1kV operating voltage. 3.5 mA current.

**CAT# LT-1 \$25.00 each**

### Laser Power Supply



Epoxy encapsulated power supply for up to 2 mW lasers.  
4 1/2" X 1 1/2" X 1 7/16".  
Input: 9 Vdc @ 1 amp  
Output starting voltage: 7 to 8 kV  
Operating voltage: 1.1 to 1.5 kV  
Operating current: 4 to 5 mA  
Recessed 0.250 quick connect terminals for output. Color coded wire leads for input. **CAT# LPS-1 \$35.00 each**

## NEW LOW PRICE!! REDUCED ELECTRONIC FLASH UNITS

ITT Magicflash. Originally designed for Polaroid One-Step and Pronto cameras. Nice bright flash can be triggered by external 3 Vdc pulse. Operates on 6 Vdc, 4 AA cells (not included).

Useful for special effects of flash lighting. Circuitry includes a very desirable 600 uF 330V photoflash capacitor which is, by itself, worth the price of the unit.

**CAT# FSH-2 \$3.00 each**



## 150 Watt SWITCHING POWER SUPPLY


TRW# 095-10001. Input: 115 Vac

Outputs:

- 5 Vdc @ 20 amp,
- 12 Vdc @ 4.2 amp,
- 12 Vdc @ 0.1 amp.


Fan cooled switching power supply with solid state relay turn-on protection. RF/EMI filter. On/off switch and reset button. Housed in vented metal cabinet. Requires IEC type power cord (our CAT# LCAC-C7 \$3.00 each or similar). UL and CSA listed. 9.5" X 7.25" X 3.45" 12" long wire leads terminate to 0.1" single row connector. Operation note: the solid state relay must be energized to operate supply. This is accomplished by jumping the dark gray and red wires.

**CAT# PS-300 \$27.00 each**

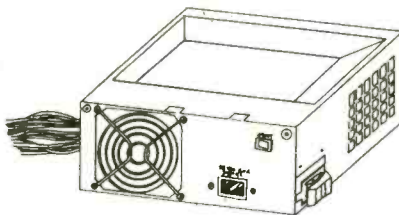
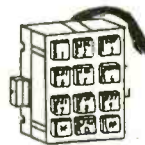
## TOUCH-TONE KEYPADS


American Telecommunications Corp. Telephone keypad assembly with circuitry for producing touch-tones.



7 wire output. Gray with white letters and numbers. 3" X 2.25" X 1.5". Hook-up diagram available. **CAT# TKP-1 \$4.00 each**
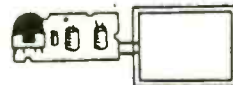
## Electroluminescent BACKLIGHTS

At last! A low cost electro-luminescent glow strip and inverter.




These brand-new units were designed to backlight small LCD TVs made by the Citizen Watch company. The inverter circuit changes 3 or 6 Vdc to approximately 100 Vac, the voltage required to light the glow-strip. Luminescent surface area is 1.7" X 2.25". The strip is a salmon color in its off state, and glows white when energized. The circuit board is 2.2" X 1". Glow strip and circuitry can be removed easily from plastic housing. Ideal for special lighting effects and backlighting. Citizen# 92TA operates on 3-6 Vdc. **CAT# BLU-92**

**\$3.50 each** **LARGE QUANTITY AVAILABLE**  
10 for \$32.00 • 100 for \$275.00
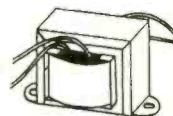
## 4.8K V HIGH VOLTAGE TRANSFORMER

Coiltron# 20956  
Primary: 240 Vac  
Secondary: 4,800 Vac  
2.5" X 3.45" X 2.92".  
Mounting holes on 4" centers.  
3 lbs 2 oz



**CAT# HVTX-1 \$9.50 each**

# TOLL FREE ORDER LINES 1-800-826-5432

FAX (818) 781-2653 • INFORMATION (818) 904-0524

Minimum Order \$10.00 • All Orders Can Be Charged To Visa, Mastercard Or Discovercard • Quantities Limited • California, Add Sales Tax • Shipping And Handling \$3.50 For the 48 Continental United States - All Others Including Alaska, Hawaii, P.R. And Canada Must Pay Full Shipping • No C.O.D. • Prices Subject to change without notice.



# Pocket PC Ref

>> **NEW 2nd Edition! November 1992** <<

An incredible shirt pocket size reference book on IBM® PC's and compatibles. If you're a PC service man, hacker, hobbyist, or general user, **BUY THIS BOOK !!!** It contains a wealth of hard to find information that took 1000's of hours to collect. 320 pp.

By Thomas J. Glover and Millie M. Young. 3.2" x 5.4" x 0.4"

- MS-DOS® 5.0 Reference (142 pages)
- PC Industry Phone Book with over 2500 main, tech support and BBS telephone numbers!
- Specifications and configuration information for over 2000 Hard Drives II
- ASCII Codes, PC Error Codes
- Interrupts-IO Map-Memory Map
- 286/386/486 Hard Disk Types
- Printer Control Codes
- Cable Wiring, Modem Commands
- And MUCH MORE

**\$14.95**




**NEW** 
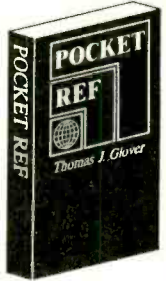
# Amazing Pocket Reference!

480 pages of tables, maps, formulas, constants & conversions and it fits in your shirt pocket! (3.2" x 5.4" x 0.6", 480 pp.)  
*The Greatest pocket reference of all time!*

- Electrical & Electronics
- Air
- Automotive
- Carpentry-Construction
- Chemistry-Physics
- Math
- Mining & Milling
- Money & Currency
- Physical Constants
- Plumbing & Pipe
- Rope-Cable-Chain
- Steel & Metals
- Geology
- Glues and Solvents
- Paints and Finishes
- Hardware
- Surveying & Maps
- Tools
- Water
- Material Weights
- Computer / Printer
- Welding
- 3200 Conversion Factors
- General Info
  - US & State Holidays
  - Signs of the Zodiac
  - Flowers of the Months
  - Anniversary Names
  - Radio Alphabet
  - Morse & TEN Radio Codes
  - Paper Sizes (Int'l)
  - Military Rank & Grade
  - State Information
  - Climate Data of the US
  - Time Zones of the US
  - Time Zones of the World
  - Telephone Area Codes
  - World Airport Elevations
  - Lost Credit Card Phone #'s
  - Airline 1-800 Phone #'s
  - Temperature Conversion
  - Sound Intensities
  - Body Weight vs Height
  - Wind Strength Scale
  - Wind Chill Factors
  - Firewood Companions
  - Frequency Spectrum
  - Sun & Planet Data
  - Earthquake Richter Scale
  - State information
- Detailed Index




**\$9.95**
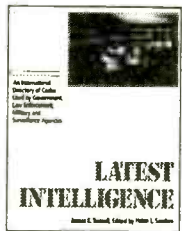
# LATEST INTELLIGENCE

Now, for the first time, the meanings of more than 35,000 terms, phrases, abbreviations, and acronyms used in the international intelligence, law enforcement, military, and aeronautics communities have been compiled into one convenient, well-indexed volume. If you have a scanner or shortwave receiver, LATEST INTELLIGENCE, by James E. Tunnell will unlock a world of listening possibilities!

- Callsign Country Prefix
- Secret Service
- Frequencies Red Cross Network
- US Military Bases / Frequencies
- Cellular Telephone Frequencies
- Goodyear Blimp Frequencies
- TV, Audio, CB Frequencies
- Aircraft / Country Codes
- Police 10 and 12 Codes
- Fire Codes / Frequencies
- Border Patrol Frequencies
- Repeater Frequencies
- Civil Aircraft Markings
- Road Condition Codes
- Mystic Star Frequencies
- Pro Words
- Security Clearance Basics
- Country Codes



**\$16.95**

# Electronics Pocket Handbook

by Daniel L. Metzger

A remarkable collection of definitions, formulas, charts, standards, symbols, codes, and conversions. 263 pp., 3.3" x 5.8" x 0.5".

**\$14.95**



# Upgrading & Repairing PC's

by Scott Mueller, et. al.

A comprehensive guide to PC's, PS2's, and compatibles, 850 pp., 7" x 9"

**\$34.95**



# Vest Pocket Guide to the National Electric Code, 1990 Ed. (current)

by Marvin J. Fischer

A convenient reference guide for all people who use the National Electric Code. 277 pp., 3.3" x 5.8" x 0.6".

**\$14.95**



Description	Quantity	Price Each	Total

Order \$	USA Shipping & Handling
\$0 to \$15.00	..... \$2.00
\$15.01 to \$30.00	..... \$4.25
\$30.01 to \$100	..... \$6.00
Canada orders add \$1 to above S&H	

Sub Total \_\_\_\_\_  
Shipping & Handling (see table at left) \_\_\_\_\_  
Sales tax (CO residents only), add 4.8% of Sub total+S&H \_\_\_\_\_  
All payments must be in U.S. funds. **ORDER TOTAL** \_\_\_\_\_

Name: \_\_\_\_\_ Company: \_\_\_\_\_  
Address: \_\_\_\_\_  
City/State/Zip: \_\_\_\_\_ Phone: (\_\_\_\_) \_\_\_\_\_  
Payment (circle one): Check Money Order Visa MasterCard Discover Prices subject to change without notice.  
Card #: \_\_\_\_\_ Exp. Date: \_\_\_\_\_ Signature: \_\_\_\_\_

**PRIZM Resources, Inc., Dept 969, P.O. Box 557, Morrison, CO 80465**  
**(303) 979-6054 Toll Free Order Line (800) 873-7157**

CIRCLE 265 ON FREE INFORMATION CARD



# MECI

## IBM PC/AT CASE

Genuine IBM Case  
Full Size AT Case  
Accepts Mini or  
Full Size Motherboards  
Slide-off Top  
8 Slot Frame. Made in U.S.A.



**\$49** ea.

Part No. 220-2759F

## AT 200 WATT SUPPLY

Factory Rebuilt  
Fits full size AT case  
only. 120/220V Input.



**\$39** ea.

Part No. 500-0041F

## 3 1/2" 720K FLOPPY DISK DRIVE

Matsushita JU-253  
Includes two 3.5"  
Face Plates (Gray & Beige).  
Comes with separate  
5 1/4" Mounting Kit




**\$49** ea.

Part No. 220-3418F
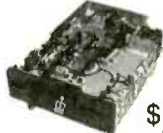
## 5 1/4" 1.2MB FLOPPY DISK DRIVE

Double Sided/  
High Density  
Hitachi HFD516C12U  
Mfg. for IBM #61X4618  
Black Face Plate only!  
Part No. 220-3421F



**\$59** ea.

## MS-DOS VER 3.30.01/GWBASIC

OEM VERSION 3.30.01 Has an  
Expanded Memory Manager for  
above 640K on 80386 computers,  
Print Spooler, Cache, & a file  
Encryption Program.  
Includes 5 1/4" & 3 1/2" disks,  
and Manuals.



**\$19.95** ea.

Part No. 229-3908F

## IBM PC/AT GUIDE TO OPERATIONS

An ideal getting started guide  
for beginners. Complete with  
Exploring The IBM Personal  
Computer Software. Learn the basics:  
keyboard commands, printer functions,  
disk storage, dos, basic programming and  
Funwriter a basic word processing package.  
Includes IBM AT Diagnostics Disk.  
(IBM #6280102) Retail ~~\$80.00~~



**\$9.95** ea.

Part No. 220-0073F

## ROOF MOUNT UHF MOBILE ANTENNA

UHF 445-470MHz  
5dB Gain.  
Complete with 14 ft.  
of cable and PL-259



**\$15.95** ea.

Part No. 110-0027F(3/4" Hole)  
Part No. 110-0028F(3/8" Hole)

## CABLE TIES



Part No.	Size	Color	Price	Price
			per 100	per 1000
320-0193F	4"	Neutral	\$1.80	\$15.00
320-0251F	4"	Black	\$1.80	\$15.00
320-0199F	5.5"	Red	\$1.80	\$15.00
320-0255F	5.5"	Black	\$1.80	\$15.00
320-0254F	6.7"	Yellow	\$2.75	\$25.00
320-0256F	6.7"	Green	\$2.75	\$25.00
320-0287F	7.5"	Neutral	\$2.75	\$25.00
320-0263F	7.5"	Black	\$2.75	\$25.00
320-0288F	8.5"	Neutral	\$2.75	\$25.00
320-0261F	11.5"	Black*	\$4.00	\$35.00
320-0286F	11.5"	Red	\$4.00	\$35.00
320-0258F	14.5"	White	\$4.75	\$40.00

\*w/ Screw Mount

## TEMPEST LETTER QUALITY PRINTER

120/240VAC 49/63HZ  
RS 232C/  
MIL-STD-188  
Serial Interface  
Letter Quality  
Daisy Printwheel  
Mfg. for Inteq by Qume  
FACTORY REFURBISHED  
Model LQP-5100B (AFP-7-T)  
55 CPS Print Speed-Wide Carriage



**\$99** ea.

Part No. 220-3702F

## SUPER 8 REPEATER PROJECTOR

USED Portable Projector.  
Includes a Super 8  
Continuous Play Cassette.  
8mm film can be replaced  
with your own Super 8 films.  
Has fold out 11-3/4" x 8-3/4"  
Glass Screen. Bulb included.  
Includes Padded Hard Sided  
Carry Case 16-1/2" x 14" x 8"



**\$9.95** ea.

Part No. 650-0139F

## SCHOOL BUS ALERT TRANSMITTER

Bus mounted Portable  
Transmitter that announces  
its location to the home unit.  
SIMON TRANSMITTER  
Mfg. TRANS ALERT 2000  
Ideal for students with special needs.



**\$49.95** ea.

Part No. 660-9404F

## SCHOOL BUS ALERT

Home Receiver to alert  
Students as to the location of  
their Bus. Receives Signal  
from Bus equipped with  
SIMON TRANSMITTER(below)  
Mfg. TRANS ALERT 2000, INC.



**\$9.95** ea.

Part No. 660-9403F

## MAGIC FLASH

Electronic flash.  
Just add a switch  
and three volts.  
Requires 4 "AA" batteries.




**\$3.50** ea.

Part No. 660-0025F
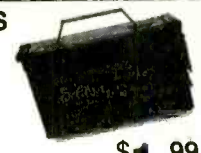
## AMMO BOXES

Great storage boxes.  
Heavy duty metal  
construction.  
Water tight.



**\$1.99** ea.

Available in two sizes:

Part No. 650-0177F	11" L. x 7" H. x 4" D.	30 Cal.
Part No. 650-0178F	12" L. x 7" H. x 6" D.	50 Cal.

## INTRUDER ALARM SYSTEM

Infrared detector plugs into AC wall  
outlet and either turns on a lamp  
(up to 155 watts), or turns on lamp  
and sounds a 90dB alarm. 6 digit  
security code allows any number of  
remotes to work with sensor(s). 45  
second activation delay gives you time to leave the 30'  
detector range of the sensor. Includes one remote control.



**\$14.95** ea.

Part No. 660-0036F

## 4 AMP TOROIDAL TRANSFORMER

Versatile, high efficiency  
transformer. 120VAC primary,  
two 24 volt secondaries, 160 watt.  
Includes mounting hardware.  
Size: 4" Dia. x 1-3/4"



**\$10.95** ea.

Part No. 600-0192F

## 20" ECL MONITOR

Non-working 20" paper  
white monitor has  
resolution of 1280x960  
and includes 80 watt  
switching power supply,  
18KV high voltage supply  
module, and fused power  
input module with voltage  
selector. Unit has  
2PCBs with a great selection of parts such as caps,  
voltage regulator, IC's, transistors, pots, etc. Metal and  
plastic case measures 14 1/2" (H) x 18" (W) x 16" (D).



**\$49** ea.

Part No. 220-2762F

## ERECTOR SET HARDWARE KIT

10-3/4" X 6" X 2-1/4" Plastic Box  
Includes 1500 8/32 Nuts,  
1500 #10 Washers, 400  
8/32 x 3/4" Slotted Screws,  
600 8/32 X 1/2" Slotted Screws,  
& 500 8/32 x 1/4" Slotted Screws.  
FREE SCREWDRIVER with each KIT.



**\$30.00 Value. \$9.95** ea.

Part No. 330-0055F

## ANGLED PROJECTION LENS

7-3/4" X 5-7/8" X 6"  
Right Angled Lens,  
designed for use in  
Rear Projection TV's.  
102mm Focal Length.  
Black Plastic Housing  
w/Glass elements. Lever Focusing.  
Mfg. by U.S. Precision Lens Delta 7T-OC



**\$9.95** ea.

Part No. 640-0007F

Order Line  
**1-800-344-4465**

## Mendelson Electronics Co., Inc.


340 E. First Street Dayton, Ohio 45402  
800/422-3525 • FAX 513/461-3391 • 513/461-3525



STORE HOURS: 8:30-5:00 (Eastern Time) Monday thru Saturday  
IBM PC/XT is a registered trademark of IBM Corp.  
TERMS: MASTERCARD/AMDISCOVER, CHECK, or MONEY ORDER  
(Checks allow two weeks for clearance.)  
Ohio residents add 6.5% State tax.  
Shipping/handling-UPS Chart Rate + \$2.00 (Min. \$4.50) (+\$4.00 if ordering COD)  
Prices subject to change without notice.  
**\$20.00 Minimum Order**  
Returns after 10 days subject to a 20% restocking fee (All returns must have RA#)  
All sales subject to prior sale.  
Call or write for a free catalog.

# "WE HAVE GREAT CONNECTIONS"
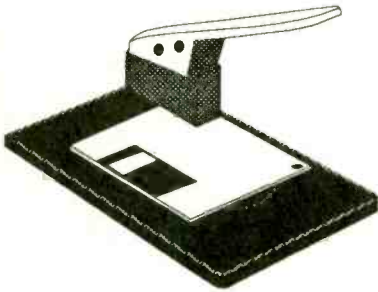
## #TM-319 DOUBLE DISK™ The original patented disk converter.



The original disk converter. 3.5" Double Density Disk to 1.44 MB High Density Disk. Made of heavy gauge steel. For all IBM/clones and Macintosh computers!

\$19.95 each 2 up \$18

## #VA-154 COPYGUARD CORRECTOR

Enjoy videotapes without flashing light and dark!

Macrovision methods often make it impossible to enjoy a clear, stable picture from prerecorded video cassettes. Picture roll, loss of tracking and flashing light & dark are the annoying side effects cured by the Copyguard Corrector. Connects easily between two VCR's, or your VCR and a video monitor, with its single video in and video out jacks. Nine volt battery included.



Reg. \$69.00

\$39 each 2 up \$35 each

Unauthorized duplication of copyrighted videotapes is prohibited by Federal Copyright law!

### "F" to "F" Video Cable

12 foot, male to male with gold connectors! clear PVC, heavy duty, quick connect great quality



#VC-12F-Q  
\$2 each 20 up \$1 each

### 3-Way TV Signal Splitter

highest quality all die cast made for the cable TV industry!




#VA-503  
.75¢ 20 up 50¢ each

Call early! Most orders shipped the same day

Hurry! Some Items Limited to stock on hand

### Data Transfer Switches

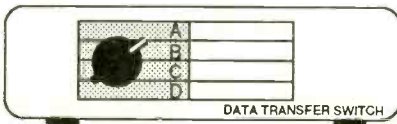

Typical Front View  
All Metal Case

DB25 Serial and Parallel Shielded with gold contacts on all connectors Gold plated contacts on all rotary switches All pins hand wired 3' to 50' DB25 Cables available other configurations available

#DS-252 3 Females Connectors \$10  
#DS-253 4 Females Connectors \$14  
#DS-254 5 Females Connectors \$18  
#DS-255 6 Females Connectors \$30  
#DS-256 7 Females Connectors \$35

### 10 Ft MIDI Cable or keyboard cable

5 pin DIN • male to male  
black • shielded



Keyboard Extension Cable available at same price

#CC-5M1  
\$4 each 20 up \$3 each

### Data Transfer Cables


use with Laplink, Brooklyn Bridge, etc.



#CC-210  
DB25 males For parallel use only 6 ft \$7 each



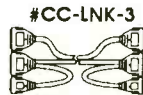
#CC-LNK  
DB25 females and DB9 females For serial use only 6 ft \$10 set



#CC-LNK-3  
DB25 females, DB9 females, DB25 males For serial and parallel use 6 ft \$20 set
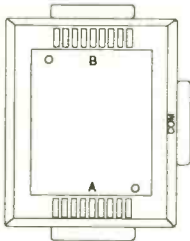
### Automatic Electronic Printer Switch


Use one printer with two computers Specify Serial or Parallel Safe for HP Laser jet No power supply required DB-25 Connectors I/O



#DS-201  
\$25 each
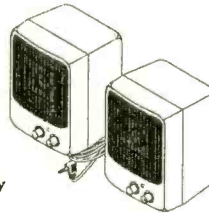
### Amplified Stereo Speaker System


built-in stereo amplifier linear volume control bass booster switch requires: 4 x 1.5v batteries or external 6v power supply styles may vary



#TM-172  
\$24 each 10 up \$22 each

### 486/AT CPU Heat Sink with Fan

clips to chip easy hook-up to power!

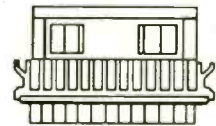

#TM-FAN-2  
\$22 each 10 up \$20 each



TV/VCR Stereo Sound Simulator simulates stereo sound from a mono source better than using a "Y" cable

.50¢ each 10 up .40¢ each

### Coiled Power Extension

6 ft Belden, Great for movable CPU's / Monitors / Printers



#CC-PWXC  
\$2 each 20 up \$1.50 each

### Surge Protector

6 Outlet Power/Modem EMI/RFI protector w/indicator.



#TM-200  
\$12 each

### P/S2 Keyboard Adapter

Mini 6 pin Male to 5 pin Female or reverse



#CA-200  
#CA-201 \$3 each

Credit Cards: Accepted 24 hours a day 7 days a week by FAX.  
Company Check or Money Orders: You must include \$3.50 shipping and your telephone number. California residents add 8.25% sales tax.



## ROGER'S SPECIALIST

27712 Pinehills Avenue, Santa Clarita, CA 91351

Voice 800•366•0579 / 805•251•3085  
FAX 800•366•0579 / 805•251•2520

Terms: Some quantities are limited. All items subject to prior sale. Minimum order \$10 plus shipping. Shipping for all orders is \$3.50 UPS surface (no PO Boxes). Customer specified shipping at carrier rate + a \$5 handling fee. Prepaid orders are shipped after the total amount due is received. If your prepaid order does not include shipping (\$3.50) and sales tax (8.25% CA residents only) your order will not be processed. Upon receipt, if you are not satisfied, you may request a RMA and return the items immediately to us for credit or exchange. We guarantee your satisfaction—sorry, due to the wholesale nature of our business we cannot offer cash refunds. If you have any questions about your order or our products, please call Customer Service at 805•251•3085 M-F, 9 am to 5 pm, Pacific Time.

CIRCLE 267 ON FREE INFORMATION CARD

www.americanradiohistory.com





# Advanced Inverter Technology from Statpower



From inverters that fit into your pocket to our powerful 1500 watt unit, there's a Statpower PROwatt model for all your portable power needs.

Statpower's use of modern high frequency switching power supply technology and the latest power MOSFETs make PROwatt inverters more compact and versatile than other inverters based on older 60 Hz transformers and bipolar transistors. Digital circuitry under quartz crystal control precisely regulates the output voltage and frequency. Unlike square-wave inverters, PROwatt inverters are suitable for most loads including sensitive electronic equipment and inductive loads.

PROwatt inverters are affordable and come loaded with handy features. Whether you're at work or at play, Statpower inverters are made for people on the go.

## PROwatt inverters are ideal for...

- ▶ **Computer and test equipment** - no need for bulky battery packs or 12V based equipment
- ▶ **Power tools, soldering irons, lighting** - use the tools of your trade while doing field service work
- ▶ **Televisions, VCRs, video games** - enjoy the comforts of home while you're on the road
- ▶ **Chargers for camcorders, laptops, and cellular phones** - Operate these products directly, or charge while you drive

Compare these features against the competition...

- ▶ **Small size and light weight**
- ▶ **Precisely regulated output voltage and frequency**
- ▶ **Low no-load current draws and 90% efficiency**
- ▶ **Automatic protection against overloads and overheating**
- ▶ **Automatic low battery alarm and shutdown**
- ▶ **High surge capability for difficult-to-start loads**
- ▶ **Modified sine wave output waveform**

### SPECIFICATIONS

PROwatt	125	250	800	1500
Continuous Power	125W	200W	800W	1500W
10 Minute Rating	150W	300W	1000W	2000W
Dimensions	1.5"x4.5"x4.5"	1.5"x4.5"x6"	3"x9"x10"	3"x9"x15"
Weight	18 oz.	20 oz.	5 lbs.	8 lbs.
Price	\$ 129.	\$ 199.	\$499.	\$849.

List prices are quoted in US Dollars. Actual dealer prices may vary.

To order, call or fax one of these Statpower distributors today!

**Northwest**  
Radar Electric Co. Inc., Seattle, WA  
Tel: (206) 282-2511 Fax: (206) 282-1598

**N. California**  
R&D Electronic Parts, Milpitas, CA  
Tel: (800) 675-1177 Fax: (408) 262-7154

**S. California/Southwest**  
All Electronics Corp., Van Nuys, CA  
Tel: (800) 826-5432 Fax: (818) 781-2653

**South/Texas**  
R&R Electronic Supply Co., Lubbock, TX  
Tel: (800) 299-7000 Fax: (806) 763-6000

**Southeast**  
Electronic Equipment Co. Inc., Miami, FL  
Tel: (800) 327-1526 Fax: (305) 871-3736

**Midwest**  
Laco Electronics Inc., Mt. Vernon, IL  
Tel: (800) 642-4960 Fax: (618) 242-7983

**Northeast**  
Barbey Electronics, Reading, PA  
Tel: (215) 376-7451 Fax: (215) 372-8622

**Midsouth**  
Radio Supply Inc., Oklahoma City, OK  
Tel: (800) 727-7247 Fax: (405) 232-8598

**Canada**  
RP Electronic Components Ltd.,  
Vancouver, BC  
Tel: (604) 738-6722 Fax: (604) 738-3002

Manufactured by

**STATPOWER**  
TECHNOLOGIES CORP.

7725 Lougheed Hwy., Burnaby, BC V5A 4V8 Tel: (604) 420-1585 Fax: (604) 420-1591

CIRCLE 298 ON FREE INFORMATION CARD




# MCM ELECTRONICS

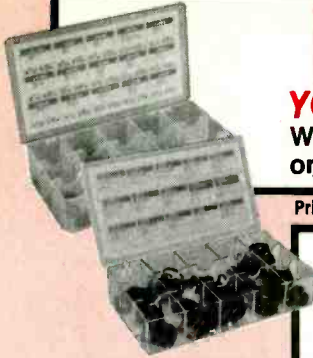**YOUR SOURCE FOR SERVICE AND COMPONENT KITS**

Whether in the shop, truck or home these kits are high-quality and neatly organized so you'll always have the right part at your fingertips.

Prices Effective March 4 thru May 4, 1993.



### Zener Diode Kit

Save 23% off list price when you purchase this kit!

#102-003 ..... \$19<sup>95</sup> (kit)

SAVE OVER \$4

SAVE \$95



### VCR Pinch Roller Kit

Save over 48% off list prices when you purchase this kit! Kit contains the most popular pinch roller replacements used to repair name brand VCRs such as Sony, Sharp, Fisher and more.

#102-016 ..... \$99<sup>95</sup> (kit)

NEW



### VCR Belt Kits

MCM has three brand new VCR Belt Kits to offer you! These kits contain the most popular belts used to repair VCRs. Purchase these kits and you'll not only save valuable repair time, but money too. Call and order today!

Order #	Type	Savings Over List Prices	Price (kit)
102-020	VCR Belt Kits	\$9.00	\$34.90
102-021	Flat	18.00	39.95
102-022	Square	13.00	34.95

SAVE \$10



### IC Protector Kit

Don't risk a sell-out on this IC Protector Kit that is now 55% off list prices! Chock full of original IC protectors found when servicing most VCRs and camcorders. Hurry and stock-up today!

#102-006  
Reg. \$39<sup>95</sup> (kit) Sale \$29<sup>95</sup> (kit)

SAVE OVER \$72

### MCM ProKit Professional VCR Idler Tire Kit

This kit contains 320 of the most frequently replaced idler tires used to service VCRs today! Durable steel kit case and comprehensive cross reference combine to make this a great value.

#102-019 ..... \$119<sup>95</sup> (kit)

To order, or to request a FREE MCM Catalog... Call

**1-800-543-4330**

To Order By Fax... Call

**1-513-434-6959**

For Product Questions... Call

**1-800-824-TECH (8324)**



YOU CAN ALSO SEE THESE AND MANY OTHER SERVICE KITS IN THE LATEST MCM CATALOG #30.



MCM ELECTRONICS  
850 CONGRESS PARK DR.  
CENTERVILLE, OH 45459-4072  
A PREMIER Company

RES-05


CIRCLE 293 ON FREE INFORMATION CARD

### SIMPLEX REPEATER

PR-50 SIMPLEX VOICE REPEATER WILL WORK AS A VEHICULAR REPEATER OR A STAND-ALONE SIMPLEX REPEATER. SIMPLY CONNECT THIS UNIT TO YOUR EXISTING MOBILE RADIO OR BASE UNIT. GREAT FOR HILLTOP OR FIELD APPLICATIONS.

DRAWS ONLY 50mA OF CURRENT.

149.00

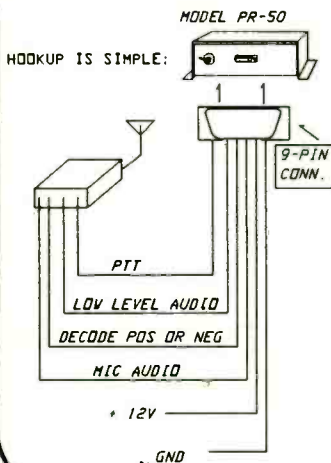

### STUN GUNS

49.00!


STUN GUN EMITS 65KV CHARGE INTO POTENTIAL ATTACKER, A MUST FOR STUDENTS, NIGHT WORKERS, MAIL CARRIERS, SECURITY GUARDS.



### QUAD SYSTEMS


P.O. BOX 690073  
HOUSTON, TEXAS  
ZIP 77269

ASK FOR FREE INFO  
(713-893-0313)

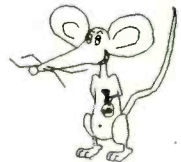

PH • 713-893-0313  
FAX • 713-583-1446

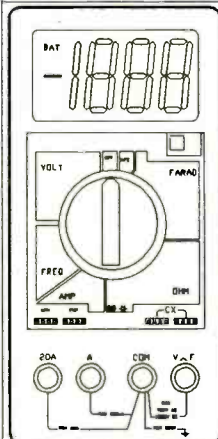HOURS: NOON TO 6:00 MON-FRI 9:00-1:00 SAT.



### DM3050 METER

- MEASURES:
- FREQUENCY
  - CAPACITANCE
  - RESISTANCE
  - AMPS
  - HFE
  - VOLTS
  - CONTINUITY

59.00!

DM-3050 **EVERYTHING METER**  
THIS ONE DOES IT ALL FOR A SUPER LOW PRICE!


### PROTEK P-3502

AFFORD A SCOPE!!!!!!

UNIQUE ONE PCB CONSTRUCTION FOR BOTH V & AMPS. 'M' AMP AND POWER SUPPLY ENABLES TESTING AS A SYSTEM FOR GREATER RELIABILITY AND REDUCED COST WITHOUT SACRIFICING PERFORMANCE OR FEATURES.

- VERT. MODES CH1, CH2, DUAL, ADD, SUB, 5mV TO 20V/DIV. IN 12 STEPS. TIME BASE .2us TO .5ms/DIV. IN 20 STEPS AND X5 MAG.
- INCLUDES 2 PROBES AND 2-YEAR WARR.

339.00!!!!

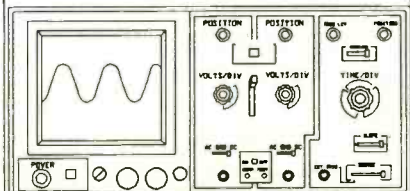


GIANT SOLAR PANEL  
3/4 AMP  
14.4V  
12x36 IN.  
44.00 EA!

March 1993, Electronics Now

CIRCLE 261 ON FREE INFORMATION CARD

# SURPLUS

10,000 12VDC/300MA  
WALL TRANSFORMERS

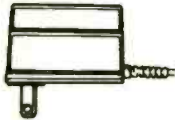

WHITE

\$1.48EA/1000 LOT

CR922

20,000 USED NORTHERN  
TELECOM 2500 PHONES



\$3.90 EA/LOT DEAL

CR930

ATTENTION: DEALERS  
1,000 SNOOPER STOPPERS



PRECISION MADE TO  
CABLE TV CO SPEC C/W  
DETAILED LITERATURE

\$9 EA/100 LOT

CR896

20,000 15' MODULAR  
HANDSET CORDS



24¢ EA FOR THE LOT

CR758


3,000 SIX CONDUCTOR  
TELEPHONE CORDS



38¢ EA/1000

CR122

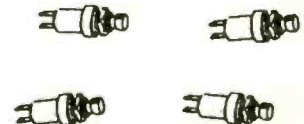3,500 MINI MOMENTARY  
PB RED CAP SWITCHES



25¢ EA/1000

DL012


3,000 24VDC/400MA  
WALL TRANSFORMERS



\$2.38EA/1000 LOT

CR915

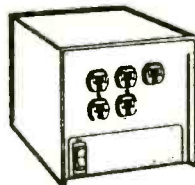1,300 220VAC/110VAC  
STEPDOWN TRANSFORMERS



\$34 EA/500 LOT

CR879

20,000 12VDC/500MA  
WALL TRANSFORMERS



\$1.75 EA/1000

WHITE

CR919

## Have you seen Surplus Dealer NewsFax?

**SDN** The nation's leading Buy/Sell Fax Newsletter for  
the Computer and Electronics Surplus Dealer.

YES.....

I enclose \$3. Please RUSH sample back issues, advertising rates and subscription details.  
**Surplus Dealer NewsFax, PO Box 777, Champlain, NY 12919**

Name \_\_\_\_\_ Company \_\_\_\_\_  
Address \_\_\_\_\_ Fax \_\_\_\_\_


Surplus Traders specializes in the re-distribution of surplus parts and equipment to OEMs, exporters, reps, distributors, surplus dealers and volume users. Additional spec. and small lot prices available on request.

We are major buyers of surplus. Send us your list today.  
Write or fax on your letterhead for free catalogs.

**SURPLUS TRADERS**  
P.O. BOX 276, WINTERS LANE  
ALBURG, VT. 05440  
514-739-9328  
(FAX 514-345-8303)

CIRCLE 271 ON FREE INFORMATION CARD



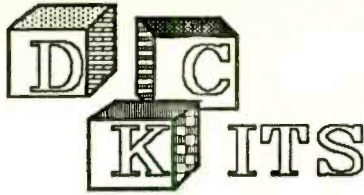


TOLL FREE ORDER  
HOT LINE  
1-800-423-0070

## KIT CORNER
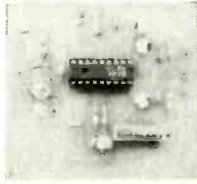
### WIRELESS FM STEREO BROADCASTER KIT


CAT. NO. SFM-II \$19.95

DC'S all new FM Stereo Transmitter Kit is based upon the unique BA1404 Stereo Broadcaster Integrated Circuit that includes all the complex circuitry to generate the stereo signal. The kit includes the new special IC, a 38 KHz crystal, circuit board, and all the small components. This fascinating project will provide many hours of enjoyment as you re-broadcast your CD/VCR/Cassette or stereo broadcasts from your satellite system thru your high-quality FM home or auto stereo system.



### FUNCTION GENERATOR KIT ORDER FG2 KIT

\$19.95

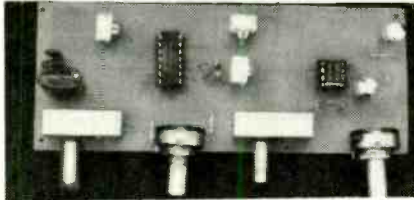

A great project to enhance your bench. This handy little function generator has a built-in buffer amplifier, a 3-decade range selector switch that covers 15 Hz to 25 kHz, output level control and function switch to select sine, square, or triangle.

### ICL7106 EV KIT LCD DIGITAL PANEL METER NOW \$24.95

The ICL7106 EV Kit is based upon a 3-1/2 digit A/D converter that includes all the circuitry to build a digital panel meter. Operates from a 9-v battery. Includes LCD, 7106 IC, circuit board and small parts. Builder must add resistors to expand to multi-meter

### POWER SUPPLY KIT PS-1 \$16.99

Output of this power supply is continuously adjustable from 1.2 to 25V DC. The LM317T voltage regulator provides excellent regulation and ripple rejection. Includes a 1 A transformer, PC board, LM317T, 2 binding posts, and all small parts.

### 70-WATT STEREO POWER AMP 35 WATTS PER CHANNEL

Now you can boost your low power car stereo with the new PM-35 module kit. Each module can provide up to 35 watts per channel while operating from the vehicle's battery into a 4 ohm speaker system. New hi-tech power op-amps are used in a unique circuit to increase voltage swings, thus more power. Additional modules can be used to increase power to 100 or 200 watts/channel.  
ORDER PM-35 KIT \$19.95

### UNIQUE IC's

NE602	\$2.00
UGN3013	.98
ULN2429	1.75
ZN414	2.00
XR2206CP	4.75
XR2212CP	4.75
MAX232	5.40
ULN3330	1.50
ICL8038	3.85
ICM7226BIPL	23.50

## PC BOARD HACKERS CORNER

### MAKE CIRCUIT BOARDS THE NEW, EASY WAY



WITH TEC-200 FILM  
JUST 3 EASY STEPS

1. Copy circuit pattern on TEC-200 film using any plain paper copier.
  2. Iron film onto copper clad board.
  3. Peel off film and etch.
- ORDER TEC-200-10 FOR TEN

### PC BOARD SUPPLIES Copper clad boards for use with TEC-200

22-250	3 x 6	\$1.62
P1-36	3 X 6	2.03
22-260	4 X 6	2.27
22-261	6 X 6	2.88
22-263	6 X 9	4.08

### POSITIVE PRESEN- SITIZED PC BOARDS

22-330	2 X 4	\$3.83
22-332	3 X 4	4.40
22-334	4 X 6	5.78
22-336	6 X 6	7.60
22-338	6 X 9	9.63

## DC'S PARTS WAREHOUSE

### UNIVERSAL DECODER (RE MAY 1990) ICs

CD22402E	7.95	CA3126E	1.95	NE564	2.29
LM733	.99	74C00N	.29	CD4053	.50
LM7805	.50	LM7812	.50	LM7905	.50
18 Uh CHOKE	.39	3.58 MHz	1.00		

ORDER ABOVE ITEMS DIRECT FROM THIS PAGE

### MORE KITS

3 DIGIT LED DVM ONLY 3" X 3" READS 0 TO 100 V DC ORDER DVM3 \$19.95  
FM WIRELESS BROADCASTER FMI \$9.95  
8038 FUNCTION GEN. KIT FGI \$9.50  
SEQUENCER PROJECT SEQKIT \$9.50

### CHRISTMAS TREE PROJECT

Build this unique seasonal project and have an unusual conversation piece. Powered by two D cells, 17 LEDs flash in a seemingly random fashion. Kit includes everything except batteries. ORDER XMASKIT \$16.95

# DC ELECTRONICS

TO ORDER FROM THIS PAGE CALL: 1-800-423-0070  
SEND MAIL ORDERS TO:  
PO BOX 3203 SCOTTSDALE, AZ 85271

**WHOLESALE SPECIALS**  
**LIMITED QUANTITIES**  
**CABLE CONVERTERS**

**Blow Out!!**

**Jerrold 400 Refurbished**

60 Channel Remote w/fine tune

6 Month Warranty New Transmitter

400 MHZ 60 Channel **\$59.95** each

\$55.00 each - 5 lot • \$50.00 each - 10 lot  
 \$45.00 each - 20 lot • \$40.00 each - 50 lot  
 \$37.50 each - 100 lot

**New Zenith SSAVI**  
**Power Supplies Available**

**MTS Stereo Processors for SSAVI**  
**Available - Works with any Cable Converter**

**VIEWSTAR IS HERE**

MXC-2520-525 MHZ remote volume  
 remote volume control  
 Audio/video Baseband **\$119.95 ea.**  
 Output, decoder loop **\$90.00 5 lot**  
 Parental Lockout **\$85.00 10 lot**  
 Favorite channel **\$80.00 20 lot**  
 Remote Fine tuning  
 'Universal' Decoder Compatible

**NEW "NORTH COAST"**

'Excel' 66 channel remote **\$99.95 ea.**  
 Fine tune remote,  
 60 min. Sleep timer **\$80.00 5 lot**  
 Display dimmer  
 Favorite channel **\$75.00 10 lot**  
 Parental Lockout,  
 HRC/STD Remote **\$70.00 20 lot**  
 Selectable Twinline A/B Select Optional  
**AMERICAN MADE** Keep *OUR* People Working

**UNITED ELECTRONIC SUPPLY**

P.O. BOX 1206 • ELGIN, ILLINOIS 60121

**24 Hour Service**

**(708) 697-0600**

**Mon - Fri 8:30 - 5 pm - CST**

CIRCLE 277 ON FREE INFORMATION CARD




# Unbeatable Discount Prices

Plus Free Voltage Detector \$19.95 Value with Any Purchase.

1 YEAR WARRANTY

15 DAY MONEY BACK GUARANTEE

## Four Instruments in One Instrument

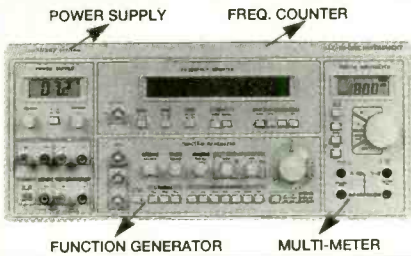

**MT-100**

Reg. \$595.

**\$395.00**

### 1 Function Generator

- Sine, Square, Triangle, Pulse, Scewed Sine, Ramp, TTL
- 0.02 Hz ~ 2MHz

### 3 Power Supply

- 3-1/2 Digit LCD
- Triple output: #1. 0-50V, 0.5A MAX
- #2. 15V, 1A #3. 5V, 2A

### 2 Frequency Counter

- 8 Digit LCD
- 1 Hz ~ 100MHz
- ± (1 Hz + 1 dgt. + Time Base Error)

### 4 Digital Multimeter

- 3-1/2 Digit LCD
- DCV, ACV, Ω, DCA, ACA
- ± (0.5% + 2 dgts)

**FG-150**

Reg. \$395. **\$225.00**

### 2MHz Sweep / Function Generator w/Built-in Frequency Counter



- 4 Digit LCD Display
- 0.2 Hz ~ 2.0 MHz
- Sine, Square, Triangle, Pulse, Scewed Sine, Ramp, TTL
- Linear or Logarithmic Sweep
- Variable DC Offset Control
- 10 MHz Frequency Counter

**FC-190 (100MHz)**

Reg. \$295. **\$149.00**

### High Resolution Frequency Counter


**FC-200 (1.0GHz)**

Reg. \$395. **\$225.00**



- 1.0 Hz ~ 1.0 GHz
- 8 Digit LCD Display
- Auto to Manual Range
- Measured Value Hold
- 4 Selectable Gate Times
- Below 20mV Input Sensitivity
- 1mΩ ~ 50Ω Input Impedance
- 10:1 Input Switchable Attenuator

### GoldStar Oscilloscopes

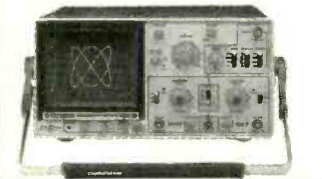

**OS-9020A. 20MHz Dual, Econo**

Reg. \$495. **\$345.00**

**OS-7020A. 20MHz Dual**

Reg. \$595. **\$375.00**

**OS-9020G. 20MHz Dual/Func. G**

Reg. \$695. **\$425.00**

**OS-9040D. 40MHz Dual**

Reg. \$795. **\$545.00**

**DM3000**  
Reg. \$69.

**\$44.00**

### Multi-Function w/Holster

- 3-1/2 Digit
- 1.5" Big LCD
- Heavy Duty, 20A
- Capacitance
- TR-hFE
- Diode
- Low Battery Mark
- Over Range Mark
- Protective Holster
- Tilt Stand

DM3050 Only

- Frequency
- Continuity Beeper

DM3100 Only

- Temperature w/ Optional Probe
- Continuity Beeper

**DM3050**  
Reg. \$99.

**\$54.00**

**DM3100**  
Reg. \$99.

**\$54.00**



**DM3200**  
Reg. \$99.

**\$54.00**

### 3200 Count w/Bargraph

- Auto & Manual
- 3-1/2 Digit
- 32 Seg. Bargraph
- Diode Test
- Continuity Beeper
- Auto Power Off
- Low Battery Mark
- Over Range Mark
- Optional Holster



**DM4100**  
Reg. \$129.

**\$69.00**

### 4000 Count w/Bargraph

- Auto & Manual
- 3-3/4 Digit
- 40 Seg. Bargraph
- Data Hold
- Min / Max
- Frequency Test
- Relative & Memory
- Diode
- Continuity
- Auto Power Off
- Optional Holster



**DM80**  
Reg. \$49.

**\$34.00**

### Credit Card Size w/Bargraph

- 3200 Count
- 32 Seg. Bargraph
- Auto & Manual
- Auto Power Off
- DCV, ACV, Ω
- Data Hold
- Continuity Beeper
- Plastic Case Included



**DM90**  
Reg. \$59.

**\$34.00**

### Pencil Type w/Logic

- 3-1/2 Digit
- Auto & Manual Ranging
- DCV, ACV, ACA, DCA, Ω
- Logic CMOS/TTL
- Data Hold
- Diode
- Continuity Beeper
- Case Included




**DM20T**

### Manual Ranging w/Temperature

Reg. \$49.

**\$29.00**

- 3-1/2 Digit
- 20 Ranges / 6 Functions
- DCV, ACV, DCA, Ω
- Diode
- Auto Polarity
- Temperature w/ Optional Probe

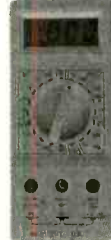

**DM30S**

### Auto Ranging w/Memory Mode

Reg. \$59.

**\$39.00**

- 3-1/2 Digit
- Data Hold
- Memory Mode
- Diode
- Continuity Beeper
- Low Battery Mark
- Case Included



### Oscilloscope Probes Switch Selectable X1 / X10



**HP-9060, 60MHz**

Reg. \$29. **\$15.00**

**HP-9150, 150MHz**

Reg. \$49. **\$22.00**

**HP-9250, 250MHz**

Reg. \$59. **\$29.00**

**DM10S**  
Reg. \$29.

**\$19.00**

### Compact w/Carrying Case

- 3-1/2 Digit
- 17 Ranges / 6 Functions
- DCV, ACV, DCA, Ω
- Diode
- Battery Checker
- Auto Polarity



**AM20I**  
Reg. \$39.

**\$24.00**

### General Purpose Analog Meter

- 20,000 Ω/V
- 21 Ranges / 6 Functions
- 10A DC
- Battery Checker
- Continuity Beeper
- Ohm Adjust



**DA400**

### 400 Amp AC Digital Clamp-On

Reg. \$89.

**\$45.00**

- 3-1/2 Digit LCD
- Auto Ranging
- Data Hold
- Continuity Beeper
- Over Range Mark
- Case Included



**BMC** High Standard Electronics  
13700 Alton Pkwy., Ste. 154-282  
Irvine, CA 92718

Call: **1-800-532-3221**

(714) 586-2310

Fax (714) 586-3399



Call for Free Catalog

CIRCLE 283 ON FREE INFORMATION CARD

March 1993, Electronics Now

Call C.S.T.  
 MONDAY thru FRIDAY  
 8:00 AM - 6:00 PM

11986 RIVERWOOD DRIVE  
 BURNSVILLE, MN  
 55337

# LAKE SYLVAN SALES

Orders: 800-800-4582  
 Service: 612-895-9944  
 FAX: 612-895-9454

SEASONS  
 GREATINGS

BUY NOW!  
 & SAVE!



## CABLE TV BOXES

CONVERTERS, DESCRABLERS & MORE AT WHOLESALE PRICES  
 CALL FOR MONTHLY SPECIALS!

### DESCRAMBLERS

	5	10	20	40+
SUPER 7 (DIGITAL IMPULSE)	\$109.00	\$ 99.00	\$79.00	CALL
TB - 3 OR 2	\$ 65.00	\$ 50.00	\$40.00	CALL
FTB - 3 OR 2	\$ 79.00	\$ 55.00	\$50.00	CALL
SA - 3B	\$ 65.00	\$ 45.00	\$40.00	CALL
SA - 3D-F	\$ 99.00	\$ 94.00	\$89.00	CALL
SB - 3 OR 2	\$ 55.00	\$ 43.00	\$38.00	CALL
SP-200 (SPECIAL PIO)	\$145.00	\$135.00	CALL	CALL
*OAK N-12 (WITH VARI-SYNC)	\$ 54.00	\$ 49.00	\$39.00	\$35.00
*HAMLIN 1200 CH. 3	\$ 65.00	\$ 46.00	\$38.00	\$30.00



\*REFURBISHED AS NEW.

### CONVERTERS


	5	10	20	40+
PANASONIC TZPC 145	\$80.00	\$75.00	\$70.00	CALL
T P550 (550 MHZ WPARENTAL)	\$80.00	\$75.00	\$70.00	CALL
*JERROLD DQN-5	\$80.00	\$70.00	CALL	CALL
*JERROLD DQN-V7 w/volume	\$85.00	\$75.00	CALL	CALL
*JERROLD DRZ-450	\$59.00	\$49.00	\$45.00	CALL
*SYLVANIA TEXSCAN 4040 (CH. 2, 3 OR 4)	\$55.00	\$45.00	\$36.00	CALL



\*REFURBISHED AS NEW. CONVERTERS AVAILABLE IN CHANNEL 2 OR 3.

### COMBINATION UNITS

	5	10	20	40+
*SCIENTIFIC ATLANTA	CALL FOR AVAILABILITY AND PRICING			
*ZENITH MODELS	CALL FOR AVAILABILITY AND PRICING			
JERROLD BASEBAND	\$329.00	\$299.00	CALL	CALL
JERROLD DPV7-212	\$249.00	\$239.00	CALL	CALL
*JERROLD DP5-DPV5	CALL FOR AVAILABILITY AND PRICING			
*JERROLD DRX-3DIC	\$119.00	\$109.00	CALL	CALL
*JERROLD DRZ-3DIC	\$124.00	\$114.00	CALL	CALL
*SYLVANIA TEXSCAN 4040-DIC (CH. 2 OR 3)	\$ 79.00	\$ 74.00	CALL	CALL
*OAK M35B (WITH VARI-SYNC)	\$ 49.00	\$ 44.00	CALL	CALL
*OAK RTC56	\$145.00	\$125.00	CALL	CALL

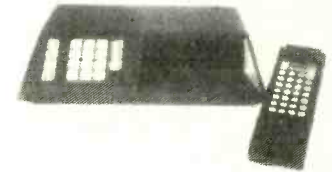

\*REFURBISHED AS NEW.

**OTHER PRODUCTS AVAILABLE:** REMOTES: JERROLD, PANASONIC, HAMLIN, TOCOM, SCIENTIFIC ATLANTA.  
 INTERFERENCE FILTERS: CHANNELS 2 OR 3 / VIDEO TAPE ENHANCERS. AC ADAPTERS: 12 & 18 VOLT / ADULT INSULT  
 BOXES / MORE. FULL SERVICE TECHNICAL SUPPORT.

NO MINNESOTA SALES  
 PRICES SUBJECT TO CHANGE WITHOUT NOTICE!

THEFT OF SERVICE IS A CRIME. INSTALLING ANY DEVICE WITHOUT PERMISSION MAY SUBJECT YOU TO CIVIL OR CRIMINAL PENALTIES. YOU MUST CHECK WITH YOUR LOCAL CABLE COMPANY AND  
 PAY FOR ALL SERVICE YOU USE. IT IS NOT THE INTENT OF LAKE SYLVAN SALES TO DEFAUD ANY TELEVISION OPERATOR AND WE WILL NOT ASSIST ANY COMPANY OR INDIVIDUAL IN DOING THE SAME.

CIRCLE 250 ON FREE INFORMATION CARD



# Don't Despair...REPAIR!

Here's how to troubleshoot and repair your electronics successfully!

## You Can Be Your Own Repair Expert!

For VCRs, camcorders, audio equipment, TV equipment, computer hardware, office equipment, home appliances, automobile electronics, and outdoor equipment.

- Pinpoint and analyze problems quickly.
- Successfully complete repairs with hands-on troubleshooting instructions.
- Become skilled understanding flowcharts and schematic diagrams.
- Confidently use test equipment such as oscilloscopes, frequency counters, and video analyzers.
- Keep your equipment in top condition with effective preventive maintenance techniques.

## Continue to Broaden Your Repair Expertise!

You'll receive quarterly supplements, up to 160 pages, with new step-by-step repair and maintenance instructions, valuable schematics and new repair techniques. Learn how to repair a growing variety of appliances with hands-on repair projects that will keep you up-to-date with later models and technology. You'll be thrilled with your ability to repair a growing list of electronic equipment! Supplements may be returned or cancelled at any time.

## Free Schematic Service!

Build a schematic library at no cost to you. As a paid subscriber you'll receive valuable coupons for your choice of schematic diagrams. No more hassles identifying manufacturers and ordering costly schematics from different sources! Redeem your coupons - through us - any time!

**Order today for your 30-day, no-risk review of The Electronics Repair Manual.**

**For Faster Service Call TOLL-FREE  
1-800-222-WEKA  
Or Fax To: 1-203-622-4187**

### MONEYBACK GUARANTEE

There's no risk in trying the **ELECTRONICS REPAIR MANUAL** to see if it's right for you. If you are not delighted, simply return the manual after the 30-day trial period and receive a prompt refund.



97 Indian Field Rd.  
Greenwich, CT 06830



## One Source For All Your Repair Needs!

Better organized than a magazine, more current than a book.

- 900-page manual
- easy-to-follow, detailed instructions
- trouble analysis flowcharts
- safety precaution checklists
- comprehensive replacement parts list
- directory of manufacturers



**Order your copy today!**

**YES!** Please rush me a copy of the new Electronics Repair Manual for only \$59.95 + \$5.50 shipping and handling. I understand that if I am not satisfied I may return the manual within 30 days for a complete refund. Supplements are sent quarterly for 25¢ per page (never more than \$30) and may be returned or cancelled at any time.

My payment is enclosed  Bill me later  
 Charge my  Visa  MasterCard

Acct. No. \_\_\_\_\_ Exp. Date \_\_\_\_\_

Signature \_\_\_\_\_

Phone ( ) \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

All payments must be in U.S. funds. Canada add \$10. All other countries add \$15. CT residents add 6% sales tax.

Mail to: WEKA Publishing, 97 Indian Field Rd.,  
Greenwich, CT 06830

Signature and phone number are required for all orders.

400030

CIRCLE 300 ON FREE INFORMATION CARD



### Grill Guides

Ball and socket type grill guides for attaching speaker grill to cabinet. To use, simply drill the appropriate size holes in cabinet and grill frame. 12 pair per package.



#RJ-260-367

\$180  
Per Pkg

### Triplet DMM

The Triplet model 2202 digital multimeter is a full function DMM with built-in transistor and battery testers. Large, easy to read LCD display. Rotary switch for easy one hand function selection. The test leads conveniently attach to meter so they are always in reach. Test leads, manual, and carrying case included.




#RJ-390-140

\$47<sup>00</sup>  
Each
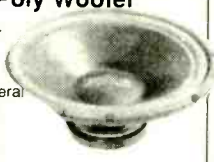
### Pyle 15" Poly Woofer

15" poly woofer with a 60 oz. magnet and 2" voice coil. Mineral filled poly cone with poly foam surround. Poly cone provides proper internal damping to help control cone motion at high power excursion. Power handling: 100 watts RMS, 145 watts max. VAS= 10.9 cu ft., QTS= .53, fs= 30 Hz. Frequency response: 20-3,000 Hz. SPL= 98 dB/1W/1M. Impedance: 4 ohm. Net weight: 9-1/2 lbs.



#RJ-292-070

\$64<sup>80</sup>  
Each

### Pickering Headphones

We made a special outout directly from the manufacturer on these super quality personal headphones. 1" dynamic high velocity element with strontium ferrite magnet. Adjustable headband with foam ear cushions. 5 ft. cord to 3.5 mm and 1/4" adaptor included.



#RJ-249-100

\$24<sup>9</sup>  
Each

### 10", Thruster Car Woofer

Heavy duty car woofer capable of handling 175 watts max (125 RMS). 4 ohm impedance. Polymerized paper cone with red poly foam surround. Resonant frequency: 26 Hz. VAS= 5.89, QMS= 4.6, QES= .27, QTS= .26. Frequency response: 30-2,000 Hz. Magnet weight: 38 oz, 2" voice coil. SPL= 92 dB 1W/1M. Net weight: 6 lbs.



#RJ-293-090

\$29<sup>95</sup>  
Each

### Pyle 10" Poly Woofer

Long throw poly woofer with poly foam surround for superb low bass. Mineral filled poly cone assures low frequency sound that is smooth, tight, and low in distortion. 2" voice coil, power handling: 85 watts RMS, 130 watts max. fs= 43 Hz. Frequency response: 25-3,000 Hz. SPL= 95 dB 1W/1M. Impedance: 4 ohm. 40 oz. magnet. VAS=1.8 cu ft., QTS= .34, QMS= 10.92, QES= .35. Net weight: 8 lbs.



#RJ-292-030

\$45<sup>80</sup>  
Each

### The Loudspeaker Design Cookbook IV

This book describes the "science" of loudspeaker design, however applying it is an "art". Using the information in this book will yield hundreds of possible variations in speaker design, with some subtle and not-so-subtle differences. 1991 copyright, fourth edition. Author: Vance Dickason. 154 pages paperback.

#RJ-500-035

\$29<sup>95</sup>  
Each

### Deluxe In-Wall Speakers

Perfect surround speakers. Customize your media room with these super quality, in-wall speaker pairs. Full size 6-1/2" woofer. Heavy duty 1" soft dome tweeter. Built-in crossover. Fits any standard 2 x 4 or larger wall. Retrofit design allows easy installation in new or existing walls. Response: 50-20,000 Hz. 8 ohm impedance. 40 watts RMS, 60 watts maximum. Includes provision for easy 70V/25V transformer mounting. Overall dimensions: 8-1/2" x 12". Net weight: 9 lbs.



#RJ-300-036

List  
\$299<sup>95</sup>

\$99<sup>95</sup>  
Pair

### Right Angle 1/4" Phone Plug (Mono)



#RJ-099-020

65<sup>c</sup>  
Each

### Honeycomb Tweeter

Unique tweeter with a square diaphragm of honeycomb material. Diaphragm is 1" square. Excellent dispersion. 13/16" voice coil. Frequency response: 2,000-20,000 Hz. Impedance: 8 ohm. Power handling: 25 watts RMS, 40 watts maximum. 4" x 3-1/4". Limited availability. Net weight: 1 lb.



#RJ-279-110

\$8<sup>70</sup>  
Each

### High Voltage Cap Kit



This 85 piece kit contains a selection of 250, 350, and 450 volt electrolytic capacitors. 5 pieces each of 1, 2.2, 3.3, 4.7, 6.8, 10, 22uf and 2 pieces each of 33, and 47uf, 250V radial caps. 5 pieces each of 1, 2.2, 3.3, 4.7, 10uf and 2 pieces each of 22, 33uf, 350V radial caps. 5 pieces each of 1, 2.2, 4.7uf and 2 pieces of 10uf, 450V radial caps. Over \$62.00 wholesale cost if purchased individually. Net weight: 1 lb.

#RJ-020-950

\$49<sup>95</sup>  
Each

### 3" x 5" Speaker

Standard radio and TV speaker. 16 ohm impedance. 3 watts maximum power handling. Limited availability.



#RJ-299-115

\$1<sup>95</sup>  
Each

### Large Input Terminal

Large input cup with push spring terminals and 4 lug terminal strip on rear. Flush mounting housing measures: 4" x 5-1/2" outside diameter. 4-5/8" x 3-1/16" mounting hole required. Limited availability.



#RJ-269-220

95<sup>c</sup>  
Each

### Fluorescent Work Light



Handy light operates on 120VAC or 12VDC. Puts light where you need it. Extra bright 15 watt tube. 15 foot oil resistant power cord with wall adaptor and cigarette lighter plug. Two hooks provided for hanging. Net weight: 2 lbs.

#RJ-360-490

\$18<sup>95</sup>  
Each

### 5-1/4", 2-Way Pioneer

5-1/4" paper cone woofer with a 1" post mounted polymer tweeter. 4 ohm impedance. Response: 100-20,000 Hz. Power handling: 35 watts RMS, 50 watts maximum. 2-3/4" mounting depth. Limited availability. Net weight: 2-1/2 lbs.



#RJ-269-065

\$12<sup>80</sup>  
Each

### Mini Super Tweeter

Super paper cone tweeter with silver mylar dust cap. Impedance: 8 ohm. Power handling capability: 2 watts RMS. 9-1/16" voice coil. 1-1/2" diameter cone with mounting tabs. Mounting holes: 1-7/8" on center. Limited availability.



#RJ-279-120

95<sup>c</sup>  
Each

### Duracell "J" Battery

Popular TV/stereo remote control battery. Size "J", 6 volt alkaline. Duracell #7K67.



#RJ-140-090

\$34<sup>00</sup>  
Each

### 15" Thruster

Super duty, 15" car audio bass driver. Low 25 Hz resonant frequency. Weather resistant polymerized paper cone with red poly foam surround and two color printed dust cap. Power handling capability is 250 watts (170 watts RMS). 2" high temp voice coil with rear vented pole piece. 4 ohm impedance, 50 oz. magnet. Frequency response: 23-2,000 Hz. VAS= 19.04, QMS= 3.96, QES= .21, QTS= .20, SPL= 97.85 dB 1W/1M. Net weight: 11 lbs.




#RJ-293-150

\$59<sup>95</sup>  
Each
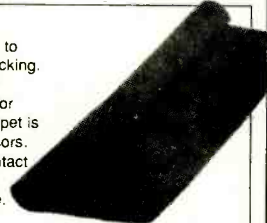
### Cabinet Carpet

This high quality carpet conforms easily to sharp corners because it has no stiff backing. You can also stretch it to cover irregular shapes. This is the covering of choice for car, stages, and amplifier cabinets. Carpet is strong yet easy to cut with knife or scissors. Adhere with spray adhesive or latex contact cements. Provides protection and good looks. Sold by the linear yard. 54" wide.



#RJ-260-765 (Dark Charcoal)

#RJ-260-767 (Medium Grey)

#RJ-260-768 (Jet Black)

\$3<sup>95</sup>

Per Linear Yard 36" x 54"

**PARTS EXPRESS**  
340 EAST FIRST ST.  
DAYTON, OHIO 45402  
LOCAL: 513-222-0173  
FAX: 513-222-4644

• 30 day money back guarantee • \$20.00 minimum order • We accept Mastercard, Visa, Discover, and company C. O. D. orders. • 24 hour shipping • Shipping charge = UPS chart rate + \$1.00 (\$3.50 minimum charge) • Hours 8:30 am - 7:00 pm EST, Monday - Friday • 9:00 am - 5:00 pm Saturday. Mail order customers, please call for shipping estimate on orders exceeding 5 lbs. • Foreign destination customers please send \$5.00 U.S. funds for catalog postage •

CIRCLE 262 ON FREE INFORMATION CARD





### Power Cord

Super duty power cord. 14 ga., 3 conductor. 4 ft. length. Limited availability. Black color.

#RJ-119-010 **\$150** Each

### 12VDC, 800mA Adaptor

Fisher Price battery charger. 120VAC input. 12VDC, 9.6W (800mA) output. 6 ft. cord with special connector. Limited availability.

#RJ-120-361 **\$4.95** Each

### VCR Parts Assortment

Convenient assortment of clips, washers, springs, and screws. 10 pieces each of 4 sizes of "E" clips, 10 pieces of 2 sizes of retaining rings, 10 pieces of 14 sizes of washers, 2 each of 8 sizes of tension and compression springs and 24 assorted screws. Total of 246 pieces.

#RJ-430-315 **\$6.50** Each

### Speaker Sealing Caulk

Special rubber compound quickly and easily seals speakers into cabinets. Eliminates vibration and air leaks. Sold in 1/4" x 36" strips. Strips are self-adhesive so they stick easily to speaker frame. Limited quantity.

#RJ-269-300 **75¢** Each

### Replacement Antenna

Hinged 7 section antenna. 19" extended, 5-1/4" collapsed. 3/16" threaded base. Excellent antenna for portable radios, TVs, and more.

#RJ-210-200 **50¢** Each

### Quality 30 Watt Iron

Economical 30 watt iron with replaceable tip. Blue plastic handle. 120VAC. A quality iron at a reasonable price. Display packaged.

#RJ-370-010 **\$4.95** Each

### Soldering Stand

Convenient weighted soldering iron stand with cleaning sponge. Display boxed.

#RJ-370-020 **\$4.95** Each

### Kester Pocket Pack

Perfect tool box solder supply. The wire feeds conveniently from the handy dispenser tube. Pocket clip attached. .031" diameter solder. .5 ounce (approximately 15 feet).

#RJ-370-050 **\$1.00** Each

### Isotip Butane Soldering Iron

The ideal soldering iron for field repairs where no AC power is present. Operates for up to 100 minutes of continuous soldering per refill. Uses standard butane (not included) available at most stores. Tip temperature is adjustable up to 1067° F. Iron also comes with a torch attachment which easily screws on in place of the soldering tip. As a torch, one refill will provide up to 1 hour of continuous flame. Temperature is adjustable up to 2372° F. A protective cap with a built-in striker is included. Limited one year warranty.



#RJ-370-235 **\$24.95** Each

### Cable Tie Mounts

Package of 10 adhesive back cable tie mounts for securing bundles of wire.



#RJ-080-515 **\$1.20** Pkg

### Monitor Power Jack

Standard computer type monitor jack. Limited quantity.



#RJ-090-446 **85¢** Each

### Spray Handle

Fits most paint and cleaner cans. Limited availability.



#RJ-340-371 **75¢** Each

### Pull-Out Radio Carry Case

Super quality nylon bag for storing pull-out radios. Padded construction with adjustable carry strap. Storage pocket will hold up to 5 CD cases. Inside dimensions: 7-1/2" x 2-1/2" x 8".



#RJ-265-950 **\$10.80** Each

### F-59 Deluxe Connector

Popular connector for cable TV systems. Full attached ferrule for hex crimp. Securely holds RG-59 cable.



#RJ-090-355 **17¢** (50-up)

### Matching Transformer

Adapts 75 ohm coax to 300 ohm twin lead (or vice-versa) at antenna or television. 5-90 MHz UHF/VHF. .3 capacitor, PC board type.



#RJ-180-010 **49¢** Each

### Belt Camcorder Battery Pack

Very high current power pack. Will run most camcorders up to 10 times longer than clip-on batteries. 12V, 6.5AH sealed lead acid type battery. Fuse protected with cigarette lighter output. Comes in padded case with quick release belt and UL approved charger. Net weight: 6 lbs.



#RJ-140-603 **\$48.80** Each

### TNC Male Crimp-On

(For RG-59 and RG-62).



#RJ-090-1000 **\$1.45** Each

### Technician's Turntable



Turntable to speed repair of VCRs, TVs and more. Lets technician easily turn unit for convenient repair. 20" diameter. White color. Net weight: 5 lbs.

#RJ-360-425 **\$19.95** Each

### Outdoor Phone Jack

Heavy duty, diecast aluminum housing withstands the harsh conditions associated with outdoor use. Form gasket under snap shut lid prevents water leakage. Complete with mounting screws. Limited availability.



#RJ-150-030 **\$2.95** Each

### Universal Video Cable

6 ft. RG-59 cable with a push-on "F" connector to a combination 75 and 300 ohm balun (switchable between 75 and 300 ohm).

#RJ-180-126 **\$2.75** Each

### AGC Fuses

San-O brand fuses. Sold in boxes of 100 pieces. Special buyout price. Limited availability and values.

#RJ-070-421 (.5A) **\$3.95**  
#RJ-070-429 (2.5A) **Per 100**

### Mini Headphone Extension


Add 6 feet to your mini headphones. Gives the user added mobility when listening to personal cassette players.



#RJ-240-090 **\$1.65** Each
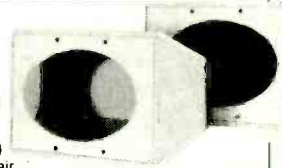
### Unfinished 6" x 9" Cabinets

You can paint or finish to your liking. Deep enough for extra large magnet speakers. Flush mount design for rear deck baffle applications. Dimensions: 11-3/4" x 8-1/2" x 6-3/4" x 5" (tapered back). Sold in pairs. Net weight: 9 lbs. per pair.



#RJ-260-450 **\$12.50** Pair

### 8 Position Dip Switch


Switch type (IE: rocker, slide, toggle) may vary, call.



#RJ-060-134 **60¢** Each
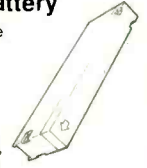
### 12V, 2.3AH Camcorder Battery

Popular battery for use with Canon, Chinon, Curtis Mathes, G.E., Magnavox, Minolta, Olympus, Panasonic, J.C. Penny, Pentax, Philco, Quasar, Sears, Sylvania, Teknika and other miscellaneous manufacturers. Dimensions: 7.17" (L) x .94" (W) x 2.42" (H). Weight: 1-1/2 lb.



#RJ-140-541 **\$41.95** Each

### Velcro Type Fasteners

2, 1" x 2" hook and loop fasteners for attaching almost anything. Great for securing radar detectors to your dash. Each piece has a self adhesive back. Thousands of uses.



#RJ-265-900 **48¢** Pkg

### Pressfit Speaker Terminal

Spring loaded, pushbutton speaker terminal in a round housing. No screws required to fasten; simply drill a hole, apply glue, and press into place.



#RJ-260-295 **95¢** Each

### 3.5 Amp DC Power Supply

A quality, compact 12VDC power supply. Perfect for testing car stereos, CB equipment, radar detectors and other 12VDC items. Regulated 13.8VDC, 3.5 amp continuous, 3 amp surge. LED power indicator. Binding post outputs. Net weight: 4 lbs.



#RJ-120-500 **\$23.80** Each

**PARTS EXPRESS**  
340 EAST FIRST ST.  
DAYTON, OHIO 45402  
LOCAL: 513-222-0173  
FAX: 513-222-4644

**CALL TOLL FREE**  
**1-800-338-0531**

CIRCLE 262 ON FREE INFORMATION CARD



FREE CATALOG

# VACUUM TUBE DEALER PRICE LIST Nov. '92

			SOVTEK®, RUSSIA			USED BY:		
5U4G	\$5.25 each	12 at \$4.75 each	25 at \$4.25 each			Mesa Boogie Dual Rectifier		
12AX7WA/7025	4.35	3.75	3.40			Hartke, Bedrock		
6922 (military 6DJ8)	6.75	5.90	5.20			Counterpoint, Convergent		
EL84/6BQ5	2.90	2.60	2.25			Peavey, Hughes & Kettner		
EL84M/6BQ5WA	5.80	5.20	4.50			Matchless		
6V6GT	4.25	3.50	3.20			SLM		
6L6GC	3.80	3.25	2.95					
5881/6L6WGC	7.25	6.50	5.95			Fender, Soldano, etc.		
811	14.00	12.75	11.50					
813	19.00	16.00	14.50					
			SINO, CHINA					
2A3	\$13.50 each	10 at \$12.50 each	25 at \$11.50 each			100 CALL FOR SPOT QUOTE		
6L6GC	4.50	3.90	3.60			" " " " "		
12AX7a	3.85	3.25	3.10			" " " " "		
12AT7	3.90	3.55	3.40			" " " " "		
12AU7	4.10	3.75	3.60			" " " " "		
6550	10.00	9.50	9.00			" " " " "		
KT88	13.50	12.50	11.50			" " " " "		
			EI, YUGOSLAVIA					
EL34/6CA7	\$5.50 each	10 at \$4.90 each	25 at \$4.50 each			100 CALL FOR SPOT QUOTE		
6DJ8	3.15	2.75	2.35			" " " " "		
12AT7/ECC81	3.50	3.10	2.75			" " " " "		
12AU7/ECC82	3.50	3.10	2.75			" " " " "		
12AX7/ECC83	3.15	2.75	2.35			" " " " "		
			SIEMENS, GERMANY					
EL34	\$7.25 each	10 at \$6.75 each	25 at \$6.20 each			100 CALL FOR SPOT QUOTE		
12AT7/ECC81	4.50	3.90	3.75			" " " " "		
			TESLA, CZECHOSLOVAKIA					
EL34	\$7.25 each	10 at \$6.75 each	25 at \$6.20 each			100 CALL FOR SPOT QUOTE		
EL34BL (COBALT BLUE)	8.25	7.75	7.20			" " " " "		
E83CC/12AX7a	5.90	5.35	4.95			" " " " "		
			GE, USA					
5U4GB	\$12.50 each	10 at \$11.60 each		6550a	\$19.95 each	10 at \$18.25 each		
6CA7/EL34	14.90	13.50		7025	13.50	11.75		
6L6GC	13.90	12.90		7027a	18.90	17.50		
6LF6	19.25	17.50		7868	17.00	16.40		
12BH7a	9.95	8.75		8417	15.85	14.75		
12AT7	7.80	6.30						

## SOLID STATE RECTIFIER

Built into tube socket. Direct plug-in replacement for all 5Y3, 5U4 and 5AR4 types. \$6.25 each 10 at \$5.90

## ODD BALL TUBES (MOSTLY USA STOCK)

5AR4	\$7.95 each	6BA6	\$1.95 each	6J7	\$5.50 each	6X5	\$3.90 each	6C33C-B	\$29.00 each
5V4GT	3.25	6BK11	11.90	6K11	6.90	6X8	3.50	(Power Triode)	
5Y3GT	3.95	6C4	3.50	6SC7	6.90	12AY7	6.50	5749	2.90
6AL5	2.40	6C10	6.90	6SG7	3.50	12AZ7	4.50	(6BA6W industrial)	
6AN8	5.50	6CA4	3.90	6SJ7	2.90	12DW7	11.90	5879	8.50
6AQ5A	4.90	6CG7	6.90	6SK7	2.90	12FQ8	8.00	6189W	4.15
6AQ8	5.85	6EU7	11.80	6SL7	3.95	OA2	3.75	(12AU7W industrial)	
6AS7	3.90	6FH8	12.50	6SN7	2.50	OA3	2.25	6267/EF86	3.20
6AU6	2.25	6GW8	6.90	6U10	4.90	OB2	2.25	6973	14.90
6AX5	4.90	6J5	4.50	6X4	3.90	OC3	3.75	7199	17.80

GIVE US A CALL ON ANY TOUGH-TO-GET TUBES. WE'LL FIND THEM FOR YOU!

**MATCHING AVAILABLE ON ALL OCTAL POWER TUBES 65¢ extra per tube.**

**"PLATINUM" MATCHING ALSO AVAILABLE WITH 24 HOUR**

**TEST AND BURN-IN, ENSURING PREMIUM MATCH. PAIRS OR QUADS \$2.00 extra per tube.**

**MINIMUM ORDER \$50.00**

**ADD \$5.00 SHIPPING VIA SURFACE (\$10.00 OUTSIDE UNITED STATES)**

**SEND CHECK OR MONEY ORDER TO:**

## NEW SENSOR CORPORATION

133 FIFTH AVENUE, NEW YORK, NY 10003

CONTACT: MIKE MATTHEWS TELEPHONE: (212) 529-0466 TOLL FREE: 1-800-633-5477 FAX: (212) 529-0486

CIRCLE 258 ON FREE INFORMATION CARD



# B & S SALES

		<b>5</b>	<b>10</b>
<b>NEW</b>	PANASONIC-145 CONVERTER .....	\$62	\$59
<b>NEW</b>	TVT-3 DIGITAL TRIBI ADD-ON..... For most Jerrold systems	51	48
<b>NEW</b>	SCIENTIFIC ATLANTA 8580-338 .....	CALL	CALL
	Converter/Descrambler		
<b>NEW</b>	SCIENTIFIC ATLANTA 8590 .....	CALL	CALL
<b>REFUR</b>	JERROLD STARCOM 6 (DPV5) .....	CALL	CALL
	Converter/Descrambler		
<b>REFUR</b>	HAMLIN 6600 or 6000-3-M.....	65	55
	MLD1200 Built-In Converter/Descrambler		
	HAMLIN-MLD-1200-2.....	25	20
<b>REFUR</b>	JERROLD DRX-3-DIC.....	89	79
	Built-In SB-3		
<b>NEW</b>	PIONEER Add-on .....	100	95
	For all Pioneer Systems		
<b>NEW</b>	SCIENTIFIC ATLANTA Add-on .....	90	85
	For 8580 Systems		
<b>NEW</b>	JERROLD STAR 7 Add-on.....	90	85

## MISCELLANEOUS

Jumper Cables, Remote Control for most Cable Converters; Interference Filters or any channel.  
90 DAY GUARANTEE — in order for the 90-day guarantee to be in effect, this form must be signed and returned.

### FOR VCR, SECOND, THIRD, ETC. HOOK UPS

YES, I agree — all units are to be used or resold in compliance with Federal and State laws.  
Signature \_\_\_\_\_ Date \_\_\_\_\_

**HOURS: MONDAY THROUGH FRIDAY 8 A.M. TO 8 P.M. EST**  
**NO MICHIGAN SALES**

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_

Zip \_\_\_\_\_ Phone No. \_\_\_\_\_

IT IS NOT THE INTENTION OF B & S SALES TO DEFRAUD ANY PAY TELEVISION OPERATOR AND WE WILL NOT ASSIST ANY COMPANY OR INDIVIDUAL IN DOING THE SAME.

46518 Van Dyke #101, Utica, MI 48317 (313) 566-7248 • FAX (24 hours) (313) 739-6047

# B. G. MICRO

P. O. Box 280298 Dallas, Texas 75228

(214) 271-5546

FAX (214) 271-2462



## SPECIALS

MAX232	2.30
1488	.45
1489	.45
DB25-(Solder Cup) M/F	2/1.00
DB25-Rt. Angle PC BD. F	.55
DB9-Rt. Angle PC BD. M/F	.35

## MONITOR

**BRAND NEW!**  
Factory Fresh  
IBM  
VGA Monochrome Monitor  
12" Paper-White  
640 x 480  
**\$79.95 plus \$9.50 S/H**  
Within the Continental U.S.

## DISPLAY DEVICES

FLAT PANEL LCD  
GRAPHIC DISPLAY  
EPSON EG-7004S-AR



640 x 200 dots - Super twisted nematic type.  
Built in drivers - 4 bit TTL interface - Capable of displaying numerics, graphics, alphabets, special characters, graphs, charts, and patterns.  
Viewing area 10-7/16" x 4-5/8" Overall 11-3/8" x 6-1/16"  
14 pins for signals and power (+5V, -12V).  
Complete 27 page manual  
**\$19.95 6/\$100.00**

### LTP 1157AE

1.2" 5x7 Matrix Displays  
5x7 Array with x,y select.  
This Red Orange Matrix Can Be Stacked Horizontally. Choice of Two Matrix Orientation-Cathode Column, Anode Row. Great For "Moving Message" Signs.  
**\$1.19 Ea., 8/\$6.95, 100/\$75.00**

## 74LS

LS00	.14	LS114	.25	LS241	.60
LS01	.14	LS122	.35	LS242	.65
LS02	.14	LS123	.45	LS243	.50
LS03	.14	LS124	1.35	LS244	.55
LS04	.14	LS125	.30	LS245	.55
LS05	.14	LS126	.35	LS251	.45
LS08	.14	LS132	.35	LS253	.40
LS09	.14	LS133	.25	LS257	.35
LS10	.14	LS136	.28	LS258	.45
LS11	.14	LS138	.35	LS259	1.00
LS12	.20	LS139	.35	LS260	.40
LS13	.25	LS145	.75	LS266	.30
LS14	.30	LS148	.35	LS273	.75
LS15	.20	LS151	.35	LS279	.30
LS20	.14	LS153	.35	LS280	.80
LS21	.16	LS154	.85	LS283	.35
LS22	.16	LS155	.50	LS290	.70
LS26	.14	LS156	.42	LS293	.50
LS27	.20	LS157	.30	LS298	.65
LS28	.15	LS158	.25	LS299	1.00
LS30	.14	LS160	.25	LS322	1.30
LS32	.16	LS161	.35	LS323	2.25
LS33	.25	LS162	.45	LS348	.75
LS37	.24	LS163	.36	LS353	1.00
LS38	.24	LS164	.45	LS357	.80
LS42	.35	LS165	.60	LS363	.75
LS51	.15	LS166	.75	LS364	.75
LS54	.20	LS169	.90	LS365	.30
LS55	.20	LS170	.45	LS366	.28
LS73	.33	LS173	.60	LS367	.35
LS74	.22	LS174	.35	LS368	.30
LS75	.25	LS175	.35	LS373	.50
LS83	.30	LS181	1.25	LS374	.45
LS85	.45	LS191	.45	LS375	.35
LS86	.20	LS192	.65	LS377	.75
LS90	.35	LS193	.65	LS378	.80
LS92	.30	LS194	.40	LS390	.80
LS93	.25	LS195	.52	LS393	.75
LS95	.30	LS196	.55	LS399	1.00
LS96	.33	LS197	.75	LS411	1.20
LS107	.28	LS221	.50	LS645	.75
LS109	.20	LS240	.50	LS646	.75
LS112	.25			LS670	.80
LS113	.25	25LS2569	1.50		

## SUPER BUYS

DTMF	
SSI-202 Decoder	2.25
8870 Decoder	2.25
5087 Generator	2.00
5089 Generator	2.10

## THE \$25 NETWORK

Try The 1st Truly Low Cost LAN

- Connect 2 or 3 PCs, XTs, ATs
- Uses serial ports and 5 wire cable
- Runs at 115 K baud
- Runs in background, totally transparent
- Share any device, any file, any time
- Needs only 14K of ram

*Skeptical? We make believers!*

## LITTLE BIG LAN

- Low cost - \$75 per LAN, not per node!
- Hardware Independent network
- ARCNET, Parallel, and Serial port support on first release
- Serial Speed: 6500(XT)-8500(AT) bytes per second
- Parallel Speed: 9000(XT)-29000(AT) bytes per second
- ARCNET Speed: 40000 plus bytes per second
- Use any PC/XT/AT/386 mix, even laptops and PS/2 machines
- Connect up to 254 computers, can mix connection methods (Serial, Parallel, Arcnet)
- DOS File and Record locking support
- Share any device, any file, any program
- Runs in the background, totally transparent
- Low memory overhead
- Typically only 28K is needed, but will vary with various setups
- Works with most software, including DBASE III, Microsoft WORD, LOTUS 123, Windows 3.1, AUTOCAD, Word Perfect, all compilers, GWBASIC, and, in fact, most anything!
- Works with DOS 2.0 to DOS 5.0 and DR-DOS
- DOS 3.1 or greater is preferred
- Open network, programmer API provided
- Example for low-level link modules - you can support special hardware
- Full specs provided on packet level protocols

CABLES & ARCNET CARDS AVAILABLE - PLEASE CALL **\$75.**

## SOCKETS

Low Profile SOLDER TAIL	
6 Pin	14/1.00
8 Pin	13/1.00
14 Pin	13/1.00
16 Pin	13/1.00
18 Pin	13/1.00
20 Pin	13/1.00
22 Pin	13/1.00
24 Pin	8/1.00
28 Pin	7/1.00
40 Pin	7/1.00

BUY \$10

GET \$1.00 - FREE CHOICE

68 Pin PLCC	.79
84 Pin PLCC	.89

## 6500/6800

6502	2.00	6821	1.00
6520	1.25	6845P	2.20
6522	2.70	6845S	2.20
6530	3.00	6850	1.75
6532	4.25	6852	3.50
6545	2.10	6860	3.95
6551	2.40	68681	3.00
6800	1.40	68A09EP	1.29
6802	2.50	68A40	4.00
6803	3.00	68A54	3.00
6805	2.95	68B09	4.00
6809EP	2.75	68B10	2.00
6809P	2.50	68B45	4.95
6810	1.25	68B54	4.00

## TEXT TO SPEECH BOARD

PC/XT COMPATIBLE. MAKE YOUR COMPUTER TALK!

**PRICE CUT \$69<sup>95</sup>**

ASSEMBLED & TESTED  
ADD \$3.50 SHIPPING & HANDLING



A VERY POWERFUL AND AMAZING SPEECH CARD. USES THE GENERAL INSTRUMENTS SPO256-AL2 SPEECH CHIP AND THE CTS256A-AL2 TEXT TO SPEECH CONVERTER.

THIS BOARD USES ONE SLOT ON THE MOTHERBOARD AND REQUIRES A COM SERIAL PORT. BOARD MAY ALSO BE USED IN A STAND ALONE ENVIRONMENT (EXTERNAL POWER SUPPLY) WITH ALMOST ANY COMPUTER THAT HAS A RS232 SERIAL PORT. TO USE THE BOARD IT IS ONLY NECESSARY TO SEND ENGLISH TEXT TO THE RS232 INPUT ON THE BOARD. THE BOARD INCLUDES A 1500 BYTE TEXT BUFFER AND HANDSHAKE LINE TO ALLOW YOU TO SEND DATA TO THE BOARD; THE SAME AS YOU WOULD SEND DATA TO AN RS232 SERIAL PRINTER. YOU CAN SET UP BATCH FILES THAT WILL MAKE YOUR COMPUTER GREET YOU WITH "GOOD MORNING MASTER," ETC. EVERY TIME YOU TURN IT ON. DEMONSTRATION SOFTWARE AND A LIBRARY BUILDING PROGRAM ARE INCLUDED ON A 5 1/4 INCH PC/XT DISKETTE. FULL DOCUMENTATION AND SCHEMATICS ARE ALSO INCLUDED.

FOR INFORMATION ON A LOW COST SPEECH SYNTHESIZER SYSTEM FOR THE VISUALLY IMPAIRED, PLEASE SEND FOR FREE PACKET T.M.1.

STAND ALONE POWER SUPPLY  
FOR ABOVE  
ADD \$2.50 SHIPPING & HANDLING

**\$19<sup>99</sup>**

## STATIC RAM

2016-2KX8 200 n.s.	1.00
2101-1 - 256X4 500 n.s.	.75
21L02-1 350 n.s.	.65
2102AL-4 L.P. 450 n.s.	.49
2111-1 256X4 500 n.s.	1.00
2112A-2	2.50
2114L-3 1KX4 300 n.s.	.45
2125A-2 1KX1 70 n.s.	1.70
2147 4KX1	1.95
6116P-4	1.00
6117	1.20
6264-15	1.40
62256 32KX8	5.75

## EPROM SPECIAL

We bought a large quantity of 2708s, 2716s, 2532s, 2732s, 2764s, 27128s, 27256s and 27512s from a computer manufacturer who redesigned their boards. We removed them from sockets, erased and verified them, and now we offer the savings to you. Complete satisfaction guaranteed.

Your Choice

2708	1.20	10/8.00
2716	1.75	10/15.00
2532	2.00	10/17.50
2732	2.00	10/17.50
2764	2.00	10/17.50
27128	3.00	10/25.00
27256	3.50	10/30.00
27512	4.75	10/40.00

## DYNAMIC RAM

2108-4 8KX1	1.50
2118-4 16KX1-5volt	.70
4027-4KX1-250 n.s.	.80
4116-16KX1-250 n.s.	.40
4116-16KX1-200 n.s.	.75
4116 16KX1-150 n.s.	.90
4164 150 n.s.	.49 or 9/3.50
4164 120 n.s.	1.10
4164-100 n.s.	1.40
TMS4416-16KX4-150 n.s.	2.75
4464-150 n.s.	1.40
4464-120 n.s.	1.45
4464-100 n.s.	1.45
4464-80 n.s.	1.45
41256 150 n.s.	1.25 or 9/9.95
41256 120 n.s.	1.30 or 9/10.99
41256 100 n.s.	1.30 or 9/10.99
41256-80 n.s.	1.30 or 9/10.99
41256-60 n.s.	1.85
1 Meg - 100 n.s.	4.40
1 Meg - 80 n.s.	4.40
414256-80 n.s. 256 x 4	4.60

## THREE CHIP SET

B.G. SPECIAL

16450, 1488, 1489 - \$6.95  
16550, 1488, 1489 - \$13.50

## 8000/80000

8031	2.95	8251	1.10
80C32 <sup>12</sup>	3.95	8253-5	1.75
8035	1.00	8254	1.80
8039	1.00	8255	1.50
8085	1.55	8255-5	1.75
8086	1.55	8257	1.50
8087	87.50	8259A	1.85
8087-1	167.50	8259C-5	2.10
8087-2	127.50	8275	10.95
8088	2.20	8279	2.25
8088-2	3.25	8284	1.49
8155	2.25	8286	3.50
8156	2.25	8287	2.49
8202A	8.00	8288	3.50
8212	1.25	8530	3.00
8214	2.00	8741	7.00
8216	1.25	8742	7.00
8224	1.25	8748	7.00
8228	1.75	8749	7.00
8237-5	2.80	8755	7.00
8243	1.75	80286-8 PLCC	8.50
8250	2.95	80287-8	125.00
(16450)	6.50	80287-10	135.00
(16550)	13.00	V-20-10MHZ	6.50

TERMS: (Unless specified elsewhere) Add \$3.25 postage, we pay balance. Orders over \$50.00 add 85¢ for insurance. No C.O.D. Texas Res. add 8 1/2% Tax. 90 Day Money Back Guarantee on all items. All items subject to prior sale. Prices subject to change without notice. Foreign order - US funds only. We cannot ship to Mexico or Puerto Rico. Countries other than Canada, add \$9.00 shipping and handling.

7/31/92

CIRCLE 219 ON FREE INFORMATION CARD

SEND FOR FREE CATALOG! OVER 150 NEW ITEMS!

SEND FOR FREE CATALOG! OVER 150 NEW ITEMS!



# AMAZING ELECTRONIC PRODUCTS and KITS

## NEW CONCEPT! Mystery Levitating Device



**Remember War of the Worlds?** Objects float in air and move to the touch. Defies gravity, amazing gift, conversation piece, magic trick or great science project.  
**ANT1K Easy to Assemble Kit / Plans . . . . \$19.50**

## Combination Solid State Tesla Coil & Variable 100,000VDC Generator

Operates 12-19 VDC for Field Use or 115 VAC For Laboratory Use



**Experiments Using Tesla Coil:**

- Plasma in a Jar/Tornado, Furnace
- Kirlian Photography
- Wireless Energy Transmission
- Induction Fields • Pyrotechnic Effects
- Corona and Brush Discharge
- Energizer for Neon Plasma Tubes

**Experiments Using Hi Volts DC:**


- Plasma Blaster Driller/Cutter
- Anti-Gravity/Force Fields
- Ion Reaction Motors
- Lightning Generation
- High Ion Source
- Ozone For Air Purification
- Electrification of People & Objects
- Particle Accelerators/Atom Smashing
- High Energy Capacity Charging

**HVM7 Plans Complete System . . . . . \$15.00**  
**HVM7K Complete System Kit/Plans . . . . \$174.50**  
**TCL4K Tesla Coil Only Kit/Plans . . . . . \$99.50**  
**115/19AC Wall Adapter for 115AC . . . . . \$15.50**
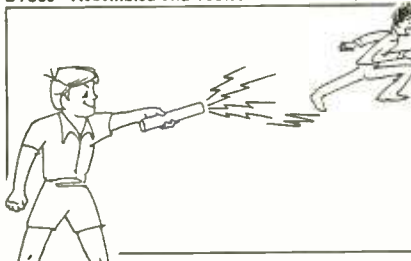
## Table Top Tesla Coil

**Spectacular - A Real Attention Getter!**  
• 250,000 Volts! • 7-10" Sparks!  
Energy even passes through windows. Great for science projects, displays, advertising.

Highly spectacular devices produces visible, audible bolts of lightning appearing to flash in the air. Causes certain materials to burn from within and glow, lights bulbs without wires, produces induction fields, St Elmo's fire corona. Clearly demonstrates high frequency high voltages yet terminal may be touched by user during operation with a metal object. 115VAC operation only.  
**BTC3 Plans .. \$15.00 BTC3K Kit/Plans \$299.50**  
**BTC30 Assembled and Tested . . . . . \$399.50**



## Shocker Force Field / Vehicle Electrifier

Neat little device allows you to make hand and shock balls, shock wands and electrify objects, charge capacitors. Great pay back for those wise guys who have wronged you!  
**SHK1KM Easy To Assemble Electronic Kit . \$24.50**

## High Voltage for the Hobbyist!



Experiment with the forces used in **hover boards, lasers, night vision, mini Tesla coils, plasma globes, magic shows, shock/stun devices, ion ray guns, anti-gravity, pyrotechnics, hypnosis, telekinetics and hundreds more.** Operates from batteries, 9-14 VDC, or 115VAC using adapter.  
**MINIMAX 4 4,000 Volts, 5ma, 4.5x1.5x1" . . . \$19.50**  
**MINIMAX 2 2,000 Volts, 5ma, 3.5x7/8" dia . . \$14.50**



## Ultrasonic Blaster

Laboratory source of acoustical shock waves. Blow holes in metal, produce "cold" steam, atomize liquids. Many cleaning uses for PC boards, jewelry, coins, small parts, etc.  
**ULB1 Plans . . . . \$10.00 ULB1K Kit/Plans \$69.50**

## 100,000V Intimidator / Shock Wand

**Module** Build an electrical device that is affective up to 20 feet. May be enclosed for handheld, portable field or laboratory applications.  
**ITM2KM Easy to Assemble Electronic Kit . . . \$49.50**  
**ITM2 Plans Only; Credit-able to Kit . . . . \$10.00**

**Ion Ray Gun** - Projects charged ions that induce shocks in people & objects without any connection! Great science project as well as a high tech party prank.  
**IOG3 Plans . . . . \$10.00 IOG3K Kit/Plans \$69.50**

## Invisible Pain Field Generator

Shirt pocket size electronic device produces time variant complex shock waves of intense directional acoustic energy capable of warding off aggressive animals, etc.  
**IPG7 Plans . . . . \$8.00 IPG7K Kit / Plans \$49.50**  
**IPG70 Assembled . . . . . \$74.50**



## Homing / Tracking Transmitter

Beeper device, 3 mile range.  
**HOD1 Plans . . . \$10.00 HOD1K Kit/Plans \$49.50**

## Listen Thru Walls, Floors

Highly sensitive stethoscope mike.  
**STETH1 Plans . . . \$8.00 STETH1K Kit/Plans \$44.50**

## 3 Mile FM Wireless

**Mike - Subminiature!** Crystal clear, ultra-sensitive pickup transmits voices and sounds to FM radio. Excellent security system, warns of intrusion. Become your neighborhood disk jockey! Monitor children and invalids.  
**FMV1 Plans . . . . \$7.00 FMV1K Kit/Plans . \$39.50**




## Telephone Transmitter - 3 Miles!

Automatically transmits both sides of a telephone conversation to an FM radio. • Tunable Frequency  
• Undetectable on Phone • Easy to Build & Use  
• Up to 3 Mile Range • Only transmits during phone use  
**VWPM7 Plans . . . \$7.00 VWPM7K Kit/Plans \$39.50**
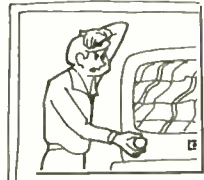
## Plasma Fire Saber



Produces the spectacular effect that captured the fantasy of millions of movie fans. Visible plasma field is controlled by grip pressure and adjusts saber length. Active energy field produces weird & bizarre effects. Excellent for special effects. Specify photon blue, neon red, phasor green, or starfire purple.  
**PFS2 Plans . . . \$8.00 PFS2K Kit/Plans \$49.50**  
**Special Offer PFS20 Assembled reg \$89.50 \$59.50**



**TV & FM Joker / Jammer** - Shirt pocket device allows you to totally control and remotely disrupt TV or radio reception. Great gag to play on family or friends. Discretion required.  
**EJK1KM Easy to Assemble Electronic Kit . \$19.50**

## Visible Beam Laser

High brightness red HeNe laser visible for miles. **Produce your own light show!** Projects a beam or red lite clearly visible in most circumstances. Can be used to intimidate by projection of a red dot on target subject. Also may be used to "listen in" using our laser window bounce method #LLIS1 below. **Easy to Build Modules Makes A Working Visible Laser:**  
**LAS1KM Kit w/1mw Laser Tube, Class II . \$69.50**  
**LAS3KM Kit w/2.5mw Laser Tube, Class IIIa \$99.50**



## "Laser Bounce" Listener System

allows you to hear sounds from an area via a lite beam reflected from a window or other similar object. System uses our ready-to-use LATR1 Laser Terminator gun site as the transmitter. The receiver section is supplied as an easy-to-build kit, including our cushioned HS10 headsets. **Order # LLIST20 System, includes our LATR1 Ready-to-Use Laser Gun Site, LLR1K Special Receiver Kit, and HS10 Headset, all for only \$299.50**

## 5mw Visible Red Pocket Laser

Utilizes our touch power control!  
**VRL3KMX Kit / Plans . . . . \$119.50**

## See In The Dark Viewing

Device uses invisible infrared illumination for seeing in total darkness. Excellent for low cost night vision, along with observing lasers and other IR sources. Functional unit, many useful applications.  
**SD5 Plans . . . \$10.00**  
**SD5K Kit / Tube / Plans . . . . \$299.50**  
**GPV10 Ready to Use Viewer . . . . \$499.50**  
**6032A Tube / Plans to build your own . . . \$99.50**



## INFORMATION UNLIMITED

Dept RES13, Box 716, Amherst, NH 03031  
Phone: 603-673-4730 FAX 603-672-5406  
MC, VISA, COD, Checks Accepted. Please Add \$5.00 Shipping & Handling


**Catalog**  
with many more items  
**FREE** with Order,  
Or Send \$1 P&H



Order by Mail,  
or by 24 Hour  
Orders-Only Phone:  
**800-221-1705**

# EARN MORE MONEY!
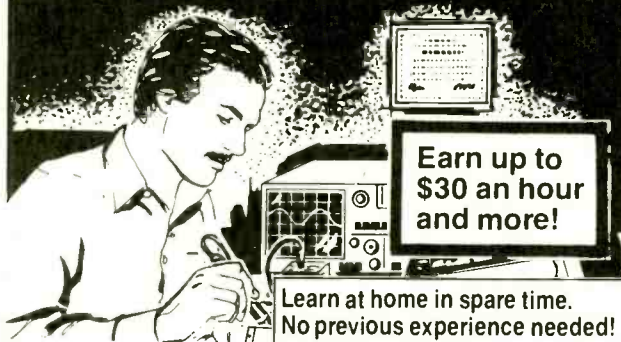
## Be an FCC LICENSED ELECTRONIC TECHNICIAN!



No costly school. No commuting to class. The Original Home-Study course prepares you for the "FCC Commercial Radio-telephone License." This valuable license is your professional "ticket" to thousands of exciting jobs in Communications, Radio-TV, Microwave, Maritime, Radar, Avionics and more...even start your own business! You don't need a college degree to qualify, but you do need an FCC License.

**No Need to Quit Your Job or Go To School**  
This proven course is easy, fast and low cost! **GUARANTEED PASS**—You get your FCC License or money refunded. **Send for FREE facts now. MAIL COUPON TODAY!**

### COMMAND PRODUCTIONS

FCC LICENSE TRAINING, Dept. 210  
P.O. Box 2824, San Francisco, CA 94126  
Please rush FREE details immediately!

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

## TECH-SYSTEMS

### QUALITY USED ELECTRONIC TEST EQUIPMENT


PH: (800)435-1516 FAX: (908)774-1009

#### DUAL TRACE PORTABLE OSCILLOSCOPES


TEK 453.....50MHZ.....\$295.00
TEK 454.....150MHZ.....\$595.00
TEK 465.....100MHZ.....\$695.00
TEK 465B.....100MHZ.....\$895.00
TEK 475.....200MHZ.....\$995.00
TEK 475A.....250MHZ.....\$1,095.00
TEK 2215.....60MHZ.....\$595.00
TEK 2445.....150MHZ.....\$1,995.00
TEK 2465.....300MHZ.....\$2,995.00

#### SPECTRUM ANALYZERS

HP 141T MAINFRAME.....\$995.00
HP 8552A IF SECTION.....\$795.00
HP 8552B.....\$995.00
HP 8553B 0-110MHZ.....\$795.00
HP 8553L.....\$795.00
HP 8554B 0-1200MHZ.....\$1,295.00
HP 8554L.....\$1,095.00
HP 8555A 0-18GHZ.....\$1,795.00
HP 8556A 20-300KHZ.....\$895.00

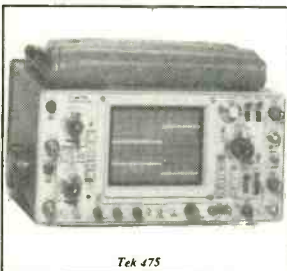

Tek 475

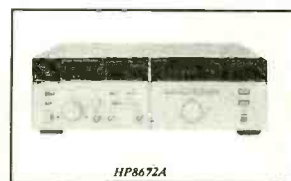

HP8672A

#### SIGNAL GENERATORS

HP 600 SERIES.....\$295.00
HP 8690 SERIES.....from \$395.00
HP 8640B 512MHZ.....\$2,495.00
HP 8601A 100KHZ-110MHZ.....\$895.00
HP 8672A 2.0-18.0GHZ.....\$9,950.00
HP 8671A 2.0-18.0GHZ.....\$5,350.00

#### LAB SCOPES

TEK 7704A.....200MHZ (includes 2 each 7A26, 7B85 delayed time base, & 7B80.....\$1,495.00
TEK 7603.....200MHZ(includes 2 ea. 7A18 & 7B53A.....\$850.00
7A18 dual trace vert. amp.....\$195.00
7A19 vertical amplifier.....\$395.00
7A22 differential amplifier.....\$495.00
7A26 dual trace amplifier.....\$295.00
7B53A delayed sweep time base.....\$295.00
7B80 delayed time base.....\$300.00
7B92A dual time base.....\$450.00


#### ASSORTED

##### Power Meters

(includes cable & sensor)
HP 432.....\$395.00
HP 435A.....\$995.00
HP 436A.....\$1,595.00
HP 400EL AC voltmeter.....\$195.00
HP 400FL AC voltmeter.....\$195.00
HP 3400A analog meter.....\$295.00
HP 1645A data error analyzer.....\$295.00
HP 3551A transmission test set.....\$1,595.00
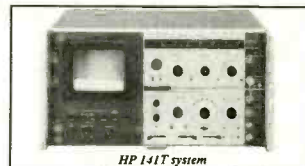
#### Transmission Impairment Test Sets

HP 4935A.....\$1,900.00
HP 4940A.....\$750.00
Navtel 9651.....\$550.00
HP 4944A.....\$650.00
Halcyon 520B/500B univ.test system.....\$550.00
HP 4955A protocol analyzer.....\$950.00
TEK 834 protocol analyzer.....\$350.00



HP 141T system


HP 8620C sweep generator.....\$595.00

#### plug-ins

HP 86222B 0.01-2.4 GHZ.....\$2,595.00
HP 86290A 2.0-18GHZ.....\$2,195.00
HP 86290B.....\$2,595.00
HP 86245A 5.9-12.4 GHZ.....\$1,495.00

#### Tektronix Spectrum Analyzer Plug-ins

Tek 7L5 20Hz-5.0 MHz.....\$3,495.00
Tek 7L12 1.0kHz-1.0GHZ.....\$3,695.00
Tek 7L13 100 kHz-1.8 GHZ.....\$3,695.00
Tek 7L18 1.5-60 GHZ.....\$4,195.00

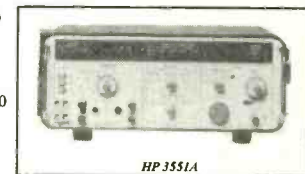

HP 3551A


### WE BUY SURPLUS EQUIPMENT!!

fax us a list of your excess inventory

**30 DAY GUARANTEE!!!!**

1 FIELD ST. AVON, NJ 07717



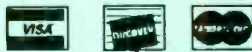

**ORDER TOLL FREE**  
**1-800-669-4406**  
 Tel. (818) 912-9469  
 FAX ORDERS: (818) 912-9598





## ID SIREN AND KEYPAD

The IDS-10 is unique programmable numeric siren that can be used for security or identification applications. When triggered the IDS-10 will first sound a seven second warble tone siren, followed by your programmed number, then back to the warble tone siren, in a continuous loop until trigger power is removed. Numerical data is backed-up internally, if loss of power occurs, for approximately 7 days.

Great for auto alarms, car or boat identifier, verbal entry / exit identifier, etc.

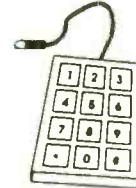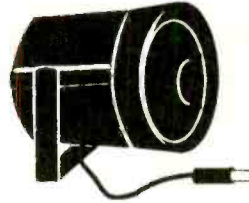Operates on 12VDC at 1A, standby current 10 micro amps.



CATALOG NO.	ITEM	PRICE
11-1155	IDS-10	\$24.99
11-1159	Programming Pad	\$9.95

## RECESSION FIGHTERS

### X-10 Lamp Module



List ~~\$14.95~~ Now! **\$9.90**  
 #11-9465

### X-10 SS5400 4pc.

Home Security Alarm Starter Kit



List ~~\$109.96~~ Now! **\$79.95**  
 #11-5400

### Medusa Infrared




Only **\$29.95**  
 #11-3300

## UNIQUE PRODUCTS


### DVM-58C w/ 1Meg Dram

The DVM-58C with its variable length message capabilities can store up to 16 individual messages for immediate playback to enhance most any electronic application or project. Use it to add real voice prompting or instructions at an affordable price.

**\$89.95**

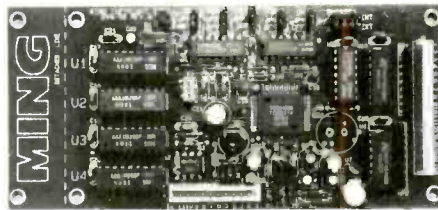

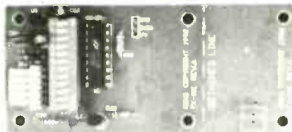The TX-01E transmitter motherboard is the base in building a high quality RF transmitter/receiver pair to fit your requirements. On-board DIP switches allow for easy coding. Combine the TX-01E with the TX-66 daughterboard, which utilizes SAW technology, for improved non-drift transmission.



TX-01E  
**\$9.95**  
 #10-001E



TX-66  
**\$10.95**  
 #10-0066E



### UPON REQUEST

### '92 FALL / WINTER CATALOG

- Board-Level Items.
  - Digital Voice Modules
  - RF Transmitters / Receivers
- Security
  - Auto Alarms & Accessories
  - X-10 Home Security Accessories
  - Infrarads
- Tools
  - Soldering Irons
  - EPROM Erasers
  - Flyke DMM
  - IC Testers
  - Ultrasonic Measuring Device
- Syntax Prototyping PCB's
  - Full line of Syntax PCB's
- Batteries
  - Alkaline
  - Ni-Cad
  - Sealed Lead Acid
  - Button Cell
- IC's
  - DRAM memory
  - Holtek Encoder / Decoder IC's
- Radio Communications
  - Motorola Spirit Radios

E1208F1

### MAIL ORDERS:

**ELECTRONICS 123**  
 17921 Rowland Street  
 City of Industry, CA 91748

**TECHNICAL SUPPORT**  
**(818) 912-9864**

ALL PRICES SUBJECT TO  
 CHANGE WITHOUT NOTICE

VISA, M/C & DISCOVER CREDIT CARDS ACCEPTED

**FREIGHT CHARGES ADD:**  
 (Up to 3 lbs. within the Continental US)  
 UPS - Ground \$ 5.00  
 Second day (blue) \$ 8.00  
 Next Day (red) \$15.00  
 C.O.D. ADD: \$ 4.00  
 CALIF. RESIDENTS ADD: 8.25% Sales Tax

### CANADIAN ORDERS:

All orders must be **PREPAID** by check or credit card (VISA, MC).  
 Add a flat rate of US\$15.00 for shipping and handling by U.S. POST OFFICE (air).

**“Electronics Workbench is pretty amazing.”**

*- Jerry Pournelle, Ph.D., InfoWorld*

**“...you can do 10 times as many experiments with Electronics Workbench than you'd get done with the real stuff.”**

*- Jerry Pournelle, Ph.D., Byte Magazine*

**“...Electronics Workbench is a marvellous learning and teaching tool for the study of electronics.”**

*- Art Salsberg, Editor-in-Chief, ComputerCraft Magazine (formerly Modern Electronics)*

**“Building a circuit is simple and intuitive.”**

*- Jeff Holtzman, Computer Editor, Radio-Electronics Magazine*

**“Electronics Workbench is the most innovative and useful software for the teaching of electronics technology that I have ever seen.”**

*- J.W. Roberts, West Georgia Technical Institute, La Grange, Georgia*

**“It's dynamite!”**

*- Ian Turner, Manager, Manufacturing Training Center, IBM Canada*



# Electronics Workbench<sup>®</sup>


*The electronics lab in a computer*<sup>™</sup>

Building and testing circuits is fast and easy with *Electronics Workbench*. Just click-and-drag with a mouse to add parts, run wires, and adjust instruments. The traces on the simulated instruments are the same as you'd get on real equipment.

*Electronics Workbench* really is an electronics lab in a computer. It's ideal for learning about electronics, experimenting, and prototyping circuits.

Includes two independent modules:

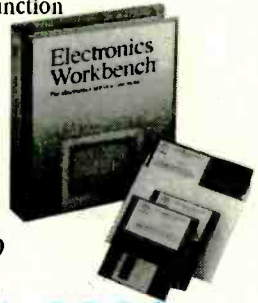- **Analog Module** with passive and active components including transistors, diodes, and op-amps; a function generator, an oscilloscope, a multimeter and a Bode plotter.
- **Digital Module** with gates, flip-flops, adders, a word generator, a multimeter, a logic analyzer and a unique logic simplifier.



DOS Professional Version - \$299  
DOS Personal Plus Version - \$199  
Macintosh Version - \$199

**Tel: (416) 361-0333**

Fax (416) 368-5799

Interactive Image Technologies Ltd.


908 Niagara Falls Boulevard,  
North Tonawanda,  
NY 14120-2060

700 King Street West, Suite 815,  
Toronto, Ontario,  
Canada M5V 2Y6

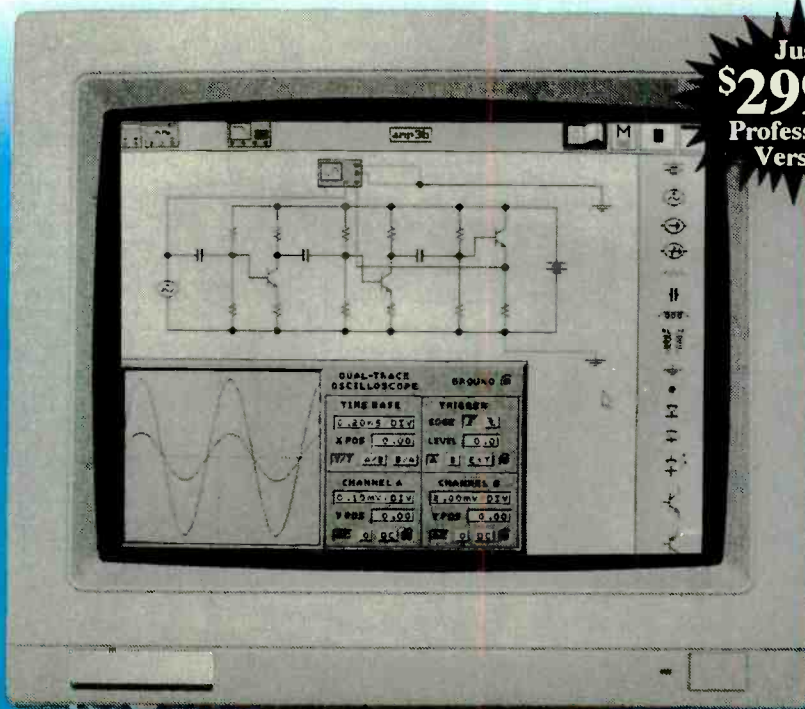**FREE DEMO**

Call or fax for your copy

*Electronics Workbench* Professional Version runs on any IBM AT or PS/2 or true compatible with 640 KB RAM; Microsoft-compatible mouse; EGA/VGA graphics; hard disk; MS-DOS 3.0 or later. Personal Plus Version (monochrome only) runs on any IBM PC/XT/AT, PS/2 or true compatible, two floppy drives or a hard disk, 512 KB RAM, Microsoft compatible mouse; CGA/EGA/VGA/Hercules graphics adapter and DOS 3.0 or later. Macintosh Version (monochrome only) runs on Macintosh Plus or greater. All trademarks are the property of their respective owners. Prices are in US dollars. Shipping \$15. Offer valid in the USA and Canada only.



# TRIPLE FIXED VOLTAGE POWER SUPPLY.



Bench Model  
TPWR-15  
PRICE \$57.95



Open Frame Model  
TPWR-15A  
PRICE \$44.87

## REGULATED LINEAR POWER SUPPLIES

each in single quantities + shipping and handling. Add tax where applicable.


### SPECIFICATIONS:

5 Volts AT 1 Ampere  
+ 15 Volts AT 1/4 Amperes  
- 15 Volts AT 1/4 Amperes  
All voltages are  $\pm 5\%$   
Short circuit protected to ground and to each output.  
TPWR-15 measures 3 x 5 x 6 Inches.  
TPWR-15A measures 2 x 3.5 x 5 Inches  
Other voltages such as 5V  $\pm 12V$  also available. Call factory.

TO ORDER CALL  
(206) 522-1733 OR FAX (206) 522-3359.  
We accept checks, VISA, MasterCard.

**ESF INDUSTRIES**  
P.O. BOX 15702 SEATTLE, WA 98115-0702

# BAREBONZ BK PRECISION BARGAINS

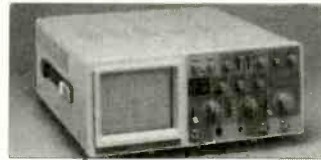

B&K 2120  
20MHz Scope  
Dual Trace

Reg. \$549

**BAREBONZ SALE \$385**

MODEL	DESCRIPTION	REGULAR	BAREBONZ SALE
1541B	40 MHz D.T. Scope	\$ 845	<b>\$ 650</b>
2160	60 MHz D.T. Scope	1099	<b>850</b>
2190	100 MHz 3 Trace Scope	1645	<b>1250</b>
2522A	20 MHz Storage	1099	<b>850</b>
3011B	2 MHz Function Generator	269	<b>210</b>
2005A	RF Generator	265	<b>210</b>
820	.1PF to 1F Cap Meter	259	<b>200</b>
510	Transistor Tester	225	<b>175</b>
1651	Tri-Output Power Supply	429	<b>330</b>
1630	30V 3A Power Supply	315	<b>245</b>
1686	14V 12A Power Supply	199	<b>155</b>
1653	150VAC 2A Power Supply	279	<b>215</b>

### ORDER TODAY!

We'll beat ANY dealer's advertised price on new B&K, Fluke, Leader, or Tektronix Equipment we stock.



## BAREBONZ DISCOUNT

8103 Elizabeth St. · Niles, IL 60714 · 1-800-392-8415  
FAX: 1-800-446-8366

# ACCORD ELECTRONIC SYSTEMS

Orders Only: 800-998-2242 Information: (305) 772-2242

1001 NW 62nd Street, Suite 306-D  
Fort Lauderdale, FL 33309

Free Catalog: included with your first order, or requests by mail only. Pre-Paid/COD orders only.

### HEAT SINK

For TO-220  
BLACK  
**40¢ ea**  
5 pcs min

### RESISTORS

50pcs for \$3.00  
1/4W 5% only. All standard values in stock.  
No mixing values.

### PUSH-BUTTON MINI - N.O.

30¢ ea / 10pcs  
25¢ ea / 100+  
1/4" panel hole

### TANTALUM CAPS

**15¢** each  
20pcs min  
no mixing  
**1uF/35V 2.2uF/35V**

### MINI TOGGLE

5pcs 100+  
SPDT.....85¢.....70¢  
on-on DPDT.....95¢.....80¢

### TRANSISTORS

PN2222A ..... 6¢  
PN2907A ..... 6¢  
2N3904 ..... 6¢  
2N3906 ..... 6¢  
2N4401 ..... 6¢  
2N4403 ..... 6¢  
MPSA05 ..... 8¢  
MPSA10 ..... 8¢  
MPSA13 ..... 9¢  
MPSA63 ..... 15¢  
MPSH10 ..... 9¢  
78L05 ..... 35¢  
78L08 ..... 35¢

50 pcs min  
No mixing  
2N2222A ..... 20¢  
20 pcs min  
No mixing

### REGULATORS

7805 ..... 35¢  
7812 ..... 35¢  
7818 ..... 35¢  
7824 ..... 35¢  
7905 ..... 45¢  
7912 ..... 45¢  
LM317T ..... 45¢  
5 pcs min per item

### DIODES

1N914B ..... 2¢  
1N4148 ..... 2¢  
1N4001 ..... (1A/100V) ..... 3¢  
1N4004 ..... (1A/400V) ..... 4¢  
1N4007 ..... (1A/1KV) ..... 5¢  
50pcs min per item

1N5401 ..... (3A/100V) ..... 10¢  
1N5408 ..... (3A/1KV) ..... 12¢  
6A10 ..... (6A/100V) ..... 19¢  
6A100 ..... (6A/1KV) ..... 21¢  
10 pcs min per item

### GERMANIUM DIODES

1N34 ..... 10¢  
1N60 ..... 10¢  
1N270 ..... 20¢  
10 pcs min per item

### ELECTROLYTICS

1uF/50V ..... 5¢    22uF/35V ..... 7¢  
2.2/25 ..... 5¢    47/25 ..... 7¢  
2.2/50 ..... 6¢    100/10 ..... 7¢  
3.3/50 ..... 6¢    100/25 ..... 9¢  
4.7/25 ..... 6¢    220/25 ..... 11¢  
6.8/50 ..... 6¢    470/25 ..... 11¢  
10/25 ..... 7¢    1000/25 ..... 20¢  
20 pcs min per item

### 7 SEG DISPLAY

.56" High - RED  
Black Face  
Common Anode  
Fits on 24pin Socket  
**60¢ ea / 5pcs**  
**50¢ ea / 50+**

### 9V BATTERY SNAP

20¢ ea / 5pcs  
15¢ ea / 20+

### SOLDER ROLL

SN60/40 .031DIA  
**\$7.50 ea**  
1 Lb roll

### 1N47XX 1Watt ZENER

1N4728A to 1N4764A  
**10¢ ea**  
20 pcs min

### CERAMIC DISC

20pF/50V ..... 5¢  
27pF/50V ..... 5¢  
33pF/50V ..... 5¢  
68pF/50V ..... 5¢  
100pF/50V ..... 5¢  
1000pF/50V ..... 5¢  
20 pcs min per item

### CABLE TIES

4" ..... \$2.00  
8" ..... \$4.00  
Holder ... 9¢ ea  
Bags with 100 pcs ea.

### 3mm or 5mm Diffused LEDs

RED ..... 7¢  
GREEN ..... 8¢  
YELLOW ..... 9¢  
20 pcs min per item

### 5mm RED BLINKER

\$0.60ea/5pcs \$0.50/50pcs

### I.C.'S

MC1488 ..... 30¢  
MC1489 ..... 30¢  
4001B ..... 20¢  
4011B ..... 25¢  
4013B ..... 25¢  
4017B ..... 25¢  
4028B ..... 25¢  
4049B ..... 25¢  
4050B ..... 25¢  
4066B ..... 25¢  
4069B ..... 25¢  
LM311 ..... 25¢  
LM324 ..... 25¢  
LM339 ..... 25¢  
LM358 ..... 25¢  
LM386 ..... 25¢  
NE555 ..... 25¢  
NE556 ..... 35¢  
LM741 ..... 30¢  
74LS244 ..... 25¢  
74LS245 ..... 25¢  
74LS273 ..... 25¢  
74LS373 ..... 25¢





**B<sup>2</sup> LOGIC V 3.0 COMING SOON!!!**  
**ANALOG & DIGITAL**  
**Circuit Design & Simulation**

**B<sup>2</sup> Spice<sup>®</sup>**

*for Microsoft<sup>™</sup> Windows and the Macintosh<sup>™</sup>*

**B<sup>2</sup> Logic<sup>®</sup>**

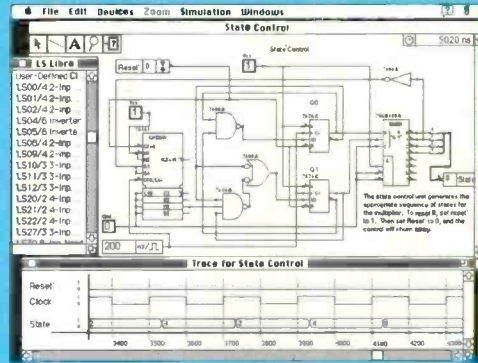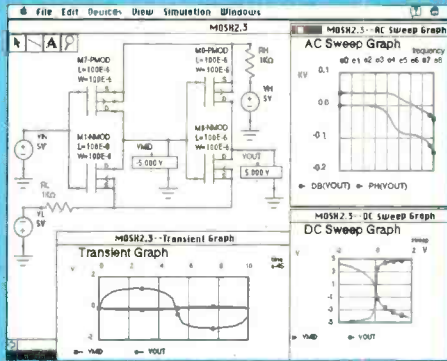

**TRANSIENT, DC & AC ANALYSES**

**OVER 100 COMPONENTS**

"Using B<sup>2</sup> Logic... my students have been able to learn more, and go much further than ever before."

-Professor F.S. Hill, Jr. University of Massachusetts, Amherst

**• INTEGRATED SCHEMATIC CAPTURE & SIMULATION •**

Now in use at over 45 major universities and leading corporations around the world.  
 (University of Michigan, Stanford, University of Illinois, NASA, Bell Labs... to name a few)

- Each program sold separately for \$149.00
- University & Student Pricing Available
- Dealer Inquiries Welcome
- VISA/Mastercard Accepted

**Beige Bag Software**

715 Barclay Ct. • Ann Arbor, MI • 48105  
 Ph: (313) 663-4309 • Fax: (313) 663-0725

CIRCLE 306 ON FREE INFORMATION CARD

# XANDI Electronics



The use of surface mount technology makes this the smallest FM transmitter you can buy! This is not a toy, it out performs most units on the market today. Our E-Z-kit has all the surface mount parts pre-assembled to the circuit board.  
**XST500(E-Z) E-Z Kit ..... \$39.95**



The Use of surface mount technology makes this the smallest telephone transmitter you can buy. Powered by the phone line, it can transmit a phone conversation upto 1/4 mile. Our E-Z-kit has all the surface mount parts pre-assembled to the circuit board.  
**XSP250(E-Z) E-Z Kit ..... \$29.95**



The XTR100 Tracking Transmitter transmits a continuously beeping tone that can be received by any FM receiver. Can be used for games, contests, or as an anti-theft device.  
**XTR100(C) Kit ..... \$39.95**



The XFM100 FM transmitter has a range of upto 1 mile. It works with any standard FM receiver. It contains a built in high gain two stage audio amplifier for maximum sensitivity.  
**XFM100(C) Kit ..... \$35.95**



The XTT100 is a battery powered phone transmitter with a range of upto one mile. It only transmits when the phone is being used in order to conserve battery life.  
**XTT100(C) Kit ..... \$35.95**



The XBD200 quickly locates hidden transmitters from 1 to 2000 MHz by emitting an audio output proportional to the transmit level.  
**XBD200(C) Kit ..... \$44.95**



Use the XPS100 to call your home from any other phone and listen in using the built in microphone and amplifier.  
**XPS100(C) Kit ..... \$45.95**



The XPB1 is a telephone transmitter capable of transmitting to any FM receiver up to a 1/4 mile away. Powered by the telephone line it requires no batteries.  
**XPB1(C) Kit ..... \$29.95**



**WE ACCEPT VISA, MC, CK, MO**  
**COD PLEASE ADD \$6.00**  
**CALL 1-602-829-8152 OR**  
**WRITE FOR A CATALOG**

**TOLL FREE**  
**PHONE ORDERS**  
**1-800-336-7389**

**MAIL ORDERS TO:**  
**XANDI ELECTRONICS**  
**BOX 25647**  
**TEMPE, AZ 85285-5647**




CIRCLE 281 ON FREE INFORMATION CARD

March 1993, Electronics Now

**EASY TO FABRICATE**  
DESIGNED FOR SMALL LOT  
PRODUCTION
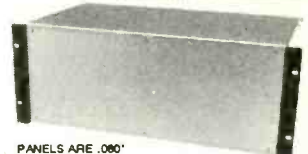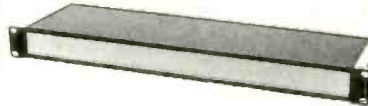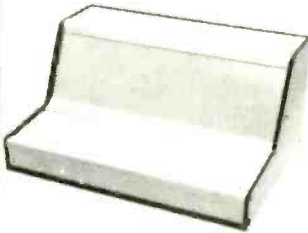
# SHEET METAL BOXES FOR CONSTRUCTION

**ALL ITEMS STOCKED**  
FOR QUICK DELIVERY  
SHEET METAL BOXES SHIPPED FLAT



PANELS ARE .063" ALUMINUM

### RACK CHASSIS

MODEL	DESCRIPTION W x D x H (inches)	PRICE \$
1RU5	19 x 5 x 1.75	30.85
1RU7	19 x 7 x 1.75	33.10
1RU10	19 x 10 x 1.75	35.25
2RU5	19 x 5 x 3.5	33.10
2RU7	19 x 7 x 3.5	35.25
2RU10	19 x 10 x 3.5	37.50
3RU5	19 x 5 x 5.25	41.90
3RU7	19 x 7 x 5.25	44.10
3RU10	19 x 10 x 5.25	46.30

PANELS ARE .063" ALUMINUM

### METAL CABINETS

MODEL	DESCRIPTION W x D x H (inches)	PRICE \$
MC-1A	4 x 3 x 2	16.50
MC-2A	6 x 3 x 2	18.75
MC-3A	8 x 3 x 2	20.95
MC-4A	4 x 4 x 3	18.75
MC-5A	6 x 4 x 3	20.95
MC-6A	8 x 4 x 3	23.15
MC-7A	4 x 7 x 4	20.95
MC-8A	6 x 7 x 4	23.15
MC-9A	8 x 7 x 4	25.75

PANELS ARE .060"  
ALUMINUM AND ARE FIELD REMOVABLE

### HEAVY DUTY RACK CHASSIS

MODEL	DESCRIPTION W x D x H (inches)	PRICE \$
3RU7 HD	19 x 7 x 5.25	118.00
3RU10 HD	19 x 10 x 5.25	121.00
3RU14 HD	19 x 14 x 5.25	134.00
4RU7 HD	19 x 7 x 7.0	121.00
4RU10 HD	19 x 10 x 7.0	129.00
4RU14 HD	19 x 14 x 7.0	134.00
5RU7 HD	19 x 7 x 8.75	126.00
5RU10 HD	19 x 10 x 8.75	133.00
5RU14 HD	19 x 14 x 8.75	143.00

### DUAL SLOPE METAL CABINETS

MODEL	DESCRIPTION MAJOR DIM. SECONDARY DIM. W x D x H x S x R x D (in)	PRICE \$
DS-1	4 x 6 x 4 x 12 x 1.9 x 2.4 x 1.6	69.00
DS-2	6 x 6 x 4 x 12 x 1.9 x 2.4 x 1.6	63.25
DS-3	8 x 6 x 4 x 12 x 1.9 x 2.4 x 1.6	67.50
DS-4	10 x 6 x 4 x 12 x 1.9 x 2.4 x 1.6	71.50
DS-5	12 x 6 x 4 x 12 x 1.9 x 2.4 x 1.6	76.00
DS-6	18 x 6 x 4 x 12 x 1.9 x 2.4 x 1.6	81.00
DS-7	4 x 8 x 6 x 2 x 3.1 x 3.5 x 1.9	69.00
DS-8	6 x 8 x 6 x 2 x 3.1 x 3.5 x 1.9	73.00
DS-9	8 x 8 x 6 x 2 x 3.1 x 3.5 x 1.9	78.00
DS-10	10 x 8 x 6 x 2 x 3.1 x 3.5 x 1.9	82.75
DS-11	12 x 8 x 6 x 2 x 3.1 x 3.5 x 1.9	87.75
DS-12	18 x 8 x 6 x 2 x 3.1 x 3.5 x 1.9	100.75

### EXTRUDED SERIES

MODEL	DESCRIPTION W x D x H (inches)	PRICE \$
ET-1	4.52 x 4.35 x 1.57	10.00
ET-1B	4.52 x 4.35 x 1.57	10.00
ET-2	4.52 x 6.00 x 1.57	24.00
ET-2B	4.52 x 6.00 x 1.57	24.00
CCET	PLASTIC CARRYING CASE	18.00

### SHEET METAL PUNCHES

MODEL	HOLE SIZE & SHAPE	PRICE \$
PUNCH 1	3/8" ROUND	9.95
PUNCH 2	7/16" ROUND	9.95
PUNCH 3	1/2" ROUND	9.95
PUNCH 4	9/16" ROUND	12.95
PUNCH 5	5/8" ROUND	12.95
PUNCH 6	11/16" ROUND	12.95
PUNCH 7	3/4" ROUND	12.95
PUNCH 8	13/16" ROUND	12.95
PUNCH 9	7/8" ROUND	12.95
PUNCH 10	1" ROUND	13.95
PUNCH 11	1-1/16" ROUND	13.95
PUNCH 12	1-1/8" ROUND	13.95
PUNCH 13	1-3/16" ROUND	13.95
PUNCH 14	1-1/4" ROUND	14.95
PUNCH 15	1-3/8" ROUND	14.95
PUNCH 16	1-1/2" ROUND	16.95
PUNCH 17	1-5/8" ROUND	21.95
PUNCH 18	1-3/4" ROUND	24.95
PUNCH 19	2-5/8" ROUND	61.95
PUNCH 20	1 1/16" SQUARE	32.95
PUNCH 21	3/4" SQUARE	35.95
PUNCH 22	1" SQUARE	46.95
PUNCH 23	2 1/32" x 15/16" RECT.	46.95
*PUNCH 24	*THURST RACES	10.95

**\$575.00**  
(shipped within  
48 states)



### BRAKE & SHEAR

CUTS METALS, PLASTIC, ETC. TO .063" THICK AND  
7 7/8" WIDE AND BENDS UP TO 90°. GREAT SHOP TOOL.

### HAND TOOLS


MODEL	DESCRIPTION	RANGE (mm)	PRICE \$
MD-1	MICRO REAMER	1.0-5.5	16.50
MD-2	REGULAR REAMER	3.0-12.0	26.00
MD-3	LARGE REAMER	10.0-25.0	48.00
RT-1	RETHREADER	3.0 x 0.5	10.50
AD-1	DRILL BIT ADAPTER FOR POWER SCREWDRIVER		6.50

SESCOM ALSO STOCKS  
HARDWARE KITS,  
TRANSFER LETTERING, AND  
MINI-POWER TRANSFORMERS  
CALL OR WRITE FOR YOUR  
**FREE 24 PAGE**  
CONSTRUCTOR'S CATALOG



SESCOM, INC.  
2100 WARD DRIVE  
HENDERSON, NV 89015 USA

CALL TODAY

 

PREPAID ORDERS SHIPPED GROUND AT NO CHARGE (48 STATES)

FOR USA AND CANADA ORDERS (800) 634-3457  
TECHNICAL INFORMATION (702) 565-3400  
24 HOUR FAX (702) 565-4828

CIRCLE 269 ON FREE INFORMATION CARD

# CELLULAR TELEPHONE MODIFICATION HANDBOOK

## How do you reprogram cellular phones?

- How to have two phones with the same number
- Descriptions of cellular phone's vulnerabilities
- Techniques for decoding & changing cellular phones' NAMS and ESN's
- Where to buy programming devices
- Chip supplier's phone numbers
- Instructions on how to change phone numbers on all models
- Cellular phone manufacturer's ESN codes



*We now offer cellular phones cloned with your existing  
number! Buy a handheld, transportable or car  
mounted phone from us or we can convert your phone!  
Call for details.*

**Complete Manual only \$79.95**

M.O. or C.O.D. to **SPY Supply** 7 Colby Court Suite 215, Bedford, NH 03110 **(617) 327-7272**

*Sold for educational purposes only*



FROM

**\$19<sup>95</sup>**

Standard



**\$199<sup>95</sup>**

High Performance

**GREAT VALUE!**

**Standard Features - Models 100, 150, 200 & 400**

- AC & DC VOLTAGES ● DC CURRENT ● RESISTANCE
- CONTINUITY TESTER - Buzzer ● DIODE TEST ● 3 1/2 Digit LCD
- LOW BATTERY INDICATOR ● ACCURACY +/- 0.5% RDG

**Kelvin Meters backed by a 2 Yr Warranty - Parts & Labor**



100 Basic



150 Basic+



200 Advanced

PRO 400



PRO 400

BATTERY TEST

TRANSISTOR hFE BATTERY TEST

TRANSISTOR hFE CAPACITANCE AC/DC CURRENT

20MHz FREQ COUNTER AC/DC CURRENT CAPACITANCE LOGIC TEST TRANSISTOR hFE LED TEST - VERIFY GOOD/BAD

**KELVIN # 990087**

**100 Basic**

**\$19<sup>95</sup>**

**KELVIN # 990090**

**150 Basic+**

**\$29<sup>95</sup>**

**KELVIN # 990091**

**200 Advanced**

**\$39<sup>95</sup>**

**KELVIN # 990092**

**PRO 400**

**\$69<sup>95</sup>**

**Protective Cases**

For Models 100, 150, 200 ..... \$4.<sup>95</sup> (990088)

Case For Model Pro 400 ..... \$9.<sup>95</sup> (990094)



Model 92 PERFORMANCE PLUS



Model 93 DIAGNOSTIC PLUS



Model 95 ENGINE ANALYZER PLUS

**Standard Features - Models 92, 93, 94 & 95**

- DC/AC VOLTMETERS ● AC/DC CURRENT ● OHM METER
- FREQUENCY COUNTER to 4 MHz ● AUDIBLE CONTINUITY TESTER
- DIODE TESTER ● MAX/MIN AVERAGE MEMORY RECORD
- RELATIVE MODE ● 10A HIGH-ENERGY FUSE PROTECTION
- DATA HOLD ● AUTO SLEEP & AUTO POWER OFF

**PERFORMANCE PLUS**

Model 92 # 990109

**\$119<sup>95</sup>**

Complete with above Standard Features plus WATER RESISTANT (92 & 94 Models only), 2 YEAR WARRANTY, YELLOW HOLSTER, PROBES, BATTERY, FUSE, STAND

**DIAGNOSTIC PLUS**

Model 93 # 990110

**\$149<sup>95</sup>**

Complete with Standard & Model 92 Features plus LOGIC PROBE, CAPACITANCE TESTER, TRANSISTOR TESTER, TEMPERATURE TESTER & K-TYPE PROBE, HIGH VOLTAGE WARNING BUZZER

**ENGINE ANALYZER PLUS**

Model 95 # 990112

**\$199<sup>95</sup>**

Complete with Standard & Model 92 Features plus TEMPERATURE, TACHOMETER & DWELL ANGLE TESTER, DUTY CYCLE, 10 MEGA OHM IMPEDANCE, ANALOG BAR GRAPH, K-TYPE TEMP PROBE, ALLIGATOR CLIP TEST LEADS, INDUCTIVE PICKUP CLIP, 6' TEST LEADS & CARRY CASE

**KELVIN**  
ELECTRONICS

10 HUB DRIVE  
MELVILLE, NY  
11747

M/C & VISA

(800) 645-9212

Established 1945

(516) 756-1750

(516) 756-1763/FAX

**The Ultimate Meter**  
TRUE RMS - LCR - Hz - dBm



**12 INSTRUMENTS IN ONE - DC VOLTMETER, AC VOLTMETER, OHMMETER, AC CURRENT, DC CURRENT, DIODE TESTER, AUDIBLE CONTINUITY TESTER, dBm, FREQ COUNTER, CAPACITANCE METER, INDUCTANCE METER, LOGIC PROBE**

**0.1% ACCURACY on DC Voltages**

**Water Resistant**

**\$199<sup>95</sup>**

MODEL 94 #990111

10 MEGA OHM IMPEDANCE  
RELATIVE MODE / DATA HOLD  
MAX/MIN AVERAGE MEMORY RECORD  
10A HIGH-ENERGY FUSE PROTECTION  
AUTO SLEEP & AUTO POWER OFF with Bypass

COMES COMPLETE WITH YELLOW HOLSTER, PROBES, BATTERY, FUSE, STAND

**Freq Counter to 20 MHz**

**Cases for 90 Series Meters**

Regular Padded Zippered ... \$9.<sup>95</sup> (#990116)

Deluxe Padded Zippered ..... \$14.<sup>95</sup> (#990115)

This meter is designed in accordance with relevant safety requirements as specified in IEC-348, UL-1244 and VDE-0411.

March 1993, Electronics Now





# JDR Microdevices®

2233 Samaritan Drive, San Jose, CA 95124

Serving you since 1979

BUY WITH CONFIDENCE FROM JDR!

- 30-DAY MONEY BACK GUARANTEE
- 1 YEAR WARRANTY
- TOLL-FREE TECH SUPPORT



## TTL LOGIC

PART#	PRICE	PART#	PRICE	PART#	PRICE
<b>7400</b>		<b>74LS</b>		74LS173	0.39
7400	0.29	74LS00	0.25	74LS174	0.39
7402	0.29	74LS02	0.25	74LS175	0.39
7404	0.29	74LS04	0.25	74LS191	0.49
7406	0.35	74LS08	0.25	74LS193	0.59
7407	0.35	74LS10	0.25	74LS221	0.59
7408	0.29	74LS14	0.39	74LS240	0.49
7410	0.29	74LS20	0.25	74LS241	0.55
7414	0.35	74LS30	0.25	74LS244	0.69
7432	0.35	74LS32	0.25	74LS245	0.69
7447	0.35	74LS38	0.35	74LS257	0.39
7473	0.49	74LS42	0.39	74LS273	0.69
7474	0.35	74LS51	0.25	74LS293	0.59
7475	0.49	74LS73	0.35	74LS367	0.39
7476	0.65	74LS74	0.29	74LS373	0.69
7483	0.59	74LS575	0.29	74LS374	0.69
7486	0.39	74LS83	0.49	74LS682	1.99
7490	0.69	74LS85	0.49		
7493	0.45	74LS86	0.25		
74116	1.49	74LS90	0.39	74500	0.29
74121	0.49	74LS93	0.39	74502	0.29
74123	0.49	74LS107	0.39	74504	0.29
74147	2.15	74LS112	0.35	74508	0.29
74150	1.29	74LS123	0.39	74532	0.35
74151	0.39	74LS125	0.39	745157	0.49
74153	0.59	74LS126	0.39	745163	0.59
74154	1.35	74LS138	0.39	745188	1.75
74157	0.45	74LS139	0.39	745287	1.69
74161	0.45	74LS151	0.39	745288	1.69
74163	0.49	74LS153	0.39	745373	1.69
74174	0.59	74LS154	1.15	745374	0.69
74175	0.59	74LS155	0.49	745387	1.75
74191	0.85	74LS157	0.39	745571	2.95
74221	0.45	74LS163	0.49	745573	2.45

## EPROMS

PART#	SIZE	Speed	Vpp	PINS	PRICE
2732A-250	4096x8	250ns	21V	24	3.95
2744A-450	8192x8	450ns	12.5V	28	3.95
2744A-250	8192x8	250ns	12.5V	28	3.95
2744A-200	8192x8	200ns	12.5V	28	4.49
27128A-200	16384x8	200ns	12.5V	28	4.95
27256-250	32768x8	250ns	12.5V	28	4.95
27256-250	32768x8	250ns	12.5V	28	5.95
27C512-150	65536x8	150ns	12.5V	28	6.75
27C101-200	131072x8	200ns	12.5V	32	7.95
27C101-150	131072x8	150ns	12.5V	32	8.25

## STATIC RAM

PART#	SIZE	SPEED	PINS	CMOS	LP	PRICE
HM6116-2	2048x8	120ns	24	Y	N	2.95
HM6116LP-2	2048x8	120ns	24	Y	Y	3.95
HM6264LP-10	8192x8	100ns	28	Y	Y	5.95
HM62256LP-12	32768x8	120ns	28	Y	Y	5.95
HM62256LP-10	32768x8	100ns	28	Y	Y	6.95
HM62832-20	32768x8	20ns	28/3"	Y	Y	13.95
HM62832-15	32768x8	15ns	28/3"	Y	Y	16.95
HM628128LP-10	131072x8	100ns	32	Y	Y	22.95
HM628128LP-85	131072x8	85ns	32	Y	Y	24.95

## PALS

PART#	SPEED	PINS	IN	OUT	I/O'S	FUNCTIONS	PRICE
16L8	35ns	20	10	2	6	AND-OR INV	2.25
16R4	35ns	20	8	4	4	AND-OR INV	2.25
16R6	35ns	20	8	6	2	AND-OR INV	2.25
20L8	40ns	24	14	2	6	AND-OR INV	2.25
20R4A	25ns	24	12	4	2	AND-OR INV	2.45
20R6	40ns	24	12	6	2	AND-OR INV	2.25
20R8	40ns	24	12	8	-	AND-OR INV	2.25
20X8	50ns	24	10	8	2	AND-OR-XOR INV	2.95
20L10	40ns	24	10	12	2	AND-OR INV	2.95

## GALS

PART#	SPEED	PINS	REPLACES	IN	OUT	PRICE
16V8	35ns	20	10L8 TO 16R8B	8	8	1.95
16V8-15	15ns	20	10L8 TO 16R8B	8	8	2.25
20V8	35ns	24/3"	14L8 TO 16R8B	20	8	2.95
20V8-15	15ns	24/3"	14L8 TO 16R8B	20	8	3.45
22V10	35ns	24/3"	PGM OUTPUTS	22	10	6.95
22V10-15	15ns	24/3"	PGM OUTPUTS	22	10	13.95

## 8000 SERIES MICROPROCESSORS

PART #	PRICE	PART #	PRICE	PART #	PRICE
8031	3.75	8742	14.95	80486-33	599.00
8032A	8.95	8748H	8.95	8087	89.95
80C32	10.95	8749H	9.95	8087-2	129.95
8155	2.85	8751H	29.95	8087-1	169.95
8251A	2.89	87C51	39.95	80287-XL	89.95
8253-5	2.75	8755A	14.95	80387-SXP	79.95
8255-5	2.69	8088-1	7.95	80387-DXP	89.95
82C55-5	3.95	R0286-16	34.95	80487-SX	389.95
8257-5	3.49	80386-33	299.95	ODP486-X24	449.95

## RS-232 BREAKOUT BOX \$34.95

- Ten bi-polar LEDs monitor TF, RD, RTS, CTS, DSR, CD, TC, RC, DTR and TC signals (2 spare)
  - 24 switches for breakout and patching
  - Includes jumper wires
  - Requires no battery
- BRBOX-B0 ..... \$34.95

## SOLDER STATION \$79.95

- 60 watts thermostatically controlled heat from 200°-900° F
  - Solder gun, gun-rest & cooling tray
- 168-3C ..... \$79.95

## SOLDER/DESOLDER STATION

- Oil-free vacuum pump
  - Adjustable temperature (200°-900° F) and vacuum (060cm/Hg)
- X7999SD-A ..... \$399.95

## JDR INSTRUMENTS

ALL JDR INSTRUMENTS CARRY A 2 YEAR WARRANTY

### 35MHZ OSCILLOSCOPE

- Exceptionally bright CRT
- TV sync filter
- Fast 10ns rise time
- Delayed & single sweep modes



MODEL-3500 ..... \$499.95  
 MODEL-2000 20MHz version, no delay ..... \$389.95  
 TAB38911 Troubleshooting w/your Oscilloscope \$18.95

### 100MHZ MULTIFUNCTION COUNTER

- Range: 10Hz to 10MHz direct, 10MHz to 100MHz prescaled by 10
- Period measurements: 10Hz to 2.5MHz, ±1 count accuracy
- Time base: 10MHz
- 8 digit LED display with decimal point



DFC-100 ..... \$179.95  
 DFC-1000 1 GHz version ..... \$199.95  
 DFG-600 Sweep function generator ..... \$189.95  
 D05-600 Audio oscillator/generator ..... \$189.95

### 3.5 DIGIT DMM \$79.95

- Basic DC accuracy ±0.25%
- DC voltage: ±1mV-1000V; AC voltage: ±1mV-750V; AC/DC current: 1µA - 20A Resistance: ±1Ω - 20MΩ
- Input impedance: 10MΩ • 28 ranges



DMM-300 ..... \$79.95  
 DMM-150 3.5 digit DMM with 14 ranges ..... \$29.95  
 LP-100 Logic probe ..... \$17.95  
 LP-200 Pulser probe ..... \$19.95

## D-SUBMINIATURE CONNECTORS

TYPE	ORDER BY	CONTACTS				
		09	15	25	37	50
SOLDER CUP	MALE DBxxP	.45	.59	.69	1.35	1.85
	FEMALE DBxxS	.49	.69	.75	1.39	2.29
R/A PC SOLDER	MALE DBxxPR	.49	.69	.79	2.27	—
	FEMALE DBxxSR	.55	.75	.85	2.49	—
W/W TYPE	MALE DBxxPW	1.69	2.56	3.89	5.60	—
	FEMALE DBxxSW	2.76	4.27	6.84	9.95	—
IDS TYPE	MALE IDBxxP	1.39	1.99	2.25	4.25	—
	FEMALE IDBxxS	1.45	2.05	2.35	4.49	—
HOODS	METAL MH00Dxx	1.05	1.15	1.25	—	—
	PLASTIC HOODxx	.39	.39	.39	.69	.75

## IC SOCKETS DIP CONNECTORS

TYPE	ORDER BY	CONTACTS							
		08	14	16	20	24	28	40	
SOLDER TAIL	xx PIN ST	.11	.11	.12	.18	.20	.22	.30	
WIREWRAPE	xx PIN WW	.59	.69	.69	1.09	1.49	1.69	1.99	
ZIF	ZIF-xx	—	6.95	6.95	9.95	10.95	11.95	14.95	
TOOLED	AUGATxx	.55	.59	.69	.85	.99	1.09	1.29	
TOOLED WW	AUGATxxWW	1.30	1.80	2.10	2.50	3.15	3.70	5.40	

## IDC CONNECTORS AND CABLE

TYPE	ORDER BY	CONTACTS				
		20	26	34	40	50
SOLDER HEADER	IDHxxS	1.29	1.68	2.20	2.58	3.24
R/A HEADER	IDHxxSR	1.35	1.76	2.31	2.72	3.39
W/W HEADER	IDHxxW	2.98	3.84	4.50	5.28	6.63
R/A W/W HEADER	IDHxxWR	3.28	4.22	4.45	4.80	7.30
HEADER SOCKET	ID5xx	.65	.75	.75	1.19	1.19
RIBBON HEADER	IDMxx	5.50	6.25	7.00	7.50	8.50
IDC EDGE CARD	IDExx	.55	.75	.89	1.29	1.69
RIBBON CABLE	RCxx	.30	.39	.51	.60	.75

To order, insert the number of contacts in the position marked "xx" of the "order by" part number listed. Ex: a 15-pin right angle male PC solder part would be D815SR.

## VOLTAGE REGULATORS

PART #	PRICE	PART#	PRICE	PART#	PRICE
UA78540	1.35	7815K	1.39	7915T	0.45
78L05	0.39	7824T	0.45	7915K	1.49
7805T	0.45	7824K	1.39	7924T	0.45
8085K	1.39	79105	0.39	7924K	1.49
78M05C	0.49	7905T	0.45	LM317T	0.57
7806T	0.45	7905K	1.49	LM323K	3.25
7808T	0.45	7906T	0.45	LM337K	2.95
78L12	0.39	7908T	0.45	LM337T	0.87
7812T	0.45	79112	0.39	LM338K	3.95
7812K	1.39	7912T	0.45	LM350K	4.60
78L15	0.39	7912K	1.69	LM350T	2.85
7815T	0.45	7915	0.39	LM723	0.49

## NEC V-20 AND V-30 SERIES

The NEC V-20/30 can improve performance by up to 30%! Pin compatible with the 8088.

- Uses superspeed of 8088 instructions
- High speed address calculation in hardware
- Low power CMOS design

PART#	PRICE
V20-8	7.95
V20-10	9.95
V30	9.95

## LINEAR

PART#	PRICE	PART#	PRICE	PART#	PRICE
MAX232	3.95	LM358	0.49	HE602AN	1.95
LM301	0.39	LM380	0.95	LM709	0.79
LM307	0.49	LM380M-B			





# JDR Microdevices®

2233 Samaritan Drive, San Jose, CA 95124

Serving you since 1979

BUY WITH CONFIDENCE FROM JDR!

- 30-DAY MONEY BACK GUARANTEE
- 1 YEAR WARRANTY
- TOLL-FREE TECH SUPPORT



## CALL FOR YOUR FREE JDR CATALOG TODAY!

FOR PC'S, SOFTWARE, MONITORS, DISK DRIVES, KEYBOARDS, MODEMS, CABLES, CONNECTORS, ICs, COMPONENTS, PROGRAMMERS, TEST EQUIPMENT, TOOLS & MORE!



## 16-BIT VGA CARD

# \$49<sup>95</sup>

- 8/16-bit 8088 or 286/386/486 compatible
- 640 x 480 in 16 colors
- 320 x 200 in 256 colors
- 256Kb video RAM



MCT-VGA-1000	.....	\$49.95
MCT-VGA-3000	1024x768, 512 Kb VGA card	\$89.95
MCT-IDEFH	16-bit IDE hard/floppy controller	\$29.95
MCT-IDEIO	16-bit IDE floppy/hard multi I/O	\$69.95
MCT-IDE-8	8-bit 8088 IDE controller	\$79.95
MCT-AIO	Serial/parallel/game port card	\$49.95
MCT-AIO-2	Two NS16550 serial/par/game port	\$89.95
MCT-FDC-HD	1.44Mb floppy controller	\$49.95
GATEKEEPER	PC security card	\$49.95
PCODE	Diagnostic display card	\$49.95

## 1024 X 768 NON-INTERLACED VGA PACKAGE

# \$499<sup>95</sup>


- 0.28mm dot pitch non-interlaced monitor and high-resolution VGA card
- Resolution up to 1024 x 768 in 256 colors
- 1Mb video RAM

VALUE



VGA-PKG-1024N	..	\$499.95
VGA-PKG-1024+	1024x768 interlaced VGA pkg.	\$469.95
VGA-PKG	640x480 interlaced VGA pkg.	\$349.95
VGA-MON-1024	1024x768 int. mon., .28mm	\$349.95
VGA-MON-1024N	1024x768 non-int. mon. .28mm	\$389.95

## MOTHERBOARDS

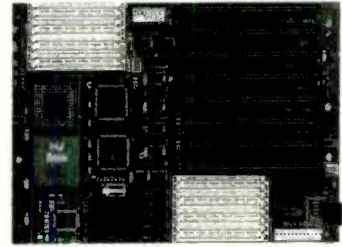

## 50MHZ CACHE 486 \$999

- 50MHz Intel 80486 CPU
- 64Kb cache memory on-board (expand. to 256Kb)
- Expandable to 64Mb on-board using 256K, 1M or 4M x 90ns SIMMs (OK installed)

MCT-M486-50	.....	\$999.00
MCT-M486-50E	50MHz EISA w/cache	\$1395.00
MCT-M486-33	33MHz cache 486	\$799.00
MCT-M486SX-25	25MHz cache 486SX	\$399.95
MCT-C386-40	40MHz cache 386	\$379.95
MCT-C386-33	33MHz cache 386	\$349.95
MCT-M386SX-25	25MHz 386SX	\$199.95
MCT-M286-16	16MHz 286	\$149.95
MCT-M286-12	12MHz 286	\$129.95

## CONNER 84Mb DRIVE PACKAGE

# \$259

- CP-30084 84Mb, 19ms IDE hard drive, 16-bit floppy/hard disk controller, cables and instructions



HDKIT80 ..... \$259.00

## IDE HARD DRIVES

PART #	BRAND	CAP.	SPEED	TYPE	PRICE
CP-3000	Conner	42Mb	28ms	3.5" IDE	\$189
ST-351A	Seagate	42Mb	28ms	3.5" IDE	\$199
CP-30084	Conner	84Mb	19ms	3.5" IDE	\$239
ST-3096A	Seagate	88Mb	16ms	3.5" IDE	\$259
CP-30104	Conner	120Mb	19ms	3.5" IDE	\$319
ST-31444	Seagate	131Mb	16ms	3.5" IDE	\$319
CP-3204F	Conner	212Mb	16ms	5.25" IDE	\$479

## FLOPPY DRIVES

FDD-1.44A	1.44Mb, 3.5", Beige	\$79.95
FDD-1.2	1.2Mb, 5.25", Beige	\$89.95
FDD-360	360Kb, 5.25", Black	\$89.95
FD-505	5.25" & 3.5" combo	\$149.95

## UNIVERSAL PROGRAMMER

- Programs EPROMs, EEPROMs, microprocessors, PROMs, PAL/GALs and other PLDs; tests logic & memory devices
- Optional adaptors available for PLCC, PGA, QFP and multiple DIP devices
- Includes host adaptor card and cable



MOD-EMUP ..... \$699.00

## EPROM PROGRAMMER

- Programs devices up to 512K bits, and 27C100, 27C101, 27C301, 27C1000, 27C1001, 27C2001, 27C4001 and more
- Ded. 8-bit 8088 & 286/386/486 PC compatible card
- ZIF socket accepts 0.6"W DIP IC's to 32 pins

MOD-MEP-1A	.....	\$199.95
MOD-MEP-4A	As above with 4 ZIF sockets	\$269.95

## EPROM ERASER \$39<sup>95</sup>

- Quickly and simultaneously erases up to 4 standard EPROMs
- Includes wall plug power supply



DATABASE II ..... \$39.95

## ENHANCED KEYBOARD

# \$49<sup>95</sup>

BTC-5339 101/102-key enhanced layout ..... \$49.95



## 3-BUTTON MOUSE

# VALUE \$14<sup>95</sup>

- Accuracy 290 - 1450 DPI
- Opto-mechanical design
- Windows 3.0 compatible



JDR-MOUSE-3 ..... \$14.95  
MOUSE-PAD ..... \$4.95

## DYNAMIC RAM

PART #	SIZE	SPEED	TYPE	PRICE
41256-80	256K x 1	80ns	DIP	1.69
41256-60	256K x 1	60ns	DIP	2.39
414256-80	256K x 4	80ns	DIP	5.49
1M8-80	1M x 1	80ns	DIP	4.99
1M8-60	1M x 1	60ns	DIP	5.49
41256A98-80	256K x 9	80ns	SIMM	14.95
41256A98-60	256K x 9	60ns	SIMM	16.95
421000A98-80	1M x 9	80ns	SIMM	39.95
421000A98-60	1M x 9	60ns	SIMM	45.95
424000A98-80	4M x 9	80ns	SIMM	149.95
424000A98-60	4M x 9	60ns	SIMM	159.95

## MATH CO-PROCESSORS



Each co-processor includes a manual, software guide and Intel's lifetime warranty.

PART #	SPEED	PRICE	PART #	SPEED	PRICE
8087	5MHz	89.95	80387-SXP	≤25MHz	79.95
8087-2	8MHz	129.95	80387-DXP	≤33MHz	89.95
80287-XL	12MHz	89.95	80487-SX	≤25MHz	389.95

## BREADBOARD ON-A-CARD

- Solderless breadboard with I/O, decode & timing circuitry



PDS-601	8-bit card	.....	\$79.95
PDS-611	16-bit version	.....	\$89.95

## WIRE-WRAP PROTOTYPE CARDS

JDR-PR2	8-bit with I/O decode layout	.....	\$29.95
JDR-PR10	16-bit with I/O decode layout	.....	\$34.95

## PORTABLE IC TESTER

- Tests the following 14 to 20-pin devices: 74 series TTL, 40 & 45 series CMOS & 41/44 series DRAM up to 1Mb
- Identifies unknown part numbers



MOD-HIC ..... \$149.95

## UPRIGHT CASE

# \$99<sup>95</sup>

- Accommodates std. motherboards
- Mounts 3 floppy and 4 hard drives
- 2 digit LED display

CASE-100A	.....	\$99.95
PS-250TW	250W p. supply	\$129.95
PS-300TW	300W p. supply	\$149.95
PS-300TW	300W p. supply	\$149.95
CASE-200A	11-drive upright	\$349.95
CASE-70	Std. 286-style case	\$89.95
CASE-120	.....	\$199.95



## POWER SUPPLIES

- U/L approved
- 110/220V, 50/60Hz



PS-150	8088 150 watt	.....	\$69.95
PS-200X	8088 200 watt	.....	\$89.95
PS-200	286/386/486 200 watt	.....	\$89.95
PS-250	286/386/486 250 watt	.....	\$129.95
PS-300	286/386/486 300 watt	.....	\$149.95

## 2400 BAUD MODEM

# VALUE \$49<sup>95</sup>

- Internal data modem
- Hayes AT compatibility
- Incl. ProComm software



MCT-241 ..... \$49.95

## 14.4K INTERNAL MODEM W/FAX

- 14,400 fax with V.32bis/V.32/V.42bis/V.42

VIVA-14A4IF ..... \$269.95

## 9600 BAUD EXTERNAL MODEM

- CCITT V.42bis/V.32/V.22bis/Bell 212A & Hayes AT compatible • Asynchronous / synchronous

VIVA-96E ..... \$299.95

## FAX/MODEM SWITCH

- Save phone line charges! • Supports fax, modem, phone and answering machine from 1 phone line

FAXM-SWITCH	.....	\$89.95
FAX-SWITCH	Without modem connection	\$59.95



# ORDER TOLL-FREE 800-538-5000

LOCAL/INTERNATIONAL (408) 559-1200 FAX ORDERS 800-538-5005

NOW ORDER 24 HOURS A DAY!





# THE \$99.95 EDUCATION

## THE PRIMER MICROPROCESSOR TRAINING SYSTEM

- TEACHES:**
- \* INTEL 8085 PROGRAMMING
  - \* DIGITAL & ANALOG INTERFACING
  - \* PROGRAMMING INTEL PERIPHERALS
  - \* MICROCOMPUTER DESIGN & ASSEMBLY
- FEATURES:**
- \* MONITOR O.S. SOFTWARE IN EPROM
  - \* OVER 100 PAGE SELF INSTRUCTION MANUAL
  - \* 6 DIGIT, 7 SEGMENT, LED DISPLAY
  - \* 20 KEY KEYPAD
  - \* DIGITAL INPUT PORT WITH DIPSWITCH
  - \* DIGITAL OUTPUT PORT WITH LEADS
  - \* ANALOG TO DIGITAL CONVERTER
  - \* DIGITAL TO ANALOG CONVERTER
  - \* TIMER/COUNTER WITH SPEAKER OUTPUT
- OPTIONS:**
- \* BASIC OR FORTH LANGUAGES IN EPROM
  - \* RS232 SERIAL PORT CONNECTS TO PC
  - \* BATTERY BACKED CLOCK AND RAM
  - \* 9 VOLT 500 MA. POWER SUPPLY

THE PRIMER IS \$99.95 QUANTITY 10 OR ONLY \$119.95 QUANTITY 1 IN KIT FORM. THE PRIMER ASSEMBLED & TESTED BY EMAC IS \$169.95.

# EMAC, inc.

618-529-4525 FAX: 618-457-0110

P.O. BOX 2042 CARBONDALE, IL 62902

DC/CAD  
introducing...

## THE TERMINATOR

Super High Density Router  
(Complete with Schematic & PCB EDITOR)

Features the following powerful algorithm & capability:

- Rip - up and Retry
  - Pre-routing of SMT components
  - Real-Time via minimization
  - Real-Time clean up passes
  - User defined strategies
  - Window 3.0 capability as DOS Task
  - 1-mil Autoplacer and Autopanning
  - Two-way Gerber and DXF
  - Automatic Ground Plane w/ Cross-Hatching
  - Complete w/ Schematic & Dolly Libraries
  - Optional simulation capability & protected mode for 386 users
- \* PCB LAYOUT SERVICE AT LOW COST \*

Call for DC/CAD price range: \$295-\$2,500  
\*promotional offer now available\*

LEASE PROGRAM & SITE LICENSE AVAILABLE



Design  
Computation

1771 State Highway 34  
Farmingdale, NJ 07727  
(908) 681-7700 • (908) 681-8733 (FAX)

"DC/CAD... The focal point of future CAD market"

# COMPUTRONEX

6122 Camino Verde Dr, #16A San Jose, Ca 95119  
(408)363-0183/0291 (Main/FAX&BBS)800-576-CHIP

## MR. CD ROM (OVER 400 CD TITLES)

- \*Sound Blaster Pro
- \*Pro Audio Spectrum
- \*Midi / Speakers
- \*CD ROM Software Titles \*\*ASK FOR CATALOG\*\*
- \*Sony Int/Ext
- \*NEC Int/Ext
- CHINON & TEXEL

CHIPS (INTEGRABLE) SIMM/SIPP	DRAM
1x3-100/90/70/60	4464K-80/70
256Kx3-80/70/60	41256K-80/70/60
1Mx1-100/90/70/60	4256K-100/90/70/60
4Mx3-80/70/60	4Mx1-80/70/60

MATH CPU	MISC. ITEMS
80387-DX40/33/26/20MHz	PS/2HP Compat/Touchin/Panasonic Mem. Modules
80287-30/10/8MHz	1048/1040 ARTS/Serial Fax
80387-20MHz/33MHz (Lap Tops)	Digit. Board 48 DB25/RJ45 (Multi-User) Unix & OS/2
80386-33/40MHz CPU	Refurbished Laser Toner (Most Same Day)
80486-33/50MHz CPU/CYRIX 486DLC Upgrade (386)	EMS LIM 4.0 6MB (2 MB SIMMS Min) 1.6/32 Bit
80486-50/66MHz DX2 (Heat sink/Fan Extra)	

Printer/Lasers	Mouse
Panasonic KK-P1124/122/Other	Logitech Scan Man 32/256 Gray Scale/OCR
Star NX-100/124/256 (inkjet color)	Microton Bus Serial/Ball Pt/Genie
Epson/NEC 6300/6300/2200 Plus	Logitech Mouse Bus/Serial/Trackman Ball
HP Series HP/II/III/IV/OKI 400/800/Panas Lasers	HP Gray Scale/Color Scanner HP Scanjet/JIC

SVGA Monitors	Floppy Disk Drives - Controllers	Modems	Cases (Misc)
New Multisync 3024/4024/4024/768	Teac 1.2 MB 3.5" 1.44MB	BOCA 14.4K/9600 Fax/Modem V.32, V.42, MNP5	External UPS 500W (Up-to-irruptible) w/Novell
ViewSonic 1024x768 SVGA 14" 17" 28"	Fujitsu 1.2 MB 3.5" 1.44MB	Evercomm 24pin/9.6KMNP6 (INT/EXT)	Desk Top/Mini Tower W/230W/67 Half-Size Drive Bay
SVGA MULTI SYNC 1024x768 Realitys	Teac Dual 1.2 & 1.44 Floppy (All In One)	US Robotics 16.6K/14.4K HST/Dual STD	Ext FD/HD Case W/66W/230W Half-Ht Drive Bay
SVGA 14" 17" 1024x768 Samsung/Mini Micro	Colorado Tape Backup 120/250MB Int/Ext	Practical Peripherals Dual 14.4K Dual STD Int/Ext	
Amber/White Mono 12" 14" Samsung/Mini Micro	AT/AT 4 Floppy (IDE CTRL w/BIOS)		
Sony SVGA (1604/1304)/Nanos .25 Dot 17" 20"	HI-DENSITY XT/AT/2ND 4.0 CTRL w/Bios		

System Kit	Options
486DX 33/50/66 MHz	486 DX/2 66MHz
4MB RAM / SVGA .28 Dot	8MB RAM / SVGA .28 Dot
120MB Harddisk	212MB HD (SCSI/IDE)
1.2/1.44MB Floppy Disk	1.2/1.44MB Floppy Disk
2 Serial, Printer port, Game	2 Serial, Printer port, Game
Fax/Modem G396/24	Boca Fax/Modem G396/14.4K
101 Enhanced Keyboard	250 Tape Backup (Colorado)
Mouse/Dos 3.0/Win 3.1 (Extra)	101 Enhanced Keyboard
\$1495/\$1795/\$1995	Mouse/Dos 3.0/Win 3.1
Class B, 42 Hz, 16V	\$2995

System Kit	Options
486DX 33/50/66 MHz	486 DX/2 66MHz
4MB RAM / SVGA .28 Dot	8MB RAM / SVGA .28 Dot
120MB Harddisk	212MB HD (SCSI/IDE)
1.2/1.44MB Floppy Disk	1.2/1.44MB Floppy Disk
2 Serial, Printer port, Game	2 Serial, Printer port, Game
Fax/Modem G396/24	Boca Fax/Modem G396/14.4K
101 Enhanced Keyboard	250 Tape Backup (Colorado)
Mouse/Dos 3.0/Win 3.1 (Extra)	101 Enhanced Keyboard
\$1495/\$1795/\$1995	Mouse/Dos 3.0/Win 3.1
Class B, 42 Hz, 16V	\$2995

System Kit	Options
486DX 33/50/66 MHz	486 DX/2 66MHz
4MB RAM / SVGA .28 Dot	8MB RAM / SVGA .28 Dot
120MB Harddisk	212MB HD (SCSI/IDE)
1.2/1.44MB Floppy Disk	1.2/1.44MB Floppy Disk
2 Serial, Printer port, Game	2 Serial, Printer port, Game
Fax/Modem G396/24	Boca Fax/Modem G396/14.4K
101 Enhanced Keyboard	250 Tape Backup (Colorado)
Mouse/Dos 3.0/Win 3.1 (Extra)	101 Enhanced Keyboard
\$1495/\$1795/\$1995	Mouse/Dos 3.0/Win 3.1
Class B, 42 Hz, 16V	\$2995

System Kit	Options
486DX 33/50/66 MHz	486 DX/2 66MHz
4MB RAM / SVGA .28 Dot	8MB RAM / SVGA .28 Dot
120MB Harddisk	212MB HD (SCSI/IDE)
1.2/1.44MB Floppy Disk	1.2/1.44MB Floppy Disk
2 Serial, Printer port, Game	2 Serial, Printer port, Game
Fax/Modem G396/24	Boca Fax/Modem G396/14.4K
101 Enhanced Keyboard	250 Tape Backup (Colorado)
Mouse/Dos 3.0/Win 3.1 (Extra)	101 Enhanced Keyboard
\$1495/\$1795/\$1995	Mouse/Dos 3.0/Win 3.1
Class B, 42 Hz, 16V	\$2995

WARRANTY: 1 Year Parts & Labor  
(UPS ONE WAY OR BRING IN)  
Terms: C.O.D., Visa-MasterCard



Electronics Now, March 1993



## The Television Gray Market

Exactly what you need to know about theft of cable, satellite, and videotape programming. This new 160-page book exposes television's hidden underground businesses, chips and test devices, buyers and sellers, and talks about the law and industry countermeasures. Actual conversations with gray market buyers and sellers! It even identifies hundreds of dealers in products, services and information.

## Underground Database

Presents more than 400 sources for cable box chips, switchblades, explosive bullets, police badges, and other items legal to make, sell, buy and own, but generally illegal to use. Lists more than 200 books with recipes for explosives, instructions for converting sporting rifles into machine guns, creating new identities, and much more. This database is at the very limit of freedom of speech.

## Scanners & Secret Frequencies

Whether you're an expert or beginner, prefer police calls or listening to private conversations, this book will help you select, modify, use, and enjoy your scanner. It discusses the law, and then defines hundreds of ways to listen to things the hobbyist was never intended to hear. Vendor list includes books, equipment, software, services, frequency lists, publishers, and much more information.

Money order or check:

**INDEX Publishing Group**  
3368 Governor Dr, #273F  
San Diego, CA 92122


**\$23.75 each,**  
including postage

Credit card orders only:



**1-800-334-8152**

CIRCLE 305 ON FREE INFORMATION CARD

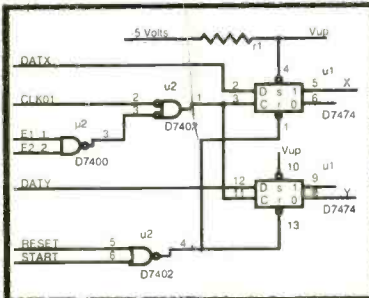

## SuperCAD™

**Schematic Entry Software for the IBM PC & Compatibles**

**\$99<sup>00</sup>**

ONLY COMPLETE PACKAGE

- ★ Easy-to-use schematic entry program for circuit diagrams
- ★ Visible on-screen and pull down menus
- ★ Supports popular graphic standards, mice and printers
- ★ Powerful editing and drawing commands
- ★ Extensive digital, analog and discrete part libraries
- ★ In-depth, readable instruction manual
- ★ Over 100 screens of on-line help information
- ★ Software includes part building and netlisting
- ★ Add P.C. board layout software and routing software for only \$99<sup>00</sup> each

Write or call for FREE demo disk:

**MENTAL AUTOMATION, INC.**

### ORDERS/INFORMATION:

Send check or money orders to:  
**Mental Automation, Inc.**  
5415 - 136th Place S.E.  
Bellevue, WA 98006

Or Call

**(206) 641-2141**



Visa & MasterCard orders accepted!



## CIRCUIT DEBUGGER

DCD-200A

### New Innovative Instrument for

- Open / Short Test
- Impedance Wave Check (R.C.L.)
- CMOS, TTL, ASIC, CUSTOM IC, In/Out Wave Check
- DIODE, TR, SCR, TRIAC, DIAC Wave Check.
- Electric/Electronic Parts Check

- \* Use on Un-Powered Boards !
- \* Repair without Circuit Diagram !
- \* You can find out a defect point by comparing wave forms only !
- \* Simple to use !
- \* If you have Oscilloscope & Multimeter, Next one you need is This Circuit Debugger

Too many application to mention !

Regional Sales Persons Wanted

**AMERIX** Electronics, Inc.

7523 Vanalden Ave., Reseda, CA 91335  
Tel.: (818) 996-8800 Fax.: (818) 996-8850



# JAN Crystals

Your reliable source for a  
world of crystal clear communication

## FOR FREQUENCY CONTROL:

FUNDAMENTAL MODE CRYSTALS 1.001-30.0 MHZ HC6/U, HC17/U, HC33/U	FROM \$11.00
FUNDAMENTAL MODE CRYSTALS 2.0-30.0 MHZ HC25/U, HC18/U MINIATURE HOLDER	FROM \$11.00
THIRD MODE CRYSTALS 18-75. MHZ ANY HOLDER	FROM \$11.00
FIFTH MODE CRYSTALS 52-125. MHZ ANY HOLDER	FROM \$12.00
SEVENTH MODE CRYSTALS 110.5-150. MHZ ANY HOLDER	FROM \$17.00

Quantity Prices Available  
On Request

## FOR MICRO PROCESSORS:

...low E.S.R....close tolerance...long-term stability...  
frequency deviation from 0° to 70°C max. ± 100 PPM...  
tolerance at 25° ± 50 PPM.

HC18/U 3.0-3.5 MHZ	FROM \$5.00
3.5-18.432 MHZ	FROM \$5.00
19.6608-24. MHZ	FROM \$7.00

When Ordering Please Specify MP-Crystal

**FREE 1993 Catalog  
of General Purpose Crystals  
Now Available**

Order Toll-Free  
**1-800-JAN-XTAL**  
FAX ORDERS: 1-813-936-3750

EXPEDITED ORDER SERVICE AVAILABLE  
CALL OR WRITE FOR FREE CATALOG  
P.O. Box 06017 Ft. Myers, FL 33906



PRICES SUBJECT TO CHANGE WITHOUT NOTICE

CIRCLE 290 ON FREE INFORMATION CARD

## C & L ELECTRONICS BUY — SELL — TRADE

**90 DAY  
Guarantee**

General Microwave 460B w/N420C	
Power Meter 10MHZ to 12.4GHZ	395.00
CR 1482R . . . Inductance Standard 5.0 H	400.00
CR 1482T . . . Inductance Standard 10.0 H	600.00
CR 1650B . . . RCL Bridge	500.00
HP 333A . . . Distortion Analyzer	500.00
HP 334A . . . Distortion Analyzer	700.00
HP 3336B w/Opt. 1,5 Synthesizer Level Generator 10HZ to 21MHZ	995.00
HP 3586B w/Opt. 1,3,4 Selective Level Meter 32.5MHZ, 50HZ to 100KHZ	2,800.00
HP 4800A . . . Vector Impedance Meter	600.00
HP 8405A . . . Vector Voltmeter	750.00
HP 8614A . . . Signal Generator 800 to 2400MHZ	900.00
HP 8616A . . . Signal Generator 1800 to 4500MHZ	900.00
Rockland 5100 Frequency Synthesizer Audio to 2MHZ	300.00
Shalltronix 817C Decade Box 01 to 100 ohms (new)	125.00
TEK 7D13 . . . Digital Multimeter, 3-1/2 digit	175.00
TEK 453 . . . Scope 50MHZ	290.00
TEK 453A . . . Scope 50MHZ	500.00
TEK 454 . . . Scope 150MHZ	500.00
TEK 465 . . . Scope 100MHZ	600.00
TEK 475 . . . Scope 200MHZ	800.00
TEK 1480R . . . NTSC Waveform Monitor	1,500.00
TEK 2213 . . . Dual Trace Scope 60MHZ	595.00

Test Equipment WANTED! Will Pay Within 24 Hours!

P.O. BOX 52153 (215) 426-0177  
PHILADELPHIA, PA 19115 FAX 1-215-464-5856


## LASERS

HELIUM NEON FROM \$19  
ARGON \* BOOKS  
CO<sup>2</sup> \* PLANS  
OPTICS \* LIGHTSHOWS  
LASER DIODES  
LASER POWER SUPPLIES

**LASER USES:**  
HOLOGRAPHY \* LIGHTSHOWS  
PRINTING \* COMMUNICATION  
WEAPON SIGHTS \* ALIGNMENT  
ALARMS \* POINTERS  
CUTTING \* CONSTRUCTION

FREE CATALOG 1-800-356-7714

**MWIK INDUSTRIES**

 

198 LEWIS COURT  
CORONA, CA 91720

CIRCLE 256 ON FREE INFORMATION CARD



# Computers, Components, Tools And Supplies

# Debco Electronics

4025 Edwards Road express order line - 1 (800) 423-4499 - orders only please  
Cincinnati, OH 45209 technical support / information - (513) 531-4499

CHIPS.....	74144	6.95	74LS08	30	74LS175	52	74LS670	1.09	74HC511	34	74HC123	99	4047	.79	14433	6.95	LM566	1.69	MC3360	1.50	2N3567	55
74xx	74145	1.09	74LS09	30	74LS181	1.99	74LS674	14.95	74HC174	39	74HC125	99	4048	.79	14451	1.51	LM567	1.69	MC3373	1.70	2N3568	25
7400	74146	2.59	74LS10	30	74LS182	4.95	74LS675	2.19	74HC175	39	74HC126	99	4049	.79	14480	4.95	NE570	3.25	MC3401	90	MP3363B	25
7401	74147	1.39	74LS11	34	74LS190	6.5	74LS683	2.19	74HC185	99	74HC131	59	4050	.79	14497	6.95	NE571	2.69	MC3403	70	PN3643	25
7402	74148	1.39	74LS12	34	74LS191	6.5	74LS684	2.59	74HC186	45	74HC132	59	4051	.79			NE590	2.69	MC3470	2.69	MPS3702	25
7403	74149	1.59	74LS13	35	74LS192	6.9	74LS685	8.00	74HC187	3.69	74HC133	59	4052	.79			NE592	7.9	MC3480	9.95	2N3703	25
7404	74150	1.59	74LS14	35	74LS194	6.9	74LS688	3.50	74HC189	4.9	74HC134	59	4053	.79			LM709	6.9	MC3486	3.00	2N3704	25
7405	74151	6.9	74LS15	47	74LS195	6.9	74LS783	25.00	74HC192	4.9	74HC135	81	4060	.69			LM710	7.9	MC3487	2.19	2N3730	50
7406	74152	8.7	74LS16	30	74LS196	5.9	25LS22	2.89	74HC193	6.9	74HC136	81	4066	.38			LM711	6.9	LM3900	6.9	2N3772	1.39
7407	74153	7.3	74LS17	34	74LS197	5.9	25LS23	3.86	74HC194	6.9	74HC137	59	4068	.49			LM723H	1.29	LM3909	1.69	2N3866	1.20
7408	74154	2.09	74LS22	34	74LS221	6.9	26LS33	2.00	74HC195	5.9	74HC138	59	4070	.38			LM733	.79	LM3911	2.19	2N3904	20
7409	74155	8.7	74LS23	34	74LS240	7.9	25LS25	2.19	74HC196	5.9	74HC139	60	4071	.34			LM741HC	1.49	LM3915	2.89	2N3906	20
7410	74156	7.9	74LS24	34	74LS241	7.9	25LS25B	2.19	74HC197	5.9	74HC140	79	4072	.34			LM747	.79	LM3916	2.69	2N3958	1.50
7411	74157	7.9	74LS25	34	74LS242	6.9	25LS25C	2.19	74HC198	5.9	74HC141	79	4073	.34			LM748	.79	LM4001	4.00	2N4123	30
7412	74158	7.9	74LS26	34	74LS243	6.9	25LS25E	2.19	74HC199	5.9	74HC142	79	4074	.39			LM704	1.39	LM1014	2.69	MC4016	2.75
7413	74159	8.9	74LS27	34	74LS244	7.9	74Sxx		74HC200	92	74HC143	79	4075	.39			LM150K	4.95	LM1303	1.69	MC4024	4.00
7414	74160	8.9	74LS28	34	74LS245	7.9	74Sxx		74HC201	92	74HC144	79	4076	.38			LM201	5.0	MC1330	1.69	MC4136	1.39
7415	74161	7.9	74LS29	34	74LS246	7.9	74Sxx		74HC202	92	74HC145	79	4077	.38			XR215	1.50	MC1349	2.09	2N4236	1.59
7416	74162	8.9	74LS30	30	74LS247	7.9	74Sxx		74HC203	92	74HC146	79	4078	.38			MAX232	5.95	MC1350	1.69	MC4274	2.19
7417	74163	8.9	74LS31	30	74LS248	7.9	74Sxx		74HC204	92	74HC147	79	4079	.38			LM307	5.9	MC1358	1.69	ICL7650	2.25
7420	74164	1.09	74LS32	30	74LS249	7.9	74Sxx		74HC205	92	74HC148	79	4080	.38			LM308	5.9	MC1372	2.69	7106	7.95
7421	74165	1.09	74LS33	30	74LS250	7.9	74Sxx		74HC206	92	74HC149	79	4081	.38			LM309	5.9	MC1374	2.00	7107	6.95
7422	74166	1.09	74LS34	30	74LS251	7.9	74Sxx		74HC207	92	74HC150	79	4082	.38			LM330	5.9	MC1456	1.50	7208	7.95
7423	74167	1.09	74LS35	30	74LS252	7.9	74Sxx		74HC208	92	74HC151	79	4083	.38			LM308	5.9	MC1458	1.47	75107	1.19
7424	74168	1.09	74LS36	30	74LS253	7.9	74Sxx		74HC209	92	74HC152	79	4084	.38			LM311	5.9	LM1488	6.9	75108	1.19
7425	74169	1.09	74LS37	30	74LS254	7.9	74Sxx		74HC210	92	74HC153	79	4085	.38			LM312H	5.50	LM1510	6.95	75110	1.69
7426	74170	1.09	74LS38	30	74LS255	7.9	74Sxx		74HC211	92	74HC154	79	4086	.38			LM316	4.00	MC1496	9.9	75138	1.69
7427	74171	1.09	74LS39	30	74LS256	7.9	74Sxx		74HC212	92	74HC155	79	4087	.38			LM317K	1.99	MC1558	3.50	75150	1.69
7430	74172	1.09	74LS40	30	74LS257	7.9	74Sxx		74HC213	92	74HC156	79	4088	.38			LM317T	7.9	LM1648	9.9	75154	1.69
7431	74173	1.09	74LS41	30	74LS258	7.9	74Sxx		74HC214	92	74HC157	79	4089	.38			LM318	1.19	MC1733CL	1.00	75160	4.25
7432	74174	1.09	74LS42	30	74LS259	7.9	74Sxx		74HC215	92	74HC158	79	4090	.38			LM322	2.19	LM1800	2.69	75189	1.19
7433	74175	1.09	74LS43	30	74LS260	7.9	74Sxx		74HC216	92	74HC159	79	4091	.38			LM323	3.99	LM1812	2.69	75199	1.19
7434	74176	1.09	74LS44	30	74LS261	7.9	74Sxx		74HC217	92	74HC160	79	4092	.38			LM324	4.45	LM1827	7.95	75453	5.9
7435	74177	1.09	74LS45	30	74LS262	7.9	74Sxx		74HC218	92	74HC161	79	4093	.38			LM325	4.45	LM1871	6.95	75451	5.9
7436	74178	1.09	74LS46	30	74LS263	7.9	74Sxx		74HC219	92	74HC162	79	4094	.38			LM331	6.95	LM1872	7.95	75452	5.9
7437	74179	1.09	74LS47	30	74LS264	7.9	74Sxx		74HC220	92	74HC163	79	4095	.38			LM334	1.69	LM1877	3.95	75453	5.9
7438	74180	1.09	74LS48	30	74LS265	7.9	74Sxx		74HC221	92	74HC164	79	4096	.38			LM335	1.99	LM1889	3.95	75454	5.9
7439	74181	1.09	74LS49	30	74LS266	7.9	74Sxx		74HC222	92	74HC165	79	4097	.38			LM336	1.99	LM1896	1.99	75477	1.39
7440	74182	1.09	74LS50	30	74LS267	7.9	74Sxx		74HC223	92	74HC166	79	4098	.38			LM337	4.25	LM2201	7.9	75491	1.89
7441	74183	1.09	74LS51	30	74LS268	7.9	74Sxx		74HC224	92	74HC167	79	4099	.38			LM337T	1.19	ULN2004	7.9	75493	9.9
7442	74184	1.09	74LS52	30	74LS269	7.9	74Sxx		74HC225	92	74HC168	79	4100	.38			LM339	5.9	XR2206	5.25	75494	1.39
7443	74185	1.09	74LS53	30	74LS270	7.9	74Sxx		74HC226	92	74HC169	79	4101	.38			LF347	8.9	XR2207	4.25	2N6251	1.10
7444	74186	1.09	74LS54	30	74LS271	7.9	74Sxx		74HC227	92	74HC170	79	4102	.38			LM350K	4.95	XR2208	3.25	2N6292	1.10
7445	74187	1.09	74LS55	30	74LS272	7.9	74Sxx		74HC228	92	74HC171	79	4103	.38			LM350T	3.95	LM2210	2.50	MC1R102	1.00
7446	74188	1.09	74LS56	30	74LS273	7.9	74Sxx		74HC229	92	74HC172	79	4104	.38			LF351	6.9	XR2212	1.50	VN10	1.95
7447	74189	1.09	74LS57	30	74LS274	7.9	74Sxx		74HC230	92	74HC173	79	4105	.38			LF352	6.9	XR2214	2.50	MC1R103	1.00
7448	74190	1.09	74LS58	30	74LS275	7.9	74Sxx		74HC231	92	74HC174	79	4106	.38			LF353	6.9	XR2216	2.50	D1K2	1.15
7449	74191	1.09	74LS59	30	74LS276	7.9	74Sxx		74HC232	92	74HC175	79	4107	.38			LF354	6.9	XR2218	2.50	D1K3	1.15
7450	74192	1.09	74LS60	30	74LS277	7.9	74Sxx		74HC233	92	74HC176	79	4108	.38			LF355	6.9	XR2220	2.50	MC1R104	1.00
7451	74193	1.09	74LS61	30	74LS278	7.9	74Sxx		74HC234	92	74HC177	79	4109	.38			LF356	6.9	XR2222	2.50	MC1R105	1.00
7452	74194	1.09	74LS62	30	74LS279	7.9	74Sxx		74HC235	92	74HC178	79	4110	.38			LF357	1.19	LM2901	6.9	BF167	5.0
7453	74195	1.09	74LS63	30	74LS280	7.9	74Sxx		74HC236	92	74HC179	79	4111	.38			LM358	5.9	LM2907	2.69	3N200	5.00
7454	74196	1.09	74LS64	30	74LS281	7.9	74Sxx		74HC237	92	74HC180	79	4112	.38			LM359	2.69	LM2917	2.19	C03Y1	1.00
7455	74197	1.09	74LS65	30	74LS282	7.9	74Sxx		74HC238	92	74HC181	79	4113	.38			LM360	1.39	CA3018	1.50	J3014	1.75
7456	74198</																					



## PROFESSIONAL SECURITY EQUIPMENT

Proven Quality & Reliability for Government, Industry, and the Do-It-Yourselfer

### Voice Record/Playback Board

Just add Speaker and 6-12 VDC Power to Record and Playback 16 seconds of audio. On Board Mike, DRAM, 1 watt amp, Volume Control, Record & Playback Buttons. The easy way to add voice to your projects! Play 1 time, or repeat with continuous trigger. 15mA @ 12VDC.

18106 ..... \$29.95

### How do the Pro's run wires?

#### ... Super-Long Flexible Drills

These Super-Long Twist Drills are used by the Pro's to drill through walls, and up into attics, or down into basement.

96287 1/4" x 58" Flex Bit ... \$29.50  
 96388 1/4" x 72" Flex Bit ... \$39.00  
 96590 3/8" x 58" Flex Bit ... \$37.50  
 96691 3/8" x 72" Flex Bit ... \$45.00  
 96893 1/2" x 58" Flex Bit ... \$39.50  
 96894 1/2" x 72" Flex Bit ... \$49.00

## ENFORCER<sup>®</sup>

### Alarm Pager System

Add to Vehicle Alarm, or use for remote signalling. Up to 2 mile range. Contains 4 Watt Vehicle Transmitter for use with existing car antenna. Output to raise automatic antennas, both (+) and (-) Trigger Inputs. 12VDC, 500mA. Pager beeps and flashes LED until reset.

94974 ..... \$99.95

### Talking Siren Driver - 127db!

Painfully Loud Siren Driver Board Blasts Siren and Talks in English, Spanish, or French. Separate Burglar ("You have violated an area protected by a Security System, Leave Immediately!") and Fire ("Fire, Leave Immediately!") Channels. Add 8 ohm 10 Watt Speaker. 12VDC, 1.3 Amps

18308 ..... \$49.95



32 Page Catalog of Professional Security Systems, Motion Detectors, Switches, Glass Protection, Fire Detectors, Sirens, Radio Links, CCTV, Access Control Systems, Special Tools, and more!

FREE with your order... or send \$2.00 handling fee refundable on first order.

### Vantage Point Technologies

1318 East Mission Rd, Ste 376

San Marcos, CA 92069

FREE shipping to continental US, California Residents add Sales Tax. All items carry 1 Year warranty against defects.




ORDERS ONLY

1-800-272-1357




FREE Technical Help (619) 565-1863

## ELECTRONIC ENCLOSURES

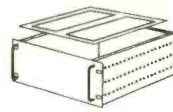

Rack Mount

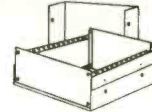


Split Case


Complete line in Aluminum, Steel & ABS Also Hardware, Silkscreening, Hand Tools Ask us about our Custom Fabricating Call for FREE Full Color Catalog (800) 800-3321 (216) 425-1228 Fax




Cage & Preamp Enclosures

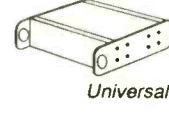

Universal

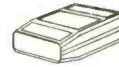

ABS

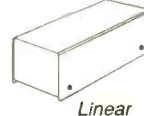

Linear



Knobs & Parts

## Project Pro

1710 ENTERPRISE PKWY TWINSBURG OH 44087

CIRCLE 301 ON FREE INFORMATION CARD

## CELLULAR TELEPHONE HACKERS GUIDEBOOK

DISCOVER HOW HACKERS ARE MAKING FREE CELLULAR PHONE CALLS WITHOUT GETTING CAUGHT

- This Step -by-Step Guide contains both Text and Graphics that anyone can use...
- Easy Techniques For Decoding and Reprogramming Phone Codes
- Proven Hacking Techniques
- Programming Instruction For Over 250 Modles
- Complete Listing of SIC and NAM Codes
- List of I.C Chip and Equipment Suppliers

DON'T GET HACKED BY OTHER, LESS COMPLETE, MORE EXPENSIVE CELLULAR TELEPHONE MODIFICATION GUIDEBOOKS

The CELLULAR TELEPHONE MODIFICATION GUIDEBOOK Contains Over 200 Pages Of Complete, Proven hacking information


THIS MANUAL IS GURANTEED TO SAVE YOU MONEY

SEND \$49.95 + \$4 S/H CHECK OR MONEY ORDER TO:


## DYNASPEK

P.O. BOX 564 WESTMONT, IL. 60559

C.O.D. CALL: (708) 971-1585

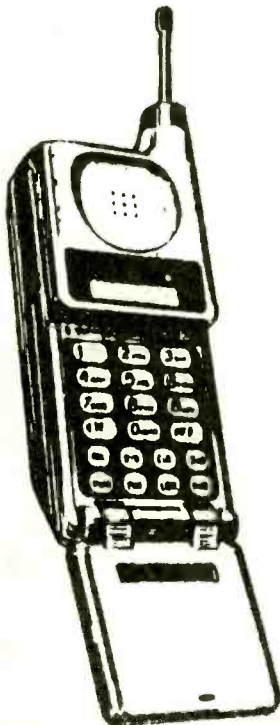



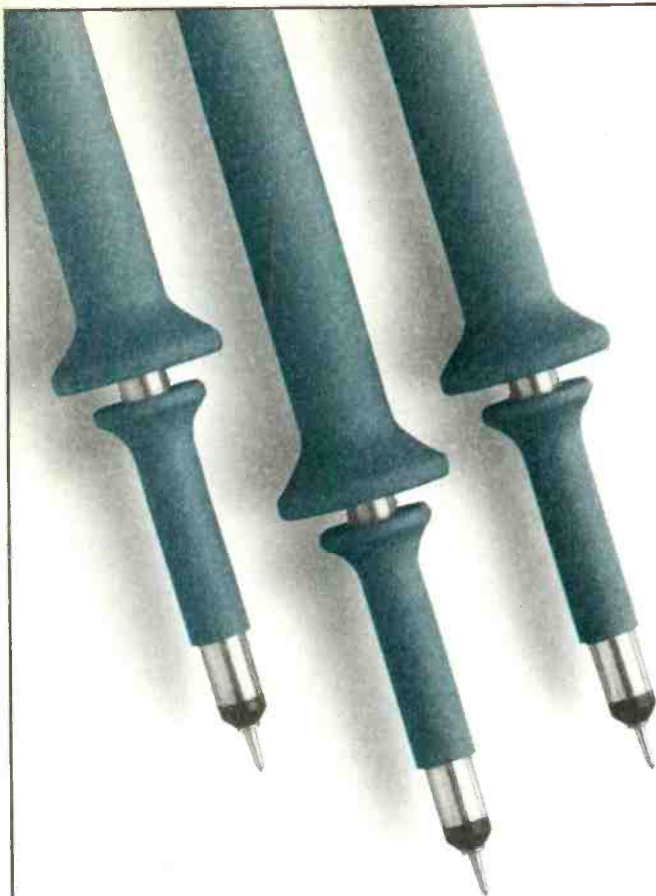

# EVEN AT \$39, THE BLUES CAN LAST A LONG, LONG TIME.

Conventional wisdom says if you spend less than forty bucks on a probe, it won't be long until the thrill is gone. But Duraprobes™ start at \$39, live practically forever, and work with almost any scope around, so it won't surprise us if you pick up a whole case.

For the name of your nearest Duraprobe distributor, call us at 1-800-426-2200. After all, some folks were just born to have the blues.

**Tektronix**

63W-188581-2


CIRCLE 303 ON FREE INFORMATION CARD

## Toner Cartridge Recharge
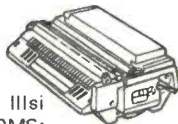
### Kits—Supplies—Service

Everything you need to recharge toner cartridges used with Canon based laser printers and personal copiers.

Use with HP: LaserJet, II, IID, IIP, III, IIIP, IIIsi  
Apple: LaserWriter, LaserWriter IINT, IINTX, QMS:  
Kiss, PS-800, PS-810, Canon: LB-P8A1, A2, II, OKI, NEC, Ricoh, etc  
With our **Kits—Supplies—Service** you can start your own profitable recharge business or just recharge your own cartridges.



Model	Recharge Kits/Supplies	Dealers Please Call	Retail
TR-300	Recharge Kit for CX type laser printer engines.	\$21.95	
TR-302	Recharge Kit for SX type laser printer engines.	\$26.30	
TR-304	Recharge Kit for HP IIP (LPB-4) laser printer.	\$21.95	
TR-325	Recharge Kit for PC-10/12/14/20/24/25 copier.	\$25.50	
TR-370	Recharge Kit for Sharp Z-50/55/70 copier.	\$34.95	
4080	Replacement Toner Kit for Ricoh 4080 laser.	\$35.95ea/5	
6000	Replacement Toner Kit for Ricoh 6000 laser.	\$14.25ea/10	
9710	200 grms of high quality black toner for CX.	\$9.95ea/10	
9730	250 grms of high quality black toner for SX.	\$12.50ea/10	
8011-Blue/Br	200 grms of Blue/Brown toner for CX & SX.	\$22.95ea/10	
8057	150 grms of high quality black toner for PC.	\$10.95ea/10	
Felt-CX,SX	replacement treated felt for all models.	\$0.90ea/10	
SS-CX,SX	seal strips for sealing in toner for reshipping	\$0.85ea/10	
DPP	Drum Padding Powder (pixie dust)	\$12.95	
EverDrum™	OPC drum life extender agent. 40+ applications	\$34.95	
C2094	3M Toner Vacuum with attachments.	\$199.95	

Instructions Available Free to Customers!

Call 800-221-3516 ask for our catalog.



Cheneko Products, Inc.

2221 Fifth Ave., Suite 4, Ronkonkoma, NY 11779

Call: 516-467-3205, Fax: 516-467-3223

# 42,398 ELECTRONIC COMPONENTS

Whether you order 1 part or  
all 42,398...MOUSER stocks  
and...ships same day!!



CALL...  
(800) 992-9943

for your  
**FREE  
CATALOG**

2401 Hwy 287 N.  
Mansfield, TX 76063

**MOUSER**  
**ELECTRONIC**  
Sales & Stocking Locations National

# LASERS

Here is a sampling of our current inventory.

## Helium-Neon

1mW He-Ne Laser, 12vdc input	\$ 49.00
1.5mW He-Ne Laser, 12vdc input	\$ 69.00
1-2mW He-Ne laser pwr supply, 9vdc input	\$ 29.00

## Visible Diode

5mW Laser Diode Module, 2.7-4.5 vdc input	\$135.00
5mW Laser Pointer Pen (12 mo. warranty)	\$129.00

## Higher Power

American 60X Argon Head (newly refurb. 200mW)	\$2650.
Argon Power Supply (newly remanufactured)	\$ 925.
Nd:YAG (new, w/ PFN, 24vdc)	\$1875.

## Light Show Equipment

Basic Light Show Projector	\$275.00
VideoWryter Disc (must specify which one)	\$ 45.00
HoloGrate Set (must specify set, A thru F)	\$ 40.00

FREE CATALOG

## Midwest Laser Products

P.O. Box 2187 Bridgeview, IL 60455 (708)460-9595  
Fax # (708) 430-9280

Poll our fax for 10 page catalog.

Email: mlp@mcimail.com

All products come with a 30 day satisfaction guarantee. Please call for shipping charges. IL Res. include 7.75% sales tax. C.O.D. orders add \$3.00

## NOW! A QUALITY SATELLITE SCPC AUDIO RECEIVER

AT AN AFFORDABLE PRICE



### UNIVERSAL SCPC-100 AUDIO RECEIVER

#### SPECIFICATIONS

STABLE, MICROPROCESSOR CONTROLLED TUNING. • 50 CHANNEL MEMORY RECALL. • COMPATIBLE WITH 950-1450 BLOCK SYSTEMS. • 3 MINUTE HOOK-UP. • LARGE L.E.D. TUNING SCALE. • RECEIVES C AND KU BAND SCPC. • DOES NOT DISABLE VIDEO WHEN IN USE.

#### SERVICES ON SCPC

HUNDREDS OF QUALITY SCPC CHANNELS ON SATELLITES - SPORTS - AP - UPI - RADIO NETS - HOME TOWN SPORTS & RADIO - RACING - TALK SHOWS - CLASSICAL, ROCK & JAZZ - RADIO STATIONS - FINANCIAL NEWS AND MORE.

INTRODUCTORY PRICE \$439 + S&H

TO ORDER CALL: 1 - 800 - 241-8171

### UNIVERSAL ELECTRONICS, INC.

4555 GROVES RD., SUITE 13, COLUMBUS, OH 43232  
(614) 866-4605 FAX (614) 866-1201

### GEARHEAD STEPPER MOTOR KIT \$26.95

The same great stepper motor kit described below, featuring a hi-torque gearhead stepper motor. The 150:1 ratio gearhead produces 0.1 degree steps for pinpoint accuracy and precision movement. Great for robotics!

**STEPPER MOTOR KIT \$16.95**  
The ever-popular stepper motor kit is your chance to learn about stepper motor operation without spending a fortune. Experiment with stepper motor control, speed, and direction. Features include variable speed, step, range, direction, and on/off controls as well as LED indicators. Kit includes 4-phase stepper motor (7-1/2 degree steps), circuit board, and components. Requires 12 VDC power source.



8123 PAGE BLVD \* ST. LOUIS, MO 63130  
(314)427-6116

8222 CHESAPEAKE DR. \* SAN DIEGO, CA 92126  
(619)279-6802

2525 FEDERAL BLVD. \* DENVER, CO 80211  
(303)458-5444

MAIL ORDERS CALL TOLL-FREE

1-800-669-5810

FAX ORDERS (314)427-3147

ELECTRONICALLY SPEAKING,  
GATEWAYS GOT IT!

### THE TELEVISION GRAY MARKET \$23.75

This 160 page book ("sold for educational and entertainment purposes only") covers the billion dollar business of stealing television programming. Whether you want information on cable, satellite, or videotape, the Television Gray Market will provide insight regarding legal issues and risks, industry countermeasures, enforcement agencies and procedures, chips, modifications, and more! Author Henry Eisenson even includes information on periodicals, specialized pamphlets, and conversations with dealers and gray market operators. Appendices include spectrum allocation in North America and suppliers of services and products. Don't miss this book!!!



### SO COOL IT'S HOT! NOW WE'VE GOT A BIGGER PELTIER JUNCTION

Can coolers, coffee warmers, mini-refrigerators, and aquarium coolers be just a few ideas folks have come up with. Big or small, this little wonder is any hobbyist or experimenter's dream come true!!

The peltier junction is a solid-state thermovoltic device. Current applied to the device will produce heat on one side of the device and a cold surface on the other side. Water placed on the surface will freeze or boil depending on polarity of applied voltage. Ideal for applications from 3-12 VDC - whip out a battery and let your imagination run wild! Can be mounted in parallel to increase the "hot" or "cold" effect or they can be stacked in multi-stage cascades to achieve high differential temperatures.

DOCUMENTATION INCLUDED!!!

**Small Peltier Junction**

(approximately 1.17" x 1.17" x .12") \$20.00

**Large Peltier Junction**

(approximately 1.56" x 1.56" x .15") \$29.50

### supermarket laser scanning unit\* \$125.00

person who has everything! Pulled from the depths of some little grocery store, this unit has all sorts of rotating multi-surface mirror 110VAC and 15 front surface mirrors) as well as a HeNe laser tube with lenses on 110VAC, laser is ready to plug in and operate.) Although you probably won't find ginsu knives or a laser light detector, two lenses (that's right, count 'em, 2!), a pc board, and two LED transmitter / receiver. You can really get creative with a device like this!! Approximate dimensions 20" x 15" x 11". All customers please include \$20.00 shipping/handling on this item. (F.O.B. Denver, CO)

THE FINE PRINT: PRICES SUBJECT TO CHANGE WITHOUT NOTICE \* GATEWAY IS NOT RESPONSIBLE FOR PRINTING ERRORS \* MASTERCARD, VISA AND DISCOVER ACCEPTED \* \$10 MERCHANDISE MINIMUM ON MAIL ORDERS \* SUPPLY OF SOME ITEMS IS LIMITED \* PRICES DO NOT INCLUDE SHIPPING \* UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$3.75 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM.

CIRCLE 243 ON FREE INFORMATION CARD



# BRIGAR electronics

\*Quantity Discounts Available




7-9 ALICE STREET BINGHAMTON, NY — 13904 OPEN 7:30-4:30 Mon. - Friday; Saturday 7:30 - 12

**SETTING THE STANDARD FOR EXCELLENCE**
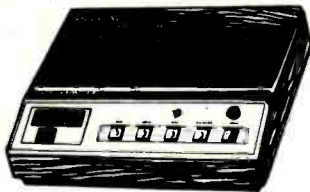
## TELEPHONE ANSWERING MACHINE

CODE-A-PHONE 1750  
 BUILT IN TAPES - (NO TAPES TO BUY)  
 ONE TOUCH MESSAGE PLAYBACK  
 RING DELAY (1 TO 4 RINGS)  
 LED LIGHT INDICATES MESSAGE RECEIVED  
 BUILT IN MICROPHONE  
 EASY OPERATION  
 REMOVED FROM SERVICE MINT CONDITION  
 BRIGAR SPECIAL PRICE \$29.95 EA.



## Rectifiers




HIGH POWER SILICON RECT.  
 1N3741  
 A190N  
 800 PIV 250 AMPS  
 1 1/4" DIAM.  
 2 1/4" LONG  
 5 1/4" COPPER LEAD

— \$9.95
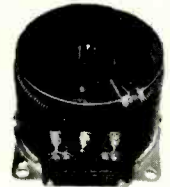
## VARIABLE TRANSFORMER

GENERAL ELECTRIC VOLT-PAC


Used for industrial and laboratory applications to control voltage, current, power, heat, speed, light and electromechanical force.



GENERAL ELECTRIC VOLT-PAC MODEL #9T92A ..... \$19.50  
 INPUT VOLTAGE : 120 VAC  
 OUTPUT VOLTAGE : 0 - 120  
 CONSTANT CURRENT LOAD: 4 AMPS  
 CONSTANT IMPEDANCE LOAD: 5.8 AMP  
 CYCLE: 60 HZ  
 SIZE: 4 3/8" DIA. X 4" HIGH  
 WEIGHT 6 LB.
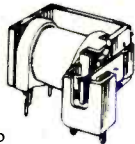
## PCTTER & BRUMFIELD RELAYS

T90 series low cost, 30 amp, DC coil PC board relay.



P&B RELAY-P/N T90NID1215-02  
 12 TO 15 VDC, SPST, NORMALLY OPEN  
 HORIZONTAL MOUNT, OPEN FRAME, 430 OHM  
 COIL RESISTANCE, CONTACT RATING 30 AMP  
 @ 250 VAC. BRAND NEW, P&B BOXED

EACH \$5.95; 10 for \$50.00; 100 for \$400.00.

## Printed Circuit RELAYS

BY P&B  
 New Nylon  
 Dust Cover  
 P.C. solder  
 terminals. No stud  
 mounting



24 VDC 4 PDT  
 P&B KHC17D11 24 VDC coil  
 650 Ohms 900 mW Gold flashed  
 4 PDT contacts Rated 3 Amps @  
 120 VAC or 30 VDC resistive.  
 Size: 19/32 x 19/32 x 1 1/4" high

## PRICE

\$1.39  
 10 for \$12.50  
 100 for \$100.00



PART # UBULJ682MTA  
 6800 UF - 63V  
 SIZE: 2.5"L X 1.187" DIAM.

PRICE  
 \$2.95

RADIAL LEADS

## Electrolytic Capacitor

## Solid-State

Opto-isolated solid state relay features synchronous zero crossover switching



## HEINEMANN

HEINEMANN MODEL #241-10A-140  
 BRAND NEW INDIVIDUALLY BOXED  
 SIZE: 2"L X 1"W X 3/4"H  
 INPUT = 3-32 VDC OUTPUT 140VAC 10AMP  
 CONNECTIONS 1/4" MALE TAB

.....\$6.00  
 10 for \$50.00



.....\$ .98  
 10 for \$7.50

AC BUZZER. Operates on 115 VAC  
 50/60 Hz. .08 amp. Mounts in 1.850"  
 round hole. Dimensions: 2" max. dia.  
 x 1" deep.



\$4.50 EA.  
 .6 @ \$4.00 EA.

MALLORY TYPE CGS  
 MADE IN U.S.A.  
 2900 UF 200 VDC  
 MAX SURGE 250 VDC  
 POS ± 85 C  
 5 3/4" HIGH X 2" DIA  
 3200 PCS. IN STOCK



TYPE CGS

COMPUTER-GRADE CAPACITORS

## EMI Suppression Filters

MURATA ERIE NORTH AMERICA, INC.

Type	Min. Cap.	WVDC @ 85°C
1250-003	1500pf	200

Minimum attenuation: 50 dB from  
 200 MHz to 10GHz. Includes  
 lockwasher, nut.

.....\$1.50  
 10 for \$12.50



## opto-22

AC OUTPUT MODULE (Black Module)



INPUT VOLTAGE: 3-8VDC MODEL # OAC5  
 MAX INPUT CURRENT: 16MA AT 5V  
 SWITCHING VOLTAGE  
 (OUTPUT VOLTAGE): 24-280 VAC  
 PEAK REPETITIVE VOLTAGE: 500V .....\$2.49 each  
 LINE FREQUENCY 50/60 HZ 10 for \$20.00  
 LOGIC VOLTAGE 5V 100 for \$175.00

To Order Call: (607) 723-3111

FAX: 24 HOURS (607) 723-5202

PHONE, MAIL OR FAX IN YOUR ORDER TODAY

SERVING MINIMUM ORDER—\$30.00

• INDUSTRY • SCHOOLS • HOBBYISTS  
 • EXPERIMENTORS • CONSUMERS

CALL FOR A FREE Catalog


OPEN ACCOUNT

C.O.D.

CHECK w/ORDER

CREDIT CARDS

CIRCLE 284 ON FREE INFORMATION CARD

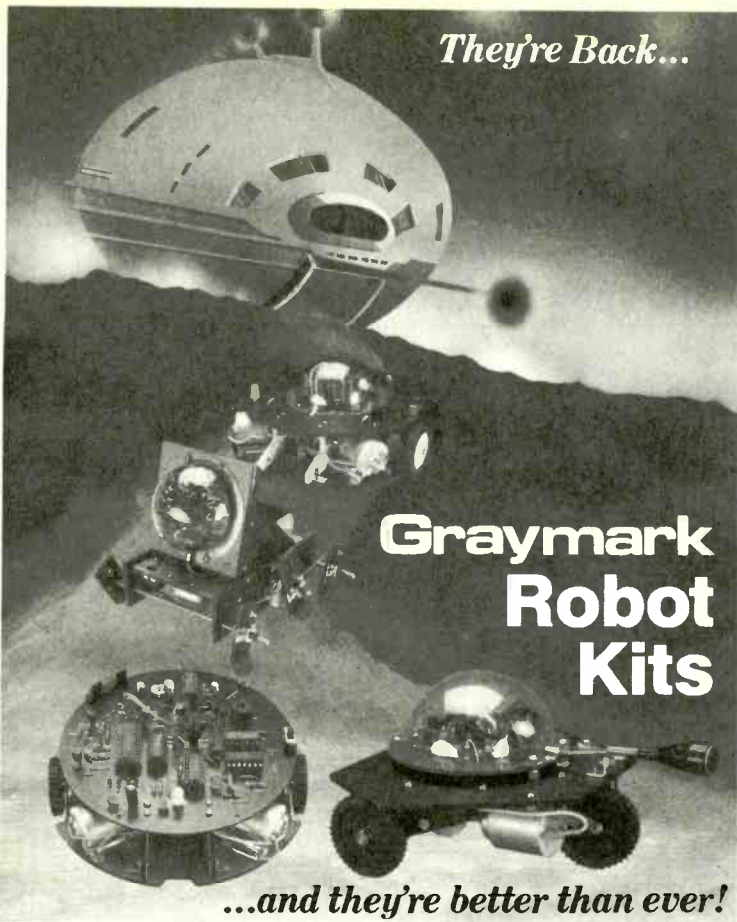

They're Back...

# Graymark Robot Kits

...and they're better than ever!

# NEW!

- ✓ Lower Prices
- ✓ Improved Designs
- ✓ More Action
- ✓ New Colors
- ✓ Refined Books

Each Robot Kit teaches different principles and applications of electronics & robotics. You do ALL electronic & mechanical assembly using an academic-level 2-color Instruction Book.

**601A "Scooter" Sound Controlled Robot \$18.95**  
 ▶ FLUORESCENT RED ▶ FAST-PACED EXCITEMENT

**602A "Blinky" Pathfinder Robot \$36.95**  
 ▶ BLACK & FLUORESCENT YELLOW ▶ BIGGER PCB  
 ▶ POWER SWITCH ON PCB ▶ RED & GREEN LEDS

**603A "Copycat" Programmable Robot \$57.35**  
 ▶ TACTILE RESET SWITCH ▶ POWER SWITCH ON PCB  
 ▶ IMPROVED CABLE CONNECTOR ▶ BETTER KEYPAD SYMBOLS ▶ CLASSIC SILVER, GRAY & BLACK

**606A "Scrambler" All Terrain Robot \$37.95**  
 ▶ EXCITING CONTEMPORARY COLORS ▶ HIGH-TECH INFRARED BEAM ▶ WALKS OVER ROUGH TERRAIN

**Call for Free 40 page CATALOG.**  
**Mention Radio Electronics Now Shopper**  
**to receive FREE Electronics Guide**  
**Graymark 800-854-7393**

Box 5020, Santa Ana, CA 92704

CIRCLE 307 ON FREE INFORMATION CARD

## MARK V ELECTRONICS, INC.

Competitive Prices \* Fast Shipping Since 1985

IN CA 1-800-521-MARK (orders only)  
 OUTSIDE CA 1-800-423-FIVE (orders only)  
 ORDER BY FAX (213) 888-6868  
 CATALOG & INFORMATION (213) 888-8988

▲ Indicates the level of difficulty in the assembling of our Products. ▲ Beginner ▲▲ Intermediate ▲▲▲ Advanced ★ Fully Assembled  
 Special offer will be given to the purchase of Amplifier + Metal Cabinet + Power Transformer:

New

**300W MOSFET AUDIO MONO POWER AMPLIFIER**  
**AF-3 ▲▲▲**



Power output: 300W into 4 ohms (0.1% THD), 200W into 8 ohms (0.02% THD). • Frequency Response: 10 Hz - 20 KHz. • Total Harmonic Distortion Less than 0.03%. • Input Sensitivity and Impedance at 1 KHz, IV 47K Ω. • Load Impedance: 4 - 16ohms. • Power Requirements: ±55 to ±65V OC 8 A • (Each Channel). • Dimensions: 287 x 205 x 60 mm.

Kit: \$185.00  
 Assembled & Tested: \$195.00

**120 W MOSFET POWER AMPLIFIER (MONO)**  
**TA-477 ▲▲**



T.H.D.: Less Than 0.007% • Power output: 120 watts into 8 ohms RMS • Frequency response: 8 Hz to 20KHz. • 0-0.4 dB 2 B Hz to 65 KHz. • 0-3dB • Sensitivity: 1V • Power requirements: 55 VDC @ 3 amps. May use Mark V Model 003 Transformer.

Kit: \$68.00  
 Assembled & Tested: \$85.00

**120W + 120W LOW TIM PRE-MAIN STEREO AMP.**  
**TA-800MKII ▲▲**



Power Output: 120 watts each channel into 4 ohm load. 72 watts each channel into 8 ohm load. Frequency response: 10 to 20 KHz. Total harmonic distortion: Less than .01%. Tone control: Bass: ± 12dB. Mid: ± 8dB. High: ± 8dB. Sensitivity: Phono input, 3mv into 47K Ω. Line. 3v into 47K Ω. Signal to noise ratio: 86 dB. Power requirement: DC: ± 40 VDC at 3.2 A. 8 ohm load. DC: ± 40 VDC at 5.4 A. 4 ohm load. AC: 28 VAC-0-28VAC at 6.5 A with 8 ohm load. AC: 28 VAC-0-28VAC at 10.8 A with 4 ohm load.

Kit: \$63.92

**100W + 100W NEW CLASS A DC STEREO PRE AND MAIN AMP**  
**TA-1500 ▲▲▲**



Power output: 80 watts per channel into 8 ohms 100 watts per channel into 4 ohms • Total harmonic distortion: Less than 0.03% Frequency response. Aux input: 5 to 50,000 Hz • 0.2dB. -2 dB • Frequency response. Power amplifier Section. DC to 200 KHz • Sensitivity Phono: 2.5 mV @ 47 K Ω. 150 mV @ 47K Ω. Mic: 6 mV @ 10 K Ω. Output: Tape 150 mV @ 47 K Ω. Preamp: 1V @ 600 ohms • Power transformer: 25V to 32 V AC x 2 @ 8 A (Mark V Model 001) • P.C. Board Dimensions: 10.5" x 6.13" x 2.25" • Heat sink 5.13" x 2.63" x 3" (Each) Use rack mount cabinet LG 1924 or LG 1925

Kit: \$73.70  
 Assembled & Tested: \$95.81

**80W + 80W PURE DC STEREO MAIN POWER AMPLIFIER**  
**TA-802 ▲▲**



Power output: 80 watts per channel into 8 ohms Total harmonic distortion: Less than 0.05% at rated power. Intermodulation distortion: Less than 0.05% at rated power Frequency response: DC to 200 KHz. -0db. -3dB. @ 1 watt Power requirements: 30 VAC x 2 @ 6 amp. May use Mark V model 001 transformer P.C. Board: 8-1/2" x 5" x 1-1/8" Heat sink: 5-1/8" x 2-5/8" x 3" (Each)

Kit: \$45.94  
 Assembled & Tested: \$59.72

**120W + 120W AC/DC STEREO HI-FI & PRE-AMP.**  
**SM-720 ▲▲★**



Power Output: 120W Peak music power output per channel. Input Sensitivity: Tape 300 mv, Aux 300 mv, Phono 3 mv, Mic 3 mv. Tone control range: Treble ± 8 dB, Bass ± 8 dB. Frequency Response: 20 Hz to 20 KHz. Power Requirements: 110 VAC, 220 VAC, 50/60 Hz 12 to 16 VDC. Dimensions: 272 x 208 x 80 mm 10 5/8 x 8 1/8 x 3 1/8 inch.

Complete Kit: \$75.00  
 Assembled & Tested: \$89.00

**VIDEO/AUDIO SURROUND SOUND PROCESSOR**  
**SM-333 ▲▲★**



Complete Kit: \$73.00  
 Assembled & Tested: \$85.00

**60W + 60W STEREO POWER AMPLIFIER (WITH MIC. INPUT)**  
**SM-302 ▲▲★**



Complete Kit: \$73.00  
 Assembled & Tested: \$85.00

Frequency response: 20 Hz to 20KHz • Total harmonic distortion: Front channel: 0.05%. Rear channel: Less than 0.25% • Input signal voltage: 0.1 to 3.5V • Output: Front channel: 0.1 to 3.5V • Output: Rear channel: 0.1 to 3.5V • • Rear channel: 6.6V • Delay time: 5 to 50 milliseconds • Input impedance: 47 K Ω • Power requirements: 100-120 VAC. 60Hz • Dimensions: 14.2" wide. 4.82" deep. 2.1" high

Frequency response: 20Hz to 20 KHz • Total harmonic distortion: < 0.1% • Power output: 60W per channel into 4 ohm load • 33W per channel into 8 ohm load • Input sensitivity: Mic 10mv • Hi 380mv • Lo 640mv • Signal to noise ratio: Better than 70 db • Power consumption: 100W. Dimension 360 mm x 75 mm x 200 mm

We provide transformers for most our Mark V amplifier kits.



Rack Mount Metal Cabinets with aluminium panel are suitable for many projects and most of our kits.

We accept VISA, MasterCard, Money Order, Check, and C.O.D. (over \$6.50). Minimum order is \$20.00. We ship by UPS ground inside US (over \$4.00) and ship by US Mail outside US. Please note: some components are made in other countries. All prices include shipping and handling charges. Quality of material discount available upon request. Residents of CA pay tax and add \$2.00. • Express Order is extra. Shipping Prices are subject to change without prior notice. We are not responsible for typographical errors.

**MARK V ELECTRONICS, INC. - 8019 E. Slauson Ave, Montebello, CA 90640**



Business & Showroom hours (Pacific Time)  
 Mon. thru Fri. 9:30 am to 5:00 pm  
 Sat. 10:00 am to 5:00 pm


CIRCLE 292 ON FREE INFORMATION CARD



# DANBAR SALES COMPANY

870 W CIENEGA AVENUE, SUITE 1  
SAN DIMAS, CA 91773

\*\*\*\*\*  
(909) 592-2940 FAX (909) 592-9518
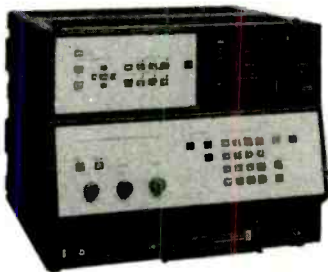
<p><b>TEKTRONIX 7623A</b></p> <p>Storage Oscilloscope, 100 MHz BW. Comes with the following plug-ins 7A26, 7A26 and 7B53A.</p> <p><b>\$1075.00</b></p>	<p><b>TEKTRONIX 576</b></p> <p>Curve Tracer, tests two and three terminal discrete semiconductors. Power capability up to 220 w. Convenient scale factor readout. Accepts test fixtures.</p> <p><b>\$2650.00</b></p>	<p><b>HEWLETT-PACKARD 141T W/ 8555A AND 8552B</b></p> <p>Spectrum Analyzer mainframe with broadband RF Section, .01 to 18 GHz and high resolution IF section.</p> <p><b>\$3200.00</b></p>
<p><b>HEWLETT-PACKARD SWEEP OSCILLATOR MAINFRAMES AND PLUG-INS.</b></p> <p>8620A Mainframe \$600.00 8620C Mainframe \$850.00 86222A 10MHz-2.4 GHz NEW \$2750.00 86222B 10MHz-2.4 GHz \$2300.00 86230B 1.8-4.2 GHz \$1200.00 86235A 1.7-4.3 GHz \$1150.00 86240A 2-8.4 GHz \$1350.00 86260A 12.4-18.0 GHz \$1100.00 86290A 2-18.0 GHz \$2650.00 86290B 2-18.6 GHz \$3250.00</p>	<p><b>HEWLETT-PACKARD 853A/8558B SPECTRUM ANALYZER</b></p> <p>Spectrum Analyzer plug-in, .1 to 1500 MHz, 1 kHz resolution, -117 to +30 dBm dynamic range. Comes in a 853A Spectrum Analyzer Display.</p> <p><b>SPECIAL \$5700.00</b></p>	<p><b>HEWLETT-PACKARD 3586B</b></p> <p>Selective Level Meter makes carrier measurements to 32.5 MHz, voice channel measurements from 50 Hz to 100 kHz, works with the 3336B level generator. Options available.</p> <p><b>SPECIAL \$2000.00</b></p>
<p><b>TEKTRONIX 485</b></p> <p>350 MHz Portable Oscilloscope, dual trace, 1 nS/div sweep rate, 2.0 div nS writing speed, switchable input impedance.</p> <p><b>\$1300.00</b></p>	<p><b>TEKTRONIX 7603</b></p> <p>100 MHz Oscilloscope Mainframe CRT readout, has the following plug-in; 7A18, 7A18 and 7B53A. Includes all manuals.</p> <p><b>\$975.00</b></p>	<p><b>HEWLETT-PACKARD 8565A</b></p> <p>10 MHz to 22 GHz range with internal mixing, internal preselection 1.7 to 22 GHz, wide choice of resolution bandwidths, simple three knob operation.</p> <p><b>\$7750.00</b></p>
<p><b>TEKTRONIX 7904</b></p> <p>500 MHz Oscilloscope mainframe with the following plug-ins. 7A24 dual trace amplifier, 7A26 dual trace amplifier, 7B85 delaying time base, 7B80 delaying time base. Includes a manual for each plug-in.</p> <p><b>\$2000.00</b></p>	<p><b>WANDEL &amp; GOLTERMANN TSA-1</b></p>  <p>Frequency Range 100 Hz to 180 MHz 5 modes of measurement. Spectrum analysis, network analysis, phase jitter, selective level, demodulation. New cost \$ 40. K.</p> <p><b>\$2750.00</b> Same as above but includes network analyzer <b>\$3550.00</b></p>	<p><b>HEWLETT-PACKARD 3336B</b></p> <p>Synthesized Level Generator, Bell STD, frequency coverage is 10 Hz to 21 MHz making the 336B useful for telephone circuit loop testing on most FDM systems. Options are available.</p> <p><b>SPECIAL PRICE \$950.00</b></p> <p><b>TEKTRONIX 7B53A</b></p> <p>Dual Time Base, 5nS to 5S/div sweep rates, CRT readout, delaying sweep. NEW, calibrated with manual.</p> <p><b>* NEW * \$300.00</b></p>

WANTED: ELECTRONIC TEST EQUIPMENT!  
CALL OR FAX US YOUR LIST.

PLEASE CALL OR WRITE FOR OUR UPCOMING CATALOG.

WE ACCEPT VISA AND MASTERCARD



**CALL TOLL FREE**  
**1-800-292-7711**  
**1-800-445-3201 (Can.)**

# TEST EQUIPMENT AT DISCOUNT PRICES

**48 HOUR  
 SHIPPING**

## DIGITAL METERS



**Dual-Display  
 LCR Meter  
 w/ Stat Functions  
 B+K Model 878**  
**\$239.95**  
 Auto / Manual Range  
 Many Features  
 with Q Factor  
 High Accuracy



**Digital Multimeter  
 w/ Inductance  
 & Capacitance**  
**\$75.00**  
**LCM-1850**  
 Ten Functions  
*by Elenco*



**Digital Capacitance Meter  
 CM-1550B**  
**\$58.95**  
 9 Ranges  
 .1pf-20,000ufd  
 .5% basic accy.  
 Zero control w/ Case  
 Big 1" Display  
*by Elenco*



**The Survivor  
 Model 2860**  
**\$89**  
 B+Ks Best DMM  
 Large 3-1/2 Digit  
 Rugged  
 Construction  
 Full Featured

**Fluke Multimeters**  
 Model 12 ..... \$79.95  
 Model 701I ..... \$65.00  
 Model 771I ..... \$145.00  
 Model 791I ..... \$169.00  
 Model 87 ..... \$289.00  
 Model 93 ..... \$1,095.00  
 Model 97 ..... \$1,695.00  
**All Models Available - Call**

## QUALITY AMERICAN MADE POWER SUPPLIES

**Digital Triple Power Supply  
 XP-765**  
**\$289**  
 0-20V @ 1A  
 0-20V @ 1A  
 5V @ 5A  
 Fully regulated, Short circuit protected  
 with 2 limit control, 3 separate supplies  
**XP-660 with Analog Meters \$195**

**12A DC Power Supply  
 B+K 1686**  
**\$169.95**  
 3-14V @ 12A  
 Fully regulated & protected  
 Separate Volt & Current Meters  
 Current Limiting, Low Ripple

**Quad Power Supply XP-580**  
**\$69.95**  
 2-20V @ 2A  
 12V @ 1A  
 5V @ 3A  
 -5V @ .5A  
 Fully regulated and short circuit protected

**Triple Power Supply XP-620**  
**Assembled \$75  
 Kit \$49.95**  
 2 to 15V @ 1A,  
 -2 to -15V @ 1A  
 (or 4 to 30V @ 1A)  
 and 5V @ 3A  
 All the desired features for doing experiments.  
 Features short circuit protection, all supplies.

## GENERATORS & VIDEO PRODUCTS

**Function Generator  
 Blox  
 #9600**  
**\$28.95**  
 Provides sine, triangle, square wave  
 from 1Hz to 1MHz  
 AM or FM capability  
**Kit \$26.95**

**Color Convergence Generator  
 SG-250**  
**\$89.95**  
**Kit \$69.95**  
 Finest in the industry  
 10 rock steady patterns  
 RF & Video output

**Wide Band Signal  
 Generators  
 SG-9000**  
**\$129**  
 RF Freq 100K-450MHz AM Modulation  
 of 1KHz Variable RF output  
**SG-9500 w/ Digital Display &  
 150MHz built-in counter \$249**

**Sweep/Function Generator  
 with Freq. Counter**  
**\$259**  
**Model GF-8026**  
 Int/Ext Operation,  
 Sine, Square, Triangle, Pulse,  
 Ramp, .2 to 2MHz, Freq Counter .1-10MHz

## EDUCATIONAL KITS - FUN & EASY TO BUILD

**Robotic Arm Kit**  
  
**Model Y-01 \$48.95**  
 Teaches basics of robotics. Arm  
 grabs & releases, lifts & lowers, &  
 pivots from side to side

**Digital Multimeter Kit  
 with Training Course  
 Elenco Model  
 M-2665K**  
**\$49.95**  
 Fun & Easy  
 to Build  
 Ideal School  
 Project  
 Full Function 34 Ranges, Includes  
 Capacitance, Transistor/Diode Testing  
 20Amp AC/DC, Extra Large Display

**Multi-Function Counter**  
**Elenco  
 F-1200**  
**\$229**  
 1.2GHz  
 Measures Frequency, Period, Totalizer  
 8 LED digits, Crystals Oven Oscillator  
 .5ppm Accuracy

**AM/FM Transistor  
 Radio Kit  
 with Training Course  
 Model AM/FM 108**  
**\$27.95**  
 14 Transistors ♦ 5 Diodes  
 Easy to build because  
 schematic is  
 printed right on the PCB  
**Makes a great school project**  
**Model AM 550 AM Only \$17.95**

**Learn to Build and Program  
 Computers with this kit**  
 Includes: All Parts,  
 Assembly and  
 Lesson Manual  
**Model  
 MM-8000**  
**\$129.00**  
 Starting from scratch you build a complete system.  
 Our Micro-Master trainer teaches you to write into  
 RAMs, ROMs and run a 8085 microprocessor, which  
 uses similar machine language as IBM PC.

**XK-500 Digital / Analog Trainer**  
 A complete mini-lab for building, testing, prototyping analog and digital circuits  
 Elenco's Digital/Analog Trainer is specially designed for school projects, with 5 built-in power  
 supplies. Includes a function generator with continuously variable, sine, triangular, square wave  
 forms. All power supplies are regulated and protected against shorts.  
**\$159.95 Assembled \$129.95 Kit**

- Power Supplies**
- Variable Power Supply
  - +1.25 to 20VDC @ 5 Amp (+1.25 to 15VDC @ 1 Amp)
  - -1.25 to -20VDC @ 5 Amp (-1.25 to -15VDC @ 1 Amp)
  - +12VDC @ 1 Amp
  - -12VDC @ 1 Amp
  - +5VDC @ 1 Amp
  - 30VAC Center tapped @ 15VAC at 1 Amp
- Analog - Section**
- Function Generator Sine, Triangular, Square wave forms
  - Frequency adjustable in five ranges from 1 to 100KHz
  - Fine frequency adjust
  - Amplitude adjust
  - DC offset
  - Modulation FM-AM
- Digital - Section**
- Eight data switches
  - Two no bounce logic switches
  - 8 LED readouts TTL buffered
  - Clock frequency 1 to 100KHz
  - Clock amplitude 5VPP square wave
- Breadboards**
- 2 breadboards, each contain: 840 tie points (total 1,680)



**WE WILL NOT BE UNDERSOLD**  
 UPS SHIPPING: 48 STATES 5%  
 IL RES 7.5% TAX (\$3 min \$10 max)  
 OTHERS CALL

**C&S SALES INC.**  
 1245 ROSEWOOD, DEERFIELD, IL 60015  
 FAX: 708-520-0085 • (708) 541-0710



**15 DAY MONEY BACK GUARANTEE**  
**FULL FACTORY WARRANTY**  
**WRITE FOR FREE CATALOG**  
 PRICES SUBJECT TO CHANGE



**LOWEST  
PRICES  
GUARANTEED**

# ELENCO & HITACHI & B+K SCOPES AT DISCOUNT PRICES

**48 HOUR  
SHIPPING**

## ELENCO S-1325



25MHz \$349  
2 Channel


S-1340 40MHz  
Dual Trace Oscilloscope



- High luminance 6" CRT
- 1mV Sensitivity
- 10KV Acceleration Voltage
- 9ns Rise Time
- X-Y Operation

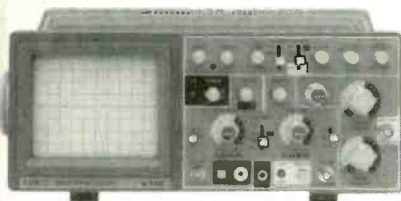**\$495**

S-1360 60MHz  
Dual Trace - Delayed Sweep



- Automatic Beam Finder
- Built-in Component Tester
- 1mV Sensitivity
- Dual Time Base
- Illuminated Internal Gradicule


**\$775**

DS-203 20MHz, 10MS/s  
Digital Storage Oscilloscope

- 2K Word Per Channel
- Plotter Output
- 8 Bit Vert. Resolution
- 2048 Pts Hor. Resolution
- Much More

**\$775**

## B+K 2120

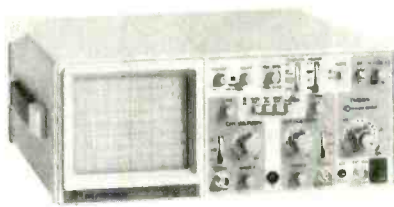

20MHz \$395 Model 2125 \$539.95  
2 Channel Delayed Sweep

40MHz DUAL-TRACE  
Model 1541B

**749.95**

- 1mV/div sensitivity
- Video sync separators
- Z axis input
- Single sweep
- V mode-displays two signals unrelated in frequency

60MHz DUAL-TRACE  
Model 2160

**949.95**

- 1mV/div sensitivity
- Sweep to 5 ns/div
- Dual time base
- Signal delay line
- V mode-displays two signals unrelated in frequency
- Component tester

100MHz THREE-TRACE  
Model 2190

**1,395.95**

- 1mV/division sensitivity
- Sweeps to 2ns/division
- Dual time base
- Calibrated delay time multiplier
- Signal delay line
- 19kV accelerating voltage

20MHz ANALOG  
WITH DIGITAL STORAGE  
Model 2522

**869.95**

- 20MHz analog bandwidth
- 10MS/s sampling rate
- 2k memory per channel
- 20MHz equivalent time sampling
- Pre-trigger capture

1.0GHz PORTABLE  
SPECTRUM ANALYZER  
Model 2610

**2,595.95**

- AC/DC operation (battery included)
- 70dB dynamic range
- Resolution bandwidth of 10kHz
- 50Ω and 75Ω input impedance (switch selectable)
- Fixed bandwidth setting for viewing TV signals
- Field calibratable with internally generated 100MHz, 80dB signal

## SPECIAL BUY HITACHI V-212



20MHz \$409  
2 Channel

Hitachi Popular Series

V-525 - 50MHz, Cursors	\$975
V-523 - 50MHz, Delayed Sweep	\$949
V-522 - 50MHz, DC Offset	\$849
V-422 - 40MHz, DC Offset	\$749
V-222 - 20MHz, DC Offset	\$625

Hitachi Compact Series Scopes


V-660 - 60MHz, Dual Trace	\$1,095
V-665A - 60MHz,DT, w/cursor	\$1,325
V-1060 - 100MHz, Dual Trace	\$1,375
V-1065A - 100MHz, DT, w/cursor	\$1,649
V-1085 - 100MHz, QT, w/cursor	\$1,995
V-1100A - 100MHz, Quad Trace	\$2,195
V-1150 - 150MHz, Quad Trace	\$2,695

Hitachi RSO Series

RSO's feature; roll mode, averaging, save memory, smoothing, interpolation, pretriggering, cursor measurements.

VC-6023 - 20MHz, 20MS/s	\$1,650
VC-6024 - 50MHz, 20MS/s	\$1,950
VC-6025A - 50MHz, 20MS/s	\$2,350
VC-6045A - 100MHz, 40MS/s	Call
VC-6145 - 100MHz, 100MS/s	Call

Logic Analysers

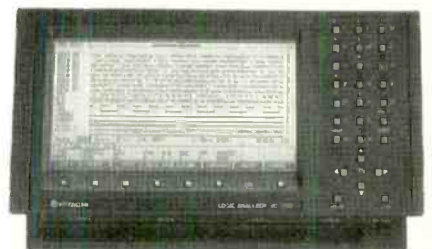

- 32 channels (VC-3120) or 48 channels (VC-3130)
- 25MHz synchronous operation on all channels
- 100MHz asynchronous operation (8 or 12 channels)
- 5ns glitch capture capability
- Multi-level trigger sequencing
- Non-volatile data and set-up memories
- Disassembler options for popular uPs
- Very low cost - Call
- 9 inch LCD screen

C&S SALES INC.

1245 ROSEWOOD, DEERFIELD, IL 60015  
FAX: 708-520-0085 • (708) 541-0710



CALL TOLL FREE 1-800-292-7711  
1-800-445-3201 (Can)

PROBES INCLUDED IN ALL SCOPES & METERS

15 DAY MONEY BACK GUARANTEE  
FULL FACTORY WARRANTY  
WRITE FOR FREE CATALOG

CIRCLE 285 ON FREE INFORMATION CARD

www.americanradiohistory.com

52A53

March 1993, Electronics Now


\$449<sup>95</sup>

# Device Programmers

\$139<sup>95</sup>

48 PIN ZIF

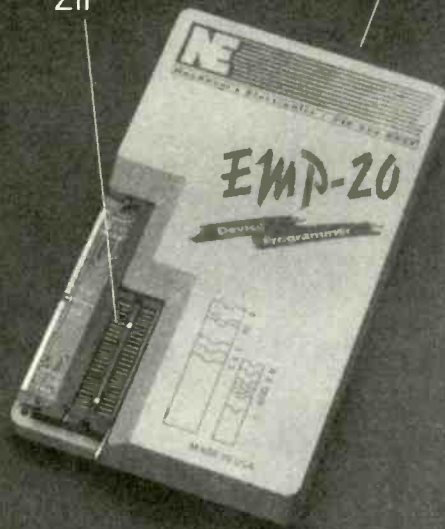Connects to standard PC parallel printer port



9 1/2 x 5 3/4 x 1 1/4

**EMP-20**

• Easy to use software, on-line help, full screen editor

• **Fast Programming (EMP-20)**

27C010A, 23 seconds

28C020, 34 seconds

27C040, 95 seconds

• **Made in USA**

• 1 Year Warranty

• Technical Support by phone

• 30 day Money Back Guarantee

• FREE software upgrades available via BBS

• Demo SW via BBS (EM20DEMO.EXE) (PB10DEMO.EXE)


• E(e)proms 2716 - 8 megabit, 16 bit 27210-27240, 27C400 & 27C800,

• Flash 28F256-28F020, (29C256-29C010 (EMP-20 only))

• Micros 8741A, 42A, 42AH, 48, 49, 48H, 49H, 55, 87C51, 87C51FX, 87C751,752

• GAL, PLD from NS, Lattice, AMD-16V8, 20V8, 22V10 (EMP-20 only)

## PB-10 Internal Card for PC

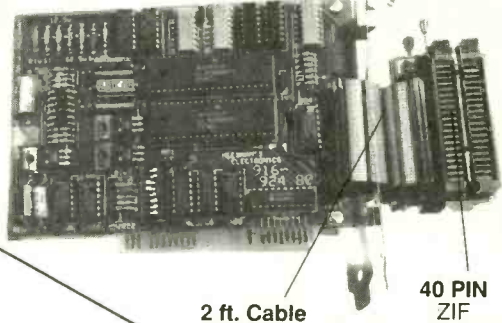

2 ft. Cable

40 PIN ZIF

**FOR MORE INFORMATION CALL**

4539 Orange Grove Ave.

Sacramento, CA 95841

(Monday-Friday, 8 am-5 pm PST)

**NEEDHAM'S ELECTRONICS, INC.**



C.O.D.



**(916) 924-8037**

**BBS (916) 972-8042**

**FAX (916) 972-9960**

CIRCLE 257 ON FREE INFORMATION CARD

# BATTERIES

# REPLACEMENT BATTERIES


(ALL NEW - MADE IN USA)

## ICOM

7S 13.2v 1200 mah \$59.00  
8S 9.6v 1200 mah \$59.00  
BP7 13.2v 600 mah \$59.00  
BP8 8.4v 1000 mah \$59.00  
SA/SAT  
BP82, BP83  
BP83A 7.2v 750 mah  
BP84 7.2v 1000 mah  
BP85A 9.6v 600 mah  
BP85B 12v 600 mah



## KENWOOD

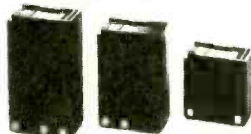

PB1 12v 1000 mah \$59.00  
KNB4 7.2v 2200 mah \$59.00  
PB6 7.2v 750 mah \$46.00  
PB7 7.2v 1500 mah \$55.00  
PB8 12v 750 mah \$55.00

## MOTOROLA

HT300 7.2v 1600 mah \$45.00  
HT90 12v 600 mah \$34.00  
HT440 12v 600 mah \$39.00  
MT500 15v 500 mah \$39.00

## RADIUS

P-10 500 mah \$28.00

## SABER

7.2v 1100 mah \$59.00

## CAMCORDER

JVC  
PANASONIC  
PVBP80/88 12v 2.3 amps  
RCA/HITACHI  
Full size  
VHS-C  
SONY  
NP22  
NP55/77  
ALL BRANDS AVAILABLE

## YAESU

FNB-2 v 500 mah \$21.00  
FNB-2 v 600 mah \$23.00  
FNB-4A  
FNB-10  
FNB-10S 7.2v 1000 mah \$43.00  
FNB-12  
FNB-12S 12v 600 mah \$45.00



## SPECIALS

### ICOM-SA/SAT

ICOM-72A CHARGER WITH  
BP-84 (Equiv.)—3" High  
7.2v @ 1000 MAH \$135.00  
or  
BP-85B (Equiv.) 3" High  
12v @ 600 MAH \$164.00

## INSERTS

### KENWOOD

BP-21 \$13.00, BP-25, 26- \$20.00



### ICOM

BP-3 \$17.00, BP-5 \$22.00  
BP-7, BP-8

## CELLULAR

MITSUBISHI \$60.00  
NEC \$45.00  
NOVATEL \$45.00  
PANASONIC \$45.00  
Bag Phone Kits \$55.00  
MOTOROLA  
"FLIP" \$60.00



\* ALL BATTERY PACKS - GUARANTEED TO HAVE THE ADVERTISED CAPACITY

SEND FOR  
FREE CATALOG  
DEALER INQUIRIES  
WELCOME

**BATTERY-TECH, INC.**  
28-25 215 PLACE, BAYSIDE, N.Y. 11360 • FAX 718-461-1978  
800-442-4275 - N.Y.S. 718-631-4275



MASTER CARD

Electronics Now, March 1993





# ELECTRONIC GOLDMINE

Minimum order: \$10.00 plus \$3.50 S&H. We accept MC, VISA and Money Orders.

CALL OR SEND FOR OUR FREE CATALOG!

## s p e a k e r s

## SPECIALS

### 5" FULL RANGE SPEAKER

Good quality 5" speaker with 6 ounce magnet and 8 ohm voice coil. Rated 8 watt RMS (12 watt peak). Great for compact applications.



G3209 \$4.95

### 4"x 6" COAXIAL

Great for many types of auto or home applications. Features built in piezo tweeter, dust cover and 8 ohm 15 watt peak rating.



G3213 \$8.00

### 6"x 8" UNIVERSAL AUTO SPEAKER


Great for replacement or new construction this speaker is rated 8 watts, 6 ounce magnet and 4 ohm impedance. Standard mounting for many FORD cars. Has built in dust screen.



G3210 \$4.75
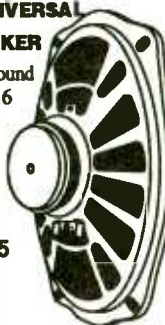
### 6"x 9" UNIVERSAL AUTO SPEAKER

Universal auto sound speaker features 6 ounce ceramic magnet, 8 watt 4 ohm voice coil and built in dust screen.



G3211 \$5.95

### SUPER WOOFERS

#### 5" SUPER SUBWOOFERS

(Pincussion Mount) Heavy duty in a very compact size! Features 1 1/4 aluminum voice coil, massive 20 ounce ceramic magnet, 4 ohm impedance, 50 watt RMS (75 watt peak) power. Response to 400 HZ vented backplate, air suspension edge and dust screen.




G3212 \$21.95

### POWER WOOFERS

GUITAR, STEREO AND AUTO APPLICATIONS

SIZE	RATING	VOICE COIL	MAGNET	STOCK#	PRICE
12" dia	100W 200W	2" 4Ω	30 oz	G3217	\$35.00
15" dia	150W 300W	2 1/2" 8Ω	56 oz	G3218	\$59.00
*15" dia	200W 400W	3" 8Ω	95 oz	G3219	\$100.00

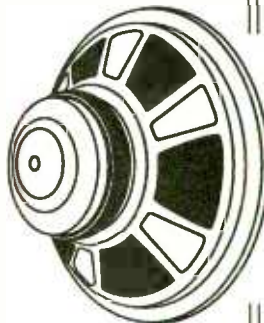\* massive cast frame-this is our most powerful speaker



### 2 WAY 75 WATT PEAK SPEAKER SYSTEM COMPONENTS

Consists of a 10" 16 ounce magnet, cloth roll, air suspension, 8 ohm woofer, a 3" square tweeter and a press fit quick connect terminal with 75 watt crossover. These were made by Pioneer for a custom manufacturer. You make your own enclosure and save a bundle. All 3 components for one low price!



G3208 \$29.95



### MISC. SMALL SPEAKERS

SIZE	IMP	WATT	STOCK	PRICE
1 3/4"	32Ω	.15	G3214	\$1.00
2 1/4"	32Ω	.25	G3215	.89
2 1/2"	8Ω	.2	G939	1.29
2 5/8"	4Ω	.3	G2851	1.50
3" dia	16Ω	.5	G3216	.75
4x6"	8Ω	.6	S2208	3.95



### COMBO TV/VCR REMOTE

Hand held remote made by zenith. We just got these in and have no other info except that they have a few scratches on the case. As is.



G2555 \$1.00

### COPPER CLAD BLOWOUT

Great for making high quality PC boards. These are standard glass epoxy double sided copper clad blanks. Size is an incredible 12"x12". Each panel is large enough to make many smaller PC boards.



A SUPER VALUE.

G2869 \$2.00

### BRIGHT ORANGE LED

Jumbo T1 3/4 diffused lens, orange LED.



G2554 10/\$1.00  
100/\$9.00  
1000/\$70

### STROBE TUBE & SCHEMATIC

Bright xenon tube for making strobe lights.




Size: 1.5"

G936 \$1.39

## BOOSTER AMPS
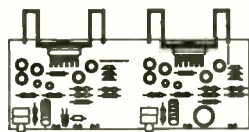
### 20W + 20W STEREO AMP KIT


Two separate high power amps on one PC board put out an incredible 20 watts RMS each. Features low distortion circuitry. Great stereo booster amp for your car sound system. Use with any speakers capable of handling at least 20 watts. Operates on 12VDC. Size of board: 6"x2.25"



C6442 \$19.95
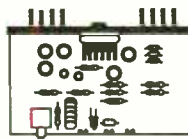
### 20 WATT RMS MONO AMP KIT


High power amp for various booster applications. Kit features short and open circuit protection and very low distortion (1% or less). Has red LED "on" indicator and will boost any tuner, radio, cassette or CD player to room filling volume! Operates from 12 VDC. Size of board: 3.75"x2.1". Complete with parts, PC board and instructions.



SKILL LEVEL 2  
C6444 \$14.95
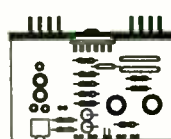
### 10W + 10W STEREO AMP KIT

Similar to the 20W+20W stereo amp only this one puts out 10 Watts RMS to each channel. Features one level control that sets level in both channels and red LED "on" indicator. Use this amp with your speakers to boost portable tape players, radios or CD players to room filling volume. Operates from 12VDC. Size of board: 3.75"x2.25". Complete with all parts, PC board and instructions.




SKILL LEVEL 2  
C6443 \$16.95

ELECTRONIC GOLDMINE ■ PO Box 5408 ■ Scottsdale, Arizona 85261 ■ (602) 451-7454

CIRCLE 241 ON FREE INFORMATION CARD



**Digital Storage scopes**

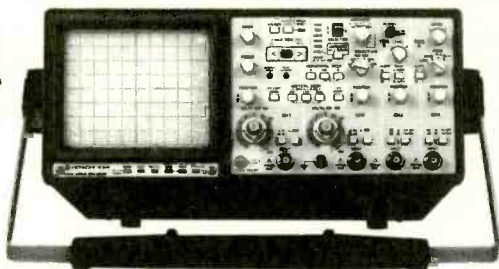

MODEL	DESCRIPTION	REGULAR	SALE
VC-6023	2 Ch, 20 MHz, 20 MS/s, 2KW/Ch, RS-232 w/HPGL support	1895.00	CALL
VC-6024	2 Ch, 50 MHz, 20 MS/s, 2KW/ch, RS-232 w/HPGL support	2195.00	FOR PRICE
VC-6025A	2 Ch, 50 MHz, 20 MS/s, 50 MHz repetitive sampling, 2 KW/ch, frequency counter, RS-232 w/HPGL support	2695.00	QUOTES!
VC-6045A	2 Ch, 100 MHz, 40 MS/s, 100 MHz equivalent sampling, 4K Mem, frequency counter, RS-232 w/HPGL support	3295.00	CALL
VC-6145	4 Ch, 100 MHz, 100 MS/s (1 ch), 4KW Mem, frequency counter, RS-232 w/HPGL support	4395.00	FOR PRICE
VC-6155	2 Ch, 100 MHz, 100 MS/s (2 Ch), 4 KW Mem, frequency counter, RS-232 w/HPGL support	3995.00	QUOTES!

**PRINT™**

Products International

8931 Brookville Rd, Silver Spring MD 20910  
800-638-2020 \* 301-587-7824 \* FAX 800-545-0058



**BK PRECISION™**  
MAXTEC INTERNATIONAL CORP.


**60 MHz DUAL-TRACE**  
Model 2160



Reg. \$1099.00  
Sale \$ 874.95


**20 MHz ANALOG WITH DIGITAL STORAGE**

Model 2522

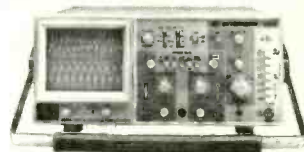

Reg. \$1050.00  
Sale \$ 882.95

**100 MHz THREE-TRACE**  
Model 2190

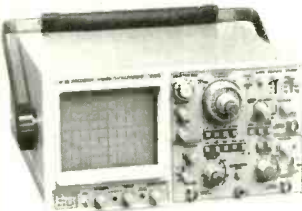

Reg. \$1645.00  
Sale \$1381.95

**1.0 GHz PORTABLE SPECTRUM ANALYZER**  
Model 2610



Reg. \$2995.00  
Sale \$2515.95

**PRINT™**

Products International

8931 Brookville Rd, Silver Spring MD 20910  
800-638-2020 \* 301-587-7824 \* FAX 800-545-0058



CIRCLE 264 ON FREE INFORMATION CARD



## LOOKING FOR TEST EQUIPMENT NIGHT VISION or ELECTRONICS?

### EQUIPMENT SPECIALS

#### TEKTRONIX MAINFRAME MADNESS STRIKES AGAIN!

- TEK 7603, 100MHz M/F with 7A18 D/T vert. amp, 7B53 T/B.....\$495
- TEK 7704, 200MHz M/F with 7A26 D/T vert. amp, 7B70 & 7B71 T/B.....\$750
- TEK 7904, 500MHz M/F with 7A26 D/T vert. amp, 7B70 & 7B71 T/B.....\$950
- TEK 7623, 100MHz Storage wuth 7A18 D/T vert. amp, 7B53 T/B.....\$995
- TEK 7633, 100MHz Storage wuth 7A18 D/T vert. amp, 7B53 T/B.....\$1295

#### PORTABLE PACKAGE DEALS

- TEK 465, 100MHz, Dual Trace, Delayed Sweep, Probe and Manual.....\$495
- TEK 465B, 100MHz, Dual Trace, Delayed Sweep, Probe and Manual.....\$575
- TEK 475, 200MHz, Dual Trace, Delayed Sweep, Probe and Manual.....\$725
- TEK 485, 350MHz, Dual Trace, Delayed Sweep, Probe and Manual.....\$995
- TEK 466/DM44, 100MHz Storage, D/T, D/S, Probe and Manual.....\$995

#### LAB POWER SUPPLIES

- TELEDYNE +15Vdc @ 300mA, Dual output, with 5 way B/P.....\$35
- TEST LEADS from E.F JOHNSON ( NEW!)
- BNC to RED & BLACK MINI HOOKS, 36" length.....\$3ea or 4 for \$10
- BNC to RED & BLACK MINI HOOKS, 60" length.....\$3ea or 4 for \$10

### LASER EXPERIMENTERS BONANZA!

**BARCODE SCANNER**, INTERMEC 2702. NEW and WORKING! Superb package includes: 2mW HeNe laser and 12VDC power supply, Collimating telescope, Bandpass filter (632nm) and detector, Resonant scanner, mini stepper motor, prism, mirrors and over 80 IC's. Operates over RS232. Can read codes moving at 400fps! Extruded aluminum housing. MANUAL and CABLES INCLUDED. System requires 12VDC. SPECIAL \$95ea. or 2/\$175 THIS MONTH.

**DC POWER SUPPLY**, 12VDC @ Xamps switching power supply. Suitable for use with our scanner or as a general purpose unit. SPECIAL \$12ea. 2/\$20

**SEE IN ALMOST TOTAL DARKNESS!** Starlight scope kit. Includes 2nd GEN. Intensifier module, new 50mm f1.7 objective and 10X focusing eyepiece. Just add our housing and 3VDC for a complete night vision system. COMPLETE KIT... \$695ea. or MODULE ONLY less optics...\$795

**BIG VOLTS SMALL PACKAGE!** ULTRA MINI 10 to 15kVDC @ 10uA to 50uA, Power supplies. Our latest state of the art designs. Perfect for IR, image intensifiers and many other areas. Four different models. 1.5Vdc, 3Vdc, 9Vdc and 12Vdc input @3mA to 50mA. Size 1" X 2" X 0.65" SPECIAL \$59ea. any model.

**EXOTIC NEW DEVICES, Call for information:**  
NO LIGHT, COVERT VIDEO CAMERA  
IR VIEWER KITS  
INTENSIFIED, COVERT VIDEO CAMERA  
IR GOGGLE POWER SUPPLY  
WIDE AREA IR ILLUMINATORS  
5mW LASER DIODE MODULES



**RESOURCES UN-LTD.**

**THE QUALITY YOU DESERVE AT PRICES YOU CAN AFFORD**

60 DAY REPAIR OR REPLACEMENT GUARANTEE. MANUALS INCLUDED IF AVAILABLE. TECH. SUPPORT AVAILABLE.  
VISA, MC, AMEX or COD. PHONE: 603-668-2499 FAX: 644-7825

CIRCLE 295 ON FREE INFORMATION CARD



# EPROM PROGRAMMING SYSTEM NEEDS NO INTERNAL CARD

EPROMS (24, 28 and 32 pins)  
2708, 2758, TMS2716\*, 2716  
27C16, 2516, 2532\*, 2564\*  
68764\*, 68766\*, 2732, 2732A  
27C32, 2764, 2764A, 27C64  
27128, 27128A, 27C128  
27256, 27C256, 27512  
27C512, 27513\*, 27C011\*  
27C020, 27C1001 (1 MEG)  
27C2001, 27C2001 (2 MEG)  
27C040, 27C4001 (4 MEG)  
40 PIN EPROMS \*1, 2 & 4 MEG  
27C1024, 27C2048, 27C4096  
27C210, 27C220, 27C240



EPROMS (SERIAL-8 BYTE WIDE)  
2804, 2816A, 28C16, 2817A\*  
2864A, 28C64, 28256, 28C256  
2401/02/04/16, 2444  
8572/82/92, 9306/46/56/66  
MicroControllers\*  
8741A, 8742, 8748(H), 8749(H)  
8751(CS1), 8752(CS2), 8753  
8744, 87C5XX, TMS7742  
68705(28 & 40 pin), 68HC705  
Bipolar Proms\*  
82SXXX, 74SXXX  
\*ADAPTER REQUIRED  
Diagrams included with manual  
Assembled adapters are available

CONNECTS TO YOUR SYSTEM'S

## PARALLEL PRINTER PORT

A FAST, EASY-TO-USE SYSTEM WORKS WITH ANY DESKTOP OR LAPTOP MACHINE  
EXPANDABLE DESIGN SUPPORTS OVER 500 CHIPS PLUS ADAPTS TO NEW DEVICES  
SUPPORTS 8, 16 & 32 BIT DATA FORMATS INCLUDING WORD SPLIT & DOUBLE WORD  
READS AND CONVERTS INTEL HEX, MOTOROLA S-RECORD AND BINARY FILES  
HARDWARE PROTECTED AGAINST DEFECTIVE AND INCORRECTLY INSERTED DEVICES  
APPROVED PROGRAMMING ALGORITHMS - MOST DEVICES PROGRAM IN UNDER 1 MIN.

## SYSTEM SOFTWARE COMMANDS

PROGRAM DEVICE(S) FROM DISK FILE READ DISK FILE INTO BUFFER READ DEVICE(S) INTO BUFFER	SAVE DEVICE(S) OR BUFFER TO DISK PROGRAM TO DEVICE(S) FROM BUFFER COMPARE DEVICE(S) WITH BUFFER	COPY DEVICE(S) VERIFY DEVICE ERASED SELECT BUFFER EDITOR SELECT DEVICE TYPE DEVICE CHECKSUM SELECT BUFFER
---	--	--

PLUS AN INTEGRATED BUFFER EDITOR WITH 18 BYTE LEVEL COMMANDS

SYSTEM INCLUDES: PROGRAMMING UNIT, POWER PACK  
CONNECTING CABLE, OPERATION MANUAL & SOFTWARE **\$289**

SOFTWARE AVAILABLE ON 3 1/2" OR 5 1/4" DISK (PLEASE SPECIFY)  
CALL ABOUT OPTIONAL ADAPTERS - A SOFT TRAVEL CASE IS AVAILABLE FOR \$19.00

TO ORDER SEND CHECK, MONEY ORDER, WRITE OR CALL:

ANDROMEDA RESEARCH  
P.O. BOX 222  
MILFORD, OHIO 45150  
(513) 831-9708  
FAX (513) 831-7562

VISA

MASTER  
CARD

ADD \$5.00 FOR SHIPPING

ADD \$4.00 FOR C.O.D.

WRITE OR CALL FOR MORE INFORMATION OR A DATA SHEET

## NOW YOU CAN "SEE" INVISIBLE FIELDS AND AVOID THEM

Most homes and offices have hot spots with strong artificial electro-magnetic fields, where chronic exposure may cause mental or physical problems. Even the EPA names these fields as suspected carcinogens. You can reduce your risk by avoiding these high-field areas.



The **TriField™** meter detects far more of these fields than any other electromagnetic pollution meter. It's the only one that independently reads AC electric fields, AC magnetic fields, and radio/microwaves. It also reads field strengths in all directions simultaneously. Every other meter that sells for under \$150 reads only magnetic and only in one direction — they can entirely miss a magnetic field unless pointed correctly and are blind to radio/microwaves and electric fields, both of which cause biological effects.

The **TriField™** meter reads all three types of fields numerically and with a SAFE/BORDERLINE/HIGH SCALE, weighted proportional to effect on the body. Thresholds are based on epidemiological and laboratory studies. (While no absolute hazard thresholds have been established, reduction of relative exposure is prudent.)

The **TriField™** meter comes ready-to-use with battery, instructions, and one-year limited warranty. The cost is \$144 postpaid.

AlphaLab / 1272 E. Alameda Avenue / SLC, UT 84102  
For literature and information, call (503) 621-9701

# TOP SECRET

## CONSUMERTRONICS

2011 Crescent Dr., P.O. Drawer 537  
Alamogordo, NM 88310  
(505) 434-0234, 434-1778

FAX: (505) 434-0234 (if you get answering machine press "#", then "1" any time)

VOICE LINES: 8 AM - 8 PM MST, Mon-Sat

FAX (orders only): 24-hour, 7 days/week

Add \$5 S/H (total USA, Canada). All items in stock. COD (UPS cash only), VISA, MC/Ord OK. New Catalog is \$2 w/order, \$4 w/o (no free catalog). In business since 1971. As seen on TV, etc. John Williams - former Lockheed Senior Engineer, NMSU Professor of Computer Science, NIH Health Physicist. Educational purposes only.

\*All software supports all IBM-PC compatible systems (8086 - 80486)

### Off-The-Shelf HARDWARE

Van Eck Systems, Automated Tempest Module, KX Radar Emitter, Carjacking Follower, Personal Body Alarm, Voice Disguiser, Shrek Module, Hearing Assistor, EM Countermeasure, TENS, 6th Sense Communicator, many Nifty Phone Boxes, Bumper Beeper, Subliminal Mixer/Amp, Super MWO, Rifle Device, Hieronymus Machine, Neurophone, MU Magnetometer, Dwelling Security System, Levitator, Stealth Paint - more! See new Catalog

### SPECIAL PROJECTS

We design, build, repair, modify, maintain and/or consult on any device, system, process or project - electrical, electronic, computer, phone, mechanical, optical, automotive. Invention prototyping. Confidentiality guaranteed. Describe and include \$25 pre-engineering fee (does not obligate you). Time and cost estimates in 7-10 days.

### CELLULAR PHONE MANUAL

How cellular phones are designed, operated, re-programmed. How cellular systems are vulnerable to hack attacks, and countermeasures. Comprehensively describes modifying NAMs and ESNs (includes specific info on 30+ popular models), scanning, scanner restorations (includes UHF TV method), freq and channel allocations, roaming, tracking, ECPS - more! \$39.

### VOICE MAIL BOX HACKING

How Voice Mail Box (VMB) systems are used and the specific ways they are hacked. Includes ASPEN, MESSAGE CENTER, BDX, EZ, SYDNEY, PHONE MAIL, AUDIX, etc. Absolutely required for all users and sysops! \$29

### PHONE COLOR BOXES

As designed by Phone Phreaks! 15 phone color boxes described. Dozens of circuits, simulator programs. Plus call forwarding, conferencing, phreak history, 50 useful and legal phone circuit plans - more! \$29.

### COMPUTER PHREAKING

TROJAN HORSES, VIRUSES, WORMS, etc. and countermeasures. Includes disk with 350K of hacker text files and utilities, and legendary FLUSHOUT - protection system (Ed. Choice PC Magazine). Dozens of computer crime and abuse methods and countermeasures. How systems are penetrated. BBS advice, password defeats, glossary - much more! Manuale + Disk\* \$39.

### BEYOND VAN ECK PHREAKING

Eavesdropping on VDT and TV video signals using an ordinary TV! Documented in security industry literature. Range up to 1 KM. Plans include both the CONSUMERTRONICS and the original TOP SECRET VAN ECK designs! \$29.

### CRYPTANALYSIS TECHNIQUES

Five powerful menu-driven crypto programs (in .COM and their .BAS sources) to analyze, decrypt "secure" ciphertexts. Worked-out examples. Recommended in prestigious COMPUTERS & SECURITY. Manual + Disk\* \$29.

### ABSOLUTE COMPUTER SECURITY

Dozens of simple, versatile, secure methods and tips. Our invulnerable Cipher Program (in .COM and its .BAS source). Plus \$1,000 CIPHER CONTEST ciphertext and rules. Manual + Disk\* \$24.

### HARD DRIVE MANUAL

Covers all hard drive and controller implementations (emphasis on PCs). How to select, interface, initialize, set up, use, maintain, troubleshoot and repair them. How to protect them from mistakes, sabotage, prying eyes and sticky fingers. How to recover damaged and lost files. How to prevent crashes to begin with. Includes software reviews. Loaded with information, advice tips \$29.

### DISK SERVICE MANUAL

Maintain, troubleshoot, repair, adjust, align floppies without special equipment or software. 3.5"/5.25"/8". PC/XT/AT/386/486, Apple, Commodore, etc systems. All floppies need regular upkeep \$29. DISK DRIVE TUTORIAL: Theory, practical facts on floppy drives, disks, including many tips, recommendations, formatting, interfacing, FDC, etc. \$19. Both \$39.

### AUTOMATIC TELLER MACHINES

ATM crimes, abuses, vulnerabilities and defeats exposed! 100+ methods detailed. Includes: Physical, Reg. E. cipher, PIN compromise, card counterfeiting, magnetic stripe, false front, TEMPEST, Van Eck, tapping, spoofing, inside job, super-cool, vibration pulse, high voltage - others. Case histories, law, countermeasures, detailed security checklist. Labeled internal photos, figures. ATMs contain up to \$250,000 in cash! Heated \$350,000 ATM crime spree still unsolved! \$39.

### CREDIT CARD SCAMS

Cardholders, merchants and banks suffer \$ billions in losses annually because of credit card fraud. Describes every known means of credit card fraud and scams. Protect yourself! \$29.

### CONS & SCAMS

Cons & scams fleece Americans of \$100+ Billion per year! The most comprehensive survival manual on cons & scams of all kinds - from the classic to the high-tech. Details on 100s and their many variations. Protect yourself! \$29.

### STOPPING POWER METERS

As reported on CBS "60 MINUTES": How certain devices can slow down - even stop - watt-hour meters - while loads draw full power! Device simply plugs into one outlet and normal loads into other outlets. Also describes meter creep, overload droop, etc. Plans \$29. THE I.G. MANUAL: External magnetic ways (applied to the meter itself) to slow down and stop watt-hour meters while drawing full loads. Plans \$19. KW-HR METERS: How watt-hour meters work, calibration, error modes (many), ANSI Standards, etc. Demand and Polyphase Meters. Experimental results to slow and stop meters by others. \$19. Any 2, \$36. All 3, \$52.

### HIGH VOLTAGE DEVICES

HV devices plans: Stun Gun, Taser, Prod, Cane, Flasher, Blaster, Zapper, Audio/RF/Radar Jammer, Jacob's Ladder, Plasma & Van de Graaff Generator, Fence Charger, Gelco Counter, Ozone Gen., Fish Stunner, Plant Stim., Kirlian, more! Shocking! \$29.

### UNDER ATTACK!

Electromagnetic Interference and Electronic Weapon Attacks can cause: Cancer, birth defects, and profound psychological, neurological, cardiovascular and immune system disorders! Destructive to people, animals, plants, equipment! Includes ACTUAL CASES OF EM ATTACKS ON PEOPLE (we investigated) - more common than believed! Includes how to verify and pinpoint EMI and electronic attack sources, and specific countermeasures. \$29.

### EM BRAINBLASTER

Tutorial and plans for powerful ELECTROMAGNETIC WEAPONS and LAB DEVICES. Optimum circuits, freqs, waveforms, duty cycles, intensities. Comprehensive. \$29.

### RADIONICS MANUAL

Exciting electrical, electronic and electromagnetic therapeutic, diagnostic and preventive devices (mostly experimental). History, descriptions, plans (dozens), availabilities of Radionics Devices from early to modern. While drugs cost \$ Hundreds, electricity costs pennies! \$29.

### ROBOFONE AUTODIALER

Powerful, versatile, menu-driven Wargames autodialer lets you dial any quantity (up to 10K) or mix of local/long distance numbers in any order, over any length of time, whether busy or answered (your choice) and log the times, commands and results to monitor, printer and/or disk. Quick-dial directory of up to 600 numbers. BUSY redial options. Direct modem command and control. All Result Codes, including VOICE and RINGING. Optional shell to terminal program upon CONNECT. Exit to menu or DOS (for batching). Manual + Disk\* \$29.

### SOFTWARE PROTECTION SYSTEM

Unique system that highly discourages costly software piracy while not interfering with legit archival copies. No known way to defeat. No special equipment required. Simple and automatic to install on your distributed software. Compatible with all other copy-prevention systems. Manual + Disk\* \$59.

### SECRET & SURVIVAL RADIO

Optimum survival and security radio equipment, methods, freq allocations and voice/data scrambling/encoding. Includes small receivers/transmitters, telemetry, antenna optimizations, remote monitoring and control, security, surveillance, and ultrasonic, fiber-optic and infrared comms. 70+ circuit plans, tables. \$29.

### STEALTH TECHNOLOGY

Police radar is fascinating! It also has error rates of 10-20%! Every known error mode - stealth method and material used to minimize radar reflections - tactic and strategy to fight unjust radar tickets (that cost you \$100s in insurance and risk cancellation) - methods to detect and jam signals - fully described! \$29.

### ROCKET'S RED GLARE

How to design and build solid-propellant amateur and survival rockets. Emphasis on formulation, manufacture, installation of propellants, motor, igniters, etc. Includes list of commonly available materials, and the design of launch pads and test beds and their electronics. \$29.

Order Today! - (505) 434-0234, 434-1778

March 1993, Electronics Now



• Same Day Shipment • Quality Brands • Low Prices

**\$34.<sup>95</sup>**  
Model ZHS



**MAGNETIC PROBE  
SENSES MAGNETIC FIELDS**

This safe non-contact probe allows you to troubleshoot AC and DC solenoid-operated devices, relays or any device using a coil. Also detects transient pulses as fast as 10mS and identifies north and south poles. Place the probe close to the coil and if the LED is on the device is energized. Probe operating frequency is DC-400Hz.

**\$179.<sup>00</sup>**  
Reg. \$199.<sup>00</sup>  
Model ZC381200

**HANDHELD  
1.25GHz  
FREQUENCY  
COUNTER**


Microprocessor-based counter measures frequency from 10 Hz to 1.25GHz and period from 0.1µs to 100ms. Includes data hold, min/max/average readings and relative frequency measurements. Complete with 4 AA batteries, manual and 1-year warranty.



**\$79.<sup>95</sup>**  
Reg. \$95.<sup>00</sup>  
Model RCDS1  
Tool Case

**\$219.<sup>00</sup>**  
Reg. \$298.<sup>00</sup>  
Model R53-CDS1  
Tool Kit

**\$249.<sup>00</sup>**  
Model Z3011B

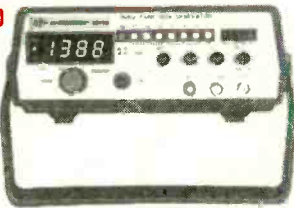


**BK PRECISION  
2MHz FUNCTION GENERATOR**

Features a 4-digit frequency counter display. Operates at 120/220/240VAC 50/60Hz. Complete with power card, one cable BNC to insulated clips, manual and 1-year warranty.

**\$55.<sup>00</sup>**  
Reg. \$59.<sup>00</sup>  
Model ZC375370

**PROGRAMMABLE  
DIGITAL TIMER**

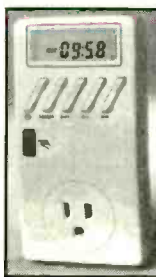Provides up to 6 on and 6 off settings per week with a minimum switch time as low as 1 minute. Plugs into 3-prong 110VAC outlet and has battery backup (AAA battery incl) to prevent programs from being cleared during power failure. Rated at 15amps. UL listed.




**DOUBLE-SIDED  
CORDURA® CASE**

One side has 45 pouches to hold your tools, the other side has a built in clipboard to hold a legal size pad of paper, a document pouch and 3 pockets to hold small items. The case also features 3 pockets on the outside of the case.

**SERVICE  
SPECIALIST TOOL KIT**

56 piece tool kit includes the case above plus commonly needed nutdrivers, hex drivers, screw drivers, pliers, cutters, wrenches, crimping tool, wire stripper, soldering tools and more. (DMM is not incl.)

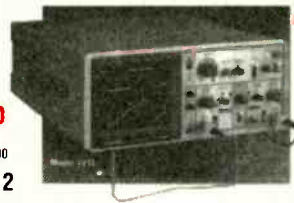**\$409.<sup>00</sup>**  
Reg. \$499.<sup>00</sup>  
Model ZV212



**HITACHI  
20MHz DUAL CHANNEL  
OSCILLOSCOPE**

Panel layout is color-coded to identify functions easily. Sensitivity 1m/div. Complete with probes, operator's manual and 3-year warranty.

**\$39.<sup>00</sup>**  
Reg. \$45.<sup>00</sup>  
Model ZSP100

**X1, X10  
SWITCHABLE  
OSCILLOSCOPE PROBE**

Monolithic probe features a 100 MHz bandwidth, a 3.5ns risetime, a wide compensation range (10pF to 60pF), a break-resistant center conductor and a sharp heavy-duty tip. Complete with sprung hook, BNC adapter, IC and insulating tip and trimming tool. Cable length is 1.5 meters.



**\$36.<sup>00</sup>**  
Reg. \$42.<sup>00</sup>  
Model ZP200

**X10 OSCILLOSCOPE PROBE**

200MHz monolithic probe provides superior performance with a risetime of less than 1.5ns and a sharp pulse response. Complete with sprung hook, trimmer tool, 6' ground line, BNC adapter, IC and isolating tip. Cable length is 1.2 meters.



**\$39.<sup>00</sup>**  
Model Z16420

**ESD FIELD  
SERVICE KIT**

Kit includes a blue static-dissipative vinyl work surface (18"x22"x0.30") with two female snap fasteners, a common-point grounding cord (15'), one adjustable wrist strap with a 1 megohm resistor, a 6' cord and a 7"x13" storage case.



**\$109.<sup>00</sup>**  
Model Z815  
**BK PRECISION  
HAND-HELD  
PARTS TESTER**

This 2000 count, 3 1/2 digit LCD display meter tests capacitance (20mF), resistance (20MΩ), transistor hFE, SCRs, diodes, LEDs and batteries. Comes with 9V battery, manual, test leads and 1-year warranty.



**\$24.<sup>00</sup>**  
Model ZPB1

**AUDIBLE  
CONTINUITY  
TESTER**

Tester gives a clear audible sound on point-to-point continuity and is suitable for Go/No-Go test for wires, cables, LEDs, switches, diodes, transistors, etc. Complete with test probes and detachable alligator clips. Operates on 9v battery (not incl.).



**contact east®**

North Andover MA 01845  
Offer Expires April 30, 1993



• Same Day Shipment • Low Prices • Money Back Guarantee

Beckman Industrial

**\$159.<sup>00</sup>**

Model ZRMS225

## 4 DIGIT TRUE RMS DMM

- 0.25 % accuracy
- 41 segment analog bargraph
- 3-year warranty

Full-function, auto-ranging DMM with 4 digit, 10,000 count resolution measures DC voltage and current, resistance and true RMS AC voltage and current. It features a continuity beeper, diode test, an Auto Min-Max mode, a relative mode and a probe hold mode. Comes complete with manual, test leads, battery(9V), and protective holster.



**\$59.<sup>95</sup>**

Reg. \$80.<sup>00</sup>  
Model RIM5 Tool Case

**\$299.<sup>00</sup>**

Regular \$365.<sup>00</sup>  
R22-IM5 117 Pc. Tool Kit



## THE PROFESSIONAL'S TOOL CASE

- Case top has built-in document holder
- Case bottom is partitioned into 3 areas
- Two removable pallets hold over 60 tools

A handsome black case to organize and transport your valuable tools and instruments. This is the same quality case used by thousands of professional field engineers. Case is made of high impact polypropylene, and has snap-action key locks and a padded handle.

Size: 17 1/2" x 12 1/2" x 5".

## 117-PC. PROFESSIONAL FIELD SERVICE KIT

The complete kit comes with the tool case described above and a complete selection of quality, brand-name tools including Diamond, Xcelite and Weller. The kit includes screwdrivers, pliers, tweezers, cutters, wrenches, alignment tools, hex driver blades and a crimping tool, wire stripper, soldering iron & supplies, socket set, penlight, inspection mirror, hammer and more.

**Lifetime Guarantee:** Any tool that fails under normal use will be replaced free of charge.

**\$109.<sup>00</sup>**

Reg. \$139.<sup>00</sup>  
Model R380912

**\$129.<sup>00</sup>**

Reg. \$159.<sup>00</sup>  
Model R38091F

## DCA/ACA CLAMP METER

### Functions as 3 1/2 Digit DMM

Transformer jaws measure up to 400A AC/DC and a peak-hold function provides recall of AC or DC current surges. As a DMM it measures AC voltage, DC voltage, AC/DC current and resistance. The meter has the following ranges: ACV: 750V; DCV: 200mV, 200V; DCA/ACA: 200A, 400A; Resistance; 2000 ohms Resolution down to 0.1mV, 0.1A and 1ohm. Comes complete with test leads, battery, carrying case and 1-year warranty. Model R38091F also has a built-in temperature function, 0-1400°F.



**\$149.<sup>00</sup>** Reg. \$183.<sup>20</sup>  
Model ZC2093



## SERVICE VACUUM CLEANER


Features a powerful 2.2 peak HP motor, easy change double-layer filter bag, shoulder strap and built in handle. Toner-safe. Complete with a 6' Tuflex hose, dusting brush, crevice tool and brush, tube adapter, snorkel tube and small dusting brush. 12"x11"x5". 8 lbs.



**\$99.<sup>00</sup>** Reg. \$128.<sup>65</sup>  
Model RWTCP5
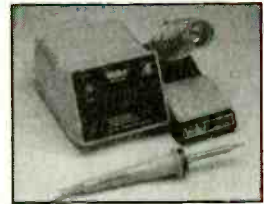
## TEMPERATURE CONTROLLED SOLDERING SYSTEM

Widely used in industry. It maintains a constant tip temperature of 700°F. Grounded tip protects components from voltage spikes. Comes with power unit, iron, stand, sponge and 700°F tip.



**\$49.<sup>00</sup>** Reg. \$58.<sup>30</sup>  
Model ZP1KB

## BUTANE POWERED SOLDERING TOOL


With cordless convenience this 4-in-1 soldering tool converts from a soldering iron to blow torch, hot blower or hot knife. Butane gas powered. Complete with tips, sponge, iron stand and carrying case.



**\$49.<sup>95</sup>**  
Model Z7201F
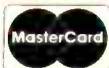
## DIGITAL THERMOMETER

Measures 0° to 159°F, has a hi-lo limit setting, an accuracy of ±1° and a built in clock function. ABS covered probe is suitable for air/immersion applications. 1.5V battery incl. 4oz.



Terms: Visa, Mastercard

**ORDER TOLL FREE: 1-800-225-5370**

In MA: (508) 682-2000

CIRCLE 227 ON FREE INFORMATION CARD

www.americanradiohistory.com

March 1993, Electronics Now

52A59


**MABUCHI R/C HOBBY MOTOR**



#RS-550.  
Wide  
Range: 4 to  
15 VDC.  
Perfect for  
R/C planes  
or cars

using either 7.2V or 14.4V Nicad.  
Approx. 12,000 RPM. Motor: 2 1/4  
In. X 1 7/16 In. Dia. \$2.95 or 4/\$10

**12VDC  
COMPUTER  
FANS**

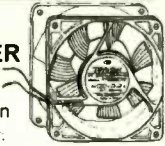

Most common  
size! TOYO.  
3 1/8 sq. X 7/8 In thick. \$6.95

**SUPER SPEAKER  
DEAL!**

8 Inch Round Woofer.  
4 Ohms - 20 Watts!  
\$4.95 ea.

**8032 MICROCONTROLLER**

Speed: 12MHZ. 44 Pin PLCC  
package. Mfg. by Signetics. 99¢  
11.059 MHZ crystal - \$1.25

**SIEMENS 4 DIGIT ALPHA -  
NUMERIC LED DISPLAYS**

4 Big 5 X 7 (.27 Inches) Displays with  
built in CMOS logic. 96 character ASCII  
format. 8 bit TTL compatible bidirectional  
Data bus. End stackable for any length  
display. Overall length package is only  
1.4 inches. Very easy to use, requires  
only an ASCII input from a microproces-  
sor. Built in ROM, memory, decoders,  
multiplexer, and drivers !!! Pins fit a  
standard .600 In. wide IC socket. W/Data  
#PD 3435 \$5.95 ea. or 5/\$24

**Computer Grade Caps  
15,000 MFD 75 VDC**

Small size, mfg. by Cornell Dubilier.  
2 In. Diam. X 4 1/4 In. Tall  
Part # DCM 153U075BC2B  
Perfect for audio amps or regulated power  
supplies. 1990 Date Code.  
\$4.95 ea. or 10 for \$35

**NICHICON HIGH VOLTAGE ELECTROLYTIC CAPS!**

Used in switching  
power supplies, Also  
perfect for vacuum  
tube circuits. VERY  
RARELY SEEN IN  
SURPLUS! Factory  
Fresh!

#1 100 MFD / 450 VDC 40 mm X 24 mm. 85° C. \$1.29	#3 330 MFD / 400 VDC 45 mm X 30 mm. 85° C. \$1.95
#2 330 MFD / 250 VDC 45 mm X 20 mm. 105° C. \$1.59	#4 330 MFD / 450 VDC 50 mm X 35 mm. 85° C. \$2.79

**HI-TECH DISPLAYS**

**OPTREX LCD  
DISPLAY**

2 Line X 16 Characters.  
7 Bit ASCII Input.  
#DMC16207H w/ Data.  
\$7.95


**SIEMENS SMART LED DISPLAY**

#DLO-7135. 5X7 Red. With built in logic!  
Requires only a chip select and an ASCII  
input. Operates on 5 VDC. 1 Inch tall. w/  
Data. New Units! Displays entire 128 char.  
set! PRICE CUT! \$2.95 ea.

**EPSON LCD**

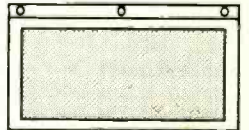**GRAPHICS DISPLAY**


640 X 240 dots - Super twisted nematic type.  
Built in drivers - 4 bit TTL interface. Viewing  
area 10-7/16" X 4-5/8". Overall 11-3/8" X  
6-1/16". 14 pins for signals and power (+5V,  
-12V). Complete 27 page manual.  
\$19.95 or 6/\$100 #EG-7004S-AR



NOT FOR BEGINNERS!

**ALPHA-NUMERIC  
RED LED ARRAY**

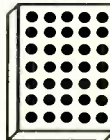7X5 LED Matrix. For moving  
message signs, Etc. By IEE.  
#2057 - c/c rows.  
#2058 - c/a rows. 2 X 1.5 In.  
w/Data. Your Choice:  
\$2.95 ea. or 8 for \$14.95



**SIEMENS 4 DIGIT  
LED DISPLAY**

Red or Green. With built  
in logic. 5X7 Matrix. Full  
ASCII Input. 5 VDC.  
.2 In. char. With Data.  
#PD2435 - RED - \$3.95  
#PD2437 - GREEN - \$3.95

**TANNER ELECTRONICS**

Phone: (214) 242-8702  
1301 W. Bellline Rd. #105 Carrollton, TX 75006



TERMS: Send check, or use Visa, MC. NO COD. USA, Canada only. Add \$3.85  
min. for UPS. Texas add sales tax. 90 day lmt. warranty on all items. \$15 min.

CIRCLE 299 ON FREE INFORMATION CARD

**CRESTWOOD PRODUCTS**

40994 GIBBEL RD. HEMET CA. 92544  
ORIGINATOR, MANUFACTURER & DISTRIBUTOR  
**VU-THRU VCR DIAGNOSTIC TOOL**

1-800-544-8583


Fax 1-714-658-8769 24HRS 7 DAYS  
USA & CANADA ORDER TOLL FREE

**UNITED STATES PATENT NO. 5,055,960**

A USEFUL AND WORTHWHILE TOOL for the  
\* \*PROFESSIONAL \* \*STUDENT \* \*EXPERIMENTOR


A PRECISION MOLDED, HIGH IMPACT, CLEAR PLASTIC TOOL THAT REPLACES  
THE VIDEO CASSETTE WHILE DIAGNOSING THE PROBLEM. THE VCR OR  
CAMCORDER WILL FUNCTION IN ALL MODES AND THE MECHANISM WILL BE  
OPEN FOR INSPECTION, MEASUREMENT & ADJUSTMENT

VHS - SVHS - VCR's & CAMCORDERS

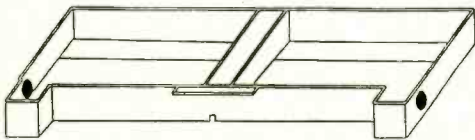


VT-103 \$9.95

BETA I II III & CAMCORDER

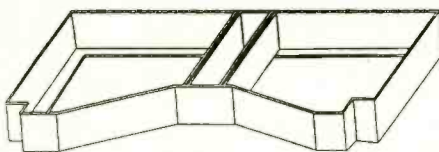


BVT-100 \$9.95

VHSC - SVHSC  
CAMCORDERS

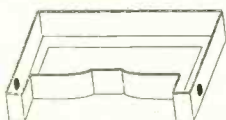

CVT 100 \$9.95

8MM - VCR's  
CAMCORDERS

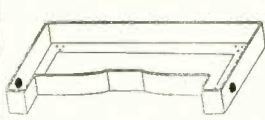

EVT 100 \$9.95

**NOTICE !!**

**THE ORIGINAL VHS VU-THRU TOOL WILL WORK  
IN ALL VCR'S, NEW UNITS OR OLDER UNITS-  
FRONT LOAD, -TOP LOAD, -SIDE LOAD, AND  
CAMCORDERS. INCLUDING THE DISCONTINUED  
"G" CHASSIS VCR'S.**

(see page 9 of our up-dated ILLUSTRATED &  
COPYRIGHTED instruction manual)

**INSTRUCTION  
MANUAL**

**HOW TO:**

- \* Clean Video Heads pg 3
  - \* Check tape end sensors pg 5
  - \* Renew drive wheels pg 4
  - \* Adjust loading posts pg 7
  - \* Renew pinch roller pg 6
  - \* Clean erase & audio heads pg 7
  - \* Check Spindle sensors pg 8
  - \* Adjust tape guides pg 9
  - \* Adjust Tracking head pg 7
  - \* USE IN "G" CHASSIS pg 9
- PLUS MANY TIME  
SAVING TIPS**

**FREE**

WITH ANY ORDER  
5 HEAD CLEANING  
SWABS  
1 OZ. HEAD  
CLEANING FLUID  
1 RUBBER  
RENEWING TOOL

ANY ONE TOOL  
\$ 9.95 ea.  
\$ 3.50 S&H  
\$ 13.45 total

ANY TWO TOOLS  
\$ 19.90  
WE PAY S&H

ORDER ALL FOUR  
\$ 29.85  
WE PAY S&H

COD add \$ 3.50  
CA. orders add 7%  
sales tax





# OPTOELECTRONICS

ALL OF OUR PRODUCTS ARE MADE IN THE U.S.A.



## Handi-Counter® 3000

The world's finest hand held multifunction counter – incorporates many unique functions usually found only in very expensive bench models.

Designed for virtually every measurement application from near DC through Microwave including measuring RF transmission frequencies at the maximum possible distance. The 3000 is also the world's first HandiCounter® with Period, Time Interval and Ratio measurement capability.

**\$259.**



## Bench/Portable Multifunction Counter Model 8030

10Hz - 3GHz extremely High Sensitivity, High Resolution and Accuracy, includes a Bargraph,  $\pm 1$ PPM TCX0, Two Inputs, Adjustable Trigger Level, Trigger Variable and Hold Button

**\$579.**

Optional  $\pm .1$  TCXO: \$135.



## HandiCounter® Model 2810

Our full range counter with bargraph 10Hz to 3GHz. Ultra-high sensitivity, 4 fast gate times, outstanding quality—low, low price.

**\$199.**



## Handi Counter® Model 2300

The Original Pocket Sized Counter. 1MHz to 2.4GHz – 8 digit LED. Maximized Sensitivity,  $\pm 1$ ppm TCXO. Includes Hold Switch, NiCads and Charger/Adapter!

**\$99.**

## R10 FM Communications Interceptor™

ALL NEW TECHNOLOGY!!

The Interceptor follows & locks on even when frequency changes and intercepts ALL FM Two-Way Transmissions without gaps in coverage. It does not have to tune through RF Spectrum to capture signals. FCC Classified as



Communication Test Instrument – Increase your RF Security!!

**\$359.**

## APS104

Our Active Preselector allows you to pick-up transmissions or frequencies at 10 times the distance. Use with our HandiCounter® or R-10 Interceptor™ 10MHz - 1GHz Tunable over 5 octaves

**\$995.**



## ACCESSORIES

### Vinyl Carry Case

CC12 - Padded Black Vinyl carrying case for 2300 size LED Counters ..... \$ 12  
CC30 - Padded Black Vinyl carrying case for 3000 size LCD counters. .... \$ 15

### Antennas

TA100S Telescoping Whip Antenna ..... \$ 12

### Antenna Packs:

Ant-Pak 1 (includes RD27, RD800, TA100S - Save \$11) ..... \$ 65  
Ant-Pak 2 (includes five assorted rubber ducks, 27-1000MHz - Save \$32.) ..... \$ 99

### Probes

P30 - Counter/Oscilloscope probe - for direct coupling to signal sources or circuit test points. 1x/10x, switchable ..... \$ 35

P101- Low-Pass probe attenuates RF noise from Audio frequencies. Has two stage low pass filter. .... \$ 20

## R20 AM Interceptor™

NEW! The R20 is both a sensitive RF signal strength meter (for ALL RF signals) and a near field AM receiver. The 10 segment LED bargraph responds with nominal 3dB increments to RF signal level received through the built in antenna.

**\$119.**



## Tone Counter Model TC200

NEW! Ideal companion for use with the R10 FM Communications Interceptor™ to measure sub audible signalling tones off the air. The TC200 can also be used with

communications receiver to monitor sub audible tones.

**\$179.**



## OPTOELECTRONICS

Factory Direct ORDER LINE

**1-800-327-5912**

305-771-2050 • FAX 305-771-2052  
5821 NE 14th Ave, Ft. Lauderdale, FL 33334  
5% Ship/Handling (Max \$10) U.S. & Canada.  
15% outside continental U.S.  
Visa, Master Card, C.O.D., Cash or Money Order only.

CIRCLE 259 ON FREE INFORMATION CARD

# Electronics Education

## Preparing You For a Job In The 90's



Part 1 DC	Digital 1 Basic Gates
Part 2 AC	Digital 2 Flip-Flops
Part 3 Semiconductors	Digital 3 Multiplexers
Part 4 Power Supplies	Digital 4 Converters
Part 5 Amplifiers	Digital 5 Memory
Part 6 Oscillators	Digital 6 MPU - IO's

Only \$34.95 each

Call Toll Free  
1-800-678-6113

Mail Check or Money Order To:

UCANDO Videos  
P.O. Box 928  
Greenville, OH 45331

Visa & Master Card Accepted

UCANDO ... "Changing The Way The World Learns Electronics"

CIRCLE 276 ON FREE INFORMATION CARD

**FREE!**  
COMPUTER TOOL KIT  
WITH EACH PURCHASE

Question: Who needs a Zenith Personal Information Terminal?  
Answer: With all these features and the low price, everyone!

**Worried about security?**  
Choose from 10,000 codes to allow only authorized users to communicate.

**Need 24 hour communications?**  
Attach a printer and use as a dedicated auto receiver terminal for unattended reception.

**Know a pilot?**  
Use to access the new DUAT service to file flight plans, check the weather, and more!

**Want to dial your regular phone automatically?**  
Stores up to 26 numbers for voice, data, or auto-logout dialing.

**Need to access multiuser computer systems?**  
Talk to mainframes and more with the ASCII and DEC VT52 terminal emulation modes.

**Want high speed communications?**  
Attach a high speed modem and communicate with other users or devices at up to 9600 baud! (Model ZTX-11-Z only).

- ASCII, DEC VT52 emulation
- Parallel printer port
- Changeable security access code
- RS-232 port (ZTX-11-Z only)
- Composite video output
- New in original box with manual
- Built-in 300 baud auto answer modem
- Phone #, dialing sequence storage
- Switch for single or multi-line phone
- Two phone jacks: line and phone
- Program in Basic by external computer

**ZTX-11-Z with RS-232 \$75**

**ZTX-1-UZ without RS-232 \$50**

### COMPUTER BUSINESS MART

10215 Buena Vista Avenue, Suite A • Santee, CA 92071

(619) 449-9040 • FAX (619) 449-7929

VISA — MasterCard — AMEX — Discover — COD — PO


CIRCLE 225 ON FREE INFORMATION CARD



## HSC leads the way to savings with the best in Silicon Valley Exotica!
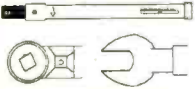
### Torque Wrench -- Industrial Strength!

Just in -- industrial torque wrenches by Mountz. These brand new items are calibrated from 20 to 200 kgf.cm and feature "click" action torque control. Snap-fit heads include useful 3/8" ratchet, 11/16", 30 mm and 13mm open ends, and 17mm box end. HSC# 13655 Set only \$19.95



### TV Modulator -- Industrial Strength!

Just what you needed to finish that home television station...this Channel 2 modulator by Telemet! These used units accept a composite video signal and audio and provide a VHF television carrier (channel 2) modulated by the input signal. 19" Rack mount chassis. Schematic included. Full Manual available. \$5 HSC#13657 \$59.95



### Test for Shock -- Industrial Strength!



Here is an unusual item...a resettable G-force gauge! This high quality item is used to detect mechanical shocks in excess of 15 G's...perfect for determining if your shipment was dropped by the shipping company, or use to calibrate your rocket sled! Measures 2" tall on a 1 5/8" square base. Detailed data sheet enclosed. HSC# 13656 \$5.95

## Perestroika Fallout...Soviet Science Collector's Items!



History on the march! Empires crumbling! Eager young scientists being trained for the new world order! We took advantage of the changing world scene to bring you these unique items that are also great values...Russian (formerly Soviet) microscopes! The manual calls them training microscopes, we would probably call them student-grade instruments, although they are not toys. They are both biological (illuminated from below via mirror) microscopes, for transparent specimens. The one on the left is of metal construction, has two objective lenses (8x, 20x) and three eyepieces (7x, 10x, 15x). A recent volume purchase allows us to lower the price to \$59.00. The one on the right is made of plastic, with fixed lenses giving 60x overall magnification. The optical assembly will store in its own base, giving a lightweight, compact (5" x 9" x 1.5") package perfect for carrying in a backpack for field trips. It comes with two specimen jars, tweezers, slides, etc. that also store in the base. The quality and workmanship on both units are surprisingly good, given the stories we've heard of Soviet labor woes. Now you can own a piece of history, or just an inexpensive, decent microscope. HSC# 13065 \$59.00



HSC# 95062 \$19.95

### For your IBM-Compatible computer...

1. Replacement Fan -- Is your computer working fine, but just noisy? You would be surprised at how much dust gets sucked through the power supply. This gums up the bearings of the fan, which then starts to howl. Don't replace the power supply, just change out the fan! Brand new 12 VDC .20A fans, 3 1/8" square body with mounting holes on 2 13/16" centers. HSC# 13712 \$9.95
2. Western Digital 16-Bit (AT) Hard/Floppy Controller with SIO, PIO ports -- Save slots, save money! WD1003S-WA4 controller will handle two MFM hard drives at 2:1 interleave, two floppy drives (up to 1.44 MB) and also gives you Serial and Parallel Ports. Drive cables included, no manual but installation is typical procedure for AT's. HSC# 13659 \$19.95

### Solar Stuff for the Sunshine-Savant!

- Check out these great items that work on free energy! Go solar & save!
- 1) Solar Battery Charger -- Small unit (2.5" x 4.5" x 1.5") has hinged lid with solar cell array for optimum sun angle. Can charge two AA or C Ni-Cd batteries (not included). LED indicates optimum charge rate. HSC#80050 \$12.95
  - 2) Solar Rechargeable Flashlight -- perfect for camping, emergencies...Never needs batteries! 2.5" x 1.25" x 3" fits in purse, backpack. HSC#80048 \$11.95
  - 3) 4-Power Radio -- Good-sounding AM/FM radio has solar panel for daytime use, or its internal dynamo can be cranked to charge internal energy source for up to a half-hour of listening time! Also runs off regular AA batteries or DC Adapter (neither included). Great for emergencies, power outages, camping, etc. 3" x 6" x 1.5" You may never buy batteries again! HSC#80051 \$29.95
  - 4) Solar Education Kit -- includes small solar cell (1.75" x 3" x .25"), booklet, small DC motor, fan blade, spinner disks, stickers, etc. Good for child's school or science fair project. HSC #80017 \$9.95
  - 5) Solar Musical Keychain -- plays melody in bright sunlight, also has LED flashlight so you can find that keyhole in the dark! HSC # 80053 \$4.95

## More from HSC's Project Locker...

We've scoured our shelves once again for rare & unusual parts that will get you thinking of the many uses to which they may be put. Many items you just won't find anywhere else, and our prices will encourage you to dream up new projects!

A. Macintosh peripheral device adaptor converts older Mac 128 & 512 style peripherals (9-pin D conn.) to the Mac Plus and higher Mini-DIN connector. Requires 15-17 VAC input (use HSC# 12916 16VAC adapter, \$3.95 and HSC# 206B 3mm plug, \$ .59) HSC#13001 \$5.95



B. Heatsink with complementary Darlington Pair transistors measures 3" x 6.25" x 1", has 2N6031 (NPN) and 2N6058 (PNP) already mounted. 80V, 12A, hFE = 750 to 18000 @ 6A. HSC#9677 \$5.95



C. Microswitch 103SR11A-1 Proximity Sensor -- Hall-effect detector operates on 5 VDC 4 mA, sources 3.5 VDC max 20mA in presence of greater than 25 Gauss magnetic field. .43" dia. x 1" (nuts not included) With spec. sheet. HSC #5319 \$ .99 ea



D. Tiny switching power supply, perfect for powering a single 3.5" hard disk drive. 2" x 6.25" x 1.25". Made by Skyenet, used, tested good. Selectable 110/220VAC input, 5VDC @ 2A and 12VDC @ 1.5A output. HSC #12758 \$17.50 ea



E. Nine-digit, eight decimal point numeric LCD with solderable connection strip. No funny sockets needed! .5" high digits, overall size of display .75" x 3". Pinout included. HSC#13518 \$1.95 ea. or 10/\$15.00



F. Miniature Toggle Switch -- SPDT 125VAC 6A or 250VAC 3A Standard type on-on switch, solder eyelet terminals. Any hobbyist should have at least a handful in his parts bin! Now you can afford it... HSC# SW104 \$10.65



G. High Value Capacitor -- .047 Farad (yes, that's Farad) at 5.5V in a package only .5" dia. and 3" tall. Good for CMOS memory back-up, etc. Made by Sohio. HSC# 10771 \$ .29 ea. or 10/\$2.49



H. Leviton 6608 touch-activated dimmer control -- Make any metal surface or contact dim an incandescent lamp (up to 150W) simply by touching it! UL Recognized 120VAC dimmer module has three connections: line, load and touch contact. Think of the applications! 1.5" x 1.5" x 2.75" HSC# 13037 \$5.95 ea



## HALTED specialties co. HSC Electronic Supply

Toll Free (Orders Only) 1-800-4 HALTED (1-800-442-5833)

Retail Stores:

3500 Ryder St., Santa Clara, CA 95051 (408) 732-1573  
4837 Amber Ln., Sacramento, CA 95841 (916) 338-2545  
6819 Redwood Dr., Cotati, CA 94931 (707) 792-2277



### Attention: Robot Builders & Hobbyists!

A. Just in! 12VDC two-speed reversible motors, perfect for your own personal R2-D2's locomotion! These motors are 3" dia. x 4.5" long with a .5" long shaft. They will provide up to 30 oz.-in. of torque at 2700 RPM, unloaded speed is closer to 5000 RPM. Depending on load they draw anywhere from 5 to 9 amps. The .31" (5/16") dia. shaft is cut with gear teeth, but you could still put a pulley or gear with a set-screw on it. Generous 33" long leads are color-coded for easy hook-up. Connection diagram and torque curve chart provided. These motors are new, but slightly dusty. HSC# 13617 \$7.95 ea.



B. 12VDC SPDT Relay -- Just the thing for controlling the above motor (in fact, they are both left-overs from a camper-jack system). C.P. Clare GP3R211ND1000 relay is rated at 10 amps, uses solderless quick-connect tabs, and has handy mounting ears. HSC# 13618 \$4.95 ea.

C. Heavy duty Coil-cords -- Two types available. Makes connections to moving fixtures easy! Rugged SJO insulation, slightly dusty. These are not easy to find, and only limited quantities are available! HSC# 13620 20AWG, 5 cond., 5' stretches to 24' \$5.95  
HSC# 13621 18AWG, 4 cond., 4' stretches to 25' \$7.95



D. Stepper Motors -- Two types, both 12VDC, sorry, no docs on either one yet... we'd appreciate info if you have it! At left, Howard Ind. Model 1-19-4200, 3.6° per step, 1.75" x 1.75" x 1.75" HSC #13036 \$7.50  
At right, Minebea Co. "Astrosyn" Model 23LM-C331-03, 1.8° per step, 2.25" x 2.25" x 3" with bracket (not shown) HSC #13594 \$4.95



### Now Available...New HSC Catalog!!

Finally, it's here! Months in the making, copiously illustrated... our new 48-page catalog, listing thousands of electronic essentials, is now available! Send \$1.00 (or get one free with any order) and thanks for waiting patiently!

Terms: Some quantities limited; all items subject to prior sale. Minimum order: \$10.00 plus shipping. Orders under \$20.00 subject to \$2.00 handling fee, in addition to shipping. All orders shipped FOB Santa Clara, CA (this means you pay freight) by UPS Surface (no P.O. Boxes) unless otherwise specified, in which case prevailing carrier rate plus \$5.00 handling fee applies. Prepaid orders that don't include shipping charges will be shipped freight COD. There is a \$4.00 UPS charge added to shipping charges for COD shipments. If you have questions about your order, please call Customer Service at (408) 732-1854 M-F 9AM to 5PM PST.



**A recession-proof business!  
Own your own  
computer repair business  
or add computer repair  
to your existing business.**

TechServ can put you into your own computer repair business quickly, economically and efficiently. Research indicates that during a recession, computer repair businesses will grow at twice the rate of hardware sales. TechServ's complete support program gives you the opportunity to be a part of this fast growing industry.

**• Proven Marketing Plan**

**• Recognition**

Nationally recognized trademarks and logos give you immediate recognition as a professional computer repair specialist in your area.

**• Training**

- Level 1    286/386/486/586  
            Troubleshooting, upgrades, advanced diagnostics
- Level 2    Networking/Novel/Unix/Multi-user/  
            Multi-tasking configuration/Installation/  
            Maintenance. Prepare for C.N.E.  
            (Certified Network Engineer) test

**• Parts and Board Repair**

Single source for OEM/generic parts and board repair. Order 7 days a week/24 hours a day. \$45 million in parts in stock, ready to ship any where, overnight if required.

**• Documentation**

We provide manuals, documentation and advanced diagnostic software.

**• New Hardware**

We provide new hardware for IBM, Compaq, Apple and compatibles at huge discounts. Custom build your own systems.

**Over 300 dealers worldwide**

Find out why the Wall Street Journal and Fortune Magazine call computer repair the business opportunity of the 1990s.

**Call TechServ at (800) 873-7378**

or (212) 967-1865 or fill out coupon below and mail to:

**techserv** AUTHORIZED DEALER SM

**America's largest chain of independent,  
licensed computer repair centers**

253 West 28th Street, New York, NY 10001


NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

TELEPHONE \_\_\_\_\_ [RE 1/93]

CIRCLE 272 ON FREE INFORMATION CARD

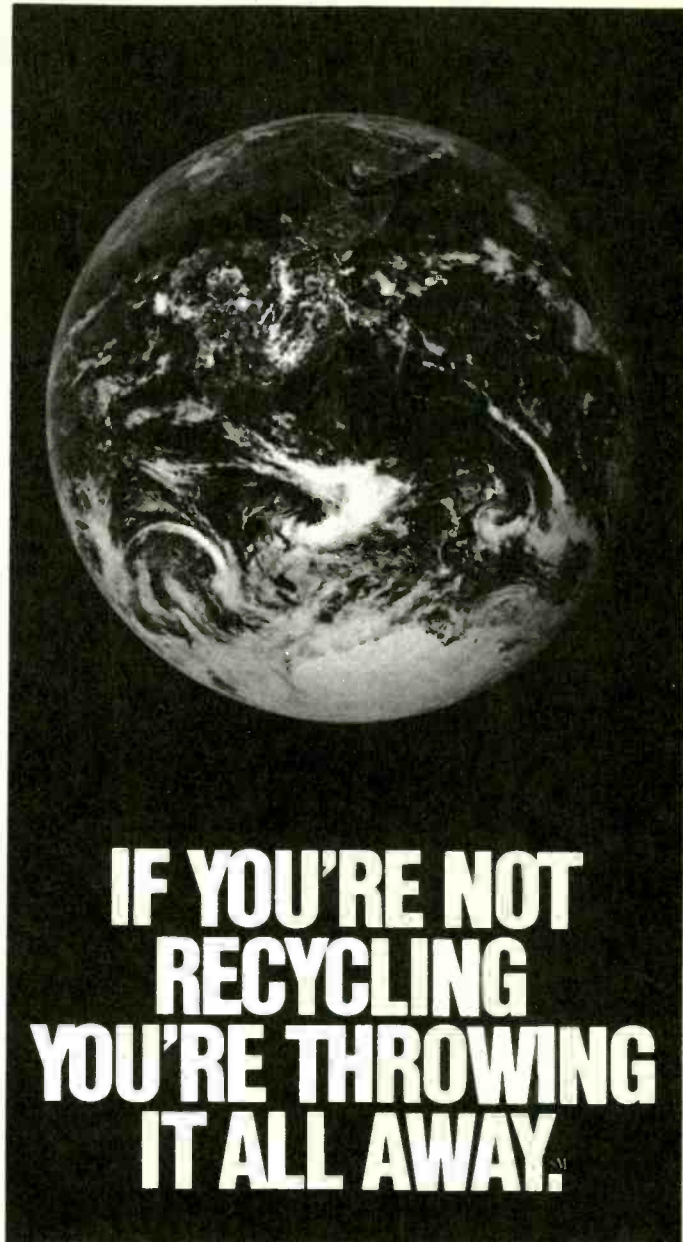

A little reminder from the Environmental Defense Fund that if you're not recycling, you're throwing away a lot more than just your trash.


You and your community can recycle. Write the Environmental Defense Fund at: EDF-Recycling, 257 Park Avenue South, New York, NY 10010, for a free brochure that will tell you virtually everything you need to know about recycling.



© 1988 EDF



# RAINBOW KITS

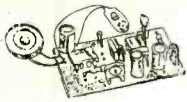

## RADAR SIGNAL DETECTOR

If you think that a sensitive radar detector is a complicated piece of equipment, take a look at this new kit. This simple, yet effective, detector circuit can be built in less than an hour and can be tuned to respond to signals between 50MHz to 500GHz. It's a fun kit to build and play with. A cigarette lighter plug is included. Size 1"x3/4" operates on 9 to 15v DC.

**KIT RSD-1 \$12.95**

## STROBE LIGHT


If you need an attention getter, or warning light, you need the strobe light kit. Use it for emergency light for autos, for model planes or radio towers. Even use it on your bicycle. Operates on 6 or 12v DC and has a variable strobe rate.

**KIT ST-1 \$8.95**

## DIGITAL THERMOMETER

Have you ever wanted to tell temperature changes fast & accurately? The DT-1 kit will turn your digital volt meter into an accurate digital thermometer with .1 degree resolution. It gives you a 250 degree window with a range from -40F to 300F degrees. It has a remote sensor .25" sq. that can be mounted many feet from the meter if need be.

**KIT DT-1 \$8.95**

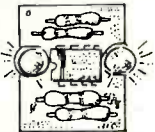

## BLINKY LIGHTS

Want to attract attention? These kits are perfect for decorating name tags, lighting up your hat, or flashing lights for your model trains. Some people use them to simulate a burglar alarm for autos. Put it in a box, set it on your dash and it looks like the real thing. Each kit contains two LEDs that alternates flashing. Operates on a 9v battery. Size .5"x.5"

**KIT RB-2 \$3.45**

## CAPACITANCE METER


This easy to build kit will turn your digital volt meter into a CAPACITOR METER. Turn that junk box of unmarked capacitors into a fortune. Measures capacitors from (2pF to 2.2uF. Operates on a 9v battery. Size 1.75"x2"

**KIT CA-2 \$12.95**

## WIRELESS FM MIKE

Small but mighty .8"x1" PCB, will really stomp out a signal well over 400 yds. This is a buffered wireless mike that operates on 80 to 120 MHz FM. Comes complete with a microphone, and 9v battery connector. Operates on 6 to 12v DC.


**KIT WM-1 \$12.95**

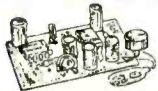

## SUPER SNOOPER-BIG EAR

Use this BIG EAR amplifier to listen through walls, hear conversations across the room. Beef up the sensitivity with a parabolic reflector and hear blocks away. Due to the size, the BIG EAR can be hidden about anywhere. Use the earphones from a pocket transistor radio to listen. Makes an ultra-sensitive intercom. Can also be used as a general purpose 1.5W amp. We supply a mini-microphone in the kit. You can also use any 8 to 45 ohm speaker. Operates on 6 to 12v DC. Size 1"x1.75"


**KIT AA-1 \$10.95**

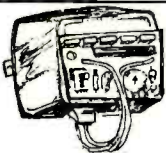

## AC LINE MONITOR

This is something every computer user, photographer, or anyone that must maintain a safe usable AC line voltage should have handy. Monitor the voltage of your motor home's 110v AC generator inside the motor home. Every technician's bench needs this item. The AC line monitor will indicate, with multi-color LEDs, what voltage is being distributed to your equipment at that particular outlet.

**KIT LM-110 \$10.95**

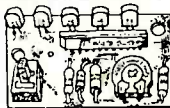

## 12V BATTERY MONITOR

Have you ever been in your car, boat, or camper — you try to start your motor but the battery is dead? The BATTERY MONITOR kit uses the cigarette lighter plug outlet to monitor the true battery voltage. Multi-color LEDs indicate the voltage in 1v steps from 11v to 15v, green means great, yellow is good, and red — call the tow truck or get out the oars. Size 1.2"x1.75"

**KIT LM-12 \$5.95**



## PHONE BUG

Small but mighty, so small it fits anywhere. Telephone line powered, never needs batteries. Transmits both sides of a phone conversation loud and clear, wireless, to any FM radio at great distances away. Variable tunes 70MHz to 130MHz. It can also be used to make any phone a speaker phone. Size .55"x1"

**KIT TEL-B1 \$10.95**



## PHONE RECORDING SWITCH

This telephone line powered switch is small enough to install anywhere only .9"x.6" Every time someone picks up the phone the tape recorder will record both sides of the conversation automatically. Use it in your office to record all phone conversations so you don't lose that important address you wrote on the back of an envelope.

**KIT TEL-SW 1 \$10.95**

## BUSY PHONE LIGHT

Add this little kit to any or all of your phones. When any extensions are in use the LED will light. Uses a 9v battery. P.C. Board 1"x1/2". Complete with etched & drilled PCB, all parts and schematics.

**KIT TEL-LIT-1 \$9.95**



## VOICE ACTIVATED SWITCH

This vox can be used to operate a tape recorder, ham radio, CB radio. Use it to turn on an alarm. The output can operate a load up to 100ma. It will operate a relay, lights, motor, or LEDs. What could you do with a sound activated switch? Size 1.5"x1.25"

**KIT VOX-1 \$6.95**

## LIE DETECTOR

This kit can be great fun at parties. Lie and an audible tone will change, the more you lie the more the tone changes. When you lie your palms & forehead sweat. This kit allows you to measure these changes. Only a very slight amount of change will cause the tone to increase in frequency. Operates on 6 to 12v DC. Size

**KIT LD-1 \$9.95**

# LASER KITS

Laser Switching Power Supply Kit, input 12V DC .75-1.25A. Output 2 to 3 KV at 3-4.5 MA, trigger voltage of approx. 8-10 KV. Complete with 6.25" x 2.25" printed circuit board, schematic and all the parts.

**LPS-1 \$59.95**

1MW Laser Tube, NEW Mini He-Ne 1.125" dia. x 5.75" long, perfect for experimenters and laser projects. Works great with above power supply LPS-1.

**LIMW-1 \$39.95**

Mirror and Motor Kit—This unique kit allows you to project Lissajous patterns on walls and ceiling. Change the pattern by changing the speed of the motors. Comes complete with 2 motors, front surface mirrors, motor brackets, rheostat control to control #1 motor, and high power resistors to use on #2 motor.

**MM-2 \$19.95**

## ★ SPECIAL ★

Laser Power Supply Kit LPS-1  
1MW Laser Tube LIMW-1  
Mirror and Motor Kit MM-2  
**ALL 3 FOR \$99.95**

9V 100MA rechargeable Ni-cad batteries. This 9V Ni-cad is truly a 9V not the standard 7.2V you're accustomed to. Use over and over.

**NEW \$4.00 ea.  
10/\$29.95**

9V battery charger kit. This kit is a must when you buy 9V Ni-cads, charges 2 batteries at once. Use on 110V AC or with a 12V DC cigarette lighter plug which is included. Comes complete with parts, P.C. board, housing and schematic.

**CH-9V \$19.95**

\*\*\*\*\*



THIS MANUAL CONTAINS ALL SCHEMATICS, PARTS & P.C. BOARD LAYOUTS FOR ALL OF THE RAINBOW KITS. USE YOUR OWN PARTS TO CONSTRUCT ANY OF OUR KITS.

**KIT BOOK \$14.95**

**\$5.00 OFF IF YOU BUY ANY KIT.**

\*\*\*\*\*

# TV NOTCH FILTERS

OUR TV FILTERS ELIMINATE UNWANTED TV CHANNELS OR ANY INTERFERENCE THAT ALTERS BOTH THE SOUND AND VIDEO.

Channels available 2 thru 6 & 14 thru 22  
Specify a specific channel when ordering

CHOICE

**14.95**  
EACH

NOTE: All TV Filter Kits are sold for educational purposes only. You must obtain permission from your local cable company before using these filters on your cable system.

\*\*\*\*\*

Please add sufficient postage

We will accept telephone orders for Visa & Mastercard



To Order Call  
**317-291-7262**



**ELECTRONIC RAINBOW**

6254 LaPas Trail • Indianapolis, IN 46268

# DR. "CHIP" MUNK SAYS



6805/68HC05/68HC11  
DEVELOPMENT TOOLS  
QUALITY + SERVICE  
+ AFFORDABILITY  
= **TECI**

Hundreds of "Chip" experts agree with Dr. Munk! TECI'S PC based micro-controller development tools are the most cost effective for veterans or beginners. Now, the same products used by the worlds largest corporations and universities are more affordable than ever. Our products offer many time saving features, a 6 month parts and labor warranty and toll free technical support. Call today for a free information package and price list.

- 6805 PRIMER FOR BEGINNERS. . . . . \$195.00
- 6805/68HC05/68HC11 CROSS ASSEMBLERS. . . . \$99.00
- 6805/68HC05 SIMULATOR / DEBUGGERS . . . . \$99.00
- 68705P3,P5,U3,U5,R3,R5 PROGRAMMERS FROM \$349.00
- 68HC705/68HC805 PROGRAMMERS FROM \$395.00
- COMPLETE PC BASED DEV. SYSTEMS FROM \$449.00
- 68HC05/68HC11 REAL TIME EMULATORS FROM \$895.00



CALL TOLL FREE 1-800-336-8321  
The Engineers Collaborative, Inc.  
Rt #3 Box 8C, Barton, VT 05822 USA  
TEL:(802)525-3458 FAX:(802)525-3451

CIRCLE 274 ON FREE INFORMATION CARD

# The Time Has Come...

...to send for the latest copy of the free Consumer Information Catalog.

It lists more than 200 free or low-cost government publications on topics like money, food, jobs, children, cars, health, and federal benefits.

Don't waste another minute, send today for the latest free Catalog and a free sample booklet. Send your name and address to:

**Consumer Information Center  
Department TH  
Pueblo, Colorado 81009**


A public service of this publication and the Consumer Information Center of the U.S. General Services Administration.
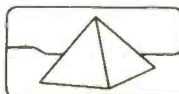
## Desk Top Enclosures



*How you start your project is important,  
But how you finish it can make a difference!*

- RIGID 1/16" ALUMINUM SHELL
- HARDWOOD TRIM
- CONTEMPORARY STYLING
- P.C.B. STANDOFFS
- \$9.99 - \$24.99
- FREE BROCHURE



**PYRAMID  
ELECTRONIC PRODUCTS**

15020 La Grange Road □ Suite 2100 □ Orland Park, Illinois □ 60462

Electronics Now, March 1993

# NEW

## TELEPHONE DECODER

### Ours is The BEST !

Here's why:

Our DS4000-MDCS includes

- Built-in Serial Port \* 2000 Dir and tone digits (displays to CALLER I.D. \* FREE soft
- \* Help screens \* Mem
- THE ONLY UNIT W
- from TV, Radio Br
- etc.) \* Operate
- Scrolling LCD
- \* 30 DAY M
- Digit Mer
- type with
- software \* A
- OFF \* OURS IS
- MICROPHONE (c
- CELLULAR - PHON
- on single 9V battery \* S
- MONEY BACK GUARAN



Here's why:

- Logs BOTH pulse
- digits \* Built-in
- data capture
- OURS IS
- ches digits
- \* - PHONES,
- \* 9V battery \*
- set on Serial Port
- Serial Port \* 2000
- tone digits (displays
- EE PC IBM-compatible
- Keeps data while turned
- ONLY UNIT WITH BUILT-IN
- TV, Radio Broadcasts, nearby
- Operates 24 hours continuous
- port Automatic Baud Set \* 30 DAY
- Guaranteed satisfaction!

from \$179.00 (Base unit)  
DEALER INQUIRIES WELCOME

## ! DON'T READ THIS AD




The IMPC-620 Converter

Attn: Caller ID Programmers/Developers

- DOS Caller ID development "Toolbox"
- \* Decode/Capture Software source - \$15
- \* CID test generator software - \$105
- \* CID generator board, rings 2 phones and delivers Caller I.D. messages - \$165

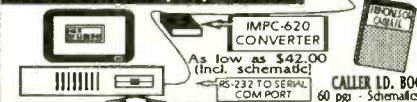**CALLER ID - COMPUTER  
Interface / Pop-Up TSR**



As low as \$42.00 (Incl. schematic) IS-232 TO SERIAL COM PORT

CALLER I.D. BOOK 60 pp - Schematic & Theory \$14.50 w/purch

International MicroPower Inc.  
65 Palm Drive, Camarillo, CA 93010  
1-800-992-3511 MC / VISA

CA Residents MUST add sales tax  
All orders add \$3.50 S&H (\$7.00 if COD)



**ACE**  
COMMUNICATIONS  
ACE Communications Monitor Division  
10707 East 106th Street Fishers, IN 46038

800 445 7717  
317 842 7115

## Scanner & Shortwave

### AOR AR1000XLT \$449.00 AM Broadcast to Microwave 1000 Channels



500KHz to 1300MHz coverage in a programmable hand held. Ten scan banks, ten search banks. Lockout on search and scan. AM plus narrow and broadcast FM. Priority, hold, delay and selectable search increment of 5 to 995 KHz. Permanent memory. 4 AA ni-cads and wall plus cig charger included along with belt clip, case, ant. & earphone. Size: 6 7/8 x 1 3/4 x 2 1/2. Wt 12 oz. Fax fact document # 205.

### AR2500 \$449.00 2016 Channels 1 to 1300MHz Computer Control



62 Scan Banks, 16 Search Banks, 35 Channels per second. Computer control for logging and spectrum display. AM, NFM, WFM, & BFO for CW/SSB. Priority bank, delay/hold and selectable search increments. Permanent memory. DC or AC with adaptors. Mtng Brkt & Antenna included. Size: 2 1/4H x 5 5/8W x 6 1/2D. Wt. 11lb. Fax fact # 305

### AR3000 \$1195.00 400 Channels 100KHz to 2036MHz



Extreme coverage, excellent sensitivity, plus processor controlled band pass filtering and attenuation to eliminate interference. Top rated receiver in its class, offers AM, NFM Wide FM, LSB, USB, CW modes. RS232 control. Lockout in search. 4 priority channels. Delay & hold & Freescan modes. AC/DC pwr cord and whip ant. included. Size: 3 1/7H x 5 2/5W x 7 7/8D. Wt 2lbs., 10oz. Fax fact document #105.

### Free Stuff

Demo disk of SCS (scanner control system) software for AR 3000 & AR2500. Call toll free to order. Also, Free with AR2500: Control software, a \$49.95 value. Allocation chart of all voice frequencies. Dial Fax Facts for doc. #999.



Dial 317 849 8683 to get instant tech information FREE from your Fax!

You can obtain specs and info on these products and more by dialing our Fax Facts automated service. Call our number from your fax, then request the document as listed below. Start your fax and the document will start printing immediately on your fax!



## Mobile Scanners

### Bearcat 760XLTM \$249.95 100 Channel 800 MHz



Five banks of 20 channels each. Covers 29-54, 118-174, 406-512 and 806-954MHz (with cell lock). Features scan, search, delay, priority, memory backup, lockout, service search, & keylock. Includes AC/DC cords, mtng brkt, antenna. Size: 4 3/8 x 6 15/16 x 1 5/8. Wt: 4.5lbs. Fax fact document #550.

### Bearcat 590XLTX \$199.95 100 Channel 11 Band




Five banks of 20 channels each. Covers 29-54, 118-174, and 406-512MHz. Features scan, search, delay, priority, memory backup, lockout, service search, & keylock. Includes AC/DC cords, mtng brkt, antenna. Size: 7 3/8 x 6 15/16 x 1 5/8. Wt: 4.1lbs. Fax fact document #570.

### Bearcat 560XLTX \$99.95 16 Channel 10 Band



Compact, digital programmable unit covers 29-54, 136-174, and 406-512MHz. Features scan, WX search, delay, priority, memory backup, lockout, review, & auto delay. Includes AC/DC cords, mtng brkt, antenna. Size: 7 3/8 x 2 1/2 x 1 5/8. Wt: 2.5lbs. Fax fact document #560.

### Trident TR-2C \$69.95

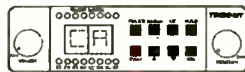

### Scan/CB. Optional laser/wide radar

Scans pre-programmed by state channels in low, high, UHF & T bands. Weather, 40 ch. CB receive plus mobile relay. Size: 5 5/8 x 4 7/8 x 1 3/4. Wt: 1.5lbs. Fax fact document #580.

**Mag Mount Antenna.** Easy to install whip antenna with 20' of coax & heavy duty magnet BNC MA 100 \$19.95  
**Base Antenna.** 25 to 1000MHz coverage with 50' of coax. All mounting hardware included. BNC AS 300 \$59.95  
**External Speaker.** Base or mobile mount. MS190 \$19.50  
**Wide Band Pre-Amp.** Variable gain up to 20dB covers 100 KHz to 1500MHz. 9Vbatt included. BNC. GW-2 \$89.00  
**Interference Filter.** Filters and eliminates common causes of interference to scanners. BNC. Model MPIF-1. \$59.00  
**Downconverter.** Converts 800MHz freqs to 400MHz for 3 band scanners. Quartz locked, 9V batt. DC89. \$89.00  
**Extended Warranties & Service.** Extended warranties available for most models. Call for quote. Out of warranty service by ex-Bearcat/Regency factory techs. Call for quote.

## Hand Held Scanners

### AOR 900 \$239.95 100 Channel 800 MHz Five scan banks 5 search banks. Covers 29-54, 118- 174, 406-512 and 830-950 MHz (no cell lock). Features scan, search, delay, priority, permanent memory, lockout, backlight, & keylock. Includes AC/DC adaptor, belt clip, antennas. Size: 5 3/4H x 2W x 1 1/2D. Wt: 12oz.. Fax fact document #650.



### Bearcat 200XLTN \$229.95 200 Channels 800MHz

Ten scan banks plus search. Covers 29-54, 118-174, 406-512 and 806 956MHz (with cell lock). Features scan, search, delay, 10 priorities, mem backup, lockout, WX search, & keylock. Includes NiCad & Chgr. Size: 1 3/8 x 2 11/16 x 7 1/2. Wt. 32 oz. Fax Facts # 450



### Bearcat 100XLTN Now \$159.95 100 Channels, Keyboard Programmable. Similar to 200XLTN above without 800MHz. Fax facts #460

### Bearcat 70XLTP Only \$139.95 20 Channels Keyboard Programmable. 10 Band Hand Held with Ni-Cads & Charger. Fax facts #470

### Bearcat 55XLTR Now \$99.95! 10 Channels Keyboard Programmable. 10 Band with LCD. Requires 5AA's. Fax facts #480

## Table Top Scanners

### Bearcat 855XLTE Now \$179.95! 50 Channels Keyboard Programmable with 800MHz LCD display, lock, priority, Search, WX, Fax facts #655

### Bearcat 142XLM Only \$87.95 16 Channels with 10 bands. LED display, lockout, priority, WX scan, review key and memory backup. Fax facts #660.

### Bearcat 147XLJ Now \$89.95 16 Channels with 10 bands. Track tuned, LED display, priority, WX search, review, memory backup. Fax facts #670.

### Bearcat 172XLM Only \$124.95 16 Channels with 10 bands. Track tuned, LED display, priority, WX search, review, memory backup. Fax facts #680.

### Bearcat 800XLX \$239.95



12 bands and 40 channels with 800MHz and nothing cut out. AC or DC. Fax facts #690.

## 2 Way Radios

VHF hi band programmable mobiles as low as \$299.95. Call for quotes or Fax Fact #755

Call Toll Free, 24 Hours a Day! Dial 1-800-445-7717. Fax Order Line 1-800-448-1084

800 numbers operational in all 50 states, plus Canada. For international voice lines, dial 317-842-7115 or fax 317-849-8794

ACE Communications 10707 East 106th Street, Fishers, IN 46038

Service & Support hours: Mon. - Fri. 9 A.M. to 6 P.M., Sat. 10-4 EST. MasterCard, Visa, Checks, Approved P.O.'s & C.O.D. (add \$5.00) & AMEX (add 5%). Prices, specifications and availability subject to change. Flat rate shipping & handling charge, \$4.95 per unit. Express shipping available, no express C.O.D. One week trial, no returns accepted two weeks after original receipt without substantial restocking charge. All units carry full factory warranty. Indiana residents add sales tax.



CIRCLE 212 ON FREE INFORMATION CARD

www.americanradiohistory.com





# Motorless Motion!

Connect Muscle Wires™ to a battery or other power source and watch them contract in length up to five percent! Remove power, and they relax and are ready for millions more cycles.

Create direct linear action without heavy gears, coils, or motors. Use Muscle Wires in robots, models, planes, railroads — anywhere you need small, strong all-electric motion.

## Q&A

### What Are Muscle Wires?

Muscle Wires are highly processed strands of a nickel-titanium alloy called *nitinol*. At room temperature they are easily stretched by up to 5% of their length. When conducting an electric current they return to their original "unstretched" shape with a force thousands of times their weight.

### How strong are Muscle Wires?

The force a wire pulls with varies with size, from 35 to 330 grams. For more strength, use several wires in parallel.

### How fast can Muscle Wires activate?

They contract as fast as they are heated — as quickly as 1/1000 of a second. To relax, the wire must cool again. Rates of many cycles per second are possible with active cooling.

### Flexinol Muscle Wire Specifications

Wire Diameter	50 $\mu\text{m}$	100 $\mu\text{m}$	150 $\mu\text{m}$
Resistance	510 $\Omega/\text{m}$	150 $\Omega/\text{m}$	50 $\Omega/\text{m}$
Contract Force	35 grams	150 grams	330 grams
Typical Current	50 mA	180 mA	400 mA

### How much power do Muscle Wires need?

Power varies with wire diameter, length, and surrounding conditions. Once the wire has fully shortened, power should be reduced to prevent overheating.

### What are the advantages of Muscle Wires?

Small size, light weight, low power, very high strength-to-weight ratio, precise control, AC or DC activation, long life and direct linear action and much more!

Get our new 96 page Book and Muscle Wire Sample Kit. It has 20 cm of 50  $\mu\text{m}$ , and 40 cm each of 100 and 150  $\mu\text{m}$  diameter Muscle Wires (1 meter total), plus crimps & instructions — everything you need to get moving today!

Ask for our FREE Muscle Wires Technical Brochure

TOLL FREE 24 Hour Order Line  
**800-374-5764**

VISA MasterCard

**Mondo-tronics**

Book and Sample Kit  
only

**\$29.90**

Plus \$4.00 P&H  
CA orders add tax

International Orders Welcome! First Class P&H: \$9.00

524 San Anselmo Ave. #107  
San Anselmo, CA 94960  
Questions: 415-455-9330  
Fax: 415-455-9333  
Internet: mondo@holonet.net

## ELECTRONIC SHOPPER CLASSIFIED

### MISCELLANEOUS ELECTRONICS FOR SALE

**TRANSIENT SURGE** and ground fault protection now in one complete unit. \$98.95 S/H \$5.00. NY residents add appr. sales tax. Safety Unlimited, 1743 Baldwin Road, Yorktown Hts., NY 10598.

**USED "Sweet Art" computer cake decorating machine.** Can reproduce photos using edible food color on cakes. Widow must sacrifice. Make offer. (619) 944-7244.

**RF EQUIPMENT:** Blonder Tongue modulators (6) \$200.00 — \$400.00, channel 6 processors (2) \$250.00, output combiners (2) \$150.00. Pico Macom band pass filters (4) \$200.00. Equipment cabinets 42" high with doors (2) \$250.00. All excellent condition. Call (602) 483-6621.


### PLANS-KITS-SCHEMATICS

**DESCRAMBLER KITS.** Complete cable kit \$44.95. Complete satellite kit \$49.95. Add \$5.00 shipping. Free brochure. No New York sales. Summit RS, Box 489, Bronx, NY 10465.

**BUILD YOUR own neighborhood FM stereo or television station.** Send SASE for complete catalog. **Sunset Electronics**, 16776 Bernardo Center Drive, Suite 110B, San Diego, CA 92128.

**BUILD — FIVE digit, ohms, capacitance, frequency, pulse, multimeter.** Board and instructions \$9.95. **Bagnal Electronics**, 179 May, Fairfield, CT 06430.

### SPY ON THE EARTH

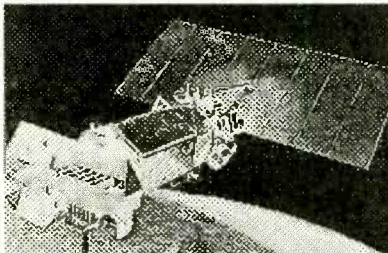

See live on your PC what satellites in orbit see

Learn how you can benefit greatly from this exciting new technology. Send \$25 (\$30 air, \$35 overseas) for our *fantastic* 12 diskette set of professional quality copyrighted programs (IBM type) that does satellite tracking, data acquisition, image processing, file conversion and much more. Diskette package includes all programs, C language source code for a popular satellite image acquisition program, hardware schematics, catalog and \$25 discount certificate.

Reception guaranteed Worldwide  
Absolutely legal  
No satellite dish needed

For FREE information log on to our bulletin board with your MODEM at (718) 740-3911 or call (718) 468-2720, to place an order. Buy with confidence. We've been in business since 1956.

**VANGUARD Electronic Labs**  
Dept. EN, 196-23 Jamaica Ave.  
Hollis, NY 11423

**FM STEREO TRANSMITTER** kit will broadcast any audio signal to FM stereo radios throughout your home. Uses unique BA1404 IC. Complete kit: PC board/components — \$24.00. Visa/MC. **TENTRONIX**, 3605 Broken Arrow, Coeur d'Alene, ID 83814. (208) 664-2312.

**BARE BONES EPROM** programmer. Plans/MS-DOS disk \$15.00. Also parts/kits/assembled. Sergeant, 809 W. San Antonio, San Marcos, TX 78666.

**Z80 SBC** \$60.00. 8K ROM, 8K RAM, 48 bits I/O. **M6809 SBC** \$60.00. 8K ROM, 8K RAM, 32 bits I/O. **64180 SBC** (surplus) \$65.00. 64K ROM, 64K RAM, One CIO, stepping motor driver, power supply. 24 output pins, 8 bit A/D converter. **J&M Inc.**, 83 Seaman Road, West Orange, NJ 07052, TEL: (201) 325-1892.

**SINGLE BOARD COMPUTERS** — An 8051AH based SBC with RS-232 circuitry; socketed 8K EPROM; 128 byte RAM; large breadboard area; 14 I/O ports. **FREE** programming software. \$29.75 (kit) or \$40.75 (assembled). Suncoast Technologies, PO Box 5835RE, Spring Hill, FL 34606.

**ASSEMBLY LANGUAGE BASICS** for the 8051. A beginners guide to the world of .ASM programming. This 60+ page booklet contains detailed instructions and working programs. Includes 8051 initialization codes, I/O. serial port and LCD module programming. Also includes schematics and programs to build; telephone dialer, LCD dialing displays and **MORE**. Only \$16.00 (includes 360K .ASM program disk) Suncoast Technologies, PO Box 5835RE, Spring Hill, FL 34606.

**DESCRAMBLING, NEW secret manual.** Build your own descramblers for cable and subscription TV. Instructions, schematics for SSAV1, gated sync, Sinewave, (HBO, Cinemax, Showtime, UHF, Adult) \$12.95, \$2.00 postage. **Cabletronics**, Box 30502S, Bethesda, MD 20824.

**STAINLESS STEEL SCREWS, nuts, & washers.** Fastener kits. Free catalog. **"RUSTY BOLT,"** Box 708S, North Attleboro, MA 02761.

**"ELECTRONICS ENGINEERING"** starter kits are here. Prepared by somebody who worked for over 20 prestigious electronics companies, he knows. Also, "Nuclear Physics" starter kits are back! Masterpiece quality. \$19.95 per kit, \$34.95 both. Try them. Customers satisfaction continues to be job one. Farah, Farah, PO Box 2464, Sarnia, Ontario N7T 7T1. (519) 332-4824.

**DESCRAMBLER KITS.** Complete cable kit \$44.95. Complete satellite kit \$49.95. Add \$5.00 shipping. Free brochure. No New York sales. Summit RS, Box 489, Bronx, NY 10465.

### SATELLITE EQUIPMENT

**VIDEOCIPHER II DESCRAMBLING** manual. Schematics, video, and audio. Explains DES, Eprom, CloneMaster, 3Musketeeer, Pay-per-view (HBO, Cinemax, Showtime, Adult, etc.) \$16.95, \$2.00 postage. Schematics for Videocypher Plus, \$20.00. Schematics for Videocypher 032, \$15.00. Collection of software to copy and alter Eprom codes, \$25.00. **Cabletronics**, Box 30502S, Bethesda, MD 20824.

### TELEPHONE

**MONITOR CORDLESS** and cellular phone conversations easily. Send \$8.00 to: Smaslar, 8 Banks Ave., Johnson City, NY 13790.

### REPAIRS-SERVICES

**CREATIVE ELECTRONIC** technician looking for R&D work that can be done at home. Analog or digital circuits. D.Cousins, 13 Tioga St., Newton Falls, OH 44444.






### DELUXE ROBOT BASE

Two reversible DC motors with 4" wheels, battery compartment with 3V and 9V out, H-Bridge driver board. TTL input. Dia. 11". Runs on six "D" cells. Schematic included. **\$29.95 each**

### SCANNER PACKAGE

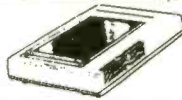

386 DX 20 MHz system, 3 MB RAM, 360K 5.25" floppy, 20MB hard drive, Hercules-compatible mono monitor. Canon flatbed scanner with J Laser AT-3 interface, drivers and software. **\$899.00**

### CANON FLATBED SCANNER

300 x 300 DPI, with PC I/O card, cable, software and documentation. Reconditioned. **\$299.95**

**WE BUILD CUSTOM SYSTEMS!**  
Call or FAX for Price Quote!

### XT CASES

Brand new in box, with hardware. **\$17.95**

### AT CASES

Brand new. Missing some hardware. **\$19.95**



**CERMETEK  
CH1770  
INTELLIGENT  
MODEM**  
300/1200 BPS.  
**\$14.95 Each**

### POCKET REFERENCES!

• **Pocket Ref** - 480 pages of tables, maps, formulas, constants and conversions that fit in your shirt pocket (3.2" x 5.4" x 0.6"). The greatest pocket reference of all time! **\$9.95 each**

• **Pocket PCRef** - 320 pages of hard to find information for IBM PC's and compatibles, including seventy pages of hard drive listings. Best of all, it fits in your shirt pocket (3.2" x 5.4" x 0.4"). **\$14.95 each**



### ATARI 5200 TRACK BALL CONTROLLER

Don't use Atari? Useful for robotics applications! Contains two 15° shaft encoders on shafts with ball bearings, 2.24" dia. ball, logic board, two 12-key membrane keypads. Resolution better than 0.015" on two axes. **\$12.95 each**



**MS-DOS 5.0**  
3.5" diskettes. New, in box. **\$24.95**

### INTECH A301

High voltage FET OP - AMP.  
Gain = 100,000 ± 115V,  
CMRR = 100dB. List over \$200. New. With spec sheets. **\$69.95**



### INTECH A2974

(CY2235) General purpose 12-bit DAC. List over \$150. New. With spec sheet. **\$49.95**

### 150 WATT REGULATED SWITCHING SUPPLY

Wow! 36 Volt DC - 4.2 Ampere output, 120-220 Volt AC input. Attractive black shockproof case, 4.75" x 3" x 10.5". Designed for Convergent Computer Co. **\$19.95 each**



### HEAT SINK ASSORTMENT

50 heat sinks. Popular sizes and styles. **\$2.95**



### 10 TURN POT KNOB

Clardial Model 400. 0.25" shaft diameter. Shown approx. actual size. **\$4.95 each**

### IR REMOTE CONTROL/RECEIVER KIT

Your imagination is the only limitation for the uses of this device. The controller is new and fully assembled. It has thirty function buttons, each of which causes the transmitter to emit a unique infra-red pulse train. Originally, the receiver was mounted in a satellite receiver; the satellite receivers are all gone but we have reproduced the IR receiver and are offering it here in kit form. The IR RECEIVER KIT can be assembled in less than an hour. We also furnish the IC which served as the IR decoder and controller. A decoder can be breadboarded around this chip. To make life easier, we have all the schematic diagrams, including the diagram of the satellite receiver. **\$19.95**



### PAY RADIO DECODER (CODART)

Pay radio? That's right. Part of a system that broadcast purchased programs late at night, these Codart units would turn on one of two tape recorders when a coded tone was broadcast. Contains a Z-80 with 4K of EPROM, 2K of battery-backed up RAM, 18-key keyboard, 8-digit display and relays for the recorders. Reprogram it to make your own stereo or lamp timer, or a time lock to keep the kids from watching too much TV. With documents. **2 for \$19.95**




### LITZ WIRE

One size only: 5x44. Ideal frequency range 350-850 KHz. Part #NELA 5/44 SPSN. We have several spools from 0.25 to 1 Lb., sold by the hundredth pound at 49¢ per unit. 0.01 Lb. = approx. 130 ft. For example, 0.27 Lb. spool at 49¢/0.01 Lb. = \$13.23, and is approx. 3500 ft. Sorry, we do not cut. Subject to stock on hand.


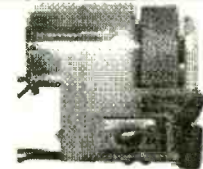
### JOHNSON PERMANENT MAGNET DC MOTOR

HG970 series. 24 VDC @ 2A (under load). Husky motor measures 2.75" L x 2" dia., with 0.25" dia. shaft on each end. New. **\$9.95 each**



### ROBOT SERVO MOTOR

5VDC bidirectional gearmotor with 3.3K SL feedback pot. Rubber drive wheel provides friction contact with outside world. **\$4.95 each**



### SWIVEL MAGNET

200 Gauss neodymium magnet mounted on a frame with ball bearing pivot. **6 for \$9.95**

### "N" TO "SMA" ADAPTER

**\$4.95 each**



### PICOFUSE BLOWOUT

1 A or 1.5 A (preformed leads) **20 for \$7.95**  
1.5 A (long leads) **10 for \$5.95**



### STUDIOLINE STEREOTRACK II BETTER THAN DBX!

Stereo separation greater than 90dB! Includes special receivers for autotrack signals, authorization codes \*FSK format). Microprocessor controlled varactor TV tuner, 10.7 MHz I.F. circuit. Includes DUAL compressor/expander circuitry for both left and right channels. Brand new! Comprehensive schematic package included!

Two Units, Schematic Pack - **Only \$49.95**  
**SOLD FOR EXPERIMENTAL USE ONLY!**  
**NOT INTENDED FOR USE ON PAY CABLE SERVICES.**



# ALLTRONICS

2300 Zanker Road • San Jose, CA 95131

VISA - MC - AMEX cards accepted. Minimum order \$15.00.

California residents add 8.25% sales tax. Shipping additional on all orders.

Phone (408) 943-9773 • Fax (408) 943-9776

Retail Store Hours:  
M-F 9-6 • Sat. 10-3

Also Visit:  
**ASCII ELECTRONICS**  
1020 Marietta Way  
Reno, NV 89431  
(702) 355-8822

# SILVER PLATING ON-THE-JOB. COOL CONDUCTIVITY. CONVENIENT ANYWHERE.

Cool-Amp is a proven product that silver-plates high amp connections (any connections) *on the job*. It is very simple to use. Simply clean the contact and apply with a damp rag. Cool-Amp adheres permanently. It is equal to electroplating in performance.



Use Cool-Amp to reduce maintenance time. Use it on all current carrying connections. Prevent power losses and overheating from copper oxide. Time-tested for over 35 years.

**ORDER FACTORY DIRECT**

## COOL-AMP

**Cool-Amp Conducto-Lube Company**


15834 Upper Boones Ferry Road • Lake Oswego, Oregon 97035  
(503) 624-6426 • Fax (503) 624-6436


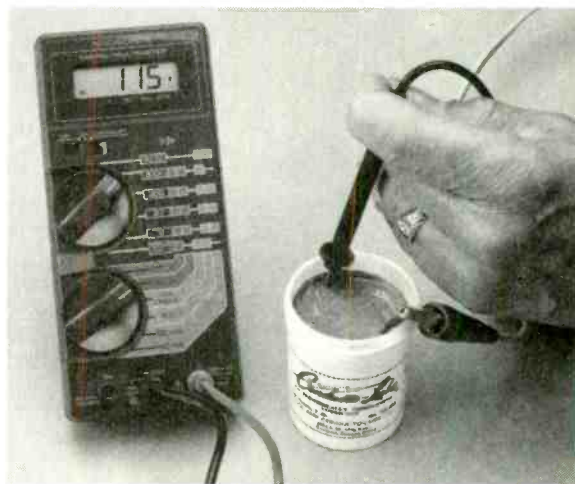
# IF YOU NEED A CONDUCTIVE LUBRICANT, YOU NEED CONDUCTO-LUBE.

Conducto-Lube is an excellent lubricant which is highly conductive because it contains pure silver. Conducto-Lube was originally developed for use in high speed air blast breakers to improve conductivity and lubrication. (Other lubricants are often non-conductive, even resistant.)

The uses of Conducto-Lube continue to expand — from switches and breakers, to electronics and virtually *any* application where a conductive lubricant is needed.



Conductivity is demonstrated by inserting 115 VAC test prongs into a container of Conducto-Lube and establishing a circuit. Photo shows low voltage (115 VAC) continuity through a container.

**ORDER FACTORY DIRECT**

## *Conducto-Lube*

**Cool-Amp Conducto-Lube Company**

15834 Upper Boones Ferry Road • Lake Oswego, Oregon 97035  
(503) 624-6426 • Fax (503) 624-6436

# ELECTRONIC SHOPPER CLASSIFIED




## Knight Patrol® II Talking Security System

A high-end alarm at an affordable price!

- Stops burglars **before** they break-in by verbally warning them away.
- High quality female voice with 220 word vocabulary.
- RS-232 port connects to any IBM PC compatible for complete customizing and status (software included).
- 24 zones monitor sensors inside and outside plus an auxiliary alarm and supervised fire zone.
- Automatically switches intercom speakers to alarm.
- Two 12 Amp. relays for sirens and control functions.
- Complete alarm status from keypad, PC, or verbally.
- Speakers announce location of prowlers.
- Alert/Sleep monitoring modes.
- Alpha-numeric LCD keypad.
- Multiple user alarm codes.
- Continuous power monitoring.
- Expandable and MORE!
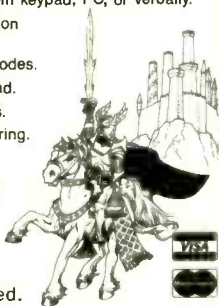
### Paladin Electronics

19425-B Soledad Cyn. Rd.  
Suite 333 Dept. RES  
Canyon Country, CA 91351  
(805) 251-8725  
Dealer enquiries invited.



## BUSINESS OPPORTUNITIES

**EASY WORK!** Excellent pay! Assemble products at home. Call toll free 1 (800) 467-5566 ext. 11068.

**GUARANTEED! \$1,000.00 weekly.** Home employment directory. Start immediately. Rush \$10.00: PW House Enterprise, Box 438764, Chicago, IL 60643.

**TELEVISION & STEREO business.** Good income year round. Ketchikan, Alaska, Box 8060 99901. Phone (907) 225-2350.

## COMPUTER HARDWARE

**IBM PC and laptops video digitizer,** connects to camcorder, 640 by 480 resolution. 256 gray levels \$89.98. Demo disk \$3.00, information \$1.00. Colorburst, Box 3091, Nashua, NH 03061. Phone (603) 891-1588.

**386/486 CPU heat sinks,** patented, best performance anywhere, u-install. Send \$18.00/1, \$30.00/2. C. NOGAL, Box 2123-re, Buffalo, NY 14240.

**COMPUTER CONTROLLED security system for home or business.** Use any IBM PC compatible computer. Includes infrared, various sensors and software. State of the Art security at a reasonable cost. Send for free brochure. Weick Products, 8132 Firestone Ste 119, Downey, CA 90241.

## COMPUTER SOFTWARE

**VIRUSFREE SHAREWARE; 29 MEGABYTES \$29.00,** add \$29.00/29MB increment up to 580 MEGABYTES. \$3.00 shipping/100MB. 24hr order/info/fax: 1 (800) 876-8496, Visa-MC. **SHARE-NET,** POB 12368, Oklahoma City, OK 73157.

**PC BOARD and schematic design software for the IBM PC/compatible.** Create professional PCB layouts (with autorouting — requires EGA) and electronics schematics (CGA) with these inexpensive shareware programs. Both for \$7.00. **SUNCOAST TECHNOLOGIES,** PO Box 5835RE, Spring Hill, FL 34606.

**PROGRAM THE 8051 microcontroller in Basic** with this PC/compatible shareware collection. Disk contains Editor, Basic Compiler, Assembler, Disassembler, Procomm plus 3 surprise programs. Only \$7.00 from **SUNCOAST TECHNOLOGIES,** PO Box 5835RE, Spring Hill, FL 34606.

**CROSS PART DATABASE SOFTWARE:** Crosses common electronic component part numbers to **SYLVANIA** and **PHILIPS** replacements. Contains approximately 31,000 part numbers. 3-3½ inch disks. **CROSS PART IDENTIFY SOFTWARE:** Crosses prefixes of electronic component part numbers to their manufacturer. **DATABASE — \$38.00 IDENTIFY — \$10.00 MC.** Visa, check, money orders accepted. **CPS SOFTWARE,** PO Box 28, Blackwell, OK 74631. (405) 363-4330.

**50-MEGABYTES programming SRC/utilities. C/ASM/PAS/Basic \$50.00,** \$3.00 shipping: 24hr order/info/fax: 1 (800) 876-8496, Visa-MC. **SHARE-NET,** POB 12368, Oklahoma City, OK 73157.

**SHAREWARE! THOUSANDS OF IBM PROGRAMS.** \$3.00 S&H for 2 disks full plus catalog disk. American Software, PO Box 509, Suite M7, Roseville, MI 48066-0509.

**ELECTRONICS SOFTWARE.** From \$2.00 per disk. IBM 5.25". Free catalog on disk. Generic Software, Box 502, Dayton, OH 45401.

**CDROM MSDOS 550+ meg shareware, games, ham-radio, programming, etc.** Sept. 92 \$24.95. Caddies \$4.95 1 (800) 786-9907 (510) 947-1644 Fax.


**VIRTUAL REALITY...** Experience the future! Demos, games, huge! 6 programs, VGA, \$15.00. **CYBERSTATION,** Dept. E1, 12124 James St., Holland, MI 49424. Specify format.

**NEVER BEFORE! 20,000 shareware programs on three CD-ROM discs.** \$69.00 plus \$5.00 shipping. Astounding value! Dealers wanted! Crosley, Box 276H, Alburg, VT 05440. (514) 739-9328.

## EDUCATION

**TEACH YOURSELF electronics and digital basics.** Programmed courses. \$17.00 each, both \$29.00. Satisfaction guaranteed. **TEK,** 6050 NW 68th St., Parkland, FL 33067.

## Give Us A Look.

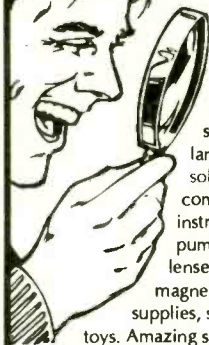

Thousands of unusual items for the electronically minded. Power supplies, batteries, lamps, switches, solenoids, electrical components, electronic instruments, tools, motors, pumps, fans, fiber optics, lenses, lab supplies, tape, magnets, containers, office supplies, science books, and toys.

Amazing secret source of surplus items 50% to 90% off original prices. Send the information card for a free catalog.



EST. ABOUT 1937

**AMERICAN SCIENCE  
& SURPLUS**

601 LINDEN PLACE • EVANSTON IL 60202

## GET ON AMATEUR TV

You don't need to take a Morse code test to transmit TV pictures. The new no-code ham license and *Secrets of ATV* is all you need to get started! The book is full of useful information on equipment, reference material and who to contact. Order *ATV Secrets* for only \$9.98 (\$2.00 S&H)

## YOU CAN PASS THE CODELESS HAM RADIO TEST AND WE GUARANTEE IT!

It's easy and fun with the **NARA Education Package.** You get Don Stoner's *Ham Radio Handbook*, IBM or Macintosh compatible software to test your knowledge after you have studied the book; an extensive list of Volunteer Examiners you can contact, the *FCC Rules and Regulations* for ham radio, a copy of *Amateur Radio King of Hobbies*, plus a bonus copy of our journal, *The Amateur Radio Communicator*, by mail. The **NARA Education Package** is only \$29.95 for the IBM or \$49.95 for the Mac version (\$3.00 S&H).

**Join NARA today** and enjoy the exciting world of ham radio — and beginners don't need to know the code! A one-year **NARA** membership & subscription to *The Amateur Radio Communicator* is only \$10.00.

**NARA**  
NATIONAL AMATEUR RADIO ASSOCIATION

**CALL US  
TODAY!!**

P.O. Box 598, Redmond, WA 98073  
Orders Only 1-800-GOT-2-HAM  
Inquiries (206) 869-8052



Save on cable rental fees!  
**CABLE TV  
DESCRAMBLERS**  
**WE'LL BEAT ANY PRICE**

JERROLD-TOCOM-ZENITH-HAMLIN-OAK  
PIONEER-SCIENTIFIC ATLANTA

- 24 HOUR SHIPMENTS!
- MONEY BACK GUARANTEE! • QUANTITY DISCOUNTS!

MASTER CARD / AMEX / VISA / C.O.D



Have make and model number of equipment used in your area ready.

CALL TOLL-FREE **1-800-284-8432**


**CABLE WAREHOUSE**

10117 West Oakland Park Blvd., Suite 515, Sunrise, FL 33351  
NO FLORIDA SALES

Anyone implying theft of service will be denied assistance.


**ACTIVE MICRO** We Want Your Excess Inventory

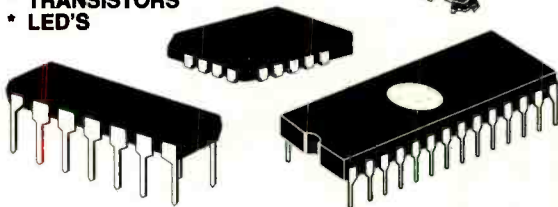- INTEGRATED CIRCUITS
- MEMORY (NEW OR USED)
- EPROMS (NEW OR USED)
- CIRCUIT BOARDS
- DIODES
- TRANSISTORS
- LED'S



Tel **310-494-4851** Fax **310-494-4913**  
1891 Obispo Ave Signal Hill, CA 90804

**Prototype it..... FAST!**

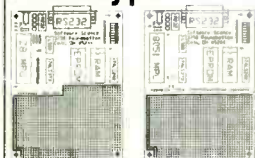

with ProtoQuick 8051 or Z8  
Complete single board computers  
Up to 32K EPROM and 64K RAM  
12 sq. in. plastic protoboard area  
RS232 C serial port w/ DB25 conn.  
On 8051 or EPROM w/ source code  
Assembled - ready to run - \$v. only  
MS-DOS cross assembler included

ProtoQuick Z8 and 8051  
**\$99.00** each  
Software Science  
3750 Roundstone Road  
Cincinnati, OH 45244  
(513) 561-2060

Run prototype applications or experimental hardware from the serial port - WITHOUT PROGRAMMING!

**Quality Microwave TV Antennas**



WIRELESS CABLE - IFTS - MMDS - Amateur TV  
Ultra High Gain 50db(+) • Tuneable 1.9 to 2.7 Ghz.  
• 55-Channel Dish System \$199.95  
• 36-Channel Dish System \$149.95  
• 20-Channel Dish System \$124.95  
• Optional Commercial Grid Antenna (not shown) Add \$50.00  
• Yagi Antennas, Components, Custom Tuning Available  
• Call or write (SASE) for "FREE" Catalog

PHILLIPS-TECH ELECTRONICS  
P.O. Box 8533 • Scottsdale, AZ 85252  
(602) 947-7700 (\$3.00 Credit all phone orders)  
MasterCard • Visa • American Express • C.O.D.'s • Quantity Pricing

Dish System  
LIFETIME WARRANTY

**CB RADIO OWNERS!**

We specialize in a wide variety of technical information, parts and services for CB radios. 10-Meter and FM conversion kits, repair books, plans, high-performance accessories. Thousands of satisfied customers since 1976! Catalog \$2.

**CBC INTERNATIONAL, INC.**  
P.O. BOX 31500RS, PHOENIX, AZ 85046

**COMPLETE "FCC" LICENSE PREPERATION**

- ★ GENERAL RADIOTELEPHONE LICENSE
- ★ RADAR ENDORSEMENT
- ★ ALL AMATEUR RADIO LICENSES

- ★ SECOND CLASS RADIOTELEGRAPH

- ★ BETTER POSITIONS
- ★ OPPORTUNITIES & HIGH PAY
- ★ EXCITING CAREERS

**GENERAL RADIOTELEPHONE OPERATOR LICENSE**

For years this FCC License has been highly sought after by ALL ELECTRONIC TECHNICIANS as required by most employers. This License has become the most highly respected "ticket" in the AVIONICS, MARINE, and ELECTRONICS field. The key to job opportunities, advancements and top pay. With the FCC license on your resume, the employer knows that the applicant has a firm grasp on RADIO ELECTRONICS.

A solid foundation that can be built upon to meet the demand of any job situation.

**1000's of Satisfied Customers**

Including tech schools, colleges, Avionics shops, military centers.

-ALSO FEATURING -

Merchant Marine Radio Officer Handbook, Landmobile and Marine Technical Handbook, and...

By popular request - "THE COMPLETE ELECTRONICS CAREER GUIDE". This will open your mind to the many job opportunities in the Electronics field. How & Where to find them. A must for beginners or anyone in electronics. (We offer Same Day Service-M.O., Cks, COD, MC/Visa & Invoice.)



**SECOND CLASS RADIOTELEGRAPH LICENSE**

The Marine Industry is continuously growing. This means lots of job opportunities. After six months training many earn \$45,000 to \$55,000 for a eight month year. Once you become a RADIO OFFICER the pay is even higher. Does this sound good? All you need is our "RADIOTELEGRAPH PACKAGE" to get started for your Second Class Radiotelegraph License.

**WHY TAKE CHANCES?**

Our most up-to-date Home Study MANUALS, AUDIOS, VIDEOS, or PC DISKS. Make it so reasonable, fast and easy.

**REASONS WHY EFFECTIVE**

- ✓ Actual test experience
- ✓ Concise and to the point
- ✓ Quick reference
- ✓ Only relevant information
- ✓ Simply and clearly written
- ✓ Seminar experience

**\*\*\*WHAT THEY SAY\*\*\***

"The day I took the test everyone who passed had your material." J.D., Puerto Rico.  
"Your study questions were nothing short of outstanding. Thank you for such a complete course." E.T., Lemon Grove, CA.  
"I was well prepared and actually enjoyed taking the exam." M.A.E., Walford, MD.

**WPT Publications FREE DETAILS**


7015 NE 61st Ave • Vancouver, WA 98661  
(206) 750-9933 • 1-800-800-7588

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

CIRCLE 280 ON FREE INFORMATION CARD

## Touch Tone Decoder Display

From  
**MoTron Electronics**

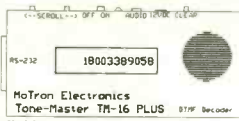

The Tone-Master™ Line of Hand Held Tone Decoder Display Products. Decode Touch Tones from a telephone, scanner, tape recorder, or nearly any audio source.

- ✓ 16 digit LCD display with 80 character scrollable memory
- ✓ High speed decoding—up to 25 digits per second
- ✓ Portable 9 volt battery or external power operation
- ✓ Completely stand-alone, no computer necessary
- ✓ Metal enclosure with built-in monitor speaker, only 2.75" x 6.1" x 1.2"
- ✓ TM-16 Plus includes RS-232 output and Software for optional automatic date/time/number logging using your computer
- ✓ 1 year Warranty on parts and labor
- ✓ 30 day Money Back Guarantee (less shipping and handling)

TM-16 Standard Model	\$229.00	PS-12 AC Power Adaptor	\$10.00
TM-16-PLUS RS-232 Model	\$299.00	C-904 Laptop Computer Cable	\$10.00
(IBM Compatible logging Software included)		C-905 Desktop Computer Cable	\$10.00

S/H \$5 USA/Canada, \$15 Foreign. Visa, MasterCard & American Express Accepted.  
MoTron Electronics • 310 Garfield Street Suite 4 • Eugene OR 97402  
Orders: (800) 338-9058 • Info: (503) 687-2118 • Fax: (503) 687-2492


## SHOPPER CLASSIFIED

---

### COMPONENTS

**ELECTRONIC COMPONENTS**, Great prices, hard to find items catalog. Large SASE to KA7QJY Components, Box 3893, Logan, Utah 84323.

**STAINLESS STEEL SCREWS**, nuts, & washers. Fastener kits. Free catalog. "RUSTY BOLT," Box 708S, North Attleboro, MA 02761.



## The Pocket Programmer

The portable Eeprom programmer that uses the printer port of your PC instead of an internal card. The software has 24 easy to use functions and programs 27/25/28/68764 & Cmos from 16K (2K x 8)—2M (256K x 8) Eproms (32 pin socket, UpGradeable to 8Meg). Adapters available for MCU's, 40-Pin Eproms, 5-Gang and Eeprom Emulator to 32K x 8.

**\$129.95**

**INTRONICS, INC.**  
Box 13723  
Edwardsville, KS 66113  
(913) 422-2094

Add \$3.00 for shipping.  
Add \$3.75 for COD.  
Visa/Master Charge

## The Time Has Come...

...to send for the latest copy of the free Consumer Information Catalog. It lists more than 200 free or low-cost government publications. Send your name and address to:

**Consumer Information Center  
Department TH, Pueblo, Colorado 81009**

## Cable Test Aids

Orders only      Information  
1-800-452-7090      (310)867-0081

Test chips for JERROLD, TOCOM, ZENITH, S.A. & more. Puts cable boxes in full service mode. Easy installation. Zenith only \$39.95. Most others under \$50ea. Quantity prices available.  
No Cx. miles. Not for use in cable co. owned equip. For use as a test aid only.

### CELLULAR TELEPHONE OWNERS

DISCOUNT PRICES: ACCESSORIES, ALL BRANDS  
CAR-HOME, TRICKLE BATTERY ELIMINATORS-  
CHARGERS, REPLACEMENT BATTERIES, LEATHER CASES, MINI-BUTTON, REPLACEMENT ANTENNAS, ETC. CALL-WRITE CAT. & \$5 DISCOUNT COUPON.

**LESS BUSTER'S ELECTRONICS**  
2039 CIVIC CENTER DRIVE STE. #178E  
N.L.V., NV. 89030 TEL: 1-702-642-0325

### AUDIO-VIDEO-LASERS

**IBM PC** and laptops video digitizer, connects to camcorder, 640 by 480 resolution. 256 gray levels \$89.98. Demo disk \$3.00, information \$1.00. Colorburst, Box 3091, Nashua, NH 03061. Phone (603) 891-1588.

### MISCELLANEOUS ELECTRONICS WANTED

**WANTED: EXCESS ELECTRONIC INVENTORY.** IC's, MEMORY EPROMS, PAL's, LED's, DIODES, TRANSISTORS. CALL ACTIVE MICRO, (310) 494-4851 OR FAX (310) 494-4913.

### SURVEILLANCE


COUNTERSURVEILLANCE Electronic Devices  
Miniature Transmitter Kits.. \$29.95  
Voice Changers, Phone Scramblers, Vehicle Tracking, Phone Recording Systems, Bug & Phone Tap Detectors, & More!

CALL IDENTIFIER device • displays callers phone number before you answer with date & time of call...\$49.95  
FOR CATALOG SEND \$5.00 TO...  
**EDF** P.O. Box 337, Buffalo, NY 14226 (716) 691-3476

## Tunable Notch Filters and Telephone Recording Equipment

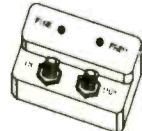**Eliminates...**

- Beeping and Buzzing
- Severe Interference



Assembled and Tested Filters as low as \$16 each in quantities of 10 or more

Kit Filters as low as \$8 each in quantities of 21 or more

**Micro Thinc.**  
P.O. Box 63-6025  
Margate, FL 33063

Brochure \$1      (305)-752-9202

Take Stock in America

# U.S. SAVINGS BONDS



## DOS IN ROM!

MVDISK1 64k.....\$75  
MVDISK2 360k...\$150  
MVDISK3 1.44m...\$195

# \$75

WORLD'S SMALLEST PC !!!



ROBOTS ALARMS RECORDERS OOS

THREE EASY STEPS: **\$27** 1K QTY  
1. Develop on PC  
2. Download to SBC  
3. Burn into EPROM **\$95** SGL QTY

## 8088 SINGLE BOARD COMPUTER

- 2 PARALLEL      -LCD INTERFACE
- 3 SERIAL        -KEYBOARD INPUT
- PC TYPE BUS    -REAL TIME CLK
- BIOS OPTION    -BATTERY OR SV

FREE SHIPPING IN U.S.  
5 YEAR LIMITED WARRANTY

**MVS** Box 850  
Merrimack, NH  
(508) 792 9507


## NEW EASY PC


SCHEMATIC and PCB C.A.D

ONLY \$195

Includes

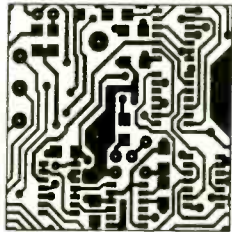- CGA, EGA & VGA compatible.
- Design large multi layer boards.
- One level pull down menu and quick keys for fast layout.
- Dot matrix, laser, plotter, Gerber & N.C. drill output
- 6 Month Free update  
Free Demo





7840 ANGEL RIDGE ROAD  
ATHENS OHIO 45701  
(614) 592 1810  
Visa & MasterCard Accepted

Electronics Now, March 1993



# NEW PRODUCTS



**ADAPTER KIT.** Aimed at lab and field-service technicians in telecommunications, data communications, and broadcast industries, the *Model 5748 Maxi-Universal Adapter Kit* from ITT Pomona allows users to adapt almost any coaxial and termination type to another, including the ability to sample uninterrupted signal continuity. Users can make their own adapter combinations, such as SMA-to-BNC or BNC-to-double banana plugs. The kit includes two male and female connectors each of BNC, TNC, SMA, "N," UHF, mini-UHF, "F," and RCA; six intermediate couplers; one double banana plug; one double banana jack; and a "T" sampler. All adapters have gold-plated center pins and silver-plated bodies. They are packaged in a durable, reusable plastic case.

The *Model 5748 Maxi-Universal Adapter Kit* costs \$199.—**ITT Pomona Electronics**, 1500 East Ninth Street, P.O. Box 2767, Pomona, CA 91769; Phone: 714-623-3463; Fax: 714-629-3317.

CIRCLE 24 ON FREE INFORMATION CARD

## PCBoards

## PCB ARTWORK MADE EASY!

"Are you tired of laying down tape or wire wrapping to make printed circuit art? End the nightmare with the *PCBoards Circuit Layout Program* for just \$99.00! Easily create single or double-sided circuit boards with professional results."

- Herc, CGA, EGA, VGA, & SuperVGA
  - Use mouse and/or keyboard
  - Built-in help screens
  - Dip and Sip footprint libraries
  - Build custom parts easily
  - Copper flood for building ground planes
  - Block move, copy, rotate, save, etc.
  - Comes with dot-matrix & laser output
  - Make your own films with 1x laser art
  - Gerber and Excellon output available
- Requirements: DOS 3.0 or later, 1 disk drive, 384k of RAM, IBM-PC or compatible

Download Demos from our 24hr BBS at (205) 933-2954

PCBoards Software Prices:		Add on Software:	
PCBoards Layout	99.00	PCRoute Autorouter	99.00
Gerber and Excellon Drivers	49.00	PCRoute+ Autorouter	149.00
Plotter Drivers	49.00	SuperCAD Schematic	99.00
Demo Package (all software)	10.00	SuperCAD+ Schematic	199.00

Use *PCBoards*, *PCRoute*, and *SuperCAD* as a "system" to create pcb art from a schematic!

PCBoards - 2110 14th Avenue South, Birmingham, AL 35205 / Ph. (800)473-PCBS Fax (205)933-2954

# Is your Cable Company Alienating You?



Say **NO** to unearthly rental fees!

Owning your cable equipment saves you the high cost of monthly equipment rental charges, and gives you control of your TV.

We have the *Best* in

## CONVERTERS and DESCRAMBLERS!

Everquest • Panasonic • Jerrold • Zenith • Pioneer  
Scientific Atlanta • Oak • Eagle • Hamlin • Tocom

# 1 800 624-1150



**FREE Catalog!**

**MP Electronics**

**CALL TODAY!**

P.O. Box 241296 • Omaha, NE 68124-5296

CIRCLE 291 ON FREE INFORMATION CARD

March 1993, Electronics Now

52A75

**MUSIC For The IBM**

- NOTATION - \$99.95
- SEQUENCING /RECORDING - From \$39.
- TRAINING - From \$39.
- MIDI Board - \$79.
- AdLib Sound Board - \$79.
- Sound Blaster Board - \$109.

**FREE CATALOG GREAT PRICES**

**OPTRONICS TECHNOLOGY**  
P.O. Box 3239  
Ashland, OR 97520  
(503) 488-5040



**B.S. & M.S.**  
**In Computer Science**

- Approved for tuition reimbursement by leading companies
- ALL COURSES THROUGH HOME STUDY
- Increase your earning power
- Approved Ada course available

**AMERICAN INSTITUTE OF COMPUTER SCIENCES**

For free information call:  
**1-800-767-2427**

**\$35 Logic Analyzer**

*The Real Logic Analyzer*

- 5 Input Capture channels via printer port
- High Speed 64K input capture buffer
- Full triggering on any input pattern
- Pre and post trigger viewing adjustable
- Automatic timebase calibration
- 4 Cursors measure time and frequency
- Save, print or export waveforms (PCX)

Turn your IBM AT or compatible computer into a fully functional Logic Analyzer. This software provides features not found on units costing thousands of dollars! A must for everyone working with digital signals. (Requires 286, 386 or 486 with EGA or VGA display)

**LOGIXELL ELECTRONICS**  
M11-2881 Richmond Rd.  
Ottawa, Ontario K2B 8J5  
Canada (613)828-4159  
Fax (613)828-8954

Specify 3.5 or 5.25" diskette and send check or MO for \$35 in US funds. Canada: send \$40 CDN. or Call/Fax/Send for FREE Info.

**AFFORDABLE DATA ACQUISITION**

**Prairie Digital, Inc.**

5 1/2 Digit - 18 Bit to RS232 Converter



**ONLY \$239**

**MODEL 70**  
Economical 5 1/2 Digit A/D Converter w/ RS232 Serial Control  
Equivalent resolution of 5 1/2 digit DVMs costing over \$1,000!

- Makes Accurate Voltage, Temp, & Pressure Measurements
- Includes User-Friendly Virtual Instrument Software
- Logs To Screen, Printer, Or Disk Data File
- Complete Package Includes Software, PC Cable, and Power Supply

For Affordable Data Acquisition, Call:  
**Prairie Digital, Inc.**  
846 Seventeenth St. reet • Prairie du Sac, WI 53578  
(608) 643-8599 • FAX (608) 643-6754



**ONLY \$79**

**MODEL 30**  
Turn your 386, XT, or AT into a data acquisition device!

- Control Relays, Lights, Motors, Robotics, & More
  - Measure Temp, Pressure, Light Levels, & Humidity
  - Can Customize Boards To Any Industrial Application
- Features:**
- 24 Lines Programmable I/O At TTL Levels
  - 8 Bit Analog To Digital Converter
  - 8 Channel Analog MultiPlexor & 12 Bit CMOS Counter

**SCHOONER SOFTWARE** - Economical Data Acquisition Program For Model 30!



**ONLY \$149**

**MODEL 150 DMM**  
True RMS Digital Multi-Meter w/RS232 Port

- Measures AC-DC Voltage & Current, Frequency, & Resistance
- Includes Data Logging Software
- Offers True RMS Reading, Diode Test, & Audible Continuity
- Features Large 3 3/4 Digit Display & RS232 Interface

**Surface Mount Chip Component Prototyping Kits—**  
Only **\$49.95**

**INDIVIDUAL VALUES AVAILABLE**



CC-1 Capacitor Kit contains 365 pieces. 5 ea. of every 10% value from 1pf to 33µf. CR-1 Resistor Kit contains 1540 pieces; 10 ea. of every 5% value from 10Ω to 10 megΩ. Sizes are 0805 and 1206. Each kit is ONLY \$49.95 and available for Immediate One Day Delivery!

Order by toll-free phone, FAX, or mail. We accept VISA, MC, COD, or Pre-paid orders. Company PO's accepted with approved credit. Call for free detailed brochure.

**COMMUNICATIONS SPECIALISTS, INC.**  
428 West Taft Ave. • Orange, CA 92665-4296  
Local (714) 998-3021 • FAX (714) 974-3420  
**Entire USA 1-800-854-0547**

**CABLE TV DESCRAMBLERS**

**DEALERS WANTED**  
**QUANTITY DISCOUNTS ON 5 OR MORE UNITS**

MODEL	5	10	20	50	100
*DTI-3	65	60	50	45	CALL
*SAT-3	55	50	45	40	CALL
*SA-80	120	110	100	95	CALL

\*DTI - Digital Tri-Mode Impulse \*SAT - SCI ATL  
\*SA-80 - SCI ATL 8580 & below

**All equipment is new and guaranteed**  
**CALL V.C.I.**  
**1-800-677-0321**  
Anyone implying theft of service will be denied assistance  
No Florida Sales





# TIMELINE INC.

Order desk only: USA: (800) 872-8878 CA: (800) 223-9977 L.A. & Technical Info: (310) 784-5488

## Liquid Crystal Displays

16 x 1, 3 for \$25. <sup>00</sup>	16 x 2 \$8.00
20 x 2 \$12.00	24 x 2 \$12.00
32 x 4 \$20.00	40 x 2, 2 for \$25.00
40 x 4 \$25.00	4 x 2 \$5.00

5V power required • Built in C-MOS LCD driver & controller • Easy "Microprocessor" interface • 98 ASCII character generator • *Certain models are backlit, call for more info.*

## Portable Micro Terminal



• Flip up LCD display (9-16 VDC) • Can communicate with any computer having RS 232 port • Can communicate with another Microterminal • Use by itself as electronic notebook • Onboard microprocessor, data RAM (32K) and Video RAM (64K) • Complex built in diagnostics and set up capabilities • Original intention for POS applications • display size 40x16 (256 x 128 pixels.) Dim: 6.3" W, 11", 2"H. (With LCD up height is 7.1")

Wow!

\$99.<sup>00</sup>

or 2 for \$149.<sup>00</sup>

## 5" COLOR MONITOR \$79.00

Flat Faceplate • 640 x 200 Dot Resolution • CGA & Hercules Compatible • 12 VDC Operation • 15.75 KHz Horiz. Freq. • 60 Hz Vert. Sync. Freq. • Open Frame Construction • Standard Interface Connector • Degaussing Coil Included • Mfg.: *Semtron*

## MAGNETIC CARD READER \$25.<sup>00</sup>

Includes: • 20 character dot matrix display with full alpha-numeric capability • keypad with full alpha-numeric entry • separate 7.5 VDC/0.5 Amp power supply • standard telephone interface extension cord • lithium battery and flat-cone speaker.

## Test Bench System \$99.00

286 - 12 Computer. Ideal for the handyman, great for the testbench.

Includes: 286-12 motherboard (Intel Chip) • built in IDE, floppy and VGA controller • 1 Mb RAM on board (expandable to 5 Mb) • Phoenix Bios • 1 serial, 1 parallel, 1 mouse port • keyboard • DOS 4.01 • real time clock • (2) 16 bit slots, (1) 8 bit slot • (Note: Does not include power supply or upper part of the case. The motherboard and case are not standard IBM footprint size. Call for more details.)

## AMPRO™ LITTLE BOARD PC \$79.<sup>00</sup>

Expandable to 768K on board (256x9 SIMMS) • 1 Floppy Controller 360K/720K/1.2Mb/1.44Mb • 2 serial ports and 1 parallel port • Keyboard input & Speaker Output • 8088 CPU Controller Socket • (requires optional pal & controller) • is the size of a 5.25" floppy drive. • Warranty and support available only from Timeline.

**SOLD OUT**

## ADAPTEC 4070A (RLL) or 4000A (MFM) SCSI Controller, your choice \$60.<sup>00</sup>

## LASER DIODE: Sharp part#: LT022MC \$5.<sup>00</sup>

5mW at 780 nm, single transverse mode

## IRMA BOARD 8 bit \$99.<sup>00</sup>

Links 3270 mainframe systems to IBM PC

## Magnavox EGA Color Monitor \$150.00

.39 dot pitch. Model #:9CM053. EGA card available.

## FLOPPY DRIVES

360 K	\$35. <sup>00</sup>
720 K	\$35. <sup>00</sup>
1.2 Mb	\$55. <sup>00</sup>
1.44 Mb	\$55. <sup>00</sup>

5.25" bracket for 720K or 1.44Mb drives \$7 extra

## Single Board 286 Computers

286-12 comes without serial and parallel ports. \$79.<sup>00</sup>

286-16 comes with serial and parallel ports. \$99.<sup>00</sup>

Both are 16 bit, plug into a passive backplane and come with 1Mb of memory on board.

## IBM PC Convertible Equipment

- PC convertible printer.....\$75.00
- PC convertible keyboard.....\$25.00
- PC convertible LCD.....\$25.00
- PC convertible Modem.....\$25.00 (Not Hayes compatible)

## 640 x 200 LCD \$29.<sup>00</sup>

The unit is the display for the Toshiba T1100+ laptop computer. Driver board to generate text and graphics not included. This is a serial interface LCD. You should be very familiar with wiring when attempting to use this unit.

## Sony Trinitron

### 9" Enclosed COLOR Monitor (\$199.<sup>00</sup>)

Model CPD9090 • CGA: 640 x 200 resolution • 28 dot pitch • 110 Volts (connector is RGB input - 8 pin)

## NON-ENCLOSED TTL MONITORS

Comes with pinout. 12V at 1.4 Amp input. Horizontal frequency 15 KHz. Ability to do 40 and 80 column.

- 5" Black & White.....\$35.00
- 9 inch (Amber).....\$29.95

## BACKLIT 640 x 400 LCD \$50.<sup>00</sup>

Panasonic # EDM DG84AA43D

## Proton ProNet-4 Model PI347 Token Ring Board \$79.<sup>00</sup>

16 bit • 4 Mbps • IEEE 802.2 and 802.5 compatible • twisted pair • interoperable with IBM Token Ring network

## Graphic & Alphanumeric Liquid Crystal Display

480 Dot x 128 Dot, (80 x 16 line) \$15.<sup>00</sup> each, or 2 for 20.<sup>00</sup> Driver board available: \$75.<sup>00</sup>

## 12" PAPER WHITE VGA MONITOR AND CARD

Incredible \$99.<sup>00</sup> VGA monitor separate.....\$65.00 VGA card separate.....\$39.00



## THE SPY IN THE SKY

1728 element CCD \$19.00

4096 element CCD \$29.00



## LASER SCANNER ASSEMBLY \$39.<sup>00</sup>

Assembly intended for a laser printer. Includes laser diode, polygon motor (6 sided) and misc. optics and lenses.

HeNe Laser Tube • 10mW (max. output) \$99.<sup>00</sup>

101 key XT keyboard.....\$24.00

85 key XT/AT keyboard.....\$24.00

XT Hard drive controller.....\$39.00

AT Hard drive controller (up to 12 Mhz only) \$19.00

## POWER SUPPLYS

300 WATT SUPPLY \$39.00 non-enclosed • Output: +5V @ 50 A, +12V @ 5 A, -12V @ 3 A, Dim: 13.5" L x 5" W x 2.5" H  
73 WATT SWITCHING \$18.00 or 2 @ \$30.00, (2) 4 pin power connectors attached • 115/230 Volt, Dim: 8.5" L x 4.5" W x 2" H • Output: +5V @ 2-9.75 A, +12V @ 0-1.5 A, -5V @ 0-0.4 A, -12V @ 0-0.5 A

## NEC N9630-P 9600 bps External Modem \$129.<sup>00</sup>

Hayes compatible • Full duplex asynchronous or synchronous operation • Dial up (voice) or lease line operation • Follows the V.32 standard • Automatic fallback to 4800 bps • Built in error correction (can be enabled or disabled) • Seven (7) mode of operation LED indicators • Seven (7) interface LED indicators • Two (2) signal quality LEDs • Eight (8) Character message display

9" composite enclosed green monitor.....\$39.00

HP bar code wand.....\$50.00

IBM 370 option XT and AT emulation boards...\$50.00

9" amber non enclosed composite monitor.....\$24.00

23605 TELO Ave, Torrance, CA 90505

Order desk only: USA: (800) 872-8878 CA: (800) 223-9977

L.A. & Technical Info: (310) 784-5488 Fax: (310) 784-7590


OEM INQUIRIES WELCOME

Minimum Order: \$20.00. Minimum shipping and handling charge \$5.00. We accept cashiers checks, MC or VISA. No personal checks or COD's. CA residents add 8.25% sales tax. We are not responsible for typographical errors. All merchandise subject to prior sale. Phone orders welcome. Foreign orders require special handling. Prices subject to change without notice. 20% restocking fee for returned orders..

March 1993, Electronics Now


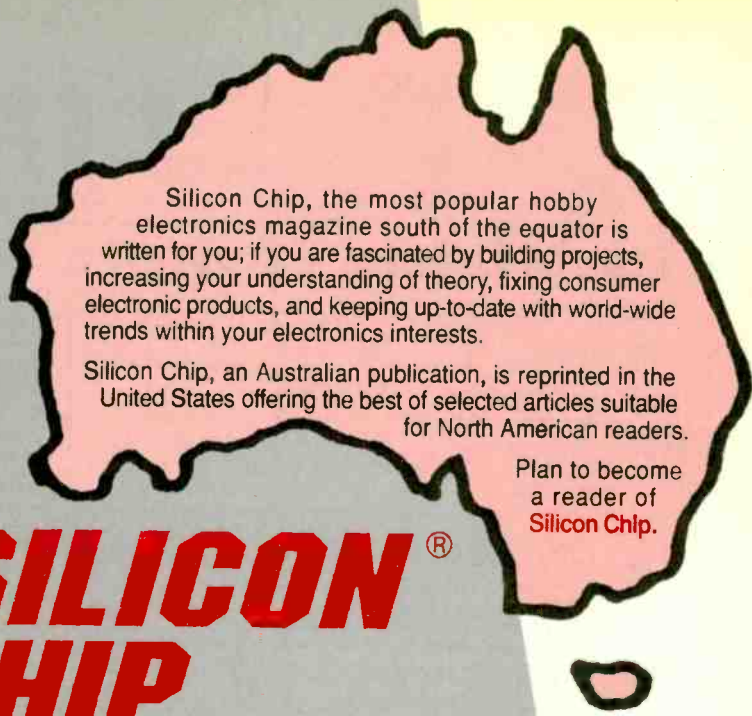
# Introducing Australia's Leading Electronics Magazine...



Silicon Chip, the most popular hobby electronics magazine south of the equator is written for you; if you are fascinated by building projects, increasing your understanding of theory, fixing consumer electronic products, and keeping up-to-date with world-wide trends within your electronics interests.

Silicon Chip, an Australian publication, is reprinted in the United States offering the best of selected articles suitable for North American readers.

Plan to become a reader of **Silicon Chip**.

# SILICON CHIP®

Packaged in a specially prepared format guaranteed to excite the electronics hobbyist with new ideas, novel projects, extraordinary features and down-right good reading.

Inside **Silicon Chip** you will discover how the other side of our world—down under—approaches the same hobby interests as you do, with ramifications that will amaze you.

Detailed construction projects to appear in upcoming issues of **Silicon Chip** include:

- 4-Channel Guitar Mixer**
- Adjustable 0-45V, 8A Power Supply**
- Interphone Digital Telephone Exchange**
- 1.5V to 9V DC Converter**
- Multi-Sector Home Burglar Alarm**
- 1-Megabyte Printer Buffer**



*Exciting and imaginative Features like:*

- Understanding Computer Memory**
- How to Interlink Musical Instruments**
- What's New in Oscilloscopes**



If you are fascinated by electronics, especially the hobby aspects related to construction projects, theory, applications in home and shop, and latest developments, if you are compelled to experiment and "fix-it," then **Silicon Chip** is your kind of magazine.

**Silicon Chip** is available exclusively by subscription. So take advantage of this great opportunity and start your Charter Subscription today.

**SILICON CHIP**, 500-B Bi-County Boulevard, Farmingdale, New York 11735

I'm convinced! Enroll me as a Charter Subscriber. Enter my subscription as designated below.

<b>United States of America</b>		<b>Canada</b>	
<input type="checkbox"/> 12 issues for \$29.95		<input type="checkbox"/> 12 issues for \$40.61	
<input type="checkbox"/> 24 issues for \$49.95		<input type="checkbox"/> 24 issues for \$70.57	
		(Includes postage & G.S.T.)	
<input type="checkbox"/> Payment enclosed	Please charge my	<input type="checkbox"/> VISA	<input type="checkbox"/> Mastercard

For your convenience, if paying by credit card: To avoid any interruption in service, your subscription will be renewed automatically at 12-issue intervals, at the then prevailing introductory rate, until you advise us to cancel it.

Signature \_\_\_\_\_

Account No. \_\_\_\_\_ Expiration Date \_\_\_\_\_

Offer valid in the U.S.A. and Canada only. No foreign Orders.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

All orders payable in U.S.A. funds only. Allow 6-8 weeks for delivery.



# A COMPLETE ELECTRONICS SUPERMARKET!

<b>Universal Programmer and Tester Module</b> .....	\$229	<b>Bench Power Supply</b> .....	NEW \$229.00
Tests TTL, CMOS, Static and Dynamic Ram Chips and programs EPROMS, EEPROMS, PALS GALS 8748 and 8751. R/MOD—MUD		0 to 30 Volts DC • 0 to 3 amps •	
<b>IC Gang EPROM Programmer</b> .....	\$199	<b>No Slot Clock</b> • With Software & Docs.....	\$19.95
Programs 24 to 32-Pin EPROMS, CMOS EPROMS and EEPROMS from 16K to 1 Meg. R/MOD-MED-16		Clock chip Fits between BIOS & Socket • Dallas DS1216 • XT Compat. •	
<b>PAL Programmer Module</b> .....	\$149	<b>CDROM Simtel20</b> • 7500 MSDOS Files • Latest Press.....	\$24.95
Programs 24 and 20 Pin PALS with software. R/MOD-MPL		<b>CDROM Windows Programs</b> • April 1992 Press.....	\$24.95
Everex VGA 800 x 600 card works with our IBM monitors 8512, 8513.....	\$39.95	<b>CDROM Amiga Programs</b> • May 1992 Press.....	\$24.95
80 Meg • IDE • 15 MS • 3 1/2 in. MDL #94354-090 CDC	NEW \$189	<b>CDROM OS/2 Archive</b> • May 1992 Press.....	\$24.95
<b>Any 486 SX-DX-DXZ CPU Mother Board</b> uses 25 MHz and up CPU • Plug and Play—No CPU on board.....	NEW \$149.00	<b>CDROM GIFFS CD 5000 + GIFF FILES</b> .....	\$24.95
<b>Any 386 DX mother board</b> uses 33 MHz and 40 MHz CPU		<b>Toshiba 1/2 HT • 318Ms Fast • SCSI Interface</b> .....	\$289.95
No CPU on board—AM1 and Bios Plug and Play	NEW \$135.00	<b>Emerson 800 watt UPS Noise, Transient Protection</b> .....	\$429.00
<b>12 Volt DC Panasonic Rechargeable Battery</b>		<b>425 Fonts for the HP LaserJet II, IID, IIP and III printers</b>	
6.5 Ah/20 Hr New Mdl #LCR12V6.5P-1	\$9.95	• Font plug-in card	\$99.00
<b>35 MHz Dual Trace Oscilloscope</b> —Delayed Sweep	\$395.00	<b>AT Backplane</b> • 6 16 bit and 2 8 bit slots	
<b>20 MHz Dual Trace Oscilloscope</b> • Component Tester	\$269.00	• w/keyboard and power conn.....	\$29.95
*All scopes come with 1 year warranty and x1 and x10 probes		<b>Monitor Stands</b> • Tilt and swivel base.....	NEW \$9.95
<b>NEC CCD Linear Image Sensor Mdl #PD3573</b>	\$9.95	<b>Printer Cables</b> • 6 foot cables	\$1.99
*On Handscanner Circuit Board with DOCS		<b>Quattro Pro Newly Packaged</b>	\$49.95
<b>Laser Power Supply</b> .....	\$39.00	<b>Duracell AA Batteries</b>	4-for \$1.79
9 VDC in 1 amp 1.1-1.5 KV out at 4MA		<b>Optical Mouse for Mac II, SE, etc.</b>	NEW \$39.95
Mini-tower 200 watt case with LED display	\$89.95	<b>2400 Baud PS/2 Modem</b>	NEW \$49.95
Mid tower 200 watt case with LED display	\$109.95	Microchannel Board • Model 50,60,70,80 • w/Bitcom Software •	
<b>PS/2 Keyboard Adapters</b>	\$5.95	<b>Multiple I/O and Floppy Controller (order #R/MIO)</b>	\$19.95
<b>Future Domain 8-Bit SCSI Kit</b>	\$69.96	XT Compat. • 360K FDC • PIO, SIO • Game port • Clock/Calendar	
R/TMC-885 DOS with CDROM/Tape software		<b>Seagate &amp; Micropolis Hard Drives:</b>	1 Year Warranty!
<b>2400 Baud Modem for Toshiba Laptops</b>	\$69.95	120 Meg • RLL • 26Ms • Full Ht. • Mdl #ST4144	\$269.00
<b>IDE with I/O Controller Card</b>	\$17.50	150 Meg • ESDI • 18Ms • Full Ht. • Mdl #1355	\$199.00
<b>ESDI Western Digital Controller.</b>	\$69.95	150 Meg • ESDI • 16Ms • Half Ht. • Mdl #1654	\$429.00
<b>MFH Hard Drive Controller Only 16-Bit</b>	\$9.95	<b>360K Floppy Drives</b> • Shugart SA455 • Black Half Ht • Floppy with full size bezel tested good.....	\$9.95
<b>16-Bit Network Cards BNC/Thick</b>	\$69.95	<b>386-25 Motherboard</b> 64K Cache, Ask for Dram/Sim/Sip	\$189.00
<b>8-Bit Network Cards BNC/Thick</b>	\$49.95	<b>286 Motherboard</b> • C&T NEAT chipset • 8MB RAM • OK inst •	
<b>Archive 60 Meg DC2000 Tape-Backups</b>	\$69.95	16MHz version (order #R/M286-16N)	\$89.00
Tape Drive only #5240		20MHz version (order #R/M286-20N)	\$109.00
<b>PS/2 Data Compression Card</b>	\$89.95	<b>XT Motherboards</b> • Baby Size • 1 Year Warranty	
Double your hard disk capacity		4.77 MHz version (order #R/XMB)	\$29.00
<b>AB Printer Switch RS232 Type</b>	\$12.95	8MHz version (order #R/TURBO)	\$39.00
<b>ABC Printer Switch Centronic Type</b>	\$16.95	10MHz version (order #R/TURBO-10)	\$39.00
<b>Epson Fonts</b> Courier/Prestige/Script	\$10.00	<b>IDE SUPER Card</b> • Hard/Floppy & I/O	\$24.95
<b>HP Memory Cards for HD IID IID III</b>	\$49.95	Hard & Floppy Support + 2 Serial, 1 Printer & Game Port	
Comes with 1 MEG upgradable to 4 Megs		<b>Future Domain SCSI Card</b> • Works with Toshiba CDROM	\$69.95
<b>Cyrix Fastmath Coprocessors 387SX</b>	\$69.95	<b>Multi Serial Card (order #R/AMS)</b>	\$39.95
<b>Kraft Joystick</b> works with Apple/IBM.....	\$12.00	AT Compat. • 4 Serial Ports • Com 1-4 • w/cables, software, docs	
<b>1400 VA UPS Emerson Back-Up</b>	\$489.00	<b>AT Memory Card (order #R/EEMS)</b>	\$59.95
<b>IBM Model 80 with 8 Meg Ram</b>	\$1495.00	4MB OK inst. • EXP. EXT. CONV • Multitask Compat. • 16 Bit	
140 Meg ESDI* and IBM 8515 SVGA monitor, 1 year warranty		<b>9600 Baud Fax Card</b> with remote on/off.....	\$69.95
<b>Rommax</b>		<b>14" EGA Color Monitor</b>	REFURB. \$139.00
1 Gang E(E)PROM programmer.....	\$159.00	<b>12" Mono Monitor Hercules Compatible</b>	REFURB. \$39.00
4 Gang E(E)PROM programmer.....	\$199.00	<b>14" Mono Monitor Hercules Compatible</b>	REFURB. \$49.95
<b>Audio Generator/Counter</b> .....	NEW \$229.95	<b>REAL IBM VGA MONITORS</b>	1 Year Warranty!
5 Ranges 10Hz to 1MHz • Output: 8Vrms sine.		8513.28 Dot pitch • 640x480 • 12" Display	\$199.00
10V p-p squarewave w/Freq. Counter 1Hz to 150MHz		8512.31 Dot pitch • 640x480 • 14" Display	\$199.00
		8515.28 Dot pitch • 1024x768 • 14" Display	\$269.00
		8514.28 Dot pitch • 1024x78 • 15" Display	\$299.00

• • • ABOUT OUR REFURBS • • •

Our refurbished inventory contains items that fall into one or more of the following categories: 1) failed primary testing, 2) was sold and returned as failed, 3) cosmetically imperfect. In any case, the item was returned to the O.E.M. (original equipment manufacturer) and was reconditioned or fixed to original manufacturers specifications. HALTEK guarantees all refurbished products for 90 days from the date of purchase. Any item may be exchanged within that period. The management of Haltek Electronics requires that any returns be in the original packaging and be complete, including any and all manuals, cables, software, etc. and must be accompanied by the original sales receipt. Prices subject to change without notice • Quantities limited to stock on hand • All items are refurbished unless indicated as "new"

BBS# (415) 969-6321



# HALTEK

ELECTRONICS



1062 LINDA VISTA AVENUE • MOUNTAIN VIEW, CA 94043 • 408-744-1333 / 415-969-0510

CIRCLE 289 ON FREE INFORMATION CARD





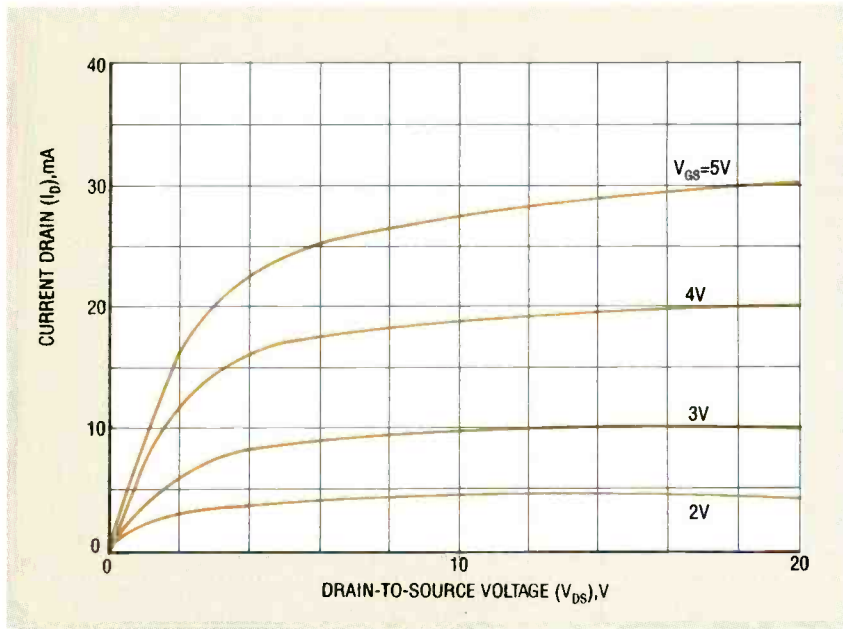


FIG. 10—DRAIN CURVES FOR AN N-CANNEL, enhancement-mode MOSFET showing the effects of increasingly positive gate bias.

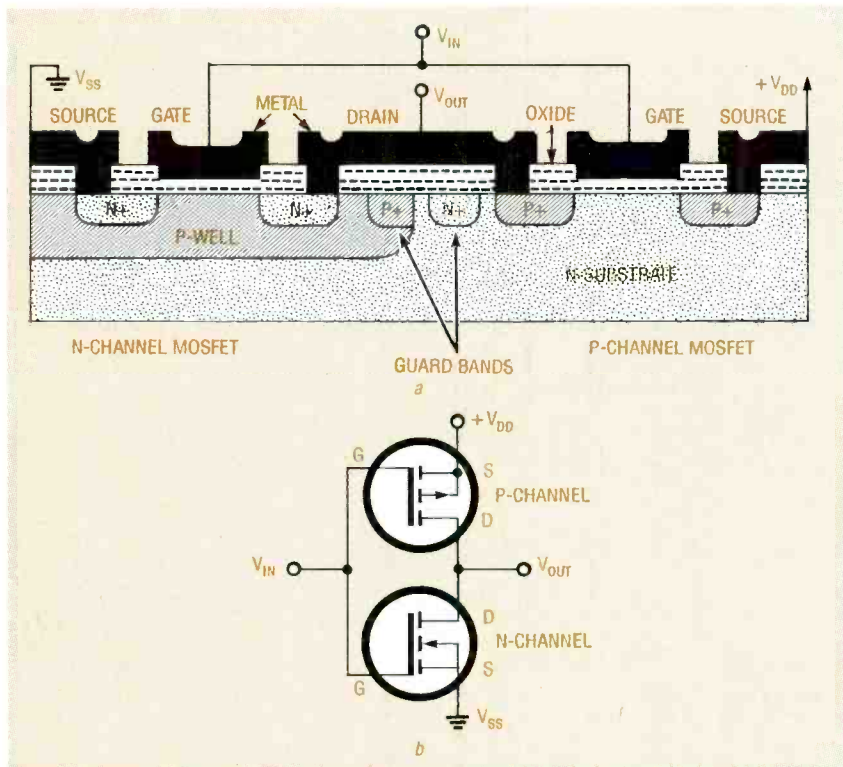


FIG. 11—CMOS INVERTER (NOT) GATE FORMED FROM N-CANNEL AND P-channel enhancement-mode MOSFET's with power, ground, input, and output connections as shown in (a), and schematic (b).

electrons has accumulated, the P-type substrate material is converted into an N-channel, and drain-to-source conduction occurs. The magnitude of the drain current depends on the channel resistance, but it is controlled by the gate voltage.

The schematic symbol for an

N-type enhancement-mode MOSFET is shown in Fig. 9-b. In this symbol, the gate does not make direct contact with the channel. The arrowhead points from the P-type substrate toward the (induced) N-type channel, shown as a line broken into three sections to indicate an in-

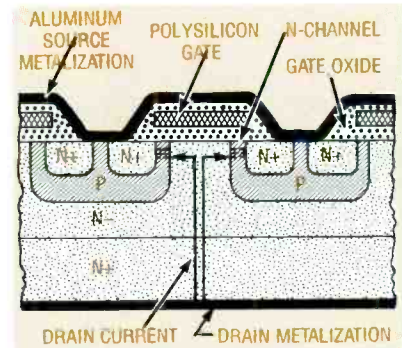


FIG. 12—SECTION VIEW OF AN N-channel DMOS power MOSFET showing its vertical structure and vertical current flow.

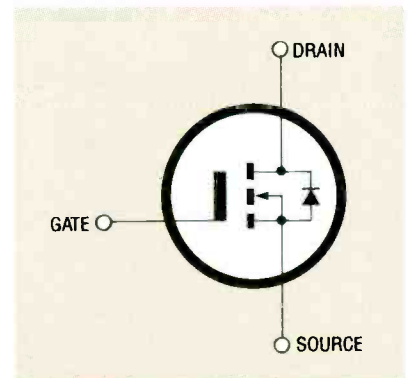


FIG. 13—SCHEMATIC SYMBOL FOR A DMOS power MOSFET including a drain-source diode.

termittent channel.

Current flow in the channels of both kinds of enhancement-mode MOSFET's is proportional to the voltage on their gates,  $V_{GS}$ . This can be seen for an N-type enhancement-mode MOSFET by examining the family of gate voltage ( $V_{GS}$ ) curves in Fig. 10. Current drain,  $I_D$ , is directly proportional to the positive value of gate voltage.

A P-channel enhancement-mode MOSFET is made the same way as the N-channel enhancement device except that P-type drain and source regions are diffused into an N-type substrate. The symbol for a P-type enhancement-mode MOSFET is the same as the one shown in Fig. 9-b except that the direction of the arrow is reversed. In the case of a P-type enhancement-mode MOSFET, the drain current is directly proportional to the negative values of its grid voltage.

The high gate impedance of all MOSFET's makes them susceptible to damage from even

low-energy electrostatic discharge (ESD). For this reason many discrete MOSFET's and IC's based on MOSFET's are protected with on-chip Zener diode circuits.

### CMOS logic devices

An enhancement-mode MOSFET can act as a switch when it is turned on or off by a voltage applied to the gate electrode: N-channel MOSFET's are switched with positive gate voltage, and P-channel MOSFET's are switched with negative gate voltage. These are known as *complementary responses*, and they form the basis for complementary MOS or CMOS digital logic families.

Figure 11-a is a section view of a complementary pair of MOSFET's on a common substrate, the basic topography for all CMOS gates. The common substrate that is used for this pair is an N-doped silicon wafer. To make an N-channel MOSFET on an N-doped substrate, it is necessary to diffuse or implant a P-doped *well* in the substrate. The smaller N-type wells can then be formed in this P-doped region.

Because the substrate is N-doped, fewer steps are required to form the P-channel FET. The P- and N-doped guard bands isolate and insulate the individual transistors in this integrated circuit to prevent mutual interference. (Although not illustrated here, these guard bands are actually N- or P-doped rings formed around the complete FET below the oxide layer in this CMOS technology.

The two transistors in the section view, Fig. 11-a, can be connected to form a CMOS logic inverter, the simplest of digital logic circuits. This is accomplished by connecting the gates together to form an input ( $V_{IN}$ ) terminal, and taking the output ( $V_{OUT}$ ) from the common drain. The source on the left side of the diagram,  $V_{SS}$ , is grounded, while the source on the right side is connected to the positive supply,  $V_{DD}$ .

Those connections are shown schematically in Fig. 11-b. How does the inverter work? Consid-

er the P-channel device to be the driver and the N-channel device to be the load. Recall that an N-channel enhancement-mode MOSFET conducts with a positive gate voltage, while a P-channel, enhancement-mode MOSFET conducts with a negative gate voltage.

When the voltage input to the inverter is low (logic 0), the gate voltage of the P-channel device is negative, equal to the supply voltage  $V_{DD}$ . As a result, the P-channel MOSFET is switched ON, and there is a low impedance path from the output to  $V_{DD}$ . Because the N-channel is off (gate voltage is zero), there is

CMOS unit is extremely low. These properties of N- and P-type enhancement-mode FET's combined to form CMOS gates provide many advantages:

- Extremely low power consumption.
- Wide power supply voltage range.
- High DC noise margin
- High input impedance
- Wide operating temperature range.

The diagram in Fig. 11-a illustrates standard CMOS metal-gate technology (74C/4000), but there are many other CMOS technologies including the high-speed silicon-gate HC,

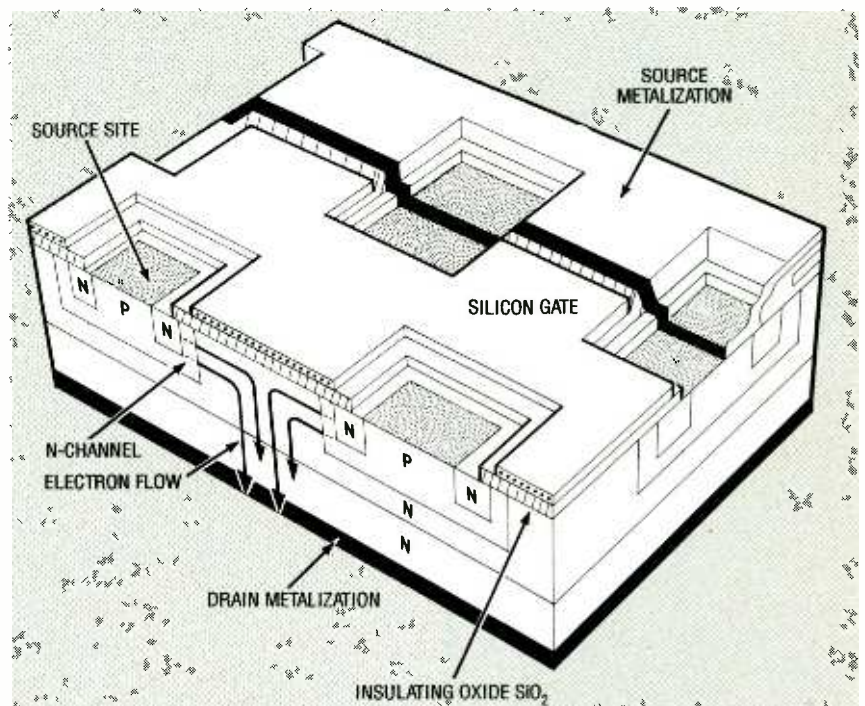


FIG. 14—CUTAWAY OF AN N-CHANNEL DMOS power MOSFET showing the arrangement of multiple cells in parallel.

a very high impedance path from the output to ground. Therefore, the output voltage rises to  $V_{DD}$ .

When the input voltage is high (logic 1), the situation is reversed. The P-channel FET is cut off, and the N-channel FET is ON, so the output voltage falls to zero. Therefore, the circuit is a logic inverter: a *low* input results in a *high* output, and vice versa.

In either logic state one FET is ON while the other is OFF. Because one FET is always turned off, the quiescent current of the

HCT, and FACT families. Another digital logic technology called BiCMOS takes advantage of the lower power consumption and higher integration density of CMOS, and the higher speed and superior drive capability of bipolar transistors.

### Power MOSFET's

Power MOSFET's exhibit the properties of small-signal MOSFET's such as high-input impedance and voltage control, and they have drains, sources and gates, but they are designed

*continued on page 89*



**Learn more about capacitors—  
how they are made,  
and how you can  
apply them more cost-  
effectively in your circuits**

# CAPACITORS

RAY MARSTON

CAPACITORS RANK NEXT TO RESISTORS as the most widely purchased electronic components. Fixed and variable capacitors for electronics available from commercial sources have capacitance values from a few picofarads (pF) to farads (F). And these components are made from an amazingly wide variety of materials.

The outstanding trend in capacitor design and manufacture over the past 85 years—particularly since the arrival of the integrated circuit—has been miniaturization. The objective of all efforts has been to cram as much capacitance as possible into ever smaller packages, while at the same time increasing their reliability.

To gain a better understanding of this trend, and to appreciate what has been accomplished, it is worth reviewing the fundamental capacitor formulas. The ability of a capacitor to store electric energy is a function of its geometry and the physical characteristics of its dielectric.

The amount of energy that a capacitor can store is given by the equation:

$$Q = CE$$

where  $Q$  = the magnitude of the stored charge in coulombs

$C$  = capacitance in farads

$V$  = applied voltage in volts

Figure 1-a shows the simplest capacitor and identifies its principal parts and physical variables; Fig. 1-b is the accepted schematic symbol in North America for a fixed capacitor.

and Fig. 1-c is the accepted symbol for a variable capacitor.

Capacitance in farads is determined by:

$$C = kA/d$$

where  $k$  is the dielectric constant (permittivity), the ratio of the ability of a dielectric material to store electrostatic energy to that stored by a vacuum between the same electrodes (see Table 1).

$A$  = directly opposing plate area



$d$  = distance between the plates

Different multiplying factors can be applied to this equation so that the value for  $C$  is in microfarads or picofarads when  $A$  and  $d$  are measured either in inches or millimeters. Nevertheless, important engineering tradeoffs can be seen from both of these equations:

- To store a given charge, more voltage is needed for a small capacitor than a large one.
- If the opposing plate area,  $A$ , is held constant, the value of capacitance can be increased by:
  - a. Decreasing the thickness of the dielectric,  $h$ .
  - b. Using a dielectric with a higher constant,  $k$ .
  - c. Doing both (a) and (b) simultaneously.

While not apparent from the formulas, other facts about capacitors to be considered are:

- The maximum voltage that can be impressed across a capacitor, without destroying it, depends on the dielectric and the separation of the plates.
- For a given dielectric, the allowable maximum voltage can be increased as the distance be-

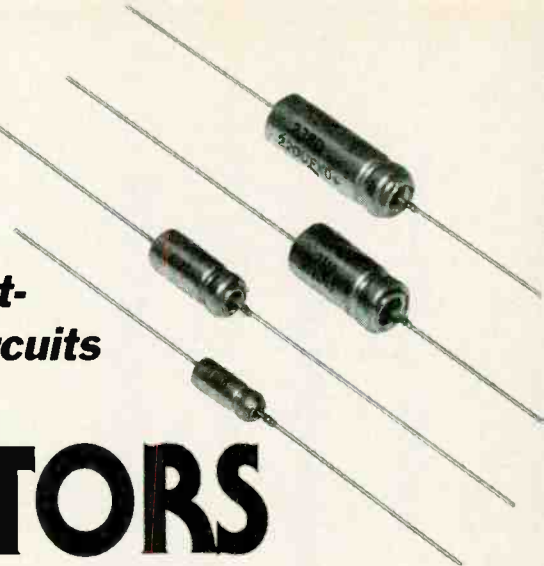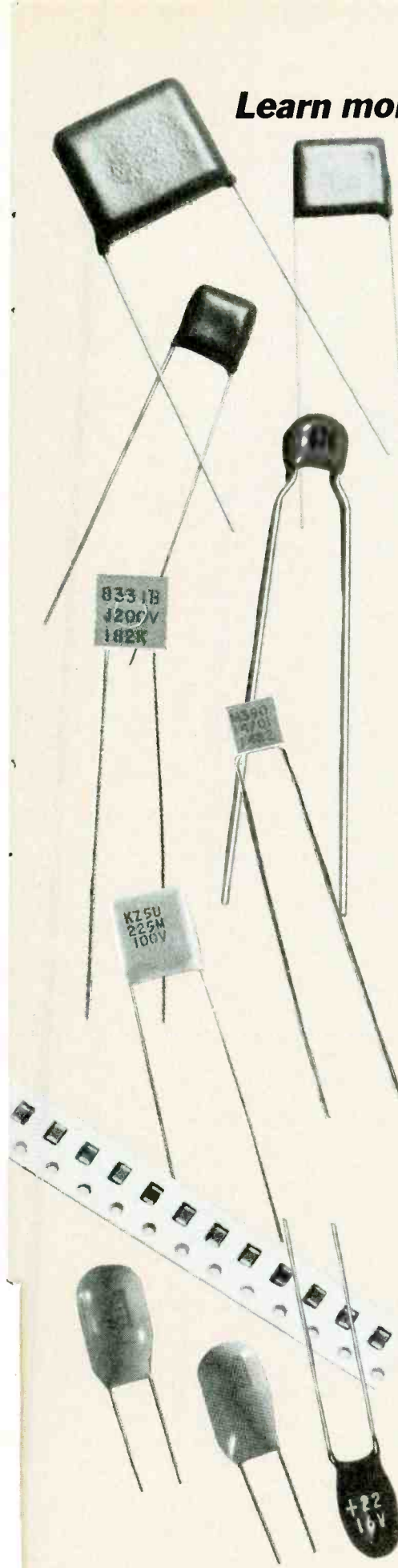

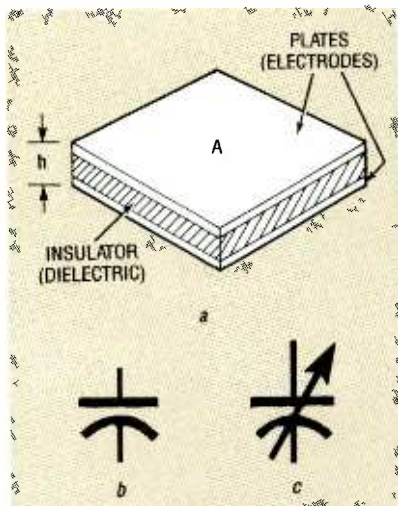


FIG. 1—A BASIC PARALLEL-PLATE capacitor has parallel metal plates or electrodes separated by a dielectric that can be air or a solid insulator.

tween the plates is increased.

The volumetric efficiency of capacitors has been improved within the constraints mentioned. How this has been done will be explained in the discussion of each of the most common capacitor manufacturing technologies.

Advanced circuit manufacturing methods have increased demand for miniature chip capacitors for hybrid circuits and surface mounting. New plastic film and ceramic dielectrics now offer a wider range of operating characteristics than was available ten years ago; metalizing has reduced capacitor weight and size by eliminating metal foil from many film capacitors now being produced.

The quality and reliability of electrolytic capacitors has been improved with more effective methods for etching foils, the introduction of better electrolytes, and improved sealing. Solid-electrolyte tantalum capacitors made as dipped radial or chip units are becoming more popular. Capacitors made from mica and glass have faded away to become specialty items, with their former functions largely performed by multilayer ceramic capacitors. Moreover, ceramic disk caps are rarely specified in new designs; they have been replaced by smaller, easier-to-place ceramic tubular capacitors.

The fabrication of increasing numbers of capacitors within very large scale integrated circuits such as microprocessors and digital signal processors has not reduced sales of discrete capacitors; in fact, the sales of certain kinds of capacitors have increased because of the proliferation of IC's. Moreover, capacitors are necessary in the external circuitry for the dedication of such multifunction linear IC's as compandor and modulation chips. Thin- and thick-film capacitors are being formed on ceramic substrates for networks and hybrid circuits that operate well into the microwave band.

Variable capacitors, still used primarily in radio-frequency circuits, are also being made from improved plastics and ceramics, a departure from their traditional dielectrics of air, glass, and ceramic, to reduce their size, extend their capacitance range, and cut cost.

#### Capacitor terms

Capacitors are widely specified with a glossary of widely accepted technical terms. A knowledge of these terms will be helpful to anyone who specifies or uses capacitors.

**Capacitance.** The basic unit for capacitance is the farad, but most capacitors for electronics applications need capacitance values that are only small fractions of a farad: microfarad ( $\mu\text{F}$ —one-millionth of a farad) and picofarad ( $\text{pF}$ —one-millionth of one-millionth of a farad).

**Ambient temperature.** The actual value of a capacitor de-

pends on the temperature of its environment, known as *ambient temperature*. *Percent capacitance change*, a function of temperature, is referred to room temperature,  $25^\circ\text{C}$ .

**Capacitive tolerance** is the variation in capacitance value of the capacitor expressed as a percentage of its value at room temperature,  $25^\circ\text{C}$ , which is referred to as the *nominal value*. **Temperature coefficient (TC)** is the change in a capacitor's capacitance per degree change in temperature, expressed in parts per million per degree Celsius ( $\text{ppm}/^\circ\text{C}$ ). The coefficient can be positive, negative, or zero. The letter P indicates that the coefficient is positive; N if negative. The designation NPO identifies a zero-temperature coefficient. **Rated working voltage** is the maximum permissible operating voltage at which a capacitor can be continuously operated at maximum rated voltage (without derating). This rating must be specified as AC or DC because they are not usually equal.

**Surge voltage** is the maximum instantaneous voltage to which the capacitor should be subjected; exceeding that voltage will cause the capacitor's breakdown. Surge voltage is higher than working voltage.

**DC leakage** is the small amount of direct current that flows in a capacitor at a specified voltage. Caused by the presence of free charge carriers within the dielectric, it is the reason why a charge cannot be stored indefinitely in a capacitor; eventually it leaks off.

**Insulation resistance (IR)** is the resistance of the dielectric. High resistance results in low leakage current. This variable is inversely related to ambient temperature.

**Capacitive reactance ( $X_C$ )** of a capacitor is inversely related to the product of capacitance and frequency in accordance with:  $X_C = 0.159/f \times C$  where 0.159 is a conversion constant

$X_C$  = capacitive reactance (ohms)

$f$  = frequency (hertz)

$C$  = capacitance (farads)

TABLE 1  
DIELECTRIC CONSTANTS  
COMMON CAPACITOR  
MATERIALS

Dielectric	k
Vacuum	1
Air	1.0006
Polystyrene	2.5
Polyester	3
Mica	5
Aluminum oxide	7
Tantalum oxide	25
Ceramic (low k)	10
Ceramic (high k)	100—10,000



**Power factor (PF)** expresses the ratio of energy dissipated to the energy stored in a capacitor, as a percent. It typically exhibits a negative slope below room temperature and positive slope above it.

**Equivalent series resistance (ESR)**, expressed in ohms, is the sum of all internal resistance values of a capacitor. These include lead resistance, terminal losses, and dissipation in the dielectric. ESR increases with frequency.

**Impedance (Z)** of a capacitor is the total opposition it offers to the flow of alternating current at a given frequency:

$$Z = \sqrt{X_C^2 + (\text{ESR})^2}$$

where  $Z$  = impedance (ohms)  
 $X_C^2$  = capacitive reactance (ohms)

ESR = equivalent series resistance (ohms)

Capacitive impedance is inversely proportional to frequency and temperature; ideally, it equals capacitive reactance.

**Dissipation factor (DF)** of a capacitor is the ratio of energy dissipated to energy stored in the dielectric. DF is a figure of merit for the quality of a capacitor.

$$\text{DF} = \text{ESR}/X_C \times 100\%$$

Ideally capacitors have low values of DF over wide temperature ranges.

**Q or Quality factor** is the ratio of energy dissipated to energy stored, so it is the reciprocal of dissipation factor at low frequencies.

$$Q = 1/\text{DF} = X_C/\text{ESR}$$

The highest quality capacitors have high Q's.

**Ripple current** is the result of a periodic AC voltage wave superimposed on the DC voltage applied to the capacitor. Ripple current flowing through the ESR of a capacitor can generate heat, raising the temperature of the capacitor.

**Volumetric efficiency** is a measure of relative capacitance per unit volume. One capacitor has a higher volumetric efficiency than another capacitor of the same size (volumetric dimensions) if it is able to store more charge, or has a higher capacitance rating.

## Capacitor applications

Capacitors have many different applications in electronic circuits:

- **Blocking**—limiting the flow of direct current or low frequency alternating current without significantly affecting the flow of high-frequency AC.
- **Bypassing**—providing a low-impedance path around a circuit component to permit the flow of alternating current
- **Coupling/decoupling**—coupling or decoupling alternating signals between circuits and systems.
- **Energy storage**—storing electric energy for later release to power a device or circuit.
- **Filtering**—removing the DC component from a signal.
- **Smoothing**—reducing the ripple on an input signal
- **Timing**—providing capacitance value in timing circuits.
- **Tuning**—providing capacitance value for tuning in a tank circuit.

## Fixed capacitors

Figure 2 is a diagram showing how fixed capacitors are classified as *electrostatic* and *electrolytic*. Electrostatic capacitors are so named because an electrostatic charge is stored between opposing plates. They are named for the dielectrics between their plates. This can be air or a vacuum or such solid

materials as plastic film, ceramic, mica, and glass.

Electrostatic capacitors are further classified by packaging method: leaded or non-leaded (chip); radial or axial leaded; molded, conformally coated, or dipped in an encapsulant, typically epoxy. A film capacitor can be further classified by the specification of its plastic film such as polyester or polycarbonate.

Electrolytic capacitors are made of metals, normally either aluminum or tantalum, that form extremely thin anodic oxide layers of high-dielectric constant and good electrical characteristics during electrolytic processing. These capacitors are classified by the metal from which their anodes are made—aluminum or tantalum—and capacitor configuration: wet foil, wet slug, or dry slug (solid electrolyte).

## Film capacitors

Film capacitors are made with thin dielectric plastic films such as polyester (Mylar), polycarbonate, polystyrene and polypropylene that is 0.06 mil (1.5 micrometers) to over 0.8 mil (20 micrometers) thick. The electrodes of film capacitors can be metal foil (film/foil) or metal directly deposited on the film (metalized). Film/foil capacitors are made of dielectric film sandwiched between tin or alumi-

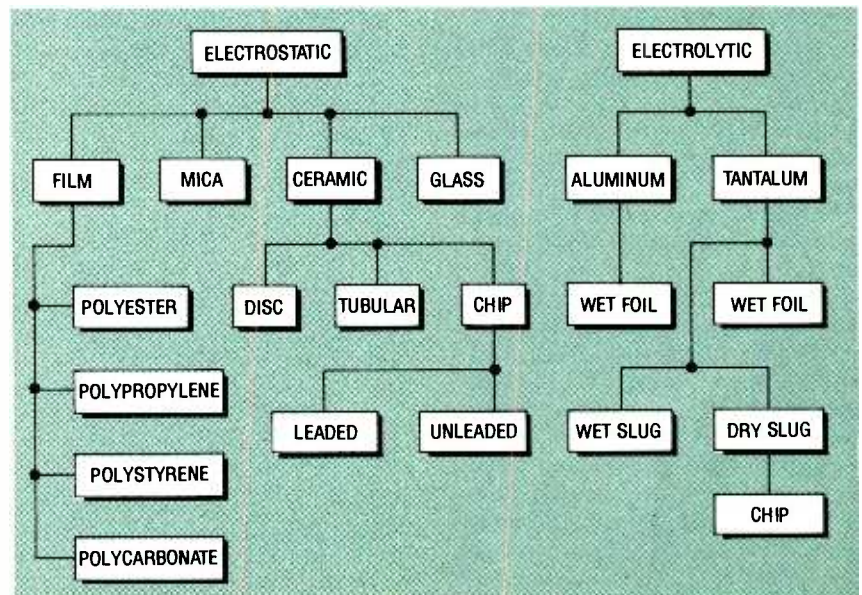


FIG. 2—POPULAR FIXED CAPACITORS are organized as electrostatic and electrolytic, and identified by their dielectric and package style.



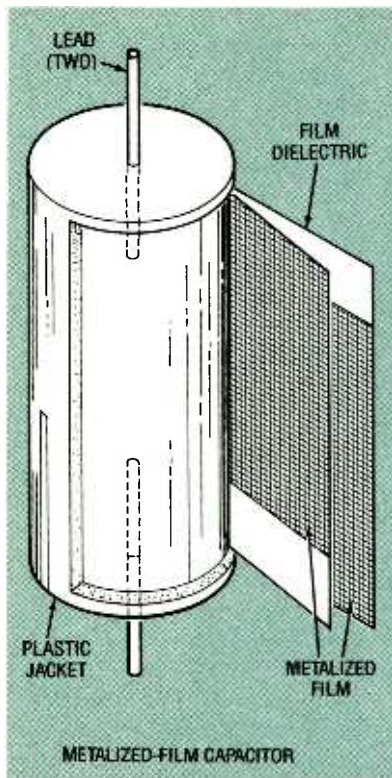


FIG. 3—VIEW OF PLASTIC-FILM capacitor shows how metalized-film dielectric (with leads connected) is rolled into a cylinder and jacketed with molded or conformally coated plastic.

num foil plates (about 0.25-mil thick). They are most widely specified for energy storage, pulse discharge, and arc suppression applications.

The plates of metalized capacitors are very thin vacuum-deposited layers of aluminum or zinc, which permits these capacitors to be smaller and lighter than film/foil capacitors with the same capacitance ratings. These capacitors can be made as shown in Fig. 3, or the metalized film can be cut into rectangles and stacked. The stacks are then leaded and molded in a protective encapsulant package.

*Self-healing* is a very important feature of metalized-film capacitors. A localized dielectric breakdown caused by a transient overvoltage will not necessarily cause capacitor failure because the metalized film around the fault evaporates without shorting the adjacent metalized plates. This response isolates the fault and effectively restores the electrical properties of the capacitor.

Both film/foil and metalized-film capacitors are made with axial or radial leads in a variety of case sizes. They can be hermetically sealed in tubular or rectangular metal cases, or encapsulated by molding or conformally coating with epoxy.

Film capacitors are most widely specified for capacitance values from 500 picofarads to 10 microfarads. (Refer to Table 2.) Their working voltages typically range from 50 volts DC to 630 volts DC—although they can have higher ratings. Capacitance tolerance is typically from  $\pm 1\%$  to  $\pm 10\%$

### Film dielectrics

The four most widely used film dielectrics are:

- *Polyester* (tradenamed Mylar) capacitors are the most popular general-purpose film capacitors. This film permits high volumetric efficiency, low leakage, and a moderate temperature coefficient. Some film/foil and metalized units can operate to 125°C at 50% of rated voltage. Metalized-polyester units can perform blocking, coupling, decoupling, bypass, and filtering.
- *Polycarbonate* capacitors have operating temperatures from -55°C to as high as +125°C with proper voltage derating.

Capacitive tolerances can be as low as  $\pm 5\%$ . This dielectric film offers high insulation resistance and stability.

- *Polystyrene* capacitors have characteristics that are similar to those of polypropylene, but they have lower volumetric efficiency. They have capacitive tolerances as low as 1%. Film/foil units are widely used in inductive-capacitive filters.

- *Polypropylene* capacitors have higher volumetric efficiency than polyester capacitors. Except for AC rating, their characteristics are similar to those made from polystyrene. They have tolerances as low as  $\pm 2\%$ . These capacitors are specified where precision, reliability, and low losses are important: e.g. tuning, filtering, and timing.

### Ceramic capacitors

There are three ceramic capacitor styles: single-layer disc, single-layer tubular, and monolithic multilayer. There are three principal classes of ceramic dielectric based on their *k* rating: Class I, II, and III. Low-*k* materials have linear characteristics, and their properties are independent of frequency over their normal range. They are suitable for resonant-circuit or filter

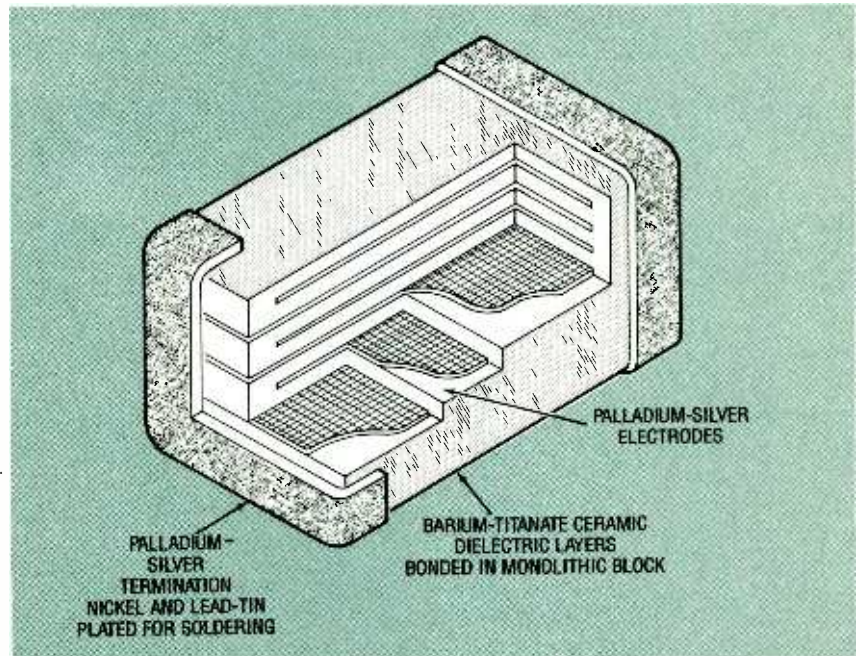


FIG. 4—CUTAWAY VIEW OF A CERAMIC MULTILAYER CHIP capacitor shows noble-metal electrodes deposited on thin layers of ceramic dielectric which are then pressed and fired to form a monolithic unit.



characteristics. High-*K* ceramics have very high effective dielectric constants. They are suitable for coupling and decoupling applications.

- *Disc ceramic* capacitors are made by metalizing both surfaces of a thin low-*k* (Class III) ceramic disc with silver-based ink to form the electrodes, firing the disk, and soldering on radial leads. They are jacketed by dipping in phenolic resin or epoxy. These capacitors are being replaced by tubular ceramic units made of the same materials that save circuit board space and permit automatic parts placement.

- *Tubular ceramic* capacitors are made by coating the inner and outer surfaces of Class III ceramic tubes with silver-based thin-film ink, firing, and attaching leads to the tube before jacketing it by epoxy dipping.

- *Monolithic multilayer ceramic* (MLC) capacitors are made by screening thin-film, precious metal-based conductive ink on thin layers of "green" or unfired layers of higher *k* (Class II and III) ceramics. The screened layers are then stacked (up to 40 layers), compressed, and fired to form monolithic capacitors, as shown in Fig. 4.

If the MLC capacitor is to be a chip capacitor for a hybrid circuit or surface-mounting, conductive-metal terminations are plated on its ends, as shown in Fig. 4. The terminals of surface-mount chips are further plated with lead-tin alloy to improve the terminal-to-pad solder joints.


Demand for MLC chips has risen with the worldwide growth of surface mounting. Chip MLC's will withstand the molten-solder temperatures encountered in reflow and wave soldering. They are available in standard sizes to fit the grasping tools in automated pick and place machines. The most common sizes are 0.08 × 0.05 inch (0805), 0.125 × 0.063 inch (1206), and 0.05 × 0.225 inch (2225).

Cylindrical leadless capacitors are also made for surface mounting. These capacitors

**TABLE 2**  
**CHARACTERISTICS OF POPULAR FIXED CAPACITORS**

Type	Capacitance Range	Working Voltage	Maximum Operating Temp. (C)	Tolerance (Percent)
<b>Electrostatic</b>				
<b>Film</b>				
<b>Polyester (Mylar)</b>				
Film/foil	0.001—1.0	80—200 VDC	+ 125*	± 5—± 10
Metalized	0.001—10.0	60—630 VDC	+ 125*	± 5—± 10
<b>Polycarbonate</b>				
Metalized	0.01—10	100—630 VDC	+ 125*	± 5—± 10
<b>Polystyrene</b>				
Film/foil	47 pF—0.039	63—630 VDC	+ 85	± 1—± 5
<b>Polypropylene</b>				
Film/foil	47 pF—0.022	63—630 VDC	+ 85	± 2—± 5
Metalized	0.001—3.3	250—100 VDC	+ 85	± 5—± 10
<b>Ceramic</b>				
<b>Multilayer</b>				
Disc	10 pF—.56	200 VDC	+ 125	± 5—± 10
Disc	.75 pF—2.2	50—6 KVDC	+ 125	± 5—± 10
<b>Mica</b>				
	1 pF—0.1	50,000	+ 150	± .25—± 5
<b>Glass</b>				
	10 pF—0.15	6000	+ 125	± 1—± 20
<b>Electrolytic</b>				
<b>Aluminum</b>				
	1.0—1 MEG	5—450	+ 105	- 10—+ 100
<b>Tantalum</b>				
Wet slug	1.7—2400	6—630	+ 125	± 5—± 20
Wet foil	.12—3500	3—300	+ 125	± 5—± 20
Solid slug	0.0023—1000	6—100	+ 125	+ 5—± 20

\* With derating

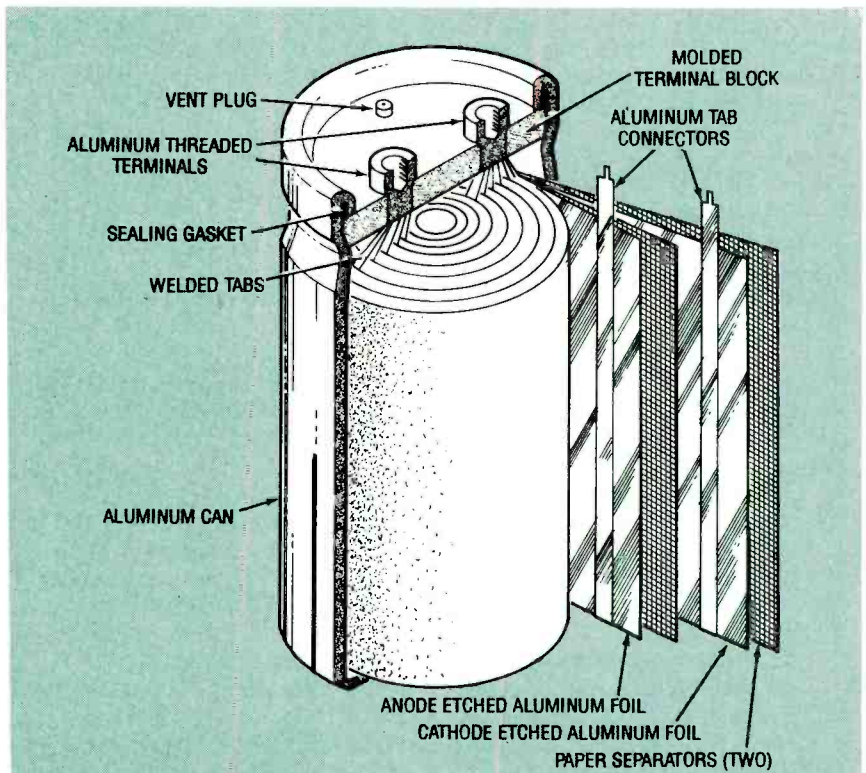

**FIG. 5—VIEW OF AN ALUMINUM ELECTROLYTIC CAPACITOR** shows how the cathode (porous paper spacer filled with liquid electrolyte) is sandwiched between the oxidized aluminum anode foil and cathode connection foil, rolled into cylinder, and then sealed in an aluminum can.

have metalized-band contacts on the ends of their epoxy-coated bodies for soldering to lands of surface-mount circuit boards.

For conventional through-hole mounting, axial or radial leads are attached, and the chip is jacketed by dipping or molding in epoxy. MLC capacitors are specified for bypassing noise to ground, timing, and frequency selection.

### Ceramic dielectrics

Ceramic dielectric materials are classified by dielectric constant  $k$  as Class I, Class II and Class III:

- *Class I* dielectrics are made by mixing magnesium titanate (for a positive temperature coefficient) with calcium titanate (for a negative coefficient) to form a dielectric material with low  $k$  values, and properties essentially independent of frequency. They exhibit ultrastable temperature coefficients of  $\pm 30$  ppm/ $^{\circ}$ C over the temperature range of  $-55^{\circ}$  to  $+125^{\circ}$ C. Class I includes NPO (negative, positive, zero), also known as COG and BY.

- *Class II* dielectrics are high- $k$  materials (called ferroelectrics) based on barium titanate. With the addition of barium stannate, barium zirconate, or magnesium titanate, their dielectric constants can be lowered from values as high as 8000 for increased temperature stability. These dielectrics include general purpose X7R (BX) and Z5U (BZ).

- *Class III* dielectrics were developed primarily for ceramic disc capacitors because they permit high volumetric efficiency. But this introduces a trade-off between high leakage resistance and low dissipation factor. Class III capacitors have low working voltages.

### Other electrostatic capacitors

The dielectric in a *mica* capacitor is mica, a natural mineral that is chemically inert and very stable. The capacitor is generally made as a "sandwich" of alternating layers of tin-lead foil plates and mica. These capacitors can operate at tempera-

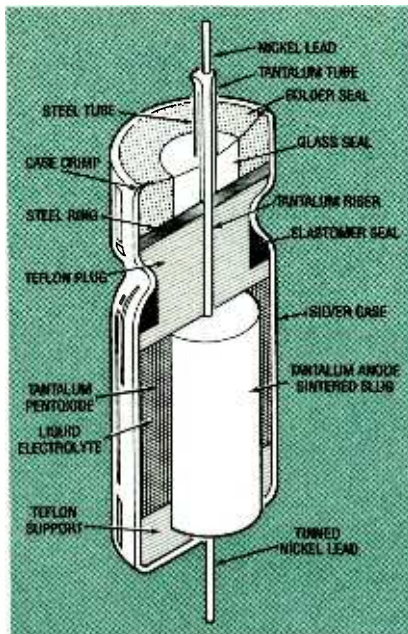


FIG. 6—CUTAWAY VIEW OF WET-SLUG tantalum capacitor shows tantalum slug filled with wet-electrolyte sealed in a silver case.

ture up to  $+150^{\circ}$ C. Silvered mica capacitors offer greater mechanical stability and more uniform characteristics. They are made by screening and firing a thin layer of silver on the surface of the mica to form the plates.

Glass capacitors are made by stacking alternate layers of thin glass dielectric in a sandwich structure similar to that of the mica capacitor. They are specified where temperature stability is a requirement.

### Electrolytic capacitors

The dielectrics of aluminum and tantalum electrolytic capacitors are oxides formed by electrochemical reaction with those metals. There are three styles of electrolytic capacitor: wet foil, wet slug, and dry or solid slug. Aluminum electrolytic capacitors are wet foil units, but tantalum capacitors are also available as wet-slug and solid slug units. They can be polarized or nonpolarized.

All electrolytic capacitors exhibit high capacitance per unit volume (high volumetric efficiency). An aluminum electrolytic capacitor can store four, five or more times the charge of an equivalent-size film capacitor, and a tantalum capacitor

can store three times as much charge as an equivalent aluminum capacitor.

However, aluminum electrolytic capacitors have higher DC leakage and lower insulation resistance than electrostatic capacitors. Moreover, they have higher power losses because of their higher equivalent series resistance (ESR).

The anodes of aluminum electrolytic capacitors are made from high-purity aluminum foil that has been electrochemically etched to increase its effective surface area. A thin aluminum-oxide-dielectric layer, about 0.01 micron, is then grown on the etched foil in another electrochemical process. The enlarged surface area of the etched foil provides a far larger dielectric surface than would be possible with unetched foil.

A porous paper spacer filled with a liquid electrolyte is sandwiched between the etched and oxidized anode foil and another aluminum cathode foil. The liquid electrolyte is the actual cathode, but the cathode foil is in contact with the liquid electrolyte and is needed to complete the electrical circuit.

After attaching a series of connecting tabs to the foils, the "sandwich" is rolled, as shown in Fig. 5, and inserted in an alu-

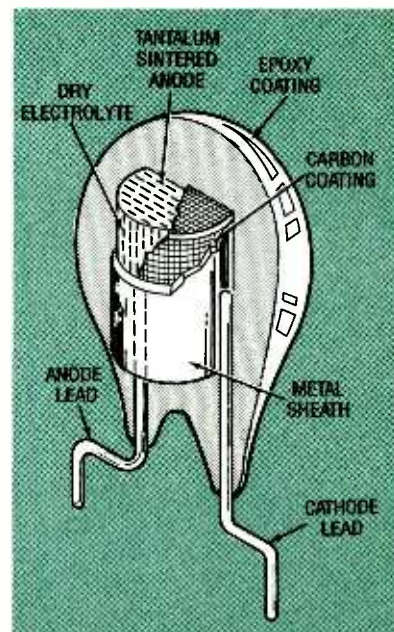


FIG. 7—CUTAWAY VIEW OF A SOLID tantalum capacitor jacketed by dipping in epoxy.



minum can, which is then sealed. However, the sealed can has an overpressure vent.

Direct current must flow in only one direction in a polarized electrolytic capacitor. Even short-term current reversal could destroy the oxide dielectric and short-circuit the capacitor. A "+" mark on the case identifies its positive terminal.

Aluminum electrolytic capacitors are made with radial or axial leads, and some styles for switchmode power supplies have spring-metal terminals that snap into circuit board holes. An external plastic sleeve permits off-ground applications for the capacitor.

*Nonpolarized* aluminum electrolytic caps are essentially two polarized capacitors back-to-back with their cathode terminals connected. The anode terminals make the external circuit connection, while the cathode terminals are isolated by an insulator. Both foils are anodized to form oxide barriers, and they share a common electrolyte-filled porous spacer.

A nonpolarized capacitor has half the capacitance of a comparably sized polarized capacitor with the same voltage rating. Although not as efficient as polarized capacitors, the nonpolarized units are used for AC motor starting and other AC control applications.

### Tantalum capacitors

Tantalum electrolytic capacitors are available in three forms: wet-foil, wet slug, and dry slug. Wet-foil tantalum capacitors are made in about the same way as aluminum electrolytics. As a group, tantalum capacitors exhibit higher volumetric efficiency, more stable characteristics, higher operating temperature ranges, and longer shelf lives than aluminum capacitors. However, they cost more and have lower voltage ratings.

Both wet and dry slug tantalums are made from porous pellets of tantalum. The anode slug is formed by pressing tantalum powder and a binder in a mold, and firing it in a vacuum furnace (*sintering*) to bond the powder and drive off the binder.

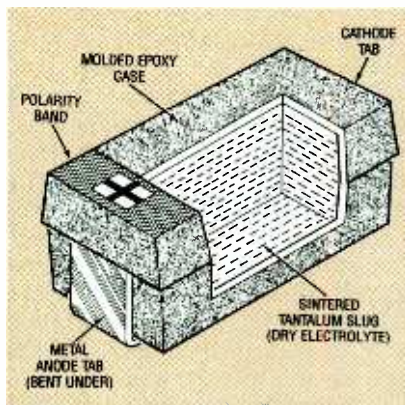


FIG. 8—CUTAWAY VIEW OF A SOLID tantalum capacitor chip for surface mounting applications.

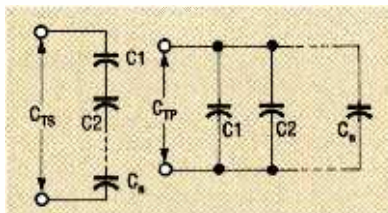


FIG. 9—CONNECTING CAPACITORS in series yields a total capacitance that is less than that of the lowest-value unit (a), but connecting them in parallel yields a total capacitance equal to the sum of all unit values.

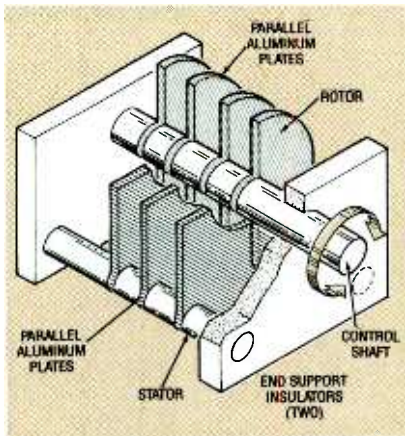


FIG. 10—SIMPLIFIED DRAWING of a tuning capacitor shows a concept that is used in many variable capacitors.

The tantalum oxide dielectric is electrochemically formed in the porous pellet.

Figure 6 is a cutaway view of a wet-slug tantalum capacitor with an acid electrolyte. Its volumetric efficiency about three times that of a comparably sized foil unit. Moreover, wet-foil tantalums are the most reliable of all capacitors.

The high cost of wet-foil and wet-slug tantalums makes

them too expensive for most consumer and industrial applications. However, those high-reliability capacitors are widely specified for military electronics and avionics. Military specifications MIL-C-3965 and MIL-C-39006 govern the procurement of military-style wet-foil and solid-slug units.

The solid-anode or dry-slug unit, shown in Fig. 7, is the most popular and economical tantalum capacitor. It has a thin film of manganese dioxide chemically deposited on its tantalum dioxide dielectric to act as a second electrode. Solid-slug capacitors can be sealed in metal cases, or protected by dipping in epoxy as shown in Fig. 7. The solid-slug units have the longest life and lowest leakage of any tantalum caps. Chip capacitors for surface mounting, as shown in Fig. 8, are made by the same process.

### Capacitor identification.

Today the capacitor's nominal value (and sometimes its tolerance) are printed on its body where space permits. Values such as 47 and 68 are typically in microfarads, while values such as 120 or 4700 are usually in picofarads. A capacitor might also be marked with its working voltage: for example, 63 V or 100 V.

Some capacitors are still marked with colored bands based on the EIA system used for identifying resistors. The colors of the bands are read from left to right. A black band represents zero, brown represents one, and red, orange, yellow, green, blue, and violet represent the digits two to seven, in that order. Grey represents eight, and white represents nine. As in resistor coding, a gold band denotes a capacitive tolerance of 5%, while a silver band denotes 10%.

You might encounter capacitors with obsolete coding schemes in old radios or TVs or at surplus sales. Some of those codes are based on colored dots, spots or "hashmarks." It is wise to consult a radio engineering handbook or data reference book published before 1970 if

you want to find out how to interpret those codes if you plan to use them in your circuits and are in doubt about their ratings.

### Connecting capacitors

Figure 9 illustrates capacitors connected in series and parallel. The formula for calculating the effective value of two capacitors in series is:

$$C_{TS} = C1 \times C2 / C1 + C2$$

For two or more capacitors in series it is:

$$C_{TS} = 1 / 1/C1 + 1/C2 + 1/C3 + 1/C_n$$

For capacitors in parallel the formula is:

$$X_{TP} = C1 + C2 + C3 + C_n$$

### Variable capacitors

For many years the most prominent variable capacitors were those used to tune radio receivers, transmitters, and oscillators. However, in the latest transistorized equipment they have been largely superseded by varactors or voltage variable ca-

pacitors. These are silicon or gallium arsenide PN junction diodes that make use of the variation of junction capacitance with reverse bias. Nevertheless, the design concept embodied in the tuning capacitor lives on in a wide range of miniature, PC board-mounted variable capacitors for many different tuning applications.

Figure 10 is a simplified sketch of an air-dielectric tuning capacitor. Its capacitance value can be changed by rotating its control shaft so that the movable set of metal plates (rotor) meshes in different positions with respect to the fixed set (stator). Its capacitance value is greatest when the rotor is fully meshed with the stator.

The rotor plates of tuning capacitors can be shaped so that, with shaft rotation, capacitance variation is linear or nonlinear. For example, it might follow a nonlinear logarithmic or square law function. Two or more tuning capacitors can be ganged to-

gether so that they vary in unison, simultaneously tuning separate circuits to different frequencies.

Trimmer capacitors are "set and forget" variable capacitors made for infrequent adjustment. Many different types are available for commercial and industrial applications. Vane types are miniaturized versions of the tuning capacitor shown in Fig. 10, except that layers of solid dielectric, typically plastic, are inserted between the rotor and stator plates.

Vane-type trimmers with body diameters of less than a half inch are made for PC-board mounting. They have plastic cases and dielectrics of polypropylene, polyethylene, polycarbonate, or PTFE films. These trimmers are made for screwdriver and/or key adjustment.

There are also simpler trimmer capacitors that permit more limited capacitance variation for high-frequency tuning applications.  $\Omega$

FREE CATALOGUE

## ACTIVE KITS

### ELECTRONIC PROJECTS

1-800-465-KITS



**A029..8-CHANNEL STEPPER MOTOR DRIVER**

**EVERY ACTIVE KIT CONTAINS:**

- All components including printed circuit board and solder
- Complete assembly instructions and schematic diagrams

<p>A001.. 1-24VDC Regulated Power Supply...\$21.95</p> <p>A002.. 16 LED Light Chaser.....\$19.95</p> <p>A003.. 2000 Watt Colour Light Organ.....\$22.95</p> <p>A004.. 2 Channel Audio LED Power Meter..\$16.95</p> <p>A005.. Variable Strobe Light.....\$16.95</p> <p>A008.. 1 MHz Function Generator.....\$33.95</p> <p>A009.. Stepper Motor Controller.....\$29.95</p> <p>A010.. 8 Watt Audio Amplifier.....\$21.95</p> <p>A011.. Electronic Siren.....\$21.95</p> <p>A012.. Power Supply +12V@2.5A; +15V..15V@1A.....\$25.95</p> <p>A013.. Digital Capacitance Meter.....\$38.95</p> <p>A014.. Digital Volt Meter.....\$23.95</p> <p>A015.. 12 Volt Fluorescent Ballast.....\$12.95</p> <p>A016.. 9 Volt Digital Dice.....\$16.95</p> <p>A017.. Battery Level Monitor.....\$12.95</p> <p>A018.. LED Light Sweeping Star.....\$16.95</p>	<p>A019.. Remote InfraRed Switch.....\$16.95</p> <p>A020.. Digital Timer.....\$29.95</p> <p>A021.. Stepper Motor Controller #2.....\$33.95</p> <p>A022.. 8 Channel 120V Light Chaser.....\$20.95</p> <p>A023.. Electronics 101.....\$38.95</p> <p>A024.. Logic Probe.....\$19.95</p> <p>A025.. Fire Ball.....\$29.95</p> <p>A026.. Bug Off.....\$8.95</p> <p>A027.. 100W High Power Audio Amplifier...\$42.95</p> <p>A028.. Low Voltage Strobe.....\$16.95</p> <p>A029.. 8 Channel Stepper Motor Driver.....\$50.95</p> <p>A030.. Unreg. Power Supply +/- 45VDC.....\$59.95</p> <p>A031.. Speaker Switch Box</p> <p>A032.. 10-30V, 3A Reg. Power Supply</p> <p>A033.. Resistor Switch</p>
--	---

**ANY MORE TO COME**  
**CALL 1-800-465-5487**

All kits quoted in U.S. dollars. No C.O.D. orders please.

**ACTIVE KITS — 345 QUEEN ST. W., TORONTO, ONT. M5V 2A4**

GET THE LATEST ADVANCES IN ELECTRONICS

WITH A SUBSCRIPTION TO

# Electronics

Radio Combined with  
**Electronics**

# NOW



ENJOY THE WORLD OF ELECTRONICS EACH MONTH!

Electronics Now looks to the future and shows you what new video, audio and computer products are on the horizon. What's more you'll find helpful, monthly departments such as Video News, Equipment Reports, Hardware Hacker, Audio Update, Drawing Board, Computer Connections, New Products, and more. All designed to give you instruction, tips, and fun.

## SUBSCRIBE TODAY

Just fill out the order card  
in this magazine and mail it in today.

**FOR FASTER SERVICE CALL TODAY**  
**1-800-999-7139** 7RC35




# FORCE-SENSING RESISTORS

ONE OF THE MANY modern sensor technologies is really keeping engineers and hobbyists quite busy designing circuits. Billed as the ultimate switch technology, the Force Sensing Resistor (FSR) is a tactile sensor that discerns variations in applied force. The harder you press this thick-film device, the more its resistance decreases. The FSR was first developed for musicians who wanted their electronic pianos to play louder when the keys were pressed harder. FSR's are temperature, chemical, and moisture resistant, and they are insensitive to vibration and electromagnetic interference. FSR's contain no moving parts to wear out, and can withstand

over ten million operations. Figure 1 shows some of the different types of FSR's.

FSR's are as thin as business cards, and can be designed to sense forces as light as a fingertip or as heavy as a truck. They can also sense variations in applied pressure and alter their response accordingly. In addition, the sensor's actuation threshold can be adjusted using simple electronics. Applications for FSR's are virtually unlimited, as you can see from Table 1. The FSR is ideally suited to keypads, computer input devices, touch switches, alarm sensors, limit switches, electronic keyboards, digitizers, and pressure sen-

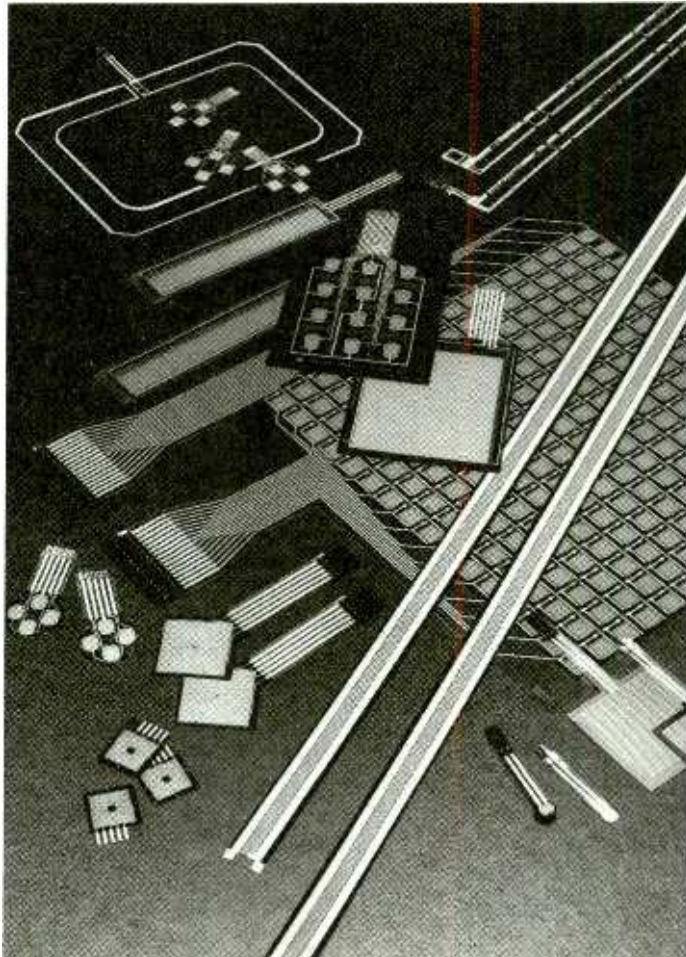

## ***Force-sensing resistors open up lots of new applications for electronics.***

T.L. PETRUZZELLIS

sors.

An FSR device typically exhibits three decades of dynamic resistance change with respect to force and it can operate at much lower currents than most

other sensors. The FSR can also be used to construct a linear potentiometer which can monitor the *position* of a force as well as the *amount* of applied force. A three-layer XYZ-type FSR device can be constructed that will give an X-Y coordinate position indication with a 0.005-inch resolution, as well as provide the force (Z) measurement. The XYZ pad is ideal for such applications as a graphic pad, pen stylus tablet, or mouse-type device for computer input. The FSR sensors can also be configured into many different types of switch arrays, with sizes up to 22 × 32 inches, at much lower cost than many other force sensors.

In the past, there were two principle types of force sensors: piezopolymers and ceramic strain gauges. The fast rise times and high sensitivities of the piezopolymers cause a lot of unwanted acoustic and vibration pickup. Piezopolymer sensors often require more complex interfacing than the FSR devices. FSR sensors are not as accurate for precise absolute measurement, but they are much more rugged and cost considerably less than strain-gauge sensors.

The construction of an FSR is a sandwich of two polymer films or sheets. A conductive pattern is deposited on one of the polymer sheets as a pattern of inter-

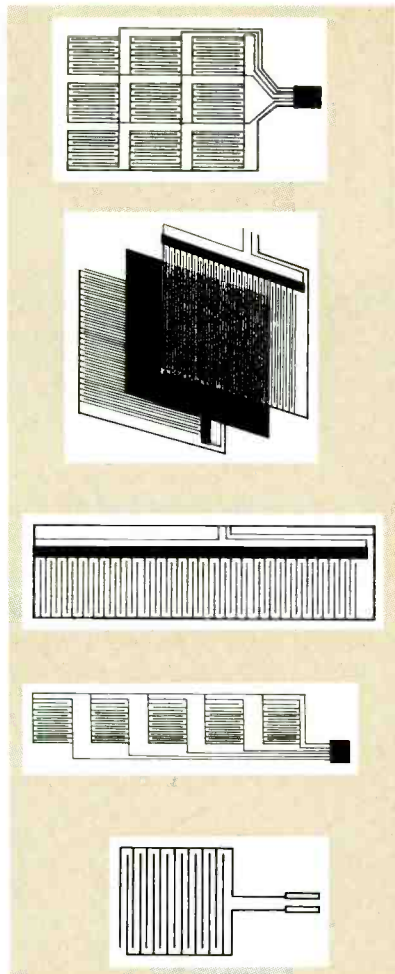


FIG. 1—FORCE-SENSING RESISTORS contain no moving parts to wear out and then can withstand over ten million operations.

digitating electrodes as shown in Fig. 2. The electrode pattern often looks like a comb, with the teeth and spacing typically being less than one millimeter. Next, a proprietary polymer is deposited on the other sheet. The sheets are then faced together so that the conducting fingers are shunted by the polymer.

The output resistance of the FSR is typically around one megohm with no external force applied. A force-versus-resistance graph is shown in Fig. 3. The graph displays the log/log characteristics of an FSR where the resistance varies from one megohm to around 50 kilohms, depending on the applied force in grams (g). (We know that a gram isn't really a force, but let's just think of it that way for the moment.) Figure 4 shows a

TABLE 1—FSR APPLICATIONS

Graphic pads	Suspension sensors
Cursor keys	Accelerometers
Mouse devices	Water-level sensors
Pen stylus tablets	Panel switches
Pressure sensors	Digital tuning controls
Piano keyboards	Joysticks
Toner-level sensors	Game controllers
Foot pedals	Steering wheels
Gait-analysis sensors	Gas pedals
Artificial-limb force sensors	Robotic touch sensors
Dental-byte sensors	Industrial keyboards
IV drip pressure sensor	Deadman safety switches
Bed weight distribution sensor	Smart brake pedals
Security tiles/alarm sensors	Oil-pressure sensors
Load cells	Limit switches

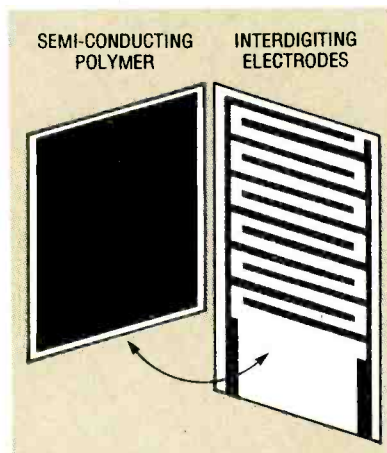


FIG. 2—AN FSR IS MADE OF two polymer films or sheets. A conductive pattern is deposited on one of the polymer sheets, and a proprietary polymer is deposited on the other sheet.

force-versus-conductance graph in which a simple linear response is shown from a force of zero grams. A key element in the design of an FSR is the fineness of the pitch of the conducting fingers. The force-versus-resistance relationship is strongly affected by sensor and actuator size, shape, and materials.

#### Linear potentiometer FSR's


When force-sensing resistors are used to make a linear potentiometer (an FSR-LP), the device can be used to sense both position and applied force. Figure 5 depicts the layered construction of an FSR-LP. When wiring an FSR-LP, a voltage is

applied between the hot lead and ground. When a force is applied to the force-sensing layer, the wiper contacts are shunted through that layer to one of the conducting fingers of the resistance strip. The voltage from the wiper is then proportional to the distance along the strip. To sense a force, a resistance measurement is made between the wiper terminal and either the hot or ground lead. Two alternative FSR-LP connection diagrams are shown in Fig. 6.


Force and position measurements are not entirely independent; however, the position measurement can be made unambiguously if the measuring device draws a negligible amount of current (less than 1 microampere) so that there is no voltage drop across the wiper resistance. Therefore, an LF411 or similar op-amp—with a low  $V_{OS}$  and  $I_{BIAS}$ —is recommended when interfacing to an FSR-LP. Because the contact between the wiper and the resistor is momentary, some kind of sample-and-hold device must be used to interface an FSR; quite often a capacitor between the wiper contact and ground is sufficient to accomplish this.

Force measurements are less ambiguous, and very good approximate measurements can be obtained by shorting the two fixed resistor ends (hot and ground) together, and measuring the resistance between the



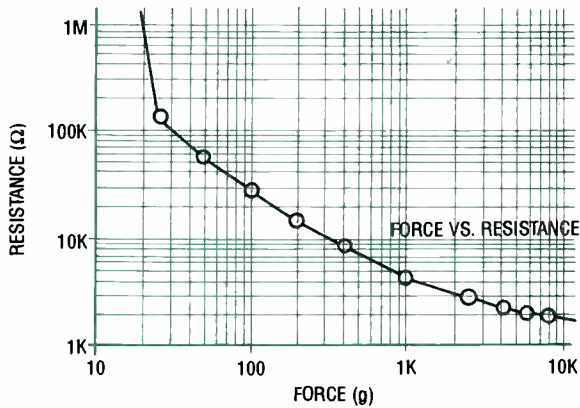

**FIG. 3—FORCE-VERSUS-RESISTANCE.** The resistance varies from one megohm to around 50 kilohms, depending on the applied force.

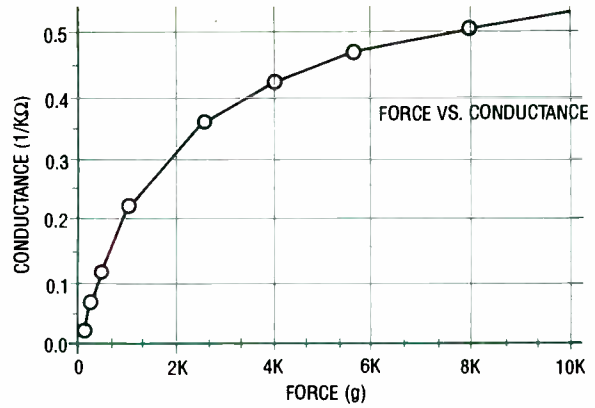

**FIG. 4—FORCE-VERSUS-CONDUCTANCE.** The linear response is shown from a force of zero grams to 10,000 grams, or 10 kilograms.

combined leads and the wiper. If the force is applied at the middle of the potentiometer, the device will have an additional resistance of one half of the total fixed resistance, because the resulting middle contact parallels the two halves of the fixed resistor. If, on the other hand, force is applied to either end of the FSR-LP's active area, the fixed resistance is essentially shorted out. That problem can be overcome by making the FSR resistance high compared to the potentiometer resistance, therefore making a low-current position measurement a must. The slight force-measurement error can also be subtracted out with a simple analog circuit or, given a position measurement, compensated for in software if a microprocessor is used with the system.

The positional resolution of a force and position sensing resistor (FPSR) depends on the width of the applied force, distribution, and the fineness of the conductive fingers, which is typically in the 10–100 micrometer range.


### FSR-LP XYZ

An XYZ pad or tablet is constructed by placing two FSR-LP's back-to-back and perpendicular to each other. An XYZ pad can measure the position of a force on an X-Y coordinate plane, as well as the applied force (Z). Figure 7 shows the layered construction of an XYZ pad. Note that an unambiguous


position can be measured only for a single applied force; multiple force contacts will cause false readings. That is not a problem for graphics pads, mouse devices, or pen stylus tablets, but the XYZ pad cannot be used for complex pattern recognition. Position accuracy of an XYZ pad based on FSR-LP's is typically about 1 percent.

A true force sensor will give a constant reading at a constant force, independent of the area over which the force is applied, or its distribution. If a constant force is applied to a true pressure sensor, the reading will be inversely proportional to the area of the applied force. An FSR has a function that is between a force and pressure sensor. A typical FSR will display the resistance of the square root of the area of the applied force. That holds true when the force footprint is smaller than the FSR's active area, and large compared to the spacing between the conductive electrodes or fingers. Because of the sensitivity of the FSR's resistance to the area and distribution of force, the force footprint must be held constant in position and distribution. An elastomeric or rubber overlay placed over the sensor can solve that problem. The FSR can be used as a pressure sensor when the applied force is large compared to the FSR's active area.

FSR devices are designed to be easily interfaced with a wide variety of circuitry. A simple

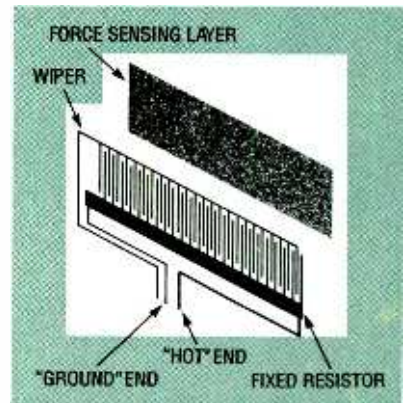

**FIG. 5—FSR-LP'S CAN SENSE** both position and applied force. This is the layered construction of an FSR-LP.

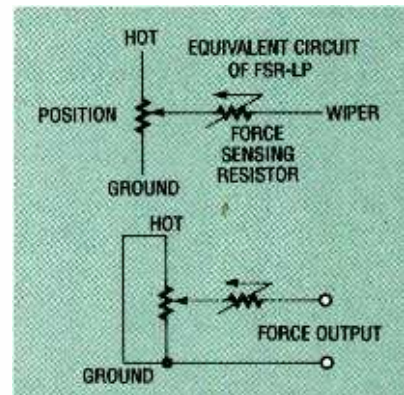

**FIG. 6—ALTERNATIVE FSR-LP connection diagrams.**

analog interface is shown in Fig. 8. A basic requirement for interfacing an FSR is to ensure that the current through the device does not exceed 1 mA/cm<sup>2</sup> of the activation footprint. The voltage measurement across the FSR is then related to the applied force, and increased pressure results in increased

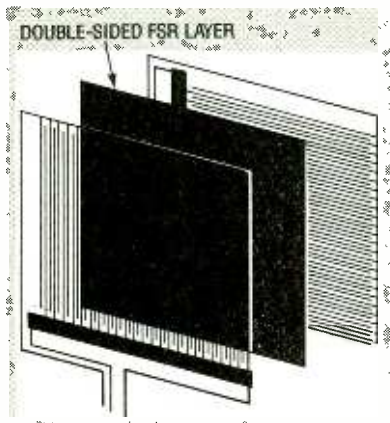


FIG. 7—AN XYZ PAD IS TWO FSR-LP'S back-to-back and perpendicular to each other.

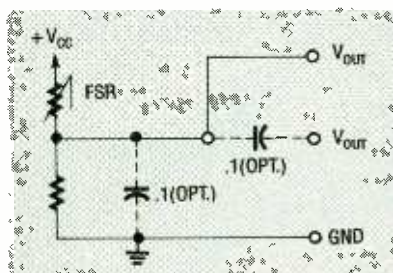


FIG. 8—FSR ANALOG INTERFACE. Increased pressure results in increased voltage output.

voltage output. Precision measurements, however, are a somewhat more difficult because of the shape of the power law curve. For higher precision measurements, it is usually wise to go into the digital domain as soon as possible, so that the log/log characteristics of the device can be translated into more linear results.

If your design calls for measurement of impact (i.e. a data keyboard), then the FSR can be placed in a voltage divider, and the divider can be capacitively coupled to the succeeding stages. That would eliminate offset problems due to a preload condition. The interface shown in Fig. 9 is useful where a higher current or a lower source impedance is necessary. The op-amp can be used either as a unity-gain buffer, or it can be configured to amplify the FSR's output. Offsets can be trimmed by the 500-ohm potentiometer. Gain is set by the ratio of the resistors  $R_F$  and  $R_S$ . Suggested op-amps for that circuit are the

LF351/353 or the TL071/72 series of low bias-current devices. The low bias currents of those op-amps reduces the possible input offsets, due to the high source impedances of the FSR.

Figure 10 shows a force-to-frequency converter. In that circuit, an oscillator is constructed with the FSR as a feedback element around a Schmitt trigger integrated circuit. At zero pressure, the FSR is an open circuit. Depending on the last stage of trigger, the

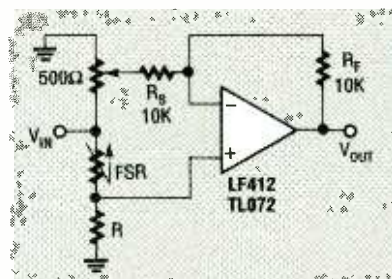


FIG. 9—THIS INTERFACE is useful when higher current or lower source impedance is necessary.

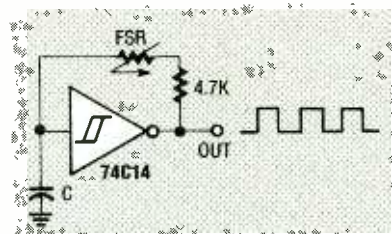


FIG. 10—FORCE-TO-FREQUENCY CONVERTER. An oscillator is constructed with the FSR as a feedback element around a Schmitt trigger.

output remains constant—either high or low. When pressure is applied to the FSR, the oscillator starts, and its frequency increases with increasing force applied to the FSR. Resistor  $R_1$  limits the current through the sensor. Bypassing  $R_1$  with a capacitor will cause the curve to be steeper at higher forces. Connecting a large-value resistor in parallel with the capacitor (C), quenches any tendency for the circuit to oscillate at low applied forces. When using the circuit with CMOS or TTL, a digital process can be controlled by counting leading or trailing edges of the oscillator output.

Industry-standard connectors, such as pin- or com-

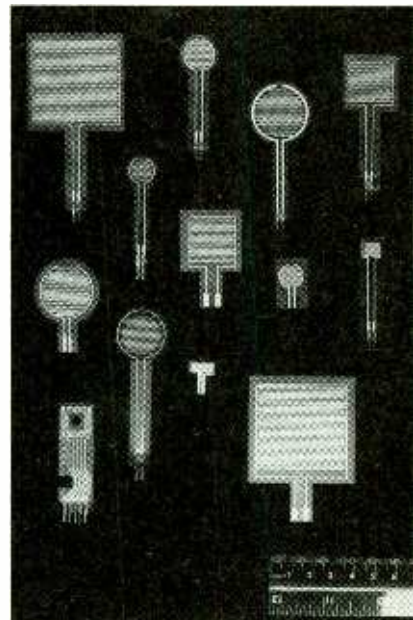



FIG. 11—THIS PHOTOGRAPH shows some of the many different shapes and sizes of available force-sensitive resistors. The ruler in the lower right-hand corner gives you an idea of their size.

pression-types, can interface the FSR devices. Conductive adhesives are also commonly used to attach leads to FSR devices. Do not attempt to solder wire leads directly to the polymer sensor, because direct heat will destroy the device.

The force-sensing resistors require a backing for activation accuracy, as mentioned previously. The most unpredictable aspect of the FSR's force/resistance characteristic is the pressure range under 100 grams/cm<sup>2</sup>. If you are going to measure small forces with your FSR, you can preload the FSR with a 100–200 gram/cm<sup>2</sup> load and measure the resistance changes. Elastomer or plastic overlays can be used to enhance the FSR's response characteristics by evenly spreading the actuator's force.

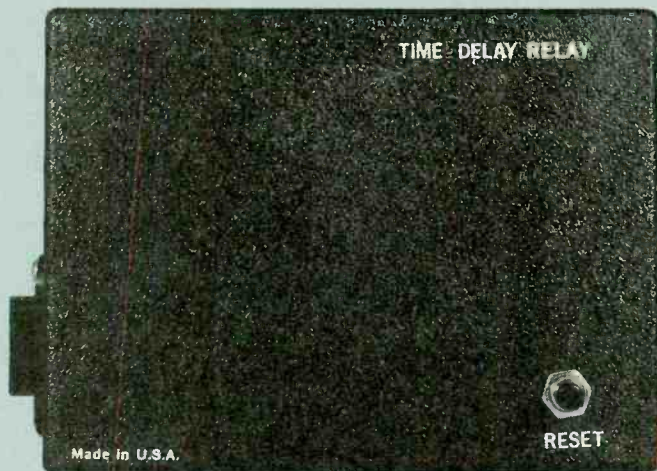FSR sensors are available in many sizes, configurations, and shapes, and custom devices can be designed by the manufacturer. For more information on FSR technology, write on your company letterhead to Interlink Electronics, 1110 Mark Ave., Carpinteria, CA 93013. An evaluation/prototype kit is also available for \$79.95.  $\Omega$





# TIME DELAY RELAY

JAMES MELTON

## Stop wasting power—turn off your appliances automatically with an electronic time-delay relay.

OUR TIME-DELAY RELAY WILL DRIVE up to a 3-ampere AC load for a specified period of time, and then shut the load off automatically. It can turn electrical appliances and lights off after a time interval ranging from just a few seconds all the way up to about an hour.

One of the many possible jobs for the relay is the control of indoor Christmas lights—just push a button and the lights will stay on for a few hours, and then automatically turn off. Outdoor Christmas lights, although a considerably larger load, can also be controlled by one of these relays.

The author has several different antennas that are connected to amateur radio equipment in his garage. As a precaution, the feedlines to the radios are routed through mechanical relays that keep them grounded when not powered, and they are connected to the radios only when the reset switch on the time-delay relay is pushed. Several hours later, if he has been called away from the radios (and forgotten that they were on), the relay drops out, and the antennas will have been automatically grounded.

One of these units can even be used with a coffee maker. Quite often coffee makers are left on

overnight or over the weekend; the owner returns to find a ruined coffee pot—and a very hot one at that. A time-delay relay in the burner circuit will solve that problem. Simply set the timer to stay on for 2 hours, and if it's not reset, it will allow the coffee pot to cool off.

### Operation

The circuit, shown in Fig. 1, is based on a 4060 CMOS 14-stage binary counter with an on-board oscillator driver. The basic frequency is set by the values of R1, R2, and C1, and it's

roughly  $1/R1 \times C1$ . Resistor R2 should be about 10 times the value of R1. The values shown generate an approximate 4.5-hertz frequency, which is then divided down by IC1. Divided outputs are available ranging from divide-by-4 to divide-by-16384 (see Fig. 1).

The chosen output is tied to the base of Q1 through current-limiting resistor R4, and to the base of Q2 through R3. Transistor Q1 is the hold transistor for the timing circuit, and transistor Q2 turns on the solid-state relay.

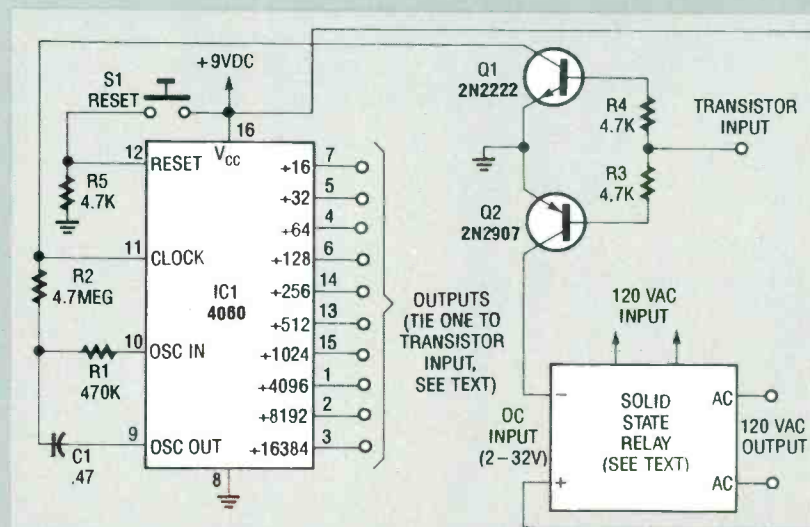


FIG. 1—THE CIRCUIT is based on a 4060 CMOS 14-stage binary counter that controls a solid-state relay.

## LETTERS

continued from page 17

When you push reset button S1, all of IC1's outputs go low (including the one you have tied to the transistor input). Transistor Q1, an NPN unit, shuts off and its collector, which is tied to timing resistor R2, presents no load to the timing circuit. Transistor Q2, a PNP unit, turns on when a low is applied to its base, thus turning on the solid-state relay.

When the chosen output of IC1 goes high, Q1 turns on, grounding the clock input to IC1, stopping any further counting until S1 is pushed again. At the same time, Q2 shuts off, which turns off the solid-state relay, thus cutting off power to the load.

### Construction

The author built his pro-

### PARTS LIST

All resistors are 1/4-watt, 5%.

R1—470,000 ohms

R2—4.7 megohms

R3—R5—4700 ohms

#### Capacitors

C1—0.47  $\mu$ F, 25 volts, tantalum

#### Semiconductors

IC1—4040 CMOS timer/divider

Q1—2N2222 NPN transistor

Q2—2N2907 PNP transistor

S1—Normally-open pushbutton switch

**Miscellaneous:** Solid-state relay (sized for the application you have in mind), perforated construction board, wire, solder, AC linecord, project case.

### The relay in action

To use the solid state relay, simply plug the relay into a 120-

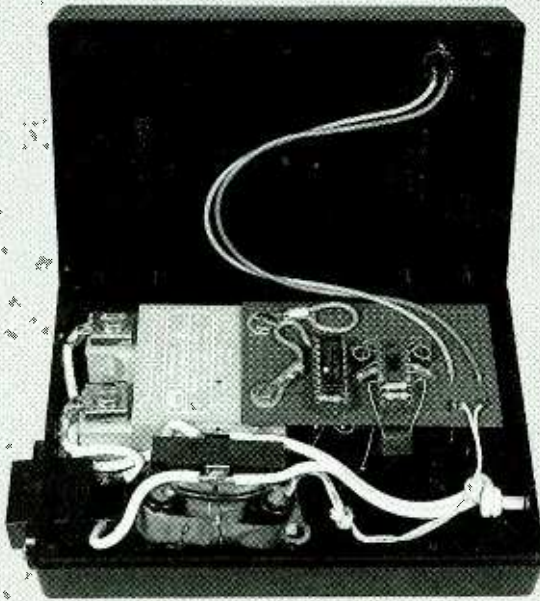


FIG. 2—THE PROTOTYPE RELAY is built on a small piece of perforated construction board mounted on the end of the solid-state relay.

totype relay on a small piece of perforated construction board using point-to-point wiring, and arranged the parts so that the board would mount on the end of the solid state relay (the input terminals are big enough to support the circuit board). Figure 2 shows the inside of the prototype. Note that the author has built in a 9-volt power supply that is not shown in the schematic.

volt outlet, plug an appliance (that draws no more than 3 amperes) into the time-delay relay, and push the reset button. The circuit will begin timing and will shut off at the end of the period you have selected. When you use the time-delay relay to shut off your appliances, you'll not only be adding a safety feature and saving money—you'll also be doing something good for the environment!  $\Omega$

diovisual phenomenon discussed anywhere. During a TV broadcast of a choir singing, my attention would inevitably focus on an individual singer (usually the cute one), and I would swear that I could hear her individual voice against a background of the entire choir.

Sure enough, when the camera zoomed in on her, she sounded exactly as I had earlier perceived she would. If there were several attractive choir members, I would be able to pick out their individual voices too. The cameraman apparently often agrees with my choices, and pans his camera on the photogenic singers during the performance. I can even keep track of their individual voices with closed eyes.

The same phenomenon seems to occur during orchestral performances, where I seem to be able to isolate individual instruments from the whole orchestra.

I cannot think of a way to test this phenomenon scientifically because what comes out of the speaker is a blended waveform. Thus, the perception must be the result of my visual clues together with the audio. I will chicken out with an escape clause: The human brain must be a wondrous organ if it is able to interpret such fine subtleties from a blended signal. But, all the same, I wonder if anyone else shares my illusions, or is there something more to this?

KELVIN MOK

Edmonton, Alberta, Canada

### SILICON CHIP

I was recently looking at *Silicon Chip*, an Australian electronics magazine that had lots of interesting projects in it. It would be good if **Electronics Now** could reprint some of these articles for readers in this country.

WILLIE JONES

Valley Stream, NY

*Good news for you! The magazine you mentioned, Silicon Chip, will soon be in print in this country. See the ad for it on page 25 of this magazine.*  $\Omega$



# BUILD THIS AUDIO EXPANDER

PHILL HAUSMAN

IT SEEMS THAT EVERYBODY IS AN audio enthusiast these days. With compact discs, stereo TV, hi-fi video tapes, and laserdiscs cheaply available to the general public, nobody wants to settle for ordinary sound. If you build our audio processor, you won't have to settle for ordinary sound either! Our audio processor, which can be built in one evening, can be installed easily between any audio output source and any audio input source, and it can "supercharge" any mono or stereo audio signal.

Some of the many uses for the audio processor include enhancing the audio output from a stereo system or any scanner, shortwave, CB, or ham radio receiver. Stereo and mono TV sound can also be greatly enhanced; a pseudo-stereo effect can be added to a mono soundtrack, and if stereo audio is already in use, you can add enhanced stereo effects. The processor also has amazing effects on old mono or pre-Dolby cassette and 8-track tapes—it's great for doing restoration of old recordings.

## Features

The audio processor provides a complete array of controls that give the user maximum flexibility in adjusting the processor. The unit has switch-selectable stereo sound from a stereo source, spatial (widened) sound from a stereo source, and pseudo-stereo sound from a mono source; LED's indicate which mode is selected.

The unit exhibits very low noise ( $-64$  dB minimum) and low total harmonic distortion (maximum THD is 0.5% at 1000 Hz). The input and output resistance is 100 kilohms, which is the standard line-level resistance. The left and right channels provide a minimum of 60 dB separation, and there's an adjustable input attenuator for



**Enhance stereo and mono audio, for under \$30, with our one-chip audio processor.**

each channel, which provides a minimum of 70.0 dB attenuation. There's independent gain adjustment of the left and right channels in the spatial stereo mode, and independent gain adjustment of the left and right channels in the mono pseudo-stereo mode.

## Theory of operation

The audio processor, whose schematic is shown in Fig. 1, is based on the Signetics/Philips TDA3810N stereo, spatial, pseudo-stereo processor IC. A block diagram of the chip is shown in Fig. 2. The device is essentially a system of internal op-amps used as active filters. The chip contains three op-amp stages, switching circuitry, power-supply regulation circuitry, and LED drivers.

The easiest way to understand how the chip works is to follow the audio signal through the chip for each individual mode.

## Stereo mode

When the stereo mode is selected, the left input signal

passes through input-attenuator R14, and is coupled via C4 to pin 2 of IC1 (the TDA3810N). The right input signal passes through R15 and C3 to pin 17 of IC1. The various active filters within IC1 serve as a unity-gain bandpass filter with a  $-3$  dB low-frequency cutoff occurring at 20 hertz, and the  $-3$  dB high-frequency cutoff occurring well beyond 20,000 hertz.

## Spatial mode

As shown in Fig. 3, when the spatial, or widened, stereo mode is selected, active op-amp circuits selectively remove certain parts of the audio spectrum. The effect is achieved by feeding the audio input to the non-inverting input of an op-amp. The inverting input is fed by the output of the internal buffer/amplifier coupled with a cross-channel signal through R2. Both channels operate in the same way. The gain of each channel can be adjusted independently: R3 adjusts the left channel and R1 adjusts the right channel.



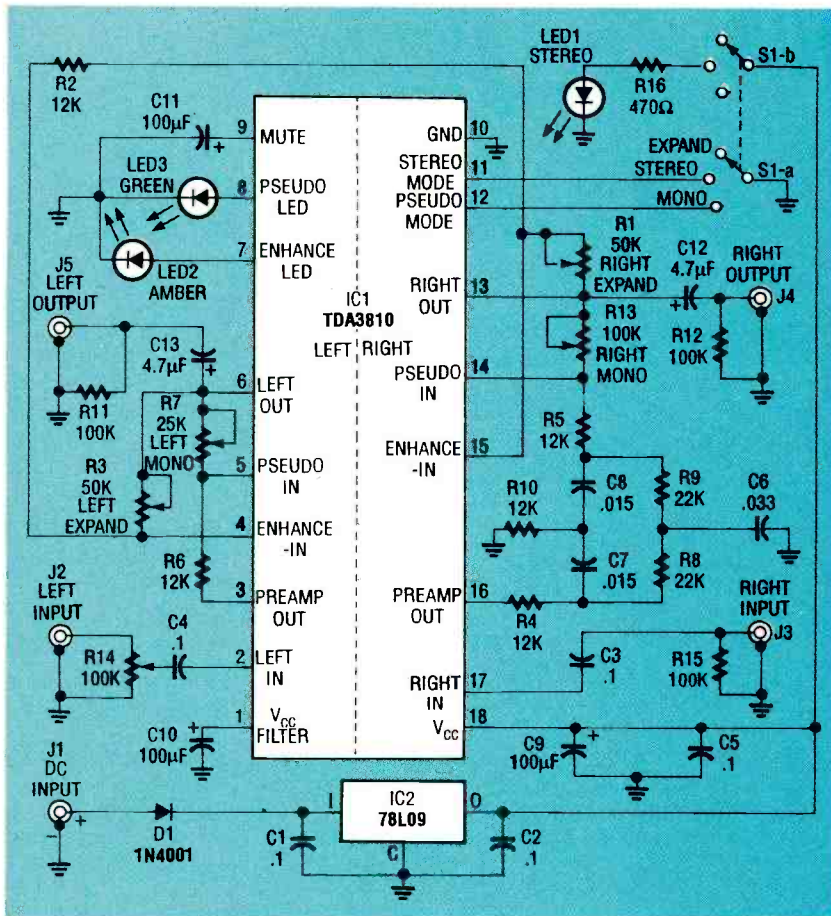


FIG. 1—THE AUDIO PROCESSOR is based on the Signetics/Philips TDA3810N stereo, spatial, pseudo-stereo processor IC.

### PARTS LIST

All resistors are ¼-watt, 5%, unless otherwise noted.

R1, R3—50,000 ohms, panel-mount potentiometer  
 R2, R4—R6, R10—12,000 ohms  
 R7—25,000 ohms, panel-mount potentiometer  
 R8, R9—22,000 ohms  
 R11, R12—100,000 ohms  
 R13—R15—100,000 ohms, panel-mount potentiometer  
 R16—470 ohms

#### Capacitors

C1—C5—.1 µF, 50 volts, metal film  
 C6—0.033 µF, 50 volts, metal film  
 C7, C8—0.015 µF, 50 volts, metal film  
 C9—C11—100 µF, 16 volts, electrolytic  
 C12, C13—4.7 µF, 35 volts, electrolytic

#### Semiconductors

IC1—TDA3810N audio processor chip (Philips)  
 IC2—78L09 9-volt regulator  
 D1—1N4001 diode  
 LED1—LED3—light-emitting diodes (use three different colors)

#### Other components

S1—DP3T panel-mount switch  
 J1—2.1 mm panel-mount power jack (optional)  
 J2—J5—panel-mount RCA jack  
**Miscellaneous:** 18-pin IC socket, metal project case, 12-volt DC wall transformer (100-mA), 6 knobs, PC board, shielded cable, wire, solder, etc.

**Note:** The following items are available from HESC, PO Box 12649, Fort Wayne, IN 46864-2649:

- A kit of parts including a PC board and all parts that mount on it (does not include potentiometers, project case, or wall transformer)—\$19.95 + \$3.05 S&H
- PC board and TDA3810N—\$14.95 + \$3.05 S&H
- TDA3810N—\$7.00 postage paid

Please allow 6 to 8 weeks for delivery.

### Pseudo stereo mode

As shown in Fig. 4, when the mono pseudo-stereo mode is selected, the processor creates a "stereo" image using the various active filters differently on each channel. The left channel is fed through a flat-response amplifier (200 Hz to 20 kHz) to achieve a constant gain across the audio spectrum. The gain is adjustable via potentiometer R7, which controls feedback. The optimum setting recommended by Philips, the chip manufacturer, is +2.00 dB at 15 kHz; R7 gives an adjustment range of -69.0 dB to +6.0 dB at 15 kHz.

The right channel uses a twin-T notch filter to give the illusion of signal separation, or the pseudo-stereo effect. Between 100 and 1600 hertz, the notch filter attenuates the audio range by -33.0 dB at its lowest point, which occurs at about 450 hertz. The gain is adjustable by R13, which controls feedback. Philips recommends 0 dB at 15,000 Hz, although R13 gives a range of -68.0 dB to +6.0 dB. Figure 5 shows the frequency response of each channel.

### Remaining circuitry

The TDA3810 contains a muting circuit with built-in hysteresis (controlled by C11) that prevents the status LED's from flickering when switching from mode to mode. Also included is the mode selection switch (S1-a and -b) and the corresponding status indicators LED1, LED2, and LED3.

The project requires an external power supply of +10.5–24.0 volts DC, which passes through polarity-protection diode D1 to the input of IC2, a 78L09 +9.0 volt DC, 0.1-amp voltage regulator. Capacitors C1 and C2 provide decoupling and anti-oscillation protection for IC2.

### Construction

Most of the parts for the audio processor are available from many electronics distributors. A foil pattern is provided if you want to make your own PC board, or you can use the board available from the source men-



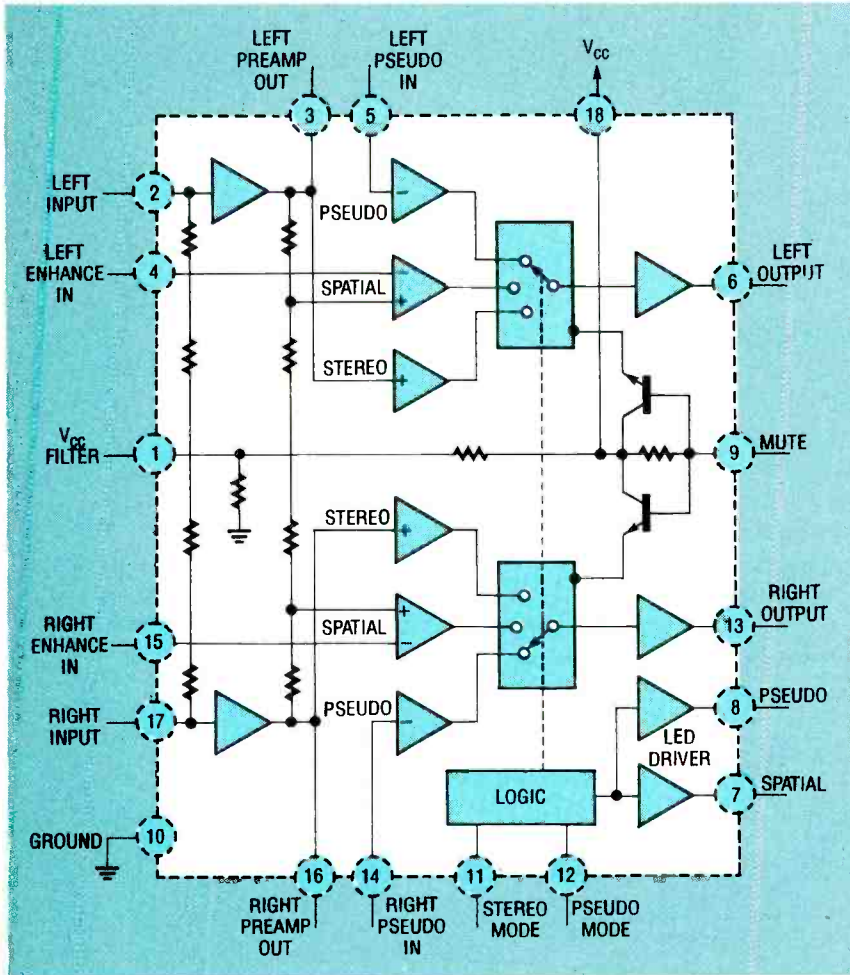


FIG. 2—BLOCK DIAGRAM OF THE TDA3810N. The device contains three op-amp stages, switching circuitry, power-supply regulation circuitry, and LED drivers.

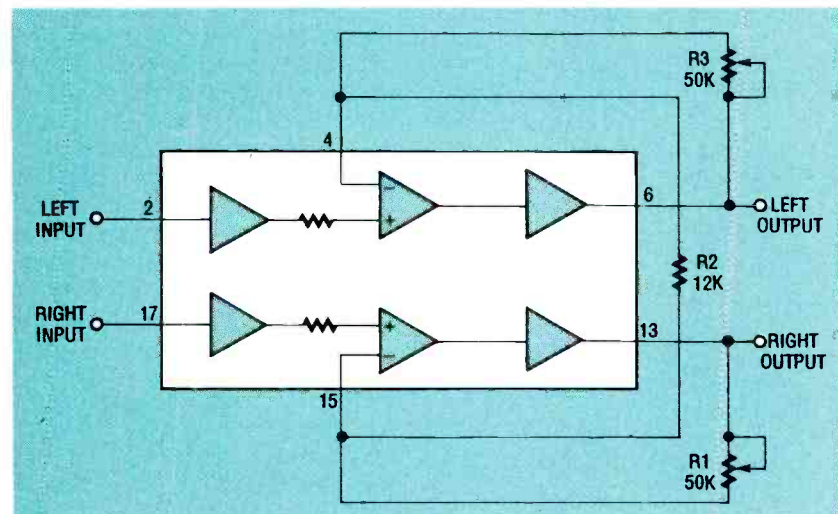


FIG. 3—IN THE SPATIAL STEREO MODE, active op-amp circuits selectively remove certain parts of the audio spectrum.

tioned in the Parts List.

Because this is an audio project, component tolerances and the matching of component values between the left and right channels is important. All re-

sistors should be within 5 percent of the listed value, and it's a good idea to check them. Be sure to use high-quality capacitors, as poor-quality capacitors can adversely effect the overall

frequency response of the circuit's processor.

Following the parts-placement diagram in Fig. 6 as a guide, install all resistors and capacitors, paying attention to the polarity of the electrolytics. Also mount diode D1, observing its polarity. Mount the 78L09 voltage regulator (IC2) with the flat side pointing toward the outside edge of the PC board. It's a good idea to use a socket for IC1, and you can install it now and then insert the IC. Observe the proper pin-1 orientation when putting the chip in its socket.

A metal enclosure will provide the best shielding from interference. However, a plastic box will probably be acceptable as well. Prepare the enclosure by laying out the front and rear panels for drilling. After drilling, deburr and clean the enclosure. The author mounted solder posts at each point on the board that must be hard-wired to another component. That made it easy to mount the board, jacks, and controls in the case, and then do the point-to-point wiring. Otherwise, all wires will have to be soldered to the board before mounting it in the enclosure. In either case, mount the completed PC board to the enclosure using appropriate hardware.

If you haven't done so yet, mount all of the potentiometers, jacks J1-J5, the LED's, and switch S1 to the enclosure. Then solder all cables and wires from the board to the jacks and controls. Following Fig. 6, pay careful attention to the places where shielded cable must be used. Hook-up wire can be used for all other connections. When connecting the feedback gain-control potentiometers (R1, R3, R7, and R13), wire them so their resistance *increases* as they are turned clockwise. Figure 7 shows the inside of the completed prototype.

### Testing

When the project is complete, check all components for proper location and polarity, and also check your soldering. Using a DC voltmeter, check for the fol-

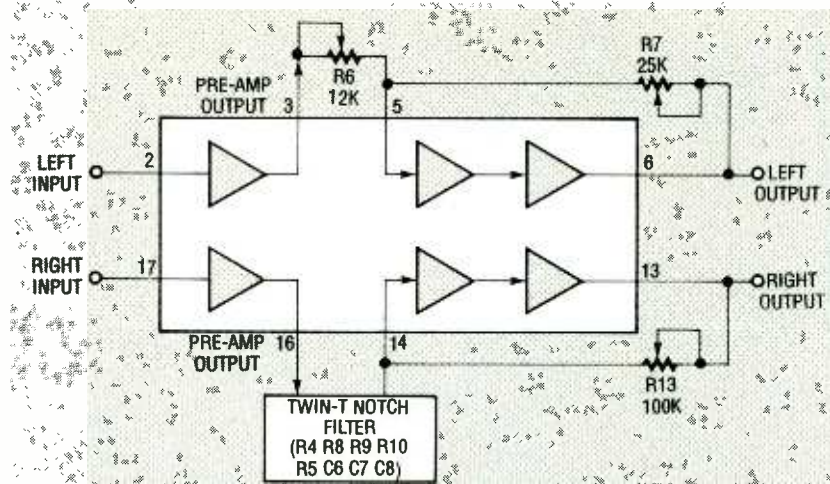


FIG. 4—IN THE MONO PSEUDO-STEREO MODE, the processor creates a “stereo” image using the various active filters in different ways on each channel.

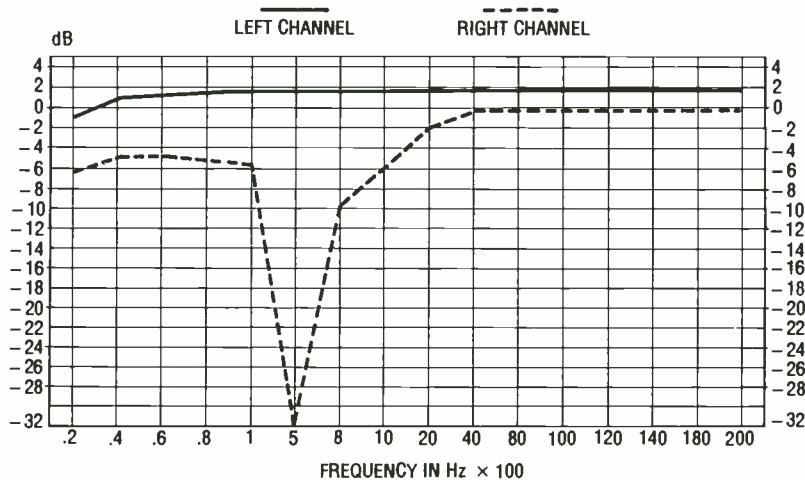


FIG. 5—FREQUENCY RESPONSE of each channel in the mono pseudo-stereo mode.

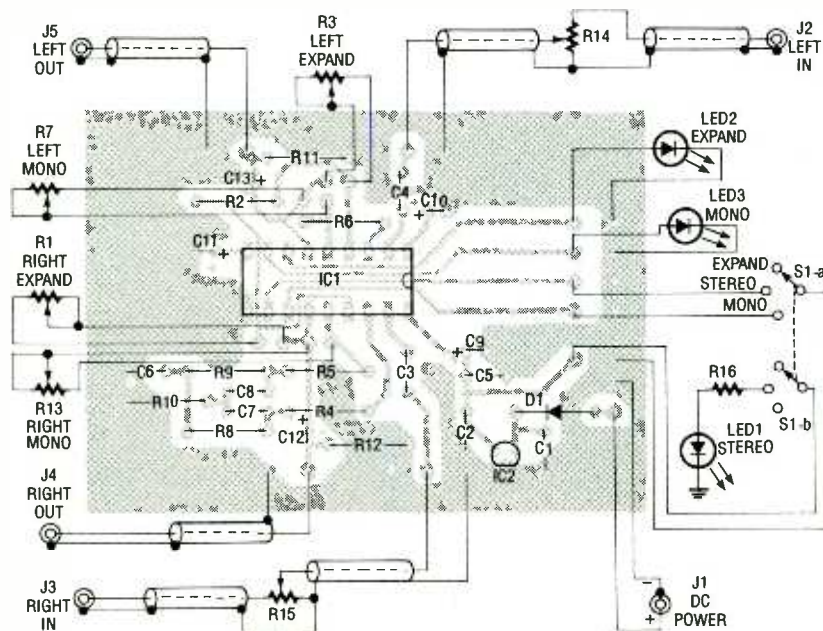


FIG. 6—PARTS-PLACEMENT DIAGRAM. Pay attention to those controls that require shielded cable for connection to the PC board.

lowing voltages after applying power to the circuit:

Power-supply output—10.5–24 VDC

IC2 output—8.55–9.45 VDC

IC1 pin 1—4.2–4.8 VDC

IC1 pin 2—4.2–4.8 VDC

IC1 pin 3—4.2–4.8 VDC

IC1 pin 4—4.2–4.8 VDC

IC1 pin 5—4.2–4.8 VDC

IC1 pin 6—4.2–4.8 VDC

IC1 pin 13—4.2–4.8 VDC

IC1 pin 14—4.2–4.8 VDC

IC1 pin 15—4.2–4.8 VDC

IC1 pin 16—4.2–4.8 VDC

IC1 pin 17—4.2–4.8 VDC

IC1 pin 18—8.55–9.45 VDC

If all of those voltages are correct, the audio processor is ready to use.

### Installation and use

If the audio processor is placed near a TV set and tends to pick up stray interference, move the processor around on the TV until the interference disappears. Also, be sure to use a well-filtered DC power pack or power supply to eliminate hum from the AC line.

Be sure all input and output cables are shielded, and well grounded to the PC board ground foil. Improper grounding can cause ground loops and other noise problems that are hard to track down. When the processor is to be installed between the TAPE IN/TAPE OUT jacks on a stereo system, hook it up the same way as if a tape deck were being installed.

Some stereo TV sets have line-level output jacks on them. In that case, all you have to do is install the audio processor unit between the TV's output jacks and the stereo's auxiliary or tuner input jacks.

If the audio processor unit will be installed between a speaker output and an amplifier input, the speaker output level must be reduced to a level that the audio processor can safely handle, which is a maximum of 2 volts rms. Always set the input-attenuator potentiometers to maximum attenuation before applying an input signal to the processor. Connect all mono audio sources to both of the inputs.

*continued on page 82*



# HARDWARE HACKER

**Nichrome and resistance wire, epoxy encapsulation myths, semiconductor suppliers III, FCC part-68 phone interface, and copy protection absurdities.**

**DON LANCASTER**

**H**istory often repeats itself, first as a tragedy and then as a farce. It sure amazes me how many hardware hackers and software types refuse to learn from the past.

For instance, over a decade ago, the Apple II community conclusively proved beyond a shadow of a doubt that *copy protection does not work*. Never did and never will.

Neither do hardware locks or similar add-ons. Yet many IBM-PC-compatible folks are hell-bent on wasting new time, dollars, and energy reproving this fundamental truth to themselves. You will find only three known effects of copy protection: (a) it annoys and inconveniences legitimate users, sending them all to unlocked competitive products; (b) it diverts time and energy that is best spent improving and updating your code; and, of course, (c) any copy protection dramatically *increases* the number of the bootleg copies of your product that get circulated.

The reason for c is simple. Copy protection *always* attracts attention to itself, causing scads of ultra-creative people to devote countless hours of time and amounts of energy toward cracking the secrets of your product.

The bottom line is this: Undoing copy protection is *fun*! Not only is the challenge fun, it is by far the fastest and most cost-effective way to learn machine-language programming. It's also one of the best and the cheapest high-quality learning experiences you will find anywhere ever—and it's a positively superb entertainment value.

For most hardware offerings, even grinding a part number off the key integrated circuit will have the exact opposite of the intended effect: All that does is cause lots of high-energy people to puzzle out

what the chip is and where to get one. The universal hacker popularity for that BA1404 stereo FM broadcaster can be directly traced to one firm stupidly grinding off one too many part numbers.

By far the most absurd notion on hardware copy protection that has been resurrected is to...

## Pot it in epoxy!

I simply can't believe the number of calls and letters I've gotten on this lately. Back in the late 1950's, it was conclusively seen that potting your circuits in epoxy offers no design security whatsoever. In fact, epoxy potting will *always* have the exact opposite effect.

First, any reasonably good design engineer could select a "black box" approach and carefully look at the inputs and outputs of the circuit. From the circuit's size and cost, and from information in trade journals, data books, distributor's catalogs, and ap notes, an engineer can easily come up with three or four methods to perform the same function—at least one of which will end up far cheaper, better, and more creative than yours.

Second, it's a simple matter to X-ray any potted project—free even, if it's a small module and you visit a reasonably curious dentist.

Third, most of the epoxy sources also supply *epoxy strippers*. These

dissolve out the potting compound, cheaply, rapidly, and conveniently so it can be quickly washed away.

Fourth, epoxy could have several disruptive effects on your circuits. It changes the heat distribution and the operating temperatures of components. It can subtly detune polystyrene capacitors and its weight shifts mechanical resonances to more destructive frequencies.

Fifth, a very little-known fact: The ferrite RF beads used on typical high-frequency analog circuits *must* be able to change in size slightly or they will not work properly. The high-frequency energy gets absorbed by magnetostriction that, in turn, converts to heat. Locking ferrite beads in epoxy can alter their response.

Used with care, there are times and places where epoxy potting is an appropriate technique. Especially for water resistance or use in hazardous environments. But epoxy potting for copy protection just does not work.

## Getting Nichrome wire

I've gotten several calls and letters recently asking for hacker sources for Nichrome wire. I'll show you some sources and alternatives in just a bit. But please note that Nichrome is a trade name for a resistive alloy from Driver Harris Co. that can be drawn into wire or sputtered on a substrate.

Most often, you'll want all of your electrical or electronic wiring to be very efficient, wasting as little energy and producing as little heat as possible. But there are other times and places when you want to cause a wire to intentionally generate heat or create a specific voltage drop.

Obvious examples include toasters, electric blankets, hot-wire plastic or foam cutters, laminating machines, space heaters, soldering irons, motor starters, thermal re-

## NEED HELP?

Phone or write your **Hardware Hacker** questions directly to:  
Don Lancaster  
**Synergetics**  
Box 809  
Thatcher, AZ 85552  
(602) 428-4073

lays, refrigerator defrosters, or for dummy transmitter loads. Some non-obvious places for carefully controlled resistance wire include current-meter shunts, and sensors that turn your printer on whenever you power your computer.

Most elements, alloys, and other materials are grouped into four types. *Conductors* can pass electricity fairly easily and have low resistances. Conductors can include both ordinary wire and resistance wire.

*Semiconductors* offer a moderately high resistance to electrical currents, with silicon and gallium arsenide being the most obvious examples. *Insulators* offer very high resistance to electrical current. Rubber, glass, plastics, and ceramics are typical insulators.

*Superconductors* can offer zero resistance to electrical currents. But most superconductors are complex formulations that work under special conditions at extremely low temperatures. You'll find more on superconductors in the *Hardware Hacker II* reprints.

MATERIAL	RESISTIVITY measured in $\mu\Omega\text{-cm}$	RESISTIVITY as compared to copper
Aluminum	2.8	1.64
Brass	7.0	4.07
Constantan	44.1	25.60
Copper	1.7	1.00
German Silver	33.0	19.18
Gold	2.4	1.42
Invar	81.0	47.00
Iron	10.0	5.81
Lead	22.0	12.79
Magnesium	4.6	2.67
Molybdenum	5.7	3.31
Music wire	11.8	6.86
Monel	42.0	24.40
Nichrome	150.0	87.20
Nickel	7.8	4.53
Platinum	10.0	5.81
Silver	1.6	0.95
Tantalum	15.5	9.01
Tin	11.5	6.69
Tungsten	5.5	3.20
Zinc	5.7	3.34

FIG. 1—THE RESISTIVITY OF ANY MATERIAL is defined as the face-to-face electrical resistance of a unit cube. Here are several resistivity values for some of the more widely used metals and alloys.

Take a one-centimeter cube of any element, alloy, or material. Next, apply a voltage from full face to the opposite full face. Then measure the current. By Ohm's Law, the ratio of the voltage to current determines the *resistance* of the cube. But we have a special name for the resistance of a unit cube. This is the *resistivity*, and is identified  $\rho$ , the Greek letter *rho*.

The resistance of a wire increases with its length and decreases in proportion to area. The metric resistivity units are ohm-centimeters (ohm-cm). I'll use a wondrously oddball unit of *microOhm-centimeters* ( $\mu\Omega\text{-cm}$ ) here so our numbers look nicer.

Resistivity values let us compare materials *independent of their actual sizes*. Some popular resistivity values are shown in Fig. 1, while Fig. 2 shows you how much resistance you can expect for various wire sizes of selected materials.

The lowest resistivity of common elements or alloys is silver, checking in at 1.6  $\mu\Omega\text{-cm}$ . But silver is fairly rare and readily tarnishes, and the

commodity price of silver changes all over the lot. So, silver isn't used too much except for RFI suppression microwave equipment, and exotic military stuff.

Copper, of course, is the universal choice for a conductor. It has a resistivity of a mere 1.7  $\mu\Omega\text{-cm}$ —only five percent worse than silver.

At first glance, aluminum appears almost as good as copper, having a conductivity only 64 percent worse. In theory, the thicker but cheaper and lighter aluminum conductors could be substituted.

But aluminum has a pair of nasty habits which include electrochemical decomposition and the building up of sapphire-hard (literally!) oxide coatings. Making a solid connection to an aluminum wire is not a trivial task. Several decades ago, a bunch of house trailers burned up after some abortive attempts at trying to perfect aluminum wiring.

Most of the other popular elements and alloys have resistivities that are moderately higher than copper. But a magic alloy of 61 per-

NEW FROM  
**DON LANCASTER**

**HARDWARE HACKER STUFF**

Hardware Hacker Reprints II or III	24.50
Midnight Engineering Reprints	18.50
Resource Bin Reprints	12.50
Incredible Secret Money Machine	18.50
CMOS Cookbook	24.50
TTL Cookbook	24.50
Active Filter Cookbook	24.50
Micro Cookbook vol I or II	19.50
Lancaster Classics Library	119.50

**POSTSCRIPT STUFF**

Ask The Guru Reprints I, II or III	24.50
PostScript Secrets (Ile/Mac/PC)	39.50
PostScript Show & Tell	39.50
Intro to PostScript VHS Video	39.50
PostScript Beginner Stuff	39.50
PostScript Cookbook (Adobe)	16.50
PostScript Ref. Manual II (Adobe)	28.50
PostScript Program Design (Adobe)	22.50
Type I Font Format (Adobe)	15.50
LaserWriter Reference (Apple)	19.50
Real World Postscript (Roth)	22.50
PostScript Visual Approach (Smith)	22.50
Thinking in PostScript (Reid)	22.50
Undet PS Pgrmmg (Holtzgang)	29.50
The Whole Works (all PostScript)	349.50

**BOOK-ON-DEMAND STUFF**

Book-on-demand resource kit	39.50
Genie PSRT sampler (Ile/Mac/PC)	39.50

FREE VOICE HELPLINE      VISA/MC

**SYNERGETICS**  
Box 809-RE  
Thatcher, AZ 85552  
(602) 428-4073



cent nickel, 24 percent iron, and 15 percent chrome provides a resistivity over fifty times higher than copper. When combined with its other useful properties, this *Nichrome* alloy makes an outstanding resistance wire.


Figure 2 shows you how much resistance to expect for various wire sizes for each of these materials. A foot of 20-gauge Nichrome wire has a resistance of 0.659 ohms. The same alloy in 30-gauge provides around 6.75 ohms total.

Resistance wire gets measured in ohms per thousand feet. Or you may prefer its equivalent of milliohms per foot. Naturally, resistance wire works just like any other resistor, obeying Ohm's law and the usual  $P = E^2/R$  power relations. A watt of electricity is, of course, a watt of heat. And a BTU of heat equals 17.58 watts. So you can easily calculate the amount of heat. BTU or *British Thermal Unit* is the amount of heat needed to raise the temperature of one pound of water by one degree Fahrenheit.

MATERIAL	10 gauge	20 gauge	30 gauge	40 gauge
Aluminum	2	17	169	1720
Brass	4	41	419	4260
Constantan	26	260	2640	26,800
Copper	1	10	103	1050
German Silver	19	194	1970	20,100
Gold	1	14	141	1480
Invar	47	477	4850	49,300
Iron	6	59	598	6080
Lead	13	130	1320	13,400
Magnesium	3	27	275	2800
Molybdenum	3	34	341	3470
Music wire	7	70	706	7180
Monel	24	247	2451	25,600
Nichrome	65	659	6750	70,240
Nickel	5	46	467	4750
Platinum	6	59	598	6080
Silver	1	10	98	991
Tantalum	9	91	928	9430
Tin	7	68	688	7002
Tungsten	3	32	330	3350
Zinc	3	33	344	3450

Values in milliohms per foot -or- Ohms per 1000 feet.

FIG. 2—SOME TYPICAL RESISTANCE VALUES for different materials and wire gauges.

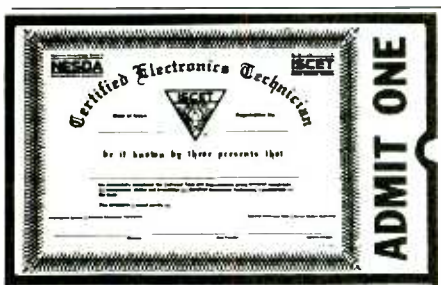

## Your Ticket To SUCCESS

Over 28,000 technicians have gained admittance worldwide as certified professionals. Let your ticket start opening doors for you.

ISCET offers Journeyman certification in Consumer Electronics, Industrial, Medical, Communications, Radar, Computer and Video. For more information, contact the International Society of Certified Electronics Technicians, 2708 West Berry Street, Fort Worth, TX 76109; (817) 921-9101.

Name \_\_\_\_\_  
 Address \_\_\_\_\_  
 City \_\_\_\_\_  
 State \_\_\_\_\_ Zip \_\_\_\_\_

Send material about ISCET and becoming certified.

Send one "Study Guide for the Associate Level CET Test." Enclosed is \$10 (inc. postage).

NO COMPLICATED ELECTRONICS, NO EXPENSIVE INSTRUMENTS:

## Home study course shows you how to make good money in VCR repair.

An amazing fact: you can do more than four out of five VCR repairs with ordinary tools and basic fix-it procedures. Our home study program shows you how.

Learn all of the systems, mechanisms, and parts of almost all brands of VCRs. With no expensive instruments. No complicated electronics. No fancy workshop. The step-by-step texts and close personal attention from your instructor make learning easy.



Texts, course materials, and tool kit are sent to your home. Graduate ready to make up to \$50.00 or more per hour in your own spare-time or full-time business.

### Send today for your free career booklet. Or call 800-223-4542

Name \_\_\_\_\_  
 Address \_\_\_\_\_  
 City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

## The School of VCR Repair

2245 Perimeter Park, Dept. VC342 Atlanta, Georgia 30341

CIRCLE 178 ON FREE INFORMATION CARD

## NAMES AND NUMBERS

### American Science & Surplus

601 Linden Place  
Evanston, IL 60202  
(708) 475-8440  
CIRCLE 316 ON FREE INFORMATION CARD

### Cermetek

1308 Borregas Avenue  
Sunnyvale, CA 94089  
(408) 752-5000  
CIRCLE 317 ON FREE INFORMATION CARD

### CircuitWerkes

6212 Southwest 8th Place  
Gainesville, FL 32607  
(904) 331-5999  
CIRCLE 318 ON FREE INFORMATION CARD

### Dallas Semiconductor

4401 Beltwood Pkwy South  
Dallas, TX 75244  
(214) 450-0400  
CIRCLE 319 ON FREE INFORMATION CARD

### Fair Radio Sales

PO Box 1105  
Lima, OH 45802  
(419) 227-6573  
CIRCLE 320 ON FREE INFORMATION CARD

### GEne

401 N Washington Street  
Rockville, MD 20850  
(800) 638-9636  
CIRCLE 321 ON FREE INFORMATION CARD

### Lor'd Industries Limited

Box 156  
Hancock, WI 54943  
(715) 249-5611  
CIRCLE 322 ON FREE INFORMATION CARD

### MWS Wire Industries

31200 Cedar Valley Drive  
Westlake Village, CA 91362  
(818) 991-8553  
CIRCLE 323 ON FREE INFORMATION CARD

### Nonlinear Nonsense

Route 1 Box 5140  
Morrisville, VT 05661  
(802) 888-5275  
CIRCLE 324 ON FREE INFORMATION CARD

### Printer's Devil

PO Box 66  
Harrison, ID 83833  
(208) 689-3738  
CIRCLE 325 ON FREE INFORMATION CARD

### Satellite Watch News

6599 Commerce Court, #103  
Gainesville, VA 22065  
(703) 347-7926  
CIRCLE 326 ON FREE INFORMATION CARD

### Scrambling News

1552 Hertel Avenue  
Buffalo, NY 14216  
(716) 874-2088  
CIRCLE 327 ON FREE INFORMATION CARD

### SRS Encoder

PO Box 30668  
Seattle, WA 98103  
(206) 362-5267 [E-mail]  
CIRCLE 328 ON FREE INFORMATION CARD

### Stanford Telecomm

2421 Mission College Blvd  
Santa Clara, CA 95054  
(408) 748-1010  
CIRCLE 329 ON FREE INFORMATION CARD

Other resistance-wire variables include the tensile strength, the temperature coefficient of resistance, and the temperature coefficient of expansion. The resistance-temperature coefficient gets important fast in such things as meter shunts. The expansion temperature coefficient becomes crucial if the wire passes through some ceramic seal. Should the wire and the ceramic expand at different rates, one or both can self destruct at high temperatures.

The fastest and simplest way to get some Nichrome wire to play with is to gently crush up a surplus power resistor in a vise and unwind the wire. Different sizes offer different lengths and gauges of wire. Resistance wire often ends up at surplus stores at bargain prices, es-

pecially at *Fair Radio Sales*. *American Science and Surplus* also offers cheap resistance wire originally intended as refrigerator defroster elements.

One big supplier of new resistance wire is *MWS Wire Industries*. Its equivalent to Nichrome is known as MWS-675. It also offer two dozen other variations. Its MWS-875 provides even higher resistivity with better temperature coefficients for both resistance and expansion. This alloy includes chrome, aluminum, and iron, with traces of carbon and silicon. It is also slightly lighter in weight.

By the way, other trade names for alloys similar to *Nichrome* are *Trophet C*, *Alloy C*, *HAI-NiCr60*, *Chromel C*, *Nikrothal 6*, and *Electroloy*.

For this month's contest, just tell me about a new or unusual hacker use for resistance wire. There'll be all of the normal *Incredible Secret Money Machine II* book prizes, along with an all-expense-paid (FOB Thatcher, AZ) *tinaja quest* for two going to the best submission of all.

As usual, send your written entries to me here at *Synergetics* and not to the **Electronics Now** editorial offices.

## A hacker interface

In several past columns, we have looked at the FCC *Part 68 Interfaces*. These are required any time you want to put voice, music, caller-ID data, or modem tones on or off of the phone line. The key component needed is just a fancy transformer with a high isolation voltage rating, a very good balance, and the ability to accept DC primary current.

There are lots of dollars, time, and effort needed to get an interface FCC type approved. And it is now illegal to make any connection to the phone line without going through an FCC approved, *Part 68* interface. At least in the U.S.

Several firms now offer "pass through" interfaces that you can include within your own circuits to get an instant and automatic type approval. The two major suppliers are now *Cermetek* and *Dallas Semiconductor*. Sadly, their pricing has been too high for most hacker uses.

A startup outfit by the name of *CircuitWerkes* is now offering a new and hacker-friendly *Part 68* interface at an acceptable price of \$29.95. And yes, it offers a full type-approval pass through. It's subject to only a few easy rules that involve component spacing, labels, documents, and modifications. Figure 3 shows you the circuit.

A small relay makes the *on-hook* and the *off-hook* state connections. To "sieze" or "answer" the line, apply 12 volts DC to the relay, providing 60 milliamperes.

The ring-detector circuit is active only when on-hook. It consists of a optoisolator that responds to the high AC ringing voltage (typically 140 volts at a frequency of 28 to 40 Hertz). The output of the ring detector is an open collector. You'll have to provide both an external pull-up



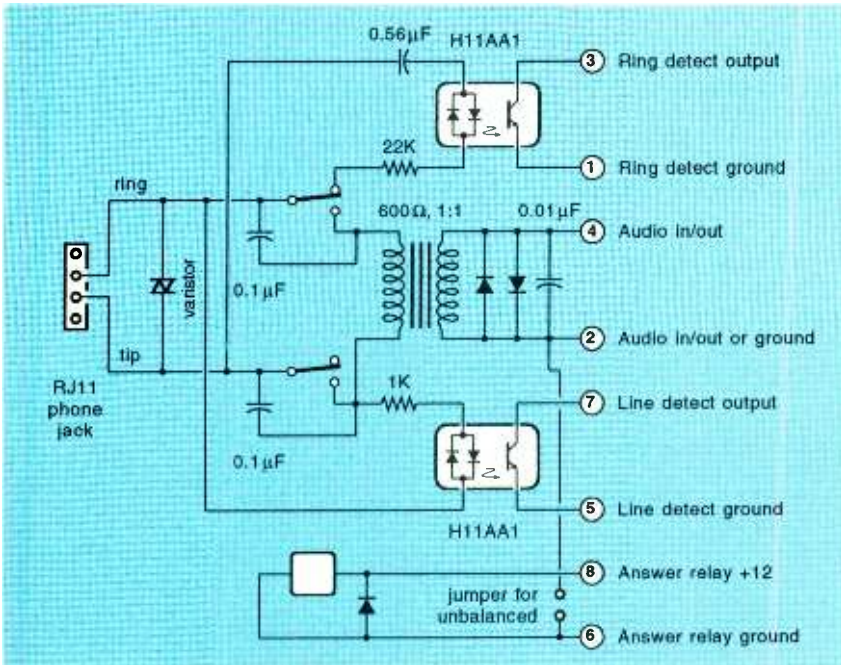


FIG. 3—THE CIRCUITWERKES MPC-2 is an FCC Part-68 telephone interface that offers a “pass through” type approval for your own hacker projects.

resistor and a filter capacitor to ground. Suitable values are 12,000 ohms and 5 microfarads.

The main data path is active both on- and off-hook. This dual feature is needed for a caller-ID compatibility. When you are on-hook, the data path is capacitor-coupled.

When off-hook, the data path is DC-coupled through the transformer primary. A second optoisolator in parallel with the primary acts as a line-current detector. The line current is detected by monitoring the DC voltage drop across the primary.

The line-current detection lets you know when your calling party hangs up. The optoisolator also offers open-collector output. A pull-up resistor is also required here.

The main data path is a special transformer with two clipping diodes that limit the maximum applied audio. A jumper option allows you to select a balanced or single-ended 600-ohm source/sink for your audio output.

Typically, your computer will first monitor the ring detector. After a ring, it seizes the line and optionally grabs the caller-ID tones. Then it will send or receive your voice or data. Finally, you can hang up by causing the relay to drop out—either by detecting the absence of line current or by hanging up on purpose.

As a second contest for this month, just tell me about a new or unusual application for a hacker-legal Part 68 interface project.

Much more information on those caller-ID applications appears in a dozen files on my *GENie* PSRT.

### More semiconductor resources

We will wrap up our continuing listing of the major semiconductor houses in a third and final sidebar.

This month, we will cover *OKI* up through *Zilog*. I've tried to zero in on those suppliers with the greatest hacker interest.

A complete list will appear in the *Hardware Hacker IV* reprints. I've also gathered them together into the ICMFGRS.PS download you'll find on *GENie* PSRT.

As we have seen before, your best bet here is to request a short-form catalog, the price list, and a literature directory. Be absolutely sure to use professionally sounding phone calls or your own custom PostScript laser letterhead. A ball-point pen on tablet paper flat out won't hack it. Much more on finding and using technical information is in my newly revised *Incredible Secret Money Machine II*.

### New tech lit

We have got some really exciting

If you thought that last piece of Test Equipment you had purchased cost too much, IT PROBABLY DID!



OS-9060D  
60MHz OSCILLOSCOPE



DM-232  
3 1/2 DGT DMM  
4 1/2 DGT FREQUENCY  
COUNTER



FG-8002  
2MHz SWEEP  
FUNCTION  
GENERATOR

Consider a sensible source.

You can choose from a variety of High Quality Analog Oscilloscopes, (20 MHz to 100MHz), Cursor Control and CRT readout Oscilloscope (20MHz & 40 MHz). Digital Multimeters (3 1/2, 3 3/4, & 4 1/2 Dgt.) reciprocating frequency counters, sweep function generators and power supplies to meet your test instrument needs.

Call, FAX, or Write today for a free catalog.

**GoldStar Precision**

13013 East 166th St., Cerritos, CA 90701  
tel: 310-404-0101 • fax: 310-921-6227

CIRCLE 181 ON FREE INFORMATION CARD

## SEMICONDUCTOR RESOURCES, PART III

### **OKI Semiconductor**

785 N. Mary Avenue  
Sunnyvale, CA 94086  
(800) 832-6654

**CIRCLE 330 ON FREE INFORMATION CARD**

### **SGS-Thomson**

1000 East Bell Road  
Phoenix, AZ 85022  
(602) 867-6100

**CIRCLE 340 ON FREE INFORMATION CARD**

### **Tektronix**

P.O. Box 500  
Beaverton, OR 97077  
(800) 835-9433

**CIRCLE 350 ON FREE INFORMATION CARD**

### **Panasonic**

1 Panasonic Way  
Secaucus, NJ 07094  
(201) 348-7000

**CIRCLE 331 ON FREE INFORMATION CARD**

### **Sharp Electronics**

10 Sharp Plaza  
Mahwah, NJ 07430  
(201) 529-8757

**CIRCLE 341 ON FREE INFORMATION CARD**

### **Teledyne Components**

1300 Terra Bella Avenue  
Mountain View, CA 94043  
(415) 968-9241

**CIRCLE 351 ON FREE INFORMATION CARD**

### **Plessey Semiconductor**

P.O. Box 660017  
Scotts Valley, CA 95067  
(408) 438-2900

**CIRCLE 332 ON FREE INFORMATION CARD**

### **Siemens Components**

2191 Laurelwood Road  
Santa Clara, CA 95054  
(408) 980-4568

**CIRCLE 342 ON FREE INFORMATION CARD**

### **Teltone**

22121 20th Avenue SE  
Bothel, WA 98021  
(800) 426-3926

**CIRCLE 352 ON FREE INFORMATION CARD**

### **Raytheon Semiconductor**

350 Ellis Street  
Mountain View, CA 94039  
(415) 968-9211

**CIRCLE 333 ON FREE INFORMATION CARD**

### **Sierra Semiconductor**

2075 N. Capitol Avenue  
San Jose, CA 95132  
(408) 263-9300

**CIRCLE 343 ON FREE INFORMATION CARD**

### **Teccor Electronics**

1801 Hurd Drive  
Irving, TX 75038  
(214) 580-1515

**CIRCLE 353 ON FREE INFORMATION CARD**

### **Rockwell International**

4311 Jamboree Road, Box C  
Newport Beach, CA 92658  
(714) 833-4600

**CIRCLE 334 ON FREE INFORMATION CARD**

### **Signetics**

811 East Arques Avenue  
Sunnyvale, CA 94088  
(800) 227-1817

**CIRCLE 344 ON FREE INFORMATION CARD**

### **Texas Instruments**

P.O. Box 401560  
Dallas, TX 75240  
(800) 336-5236

**CIRCLE 354 ON FREE INFORMATION CARD**

### **ROHM Corporation**

3034 Owen Drive  
Antioch, TN 37013  
(615) 641-2020

**CIRCLE 335 ON FREE INFORMATION CARD**

### **Silicon General**

11861 Western Avenue  
Garden Grove, CA 92641  
(714) 898-8121

**CIRCLE 345 ON FREE INFORMATION CARD**

### **Toshiba America**

9775 Toledo Way  
Irvine, CA 92718  
(714) 455-2000

**CIRCLE 355 ON FREE INFORMATION CARD**

### **Samsung Semiconductor**

3725 North First Street  
San Jose, CA 95134  
(408) 435-5400

**CIRCLE 336 ON FREE INFORMATION CARD**

### **Siliconix**

2201 Laurelwood Road  
Santa Clara, CA 95054  
(800) 554-5565 **CIRCLE 346 ON FREE INFORMATION CARD**

### **Unitrode Integrated Circuits**

7 Continental Blvd.  
Merrimack, NH 03054  
(603) 424-2410

**CIRCLE 356 ON FREE INFORMATION CARD**

### **Sanyo**

80 Commerce Drive  
Allendale, NJ 07401  
(201) 825-8080 **CIRCLE 337 ON FREE INFORMATION CARD**

### **Sony Corporation**

10833 Valley View Street  
Cypress, CA 90630  
(714) 220-9100  
**CIRCLE 347 ON FREE INFORMATION CARD**

### **Western Design Center**

2166 East Brown Road  
Mesa, AZ 85213  
(602) 962-4545  
**CIRCLE 357 ON FREE INFORMATION CARD**

### **SEEQ Technology**

47131 Bayside Pkwy.  
Fremont, CA 94537  
(510) 226-7400  
**CIRCLE 338 ON FREE INFORMATION CARD**

### **Standard Microsystems**

80 Arkay Drive  
Hauppauge, NY 11787  
(516) 273-3100  
**CIRCLE 348 ON FREE INFORMATION CARD**

### **Xicor**

1511 Buckeye Drive  
Milpitas, CA 95035  
(408) 432-8888  
**CIRCLE 358 ON FREE INFORMATION CARD**

### **Seiko Instruments**

2990 West Lomita Blvd.  
Torrance, CA 90505  
(310) 517-7770  
**CIRCLE 339 ON FREE INFORMATION CARD**

### **Stanford Telecommunications**

2421 Mission College Blvd.  
Santa Clara, CA 95056  
(408) 748-1010  
**CIRCLE 349 ON FREE INFORMATION CARD**

### **Zilog**

210 Hacienda Avenue  
Campbell, CA 95008  
(408) 370-8000  
**CIRCLE 359 ON FREE INFORMATION CARD**



new publications for this month. The first is Dick Oliver's new *Nonlinear Nonsense*, a free quarterly newsletter on fractal modeling, chaos science, artificial life, and creative graphics. His 3-D fractal design software is also being offered commercially.

Also free on professional request is the new *Spread Spectrum Handbook* from *Stanford Telecomm*. This is a dozen pages of ap-notes and useful references, along with bunches of data sheets for the company's high-end digital spread-spectrum chips.

The *Scrambling News* has detailed insider information on the current TV video scrambling and descrambling methods. It also offers books full of schematics, modifications, and related technical information. A competing newsletter is the *Satellite Watch News*.

The *SRS Encoder* is a new monthly newsletter from the *Seattle Robotics Society*. Lots of regional information on great surplus buys are included here.

Joe Singer's *Printer's Devil* is a

superb alternative publication on home printing and presswork. "A press in every home; a home in every press." It is published quarterly at a bargain \$10 per year subscription price.

Finally, the *New Age Alternatives Discount Catalog* is another resource for pseudoscience devices and information. Fascinating reading for sure. This one is offered by *Lor'd Industries*.

A reminder here: I have reprints available for most of my columns. Both in *Book-on-demand* published hard copy and on-line at *GENie PSRT*. The titles now include my *Ask the Guru*, *Hardware Hacker*, the *Blatant Opportunist*, *LaserWriter Secrets*, and the new *Resource Bin*. Check my nearby *Synergetics* ad for more details.

As usual, I have gathered most of the mentioned resources together into our *Names and Numbers* and *Semiconductor Manufacturer's Ill* sidebars. Also, as usual, you can get technical help, consultant referrals, and lots of off-the-wall networking by calling my helpline. Ω

# Be an FCC LICENSED ELECTRONIC TECHNICIAN!



No costly school. No commuting to class. The Original Home-Study course prepares you for the "FCC Commercial Radiotelephone License." This valuable license is your professional "ticket" to thousands of exciting jobs in Communications, Radio-TV, Microwave, Maritime, Radar, Avionics and more... even start your own business! You don't need a college degree to qualify, but you do need an FCC License.

**No Need to Quit Your Job or Go To School** This proven course is easy, fast and low cost! **GUARANTEED PASS**—You get your FCC License or money refunded. **Send for FREE facts now. MAIL COUPON TODAY!**

## COMMAND PRODUCTIONS

FCC LICENSE TRAINING, Dept. 90  
P.O. Box 2824, San Francisco, CA 94126  
Please rush FREE details immediately!

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

Exciting Features, Projects, Reviews  
& Columns And Much More!

In the Next Issue of

# Popular Electronics®

ON SALE

FEBRUARY 18, 1993

WATCH FOR IT!

Pick up *Popular Electronics* at your favorite  
Newsstand Bookstore or Supermarket

## The World is Talking!



**Shortwave Listening Guidebook**  
by Harry Helms

Here's your guide to getting the most from a shortwave radio! In clear, nontechnical language, Harry explains how, when, and where to listen in. Its 320 heavily-illustrated pages are packed with advice on:

- antennas
- selecting the right radio
- accessories
- reception techniques

Learn how to hear the BBC, Radio Moscow, ham operators, ships, even spies and "pirate" radio stations! Includes hundreds of station frequencies and the times you can hear them.

Only \$16.95 at radio equipment dealers, or order direct from HighText! Add \$3 shipping (\$4 Canada, \$5 elsewhere). CA add sales tax. U.S. funds only please.

**HighText**  
publications inc.

7128 Miramar Road, Suite 15L  
San Diego, CA 92121

## SUPER 12 HOUR RECORDER

CALL TOLL FREE

Modified Panasonic Slimline,  
6 hrs per side  
120 TDK tape furnished.  
AC/DC Operation.  
Quality Playback.  
Digital Counter.  
Durable Lightweight Plastic.



\$119.00\*

## PHONE RECORDING ADAPTER

Starts & Stops Recorder  
Automatically When  
Hand Set is Used.  
Solid State!



FCC Approved

\$28.50\*

## VOX VOICE ACTIVATED CONTROL

Solidstate Adjustable  
Sensitivity. Voices &  
Sounds Activate Recorder  
Adjustable Sensitivity  
Provisions for Remote  
Mike



\$28.50\*


\* Add for ship. & handling. Phone Adapter & Vox \$2.00 each, Recorders \$5.00 each. Colo. Res add tax. Mail Order, VISA, M/C, COD's OK. Money Back Guar. Qty Disc. available. Dealer inquiries invited. Free data on other products.

AMC SALES INC. 193 Vaquero Dr.  
Boulder, CO. 80303  
Phones (303) 499-5405 1-800-926-2488  
FAX (303) 494-4924  
Mon-Fri 8-5 MTN. TIME

CIRCLE 108 ON FREE INFORMATION CARD
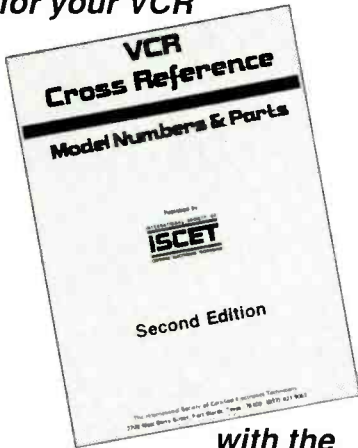
# VCR Cross Reference

**NOW Find the right Part  
for your VCR**



**with the  
ISCET VCR**

## CROSS REFERENCE

This 272-page reference contains both model and part-number cross-references and now includes the FREE 56-page 1991 updates.

VCR's are made in a few factories from which hundreds of different brand names and model numbers identify cosmetically-changed identical and near-identical manufactured units. Interchangeable parts are very common. An exact replacement part may be available only a few minutes away from you even though the manufacturer supplier is out-of-stock. You may be able to cannibalize scrap units at no cost!

The ISCET VCR Cross Reference and 1991 Update pages are pre-punched for standard loose-leaf binding...\$38.00 plus \$3.00 for shipping for each reference.

Electronics Technology Today Inc.  
VCR CROSS REFERENCE OFFER  
P.O. Box 240,  
Farmingdale, New York 11735

Name \_\_\_\_\_

Business \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

Phone \_\_\_\_\_

Enclose \$38.00 for the ISCET VCR Cross Reference and 1991 Update Reference and \$3.00 for shipping for each reference.

I have ordered \_\_\_\_\_ ISCET VCR Cross Reference(s).

The total amount of my order is \$ \_\_\_\_\_

Check enclosed—do not send cash.

or please charge my credit card:

Visa  MasterCard Exp. Date \_\_\_\_\_/\_\_\_\_\_/\_\_\_\_\_

Card No. \_\_\_\_\_

Signature \_\_\_\_\_

New York State residents must add applicable local sales tax to total.

## AUDIO EXPANDER

*continued from page 74*

In the stereo mode, the only adjustments are the input-attenuator controls (R14 for the left and R15 for the right). For a line-level input, set them for 0 attenuation. Other higher-level sources should be adjusted as desired by the user (without exceeding the 2-volt rms maximum input limit).

In the spatial stereo mode, the

input attenuator controls should be adjusted the same way as in the stereo mode. The spatial controls (R3 for the left and R1 for the right) can then produce very interesting spatial effects. Also, adjusting the input-attenuator controls produces interesting effects due to the cross-channel coupling provided by resistor R2. Experiment with those four controls to determine their optimum settings.

In the mono pseudo-stereo mode, the input-attenuator


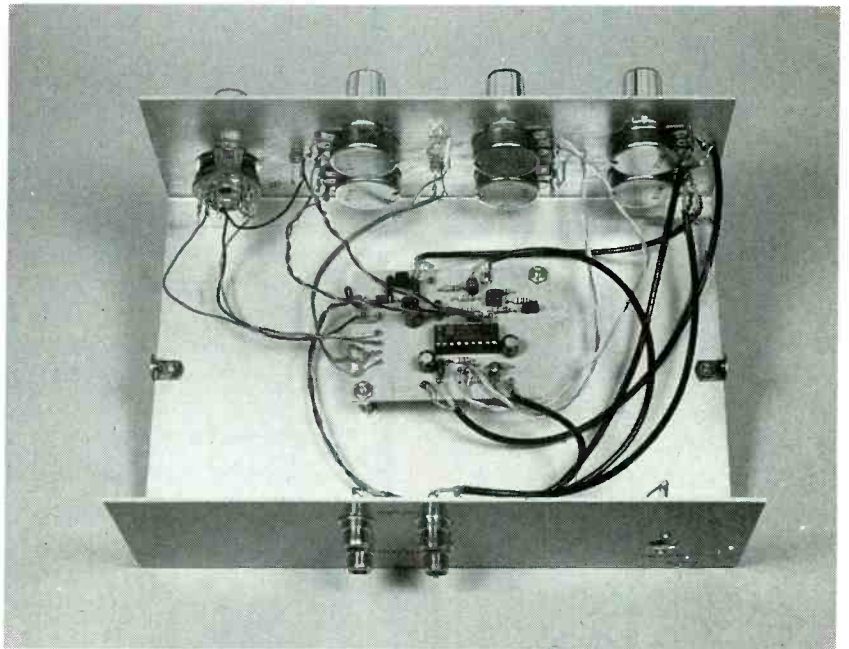


FIG. 7—A METAL ENCLOSURE provides the best shielding from interference. Here's the inside of the completed prototype.

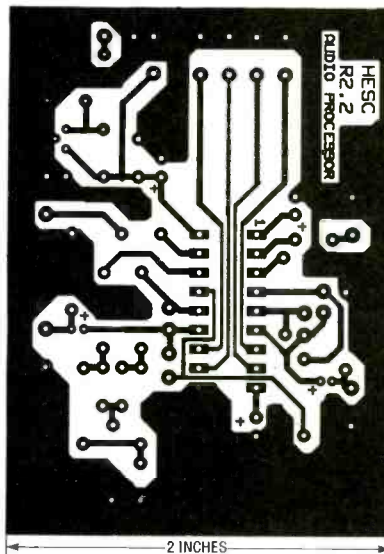

FOIL PATTERN for the audio processor.

controls should be adjusted the same way as in the stereo mode. The pseudo stereo controls (R7 for the left and R13 for the right) should be set as follows: R7 should be set to give a +2.0 dB higher output level versus the right output channel control (R13). For example, set R7 for an output of +2.0 dB, and set R13 for an output of 0 dB. The specific levels are not critical; just keep a 2.0 dB differential between the left and right output channels.

When using a mono input source, the spatial stereo mode will produce some very interesting and useful effects. The input attenuator controls will also have interesting effects.  $\Omega$





# REMOTE CONTROL TESTER

BY A.E. PLAVCAN

INFRARED REMOTE CONTROLS ARE very common these days, thanks to all the video, audio, and VCR equipment on the market that can be controlled with an infrared remote. Remote controls are great when they work properly. However, it's very frustrating when you press a button on the remote control and nothing happens. If you've ever had that problem, then you know what we mean when we say it's frustrating.

It's always hard to know

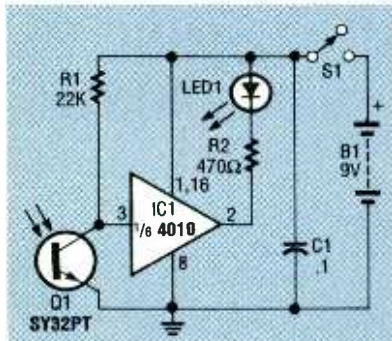


FIG. 1—THE IR TESTER circuit lets you know if the button you press on a remote control is working.

## PARTS LIST

- R1—22,000 ohms, 1/4-watt, 5%
  - R2—470 ohms, 1/4-watt, 5%
  - C1—0.1  $\mu$ F, ceramic
  - IC1—4010 CMOS hex non-inverting buffer
  - LED—light-emitting diode, any color
  - Q1—SY32PT IR phototransistor or equivalent
  - B1—9-volt battery
- Project case, PC board or perforated construction board, battery clip, wire, solder, etc.


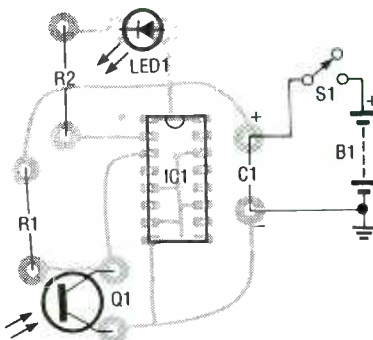


FIG. 2—PARTS-PLACEMENT diagram for the IR tester. Point-to-point wiring can also be used.

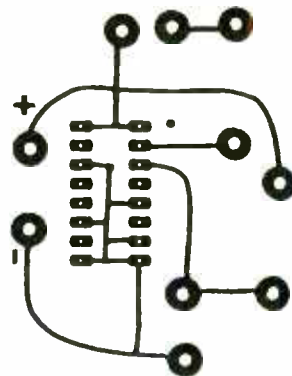

FOIL PATTERN for the IR tester circuit.

whether a malfunction is due to the remote control or the device you are trying to control. After all, infrared (IR) is invisible to the human eye, so how do you know if the control is working?

The answer is simple: Build our IR remote-control tester. It will let you know if, when you press the button, the control is emitting an IR signal.

The IR tester circuit is shown in Fig. 1. IR phototransistor Q1 receives the signal from a re-

## DIGITAL VIDEO STABILIZER ELIMINATES ALL VIDEO COPYGUARDS



While watching rental movies, you will notice annoying periodic color darkening, color shift, unwanted lines, flashing or jagged edges. This is caused by the copy protection jamming signals embedded in the video tape, such as Macrovision copy protection. THE DIGITAL VIDEO STABILIZER: RXII COMPLETELY ELIMINATES ALL COPY PROTECTIONS AND JAMMING SIGNALS AND BRINGS YOU CRYSTAL CLEAR PICTURES.

### WARNING

THE DIGITAL VIDEO STABILIZER IS INTENDED FOR PRIVATE HOME USE ONLY. IT IS NOT INTENDED TO COPY RENTAL MOVIES OR COPYRIGHTED VIDEO TAPES THAT MAY CONSTITUTE COPYRIGHT INFRINGEMENT.

### FEATURES

- Easy to use and a snap to install
- State-of-the-art Microchip technology
- 100% automatic
- Compatible to all types of VCRs and TVs
- The best and most exciting Video Stabilizer in the market
- Light weight (8 ounces) and compact (1x3.5x5")
- Uses a standard 9 Volt battery (last 1-2 years)
- Fast UPS delivery
- Air shipping available
- UNCONDITIONAL 30 day money back guarantee
- 1 year warranty

(Dealers Welcome)  
**FREE 20P Catalog**

To Order: \$39.95 ea +\$4 for p & h  
Visa, M/C, COD Mon-Fri: 9-6 EST

**1-800-445-9285**

ZENTEK CORP. DEPT. CRE0393

3670-12 WEST OCEANSIDE RD. OCEANSIDE, NY 11572

CIRCLE 186 ON FREE INFORMATION CARD

## CABLE TV DESCRAMBLERS How You Can Save Money on Cable Rental Fees Bullet Proof



1 Unit 5+

BEST Super Tri-Bi Auto/  
Var. Gain Adjustment \$119.95...\$85  
Jerrold Super Tri-Bi ... \$109.95...\$79  
Scientific Atlanta ..... \$109.....\$79  
Pioneer ..... \$109.....\$79  
Panasonic TZPC145..... \$99.95...\$79  
Stargate Converter..... \$95.....\$69  
Digital Video Stabilizer. \$59.95...\$29  
Wireless Video Sender...\$59.95...\$49.95

US Cable'll Beat  
Anyone's Price  
Advertised in  
this Magazine!

### 30 Day Money Back Guarantee

FREE 20 page Catalog

Visa, M/C, COD or send money order to:

**U.S. Cable TV Inc.** Dept. KRE0393

4100 N. Powerline Rd., Bldg. F-4

Pompano Beach, FL 33073

**1-800-772-6244**

For Our Record

I, the undersigned, do hereby declare under penalty of perjury that all products purchased, now and in the future, will only be used on Cable TV systems with proper authorization from local officials or cable company officials in accordance with all applicable federal and state laws. FEDERAL AND VARIOUS STATE LAWS PROVIDE FOR SUBSTANTIAL CRIMINAL AND CIVIL PENALTIES FOR UNAUTHORIZED USE.

Date: \_\_\_\_\_

Signed: \_\_\_\_\_

No Florida Sales!


CIRCLE 187 ON FREE INFORMATION CARD




**GET YOUR RECHARGE CATALOG FREE...EARN BIG \$\$ IN YOUR SPARE TIME**—All supplies and Do-It-Yourself kits with complete instructions available. Supplies cost from \$9.95 in qty and you can sell recharged toner cartridges for \$40.00 to \$55.00 each. Printers include HP LaserJet and Series II, Apple LaserWriter, QMS, etc. Canon PC-25 Copier also. **CHENESKO PRODUCTS, 2221 Fifth Ave., Suite #4, Ronkonkoma, NY 11779, 516-467-3205. FAX 516-467-3223, 1-800-221-3516**  
CIRCLE 110 ON FREE INFORMATION CARD



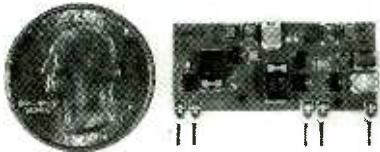**CABLE TV 50dB NOTCH FILTERS** for interference removal or channel censoring. Filters are user-adjustable to desired channel # or frequency. Eight Models available, each for certain channels: 2 & 3; 4 to 6; 7 to 13; 14 to 17; 18 to 22; 23 to 29; 30 to 36; 95 to 99 plus 0 & 1. Just \$30 each or 3 for \$75, includes shipping. ONE MONTH MONEY BACK, fast delivery. Visa, MC, check or M.O. (C.O.D. is \$5 extra) Huge discounts for higher quantities. **STAR CIRCUITS, P.O. Box 94917, Las Vegas, NV 89193. Call 24 hours 1-800-535-7827.**



**TWO TRANSMITTERS IN ONE! 5 MINUTE ASSEMBLY! MONEYBACK GUARANTEE!** New Law Enforcement grade device on a single chip is the most sensitive, powerful, stable room transmitter you can buy. Uses any 3V-12V battery. Or attach to telephone line to monitor all telephone conversations over 1 mile away without batteries! 100mW output! 80-130MHZ. Receive on any FM radio or wideband scanner. VT-75 microtransmitter. \$49.95 + 1.50 S&H. VISA, MC, MO. COD's add \$4.00. **DECO INDUSTRIES, Box 607, Bedford Hills, NY 10507. 914-232-3878.**  
CIRCLE 127 ON FREE INFORMATION CARD

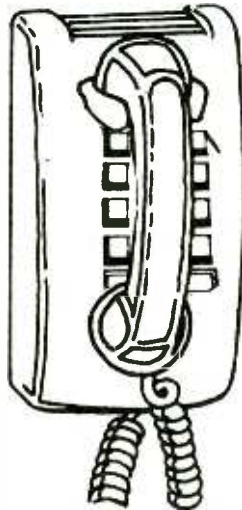

## CALL NOW AND RESERVE YOUR SPACE

- 6 x rate \$940.00 per each insertion.
- Fast reader service cycle.
- Short lead time for the placement of ads.
- We typeset and layout the ad at no additional charge.

**Call 516-293-3000** to reserve space. Ask for Arline Fishman. Limited number of pages available. Mail materials to: mini-ADS, ELECTRONICS NOW, 500-B Bi-County Blvd., Farmingdale, NY 11735.

**FAX: 516-293-3115**

mote control and sends it to one gate of a CMOS 4014 non-inverting hex buffer. The output from the buffer drives an LED that flashes the received signal to let you know that the remote control (or at least the one button you pressed) is working and emitting an IR signal.

We've provided a foil pattern to make a PC board for this project, but the circuit can easily be made using point-to-point wiring. Figure 2 shows the parts-placement for the PC board, should you decide to use it. The completed circuit can be installed in any suitable case. Mount the IR phototransistor where it can easily receive the IR signal, and mount the LED where it's easy to see. A 9-volt battery powers the circuit, but you can certainly build an AC-powered supply if you wish.

Once constructed, the tester will determine if your remote control is causing the problem. Simply point the remote control at the IR phototransistor, and press each button. The LED will flash for proper operation. Ω

## COMING NEXT MONTH

The April 1993 issue goes on sale March 4, 1993

### BUILD THE ACOUSTIC FIELD GENERATOR II

This device brings surround sound to your car!

### BUILD SMART GAGES FOR YOUR CAR

Your dashboard will be the envy of any electronics-minded person!

### BUILD A POST CARD

Power-On Self Test card for your PC is an ideal troubleshooting tool

### JFET's

A look at JFET devices and their applications

**AND LOTS MORE!**



## The Audio Answerman: Part 1

LARRY KLEIN

**H**ere is another collection of helpful (or at least interesting) audio questions and answers from reader mail and my files.

### Audio education

*I've been intensely interested in music recording and audio technology ever since my early teens. At this point, I'm seriously considering entry into the audio field in a professional capacity. Where can I get information about my options and the educational requirements?*

T.M.

Norwalk, CT

You're in luck. A definitive *Directory of Educational Programs* has been published by the Education Committee of the Audio Engineering Society (AES) that covers courses ranging from seminars to four-year graduate programs that grant degrees. Institutions, facilities, courses, degrees, and tuition are listed in a convenient format.

As a bonus, there are helpful articles that discuss the variety of job opportunities within the field and ways to approach the education process. The postpaid cost of the directory is \$5 for AES members, \$6 for nonmembers. Delivery is 4 to 6 weeks. Send your check to Audio Engineering Society, 60 E. 42nd St., Room 2520-RE, New York, NY 10165. While you are writing, you might also ask for an AES membership application.

### Flat sound

*Recently I told a friend that I built my own speakers from scratch. To my annoyance, he immediately asked, "How flat are they?" Are we getting so wrapped up in specifications that we forget the basic goal—good sound the way we like to hear it? I spent over 50 hours reworking my ported speakers so I could have a lot of bass—the way I like it. Don't*

*get me wrong; specs and test reports are definitely helpful, but keep in mind that I'm spending money to have sound the way I want to hear it—not as some expert says it should be heard.*

P.W.

Rochester, NY

If P.W. had written about choosing the paint color for his living room walls or selecting a blend of coffee—or a wife—I would not argue with the subjectivity of his approach, although my own tastes would probably differ. Everyone has a right to his own tastes—however absurd they might be. I assume you are using "good" in the sense that it satisfies you. However, when the goal is to reproduce a recorded sound, then the system that's doing it must not add any special sound characteristics of its own. If P.W. prefers speakers that readjust the original tonal balance of the program material in a given direction, that's his privilege. But I must point out that his speakers, by definition, are then not providing high-fidelity reproduction. Theoretically, fidelity to some original is what hi-fi is all about.

### Planned obsolescence

*I use my audio equipment at least four hours a day, and next year my receiver will be 10 years old. How does wear affect audio equipment, and how long will it be before planned obsolescence sets in?*

H.S.

Elliston, VA

Congratulations to your receiver on its 10th birthday! Before I answer your question on wear, I'd like to discuss "planned obsolescence," a term that seems to be fading from popular use. Actually, the alleged practice that the term describes never did make much sense; what most people really meant by it was

planned deterioration. In other words, certain parts or components in a device supposedly were designed to have both a short life and a high replacement cost, thereby encouraging the purchase of a new replacement. But it seems to me that the ill will engendered by premature breakdown would cause consumers to avoid the faulty brand when considering a replacement—thus defeating the purpose of the alleged planned obsolescence.

The loudest complaints of planned obsolescence usually occur when a new audio format threatens to render obsolete someone's treasured collection of program material. For example, the industry switched from 78 rpm's to LP's, LP's to cassettes, and then cassettes to CD's. The obsolescence in those cases was, truthfully, planned to obtain higher fidelity—or in the case of cassettes, greater convenience—for the music collector and listener.

The general public (unlike some of the audio magazines and syndicated columnists) does not automatically extend a warm welcome to every new trend in audio. Witness, for example, the marketplace fiascoes of such components as the "elcassette" and, lately, DAT. I suspect that there are other fiascoes of the digital variety now waiting in the wings.

In regard to your question about wear, solid-state devices, unlike high-power vacuum tubes, do not have an inherently short life. This is not to say that transistors never fail, but rather that their predicted life span extends far beyond that of tubes. Because of minute manufacturing flaws, small-signal transistors (and integrated circuits) can develop leakage over time, and power devices ultimately can flex themselves to death from repeated heat-


ing and cooling cycles during normal use. Other components, such as electrolytic capacitors, fail over time for a variety of mechanical and electrochemical reasons.

### Whizzers

*I'm curious about the speakers installed in the lower front-door panels of my car. I removed the grille from one of the speakers and found it to have a single gray 6-inch cone with a separate small white cone cemented to its center. Does the smaller cone serve as a tweeter?*  
D.C.

Lancaster, PA

Sort of, but not really. What you've described is known as a "whizzer," and its purpose is to enhance the high-frequency sound from your speakers. A whizzer is a small, light, and stiff subsidiary cone with an unsupported outer edge that is cemented to the center of the main cone. The area of attachment is directly over the driver's voice coil. The whizzer picks up the higher frequency vibrations from the voice coil, and helps to send them out into the world as sound.

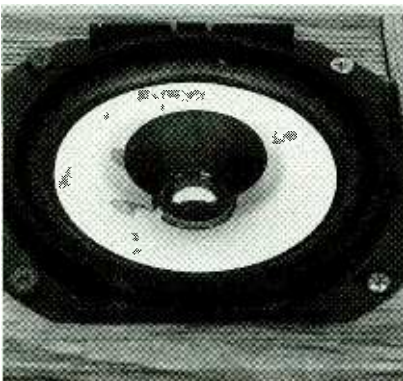

**HERE IS A WHIZZER CONE attached to a low-cost speaker.**

If carefully designed, a whizzer can provide improved highs from larger, full-range drivers. Obviously, the manufacturing cost of adding a whizzer to a driver is very low compared with the cost of a separate tweeter with its crossover and mounting complications. On the other hand, a separate or coaxially mounted tweeter is able to put out significantly more high-frequency energy—which you could probably use considering the calf-high mounting location of your speakers.

### X-ray problems

*Despite the printed reassurances posted at the passenger inspection areas of airports, I've always tried to keep my films and tapes from being X-ray inspected. I recently heard that color TV sets can also produce X-ray radiation. How far away from my TV should I keep my audio and video tapes to be safe, or will it not make a difference?*

M.O.

Burlington, VT

As far as I can determine, X-rays at the levels used in baggage examination have no effect on tapes or the signals recorded on them. It's true that the stray magnetic fields produced by X-ray equipment and color TV cathode ray tubes might affect a recorded signal, but one expert told me that the tapes would have to be stored inside the operating equipment in close proximity to a transformer or deflection coil before an erasure is likely to occur. However, metal detectors, also used in airports, can be hazardous to the health of your recorded tapes.

### Parameters

*"Parameter" seems to have become a new catchword among those involved with politics and/or the Pentagon. Is "parametric" derived from the same word, and exactly what does it have to do with equalizer design?*

J.H.

Chevy Chase, MD

My copy of Webster's dictionary defines parameter as "A (mathematical) quantity or constant whose value varies with the circumstances of its application, as the radius line of a group of concentric circles, which varies with the circle under consideration." The adjectival form is "parametric." In other words, a parametric equalizer does not limit you to the specific built-in fixed operating frequencies and bandwidths of a conventional graphic equalizer. Instead, you can assign "arbitrary values" as the equalization needs arise. This can be very handy, for example, when the frequency of the peak that you want to reduce doesn't line up very well with one of the sliders on a standard 1/3-octave graphic equalizer.  $\Omega$

### Q&A

*continued from page 12*

graphics image. The second, less expensive alternative is to print at 150-dpi resolution—half the number of dots means half the memory requirements. If you can live with the lower resolution, the latter is a cheap, quick fix for the problem.

There's one more possible answer to your problem but I doubt that it's applicable. It may be that you have enough memory in the printer to do 300-dpi, but you're using the memory to hold downloaded fonts and other things. Remember that memory used for fonts isn't available for graphics. Check your software (and not just the graphics stuff) to see whether this is true or not. If it is, unloading the fonts may free up enough printer memory to permit you to print graphics at the maximum 300-dpi resolution.  $\Omega$

Try the

**Electronics  
NOW<sup>®</sup>**

bulletin board  
system

(RE-BBS)  
516-293-2283

The more you use it the more  
useful it becomes.

We support 1200 and 2400 baud  
operation.

Parameters: 8N1 (8 data bits, no  
parity, 1 stop bit) or 7E1 (7 data  
bits, even parity, 1 stop bit).

Add yourself to our user files to  
increase your access.

Communicate with other R-E  
readers.

Leave your comments on R-E with  
the SYSOP.

RE-BBS  
516-293-2283



# DRAWING BOARD

Our descrambler is almost finished.

ROBERT GROSSBLATT

**B**elieve it or not, there's not a lot more to the design of the basic descrambling circuit than the subject matter we've covered over the past few months. But if you're really interested in video, there's much more for you to learn—the video-scrambling stuff we've been going through is just one small part of the subject. Video is a complex business, and once you get the hang of how signals can be manipulated, you'll find that there's no end to the kind of circuitry you can design. There's also a huge market for it as well. But back to the subject at hand.

When we first started work on the SSAVI descrambler, the block diagram probably looked quite complex. But if you look at Fig. 1, you'll see that most of the work has been done. The most difficult job left for us is to come up with the counter that's needed by the phase-locked loop. It's a job we have to do carefully because the success of the descrambler depends on how well we can maintain the stability of the horizontal-sync signal.

The phase-locked loop in our design is driven by a 504-kHz clock based on an R-C network. That frequency was chosen for two basic reasons: The first is that it's exactly 32 times the NTSC line frequency of 15,750 Hz, and that makes it easy for us to do the division necessary to produce horizontal sync pulses. The second, and somewhat more subtle reason, has to do with the period rather than the frequency.


A 504-kHz clock has a period of 1.98 microseconds. That's interesting because, by using five of the counts, we can get a pulse that has a width of 9.92 microseconds, which is close enough to the NTSC's established standard of 10.7 microseconds for a horizontal

blanking pulse.

Before we go any further, I have to comment on my apparent disregard for precision. I've been using language and design techniques that are loaded with phrases like "close to," "pretty much the same as," "in the ballpark," and so on. Now, I'm as impressed with standards as anyone I know, but numbers have to work in the real world as well as on

amazed at how sloppy the signal really is. The average horizontal frequency might be 15,750 hertz, but there's considerable jitter from line to line in the signal. The same is true for burst, blanking, and all the other components in the line.

Despite these variations in the signal, the picture that shows up on your TV screen is apparently unaffected by them. The difference be-

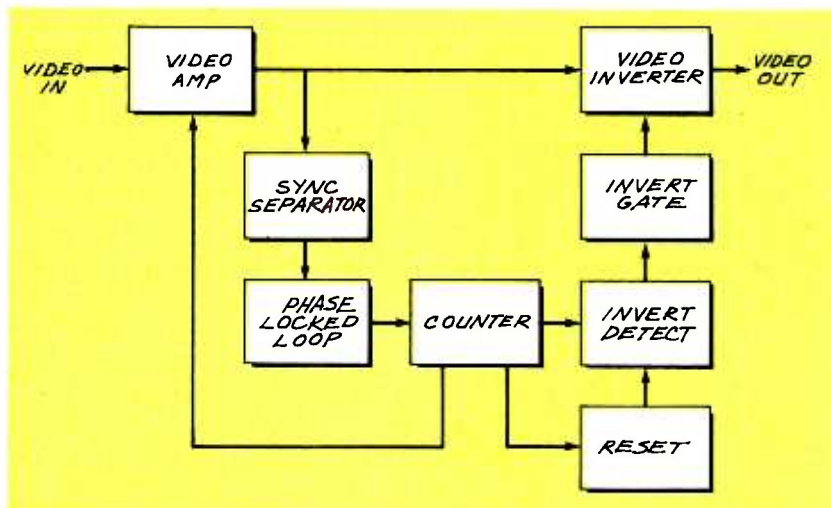

**FIG. 1—MOST OF OUR BLOCK DIAGRAM** has already been turned into actual circuitry. Now we need a counter for the phase-locked loop.

paper. You have to keep things like cost in mind when you're designing a circuit.

The NTSC standards for a video signal have a precision of several decimal points, and every broadcaster in the country spends a lot of time and effort making sure his signal adheres to that standard. The same is true of TV manufacturers, as well. The theory for standardization is terrific but, as is usually the case, what happens in reality is different. All you have to do to see what I mean is put a scope on the video signal received by your TV set; you'll find an overall similarity to the video standard, but you'll be

tween studio-quality video (the stuff on the monitors in the broadcaster's control room) and received video (the stuff you see on your TV) is minimal.

Keeping all that in mind, let's design the rest of the descrambler.

The next thing we need is a divide-by-32 counter to complete the phase-locked loop section of the circuit. After my discussion of the relative importance of precision, you should understand why the phase-locked loop's oscillator is only RC-based, and not crystal controlled: It's just cheaper and easier.

The divide-by-32 circuit (the "Counter" in Fig. 1) can be built in





## FET'S

continued from page 56

to handle higher currents. As majority-carrier devices that store no charges, they can switch faster than bipolar power transistors.

Figure 12 is a section view of an N-Channel, enhancement-mode power MOSFET. Unlike its small-signal counterpart, the latest power MOSFET's are fabricated with vertical rather than planar structures. They are made with the double-diffused (DMOS) process, and they have conductive silicon (polysilicon) gates. The gate of this device is isolated from the source by a layer of insulating silicon oxide.

When a voltage is applied between the gate and source terminals, an electric field is set up within the MOSFET. This field alters the resistance between the drain and source terminals, and it permits conventional current to flow in the drain in response to the applied drain circuit voltage. There are also P-channel, enhancement-mode power MOSFET's in which conventional current flows in the opposite direction of the N-channel device. Figure 13 is the schematic symbol for a DMOS enhancement-mode, N-channel power MOSFET.

Figure 14 is an cutaway view of a typical DMOS power MOSFET. It is made up of many cells or transistor elements connected in parallel. Each source cell consists of a closed rectangular or hexagonal channel which separates a source region from the substrate drain body. The cells are formed in an integrated circuit process, and there might be more than a half million cells per square inch of substrate. All of the source cells are connected in parallel by a continuous deposition of aluminum metalization, which forms the grid-like common source terminal.

The DMOS power MOSFET contains an inherent PN junction diode, and its equivalent circuit can be considered as a diode in parallel with the

source-to-drain channel, as shown in the schematic symbol of Fig. 13.

International Rectifier (IR) makes DMOS power MOSFET's that have hexagonally shaped cells, so it calls its products HEXFET's. Motorola Semiconductor also offers DMOS power MOSFET's, but its devices have rectangular rather than hexagonal cells. Motorola named its power MOSFET's TMOS to call attention to the T-shaped current flow that occurs in the cells between the common drain and the channels to the multiple sources.

Power MOSFET's are widely specified for high-frequency switching power supplies (generally those that switch at frequencies above 100 kHz), AC and DC motor speed controls, high-frequency generators for induction heating, ultrasonic generators, audio amplifiers, and amplitude modulation transmitters.

The advantages to using power MOSFET's over power bipolar transistors include:

- Faster switching speeds and lower switching losses.
- Absence of the bipolar's second breakdown
- Wider safe operating area
- Higher input impedance
- High, if not higher, gain
- Faster rise and fall times
- Simple drive circuitry

The principal disadvantages of power MOSFET's are their higher cost and a higher static drain-to-source on-state resistance, which can cause unacceptable power losses in certain switching applications. However, the manufacturers have made progress in reducing those resistance values. DMOS geometry has largely replaced the V-groove or VMOS process that was widely used to fabricate power MOSFET's back in the 1970's.

Radio-frequency power MOSFET's are now available that will operate over the 2 to 200 MHz frequency range. The high power and high gain of these devices makes them suitable as power amplifiers in solid-state transmitters for FM and TV broadcasting. Ω

# 42,398

## ELECTRONIC COMPONENTS

Whether you order 1 part or all 42,398...MOUSER stocks and...ships same day!!

CALL...  
(800) 992-9943

for your  
FREE  
CATALOG

2401 Hwy 287 N.  
Mansfield, TX 76063

## MOUSER<sup>®</sup>

### ELECTRONICS

Sales & Stocking Locations Nationwide

CIRCLE 117 ON FREE INFORMATION CARD

## Choose from 45 Career Opportunities!

Get Your Specialized Associate Degree or Career Diploma at Home in Spare Time

Now without attending college classes and with no previous experience, you can train for a money-making career...even get a Degree. Send for free facts and color brochure on employment opportunities in the field that interests you most. See how easy it is to train at home for a great career or advancement in your present job.



CALL TOLL FREE

1-800-234-9070 Ext. 693

CALL ANYTIME—24 hours a day, 7 days a week

OR MAIL COUPON TODAY!

**ICS** International Correspondence Schools

Dept. ADES23S, 925 Oak Street, Scranton, PA 18515

Please send me free facts, color brochure and full information on how I can study at home for the career I have chosen.

No obligation. CHECK ONE BOX ONLY!

#### ASSOCIATE IN SPECIALIZED BUSINESS DEGREE PROGRAMS

- Business Management
- Accounting
- Bus. Mgmt.—Finance Option
- Bus. Mgmt.—Marketing Option
- Applied Computer Science

#### ASSOCIATE IN SPECIALIZED TECHNOLOGY DEGREE PROGRAMS

- Civil Engineering Technology
- Mechanical Engineering Technology
- Electrical Engineering Technology
- Electronics Technology

#### CAREER DIPLOMA PROGRAMS

- High School
- Auto Mechanics
- Surveying and Mapping
- Drafting
- Air Conditioning & Refrigeration
- Wildlife/Forestry Conservation
- Police Sciences
- Diesel Mechanics
- Electrician
- Small Business Management
- Gun Repair
- Electronics
- Hotel/Restaurant Management
- Child Day Care
- Legal Assistant
- Interior Decorating
- Medical/Dental Office Assistant
- Secretary
- Bookkeeping
- Art
- Motorcycle Repair
- Catering/Gourmet Cooking
- Computer Programming
- Personal Computer Specialist
- Computer-Assisted Bookkeeping
- PC Repair
- Desktop Publishing & Design
- Fitness & Nutrition
- TV/VCR Repair
- Animal Care Specialist
- Photography
- Journalism/Short Story Writing
- Florist
- Teacher Aide
- Medical Transcriptionist
- Real Estate Appraiser

Name \_\_\_\_\_ Apt. # \_\_\_\_\_

Address \_\_\_\_\_

City/State \_\_\_\_\_ Zip \_\_\_\_\_

Phone ( ) \_\_\_\_\_

CIRCLE 177 ON FREE INFORMATION CARD

# COMPUTER CONNECTIONS

## The Emerging PC

JEFF HOLTZMAN

**1**992 drew to a close with some of the most exciting developments in the PC industry in years. There is no single overarching product or technology, but lots of little bits and pieces that together point to the emergence of a new class of personal computers with unprecedented power, versatility, and connectivity. Core technologies include powerful and upgradeable CPU's, general-purpose digital signal processors (DSP's), rapid acceptance of local buses and corresponding decrease in the ISA/EISA/MCA bus wars. Other trends involve accelerated true-color graphics, motion video compression and decompression, drastically reduced power consumption, increased semiconductor and magnetic storage, full-featured operating systems, built-in local-area network connectivity, 100-MHz + LAN speeds, and wireless cellular networking.

### PC architecture

During the past year, the 486 has quickly surged ahead of the 386 as the platform of choice. Spurred on by competition from Cyrix, AMD, and others, Intel has released a wide variety of 486-based devices, with many more to come. Prime features of all include low power and performance enhancement through clock-doubling—and -tripling, as demonstrated by IBM recently—technology. The clock doublers have been well received, even though pricing continues to hover near that of full motherboard upgrades that provide better performance.

And speaking of Intel, you may think of the company primarily in terms of CPU's, but during the past few years, Intel has stuck its corporate thumbs in numerous pies—and

has come out holding several juicy plums. Of course, there are the CPU's. There is also video-compression technology, exhibited first as the Digital Video Interactive (DVI) boards for digitizing and displaying full-motion video on desktop computers. Part of DVI is Real Time Video (RTV), which Intel has ported from the i750 video processor to the 386/486/Pentium architecture, and now calls Indeo. Indeo is one of the compression algorithms included as part of Microsoft's Video for Windows; Indeo is also being supported by Apple's QuickTime, and by IBM's recently announced Ultimotion. As discussed here in the preceding few months, software-only video is gimmicky, but an important first step in computer video.

Then there are network cards; Intel's cards are highly regarded, and are available for extremely competitive prices. Next come faxes and modems. Intel's SatisFAXion 400 is the highest-performing general-purpose modem and fax card combination on the market, although its bundled software leaves something to be desired. And let's not forget about PC integration chip sets, especially the upcoming Peripheral Component Interconnect (PCI) devices that will provide a standard local-bus architecture for 32- and 64-bit microprocessors. PCI-based systems should start appearing about the time you read this.

Of course, PCI is not the only kid on the block; a competing standard is the VL bus, named after the Video Electronics Standards Association's local bus. Both VL bus and PCI provide high-performance links between a CPU and its peripherals (such as network, video, and disk controller cards). In the words of one industry analyst, VL-bus seems to be better supported by expan-

sion-card manufacturers, and PCI by systems developers. Despite the lack of accepted standards, local-bus video is catching on. At last fall's Comdex, the computer industry's leading trade show, numerous video-card manufacturers announced VL-Bus products, including ATI, Cardinal, Genoa, Matrox, VideoLogic, and VidTech. Nonetheless, Intel's influence should not be underestimated. It will probably take 18–24 months for VL bus or PCI to emerge as a clear victor; in the meantime, both will be well supported by many manufacturers. One irony of all this is that the ISA vs. EISA vs. MCA bus war initiated with IBM's April 1987 introduction of the PS/2 line has become moot. The traditional expansion bus will be relegated to mouse, modem, and other low-speed devices.

The emergence of Windows (and to a lesser extent OS/2) has driven video card manufacturers to unprecedented levels of price/performance in just a few short years. Little more than two years ago, high-speed, high-resolution, high-color (24-bit) cards were available only on coprocessor-based boards, with prices beginning around \$1000. Today, you can get "accelerated" video adapters that provide 80% of the performance for 20% of the price of the coprocessed boards.

High-resolution monitors have also fallen in price, but not nearly as much as required. In addition, screen sizes greater than 16 inches invariably mean bulky, heavy, power-hungry devices. The monitor remains the weakest overall component of today's computer system.

One area of potential concern is semiconductor memory. The U.S. Department of Commerce recently instituted import duties on memory chips from several Korean manufac-



urers; street prices have already risen 25–30%. The DoC is expected to make a final ruling in early spring about whether those manufacturers are “dumping” chips below market value. If so, growth of Windows, OS/2, and corresponding applications software will likely slow. On the other hand, IBM and other manufacturers have started shipping 16-Mbit DRAM’s on various systems. Clearly, the day of 16-, 64-, and 128-megabyte systems is not far off.

Digital-signal processing is poised to change dramatically the way PC’s deal with analog data. Texas Instruments recently introduced a DSP chip and several corresponding boards that provide fax, modem, sound synthesis, speech-recognition, and data-compression capabilities. If this chip were made a standard part of every motherboard, it would eliminate the need for dedicated fax, modem, sound, and compression boards.

### **Pervasive networking**

It won’t be long before every desktop and portable PC, Macintosh, and workstation comes with built-in network capability. Chips & Technologies and Standard Microsystems have joined AMD, Artisoft, and National Semiconductor in the market for low-cost, single-IC Ethernet interfaces. These devices provide a complete network interface in a \$20 package (in lots of 1000+ pieces). Zenith Data Systems was the first to include a built-in Ethernet port, but other manufacturers are following suit.

In the local-area networking arena, Microsoft released Windows for Workgroups (WfW), a version of Windows with built-in peer-to-peer networking. Although not as robust as market leader Lantastic, WfW has built-in scaled-down versions of Microsoft’s widely regarded E-mail and group-scheduling applications. The main thing lacking is a DOS client (i.e., it is not possible to attach to a WfW server from a DOS-only machine). However, Microsoft will sell one separately, and may well bundle it with the forthcoming DOS 6.0, which will also include anti-virus, disk-compression, and robust backup utilities. That should further

squeeze Symantec/Norton and Central Point Software, providers of popular utility programs. WfW will not likely displace large NetWare (or other brand) LAN’s. Microsoft appears to be targeting first-time network users and corporate workgroups with traditional client-server systems (e.g. NetWare) that also need peer-to-peer services.

Wireless networking is on the verge of exploding. There was a burst of interest on this subject at Fall Comdex. For example, two leading computer companies (IBM and Apple) have teamed up with several cellular telecommunications providers (McCaw, Ram Mobile Data, Ardis—itsself a joint venture between Motorola and IBM—and others) to support Cellular Digital Packet Data, a way of delivering digital data (e.g. E-mail) to one or more recipients anywhere, on demand, and in real time. IBM, Apple, Motorola, and a startup called Eo demonstrated various notebook computers, stylus-input devices, and personal digital assistants (PDA’s) performing CDPD activities with attached cellular modems and cellular telephones.

### **Portables and printers**

More manufacturers are supporting the PCMCIA (Personal Computer Memory Card Industry Association) standard. One vendor has gone so far as to call PCMCIA the ISA bus of the 90’s. PCMCIA is not, however, without problems. The technology has gone through several fairly rapid evolutionary stages, PCMCIA 1 and PCMCIA 2, the latter being the current version. PCMCIA 1 was originally designed for memory expansion; but the idea of credit-card-size expansion devices quickly caught on and was expanded. IBM, for example, recently introduced several products called Credit Card Adapters that provide Token Ring and Ethernet connectivity, and 3270 terminal emulation. Other vendors also provide fax and modem adapters.

The technology has evolved more rapidly than the standards, so there is a potential for incompatibilities. To help avoid those problems, Intel developed an enhancement to PCMCIA 2, the Exchangeable Card

Architecture (ExCA), which appears to be catching on. In addition to basic PCMCIA 2 compatibility, ExCA addresses several other issues, including the use of multiple cards in a system, and hot swapping (the ability to insert and remove cards with power on). Caveat emptor if you plan to buy new systems with PCMCIA expansion capabilities.

On the other hand, pen-based computing (as discussed here in the February 1992 issue), has taken off much slower than expected. Originally, the industry expected to see significant activity by the end of 1992, but now it looks as if little will happen before late 1993. However, as one manufacturer puts it, “The timing for our projections was off—not the projections themselves.”

Hewlett-Packard has once again created a ground-breaking product: The LaserJet IV. It is a true 600-dots per inch laser printer, with street prices starting around \$1300; for PostScript, add about \$500. You don’t have to look twice to see the difference between 300 and 600 DPI, especially when reproducing fine curves and gray-scaled photographs. Another innovation is bidirectional communications, which allows the printer to inform a host computer of such printer faults as paper out and paper jamming.

Compaq also broke into the high-resolution market last summer with an extremely competitive, large-format laser printer that accepts useful add-ins including a send/receive fax modem. That idea quickly spread to the retrofit market for older LaserJet II’s and III’s, which now have several choices for faxes that interface through font-cartridge slots. Microsoft will shortly introduce a II/III upgrade cartridge of its own. The company claims that this cartridge will print Windows graphics much quicker than with the use of either PostScript or PCL. It will also provide a voice interface that will, for example, inform the user aurally that paper is out.

On the workstation front, DEC recently released seven computers ranging from \$10,000 workstations to \$300,000 mainframes, all based on the long-awaited 64-bit Alpha microprocessor. DEC has also publicly


demonstrated Windows NT running on an EISA-based Alpha PC—that, incidentally, includes a PCI-based local bus. Sun and HP simultaneously announced competitive upgrades to their lines. Sun appears to be going after the high-end PC market, claiming much better AutoCAD performance than with a 50-MHz 486. Industry feeling is that HP provides the performance edge—but Sun still holds the largest market share, about 34%. IBM has been strangely silent about its well-received RS/6000 line throughout these recent scuffles.

### Conclusions

Together, all these developments add up to a new era of power and convenience for personal-computer users. The day is not far off when you will be able to connect to a worldwide network from anywhere, at any time, and obtain any available information. The rate of approach to this goal has increased rapidly during the past year, and the trend is likely to continue. More next time.

### Product watch

Figure 1 shows a screen shot of a ground-breaking new Windows database: Microsoft's Access. This is a product made to order for people whose needs exceed the capabilities of typical flat-file databases, but who don't enjoy writing code in dBASE (or whatever), and who, in any case, want a wholly Windows-based solution. To understand Access, imagine uniting a powerful, multilingual, multiuser

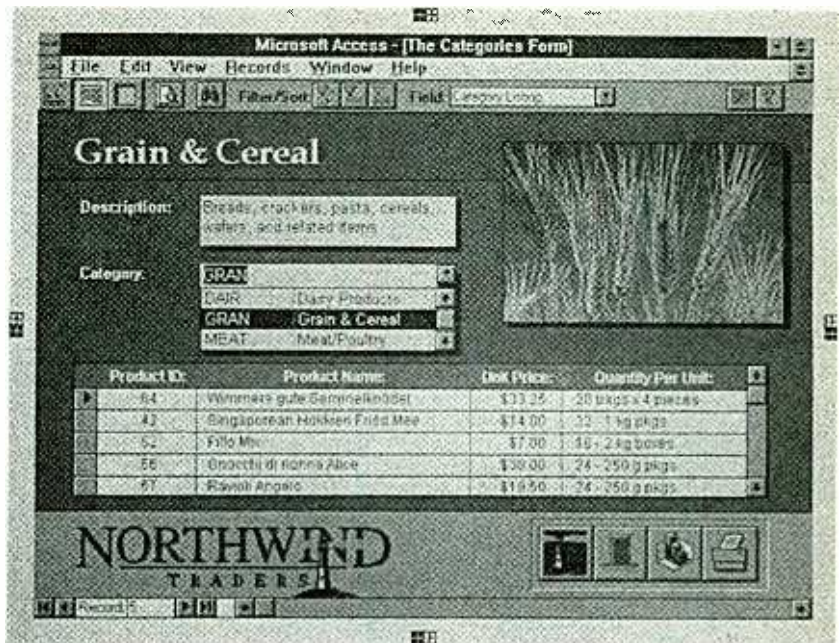

**FIG. 1—MICROSOFT'S ACCESS HERALDS A NEW ERA IN DATABASE MANAGERS. This program provides power, ease of use, and ease of learning for Windows users. It spells trouble for Borland's dBASE and Paradox lines, both of which still have no Windows versions.**

database engine with a visual development environment like that in Visual Basic, giving it a good dose of object-oriented behavior, and topping it all off with extensive help and tutorial information suitable for occasional database developers.

In addition to its own format, Access can read and write ASCII, Btrieve, dBASE, Excel, and Paradox files in their native formats. Access can also attach to SQL databases (at present, only Microsoft's SQL server, but Oracle support is scheduled soon). Access has extremely intuitive form-, report-, and query-building tools. For example, the form builder lets you draw fields, attach attributes (e.g. color and input validation criteria), and go.

Like Microsoft's other major Windows applications (Word and Excel), Access has just the right balance of power and ease of use. As with the other products, Access makes it easy to get started, and macros and a full development language called Access Basic provide lots of room for growth as your needs evolve. Access supports typical data types (character, date, numeric, logical), as well as binary objects including images, sound, and video.

Access is a fully relational prod-

uct that allows one to create "virtual" tables, called Dynasets, that consist of records concatenated from other tables joined by common fields. Any updates to a Dynaset propagate back into the source tables from which the data came. Access also provides multiuser network access (including WFW support) and record-level locking. Initial pricing was set at about \$100. If you can get a copy at that price, grab it. It's one of the best software deals around.

Home hardware hackers will want to check out Home Automation Laboratories, which publishes a catalog chock-full of information and product listings for devices that control lights and other electrical appliances remotely through special control panels or your PC. Simply reading the catalog can be an education in itself.

If you're looking for special laser printer paper or labels, check out the Paper Direct catalog. It lists numerous specialty items including foils that you can run through your laser printer to add color to presentations, prefolded brochure blanks that go through your laser printer and have business-card cutouts, and lots of other goodies. In both cases, tell 'em we sent you. Ω

### Resources

- Microsoft Access (\$495), Microsoft Corp., One Microsoft Way, Redmond, WA 98052. (800) 426-9400, (206) 882-8080.  
CIRCLE 41 ON FREE INFORMATION CARD

- Home Automation Laboratories, 5500 Highlands Parkway, Suite 450, Smyrna, GA 30082-5141. (800) YEL-4-HAL (catalogs), (800) HOME-LAB (orders), (404) 319-0600 (general).  
CIRCLE 42 ON FREE INFORMATION CARD

- Paper Direct, 205 Chubb Avenue, Lyndhurst, NJ 07071. (800) A-PAPERS, (201) 507-1996.  
CIRCLE 43 ON FREE INFORMATION CARD



# BUYER'S MART

## FOR SALE

**TUBES.** "oldest", "latest." Parts and schematics. SASE for lists. **STEINMETZ**, 7519 Maplewood Ave., Hammond, IN 46324.

**TUBES**, new, up to 90% off, SASE, **KIRBY**, 298 West Carmel Drive, Carmel, IN 46032.

**T.V.** notch filters and bullet stopper, free brochure. **MICRO Thinc**, Box 63/6025, Margate, FL 33063. (305) 752-9202.

## CLASSIFIED AD ORDER FORM

To run your own classified ad, put one word on each of the lines below and send this form along with your check to:

**Electronics Now Classified Ads**, 500-B Bi-County Boulevard, Farmingdale, NY 11735

**PLEASE INDICATE** in which category of classified advertising you wish your ad to appear. For special headings, there is a surcharge of **\$25.00**.

Plans/Kits     Business Opportunities     For Sale  
 Education/Instruction     Wanted     Satellite Television

Special Category: \$25.00

### PLEASE PRINT EACH WORD SEPARATELY, IN BLOCK LETTERS.

(No refunds or credits for typesetting errors can be made unless you clearly print or type your copy.) Rates indicated are for standard style classified ads only. See below for additional charges for special ads. **Minimum: 15 words.**

1	2	3	4	5
6	7	8	9	10
11	12	13	14	15 (\$46.50)
16 (\$49.60)	17 (\$52.70)	18 (\$55.80)	19 (\$58.90)	20 (\$62.00)
21 (\$65.10)	22 (\$68.20)	23 (\$71.30)	24 (\$74.40)	25 (\$77.50)
26 (\$80.60)	27 (\$83.70)	28 (\$86.80)	29 (\$89.90)	30 (\$93.00)
31 (\$96.10)	32 (\$99.20)	33 (\$102.30)	34 (\$105.40)	35 (\$108.50)

We accept MasterCard and Visa for payment of orders. If you wish to use your credit card to pay for your ad fill in the following additional information (Sorry, no telephone orders can be accepted.):

Card Number \_\_\_\_\_

Expiration Date \_\_\_\_\_

Please Print Name \_\_\_\_\_

Signature \_\_\_\_\_

**IF YOU USE A BOX NUMBER YOU MUST INCLUDE YOUR PERMANENT ADDRESS AND PHONE NUMBER FOR OUR FILES. ADS SUBMITTED WITHOUT THIS INFORMATION WILL NOT BE ACCEPTED.**  
**CLASSIFIED COMMERCIAL RATE:** (for firms or individuals offering commercial products or services) \$3.10 per word prepaid (no charge for zip code)...**MINIMUM 15 WORDS.** 5% discount for same ad in 6 issues; 10% discount for same ad in 12 issues within one year; if prepaid (not applicable on credit card orders). **NON-COMMERCIAL RATE:** (for individuals who want to buy or sell a personal item) \$2.50 per word, prepaid...no minimum. **ONLY FIRST WORD AND NAME** set in bold caps at no extra charge. Additional bold face (not available as all caps) 55¢ per word additional. Entire ad in boldface, \$3.70 per word. **TINT SCREEN BEHIND ENTIRE AD: \$3.85 per word. TINT SCREEN BEHIND ENTIRE AD PLUS ALL BOLD FACE AD: \$4.50 per word. EXPANDED TYPE AD: \$4.70 per word prepaid.** Entire ad in boldface, \$5.60 per word. **TINT SCREEN BEHIND ENTIRE EXPANDED TYPE AD: \$5.90 per word. TINT SCREEN BEHIND ENTIRE EXPANDED TYPE AD PLUS ALL BOLD FACE AD: \$6.80 per word. DISPLAY ADS:** 1" x 2 1/8"—\$410.00; 2" x 2 1/8"—\$820.00; 3" x 2 1/4"—\$1230.00. **General Information:** Frequency rates and prepayment discounts are available. **ALL COPY SUBJECT TO PUBLISHERS APPROVAL. ADVERTISEMENTS USING P.O. BOX ADDRESS WILL NOT BE ACCEPTED UNTIL ADVERTISER SUPPLIES PUBLISHER WITH PERMANENT ADDRESS AND PHONE NUMBER.** Copy to be in our hands on the 1st of the third month preceding the date of the issue. (i.e., Aug. issue copy must be received by May 1st). When normal closing date falls on Saturday, Sunday or Holiday, issue closes on preceding working day. Send for the classified brochure. Circle Number 49 on the Free Information Card.

**ENGINEERING** software and hardware, PC/MSDOS. Circuit design/drawing, PCB layout, FFT analysis, mathematics, circuit analysis. Data acquisition, generation, I/O PCB's. Call or write for free catalog. (614) 491-0832, or fax (614) 497-9971, **BSOFT SOFTWARE, INC.**, 444 Colton Rd., Columbus, OH 43207.

**CABLE test chips.** Jerrold, Tocom, S.A., Zenith. Puts cable boxes into full service mode! \$29.95 to \$59.95. 1 (800) 452-7090, (310) 867-0081.

## Cable TV DESCRAMBLERS

**30-day  
Money Back  
Guarantee**



**ORDER  
NOW!**

- The Most Complete Line of Descramblers
- Friendly, professional service
- **FREE Catalog**



# 1-800-228-7404

Go to the Source  
**NU-TEK ELECTRONICS**  
3250 Hatch RD  
Cedar Park TEXAS 78613

**TOCOM-Jerrold Impulse-Scientific Atlanta** Converters, two year warranties, also test modules for your converters. Contact **NATIONAL CABLE**, (219) 935-4128 full details.

**SECRET cable descramblers!** Build your own descrambler for less than \$12.00 in **seven easy steps.** Radio Shack parts list and free descrambling methods that **cost nothing** to try, included. Send \$10.00 to: **HARRY WHITE**, PO Box 1790, Baytown, TX 77522.

## CB RADIO OWNERS!

We specialize in a wide variety of technical information, parts and services for CB radios. 10-Meter and FM conversion kits, repair books, plans, high-performance accessories. Thousands of satisfied customers since 1976! Catalog \$2.

**CBC INTERNATIONAL**  
P.O. BOX 31500RE, PHOENIX, AZ 85046

**300 Experimenters Circuits** — Complete in 6 practical books using diodes, relays, FET's, LED's, IC 555's, and IC CA3130's for building blocks. Only \$33.00 plus \$5.50 for shipping. USA and Canada only. US funds. **ETT, INC.**, PO Box 240, Massapequa Park, NY 11762-0240.

**EPROMS**, Assorted, i.e., 27128A-15 \$3.00 each minimum quantity 13 pieces. C.O.D., American Express. **H.E.A.R.T. Inc.**, 1 (800) 677-3773.

## THE ELECTRONIC GOLDMINE



The Electronic Goldmine has one of the greatest selections of unique electronic project kits available in the world! We have over 65 kits and over 1900 unique bargain priced components in our new 80 page catalog!

**FREE CATALOG**  
with over 1900 different items including 65 kits!  
Request your copy TODAY!

---

### BIKE FLASHER KIT

Be seen night or day with our flashing bright xenon strobe tube with 2 3/4" square red lens. 2AA batteries not included.

**C6475 \$12.50**




---

### Filtered Ultraviolet BLACKLIGHT TUBE

Brand new 9" long (including terminals). Great for posters, U.V. inks and minerals. To operate on DC use the medium inverter transformer.

**G3008 Reg. \$8.50  
SALE \$7.00**





---

### Medium Inverter TRANSFORMER

Converts 9V or 12 VDC to over 250 V when used with a 555 IC circuit. (Schematic included) Perfect for portable strobes, blacklight etc.

**G993 \$1.75 EA. 100/\$160.00**





---

### Ultraviolet Sensor Sun EXPOSURE METER

Small electronic device detects UV energy from the sun and sounds a signal when you've had enough exposure. 9V battery not included.

**G934 Reg. \$8.95 10 for \$45.00  
SALE \$5.00**



**NEW!**

MINIMUM ORDER: \$19.00 plus \$3.50 shipping and handling \$5.00 for U.S. Mail. We accept MC, VISA and Money Orders.  
SEND ORDERS TO: THE ELECTRONIC GOLDMINE  
P.O. Box 5408 Scottsdale, AZ 85261  
PHONE ORDERS (602) 451-7454 FAX ORDERS (602) 451-9495

CIRCLE 125 ON FREE INFORMATION CARD

**TEST equipment** pre-owned now at affordable prices. Signal generators from \$50.00, oscilloscopes from \$50.00. Other equipment including manuals available. Send \$2.00 U.S. for catalog refunded on first order. **J.B. ELECTRONICS**, 3446 Dempster, Skokie, IL 60076. (708) 982-1973.

**CABLE TV converters:** Jerrold, Oak, Scientific Atlantic, Zenith & many others. "New MTS" stereo add-on: mute & volume. Ideal for 400 and 450 owners! 1 (800) 826-7623, Amex, Visa, M/C accepted. **B & B INC.**, 4030 Beau-D-Rue Drive, Eagan, MN 55122.

### WIRELESS CABLE RECEIVERS 1.9 to 2.7 GHz

36 CH 20" Parabolic Dish Sys.....	\$173.90
36 CH 18" Rod Ant. Sys.....	\$193.90
36 CH 16x20" Grid Ant. Sys. [photo].....	\$289.00
36 CH 24x36" Grid Ant. Sys.....	\$314.95

**SUN MICROWAVE INT'L. INC.** Send \$10\* for product catalog.  
PHOENIX, AZ 85067 Dealer discounts available.  
(602) 230-1245 FAX (602) 269-6069  
ORDERS ONLY 1-800-484-4190 code 9793



VISA/MC/AMEX

**"SPEAKUP."** Voice recorder board. Assembled, with mike and speaker, 8 seconds speech. Push-button record/play. Inputs for external rec/play/pause/stop. With schematic. Experiment, build novelty toys, games. \$21.95 + \$2.00 S&H. Check or MO to **ELECTROGADGETS INC.**, PO Box 2065, Morris Township, NJ 07962.

**PLATED** thru hole PCB's prototype quantities. Two board minimum, fast, economical. For complete information call **AP CIRCUITS LTD.**, (403) 250-3406. BBS (403) 291-9342 (8,N,1).

**CABLE Converters, accessories below wholesale!** Immediate delivery from giant stock! COD orders only. 1 (800) 995-1749.

## FREE CATALOG

### FAMOUS "FIRESTIK" BRAND CB ANTENNAS AND ACCESSORIES. QUALITY PRODUCTS FOR THE SERIOUS CB'er. SINCE 1962

### FIRESTIK ANTENNA COMPANY

2614 EAST ADAMS  
PHOENIX, ARIZONA 85034

**OAK** Sigma descrambler, CH3 output, rare hard-to-find units, \$100.00 postpaid, only moneyorders please. **SURPLUS ELECTRONICS**, Box 10009, Colorado Springs, CO 80932.

**TEST-Aids** for testing units in full service mode. Starcom VII, \$40.00; Starcom VI, \$30.00; Starcom DPBB, \$50.00; Pioneer, clears error codes E2 E3 E4 E5, \$60.00; Pioneer cubes, will not alter internal serial number, \$125.00; Tocom VIP 5503/5507, \$25.00; S.A. 8500, \$25.00; 8550 \$30.00; 8580, \$40.00; 8570/90, \$50.00; 8600, \$50.00; Zenith ZTac, \$25.00; security tools and remotes. **N.E. ENGINEERING**, (617) 770-3830.

**RESTRICTED technical information:** Electronic surveillance & schematics; locksmithing; cable phreaking; hacking; etc. **Free brochures:** **MENTOR**, Box 1549-Z, Asbury Park, NJ 07712.

### Quality Microwave TV Antennas

**WIRELESS CABLE - LPTS - MMDS - Amateur TV Ultra High Gain 50db(+)** • Tuneable 1.9 to 2.7 GHz

- 55-Channel Dish System \$199.95
- 36-Channel Dish System \$149.95
- 20-Channel Dish System \$124.95
- Optional Commercial Grid Antenna (not shown) Add \$50.00
- Yagi Antennas, Components, Custom Tuning Available
- Call or write (SASE) for "FREE" Catalog

**PHILLIPS-TECH ELECTRONICS**  
P.O. Box 8533 • Scottsdale, AZ 85252  
(602) 947-7700 (\$3.00 Credit all phone orders)  
MasterCard • Visa • American Express • COD's • Quantity Pricing



Dish System  
LIFETIME WARRANTY

**CABLE TV converters.** Jerrold, Zenith, Pioneer, Oak, Scientific Atlanta, and many more. 12 years experience gives us the **advantage**. Visa/MC Amex COD **ADVANTAGE ELECTRONICS, INC.**, 1 (800) 952-3916 1125 Riverwood Dr., Burnsville, MN 55337.

**PC boards:** Professional quality, 30 day guarantee, beat all prices. **A&D**, PO Box 311, Auburn, MI 48611. (517) 662-6633.

**RADIO** Television magazines from 1940. Best offer. **T. LOBOSCO** (718) 266-7460.

**VIDEO** tapes covering electronics, computers and communications. Demo \$3.50. **OCS**, PO Box 292, Fort Mill, SC 29715.

**AERONAUTICAL** and maritime frequency directories now available at Radio Shack. See page 23 of 1993 catalog.

**PREVENT** descrambler damage. Don't bite the bullet! Snooper Stopper Data Pulse Blocker \$33.95, with Surge Protector \$44.95 ... Wireless Video Sender \$54.95. VCI, 1 (800) 925-9426.

## PLANS AND KITS

**FASCINATING** electronic devices! Voice Disguiser! Vocal truth indicator! Lasers! Transmitters! Detectors! Free energy! High voltage! More! Kits/Assembled! Catalog \$4.00 (refundable). **QUANTUM RESEARCH**, 17919-77 Ave., Edmonton, AB. T5T 2S1.

**SURVEILLANCE transmitter kits** tune from 65 to 305 MHz. Mains powered duplex, telephone, room, combination telephone/room. Catalog with **Popular Communications, Popular Electronics** and **Radio-Electronics** book reviews of "Electronic Eavesdropping Equipment Design," \$2.00. **SHEFFIELD ELECTRONICS**, PO Box 377785-C, Chicago, IL 60637-7785.

**60 SOLDERLESS Breadboard Projects** in two easy-to-read pocket books. Complete with circuit descriptions, schematics, parts layouts, component listings, etc. Both books (BP107 & BP113) only \$11.90 plus \$3.50 for shipping. USA and Canada only. US funds. **ETT, INC.**, PO Box 240, Masapequa Park, NY 11762-0240.

**HOBBY/broadcasting/HAM/CB/surveillance** transmitters, amplifiers, cable TV, science, bugs, other great projects! Catalog \$1.00. **PANAXIS**, Box 130-F3, Paradise, CA 95967.

**DESCRAMBLER** kits. Complete cable kit \$44.95. Complete satellite kit \$49.95. Add \$5.00 shipping. Free brochure. No New York sales. **SUMMIT RE**, Box 489, Bronx, NY 10465.

### REMOTE CONTROL KEYCHAIN

Complete w/mini-transmitter and x5 vdc RF receiver Fully assembled including plans to build your own auto alarm

**\$24.95** Check, Visa or M/C Add \$3 shipping  
5 @ \$19.95, 10 @ \$14.95

Visitect Inc. Box 14156, Fremont, Ca. 94539  
(510) 651-1425 Fax (510) 651-8454



**DESCRAMBLING**, new secret manual. Build your own descramblers for **cable and subscription TV**. Instructions, schematics for SSAVI, gated sync, Sinewave, (HBO, Cinemax, Showtime, UHF, Adult) \$12.95, \$2.00 postage. **CABLETRONICS**, Box 30502R, Bethesda, MD 20824.

**PROJECTION TV**...Convert your TV to project a 7-foot picture. **Easy!**...Results comparable to \$2,500.00 projectors...**Plans and 8" lens \$29.95**...Professional systems available. Illustrated catalog...**free**...**MACROCOMA**, 15-GF Main Street, Washington Crossing, PA 18977. Credit card orders (215) 736-3979.

**VHF-FM amplifier** plans. 75-110 MHz, 15-25 watts. \$16.00. **PROGRESSIVE CONCEPTS**, 1313 North Grand Ave., #291, Walnut, CA 91789.

**WORLD famous!** "Spy Shop the best in surveillance and countersurveillance equipment." Send \$6.00 for 140 page catalog. "SPY SHOP," PO Box 6703, Panama City, FL 32404.

### REMOVE LEAD VOCALS

Build this kit which removes lead vocals from standard stereo records CD's, tapes or FM broadcasts. Sing along with the background music. Use with any home component stereo. Additional kit adds reverb to your voice, then mixes it with music. **Pre-assembled boards** also available. Write for free info. **Weeder Technologies, P.O. Box 421, Batavia, Ohio 45103.**



**SOLAR** electric power catalog \$1.00. Become dealer in your area. Box 80063, Ontario, CA 91758.

**LASER** Speed Gun Jammer. Complete schematics, parts list and sources. \$9.95 **MCS RESEARCH**, 608 West Oak, Lafayette, CO 80026.

## SATELLITE TV

**FREE** catalog — Lowest prices worldwide. **SKYVISION**, 1012 Frontier, Fergus Falls, MN 56537. 1 (800) 334-6455. See full page ad the Shopper section.

**SATELLITE TV** — Do it yourself — major brands discounted, we'll beat everyone's price. Call **LARRY** (609) 596-0656.

**VIDEOCYPHER II descrambler manual.** Schematics, video, and audio. Explains DES, Eprom, CloneMaster, 3Musketeer, Pay-per-view (HBO, Cinemax, Showtime, Adult, etc.) \$16.95, \$2.00 postage. Schematics for Videocypther Plus, \$20.00. Schematics for Videocypther 032, \$15.00. Collection of software to copy and alter Eprom codes. \$25.00. **CABLETRONICS**, Box 30502R, Bethesda, MD 20824.

**SUPER** low satellite prices. Free U.S. and International catalog. **SATMAN**, (309) 692-4140 (Int'l), 1 (800) 472-8626 in U.S.



## BUSINESS OPPORTUNITIES

**YOUR** own radio station! Licensed/un-licensed AM, FM, TV, cable. Information \$1.00: **BROADCASTING**, Box 130-F3, Paradise, CA 95967.

**LET** the government finance your small business. Grants/loans to \$500,000. Free recorded message: (707) 449-8600. (KS1).

**EASY** work! Excellent pay! Assemble products at home. Call toll free 1 (800) 467-5566 Ext. 5192.

**HOME** assembly work available! Guaranteed easy money! Free details! **HOMEWORK-R**, Box 520, Danville, NH 03819.

## CABLE TV DESCRAMBLER LIQUIDATION!

**FREE CATALOG!**  
Hamlin Combos \$44, Oak M35B \$60 (mfn. 5), etc.  
**WEST COAST ELECTRONICS**  
For Information: 818-709-1758  
Catalogs & Orders: 800-628-9656

**MAKE** \$75,000.00 to \$250,000.00 yearly or more fixing IBM color monitors. No investment, start doing it from your home (a telephone required). Information, USA, Canada \$2.00 cash for brochure, other countries \$10.00 US funds. **RANDALL DISPLAY**, Box 2168-R, Van Nuys, CA 91404 USA. FAX (818) 990-7803.

**NEW** products wanted. Advanced specialized electronic products sought for distribution in Canada. Send details. **S.E.S.**, 2272 Lawson, West Vancouver, B.C. V7V 2E4.

## ANTIQUE RADIO CLASSIFIED

**Free Sample!**  
Antique Radio's  
Largest Circulation Monthly.  
Articles, Ads & Classifieds.  
6-Month Trial: \$15. 1-Yr: \$27 (\$40-1st Class).  
A.R.C., P.O. Box 802-L9, Carlisle, MA 01741

## WANTED

**INVENTORS:** We submit ideas to industry. Find out what we can do for you. 1 (800) 288-IDEA.

**ATTENTION!** No fees to inventors! Call **INVENTORS AWARENESS GROUP, INC.** for a free brochure. 1 (800) 288-3938.

## INVENTORS

**INVENTORS!** Can you patent and profit from your idea? Call **AMERICAN INVENTORS CORP.** for free information. Serving inventors since 1975. 1 (800) 338-5656.

## EDUCATION & INSTRUCTION

**F.C.C. Commercial General Radiotelephone** license. Electronics home study. Fast, inexpensive! "Free" details. **COMMAND**, D-176, Box 2824, San Francisco, CA 94126.

## Be a TV/VCR Repair Specialist

**N**ow you can train at home in spare time for a money-making career as a TV/VCR Repair Specialist. No previous experience necessary. No need to quit your job or school. Everything is explained in easy-to-understand language with plenty of drawings, diagrams and photos. We show you how to troubleshoot and repair video-cassette recorders and TV sets. how to handle house calls and shop repairs for almost any make of television or VCR. Tools are included with your course so you can get "hands-on" practice as you follow your lessons step by step. Send for free facts about the exciting opportunities in TV/VCR Repair and find out how you can start making money in this great career. **MAIL COUPON TODAY** K03C

**ICS SCHOOL OF TV/VCR REPAIR**, Dept. ADE023S  
925 Oak Street, Scranton, PA 18515  
Please send me full information and color brochure on how I can learn TV/VCR Repair at home in my spare time. I understand there is no obligation and no salesman will visit me.

Name \_\_\_\_\_ Age \_\_\_\_\_  
Address \_\_\_\_\_ Apt. # \_\_\_\_\_  
City/State \_\_\_\_\_ Zip \_\_\_\_\_  
Phone ( ) \_\_\_\_\_

**ELECTRONIC** engineering. 8 volumes complete. \$109.95. No prior knowledge required. Free brochure. **BANNER TECHNICAL BOOKS**, 1203 Grant Avenue, Rockford, IL 61103.

**LEARN** to earn. Electronic skills bring income. As low as \$49.50. Send \$2.00 for catalog to **A&A PRODUCTS**, Rt1 Box 482-L, Rockdale, TX 76567.

## CABLE TV DESCRAMBLERS ★ CONVERTERS ★ and ACCESSORIES.

## SAVE MONEY. DON'T RENT!

PANASONIC, JERROLD, OAK,  
PIONEER, SCIENTIFIC ATLANTA  
AND MORE. LOWEST PRICES. FREE CATALOG.  
**CABLE READY (800) 234-1006**  
COMPANY

## TELEPHONE LISTENING DEVICE



Record telephone conversations in your office or home. Connects between any cassette or tape recorder and your telephone line. Starts automatically when phone is answered. Records both sides of conversation. Stops recorder when phone is hung up.

**\$19.95** EACH Div. Disc Avail



**Super Powerful FM TRANSMITTER**  
Many times more powerful than other transmitters. Transmits up to 1/4 mile to any FM radio. Easy to Assemble Kit - up to 9V battery (not incl.) For catalog of Transmitters, Voice Scramblers and other specialty items, enclose \$2.00 to USI Corp.

Call 407-725-1000 or send \$19.95 + \$1.00 shipping per item to: USI Corp., PO Box EN-7072, Melbourne, FL 32902. C.O.D.'s OK.

Courteous Service • Discount Prices • Fast Shipping


## ALL ELECTRONICS CORP.

Mail Order Electronic Parts And Supplies  
P.O. Box 567 • Van Nuys, CA 91408
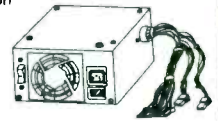
## 130 Watt Switching POWER SUPPLY

Youngone Communication  
Model # YP131-05  
Input: 90-120 Vac or  
180-250 Vac

Output: +5 Vdc/15 amp  
-5 Vdc/0.3 amp  
+12 Vdc/4.2 amp,  
-12Vdc/0.3 amp.



Fan cooled switching power supply. Housed in vented metal cabinet 6" x 5.5" X 3.65" high. Requires IEC type power cord. CSA and UL listed. Output leads terminate to 0.1" single row connectors. **CAT# PS-130 \$23.50 ea.**

## 85 BUTTON KEYBOARD



Honeywell# 85ST23-L-J. 85 key computer-type keyboard. Standard QWERTY keyboard with 10 function keys across the top and number pad on right side with other function keys. Solid 14" X 5" metal frame. Charcoal keys with white lettering. Terminates to two vinyl ribbon cables, 25 conductors. Logic board with 3 green leds can be easily removed if desired.  
**CAT# KP-85 \$3.00 each**

## 12 VDC GEAR MOTORS

Designed for automobile power windows, these worm gear driven motors were installed, but never used due to a defect in the mounting screws. Many of them still have broken screws in the mounting holes, but we have found that they remove easily with "easy-out" type bolt



removers. The motors and gear mechanisms are in excellent condition. 90 RPM @ 12 Vdc, 2 amps. 7.25" long X 3 3/4" wide 1.45" thick. Three mounting holes in triangular pattern. The final drive is a 0.75" diameter gear. There are two mirror-image styles, one for left and one for right hand windows.

Right side motor **CAT# MOT-9R \$10.00 each**  
Left side motor **CAT# MOT-9L \$10.00 each**  
One of each **CAT# MOT-9RL \$18.00**

## SPECIALS!

### 1/4" HEATSHRINK

6 ft. length. Shrinks to 1/8".  
**CAT# HUG-146 \$1.25 each • 10 for \$10.00**

## 2N6028 TO-92 PROGRAMMABLE UNIUNCTION TRANSISTOR

**CAT# 2N6028 3 for \$1.00 • 100 for \$25.00**

## 1,500 MFD 350 VDC COMPUTER GRADE CAPACITOR

4 1/4" high X 2 1/2" dia.  
**CAT# CG-32 \$5.50 each**



## TOLL FREE ORDER LINES

**1-800-826-5432**

CHARGE ORDERS to Visa, MasterCard or Discover

**TERMS:** Minimum order \$10.00. Shipping and handling for the 48 continental U.S.A. \$3.50 per order. All orders including AK, HI, PR or Canada must pay full shipping. All orders delivered in CALIFORNIA must include state sales tax (7.25%, 7.5%, 7.75%, 8.25%, 8.5%). Quantities Limited. NO C.O.D. Prices subject to change without notice.

Call or Write For Our  
**FREE 64 Page Catalog**  
(Outside The U.S.A. Send \$2.00 Postage)  
**ALL ELECTRONICS CORP.**  
P.O. Box 567 • Van Nuys, CA • 91408

CIRCLE 107 ON FREE INFORMATION CARD

## CABLE TV DESCRAMBLERS

\*\*\* VIDEO STABILIZERS AVAILABLE & Bullet Protectors \*\*\*  
MULTI-VISION ELECTRONICS, 2730 SO 123RD CT, STE. #126 OMAHA, NE, 68114  
**1-800-835-2330** BEST BUYS BEST SERVICE STARTS WITH A FREE CATALOG  
**1-800-327-8544** TECH LINE (402) 331-3228

- ((FEATURING))
1. Call Identifiers
  2. Power Antennas
  3. Mind-Machines
  4. Wireless Cable Receivers, T.V. 1.9-2.7 GHz
  5. Stun-Guns
  6. Surveillance
  7. Dual Deck VCR

Enter A World Of Excitement with a Subscription to

# Popular Electronics<sup>®</sup>

Get the latest electronic technology and information monthly!

Now you can subscribe to the magazine that plugs you into the exciting world of electronics. With every issue of Popular Electronics you'll find a wide variety of electronics projects you can build and enjoy.

Popular Electronics brings you informative new product and literature listings, feature articles on test equipment and tools—all designed to keep you tuned in to the latest developments in electronics. So if you love to build fascinating electronics, just fill out the subscription form below to subscribe to Popular Electronics... It's a power-house of fun for the electronics enthusiast.

EXCITING MONTHLY FEATURES LIKE:

- CONSTRUCTION
- FEATURES
- HANDS-ON-REPORTS
- SPECIAL COLUMNS

PLUS: ALL OUR GREAT DEPARTMENTS!

FOR FASTER SERVICE CALL TODAY  
**1-800-827-0383**  
 (7:30AM-8:30PM)  
 EASTERN STANDARD TIME



## Popular Electronics<sup>®</sup> SUBSCRIPTION ORDER FORM

P.O. Box 338, Mt. Morris IL. 61054

PLEASE PRINT BELOW:

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

Allow 6 to 8 weeks for delivery of first issue. U.S. Funds only. In Canada add \$5.00 Postage. All Other Foreign add \$7.50 Postage.

**YES!** I want to subscribe to Popular Electronics for 1 Full year (12 Issues) for only \$18.95. That's a savings of \$23.05 off the newsstand price. (Basic Subscription Rate—1 yr/\$21.95)

Payment Enclosed  Bill me later

Please charge my:  Visa  Mastercard

Acct. # \_\_\_\_\_

Signature \_\_\_\_\_ Exp. Date \_\_\_\_\_

**PAY TV AND SATELLITE DESCRAMBLING**  
 \*\*\*\*\* 1993 EDITION \*\*\*\*\*

Includes programming cable box chips, hacking @-MAC, wireless cable (MMDS) descrambling, butlets, PLUS fixes and much more. ONLY \$18.95. Other PAY TV and SATELLITE DESCRAMBLING volumes. Volume 1 (BASICS), 1989, 1991, and 1992. \$15.95 each. Different turn-ons, bypasses, ECM's, schematics and counter ECM's in each. **"THE TIME IS NOW!"** Using the VCI data stream. \$15.95. Any 3/\$32.95 or 5/\$54.95. **STAY UP TO DATE!** monthly. Keep up with the latest in satellite and cable descrambling. Everything that's new. \$32.95/yr. **OUR BEST DEAL** everything here, the video and much more only \$129.95. New catalog \$1.

Scrambling News, 1552 Hertel Ave., #123, BUFFALO, NY 14216  
 Voice/FAX (716) 874-2088 CUD's are OK. ADD \$6

MASTERCARD AND VISA are now accepted for payment of your advertising. Simply complete the form on the first page of this section and we will bill. \$15.00 minimum.

## BUY BONDS

**ENROLL NOW — GET UP TO 50% OFF!**

**YOU TRAIN AT HOME**



Master the skills you need with NEI. Personal service. Low tuition.

- Bookkeeping
- C Programming
- QBasic Programming
- PC Servicing

**CALL TODAY!**  
**1-800-552-0782**

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

City/State/Zip \_\_\_\_\_

**NEI** Dept. 7021-0393  
 2929 Windom Place, Washington, DC 20008



Whether you wish to save money, boldly go where no guitarist has gone before or simply have fun building electronic gadgets designed for your musical pleasure, then read

## Electronic Projects for GUITAR

Some of the add-on guitar gadgets you can build are:

- Preamplifier • Headphone Amplifier • Soft Distortion Effects Unit • Compressor • Auto-waa • Waa-waa Pedal • Phaser • Dual Tracking Effects • Distortion Unit • Expander • Dynamic Treble Booster • Direct Injection Box • Dynamic Tremelo • Thin Distortion Unit • and Guitar Tuner.

Anyone with some previous electronic project building experience should have no problem assembling the projects.

**ELECTRONICS TECHNOLOGY TODAY INC.**  
 P.O. Box 240, Massapequa Park, NY 11762-0240

Yes, send my copy of ELECTRONIC PROJECTS FOR GUITAR by RA Penfold to the address at right. I am enclosing \$12.95 plus \$2.95 for shipping charges in USA and Canada. All payments must be made in US funds. Sorry, no orders accepted outside of USA and Canada. New York State residents add local sales tax. Allow 6-8 weeks for delivery.

Check enclosed.

Please charge my  Visa  MasterCard

Signature \_\_\_\_\_

Account No. \_\_\_\_\_ Expir. Date \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ ZIP \_\_\_\_\_




# 1-800-831-4242

## Your Resource for Value. Only a Phone Call Away.
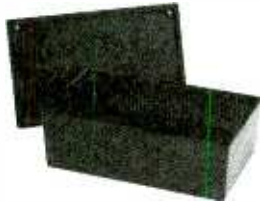
### ABS SPEEDY BOXES

Will not crack or split when drilled or punched. Complete with four screws and lid. All sizes below are for interior dimensions. Color: black



Part No.	Size (L x W x H)	Price
3R18921	3.125" x 2.0" x 0.875"	\$1.95
3R18913	4.875" x 2.5" x 1.5"	2.75
3R18892	6.0" x 3.5" x 1.875"	2.49
3R18905	7.5" x 4.25" x 2.25"	3.25

### VECTOR PROTOTYPING BOARDS




3R37604

Prototyping boards with punched holes are convenient, economical tools for assembling circuit components — and cost effective alternatives to custom designs.

Part No.	Description	Size	Price
3R63221	Epoxy Glass PC Board	4.5 x 6.5.....	\$4.75
3R37604	Epoxy Glass PC Board	4.5 x 17.....	10.95
3R37621	Epoxy Glass PC Board	8.5 x 17.....	19.95
3R37612	Phenolic PC Board	4.5 x 17.....	7.95
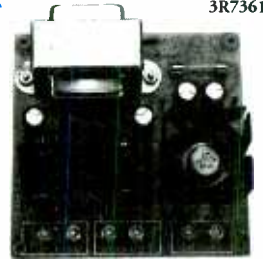
### REGULATED POWER SUPPLY KITS

Build the power supply you've been needing for years. Ideal for home or instructional use. Select from three different versions. Each kit is complete with printed circuit board, electronic components, and user assembly instructions.




3R37613

Part No.	Product No.	Input Voltage (VAC)	Output Voltage (VDC)	Current (mA)	Dimensions (L x W x H inches)	Price
3R20360	JE200	120	+5	1000	3.5 x 5.0 x 2.0	\$14.95
3R20626	JE215	120	+5 to +15 -5 to -15	750 to 175 750 to 175	3.5 x 5.0 x 2.0	19.95
3R37613	JE225	120	+5 fixed +3 to +12 -3 to -12	1000 100 100	5.12 x 5.12 x 2.25	29.95

See our Catalog for more kits

### Capacitors

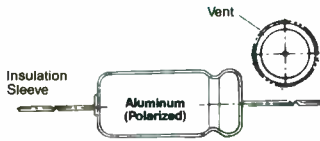

#### Axial Lead Electrolytic Capacitors

Part No.	Cap.	Volt.	Price
3R10866	1µF	50V.....	\$.15
3R10997	22µF	50V.....	.29
3R10911	100µF	50V.....	.29
3R11121	470µF	50V.....	.49
3R11033	2200µF	16V.....	.69



#### Mylar Capacitors

Part No.	Cap.	Volt.	Price
3R26833	.001µF	100V.....	\$.10
3R26884	.01µF	100V.....	.11
3R26956	.1µF	100V.....	.19
3R27001	1µF	100V.....	.69

### Linear ICs\*

Part No.	Product No.	Price
3R33241	TL082CP.....	\$.59
3R23579	LM317T.....	.65
3R23683	LM324N.....	.35
3R23771	LM336Z.....	1.09
3R23851	LM339N.....	.45
3R27422	NE555V.....	.29
3R24328	LM556N.....	.49
3R24467	LM723CN.....	.49
3R24539	LM741CN.....	.29
3R23131	LM1458N.....	.39
3R23157	LM1488N.....	.45
3R23181	LM1489N.....	.45
3R34278	ULN2003A.....	.69
3R24230	LM3914N.....	2.49
3R27385	NE5532.....	1.19
3R51262	7805T.....	.45
3R51334	7812T.....	.45

\* Name brand IC's in stock

### IC Sockets

Part No.	Product No.	Description	Price
3R51570	8LP	8-pin low profile.....	\$.10
3R37161	14LP	14-pin low profile.....	.11
3R37372	16LP	16-pin low profile.....	.12
3R39335	24LP	24-pin low profile.....	.19
3R40301	28LP	28-pin low profile.....	.22
3R41110	40LP	40-pin low profile.....	.28

### LEDs

Part No.	Product No.	Description	Price
3R34761	XC556G	T1 3/4, (green).....	\$.16
3R34796	XC556R	T1 3/4, (red).....	.12
3R34825	XC556Y	T1 3/4, (yellow).....	.16

### Transistors And Diodes

Part No.	Product No.	Description	Price
3R28628	PN2222	TO-92 case.....	\$.12
3R28644	PN2907	TO-92 case.....	.12
3R35991	1N4004	DO-41 case.....	.10
3R38236	2N2222A	TO-18 case.....	.25
3R36126	1N4735	DO-41 case.....	.25
3R38359	2N3904	TO-92 case.....	.12
3R36290	1N751	DO-35 case.....	.15
3R38421	2N4401	TO-92 case.....	.15
3R36038	1N4148	DO-35 case.....	.07
3R38308	2N3055	TO-3 case.....	.69



3R26622

3R21936

### Switches

Part No.	Product No.	Description	Price
3R21936	JMT123	SPDT, on-on (toggle).....	\$.15
3R38842	206-8	SPST, 16-pin (DIP).....	1.09
3R26622	MS102	SPST, momentary (push-button).....	.39

\* Additional components available

### Carbon Film 1/4 Watt 5% Resistors

Part No.	Ohms	Price	Part No.	Ohms	Price
3R29946	100	1.95/C	2R29911	10K	1.95/C
3R30867	330	1.95/C	2R30453	22K	1.95/C
3R29663	1.0K	1.95/C	2R29997	100K	1.95/C
3R30314	2.2K	1.95/C	2R29698	1.0M	1.95/C

Sold in packages of 100 pcs.

### 3/4 Watt Linear Taper-15 Turn Cermet Potentiometers

Part No.	Resistance Ω	Price
3R41785	1K	\$.99
3R41822	10K	.99
3R41849	100K	.99
3R41806	1MEG	.99



Order toll-free 1-800-831-4242

Call or write for your  
**FREE 1993 Annual Catalog:**  
1-800-637-8471



For International Sales, Customer Service, Credit Department and all other inquiries: Call 415-592-8097 between 7AM-5PM P.S.T.

CA Residents please add applicable sales tax.

#### \$30.00 Minimum Order

Terms: Prices subject to change without notice. Items subject to availability and prior sale. Complete list of terms/warranties is available upon request.

© 1993 Jameco 3/93 All trademarks are registered trademarks of their respective companies.

### Other Jameco Resources

- Test/Measurement and Prototyping Equipment
- Computer Upgrade and Accessory Products
- Full line of Integrated Circuits and Electronic Components
- Call for kit pricing


**JAMECO™**  
ELECTRONIC COMPONENTS  
COMPUTER PRODUCTS

1355 Shoreway Road  
Belmont, CA 94002

FAX: 1-800-237-6948 (Domestic)  
FAX: 415-592-2503 (International)



# FUN WITH ELECTRONICS

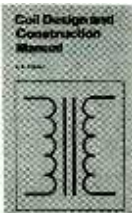

◀ **160—COIL DESIGN & CONSTRUCTION MANUAL** .... \$5.95. How to make RF, IF, audio and power coils; chokes and transformers. Practically every possible type is discussed.

◻ **PCP113—THE PC MUSIC HANDBOOK** .... \$13.95. Learn the basics of computer music systems. For the professional musician, gifted amateur or just plain curious.



◻ **BP297—LOUDSPEAKERS FOR MUSICIANS** .... \$6.25. Loudspeaker design from the musician's point of view! All you need to know, and you should be able to design your own after reading this.

◻ **BP277—HIGH POWER AUDIO AMPLIFIER CONSTRUCTION** .... \$6.25. Here's background and practical design information on high power audio amplifiers capable of 300±400 watts r.m.s. You'll find MOSFET and bipolar output transistors in inverting and non-inverting circuits.



◻ **BP302—A CONCISE USER'S GUIDE TO LOTUS 1-2-3 RELEASE 3.1** .... \$6.25. If you are a PC user and want to upgrade to Lotus 1-2-3 release 3.1, this book can teach you how to do that in the shortest and most effective way.

◻ **BP298—A CONCISE INTRODUCTION TO THE MACINTOSH SYSTEM AND FINDER** .... \$6.25. This introduction for those new to the Mac, this book also serves as a quick refresher for experienced owners that have not used the machine in some time.



MAIL TO: **Electronic Technology Today, Inc.**  
P.O. Box 240  
Massapequa Park, NY 11762-0240

### SHIPPING CHARGES IN USA AND CANADA

\$0.01 to \$5.00	... \$1.50	\$30.01 to \$40.00	\$5.50
\$5.01 to \$10.00	... \$2.50	\$40.01 to \$50.00	\$6.50
\$10.01 to \$20.00	... \$3.50	\$50.01 and above	\$8.00
\$20.01 to \$30.00	... \$4.50		

**SORRY, No orders accepted outside of USA and Canada**

Total price of merchandise	..... \$	_____
Shipping (see chart)	..... \$	_____
Subtotal	..... \$	_____
Sales Tax (NYS only)	..... \$	_____
Total Enclosed	..... \$	_____

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

# ADVERTISING INDEX

Electronics Now does not assume any responsibility for errors that may appear in the index below.

Free Information Number	Page
108	AMC Sales ..... 81
188	Active Surplus Electronics ..... 64
107	All Electronics ..... 95
185	B&K Precision ..... 13
98	B.I.—A Division of WaveTech .. 23
—	CIE ..... 21, 39
54	Chemtronics ..... 5
110	Cheneko Products ..... 84
—	Claggk Video Offer ..... 46
—	Command Productions ..... 81
127	Deco Industries ..... 84
125	Electronic Goldmine ..... 94
—	Electronic Tech. Today ..... 98
—	Electronics Book Club ..... 26, 45
121	Fluke Manufacturing ..... CV2
184	Global Specialties ..... 7
181	Goldstar Precision ..... 79
—	Grantham College ..... 17
176	Hewlett Packard ..... 3
—	HighText Publications, Inc. .... 81
177	ICS—Computer Training .... 89, 95
—	ISCET ..... 77
114	Jameco ..... 97
183	Mini Circuits ..... CV4
117	Mouser ..... 89
—	NRI Schools ..... 8, 96
182	Optoelectronics ..... CV3
179	People's College ..... 31
78	Radio Shack ..... 32
—	Star Circuits ..... 84
180	Tech Spray ..... 31
92	Tektronix ..... 14
178	The School Of VCR Repair ..... 77
187	U.S. Cable ..... 86
186	Zentek Corp. .... 86

**Gernsback Publications, Inc.**  
500-B Bi-County Blvd.  
Farmingdale, NY 11735  
1-(516) 293-3000  
**Larry Steckler, EHF/CET**  
President

**Christina Estrada**  
assistant to the President

**For Advertising ONLY**  
516-293-3000  
Fax 1-516-293-3115

**Larry Steckler**  
publisher

**Arline Fishman**  
advertising director

**Denise Mullen**  
advertising assistant

**Kelly McQuade**  
credit manager

**Subscriber Customer Service**  
1-800-288-0652

**Order Entry for New Subscribers**  
1-800-999-7139  
7:00 AM - 6:00 PM M-F MST

## ADVERTISING SALES OFFICES

**EAST/SOUTHEAST**  
**Stanley Levitan**  
Eastern Advertising  
1 Overlook Ave.  
Great Neck, NY 11021  
1-516-487-9357  
Fax 1-516-487-8402

**MIDWEST/Texas/Arkansas/Okla.**  
**Ralph Bergen**  
Midwest Advertising  
One Northfield Plaza, Suite 300  
Northfield, IL 60093-1214  
1-708-446-1444  
Fax 1-708-559-0562

**PACIFIC COAST**  
**Pamela Kuster**  
Pacific Advertising  
Pattis/3M  
1800 North Highland Avenue  
Suite 717  
Hollywood, CA 90028  
1-213-462-2700  
FAX 1-213-463-0544

**Electronic Shopper**  
**Joe Shere**  
National Representative  
P.O. Box 169  
Idyllwild, CA 92549  
1-909-659-9743  
Fax 1-909-659-2469



# ELIMINATES SEARCHING, SCANNING, TUNING INTERCEPTOR™

INTERCEPT, DETECT & CAPTURE  
Near Field Transmissions with  
Optoelectronics' New  
**INTERCEPTOR™**

## NEW TECHNOLOGY

- Follows & Locks on even when frequency changes.
- Intercepts ALL FM Two-Way Transmissions without gaps in coverage.
- Does Not have to tune through RF Spectrum to find signals.

### FCC Classified as Communication Test Instrument for:

- Deviation, FM, FMN
- Relative Signal Strength
- Signaling Tones (CTCSS)
- Modulation Monitor
- Great for testing VHF, UHF & Cellular transmitters

**A New Dimension in Recreational Monitoring – Intercept the Two-Way Communication that Surrounds You.**

**Increase Your RF Security.**



**Hand Held/Shirt Pocket Size**

**INTRODUCTORY OFFER**  
**Interceptor™ R10 FM Communications**  
 Interceptor (Includes NiCads, AC/Charger Adapter, Antenna, Earphone) ..... **\$359.**

#### OPTIONS

Headphones (Lightweight personal headphones).....	\$ 15.
Antenna Pak 2 (Five assorted rubber duck antennas – save \$32.).....	\$ 99.
TC200 Tone Counter (CTCSS signalling tones).....	\$ 179.
APS-104 (Extends RF detection distance 10x).....	\$ 995.
CF800 Cellular Band Pass Filter/Amplifier.....	\$ 299.

# OPTOELECTRONICS

FACTORY DIRECT ORDER LINE **1-800-327-5912**

305-771-2050 • FAX 305-771-2052 • 5821 NE 14th Ave., Ft. Lauderdale, FL 33334  
 5% Ship/Handling (Max\$10.) U.S. & Canada. 15% outside continental U.S. Visa & Master Card accepted

CIRCLE 182 ON FREE INFORMATION CARD

www.americanradiohistory.com



MADE IN THE U.S.A.

# TOUGHER SBL MIXERS

25KHz to 2000MHz  
from \$450

**ULTRA-REL™  
MIXERS**  
5-YR. GUARANTEE\*

Our tough SBL-mixers just got tougher, by including Mini-Circuits' exclusive Ultra-Rel diodes that can endure 160 hours of test at a scorching 300°C. Rugged, more reliable mixers in your systems lower production and test costs and increase systems reliability.

Over the past fifteen years, millions of SBL-units were installed in formidable industrial and commercial applications. Under severe operating conditions, they have earned the reputation as the world's most widely accepted mixers, based on quality, consistent performance in the field, and lowest cost.

In addition to the Ultra-Rel diodes, each SBL contains components that can withstand the strenuous shock and vibration requirements of MIL-STD-28837 along with more than 200 cycles of thermal shock extending from -55 to +100°C. Every Ultra-Rel™ SBL-mixer carries a five-year guarantee.

Unprecedented 4.5 sigma unit-to-unit repeatability is also guaranteed, meaning units ordered today and next year will provide performance identical to those delivered last year.

Tougher SBL-mixers, spanning 25KHz to 2000MHz, with +7dBm, +10dBm, and +13dBm LO models, priced from \$4.50 (10 qty) are available only from Mini-Circuits. Don't settle for a substitute or equivalent... insist on Ultra-Rel™ SBLs.

finding new ways ...  
setting higher standards

**Mini-Circuits**

P.O. Box 350166, Brooklyn, New York 11235-0003 (718) 934-4500 Fax (718) 332-4661 Telexes: 6852844 or 620156

CIRCLE 183 ON FREE INFORMATION CARD

www.americanradiohistory.com



#### SBL SPECIFICATIONS (typ.)

Model	Frequency (MHz)	Conv. Loss (dB)	Isolation (dB)		LO Level (dBm)	Price, \$ ea. (10 qty)
			L-R	L-I		
SBL-1	1-500	5.5	45	40	+7	4.50
• SBL-1X	10-1000	6.0	40	40	+7	6.25
SBL-1Z	10-1000	6.5	35	25	+7	7.25
SBL-1-1	0.1-400	5.5	35	40	+7	7.25
SBL-3	0.025-200	5.5	45	40	+7	7.25
• SBL-11	5-2000	7.0	35	30	+7	18.75
SBL-1LH	2-500	5.8	68	45	+10	5.50
SBL-1-1LH	0.2-400	5.2	64	52	+10	8.25
• SBL-1XLH	10-1000	6.0	40	55	+10	7.25
SBL-2LH	5-1000	5.9	61	54	+10	8.25
SBL-3LH	0.07-250	4.9	60	53	+10	8.25
• SBL-11LH	5-2000	7.0	45	30	+10	19.75
SBL-1MH	1-500	5.5	45	40	+13	9.80
SBL-1ZMH	2-1100	6.5	40	25	+13	11.70
• IF not DC coupled						

#### \*ULTRA-REL™ MIXERS 5 yr. Guarantee

with extra long life due to unique HP monolithic diode construction, 300°C high temp. storage, 1000 cycles thermal shock, vibration, acceleration, and mechanical shock exceeding MIL requirements

#### Designers Kit, KH-2

available only \$59.95 includes: 12 MIXERS covering DC to two GHz, 5 SBL-1, 5 SBL-1X, 2 SBL-11. 740 page RF/IF DESIGNER'S HANDBOOK Contains application notes using mixers as electronic attenuators, frequency doublers, switches, and bi-phase modulators.

F143 REV. ORIG.