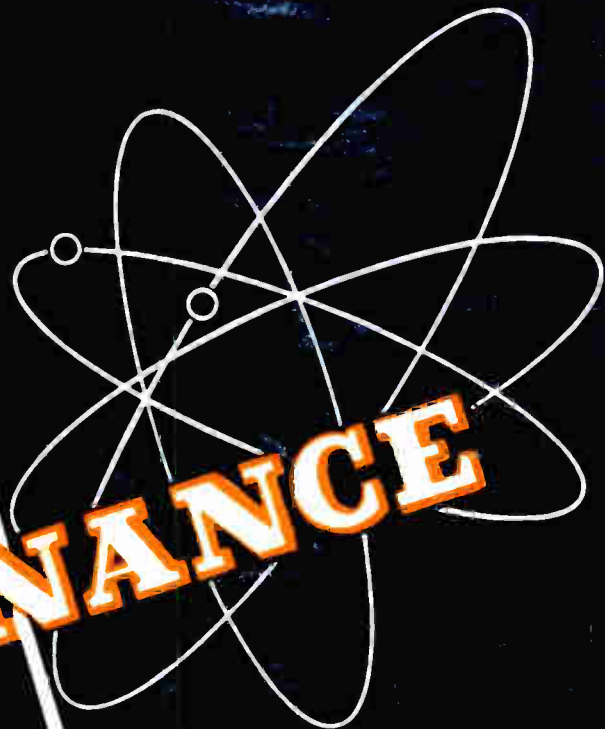


JANUARY 1948

35 CENTS

**EVERYTHING IN TELEVISION • RADIO • ELECTRONICS
FOR THE RADIO SERVICE • TECHNICIAN**

RADIO MAINTENANCE



**HOW TO IMPROVE
YOUR SIGNAL TRACING
TECHNIQUES**

**SPECIAL FM
CIRCUITS**

**WHAT'S NEW IN
VIDEO SECTIONS?**

YEARLY SUBSCRIPTION \$3.00

BOLAND & BOYCE INC., PUBLISHERS MONTCLAIR, N. J.

World Radio History

Quiet as a Moonbeam Falling on Velvet




It's Impossible to Hear a Mallory Control Operate!

Ultra-sensitive sound testing meters built for the U. S. Navy prove that the noise level of the Mallory control in operation is so low as to be totally inaudible!

Contact with the talcum-fine carbon element is made by a special Mallory Alloy that passes over it smoothly and silently.

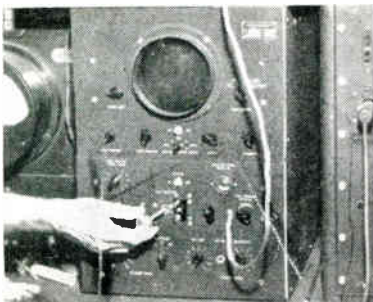You can use Mallory Volume Controls, Capacitors and Vibrators with complete confidence. They are carefully built to assure ease of installation and complete customer satisfaction. Mallory's standardized range of sizes and types makes the Mallory line a profitable line to stock.




Meter used in the noise level test. Readings were taken on volume controls of all leading manufacturers. Mallory controls gave no audible sound, registered 22% below all others in inaudible sound vibrations.

The things you look for in a control are low noise level, long life, accurate resistance values and smooth, uniform tapers. Competitive tests prove that Mallory leads the field on all four points!

"Good Service for Good Business"

A Mallory plan to build business for radio-electronic service shops.

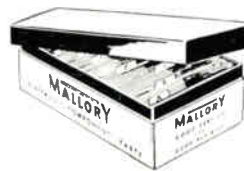There's a unique customer follow-up system that will produce repeat business. There's a close tie-in with the Mallory trade mark. Ask your distributor about it!



P. R. MALLORY & CO. Inc.
MALLORY

CAPACITORS . . . CONTROLS . . . VIBRATORS . . .
SWITCHES . . . RESISTORS . . . RECTIFIERS . . .
VIBRAPACK® POWER SUPPLIES . . . FILTERS

*Reg. U. S. Pat. Off.

APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO., Inc., INDIANAPOLIS 6, INDIANA

DOBLER BROS.
RADIO
SALES & SERVICE

A SIGN OF SUCCESSFUL *Servicing*

**DOBLER has all
16 RIDER MANUALS!**

"Successful radio servicing means fast servicing. Fast servicing means quick diagnosis. Quick diagnosis means access to dependable data. Dependable data suggests Rider Manuals. That's why we have all sixteen volumes," says R. W. Dobler of Dobler Bros., San Diego, Calif.

Three times a year Rider Manuals are published. Hundreds and hundreds of times a year they supply time-saving servicing information to each of the thousands upon thousands of men at the benches of Successful Servicing shops throughout the world.

This because nowhere else—nowhere else but in Rider Manuals, can be found the wealth of authoritative* radio service data needed to quickly diagnose the troubles in ailing American-made receivers issued since 1920. Here is all the material our "Seventeen Years of Continuing Service to the Servicing Industry" has proved necessary.

Rider Manuals keep pouring out profits for servicemen year after year. They're a sound investment. They're a sign of Successful Servicing. Your shop should have all sixteen. Order from your jobber today.

* Rider Manual data is the OFFICIAL AUTHORIZED servicing data right from the service departments of the companies that made the sets. No one knows better than the manufacturer what servicing procedures are best for his product. This is the basis for the authority and the success of Rider Manuals.

JOHN F. RIDER PUBLISHER, Inc., 404 Fourth Avenue, N. Y. 16
Export Agent: Rocke International Corp., 13 E. 40th St., N.Y.C. Cable ARLAB

RIDER MANUALS

MEAN SUCCESSFUL SERVICING

YOU NEED ALL 16

- Volume XVI . . . \$ 6.60
- Volume XV . . . 18.00
- Volumes XIV to VII (ea. Vol.) . . 15.00
- Volume VI 11.00
- Abridged Manuals I to V (one volume) 17.50
- Record Changers and Recorders . . . 9.00
- Master Index, covering Rider Manuals, Vols. I to XV 1.50

**PUT THIS OVER
YOUR BENCH TODAY!**

VOL. XVI
768 Pages
PLUS SEPARATE
'HOW IT WORKS'
BOOK
\$6.60




Vol. XVI contains data from 94 manufacturers—a greatly increased percentage of "clarified-schematics"—a generous number of photographs on small table models and a separate "How It Works" book, in addition to the usual authoritative information you have come to depend upon in previous Rider Manuals—and this is made available to you in Volume XVI at the greatest possible economy; less than a penny a page. Get it from your jobber today!

24 HOUR DATA SERVICE

On November 30, 1947 we instituted our new photostat service to supply you with information on any newly issued, or old, receivers. For 10c (stamps are OK) we will send you the schematic, voltage data and parts list and everything else which will fit on the two pages. Additional manufacturers' data is 5c a page with a maximum charge of 35c for everything up to seven pages. If the manufacturers' data requires more than seven pages, each additional page is 3c. Here is a way to get whatever service data you need between Rider Manual publication dates.

ADDING FURTHER WEIGHT TO THE VALUE OF OUR "SEVENTEEN YEARS OF CONTINUING SERVICE TO THE SERVICING INDUSTRY"

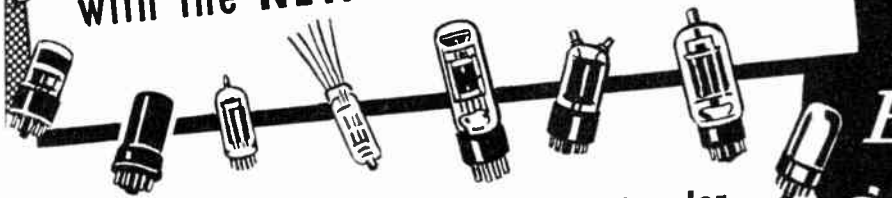Protect Your Tube Testing Investment
with the **NEW** Precision Series 10-12



Unparalleled and highest practical order
of obsolescence insurance — thru use of
the Precision 12 element, free-point
Master Lever Selector System.

**Truly
free-point
Electronamic*
Tube
Master**

REG. PEND.
U. S. PATENT OFFICE




Testing a tube for just one selected characteristic does not necessarily reveal its overall performance capabilities. Electronic tube circuits look for more than just Mutual Conductance or other single factor. In the Precision MASTER Electronamic Tube Test Circuit, the tube under test is subjected to appropriately phased and selected individual element potentials and is electro-dynamically swept over a complete Path of Operation, on a sinusoidal time base. Encompassing a wide range of plate family characteristic curves, this complete Path of Operation is automatically integrated by the indicating meter in the positive, direct and non-confusing terms of Replace-Weak-Good.

Compare These Features

THE NEW SERIES 10-12 TUBE MASTER

- ★ The POSITIVE solution to tube PERFORMANCE testing plus optimum anti-obsolescence insurance
- ★ Direct facilities to 12 element prongs
- ★ Filament voltages from 75 to 117 volts.
- ★ Tests the new Noval 9 pins, 5 and 7 pin acorns; double-capped H.F. amplifiers; low power transmitting tubes; single-ended F.M. and TV amplifiers etc. REGARDLESS of FILAMENT OR ANY OTHER ELEMENT PIN POSITIONS.
- ★ ISOLATES EACH TUBE ELEMENT REGARDLESS OF MULTIPLE PIN POSITIONS
- ★ DUAL (HIGH-LOW) short check sensitivity for special purpose tube selection.
- ★ INDIVIDUAL TESTS OF MULTI-SECTION TUBES including F.M. and A.M. cathode-ray tuning indicators.
- ★ Simple, direct Ballast Unit Tests.
- ★ Battery Tests under dynamic load conditions.
- ★ Built-in Double Window, brass-gear roller chart.
- ★ 4½" Full Vision Meter, 1 MA sensitivity.
- ★ Panel-Mounted Extractor Fuse Post.

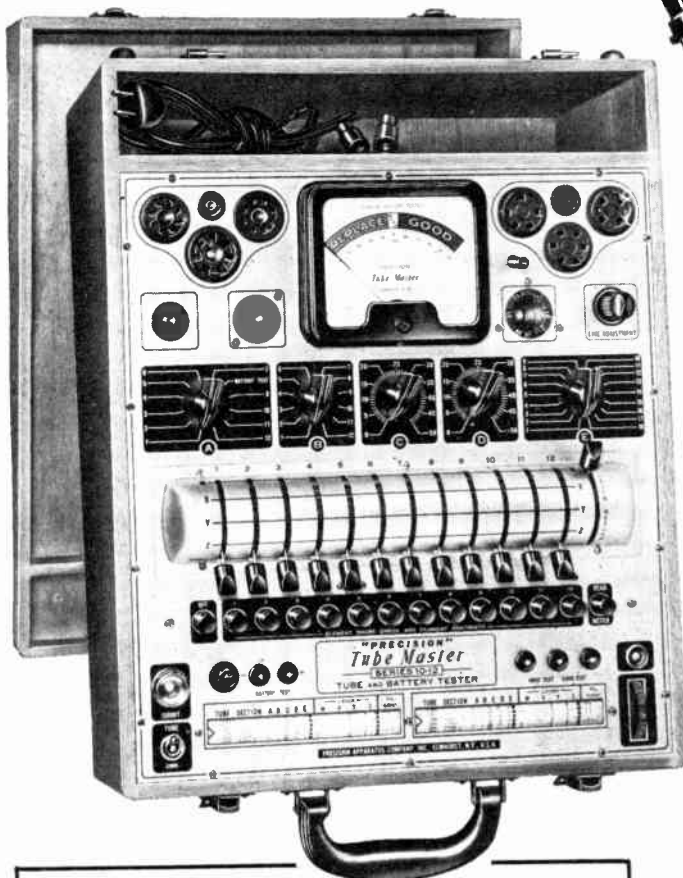

MODEL 10-12-P; (illustrated) in sloping, portable hardwood case with tool compartment and hinged removable cover. Size 13¾ x 17¼ x 6¾" ————— **\$86.15**
Also available in modern counter and standard rack-panel mountings.

Ask to see the new "Precision" Master Electronamic Test Instruments now on display at all leading radio parts and equipment distributors, or write directly for the new Precision 1948 catalog fully describing the Precision Electronamic tube performance testing circuit.



PRECISION
APPARATUS COMPANY INC.
92-27 HORACE HARDING BOULEVARD
ELMHURST 5, NEW YORK

Export Division: 458 BROADWAY, NEW YORK CITY, U. S. A. • Cables: MORHANEX

RADIO

MAINTENANCE

INCLUDING
ELECTRONIC
MAINTENANCE



Volume 4

JANUARY 1948

Number 1

Contents

| | | |
|--|------------------------|-----------|
| How to Improve Your Signal Tracing Techniques Some helpful pointers | Irving Dlugatch | 4 |
| Special FM Circuits New circuits found in FM receivers | Milton Kaufman | 8 |
| What's New in Video Sections? New developments in video IF amplifiers | Morton Scheraga | 12 |
| Simple FM Converter Will Make You Money Conversion from old to new bands | | 18 |
| Electronically Speaking News of the industry | | 16 |
| Industry Presents New products | | 26 |
| The Notebook Practical suggestions from readers | | 30 |
| Review of Trade Literature Catalogs, books, etc. | | 33 |
| Over the Bench A Serviceman's Opinion | John T. Frye | 35 |
| The Organizations News of group activities | | 37 |

WILLIAM F. BOYCE
Publisher

PAUL WENOEL
Business Manager
Advertising

STUART J. OSTEN
Midwestern Advertising
Manager

Eastern Advertising Office
460 Bloomfield Ave.,
Montclair, N. J.
Tel.: Montclair 2-7101

JOSEPH J. ROCHE
Editor

J. RICHARD JOHNSON
Managing Editor

A. J. POLHEMUS
Assistant Editor

VICTOR M. TURNER
Art Director

MORTON SCHERAGA
Contributing Editor

THOMAS A. BYRNES
Director Of Field Services
And Quality Control

AL JOHNSTON
Circulation Manager

FRANK VAN SEETERS
Circulation

Midwestern Advertising
Office
228 No. La Salle St.
Chicago, Ill.
Tel.: Dearborn 3507

Copyright 1947, Boland & Boyce, Inc.


Radio Maintenance is published monthly by Boland & Boyce, Inc., at 34 No. Crystal St., East Stroudsburg, Pa., U.S.A.; Executive and Editorial Office, 460 Bloomfield Ave., Montclair, N. J. Subscription Rates: In U. S., Mexico, South and Central America, and U. S. possessions, \$3.00 for 1 year, \$5.00 for two years, single copies 35 cents; in Canada, \$3.50 for 1 year, \$6.00 for 2 years, single copies 40 cents; in British Empire, \$4.00 for 1 year, \$7.00 for 2 years, single copies 50 cents; all other foreign countries, \$5.00 for 1 year.

Change of address: Four weeks' notice required for change of address. When ordering a change, please furnish an address stencil impression from a recent issue if you can. Address changes cannot be made without the old stencil as well as the new one.

RADIO MAINTENANCE • JANUARY 1948

HIGHER VOLTAGE

ELECTROLYTICS

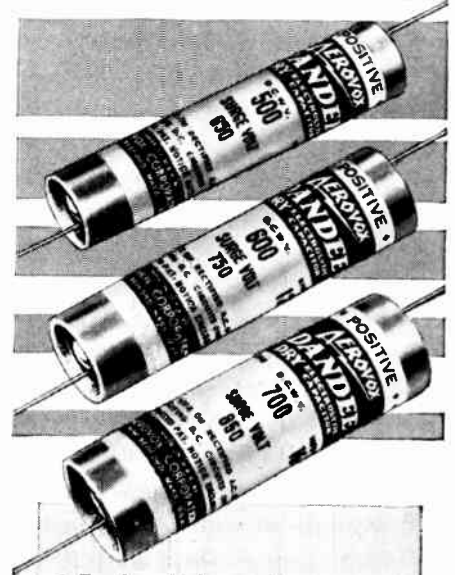

• For those higher working voltages—particularly television receivers, oscillographs and other latter-day electronic circuits—with high capacitance values for filtering or by-passing—Aerovox has the answer:

Popular Aerovox Type PRS Dandees are now available in extended D. C. working voltages of 500, 600 and 700 D. C. W., or 650, 750 and 850 surge. Capacitance values are 8, 10, 12 and 16 mfd.

And of course the tried-tested-proven Dandee construction: hermetically-sealed aluminum can; waxed paper jacket; spun-over ends eliminating "shorts"; bare pigtail leads that won't work loose.

• See Our Jobber . . .

These extended-voltage Dandees are being stocked. Our jobber can supply them. Order your requirements NOW.



**FOR RADIO - ELECTRONIC AND
INDUSTRIAL APPLICATIONS**

AEROVOX CORP., NEW BEDFORD, MASS., U.S.A.
Export: 13 E. 40th St., New York 16, N.Y. • Cable: 'ARLAB'
In Canada: AEROVOX CANADA LTD., Hamilton, Ont.

How to improve your SIGNAL TRACING techniques



by
Irving Dlugatch

**Tracing instruments
can be most profitable
if thoroughly understood**

THE service technician has for some time found the signal tracer a valuable aid in his business. Recent advances in equipment design are increasing the scope of this servicing approach. By keeping up to date about signal tracer problems the serviceman will find extra opportunities for efficiency and greater profits. In the following discussion, we will consider some of the problems involved in signal tracing and how to solve them.

Past and present methods of troubleshooting both consist of (1) localization of the trouble, (2) identification of the defective part. The localization can be done either by *static* or *dynamic* methods. In static systems we check operation by meter readings. In dynamic testing, we trace the course of an actual signal through a receiver, thus locating the point at which the signal stops.

Oddly enough, the first dynamic signal tracing was introduced by the so-called "screwdriver mechanics" who had very little equipment. The procedure they used is to touch the grid of each tube and listen for the resulting click in the loudspeaker. The first grid that gives no click indicates a defective stage. Tubes without grid caps and present day high voltages make this system less practical. Also, this

method cannot measure stage gain, test superhetrodyne oscillators, or any other special circuits.

Static Methods

As the use of testing meters increased, we turned to static troubleshooting. Early receivers were simple and adapted to multimeter servicing. Meter servicing means we must test at every socket until the fault is located. Results often depend on the amount of information we have from the manufacturer. Many troubles do not show up on voltage or resistance tests. Open coupling condensers, open bypass condensers, shorted coils, and low capacity filter condensers are hard to find with the multimeter.

The "point to point" system of testing is also a static type. It calls for measuring the resistance be-

tween tube socket terminals and the chassis, B plus or any other convenient point and comparing with factory data. This method is not very useful because it requires full data on resistance values. These data are not usually available.

Dynamic Testing

Dynamic signal tracing "arrived" with reliable signal generators. Now, instead of the audio click supplied by the serviceman's finger at a tube grid, we can feed a modulated signal of the correct frequency into a receiver at any point. We can tell where the signal stops and then proceed to find the defective part with a meter. Defective coils, interstage transformers, tubes, and coupling condensers can be quickly located.

We can use signal generator output to check for oscillator trouble. To do this: Break the circuit at point A (See Fig. 1) and connect the output of the signal generator between point B and ground. Stage gain can be checked by comparing the strength of the signal when the generator is fed into the stage output and input circuits respectively. An output meter is desirable for this purpose; but, in any case, watch out for AVC effects!

Dynamic testing with just a signal generator has limitations. It

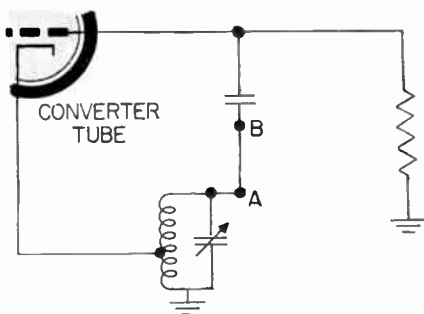


Fig. 1 A signal generator substituted for the local oscillator can be used to check for oscillator failure. The wire between A and B is broken and the signal generator connected to those points.

won't often find the causes of distortion, hum or noise. The selection of the proper frequency and modulation slows down the process of troubleshooting. The overloading of tubes which occurs with excessive signal may give confusing results.

Tracing Equipment

The first signal tracing equipment especially designed for the purpose was the Rider Chanalyst which is a tuned signal tracer (see Fig. 2). A special probe is connected to an untuned amplifier followed by three stages of tuned RF amplification. These stages have a flat response over the broadcast band. A detector, followed by a 6E5 "eye" tube indicates signal strength. Sufficient gain is available to observe minute signals from a test oscillator or from a station on the air. Separate circuits are provided for audio amplifier and oscillator checking so the signal can be "watched" at more than one point at the same time. Power supply operation can also be checked. A tuning eye watt meter shows power drain and a DC voltmeter monitors the plate voltage. The serviceman can thus find intermittents as they happen. Fig. 3 illustrates by block diagram how this is accomplished.

Signal tracers which use untuned amplifiers are now available at low cost. This type has the advantage of speed and ease of operation. Since no tuning is necessary, the same probe can be used anywhere in the receiver. But there is no multichannel feature which makes the Chanalyst so useful for finding intermittents. Tuned and untuned tracers have the common disadvantage of requiring an external signal source. On the other hand, using a signal generator for signal tracing does not eliminate the necessity for an output indicator. The signal tracer is in effect a sensitive output indicator. A complete shop must include a signal generator and a signal tracer.

Requirements

It is important that you understand the signal tracer you use and realize its limitations. The requirements of a good signal tracer can be listed as follows:

1. Connecting the instrument to the receiver should not detune, load

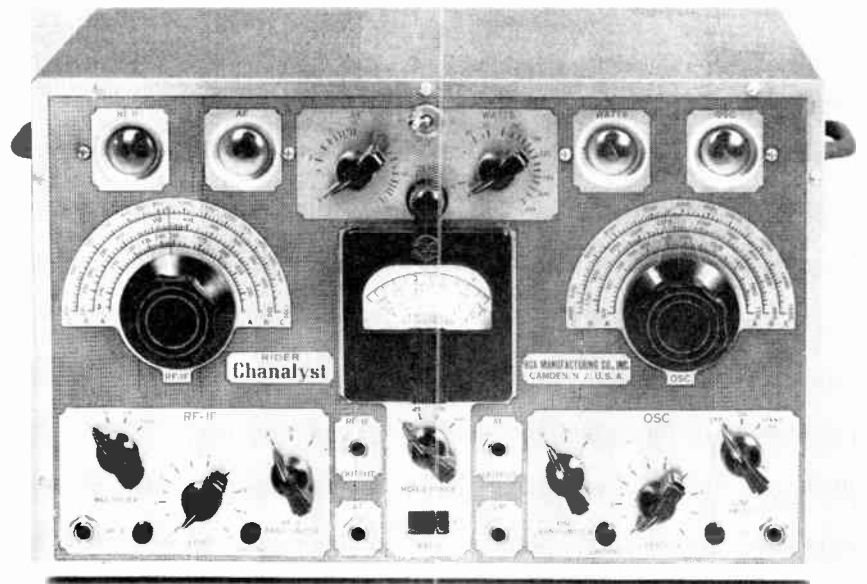


Fig. 2 The Rider Chanalyst is an example of the tuned multichannel type of tracer.

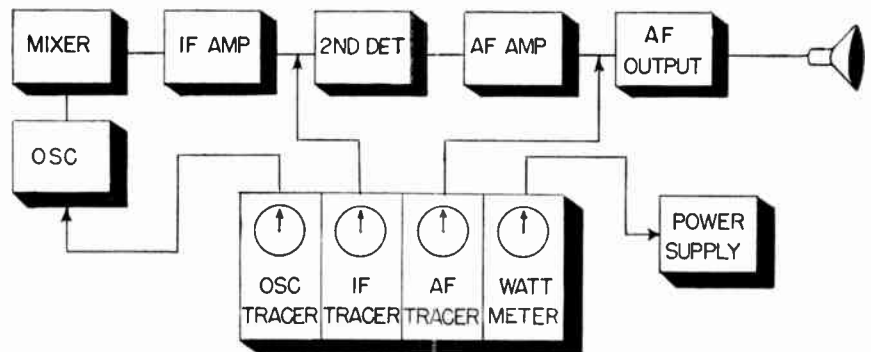


Fig. 3 How the Chanalyst is used to localize intermittents in a superheterodyne receiver.

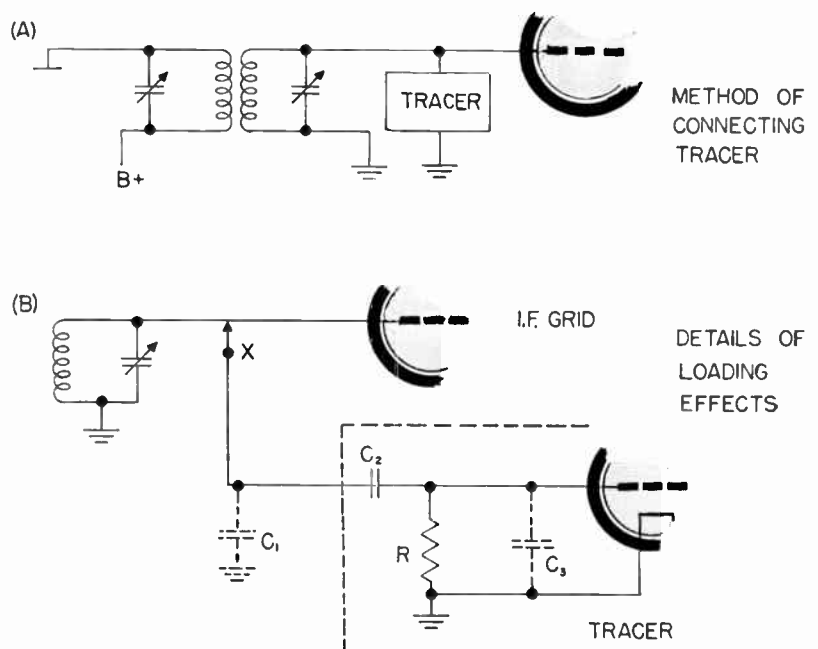


Fig. 4 How the tracer is connected to an IF stage and its effect on the circuit. A, where to connect tracer; B, details of loading effects.

or otherwise affect the operation of the receiver.

2. The gain of the tracer should be sufficient to permit its use with extremely weak signals.

3. The tracer should have a sensitive signal strength indicator.

4. It should provide means for listening to the signal.

Suppose we connect the input lead of the tracer across the secondary of an IF transformer as in Fig. 4A. The result will be as though

a capacitor were placed in parallel with the tuning condenser. Increasing the capacity lowers the frequency to which the secondary is tuned and reduces the signal. It is the same effect you get when aligning receivers if your hand is placed close to the coil being tuned or you are using a metallic screwdriver to adjust trimmers.

Fig. 4B shows in detail what is taking place. C1 is the capacity between the test lead and the chassis.

The use of shielded cable may increase this capacity considerably. C3 is the input capacity of the tracer's amplifier tube, and depends on what tube is used. R is the grid resistor shunted by the input resistance of the tube. We have C2 in series with C3; this combination is in parallel with C1 and detunes the transformer. The effect of R is to reduce the Q of the circuit, thus reducing the signal further. By making C2 small, the effect of C3 is made negligible, but C1 can only be offset by the use of special probes.

Reducing Capacity Effects

The probe illustrated in Fig. 5A is one means of reducing the effect of C1 (Fig. 4B) since the isolating condenser will be in series with C1 when placed in the circuit at point X in Fig. 4B. Being small in value and placed right at the tip of the probe, it offsets hand capacity introduced in holding the probe. The small value of capacity (large reactance) cuts down the amplitude of the signal carried by the test lead; and, therefore, prevents feedback by induction from the lead to receiver wiring. Otherwise even with shielded wire, high signal levels can introduce feedback. Further reduction of the signal can be obtained by holding the probe near the terminal without touching it. At audio frequencies, the input capacity of the tracer offers a high impedance and there are no detuning effects.

Probe leads which carry RF current are inefficient and radiate too much. That's why the detector probe was developed. This type of probe changes modulated RF to AF; detection takes place right in the probe. The shielded lead then carries only audio frequency currents. A typical probe for use in testing high frequency circuits is shown in Fig. 6.

Fig. 5B shows one type of probe containing a grid leak detector. The tube used is a 1T4 pentode, connected as a triode. A probe of this type is used in the Feiler "pocket stethoscope" shown in Fig. 7. Another tracer with a detector probe is illustrated in Fig. 8.

The response of vacuum tube probes is usually flat to about 10 mc; above this frequency, the output drops off. This makes them

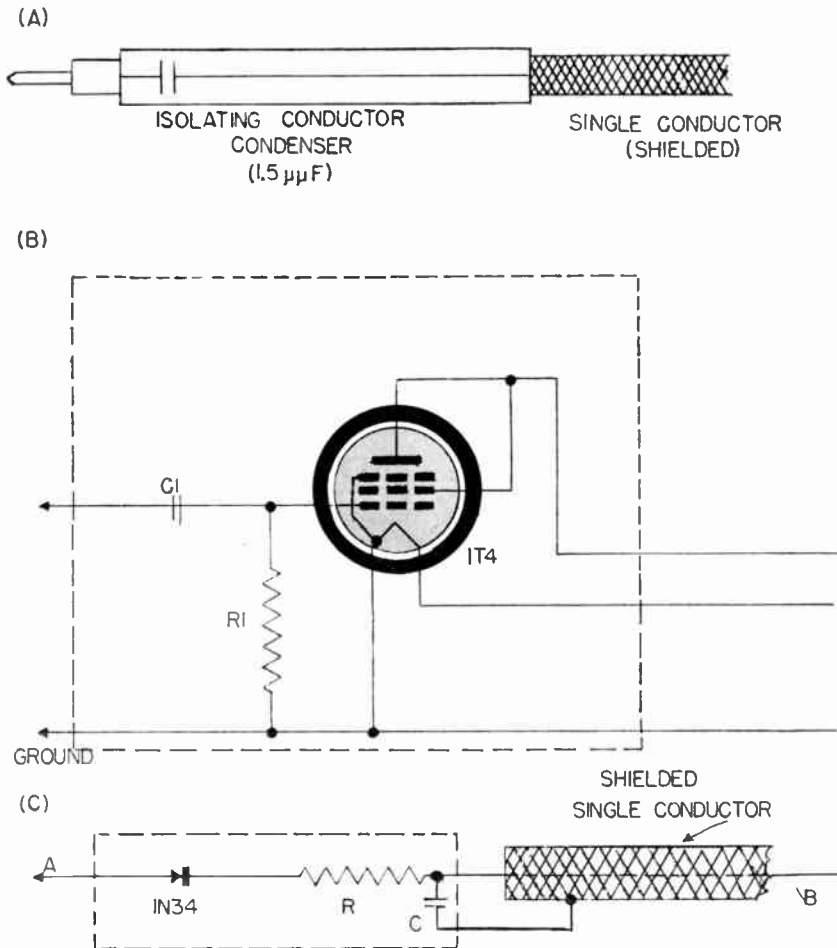


Fig. 5 Three types of probes used in signal tracers. A, capacity type; B, tube detector type; C, Germanium crystal type.

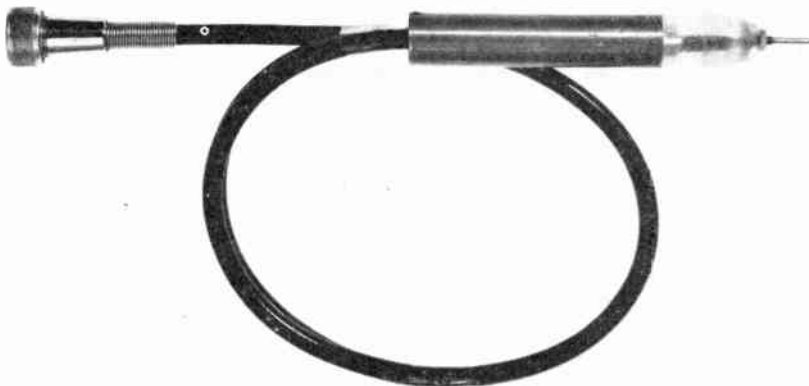


Fig. 6 A high frequency probe used with Jackson signal tracers.

unsuitable for signal tracing in modern FM and television receivers. While high frequency tubes are available, a much simpler substitute is the germanium crystal "diode."

Crystal Probes

Those of us who have used crystal sets are familiar with the galena crystal detector. Its ability to pass current readily from the cat's-whisker to the crystal, but not so easily in the reverse direction, makes it suitable as a detector. During the war, the crystal detector became valuable in high frequency work; and, therefore, its development was speeded. The germanium crystal detector is the result. The construction of a 1N34 germanium crystal is shown in Fig. 9A, and its equivalent electrical circuit in Fig. 9B. C1 is the capacity of the crystal's container. L is the inductance of the whisker used to make contact with the crystal. The whisker is necessary to maintain constant pressure on a small area. C2 is the capacity between the anode and cathode of the "diode." R1 and R2 are equivalent series and parallel resistance of the crystal respectively. Some representative values are:

C1 — 0.4 mmf

L — 0.01 mh

R1 — 10 ohms

R2 and C2 depend on the voltage and frequency, but C2 may be around 2 mmf.

From the above, it is apparent that the crystal does not introduce any serious capacity effects. The 1N34 can be used to over 200 mc. Being no larger than a 1 watt carbon resistor, it is especially suited for use in a signal tracer probe. The circuit is shown in Fig. 5C. Since there is no heater voltage needed, the probe cable is reduced to a single shielded conductor. R is needed to reduce loading while C is to prevent RF from getting through. In using it, a complete DC path must be provided between points A and B. From B to ground, the grid resistor of the tracer amplifier will act as a "diode" load. From A to ground, there must be a DC return in the circuit under test. The crystal does not amplify the signal as does the 1T4; therefore additional gain must be available in the tracer amplifiers.

An important characteristic of a signal tracer is its sensitivity. The

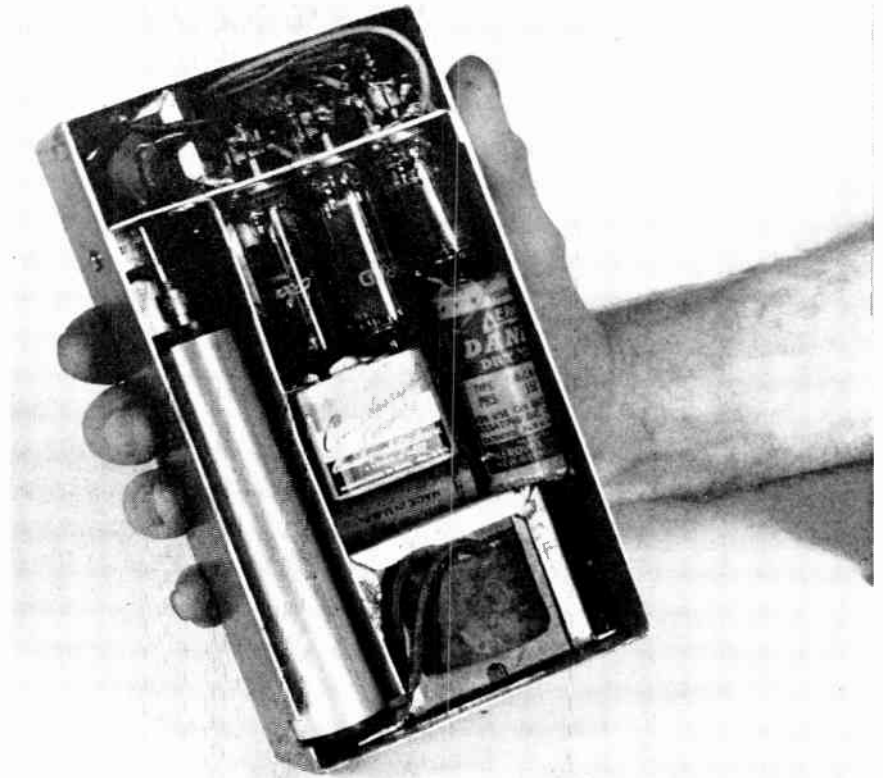


Fig. 7 Internal view of the Feiler "pocket stethoscope."




Fig. 8 A Radio City Products tracer which uses a detector probe.

HF voltage output of a converter may vary from 150 to, say, 1000 microvolts. Sufficient tracer gain must be provided to give a good meter reading. You cannot test parts of a receiver in which even normal signals do not produce an indication. A tracer with a gain of 300 or better will usually produce results even with weak broadcast stations. When crystal or diode de-

tectors are used, there is no gain in the detector and the rest of the tracer must be that much more sensitive. Of course, with high gain, the usual care in shielding and decoupling is necessary.

A high gain tracer can test antenna coils or loops. If the tracer is across the primary, no signal, but a loud hum, indicates an open.

→ To Page 22

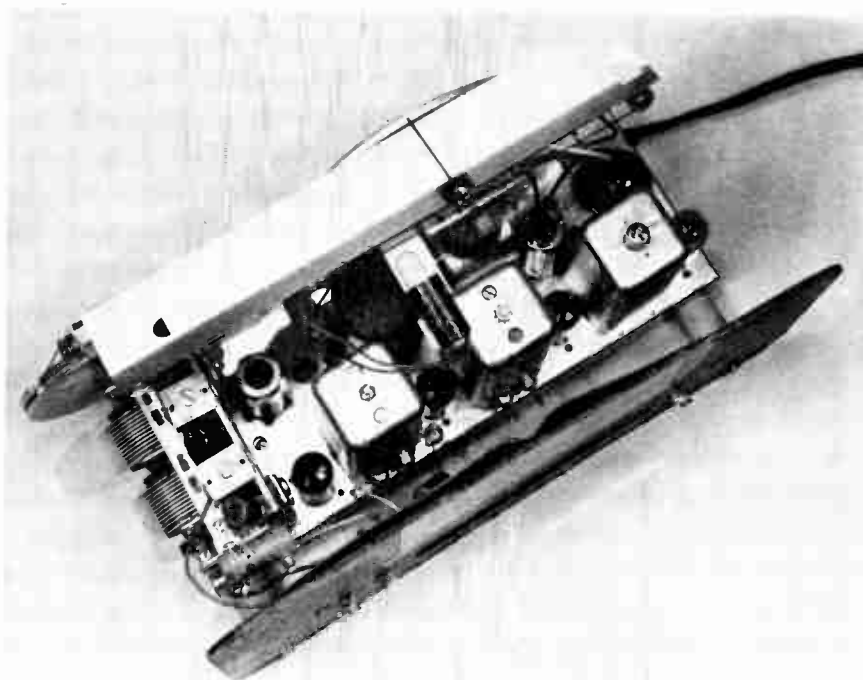

New and different circuit ideas are incorporated in the latest FM receivers

SPECIAL FM CIRCUITS

by Milton Kaufman

A SPECIAL circuit designed by G. L. Beers for FM detection is known as the "Locked-In" oscillator. Advantages of this system are: (1) a substantial improvement in selectivity over conventional circuits, (2) an output which is free of amplitude variations when the input voltage is from about .5 to 1 volt and (3) a voltage step up of approximately 20 under weak input signal conditions.


A block diagram of this system is shown in Fig. 1. Here it is seen that the conventional limiter-discriminator combination is replaced by the Locked-In oscillator and reduced range discriminator respectively. The basic operation is as follows: In the second detector, a local signal is provided by an oscillator which is operating continuously and at a constant amplitude. After the received signal has been selected and amplified by the RF and IF amplifiers, it is applied to this oscillator. This causes the oscillator frequency to change in accordance with the incoming signal. The frequency at which the oscillator locks in with the received signal is equal to 1/5 of the IF.

Thus in a receiver using a 10.7 mc IF, the oscillator locks in at 10.7 divided by 5 or 2.14 mc. In this way the maximum frequency deviation is reduced from plus and minus 75 kc to plus and minus 15 kc. It should be noted that this does not change the *modulation frequency* in any respect. The oscillator is designed to lock in only with frequency deviations occurring within the desired signal channel. It is this feature which provides the improvement in selectivity by preventing the oscillator from following frequency deviations on an adjacent channel.

A simplified schematic of this system is shown in Fig. 2. As-

suming an intermediate frequency of 10.7 mc, the oscillator plate tank circuit, L3-C3 is tuned to 1/5 of this or 2.14 mc. With no signal input, this circuit will function as a normal oscillator at 2.14 mc, and at this center frequency the discriminator output will be zero. Because the amplitude of oscillations is rather large, the tube is driven into the cut off and saturation regions of its characteristic. The oscillator operates at class "C" bias which is established by No. 3 grid drawing current on the positive swings of the oscillations. This bias is maintained by the combination of R1 and C4. Since the tube operates class "C," the plate current flows in

Fig. 1. Block diagram of an oscillator detector receiver.

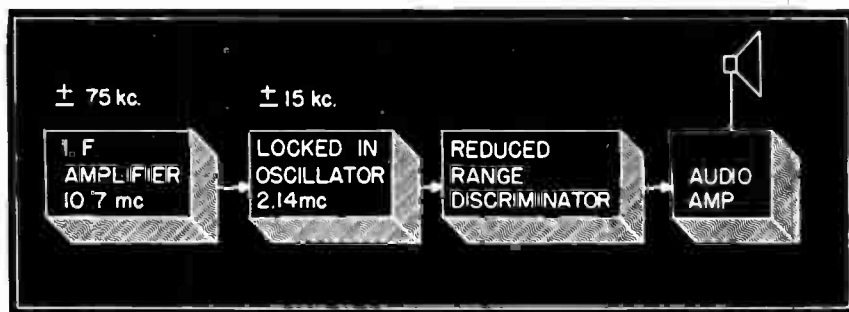

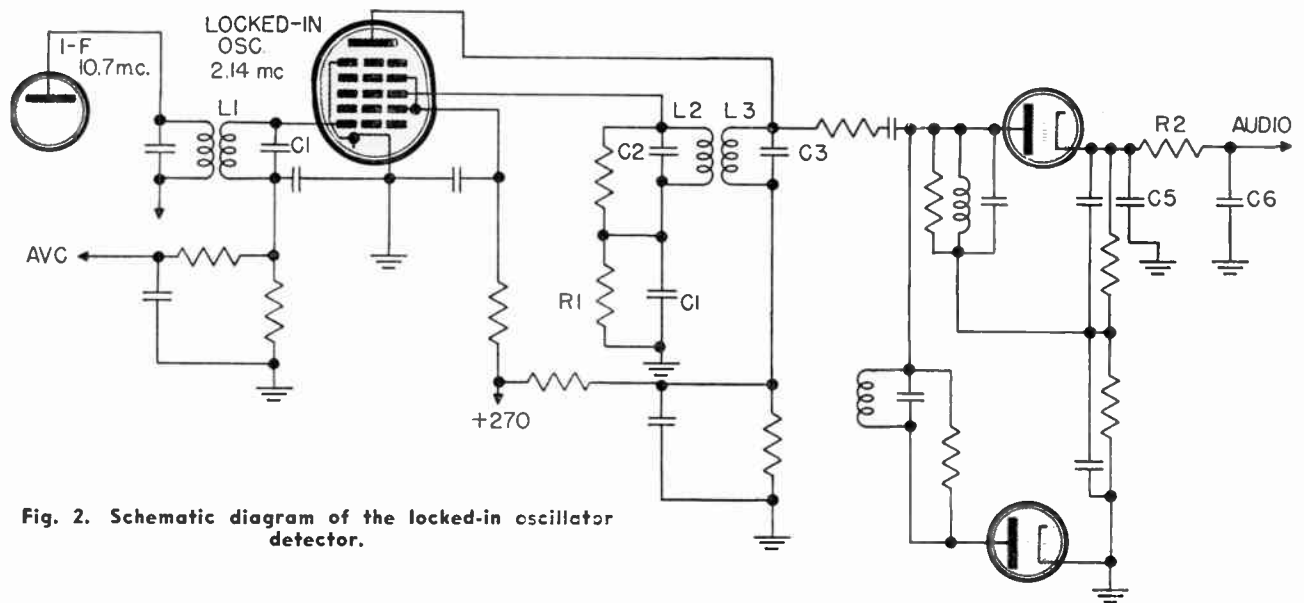


Fig. 2. Schematic diagram of the locked-in oscillator detector.

short pulses. The pulses not only contain the fundamental frequency of 2.14 mc, but also the 2nd, 3rd, 4th, 5th, etc., harmonics of 2.14 mc. The grid tank circuit L2-C2 is tuned to the second harmonic of the oscillator or 4.28 mc. This is done in order to increase the range of frequencies to which the oscillator will lock in and to accentuate the even harmonic (2nd, 4th, etc.) output of the oscillator.

If an input signal of 10.7 mc is now applied to the No. 1 grid, the tube will act as a mixer and combination frequencies will be produced. However, it must be remembered that the plate circuit L3-C3 is tuned to 2.14 mc, and this is the only frequency which will be amplified. All other frequencies will be effectively by-passed. This means that in order to have an output frequency of 2.14 mc due to the mixing process, the incoming 10.7 mc signal must beat against either the 4th or 6th harmonic of the oscillator.

4th harmonic = 8.56 mc
 10.7 minus 8.56 = 2.14 mc
 6th harmonic = 12.84 mc
 12.84 minus 10.7 = 2.14 mc

This additional 2.14 mc component caused by the incoming signal beating against the 4th or 6th harmonic of the oscillator is in phase with the original 2.14 mc oscillation. Therefore, the incoming 10.7 mc will lock in the 2.14 mc of the normal oscillations, and the only result will be an increased output from the plate circuit. If the incoming signal deviates above

the center frequency to a maximum of 10.7 mc plus 75 kc or 10.775 mc, the oscillator will lock in at 1/5 of this frequency of 2.14 mc plus 15 kc. Similarly the oscillator will follow the incoming signal toward the low frequency deviation of 2.14 mc minus 15 kc.

Thus a deviation of plus and minus 75 kc is reduced by the Locked-In oscillator to plus and minus 15 kc. The use of a reduced range discriminator operating at a much lower frequency than the IF permits greater adjacent channel selectivity.

De-emphasis

In a previous article it was stated that most of the noise present in FM systems is concentrated in the higher audio frequency range and to help overcome this noise, a pre-emphasis network is used at the transmitter. By this means, the higher audio frequencies are amplified to a greater degree than the lower audio frequencies. At the receiver, therefore, it is necessary to incorporate a de-emphasis network which will have the opposite effect and serve to bring the highs

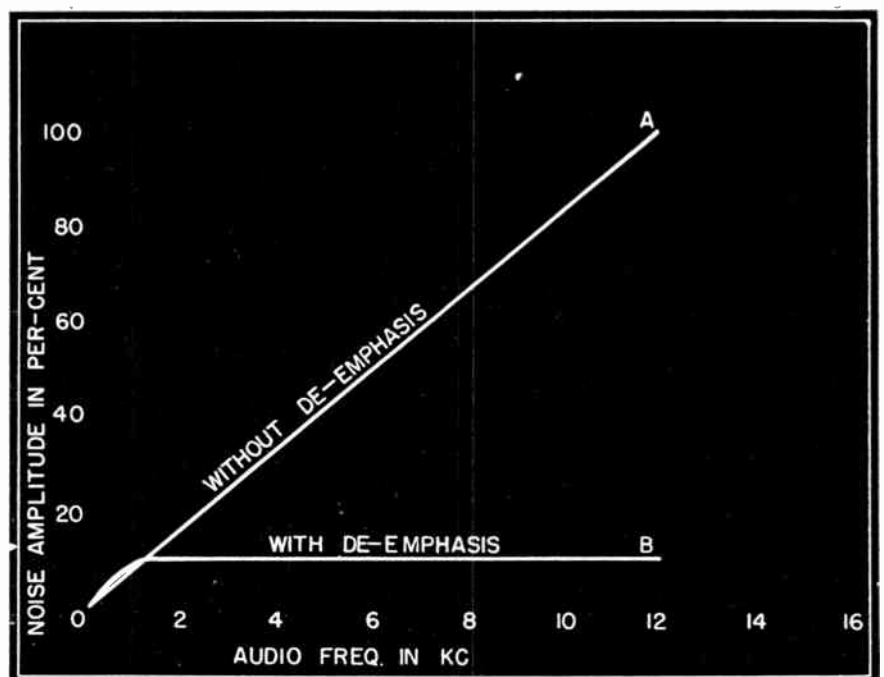


Fig. 3. Effect of de-emphasis on receiver noise content.

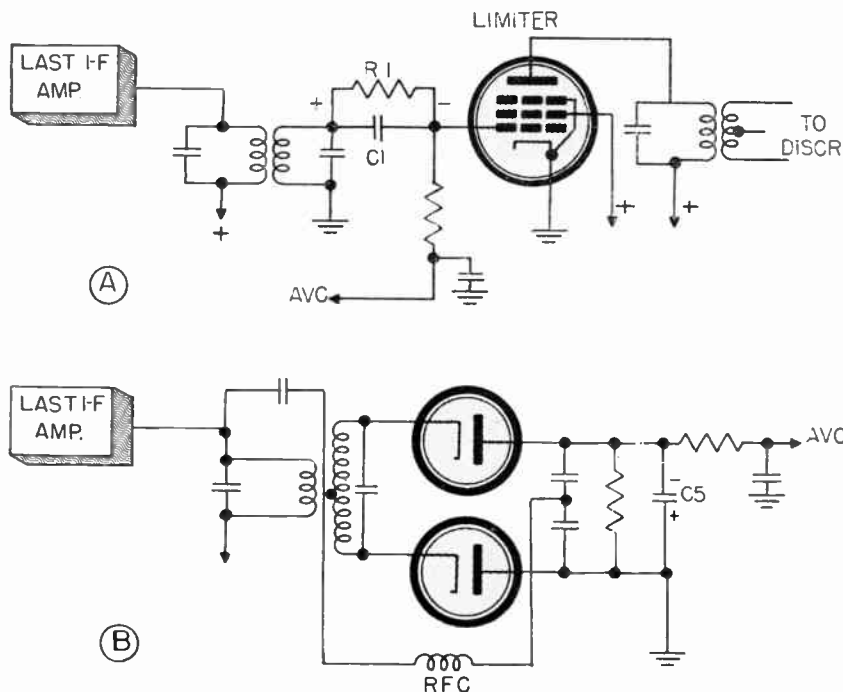


Fig. 4 How AVC is obtained in FM receivers.

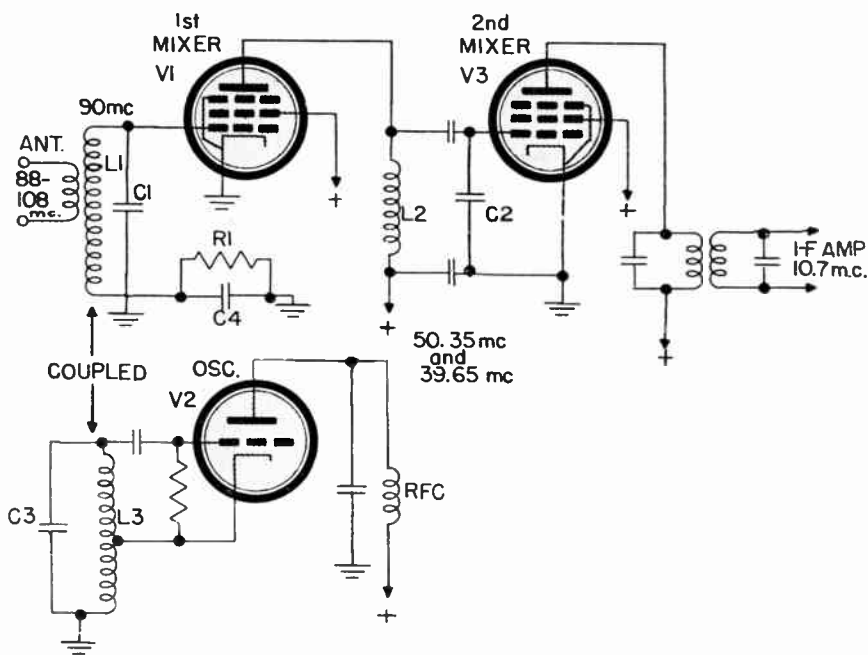


Fig. 5 Double superheterodyne circuit.

down to the proper level with respect to the low frequencies. Such a network is made up of an RC combination and may be identified in Fig. 2 as R2, C5, C6. The de-emphasis network must have the same time constant as the pre-emphasis network, and this is at present standardized at 75 μ s for FM broadcasting. With capacitors C5 and C6 connected across the audio output to ground the higher audio frequencies will be partially

by-passed and thus attenuated to the proper degree. The graph of Fig. 3 shows the effect of the de-emphasis circuit on high audio frequency noise components. By reference to curve "B," it is clearly seen that the use of de-emphasis reduces the noise level at 15,000 cycles to 1/10 of its original value.

AVC in FM

It might be thought that since all amplitude variations are removed

from the FM wave before or during detection, it is not necessary to provide any AVC action for the receiver. All signals exceeding a certain minimum strength will be held to the same amplitude, thus preventing fading. However, the use of AVC is desirable, because first, AVC aids in keeping interference bursts below a certain critical level at each AVC controlled tube grid. These interference bursts may become phase modulated by changing the tube input capacitance and will be detected and heard. AVC also reduces the possibilities of cross modulation of an FM signal by noise in the first stages of the receiver. The method of obtaining AVC control voltage will depend entirely upon the detection and limiting system used.

Two methods of obtaining AVC control voltage are illustrated in Fig. 4. In Fig. 4A, AVC is obtained from the limiter grid biasing network. A negative potential is developed across R1-C1 which is proportional to the average strength of the incoming carrier wave. This potential may be fed through RC filters to the grids of IF and RF amplifiers in the conventional manner. Fig. 4B illustrates the method used to obtain AVC when the Ratio Detector is employed. The charge in capacitor C5 is proportional to the average carrier strength and is, therefore, suitable for AVC.

Double Superheterodyne

It is sometimes desirable to design an FM receiver of exceptionally high sensitivity. This is especially true when the receiver is to be used in outlying districts where the signal strength may be quite low. However, as previously mentioned, there is a definite limit to the amount of gain which can be accomplished at any one frequency because of the danger of regeneration or oscillation. If the desired amplification can be distributed among stages operating at different frequencies, this difficulty will be greatly minimized. This system is called the "double superheterodyne" and is shown in Fig. 5.

Basically, the principle of operation is as follows: The incoming signal at 88-108 mc is first heterodyned to a lower IF of moderate value amplified and then hetero-

dyned again to the standard IF of 10.7 mc. The same oscillator is used for both mixing operations. Regeneration is minimized and sensitivities in the order of 1/10 microvolt or less may be realized. In the illustration of Fig. 6 are shown the relationships between the various frequencies, and the frequencies for one FM station operating at 90 mc. To find the oscillator frequency for any given station, subtract 10.7 mc from the station carrier frequency and divide by two. In order to find the 1st IF for any station, add the carrier frequency to the 2nd IF (10.7 mc) and divide by two.

Assume that the station carrier is equal to 90 mc (Fig. 6). This signal is first applied to the control grid of V1, which is called the first converter stage. L1-C1 is tuned to 90 mc. Grid leak bias is used for this stage which operates along the lower bend of the tube characteristic curve. This bias is furnished by R1-C1 from grid current. The oscillator V2 is a shunt fed Hartley of conventional design and is tuned to 39.65 mc by L3-C3. The two coils L1 and L3 are loosely coupled and thus the oscillator frequency (39.65) is impressed on the grid of V1 together with the carrier frequency of 90 mc. The difference frequency of 50.35 mc is produced by mixing, and is the first IF. The first IF is passed along to L2-C2, which is resonant to this frequency together with some of

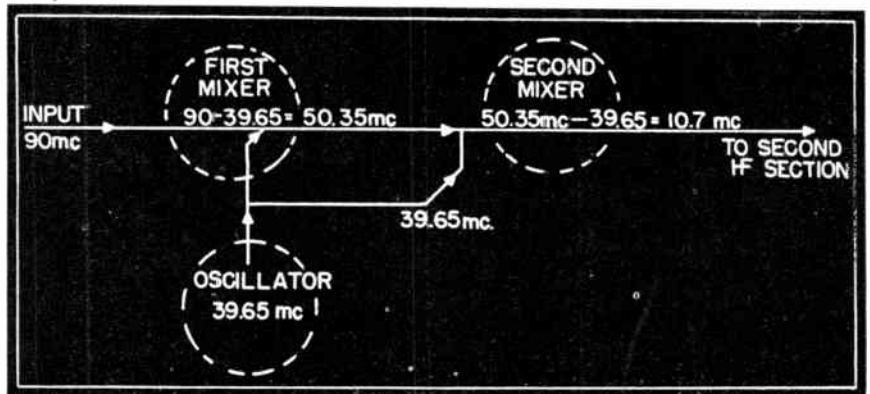


Fig. 6 Relation of various frequencies in a double superheterodyne receiver.

the original oscillator frequency (39.65). V2 acts as a second converter stage producing the difference frequency, (10.7 mc), which is fed to the IF amplifier.

Automatic Squelch System

Most FM receivers have a very high noise level when not tuned to a station. This will be accentuated in receivers which use AVC. If AVC is employed, the receiver will operate with maximum sensitivity when no carrier is present. This noise is evident when the receiver is tuned between stations and is extremely annoying. This undesired interstation noise may be eliminated by using a squelch system. One of the many varieties of suitable squelch circuits is illustrated in Fig. 7.

Whenever a signal is being received, the rectifier tube V1 con-

ducts strongly and a high negative bias is developed across R1-C1. This negative voltage is sufficient to cut off the squelch tube V2. Under this condition the normal fixed bias is supplied to audio amplifier tube V3 and amplification of the audio takes place. If there is no bias developed at the grid of the squelch tube due to the lack of a station carrier, the squelch tube conducts heavily and plate current flows through R2, R4, and R3 to B plus. The added drop across R3 is sufficient to cut off the audio amplifier V3.

A disadvantage of squelch systems is that weak signals cannot be heard, in which case the squelch circuit may be made inoperative by opening switch S1. When a Ratio Detector is employed, a squelch system is unnecessary because the Ratio Detector is quiet even when the carrier wave is not present.

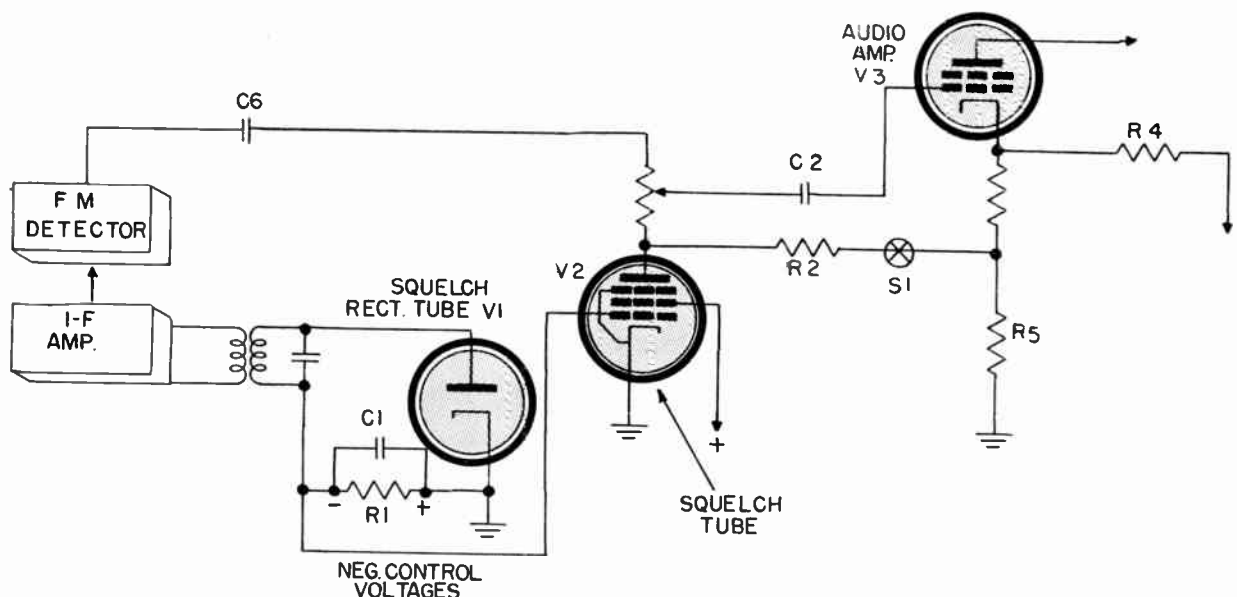


Fig. 7 Schematic diagram of a squelch system.



what's new in VIDEO SECTIONS?

by **Morton Scheraga**
Allen B. DuMont Labs.

Amplifiers designed to pass a wide range of frequencies offer a new challenge to the serviceman.

A NOTABLE change in the new television receivers is the shifting of the sound and video IF carrier frequencies from their prewar values. The sound IF has been changed from 8.25 mc to its present frequency of 21.9 mc; the video IF has been changed from 12.75 mc to 26.4 mc. The lower frequencies were subject to many interference effects. Image frequencies, FM stations, the amateur and aviation channels, and local oscillator radiation were all found to create spurious signals in prewar receivers. The new IF frequencies are chosen to give good operation with the least interference from other services. Fig. 1 shows the relative position of the picture and sound carriers for channels 2, 3, and 4. The sound and picture carriers are separated by 4.5 mc in each channel. A station transmitting video modulation frequencies of up to 4 mc on channel 3 has side

band frequencies up to 65.25 mc, with the lower side bands being suppressed at the transmitter.

Most manufacturers operate the receiver RF oscillator at a higher frequency than the received channel so that the IF frequency relation of picture to sound carrier is reversed as shown in Fig. 2. The IF carrier frequencies indicated in

the diagram are 21.25 mc for the sound, and 25.75 for the video. These are the frequencies employed by RCA in their model 630TS and are shown here because this circuit will be described below. It will be found that different manufacturers do not use the same IF carrier frequencies. For example, Philco receivers are designed with

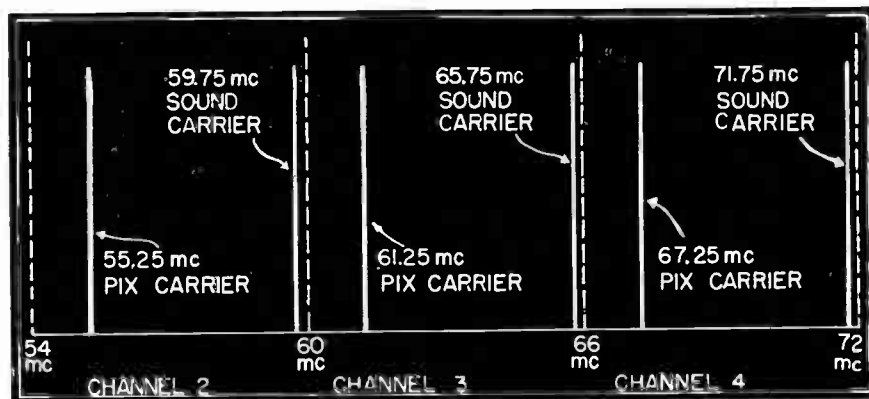


Fig. 1 Location of sound and picture carriers for television channels 2, 3, and 4.

IF carrier frequencies of 22.1 mc and video IF carriers of 26.6 mc. G.E. and DuMont employ 21.9 and 26.4 sound and video IFs, respectively.

Basic IF Circuits

Two basic circuits are now common to the design of television IF amplifiers. The more conventional type is the over-coupled band pass amplifier, using double tuned transformers. The second type is the stagger-tuned amplifier which was perfected during the war and is now becoming popular in television receiver circuits because it offers improved economy, simplicity, and ease of adjustment. Stagger-tuned amplifiers can now be made to have as good selectivity and phase characteristics as double-tuned or multiple-tuned coupled circuits.

The G.E. Model 801 television receiver uses the over-coupled amplifier design. See Fig. 3. Three 6AC7 tubes are used in the three-stage video IF amplifier. The transformers T1 and T2 are overcoupled and then loaded with resistance R1 to obtain the approximate

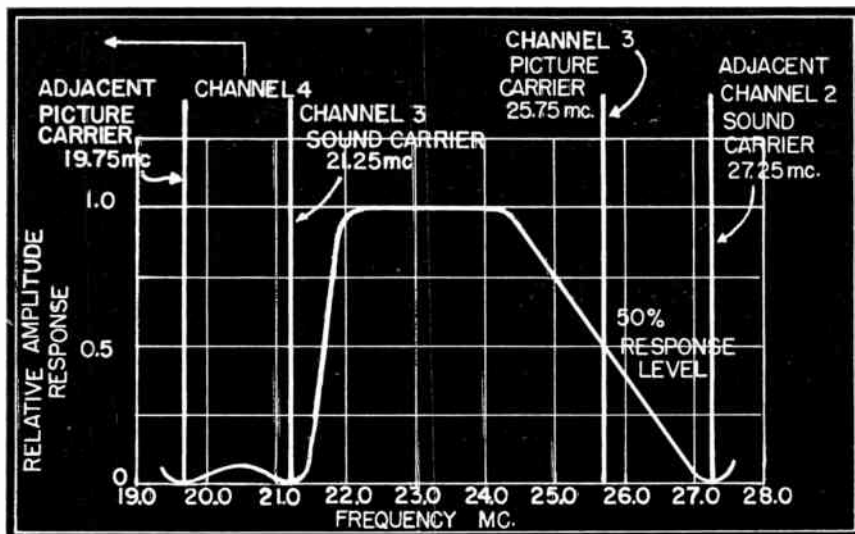


Fig. 2 Ideal picture intermediate frequency response.

4 mc band-pass frequency characteristic. These stages have the response curve shown in Fig. 4. With such a band-pass characteristic, not enough attenuation of the sound carriers on the same and adjacent channels is obtained. Sound traps are therefore used to shape the response curve. A third winding is

added to each video transformer and tuned to trap out the audio carrier and its sidebands. The trap on T1 is tuned to 27.9 mc to reject the adjacent channel audio IF. The traps at T2, T3, and T4 are tuned to 21.9 mc to reject the same channel audio IF. The combination of sound traps and overcoupled trans-

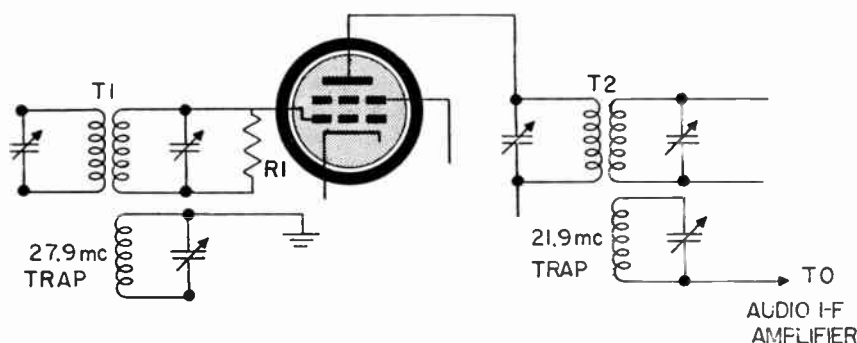


Fig. 3 Single stage of the video IF amplifier in the G.E. Model 801 receiver.

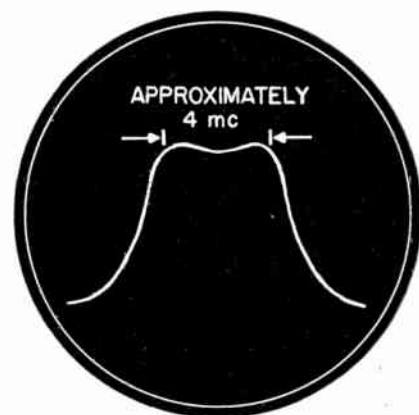


Fig. 4 Video IF response curve of circuit in Fig. 3, without effect of sound traps.



Fig. 5 Effect of sound traps on video IF response curve for G.E. Model 801 circuit.

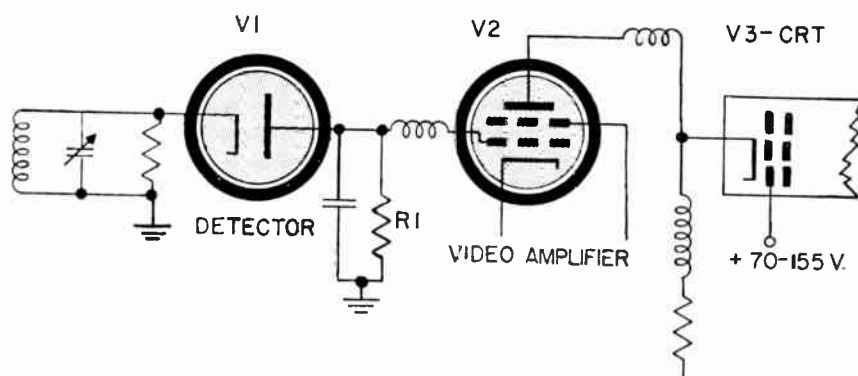


Fig. 6 Direct coupling of video amplifier to cathode of picture tube, eliminating need for DC restorer.

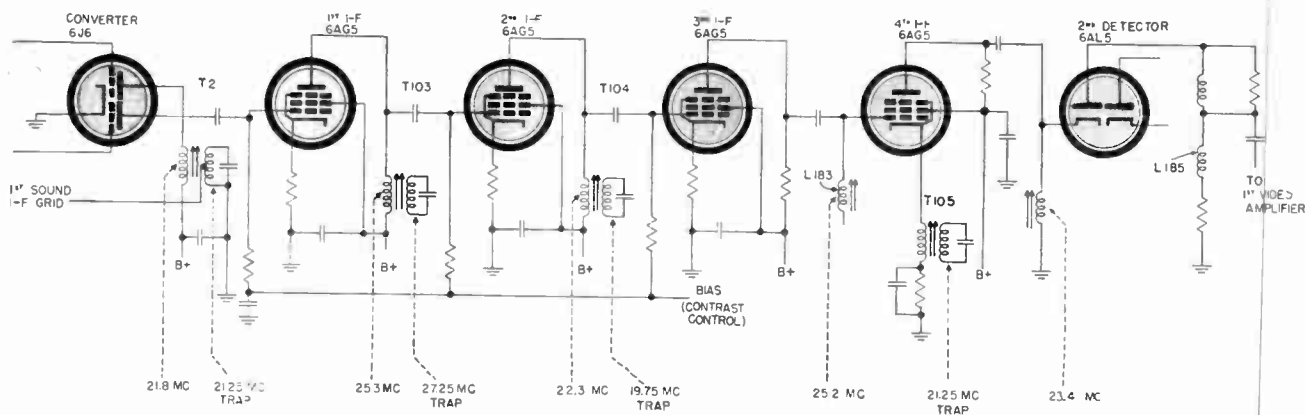


Fig. 7 Schematic of video IF stagger-tuned amplifiers.

formers then results in the response curves shown in Fig. 5.

Separation of the audio IF frequency from the video IF frequency is achieved by taking the 21.9 mc signal developed across the trap on T2 and feeding it to the grid of the first audio IF amplifier tube. See Fig. 3. There is no automatic gain control in this receiver.

An interesting feature of the G.E. video circuit is that DC restoration at the picture tube is not necessary. Fig. 6 shows the video detector, amplifier, and picture tube. The video IF amplifier output is applied to a diode rectifier, V1, and the diode load, R1, is connected to develop a negative video signal at this point. The signal is amplified by tube V2 and then applied directly to the cathode of the picture tube, V3. The DC level of the video signal is preserved and no DC re-insertion is necessary. Since the cathode of the cathode-ray tube is directly coupled into the plate circuit of the video amplifier, V2, a variable positive voltage must be applied to the control grid of the picture tube to change the grid bias and provide a brightness control.

Alignment of overcoupled amplifiers was previously described in RADIO MAINTENANCE. (*Television Receivers—The Video Channel*, by Morton Scheraga, Jan. 1947, p. 4.)

Stagger Tuning

The stagger-tuned video IF amplifier used in the RCA Model 630TS receiver differs considerably from the conventional overcoupled amplifier. In a stagger-tuned system, each stage is peaked to a particular frequency, and the overall response curve is the result of the combination of peaked stages. In

the RCA circuit, four stages of IF amplification are employed to obtain the necessary wide band characteristic with adequate gain. The converter plate and the successive IF transformers use only one tuned circuit and each is tuned to a different frequency. These stages are shown in Fig. 7. Fig. 8 shows the relative gain and selectivity of each coil. The overall response curve which results from these combined curves is shown dotted.

In order to obtain this band pass characteristic, the picture IF transformers are tuned as follows:

- Converter transformer, 21.8 mc (T2 primary)
- First pix IF transformer, 25.3 mc (T103 primary)
- Second pix IF transformer, 22.3 mc (T104 primary)
- Third pix IF coil, 25.2 mc (L183)

- Fourth pix IF coil, 23.4 mc (L185)

Traps

Attenuation of unwanted sound and picture IF carriers is accomplished by four traps. The first three are absorption circuits which are tuned as follows: The first trap (T2 secondary) is tuned to the sound IF frequency of 21.25 mc; the second trap (T103 secondary) is tuned to the adjacent channel sound IF frequency of 27.25 mc; the third trap (T104 secondary) is tuned to the adjacent channel picture IF carrier frequency of 19.75 mc. The reader should refer to Fig. 2 to see the relative effects of these traps on the IF response curve. The fourth trap (T105 secondary) is in the cathode circuit of the

→ To Page 20


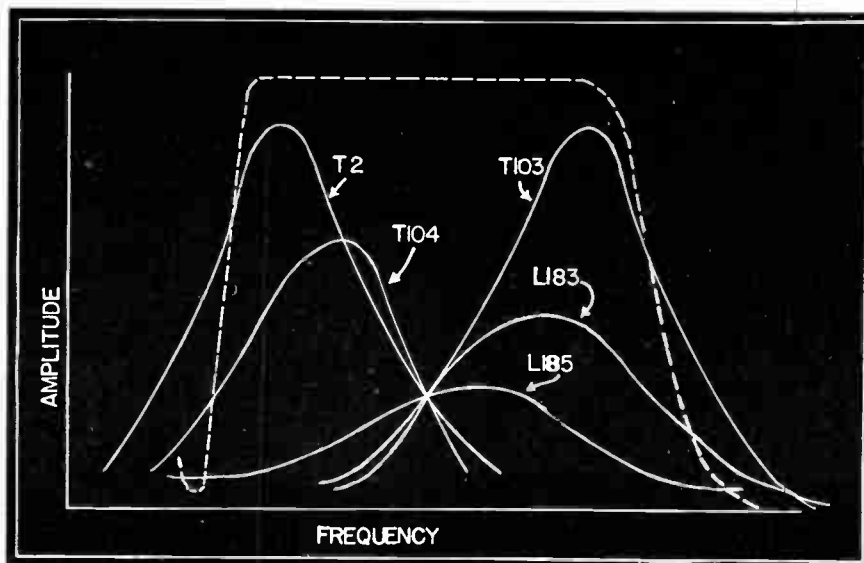
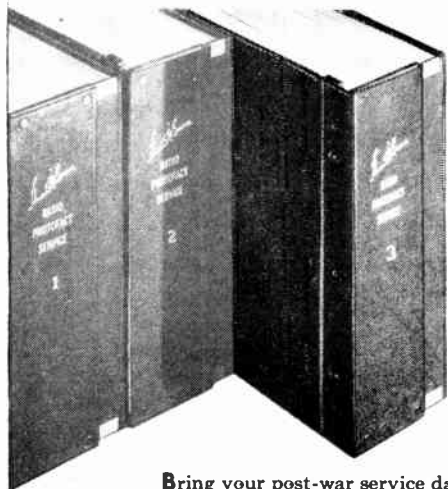


Fig. 8 Relative gain and selectivity of each coil in staggered video IF amplifier in RCA 630-TS receiver. Resulting overall response curve is shown dotted in background.

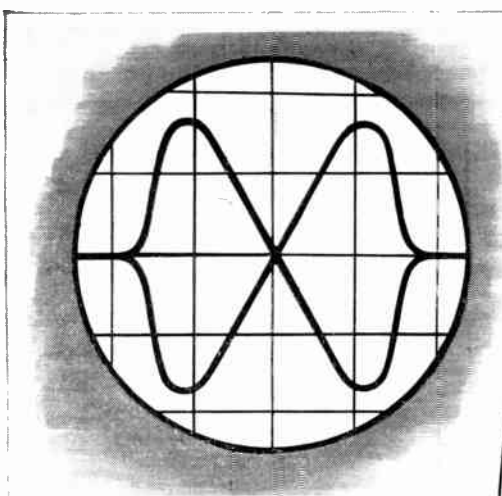

EXCLUSIVE IN PHOTOFAC Oscilloscope Wave Forms!

2 Alignment Procedures for All FM Receivers!

EXCLUSIVE! PHOTOFAC now brings you both professional methods for aligning FM receivers—the "visual" oscilloscope method, and the meter method using an AM generator and vacuum tube voltmeter. PHOTOFAC Folders now include large, clear, specially prepared diagrams of actual oscilloscope wave forms for each visual alignment described. These wave forms show you how to secure absolute maximum circuit performance in minimum time. This revolutionary development, available in no other radio data service, has been acclaimed by servicemen everywhere since its first appearance in PHOTOFAC Set No. 28, published in November 1947. Here's more powerful proof that you can't afford to be without PHOTOFAC—the complete, practical, profitable radio data service.

Howard W. Sams

World's Most Practical Radio Service Data

Bring your post-war service data library right up to January 1948! PHOTOFAC Volume 3 is ready for you—companion to Volumes 1 and 2—the most accurate and complete Radio Data ever compiled. Here is everything you need for fast, efficient, profitable servicing—bound in easy-to-use volumes. Large size schematics with the exclusive PHOTOFAC Standard Notation; photo views keyed to parts lists and alignment data; complete listings of parts values and proper replacements; alignment, stage gain, circuit voltage and re-

sistance analysis; coil resistances; dial cord stringing; disassembly instructions; record changer analysis and repair data. Send in your order today for PHOTOFAC—the only Radio Service Data that meets all of your actual needs!

VOLUME 1. All post-war models up to Jan. 1, 1947.

VOLUME 2. Models from Jan. 1, 1947 to July 1, 1947.

VOLUME 3. Models from July 1, 1947 to Jan. 1, 1948.

YOUR PRICE, EACH VOLUME, IN EASY-TO-USE DELUXE BINDER... **\$18³⁹**

INDUSTRY ACCLAIMS NEW HOWARD W. SAMS MANUALS

Servicemen: "Terrific is the only word that adequately describes both books. Absolutely "musts" for servicemen."—*S. L., Chicago.*

"I think your AUTOMATIC RECORD CHANGER MANUAL and DIAL CORD books are great!"—*H. O., Maquota, Iowa.*

Manufacturers: "Your Record Changer Manual is one swell book. Should be very well received among the trade."—*Astatic.*

"The Record Changer Manual is a commendable job. Subject is well-covered."—*Jensen.*

"We have received copies of your AUTOMATIC RECORD CHANGER SERVICE MANUAL and DIAL CORD GUIDE. A great deal of hard work and thorough analysis has gone into the making of these two books. They should certainly fill an urgent need in the service industry. Extremely easy to read and should prove most helpful to our service dealer customers."—*Sylvania.*

"Your Record Changer Manual is beautifully prepared. Our compliments to you and your organization."—*Webster-Chicago.*



SPECIAL OFFER

If you haven't a complete file of all PHOTOFAC Folder Sets to date, you can trade in the individual Folder Sets you now own for complete Volumes at amazingly low cost. Write today for special offer, stating what Sets of Folders you now own (use coupon below).

BOOST YOUR EARNING POWER!

Mail This Order Form to HOWARD W. SAMS & CO., INC. 2924 E. Washington St., Indianapolis 6, Indiana.

My (check) (money order) for \$ enclosed.

- Send PHOTOFAC Volume 3 (including Sets Nos. 21 through 30) in DeLuxe Binder, \$18.39.
- Send Volume 2. Send Volume 1 (each in DeLuxe Binder, at \$18.39 per volume).
- Send . . . SAMS' 1947 AUTOMATIC RECORD CHANGER MANUAL(S) at \$4.95 each.
- Send . . . SAMS' DIAL CORD STRINGING GUIDE(S) at \$0.75 per copy.
- Send FREE PHOTOFAC Cumulative Index.
- Send details of your Special Trade-in Offer. I own PHOTOFAC Sets Nos.

Name

Address

City State

HOWARD W. SAMS & CO., INC.
INDIANAPOLIS 6, INDIANA

Export—Ad. Auriema—89 Broad St., New York 4, N. Y.—U. S. of America
Canada—A. C. Simmonds & Sons, 301 King St., East—Toronto, Ontario

PHOTOFAC SERVICE

"The Service that pays for itself over and over again"

FOR FASTER SOLDERING
2 NEW WELLER
SOLDERING GUNS
 with

Solderlite



The new Weller Soldering Guns with Solderlite plus the fast 5 second heating help make service work more profitable for radio, television and appliance service men, electrical maintenance men, electric motor rewinding and repair shops automotive electrical service.

A useful and time-saving tool for laboratory workers, experimenters, hobbyists, telephone installation and maintenance men. S107 100 watts single heat, D207 100/135 watts dual heat.

See your radio parts distributor or write for bulletin direct.

WELLER
MANUFACTURING CO.
 812 Packer St., Easton, Pa.

ELECTRONICALLY SPEAKING



Electronics engineers in cooperation with General Electric distributors conducted a nation-wide tour of the traveling "FM radio workshop." Also referred to as the "FM caravan," the workshop was equipped with radio sets of different types, servicing and test equipment, and a complete sound system. It was accompanied by experienced G-E commercial and engineering personnel.

Starting at Hartford, Connecticut, in September, the caravan stopped at Boston, New York, Pittsburgh, Cleveland, Columbus, Detroit and Chicago. It then continued through Denver and the West Coast, Texas and Southern cities before returning early in December.


A three-hour program for radio service technicians was divided into three parts as follows:

1. Description of the characteristics of frequency modulation reception compared to those of ordinary amplitude modulation reception.
2. Technical discussions of servicing operations.
3. Demonstration of actual test procedure. An FM receiver which was first put out of alignment was used as a model.

The program was prompted by the realization that FM receiver servicing has reached a large volume and requires the latest in skills and techniques.

A few weeks from now in Philadelphia hundreds of servicemen will attend a three-day Town Meeting of Electronic Technicians. While primarily of interest only to the radio technicians of the Philadelphia area, it is also of great im-

→ To Page 39

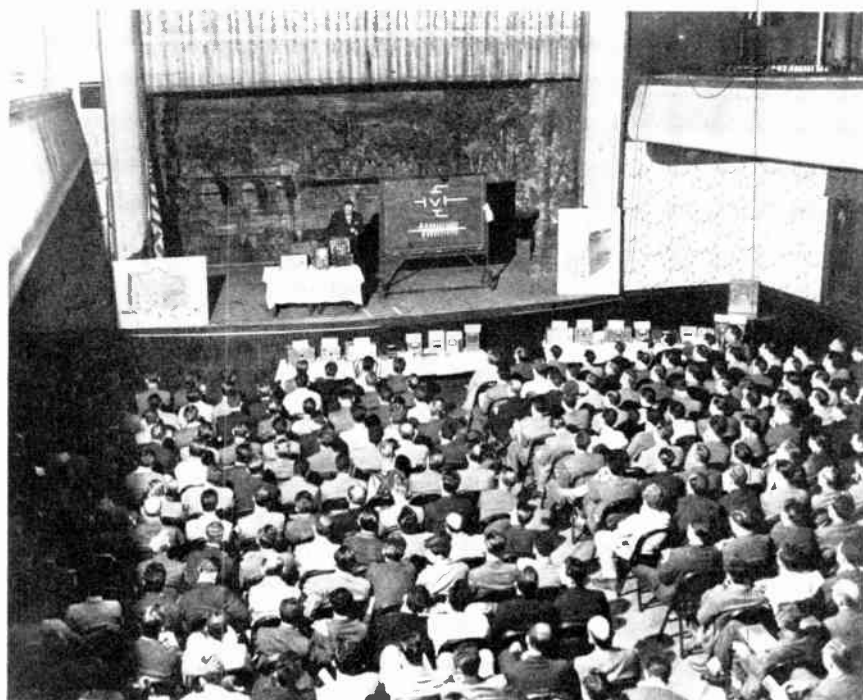

A. The New York City meeting of the G-E FM caravan. Servicemen were given information on theory and practical demonstrations of the use of test equipment.

BOBBY-SOXERS

play their radios long and hard
.. buy plenty of tubes, parts, and repair time
.. will patronize your shop once they see the G-E monogram



RADIO TUBES


DON'T begrudge 'em their fun. It's the last fling before demure seventeen, studious nineteen, and engaged twenty-one... Jive aside, they're smart kids—and loyal. When they buy, it's with an eye to established reputation.

General Electric? *Natch!*... Brought up in homes bright with G-E lamps, where breakfast toast—when they take time to eat it—jumps up out of a G-E toaster, where food stays fresh in a G-E refrigerator, time is kept by G-E electric clocks, and G-E fans hum softly in summer... these youngsters know the familiar G-E monogram as a friend to be trusted.

Their radio tube and repair business—plenty of it in your area!—goes to the serviceman with the General Electric sign. And years from now they'll still be customers.

Only with larger home sets, meaning a bigger service potential. Start now to make these clients-of-tomorrow patrons of *your* shop. Display and handle General Electric radio tubes! *General Electric Company, Electronics Department, Schenectady 5, New York.*

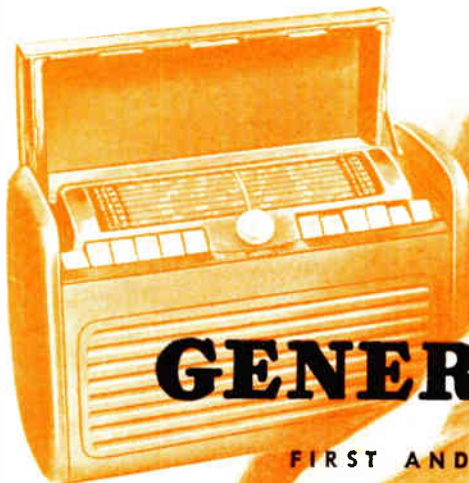G-E miniatures, other tubes of all types for servicing portables and home receivers are listed, rated, and described in G.E.'s complete Tube Characteristics Booklet ETR-15. Write for your free copy.



GENERAL  **ELECTRIC**

FIRST AND GREATEST NAME IN ELECTRONICS

SIMPLE FM CONVERTER WILL MAKE YOU MONEY

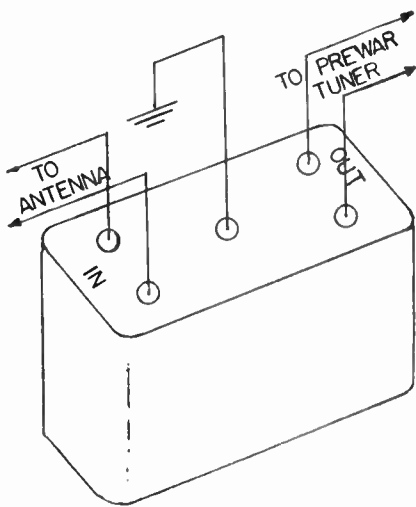
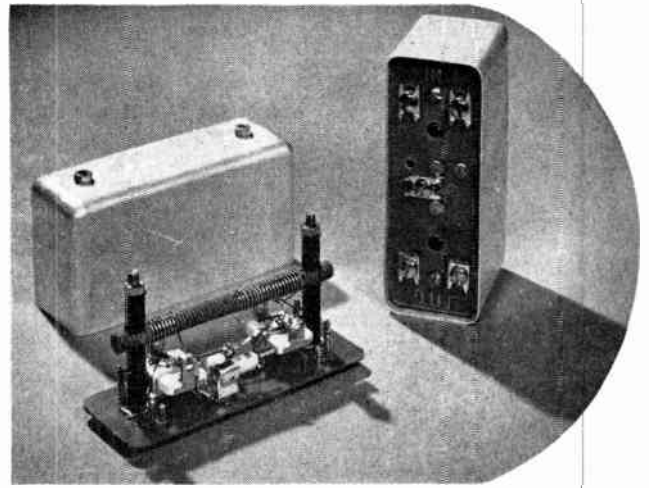


FIG. 1

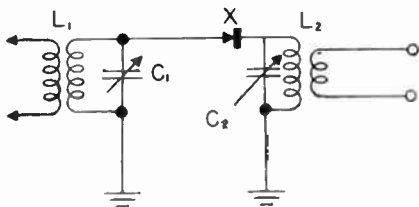


FIG. 2

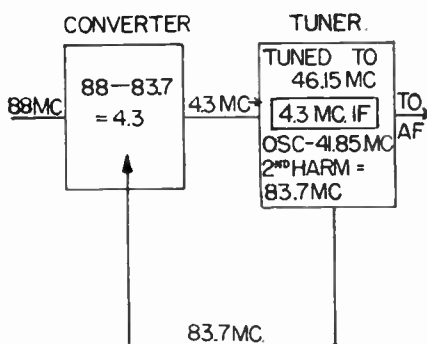


FIG. 3

A LARGE number of pre-war FM tuners and receivers are still in operation in many areas. When the FM band was changed from 42-50 mc to the new range of 88-108 mc, a demand for some simple method of conversion for the older tuners arose. Without such a converter, the pre-war receivers are rendered useless except for the few low band stations now operating, and which will soon go off the air.

Several simple devices were developed to solve the problem. One of the simplest and most compact is the crystal converter shown in the photograph. This converter is manufactured by the Crystal Devices Company of New York City. Using a crystal detector as a mixer, it requires no power of any kind except the signal from the antenna and oscillator voltage coupled from the tuner or receiver.

The service technician is likely to find opportunities to install and service these devices. The job is simple and easy if the operation is thoroughly understood. This operation is as follows:

1. The antenna is connected to the converter input; the converter output is connected to the pre-war tuner antenna posts. (See Fig. 1.)
2. Input tuned circuit L1-C1 resonates broadly in the new FM band and passes the signal along to crystal detector X (Fig. 2).
3. RF voltage at the second harmonic frequency of the tuner oscillator is fed back to the input circuit of the converter.
4. When the tuner dial is adjusted properly, this oscillator sec-

ond harmonic frequency differs just 4.3 mc from frequency of the incoming signal.

5. The oscillator harmonic and the received signal mix and produce a 4.3 mc signal, which is picked up and amplified by the tuner IF section.

A block diagram illustrating these operations is given in Fig. 3. An 88 mc received signal is used as an example, with a tuner using the standard 4.3 mc IF (pre-war). The tuner oscillator frequency is 4.3 mc lower than the tuner mixer circuit resonant frequency, which puts it at 41.85 mc when the tuner is adjusted to 46.15 mc.

Installation


Before making the installation, we should determine the intermediate frequency of the tuner to be converted. Although 4.3 mc was the standard FM IF before the war, some FM tuners and receivers used other frequencies.

After conversion, tuning is still done with the old tuner. The dial setting of the tuner will depend on the IF it uses. Tuner dial coverage for 88-108 mc is as follows:

- 3.0 mc IF—45.5 mc to 55.5 mc
- 4.3 mc IF—46.15 mc to 56.15 mc
- 5.0 mc IF—46.5 mc to 56.5 mc

These values can be checked and new ones calculated from the information given above.

Oscillator voltage is coupled from the tuner into the converter through the converter output leads. Better coupling is obtained by running a lead from one antenna connection to the tuner, where it is formed into a loop which couples to the oscillator. ✓ ✓ ✓

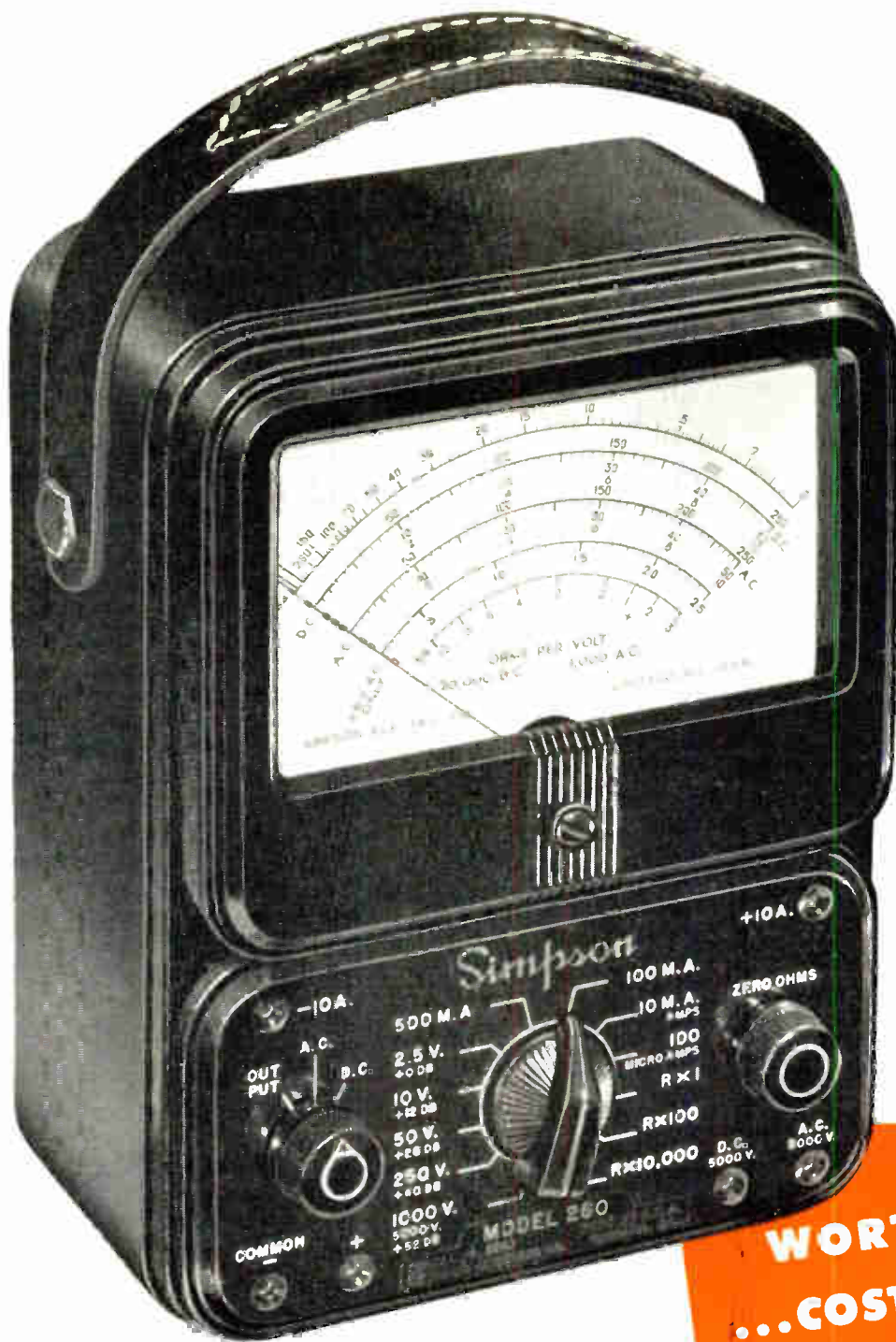

**MODEL 260
VOLT-OHM-MILLIAMMETER**

20,000 Ohms per Volt D.C.
1,000 Ohms per Volt A.C.

Volts, A.C. and D.C.: 2.5, 10, 50,
250, 1000, 5000.

Milliamperes, D.C.: 10, 100, 500.

Microamperes, D.C.: 100.

Amperes, D.C.: 10.

Decibels (5 ranges): —10 to 52 D.B.

Ohms: 0-2000 (12 ohms center).

0-200,000 (1200 ohms center).

0-20 megohms (120,000 ohms
center).

Model 260—Size 5 1/4" x 7" x 3 1/8"
\$38.95

Model 260 in Roll Top Safety Case
—Size 5 3/8" x 9" x 4 3/4". \$43.75

Both complete with test leads and
32-page Operator's Manual*

ASK YOUR JOBBER

**WORTH MORE...
...COSTS NO MORE!**

For what it buys in sensitivity, precision, and useful ranges, the price of Model 260 has always purchased value far beyond that of even remotely similar test instruments. Today this famous volt-ohm-milliammeter is a finer instrument than ever, with added ranges and with a new sub-assembly construction unmatched anywhere in strength and functional design.

The price is the same. That means, of course, that your investment today buys even more in utility and the staying accuracy that distinguish this most popular high-sensitivity set tester in the world.

*No other maker of test instruments provides anything to approach the completeness of the pocket-size 32-page Operator's Manual that accompanies Simpson Model 260. Illustrated with 12 circuit and schematic diagrams. Printed on tough map paper to withstand constant usage.

Simpson
INSTRUMENTS THAT STAY ACCURATE


SIMPSON ELECTRIC COMPANY • 5200-5218 W. Kinzie Street, Chicago 44, Ill.
In Canada, Bach-Simpson Ltd., London, Ont.

there's a new horizon for PROFITS!

ESPEY


CUSTOM-BUILT CHASSIS

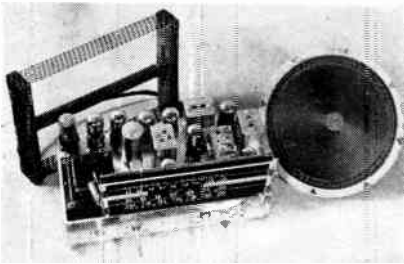Keep in step with the times! Custom installations allow the serviceman to cash in on a profitable and untapped field. Write us today for full information on these custom-sales opportunities.



Model 7-B: Here is a beauty! AM-FM superheterodyne, with 11 tubes, including rectifier. Operates on 105-125 volts AC, 50-60 cycles. Features automatic volume control, tone control, 10" Alnico No. 5 speaker, slide rule dial, loop antenna for AM, and folded Dipole for FM reception. Wired for phonograph operation. RMA listed. This superbly engineered receiver is supplied, ready to operate, with tubes, speaker, antennas, and all necessary hardware for mounting in a table or console cabinet.

Model RR-14: Another "natural"! Eight-tube (inc. rectifier) superheterodyne receiver covering AM and two shortwave bands. Operates on same current as 7-B above. Volume and tone controls, 10" Alnico No. 5 speaker. Wired for phonograph operation. Built-in loop antenna, with provision for external antenna if desired. Lighted slide rule dial. Supplied complete with tubes, knobs, speaker, antenna and all necessary hardware to install in table or console cabinet.

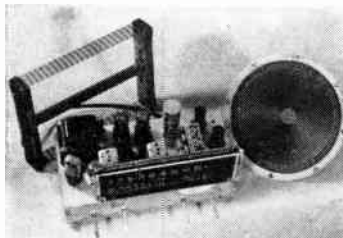

Model 97-A: 6-tube (inc. rectifier) superheterodyne receiver, operating on same current requirement as models above. Features Alnico No. 5 speaker, automatic volume control. Receives on broadcast and one shortwave band. Wired for phonograph, lighted slide rule dial, built-in loop antenna. Like both models above, the 97-A is licensed under RCA and Hazeltine patents, and is RMA listed. Supplied complete with tubes, fully wired, and ready for operation.

For full details about these chassis, and the custom field, WRITE TODAY

ESPEY MANUFACTURING COMPANY, INC.
528 EAST 72ND STREET-NEW YORK 21, N. Y.

What's New In Video Amplifiers?

→ From Page 14

fourth picture IF amplifier and is tuned to the accompanying sound carrier IF frequency. Fig. 9 shows the response curves of each stage in the stagger-tuned system and the effects of the various traps.

Alignment of the IF section consists of peaking the transformers to the specified frequencies with a signal generator. The overall response is then observed by use of a sweep generator and cathode-ray oscillograph. Because of slight deviations from standard circuit Q, the overall response may have to be adjusted a bit by shifting the transformer center frequencies slightly.

An oscillograph is not necessary to peak each stage. Instead, a vacuum tube voltmeter is connected across the picture sound detector load resistor. If you know the RF stage is correctly aligned, connect an accurately calibrated signal generator to the receiver antenna terminals. If you are not sure of the RF alignment, the signal generator may be applied directly to the converter grid through a small capacitor.

Set the IF bias voltage at the value prescribed by the manufacturer for alignment (—3 volts in this case). The signal generator is successively set at the frequency of each trap, and the trap coil is adjusted for minimum indication on the vacuum tube voltmeter. The signal generator is then set at the frequencies required to peak IF coils for maximum indication on the vacuum tube voltmeter. ✓ ✓ ✓

GREYLOCK

A Dependable Name in RADIO TUBES

GT, Glass, and Miniature Types
12SA7, 12SK7, 12SQ7, 50L6, 12AT6,
12BA6, 12BE6, 35W4, 50B5 each 39c
1R5, 1S5, 1Y4, 354, 3Q4, 6AK5, 6AC5,
6AC7, 6AQ5, 6BE6, 6BA6, 6AU6,
6BJ6, 6X4 each 49c
32L7, 70L7, 117L7 each 59c
All Tubes Carry RMA 90-Day Guarantee

PM SPEAKERS

4" Alnico No. 5 each \$1.19
5" Alnico No. 5 each 1.29

TERMS: Net C.O.D. No order accepted for less than \$5.00.
WRITE FOR BARGAIN CATALOG M-1
GREYLOCK ELECTRONIC SUPPLY CO.
30 Church Street New York 7, N. Y.

TUBULAR ELECTROLYTICS

Fresh stock Fully guaranteed

20 mfd. 150 V. 10 for \$1.79
20-20 mfd. 150 V. 10 for 2.49
8 mfd. 450 V. 10 for 1.85

Postage extra, 25% deposit on C.O.D.
Write for our free bargain lists featuring "AMERICA'S BEST BUYS"
POTTER RADIO CO.
1314-M McGee Street Kansas City 6, Mo.

Permoflux SPEAKERS

YOUR JOBBER CAN SUPPLY YOU!

Permoflux quality and dependability—the same as supplied to the major set manufacturers—is your assurance of complete customer satisfaction. You'll find Permoflux Speakers easy to install and readily available in both PM and Electrodynamic types. You'll find too, that it pays to give your customers "tops in tone" with a Permoflux Replacement Speaker.

TWO COMPLETE FACTORIES TO SERVE YOU



WRITE FOR FREE BULLETIN

PIONEER MANUFACTURERS OF PERMANENT MAGNET DYNAMIC TRANSDUCERS

PERMOFLUX CORPORATION

4900 WEST GRAND AVE., CHICAGO 39, ILLINOIS
236 SOUTH VERDUGO ROAD, GLENDALE 5, CALIFORNIA

Seven to Twenty Times

MORE SENSITIVE


than

Comparably Priced

OSCILLOGRAPHS

Only .03 volts to get 1" deflection, or 0.15 to get full-scale (5") deflection.

Wide range sweep circuit oscillator

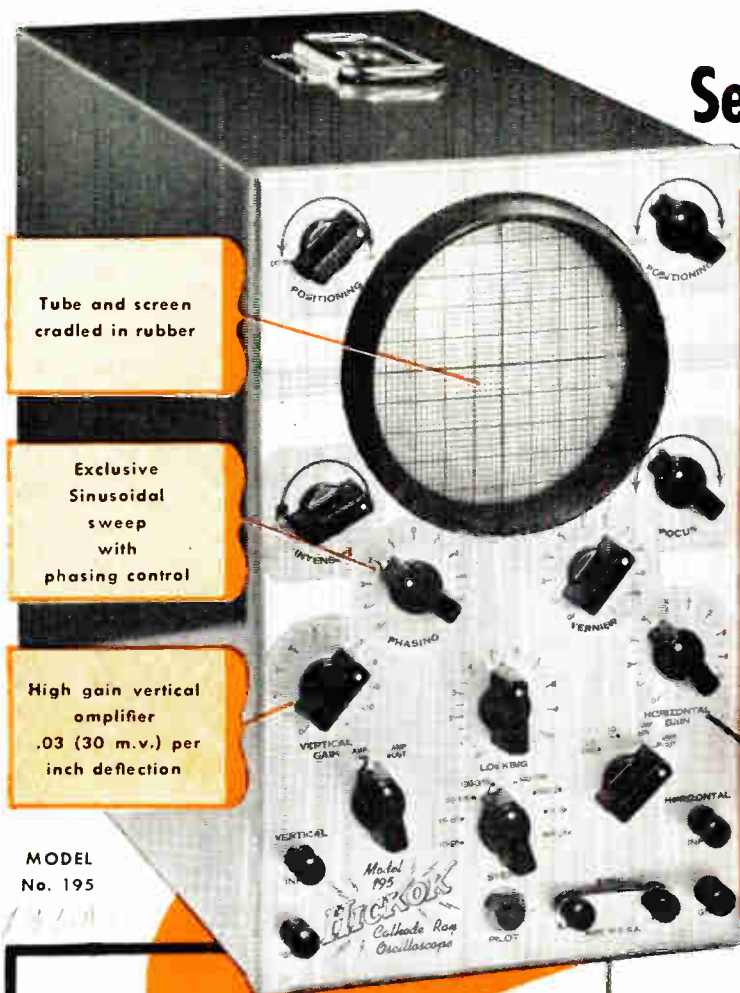

MODEL
No. 195

TECHNICAL CHARACTERISTICS

- Power supply required: 105-125V, 50-70 cycles, A.C.
- Power Consumption: 50 Watts at 115 Volts
- Deflection Sensitivity:
 - Vertical—.03 Volts (rms) per inch
 - Vertical, Direct—1.5 Volts (rms) per inch
 - Horizontal—.15 Volts (rms) per inch
 - Horizontal, Direct—20 Volts (rms) per inch
- Input Impedance:
 - Vertical—1 meg, 25 mmf
 - Vertical, Direct—2.2 meg
 - Horizontal—4 meg, 35 mmf
 - Horizontal, Direct—2.2 meg
- Frequency Range:

Amplifier, Vertical—30 cycles to 50 kc
Amplifier, Horizontal—10 cycles to 50 kc
- Tube Complement:

| Tube | Function |
|--------|--------------------------|
| 1 6SJ7 | Horizontal Amplifier |
| 1 884 | Sweep Circuit Oscillator |
| 1 6AC7 | Vertical Amplifier |
| 1 6X5 | Low Voltage Rectifier |
| 1 5Y3 | High Voltage Rectifier |
| 1 SUP1 | Cathode Ray Tube |
- Size: 8 $\frac{1}{16}$ " wide x 18 $\frac{1}{2}$ " deep x 13" high
- Weight: Approximately 25 lbs.

THE

HICKOK

ELECTRICAL INSTRUMENT COMPANY

10634 DUPONT AVENUE · CLEVELAND 8, OHIO

For proper visual alignment, there is no perfect substitute for the HICKOK 195—5-inch Oscilloscope with phasing control and the unusually high sensitivity of .03 volts per inch. As a test instrument also for FM, AM and television receivers, you will find it to be in a class by itself.

This HICKOK Model 195—5-inch Oscilloscope embodies so many advanced improvements that it is already being recommended by five leading manufacturers of FM receivers.

USING THIS OSCILLOGRAPH YOU CAN

- Align R.F., I.F. and discriminator stages.
- Determine causes of trouble in a receiver.
- Analyze wave shape of signal.
- Determine unknown frequencies.
- Easily view the images on the screen.
- Amplify and view very weak signals.

FEATURES OF MODEL 195

- Big 5" screen—using the new 5 UP-1 Cathode Ray Tube, completely cradled in rubber.
- Extra high gain vertical amplifier.
- Sinusoidal sweep circuit.
- Phasing control for proper I.F., R.F. and discriminator alignment.

We take pride in offering this instrument with its extremely high sensitivity of .03 Volts per inch for use in visual alignment with FM receivers. Being recommended by five leading manufacturers of FM receivers it comes to you with added assurance of superior performance. No progressive, well-equipped radio dealer's service department can afford to be without it.

mcmurdo
SILVER

LCETI

MAKE
FM and TV
SERVICING
Easy!


MCMURDO SILVER Laboratory Caliber Electronic Test Instruments are designed to make FM and Television servicing easy. Each is accompanied by comprehensive instructions . . . the added "know-how" to transform your shop into a modern service laboratory. The new instruments used in laboratories and factories building the radios you must service, they are proven in use by tens of thousands of smart service technicians. Despite unequalled quality, accuracy and completeness, prices are the lowest.

906 FM/AM SIGNAL GENERATOR

Vital to AM, FM and Television service. 90 kc. thru 210 mc. in 8 ranges directly calibrated $\pm 1\%$ accurate. Variable 0-100%, 400 cycle AM and 0-500 kc. electronic FM sweep, output less than 1 microvolt to over 1 volt spells low strays which put it in the \$500 class. Yet only \$99.50 net.



900 "VOMAX"

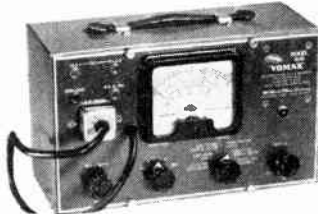


Superior quality, range and accuracy make this universal VTVM predominant choice of research and service users. 51 ranges; d.c., a.c., a.f., i.f., r.f. volts; current; db. and resistance. New flexible pencil-thin r.f. probe reaches tightest spots for meter signal tracing thru 500 mc. The outstanding meter, yet only \$59.85 net.

905 "SPARX"

Thousands in daily use prove it the big-money earner. Visual and audible AM, FM and TV signal tracing 20 cycles thru 200 mc. Locates trouble in 30 seconds per tube/stage! Is your shop test speaker; tests phono pickups, microphones, speakers, PA amplifiers, too. Only \$39.90 net.



904 CONDENSER-RESISTANCE TESTER

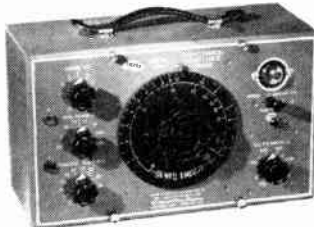

Laboratory accuracy of $\pm 3\%$. Range $\frac{1}{4}$ mmfd. thru 1000 mfd., $\frac{1}{4} \Omega$ thru 1000 meg. Ω . Measures all condensers with internal 0-500 v. rated d.c. applied. Utterly unmatched at only \$49.90 net.

SILVER FM-TV "SCOOP"

MODEL 909 FM AND TELEVISION SWEEP SIGNAL GENERATOR
1 thru 228 mc., true electronic FM & TV sweep variable 0 thru 9 mc. Size and appearance like MODEL 906. Equips you to earn big FM—and TV—service profits, yet only \$48.50 net.

WRITE FOR NEW LCETI AND AMATEUR CATALOG.

OVER 36 YEARS OF RADIO ENGINEERING ACHIEVEMENT

McMurdo Silver Co., Inc.

EXECUTIVE OFFICES: 1240 MAIN ST., HARTFORD 3, CONN.
FACTORY OFFICE: 1249 MAIN ST., HARTFORD 3, CONN.

How To Improve Your Signal Tracing Technique

→ From Page 7

No hum and no signal mean a short. Very low hum and no signal would be observed if no station were on the air, and the primary were in good condition. If the coil is good and the stations are transmitting, signals will be heard. At the secondary, a gain of 3 to 10 in home receivers is usual while in auto sets it may be from 10 to 50.

Measuring Gain

Because of the wide range of frequencies to be covered, it is impossible to calibrate tracers accurately for gain measurements. However, all of them provide an attenuator control which regulates the gain of one of the amplifiers. An approximate indication of gain

→ To Page 24

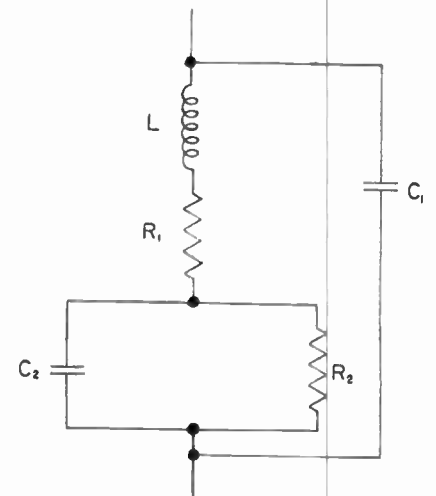
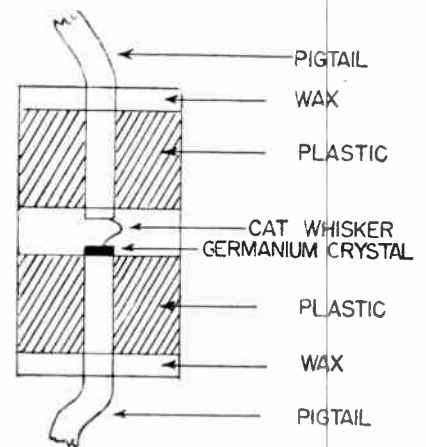



Fig. 9 The germanium crystal—its construction and equivalent circuit.

NOW!

in 1,000 pages:

All data and basic knowledge in radio and electronics digested into 12 sections... in a complete, quick to find, easy to read, handbook form.

Plan every operation in radio and electronics with the *Radio Data Book*. This new radio bible will be your lifelong tool... you will use it every day, on the board, at the bench, in the field! Use it for construction, troubleshooting and testing. The RADIO DATA BOOK will be your invaluable aid in design, experiment and in layout. It will help make your production better, faster and easier. In any and every operation in radio and electronics, you will use the RADIO DATA BOOK!

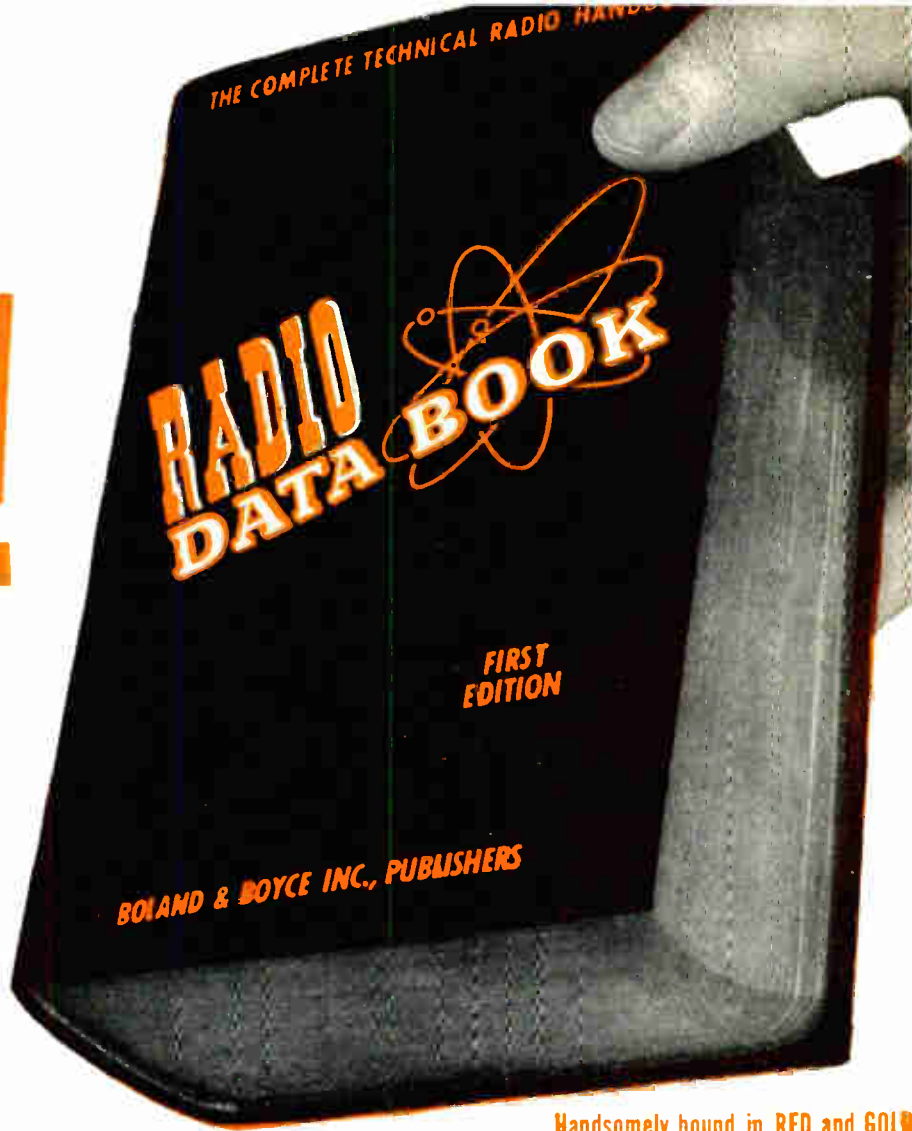

Handsomely bound in RED and GOLD

The RADIO DATA BOOK is a work of complete authority, prepared by engineers with many years of practical experience. They have been assisted by the Boland & Boyce staff of editors skilled in preparing electronics manuals for the U. S. Signal Corps for many years. These men have worked for several years gathering material for this book... all the knowledge of radio principles and operation... all the statistics... all the newest developments in electronics... every possible angle and detail. Eighteen months were spent digesting this material into the most concise, the clearest, and the most readable form. The result is this invaluable manual... The RADIO DATA BOOK. Whether you use this book for general reference, for scientific instruction, or for education, one thing is certain—the practical help, the daily usefulness you will derive from it will prove to be worth many, many times its astonishingly low price!

Advanced Sale... first printing, Only 10,000 available... To make sure to get your RADIO DATA BOOK, mail your order **NOW!**

12 complete books in one only **\$5.00!** Less than 42c per book!

MAIL THIS COUPON TODAY

BOLAND & BOYCE INC., PUBLISHERS
460 BLOOMFIELD AVE. MCNTCLAIR 3, N. J.

Please send me a copy of
THE RADIO DATA BOOK Enclosed is \$5.00.

NAME
ADDRESS
CITY ZONE
STATE

BOLAND & BOYCE INC., PUBLISHERS

CONTENTS

Each section is a COMPLETE coverage of its subject... 12 sections... 12 books in ONE! 1000 pages... Schematics... Accurate photographs... Specially prepared drawings... White on black charts... Diagrams... Isometric projections and exploded view...

- Section 1. **THE 150 BASIC CIRCUITS IN RADIO.**
Every circuit is analyzed and explained in a Johnny-on-the-spot reference for any occasion.
- Section 2. **COMPLETE TEST EQUIPMENT DATA.**
Know more about the test instruments you now have... Find the new ones you want to buy... They're All in here—impartially described!
- Section 3. **TESTING, MEASURING AND ALIGNMENT.**
Simplified operation of the Oscilloscope... See what's happening inside any radio circuit... Dynamic alignment—AM, FM and TELEVISION made easy with the Oscilloscope... Scientific use of the Vacuum Tube Voltmeter, Signal Generating Equipment and other basic instruments.
- Section 4. **ALL ABOUT ANTENNAS.**
AM-FM-Television... design, installation, characteristics, construction and feed.
- Section 5. **SOUND SYSTEMS.**
Planning, installing and servicing a PA System. A complete chapter on every component... How to select and combine components... estimating costs... even acoustic requirements!
- Section 6. **ELECTRICAL AND PHYSICAL CHARACTERISTICS OF RADIO COMPONENTS.**
Know the size, the power, the shape! A quick reference on the construction and design of any circuit or equipment.
- Section 7. **COMPLETE TUBE MANUAL.** Receiving, transmitting and Commercial.
A flick of the pages brings you to all the data and ratings of any tube made!
- Section 8. **CHARTS, GRAPHS AND CURVES.**
Quick calculation devices... Plotting curves, nomographs, rules and tables for speedy solutions to radio problems.
- Section 9. **CODES, SYMBOLS AND STANDARDS.**
Handy reference to all radio symbols and abbreviations; code symbols, phrases and characters... Where you want them... When you want them!
- Section 10. **50 TESTED CIRCUITS DESIGNED FOR OPTIMUM PERFORMANCE.**
Find any circuit you want with complete parts lists and specifications... One tube receivers to complete AM, FM and Television receiver circuits... Amplifiers... Transmitters... Test Equipment and Control Circuits... All with the latest engineering refinements.
- Section 11. **DICTIONARY OF RADIO AND ELECTRONIC TERMS.**
- Section 12. **RADIO BOOK BIBLIOGRAPHY.**

GHOSTS...




GHOSTS that haunt your television customers can be laid at rest. Workshop antennas, *custombuilt for television*, eliminate ghosts, fading, noise and interference. In many locations the "signal strength" of ordinary "broad-band" antennas is insufficient for sharp detail and contrast. Workshop TV antennas, because of their inherent high gain and precise impedance matching, provide clear, brilliant reception. Even on adjacent channels their performance is exceptional.

FEATURES

- Three elements for "high-gain" performance.
- Engineered for each channel, but sufficiently broad-band to cover all present channels (should be installed for the weakest channel).
- The "feed point" is completely protected from the weather by a rugged plastic head.
- Elements made of 1/2-inch duralumin tubing.
- Rigid tubular steel mast 7 1/2 feet high. No guy wires necessary. Withstands high winds and ice loading.
- Streamlined design makes clean-cut, attractive installation.

AVAILABLE AT YOUR DEALER

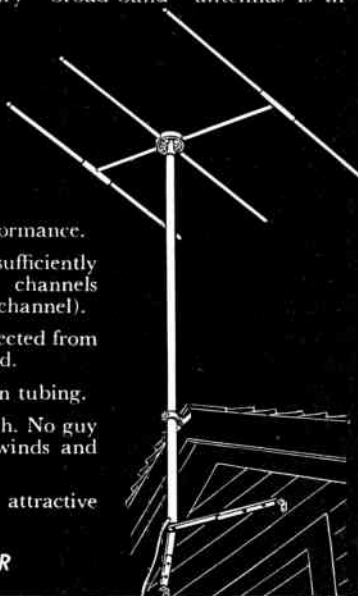

DEALERS...

You know and we know that almost any "AM wire" will bring in TV if it is close to the transmitter. For the suburbs or out-of-town installations a Workshop TV antenna will bring in a much stronger signal. This means increased sales opportunities for you — plus superlative reception that you can sincerely recommend. Your local jobber has Workshop antennas. Get in touch with him or write direct.

THE WORKSHOP ASSOCIATES, INC.
Specialists in High Frequency Antennas
66 Needham Street • Newton Highlands 61, Mass.



close the "eye" tube shadow when the tracer probe is at the grid of the stage being tested. Then, move the probe to the plate. Reset the gain control of the tracer to get the same meter indication or to close the "eye." The ratio of the two settings of the gain control is the gain of the stage. Some sample gains are helpful in tracing:

| | |
|---|-----|
| Antenna coils (home receivers) | 5 |
| Antenna coils (auto receivers) | 30 |
| RF amplifiers (broadcast) | 30 |
| RF amplifiers (shortwave) | 15 |
| Mixer grid to 1st IF grid | 50 |
| IF amplifiers | 120 |
| IF amplifier to diode | 100 |
| 1st AF amplifier (medium mu) | 20 |
| 1st AF amplifier (high mu) | 50 |
| Pentode output tube | 15 |
| Triode output tube | 3 |
| Output transformer, a loss of 30 | |
| Considerable variation from these values will be found. | |

Indicators

The choice of an indicator to be used in a tracer is important. Some use the "eye" tube since only the relative strength is to be determined. It can be located at any point in the tracer such as directly after the detector or at the output of the amplifiers depending on the signal strength. Also, without the detector, it can be used to indicate relative DC potentials without using additional test equipment.

A milliammeter is a less flexible indicator since it can be used only in a vacuum tube voltmeter requiring additional circuits to permit the same versatility as the "eye" tube. It can be used as a VTVM in combination with the probe but this limits the sensitivity.

All tracers should provide aural indicators, either a speaker, headphones or both. This is necessary to determine whether the signal being traced is actually a signal and not a hum or noise voltage. Also, when the complaint is distortion, the signal must be heard to find at what stage the distortion is originating.

The instruction books given with signal tracers will supply a long list of uses as, for example, if when the probe is placed at the screen grid of any stage in a receiver, a

How To Improve Your Signal Tracing Technique

→ From Page 22

is then possible. The gain of the tracer should have to be reduced, step by step, as the tracer is moved from the antenna to the speaker. For such measurements, set the gain control of the tracer to give a convenient meter reading or to

→ To Page 28

S.S.S.

"Servicing by Signal Substitution"

Learn about this modern dynamic approach to radio servicing with ONLY BASIC TEST EQUIPMENT.

... Fully described in a 120 page book available from your Precision Distributor or factory at 40c.

... Schools are invited to inquire regarding quantity orders from our Educational Division.

PRECISION

APPARATUS COMPANY INC.
ELMHURST 2, N. Y.

Manufacturers of Fine Test Equipment
RADIO • TELEVISION • ELECTRICAL • LABORATORY

Compare "Hi-Kaps"

See why Centralab's ceramic by-pass and coupling capacitors are your best buy for **QUALITY!**


| "HI-KAP" FEATURES | DESCRIPTION | ADVANTAGES |
|----------------------------|--|---|
| 1. Impervious to moisture | Ceramic-X is non-hygroscopic. Moisture absorption is .007% or less. | No deterioration, no shorting. Longer life even under the most adverse conditions. |
| 2. Low mass weight | Av. Wt. .029 oz. | For unit size and weight, Centralab BC "Hi-Kaps", made with Ceramic-X, are the only capacitors on the market which provide these voltage ratings. |
| 3. Small size | Dimensions D—.315" L—.540" | |
| 4. High capacity | Values .00005— .00025 mfd. | |
| | D—.315" L—.830" | |
| | .044 oz. | .0005 mfd. |
| | .050 oz. | .000750— .005 mfd. |
| | .082 oz. | .01 mfd. |
| | D—.400" L—1.305" | Rating: 600 WVDC — 1000 VDC flash test. |
| 5. Special insulation | Wax impregnated, lacquered, dipped in special phenolic resin, cured and wax impregnated. | Prevents any possibility of shorting to adjacent leads, chassis or components. |
| 6. Convenient side leads | Heavy #22 gauge tinned copper. | Permit rapid, close-coupled connections. No tricky bending or fitting required. |
| 7. Low power factor | Initial — .6%. After 100 hours, 95% humidity test — 3.0%. | More efficient circuit operation, fewer failures. |
| 8. High leakage resistance | Initial — 5000 megohms. After humidity — 500 megohms. | Long life, more efficient performance. |
| 9. Maximum dependability | One-piece construction. Leads soldered directly to electrodes. | Will not short or become intermittent. |
| 10. Factory tested | For your protection, all units 100% factory tested before packaging and shipping. | Your guarantee to your customers of reliable service and performance. |



See why Centralab's ceramic by-pass and coupling capacitors are your best buy for **PRICE!**

NEVER BEFORE has the dependability, permanence and convenience of ceramic by-pass and coupling capacitors been offered to Radio Service Dealers at a favorable price! As more and more manufacturers turn to BC "Hi-Kaps" for longer life and better set performance, Centralab now offers you this opportunity to give yourself and your service customers the newest and finest in capacitor components! Made with high dielectric constant Ceramic-X, BC "Hi-Kaps" are rated at 600 WVDC — 1000 V. flash tested. Values from .000050 to .010000 mfd., list priced from \$1.25 to \$1.50 per envelope of five.

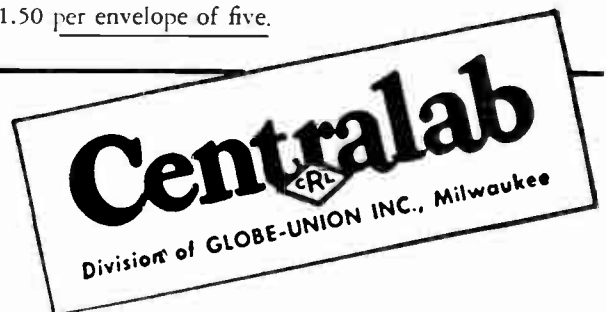Look for large counter display at your Centralab Distributor. Write today for new free booklet, "Why Ceramic Capacitors", containing complete history of origin and development of ceramic capacitors!





What Kind of Serviceman WILL YOU Be 5 Years from Now?

Prepare for Opportunities! CREI Home Study Courses in Practical Radio-Electronics and Television Will Equip You to Do a Better Job—Enjoy a More Secure Future—Start a Business of Your Own.

25 years of radio development packed in 5 years! No wonder thousands of highly-trained, expert electronics technicians are required right now—and the field is wide open.

Little competition is to be expected from the pre-war serviceman who has not modernized his knowledge through training. The average "screw-driver" serviceman is on his way out, and the trained serviceman is on his way in. Honestly ask yourself if you are equipped to qualify for maintenance and service work in this new, broadened service field. If not you are limiting your own opportunities in a field that drastically needs trained men.

Join the many servicemen who are now studying CREI courses in spare time... protecting their future jobs, their businesses, by acquiring new "know how" now. CREI's reputation for home study training has been proved over 20 years. No matter how little or great your practical experience there's a CREI course suited for your personal needs. Read the revealing facts—learn how CREI can help you enjoy the future you want. Write today.

FREE SAMPLE LESSON

Now, see for yourself! Mail the coupon for free sample lesson and see how simple it is to study at home and improve your ability the CREI way.

MAIL COUPON
FOR FREE
BOOKLET &
SAMPLE LESSON



Veterans! CREI is "G.I." Approved

CAPITOL RADIO ENGINEERING INSTITUTE
16th & Park Rd., N.W., Dept. RT-1
Washington 10, D. C.

Mail me ONE FREE sample lesson and your 24-page booklet, "CREI Training for Your Better Job in Radio Electronics." I am attaching a brief resume of my radio experience, education and present position.

Check Practical Radio-Electronics

Course Practical Television


Name

Street

City Zone State


I am entitled to training under the G.I. Bill.

THE INDUSTRY PRESENTS

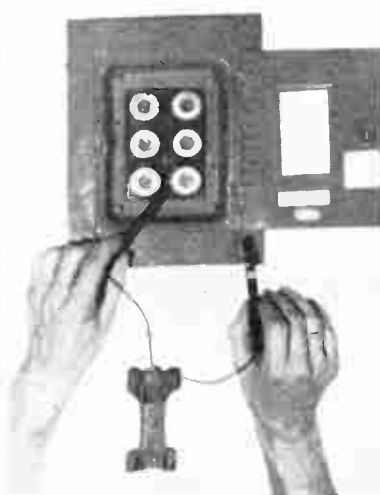

CONTINUITY TESTER

The new Star Suretest Universal Tester is a vest pocket continuity checker which operates directly from any 110 volt receptacle. It is also adapted to line testing for voltages from 75 to 600 volts. A neon lamp is used as the indicator and is located in one of the two test prods, which have 100,000 ohm protective resistors in them. For further details, write to the Star Fuse Corp., 235 Canal St., New York, N. Y.

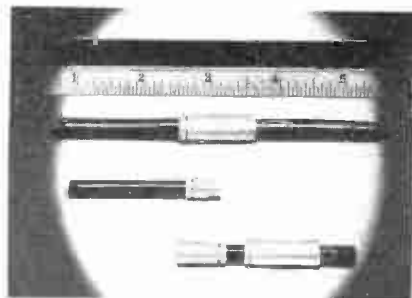


COAXIAL CONNECTOR

H. H. Buggie & Company manufacture a miniature connector designed for either RG 58/U or RG 59/U cable. It has an overall diameter of 23/64 inches and a

length of 1/4 inches when mated. It is small in size and light in weight and has a voltage rating of 500 volts peak with a low loss. It is solderless and requires minimum cable preparation. No special tools are required for assembly. The separation force of the quick disconnect lock more than satisfies normal requirements. A panel mounting plate is optional. For further information, write to H. H. Buggie and Company, 2145 Madison Ave., Toledo 1, Ohio.

PORTABLE AMPLIFIER

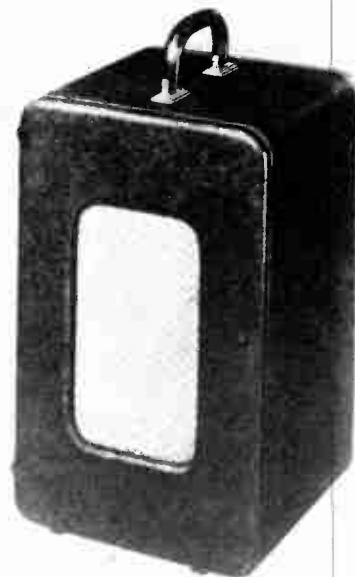A portable amplifier designed for recorded music is announced by the Webster-Chicago Corp. This unit, known as Model 66, contains three tubes and rectifier. It is



suitable for use with Model 65 portable record changer or Model 80 wire recorder. Separate tone and volume controls are provided, and the control panel is recessed to keep the knobs flush with the case. Dimensions are 15 3/4" x 9 1/2" x 9 1/4", and the weight 18 pounds. Operation is on 105-125 V 50 or 60 cycles. For further information, write to Webster-Chicago Corp., 5610 Bloomingdale Ave., Chicago 39, Ill.

→ To Page 34

SPRAGUE TRADING POST

SWAP—BUY OR SELL

FOR SALE—Precision E-200⁰ signal generator, 88 cycles to 120 mc and Precision 912MCP tube tester. Both instruments new and unused. Generator \$30 tube tester \$35. James S. Kirk, 623, 15th St., Bedford, Ind.

FOR SALE—Engineering Electronics, Fink; Radio Engineering, Terman; Radio Engineering Measurements, Terman; Television Simplified, Kiver; Principles of Television Engineering, Fink; Radio Mathematics, Cooke; Micro-Wave Transmission, Slater; Time Bases, Puckler; Calculus Book, Grandville, \$25 for lot; also Triplett tube tester 2413 like new \$40. J. Herzon, 3142 W. 16th St., Chicago 23, Ill.

FOR SALE—New 7" and 12" transvision television sets, expertly wired in a-1 operating condition, less cabinets, 7", \$185; 12", \$325. Wiener Lab., 1818 Bryant Ave., Bronx, N.Y.C.

FOR SALE—R.C.P. model 802N tube and set tester, tube tester takes them all, new condition 7 months old, \$50, with Rollindex tube chart. Rudolph Hardy, Sea View Hospital, Staten Island 10, N. Y.

FOR SALE—NC-46 receiver and matching speaker, rebuilt for a-c operation only; equipped with tuning eye and phono jack. Uses 6X8, 2-68G5, 6116, 68F7, 615, 68X7, 2-6V6, 5U4G; and 615G; tuning range 540 KC to 30 mc in 4 bands, \$125 plus shipping charges. Theodore R. Faulk, 1728 Ohio St., Owensboro, Ky.

FOR SALE—Dial scales for G-E GD-60 Midgets; ten sheets \$1 with 2 complete sets including push buttons on each sheet. I. Susman, 1052 Blake Ave., Brooklyn 8, N. Y.

WANTED—Rider's manuals complete set of separate volumes. Thomas Lamb, 17 Clinton Ave., Kingston, N. Y.

WILL TRADE—New 200-OM variac trans. volts from 0-135. Want 450 used Superior tube tester, Jack's Radio Service, 7237 Marjorie St., Detroit 13, Mich.

FOR SALE—Television receiver 5" improved Vision Research, 20 tubes — FM sound, 7" tube may be used with no changes, \$100 with all tubes but less cabinet. I. Pickell, 714 Newton Place, N.W., Washington 10, D.C.

SELL OR TRADE—Instructograph code machine slightly used; complete with tapes. Want voltmeter or radio manuals. Frank Reaves, 402 West St., Haledstead, Kans.

FOR SALE—Stewart-Warner auto radio, R-131, \$20; Superior signal generator OMC-12, \$35; NRI radio course, 1928, \$15; Sprayberry 3, 4 & 5 (16 magazines), \$7; Gernsbeck's manuals 2, 3 & 4 also Encyclopedia \$10. Massett's Radio Service, 552 Clinton Hts. Ave., Columbus 2, Ohio.

FOR SALE—1936 Ford, Philco receiver, \$25. C.O.D. in perfect condition. Grant LaMaye, 548 E. 6th St., Erie, Pa.

FOR SALE—Turner contact microphone for string instruments 10"x10"x6", speaker cabinet black crackle finished with 6" P.M. speaker; also 4 tubes 6SL7-GT, 2-26GT/G, 2L6-GT/G and 78, \$13 postpaid. Bonnie Farmer, Good Hope, Ga.

FOR SALE—6 months old Webster 56 deluxe record changer in cabinet with 5 tube amplifier and Alnico V speaker. Cost \$60 to construct, will sell \$45. A. Gin-burg, 3245 Perry Ave., Bronx 67, New York.

URGENTLY NEEDED—Two 6v storage batteries or one 12v or two-bank substitute used or new to power Mark II transmitter. Joseph A. Benko, 349 Success Ave., Bridgeport, Conn.

SELL OR TRADE—National NC100Xa with crystal filter, 11 tubes, matching speaker in best condition. Want wire recorder or \$90. R. R. Day, Solon, Ohio.

FOR SALE—RCA Rider channelyst used only 2 weeks with all cords and instructions. Cost \$162.50 will sell \$100. Charles H. Dietrich Alanson, Mich.

FOR SALE—Complete 45 watt Concord add-a-unit pa system A-1 condition with four speakers. Harry Zink Jr., 414 E. Market St., Marietta, Pa.



A GIANT WALL CHART FOR YOUR SHOP!

This giant 22" x 28" Sprague Wall Chart puts handy service data at your fingertips. Contains helpful technical information of the kind you need almost every working day—and helps dress up your shop in the bargain. Includes data on common circuit troubles involving capacitors; general replacement information about electrolytics; formulas; schematics; transformer, resistor, and capacitor color codes, etc.—all attractively arranged for easy reference. Beautifully lithographed in colors. Ask the nearest Sprague jobber for your copy today. It's free!

FOR SALE—Good radio and appliance service station; top merchandise and old established service. Balfey's Radio Sales & Service, 176 West 2nd St., Weston, W. Va.

FOR SALE—Speco signal tracer used only 2 months, \$20. Hopper's Radio Shop, 301 Hollis St., Framingham, Mass.

WILL TRADE—Radio tubes, meter tested, new cartons. Want radio receivers, test equipment. Best Radio Shop, 3349 Fulton St., Cleveland 9, Ohio.

FOR SALE—UTC high fidelity input transformer, multiple line to grids, single or pushpull \$5 and \$7. Jensen high fidelity PM-8CT pm design, \$6. Herbert Jacobowitz, 1412 Franklin Ave., Bronx, 56, N. Y.

FOR SALE—Turner crystal microphone with high quality desk stand (chrome and black crackle finish), cable, and connector, \$8; Kelton watch, \$8 with guarantee; used radio and old type tubes for sale. Peter Bedrosian, 2 Unicorn St., Newburyport, Mass.

FOR SALE—Complete N.R.I. course in radio and television also back issues of Radio News. Gerald Spector, 158 Chestnut St., Lakewood, N. J.

FOR SALE—UTC S-9 Driver transformer, new pp plates to class B grids, \$3.50 postpaid. Leland Steiber, Box #505, Findlay, Ohio.

WILL TRADE—Two 814 tubes and 1 807 tube, \$10 or what you want. Jim Pierce, 402 N. Mulberry, Elizabethtown, Ky.

FOR SALE—Precision E 200 signal generator, range 88kc to 120 mc never used; also Radio City Products multi-meter, 20,000 ohms, per volt 461AP, \$100. Albert Mraz, 301 Third St., Glassport, Pa.

FOR SALE—GRI signal tracers as featured in December 1947 issue of Popular Science, \$14.25 ea. Also radio tubes, guaranteed new. J. T. Cataldo, 222 St. Marks Ave., Brooklyn 17, N. Y.

SELL OR TRADE—DeForest training course, covers Radio and Television also includes questions and answers in good condition. Want multi-tester. John Saul, 111 Pollock Ave., New Castle, Pa.

WANTED—Position as radioman's helper in radio service shop. Benjamin Reyes, General Delivery, McFarland, Calif.

FOR SALE—Silver 900 Vornax; Solar CP-1-60 condenser checker, RCA 1550; 3" oscilloscope and army BC-612 oscilloscope. All instruments in A-1 like new condition with leads and instruction manuals. Porter Davis, 5859 Calumet Ave., Chicago 37, Ill.

FOR SALE—Webster wire recorder #150. M. Metzerek, Chicago & Vine, Arlington Heights, Ill.

SELL OR TRADE—Fishing rods and reels. Want electronic V.O.M. or Rider's 7, 8, 9, 18, 11, 12. Fred M. Merrill, Box 92, Callroom, N. Y.

FOR SALE—RME 9D receiver in good condition, \$25. Robert Rosenblum, 376 22nd Place, Clinton Iowa.

FOR SALE—BC454 receiver in perfect condition with 24v dynamotor, \$4.95. Has 6 tubes and operates on 80 meters. Mike Freeman, 1210 S. 13 1/2 St., Fargo, N. Dak.

SELL OR TRADE—Few each European tubes, E143, ECF1, CY2, DCH11, DF1, DL11, DDD25, DC25, DF25, D1425, DAC25, UY11, UY21, UBL21, UCE21, 12A8 and 955; have base diagrams for these and other tubes as well as RF X-tals. E. P. Smiley, Radio & Sound, 15310 Eldamore Ave., Cleveland, Ohio.

FOR SALE—Precision 910 dynamic electro-magnet tube tester, perfect, \$40 or will trade for Volt-ohm milliammeter. Harold W. Dalton, RFD 1, Box 168-A, Blacksburg, Va.

SELL OR TRADE—Complete radio control unit, transmitter, receiver, escapement, power supply Electronic Lab 2606 6v input, 2000 or 100ma. output, receiver operates on dry batteries; has tubes and all connecting cables, not surplus, \$50. J. G. Thomas, 1047 Hammond, San Antonio, Texas.

FOR SALE—Battery eliminator to change 110v a-c to 300 v-dc and 1 1/2 v.a.c.; used less than month, \$7. Peter L. Anderson, P. O. Box 685, Beloit, Wisc.

FOR SALE—RCA New Rider channelyst, \$120. Paul H. Schisler, Box 541, Westminster, Colo.

SELL OR TRADE—Nearly new outside neon sign 3' x 1 1/2' with Radio in 67 noon on two sides \$60 or will trade for late RCA voltmeter, Jr. or what have you? Herbert J. Hanson, 5007 26th Ave S.W., Seattle 6, Wash.

FOR SALE—Rider manuals 6 to 12, \$80, volumes 1 and 2 \$5 ea. Frank Kedi, Box 122, Sheridan, Wyo.

FOR SALE—Gears for converting Presto-K-8 recorders to cut 96 lines per inch, can be pressed on turntable shaft by any machinist. Willoughby W. Moyer Jr., Box 71, Creamery, Pa.

FOR SALE—Browning RJ-12 FM-AM tuner chassis with IF-12 matched power supply, perfect, \$95. Edward Brzezinski, Krakow, Wisc.

TRADE OR SELL—Zenith record demagnetorator with cobra pickup, special tone circuit, 5 tube 15 watt amplifier, phono table and motor and 8" speaker in case and original carton. Want BC-348 re-amp, surplus transmitter, scopes or what have you? Bill Rex, Box 488, Odebolt, Iowa.

FOR SALE—Two BC-222 walkie talkie, 28 to 52 mc complete less batteries, \$40 ea or \$75 for two. Alvin E. Allen, 1069 West 105th St., Los Angeles 41, Calif.

FOR SALE—Complete radio service shop in downtown section doing good business. Will sell all or part. R. W. Nelson, Radio Service, 109 S. Edgewood Ave., Somerset, Pa.

SELL OR TRADE—Triumph signal generator perfect, \$38 or 30-30 or 303; also Savage rifle in good condition. Roberts Radio Service, Wheeler, Mich.

WANTED—Zenith chassis 5907, less tubes, need not be in playing condition. Speaker not wanted. Kearns Radio Service, 7510 Memphis Ave., Cleveland 9, Ohio.

FOR SALE—G-E UM-2 set tester new condition, \$23; Hickok T-53 tube tester, modernized to test 11T28, local, 1R5, etc. was factory reconditioned 2 months ago, \$35; new St. Clair vacuum tube voltmeter, \$30; new Hudson car radio DB-40 complete, but less speaker, \$20. Will sell lot for \$100. Don J. Arata, 944 E. 41st St., Chicago 15, Ill.

WANTED—Riders manual #2; state price and condition. Rex Radio Service, 2813 Forest, Great Bend, Kans.

FOR SALE—Precision 920 P tube and radio analyzer in original carton, also Precision EC signal generator. John T. Levine, 15-17 Kelley Square, Worcester 4, Mass.

WILL TRADE—R.M.E. receiver 45; 1 year old with speaker like new for metal bottle with 9" swing or better. Jos. Lang, 309 Evergreen Ave., Millvale 9, Pa.

ASK FOR SPRAGUE CAPACITORS and *KOOLOHM RESISTORS by name!

*Trademark Reg. U. S. Pat. Off.

ONLY AT *Walter Ashe*... "SURPRISE" TRADE-IN ALLOWANCE
ON YOUR **USED TEST EQUIPMENT**



FOR AMAZING BARGAINS IN TOP CONDITION, SLIGHTLY USED TEST EQUIPMENT, CONTACT WALTER ASHE RIGHT AWAY. WIDE SELECTION OF GOOD-AS-NEW MERCHANDISE AVAILABLE.



Ferret Signal Generators
Model 701
Range 170 KC to \$74.95
115 MC NET

Model 600
Range 165 KC to \$49.95
56 MC NET

TIME PAYMENTS AVAILABLE



IT'S HERE!

... The new 1948 Walter Ashe Catalog — greatest in Walter Ashe History. Nearly 150 pages. Order your Free copy today.



Ferret Deluxe Test Speaker and Substitutor
Model 721
\$29.95 NET

ALL THE BIG NAME BRANDS OF NEW TEST EQUIPMENT IN STOCK (READY FOR IMMEDIATE DELIVERY)

| | |
|------------------|----------------------|
| Hickok | Triplet |
| Simpson | Weston |
| Industrial | Precision |
| Equipment | Special Products Co. |
| Waterman | Coastwise Electronic |
| Meissner | Feller |
| Bliley | R.C.A. |
| Jackson | Sprague |
| Mc Murdo Silver | Supreme |
| Cornell Dubilier | Superior |
| Du Mont | |

REMEMBER


your trade-in's worth more at the Walter Ashe Store. So get Walter Ashe's offer before you make that trade!

ALL PRICES F. O. B. ST. LOUIS

Walter Ashe
RADIO CO.
1125 PINE ST. • ST. LOUIS 1, MO.

Over 300 TYPES
Vacuum Sealed
TRANSFORMERS

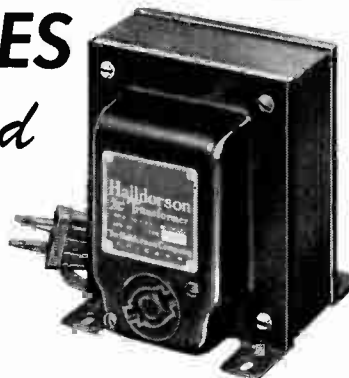- Adjustable mounts make your Service work easier.
- Sealing under Vacuum means 100% Protection.
- No skimping, to give you brilliant and lasting performance.



Step-down Transformer in S2 Mounting

Halldorson offers a complete line of replacement and amateur transformers . . . all *vacuum sealed*. More than 300 different types including new high fidelity. See your parts jobber and select the type best suited for your needs. Get the best. Get Halldorson *Vacuum Sealed* Transformers.

For new catalog, write
The Halldorson Co., 4500 Ravenswood Ave., Chicago, Ill.




How To Improve Your Signal Tracing Technique

→ From Page 24

signal or hum is heard. It indicates insufficient bypassing. Likewise, the efficiency of the power supply filter can be tested by listening to the ripple at various points in the filter circuit.

The greatest usefulness of the signal tracer is in locating faults in intermittent receivers. Connecting the instrument to one stage at a time and waiting for the receiver to "stop," the defective stage can be found in a minimum of time. Static measurements usually unbalance circuits enough to prevent as rapid troubleshooting of such a receiver.

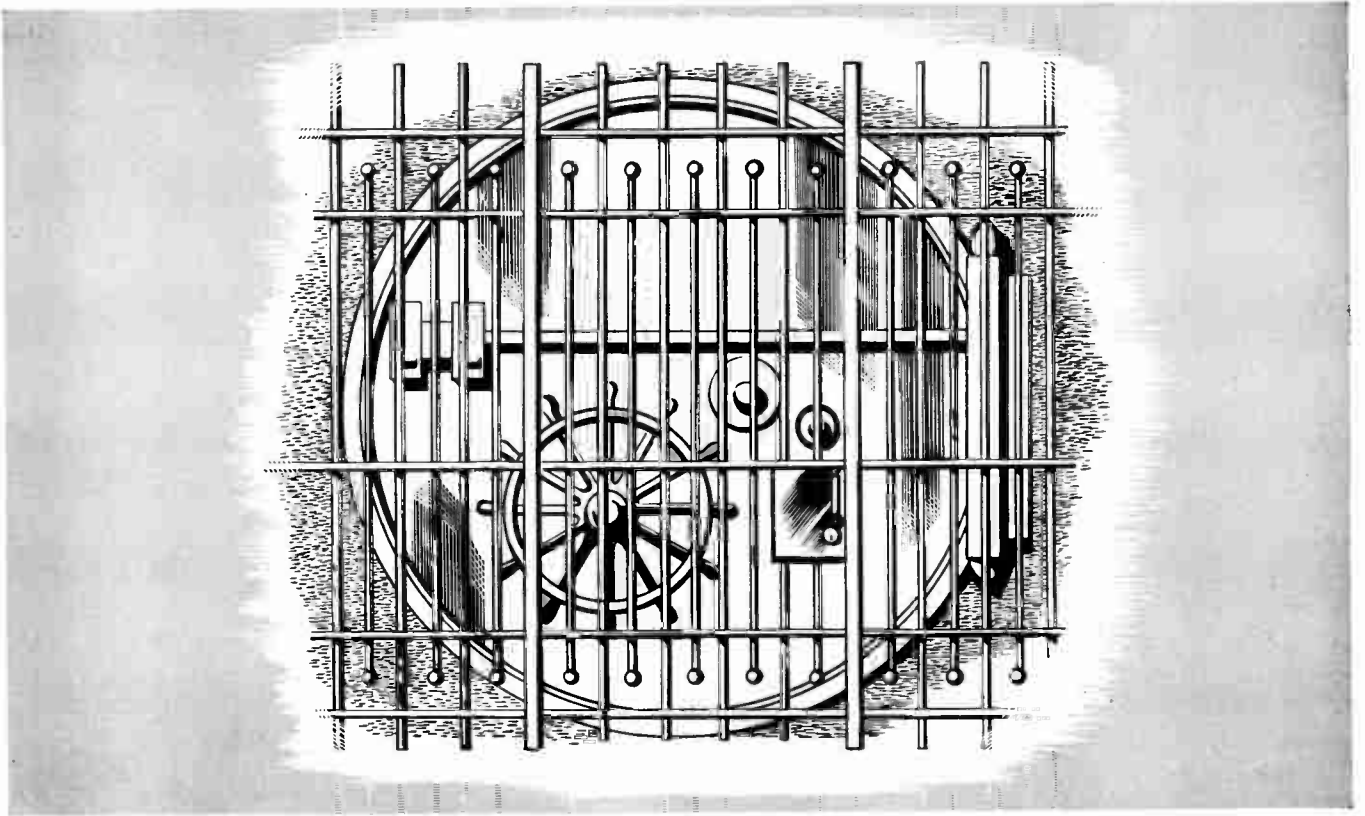It is hoped that the information in this article will help the serviceman to get the most out of the signal tracing system of servicing and assist him in selecting signal tracing equipment ✓ ✓ ✓



Sealed

As effectively sealed from foreign entry as the heaviest bank vault door, the precision workings of each Radiart VIBRATOR is held free from dust laden air and moisture by the celebrated Red Seal! This three layer protective seal of sponge rubber, bakelite and metal excludes foreign particles and moisture that ordinarily impair the efficiency of vibrator operation. Because Radiart VIBRATORS are assembled under controlled conditions, this highly effective seal prevents point oxidation and insures more dependable performance for far longer periods. Another feature that has established Radiart leadership and has made them the biggest sellers among all servicemen who insist that their customers get the best.



The Radiart Corp.

CLEVELAND 2, OHIO




Patching Ribbon Line

More and more use is being made of twin lead, ribbon type feed line. The insulation becomes soft when you make a soldered connection. This is because the heat of your iron melts the insulating material. Joints and connections may be mended and weather-proofed by insulating material from another piece of the same type of line. Just melt the material and let it drip onto your joint. It burns while it drips, so be sure you choose a safe spot and guard against fire.

M. A. Tuksal
Detroit 2, Mich.

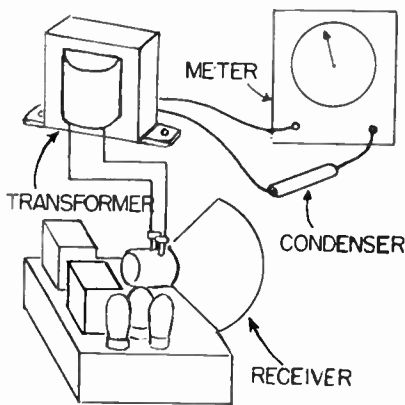Each month the reader sending in the best suggestion receives a crisp ten dollar bill. For all others published, RADIO MAINTENANCE will pay five dollars. Let's hear from you.



Output Meter Readings


IT IS desirable to make output meter readings across the voice coil leads of the output transformer. This is an accessible spot and there is no B plus around. However, because this is a low impedance circuit, there is often not enough voltage to give a good reading.

This problem can be solved by feeding the output from the voice coil leads through another output transformer as shown. Connect the voice coil leads from the receiver to the voice coil leads on the extra transformer. The plate side of this transformer will then give a stepped-up voltage and a good reading on your AC meter.

R. N. Knowland
Knowland Radio Service
East Alton, Illinois

Soldering Iron Rest

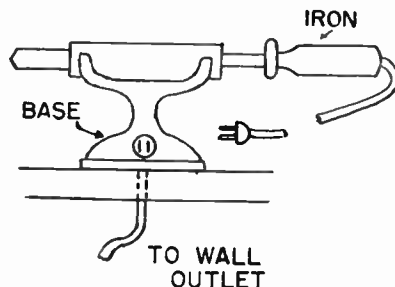An old telephone base of the French type makes a good soldering iron rest. It can be used plain or an AC female plug can be mounted where the dial assembly has been removed. An AC cord is then connected inside the base to




the female plug, and the other end fitted with a plug which is placed in a convenient wall socket. The plug from the iron cord is then in a convenient position.

Fred Stolze
Flushing, N. Y.

Loop Antenna

One way to pep up a small radio on weak stations is as follows. Wind about 15 or 20 turns of small cotton covered wire in random fashion around the loop antenna. Weak station pickup will be much better, especially if this wire is externally grounded on one end. The other end can be left loose.

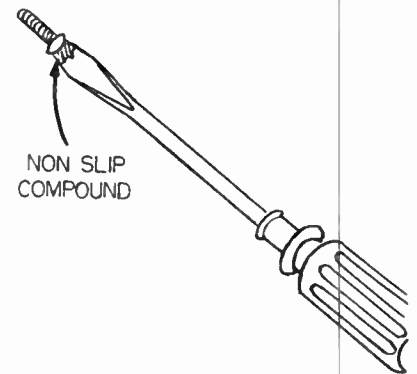R. J. Oja
Bob's Radio Electric Shop
Laurium, Mich.



Screw Holder

When trying to hold screws that are to be put in out-of-the-way places, touch the tip of the screw driver in the non-slip compound used for dial cords, allowing some of it to stick to the tip of the screw driver. When the screw driver is placed in the screw head, it will stick to the screw well enough to hold it there. This trick works with both Philip's head and single slot screw heads.

Alva H. Clark
Tarboro, N. C.

Antenna Wire Anchor

Many receivers have an antenna wire coming from the back of the cabinet. This wire connects to the antenna coil. You seldom find any mechanical protection to prevent the wire from pulling loose. A small piece of string will give this protection. First tie a knot in the antenna wire. Then tie your string to

→ To Page 32

Here They Are!

THE BINDERS YOU HAVE BEEN ASKING FOR

Now You Can File Your Radio Maintenance Magazines To Use for Reference

Each binder holds from 12 to 24 issues, protecting and preserving them. Your valuable copies of RADIO MAINTENANCE will be accessible at all times in these handsome simulated leather binders. Each binder is sturdy and durable with bright gold lettering stamped on front and side. It holds your magazines firmly without puncturing holes or defacing them in any way. Your copies of RADIO MAINTENANCE in these attractive binders will form a lasting, invaluable library! The price is right, too. By ordering in

quantity we can offer these binders to you for less than retail price — only \$2.25 each postpaid. Get yours from the first shipment — Send in your order TODAY!

RADIO MAINTENANCE
460 Bloomfield Ave.,
Montclair, N. J.

Please send me binders at \$2.25 each
Total amount enclosed

Name

Address

City Zone

State

Fixing Radios the Old Hard Way?



The Feiler Stethoscope does everything but make the actual repair. And the Stethoscope does it faster, better and much easier. Thousands of radio men, many with little experience, are already fixing radios and other electronic equipment this new way.

You will find that just this one low priced unit and a few basic hand tools are all you need to fix practically any radio.

Here is the new Model TS-5 "Pocket Stethoscope" built to take out on the job. It's light, compact and rugged yet performs like the bench models. Stethoscopes are available in 4 types ranging from \$9.85 to \$34.95.



The "Inside Story" of the STETHOSCOPE — how it works—how it instantly locates trouble in any circuit—is yours for the asking. The "Inside Story," a 24 page illustrated booklet, is full of practical tips and hints on radio servicing. To get your free copy, send your name and address on penny post card today.

"MAKES RADIO REPAIRS AUTOMATIC"

Available for Export—Choice Territories Still Open




FEILER ENGINEERING COMPANY

945 George St. Dept. 1M8 Chicago 14, Illinois

The Notebook

— From Page 30

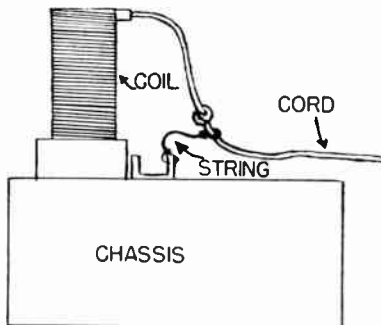

the far side of the wire. Anchor the other end of the string to the chassis.

Junichi Takahashi
Stockton, Calif.

Have You A Useful Suggestion?

Send it to The
NOTEBOOK
(see page 30)

STARTING NEXT MONTH
A NEW COLUMN OF

PRACTICAL HINTS

WHICH WILL HELP YOU IN YOUR WORK

These hints will be illustrated with photographs. This new department will show how little short cuts and time-savers can make your work easier and more profitable.

Our Most Popular Department

THE NOTEBOOK


Will continue as usual to present the best suggestions from readers. Each suggestion received will be given careful consideration. Each one printed will earn the suggester \$5. For the one adjudged best each month we will pay \$10.

Everything for the Serviceman in

RADIO MAINTENANCE

Photograph Credits

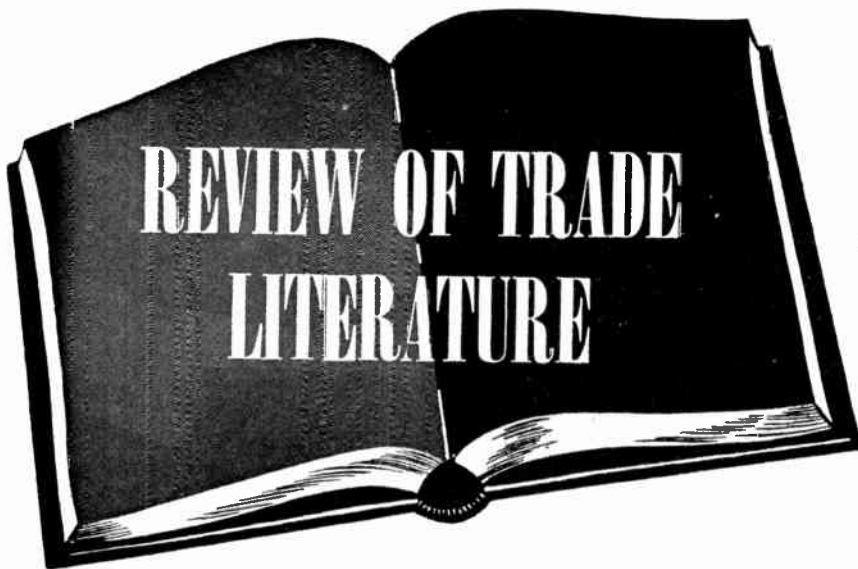- Page 4 Supreme Instrument Corporation
- Page 5 Radio Corporation of America
- Page 6 Jackson Electrical Instrument Company
- Page 7 Top—Feiler Engineering Company
Bottom—Radio City Products
- Page 8 Stewart-Warner Corporation
- Page 12 Allen B. DuMont Labs.
- Page 18 Crystal Devices Company



To avoid delay when writing to the manufacturer give issue and page number.

HOWARD W. Sams & Co., publishers of "Photofact Folders" have recently published two new books. The Sams "Automatic Record Changer Service Manual" features servicing information about 42 different makes and models. For each model there are parts list, general information, the change cycle, adjustments, troubles, lubrication and two full pages of exploded views labeled and keyed to the parts list. In addition there are several photographs of each model. Data on wire and tape recorders are included. The manual is bound in a smooth, hard cover and contains 400 pages. It is priced at \$4.95.

The other new Sams publication is the "Dial Cord Stringing Guide." This booklet contains information on dial cord arrangements for all regular types of receivers available. A separate diagram of each dial and pulley design is given, with 552 of these diagrams included. Each diagram is numbered. The various models of receivers are listed in the front of the book with the numbers of the dial cord arrangements used. The introduction includes servicing information about causes of slipping, properties of dial cord, selection of proper size, etc. The Dial Cord Stringing Guide sells for 75 cents.

A continuous service on new receiver schematics is now being offered to servicemen by John F. Rider, publisher of the Rider "Per-

petual Troubleshooter's Manuals." Starting on November 30 photostatic copies of schematics and service data were made available by mail to take care of new material which has not yet appeared in the Rider Manuals. This is an in-between-manuals-service for diagrams and service data and follows adoption of the policy of three Rider Manuals each year instead of an annual publication.

The photostats of diagrams available will sell for 10 cents for two pages consisting of schematic, alignment and voltage data, parts list (if available) and whatever else can be included in these two pages. There will be a charge of 5 cents for any additional pages up to seven pages, and 3 cents for any additional pages above seven. The photostats will be $8\frac{1}{2} \times 11$ inches, with the double-page (17×11 inches) schematic spreads being counted as two pages. Photostats will be mailed on the day the order is received and by postpaid first-class mail. Servicemen desiring this service are asked to send twenty cents with each order, either in stamps, coins or postal note. The difference in cost, if less, will be returned with the photostats. If the cost is higher—depending upon the number of pages necessary—this information will be given in the letter bearing the photostats. Printed copies of schematics and servicing data that have already appeared in Rider Manuals will also be available under the above

→ To Page 36



Servicemen's choice!
in . . .



● Servicemen in Oklahoma are casting their votes for Cunningham—the tube that's "built for service." For top quality and performance, you can't beat Cunninghams. They've been satisfying particular customers since 1915. They'll bring more preferred customers your way.

See your
CUNNINGHAM DISTRIBUTOR
MUSKOGEE ELECTRONIC SUPPLY CO.
Muskogee
SOUTHERN SALES CO.
Oklahoma City

Cunningham Tubes
A product of
RADIO CORPORATION OF AMERICA
Harrison, N. J.

free! New! Complete!



Concord Radio Catalog

160 VALUE-PACKED PAGES
of the **LATEST and BEST** in
RADIO-TELEVISION
ELECTRONIC EQUIPMENT

- Thousands of items for every Radio and Electronic need.
- Special Bargains—money-saving values in top quality Radio Parts.
- Immediate delivery from huge stocks at Chicago and Atlanta.

MAIL COUPON FOR FREE COPY

TROUBLE-FREE SERVICE from **STANDARD BRAND PARTS**—RCA • AMPERITE • SIMPSON-JENSEN • STANCOR • OHMITE • SHURE BLILEY • DUMONT • IRC • TRIPLETT • SPRAGUE and hundreds of other well known brands

CONCORD

RADIO CORPORATION

CHICAGO 7 • ATLANTA 3
901 W. Jackson Blvd. 265 Peachtree St.
Downtown Chicago Branch—229 West Madison St.
LAFAYETTE RADIO CORP.

CONCORD RADIO CORPORATION, Dept. RM-18
901 W. Jackson Blvd., Chicago 7, Ill.

Yes, rush **FREE COPY** of the comprehensive new Concord Radio Catalog.

Name _____
Address _____
City _____ State _____

GET YOUR FCC Commercial Radio Operators' LICENSE

Now...

**How To Pass
FCC
LICENSE
EXAMINATIONS**
CLEVELAND INSTITUTE
OF
RADIO ELECTRONICS
Terminal Tower Cleveland, Ohio

IT'S EASY IF YOU FOLLOW OUR PLAN
Thousands of new jobs are opening up—FM, TELEVISION, MOBILE COMMUNICATION SYSTEMS, POLICE RADIO SERVICING, are only a few of the radio fields which require licensed operators.

TIME IS IMPORTANT TO YOU!
You can get your License quickly with **NILSON'S MASTER COURSE** in RADIO COMMUNICATIONS and exclusive **CIRE** Workbooks of Instructional Aid. Saves you many hours of random, undirected study. Assures a **MINIMUM** of time in getting your ticket. **FREE BOOKLET** tells you the Government Requirements for all classes of commercial licenses—Sent immediately upon receipt of coupon.

Approved for Veteran Training under GI Bill of Rights
CLEVELAND INSTITUTE OF RADIO ELECTRONICS
RM-1 TERMINAL TOWER MAIL THIS COUPON CLEVELAND 13, OHIO

**Don't Delay—
Write Today!**

CLEVELAND INSTITUTE OF RADIO ELECTRONICS
RM-1 Terminal Tower, Cleveland 13, Ohio
Gentlemen: Please send information about your Home Study Course for preparation for FCC Commercial License Examinations. (Does not cover Amateur License Exams.)

NAME _____
ADDRESS _____
CITY _____ Zone _____ STATE _____
 If a Veteran Check here.

**ILLINOIS
CONDENSER CO.**
NOW HAS **UMP!**



TYPE UMP

A popular replacement twist prong line of **COMPACT, HERMETICALLY SEALED**, efficient, dry electrolytic condenser, is now a member of the **ILLINI** line of highest quality capacitors.

The "Illini" UMP capacitors are now available at your local jobber. Our latest catalog, listing complete Illini line, will be mailed to you upon request.



ILLINOIS CONDENSER CO.
1616 NORTH THROOP STREET - CHICAGO 22, ILL.

RADIOMEN! YOU EARN MORE WHEN YOU KNOW Modern RADIO-INSTRUMENTS



JUST PUBLISHED!

Here is the book every radioman needs. Brand new, up-to-the-minute. Tells all about modern radio and electrical testing equipment and how to use it. Money-making short-cuts on trouble-shooting, servicing, construction, and other jobs. Over 350 pages, 220 photos and diagrams. Covers Multipliers, Resistors, Ohmmeters, Oscilloscopes and many others. You see actual equipment torn down in step-by-step photos. All data pre-tested in the Coyne radio shop.

SEND NO MONEY!

Coupon is just a request to see and use this great book for 7 days at our expense. Fill out the coupon and send it in. Then examine **MODERN RADIO INSTRUMENTS** for 7 days, **FREE**, before deciding if you want to keep it. **ACT NOW!**

**7 DAY
FREE
TRIAL**

SEND COUPON TODAY!

COYNE ELECTRICAL & RADIO SCHOOL
500 S. Paulina St., Chicago 12, Ill. Dept. 18-E6
Yes! Please send "Modern Radio Instruments and Testing Methods" on **FREE TRIAL**. If satisfied after 7 days, I will pay you \$3.50, plus postage. If not, I'll return book and owe nothing.
Name _____ Age _____
Address _____
City _____ Zone _____ State _____
() Check here if you want book sent C.O.D.
—you pay postman \$3.50—Coyne pays postage. Same 7 days' examination and return privilege.

OVER THE BENCH

by John T. Frye

THE fellow had asked me to come down and look at some radio parts that he thought I might be interested in buying. I had gone, not with the idea of buying anything, but more out of curiosity. The fellow worked on the railroad, and I could not understand what he would be doing with a stock of "new radio parts still in their original boxes," as he put it.

As I sat there in the garage and looked at the stock of parts, I had a hard time smothering a grin. He had not misled me for the parts were still in their original cartons; but what parts! There were about five huge cone-type speakers with paper cones that measured nearly three feet across. A neat stack of tubes had "71A," "01A," "112A," and even "200A" written across the ends. Another group of boxes were labelled "New Straight-Line-Frequency Tuning Condensers." There was even a servicing instrument, a compact Readrite Tester housed in an elliptical-shaped metal case and having a metal cover. There were three meters: a milliammeter, a voltmeter, and an AC voltmeter.

"I used to be in the radio service business," the man explained. "Did quite a lot of it, too. Built several sets. But when battery sets began to go out and the new AC sets came in, I gave up. That AC stuff is too complicated for me. At first, I figured on studying up and staying in the game. That is why I bought that tester with the AC meter. But I just couldn't seem to get the hang of it, so I quit the whole deal."

I explained as gently as I could that I would have practically no use for the parts, with the possible exception of the cone speakers. I knew by experience that the flat driving units of the speakers could

easily be converted into surprisingly satisfactory pillow speakers. We came to terms on those, and I started home with my purchase.

As I drove along, a quotation kept going through my head. It was spoken by Governor Bradford as he watched a wretched criminal being led to his execution.

"There, but for the grace of God, go I," said the wise executive.

As I thought about this ex-serviceman, shunted off into a stagnant pocket by the hurrying current of radio progress, left hopelessly behind simply because he made too little effort to keep abreast of developments, the words of the good governor took on a sharp, almost a warning significance.

Right now, I mused, radio is taking another leap forward that is even greater than the change from battery to AC power for sets. On the one hand, we were changing the very method of impressing modulation upon the carrier, and this was accompanied by a corollary change in the method of reception. A change still more abrupt, though, is in the actual nature of the intelligence being transmitted. In addition to the aural intelligence that we have come to think of as being the basis of radio transmission, there is now added the transmission of visual intelligence! Your radio receiver not only allows you to hear but also to see!

What a small step-up was the change from batteries to alternating current when compared with these sweeping changes in the radio art! Yet that small advance was sufficient a barrier to terminate the radio service career of the man I had just left. How many more servicemen, now active, would allow these new developments to leave

→ To Following Page



Servicemen's choice!
in . . .



● Cunningham's constituents in Pennsylvania favor the tube that's "built for service." Replace with top quality Cunninghams and your customers will give you a vote of thanks.

See your
CUNNINGHAM DISTRIBUTOR

RADIO ELEC. SVC. CO. of Pa., Inc. Allentown
KENNEDY'S RADIO SUPPLY Altoona
RADIO ELEC. SVC. CO. of Pa., Inc. Easton
JORDAN ELECTRONIC CO. Erie
RADIO DISTRIBUTING CO. Harrisburg
GEORGE D. BARBEY CO. Lancaster
RADIO ELEC. SVC. CO. of Pa., Inc. Philadelphia
RADIO PARTS CO. Pittsburgh
GEORGE D. BARBEY CO. Reading
SCRANTON RADIO & TELEV. SUPPLY CO. Scranton
YORK RADIO & REFRIGERATION PARTS York



SERVICEMEN Use

QUIETROLE

Radio's
Finest
Lubricant and
Cleaner

QUIETS NOISY
VOLUME
CONTROLS

WITHOUT
REMOVAL
FROM CHASSIS

Stops noise in all moving parts. Quietrole will make you an extra profit on every radio, if you include a small charge for lubrication which all radios need. 2 oz. bottle \$1.75.

WRITE FOR FREE SAMPLE

Distributors' Inquiries invited

QUIETROLE DISTRIBUTING CO.
395 St. John Street, Spartanburg, S. C.

Technicians Everywhere
agree that when
BETTER AMPLIFIERS
are made,
it's A. C. Shaney
who's "a-goin' to make them"

A. C. Shaney, long known as the outstanding designer of high-quality amplifiers, and his associates at the Amplifier Corp. of America, are getting ready to announce the completion of the finest line of public address and electioneering amplifier equipment ever produced. New standards of quality and workmanship, new circuits, new materials, and new manufacturing processes have been combined to make this soon-to-be-announced amplifier line the answer to all requirements. Specifications and performance ratings of these popular-priced models will equal or surpass those formerly found only in high-cost, custom-built equipment. And Amplifier Corp. of America will guarantee every amplifier for 5 full years—an expression of confidence that only the country's leading and most thorough manufacturer of the most modern amplifier designs would dare make.

You can't afford to buy any amplifier until you have investigated the new concept in amplifier design and construction offered by A. C. Shaney and the Amplifier Corp. of America.

Join the many thousands who are "watching and waiting" for the latest in amplifiers from

AMPLIFIER CORP.
of AMERICA
398-29 Broadway
New York 13, N. Y.

A postal card will put you on our mailing list to be among the first to know.

Over the Bench

→ From Preceding Page

them behind in the dust, I wondered.

It is nothing to be complacent about. The changes, abrupt as they are in theory, take place so gradually and smoothly in the servicing field that a fellow scarcely knows what is going on until he wakes up some fine morning and discovers that his equipment, his technique, and even his fund of knowledge, are obsolete. If he does decide to do something about it and makes a really sincere effort to catch up, he can do so; but it requires tremendous and unremitting effort to overtake those who have gone right along with the progress of their art *and are still going*. Anyone who has attempted to catch up with his class in school after missing a few weeks will know exactly what I mean when I say it is infinitely harder to *catch up* than it is to *keep up*.

As I turned the problem over in my mind, I decided that there is one bright aspect: Servicemen now have more aids to help them in keeping up with the swift pace of radio advancement than they had when this battery-serviceman was left in the lurch. Every radio magazine you pick up these days is filled with articles on FM and Television. An attempt is made to acquaint the serviceman with every phase of these advancements. You find articles on theory, on construction, and on actual service of these new receivers. Analogies are used to impart this information as painlessly as possible, and every attempt is made to relate the new techniques to those the serviceman already possesses.

Yes, the serviceman who subscribes to a service magazine—and surely that includes every radio repairman who makes the least pretence of being up to date—has at hand wonderful help in marching right along with radio's swift movement; but he still has to take advantage of this proffered aid; he still has to read and to understand the articles. Let him not keep putting off this study on the grounds

that he has little call for service on FM and Television sets yet. The time to prepare for such service is *before* the sets start coming in—and they will be coming in sooner than many of you imagine.

Start studying *now*, lest one of these days you hear yourself saying, "Yes, I used to be a radio serviceman. Did a lot of it, too; but when FM and Television started coming in, I gave up. That stuff was too hard for me to get into my head, or at least I thought so at the time. I've always been sorry I didn't keep up with servicing." ✓✓✓

Review of Trade Literature

→ From Page 33

cost schedule, also effective November 30. To obtain this service, write to John F. Rider Inc., 404 Fourth Ave., New York 16, N. Y.

Articles for Radio Servicemen

RADIO MAINTENANCE is in the market for good articles for radio servicemen and will welcome new manuscripts for approval.

Articles on radio are plentiful, but RADIO MAINTENANCE magazine will continue its policy of publishing only material that is of direct value to the Radio Serviceman and his business. We are constantly searching for more and better material of this kind.

It has been our experience that the best men to write such articles are radio servicemen themselves and if you have something you feel will meet our requirements, or if you have an idea for an article, get in touch with the editor.

Of the Organizations

Reports from all over United States and Canada are making it clear that the Radio Service Technician is finding membership in an organization of great benefit. Radio Maintenance has kept you informed by starting this column many months ago, and we have watched group activity grow. If you are an organization member, let's hear from you about your group activities.

HERE'S that information we've been promising you about the Philadelphia convention in January. "The Federation of Radio Servicemen's Associations of Pennsylvania will hold its first annual convention of radio servicing technicians in Philadelphia simultaneously with the Town Meeting of Radio Technicians in the Bellevue-Stratford Hotel on January 11, 12 and 13, 1948. The Philadelphia Radio Servicemen's Association, local Federation group, will act as convention host.

"The Town Meeting of Radio Technicians is being held to discuss many of the fundamental technical advances which have taken place in the electronics industry as they apply to the technician's needs as well as the changing pattern for small businesses.

"The Federation urges all radio technicians and associations who are interested in furthering their welfare and that of their members to have representatives present at

both the Convention and the Town Meeting sessions.

"New developments in the field of electronics and all types of modern test equipment will be demonstrated in their practical application to shop procedures.


"Well known authorities on technical developments, engineering, and merchandising will speak on subjects including F.M. television, and various phases of business management. The Town Meeting is being programmed for its practical usefulness to the technician's earning power, and the convention is being planned to clear up many areas of confusion in the industry today. Efforts are currently under way, with top industry sponsorship, to obtain some of the latest available electronic exhibits for the Town Meeting, which will eliminate any exploitation by any factor in the radio industry.

"The Federation's Convention Committee would like to receive from all cooperating associations and individuals, including those who cannot attend the convention or Town Meeting, ideas concerning practical or technical problems confronting them, as radio servicing technicians, which they would like to have discussed at the Town Meeting. The Committee will either include them on the Convention's agenda or turn them over to the Town Meeting's program committee for discussion.

"Early applications for accommodations are requested in order that they may be handled properly. The hotel has been able to reserve for the Federation only a limited number of rooms. Address all communications to David Krantz, 2109

→ To Following Page

Built for Service

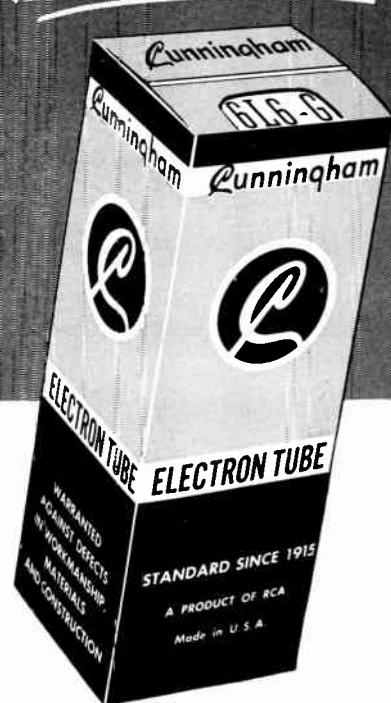

Servicemen's choice!

in . . .



● Since 1915, thousands of set owners in New Hampshire have relied upon Cunningham tubes. That's why Cunningham tubes have such a high reputation today. Their top quality and performance makes them the favored tubes when replacements are called for. You'll catch more customers if you campaign for Cunningham.

See your
CUNNINGHAM DISTRIBUTOR
AMERICAN RADIO CORP.
Dover

Cunningham Tubes

A product of
RADIO CORPORATION OF AMERICA
Harrison, N. J.

The ONLY POWER SUPPLY

that gives these ratings*
without overheating

ELECTRO
ELECTRICAL AND RADIO EQUIPMENT

MODEL "A"


- ★ 6V at 15 amps. in series
- ★ 12V at 7½ amps. in parallel
- ★ 6V at 7 amps. separately

Operates auto radios with solenoid tuning and tone controls — also 12 volt marine and aircraft radios.

Oversize transformers, chokes and rectifiers insure against overheating. Large capacity condensers for wide-range voltage regulation. Instantaneous power for solenoid operation. Two separately filtered DC output sources.

Compact. Sturdy. 18-gauge steel construction. Handsome blue Hammerloid finish. Comes completely equipped including 6' rubber cord and plug. Vastly superior and costs no more than batteries for equal service.

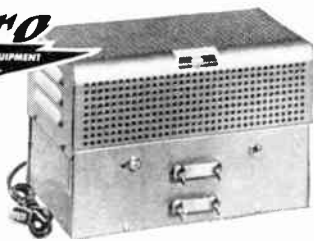Send for complete description of this up-to-the-minute power supply.



Height: 7¾" Length: 11¾"
Width: 7¾" Ship. wt. 31 lbs.

DC OUTPUT

ELECTRO PRODUCTS LABORATORIES

Pioneer Manufacturers of Battery Eliminators

549 West Randolph Street

Chicago 6, Illinois

SMASH Values from MID-AMERICA

Look at these sensational buys in brand-new, unused, top-quality radio parts and electronic equipment. You've never seen big buys like these before! And that's only the beginning. These values are but a few of the hundreds and hundreds of items Mid-America has in stock right now. Write for free catalog. You'll save money!



DACO Tube Tester

Tests performance, leakage and shorts in ALL receiving tubes, even sub-miniature and acorn. PLUS provision for tubes that may be invented. Durable construction is fully shielded; dust-proof case, high-visibility meter. Illuminated chart; no books or charts to be misplaced. Simple, fast operation with positive contact slide-switches; tests EVERY tube element. 110 volt AC. 16½" x 14½". MA-2193. **\$2950**


PORTABLE DACO TUBE TESTER

Same construction and operating features as counter model. Enclosed in sturdy case with durable black leatherette covering. 12½" x 12½". MA-2194. **\$3250**

PHONO AMP and RECORD CHANGER



Inexpensive phono amplifier and record changer with "big set" features. Positive-action Crescent changer handles 10" and 12" records without jamming; finger-tip reject button. Lightweight counter-balanced pickup arm with Shure crystal and lifetime floating sapphire needle. 78 RPM constant-speed motor. 5" PM speaker and high-quality amplifier complete with tubes. Base measures 15½" x 12½" x 6". MA21. Base with motor, turntable and record changer. MA-2192. **\$2395**
\$1495

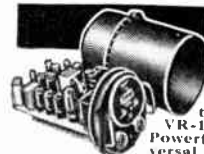

Great Parts Value!

Indicator Amplifier AM-61. All brand new, valuable parts. 15 popular tubes, including: 6SL7GT, 6X4, 6X5, 6X6, 6X8, 6X9, 6X10, 6X99, 6X100. MA-2102. **\$895**



15" HIGH-FIDELITY DYNAMIC SPEAKER

Husky 25-watt dynamic speaker for use where perfect reproduction is desired. Ideal for both indoor and outdoor installations. 12,500 ohm field, 16 ohm voice coil. Regular \$40.00 **\$1895** list. MA-2190.

FM and HAM ANTENNA



AN-104-B. ¼-wave at 100-156 MC; formerly used with SCR-522, 274-N, ARC-5. A pair make an excellent broad-band dipole for FM reception. Coaxial connector in base. Very sturdy; use anywhere. MA-2153. **39c**



Battery Audio Amplifier

Telephone Repeater EE-99-A, designed for telephone and intercom systems, either portable or fixed station. Complete with tubes, battery cable and plugs, carrying case and strap, less batteries. Brand new. MA-E99. **\$1995**

FREE CATALOG

Order now—right from this ad! Send 25¢ deposit—we ship C.O.D. for balance plus postage. Write, too, for Mid-America's big, complete catalog that lists hundreds and hundreds of hard-to-get items—ALL AT UNBEATABLE LOW PRICES! Mail orders and catalog requests to store address—Dept RM-18.

MID-AMERICA CO. Inc.

STORE: 2412 S. MICHIGAN AVE. CHICAGO 16, ILL.
WAREHOUSE: 2307 S. ARCHER AVE. CHICAGO 16, ILL.

→ From Preceding Page

man of the day. This round table meeting was a highlight of the year. Ordinarily not liking to talk when we have a guest speaker, many members had previously withheld good information that came out under Mr. Gregson's direction.

"Another meeting on October 22 was under the chairmanship of Past President P. N. Nibbelin who introduced the speaker of the evening, Mr. Ralph Seilers of Sues Young Brown Company, Zenith Distributor of Los Angeles. His topic was FM circuits and how to balance them. Inasmuch as Mr. Seilers is the head of Zenith Service, he really can pick up the questions and lay down the answers.

"Mr. Seilers introduced Art Kraft of S.Y.B. Company and Sales Representative George Guest of the same company. In order to bring out the points of radio circuits better and to give a more comprehensive explanation of FM problems, Mr. Seilers used a series of slides. This I believe covered the problems completely.

"President Wes Ferrill was in

charge of the meeting."

Harry Ward,
Public Relations

"The Whaling City Chapter of the Radio Technicians Guild has just undergone a reorganization program. At the November meeting, the newly elected officers took over the running of meetings. Al Wobecky is now the new president.

"A lecture on the theory of radio tuned circuits, presented by Frederick S. Baker, electrical instructor at Vocational High School, was featured at the regular monthly meeting of the Radio Technicians Guild held at Carpenter's Hall in November. Albert Wobecky presided.

"John Santos, Harry Wood and Albert Gagnon were appointed as a committee to study the revision of the by-laws, John Santos acting as chairman. Arrangements were made to conduct a Christmas party at the next meeting and to prepare a food basket for donation to some needy family."

James L. Shepley,
Secretary

Electronically Speaking

→ From Page 16

portance to all radio technicians in the United States. It marks the beginning of an organized industry-wide effort to help the serviceman solve the problem being thrust upon him by the advent of FM, television, and other new, expanding,

Every Radioman Needs— "RANGE MASTER" Model 10 The 8-in-1 Service Instrument

A precision instrument for RADIO TESTING, Appliance Repairing, Service Calls, Amateur and Experimental Work.



"RANGE MASTER"

covers these 25 ranges.

- (1) CAPACITY .001-.1, .01-1, .1-10 Mfd.
- (2) A.C. CURRENT 0-.150, 0-.15, 0-15 amps.
- (3) A.C. VOLTAGE 1-10 100 500 1000 volts.
- (4) D.C. VOLTAGE 10 100 500 1000 volts.
- (5) D.C. CURRENT 1 10 100 1000 milliamps.
- (6) RESISTANCE 0 to 10,000 100,000 1 megohm.
- (7) Special High range ohmmeter to 2 megs and 20 megs.
- (8) Sensitive A.C. microammeter to 900 microamps.

TELEVISION SERVICEMEN


Why guess, measure! This is the only instrument in its class that can be used as an OSCILLOSCOPE CALIBRATOR. A standard bleeder will deliver 1-10-100 accurate RMS volts from AC line.

Available in KIT form, or assembled.
Complete KIT and Instruction \$17.95 net
Bench Model (assembled) 23.50 net
Foundation Mefer with 3-color scale, schematic and operating instructions 7.85 net
Test Leads85

Ask your local distributor, or write to Dept. R.M.,
BRADSHAW INSTRUMENTS CO.
942 Kings Highway, Brooklyn 23, N. Y.

Cash in on F. M.

WITH THIS
NEW FRONT END

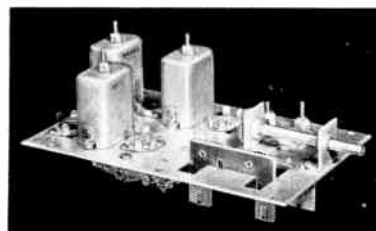

Here's a unit that gives high fidelity, true F.M. . . . Use it to build high quality F.M. receivers for your own use and for re-sale as **PROFITABLE CUSTOM-BUILT JOBS.**

This new F.M. Front End is a complete Tuner and 10.7 mc IF Amplifier on one chassis. A custom-made unit, high quality parts used throughout. **FEATURES:**—Chassis size, 7 1/4" x 4 1/2" . . . Permeability tuned . . . Uses 5 miniature tubes . . . Completely wired and aligned . . . No perceptible frequency drift . . . A 10 microvolt signal will give absolute maximum quieting . . . Can be used with any audio amplifier and power supply.
Model No. FM-2107 — Write today for prices and further details, attention Dept. RM1.

BEACON TELEVISION, INC.
785 Third Avenue, New York 17, N. Y.

phases of the radio industry.

The meeting will be the result of joint effort on the part of the Radio Manufacturers' Association, the Sales Managers Club, the Philadelphia members of the National Electronic Distributors Association, the Mid-Atlantic Chapter, The Representatives, the Federation of Radio Servicemen's Associations of Pennsylvania, the Philadelphia Radio Servicemen's Association and others.

The purpose of the Town Meeting is to provide the radio technicians of greater Philadelphia and all others who wish to attend with the latest technical information and expert advice on various phases of small business management.

H. W. Clough, chairman of the Radio Parts Industry Coordinating Committee, recently stated, "Success of the Philadelphia show will be watched by the entire industry, for too many years, we in the radio industry, preoccupied with the problems of building a new industry in a new and rapidly developing field, have neglected the needs of the radio technician.

"I consider the Philadelphia experiment a significant step forward in terms of industry relations. It is a sign of industrial maturity and a recognition of industrial responsibility."

While the immediate purpose of the Philadelphia meeting is to assist the radio technicians of the Philadelphia area, the program has another and perhaps more important long-range purpose. It is essentially an experiment. According to Harry A. Ehle, chairman of the Coordinating Committee's Subcommittee on the Town Meeting of radio technicians, success in Philadelphia will probably result in a continuing series of similar projects in all the major business centers of the country. According to Mr. Ehle, one of the most encouraging factors encountered during the planning and preparation of the meeting has been the excellent cooperation and total lack of special interest shown by the various groups participating. The program will de-emphasize brand names and all participating manufacturers have agreed to abstain from merchandising during the sessions.

Built for Service



Servicemen's choice!

... the new
"RC-15"

● The new RC-15 Receiving Tube Manual is unquestionably the most authoritative reference guide to receiving-type tubes ever published . . . and it costs only 35 cents!



Successor to the famous "RC-14", it has been extensively revised and expanded. Features RCA's complete receiving line including miniatures and kinescopes. The popular introductory section on tube and circuit theory has been increased to 55 pages. The widely used Resistance-Coupled Amplifier Charts are in improved new form. The completely revamped circuit section gives diagrams and parts values for up-to-date receiver and amplifier designs.

GET YOUR COPY TODAY FROM
YOUR CUNNINGHAM DISTRIBUTOR

Cunningham Tubes

A product of
RADIO CORPORATION OF AMERICA
Harrison, N. J.



BINDERS!

PRESERVE YOUR
RADIO MAINTENANCE
MAGAZINES IN
THEM

RADIO MAINTENANCE
460 Bloomfield Avenue
Montclair, N. J.
Please send me . . . binders at \$2.25
each.

Total amount enclosed
Name
Address
City Zone
State

30,000

SERVICE TECHNICIANS

Read

RADIO MAINTENANCE

Every Month

Every day is

RADIO MAINTENANCE

day in your shop!

RADIO MAINTENANCE
460 Bloomfield Ave.,
Montclair 1, N. J.

Please send me RADIO MAINTENANCE for:

- 2 years at \$5.00
 1 year at \$3.00
 Check enclosed
 Bill me later

Name
Occupation
Address
City Zone
State

BACK NUMBERS

Get Them While They Last

JANUARY 1946

THE PROBLEMS OF ORGANIZATION
TELEVISION RECEIVER INSTALLATION
RADIO MAINTENANCE IN AVIATION
USING THE OSCILLOGRAPH FOR
DISTORTION MEASUREMENTS

APRIL 1946

A MIDGET AUDIO FREQUENCY
OSCILLATOR
IF I WERE A SERVICEMAN
AN EQUALIZED AMPLIFIER FOR
MAGNETIC PICKUPS

MAY 1946

PA SYSTEMS
TEST PANEL FOR THE MODERN BENCH
RINGING THE BELL

JUNE-JULY 1946

FUNDAMENTALS OF TELEVISION
VOLUME CONTROL TAPERS
THE ELECTRONIC OHMMETER
VECTOR ANALYSIS

AUGUST 1946

AVC CIRCUITS
FM TROUBLESHOOTING
TELEVISION RECEIVER FUNDAMENTALS
RECORD CHANGERS

NOVEMBER 1946

PART II TEST & ALIGNING TELEVISION
RECEIVERS
DON'T FORGET THE DIAL LAMP
THE OSCILLOGRAPH . . . HOW TO USE IT
CRYSTAL PICKUPS

DECEMBER 1946

TELEVISION RECEIVERS . . .
THE RF SECTION
TUNING THE INDICATORS
PART II—THE OSCILLOGRAPH
HOW TO USE IT
REPLACING AUTO CABLES

JANUARY 1947

SERVICING BY EAR
TELEVISION RECEIVERS . . . VIDEO
CHANNEL
PART III THE OSCILLOGRAPH . . .
HOW TO USE IT
MINIATURE TUBE CHART

FEBRUARY 1947

THE OSCILLOGRAPH . . . HOW TO USE
IT PART IV
TELEVISION RECEIVERS . . . THE SOUND
CHANNEL
THE AUDIO OSCILLATOR
SELENIUM RECTIFIERS

MARCH 1947

ANTENNAS . . . FM AND TELEVISION
PART I
SERVICING AUTOMATIC RECORD
CHANGERS
OSCILLATORS AND CONVERTERS
TELEVISION RECEIVERS . . . THE VERTICAL
SWEEP

APRIL 1947

ANTENNAS . . . FM AND TELEVISION,
PART II
PHASE INVERTER CIRCUITS
A UNIVERSAL SPEAKER
TELEVISION RECEIVERS . . .
THE HORIZONTAL SWEEP

MAY 1947

THE OPEN AND CLOSE CASES
VOLTAGE DOUBLERS
SIGNAL TRACER
TELEVISION RECEIVERS . . . THE
CATHODE RAY TUBE

JUNE 1947

WHEN THE CUSTOMER ISN'T RIGHT
TEST EQUIPMENT MAINTENANCE
CRYSTAL CONTROLLED SIGNAL
GENERATOR
TELEVISION RECEIVERS . . . THE
POWER SUPPLY

JULY 1947

SERVICING FM RECEIVERS
TEST EQUIPMENT MAINTENANCE, PART II
TELEVISION RECEIVERS . . .
FLYWHEEL SYNC

AUGUST 1947

SPEAKER MATCHING
TEST EQUIPMENT MAINTENANCE, PART III
SERVICING FM RECEIVERS
TELEVISION . . . HF POWER SUPPLIES

SEPTEMBER 1947

AUTO ANTENNA INSTALLATION
ANTENNA SYMPOSIUM
RADIO SERVICING IS BIG BUSINESS
THE TELEVISION PICTURE TUBE
SERVICING FM RECEIVERS

RADIO MAINTENANCE MAGAZINE
460 BLOOMFIELD AVE.,
MONTCLAIR, N. J.

Please send me the back
numbers checked here . . .
I am enclosing 35c for each
copy, or \$2 for any 8 copies,
or \$3.75 for all 16.

- | | | |
|---|--|---|
| <input type="checkbox"/> January 1946 | <input type="checkbox"/> November 1946 | <input type="checkbox"/> June 1947 |
| <input type="checkbox"/> April 1946 | <input type="checkbox"/> December 1946 | <input type="checkbox"/> May 1947 |
| <input type="checkbox"/> May 1946 | <input type="checkbox"/> January 1947 | <input type="checkbox"/> July 1947 |
| <input type="checkbox"/> June-July 1946 | <input type="checkbox"/> February 1947 | <input type="checkbox"/> August 1947 |
| <input type="checkbox"/> August 1946 | <input type="checkbox"/> March 1947 | <input type="checkbox"/> September 1947 |
| | <input type="checkbox"/> April 1947 | |

Have selected 8 copies . . . enclosing \$2.00
 Send me all 16 . . . enclosing \$3.75

NAME
ADDRESS
CITY
ZONE STATE


THIS MONTH'S BEST BUYS IN RADIO!



TEL-OHMIKE

Sprague Model TO-2 TEL-OHMIKE is a complete bridge-type resistance and capacitance analyzer with built-in DC volt-milliammeter. Permits quick, easy and accurate measurements of every resistor and capacitor used in modern electronic equipment. Your cost, \$84.00.

ESPEY MODEL 7-B

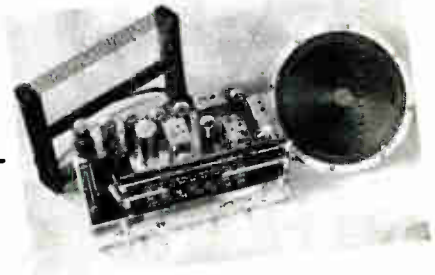


Espey Model 7-B superhet AM-FM receiver features a complement of eleven tubes, including four dual-purpose tubes . . . to give 15 tube performance. Big ten inch Alnico speaker on 13 watt push-pull output gives unusually fine sensitivity. There's AVC, illuminated "slide-rule" dial and loop antenna included along with a folded FM dipole. Stop in to see this fine radio. List is \$140.



NEW HICKOK MODEL 288X

New Hickok Model 288X provides the necessary test voltages for servicing AM, FM and television equipment. Fundamentals are used throughout entire range 100 Kc to 160 mc for FM output, variable audio output, 0 to 15kc is produced by heterodyne type circuit. Your cost \$159.06.

HICKOK MODEL 505

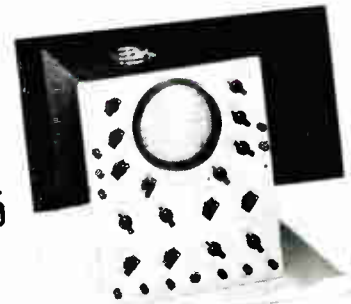

Hickok has the only complete cathode ray oscilloscope with a five inch tube. You can generate an FM signal, align I.F. and R.F. transformers, align discriminator circuits, visually analyze each section of a receiver, trace a signal through, check for gain, and quickly determine cause of trouble. Your cost of Hickok 505 at Almo, \$199.00.

PHONE WRITE OR WIRE TODAY TO:

Phone
LO 3-9225

Almo **RADIO CO.**

509 ARCH STREET
PHILADELPHIA, PENNA.

SAY YOU SAW IT IN RADIO MAINTENANCE!



**We can help
you with
that Job!**

Phonograph pick-ups, motor and other phono parts are included in our stock . . . a stock especially compiled to supply radio servicemen with everything needed. We specialize in good quality . . . all the best lines of products and plenty of each. Any order, large or small, is filled promptly and we guarantee satisfaction. Why not stop in, or call us, or write today? Say you saw this ad in **RADIO MAINTENANCE** and try us for faster, better service!

DYMAC, INC.

RADIO PARTS & ELECTRONIC EQUIPMENT

2329-31 MAIN ST., BUFFALO 14, N. Y.

TEL. PA 2300