

ELECTRONIC SERVICING



MAY
1958 • 50¢











shop hints and service notes

Answers

Schematics

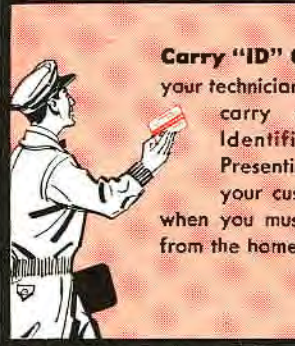JAP-76 655-27 JUN 59SX
ROBERTS RADIO TV SVC
A.C. ROBERTS PROP
1300K RD
PRING MD

How to make more money as an independent RAYTHEON BONDED ELECTRONIC TECHNICIAN

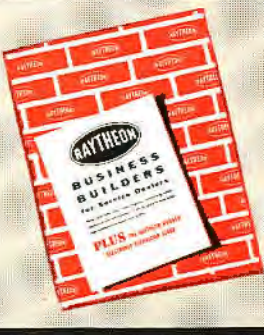 <p>Prominently display your Raytheon Bonded Certificate. It impresses your customers just like a doctor's diploma or lawyer's certificate.</p>	<p>Feature the Raytheon Creed Display and the Bonded Dealer Decal in your windows. The Creed Display shows potential customers your Code of Business Ethics. The Decal identifies you as a nationally advertised Bonded Dealer.</p> 
<p>Carry "ID" Cards. You and your technicians should always carry your Raytheon Identification Cards. Presenting the card puts your customers at ease when you must remove a set from the home.</p> 	<p>Advertise your Bonded Dealer standing. Use the newspaper mats Raytheon makes available to you for local newspaper advertising. Rates are low, results high. Scripts for radio and TV spots are also available to you at no cost.</p> 
<p>Use the Yellow Pages. List your shop as a Bonded Dealer shop in the Classified Telephone Directory — many customers select service dealers from this source.</p> 	<p>Make Mailings to Potential Customers. Raytheon has available to you many attractive Past Card mailers and a special Bonded Dealer self-mailer. Regular mailings stimulate service business.</p> 
<p>Identify your shop. This traffic stopping metal sign will tell all passersby that you are the Bonded Dealer in your community — the Bonded Dealer that Raytheon is presenting to America as the top TV-Radio technician in the country.</p> 	<p>Finally, make the most of the hundreds of helpful sales and shop aids Raytheon has available to you. They're all shown in this Raytheon Business Builders booklet. Get a copy from your Raytheon Tube Distributor, today.</p> 

P.S. If you're not a Raytheon Bonded Dealer call the Raytheon Tube Distributor who sponsors the Bonded Program in your neighborhood. He'll tell you if you can qualify.



RAYTHEON MANUFACTURING COMPANY

Receiving Tube and Semiconductor Operations

NEWTON 58, MASS. 55 Chapel Street
 CHICAGO, ILL. 9501 Grand Ave. (Franklin Park)
 ATLANTA 6, GA. 1150 Zanolite Rd. N.E.
 LOS ANGELES 7, CALIF. 2419 So. Grand Ave.

Raytheon makes all these
 Receiving and Picture Tubes, Reliable Subminiature and Miniature Tubes, Semiconductor Diodes and Transistors, Nucleonic Tubes, Microwave Tubes.



ELECTRONIC SERVICING

VOL. 19, NO. 5

Member

MAY, 1958



Looking for Trouble? by Cyrus Glickstein	3
Answerman	4
RCA KCS 113—Grainy picture Motorola TS 542—AGC problem Admiral 18XP4BZ—Unstable sync Emerson 12038OH—Drive lines Prevention of dust collection on crt face	
Shop Hints and Short Cuts	10
Complete Manufacturer's Schematics	
Studebaker Auto Radio Model AC 2905	11, 12
RCA KCS 100	14, 19
Admiral 16H1	16, 17
Dumont Hi-Fi RA 378/379	21, 22
Video Speed Servicing Systems	23-26
Motorola TS422 Westinghouse V2382	

Entire Contents, Copyright 1958, Cowan Publishing Corp.

COWAN PUBLISHING CORP., 300 West 43rd Street, New York 36, N.Y.

Before you buy any capacitor checker see and try the

ALL-NEW MODEL 97 AEROVOX LC-CHECKER



\$69.95

The all-new Model 97 LC-Checker represents the ultimate in r-f circuit and component testing. In a single instrument it covers the widest range of checking functions. It's the only instrument that will test for capacitance without disconnecting capacitors from the circuit. Incorporates latest printed-circuit techniques.

THE ALL-NEW MODEL 97 LC-CHECKER CAN DO ALL THESE JOBS...

- 1—Measure capacitance and relative "Q" of capacitors.
- 2—Measure capacitor insulation resistance.
- 3—Align r-f and i-f circuits.
- 4—Check super-het oscillator tracking with set "hot-or-cold."
- 5—Align i-f channels in FM receivers and independent alignment of i-f transformers.
- 6—Determine resonant absorption points.
- 7—Locate resonant points in unused portions of coil assemblies in multi-range oscillators.
- 8—Align video and sound i-f systems in TV sets.
- 9—Precise alignment of 4.5 mc intercarrier sound i-f channels.
- 10—Determine natural resonant points of r-f chokes.
- 11—Determine natural period of antennas and transmission lines.
- 12—Measure fundamental crystal frequencies and operation at harmonic levels.
- 13—Measure transmitter buffer, amplifier and tank circuits for parasitic current loops with power off.
- 14—Measure correct wave-trap and filter tuning.
- 15—With a standard plug-in crystal, can be used as an accurate signal generator for signal substitution and precise signal sources.

Write for name of nearest Distributor.

AEROVOX CORPORATION
 DISTRIBUTOR DIVISION
 NEW BEDFORD, MASS.

look what **\$24⁵⁰** buys
in test equipment!



**HEATHKITS
GIVE YOU
TWICE AS MUCH
equipment for
every dollar
invested**

The famous model V-7A Vacuum-Tube-Voltmeter is a perfect example of the high-quality instruments available from Heath at 1/2 the price you would expect to pay! Complete, only **\$24⁵⁰**



Get the most out of your test equipment budget by utilizing HEATHKIT instruments in your laboratory or on your production line. Get high quality equipment, without paying the usual premium price, by dealing directly with the manufacturer, and by letting engineers or technicians assemble Heathkits between rush periods. Comprehensive instructions insure minimum construction time. You'll get more equipment for the same investment, and be able to fill your needs by choosing from the more than 100 different electronic kits by Heath. These are the most popular "do-it-yourself" kits in the world, so why not investigate their possibilities in your particular area of activity! Write for the free Heathkit catalog now!



Contains detailed descriptions of Heathkit models available, including VTVM's, scopes, generators, testers, bridges, power supplies, etc.



Also describes Heathkit ham gear and hi-fi equipment in kit form. 100 interesting and profitable "do-it-yourself" projects!

FREE catalog

Mail coupon below for your copy—Now!

HEATH COMPANY
A SUBSIDIARY OF DAYSTROM, INC.
BENTON HARBOR 29, MICHIGAN

Name _____

Address _____

City & Zone _____

State _____

EDITORIAL STAFF

Sanford R. Cowan Publisher
Oscar Fisch Editor
Irving Tepper Associate Editor
Robert T. Dargan Technical Editor
San D'Arcy Contributing Editor
Paul Goldberg Contributing Editor
Elbert Robberson Marine Communications Editor
Lawrence Fielding Hi-Fi & PA Editor
David Fish Art Director
Selma Uslaner Research

BUSINESS STAFF

Advertising Sales

New York and East
Richard A. Cowan
Jack N. Schneider
300 West 43rd Street
New York 36, N. Y.
JUdson 2-4460

Chicago and Midwest
Jim Summers
Suite 556
Pure Oil Building
35 E. Wacker Drive
Chicago 1, Ill.
ANdover 3-1154

West Coast
Ted E. Schell
2700 West 3rd Street
Los Angeles 57, Calif.
DUnkirk 2-4889

Charles W. Hoefler
1664 Emerson Street
Palo Alto, Calif.
DAvenport 4-2661

Charles W. Gardner, Jr. Production Mgr.

CIRCULATION

Harold Weisner Circulation Mgr.
Carol J. Blinderman Ass't Circulation Mgr.
Rose Mercurio Circulation Dept.

ELECTRONIC SERVICING (formerly Radio-TV Service Dealer) is published monthly by Cowan Publishing Corp., 300 West 43rd Street, New York 36, New York, JUdson 2-4460. Subscription Price: \$2.00 one year, \$5.00 two years in the United States, U. S. Possessions, Canada and Mexico. Elsewhere \$1.00 per year additional. Single copies 50¢. Second Class Mail privileges authorized at New York, N. Y. Copyright 1958 by Cowan Publishing Corp.

POSTMASTER: SEND FORM 3579 TO
ELECTRONIC SERVICING, 300 WEST
43rd STREET, NEW YORK 36, N. Y.

ELECTRONIC SERVICING • MAY, 1958



Looking for Trouble?

by Cyrus Glickstein*

Second of a series presenting useful and practical service information in an entertaining manner. Can you solve the problem?

TRY your hand at fixing TV sets by remote control simply by answering the questions in this TV trouble-shooting quiz. A defective receiver is being serviced on the bench and the quiz follows the usual servicing procedures. To make the quiz more interesting, it is suggested that each question be answered before going on to the next and all questions answered before referring to the answers. If there is more than one correct answer to a question give all the correct answers. The answers, discussion and trouble-shooting hints follow after the questions.

Receiver: Spartan, Chassis 23U214, transformer-type low voltage power supply.

Complaint: Blank screen, sound output present.

Questions:

1. The set, which is tuned to an active channel, is turned on. The screen is blank but sound is heard. Turning up the brightness and contrast controls have no effect on bringing in a picture or raster.

A blank screen with sound present can be caused by a defect in the:

- a. High voltage power supply;
- b. Low voltage power supply;
- c. Horizontal sweep circuit (horizontal oscillator, horizontal output, damper);
- d. Video section (video if stages, video detector, video amplifier, crt);
- e. *agc* circuit (*agc* stage or stages).

Control Action

2. To clarify which section is probably defective on the basis of the observed symptoms, the most important control(s) to check next is (are):

- a. Horizontal drive;
- b. Channel selector and fine tuning;
- c. Width;
- d. *agc* (performance) control;
- e. Vertical hold.

3. The volume seems normal but there is a 60-cycle buzz in the sound. As the fine tuning control is varied on the channel to which the set is tuned, small streaks of light flash on the screen. When the channel selector is turned to an inactive channel, a normal raster fills the screen and the normal background rushing noise can

be heard, with no buzz or hum.

On other active channels, which normally produce strong signals, the same symptoms as described above are noted—blank screen with sound output containing a buzz. On a weaker channel, a dark, over-contrasty picture is visible and the sound has the usual buzz.

The brightness control has the normal range of control on inactive channels but has no effect on unblanking the screen on active channels. Varying the contrast and *agc* (performance) controls on active channels had no effect on unblanking the screen. On a weaker channel with the over-contrasty picture, rotating the *agc* control had no effect on picture or sound, while turning the contrast control to minimum blanked out the screen but had no effect on the sound.

The symptoms point to trouble in:

- a. Video section;
- b. Front end (*rf* amplifier, *rf* oscillator, mixer);
- c. *agc* circuit;
- d. Horizontal sweep circuit;
- e. High voltage power supply.

4. The following tubes were changed: *rf* amplifier, 1st and 2nd common if amplifiers, keyed *agc* and 1st audio. The symptoms remained unchanged. An oscilloscope applied to the video detector load, video amplifier plate, and to the plate and control grid of the *agc* keyer tube showed the waveforms in Fig. 1.

Voltage Analysis

Voltage readings around V7, the *agc* [Continued on page 6]

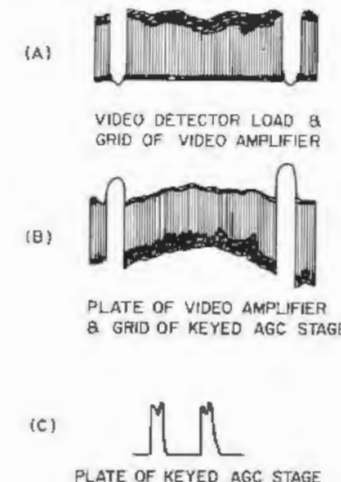


Fig. 1—Waveforms as seen in the video amplifier and *agc* stage.

LEADING
SET
MAKERS
SPECIFY
TUNG-SOL

HIGH
IN PERFORMANCE



TUNG-SOL[®]
Magic Mirror Aluminized
PICTURE TUBES

ELECTRON TUBE DIVISION **TUNG-SOL ELECTRIC INC.**
NEWARK 4, NEW JERSEY

ANSWERMAN

Answerman
Dear Sir:

My problem is in the picture of a new receiver. The presentation contains something which is in appearance similar to "snow" as is commonly seen when the signal strength is weak. However, my trouble is not exactly of that nature because the signal I am receiving is quite strong and the same effect does not appear on other receivers I have in my shop. In fact, I have noticed that this so called "snow" disappears when the picture modulation is removed as during a program change or when a commercial is about to be switched on. That is, a blank screen does not exhibit the "snow." If the trouble was being caused by a weak signal the "snow" would remain with the removal of the picture information. On this basis I believe the trouble is in the receiver, but I am at a complete loss to know what to do about it. The receiver uses the RCA KCS113 chassis.

C. O.
Houston, Texas

As you point out the problem is not that of a snowy picture as could be caused by a weak *rf* tube, improper *agc* bias or an open antenna line. What you evidently are experiencing is termed "picture agitation" and is frequently also called graininess or background noise. Picture agitation is the result of a noise voltage being prevalent along with the video voltage and is frequently seen in some closed circuit TV systems. On TV receivers with narrow *if* and video bandpass circuits the noise is not visible because the high frequency information is not presented in the picture and thus the snow is not presented as a grainy background. On the other hand it can be seen on high resolution receivers that have the ability to present a broad band of video frequencies.

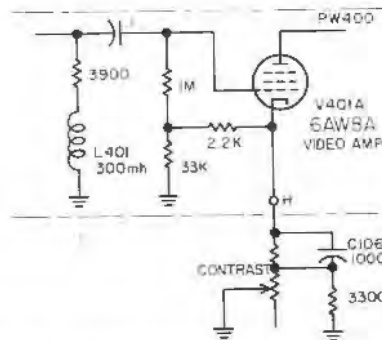


Fig. 1—Partial schematic of RCA KCS 113 video amplifier

Since the background noise is transmitted as modulation along with the video signals the receiver cannot be considered to be at fault. However, since the noise is presented because of the receivers' ability to present all of the transmitted video it is possible to modify the receiver, to reduce the bandpass and thus block the presentation of the high frequency noise. The changes necessary are shown in Fig. 1 and involve two components, L401 and C106. Inductance L401 should be changed to 120 microhenries and condenser C106 should be changed to 330 *u*f.

Dear Mr. Answerman:

I have a condition in a TV receiver that is causing me considerable difficulty. The picture is poor with a small

amount of smear and the receiver performs as though the *agc* circuit wasn't functioning, in that the picture is overdriven with full contrast. I know there is trouble in the *agc* circuitry and that the *agc* voltage is insufficient because I am able to compare it with an identical properly functioning model I have along side this one on my repair bench. Unfortunately, I can't determine whether the trouble is occurring in the *if* strip or not. In addition, the sync action is somewhat disturbed by video. Some of the voltages in the video amplifier and *agc* circuit differ a small amount from the properly operating receiver. It is difficult to determine whether I have one common trouble or two separate ones. The receiver is a Motorola chassis TS-542.

B. T.
Miami, Fla.

Although the possibility exists that two different circuit failures are causing the improper operation of the receiver it is not likely. Rather, one component failure is most probably causing the entire problem. The circuit where the component failure is probably occurring is the video plate load resistor, R126 shown in Fig. 2. The resistance increased in the video amplifier, the smear or loss of high frequency components of the video signal would result with an accompanying larger sync signal to disrupt the sync action. In addition, the *agc* amplifier would be affected by the reduced voltage applied to the suppressor, again the result of a resistance increase in the

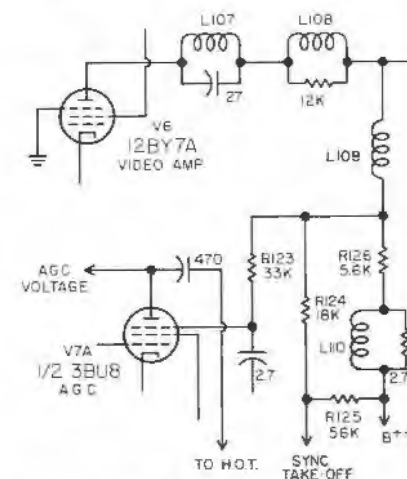


Fig. 2—Motorola TS542 *agc* and video amplifier circuit

video plate load resistor, R126 shown in Fig. 2. The reduced suppressor voltage would lessen tube conduction and cause the circuit to develop less *agc* voltage. On the basis of this analysis the resistors in the involved circuit are R124, R125, R126 and the parallel combination of inductance L130 and the 2.7K resistor. If either R124 or R125 had changed value the above mentioned symptoms would not be produced. An increase in their resistance would affect the sync voltage but not the video signal and the *agc* voltage. On the other hand, if resistor R126 shown in Fig. 2 should increase or become open the symptoms described would develop. It is suggested that resistor R126, a 5.6 K resistor be checked.

[Continued on page 30]

LEADING
INDEPENDENT
SERVICE
DEALERS
CHOOSE
TUNG-SOL

LOW
IN CALLBACKS



TUNG-SOL[®]
RECEIVING TUBES

ELECTRON TUBE DIVISION **TUNG-SOL ELECTRIC INC.**
NEWARK 4, NEW JERSEY

LOOKING FOR TROUBLE?

[from page 3]

stage (Fig. 2) taken while the set was tuned to an incoming signal showed the following:

Measured Voltages—V7 (With Signal)

Cathode (pin 7)	146 v
Control grid (pin 1)	146 v
Screen grid (pin 6)	465 v
Plate (pin 5)	0.6 v

On the basis of the above, the general location of the trouble seems to be in the:

- a. input line from the horizontal output transformer to the plate of the *agc* keyer tube;
- b. video amplifier line connecting to the grid of the *agc* stage or elsewhere in the video section;
- c. cathode circuit of the *agc* stage;
- d. *agc* bus;
- e. +150-volt line of the low voltage power supply.

5. To narrow down further the possible location of the trouble, the following resistance readings were taken around the *agc* stage (normal resistance of 150-volt line to ground approximately 30K):

V7 Resistance Readings (To Ground)

Cathode (pin 7)	32K
Control grid (pin 1)	90K
Screen grid (pin 6)	360K
Plate (pin 5)	176K

A further resistance check at test point 7 (across capacitor C48) gave a reading of 2.9K.

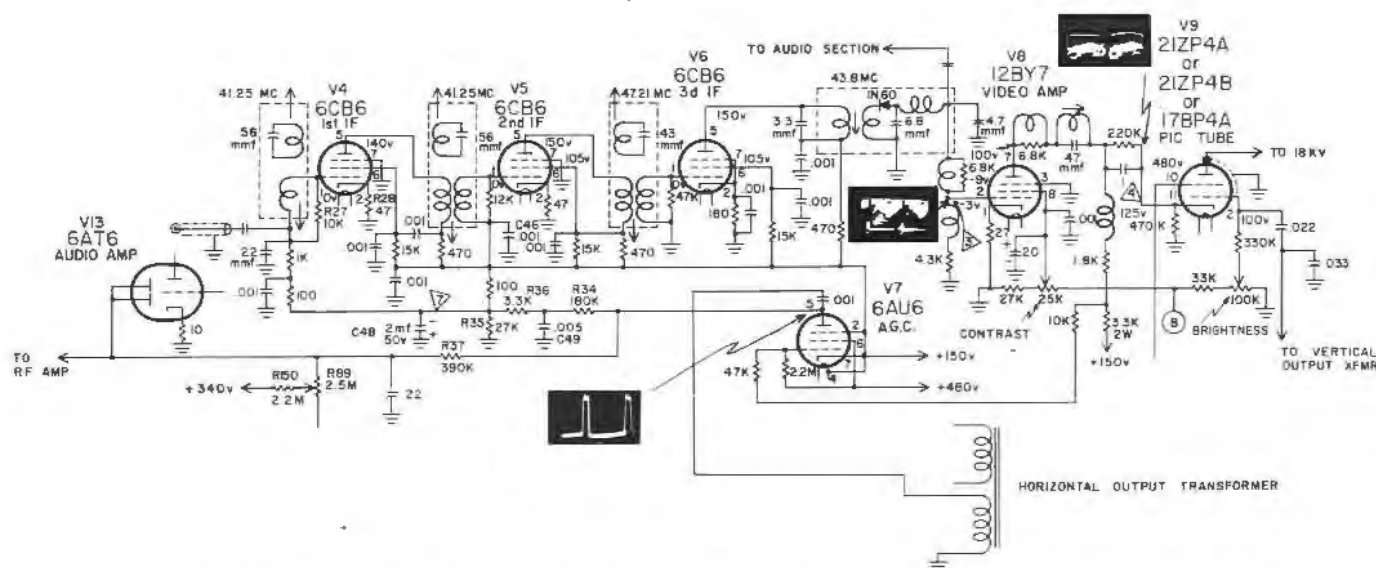


Fig. 2—Partial schematic of the Spartan chassis 23U214 showing the video and the keyed *agc* stages.

On the basis of the above readings, the most likely cause of trouble is:

- a. Shorted C49;
- b. Shorted C48;
- c. Short across R34;
- d. Open R35;
- e. Open C46 (grid circuit of V5).

Answers and Discussion

1. a, c, d, e

A blank screen with sound present can result from a fault in several sections of the TV set. A defective high voltage power supply can cause a blank screen with sound remaining normal by not supplying the necessary high voltage to the *crt*. The blank screen would be present on all channels—active and inactive.

A faulty low voltage power supply usually affects the sound, picture and raster.

A fault in the horizontal sweep circuit causes a blank screen when the horizontal sawtooth signal is lost or distorted and either insufficient or no high voltage is developed. Usually, sound output is normal. But a fault in the horizontal circuit may also cause a loss of sound on active channels where the set uses keyed *agc* and the sound takeoff is in the plate of the video amplifier. In such cases, the symptoms of blank screen and no sound may be somewhat confusing. The reason for the loss of sound is exactly the same as outlined above in the description of *agc* faults. A keyed *agc* stage receives its keyer pulse from the horizontal sweep circuit. Loss of this pulse causes a complete loss of *agc* bias. With no *agc* bias, there is excessive video amplification, and the large signal at the video detector cuts off the video amplifier. Since the

screen is blank anyhow, this has no effect as far as the video signal is concerned. However, if the sound takeoff is at the video amplifier plate, there is also a loss of sound.

Video Amp Faults

Two video section troubles can cause a blank screen with normal sound—a faulty video amplifier stage and a defective *crt* (or circuit associated with the *crt*). A defect in the video amplifier stage of certain sets (a fault such as an open filament, open coil in the 4.5 mc trap in the plate, etc.) can produce a blank screen on all channels. If the video amplifier plate is direct-coupled to the *crt* cathode, the loss of video amplifier plate current causes a more positive voltage at the junction of the plate circuit and the *crt* cathode circuit, raising the voltage at the *crt* cathode and thereby possibly causing the picture tube to cut off (see Fig. 2). In addition to the blank screen, there is a loss of sound on all channels if the sound takeoff circuit is in the plate of the video amplifier stage. However, if the sound takeoff coil is in the video detector circuit, the symptoms would be a blank screen with normal sound.

A defective *crt* (open filament, etc.) can cause a blank screen and normal sound, as can a defect in the circuits associated with the *crt*. Faulty brightness control circuit, incorrect ion trap placement are some other possibilities.

AGC Faults

A defect in the *agc* circuit which causes a complete loss of *agc* voltage may result in extreme amplification in the video channel, since no *agc* bias

is applied to the controlled *rf-if* stages. An extra-large video signal appears at the video detector (Fig. 3) and is direct-coupled to the control grid of the video amplifier stage. Since this detected video signal is a pulsating negative *dc* voltage, it provides bias as well as a signal to the video amplifier grid. Because of the large negative voltage, the video amplifier stage may be almost or completely cut off, thus causing the loss of video. In addition, the higher voltage at the plate due to the drop in plate current is, in many sets, direct-coupled to the *crt* cathode, cutting off the *crt* and causing a blank screen on active channels. Of course, when the set is tuned to an inactive channel, a normal raster is visible. Furthermore, if the sound takeoff coil is at the video amplifier plate, there is a loss of sound as well. If the sound takeoff coil is in the video detector circuit, sound is present on active channels but usually with a noticeable buzz because of the large amplitude of the 60-cycle sync pulses in the detected video signal.

In some receivers, the detected video signal may not be large enough to cut off the video amplifier stage. In such cases, either a weak picture is seen if the video amplifier is biased close to cutoff or an over-contrasty picture is seen if the bias is not large enough to reduce the amplification of the stage substantially. In either case, sound is usually heard, approximately at normal volume but possibly distorted and generally with a pronounced 60-cycle buzz.

Blank Screen

The methods for localizing the faulty section when sound is present but the screen is blank are discussed in the following answers.

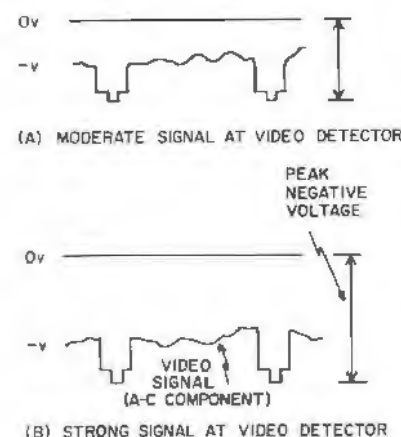


Fig. 3—Peak voltages with normal and excessive video signals.

important ANNOUNCEMENT about the TOBE contest ads on the next two pages!




Did you know that Tobe is the fastest growing service capacitor line in the U.S.? Even so, we still are getting letters every day from dealers who want to enter our big 50-Prize contest (see ad on next spread) but can't... because their nearest distributor is not yet stocking new Tobe Service Capacitors.

For this reason we are *extending* the Tobe contest from May 30 to June 30—and *making a very special offer besides!* We want YOU to have a chance at that Ford Ranch Wagon, the mink stole and all the other prizes. And we want you to familiarize yourself with Tobe—since 1922 one of America's most popular original equipment capacitor lines.

SPECIAL OFFER! THREE FREE CAPACITORS.

Send in your contest entry (entry blank on next page) today... *without a boxtop*. It only takes a minute to write a good entry. Enclose with your entry an order for any Tobe capacitor described below. We will remove the boxtop and attach it to your entry. Send no money—we will bill you through your distributor. And we will also include, with your Tobe Capacitor, *three* of our tough little "Tobemite" molded plastic tubulars for popular applications *absolutely free*. Send in your entry—and order as many Tobe's described below as you want—today!

WRITE FOR THESE TOBE SERVICE CAPACITORS TODAY (all prices are dealer net)

 <p>TWIST-PRONG BASE ELECTROLYTICS</p> <p>Each with a bakelite and a metal mounting washer. Popular "Preferred Type" plan.</p>	 <p>"JET" ELECTROLYTIC TUBULARS</p> <p>Tubular electrolytics hermetically sealed into aluminum containers protected in a transparent red plastic sleeve.</p>	 <p>MYLAR * TUBULARS</p> <p>These brilliant capacitors are ideal for use in humid climates—thanks to DuPont's Mylar, world's finest insulation.</p> <p>*A DuPont Trademark</p>
<p>ALSO: Metal Cased Paper Capacitors, Threaded Neck Capacitors, Disc Ceramic Capacitors, Metal Cased Tubulars, Phenolic-Cased Printed Circuit Capacitors.</p>		
<p>YOU'LL RECEIVE FREE: 3 "TOBEMITE" MOLDED PLASTIC TUBULARS in popular applications. These are America's finest molded tubulars, and they're far smaller than other equally rated capacitors.</p>		

TOBE SERVICE CAPACITORS

CLIP THIS ORDER FORM TO YOUR CONTEST ENTRY BLANK (SEE NEXT PAGE)

TOBE DEUTSCHMANN, Service Division, 2900 Columbia Ave., Indianapolis 5, Ind.

Please send me _____ Tobe Replacement Service Capacitors as follows:

Quantity	Indicate Rating & Characteristics
Mylar	
Jet Electrolytic	
Twist-Prong	
Tobemite	

Remove the boxtop before shipping and hold with my contest entry attached.

Please send me the complete Tobe Capacitor Catalog.

FIRM NAME _____

ADDRESS _____

CITY _____ ZONE _____ STATE _____

SIGNED _____

MY JOBBER IS _____

I understand I will also receive 3 Tobe Molded Tubular Capacitors absolutely FREE. My jobber will bill me for the other capacitor(s) indicated. (Offer ends midnight, June 30, 1958.)

25 WORDS



Tell Why You Like Tobe Service Capacitors

Your 25 words can win the Ford Ranch Wagon

And Here Are the TSC* Features to Help You Win • No standard materials can possibly enter the manufacture of TOBE SERVICE CAPACITORS, because *everything* is quality-checked beforehand • Highest grade dielectric materials prevent voltage breakdown in service • TSC's are designed for high-temperature operation — will not dry out or deteriorate in service • Copperweld leads soldered directly to foil insure you against opens • Moisture-tight seals guard against shorts • Pigtail leads will not pull out or break off • No danger of hot soldering iron opening internal connection or melting sealing compound • TSC's will maintain specified capacity over entire operating temperature range • TSC's receive 100% quality-control inspection prior to shipment • Continuous production-line testing automatically rejects "duds" • Maintenance of large inventories on complete line means faster delivery to your TOBE DISTRIBUTOR and you.



HERE'S YOUR
ENTRY BLANK

Tobe Deutschmann Corporation, Dept. C
2900 Columbia Avenue, Indianapolis 5, Indiana

"I prefer Tobe Service Capacitors in my work because _____

NAME _____

ADDRESS _____

CITY _____ ZONE _____ STATE _____

I enclose a Tobe boxtop

2. b
To determine which of the four circuits mentioned above is probably faulty, the set is turned on and the initial symptoms noted. The most important checks in the order named are:

1) Turning up the brightness and contrast controls to check if a picture or raster can be brought in. The volume control is varied to determine if sound is approximately at the normal level.

2) Rotating the channel selector and fine tuning to check the situation on both active and inactive channels. If sound is normal but there is no picture or raster on any channel, the trouble is probably in the high-voltage power supply, the horizontal sweep circuit, video amplifier stage, *crt* or circuit associated with the *crt*. A faulty *agc* circuit is indicated if there is a normal raster and normal background sound on inactive channels but a blank screen with normal sound (or sound with a buzz or no sound) on active channels.

3) If a weak or over-contrasty picture is found on any active channel, the contrast and *agc* controls are rotated through their range to note the effect on the picture. If varying the respective control does not have the usual effect, this points to possible trouble in the associated circuit.

The horizontal drive control is rotated usually to check faults such as low brightness, overdrive line(s) on raster, non-linearity, etc. Rotating the vertical hold control is important only when a picture is visible and a check is being made on the hold-in range. The width control also is checked mainly when there is insufficient width or a horizontal sweep trouble is evident in the picture and raster.

3. c
The symptoms point to trouble in the *agc* circuit. As noted above, an over-contrasty picture on some active channels and a blank screen on others is caused by an excessive signal applied to the grid of the video amplifier stage. In sets where the plate of the video amplifier is not directly coupled to the cathode of the *crt* (*rc* coupling used), the symptoms may be no picture, normal raster on an active channel in a strong signal area. A complete loss of sound may also occur if the sound takeoff coil is in the plate of the video amplifier. When the sound takeoff is in the video detector circuit, sound is present on all channels but usually with a buzz.

Oscilloscope Checks

4. d
A number of precautions are ad-

ELECTRONIC SERVICING • MAY, 1958

visible in making checks on *agc* circuits.

In the first place, it is important to keep in mind that oscilloscope checks may be misleading if they are not carefully analyzed. For example, a correct waveshape is found at the plate of the keyer tube while the video signal at the control grid is obviously distorted (Fig. 1). This may seem to indicate that the trouble is in the video line connected to the grid of the keyer stage or in the preceding video section. However, the fact that a correct waveform appears at the plate of the keyer tube does not necessarily mean that there is no fault in the *agc* bus. Many faults in the *agc* bus do not affect the plate waveform but cause a loss of *agc* bias. This loss of bias results in excessive video amplification which, in turn, causes a distorted video signal (or no video signal) to be applied to the grid of the keyer stage. In such cases, the defective video signal applied to the *agc* tube grid is an effect of the basic trouble, not the cause.

This does not mean that oscilloscope checks are misleading for *agc* troubles. They simply must be interpreted correctly. In this case, the scope definitely helped localize the trouble. It established the fact that the keyer pulse at the plate is normal while the video signal at the grid is abnormal, thereby ruling out the possibility that the trouble is caused by a fault in the horizontal keyer pulse input to the *agc* stage. The checks therefore pointed to possible trouble in the *agc* bus.

Pix Bend

In cases of picture bend or video pickup (lines in the picture, etc.), it is advisable to apply the oscilloscope to the *agc* bus to check for the presence of hum, poor filtering of the *agc* bias voltage, etc. Any *ac* component in the *agc* line points to a defect in the *agc* filter circuit or in components connected to this line.

AGC Voltage Analysis

In taking voltage checks around the *agc* stage, an additional precaution should be kept in mind. *Agc* voltage readings are most helpful when taken with a signal coming in; that is, with the set connected to an antenna and tuned to an active channel, even if the screen is blank and there is distorted or no sound output. A defective keyed *agc* stage may have almost the same voltage readings as a normal stage with no signal coming in (set

[Continued on page 27]

ELECTRONIC SERVICING • MAY, 1958

WIN THIS FORD



RANCH WAGON

Or one of 49 other valuable prizes

Here's all you do... In 25 words or less, tell us why you prefer TOBE SERVICE CAPACITORS.

Then, send your entry to us with the top from any TOBE capacitor carton, or the plastic box some TOBE capacitors are packed in.

That's all there is to it. Enter as many times as you wish, providing each entry is accompanied by a TOBE carton top or the plastic box. Use entry blank below. Additional entry blanks can be obtained from your TOBE DISTRIBUTOR.

Contest Closes June 30

Contest is open to all service-men over 21 years of age residing in the continental United States. Employees of the TOBE DEUTSCHMANN CORPORATION and their advertising agency are excluded. All entries become the property of TOBE DEUTSCHMANN CORPORATION. Decisions of the judges are final. In case of ties, duplicate prizes will be awarded. Contest closes June 30, 1958. Winners will be announced July 31st.



HERE'S YOUR
ENTRY BLANK

Tobe Deutschmann Corporation, Dept. C
2900 Columbia Avenue, Indianapolis 5, Indiana

"I prefer Tobe Service Capacitors in my work because _____

NAME _____

ADDRESS _____

CITY _____ ZONE _____ STATE _____

I enclose a Tobe boxtop

CORNELL-DUBILIER VIBRATORS



Built to last... a type for every radio

The C-D brand name on a vibrator is your guarantee of dependable performance, long trouble-free service. Because C-D vibrators are built to last, you can use them with full confidence. That's why it pays to reach for a C-D when a replacement is called for.

Remember, too, that there's a C-D vibrator type for every make and model car on the road. And the C-D VIBRATOR REPLACEMENT GUIDE makes it quick and easy for you to select the exact type required. Ask your local C-D distributor for a free copy of VIB-3, or write to Cornell-Dubilier Electric Corp., South Plainfield, N. J. Dept. ST-48B.




CORNELL-DUBILIER VIBRATORS

Old Hands at Dependability


Shop Hints and Short Cuts

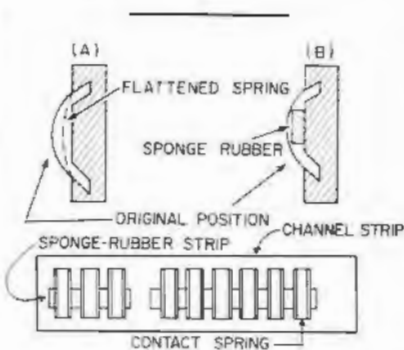We would welcome hints and short cuts from our readers. ES will pay \$5 for each hint used. Sorry, but we cannot be responsible for unaccepted material. In case of duplication, first received will be accepted.



After use, the contact springs in the Neutrode Tuner flatten out and are pushed into the upper groove, as shown in (A). The bottom part of spring is rivetted to the channel strip and connections. After the contact spring is brought back to the original position, a sponge-rubber strip, shown in (B), is placed under the contact springs. When the drum is revolved, the sponge-rubber is soft enough to allow a good wiping contact, and firm enough to push out the thin contact spring, between channels. Two pieces of sponge rubber are required. Each is 1/4" wide, and 1/2" thick.

H. H. Brooklyn, N. Y.

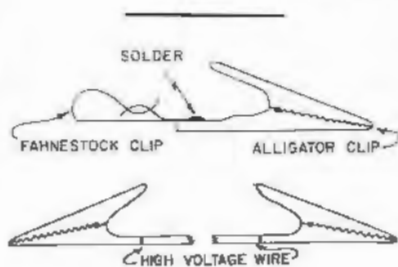


I frequently find it necessary to insert parts in a TV or radio chassis, temporarily, for test purposes. Soldering the part in is time consuming, but wrapping the pigtails is unreliable.

[Continued on page 28]


1958 STUDEBAKER MODEL AC-2905
1958 STUDEBAKER-PACKARD MODEL AC-2906
1958 STUDEBAKER-PACKARD MODEL AC-2907

STUDEBAKER

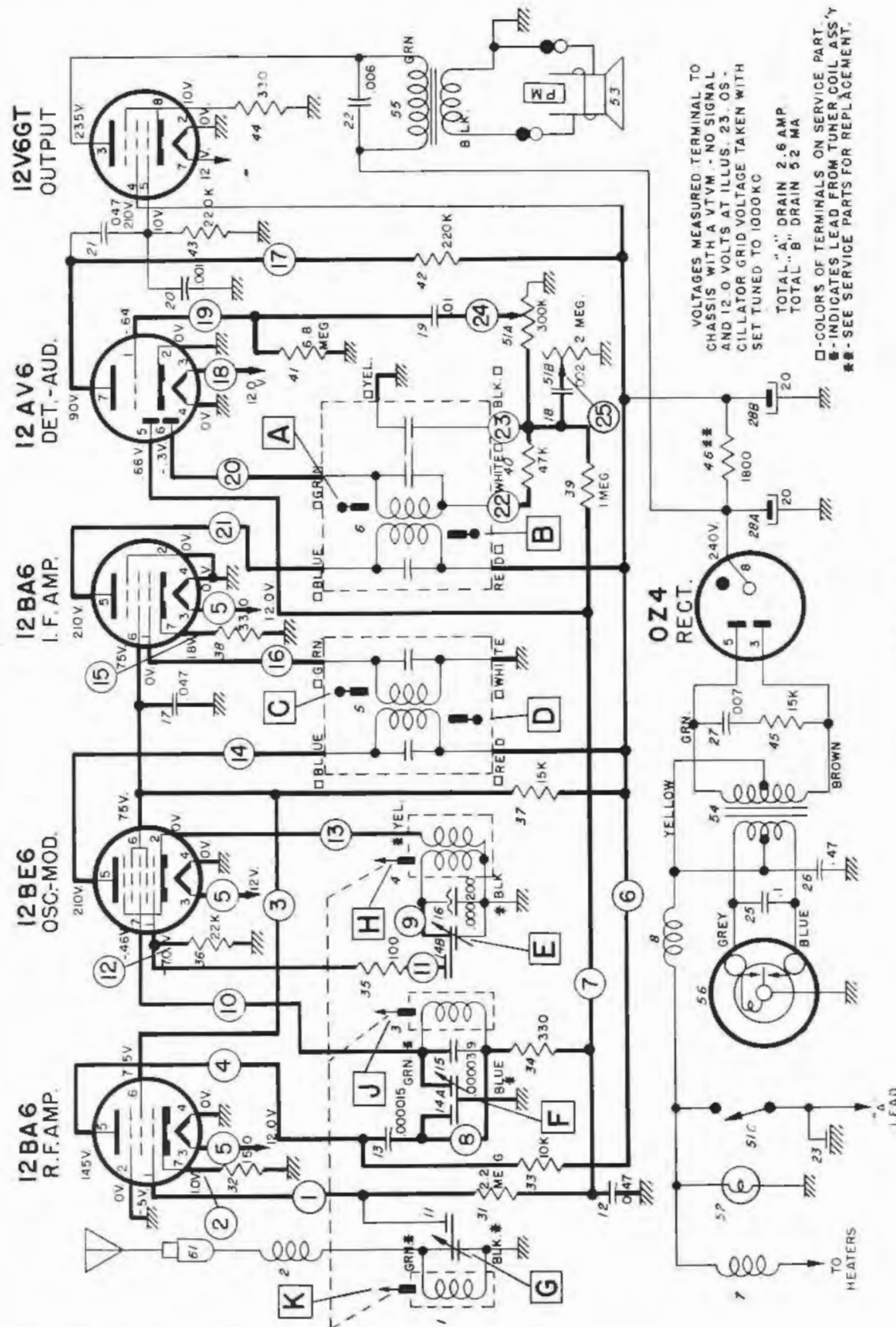


STUDEBAKER AC-2905

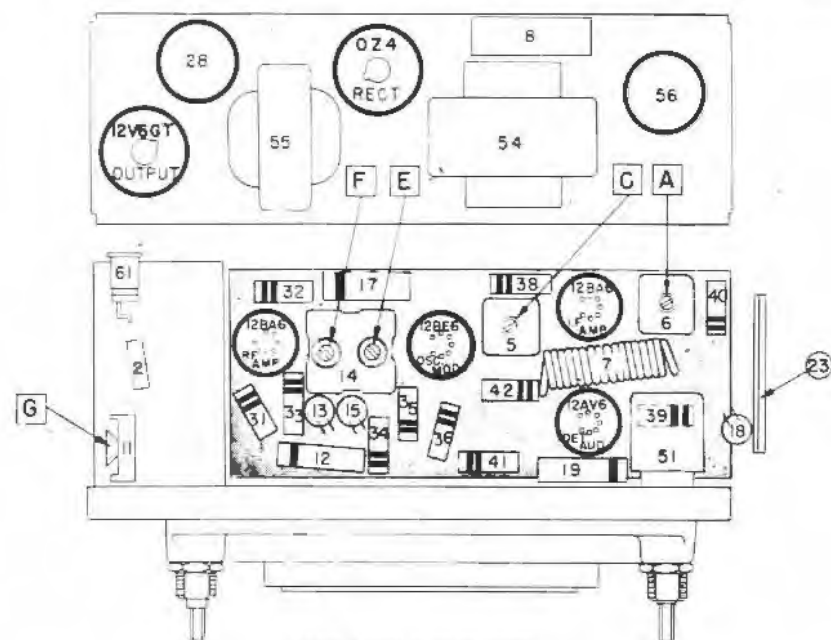
1958 STUDEBAKER MODEL AC-2905
 1958 STUDEBAKER-PACKARD MODEL AC-2906
 1958 STUDEBAKER-PACKARD MODEL AC-2907




PARTS LAYOUT—TUBE VIEW

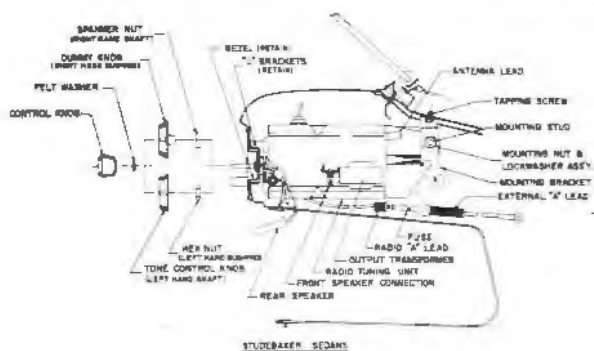

STUDEBAKER SEDANS

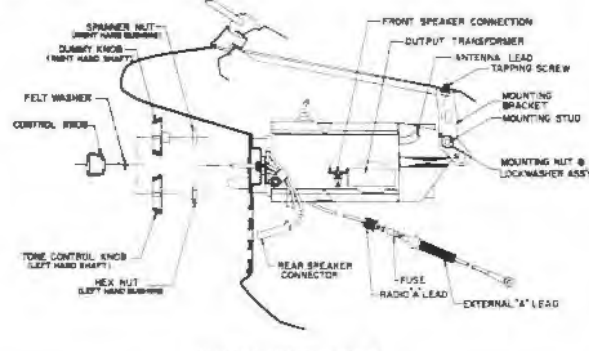

PACKARD & STUDEBAKER COUPES

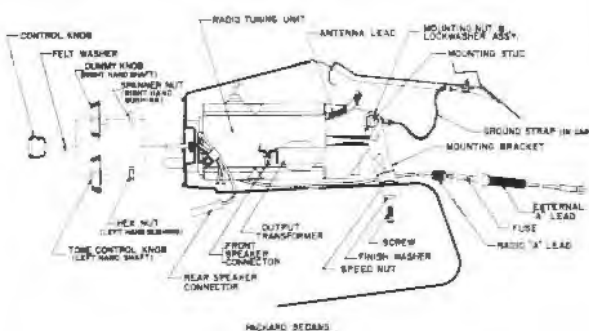

PACKARD SEDANS

Suppression Equipment—

- Generator capacitor (Part #1925118)
- Voltage regulator capacitor (Part #1931648)
- Ignition coil capacitor (Part #1931648)
- Fuse, 7½ amperes (Part #455640)

Mounting—

These models are one unit sets with a separate speaker. The receiver unit is held in place by a mounting bracket at the rear of the set and the two control bushing nuts.

The speaker is held in place by four studs on the back of the instrument panel and four nuts and lockwashers.



In removing the receiver, the glove box must be removed except on the cars which have the Fiberglass instrument panel, the speaker lead must be disconnected from the connector on the output transformer, and the

"A" lead must be removed from the external "A" lead connector. Also disconnect the antenna lead-in from the connector next to the mounting bracket at the rear of the set.



The antenna trimmer is located on the bottom of the receiver and may be adjusted through the hole in the top of the glove compartment.

FRONT CHASSIS WIRING VIEW

Chassis No. KCS100B, KCS100D or KCS100K

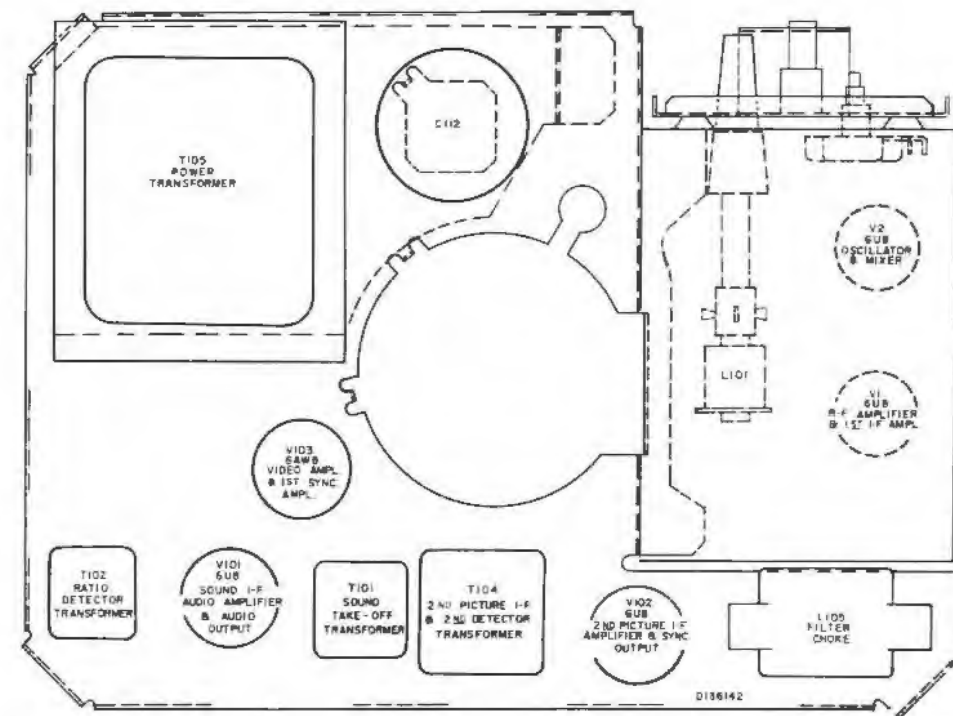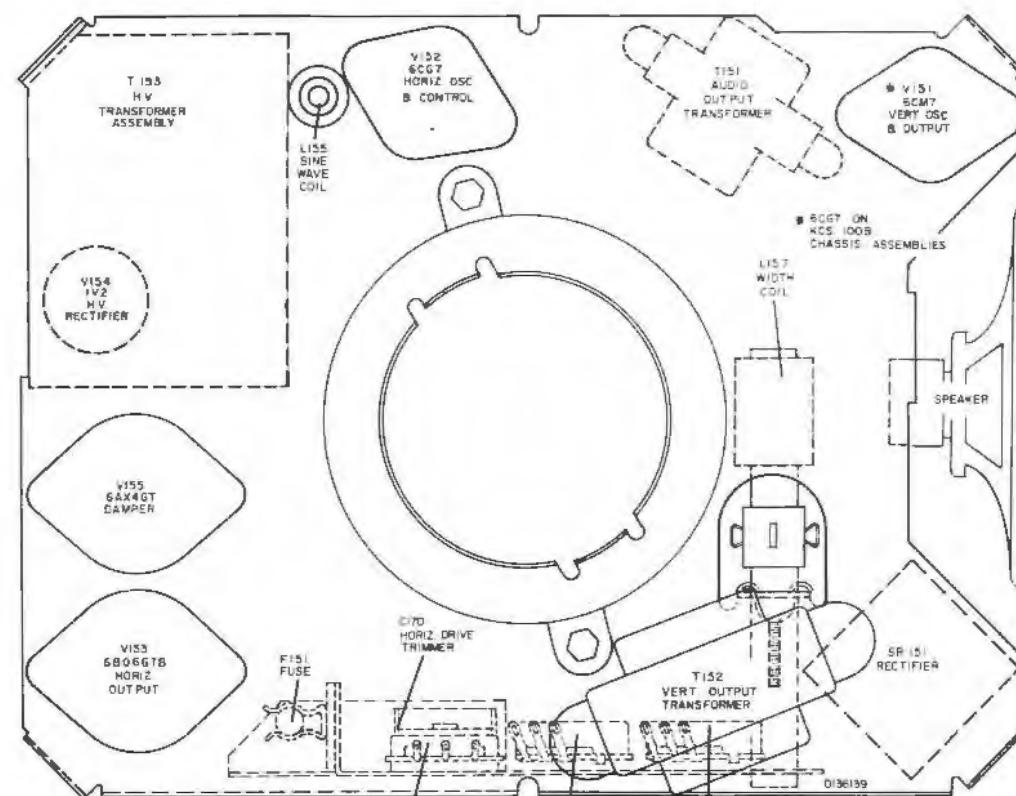

Rear Chassis (Tube side)

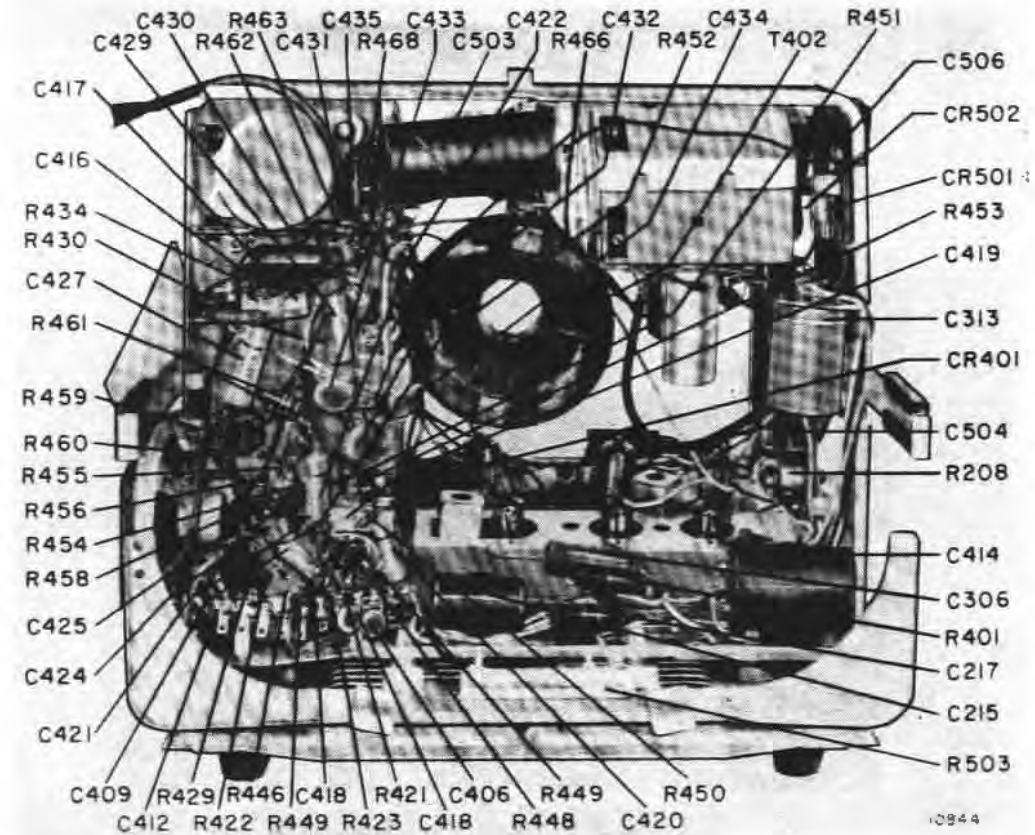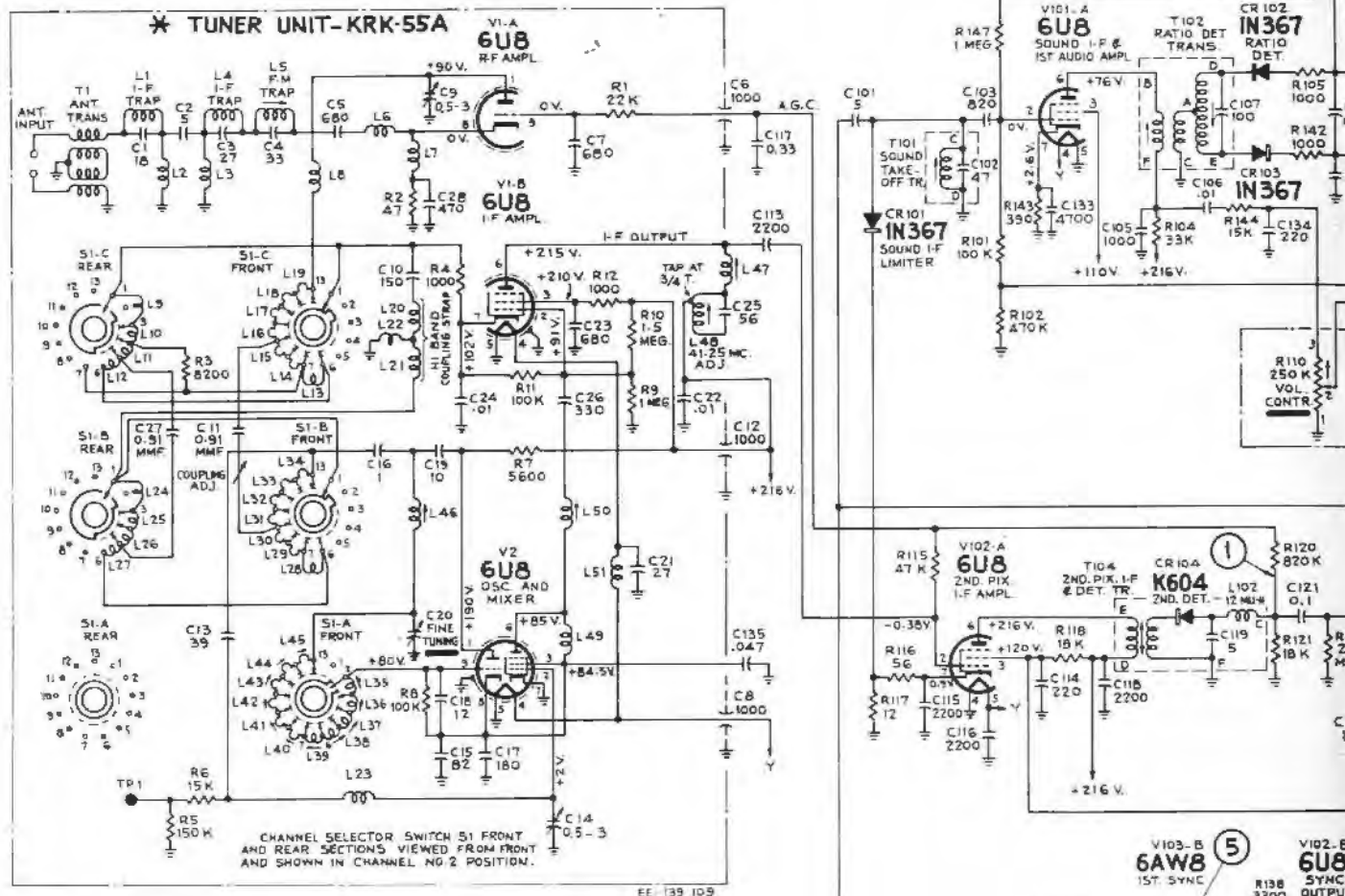

Wiring Side of 14" Picture Tube Chassis.

PRODUCTION CHANGES IN KCS100B CHASSIS


- In some receivers the following differences exist from the latest schematic shown above:
- C160 . . . connected to the junction of the Horizontal Yoke Coils L153 and L154 . . . was 68 mmf.
- C175 . . . at terminal F of L157 Width Coil . . . was .033 mf.
- R154 . . . at pin 6 of V151A Vertical Oscillator . . . was 1 megohm.
- R157 . . . at the junction of C132 and C155 in kinescope screen circuit . . . was 15,000 ohms.
- R165 . . . connected between L157 Width Coil and the red lead on T152 Vertical Output Transformer . . . was 8200 ohms.

Balloons ① ② etc., shown on schematic above, and on Figure 48, indicate points of observation of the waveforms

The schematic is shown in the latest condition at the time of printing.

All resistance value in ohms. K = 1000.

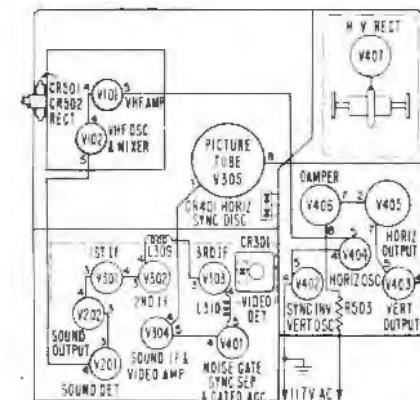All capacitance values MF and above 1 in MMF noted.



TUBE LOCATIONS AND HEATER CIRCUIT


- V101—4BC8
- V102—5CG8
- V201—3DT6
- V202—12CU5
- V301—3BZ6
- V302—3BZ6
- V303—3CB6
- CR301—1N60, 1N87 or 1N295
- V304—6AW8A
- V305—14ASPA or 14AVP4
- CR401—Dual Selenium Diode 93B5-4
- V401—3BU8
- V402—6CG7
- V403—12DB5
- V404—6CG7
- V405—12DQ6A
- V406—12AX4GTA
- V407—1B3GT

REMOVING CHASSIS FROM CABINET

The cabinet enclosure of these receivers consists of a cabinet wrap-around (shell) bottom plate, front bezel and masonite back. The chassis, speaker and picture are mounted as a complete assembly to the bottom plate of the cabinet.


To remove the chassis from the cabinet, proceed as follows:

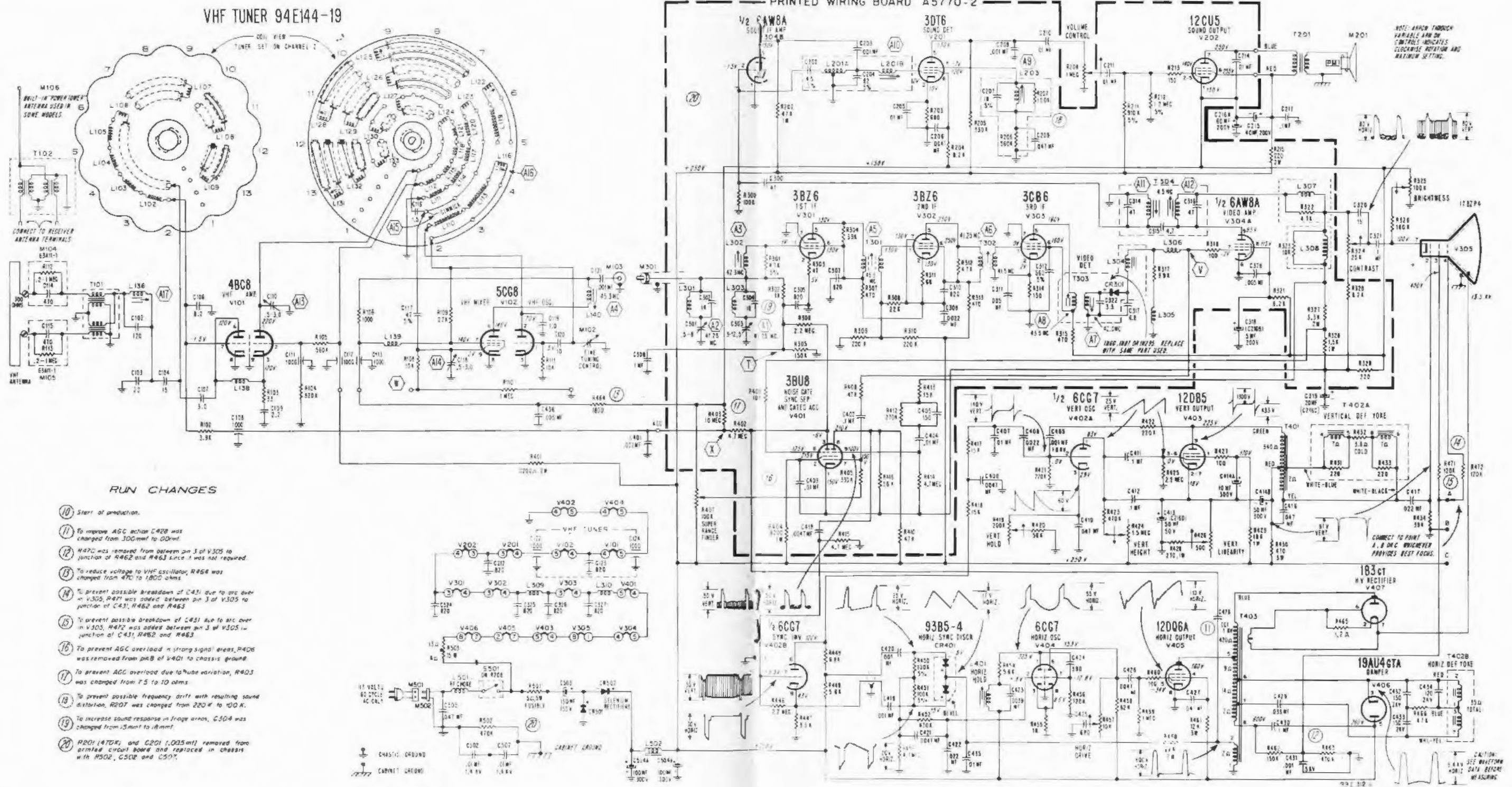1. Remove tuning knobs at side of cabinet.
2. Remove cabinet back, using care so as not to damage interlock socket or plastic shaft of Horizontal Lock control.
3. Remove picture window and bezel after removing screws at sides and bottom of bezel. Pull bottom of bezel away from cabinet. Lift up to free top of bezel from cabinet.
4. Remove top cabinet mounting screw located below carrying handle.
5. Remove reinforcing brackets at top corners of cabinet.
6. Disconnect antenna connector leads from plug-in terminal at top of tuner.
7. Remove cabinet wrap-around after removing screws which mount it to the bottom plate of cabinet.
8. To remove bottom plate from chassis, remove screws which mount it to chassis bottom. **Caution:** Do not allow bottom surface of chassis (printed wiring) to come in contact with metal bench, tools or metal chips which may be lying on surface of bench.
9. To reassemble chassis in cabinet, follow above procedure in reverse order.




Schematic for 16H1 Television Chassis Stamped Run 10 through 20.

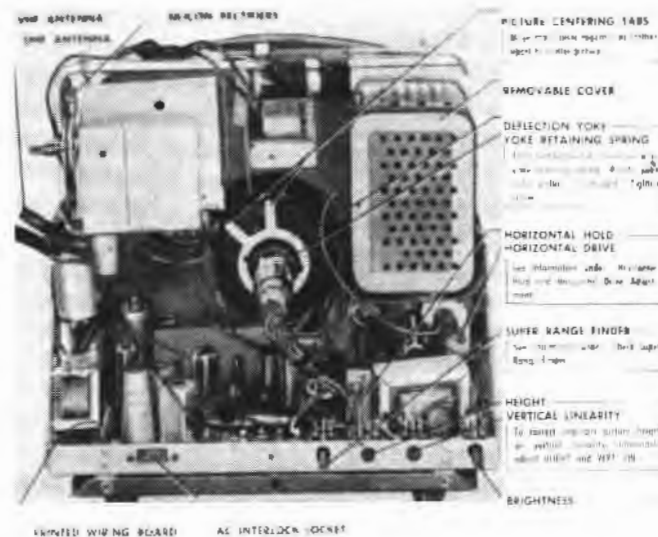
ELECTRONIC SERVICING COMPLETE MANUFACTURERS SCHEMATICS. A service of Cavan Publishing Corp.



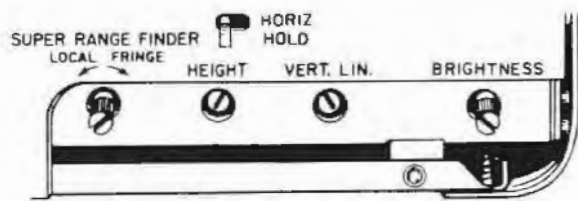
Rear View of 14" Picture Tube Sets Showing Adjustment Locations. UHF Antenna Terminals in VHF-UHF Sets Only.



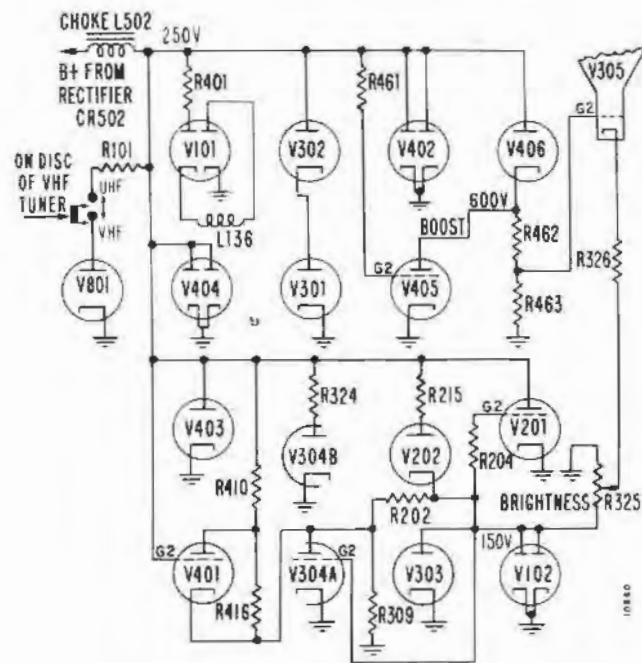Auxiliary Controls at Rear of 14" Picture Tube Sets.



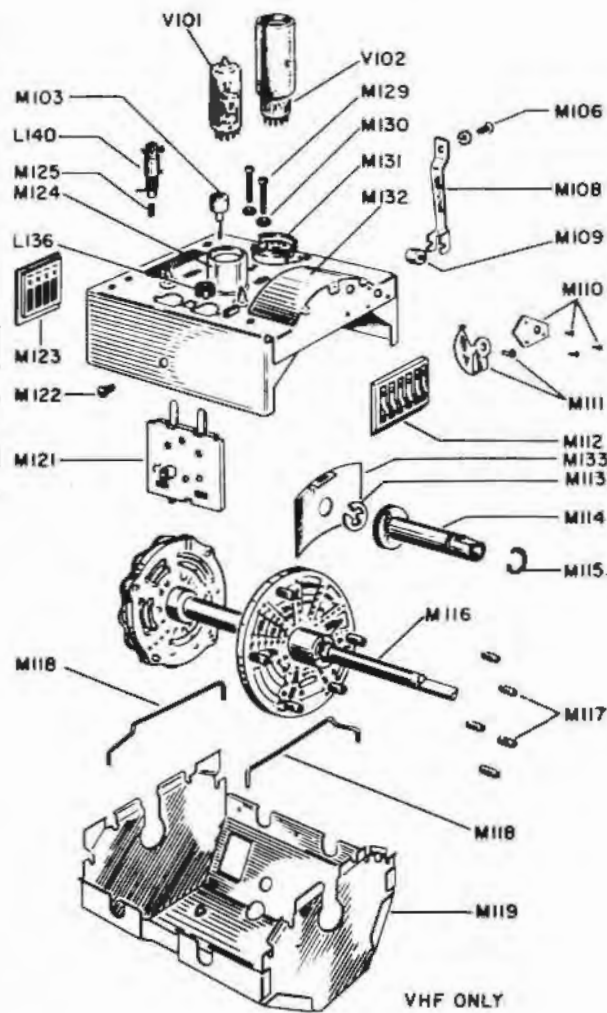
Simplified B+ Distribution Diagram for VHF-UHF Receivers.



Exploded View of VHF Tuner 94E144-19.


To replace a picture tube, proceed as follows:

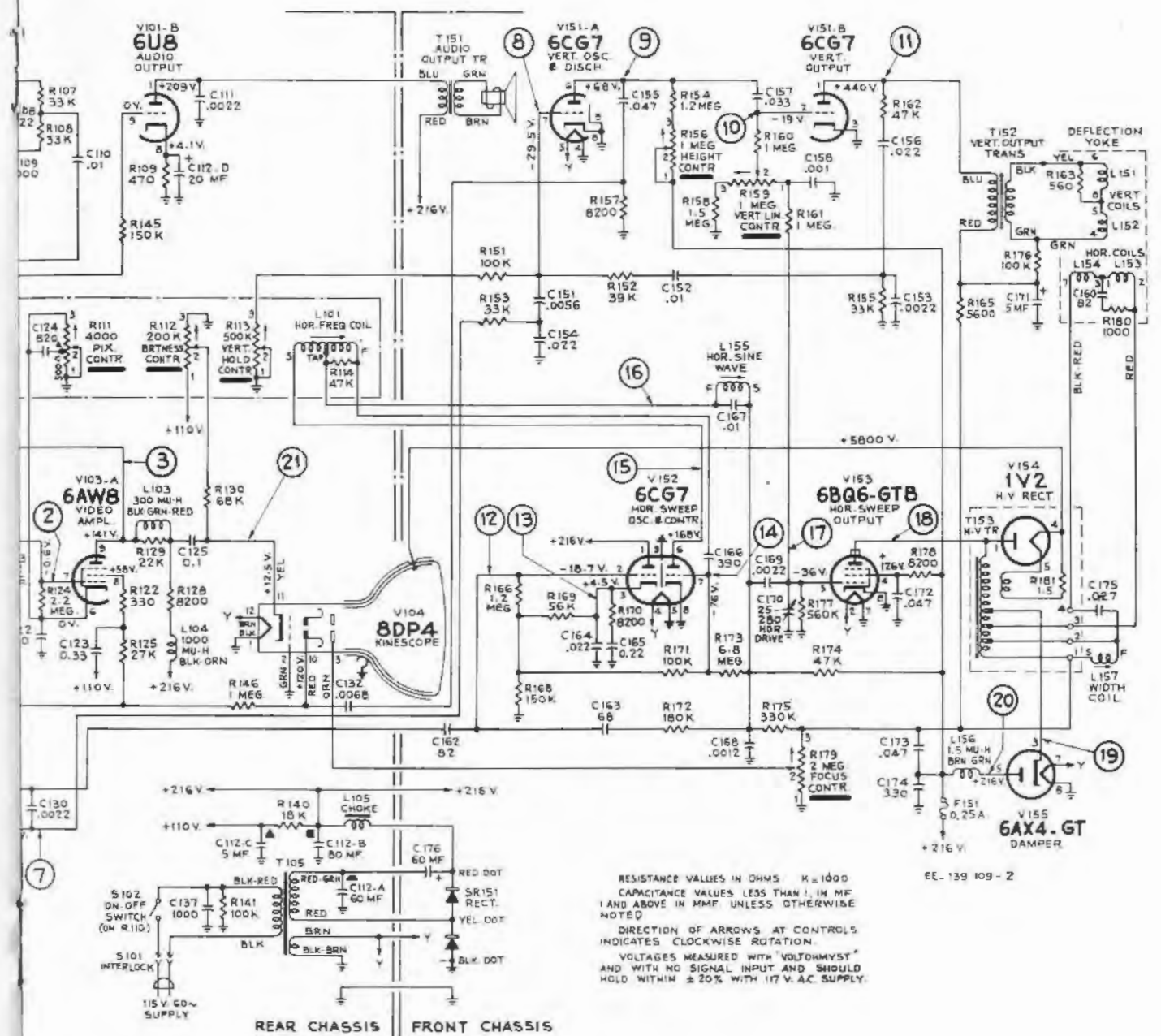1. Remove cabinet back, front bezel and cabinet wrap-around as instructed under separate heading on "Removing Chassis From Cabinet".
2. Remove static charge from picture tube by discharging second anode well to chassis ground with an insulated wire lead or screwdriver.
3. Disconnect the second anode lead and picture tube socket.
4. Loosen mounting clamp at rear of deflection yoke cap by loosening screw or nut on clamping band.



CIRCUIT SCHEMATIC DIAGRAM KCS 100B

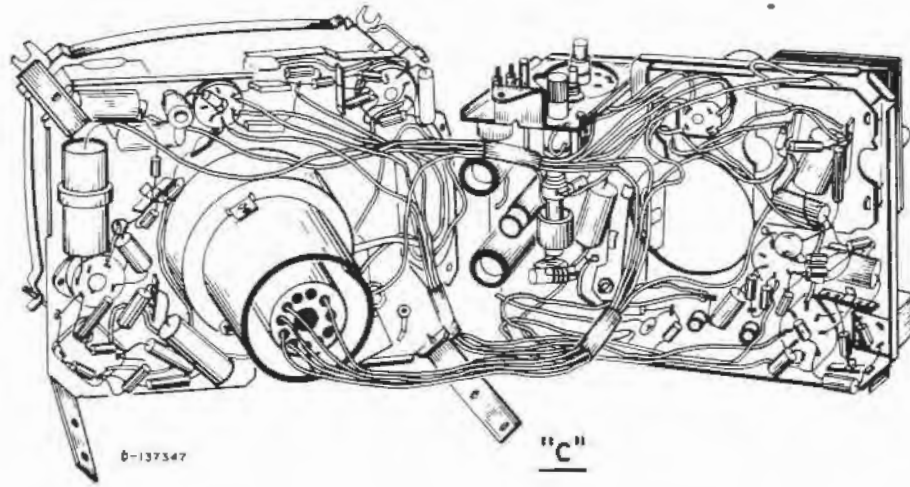less than 1 in unless otherwise
 Direction of arrows at controls indicates clockwise rotation.
 All voltages measured with "VoloHmyst" and with no signal input. Voltages should hold within ±20% with 117 v a-c supply.



Chassis Removal

CHASSIS REMOVAL.—The chassis must be removed from the cabinet to replace tubes or the kinescope and to perform certain adjustments as explained above.

Models With Attached Stand

Take the receiver off its stand and completely remove the two knurled screws at the sides of the cabinet. Never attempt to remove the chassis unless these two screws are completely removed, as their projection inside the cabinet may result in internal damage as the chassis is pulled from the case. See Figure 2A.

All Models

Remove the knobs on the controls located in the cover and case assembly and take out the three screws holding the assembly to the cabinet. Their location is indicated at "A" in Figure 2A. Lift the control case and cover directly upward to remove.

Take off the carrying handle by removing the two screws at the ends of the handle. Also, remove the screw at the bottom front edge of the receiver case. These three screws are indicated at "B" in Figure 2A.

The antenna lead must be internally disconnected on the following models before removing the chassis from the cabinet: Models 8-PT-7010, 8-PT-7011, 8-PT-7012 and 8-PT-7014.

Remove the plate to which the antenna terminal board is fastened. Pull the clips at the end of the antenna lead off the terminals on the rear of the antenna or terminal board assembly.

On all models not listed above, the antenna will automatically disengage as the receiver chassis is removed from the cabinet.

Slide the chassis assembly, which includes the front frame and kinescope, out of the receiver cabinet. The A.C. interlock will automatically disengage as the chassis is removed.


CHASSIS SERVICING.—Adjustment of the yoke position, centering magnets and the ion trap magnet may be made with the chassis completely assembled. The location of these adjustments is shown in Figure 4.

Replacement of the tubes in the tuner section requires removal of the speaker. To remove the speaker, loosen the speaker clamp screw shown in Figure 4 and slide the speaker out of its clamp. This will allow room to make tube replacement in the tuner unit.

Service which requires circuit tracing or voltage measurements must be performed with the front and rear chassis

sections separated. To do this, remove the six (6) self-tapping screws holding the front and rear chassis sections together. See Figure 2B. The positions of the insulating boards should be noted for replacement when reassembling the chassis.

Unplug the kinescope socket and slide the rear chassis section off the end of the kinescope neck. Turn the chassis around making the bottom wiring side visible. Slip the kinescope socket leads out of the hole in the chassis, through which they are normally dressed, and pass the socket through the large opening in the chassis and reconnect to the kinescope. With the chassis in this position, which is shown in Figure 2C and Figure 3, all points will be accessible for servicing. Greater separation of the two chassis sections may be accomplished by the use of a short extension cable for the kinescope leads if desired.


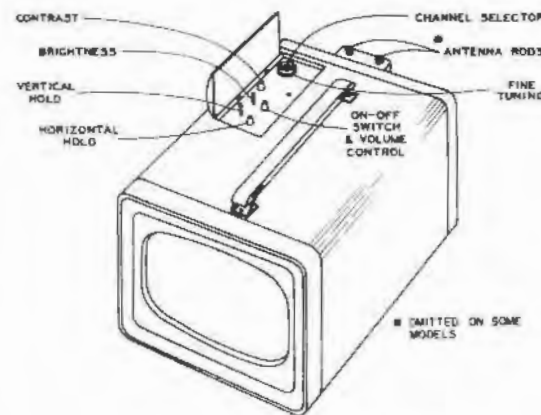


Receiver Operating Controls


Resistance Measurements
All Readings to Ω

V101	INF	8	0	INF	150K	3.9K
V102	INF	0-1M	2.2K	8	20	INF 33K 2.2K NC
V103	B2	420K	20	65	470K	INF INF
V104	B2	470K	65	110	470K	INF INF
V201	47K	8	35	25	INF	INF 2.7M
V302	2.7M	0	25	1.3	INF	INF 68
V303	0	0	1.3	580K	580K	0

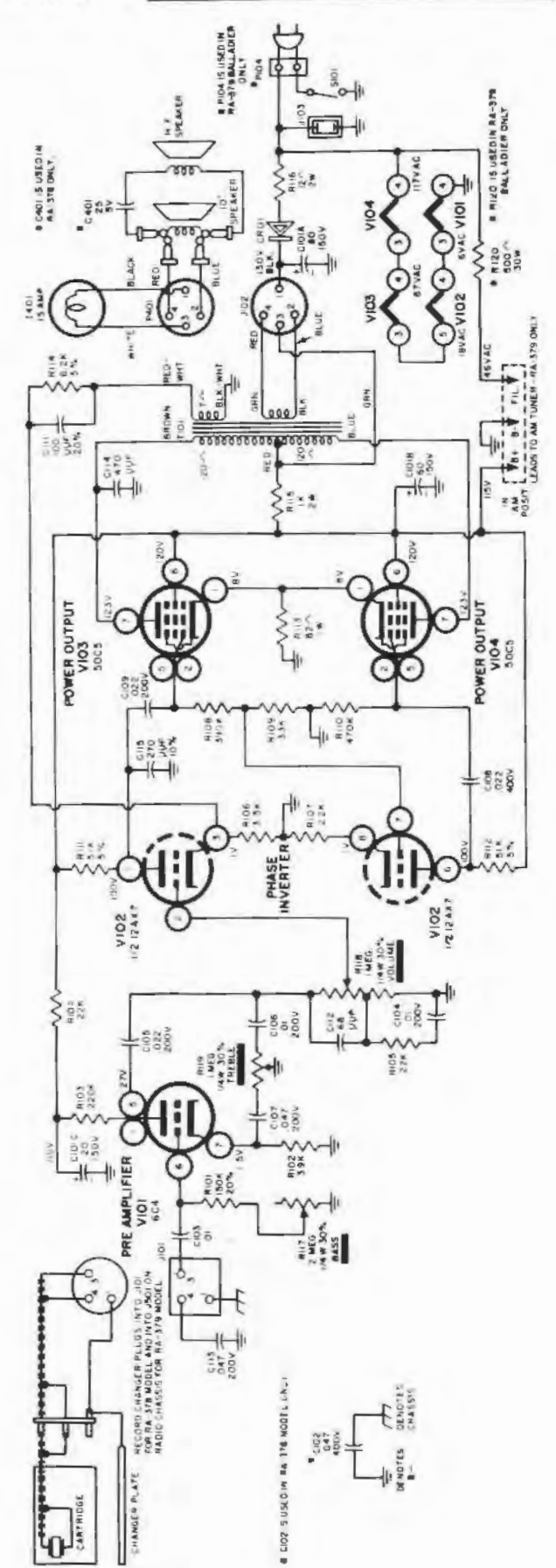
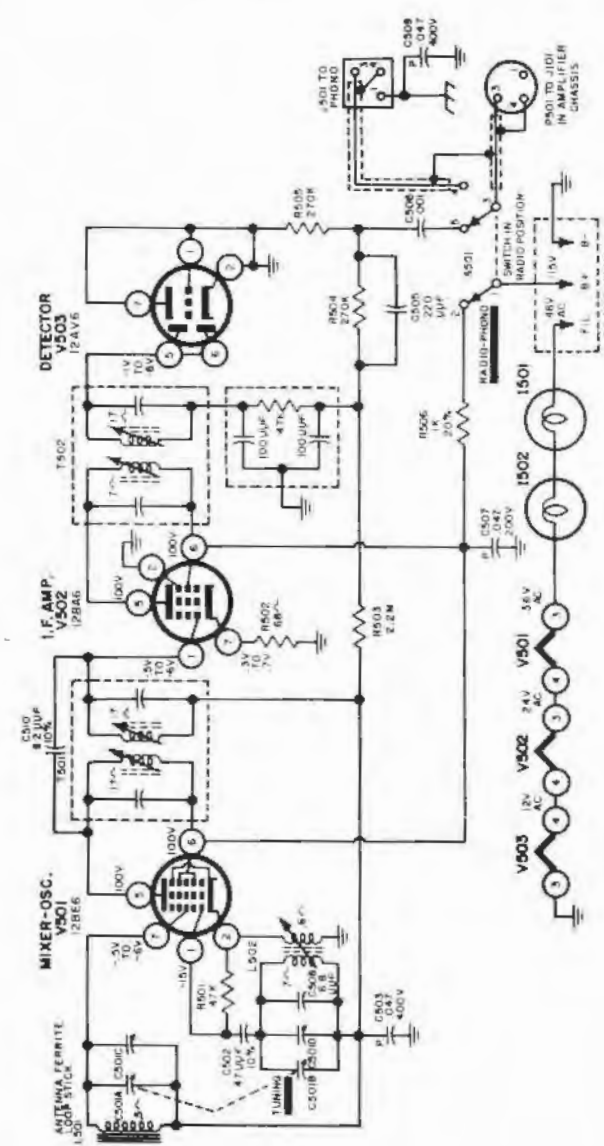
The above resistance readings were taken with an RCA model W197A VTM. All readings are in ohms. K = 1000, M = 1 million.
NOTE: RA-379 measurements of V101 to V104 were taken with the Radio Photo switch in the Photo position. V201 to V303 were measured with the switch in the Radio position.



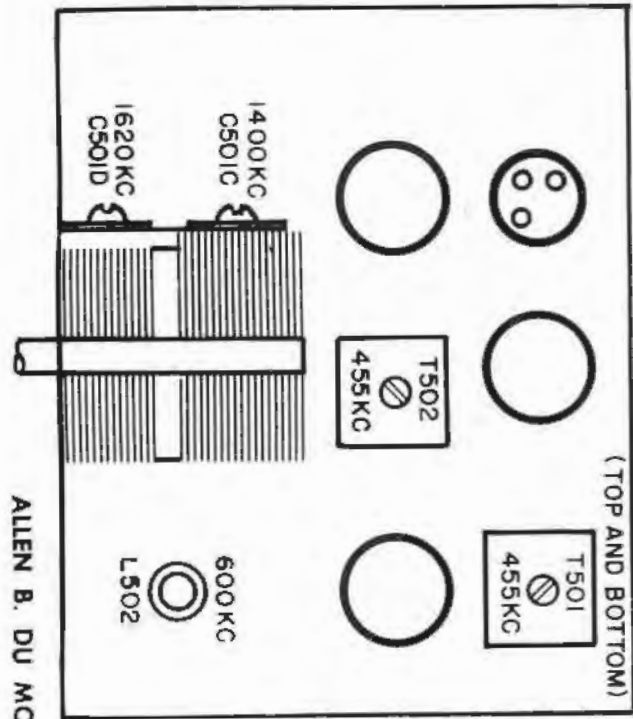RA-378/379 AMPLIFIER SCHEMATIC RA-379 AM RADIO SCHEMATIC



ALLEN B. DU MONT LABORATORIES, INC.

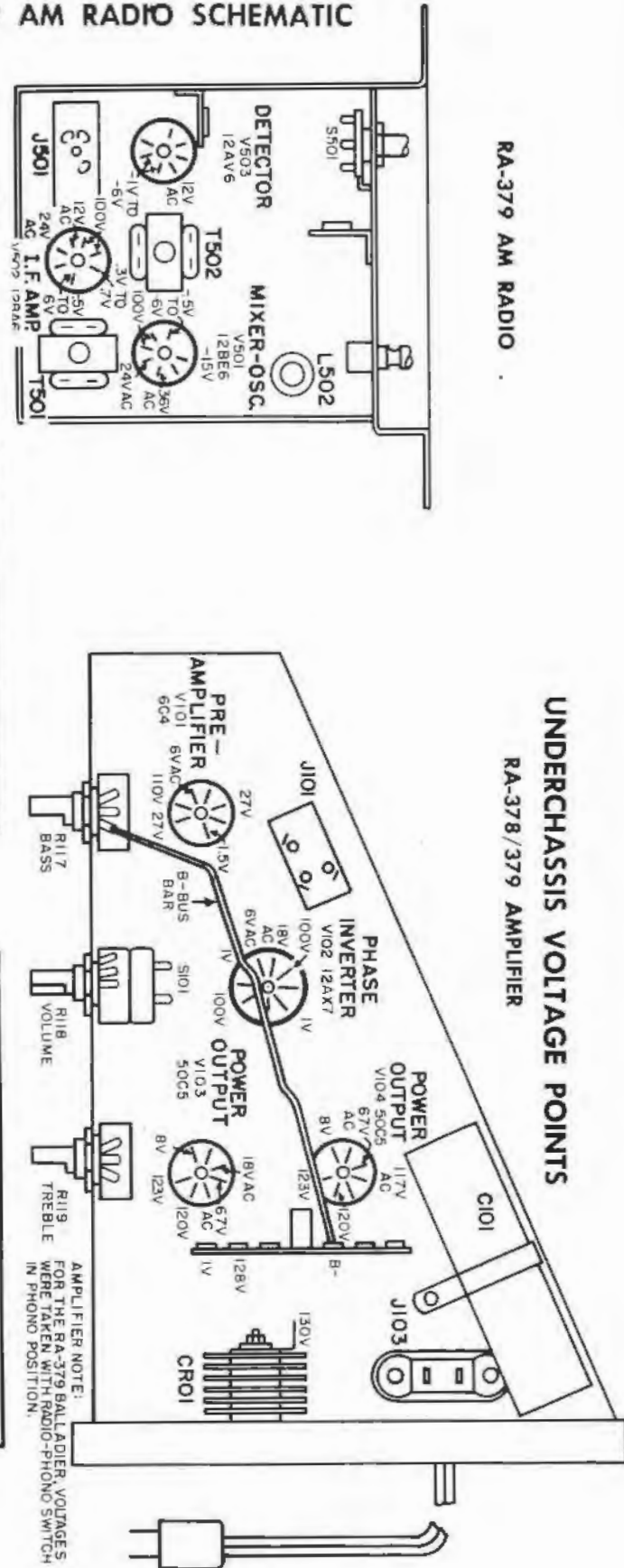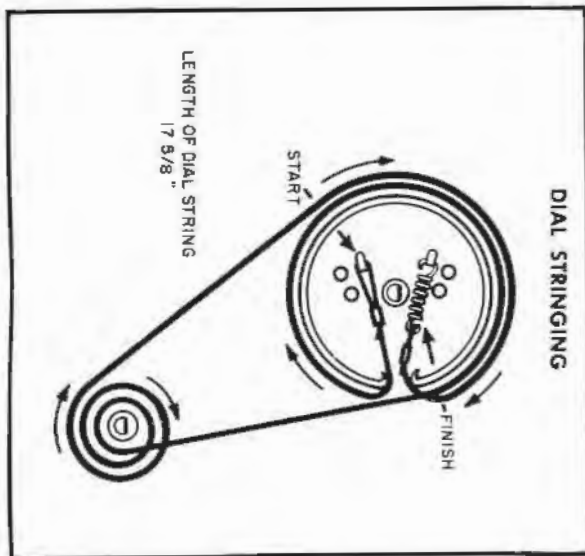

Mfr: Motorola Chassis No. TS422


Card No: MO-422-1

Section Affected: Raster

Symptoms: Insufficient width.

Reason For Change: To increase width.

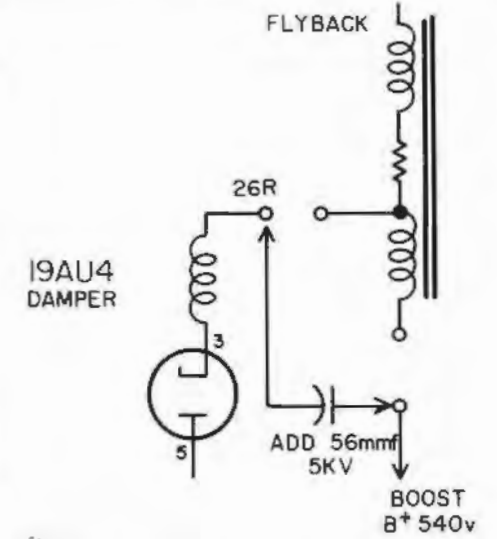What To Do: Connect a 56 mmf 5KV condenser across lugs 26R and 27R of the fly back transformer.



Mfr: Motorola Chassis No. TS422


Card No: MO-422-2

Section Affected: Pix

Symptoms: Poor sensitivity

Reason For Change: To improve sensitivity by increasing voltage at tuner.

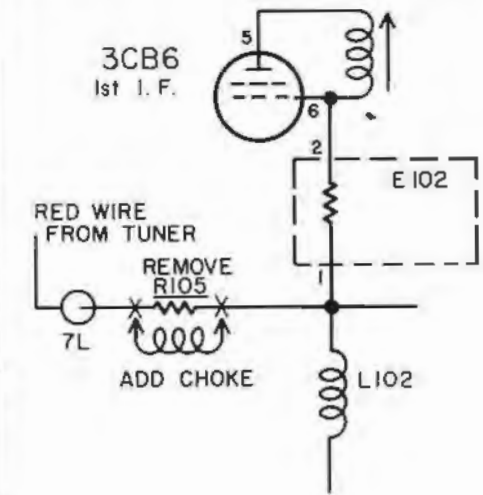What To Do: Change R105, 1K, to a .52 microhenry choke, part #24K730391.



Mfr: Motorola Chassis No. TS422


Card No: MO-422-3


Section Affected: Sound

Symptoms: Distortion, weak sound.


Cause: Open filter condenser, C303, in ratio detector.

What To Do: Replace C303, 10 mfd, 50V.

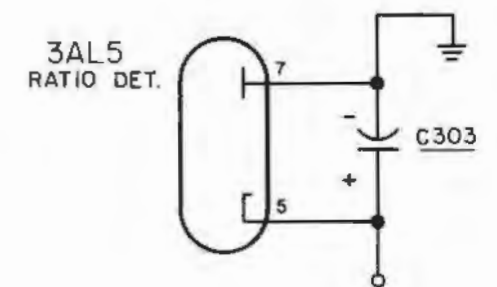

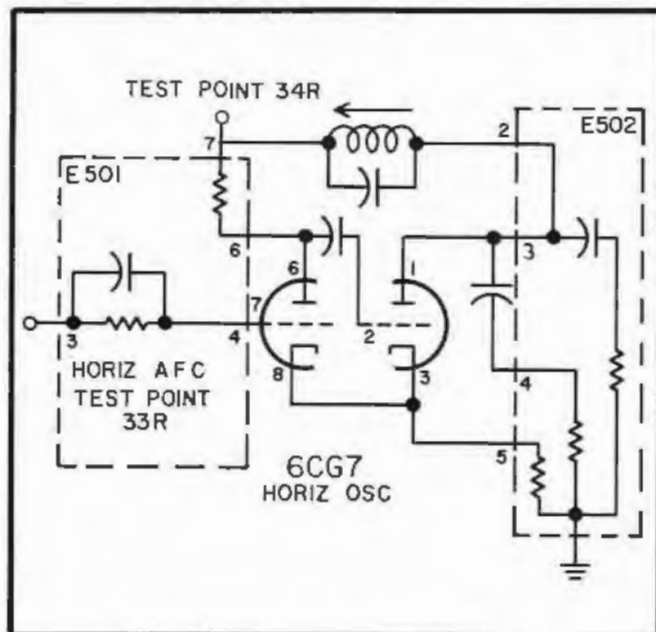


Mfr: Motorola Chassis No. TS422
 Card No: MO-422-4
 Section Affected: Horizontal sync.
 Symptoms: Hold control effective for less than 50° of rotation.
 Cause: Improperly adjusted horizontal *afc* circuit.
What To Do:
 1. Set all controls for a normal picture.
 2. Short out *afc* control voltage with jumper from test point 33R to ground.
 3. Connect .1 condenser from test point 34R to ground.
 4. Adjust front panel hold control for almost stationary picture.
 5. Remove .1 cond. Adjust oscillator coil to center of range in which picture almost remains in hold.
 6. Remove short from *afc* voltage at 33R and adjust front panel hold control so that there is no foldover on either side.

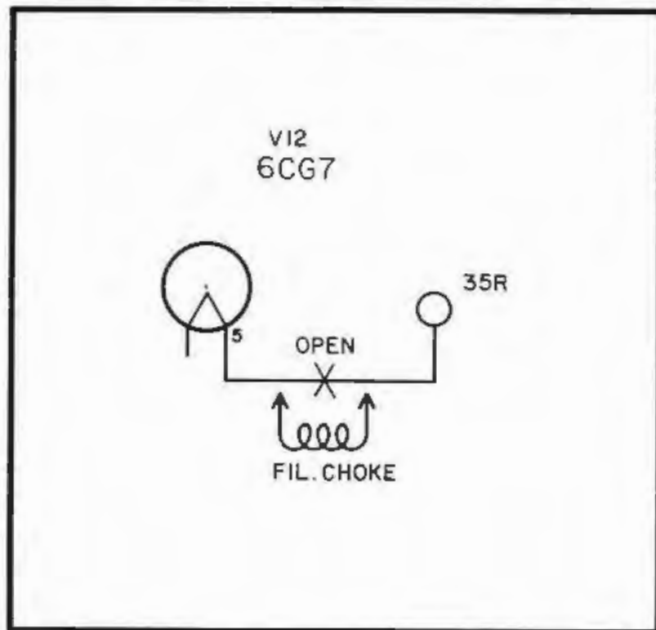

Mfr: Motorola Chassis No: TS422
 Card No: MO-422-5
 Section Affected: Pix
 Symptoms: Herringbone pattern.
 Cause: *IF* interference.

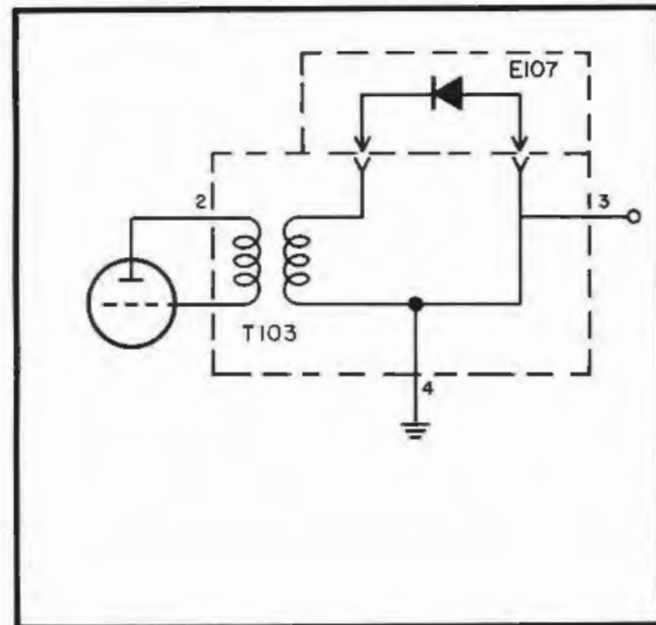What To Do: Add a filament choke, part #24K730391, between pin 5 of V12 6CG7 and 35R. This is effective only in sets with *uhf* tuner.



Mfr: Motorola Chassis No: TS422
 Card No: MO-422-6
 Section Affected: Pix
 Symptoms: Negative picture. Unstable sync.
 Cause: Defective crystal detector.

What To Do: Replace plug in crystal E107 mounted on transformer T103.

Mfr: Westinghouse Chassis No. V2382


Card No: WE-V2382-1

Section Affected: Fine tuner.

Symptoms: Manual fine tuner inoperative.

Cause: Defective crystal X100.

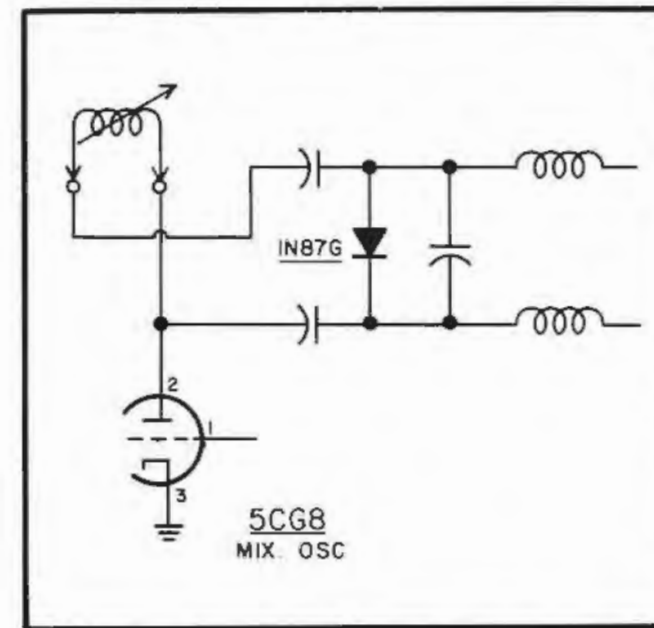What To Do: Replace crystal X100 a 1N87G.



Mfr: Westinghouse Chassis No. V2382


Card No: WE-V2382-2

Section Affected: Fine tuning.

Symptoms: No manual fine tuning. Replacement crystals are blown out.

Cause: Short on the anode side of *AFT* crystal may be C118, C204, or filament to cathode short in 6AU8.

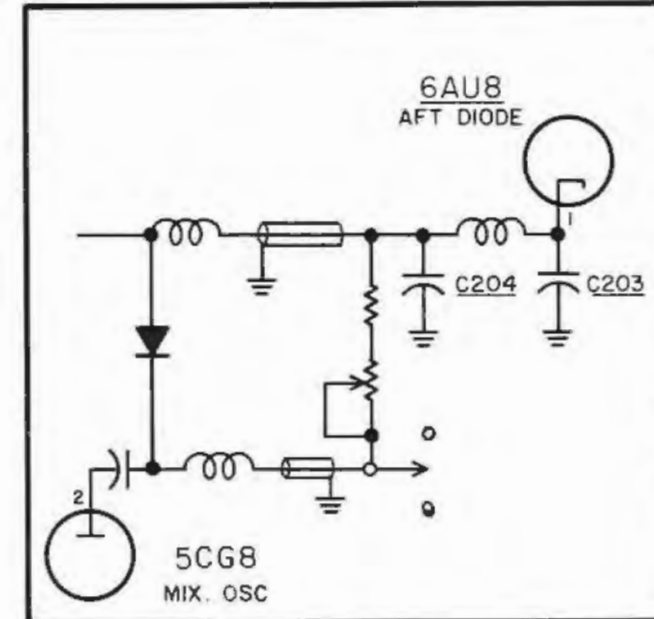What To Do: Check for filament to cathode leakage in 6AU8 *AFT* diode. Check C118, 800 mmf. feed through condenser on tuner and C204, .001 mfd.



Mfr: Westinghouse Chassis No. V2382


Card No: WE-V2382-3


Section Affected: Automatic fine tuning.

Symptoms: *AFT* remains locked on same channel when the next channel is selected.

Cause: Tuner oscillator setting is improper.

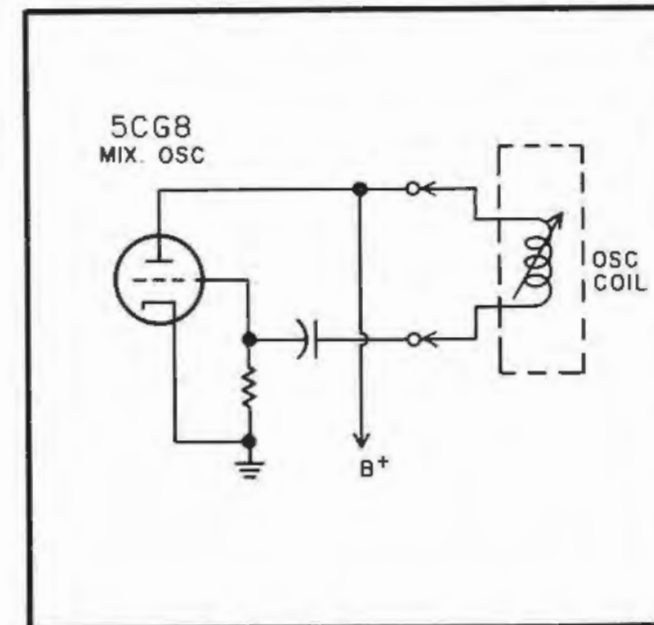What To Do: Readjust oscillator slug for desired channel.



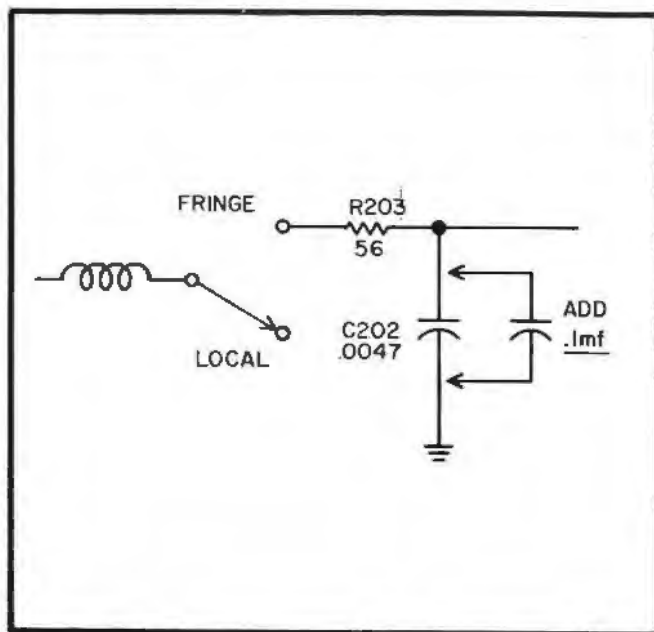

Mfr: Westinghouse Chassis No. V2382


Card No.: WEV-2382-4

Section Affected: Pix

Symptoms: Streaking in picture.

Cause: Local—Fringe switch, on program wheel, in fringe position.

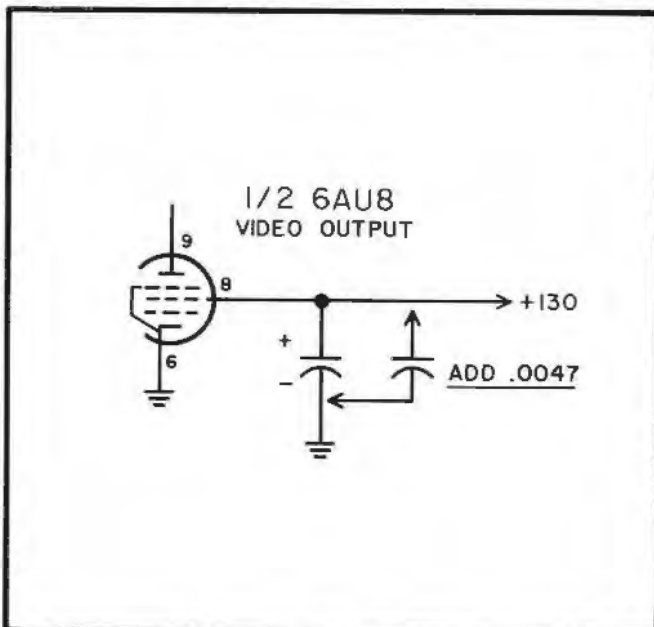What To Do: Change Local—Fringe switch to local position if possible. If switch must be in fringe position add a .1 mfd. 400V condenser as indicated in diagram. Place the condenser on the terminal strip below the tuner.



Mfr: Westinghouse Chassis No. V2382


Card No: WE-V2382-5

Section Affected: Pix

Symptoms: Herringbone interference patterns generated internally. (Called tweets).

Reason For Change: To eliminate interference patterns.

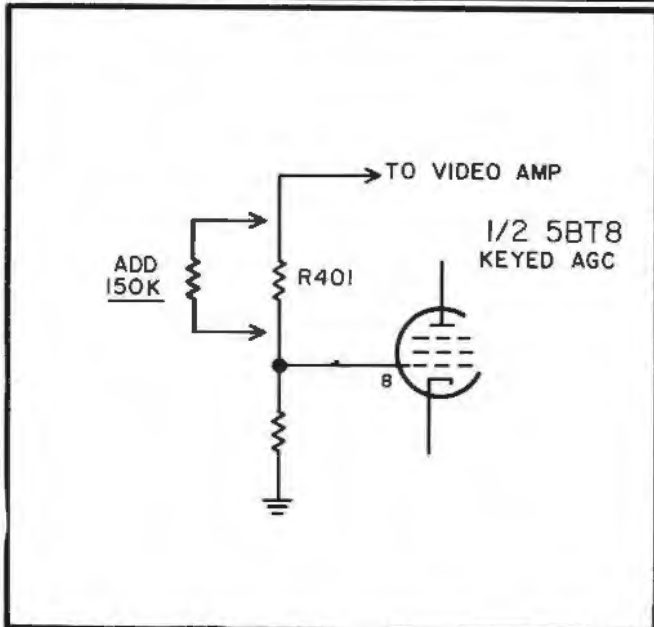What To Do: Add a .0047 mfd. 400V from the low B plus to B minus. The most effective point to place the condenser is at the screen of the video amplifier.



Mfr: Westinghouse Chassis No. V2382

Card No: WE-V2382-6

Section Affected: Pix

Symptoms: Negative pix, erratic sync and excessive contrast.

Cause: Local—Fringe switch in fringe position.

What To Do: Switch to local position (switch is on program wheel). If overload occurs in local position shunt a 150K resistor across R401.

LOOKING FOR TROUBLE?

[from page 9]

tuned to an inactive channel). But with a signal coming in, the defective portion of the stage is usually much more obvious for many types of troubles. This is illustrated in the following figures for the keyed *agc* stage with the given trouble in it compared to the normal readings.

V7 Voltage Readings (No Signal)

	Faulty Stage	Normal Stage
Plate	0.6 v	0.6 v
Screen	465 v	465 v
Control grid	122 v	122 v
Cathode	146 v	146 v

V7 Voltage Readings (With Signal)

	Faulty Stage	Normal Stage
Plate	0.6 v	-12 v
Screen	465 v	465 v
Control grid	146 v	128 v
Cathode	146 v	146 v

Obviously, on the basis of the voltage readings above, the most glaring discrepancies are in the plate and control grid circuits of the keyer stage. Trouble is indicated in the *agc* keyer bus, which is connected to the plate circuit, since a normal keyer pulse was observed at the plate. Since the voltage checks with an incoming signal show a complete loss of *agc* bias at the plate of the keyer tube, this would account for the higher than normal voltage at the control grid. Loss of *agc* bias causes excessive video signal at the grid of the video amplifier stage which almost cuts off the tube and raises its plate voltage. This

higher voltage is direct-coupled to the control grid of the keyer tube.

Where low negative voltage readings are measured at the plate of the keyer stage, further voltage readings are taken at various points along the *agc* bus. This may localize the point in the bus where the trouble is located.

If a low positive voltage is measured on the *agc* bus, this is usually caused not by a fault in the *agc* circuit proper but in a component connected to the *agc* bus—such as a defective *rf* or *if* amplifier tube (control grid to screen grid short, etc.), a leaky coupling capacitor (plate to control grid of a controlled stage) or similar trouble. This type of trouble can usually be tracked down by spot voltage checks along the *agc* bus or, if necessary, by opening the *agc* line at various points to find where the trouble is originating.

AGC Resistance Analysis

5. a

The resistance readings point definitely to a shorted capacitor C49. The reading at test point 7 is 2.9K because R36 is effectively in parallel with R35 since C49 is shorted. To verify this, a further resistance check is made across C49 with one end disconnected. The capacitor was found shorted.

A shorted C48 would have caused a zero resistance reading at test point 7. The other choices listed would also have resulted in different resistance readings than those listed. A short across R34 would have shown readings of 30K and 27K at the keyer plate and test point 7 respectively. An open R35 would have resulted in very [Continued on page 32]

Video Detector Voltage	AGC Bus Voltage	Possible Fault
Approx. -5 v	-3 to -7 v	Normal
Excessive°	Very low or zero	Fault in <i>agc</i> bus (<i>agc</i> filter network), <i>agc</i> stage, or loss of horizontal keyer pulse input to keyed <i>agc</i> stage
Excessive°	Positive voltage	Defective <i>rf</i> or <i>if</i> amplifier tube, leaky coupling capacitor connected to control grid of an <i>agc</i> -controlled stage
Low or zero	Excessive°	Caused by loss of bias in keyed <i>agc</i> stage itself: defective keyer tube; video amplifier fault causing too high a voltage applied to keyer tube control grid; defect in keyer tube cathode circuit

° Negative voltage too high

Table 1—Analysis of *agc* troubles based on *agc*-detector voltages.

Cut Down Call Backs...

INSTALL A **GE** WUERTH **SURGISTOR** ON EVERY SERVICE CALL



Stops harmful voltage surges to picture and radio tubes. Sell your customers tripled tube life and you'll profit on each installation. Simply connect directly into power line. Functions like a combination resistor-relay to preserve electrolytic capacitors, dry disc rectifiers, transformers, pilot bulbs and other components as well as tubes.

G-C Wuerth No. 5301 ... For Black & White TV List \$1.65

G-C Wuerth No. 5302 ... For Color TV Sets List \$1.95

Available right now from your local electronics parts distributor or write direct to:

G-C ELECTRONICS MFG. CO.

Division of G-C TEXTRON INC.
Western Plant: Los Angeles 18, Calif.
Main Plant: ROCKFORD, ILLINOIS, U.S.A.

FREE Information About This

BUSINESS OPPORTUNITY



key to car radio service market

How many car radios have you serviced lately? Most service operators are missing this tremendous market because they have no regular contact with car owners!

This VIS-U-ALL Auto-Radio Service Merchandiser literally moves your shop into the gas stations and garages where car owners must go. It multiplies your sales of parts—booms your repair volume, too. And without increasing your overhead!

Let us tell you how easy it is to increase your net profit by \$50 a week. See distributor or write us.

VIS-U-ALL products company
305 Fuller N.E., Grand Rapids 3, Mich.



... Superbly made and designed, for Radio, T.V. and Electronic Technicians. See your Distributor ... only one quality ... the finest — whether you choose individual items or the handy kits ...

Use the Tools the Professionals use!



XCELITE, INCORPORATED
ORCHARD PARK, NEW YORK
Canada: Charles W. Pointon, Ltd., Toronto

XCELITE
Quality Hand Tools
PREFERRED BY THE EXPERTS

VSSSS*

*A compilation of specific receiver service repairs, "bugs," chronic troubles, field circuit changes, manufacturers' production revisions, etc. The compilation enables the service technician to pinpoint what is wrong with any given TV set and to correct the fault in the shortest possible time.

Video Speed Service Systems is guaranteed to simplify servicing all TV sets. Contains over 600 service items representing over 2500 of the most serviced TV models now in use. Over 25 different manufacturers' lines are covered.

CUT OUT AND MAIL

COWAN PUBLISHING CORP., 300 WEST 43rd STREET, NEW YORK 36, N. Y.

Please send me postpaid Video Speed Servicing Systems

Vol. 1 in Hard Cover Ring-Binder Edition for \$4.95

Vol. 2 in Paper Bound Edition for \$2.95

My Check for \$..... is enclosed.

New York City residents add 3% sales tax

Name

Address

City..... Zone..... State.....


SHOP HINTS

[from page 10]

To solve this problem I keep a half dozen combined alligator and fahnestock clips on hand. These can be assembled simply by flattening the wire end of the alligator clip in a vise and soldering a fahnestock clip to the alligator clip.

A piece of high voltage wire (from 4" to 15" long) with an alligator clip at each end is also a handy device for extending the high voltage lead when a set is on the bench. Insulated sleeves may be placed over the clips for greater safety.

B. T.
Brooklyn, N. Y.

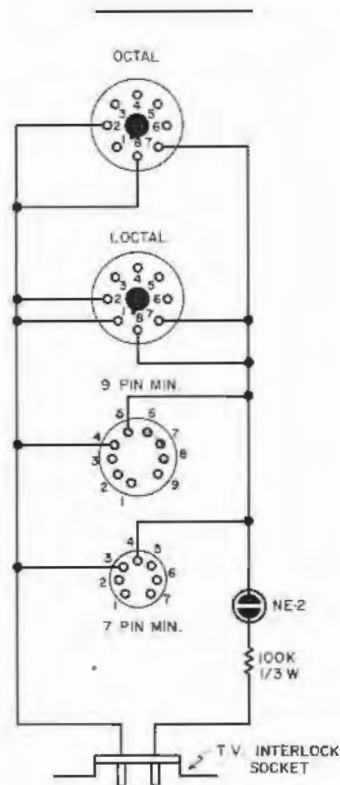

A tube filament and continuity tester that can be built from "junk box" parts is shown above. It can be assembled in a box as small as 3/4" x 5" x 2". If a pair of pin jacks are connected to pins 2 and 7 of the octal socket, the unit may also be used as a continuity tester.

R. P.
Plattsburg, N. Y.

A quick and easy way to locate noisy components, tubes and solder connections in a radio is to feed in an unmodulated rf signal from a signal generator. With the radio tuned to this signal, tap and probe the chassis with a non-metallic probe such

Operate your...


- tape recorder
 - P. A. system
 - portable TV set
 - hand tools
- FROM YOUR CAR, Boat or Plane!

with ATR INVERTERS

FOR CHANGING YOUR STORAGE BATTERY CURRENT TO A.C. HOUSEHOLD ELECTRICITY ANYWHERE... in your own CAR, Boat or Plane!



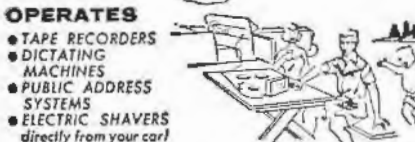OPERATES PORTABLE TV SET directly from your car!




OPERATES TAPE RECORDERS, DICTATING MACHINES, PUBLIC ADDRESS SYSTEMS, ELECTRIC SHAVERS directly from your car!

MAKE YOUR CAR, BOAT OR PLANE "A ROLLING OFFICE!"



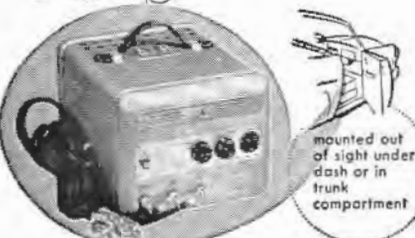OPERATES RADIOS, RECORD PLAYERS, MIXMASTERS, ETC. directly from your car!



mounted out of sight under dash or in trunk compartment

ATR UNIVERSAL INVERTERS

Especially designed to change 6 or 12 volt D.C. to 110 volt A.C. 60 cycles.

- for...
- EXECUTIVES
 - SALESMEN
 - OUTDOOR MEN
 - POLICEMEN
 - REPORTERS
 - FIREMEN
 - PUBLIC OFFICIALS

MODELS 6U-RHG (6 volts) 125 to 150 watts, Shipping weight 27 lbs. List price.....\$89.95

DEALER NET PRICE.....\$59.97

12U-RHG (12 volts) 150 to 175 watts, Shipping weight 27 lbs. List price.....\$89.95

DEALER NET PRICE.....\$59.97

Write for literature on other Sizes and Models of ATR INVERTERS, priced as low as \$9.95 list.


SEE YOUR JOBBER OR WRITE FACTORY

NEW MODELS NEW DESIGNS NEW LITERATURE
"A" Battery Eliminators • DC-AC Inverters • Auto Radio Vibrators

ATR AMERICAN TELEVISION & RADIO CO.
Quality Products Since 1931
SAINT PAUL 1, MINNESOTA, U. S. A.

as a plastic knitting needle. I have been using this system for many years and find it a real time saver.

L. C.
Newton, Miss.

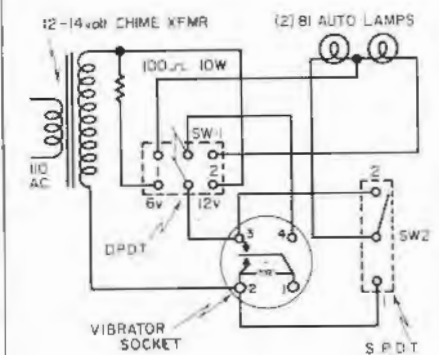

Either 6 or 12 volt vibrators may be tested with the circuit, shown above. Switch SW-1 in position #1 is for 6 volts and in position #2, which uses the full secondary voltage, is for 12 volt vibrators. Switch SW-2 in position #1 will light the auto lamps using the transformer voltage. One bulb lights in the 6 volt position and both in the 12 volt position of SW-1. When SW-2 is in position #2 the lamps are lighted through the vibrator action. If the vibrator is in good condition the lamps will light with the same intensity as in position #1. A weak vibrator will cause a fluctuating light while a defective vibrator will prevent the lamps from lighting at all.

H. H.
N. Y. C.


When any tools become magnetized, they may be demagnetized with a soldering gun. Simply insert the tool through the loop of the soldering gun, pull the trigger and slowly withdraw the tool from the loop.

S. C.
E. Bradenton, Fla.



It says E equals I times R.

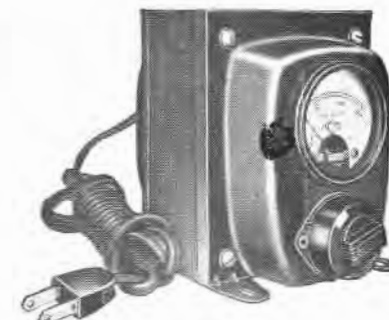WHEN PERFORMANCE IS AFFECTED BY LOW VOLTAGE CONDITIONS



SELL THIS ACME ELECTRIC VOLTAGE ADJUSTOR

TV sets are designed to operate best when voltage holds closely to 115-117 volts. Overloaded supply lines (the power industries greatest problem) may result in a voltage drop of 10 to 15% at certain times of day. Usually the TV set will function in a fashion under such low voltage conditions but with a great strain on its components. For example; narrowing of picture, output stage tube life shortened, frequent burn-out of filaments, fuzzy focus have been traced to lack of proper voltage.


These conditions can be corrected with an Acme Electric T-8394M Voltage Adjustor. Simply plug-in to convenient outlet. Plug-in television set cord into female receptacle built into adjustor. Voltmeter indicates output voltage. If voltage is incorrect turn regulating control until proper voltage is reached for best performance. Voltage range 95 to 125 volts. Tell your supply dealer you want the Acme Electric T-8394M. No other so compact, practical, inexpensive.

ACME ELECTRIC CORPORATION
465 WATER STREET CUBA, NEW YORK

Acme Electric TRANSFORMERS

FREE by subscribing to **ELECTRONIC SERVICING** **FREE**
now on this special order form you will get **FREE!**

96 PAGE TV SCHEMATIC PACKET

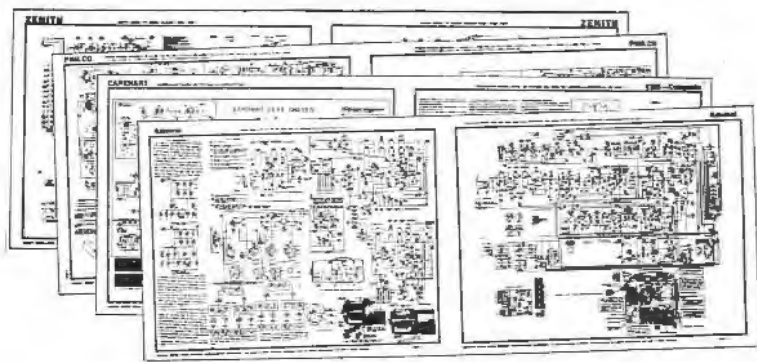

Many of these will not be available from any other source for months. Each schematic is crystal clear and accurate — (prepared by John F. Rider) — ready for immediate use and easy filing for future reference. The schematics include Alignment Data, Waveforms, Operating Voltages, Tube Location Guide, Essential Parts Numbers, etc.

In addition you'll get 4 more new pages of **VIDEO SPEED SERVICING SYSTEMS Data Sheets** in each issue

HURRY . . . HURRY . . . This Special Offer Good Only While The Present Supply of Schematic Packets Last

—TEAR OFF — MAIL TODAY — GET YOUR FREE 96-PAGE TV SCHEMATIC PACKET FREE—

ELECTRONIC SERVICING, 300 W. 43rd St., New York 36, N. Y.

I accept your FREE OFFER . . . a complete 96 PAGE TV SCHEMATIC PACKET together with a 2-year subscription to Electronic Servicing. Here is my \$5.00

CHECK YOUR CLASSIFICATION

- | | |
|--|---------------------------------------|
| <input type="checkbox"/> Independent Radio-TV Serviceman | <input type="checkbox"/> Owner |
| <input type="checkbox"/> Radio-TV Service Organization | <input type="checkbox"/> Employee |
| <input type="checkbox"/> Retail Store having Service Department | <input type="checkbox"/> Service Mgr. |
| <input type="checkbox"/> Industrial Electronic Service Firm | <input type="checkbox"/> Student |
| <input type="checkbox"/> Firm having electronic equipment which I service and maintain | |

If some other type of company describe: _____

- Check if New Subscriber
 Check if this is to renew or extend your present subscription when it expires

(Please Print)

Name _____

Address _____

City _____ Zone _____ State _____

Name of firm _____

Firm's business address _____

City _____ Zone _____ State _____

ANSWERMAN
[from page 5]

Dear Sir:

I have an Admiral chassis 18XP4BZ which worked fine in the original location. When the customer uses it at his resort bungalow it develops a horizontal jitter. I appreciate that the receiver is being operated in a weak signal area and therefore may not work as well as in the city but he would like to use it at the bungalow and therefore wants to improve its weak signal performance. The noise in the area is high as he is just off a heavily traveled highway. The ignition noise seems to particularly affect

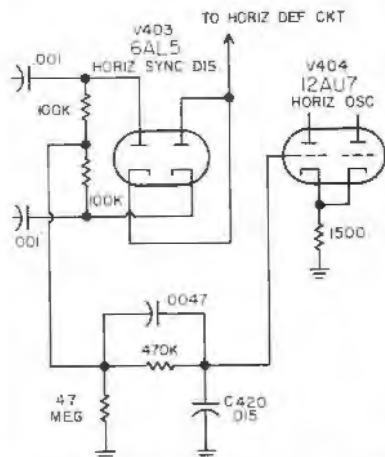


Fig. 3—Increased value of C120 improves noise immunity.

the horizontal lock-in of the picture making it quite unstable. What I would like to know is whether there is anything you can recommend for me to do to improve the horizontal sync action for operation in this weak signal area.

S. D.
Washington, D. C.

An improvement can be achieved in the horizontal sync action in the receiver by changing the filter condenser in the grid circuit of the multivibrator circuit shown in Fig. 3. This condenser, C420, for normal operation is 0.015 uf. The value of the condenser can be increased from the original capacitance shown as 0.015 to 0.047 uf. If an even further increase is desired the capacitance can further be increased to 0.1 uf without causing a detrimental affect in its operation in weak signal areas. However, the condenser should not be increased in value if the receiver is to be used in strong signal areas as it may possibly produce bending in the picture.

Dear Sir:

I have an Emerson chassis

120380H which has a horizontal drive line that I can't remove. The receiver does not have a drive trimmer and works quite well on normal line voltage, but the customer has a very high line voltage which provides the horizontal oscillator and horizontal output stages with higher than normal B plus voltages. This most probably causes the drive line in the picture. I believe I can reduce the B plus voltage in some way but I thought I'd rather have your opinion first on how to remove the drive line before I made any changes.

E. M.
Philadelphia, Pa.

Although there are a number of methods from which you could choose to remove a horizontal drive line perhaps one of the best is to install a control which will permit adjusting the circuit for its elimination. This modification can easily be incorporated by

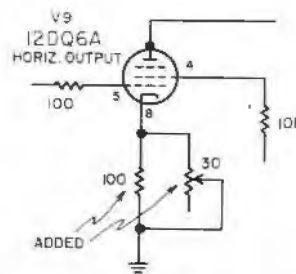


Fig. 4—Circuit modification to help eliminate drive lines.

installing a 30 ohm potentiometer in parallel with a 100 ohm, 1/2 watt resistor in the cathode circuit of the horizontal output 12DQ6A tube. The control permits positive adjustment of the stage and is usually adjusted to the position where the vertical bar is just removed from the picture tube presentation.

Dear Sir:

Is there anything I can do to reduce the accumulation of dust on the faces of picture tubes? In some locations picture tubes cloud up in a very short time. My customers rightly object to paying for a service call just to have the face of the picture tube cleaned. Is there a coating that can be used to help reduce this collection of dust on the picture tube face?

Pittsburgh, Pa.
S. P.

Some technicians have found that the spray they use for anti-static purposes on record players can also be helpful in such instances. Anti-static spray is usually available from electronic distributors. ■ ■

- 1 AVAILABLE LIGHT PHOTOGRAPHY by H. M. Kinzer . . . The most authoritative book on available light.
- 2 THE AMATEUR'S 8MM MOVIE GUIDE by Sid Norinsky . . . The one complete book on the art of 8mm movie making.
- 3 FLASH FOR BETTER PHOTOGRAPHY by Bill Bouie . . . Your complete guide to better flash pictures, including speedlight.
- 4 MOUNTING, PROJECTING & STORING SLIDES by N. Rothschild and G. B. Wright . . . Fully explains and illustrates how to mount, file and show all sizes and types of slides.
- 5 OFFICIAL 35MM CAMERA RATING GUIDE by Herbert Keppler . . . The only authoritative guide . . . lists complete facts and specifications.
- 6 GUIDE TO PERFECT EXPOSURE by George and Cora Wright . . . All you need to know for correct exposure, with step-by-step instructions.
- 7 COLOR PHOTOGRAPHY TECHNIQUES by Arthur Kramer . . . Complete how-to-do-it explanations including processing and printing techniques.

SPECIAL

"Care and repair of HI-FI"

Plus any 3 of these books

for only \$6.00

(SPECIAL FOR OUR READERS)



The above paper bound books are regularly sold for \$1.95 each.

To purchase three of them, plus "Care and repair of HI-FI" for \$2.50, would cost \$8.35.

ALL OF THESE BOOKS AVAILABLE IN SINGLE COPIES AT LIST PRICE, ALSO AT YOUR PHOTO BOOKSHOP AND/OR PARTS JOBBER.

COWAN PUBLISHING CORP.
Book Division
300 West 43rd St., New York 36, N. Y.

I enclose _____ for _____ copies of Vol. 1 "Care and Repair of HI-FI" (Postpaid) plus the three books I have circled

1 2 3 4 5 6 7

Name _____

Address _____

City _____

Zone _____ State _____

FULL RANGE FM RECEPTION!



Completely Preambled
Non-rusting gold anodized aluminum elements snap into place. Everything is furnished; there is nothing else to buy. You get perfect reception up to 50 miles from transmitters.

COMPLETE KIT NO. A-125
(shown above) List \$18.95
TURNSTILE KIT NO. A-124
standard aluminum elements List \$15.95

FM Golden Dipole Kit
No. A-267 List \$17.25
Dipole Kit No. A-261
standard aluminum
elements List \$14.95

AT YOUR DEALER OR WRITE DIRECT
TELCO ELECTRONICS MFG. CO.

Division of G-C Textron Inc.
Los Angeles—Rockford, Illinois

SENCORE Handy "36" R-C Substitution Unit



Most Often Needed Components At YOUR Fingertips!
3 pole, 12 position switch individually selects one of the "36" components for direct substitution.
Contains:
★ 12-1 watt 10% resistors from 10 ohms to 5600 ohms
★ 12-1/2 watt 10% resistors from 10K ohms to 5.6 megohms
★ 10-600 volt capacitors from 100-mfd. to .5-mfd.
★ 1-10mfd., 450V Electrolytic
★ 1-40mfd., 450V Electrolytic
★ For Shop, Lab, or outside service AVAILABLE AT ALL PARTS DISTRIBUTORS!

ONLY \$12.75
DEALER NET

POPULAR SENCORE PRODUCTS
• Transistor Tester
• Leakage Checker
• Filament Tester
• Voltage Regulator
• Bias Supply

SENCORE SERVICE
INSTRUMENTS CORP.
171 OFFICIAL RD., ADDISON, ILL.

Cut out this ad now for further information.

LOOKING FOR TROUBLE?

[from page 27]

large resistance readings to ground (through R37, R89, R150 and the electrolytic capacitors of the medium voltage power supply). An open C46 would have had no effect on the normal resistance readings of the circuit.

AGC Servicing Hints:

1. When there is any doubt if the trouble is in the *agc* circuit, measure the *dc* voltage at the video detector load and on the *if agc* line (with the set tuned to an active channel). The reading at the video detector load should be approximately -5 volts and about -3 to -7 volts on the *agc* line. Incorrect voltages measured at these points indicate various kinds of trouble as outlined in Table 1.

2. A quick check to localize trouble in a keyed *agc* stage is to short the control grid to the cathode of the keyer tube just long enough to measure the negative *dc* voltage which is developed at the keyer tube plate. Shorting the two pins together allows the tube to conduct throughout the keyer pulse instead of only when the horizontal sync pulses of the composite video signal are applied to the control grid. In a normally-operating stage with this cathode-grid short, the negative voltage at the keyer tube plate should measure about -40 to -70 volts. If this voltage is present, the trouble is probably in the input video line connected to the grid of the keyer tube. If the negative voltage is too low or not present, the trouble is either a fault in the horizontal pulse input to the keyer tube, the keyer stage itself or the *agc* bus.

3. In checking tubes for *agc* troubles, don't overlook *agc* diodes which may be part of a multi-purpose tube and located in some other section of the chassis. The *agc* diode, when used, is often found in combination with the 1st audio amplifier.

4. In particularly difficult *agc* troubles, a bias box can be connected to the *agc* bus while the *agc* stage is disconnected from the circuit. If the set operates normally, the *agc* bus is probably good, and either the *agc* stage or one of the input lines to the *agc* stage is defective. If the set is still abnormal, the trouble is most likely in the *agc* bus.

SELF-SERVICE TUBE TESTERS \$25 to \$50

Used—reconditioned complete with signs and floor model cabinets. Get into a profitable business with a minimum investment. Write, ED MOERKE, P. O. Box No. 264, Zion, Ill.

Advertiser's Index

Acme Electric Corporation	29
Aeravox Corporation	1
American TV & Radio Co.	29
Belden Mfg. Co.	Cover 3
Cornell-Dubilier Elec. Corp.	10
General Cement Mfg. Co.	27, 32
Heath Company	2
RCA Electron Tube Division	Cover 4
Raytheon Mfg. Co.	Cover 2
Service Instruments Corp.	32
Tabe-Deutschmann Corp.	7, 8, 9
Tung-Sol Electric, Inc.	4, 5
U-Test-M Mfg. Co.	32
Vis-U-All Prods. Co.	27
Xcelite, Inc.	28

GE ELECTRONIC HARDWARE



SAVE MONEY THE HANDY HUNDRED WAY!
ANGLES • BRACKETS • CLAMPS • CLIPS • FELTS • GROMMETS • LUGS • NUTS • PULLEYS • RETAINING PINS • RIVETS • SCREWS • SPRINGS • TERMINAL STRIPS • WASHERS ... 315 DIFFERENT PRODUCTS IN

G-C ECONOMY PAKS!

ASK YOUR G-C JOBBER... LOOK FOR THE G-C HARDWARE RACK

GENERAL CEMENT MFG. CO.
Division of Textron Inc., Los Angeles—Rockford, Illinois

FREE CATALOG... send postcard today!

If it's worth Engineers' time...

... It's worth Engineered Cable

Belden INTERCOMMUNICATING AND SOUND SYSTEM CABLES


Indoor-outdoor, phones or speakers—there is a Belden engineered cable to meet your needs for a permanent, trouble-free installation.

"Items from the Complete Belden Line"

The TV station, the systems for music, paging, and intercommunication in the new Prudential Insurance Company of America's Building in Chicago have been—wired by Belden.

Belden WIREMAKER FOR INDUSTRY SINCE 1902 CHICAGO

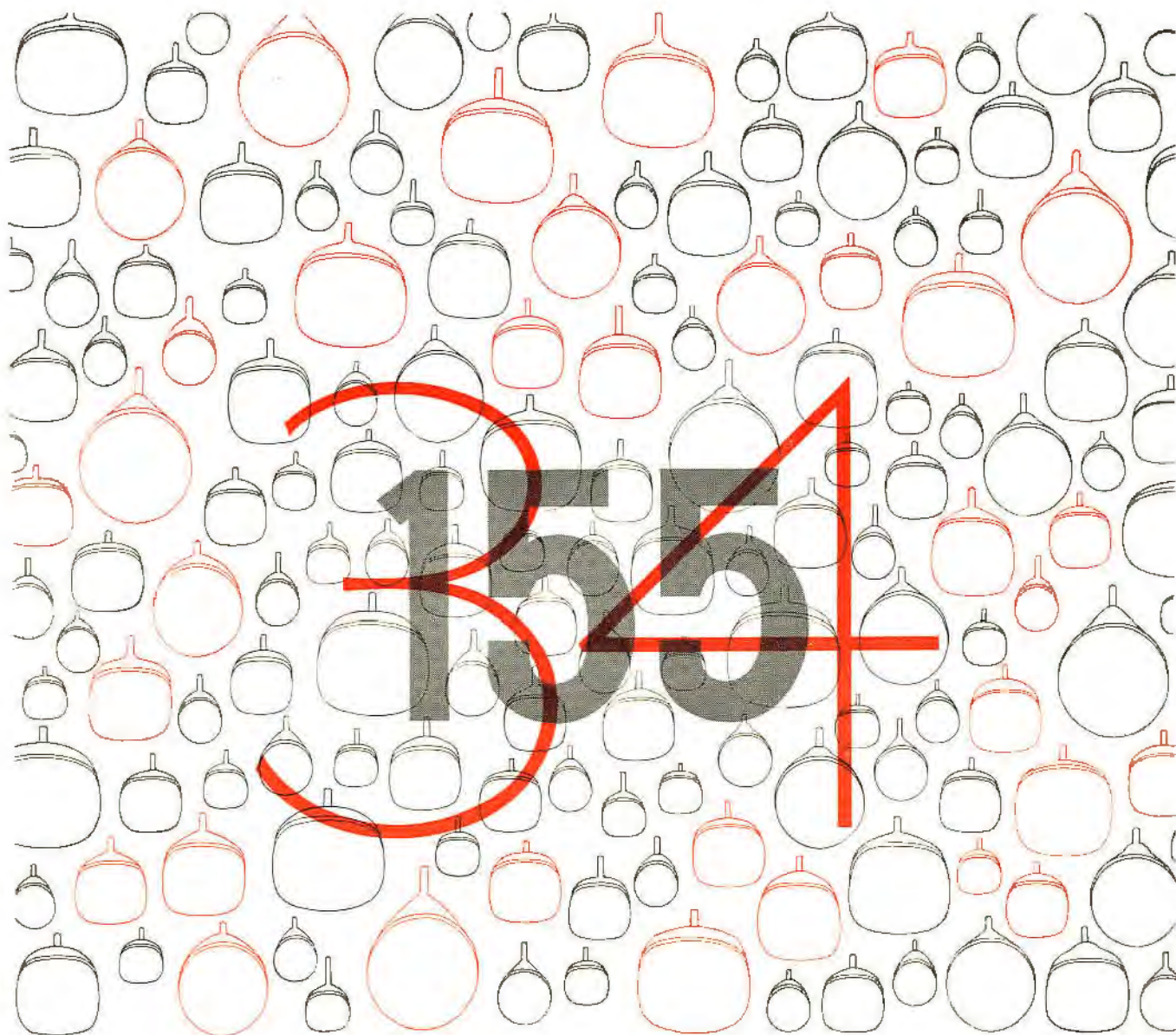Magnet Wire • Lead and Fixture Wire • Power Supply Cords, Cord Sets and Portable Cord • Aircraft Wires
Welding Cable • Electrical Household Cords • Electronic Wires • Automotive Wire and Cable




Just 34 RCA Silverama Picture Tubes now replace 155 types!

RCA cuts Picture Tube inventory and complex replacement problems, by nearly 80%. Simplification—that's like money in the bank—as every TV service technician knows.

Best of all, your customer is satisfied, too. He gets a brand name he knows and trusts... that gives his old set a picture that's often clearer and brighter than when the set was new... and that carries a full year's warranty, backed by RCA.

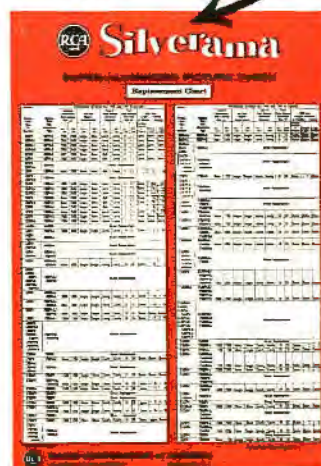See your local Authorized
RCA Distributor for your
copy of the Silverama
Replacement Chart



RADIO CORPORATION OF AMERICA

Electron Tube Division

Harrison, N. J.

Silverama®