

SEPTEMBER, 1953

SEP 29 1953

# Radio-Television SERVICE DEALER

095-03-02  
90 OCT 15 1953  
AMERICAN  
RADIO-TELEVISION  
SERVICE  
DEALERS  
ASSOCIATION  
CHICAGO, ILL.  
2




The Professional Radio-TVman's Magazine

## IN THIS ISSUE:

- Sync Circuits, Part 2  
(TV Symposium Series No. 7)
- Flyback Transformer Tester
- 3 Speed Changer Conversion
- Q Measurements and Meters, Part I
- Looking For Trouble?
- Television Interference Aids
- Servicing Clock—Radio Timers
- Video Speed Servicing Systems

**AM-FM-TV-SOUND**
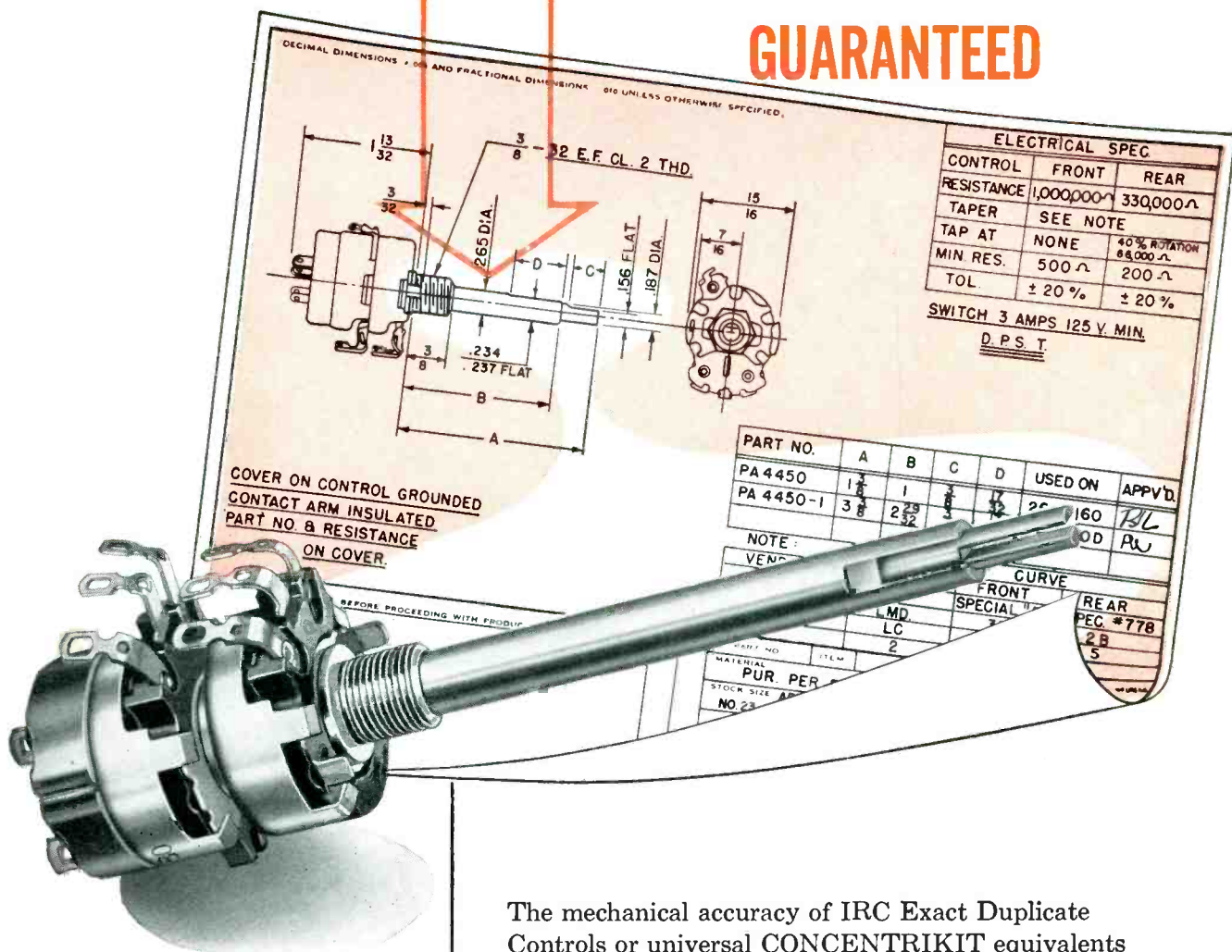
# HERE'S WHY IRC EXACT DUPLICATES ARE DOUBLE-MONEY-BACK GUARANTEED



**ONLY IRC GUARANTEES SATISFACTORY MECHANICAL FIT AND ELECTRICAL OPERATION OR DOUBLE-YOUR-MONEY-BACK**

The typical manufacturer's specifications shown here are exactly duplicated by IRC QJ-180 control. CONCENTRIKIT assembly includes P1-229 and R1-312 shafts with B11-137 and B18-132X Base Elements, and 76-2 Switch.



*Wherever the Circuit Says* ~~~

The mechanical accuracy of IRC Exact Duplicate Controls or universal CONCENTRIKIT equivalents is based on set manufacturers' procurement prints. Specifications on those prints are closely followed.

Shaft lengths are *never less* than the set manufacturer's nominal length—*never more* than  $\frac{3}{32}$ " longer.

Shaft ends are precisely tooled for solid fit.

Inner shaft protrusion is accurately duplicated for perfect knob fit.

Alterations are never needed.


For Exact Duplicate Controls, specify IRC. Most Service Technicians do.

## INTERNATIONAL RESISTANCE CO.

404 N. Broad Street, Philadelphia 8, Pa.

In Canada: International Resistance Co., Ltd., Toronto, Licensee

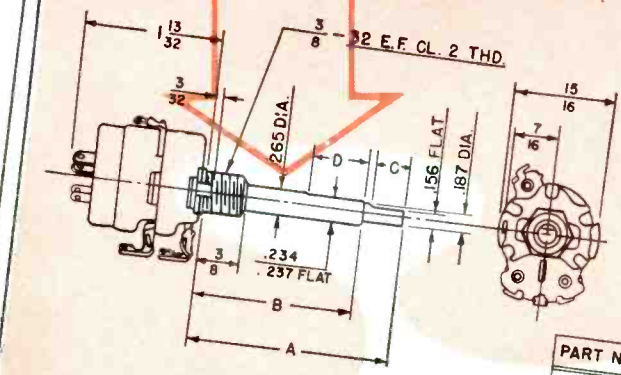DECIMAL DIMENSIONS IN INCHES AND FRACTIONAL DIMENSIONS IN INCHES UNLESS OTHERWISE SPECIFIED.



ELECTRICAL SPEC		
CONTROL	FRONT	REAR
RESISTANCE	1,000,000 $\Omega$	330,000 $\Omega$
TAPER	SEE NOTE	
TAP AT	NONE	40% ROTATION
MIN RES.	500 $\Omega$	200 $\Omega$
TOL.	$\pm 20\%$	

SWITCH 3 AMPS 125 V. MIN.  
D. P. S. T.

COVER ON CONTROL GROUNDED  
CONTACT ARM INSULATED  
PART NO. & RESISTANCE ON COVER.

PART NO.	A	B	C	D	USED ON	APPV'D.
PA 4450	1	1	1	1	160	PL
PA 4450-1	3	2	2	2	160	PW

NOTE: VENDOR CURVE FRONT SPECIAL REAR SPEC #778

MATERIAL L.M.D. LC 2

PUR. PER STOCK SIZE

NO. 23

Depend on Mallory  
for  
Approved Precision Quality



“...and **BE SURE**

**the VIBRATORS are MALLORY!”**

That's the best way to be sure your service jobs stay "sold". You can depend on Mallory Vibrators to give more years of service. Their precision quality is the answer to time-wasting call backs. These are just two of the reasons why 5 out of 6 service men prefer Mallory for all their service work.

And the preference doesn't end there. They are more widely used as original equipment than all other makes combined. The patented, tuned mechanism in Mallory Vibrators gives better performance because:

*Slow contact make . . .  
means less wear*

*High contact pressure . . .  
means low resistance*

*Fast clean break . . .  
means reduced arcing*

The next time you order vibrators . . . be sure to ask for Mallory. You'll get better vibrators, available in a complete line, meeting original equipment specifications . . . yet they cost no more. You can be sure that every service job is done right the first time.

P. R. MALLORY & CO. Inc.  
**MALLORY**

CAPACITORS • CONTROLS • VIBRATORS • SWITCHES • RESISTORS  
RECTIFIERS • POWER SUPPLIES • FILTERS • MERCURY BATTERIES

**APPROVED PRECISION PRODUCTS**

**P. R. MALLORY & CO., Inc., INDIANAPOLIS 6, INDIANA**



# the CDR Rotor

**sells faster...sells easier**

*because.....*

## **The best line of TV Rotors money can buy**

It is the complete line of quality rotors, with a model and type to best serve 'most every type application.

## **TV Spot Campaign**

To reach the buying public, an intensive campaign on Television in key markets pre-selling CDR ROTORS for you.

## **Newspaper Advertisements**

Also directed at the consumer, a supporting campaign in key city newspapers exploiting the advantages of the CDR ROTOR.

## **Moving Displays**

It's causing excitement everywhere, this display that is an eye and traffic stopper, a silent salesman for the CDR ROTOR.

## **Envelope Stuffers**


Here's another selling tool that may be mailed directly to your customers, selling them the CDR ROTOR in their home.

## **Newspaper Mats**


A full set of completely prepared advertisements for dealers and distributors to capture extra CDR ROTOR business.
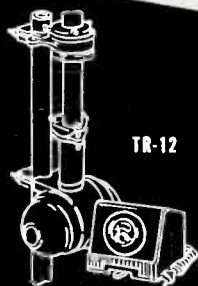
## **Window Streamers**


They let everybody going into and by your store know that you have the CDR ROTORS, a colorful and eye-catching streamer.



TR-12

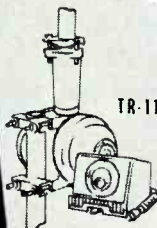

TR-11

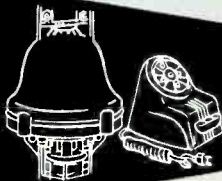


TR-2



**THE RADIART CORPORATION**  
CLEVELAND 13, OHIO



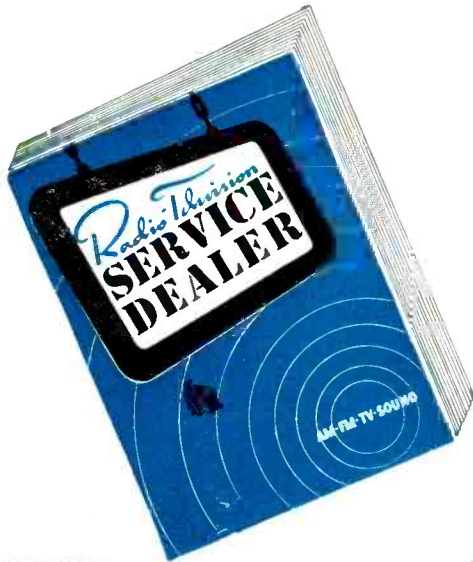**CORNELL-DUBILIER ELEC. CORP.**  
SOUTH PLAINFIELD, NEW JERSEY



**Sanford R. Cowan**  
**EDITOR & PUBLISHER**

•  
**SAMUEL L. MARSHALL**  
**MANAGING EDITOR**

•  
**LEONARD LIEBERMAN**  
**Contributing Editor**

•  
**COWAN PUBLISHING CORP.**  
 67 WEST 44TH ST.  
 NEW YORK 36, N. Y.



15 or 12 in.  
 Bass Reflex Cabinet


*High Fidelity*

**at moderate cost\***

Every essential for superb tone— $\frac{1}{2}$ " wood sides,  $\frac{1}{2}$ " acoustic lining, 4.3 cu. ft. capacity, heavy construction (wt. 31 lbs).

But moderate cost with leatherette covered sides. Hand rubbed solid mahogany or blonde hardwood around front adds genuine richness. Compare it with any other and see for yourself. Only \$45.00 net (slightly higher west of Rockies).

**Send for FREE Folder**

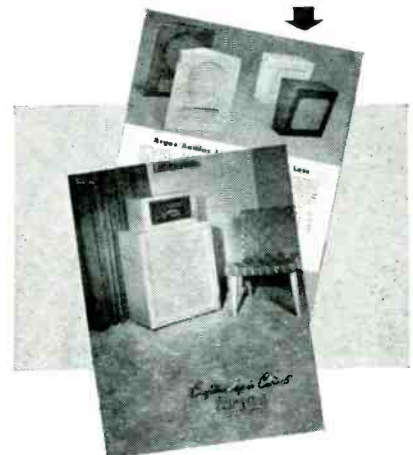

\*By makers of famous TV Tube Caddy®



**Vol. 14, No. 9**

**SEPTEMBER, 1953**

Trade Flashes .....	6
Editorial .....	10
Symposium No. 7—Sync Circuits, Part 2, by Leonard Lieberman .....	19
Concluding installment on various types of sync circuits used in commercial television receivers.	
Flyback Transformer Tester, by Harry Casey .....	23
Description and applications of a new instrument that aids the serviceman in testing the horizontal output section of a TV receiver.	
3 Speed Changer Conversion, by L. C. Burdick .....	26
Excellent hints for servicemen in the conversion of phonographs to accommodate three speed record changers.	
Q Measurements and Meters, Part 1, by Rufus P. Turner .....	29
Pertinent data regarding the measurement of coils and capacitors.	
Looking for Trouble?, by Cyrus Glickstein .....	32
Troubleshooting quiz on interference.	
Television Interference Aids .....	36
A valuable wall chart for the service technician.	
Video Speed Servicing Systems Data Sheets (VSSS) .....	38
Information this month covers the Admiral Model No. 19 series, Sentinel Model No. 454, Sylvania No. 1-274 chassis, and Sylvania No. 1-437 chassis.	
Servicing Clock—Radio Timers, by Telechron Dept., General Electric Co. .....	48
Servicing Telechron clock-radio timers illustrated with pictures.	
New Tubes .....	50
Circuit Court .....	52
Capehart CX-37-AGC; horizontal oscillator and AFC.	
Personnel Notes .....	54
New Products .....	56
Association News .....	63
Advertisers' Index .....	72

RADIO-TELEVISION SERVICE DEALER is published Monthly by Cowan Pub. Corp., 67 West 44th St., New York 36, N. Y. Subscription price: \$2 per year in the United States, U.S. Poss. & Canada; elsewhere \$3. Single Copies 25c. Reentered as second class matter Sept. 25, 1950 at the Post Office at New York, N. Y. under the Act of Mar. 3, 1879. Copyright 1953, Cowan Pub. Corp.

SANFORD L. CAHN, Advertising Director HARRY N. REIZES, Advertising Manager

DAVID SALTMAN, Production Manager NATHAN BOYCE, Circulation Mgr.

BEN WALKER, Editorial Assistant

TED E. SCHELL, 2700 West 3rd St., Los Angeles 5, Calif., Dunkirk 2-4889

HAROLD F. MANN, Mid-West Sales, 333 No. Michigan Ave., Chicago. Franklin 2-7100

POSTMASTER: SEND FORM 3579 TO RADIO-TELEVISION SERVICE DEALER,  
 67 WEST 44TH ST., NEW YORK 36, N. Y.


# 3 New Electrical Advances!

## CHANNEL MASTER'S all-new UHF BOW-FLECTOR


model no. 408

The highest gain Bow and Screen antenna ever developed — single or stacked!

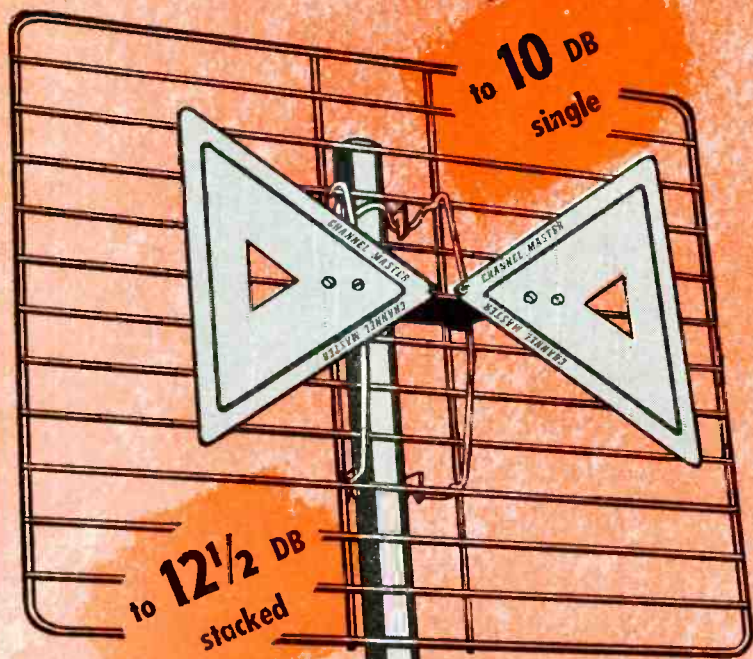
- 1. Enlarged Reflecting Screen.** 53% more reflecting area — higher, flatter gain level.
- 2. Full-Wave Spacing** of stacked antennas. Provides highest stacking gain ever obtained in an antenna of this type.
- 3. 2-Stage Stacking Transformers** for broad-band impedance match. Delivers high stacking gain over entire UHF band.



**Terrific gain!**

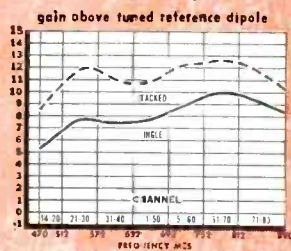

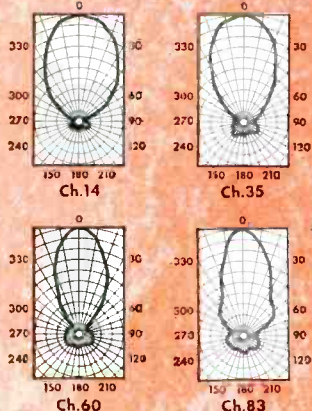Horizontal Polar Patterns  
(Relative Voltage)



## New Mechanical Features

- Deep-embossed "rigidized" aluminum dipoles.
- Snap-in assembly. No U-Bolts.
- High-impact molded insulator.

**PLUS** "Free-Space" terminals that prevent picture dim-out caused by the accumulation of dirt, ice or rainwater between antenna terminals.



**Only 20 seconds to install!**

Just snap Bow into Screen, then fasten entire assembly to mast with Channel Master's exclusive "SPEED-NUTS." The antenna cannot move, twist, flutter, or vibrate! The light-weight Bow Flector is the most rugged, fastest-installing antenna of its type.



One of 5  
Great New  
Channel Master  
Products  
For Fall!

**CHANNEL MASTER CORP.**

ELLENVILLE, N. Y.



Ask your Channel Master distributor for complete technical literature.

# You've never seen a mast like it!

## CHANNEL MASTER'S

*all-new*

# STRATO-MATIC

## TELESCOPING MAST

for antenna installations  
that are  
*easier • faster*  
*• safer*



### Featuring the Amazing "Third Hand!"

— an automatic, removable locking device that actually acts as your "third hand," holds mast sections up when you let go! The Third Hand converts each guy ring, in turn, into a "safety lock." This permits you to raise sections freely, using only one hand. And . . . sections cannot slide down when you let go.

### Automatic Mast Extension

The Step-Up Key, inserted through the bottom of the mast tubing, automatically extends each mast section 6 inches. Mast sections are kept partially extended even after mast is placed in vertical position — without using hardware or locking bolts!

### World's Finest Mast Protection!

16-Gauge Mastings  
**HOT-DIP  
GALVANIZED**

Most permanent type of mast corrosion protection available today. Sections are immersed in cauldron of molten zinc, until a thick layer of pure zinc is fused to inner and outer surfaces — so thick it actually adds to the weight of the mast; gives long-term protection!


**ZINC IS  
SELF-HEALING!**

When the protective zinc coating is scratched or broken, the surrounding zinc actually goes to work to "heal" the wound. Thus, the base metal is automatically protected against damage due to installation or handling. The only coating with this ability.


18-Gauge Mastings  
**HEAVY ZINC  
ELECTRO-PLATING**

Heavy layer of bright zinc, exceeding Army-Navy specifications, provides effective long-lasting protection against elements. A chromate dip adds brightness; increases corrosion resistance. The strongest, most durable protection jacket of its type.

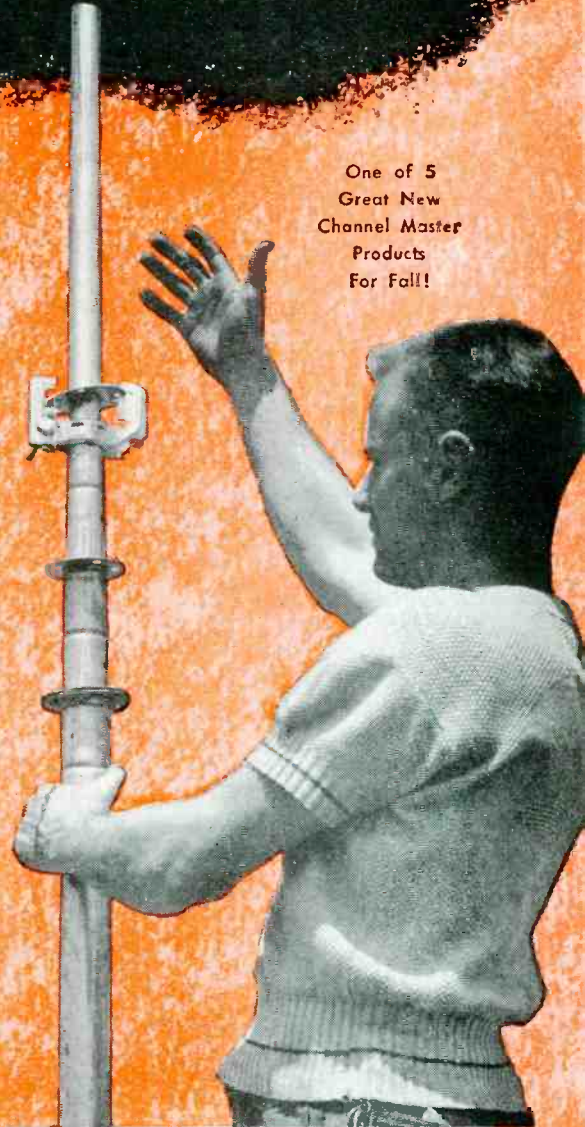One of 5  
Great New  
Channel Master  
Products  
For Fall!




Inter-Locked Sections

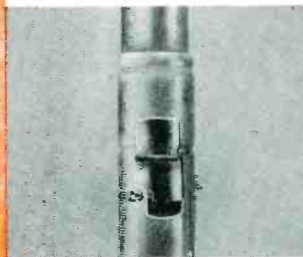

Safety Rings prevent sections from pulling out of each other. Natches in sections engage bolt — no twisting.

No Hidden Holes

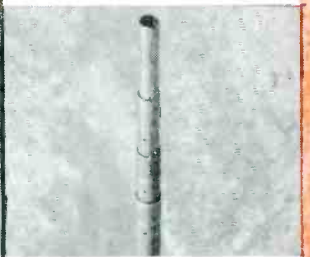

Step-Up Key automatically extends mast sections high enough to provide easy access to bolt holes. You don't have to pull up next section to insert bolt!

Model No.		Sections	Lengths	Weights	
16-Gauge	18-Gauge			16-Gauge	18-Gauge
1620	1820	A, B	20'	20 lb.	15 lb.
1630	1830	A, B, C	30'	32 lb.	25 lb.
1640	1840	A, B, C, D	40'	46 lb.	35 lb.
1650	1850	A, B, C, D, E	50'	61 lb.	47 lb.



**CHANNEL MASTER CORP.** ELLENVILLE, N. Y.

Ask your Channel Master distributor for complete technical literature.

# Thousands depend on PHOTOFACT! THEY TELL YOU WHY

Unsolicited letters tell what the world's finest TV and Radio Data means to Service Technicians



**L. A. Moe**  
American Engineering Co.  
13 S. Barstow  
Eau Claire, Wisc.

"SAMS PHOTOFACTS are without a doubt one of the most valuable tools in our service organization. Keep up the work."



**Raymond Murphy**  
Tampa TV Mart, Inc.  
8131 Nebraska Ave.  
Tampa 4, Fla.

"Running a service shop efficiently is a tough job. The people can't realize what a tremendous help you are. Our shop, without your complete set of SAMS, would be like back in the days of radio and the screw-driver technician. We really would be lost without your SAMS Library... you're doing a splendid job."



**Harry J. Kolodney**  
TV-Radio Service  
266 Belmont Street  
Fall River, Mass.

"In regard to PHOTOFACT Sets—I can only add my voice to thousands of others in praise. It is a pleasure to work from your schematics. Your folders are far superior to all others, including the manufacturer's own service notes."

## NOW! GET THE PROOF FOR YOURSELF!

**FREE**

We'll send you a Free Photofact Folder on any receiver covered in Sets No. 101 and following

Learn for yourself—at our expense—how PHOTOFACT pays for itself by earning bigger profits for you! Select any Folder appearing in PHOTOFACT Sets Nos. 101 and following, from the PF Index. (If you haven't a copy, see your distributor.) When you write for your Free Folder, be sure to state Photofact Set and Folder Number as shown in the Index (offer limited to Folders in sets subsequent to No. 101). Get your Free Folder now. Examine, use, compare—see why PHOTOFACT belongs in your shop!

HOWARD W. SAMS & CO., INC.  
27 E. 46th St., Indianapolis 5, Ind.

**HOWARD W. SAMS & CO., INC.**



## Raytheon Announces The "Service-Saver" — A New Aid To Television Receiver Servicing

A new and unique method of helping television servicemen diagnose, and repair troubles with a television set was unveiled by Carrol W. Hoshaur, Director of Raytheon Sales Engineering at the Raytheon National Sales Conclave held at the Chicago Opera House. This new device consists of a booklet containing photographs of 40 possible troubles with a TV set's picture. Each picture is numbered for easy identification. When something goes wrong with the set, the owner calls his serviceman and tells him, "My picture looks like number seven or twenty-four as the case may be."

In the Raytheon Service manual that is distributed to all TV servicemen, there is also a "Service Saver" section that shows the same numbered 40 conditions, and gives schematic diagrams of the circuits and what causes the trouble, plus a complete list of parts and tubes that might be involved. It also contains hints and kinks for quick repair—what to test, what to change, what component might be causing the difficulty. This method of television service enables the serviceman to quickly diagnose and remedy the great majority of troubles and he will be able to effect a solution in ten to twenty per cent of the time he normally did without this unique approach."

Before introducing the "Raytheon Service Saver" to the public, Raytheon tested Mr. and Mrs. America's ability to describe correctly the picture condition they saw on their TV set. 92% of the subjects described the picture condition accurately.

## RMS Conducts Servicemen's Forum

A half-hour telecast of a section of a servicemen's forum conducted by an official of Radio Merchandise Sales, Inc., was held at the studios of WHIZ-TV, Channel 50, Zanesville, Ohio. The combined RMS forum and WHIZ telecast is claimed to be one of the most unique presentations made by members of the TV industry. Martin Bettan, RMS engineering head, lead over 125 dealers at the studios of WHIZ in a technical discussion on

UHF. In the latter 15 minutes of the program technical questions were then answered by the RMS technical chief.

At this early date, accurate results are not available, but immediate responses to the broadcast (phone calls and letters from the viewing public) and the enthusiasm of the local technicians, indicate that public interest "live" telecasts, when coupled with stimulation at the technical levels, is a most effective "hypo" for the TV business.

## Television Interference Aids Distributed

RETMA, in cooperation with the Washington Television Interference Committee and the Electric Institute of Washington, has prepared two educational aids on the causes and cures of television interference for distribution to all TV service dealers and technicians in the greater Washington, D. C., area. It is pointed out in a pamphlet on the general subject of TVI that the radio amateur is actually involved in "only a small portion" of the television interference picture. A number of other causes of the complex TVI problem are detailed, leading to the conclusion that "the average television receiver owner is not trained either to diagnose or to understand his personal interference situation. He requires honest and intelligent advice from his service technician."

## Niagara Frontier Gets UHF Techniques Preview

Television technicians of the Niagara area were given a preview on the techniques of UHF television reception recently in Buffalo, N. Y. The preview was another of the well-received Taco UHF Television Clinics presented in all parts of the country. Following talks by Taco and WBUF officials outlining the general theories of UHF and local conditions associated with television, a round table discussion was held during which the technicians enjoyed the opportunity of presenting their specific UHF problems.

## Viewing Distances For Television

Experts at Emerson Radio and Phonograph Corporation report thousands



of observations revealing that the proper viewing distances for television range between four and eight times the size of the picture tube. For example, a 17-inch receiver gives the most satisfactory service when viewed from a distance of five to eleven feet. In a similar manner, a 21-inch TV set is best viewed from distances between seven and fourteen feet, while the 27-inch receiver's most satisfactory viewing range is nine to eighteen feet. One conclusion drawn from the Emerson survey is that the 27-inch video receiver is not too readily adaptable for home usage since a viewing range of such distance is rare in the average home.

#### Philco Test Equipment Line

The second double-page advertisement appearing in this issue culminates the first phase of the Philco campaign. Combining new circuits, accuracy and versatility with low cost, the advanced design Philco line of test equipment offers the service technician a great variety of units that, when combined, can form a complete service laboratory to meet every VHF and UHF servicing requirement. Among the Philco test equipments previewed are completely redesigned versions of standard Philco test units. Entirely new models, among them the Model G-8000 *vhf* to *uhf* Signal Generator Adapter and Model G-8002 Auto-Level Sweep Generator, lend a revolutionary approach to *uhf* servicing by providing the most modern tools for this newest advance in servicing.

Availability for purchase of new model test equipments will be announced by Philco through the medium of advertising in this publication.


#### JFD Holds UHF-VHF Antenna Clinic

TV service-dealers in the Greenville, Spartanburg, Asheville areas of North and South Carolina attended a "JFD Antenna Clinic" sponsored jointly by Dixie Radio Supply Company and the JFD Manufacturing Company in Greenville, South Carolina's Poinsett Hotel. JFD's Mort Leslie discussed UHF and VHF antenna installation problems, pointing out individual antenna designs best adapted to various installation requirements. More than 600 attending service-dealers participated in the lively forum, which was preceded by a Buffet Supper.

#### Sylvania Offers "TNT Chest" For Servicemen

A handsome, new tube and tool carrying case, designed particularly to meet the needs of TV-radio servicemen, is being offered by Sylvania Electric Products Inc., in a premium promotional campaign, which will run through November 15. The sturdy,

## single test — double check

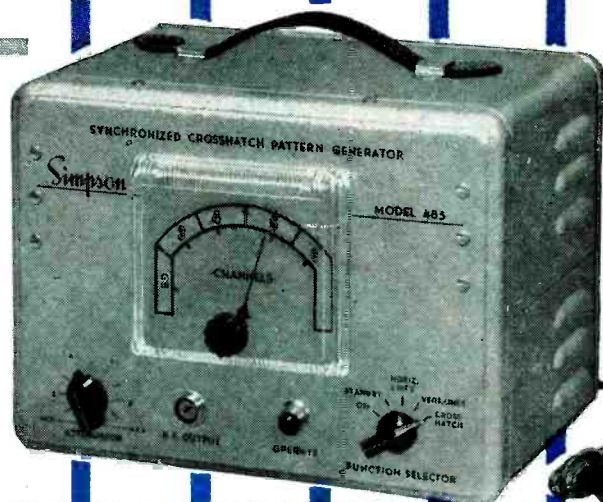

new

Simpson

MODEL 485

### synchronized crosshatch pattern generator

You control your own broadcast test pattern for initial installations and linearity adjustment calls with the Simpson Model 485. Newly developed Model 485 provides a synchronized signal, modulated on the carrier frequencies of channels 2 through 6, which can be tuned and sent through the receiver under test — anywhere, at any time! The vertical and horizontal sync pulses provide means by which the pattern is locked in on the TV receiver. Since this is a transmitted TV signal, it is not necessary to check against a broadcast pattern. Linearity is double checked with a single test — no call back to cut service profits.

Dealer's net price, including special output cable for 75 and 300 ohm terminations, only \$147.50. Ask your jobber for full information or write —


#### SIMPSON ELECTRIC COMPANY

5200 West Kinzie Street, Chicago 44, Illinois  
CO 1-1221

BURTON BROS. ADVERTISING

Another reason why Simpson is world's largest manufacturer of test equipment

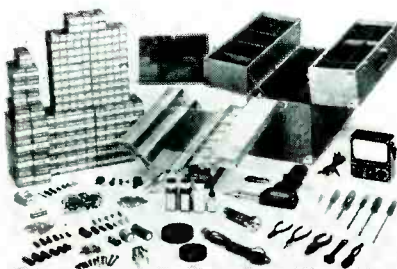new Sylvania case, or "TNT Chest", will hold 187 tubes, meter, a complete set of tools, soldering guns, and a



Sylvania "TNT" Chest


sufficient number of parts for any house call. A convenient feature of the case is its aluminum tool and parts tray, divided into 14 separate compartments, which holds all needed tools and parts. The case is light and roomy, measures only 9" wide, 15" high, and 20" long.

#### Boise Ordinance Passed

An ordinance was adopted by the Boise, Ida., City Council! (July 13) amending the city building code to provide regulations and standards for the installation and maintenance of television antennas. Approved without any protests being heard, the ordi-
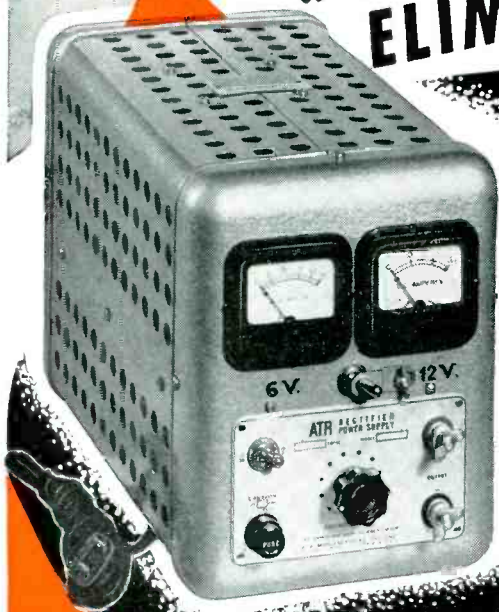
# ATR

Makes it easy to  
**DEMONSTRATE and TEST**  
 D.C. apparatus from A.C. lines  
 with "A" BATTERY  
**ELIMINATORS**



for  
**Demonstrating  
 and Testing  
 Auto  
 Radios**

**6 VOLT  
 OR 12 VOLT!**

6 or 12 volt D.C. combination out-  
 put available by means of simple toggle  
 switching arrangement, properly safe-  
 guarded to prevent accidental switching.

*See your jobber  
 or write factory*

New Models . . . Designed for testing  
 D.C. Electrical Apparatus on Regular A.C. Lines.  
 Equipped with Full-Wave Dry Disc Type Rectifier,  
 Assuring Noise-less, Interference-Free Oper-  
 ation and Extreme Long Life and Reliability.

✓ NEW MODELS    ✓ NEW DESIGNS    ✓ NEW LITERATURE  
 "A" Battery Eliminators, DC-AC  
 Inverters, Auto Radio Vibrators

# ATR


## AMERICAN TELEVISION & RADIO Co.

*Quality Products Since 1931*  
 SAINT PAUL 1, MINNESOTA—U. S. A.

nance provides that any person instal-  
 ling or repairing any outside televi-  
 sion or radio receiving antenna over  
 15 feet in height must obtain a per-  
 mit from the city building inspector.  
 The ordinance provides further that  
 the city building inspector conduct  
 inspections of television antennas and  
 that metal mast structures supporting  
 outside television or radio antennas  
 be of non-corrodible material and  
 effectively grounded. Use of chimneys  
 or vents for supporting mounts is  
 made illegal by the ordinance.
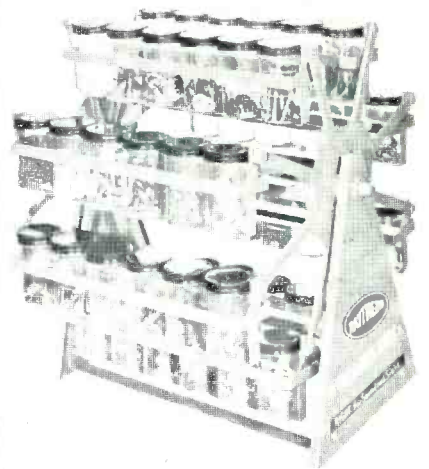
### Raytheon Promotion For Service Dealers

Raytheon has recently announced a  
 new tube promotion item. This item,  
 the Raytheon Tele-Jar Rotor, is a most  
 unique and necessary shop aid for  
 dealers. Specially designed for service  
 dealers, this exclusive promotion item  
 will save them much time, space, and  
 money in small parts storage. Approxi-  
 mately 17" high x 15" wide x 13" deep  
 the Tele-Jar Rotor has 48 transparent  
 plastic, unbreakable jars which are



ideal for storing transistors, crystal  
 diodes, subminiature and miniature  
 tubes, panel lamps, resistors, small con-  
 densors, insulators and hardware. De-  
 signed to give dealer shops a neat "pro-  
 fessional" look, this versatile Tele-Jar  
 Rotor has been manufactured so that  
 it can be used on the bench or on the  
 wall. The Rotor's ferris-wheel motion  
 gives a constant, visible inventory  
 check and facilitates small parts stock-  
 ing.

### Philco Releases New UHF Film

"When UHF Comes to Town" is  
 the title of a new 15-minute film pro-  
 duced by Philco Corporation for re-  
 lease to distributors in areas through-  
 out the country where new UHF  
 air. It is available in 16mm sound for

[Continued on page 13]



# NICE GUY... with a <sup>not</sup> undeserved black eye

*If you understood what your  
RADIO AND TELEVISION SERVICE DEALER  
is up against, you'd buy him a steak for his eye*

WE'LL WAGER DOLLARS to doughnuts you approach a TV-Radio Service Dealer with apprehension — feeling sure he's scheming to "do" you out of an unfair portion of your hard-earned money. This mental black eye given the TV-Radio Service profession by the public is undeserved. When TV-Radio Service Dealers were swept into the spectacular growth of the nation's fastest developing new industry, some made mistakes, but the misguided were mighty few. The vast majority of Television and Radio Service Technicians are capable, efficient, thoroughly trustworthy businessmen doing a magnificent job of keeping pace with a rapidly expanding new industry.

And we know what we're talking about. Since 1945 — that's way back before nationwide TV — the Raytheon Manufacturing Company, through several of America's largest surety companies has been Bonding the repair work of Radio and Television Service Dealers. More than 30,000 Registered Bond Certificates have been issued to service dealers all over the United States, and of the millions of jobs these qualified Bonded dealers have handled we've received less than 50 complaints. We consider this amazing record a marvelous indication of the skill, integrity and ability of these selected service dealers.



*Excellence in Electronics*

RAYTHEON MANUFACTURING COMPANY, RECEIVING TUBE DIVISION  
NEWTON CHICAGO ATLANTA LOS ANGELES



The service dealers that are bonded through Raytheon are nationally known as RAYTHEON BONDED ELECTRONIC TECHNICIANS. They must be skilled technicians, have modern, efficient test equipment, and a wealth of experience to qualify for this coveted classification. They adhere to a strict 8-point Code of Ethics designed to protect you. Here it is:

1. Guarantee all Radio and Television repair work for 90 days.
2. Use only parts of recognized quality.
3. Charge not more than list price for parts installed.
4. Test customers' tubes as accurately as possible.
5. Keep labor charges at a reasonable level.
6. Perform only such work as is necessary.
7. Maintain proper equipment for good repair work.
8. Maintain the highest quality service.

Whatever the make and model of your radio or television sets, next time you need service we'd like to suggest you call a Raytheon Bonded Electronic Technician. Look for his seal. It's the symbol of a service man whose work, way of doing business, and integrity are above reproach. We're sure he'll satisfy you.

RAYTHEON MANUFACTURES TELEVISION AND RADIO TUBES, INDUSTRIAL AND POWER TUBES, TELEVISION AND RADIO SETS, GERMANIUM PRODUCTS, DIATHERMY EQUIPMENT, ELECTRONIC COOKERS, ELECTRONIC MARINE EQUIPMENT, ELECTRONIC DUPLICATORS, INDUSTRIAL EQUIPMENT, ULTRASONIC MACHINE TOOLS AND ELECTRONIC TUBES, SONAR, RADAR AND COMMUNICATIONS EQUIPMENT FOR THE UNITED STATES GOVERNMENT

Raytheon Is Telling Your Side of the Story to over

# 25,000,000 Readers of LIFE

The September 21st issue of LIFE will carry the full page, two color advertisement pictured above, telling your side of the Radio-TV Service story to LIFE'S vast audience. We gladly run this advertisement to help you combat the unjust attacks that have been made on

your profession and to give the public a true picture of the really good job you are doing. It's our way of saying "thank you" for your loyalty to Raytheon Radio and Television Tubes. We assure you their quality and performance will continue to meet your most exacting requirements.



*Excellence in Electronics*

**RAYTHEON MANUFACTURING COMPANY**


Receiving Tube Division

Newton, Mass., Chicago, Ill., Atlanta, Ga., Los Angeles, Calif.

RAYTHEON MAKES ALL THESE:

RECEIVING AND PICTURE TUBES • RELIABLE SUBMINIATURE AND MINIATURE TUBES • GERMANIUM DIODES AND TRANSISTORS • NUCLEONIC TUBES • MICROWAVE TUBES

by S. R. COWAN

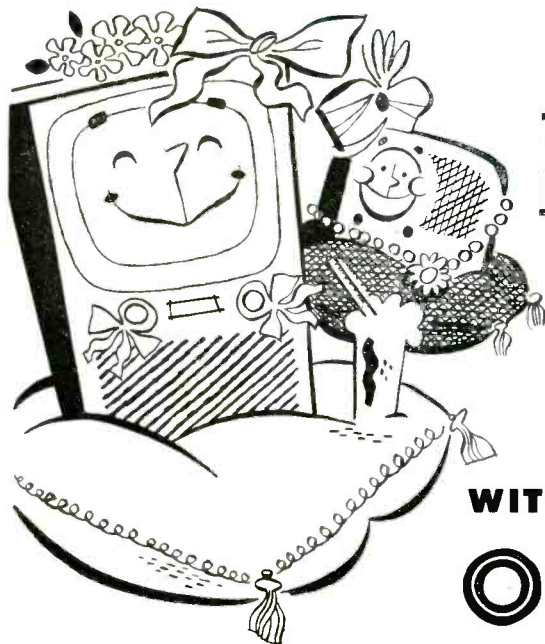

## PAMPER

YOUR TV

AND

RADIO SETS

WITH DEPENDABLE

# OHMITE®


REPLACEMENTS

## Little Devil® COMPOSITION RESISTORS




Tiny, yes... but what dependability, ruggedness, and stability! And they provide an *extra* margin of safety—being rated at 70C rather than 40C. Completely sealed and insulated by molded plastic, they meet all JAN-R-11 requirements... are available in 1/2, 1, and 2-watt sizes in all RTMA values.

## TYPE AB NOISE-FREE POTENTIOMETERS

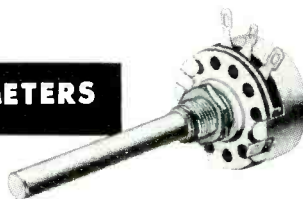

Because the resistance material in these units is solid-molded—not sprayed or painted on—continued use has practically no effect on the resistance. Often, the noise-level *decreases* with use... and they provide exceptionally long, trouble-free service. Rated at 2 watts, with a good safety factor.

## BROWN DEVIL® AND DIVIDOHM® RESISTORS

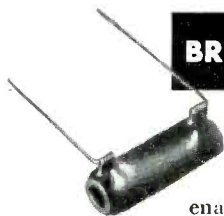

BROWN DEVIL fixed resistors and DIVIDOHM adjustable resistors are favorite vitreous-enameled units! DIVIDOHM resistors are available in 10 to 200-watt sizes; BROWN DEVILS in 5, 10, and 20-watt sizes.



WRITE FOR  
STOCK  
CATALOG



OHMITE MFG. CO

4846 Flournoy St.  
Chicago 44, Ill.

Be Right With...

# OHMITE

RHEOSTATS • RESISTORS • TAP SWITCHES

### UHF Conversion Problems

Many new *uhf* stations are nearing the operations stage, giving rise to many acute problems for service dealers and servicemen. Primarily, they must have or acquire the technical competency to make these conversions; then they must determine how much customers should be charged for such conversion service work. A very comprehensive story on this subject, a report on how Norfolk, Va. servicemen met the challenge, will appear in October "Service Dealer." Don't miss it!

Meanwhile, the happenings at Houston, Tex., where a new *uhf* station is nearing completion, warrant discussion. In Houston, recently, the Appliance Dealers Ass'n held a meeting at which there was present representatives of the Texas Electronics Technicians Ass'n, the BBB and the Retail Merchants Ass'n. It was brought out, from the serviceman's angle, that no pre-planned scale of rate charges for conversions should be decided upon. And rightly so! The general consensus that sets having turret-type front ends could be converted for a charge of \$15 while non-turret-type sets could be converted for \$50 is too low, to our way of thinking. Re-examine your cost figures, fellows!


That no antennas should be installed until a test pattern is actually on the air was decided upon. This is smart, as experience in other areas has shown. That a booklet designed to enlighten the public on set conversions, published by BBB and NAM, is to be offered to dealers and technicians, also meets with our favor... but even that book has some shortcoming in that it works more to the disadvantage of the serviceman, while favoring dealers. This is something that technicians should be forewarned about.

However, one point raised at the Houston meeting deserves special comment and criticism. The Appliance Dealers Ass'n stressed that there was "an ever-increasing number of 'unauthorized' and 'unscrupulous' repairmen operating in the area." It was mentioned that BBB was checking all servicemen listed in the telephone directory and technicians associations. We ask, "Who is qualified to judge as to who is an 'authorized' repairman?"

We advocate association membership for all technicians, even part-time independents and we strongly object to any group setting itself up to adjudge any independent servicemen as being "unauthorized" providing the man has the proper ability and integrity. We're for free enterprise as strongly as we are for unity and association membership. More important—we're for servicemen as such, and want to see them all enjoy higher living standards.

**GOLD-COLORED ANTENNA...  
 FULL-YEAR GUARANTEE AGAINST  
 RUST AND CORROSION...  
 ADVANCED HIGH-GAIN ANTI-VIBRATION  
 DESIGN...**

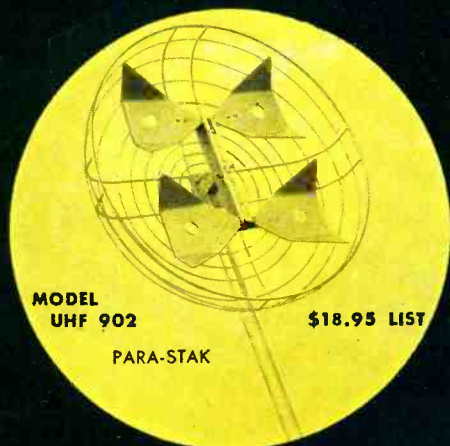These revolutionary features are your identification of the new JFD "Gold Shield" UHF antennas—introducing to the TV antenna field an unprecedented consumer attraction.



MODEL UHF 902 \$18.95 LIST  
 PARA-STAK



MODEL UHF 400 \$14.95 LIST  
 GOLDEN MAXI-COR



MODEL UHF 900 \$14.95 LIST  
 PARA-BOW




MODEL UHF 633 \$7.50 LIST  
 GOLDEN MINI-COR WITH FREE JUMPER



MODEL UHF 411 \$11.75 LIST  
 GOLDEN BRIDGE



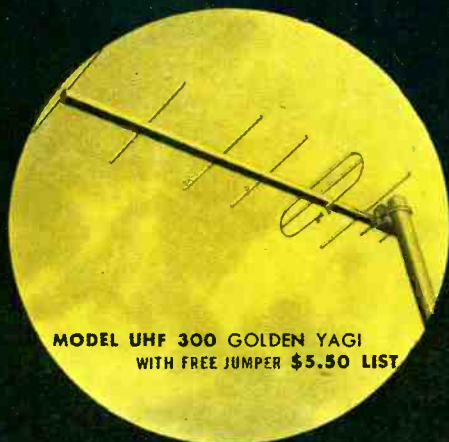MODEL UHF 611 \$6.95 LIST  
 GOLDEN BOW-FLECTOR WITH FREE JUMPER



MODEL UHF 300 GOLDEN YAGI  
 WITH FREE JUMPER \$5.50 LIST



Here's what the JFD "Gold Shield" UHF antennas offer you: An individual antenna for each installation requirement, ranging from the "Golden Para-stak" with 15 DB. gain and 20.5 DB. front-to-back ratio for fringe areas to the "Golden Bow-flector" with 6.5 DB. gain and 10 DB. front-to-back ratio for local signal areas. Add "Bronzidite" protective plating, and you have the antennas for greater UHF profits—without call-backs. See them at your jobber or write for Catalog No. 218.

**JFD MANUFACTURING CO., INC.**  
 BROOKLYN 4, N.Y.

World's largest manufacturer of TV antennas and accessories

**B R O N Z I D I T E**

Burton Browne advertising

**YOU'VE HEARD ABOUT THE** *Telechief*<sup>®</sup>



It's HERE—Sangamo's new premium molded paper tubular capacitor that will outlast and outperform any other tubular . . . built for better TV performance.



**NOW...**

see your jobber  
for this

**SPECIAL  
INTRODUCTORY  
OFFER!**

**Only  
\$24.00**

Slightly higher in Canada

Here's a deal you can't afford to miss. You get a basic balanced inventory of fast-moving "Telechiefs"—assortment based on national popularity—PLUS a heavy gauge steel chest with two extra drawers for small parts—PLUS 100 attractive folders of your choice to promote your business. You get all this for only \$24.00—the dealer net price of the capacitors alone. (They list at \$40.00.)

Get acquainted with the Telechief today—your Jobber has these kits in stock.



You can have 100 of any of these business-building folders without extra cost—a sample of each is enclosed in the kit.

*Those who know...choose Sangamo*



**SANGAMO ELECTRIC COMPANY** MARION ILLINOIS

RADIO-TELEVISION SERVICE DEALER • SEPTEMBER, 1953

## TRADE FLASHES

[from page 8]

showing to television dealers and others interested in building up enthusiasm for new UHF television service.

### NTSC Proposes New Color TV Standards

The National Television System Committee, an industry-wide group of scientists and engineers, announced it will ask the Federal Communications Commission to adopt new improved standards for commercial color television broadcasting. The standards proposed are an improvement over existing television standards in that they permit the broadcasting of color and simultaneously provide black and white sets with a high-quality black and white picture. No changes would be necessary in present sets to permit them to continue to receive a black and white picture from transmissions in color.

### RTMA Changes Name to RETMA

Members of the Radio-Television Manufacturers Association voted to change their name to the Radio-Electronics-Television Manufacturers Association and approved a reorganization plan which will expand the Board of Directors and provide larger representation for new segments of the industry. The changes become effective immediately.

### WNHC-TV Scheduled For Power Increase

The Elm City Broadcasting Corporation, owner of VHF television station WNHC-TV, has received permission from the FCC to increase its visual power output from 18,000 to 316,000 watts and to telecast on Channel 8. In changing from Channel 6 to Channel 8, WNHC-TV will provide stronger power which will eliminate any possible interference from other stations. The increase in telecasting power will enable WNHC-TV to penetrate, in a deeper and broader sense, the areas it now serves. The increase in power will, of course, bring about a further penetration of Southern New England and Eastern New York State. Target date for change is set for some time in November of this year.

### January-June Television Production Record Set

Television set production during the first six months of this year set a new record for the period, the Radio-Electronics-Television Manufacturers Association announced. At the same time, radio production topped the comparable 1952 period by over 1.8 million sets. For the first 26 weeks of this year, RETMA estimated that 3,834,236 TV receivers and 7,266,542 radios were



# TOWN

# Simpson

## MODEL 488 FIELD STRENGTH METER


Saves service time in TV antenna installation—makes service profits longer...Whether installation is fringe in the hills or in the bounce-filled canyons of the city, Model 488 gives you the best location quickly, accurately...Location of maximum signal areas, antenna orientation, comparison of antenna systems, adjustment of boosters and checking antenna and lead-in installations are only a few of the many functions of Model 488.

You're losing profits without one...Dealer's net price including operating instructions and shoulder strap, \$115.00

See your jobber for full information or write Simpson Electric Company, 5200 West Kinzie Street, Chicago 44, Illinois. Phone ESTebrook 9-1121.

In Canada: Bach-Simpson, Ltd., London, Ont.

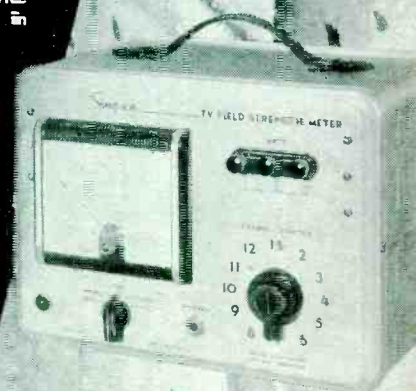Another reason why Simpson is the world's largest manufacturer of test equipment



# Country


manufactured. This compares with output of 2,318,235 television sets and 5,456,035 radio receivers in the same 1952 period. The previous January-June high in television production was set during 1951 when 3,457,519 sets were manufactured. For the month of June, RETMA reported that 524,479 television sets and 1,163,831 radios were produced compared with 361,152 TV receivers and 986,603 radios in the same 1952 month. Radios with FM circuits manufactured during June totaled 49,875 units. In addition, 1,384 television sets with FM facilities were produced.

### RCA Features Hi-Fi Victrola Phonographs At NAMM Convention

Newly-developed high fidelity Victrola phonographs and new-type extended range phonograph records—both products of the RCA Victor Division were featured at the annual convention of the National Association of Music Merchants. The occasion marked the first demonstration to a large group of RCA Victor's new high fidelity Victrola phonographs, developed after

[Continued on page 60]

# Servicemen!

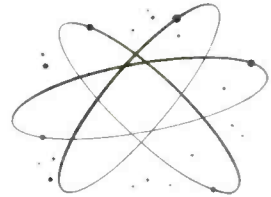

Field Strength Meter


**Model M-8104.** More new features than any other unit at this popular price. Reads signal strength directly from the dial from 10 to 100,000 microvolts. A serviceman's time saver to measure actual TV picture signal strength.

## CHECK THESE PHILCO TEST EQUIPMENT FEATURES

- ✓ New Low Prices
- ✓ New Ruggedness
- ✓ New Circuitry
- ✓ New Versatility
- ✓ New Styling
- ✓ New Accuracy
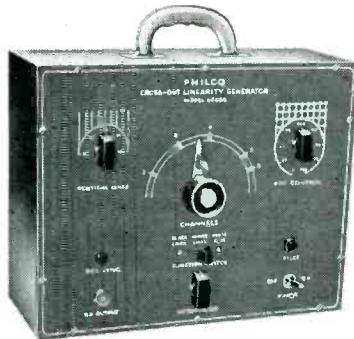
### Cross Dot Linearity Pattern

**Model G-8004.** Philco's new unit for the finest possible linearity adjustments when a station pattern is not available. It provides extreme versatility of performance and design at amazing economy of operation. Light, rugged and portable it's the new leader in test equipment.



## NOW YOURS ON NEW EASY PAYMENT PLAN



VHF to UHF Signal Generator Adapter

**Model G-8000.** The most economical system yet designed to produce UHF signals for TV receiver tests. Through a conversion process using any VHF meter this unit produces from an input VHF signal. UHF signals having the same characteristics as the VHF signal.



Mutual Conductance Tube Checker

**Model 7052.** Tests more different type tubes than any unit on the market, from subminiature to acorn low power transmitting tubes. Shorts on tube elements can be easily determined, employs roll chart instead of cards, for use as a portable or counter top unit.



Dynamic Signal Tracer


**Model 7031.** An extremely versatile instrument... this unit is designed for fast diagnosis of radio trouble by audibly monitoring RF and AF circuits. Can be used to accurately check P.A. systems, microphones and phonograph pick-up circuits, also localizes distortion.





5-inch High Gain Oscilloscope

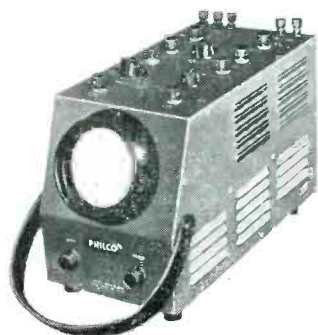**Model S-8202.** This outstanding scope is built to the very highest standards of test instruments. . . It features the highest gain 10 millivolts/inch, and widest frequency range at its popular price. Wide sweep ranges allow extreme flexibility in sweep circuit trouble shooting.



3-inch TV Oscilloscope

**Model S-8200.** The most practical portable unit available for bench or field servicing. Preset horizontal and vertical sweep rates take the guesswork out of trouble shooting, aligning and measuring. Ideal for television because of its high sensitivity and wide response.




Philco Circuit Tester

**Model 8102.** A general purpose voltmeter that challenges comparison. Utilizes 1% resistors throughout to insure maximum accuracy. Tests AC voltage ranges of audio and high impedance AC circuits where a vacuum type voltmeter would normally be required.



Philco Circuit Master

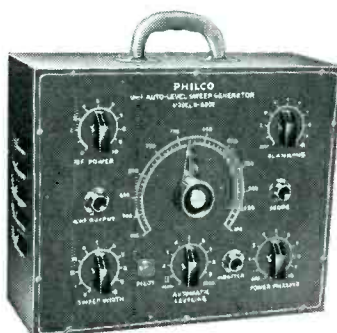**Model 8100.** Designed to the most rigid of engineering specifications, this rugged metal-cased vacuum tube voltmeter is by far the finest in its price class. Provides unmatched accuracy for measuring and aligning where plus and minus indications are required.



UHF Auto-Level Sweep Generator

**Model G-8002.** The most modern, most inexpensive UHF sweep generator on the market. Checks sweep alignment with any test oscilloscope. Its output is controllable and leakage is negligible. . . makes possible over-all trouble shooting and testing of low level units.



Cathode Ray Tube Checker

**Model 7053.** Will accurately test all picture tubes used in home TV receivers. Special cathode-ray tubes are easily checked by using plug-in adapters. Eliminates trouble shooting guesswork. Neon lamp indicates shorts and open elements in the electrodes of the gun.



Visual Alignment Generator

**Model 7008.** Combines in one economical instrument functions that can be approached only in a cumbersome collection of costly devices. No special scope connections are required for the most accurate visual alignment and calibration that is possible to achieve.



Appliance Tester

**Model 5007.** The ultimate in versatility. A one package, all purpose, portable appliance service unit. Permits over-all analysis of refrigerators, ranges, air conditioners and household appliances. With "pick-up" elements to determine temperature and built-in voltmeter.

**MAIL THIS COUPON FOR NEW FREE BOOKLET or see your Philco Distributor**

PHILCO CORPORATION  
Accessory Division  
Allegheny Ave. & "A" St., Phila. 34, Pa.

I am interested in the Philco Test Equipment shown here. Please send me details of your SPECIAL PURCHASE PLAN for obtaining these units.

Please send FREE copy of your new booklet on Philco Test Equipment.

NAME .....  
ADDRESS .....  
CITY ..... STATE .....



If you could advertise nationally, chances are you'd do just what CBS-Hytron

is doing for you. You'd tell the world in



and



Half-page advertisements will appear in LIFE Sept. 28, POST Oct. 3, LIFE Oct. 19, POST Oct. 31, LIFE Nov. 16, and POST Nov. 28. Reaching over 28,583,290 readers!

that you promise quality TV and Radio service, parts, and tubes . . . and

at fair charges. And that's just what CBS-Hytron is doing for you with

advertisements like these.



You'd identify your service repair

These are just some of your *Certified Quality Service* advertisements. They sell you . . . and without a lot of sell for CBS-Hytron, although CBS-Hytron gladly pays the bill. Why? Because as we build *public confidence* in *Certified Quality Service*, we build greater faith *in you* and more business *for you* . . . our customers.

shop as the *one* people are reading about in the magazines. You'd use this

*Certified* QUALITY SERVICE decalcomania on your door.

This *Certified Quality Service* decalcomania identifies you as a dealer with hard-earned technical knowledge and the latest in equipment. A dealer to whom the public can go for *Certified Quality Service*. It helps you cash in on your big *Certified Quality Service* plan.




You'd use

this *Certified* QUALITY SERVICE window streamer.



And

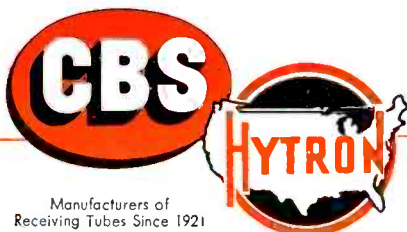Let folks know you *Certify* the quality of your service, parts, and tubes . . . and at fair charges. Use all the *Certified Quality Service* sales material available to you. Be sure this window streamer is *up* during your consistent advertising campaign this Fall.



Manufacturers of Receiving Tubes Since 1921

CBS-HYTRON, Danvers, Massachusetts

A DIVISION OF COLUMBIA BROADCASTING SYSTEM, INC.

A member of the CBS family . . . CBS Radio • CBS Television • Columbia Records, Inc. • CBS Laboratories • CBS-Columbia, Inc. • and CBS-Hytron

above all *you'd* use these *Certified* **QUALITY SERVICE** tags.

This plan goes *all* the way to do the job. When *you* use these *Certified* Quality Service tags you're putting right into your customer's hands convincing *proof* . . . Proof that *Certified* Quality Service means *more* for your customer's money.



They tell *your*

customer he is getting more for his money when he calls *your* service repair

shop . . . because *you* *Certify* the quality of service, parts, and tubes . . . and

at fair charges. Yes, by using all this material, and more to come, *you*

cash in on *your* big *Certified* **QUALITY SERVICE** advertising campaign.

Get *your* kit.



It contains all the material

Make the most of *your* big *Certified* Quality Service advertising campaign. Be sure you have *all the facts* . . . and *all* the material you need. Get this sales promotion kit, today!

*you* need to identify *you* as a *Certified* **QUALITY SERVICE** dealer. Ask your

CBS-Hytron distributor for *special deal*. Or use coupon to order direct.

**SEE YOUR  
CBS-HYTRON  
DISTRIBUTOR  
... OR MAIL  
COUPON  
TODAY!**

**CBS-HYTRON**, Danvers, Mass.

Please rush me the *Certified* Quality Service promotion kit, containing:

1. 18- by 28-inch LIFE and POST easel display . . .
2. New *Certified* Quality Service decal . . .
3. 8- by 23-inch window streamer . . .
4. AND 250 *Certified* Quality Service tags imprinted with MY name and address.

HERE IS MY 3-LINE IMPRINT:


Name \_\_\_\_\_  
(please print)

Street \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_

I enclose \$2.00 to cover the cost of imprinting.

Signed: \_\_\_\_\_

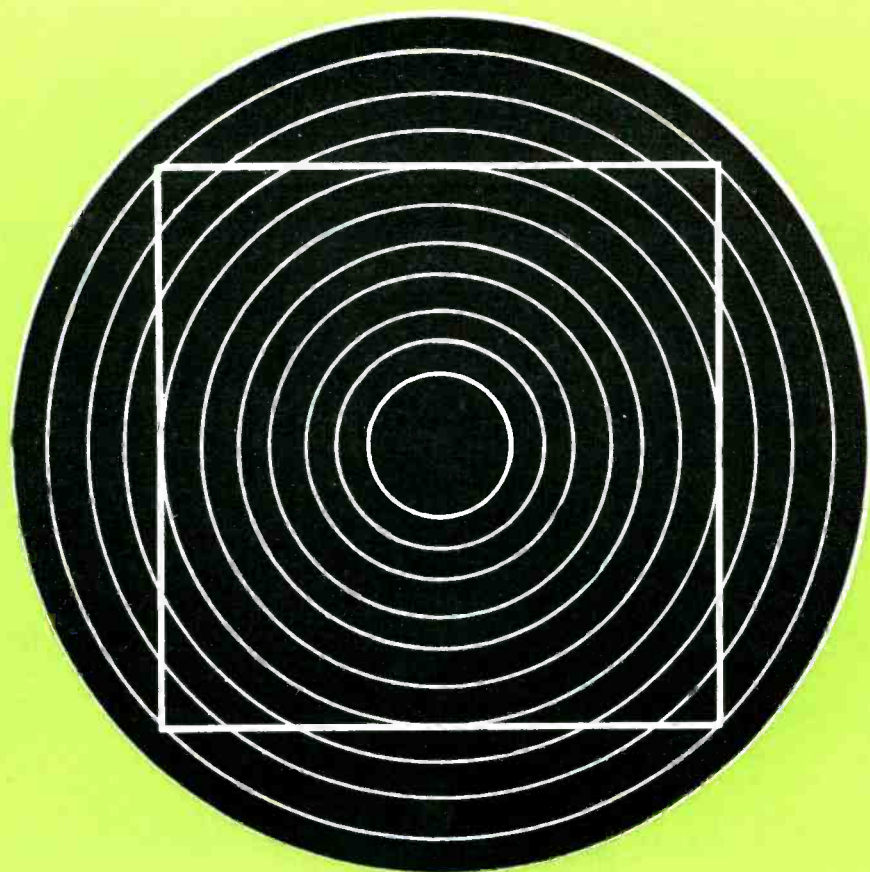

*things are NOT as they seem . . .*

This is a perfect square within the circle  
—it is an optical illusion that the sides bend.



Things are not as they seem . . .  
These two fuses look alike . . .  
*But they are not.*



This fuse may burn out anywhere along the length of the filament even in the cap—this blown fuse is impossible to detect visually.



This Littelfuse has a controlled blowing point—the filament is plated throughout its length except in the very center—the fuse will always blow here. A blown Littelfuse can be detected immediately—a Littelfuse feature.


*Littelfuse holds more design patents on fuses than all other manufacturers combined.*

# LITTELFUSE

DES PLAINES, ILLINOIS

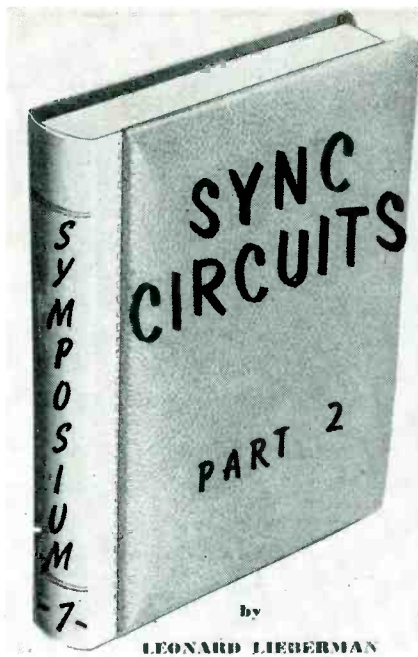**This concluding installment on Sync Circuits gives a circuit analysis of various types used in commercial**

**Erratum:** The first installment of "Sync Circuits" in the August, 1953 issue should be corrected as follows: Text matter (not illustrations) reading Figs. 5, 6, 7, and 8 should read Figs. 6, 7, 8, and 9 respectively. Page 20, 5th par., last line—Fig. 5b should read Fig. 5. Page 21, 5th par., 2nd line—delete Fig. 9.



**television receivers. An overall picture of the different types of sync circuits one may expect to service is thereby obtained.**

#### Silvertone Model 1176-21

The Silvertone Model #1176-21 (Fig. 11) is an example of a cathode driven stage followed by a direct coupled stage. The composite video signal is fed to half of a 6SN7 through a double time constant network. It consists of a 270K resistor paralleled by a 270  $\mu$ f condenser which is in series with a .01  $\mu$ f condenser and a 2 meg resistor to ground. The cathode is grounded and the 2 meg grid leak resistor develops a high bias. The plate voltage is kept low by means of a 68K resistor.

The signal is fed to the grid sync phase positive. As a result of the high bias, most of the video portion of the signal falls in the cut-off region. Due to the low plate voltage and resulting plate saturation, there is some compression of the top of the sync pulse. In this manner, noise on the sync pulse is compressed.

The signal is then fed through a .05  $\mu$ f condenser to the cathode of the following stage, half of a 12AU7. This stage has the cathode at +125 volts, the grid is at +120 volts and the plate is at +145 volts. As a result of these voltage relationships, this stage cuts off part of the sync signal to flatten the top and also compresses the remaining video by plate saturation. The grid of the last stage is direct coupled to the plate of V2 in order to retain the original shape of the pulse. The output of this stage is fed to the horizontal and vertical sweep circuits.

#### Sparton Model 5212

The Sparton Model #5212 (Fig. 12)

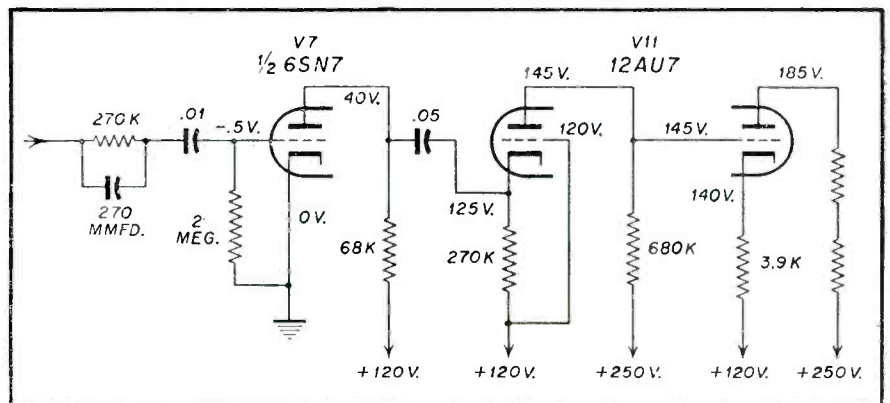


Fig. 11—Silvertone Model 1176-21. Note the cathode driven stage followed by a direct copuled stage. This method eliminates noise triggering of sweep oscillators.

operates in a similar manner, with the following variations:

1. A pentode (6AU6) is used instead of the two triode sections for both clipping the top of the sync pulse and stripping the video information from the sync.
2. The grids of both stages are returned to positive points to present less of a charging impedance to noise pulses. The composite signal is fed sync phase positive to the grid of the 6AU6 through a double time constant circuit which discriminates against noise pulses.

The grid return resistor (2.2 meg) is returned to a tap between two 22K cathode resistors (See Fig 12, point A). Approximately 9 volts of grid to cathode bias is developed across the

second resistor. The plate and screen are at 100 volts resulting in quick plate saturation.

The grid of the second stage is coupled to the plate of the first stage by means of a .1  $\mu$ f condenser. The grid return of the second stage goes back to +110 volts through a 2.2 meg resistor. Grid current establishes a voltage in the order of 9 volts positive at this grid. Cathode current develops 12 volts at the cathode resulting in a .3 volts grid to cathode bias. The plate is at 70 volts positive. The horizontal phase detector is fed from both cathode and plate resistors and the vertical is taken off the top of the plate load.

#### RCA KCS 66C

The sync circuit of the RCA Model #KCS 66C (Fig. 13) uses 2½ tubes. It

has separate horizontal and sync pulse systems, has a noise limiting circuit and is also used to set the bias of the *agc* circuit. Therefore, it fulfills the initial requirements of increased efficiency and circuit reduction.

First, let us examine the noise suppression circuit. By means of this circuit, noise pulses whose amplitude exceeds the sync pulse are eliminated. This circuit works in the following manner:

One input to the vertical sync stripper is fed from the video amplifier in sync phase positive. The screen of the fourth video *if* amplifier is also connected to this grid. The video *if* amplifier is so biased that the normal sync pulses will not drive the tube to grid current. Any pulses of greater amplitude than the sync pulse will cause grid current. The screen is not fully by-passed, and this pulse will cause the screen voltage to drop. This, in turn, causes a negative going pulse to appear at the vertical separator grid at the same time as the pulse which was passed through the video amplifier. In this manner, a negative noise pulse and the same pulse phased positively appear simultaneously at the grid and cancel each other out.

The composite signal is taken off the video amplifier and is fed to 2 tubes both separated by a 56K isolating resistor. The upper tubes in (Fig. 13) are the vertical sync string, the lower set is the horizontal sync string,

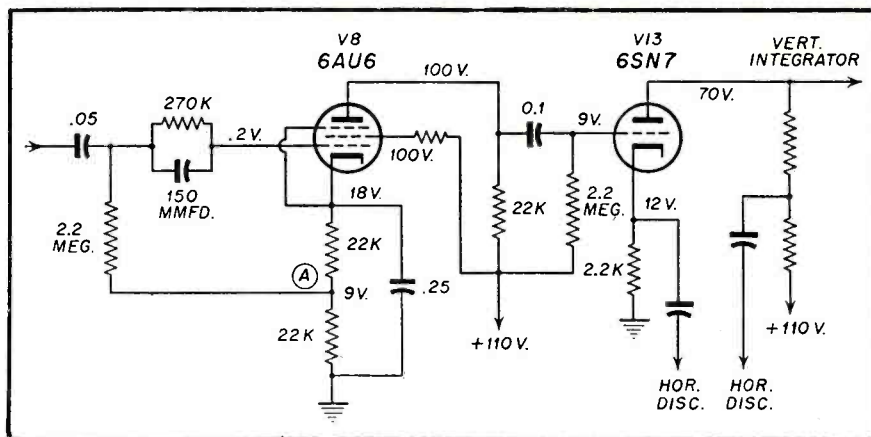


Fig. 12—Sparton Model 5212

The cathode of the vertical sync separator is connected by a 1.8 resistor to a tap on a bleeder from ground to +150 volts. The voltage at the cathode is approximately 95 volts. The grid is at +75 volts. The plate is connected to the boost voltage through a 120K and a 1 meg resistor and is nominally approximately 400 volts.

This stage, because of the heavy grid to cathode bias, tends to cut off all the video signal. The second stage, which has a very low plate voltage (+12 volts), compresses the video to the extent that only the vertical pulses are fed to the vertical integrator. Although, all the RC time constants in this circuit tend to discriminate against the horizontal pulse, the

integrator network is featured by a differentiator circuit which shunts any higher frequency (horizontal) pulses to ground.

The horizontal circuit, in addition to its function of passing, amplifying, and shaping the horizontal sync pulses, also is the take-off point for the keyed *agc* system. In addition, it serves to set the *agc* bias level. The first sync stage is heavily biased (grid to cathode) by the insertion of a 150K cathode resistor. This brings the cathode voltage to +85 volts. The grid is at +75 volts. This results in the video portion of the composite signal being in the cut-off region. The second stage voltage, cuts off and clips the pulse fed to it. The third stage is also grid leak biased and is a cathode follower which feeds the signal to the horizontal *afc* tube.

The biased level for the *agc* is set in the following manner: The potentiometer (*agc* control) determines the bias level of the grid of the first horizontal sync stripper. The positive *dc* level of the *agc* tube grid is taken off the junction of the 150K and .01  $\mu$ f condenser at the stripper tube's cathode. Since the level of tube conduction is determined by the grid to cathode voltage relationship, setting the grid level thus determines the voltage at the cathode. Once this level is set, the *agc* tube operates on the peaks of the sync pulse which is then led to the grid of the *agc* tube.

#### Philco Model 52T2110

The Philco Model #52T2110 (Fig. 14) is one of the most interesting examples of sync circuitry. The principle of operation depends on an action opposite to the usual diode action. Usually the portion of the signal appearing across the diode load resistor during conduction is the one used. In this case, it is the signal appearing across the load resistor during the

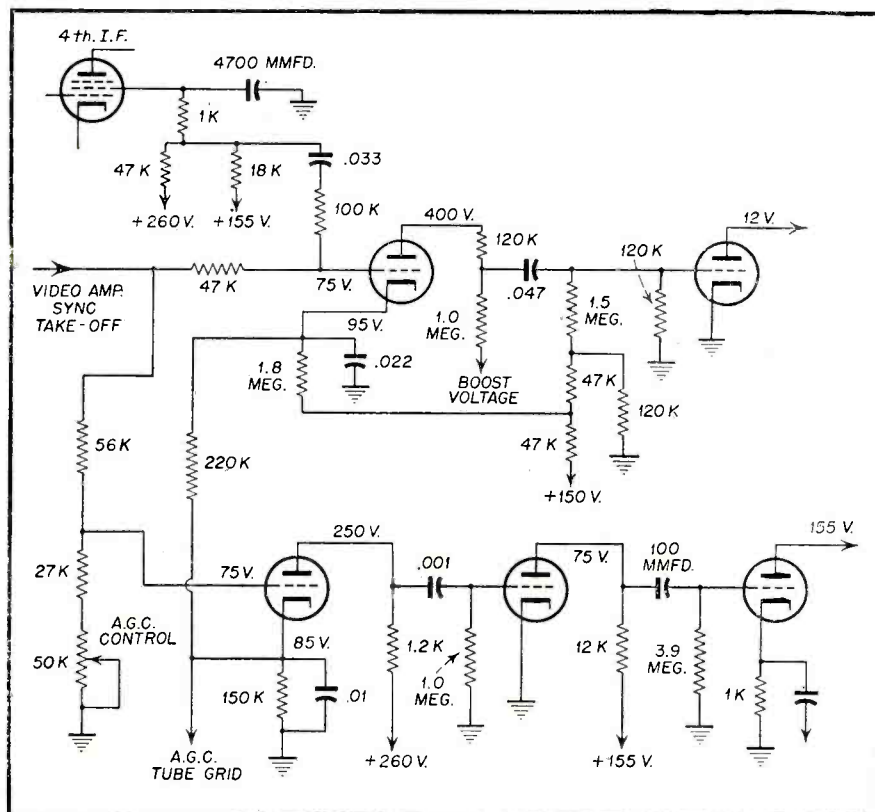


Fig. 13—RCA Model KCS66C

time that the tube is *not* conducting which is utilized.

This circuit works in the following manner: The composite signal is taken off the plate of the video amplifier sync phase positive. It is fed to half of a 12AU7. The cathodes of both halves of the tube have a common cathode resistor. The second section of the 12AU7 is diode connected. The plate resistor of the second section (180K) goes to + 240 volts. It is large enough so that any plate current sends the plate voltage to approximately cathode potential. The plate also goes to ground through a 39K resistor.

The diode will only conduct during the negative (or video) portion of the composite signal. This conduction through the 39K resistor causes the .015  $\mu$ l coupling condenser to discharge and sets up a heavy bias on the following grid. When the upper or sync portion of the signal appears on the common cathode resistor, the diode stops conducting. The 39K resistor acts as the charging resistor for the coupling condenser. This brings the grid of the following tube above cut-off and into conduction. The RC time of the diode load is such that recovery time is equal to approximately sync pulse time.

The output of the final stage is an amplified pulse equal to sync pulse. The feedback resistors from the plate of the final tube and the grid of the first tube sharpens and shapes the output pulses. The 270K resistor and 180  $\mu$ l condenser in the grid of the

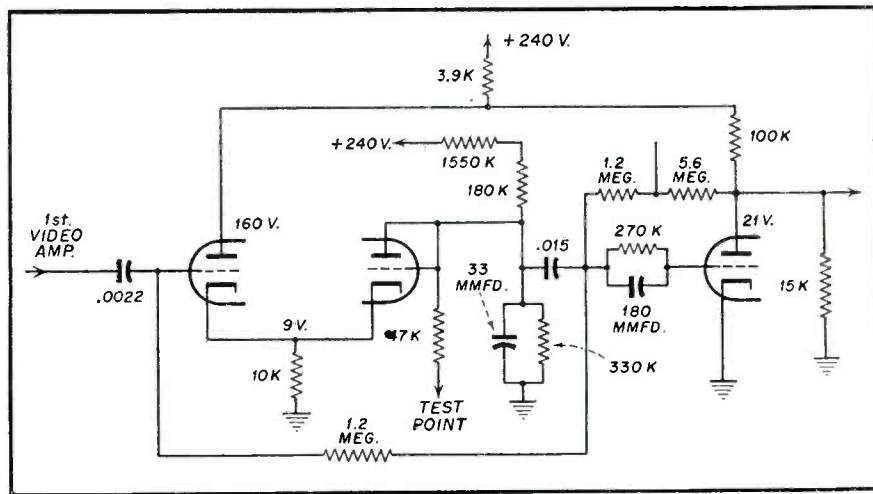


Fig. 14—Philco Model 52T2110

final stage presents a high impedance to noise pulses.

By constantly testing new models as they come into the shop, observing the voltage relationships with a meter and the sync signal by means of a scope, almost all sync circuits can be analysed. It might be advisable, when a receiver with a new and complex circuit comes into the shop and there are no voltage or scope measurements on the schematic, to note these items down so that the operation of the circuit can be studied and troubles in the sync located much more quickly.

#### Capehart CT52 & CT57— Heptode Sync Stripper

From the looks of the sets recently reaching the market, more and more of the manufacturers are hopping on

the heptode sync stripper bandwagon. The Capehart CT52 (Fig. 15) is another in the parade. There are, some noteworthy features in this receiver.

In order to keep from loading the video amplifier output, and at the same time obtain better control of the two signals, the sync stripper signal is taken off the video detector. To obtain phase reversal and greater amplitude needed for the second control grid of V14 the sync stripper, the signal from the detector is fed to a 6BA6 sync amplifier, V13.

The cathode of V13 is grounded. The grid leak resistor R52 (47K) with a signal across it causes the tube to cut off on the sync pulses. The plate is kept at approximately 25 volts due to the *dc* voltage across R54 and R55. This results in a high plate voltage signal during cut-off. The output is a positive going sync pulse with accompanying video information. In addition to driving the 6BE6 sync stripper this signal also drives a keyed *agc* tube.

The 6BE6 first control grid is driven from the video detector with a 2-volt peak to peak negative sync signal. This will hold the tube close to cut-off except when the positive signal from the sync amplifier appears at the second control grid at an amplitude corresponding only to the sync pulses. The feature of this circuit is the presence of R57 (4.7 meg) which goes back to 130 volts B+. The purpose of this resistor is to buck out the negative voltage which would appear across R52 the 6BA6 grid resistor as a result of heavy noise pulses which would bias V14 to cut-off. This bucking voltage is applied in weak signal areas by means of the switch S. This action does not occur during an ordinary sync pulse because the network R56, C55 does not discriminate against sharp noise pulses.

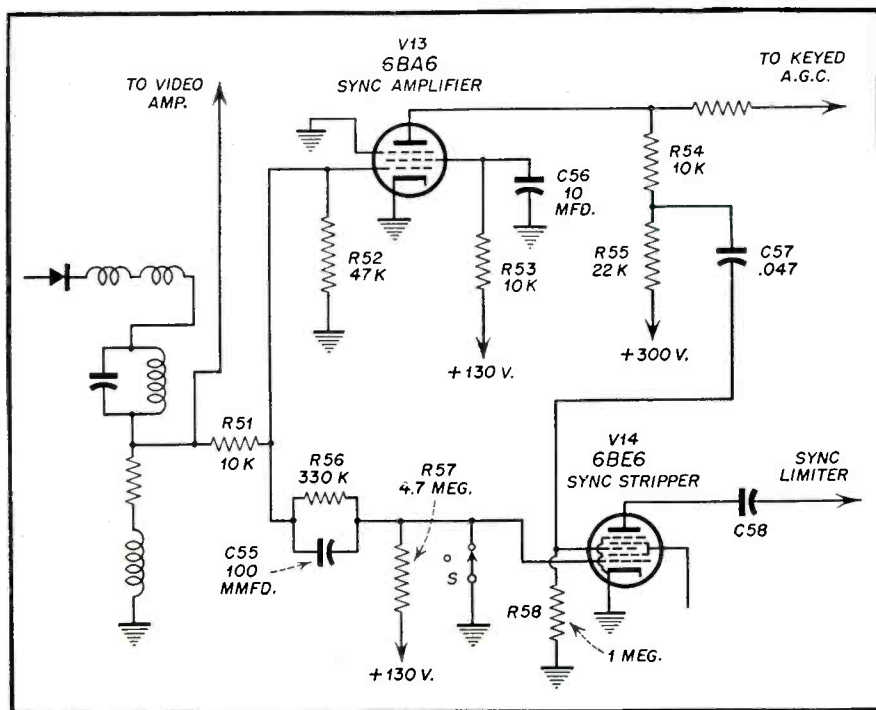


Fig. 15—Partial schematic Capehart CT52

# WE'LL TELL THE WORLD!

ONLY *Regency*  
HAS **5** WAY  
CONVERSION!

*Saturday Review*  
**LIFE** *House Beautiful* Har  
**House & Garden**

*Saturday Review*  
**THE Atlantic**  
**Harper's**  
*use & Garden*

**LIFE**  
*Saturday Review* **Atlantic**  
**House Beautiful**

**Harper's House & Garden**

**LIFE**

*Saturday Review*


**THE Atlantic**

*Saturday Review*

**LIFE**

**LIFE**

*Review*

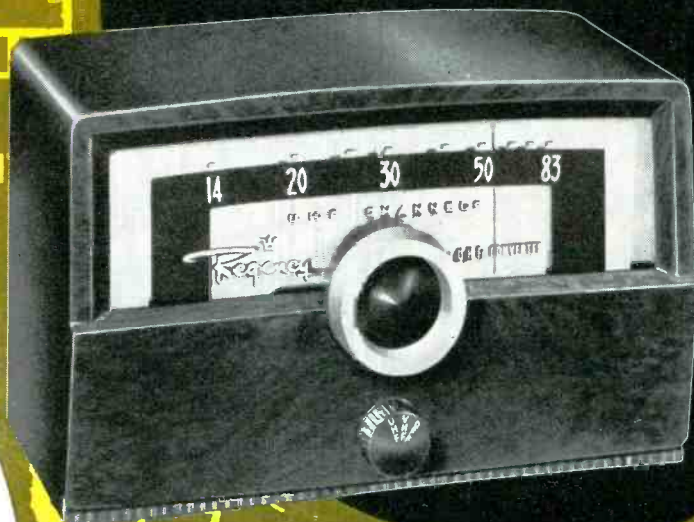

We'll tell them not to take chances with 2-way Conversion . . . that the Regency Quintuplet Converter, unlike *all* others, is designed to utilize any of 5 VHF channels in converting to UHF; other converters work only on 2 channels. Insure your customers against image interference, obsolescence! Sell them **REGENCY'S** Quintuplet Converter! . . . and at \$49.95 list, there's greater profit for you!

Yes you'd better be ready for a big turnover this fall, because **REGENCY'S** promotional program is directing more traffic than ever *your way!*

*Atlantic*

*Harper's*

**LIFE**  
*Saturday Review*

**THE Atlantic**

*Saturday Review*

**Harper's**  
**LIFE**


**House**

**LIFE**  
*Saturday Review*

Makers of VHF Boosters, FM Boosters, UHF Converters, Professional High Fidelity Equipment and Remote Control for Selectors  
**Regency**  
DIVISION OF I. D. E. A. INC.



# FLYBACK TRANSFORMER TESTER

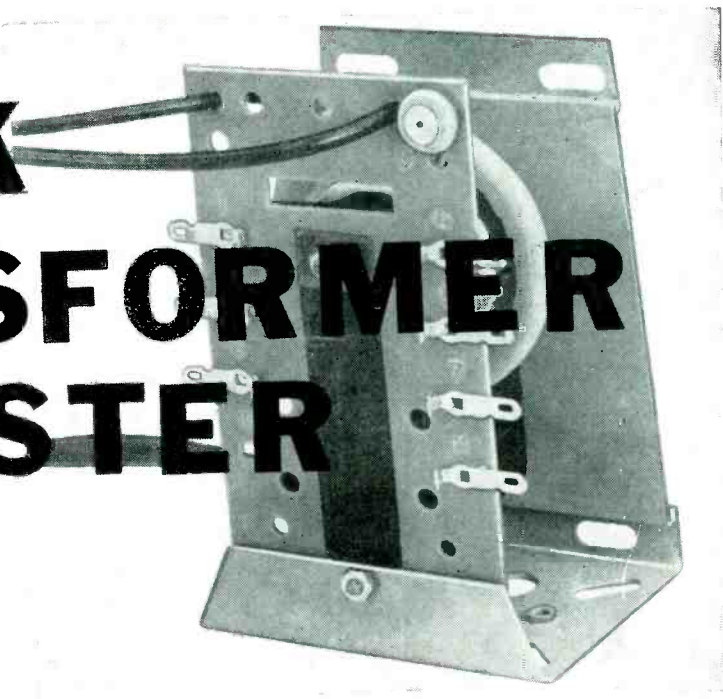

by **HARRY CASEY**

(Chief Engineer, Kirby Products Corp.)

AS any television serviceman will agree, the horizontal output section of a television receiver contains the circuits most likely to become defective much sooner and most often. Due to high peaks in operating voltages and other factors that subject circuit components and tubes to extreme operating conditions, marginal parts and tubes will break down faster.

Troubleshooting the horizontal sweep section of a TV receiver is fairly straightforward up to the flyback transformer. Some difficulty is presented in the horizontal sweep systems that employ regenerative types of B plus circuits. See Fig. 1. In these circuits the boosted B plus from the damper rectifier tube is used as B supply for all the tubes in the horizontal sweep system. This type of circuit can be successfully worked on in case of trouble by either feeding an external B plus to the horizontal oscillator plate load which causes it to oscillate if it is normal, or by removing the horizontal output tube from its socket. This decreases the B current drain enough to raise the B supply to a voltage high enough to permit the horizontal oscillator to operate.

If the trouble is not in the horizontal oscillator circuit, and after the horizontal output tube has been replaced and the circuit voltages checked, then the serviceman is generally up against a stone wall. From this point on he usually starts to check the flyback

**This article describes an effective piece of apparatus which simplifies horizontal output transformer testing.**

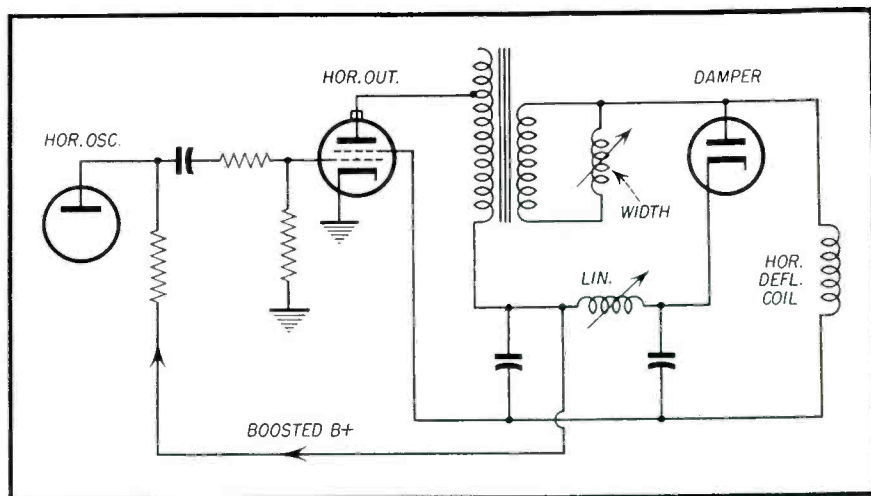


Fig. 1—Simplified schematic illustrating how the boost voltage from the horizontal output transformer feeds the plate circuit of the horizontal oscillator.

transformer for continuity and even if it appears satisfactory he removes it anyway and replaces it with one he thinks is good. This process is not only long drawn out, but does not always supply the answer. The author has had some very embarrassing experiences where a supposedly good replacement flyback transformer proved to be defective.

Recently a novel test instrument was developed which provides the answer to fast and sure horizontal output circuit troubleshooting. This in-

strument, called the Model 98, Flyback Transformer Tester, designed and produced by the Kirby Products Corporation of Philadelphia and New York, is a simple inexpensive test unit for checking the efficiency of flyback transformers. See Fig. 2. This unit is so sensitive that it will actually detect the presence of one or two *shorted turns* in a flyback transformer. *Shorted turns* are the major reason for TV servicemen's headaches in flyback transformers, for they cause a large percentage of troubles and will not



Fig. 2—Flyback transformer tester.

show up with ordinary continuity tests made with an ohmmeter. For example see Fig. 3. Notice that any of the flyback transformer windings has a relatively low *dc* resistance. If just one or two of the turns were shorted as is shown in the figure the overall *dc* resistance would not decrease more than the barest percentage; a difference no ohmmeter could detect. However, the one or two shorted turns while not affecting the *dc* resistance to any degree have a considerable effect on the ac operating efficiency. They act the same as putting

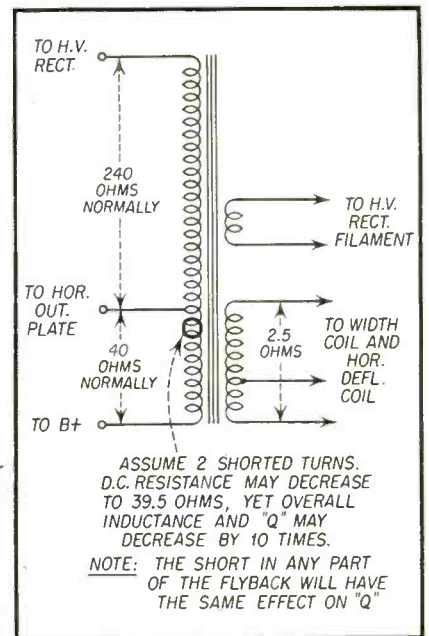


Fig. 3—Flyback resistance values.

a closed loop into a magnetic field. The energy in the field is shortcircuited, and the effective inductive reactance which determines the efficiency of the transformer is lowered tremendously. As a matter of fact, it is lowered to the point where the energy absorbed by the closed loop or shorted turn is so great that the horizontal output circuit fails to operate. This means a greatly decreased horizontal sweep width, a great reduction of subsequent high voltage or both.

The Model 98 contains very novel but simple circuitry. See Fig 4. A 6K6

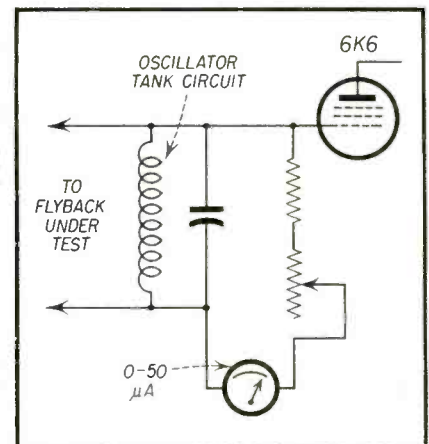


Fig. 4—Simplified schematic of flyback transformer tester.

tube is used as a special type of oscillator at a predetermined frequency and repetition rate.

A sensitive zero to fifty microampere meter is used as the indicating device. It is connected in the circuit to indi-

[Continued on page 63]

# SERVICEMEN NOW...you can have your own needle inspection Kit...FREE!

Here's a chance to have the new 50 Power large field and microscope for nothing...a scope with a wide angle lens which makes it easy to examine needles—no difficulty in bringing the needle into view quickly to tell if it is worn! But that's not all! You also receive a plastic carrying case; a new

amazing ELECTRO-WIPE cloth; a professional tool for quickly replacing needles. All of this is free if you accept a real bargain, DUOTONE's offer of \$25.00 worth of needles for only \$12.50. Place your order today direct with your jobber!

- replacement needles — \$25.00
  - one microscope — 5.00
  - one electro-wipe cloth — 1.50
  - one plastic kit — .50
  - one professional tool — .50
- ~~\$37.50~~


**ONLY \$12.50**

**DUOTONE**  
KEYPORT, NEW JERSEY

Canadian Representative: CHARLES W. POINTON, TORONTO, CANADA  
Export Division: AD. AURIFEMA, INC., NEW YORK CITY, N. Y.

Terrific wide angle 50 power scope makes it easy to examine needles without even removing them from the cartridge!


# You can see the difference...

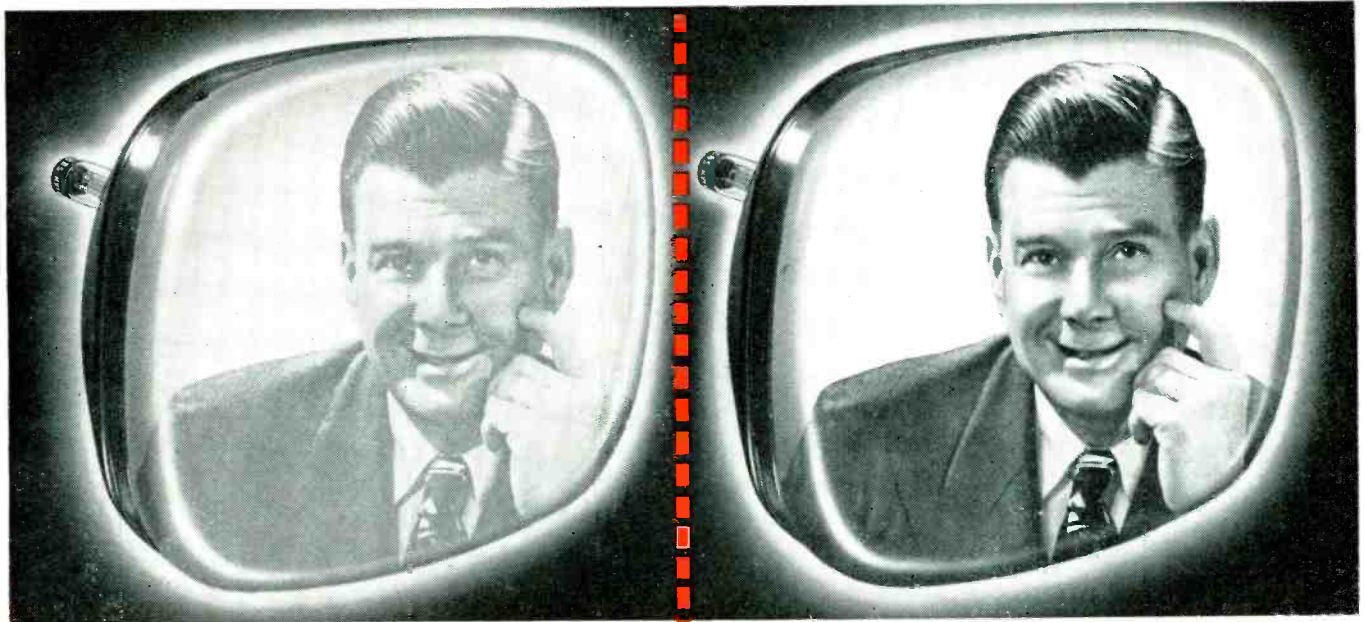

ARTHUR GODFREY, FAMOUS CBS-TELEVISION STAR

## NOW CBS-HYTRON **MIRROR-BACK** BIG-SCREEN TUBES 27EP4 . . . 24TP4 GIVE YOU BRIGHTER PICTURES !

### HOW MIRROR-BACK TUBES ARE MADE

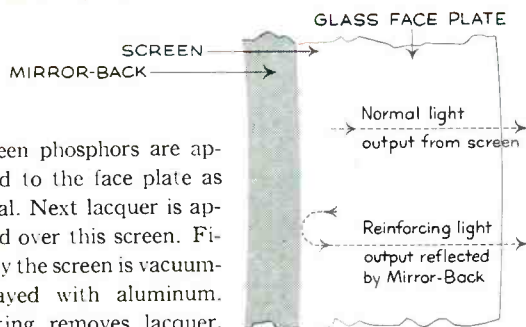

MAGNIFIED CROSS-SECTION

Screen phosphors are applied to the face plate as usual. Next lacquer is applied over this screen. Finally the screen is vacuum-sprayed with aluminum. Baking removes lacquer, leaving the brilliant Mirror-Back coating. Mirror-Back reflects light that would otherwise be lost to the rear of the screen. Boosts light output. Brightens picture.

#### ADVANTAGES OF CBS-HYTRON MIRROR-BACK TUBES

1. Stepped-up light output.
2. Brighter picture.
3. Greater contrast.
4. Reduced strain on component parts.
5. Full effective screen potential maintained by metallic contact between anode and screen.
6. Longer life . . . drain on cathode materially reduced.

Leading TV set makers demand maximum brightness from their large-screen sets — without strain on component parts. For them, CBS-Hytron introduced its Mirror-Back 27EP4 and 24TP4 (both spherical, electro-magnetic types). Mirror-like effect of their aluminum-backed screens reinforces light output. Gives brighter, sharper pictures.

You, too, will want CBS-Hytron Mirror-Back big-screen tubes for replacement. In 27- and 24-inch sizes, they are a must. Take a tip from leading TV set makers. Try the CBS-Hytron 27EP4 and 24TP4. See the difference for yourself. Let your customer see it too. Order performance-tested Mirror-Back tubes from your CBS-Hytron distributor.

**New . . . FREE CBS-HYTRON TRANSISTOR MANUAL** Just what you have been looking for: A down-to-earth, complete, 8-page introduction to transistors. In three parts: 1. Theory. 2. Data. 3. Application. CBS-Hytron Transistor Manual is profusely illustrated. Contains nine basic transistor applications. Explains by vacuum-tube analogy both point-contact and junction transistor operation . . . conduction by "holes" . . . P-N-P and N-P-N transistors . . . advantages and limitations of transistors.

An easy-to-take introduction to how transistors work . . . their characteristics . . . and how to apply them, this CBS-Hytron Transistor Manual is also free. Get it from your CBS-Hytron distributor. Or write direct today.



Manufacturers of Receiving Tubes Since 1921


**CBS-HYTRON** Main Office: Danvers, Mass.

A Division of Columbia Broadcasting System, Inc.

RECEIVING . . . TRANSMITTING . . . SPECIAL-PURPOSE AND TV PICTURE TUBES • GERMANIUM DIODES AND TRANSISTORS

RADIO-TELEVISION SERVICE DEALER • SEPTEMBER, 1953

# 3 SPEED CHANGER CONVERSION

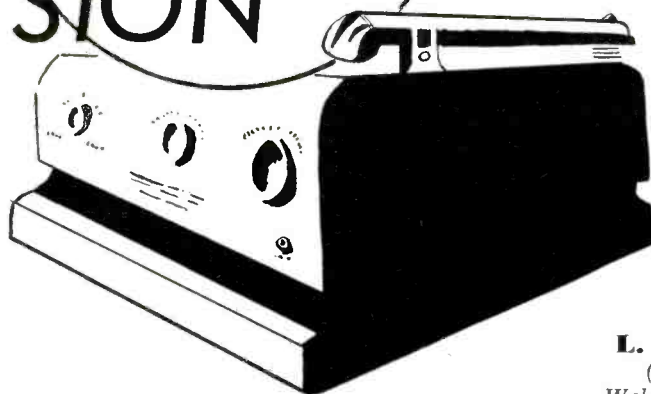

Valuable hints and procedures on the conversion of valuable phono cabinets to accommodate modern 3-speed changers.

by  
**L. C. BURDICK**  
(Sales Engineer,  
Webster-Chicago Corp.)

THE increasing demand of a growing "music conscious" public for complete and faithful reproduction of all types of records has made the record changer replacement business a profitable venture. Old consoles with single and dual speed changers represent a sufficient investment on the part of the owners to seek modernization with a good three speed diskchanger capable of playing all sizes of records. A follow up on a sale with an installation job makes the venture even more attractive. Any service organization can easily handle such an installation.

### Basic Requirements

While variations of cabinet and circuit design exist, it is not difficult to adapt an old console to accept the modern 3-speed record changer. There are only two basic considerations in replacing the old unit and installing the new.

1. Space Requirements.
2. Electrical Requirements.


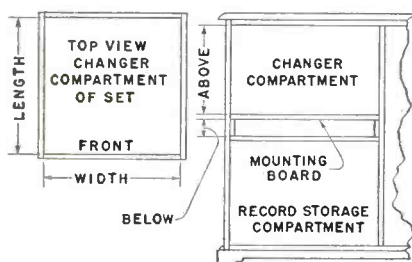


Fig. 1—Interior specifications of cabinet that should be carefully measured.

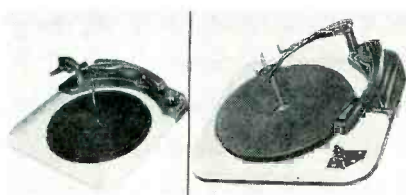

Diskchanger Chassis

MODEL	MIN SPACE REQUIRED				PICK UP	CORD LENGTHS	MOUNTING BOARD NO
	A	B	C	D			
121-1	14½"	13½"	2½"	5¼"	Crystal	3'	1909
121-270	14½"	13½"	2½"	5¼"	G.E. Triple Play	3'	1909
126-1 HF	15"	15"	2½"	6¼"	Crystal	3'	1910
126-27 HF	15"	15"	2½"	6¼"	Plug-in Heads for Magnetic Cartridge	3'	1910

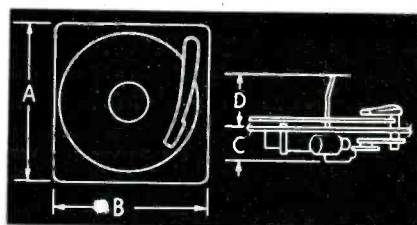


Fig. 2—Complete specifications of Webcor diskchangers. Measurements relating to space requirements are shown in center.

These considerations will determine the selection of the correct changer.

Webcor diskchangers are made with two different size mainplates (chassis) that will match the physical dimensions of virtually any type cabinet. Although the dimensions of the original changer plate are usually a good indication of the required size of the replacement

unit, it is best to accurately measure the record changer compartment. These measurements take into consideration the length and width of the interior and, in addition, the space available above and below the mounting board or platform. See Fig. 1. Shown in Fig. 2 are complete specifications of Webster-Chicago diskchangers. The minimum space requirements include the 12" record overlap and top parts overhang during manual or automatic operation.

The large majority of changers in older phono-radio combinations are equipped with crystal type cartridges. A modern 3-speed unit, using a similar cartridge, is electrically interchangeable with this type older changer. In some instances the customer may express a desire for the variable reluctance or magnetic cartridge. The installation will then require a pre-amplifier to compensate for low output and other characteris-

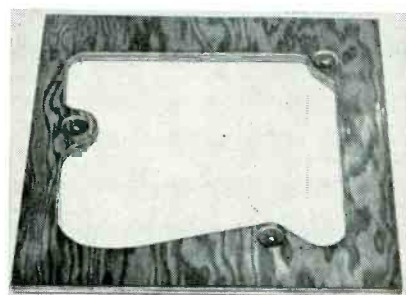


Fig. 3—Mounting board is provided to make installation easier.

here is the  
new →

**VEE-D-X**


# mighty match

FOR CONNECTING SEPARATE  
UHF AND VHF ANTENNAS  
TO A SINGLE TRANSMISSION LINE.

With entirely new patented\* circuits and new construction, the MM-40 and its companion (MM-40-A) are by far the finest, most efficient isolation filters for combining separate UHF and VHF antennas for single line installation. The MM-40 in new yellow weather-resistant case is quickly and easily mounted on antenna mast. The MM-40-A is used at converter or TV set that has separate UHF and VHF terminals.

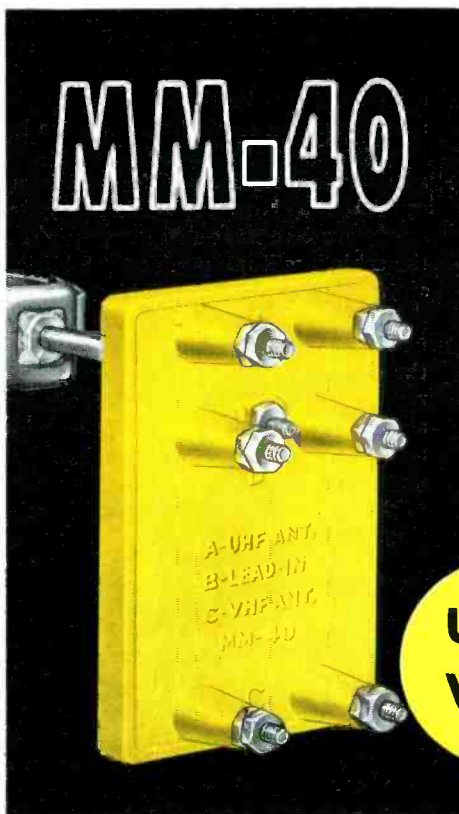
## FACTS ABOUT THE NEW MIGHTY MATCH

- New improved patented\* printed circuits
  - Amazingly *LOW* insertion loss
  - Weather-resistant case
  - New larger terminals for easy line connections
  - No critical lengths of connecting lines
  - Loss preventative stand off.
- VEE-D-X was first to introduce the isolation filter (Mighty Match). Every Mighty Match is fully protected under\* A.A.K. Pats. 2,422,458; 2,282,292; 2,611,086. The new models greatly minimize insertion loss, and are the result of constant research and engineering. Accept no substitute—insist on Mighty Match.





**UHF  
VHF**

...and its companion

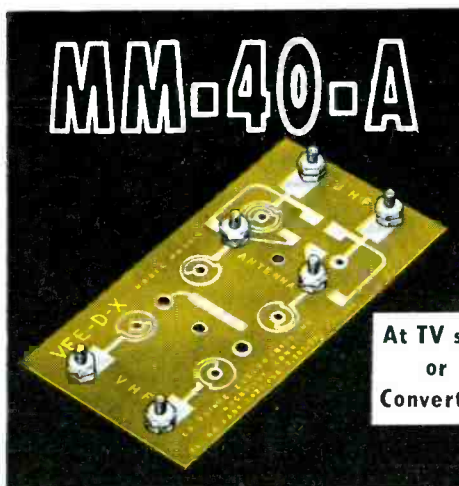

At TV set  
or  
Converter

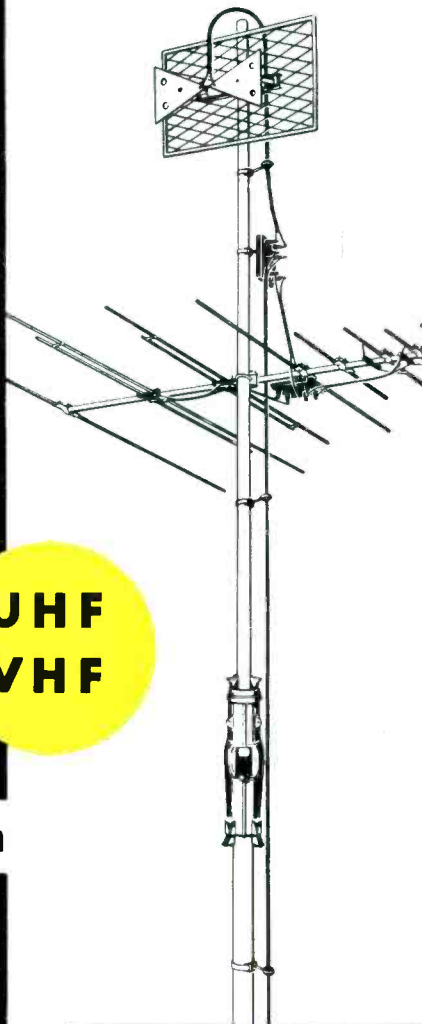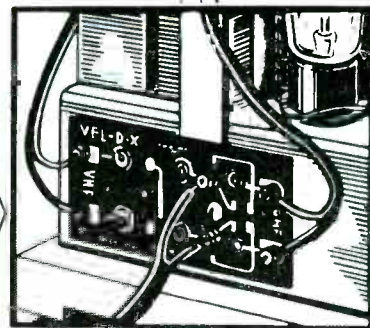


SEVEN MODEL VARIATIONS FIT EVERY TYPE OF INSTALLATION.

also the new

**VHF**

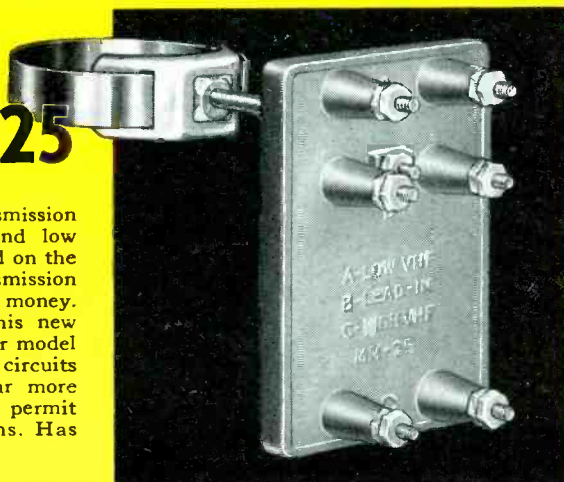**MM-25**

Permits the use of single transmission line between separate high and low channel VHF antennas mounted on the same mast. Saves 300 ohm transmission line. Saves installation time and money. Saves extra accessory cost. This new model MM-25 replaces the older model MM-20. With new improved circuits and case construction, it is far more efficient. New raised terminals permit easier, faster line connections. Has weather-resistant green case.



**NEW!**  
Printed Circuits  
and amazingly low insertion  
loss make Mighty Match  
by far the finest, most  
efficient crossover  
network.



**LaPointe** ELECTRONICS INC.  
ROCKVILLE, CONNECTICUT

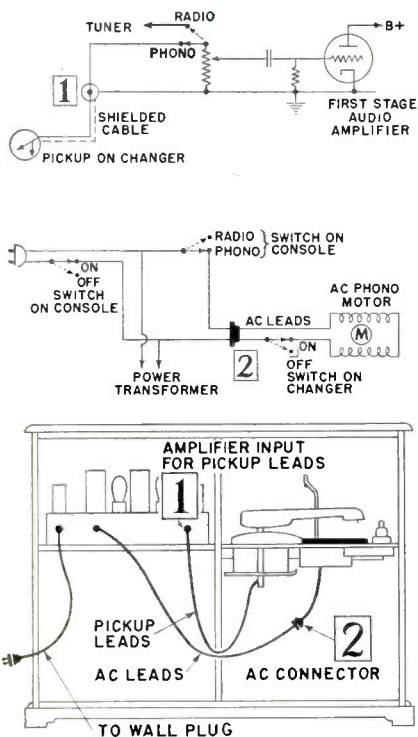


Fig. 4—(Top) Lead connection diagram—typical circuit. (Center) AC lead connection diagram—typical circuit. (Bottom) AC and pickup leads, changer chassis to radio chassis.

tics of this cartridge. Detailed electrical connections for both type cartridges will be treated later in this article.

#### Physical Installation

The physical and electrical basis for the diskchanger selection now established, removal of the old unit and actual installation of the new changer can be accomplished. (The *ac* cord should be disconnected from the wall socket while working on the installation). Almost all changers are secured to the mounting platform with removable bolts. If the unit is part of a slide-drawer assembly, removal of the entire drawer will facilitate the work. This can be done after first disconnecting the *ac* and pickup leads. Usually both sets of leads are connected to plugs that conveniently pull out from receptacles on the radio or amplifier chassis. Should the leads be soldered directly to the circuit, unsolder them but note the exact connections so that proper lead connections can be made when installing the replacement diskchanger. After the obsolete changer has been removed, the mounting platform (board) can be modified to properly mount the new unit. A template, supplied with the diskchanger, shows the correct cutout form. In the event a new board is needed the template provides a tracing for easy construction.  $\frac{5}{8}$ " plywood is recommended for this purpose. Mounting boards, cut to fit the exact mounting requirements of Webcor

diskchangers, are available. The photograph in Fig. 3 shows a Webcor board that will serve as a replacement for the original and make the installation even more simple. The old board may be left in place, however, and most of the inside portion cut away. The new board can be placed on top of it and wood screws used to secure the mounting. If the cabinet will not permit the additional  $\frac{5}{8}$ " vertical space required, removal of the old board and replacement with the new will be necessary. Alterations of the outside board dimension may be required in order to fit it properly into a particular cabinet. Sanding, staining, and otherwise finishing the board to match the cabinet interior can be accomplished to complete the physical installation.

#### Electrical Installation

As stated previously, a modern changer, equipped with a crystal tape cartridge, will be electrically interchangeable with an old unit using a crystal cartridge. The small problem involved then is that of making correct *ac* and pickup lead connections. The *ac* leads, usually color coded, carry the

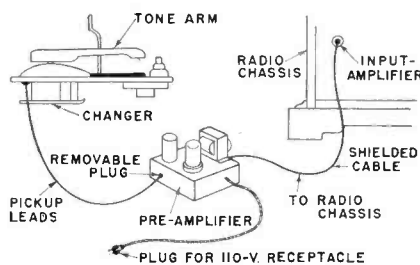


Fig. 5—Electrical position of typical pre-amp in a circuit comprising a changer and an input amplifier.

power to the motor of the diskchanger and the pickup leads deliver the electrical impulses, picked up by the cartridge, to the voltage amplifier (input) of the audio amplifier. The pickup leads are generally in cable form with the conductor insulated within a braided metal shield. Usually special plugs are used on


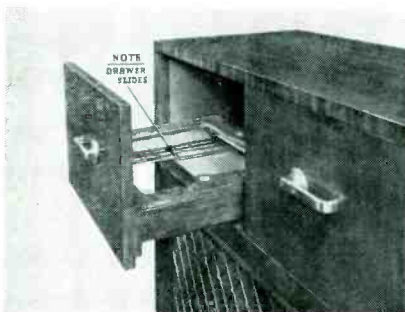


Fig. 6—Slide drawer type of mounting for changer mechanism.

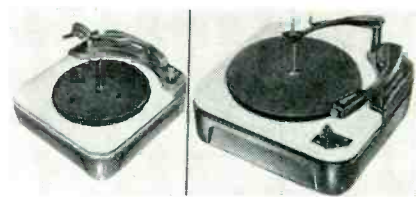

#### Base-Mounted Fonographs

MODEL	MIN. SPACE REQUIRED			PICK-UP	CORD LENGTHS
	A	B	C		
122-4	14½"	13½"	8¾"	Crystal	3'
122-270	14½"	13½"	8¾"	G.E. Triple Play	3'
127-1 HF	15"	15"	9½"	Crystal	6'
127-270 HF	15"	15"	9½"	G.E. Triple Play	6'
127-27 HF	15"	15"	9½"	Plug-in Heads for Magnetic Cartridge	6'

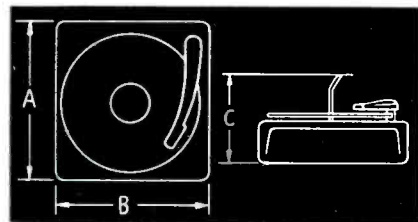


Fig. 7—Specifications for base pan models. Measurements relating to space requirements are shown in center.


the leads that connect the old changer to the audio amplifier. The leads on both new and old changers must be identified and matched so that these plugs can be correctly used on the new diskchanger leads. The shield of the pickup cable is chassis grounded while the conductor will connect to the terminal of the plug that leads the amplifier input. Quite often the bayonet plug on the end of the pickup cable of Webcor diskchangers will be the same type used on the original changer and will fit directly into the chassis receptacle. In Fig. 4 the illustration and circuits shown are typical of those found in most consoles.

If a variable reluctance (magnetic) cartridge is used in a replacement unit, it will be necessary to install a pre-amplifier that will match the electrical characteristics of a particular magnetic cartridge. Several Webcor models are available equipped with either the General Electric triple-purpose cartridge or plug-in shells that will accept other magnetic cartridges. Cartridge manufacturers supply self-powered, matching pre-amps that can be easily mounted on the inside of the cabinet. The diagram in Fig. 5 shows the electrical position of the pre-amp in the circuit.

#### Special Considerations

**Cabinet Design:** In a few instances the cabinet may be designed so that the record changer will come forward as the compartment door is pulled down. The redesign of this particular section of the cabinet may, in some cases, be easier than

[Continued on page 71]

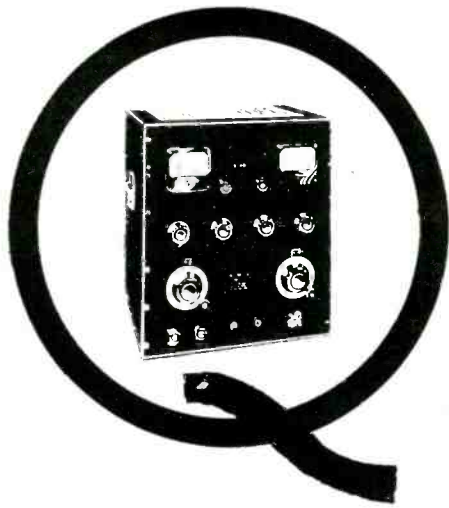

# MEASUREMENTS and METERS

PART I

by RUFUS P. TURNER

INNUMERABLE coils and capacitors are employed in radio, television, and electronics. Efficient functioning of the circuits in which they operate depends upon the goodness of these components. The measurement of coil and capacitor quality therefore is as important as the measurement of inductance and capacitance. And often the quality is more important than absolute inductance and capacitance values.

There are several methods of checking the quality of these reactive components. But, when coils and capacitors are to be used at radio frequencies, the best test by far is the measurement of "Q."

### What is "Q"?

The Q factor is the ratio of reactance ( $X$ ) to resistance ( $R$ ). It is expressed by the simple fraction  $X/R$ . The Q unit has no name comparable to the ohm for resistance, the ampere for current, and the cycle for frequency. It is merely numerical. The higher the Q, the better the grade of the component.

In either a coil or a capacitor, reactance is what we want (inductive reactance,  $X_L$ , in a coil; capacitive reactance,  $X_C$ , in a capacitor). But, we are forced to accept a certain amount of resistance also as an unavoidable by-product. Radio-frequency resistance results from characteristics of the wire with which a coil is wound; the metal plates, leads, terminals, and fittings of a capacitor; metal platings, corrosion, and presence of solder in circuit leads; skin effects; dielectric losses; moisture (surface, absorbed, and absorbed); proximity of shields and other metallic objects; and similar causes. RF resistance (which is what is meant by the term  $R$  in the Q fraction) can, under some condi-

The meaning of Q and various methods by which it may be measured is contained in this first installment. The subject matter is presented in a comparatively simple form.

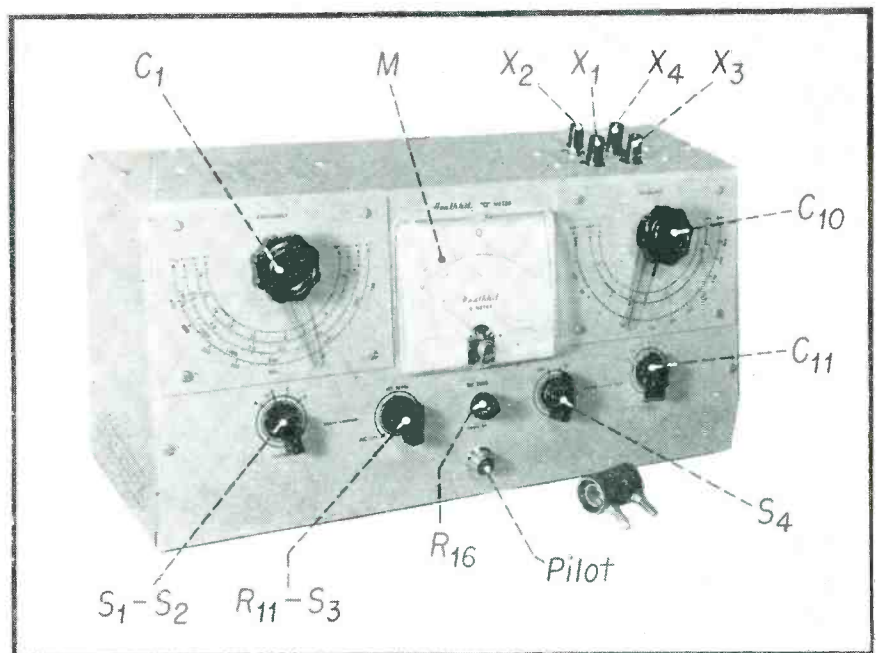


Fig. 1—Custom-Built Q-Meter. A description of this instrument will appear in the second installment next month.

tions, be many times higher than any simple *dc* resistance present. It cannot be measured by any simple means, such as an ohmmeter.

If we expand the expression  $X/R$ , we obtain for a coil:

$$Q = 6.28fL/R$$

and for a capacitor:

$$Q = 1/6.28fCR$$

Frequency  $f$  is expressed in cycles,  $L$  in henries,  $R$  in ohms, and  $C$  in farads.

If we use the units more commonly employed in radio-frequency work (that is:  $f$  in megacycles,  $L$  in microhenries, and  $C$  in micromicrofarads), the Q equations become:

$$(1) Q = 6.28fL/R \text{ for a coil}$$

$$(2) Q = 159,000/ICR \text{ for a capacitor}$$

From the appearance of these equations, it would seem that all that is necessary is to calculate the reactance

from inductance or capacitance measurements at a known frequency, check the resistance in some simple manner, and divide the one by the other. Actually, the job is not that easy, since *rf* resistance is not measured in any simple way.

Conventional *Q* measurements at radio frequencies involve the checking of a test component in a resonant circuit. Several methods have evolved from laboratory techniques and have given rise to *Q*-meters as definite instruments.

The following paragraphs describe the most widely used methods of measuring *Q*, and the instrumentation required.

### Susceptance Variation Method

Figure 2 illustrates a method of *Q* measurements employed occasionally in laboratories without standard *Q*-meters. While it usually consists of a temporary laboratory bench setup of signal generator, tuning capacitor, and v. t. voltmeter, the circuit has been incorporated into a permanent *Q*-meter by some experimenters.

In this arrangement (see Fig. 2A), a test coil, *L* for which the *Q* Value is required, is connected in series with a low-loss air-dielectric variable capacitor, *C*. A signal voltage, at the desired *rf* test frequency, is loosely-coupled into the circuit via the coil. A high-impedance *rf* vacuum-tube voltmeter then is connected across the tuning capacitor.

The circuit first is resonated to the test frequency by adjusting *C* for a peak deflection (E) of the v. t. voltmeter. The frequency at which this deflection is obtained is designated *f<sub>r</sub>* in Fig. 2B. The signal generator then is detuned to a lower-frequency setting (*f<sub>1</sub>*) at which the meter deflection drops to 0.707E, being careful to keep the generator output constant. This is termed a half-power point. The generator next is tuned to a point (*f<sub>2</sub>*) higher in frequency than *f<sub>r</sub>*, at which the meter deflection again drops to a half-power point (0.707E).

The spread (*f<sub>2</sub>*-*f<sub>1</sub>*) between the half-power points shows the selectivity of the *LC* circuit, being narrow for a sharp (highly-selective) combination, and widely-spaced for a broad circuit. This spread also is proportional to the *Q* of the circuit, since the selectivity is proportional to the ratio of reactance to resistance in the circuit. The *Q* of the circuit may be expressed in terms of the three test frequencies according to the following equation:

$$(3) Q = f_r / (f_2 - f_1)$$

All *f* values are in the same units (cycles, *kc*, or *mc*, whichever is the most convenient to use)

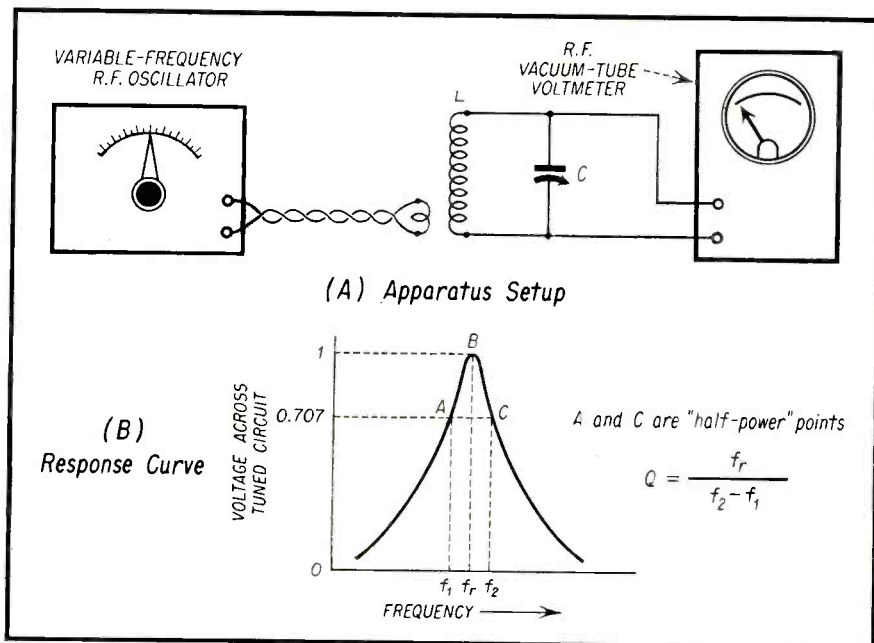


Fig. 2—Measuring *Q* without standard *Q*-Meter

A low-loss capacitor is employed at *C* in Fig. 2A. The capacitor *Q* therefore will be high. For this reason, the *Q* value obtained by means of Equation (3) may be assumed to be that of coil *L*.

### Fixed Frequency Susceptance Method

An alternative scheme employing the susceptance variation method utilizes capacitance changes, instead of frequency changes, in checking *Q* values. The frequency is held to a fixed value. In this scheme, the same circuit arrangement (Fig. 2A) is used. However, capacitor *C* must be provided with a dial reading directly in micromicrofarads.

The signal generator is set to the desired test frequency, and the *LC* circuit is resonated by adjusting capacitor *C* for peak deflection (E) of the v. t. voltmeter. The dial reading of capacitor *C* then is recorded as *C<sub>r</sub>*. Next, *C* is detuned to a capacitance setting lower than *C<sub>r</sub>* to obtain a drop in meter deflection to 0.707E. This second capacitance setting is recorded as *C<sub>1</sub>*. Finally, *C* is tuned to a capacitance setting higher than *C<sub>r</sub>* again to obtain a meter deflection of 0.707E. This third capacitance setting is recorded as *C<sub>2</sub>*. The circuit *Q*, which (because the losses in capacitor *C* are kept low) may be assumed to be the *Q* of coil *L*, may be determined from the successive capacitance settings, thus:

$$(4) Q = 2C_r / (C_2 - C_1)$$

All *C* values are in the same units ( $\mu$ f or  $\mu\mu$ f whichever is the more convenient to use)

When the maximum capacitance of the tuning unit, *C*, is very high, the increment *C<sub>2</sub>*-*C<sub>1</sub>* may be so small that it cannot be read accurately on the tuning capacitor dial. In order to facilitate the measurement, a small calibrated trimmer capacitor often is operated in parallel with *C*, and the capacitance-shift values read on the dial of the trimmer, rather than on the main dial.

### Measuring Q by Susceptance Method

When it is desired to use the susceptance variation method of measuring *Q*, a choice must be made between varying the frequency or varying the capacitance. Often, the decision will be governed upon which pieces of equipment are available. Some engineers favor the variable-frequency scheme because it allows a constant circuit capacitance. However, the frequency increments which must be read for high-*Q* values often are too small to be observed accurately on ordinary signal generator dials. The variable-capacitance scheme requires a dial-calibrated low-loss tuning capacitor and usually a dial-calibrated trimmer as well. For high and medium *Q* values, the same *Q* should be obtained with each scheme if provision is made for the close reading of capacitance or frequency increments. At low *Q* values, there may be some difference in final results because of the larger *f* and *C* increments which might not necessarily be in direct correspondence. In the latter case, the balance is tipped slightly in favor of the capacitance-variation scheme.

### Measuring L and C

The *Q* circuit may be used addi-



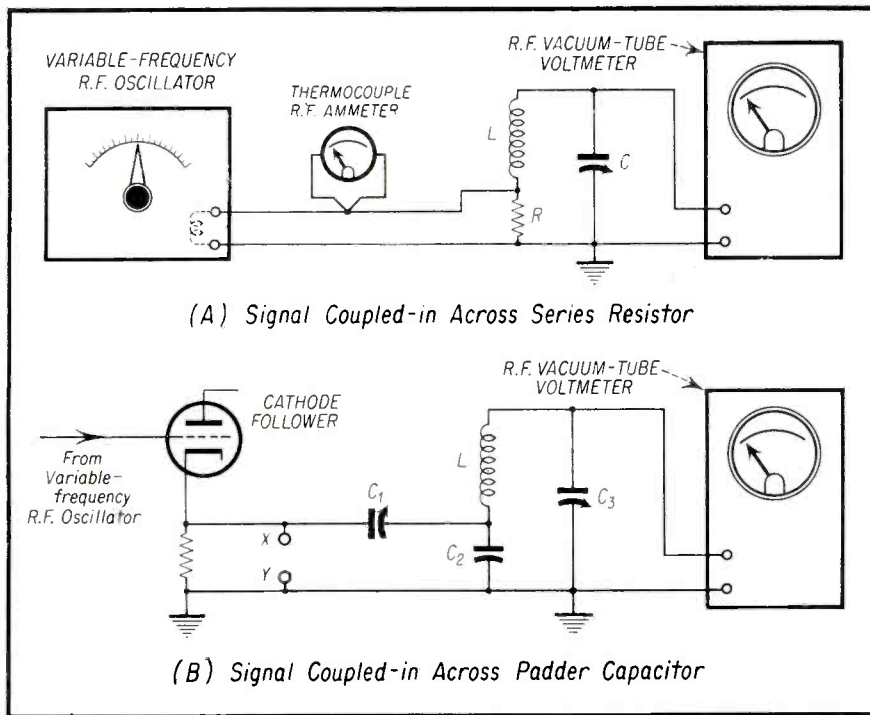


Fig. 3—Q-Voltmeter method of Q measurement.

tionally for the convenient measurement of capacitance and inductance at radio frequencies. If the capacitance value of  $C$  in Fig. 2A is known accurately, a coil of unknown inductance  $L_x$  may be connected at  $L$ . Either capacitor  $C$  or the signal generator frequency,  $f$ , then may be varied to obtain a peak deflection of the v. t. voltmeter. At this resonance, the unknown inductance may be determined in terms of the frequency and circuit capacitance:

$$(5) L_x = 25,400 / f^2 C$$

Where,  $L_x$  is in microhenrys

$f$  is in megacycles

$C$  is in micromicrofarads

As will be shown later in this article, the inductance value calculated by means of Equation (5) does not take into consideration the distributed capacitance of the coil. Further instructions will be given for increasing the accuracy of the measurement by checking the distributed capacitance.

For capacitance measurement, the unknown capacitance is connected into the Q circuit in place of  $C$  (Fig. 2A), and a coil of accurately-known inductance connected in position  $L$ . The signal generator then is tuned for resonance, as indicated by peak deflection of the meter. The unknown capacitance value then is calculated from the corresponding frequency and inductance values, as follows:

$$(6) C_x = 25,400 / f^2 L$$

Where,  $C_x$  is in  $\mu\mu\text{f}$

$L$  is in microhenrys

$f$  is in megacycles

It should be borne in mind that this unavoidably is a measurement of the total circuit capacitance which includes circuit strays, lead capacitance, distributed capacitance of the coil, and input capacitance of the v. t. voltmeter, as well as the capacitance of the test unit. The accuracy of measurement can be high only when  $C_x$  is large compared to the total circuit capacitance due to other sources.

#### Measuring C by Substitution

Better accuracy of measurement is obtained when the substitution method is used. In this case, the circuit (Fig. 2A) is set up with a dial-calibrated variable capacitor at  $C$ . Coil  $L$  need not be an accurately-known standard inductor. Resonance is obtained first with only  $L$  and  $C$  in the circuit, by setting  $C$  to its maximum value ( $C_1$ ) and tuning the signal generator for peak deflection of the v. t. voltmeter. The unknown capacitance,  $C_x$ , then is connected in parallel with tuning capacitor  $C$  and the latter detuned to a setting  $C_2$  required to re-establish resonance. The unknown capacitance then is:

$$(7) C_x = C_1 - C_2$$

In order to minimize stray shunting capacitances, the shortest possible leads must be used in connecting the unknown capacitor into the circuit.

While possessing increased accuracy, the substitution method is limited to capacitance values which do not exceed the value equal to the difference between maximum and minimum ca-

pacitances possible with the calibrated capacitor,  $C$ . Thus, in the case of a tuning capacitor having a maximum setting of 500 and a minimum of 35  $\mu\mu\text{fd}$ ., the maximum unknown value which might be measured by the substitution method would be 500-35, or 465  $\mu\mu\text{fd}$ .

#### Q-Voltmeter Method

The second method of Q measurement, which is becoming the more widely used in current practice, is termed the Q-voltmeter method. While based upon the same underlying relationships as the susceptance variation method involving series resonance at radio frequencies, the technique of the Q-voltmeter method differs somewhat from the other, especially in the method of arriving at final Q values.

Fig. 3 shows two schemes used in this method. In Fig. 3A, the rf test signal is injected into the Q test circuit ( $L$  and  $C$  in series) by means of a very low non-inductive resistor,  $R$ , across which the signal generator output voltage is developed. This resistor has an ohmic value of the order of a few hundredths of an ohm, so its presence will not lower the circuit Q drastically.

Capacitor  $C$  is adjusted to resonate the circuit at the test frequency, resonance being indicated as usual by peak deflection of the v. t. voltmeter. Since  $L$  and  $C$  are components of a series resonant circuit, both capacitive and inductive reactances are cancelled at resonance and only the small resistance of the coil and capacitor remains in the circuit to limit current flow. The circulating current accordingly is high, and the voltages  $E_c$  (appearing across the capacitor) and  $E_L$  (across the coil) are many times higher than the signal voltage  $e$  set up across the coupling resistor,  $R$ . Since at resonance the voltage across the coil equals the voltage across the capacitor, the v. t. voltmeter might be connected across either  $L$  or  $C$ . However, connection of the meter across the capacitor provides a common ground.

Since the voltage ( $E$ ) across either the coil or capacitor will be proportional to the ratio of reactance to resistance, the meter deflection will be proportional to circuit Q. In fact, the following relationships exist:

$$(8) E = Qe, \text{ and } Q = E/e$$

Where,  $E$  is the meter deflection, and  $e$  is the small voltage developed across coupling resistor,  $R$

Thus, the v. t. voltmeter scale may be calibrated to read Q values directly,

[Continued on page 71]



# LOOKING for TROUBLE?

NO. 13 -

By CYRUS GLICKSTEIN

**Y**OU can join in the search for trouble in a TV receiver by answering the questions in this troubleshooting quiz. Answer each question before going on to the next. If there is more than one correct answer to a question, give all correct answers.

Answers and discussion follow.

**Complaint:** The receiver, which is being serviced in a home visit, has diagonal black and white lines across the picture on Channel 5. Other channels and sound normal.

**Model:** Receiver is a split sound (not intercarrier); video *if* is 25.75 *mc*, sound *if* is 21.25 *mc*.

1. The black and white bars are evidently an interference pattern on the screen. Which of the following is the best way(s) to deal with interference:

- (a) Advise owner to communicate with the FCC.
- (b) Inform the owner the design of the receiver is defective.
- (c) Determine the nature of the interference.
- (d) Inquire if there are any Ham radio operators in the neighborhood.
- (e) Check with the owner to determine at what times and on what channels the interference has been noticed.

2. The owner stated the interference was present whenever Channel 5 was tuned in. This was confirmed by observation. In general, this type of interference pattern is most likely caused by which of the following:

- (a) Ignition noise.
- (b) Diathermy.
- (c) Local oscillator interference from a neighbor's set.
- (d) A *tweet*.
- (e) Other *rf* signal interference.

3. The observed pattern is most likely a *tweet* (internally generated interference), local oscillator interference

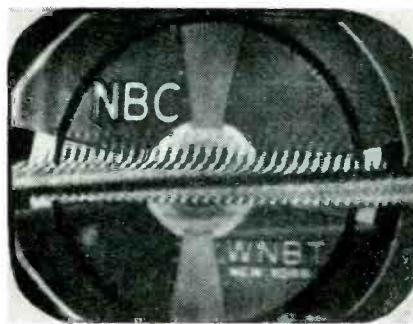


Fig. 1—Mild diathermy interference.

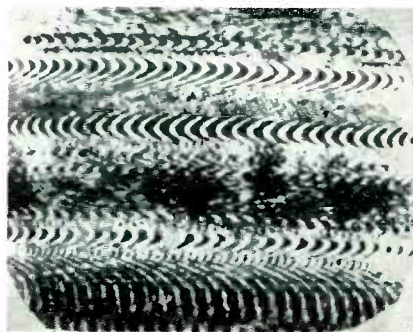


Fig. 2—Severe diathermy or FM interference.



Fig. 3—One type of *rf* interference pattern (radio transmission, oscillator radiation, etc.).

ence from a neighbor's set, or some other type of steady *rf* interference. As a further check in determining the origin of the interference (internal or external), which of the following step(s) is helpful:

- (a) Rotate the fine tuning control.
- (b) Check the signal on each channel.
- (c) Disconnect the antenna leadin from the antenna terminals.
- (d) Take out the *rf* oscillator tube.
- (e) Take out the last video *if* tube.

4. The channel selector was rotated through its range to check if the interference appeared on any other channel. It appeared only on Channel 5. The fine tuning control was rotated while tuned to Channel 5. The interference pattern superimposed on the picture changed from narrow slanting lines to broad horizontal stripes and back to narrow slanting lines as the fine tuning was rotated through its range. Toward the extremes of tuning rotation, the interference pattern disappeared. The broadcast horizontal stripes were noted at the point of best sound. This is characteristic of a *tweet* in this model.

To determine whether the *tweet* originates in the video or sound *if* strip, which of the following is done:

- (a) Check the video and sound intermediate frequencies.
- (b) Apply a scope to the video detector.
- (c) Apply a scope to the discriminator output.
- (d) Remove the video detector tube.
- (e) Remove the first sound *if* tube.

5. The *tweet* originated in the video detector as could be verified by checking the video intermediate frequency (25.75 *mc*). The 3rd harmonic of this frequency (77.25 *mc*) beating with the video carrier of Channel 5 (77.25 *mc*) caused the beat-frequency interference

over **99%\***  
 hit the bull's-eye  
 for quality!

that's why we call

**Federal**  
 PICTURE TUBES

**"BEST-IN-SIGHT"**

Thousands of famous-name picture tubes were quality-tested by a famous-name TV set manufacturer.\* When the scoring was over, Federal led all the brands tested . . . with an "OK" on over 99% of its tubes!

Here's proof, Mr. Serviceman, that it pays to replace with *Federal* . . . here's assurance of top performance . . . of less time wasted on call-backs . . . of more profit per tube replaced!

Federal quality brings to servicemen a tremendous opportunity to create customer-goodwill . . . to build steady replacement business.

Federal quality *stands by* servicemen, because it *stands up* in service . . . backs up their years of experience and know-how . . . their *trained* judgment. That's one of many big reasons why more and more servicemen are specifying Federal "Best-in-Sight" picture tubes.

Join the trend today . . . ask your Federal Distributor about the popular-size line that takes care of over 90% of all TV replacements . . . ! For information, write to Dept. N-385.


**"Federal always has made better tubes"**

**Federal**  
 Telephone and Radio Company




100 KINGSLAND ROAD, CLIFTON, N. J.

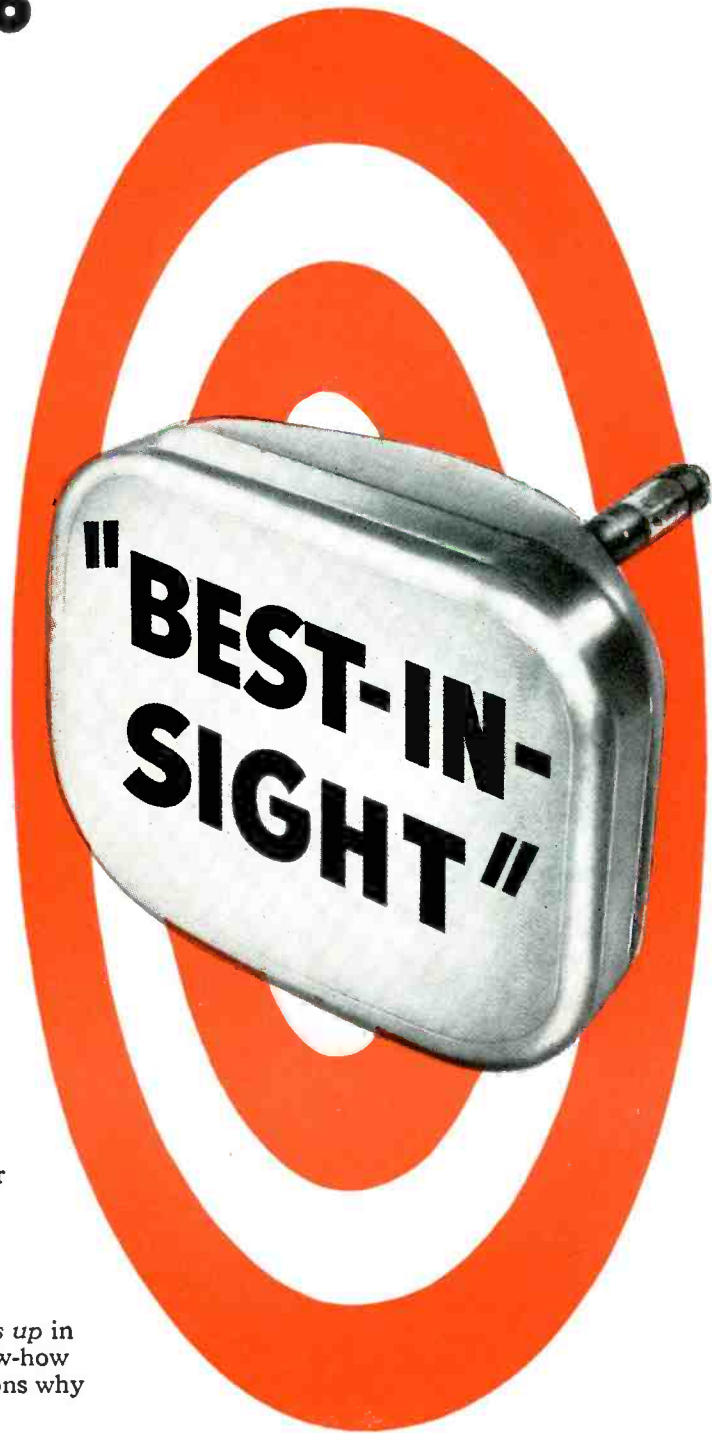In Canada: Federal Electric Manufacturing Company, Ltd., Montreal, P. Q.  
 Export Distributors: International Standard Electric Corp., 67 Broad St., N. Y.



Get Your Copy of  
 Federal's  
 TV Picture Tube  
 DATA BOOK

12-page booklet with information on interchangeability, basing diagrams, bulb outlines, dimensions, characteristics. Address your inquiry to Dept. listed above.

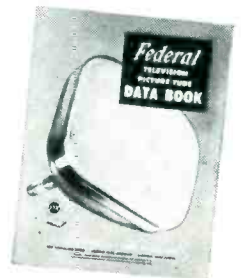

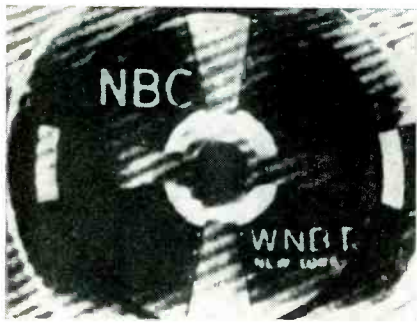


Fig. 4—Another type of *rf* interference.

noted on the screen. Which of the following method(s) can be used to eliminate the tweet:

- (a) Shield *if* and detector tubes.
- (b) Use a tweet trap.
- (c) Reorient power supply leads in the chassis.
- (d) Reorient antenna leadin to the tuner.
- (e) Bypass filament line at the detector.

#### Answers and Discussion

##### 1. c, e

The first step in servicing a TV receiver for an interference problem is to determine the nature of the interference by careful observation of the pattern. At the same time, it is helpful to secure from the owner information concerning the periods when the interference is seen (and possibly heard) and the channels affected.

A comparatively small proportion of TVI is caused by Ham operators. Where the interference does originate in a Ham transmitter, the fault is often in the TV receiver rather than the transmitter. Amateur operation is entirely legal on the regularly assigned frequencies. If interference is caused at the receiver due to poor selectivity or similar reasons, the correction must be made at the receiver. Only when the Ham is guilty of transmitting harmonics or other spurious signals can he be required to adjust his equipment.



Fig. 5—Enlarged section of picture showing 4.5 mc interference.

##### 2. c, d, e

There are many kinds of interference which can affect a TV receiver. Interference can be external or internal, depending on the origin.

External interference, which comes into the receiver from an outside source, includes:

- (1) Ignition and similar noise causing random flashes across the screen.
- (2) Diathermy, *rf* (dielectric) heater, etc. Usually causing a herringbone pattern through a part of the picture. However, this interference may show up in other ways (depending on the strength of the signal), from a slight

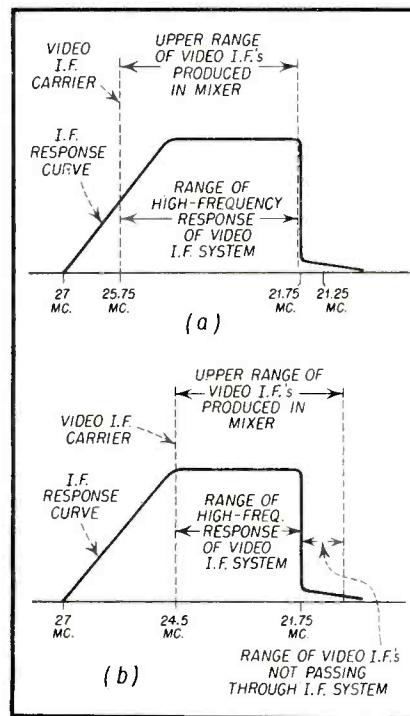


Fig. 6—High frequency response of video *if* system as affected by fine tuning.

- (a) Full range of high frequencies pass through *if* stages with fine tuning at correct point.
- (b) Higher video intermediate frequencies unable to pass through *if* system when fine tuning is rotated to minimize 4.5 mc interference.

horizontal pulling at the top of the picture to a black and white marble-striped pattern covering the entire screen. (Figs. 1 and 2)

(3) Local oscillator interference from a neighbor's set—narrow vertical or diagonal black and white stripes. (Figs. 3 and 4)

(4) Amateur or other radio transmission—similar to local oscillator interference, but may be keyed on and off (code) or intermittent (voice broadcasting).

(5) FM interference—wavy vertical line pattern. (Fig. 2)

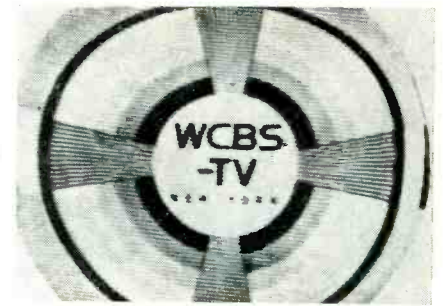


Fig. 7—Interference pattern caused by *rf* power supply.

(6) Adjacent channel interference—there are two types of interference caused by TV stations on adjacent channels. Interference from the adjacent lower channel is caused by the sound carrier and gives a herringbone pattern which varies according to the sound in the adjacent channel program. Interference from the adjacent higher channel is from the video carrier and results in a superimposed picture (stationary or slowly moving) or in a number of diagonal lines or in a vertical moving bar.

(7) Co-Channel interference—this results in a venetian blind effect, usually, with a superimposed picture.

Co-Channel and adjacent channel interference are generally problems only in fringe areas, which receive signals from widely separated stations.

F-M interference has a typical wavy or herringbone pattern. The instantaneous changes in the *rf* frequency from line to line cause the interference signal to shift slightly to the right and left from one line to the next. This wavy pattern is also typical of diathermy, dielectric heaters, and similar sources of interference since the frequency shifts somewhat with changes in load.

There are several types of interference patterns which are generated internally in a TV receiver. Internal interference has probably not received as much attention in technical litera-

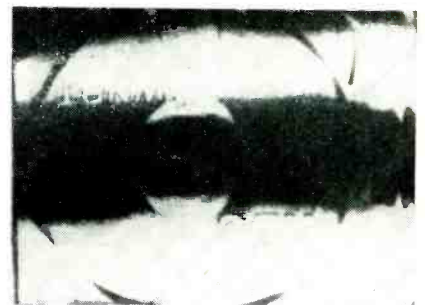



Fig. 8—120 cycle hum picked up in video stages.

# NEW

# WALSCO *Imperial*

\*
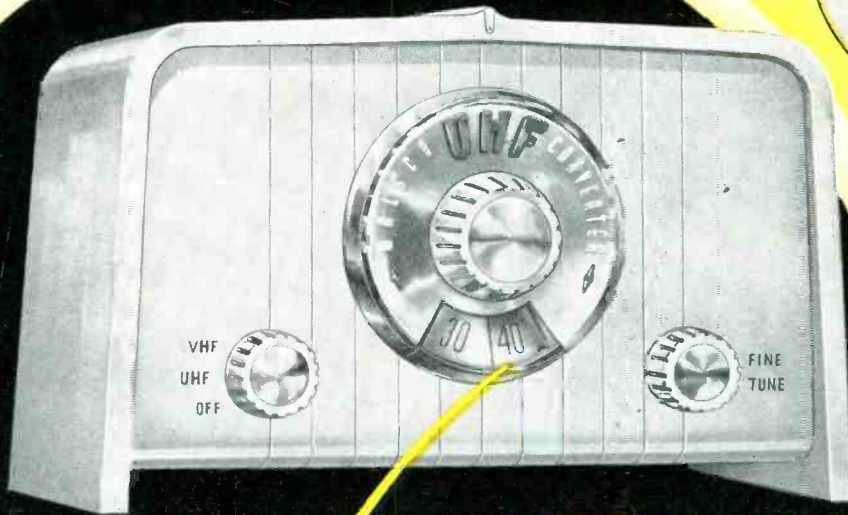
## PROVEN THE MOST ADVANCED UHF CONVERTER IN AMERICA



NEW distinctive cabinet design available in beautiful assortment of COLORS

WITH EXCLUSIVE

*Surreture*

UP TO

**98%**  
GREATER POWER  
GAIN

UP TO

**88%**  
LESS NOISE  
FACTOR

**\* FACTS**

from one of America's leading, independent research laboratories proved the WALSCO Imperial will out-perform all other UHF converters... anywhere!

	Average Power Gain DB			Average Noise Factor DB		
	500 mc	650 mc	800 mc	500 mc	650 mc	800 mc
WALSCO Imperial	10.0	9.5	9.5	15.0	15.5	16.0
Converter A	6.0	5.2	3.5	18.5	20.0	21.0
Converter B	7.0	3.5	5.0	18.0	18.5	20.0

WRITE FOR COMPLETE INFORMATION

## WALSCO ELECTRONICS CORPORATION

3602 Crenshaw Blvd. • Los Angeles 16, California

# TELEVISION INTERFERENCE AIDS

## TV Causes, Effects and Solutions...

1. Diathermy, industrial heaters, etc.

**Solution:** High pass filter. AC line filter. If these measures are ineffective contact owner of interfering equipment and recommend manufacturer be advised.

2. Radiation from local oscillator of nearby TV and FM broadcast receivers.

**Solution:** Re-alignment of offending receiver.

3. Strong signals from nearby radio stations, including FM broadcast, amateur, police, taxi, government, airways and military services.

**Solution:** Install high pass filter, line filter, or in extreme cases install an absorption filter tuned to the interfering signal. If these measures ineffective locate and contact owner of equipment.

4. Cross modulation external to the receiver, but possibly including external rectification sources such as corroded antenna and transmission line connections.

**Solution:** Check lead-in or antenna for broken or corroded connections. Additional possibilities are poor connections in house wiring, plumbing, stovepipes, etc.

5. Multiple images.


**Solution 1:** Reorient or relocate antenna and/or lead-in.

**Solution 2:** May be caused by standing waves due to an impedance mismatch between antenna, transmission line and receiver impedance. This condition can be detected by wrapping a piece of metalized paper around lead-in, watching for variations in reflections and signal strength while sliding metalized paper along lead-in.

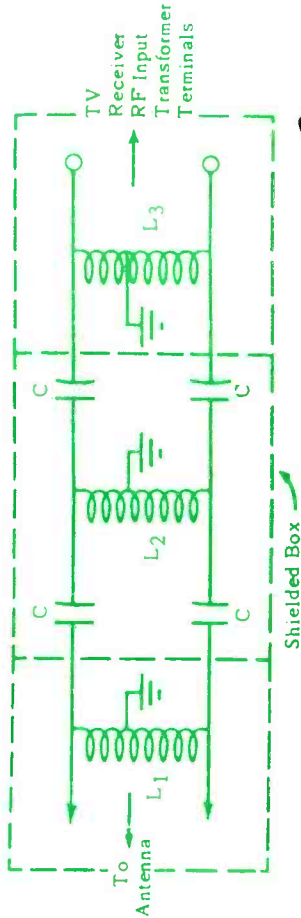6. Direct I.F. pickup.


**Solution 1:** Shield section responsible. (Shielding must be complete).

HIGH PASS FILTER FOR 300 OHM TELEVISION RECEIVER INPUT



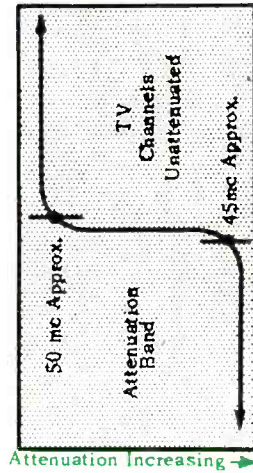**Caution!**

- No. 1 Be certain to supply a good electrical ground with an absolute minimum of lead, preferably to set ground. Where receiver has AC/DC chassis, ground through 0.001 mfd, 600 Volt mica condenser.
- Place filter as close as possible to r.f. input transformer.



C = 15 mmfd Ceramic

L<sub>1</sub>, L<sub>3</sub> = 1.2 mh (21 Turns No. 24

Enamel Wire Close Wound on 1/4" Diameter

Polystyrene Rod)

L<sub>2</sub> = 0.6 mh (15 Turns No. 24


Enamel Wire Close Wound on 1/4" Diameter

Polystyrene Rod)

Commercial filters are available in the following ranges both fixed and tunable

0-30 Mc      0-50 Mc      20-30 Mc      40-50 Mc      88-174 Mc


STUB WITH 300 OHM TWIN LEAD IN

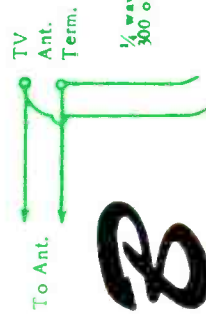

Open End

Length of stub in inches =  $\frac{2450}{f}$  in mc

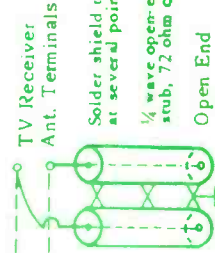1/4 WAVE OPEN-ENDED STUB WITH 2 PARALLEL LENGTHS OF 72 OHM COAX FOR USE WITH 300 OHM INPUT



Formula for stubs shown are approximate, being empirically derived from  $L = 492 \times \frac{f}{v}$  in mc and are based upon average values of velocity factor for typical transmission lines.

Length of stub in inches =  $\frac{1945}{f}$  in Mc.

This type of stub has several advantages over 300 ohm tape.

\* Refer to Caution No. 1 on High Pass Filter (Above)

**Solution 2:** Realign I.F. (See section C for more detailed information).

**Solution 3:** Check lead dress, particularly of long leads.

**7. Image interference** (This situation exists when a strong signal occurs at the oscillator frequency plus or minus the I.F.)

**Solution:** Use appropriate stub or tuneable trap. (Refer to section B. High pass filter is ineffective in this specific application.

**8. Signal operating in normal receiver pass band.**

**Solution:** Find offending source and if unable to obtain cooperation, report to FCC.

**9. Misadjustment of I. F. traps, I. F. tuned circuits, or misadjustment of TV receiver controls** (traps may be faulty).

**Solution:** Correct misalignment or replace, or repair, defective component.

**10. Faulty neutralization, particularly in triode or triode connected pentode cascade type tuners, may cause cross-hatch pattern on picture tube.**

**Solution:** Locate defective component and replace.

**11. Audio rectification characterized by audio from other than TV stations, such as police broadcast, taxi, utility, amateur stations, etc.**

**Solution:** Since this rectification normally occurs at the grid of the first audio amplifier it can be eliminated by insertion of an RC filter placed as close as possible to the grid of the first audio tube (100 k resistor in series with the audio grid lead and 500 mmfd condenser direct from grid to cathode. It may be necessary to increase the value of the inserted by-pass condenser to as much as 1000 mmf and in the case where the manufacturer has used an extremely high value grid resistor in the order of 10 or more megohms, it may also be necessary to decrease this value. It is not usual for the audio signal to be degraded by changing the value of the grid resistor, for example, from 10 to 5 megohms).

**12. Ignition (Pulse) type interference sources including electric motors and other power equipment, household appliances, thermostatic devices and fluorescent lighting and fixtures.**

**Solution:** Line filters, change location of antenna, more directive antenna, use of coaxial in place of flat line. If these measures do not correct the condition locate the source and contact owner for his cooperation in eliminating the interference at the source.

This chart has been provided for your use through the coordinated efforts of the Washington Interference Committee, the Radio-Electronic-Television Manufacturers Association, and the Federal Communications Commission. It has been published as a public service by the Electric Institute of Washington, and is presented for wall chart use by Radio-TV Service Dealer Magazine.

**EXAMPLE**  
For an interfering signal at 75.5 mc: 2450 ÷ 32.5 approx. = 75.5

1. It can be moved or rolled up with negligible change in characteristics.  
2. It is completely shielded, and it will not re-radiate, nor itself pick up signals.

Table of lengths of 1/4 wave open, 300 ohm line covering the FM band:

Frequency in Mcs	L in inches
88	27.8"
95	25.8"
108	22.7"

When a television receiver is in a strong field of r.f. close to the intermediate frequency of the receiver, direct pickup in one or more of the i.f. stages is likely. For example, a signal on 21.9 Mc would probably be picked up in the i.f. of a television receiver using a 21.9 audio i.f. channel. If a high pass filter is ineffective in eliminating the interference the i.f. should be re-aligned to a frequency different from the interfering signal by a few hundred Kc (As an example, in this case, to 22.2 Mc).

R.F. OSCILLATOR SETTINGS, NOMINAL FOR 20 to 30 Mc AND NOMINAL FOR 40 to 50 Mc.

Channel	Channel Frequency	Pix Carrier	Sound Carrier	Rcvr. rf Oscillator (21.9 mc I. F.)		Rcvr. rf Oscillator (41.25 mc)
				Low	High	
2	54-60	55.25	59.75	37.85	81.65	101
3	60-66	61.25	65.75	43.85	87.65	107
4	66-72	67.25	71.75	49.85	93.65	113
5	76-82	77.25	81.75	59.85	103.65	123
6	82-88	83.25	87.75	61.85	109.65	129
7	174-180	175.25	179.75	157.85	201.65	221
8	180-186	181.25	185.75	163.85	207.65	227
9	186-192	187.25	191.75	169.85	213.65	233
10	192-198	193.25	197.75	175.85	219.65	239
11	198-204	199.25	203.75	181.85	225.65	245
12	204-210	205.25	209.75	187.85	231.65	251
13	210-216	211.25	215.75	193.85	237.65	257

The Washington Television Interference Committee is an organization which has volunteered to act as a clearing house for television interference complaints involving radio amateurs.

The Committee maintains close liaison with industry, communication services, the FCC and others. This committee set-up gives both the amateur and the receiver owner a third party group of experts who will investigate the complaint promptly.

For assistance in resolving interference complaints involving amateur radio, call **RE 7-2000** or write to The Washington Television Interference Committee, 129 Joliet street, S.W., Washington (20) D.C.

# VIDEO SPEED SERVICING SYSTEMS

## 12th INSTALLMENT

### INDEX FOR JULY, AUGUST and SEPTEMBER ISSUES

<i>Mfr.</i>	<i>Chassis No.</i>	<i>Section Affected</i>	<i>Month</i>	<i>Page</i>	<i>Card No.</i>
Admiral	19 Series	Sync	Sept.	39	AD19-1
Admiral	19 Series	Sync	Sept.	39	AD19-2
Admiral	19 Series	Pix and Sound	Sept.	39	AD19-3
Admiral	19 Series	Sync and pix	Sept.	40	AD19-4
Admiral	19 Series	Pix	Sept.	40	AD19-5
Admiral	19 Series	Sound	Sept.	40	AD19-6
Belmont Raytheon	20AY21	Pix	July	27	BE-Y21-1
Belmont Raytheon	20AY21	Pix	July	27	BE-Y21-2
Belmont Raytheon	20AY21	Pix	July	27	BE-Y21-3
Belmont Raytheon	20AY21	Pix	July	28	BE-Y21-4
Belmont Raytheon	20AY21	Sync	July	28	BE-Y21-5
Belmont Raytheon	20AY21	Raster	July	28	BE-Y21-6
CBS-Columbia	2000-1	Pix	August	31	CB2000-1
CBS-Columbia	2000-1	Pix	August	31	CB2000-2
CBS-Columbia	2000-1	Pix	August	31	CB2000-3
CBS-Columbia	2000-1	Pix	August	32	CB2000-4
CBS-Columbia	2000-1	Pix	August	32	CB2000-5
CBS-Columbia	2000-1	Pix	August	32	CB2000-6
Capelhart-Farnsworth	CX33	Pix	August	33	CA33-19
Capelhart-Farnsworth	CX33	Pix	August	33	CA33-20
Capelhart-Farnsworth	CX33	Pix	August	33	CA33-21
Capelhart-Farnsworth	CX33	Pix	August	34	CA33-22
Capelhart-Farnsworth	CX33	Pix	August	34	CA33-23
Capelhart-Farnsworth	CX33	Pix	August	34	CA33-24
DuMont	RA117	Pix	July	29	DM-117-1
DuMont	RA117	Pix	July	29	DM-117-2
DuMont	RA117	Raster	July	29	DM-117-3
DuMont	RA117	Pix	July	30	DM-117-4
DuMont	RA117	Sync	July	30	DM-117-5
DuMont	RA117	Sync	July	30	DM-117-6
Emerson	120144	Pix	July	31	EM-144-1
Emerson	120144	Pix	July	31	EM-144-2
Emerson	120144	Sync	July	31	EM-144-3
Emerson	120144	Sync	July	32	EM-144-4
Emerson	120144	Pix	July	32	EM-144-5
Emerson	120144	Sync	July	32	EM-144-6
RCA	KCS34	Pix	August	35	RC34-7
RCA	KCS34	Pix	August	35	RC34-8
RCA	KCS34	Pix	August	35	RC34-9
RCA	KCS34	Sound	August	36	RC34-10
RCA	KCS34	Raster	August	36	RC34-11
RCA	KCS34	Pix	August	36	RC34-12
Sentinel	Model No. 454, 5, 6, 7	Sync	Sept.	41	SE454-1
Sentinel	Model No. 454, 5, 6, 7	Pix, or pix and sync	Sept.	41	SE454-2
Sentinel	Model No. 454, 5, 6, 7	Pix	Sept.	41	SE454-3
Sentinel	Model No. 454, 5, 6, 7	Pix	Sept.	42	SE454-4
Sentinel	Model No. 454, 5, 6, 7	Sound	Sept.	42	SE454-5
Sentinel	Model No. 454, 5, 6, 7	Sync	Sept.	42	SE454-6
Sylvania	1-274	Audio	Sept.	43	SY274-1
Sylvania	1-274	Pix	Sept.	43	SY274-2
Sylvania	1-274	Sync	Sept.	43	SY274-3
Sylvania	1-274	Pix	Sept.	44	SY274-4
Sylvania	1-274	Audio	Sept.	44	SY274-5
Sylvania	1-274	AM/FM Radio	Sept.	44	SY274-6
Sylvania	1-437	Pix	Sept.	45	SY437-1
Sylvania	1-437	Audio	Sept.	45	SY437-2
Sylvania	1-437	Pix	Sept.	45	SY437-3
Sylvania	1-437	Audio	Sept.	46	SY437-4
Sylvania	1-437	Pix	Sept.	46	SY437-5
Sylvania	1-437	Sound	Sept.	46	SY437-6
Stromberg-Carlson	17 Series	Pix	August	37	SC17-1
Stromberg-Carlson	17 Series	Pix	August	37	SC17-2
Stromberg-Carlson	17 Series	Pix	August	37	SC17-3
Stromberg-Carlson	17 Series	Pix	August	38	SC17-4
Stromberg-Carlson	17 Series	Pix	August	38	SC17-5
Stromberg-Carlson	17 Series	Pix	August	38	SC17-6
Transvision	"A" Series	Raster	July	33	TA-A-1
Transvision	"A" Series	Raster	July	33	TA-A-2
Transvision	"A" Series	Sync	July	33	TA-A-3
Transvision	"A" Series	Pix	July	34	TA-A-4
Transvision	"A" Series	Pix	July	34	TA-A-5
Transvision	"A" Series	Pix	July	34	TA-A-6



# TROUBLE?

[from page 34]

ture as it deserves. Internally generated interference includes:

- (1) Tweets.
- (2) 4.5-mc interference.
- (3) RF power supply pickup.
- (4) 60-cycle and 120-cycle pickup.
- (5) Arcing.
- (6) Double conversion interference.

Tweets are harmonics of the video or sound *if* carrier which are fed back to the front end. These harmonics are in the tuning range of the incoming signals and therefore beat with the local oscillator producing a separate signal. For example, the video *if* carrier is 27.75 mc. The third harmonic is 77.25 mc. Channel 5 covers the range from 76-82 mc, with its video *if* carrier at 77.25 mc. The third harmonic and the video *rf* signal beat with the local oscillator each producing a video *if* signal. The two video *if* signals beat in the video detector to form a beat output appearing on the screen in the form of black and white stripes. When the fine tuning control is not rotated, these stripes are usually continuously in motion and vary in number and position. They vary from a diagonal to a vertical position and sometimes become horizontal. This interference can only be seen when a station channel is tuned in (and usually on one channel only), since the *if* harmonic can only be generated if a signal comes in and first produces the fundamental video (or sound) *if*. A tweet can appear on almost any channel, depending on the intermediate frequencies used in the receiver and the harmonic relationship of these frequencies to the tuned-in channel. The tweet pattern is affected considerably by the rotation of the fine tuning control.



Fig. 9—Sound bars (audio frequencies) in picture.

Interference of the 4.5 mc variety consists of very fine black and white stripes, slanting or vertical (Fig. 5) which has an effect similar to poor focus. This type of interference is caused when the beat between the video and sound *if* carriers in the video detector (the two frequencies are always 4.5 mc apart) gets through the video amplifiers to the screen. 4.5 mc interference appears in both intercarrier and split sound receivers, is quite common, and may at times be overlooked.

In split sound sets, this interference often results in a smeared picture. To minimize 4.5 mc interference, the viewer usually turns the fine tuning control past the best sound (and best picture) point. At the position where the fine interference lines are no longer visible, the high frequency response has been considerably reduced. The resulting picture has little fine detail and is smeared. This occurs because by tuning past the correct point, the sound *if* carrier is no longer at the skirt of the video response curve but beyond the video *if* bandpass. Therefore no sound *if* signal goes through the video strip to beat with the video *if* carrier and practically no 4.5 mc interference is produced. The video car-

rier is up on the response curve, giving an accentuated low frequency response and a reduced high frequency response (Fig. 6).

Another type of internally generated interference may occur in receivers having an *rf* type of high-voltage power supply. Diagonal or vertical black and white bars may be caused by leakage from this circuit. (Fig. 7) This type of interference is usually identified without difficulty by the frequency of the interference signal (approximately 300 kc) and by the knowledge that the receiver has this kind of supply.

60-cycle and 120-cycle power supply interference is readily recognizable (Fig. 8), and is generally caused by an internal defect—bad tube, hum in B+, etc.

Arcing in the high-voltage system appears like ignition interference on the screen but is usually heard in the sound also. It can easily be identified by being present when the antenna is disconnected. In addition, arcing can usually be seen and heard when examining the high-voltage cage with the set operating.

Double conversion interference is caused by a second TV channel being received when tuned to a desired channel. For example, a receiver is tuned to Channel 5 (76-82 mc). In this receiver, the oscillator is at 103 mc. A small amount of oscillator voltage may appear at the grid of the *rf* amplifier tube. This beats with the incoming signal of Channel 7 (174-180 mc), more specifically the sound *rf* carrier, 179.75 mc. The difference frequency between 103 and 179.75 mc, or 76.75 mc, appears at the mixer grid together with the desired signal from Channel 5. Both the desired signal from Channel 5 and the undesired beat from the Channel 7 sound carrier then beat with the oscillator frequency, are converted to *if* signals, and go through the video strip.

It is helpful in dealing with interference problems to know the approximate frequency of the interference pattern on the screen. Since the vertical sweep frequency is 60 cycles and the horizontal frequency is 15,750 cycles, it is simple to compute the frequency of any continuous *ac* signal on the screen. For example, a 60-cycle hum signal has one broad horizontal black and white bar (or one black and two white or one white and two black, depending on the phase of the hum signal). A 120-cycle signal (Fig. 8) has two black and two white horizontal bars, etc. All frequencies over 60 and less than 15,750 cycles give horizontal bars. Since 15,750 cycles is approximately the upper limit of human hearing, it can be said that any *audio* frequency

[Continued on page 63]

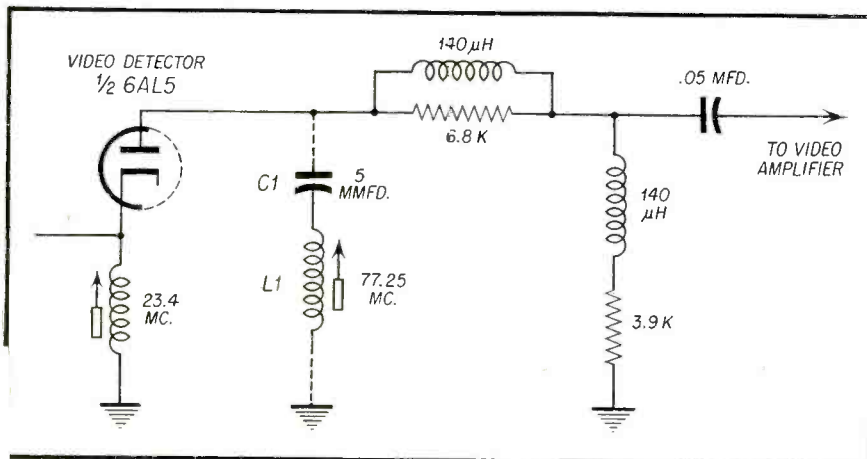


Fig. 10—Circuit diagram showing how tweet trap is installed across video detector load (see text).

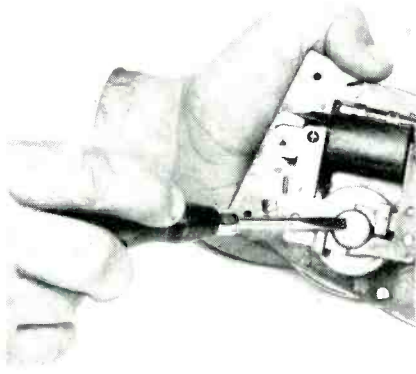


Fig. 1—The screwdriver in the workman's hands is pointing to the rotor, the motor which runs the timer.

**H**OW does a dealer or distributor handle the servicing of Telechron clock-radio timers? That is becoming an increasingly important question as the number of clock-radios in use rapidly mounts.

There are between 6 million and 7 million clock-radios in use today, according to Russell T. Woodward, Manager of Marketing, Telechron Department, General Electric Company, and by the end of next year this figure will be up around the 10 million mark.



"It isn't the percentage of Telechron timer repairs that makes this subject of so much interest to service people," Mr. Woodward points out, "but rather the combination of two facts: (1) the number of clock-radios in use is large and fast becoming larger and (2) the clock-timer part of the clock-radio is unfamiliar to many radio repair specialists."

The question, "How does a dealer or distributor handle the servicing of Telechron clock-radio timers?" breaks down into two answers: one on in-warranty repairs; another on out-of-warranty repairs.

**In-Warranty Repairs**

Any Telechron clock-radio timer returned to a dealer or distributor with-

Fig. 2—You need only to take out two screws in order to remove the rotor.

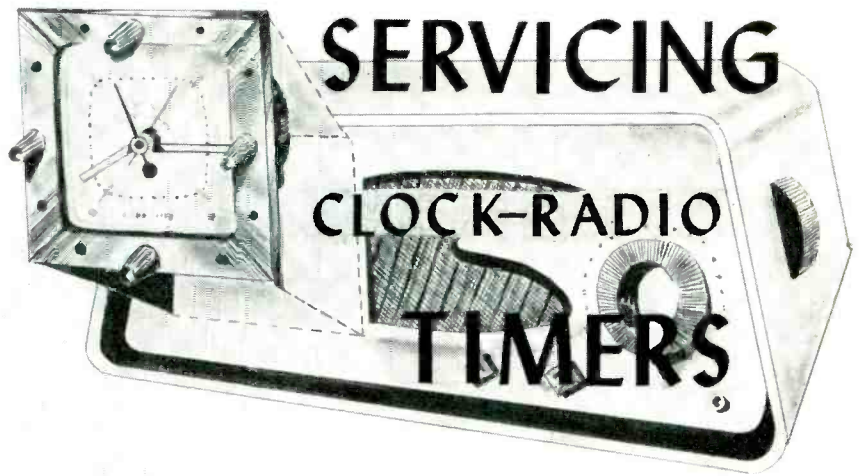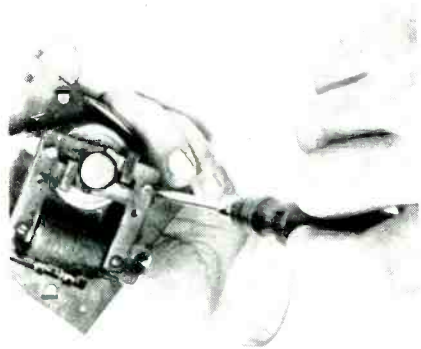

By Telechron Dept., General Electric Co.

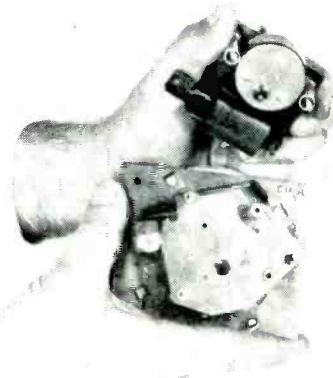


Fig. 3—The old rotor and field and coil assembly lifts out in one piece.



Fig. 4—Press with thumb on neck of rotor and it slips out smoothly and easily from the field.

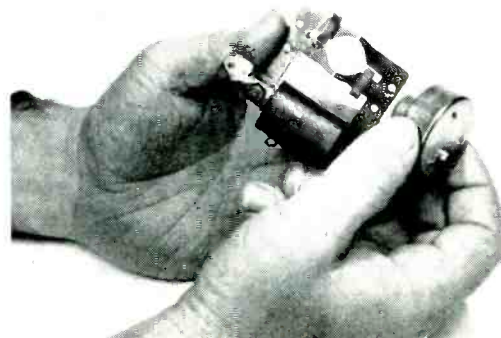


Fig. 5 — Disassembled the field and coil assembly is in the man's left hand, the rotor that runs the timer is in the right. Occasionally, the oil leaks out, or it wears and you have to replace it with a new one.

in the warranty period must be serviced by an authorized Telechron clock and timer service station. There are 121 of them located in principal cities all over the country. A list of these authorized service stations can be obtained by dealers and distributors by addressing a request to Product Service, Telechron Department, General Electric Company, Ashland, Mass.

Telechron timers are warranted for a period of one year.

If a customer, dealer or distributor tries to repair an in-warranty timer, he voids the warranty.

#### Out-of-Warranty Repairs

A different procedure is recommended for servicing of out-of-warranty timers. Recommended procedure is for the dealer or distributor to remove the timer from the clock-radio and send it to the nearest authorized service station, along with full information about its faulty behavior. Of course, if desirable, the complete clock-

radio can be sent to the service station. In such cases, however, there is a nominal extra charge for removal and replacement of the timer.

The above procedure should always be followed when the timer has failed because of defective friction, switches or gears. Such repairs call for the highly specialized skill of the authorized service station.

Simple out-of-warranty repairs may be handled by the dealer or distributor. It's relatively easy to replace broken crystals, damaged bezels and knobs, inoperative rotors and open coils. Vibrators and alarms are also easy to adjust. Parts for simple repairs can be obtained from authorized service stations.

Some manufacturers of clock-radios supply their own appearance items: crystals, bezels and knobs. In such cases, these parts must be obtained directly from the clock-radio manufacturer or a representative. Authorized

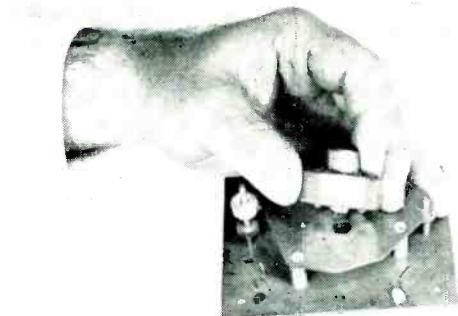


Fig. 6—The way to do it is to fit the rotor in position on the movement base plate. The gears must mesh first. If not done this way you are likely to fail to get your gears in mesh—they will jam up—the timer will fail to run.

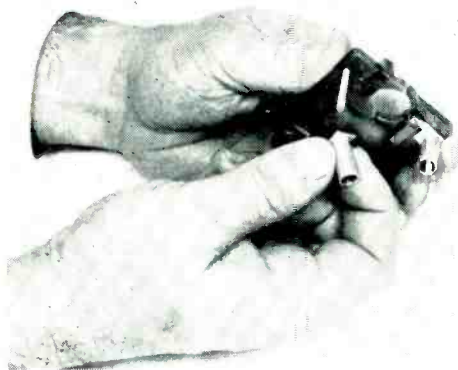


Fig. 7 — The aluminum spacers are used to hold the field in the correct position.

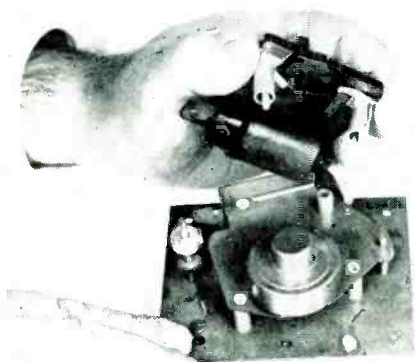


Fig. 8—Fit the field down over the rotor holding aluminum spacers with fingers so they won't slip off.

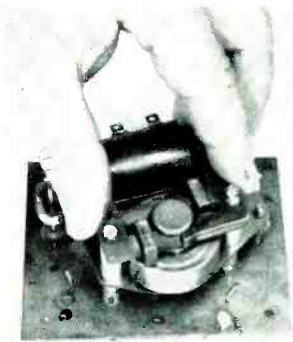


Fig. 9—Press into position, replace holding screws and the job is done.

Telechron clock and timer service stations do not stock them for resale.

#### How To Replace A Rotor Unit

1. Rotor Unit, heart of the timer's motor, is recognized by its small-nosed sealed case.

2. Motor is detached from base plate by removing two screws.

3. Rotor And Field Assembly, in left hand, lifts out in one piece.

4. To Remove Rotor from field, press neck of rotor with thumb. It slips out smoothly and easily.

5. Disassembled Motor shows rotor in right hand, field assembly in left.

6. New Rotor is fitted into position in base plate. Be sure gears mesh and rotor is pressed flat against base plate.

7. Aluminum Spacers make sure field assembly is in proper position.

8. Hold Spacers on screws with fingers while fitting field to rotor nose.

9. Press Field firmly over rotor nose and tighten screws. That's all.

10. Adjusting Alarm. a) Place long-nosed pliers on horizontal flat of vibrator. b) Energize field. c) Bend vibrator slightly up or down to make sound louder or softer.


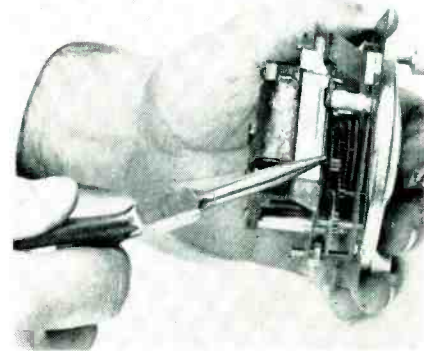


Fig. 10—Long nosed pliers are placed on the horizontal flat of the vibrator for adjustment. Energize the field. By bending the vibrator slightly up or down will increase or decrease the tone to the proper sound.

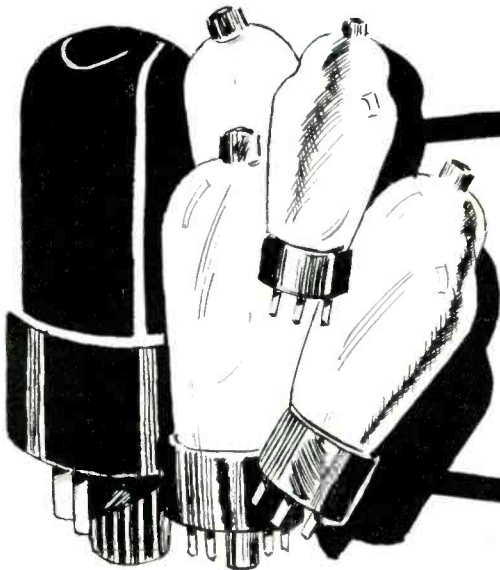


# NEW TUBES

## CBS-Hytron Type 24TP4

The CBS-Hytron type 24TP4 is a 24" rectangular, 90°, all-glass, magnetically focused, picture tube providing an effective screen area of over 370 square inches.

Other features of the tube are:

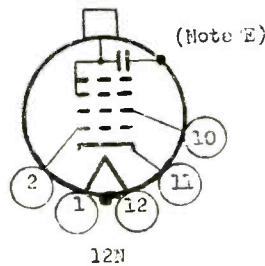
1. An aluminized screen for increased brightness.
2. Spherical filter-glass face plate.
3. Single ion-trap gun design.
4. External conductive coating which serves as a filter capacitor.



Tube basing diagram of 24TP4.
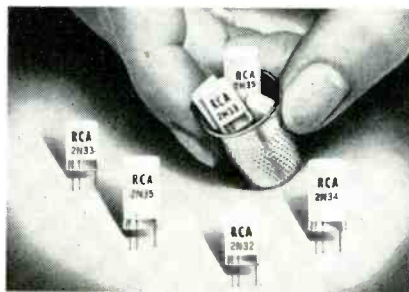
## RCA Transistors

RCA's commercial entry into the transistor field, after years of extensive research and development on semiconductors, is marked by the introduction of four types of germanium transistors—two point-contact and two junction.



RCA's new transistors.

Type 2N32 is a point-contact transistor intended for use in pulse or switching applications where an operating frequency for voltage-gain cutoff of 0.9 *mc*, an operating frequency for current-gain cutoff of 2.7 *mc*, and a high current amplification factor are important design considerations.

Type 2N33 is a point-contact transistor intended for use in oscillator service at frequencies up to 50 *mc*.


Types 2N34 and 2N35 are junction transistors of the p-n-p type and n-p-n type, respectively. Both types are intended for use in low-power, audio-frequency applications. These transistors operate at extremely low voltages, have a current amplification factor less than but approaching unity, and provide high operating power gain—features of primary importance in audio-frequency amplifier applications.

Each of the four types has a base with three small pins in line and spaced to provide mechanical indexing for socket insertion.

A copy of the 8-page booklet describing these new RCA Transistors may be obtained on request from Commercial Engineering, RCA Tube Department, Harrison, N. J.
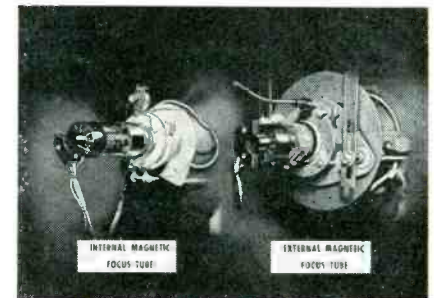
## GE Internal Magnetic Focus Tube

For the first time, permanent magnets are being built into new television picture tubes, thereby eliminating the need for external focusing controls



Comparison between new and old tube focus requirements.


and decreasing production costs by discarding three assembly units.

In a new General Electric TV 21JP4 tube displayed at the 1953 meeting of

[Continued on page 61]

GENERAL DATA		
Heater voltage	8.3 10%	volts
Heater current	0.8	ampere
Average direct interelectrode capacitances		
Grid-No. 1 to all other electrodes	6	uuf
Cathode to all other electrodes	5	uuf
External coating capacitance (Note E)	250 min. 400 max.	
Phosphor		No. 4 white
Fluorescence		medium
Persistence		magnetic
Focusing method		diagonal 90°
Deflection method		
Deflection angle (approx.)	17 1/8"	
Face plate light transmission (neutral density filter) (approx.)	72%	
MECHANICAL DATA		
Overall length	21 1/8 3/8"	
Outside diagonal	24"	
Screen width (bogey)	21 7/16"	
Screen height (bogey)	17 1/16"	
Cap	Recessed small cavity (11-21)	
Base	Small shell duodecal 5-pin (B3, S7)	
Biasing	JETEC designation 12N	
Mounting	any	
ELECTRICAL DATA		
Maximum Ratings (Design-Center Values)		
Anode voltage	20,000 d-c max. volts	
Grid-No. 2 voltage	500 d-c max. volts	
Grid-No. 1 voltage		
Negative bias value	125 d-c max. volts	
Positive bias value	0 d-c max. volts	
Positive peak value	2 a-c max. volts	
Peak heater cathode voltage:		
Heater negative with respect to cathode (Note A)	180 max. volts	
Heater positive with respect to cathode	180 max. volts	
Grid-No. 1 --circuit resistance	1.5 max. volts	
JETEC Test Conditions		
Anode voltage	11,000 d-c	volts
Grid No. 2 voltage	300 d-c	volts
Grid No. 1 voltage (Note B)	-33 to -77 d-c	volts
Focus Coil Current (approx.) (Note C)	110 10 d-c	ma
Ion-trap current (Note D) (approx.)	85 50%	d-c ma

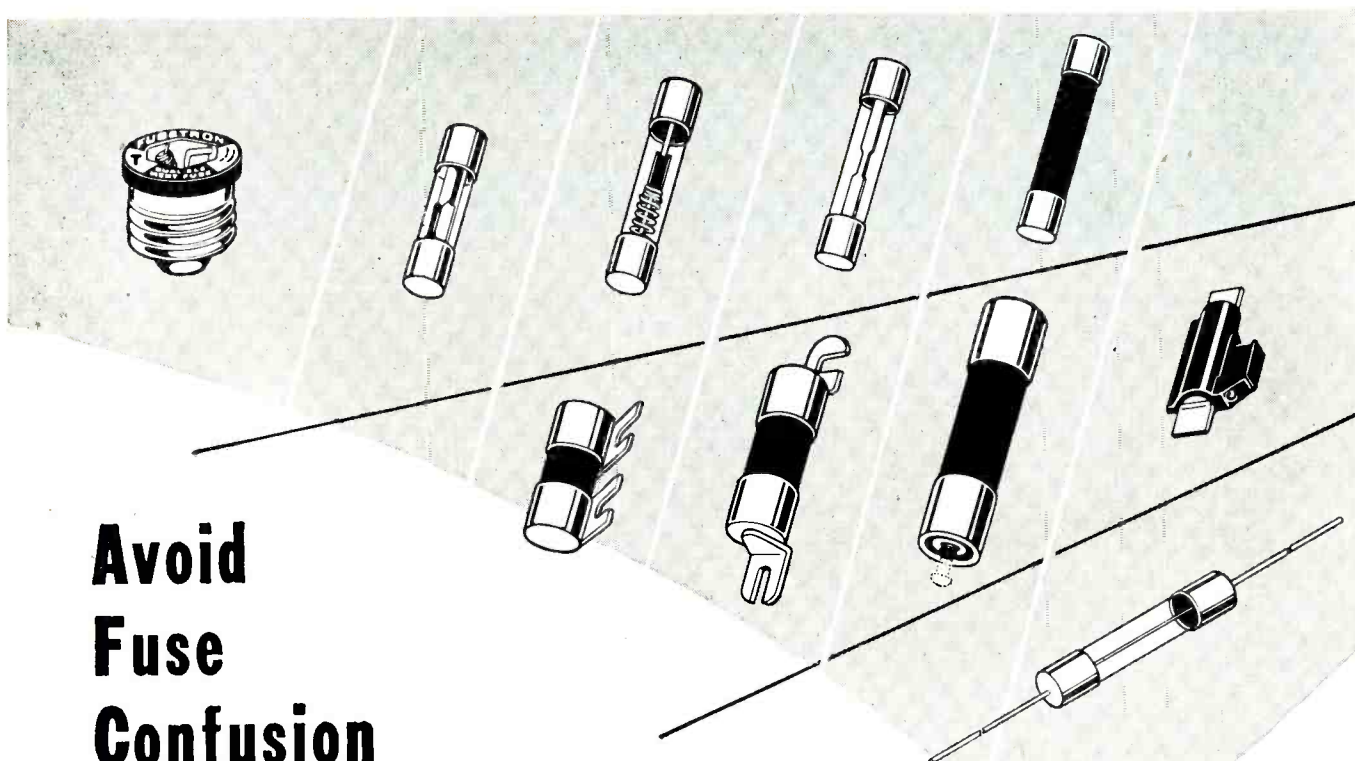Characteristics chart of CBS-Hytron type 24TP4.



**Avoid  
Fuse  
Confusion**

# Standardize on **BUSS** for *every*

protection need in TELEVISION • RADIO • RADAR • INSTRUMENTS • CONTROLS • AVIONICS

**BUSS** is the one dependable source for any fuse you need: standard type, dual-element (slow-blowing), renewable and one-time types...in sizes from 1/500 amp. up.


To make sure the highest standards of quality are maintained, every BUSS fuse is electronically tested. A sensitive testing device automatically rejects any fuse that is not correctly calibrated, or not right in all physical dimensions.

## Why Risk Your Reputation?

Give your customers the fuse they know. For more than a third of a century the BUSS name has been famous for dependable protection in homes, in industry and on the farm.

BUSSMANN MFG. CO., Division McGraw Electric Company  
University at Jefferson St. Louis 7, Mo.

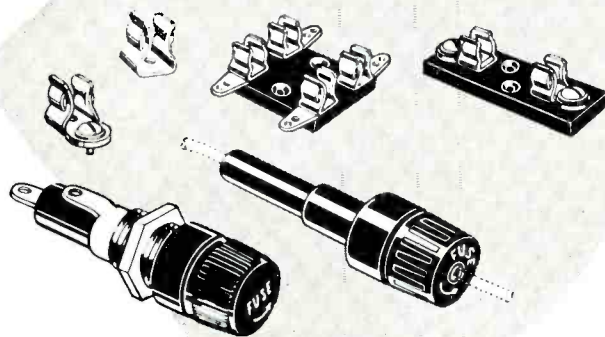**PLUS** a complete line of fuse clips, blocks and holders....



**FOR MORE INFORMATION — Mail this Coupon Today.**

BUSSMANN Mfg. Co. (Division of McGraw Electric Co.) 8D-953  
University at Jefferson, St. Louis 7, Mo.

Please send me bulletin SFB containing facts on BUSS small dimension fuses and fuse holders.

Name \_\_\_\_\_


Title \_\_\_\_\_

Company \_\_\_\_\_

Address \_\_\_\_\_

City & Zone \_\_\_\_\_ State \_\_\_\_\_ 953

# CIRCUIT COURT

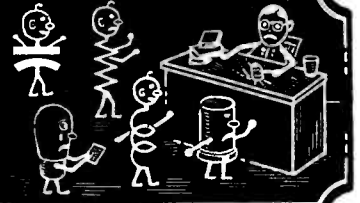

## Capehart CX-37-AGC


This *agc* system while containing many features common to all keyed *agc* systems also has some which are unique. The *agc* tube is a 6AU6. The grid of this tube is *dc*-coupled to the plate of the first video amplifier tube. The signal at this point is sync phase positive. The screen voltage of the first video amplifier is supplied from +300 volts through R241 and the *agc* control R238. By varying the screen voltage on the video amplifier, the amplification of that stage and therefore the amount of signal led to the grid of the *agc* tube can be set.

The plate of the *agc* amplifier is pulsed with a 700 volt positive pulse through a winding on the width coil. The pulse width is that of the re-trace time of the horizontal deflection network. Since the horizontal pulse is so placed in time that it arrives during horizontal re-trace, the amplifier only operates during that portion of the video signal containing the horizontal sync pulse.


During the time this tube conducts, C403 is charged negatively. When the pulse is over and the tube stops conducting C403 discharges through R406 and R407. This develops a voltage across these resistors which is negative with respect to ground and can be applied as bias to the *if* and *rf* tubes. The amount of charge on C403 is determined by the amplitude of the sync signal and the resulting discharge voltage which is used for bias is therefore proportional to the received signal.

Bias for the *rf* amplifier is taken off the top of R406 and R409. Bias for the *if* stage is taken off the junction of the two resistors. The diode section of a 6BF6 tube is used as an *agc* clamp. The plate of this diode is connected to the *rf* bias point. It is also connected to R409 and R410 which return to +300 volts. With a weak signal input, this diode keeps the *rf* bias at or about zero volts. If the signal is large the voltage developed across R406 and R407 becomes sufficiently negative to cause the diode to be cut off. With the diode negative the full bias can be developed at the *rf* point and the *rf* amplifier is controlled by the *agc*. The

[Continued on page 70]

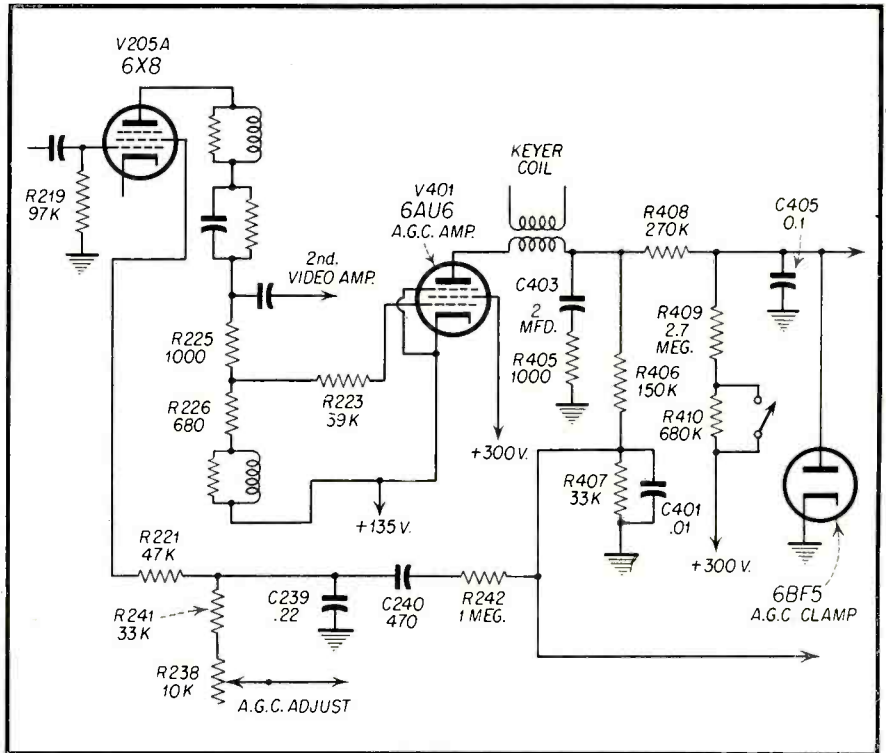

Partial schematic of CX-37 *agc* System

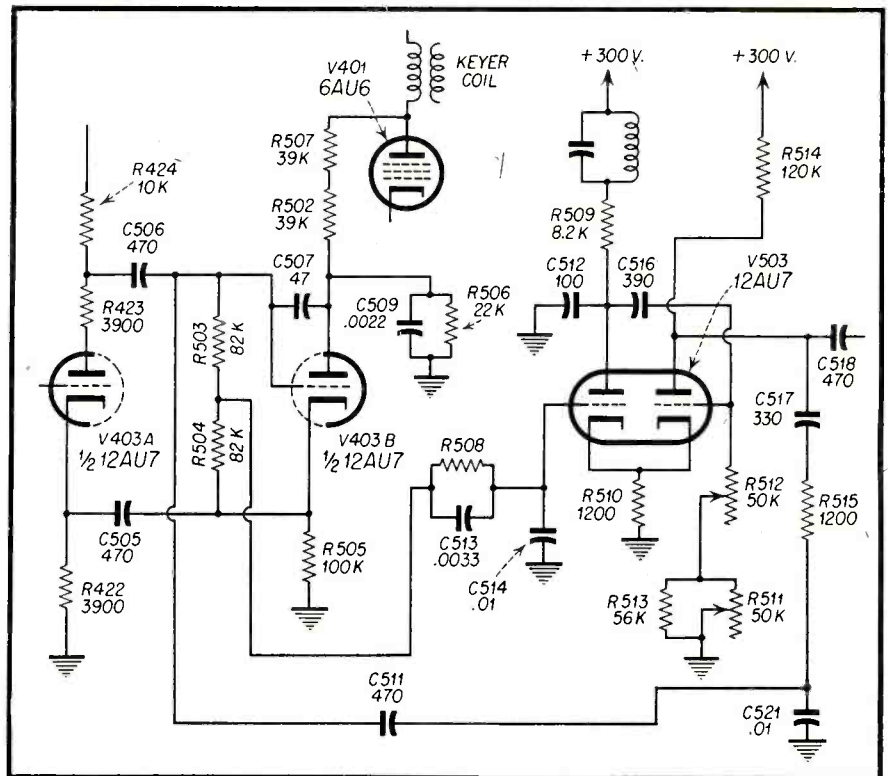

Partial schematic of CX-37 horiz. osc. and afc

# 12 reasons why it pays to replace with SYLVANIA PICTURE TUBES

## Independent laboratory tests show these 12 outstanding qualities of Sylvania Picture Tubes

- |   |   |
|---|---|
| 1. No tube failures (after 1500 hours).                   | 7. No stray emission.                   |
| 2. No trend toward slumping emission or low light output. | 8. Low electrical breakdown.            |
| 3. No excessive leakage.                                  | 9. Very good color control.             |
| 4. No excessive gas present.                              | 10. Excellent spot centering.           |
| 5. Excellent grid control.                                | 11. Low screen burning (no rejections). |
| 6. Excellent emission characteristics.                    | 12. Excellent physical conditions.      |

**Only Sylvania showed  
no tube failures**

Here is proof that Sylvania Picture Tubes are *first* in long life and *finest* in all around performance of all tubes tested.

The above record was established in comparison tests of the tubes of 9 different manufacturers. All tests were conducted under identical conditions by an outside testing agency.

Set owners everywhere are being told again and again about Sylvania's superiority on the big, nationwide TV show "Beat the Clock."

### The Picture Tube for Reliable Replacement

Of course, the name Sylvania has always stood for highest quality. Now, more than ever before, Sylvania Picture Tubes mean better business for jobbers and service-dealers alike. If you would like the full story of these recent tests to show your customers how Sylvania Picture Tubes won over all others tested, simply mail the coupon now.



Send  
for this  
report



Sylvania Electric Products Inc.  
Dept. 3R-2209, 1740 Broadway, N.Y. 19, N.Y.

Please send me the official report of the tests made on Sylvania Picture Tubes in competition with other makes.

Name \_\_\_\_\_  
Company \_\_\_\_\_  
Street \_\_\_\_\_  
City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

# SYLVANIA

LIGHTING • RADIO • ELECTRONICS • TELEVISION

In Canada: Sylvania Electric (Canada) Ltd., University Tower Bldg.  
St. Catherine St., Montreal, P. Q.

# PERSONNEL NOTES

Meet the key men responsible for the manufacture and distribution of servicemen's products.

Appointment of Edwin A. Freed as Manager of Operations of General Instrument Corporation's headquarters plant in Elizabeth, N. J., was recently announced. Mr. Freed will continue to direct sales and will be in complete charge of all operations at the home plant. He joined General Instrument in 1951 as Sales Manager, after nine years with RCA where he was Manager of Sales of Component Parts.



Douglas Carpenter (left), has been appointed Chief Antenna Development Engineer of the JFD Manufacturing Company, Inc. Doug is inaugurating an expanded engineering program at JFD. He formerly served as Chief Engineer for the Vee-D-X Division of the La Pointe Plasmocold Corp. Jim Hall (right), has been appointed Associate Antenna Test Engineer, assisting in development and field testing of antennas. Jim previously was associated with the CAA and Aviation Electronics operations of the Navy, both in the capacities of design and research engineer.

Karl W. Jensen, Vice President of Jensen Industries, Inc., Chicago, was elected Chairman of the Association of Electronics Parts & Equipment Manufacturers. Jensen also was named EP&EM representative on the Board of Directors of the Radio Parts & Electronic Equipment Shows, Inc., through which the association co-sponsors the annual Electronic Parts Show with four other trade groups.



Les Wildberg, President of Leader Electronics, Inc., of Cleveland, Ohio, recently announced plans for his firm to enter into the manufacture and sale of TV equipment. It can be reported at this time, however, that the items will be primarily for consumer use, and that national sales are planned. Wildberg has been a well-known figure in the electronics field for over 30 years. He was the founder and former president of Radiart Corporation.



King Dendy, whose recent appointment to the research staff of the engineering division of the Edwin I. Guthman Company is shown (left), being welcomed to the department by chief engineer Frank A. Iverson. Mr. Dendy, who formerly was head of research and development for PCA Electronics, Inc., will specialize in delay lines and pulse transformers for the Guthman Company.




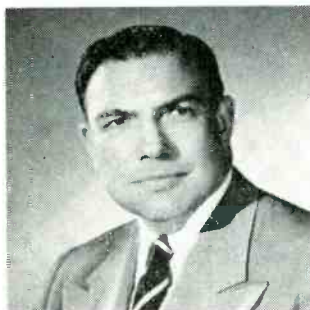I. M. J. Kaplan has been appointed Vice-President of Copperweld Steel Company with headquarters in Pittsburgh. Prior to his new assignment Mr. Kaplan was Manager of Sales—Special Products—of the Wire and Cable Division at Glassport, Pa. For over 12 years he has served in important capacities with the Wire and Cable Division as well as the Steel Division at Warren, Ohio.



Announcement has been made by Snyder Manufacturing Company, of the appointment of John Schweighauser as a company Antenn-engineer. Among his duties, Mr. Schweighauser will call upon distributors and service dealers in the capacity of a sales engineer. He will acquaint the trade with new Snyder products and also do work on engineering problems. In addition, he will be engaged in field survey and sales promotion activities.


Grady L. Roark of Schenectady has been appointed Manager of Marketing for the General Electric Company's Tube Department, with headquarters here, it was recently announced. Mr. Roark has been manager of equipment tube sales for the department since last December, before which he was central regional sales manager with equipment tube sales with headquarters in Chicago. He joined G.E. on the company's test engineering program in 1933.



Sylvania Electric Products, Inc., announced recently the appointments of Ralph R. Shields (left), to the newly created post of Product Sales Manager of television picture tubes and D. W. Gunn (right), to the new post of Assistant General Sales Manager, Radio Tube and TV Picture Tube Sales. Mr. Gunn has been a member of Sylvania since 1931, and Mr. Shields joined in 1948. Both have worked successively at various engineering and supervisory capacities within the organization.




Vinton K. Ulrich (right), has joined the David Bogen Company as General Sales Manager. It was announced by David Bogen, President, who also reports that Mortimer Sumberg (left), has been promoted to distributor Sales Manager. Mr. Ulrich, formerly renewal sales manager of the National Union Radio Corp., brings to his new position an unusual combination of sales and engineering experience. Mr. Sumberg has been identified with Bogen jobber sales for more than four years. He has been active in the electronics field for nearly twenty years.

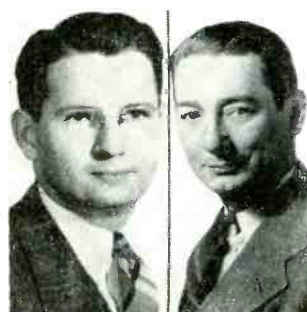

Robert L. Klabin, Controller of General Instrument Corp., major producers of television, radio and electronic products, has been elected by its management to manage the Company's new and expanding Sickles Division plant at Danielson, Conn. The new Division Manager has served General Instrument since 1935, progressing as Budget Director, Assistant to the President and Controller. Mr. Klabin is a member of several technical and management associations.





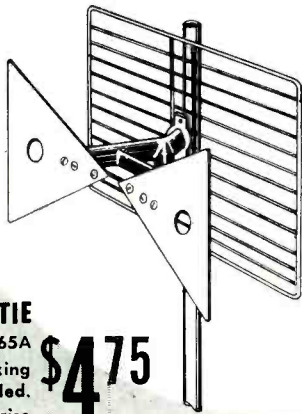


**Admiral BOW TIE**

UHF Antenna, No. AN65A

Each antenna furnished with stacking bar. Mast mounting bracket included. Mast not included. Suggested List Price

**\$4.75**

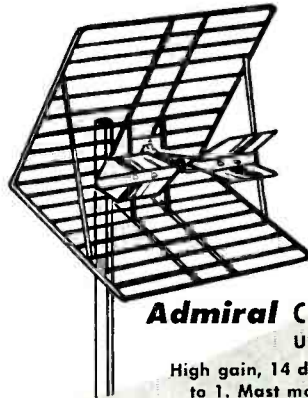

**Admiral CORNER REFLECTOR**

UHF Antenna No. AN56A

High gain, 14 db. Front to back ratio 15 to 1. Mast mounting bracket included. Mast not included. Suggested List Price

**\$9.95**

# Admiral all-channel antennas


**HIGH GAIN**

**LOW COST**

Now you can make an extra profit on installations using these high gain UHF antennas. In good signal areas, the Admiral Bow-Tie No. AN65A gets excellent reception on any of the 70 UHF channels...and lists for only \$4.75! For troublesome locations, where ghosts, reflections and interference are encountered, install the Admiral Corner Reflector Antenna No. AN56A. It lists for only \$9.95.

Both these antennas are made with aircraft aluminum antenna elements and vibration-proof reflectors. Both come completely assembled, ready to mount. "A-frame" insulators provide plenty of free air space around elements. The units have high mechanical strength, low wind resistance, and are treated to resist weathering. They can be easily fastened to existing masts and towers.

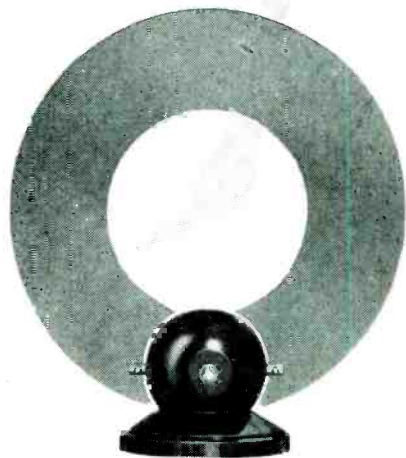Where an indoor UHF antenna is needed, give your customer the Admiral Target No. 94A10-7. Smartly styled in rose-gold colored anodized aluminum with mahogany phenolic base, it stands only 10 inches high. The base is weighted and felt padded...can be placed on top of receiver...picks up all UHF channels. Order by part number from your Admiral distributor.



**Admiral TARGET**

Indoor Antenna No. 94A10-7

Complete with lead-in


Suggested List Price

**\$4.95**


**Admiral Corporation**

Accessories and Equipment Division • Chicago 47, Illinois

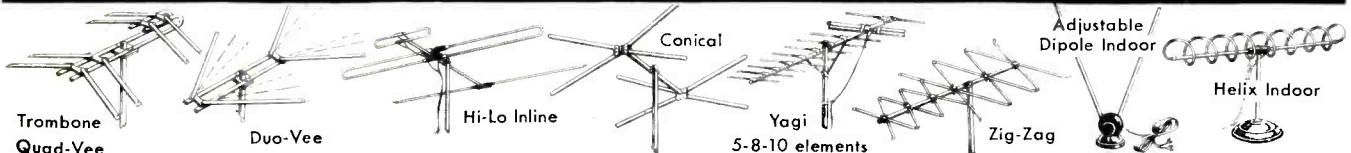**A COMPLETE LINE OF ADMIRAL TV ANTENNAS . . . NOW AVAILABLE FROM YOUR ADMIRAL DISTRIBUTOR**




# New

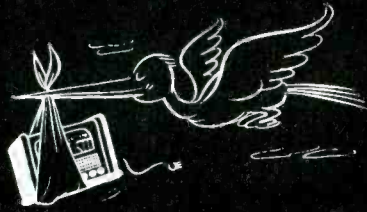

# Products
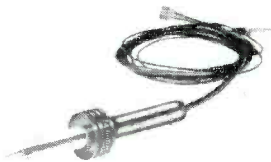
### TV Safety Test Probe

Precision Apparatus Co., Inc., announces that a patent has been issued on the "Precision" Series TV High Voltage Safety Test Probe. The product was developed to afford convenient and direct measurement facilities up to 60,000 volts d.c., with complete safety to the operator, with utmost simplicity, speed and accuracy. These probes provide direct kilovoltmeter facilities for most high sensitivity test sets and vacuum tube voltmeters.



### Rack-Mounted Oscillograph

Du Mont Laboratories, Inc., announces that the Du Mont Type 304-AR Cathode-Ray Oscillograph is now available as a rack-mounted unit. The unit features built-in voltage calibration. The illuminated screen is specially calibrated for reading any portion of the signal directly in volts by a push-button control on the operating panel. The rack-mounted oscillograph requires only 8 3/4" vertically in a standard relay-rack.




### New HI-FI Speaker

The Oxford Electric Corporation announces a new, high-fidelity 15" speaker. Model #HF15LN has the following specifications and characteristics: Frequency range—50 to 10,000 C.P.S. Magnet Weight—14 oz. Alnico V; Power Rating—25 watts; Input Impedance 8 ohms; Voice Coil—1 1/2" diameter. The unit is attractively finished with a silver "hammerloid" enamel and has a blue pot cover.


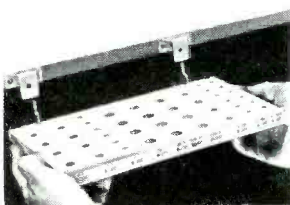
### Vari-Board Shelf Brackets

New brackets are announced by Vaco Products Co., which permit mounting a Vari-Board shelf to regular shelf edges anywhere in the store, as desired, when regular Vari-Board punched panel is not used as a backboard. Made of wood, 11" x 5 3/4" x 7/16" thick, the brackets are simply attached by screws to the regular stock shelf edge, as illustrated, and the shelf hooks inserted into the front bracket holes for supporting the unit.




### New Tube Britener

A universal TV tube britener has been developed by Perma-Power Co. Its isolation type transformer gives normal 6.3V to filament to relieve cathode short problems or 7.8V to increase cathode emission and restore lost brightness. Simple switch allows quick selection . . . unique design allows operation as constant voltage (parallel wired sets) or constant current (series wired sets) transformer.



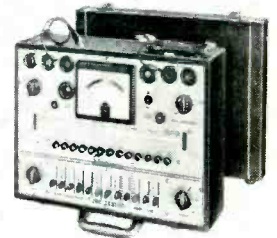
### Tube Tester

Manufactured by the Simpson Electric Company, the new Model 1000, features fast testing with convenient ohms readings for leakage and shorts. The unit will test any receiving tube including 9 pin miniatures and subminiatures with base arrangements in line or circle. The Model 1000 tests plate conductance. The dial indicates percentage of rated plate conductance, which is closely related to mutual conductance.


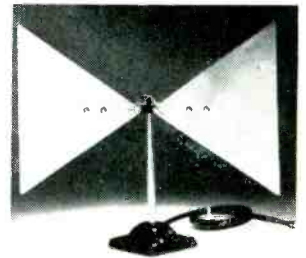
### UHF Indoor Antenna

The Brach Manufacturing Corporation has announced the introduction of their new uhf Indoor Antenna, the #483 Bow-Tie. The same design that is used on outdoor uhf Bow-Tie antennas has been applied to the #483 in order to insure the highest possible gain. The Bow-Tie elements are mounted on an attractive black porcelain base that gives the entire unit a modernistic finish.




### TV Set Roll-Around

Designed to add welcome mobility to present stationary television sets of the console variety is the new Telco TV Roll-Around, a product of Television Hardware Mfg. Co. The strong, rigid adjustable metal frame is equipped with heavy duty ball bearing casters that are smooth running and will not mar wood or composition floors. Constructed to fit under any floor model up to 30" x 24", the unit raises any set merely a half-inch from the floor.


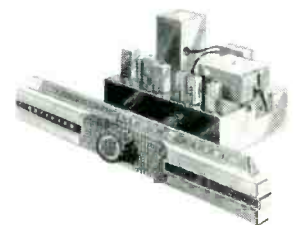
### Vu-Matic Control Unit

The Vu-Matic Control Unit combines Raytheon Manufacturing Company latest tuning discoveries with recently developed chassis elements. Principal advantage of the feature is that one knob tunes all 82 vhf-uhf channels and switches in vhf-uhf antennas, circuits, and extra amplifiers—all automatically. The Vu-Matic chassis also shuts out picture interference and stops oscillator radiation.



### IF Signal Booster

Grayburne Manufacturing Co., Inc., announces the production of their Model TSB-1, an I.F. signal booster for uhf and vhf. The unit, provides an extra stage of I.F. to amplify both uhf and vhf signals without switching. The booster, which is supplied in adaptor form, is installed in an existing tube socket and requires but one wire connection to ground. It is said to increase picture brightness, amplify signals over 20%, and clear "snow" effects.



# NEW



**TIGHTEST SEAL**  
LOCKS IN PERFORMANCE

**TOUGHEST SHELL**  
LOCKS OUT TROUBLE




**ATTRACTIVE YELLOW MOLDED PLASTIC SHELL**

Non-inflammable. Will not burn or melt under soldering iron or flame.

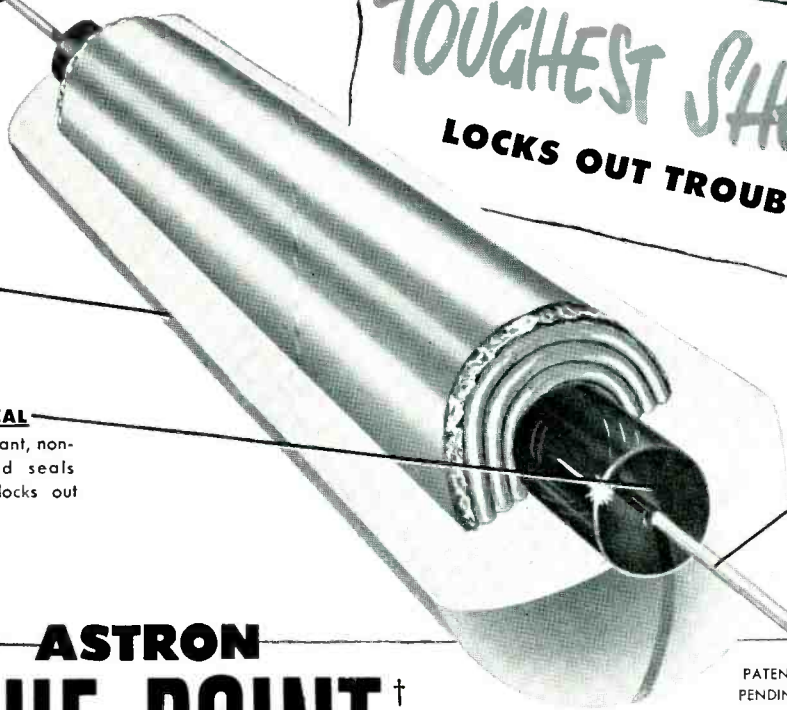**BONDED SEAL**

Positive, heat resistant, non-inflammable bond seals leads and shell, locks out humidity.

**FIRMLY SECURED LEAD**  
Can't be pulled out, even under soldering iron heat.



PATENT PENDING

## ASTRON BLUE-POINT<sup>†</sup> MOLDED PLASTIC PAPER *Capacitors*


THE NEWEST ADDITION  
TO THE **SM<sup>†</sup>** LINE

Yes, the ASTRON BLUE-POINT's *tighter seal* and *tougher shell* give you heat and moisture protection to a degree never before possible—providing a longer life and greater dependability than has ever been achieved in a molded plastic capacitor! BLUE-POINT is a capacitor you can rely on *completely*, under every condition.

BLUE-POINT is suitable for continuous operation at 85°C. The bonded seal uses a special thermo-setting, heat-resistant, non-inflammable bonding agent—*positive* protection

against moisture. Solder leads as close to the capacitor as you like—they *won't* pull out! Every BLUE-POINT is clearly marked with voltage and capacitance, bears outside foil identification. Every BLUE-POINT is *tested* and *guaranteed*. Look for the ASTRON BLUE-POINT when you buy capacitors from your jobber, or if he doesn't carry it, send us his name. Insist on ASTRON BLUE-POINT, the capacitor you *know* you can depend on. Order a supply today.

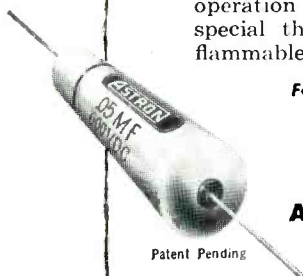For complete performance characteristics, specifications and listings, write for Bulletin AB-20A



Patent Pending

DEPEND ON—INSIST ON


ASTRON CORPORATION



255 Grant Ave., E. Newark, N. J.


†Trade Mark

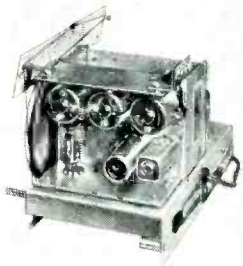Safety Margin capacitors for every radio, television and electronic use.



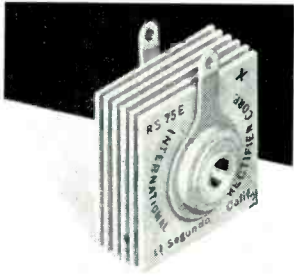
### UHF Cavi-Tuner

The "Cavi-Tuner" is now available from the Radio Receptor Co., Inc. Field tests indicate superiority of the unit in overall noise figure, image rejection, oscillator radiation and gain. The unit has shown unusual sensitivity and gives excellent reception in fringe areas. Some of the outstanding features are as follows: no moving electrical contacts; completely shielded construction; excellent frequency stability and uniformly broad bandwidth and high selectivity over entire tuning range.



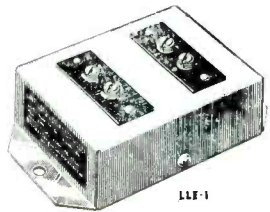
### New Selenium Rectifiers

International Rectifier Corporation has developed a complete line of selenium rectifiers for use in Radio, Television, TV Boosters, and uhf Converters. The rectifier shown in the photograph is a Type RS75E and is rated as follows: maximum input, 130 volts RMS; maximum peak inverse, 380 volts; maximum output current, 75 MA. A series resistor of at least 22 ohms is recommended as a current limiter when used with a capacitive filter.



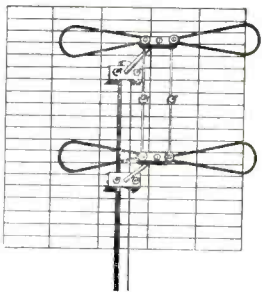
### TV Line Loss Equalizer

A new TV accessory for equalizing high and low channel losses in transmission lines is now available from Blender-Tongue Laboratories. Model LLE-1, Line Loss Equalizer, maintains balanced signal levels, and prevents over-loading and cross-modulation by offsetting high channel losses with attenuation varying from 17 db on Channel 2 to less than 1 db on Channel 13. May be inserted at any point in the transmission line.



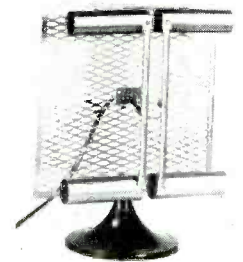
### Mi-Tee-Ray Screen Antenna

Model MR-S, produced by Fretco Inc. designed for channel coverage 2 to 83 with ultra high gain. The front to back ratio is 50 to 1 and is also used in ghostly areas where others fail. A special ingredient is being used in the insulators to reduce any possibility of dielectric loss. The construction is wind and ice proof. This antenna needs no assembly, but comes collapsed.


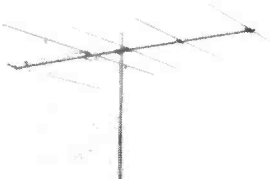
### UHF Indoor Antenna

Tricraft Products Co., now offers a new uhf indoor antenna consisting of a two element array with a reflector. The unit, measuring only 12 inches from side to side, considerably less than the size of most indoor vhf antennas, may be conveniently placed atop the T. V. receiver. The antenna covers all 70 uhf channels and provides excellent impedance match over the band.



### 2-Channel Twin-Tuned Yagi

Channel Master Corporation has announced the development of Model No. 525, an antenna peaked for both channels 2 and 5. The antenna, featuring a transformer-type dipole, has a gain of 6 1/2 db on Channel 2 and almost 8 db on Channel 5, for a single bay. Stacking provides substantially higher gain. Directivity and rear rejection are excellent. Antenna operates with just a single transmission line, and there is no switching necessary.

### TV Voltage Regulator.

Recently released by Perma-Power Company, this voltage regulator has been designed to insure maximum performance of any television set by returning full height and width of picture when low line voltage distorts picture. Features include . . . reduction of tube failures; increasing of set sensitivity and elimination of intermittent sync and oscillator drift caused by low line voltage.



### UHF Converter

A completely new uhf converter is being introduced by the Walsco Electronics Corporation. The Walsco unit is said to be able to amplify the signal almost three times while it converts. Tests revealed that the unit will offer a lower noise level. Exclusive Turretune feature of this converter is the new turret-type band spread tuning unit with a double tuned pre-selector that has been labeled as an entirely new concept in uhf tuning. This tuning unit has a constant lc ratio. Walsco Imperial covers the entire uhf frequency spectrum.



### 3-D Phonograph Music

Webster-Chicago Corp., announce their new high-fidelity model. The Webeor three-dimensional "Musicale" provides a uniform audio response of from 50 to 12,500 cycles. In contrast to the average phonograph's reproduction of a maximum of 6,000 cycles. The unit has three speakers that provide what Webeor engineers describe as stereophonic sound—full reproduction of all frequency cycles in all parts of the room.



### Miniature UHF Capacitor

JFD Manufacturing Company, Inc., announces production of the "Mighty Midget" piston type variable trimmer capacitor for uhf television set manufacture and replacement parts requirements. Some features of the JFD model VC3-G are as follows: one inch overall length at maximum capacitance; capacitance range 1.0 to 8.0 mmf; universal mounting design fits any uhf receiver.




### TV Lead-In Wall-Feed

Production of a new type weather-proof television transmission line wall entrance for house and trailer has been announced by Mosley Electronics, Inc. Product will accommodate either flat or tubular line and will completely seal out rain and snow. The new Wall-Feed permits the entrance of such wire directly under the eave into the attic.


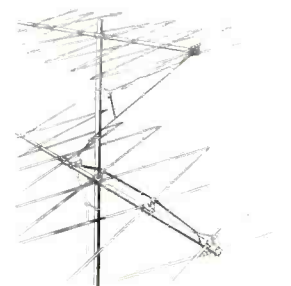
### Zig-Zag Re-Entrant Network

Improved performance of the Zig-Zag TV antennas has been announced by Trio. The Trio Re-Entrant Network shows no measurable loss when stacking for all channel—single feed-line operation. It is a method of broadening the impedance characteristics of a multi-channel antenna to the point where that impedance remains practically constant throughout the channels covered.



# RCP VTVM

## Model 655

**READS PEAK-TO-PEAK  
VOLTAGES DIRECTLY**

### ACCURATE MEASUREMENT OF COMPLEX WAVESHAPES

#### SINE WAVE

RMS or Peak-To-Peak...  
Useful and Necessary—Read  
Directly With Model 655

#### PEAKED SAWTOOTH WAVE


TV Horizontal Signal...  
Peak-To-Peak Reading Re-  
quired—Easily Done Directly  
with the Model 655.

#### PULSE WAVE

TV Horizontal Deflection...  
Peak-To-Peak Measurements  
Needed—Read It Directly  
on the Scale—Model 655.
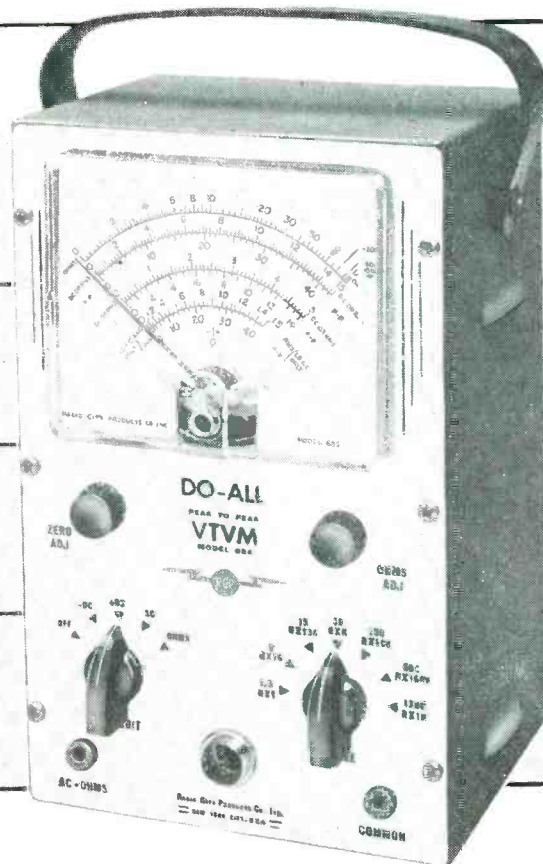
#### COMPOSITE VIDEO WAVE

Video Amplifier... Peak-To-  
Peak Measurements A Must  
—Do It Directly With The  
Model 655.



*Quickly... Accurately*

**DO-ALL Model 655.**

**ONLY \$59.50**

... gives a true reading measurement of complex and sinusoidal voltages with necessary peak-to-peak or RMS value read directly, for the analysis of waveforms in video, sync and deflection circuits.

Now TV efficiency is given greater effectiveness because sets can be serviced as the manufacturers say—the peak-to-peak way. The combination of this P. to P. meter and service notes to match, take the guesswork out of service and speed up your service operation.

Versatility of measurement, built into each Model 655, serves a variety of industrial applications in the service of vibrator power supplies, AC generators and all equipment utilizing any type of waveform or DC.

Match the Model 655 with any peak-to-peak VTVM—You will find that comparable performance can only be found

in much higher priced instruments. Of high impedance design, the Model 655 makes use of an electronic balanced push-pull circuit and peak-to-peak rectification. The result is an absence of circuit loading, waveform error or frequency distortion.

This handsome looking unit has a brushed aluminum panel, etched for durability and uses an attractive clear plastic meter. Comes complete with our new "RCP SOLDERLESS TEST LEADS" for operation on 105 to 125 V AC.

#### FOR TELEVISION SERVICE AND INDUSTRIAL MAINTENANCE

- PEAK-TO-PEAK AC measurements of from .2 V to 4200 V on 7 ranges.
- AC RMS measurements of .1 V to 1500 V on 7 ranges.
- DC measurements of from .02 V to 1500 V on 7 ranges.
- RESISTANCE measurements of from .2 ohms to 1000 Megohms on 7 ranges.

Remember You can do more with a "DO-ALL".

See It at Your Parts Distributor. Write Dept. SD9 for RCP '53 Catalogue.

**RADIO CITY PRODUCTS CO., INC.**

152 WEST 25th STREET • NEW YORK 1, N. Y.



# KESTER



# SOLDER

## TRADE FLASHES

[from page 13]

years of research, in combination with RCA Victor's new Orthophonic Sound phonograph records, designed to achieve the utmost in wide range sound reproduction.

### La Pointe Purchases Printed Circuit Company

LaPointe Electronics Inc. has purchased a 95 per cent interest in Circuitron, Inc., a New Jersey corporation which is engaged in the manufacture of printed circuits, it was announced by Jerome E. Respass, President. "By acquiring and managing Circuitron," Mr. Respass stated, "LaPointe is assured of a continuing supply of the printed circuits used in the Vee-D-X Mighty Match and other television accessory equipment. In addition," he said, "LaPointe will manufacture printed circuits for a wide variety of fields within the electronic industry."

### Hallicrafters Builds New Plant

The Hallicrafters Company have announced that construction had begun on a new \$400,000 plant in Toronto, Canada.

The new plant will be a one story brick building of modern design and is expected to be completed in October.

### RCP Offers Special Purchase Plan

Radio City Products Company, Inc., has just introduced to their distributors a plan that makes it very easy to finance carrying an adequate stock of their products. The new plan will permit the jobber to pay for stock over a period of 90 to 150 days without any interest. Trade Acceptances will be the medium to cover such purchases. In addition, the distributor has a guarantee of a liberal obsolescence protection.

### NEDA Battery Index

National Electronic Distributors Association reports continued enthusiasm among radio-TV servicemen, distributors and others regarding the new NEDA Battery Index. Single copies are still available from National Electronic Distributors Association, 228 North La Salle Street, Chicago 1, Illinois.

### General Instrument Meeting

General Instrument Corp., complete the first quarter, ended May 31, with record sales, Abraham Blumenkrantz, Chairman of the Board, told the annual meeting of stockholders. Net profit was the greatest for any initial quarter in the 30-year history of the company, he added. The company has broadened its activities in such fields as components for transistor application, printed circuits, color TV equip-

**Biggest AUDIO and HI-FI Event of the Year!**

# AUDIORAMA 1953

Presented by **THE AUDIO FAIR**

**20,000 HI-FI FANS WILL VISIT IT! YOU, MR. SERVICE DEALER, MUST SEE IT, TOO!**

The AUDIO FAIR is the largest and most concentrated exhibition of Audio Equipment ever held under one roof. More than 125 manufacturers will be represented, and every up-to-the-minute development will be seen and heard.

At least 20,000 serious Hi-Fi customers—including Governmental and Military Agencies, Broadcast Engineers, Recordists, Sound-on-Film Men and Hobbyists will attend this important event. Here is the once-in-a-year opportunity for you to view all the equipment from all important manufacturers; here is an opportunity for you to make profitable contacts; here is an opportunity to learn more about and earn more from the fastest growing consumer interest in the country—high fidelity.

Come—and Bring the Family!

P.S. . . . New York is a fine place to visit in October

SPONSORED BY



The General Public is invited to Attend

**NO ADMISSION CHARGE**

AUDIORAMA is presented by THE AUDIO FAIR HARRY N. REIZES, Marketing Director, 67 W. 44 St., N. Y.

**TIME:**  
Oct. 14, 15, 16, 17  
**PLACE:**  
Hotel New Yorker  
New York City  
Registration On  
5th, 6th  
and 7th Floors

ment and electronic materials for the defense program, Mr. Blumenkrantz stated. In this connection, he emphasized: "G. I. is fully prepared right now to play an important role as a component manufacturer for the makers of color TV sets."

#### G.E. Ready For NTSC Color Signals

The General Electric Company has announced that its television transmitting equipment will satisfactorily rebroadcast network color TV programs under the compatible system now being recommended to the FCC by the National Television System Committee, without any additional equipment, provided the network signals arriving at the local station are of reasonable quality. For color reception, only minor changes must be made to existing equipment.

## TUBE NEWS

[from page 50]

the Institute of Radio Engineers, the external ion trap, focusing unit, and mechanical support have been replaced by a simplified ion trap and focusing unit, both built within the tube. Key to this new design are the tiny but powerful Carboloy permanent magnets now encased within the tube.

Size of the Carboloy Alnico 5 magnet used in the ion trap has been reduced to one-tenth that of the magnet previously employed. The new magnet is  $\frac{1}{8}$  inch in diameter and  $\frac{3}{8}$  inch in length. The former Carboloy magnet was rectangular, approximately  $\frac{1}{2}$  inch in length,  $\frac{1}{4}$  inch thick and  $\frac{3}{8}$  inch wide.

The internal focusing device employs three Carboloy permanent magnets, measuring only  $\frac{1}{4}$  inch in diameter and  $\frac{5}{8}$  inch long. Optimum clarity of focus is achieved through factory fixed focusing which eliminates the necessity for any external focusing control requiring adjustment by the set user.

#### Sylvania Type 40B2

A new horizontal deflection stabilizer tube, Type 40B2, has been released by the Radio Tube Division of Sylvania Electric Products Inc.

The Type 40B2 is similar in application to earlier released Sylvania Type 40A1. However, the new 40B2 has different voltage and current ratings, thus providing more versatile circuit design.

In circuits designed for its use, the 40B2 serves as the cathode bias resistor for the horizontal output tube. The non-linear resistance characteristic of the filament tends to hold the cathode current of the horizontal output tube



Sylvania Type 40B2.

relatively constant despite line voltage variations. The result is a stabilized horizontal deflection and second anode voltage. It also becomes possible, therefore, to operate the horizontal output tube near full scan capabilities at low line voltage without subjecting it to operating conditions which exceed the maximum ratings at high-line voltage. This insures greater reliability and trouble-free operation.

The Sylvania Type 40B2 is contained in a T-9 bulb. Average operating conditions are 40 volts at 150 ma.

## RADIO and TV MEN ASKED FOR THIS KIT!



- 7 Nut Drivers
- 2 Phillips Drivers
- 3 Regular Drivers
- and
- Extension
- In One Package

**VACO**  
RT-14  
**SERVICE KIT**

You'll like this kit! Sales prove it! The RT-14's built-in convenience, easy storage and versatility have made it a favorite in both radio and TV fields. In one package you have all the nut drivers, Phillips and regular drivers you need for almost any situation. And every driver fits the one, heavy duty Vaco shock-proof, break-proof handle . . . fits the famous Vaco 6" extension that enables you to get into awkward recesses and tight spots. For full details, see your jobber or write, today!

#### Extension Doubles the Use of Each Driver!



Nut Driver—Less Extension—  
Length 3" out of handle



Regular or Phillips Screw Driver  
Less Extension—  
Length 3 $\frac{3}{4}$ " out of handle



Nut Driver—With Extension—  
Length 8" out of handle



Regular or Phillips Screw Driver  
With Extension—  
Length 8 $\frac{3}{4}$ " out of handle

**VACO PRODUCTS CO., 317 E. Ontario St., Chicago 11, Ill.**

In Southwest: 1325 McKinney Ave., Dallas 2, Texas  
In Canada: 204 Laurier Ave., W., Montreal 8, Quebec



# ASSOCIATION NEWS

## FRSMAP

At a recent meeting at Lily Lake, Luzerne County, the Federation of Radio Service Men's Associations of Pennsylvania was informed by Milian J. Krupa, President that the State's proposed licensing bill for Radio-TV technicians has been tabled for this session of the legislature. Also announced were plans to hold an Eastern conference here in January, 1954, to discuss television-radio servicing and related industry problems. Representatives of similar servicing organizations from Maine to Florida are expected to attend.

William Morgan, President of FRSMAP's Wilkes-Barre chapter, was appointed editor of the organization's news bulletin, with immediate publication being planned. Cities represented at the meeting included Philadelphia, Pittsburgh, Scranton, Altoona, Harrisburg, Williamsport, Hollidaysburg, Carbondale, Reading, Chambersburg, Wilkes-Barre and Steelton.

## TSDA

The Television Service Dealers Association of Philadelphia has launched a series of 18 newspaper advertisements promoting TSDA's members' facilities. The association headed by Louis J. Smith of Louis J. Smith Co., has voted unanimously to appropriate \$1,200 from their advertisement fund for this advertising campaign in the Evening Bulletin. Ad copy will be of the institutional type, promoting TSDA services and explaining to the reader the advantages of using qualified radio and television service dealers. A grievance committee also has been appointed to investigate any consumer complaints that may arise concerning members' service work. The association has set up offices at 6021 Ogentz Ave., with a central telephone system to channel all requests for service to the nearest member. A standard rate charge for all calls cleared through the office only has been established. Dave Krantz has been named chairman of a new Industrial Relations Committee and Edward Strychowski, will head the association's Public Relations Committee.

## Texas Electronic Association

TEA was the sponsor of the Texas radio and TV service clinic and electronic fair held recently at Fort Worth, it was reported by Leonard Smith, President. Talks by John F. Rider, President, Rider Publication and Al Robertson, Robertson's, Oklahoma City, opened the parley. Other talks given were by James D. Secrest, official of RETMA on "Let's Build Our Industry Together," William D. Renner, field technical sales director, and Howard W. Sams Co., who discussed UHF and color television. Advice to new television dealers was offered by Mort Farr, Upper Darby, Pa., and Hal Chase, President, Television Service Association of Detroit, Michigan. Russ Hansen, contract section manager, Motorola, Inc., and Ray Yeranko, radio and television service manager. The Magnavox Co., participated in a panel discussion on service.

## Radio and Television Technicians Guild of Florida, Inc.

### Suggested Charges for Television Service-Repairs

This schedule of suggested prices covers labor charges only, but includes all testing necessary to locate faulty part or circuit. Parts and tubes are extra.

Home Call		
1st 1/2 hour \$5.00 minimum	After 1st 1/2 hour	5.00
Pickup, delivery, pull, install and adjust		7.50
Projection		10.00
Warranty		
Parts exchange — minimum per set		1.00
Maximum per set		2.50
Call Backs		
All call backs regardless of trouble		2.00
Call back, other trouble		5.00
Bench		
Minimum \$3.00	Hourly rate	5.00
Tube		
Replacement, locate and replace defective tube		1.00 minimum
Alignment		
Audio Section IF complete		4.50
RF tuner		Hourly rate
Video section		5.00
Capacitor and Resistor		
RF section		7.50
Audio		5.00
Sweep Section		7.50 maximum
Video section		5.00
Power section		5.00 maximum
Choke Coils		
Power section		3.50
Wave trap and adjustment		3.00
Audio section		4.00 minimum
Sweep section		4.50
Focus coil		4.50
Video section		5.50
Controls		
Clean controls		1.50
Connection		
Locate and repair		6.50
Modifications		
Modify to remove retraces	Pts Labor	3.15
	65 2.50	
Picture Tube		
Resolder pins		2.00
Install and adjust CRT up to 9"		3.00
10" to 17"		5.00
18" to 27"		8.50
Projection		Hourly rate
Rectifiers		
Selenium-replace		3.50
Sho		
*All circuits — locate and clear		6.50
(*except tuner)		
Transformer		
A0 section		4.50
Power section — mounting charge \$4.50		
plus 25c per connection		8.00 minimum
Sweep section — output — horiz		6.50
oscillator, horiz		6.50
output, vertical		3.50
oscillator, vertical		3.50
IF transformer, video		6.00
Tune		
Pull and install		12.50
Clean, lubricate and adjust contacts		3.50
Locate and replace defective capacitor or resistor		7.50
Locate and repair loose connection or short		Hourly rate
Yoke		4.50

The accompanying chart was made available by Thurow Distributors of Miami, Florida to the members of the Radio and Television Technicians Guild of Florida, Inc.

## Radio and Television Association of Springfield, Ohio.

It was reported by Paul Boller, Secretary, that a vote taken at the last regular meeting resulted in a majority of members opposed to licensing, no matter in what manner, by this city. The association was born at a mass meeting held in the summer of 1949 which at that time had been organized to protest attempts of licensing and inspection of aerial installations by the city commission. Our violent opposition plus our proof of reliable workmanship without city inspection caused the city commission to drop the licensing matter entirely and has never since been brought up at a city commission meeting.

## NATESA

Plans for the fourth annual convention of the National Alliance of Television and Electronic Service Associations, to be held at the Morrison Hotel, Chicago, October 9th, 10th and 11th, are nearing completion, according to Frank J. Moch, National President. More than one thousand members of the thirty-five affiliated state groups are expected to accompany the seventy delegates, with an additional five hundred persons representing Chicago area companies, John Cecich, Convention Chairman estimated. This year's plans call for both an industry convention and product display and an open forum, to which the public is invited, and where leading authorities on television maintenance and repair will give set owners an opportunity to air their comments on TV repair service.

## Television and Radio Electronics

### Institute of Washington

Radio and television repairmen in Tacoma, Washington, have formed a unique trade association aimed at raising the standards of their field. Forty firms in Tacoma, have formed the Television and Radio Electronics Institute of Washington, the first in the Pacific Northwest and believed unique in organization nationally. Administrator of the Institute is R. E. Johnson, with headquarters in Tacoma. The Tacoma group is setting out on a program of tests for membership and a rigid code of ethics to follow.



Impetus for the organization came from the repairmen. After formation



of the institute they set up a 12-man board of governing executives. They adopted a seal of approval, which they will display and also attach to all repaired sets. Members agree to conform to the Minimum Classified Standards of Quality Products and Services of leading technicians and authoritative service bureaus.

Similar organizations have sprung into being since the advent of TV, but the Pacific Northwest group says that study shows that most of them are "mutual admiration societies" with no teeth in their organizational operation. Interest from Yakami and Seattle in a similar organization makes the Tacomans confident that in a short time they will have a statewide organization as new stations are assured for Seattle, Tacoma, Yakima, Bellingham, Spokane and Portland, Oregon.

## FLYBACK TESTER

[from page 24]

cate oscillator efficiency.

When the unit is first turned on the 6K6 will oscillate. The flyback transformer under test is effectively connected by test leads across the oscillating tank circuit. If shorted turns are present in the flyback transformer under test the overall "Q" of the oscillating circuit will be lowered and the meter needle will indicate in the "BAD" region on the meter scale.

A flyback transformer may be checked in the TV receiver without disconnecting or removing it. In most cases it is only necessary to connect the two leads from the tester to the plate caps of the horizontal output tube and high voltage rectifier. To achieve greater accuracy in measurement the following procedure is used:

1. The TV receiver is turned off and disconnected from the ac line.
2. The HV RECT. and HOR. OUTPUT tube plate caps are removed.
3. The HV RECT. tube is removed from its socket.
4. The Deflection yoke assembly is unplugged.
5. One side of the WIDTH coil is disconnected.

The test leads from the Model 98 are connected across the two plate cap terminals on the flyback transformer. No polarity observation is necessary. If the meter needle indicates in the "BAD" region on the SHORT test scale the transformer has an internal short or low efficiency and should be replaced.

If the meter needle indicates in the "GOOD" region on the SHORT test scale then the trouble is not in the flyback. To quickly determine whether the trouble is in the deflection yoke reconnect it and notice the meter indication. A short in the yoke will reflect a short due to mutual inductance or reflected impedance and the meter will indicate in the "BAD" region. Thus by means of this unit the trouble can be quickly isolated.

The test described above specifically pertains to flyback transformers in a TV receiver under troubleshooting

tests; however, the same procedure can be applied to transformers from stock to prevent installing a replacement transformer in a set only to find out that the replacement isn't any good.

## TROUBLE?

[from page 47]

produces horizontal stripes or "sound bars" on the screen. (Fig. 9) shows sound bars of approximately 960 cycles.


A 15,750-cycle signal produces one

# A Revolutionary Cartridge at a Revolutionary price...

THE **FAIRCHILD** SERIES 215

## DIAMOND CARTRIDGE

Now Only  
**\$37.50**

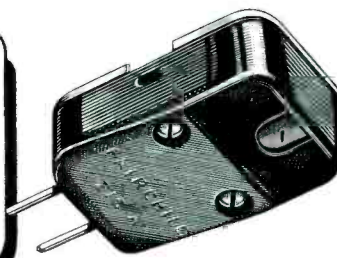

with 1.0, 2.5 or 3.0 mil stylus for 33, 45 and 78 rpm records and transcriptions

Instant widespread acceptance of the new Fairchild Moving Coil Cartridge has made possible substantial economies in production. These are being passed on to the consumer in the form of lowered price...and to the dealer in the form of increased discount.

Why has the Fairchild Series 215 made such an instant hit? The answer: It embodies an entirely new principle of design which brings *immediately recognized improvement in reproduced sound*. This high standard of performance has never before been achieved by any cartridge, regardless of the quality of other components in the system.

The benefits in terms of improved sound for music lovers are enormous. The benefits in terms of increased sales and profits for dealers can be equally impressive. If you do not yet stock the Fairchild Series 215, place your order now. We guarantee prompt shipment, and our regional representative will see you as soon as possible.

What users hear  
with the  
Fairchild Series 215:

- All shades of tone color in fine recordings
- From choice records—low frequencies never before heard
- A new clear character in high volume piano chords
- Absence of bass concentration caused by arm resonance
- Needle talk, record hiss, surface noise, reduced to a new low
- And above all... Tracking distortion eliminated!

# FAIRCHILD RECORDING EQUIPMENT

155th St. & 9th Ave., Whitestone, N. Y.

VISIT US AT THE AUDIO FAIR, HOTEL NEW YORKER, OCT. 14-17.

Engineered for the Purpose . . .

# Copperweld GUY STRAND

provides REAL GUYING CONFIDENCE



## Copperweld DOESN'T STRETCH

Soft wire guys frequently stretch badly in service and go slack. This means a wobbly antenna and poor reception. Copperweld Guy Strand is hard drawn—has the strength to stay taut—holds the antenna firmly in place—improves reception.


## Copperweld COMBATS RUST

A guy weakened by rust may go unnoticed until a storm brings down the antenna, causing damage many times the cost of the guy. Copperweld Guy Strand is protected against rust by a molten-welded layer of pure copper on each wire. Its strength is lasting.

SOLD BY  
RECOGNIZED  
PARTS DISTRIBUTORS
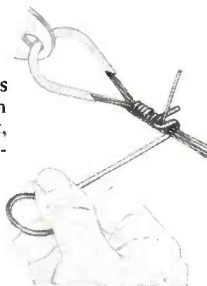
## Copperweld is EASY TO INSTALL

No clamps or clips are needed. An ingenious serving tool—one furnished free with each standard length of strand—turns out neat, tightly wrapped dead-ends as strong and permanent as the strand itself.




Write today for further details.

**COPPERWELD STEEL COMPANY**

Glassport, Pa.

Service Men!

# THE GUARDIAN SERIES 200 RELAY...

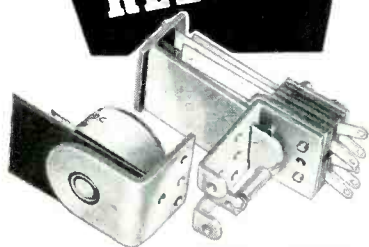

## Interchangeable COIL and CONTACT SWITCH ASSEMBLIES Save Time—Cut Costs!

★ Coil assembly includes coil and field piece. Contact assembly consists of switch blades, armature, return spring and mounting bracket. Standard and Midget contact assemblies in either S.P.D.T. or D.P.D.T. are *interchangeable* and can be used with any of 13 coils described below.

### CONTACT SWITCH ASSEMBLIES

CAT. NO.	TYPE	AMPS	COMBINATION
200-1	Standard	8 amps	Single Pole Double Throw
200-2	Standard	8 amps	Double Pole Double Throw
200-3	Standard Contact Switch Parts Kit with complete assembly and wiring details		
200-4	Standard	12.5 amps	Double Pole Double Throw
200-5	Standard	8 amps	Four Pole Double Throw
200-M1	Midget	8 amps	Single Pole Double Throw
200-M2	Midget	8 amps	Double Pole Double Throw
200-M3	Midget Contact Switch Parts Kit with complete assembly and wiring details		

### 13 COILS ASSEMBLIES

A.C. COILS*		D.C. COILS	
CAT. NO.	VOLTS	CAT. NO.	VOLTS
200-6A	6 A.C.	200-6D	6 D.C.
200-12A	12 A.C.	200-12D	12 D.C.
200-24A	24 A.C.	200-24D	24 D.C.
200-115A	115 A.C.	200-32D	32 D.C.
		200-110D	110 D.C.
		200-5000D	for current type

\*All A. C. coils available in 25 and 60 cycles

# GUARDIAN ELECTRIC

1606-K W. WALNUT STREET CHICAGO 12, ILLINOIS  
A COMPLETE LINE OF RELAYS SERVING THE RADIO INDUSTRY

vertical black and one vertical white stripe on the screen (though one black and two white stripes or one white and two black stripes might be produced, depending on the phase of the signal). At twice the horizontal frequency, there would be two black vertical stripes and two white ones, etc. If the frequency on the screen is an exact multiple of 15,750 the lines are *vertical*; if not, they are *slanting*. To find the frequency of the interference signal on the screen, simply count the number of black (or white) stripes. If the bars are horizontal, multiply by 60; if vertical or diagonal, multiply by 15,750. While the frequency will not be exact, because of the blanking periods, it will be close enough for the purpose of estimating the approximate frequency.

### 3. a, b, c

The main steps in dealing with interference problems are:

- (1) Identifying the type of interference (steady *rf*, *fm*, ignition, etc.);
- (2) Identifying the origin of interference (internal or external);
- (3) Checking on how the interference, if external, comes into the receiver.

(1) Applying the correct remedy.


The type of interference is identified by observing the pattern on the screen. The appearance of the main types of interference was listed in the preceding answer.

When there is any question whether the interference is being generated internally or externally, identification is most easily accomplished by a simple process of elimination. This can be done by first checking the possibilities of internal interference.

For example, a tweet pattern can be recognized by careful observation and by rotating the fine tuning control. The tweet pattern changes considerably when the fine tuning control is rotated. At the point where the tweet harmonic becomes equal to the video carrier, zero beat is approached (broadest horizontal black and white bars indicating the lowest frequency). The line pattern becomes diagonal and vertical with thinner stripes as the fine tuning is rotated further away from the zero-beat point.

In some receivers the tweet harmonic zero beats with the video carrier at the best sound point. In other cases, the zero beat occurs when the fine tuning is rotated away from the best sound point, while at the best sound point the stripes may be thin and diagonal. An example of this is a receiver with a sound *if* of 22.1 *mc*. The third harmonic of 22.1 *mc* (66.3 *mc*) beats with 67.25 *mc*, the video carrier of Channel 4. At the best sound point, an inter-

# FOR GREATER PROFITS

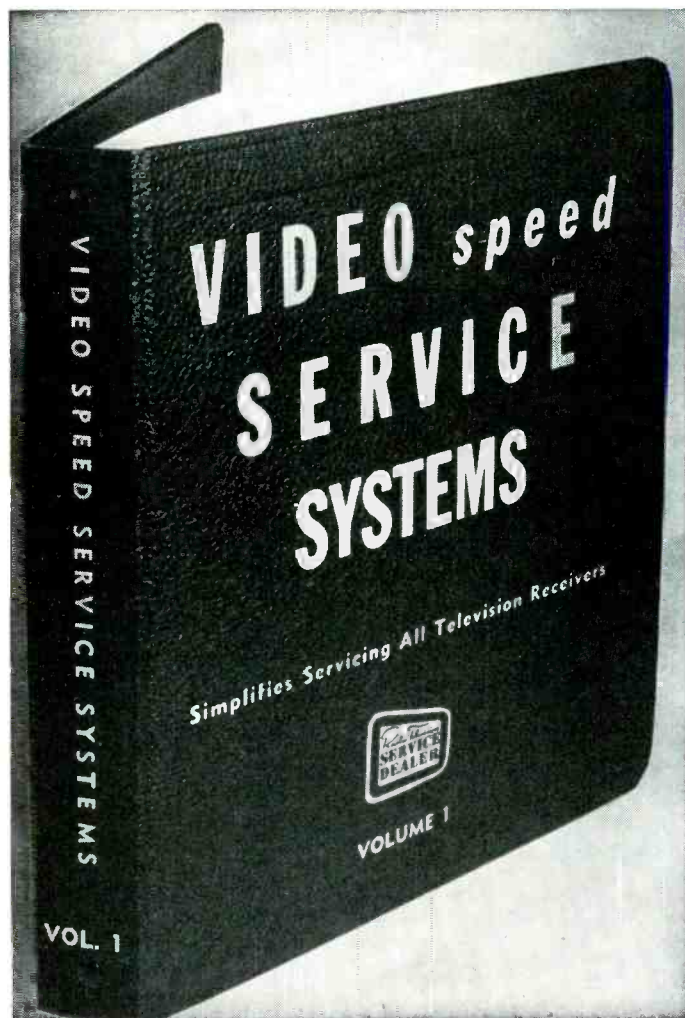

## SPEED UP YOUR SERVICING with THIS NEW BOOK

which shows you how to take care of and repair in the quickest possible time:

- Troubles commonly found in certain receivers
- "Bugs" which might take you hours to find
- Factory and field service changes

SET UP SO THAT YOU CAN MAKE THESE REPAIRS IN THE SHOP OR IN THE FIELD WITHOUT REFERENCE TO ANY OTHER SOURCE.

**\$4.95** (postpaid)

**Distributors—order your supply now!**

Service Dealers—get your copy of VSSS from your Distributor. If he can't supply you, order direct by mail from us.

Contains over 600 Service Items representing over 1000 of the most-serviced Television models now in use. Over 25 different manufacturers' lines are covered.

Video Speed Servicing Systems IS GUARANTEED to Simplify Servicing All TVsets. 24 (or more) new Data Items are published in every issue of "Radio-Television Service Dealer" as a regular monthly feature.

### TEAR OFF AND MAIL NOW

RADIO-TELEVISION SERVICE DEALER

67 West 44th Street, New York 36, N. Y.

Please send me post-paid VIDEO SPEED SERVICING SYSTEMS Volume 1. Enclosed herewith is

my  check  money order for \$\_\_\_\_\_ for \_\_\_\_\_ copies at \$4.95 each.

Name .....

Address .....

City ..... Zone ..... State .....

ference frequency of approximately 1 mc is produced. A zero beat is generated when the fine tuning is rotated to one side of this point.

In all cases, rotation of the fine tuning gives a wide variation of the interference pattern which is typical of internally generated tweets.

Double conversion interference may resemble in appearance oscillator radiation from another TV receiver. However, local oscillator radiation is observed *only* when the interfering set is tuned to the channel capable of producing interference (the offending local oscillator must be at a frequency falling within the frequency range of the channel being tuned in at the re-

ceiver being serviced). Double conversion interference is always present as long as the interfering channel is on the air. A further check can be made by noting the intermediate frequency of the receiver and computing whether there is a channel capable of giving this type of interference.

When arcing or rf power supply interference is suspected, the antenna is disconnected from the antenna terminals. In both cases, the interference will still be seen. The other two types of internal interference—4.5 mc and 60-cycle or (120-cycle) interference are readily recognizable.

Disconnecting the antenna in itself does not automatically tell whether the

interference is internally generated. Two types of internally generated interference, tweets and double conversion signals, do not appear unless the antenna is connected and TV signals are received. For the same reason, taking out the rf oscillator and video if tubes do not provide conclusive information whether interference is internally or externally generated. However, as previously indicated, disconnecting the antenna may be helpful in distinguishing between two similar types of interference, one external and one internal—like ignition noise (external) and arcing (internal).

Disconnecting the antenna is also helpful in the next step—determining by what path external interference is coming into the receiver.

External interference can come in by three paths: a) antenna-transmission line; b) line cord (power line); c) directly to the chassis.

Since the remedy for external interference depends on knowing how the interference is coming into the receiver, it is necessary to check the path of entry. The simplest way is to detach the antenna. If the interference is still seen, it is either coming from the power line or directly to the chassis. (Internal interference possibilities have been eliminated previously.)

The next step is to plug in a good low-pass filter (which should be in your kit when checking interference troubles) between the receiver and power line. If this attenuates the interference noticeably, then most or all of the interference is coming through the power line. If the interference is still visible, then direct pickup is indicated. On the other hand, if detaching the antenna reduces the interference, it is coming in by way of the antenna and/or transmission line. A high-pass filter and tuned stubs should then be tried. Interference remedies are listed in Answer 5.

4. a, e

When a tweet pattern is suspected as originating in the sound *if* on the basis of observation of the screen and checking the video and sound intermediate frequencies, further verification can be made by removing the first sound *if* tube. If the tweet disappears, it is originating in the sound detector. This will not work in the video strip, since removing the video detector, of course, kills both the picture and the interference.


5. a, b, c, d, e

The steps to take to eliminate tweets depend on the design and layout of components in individual receivers. Several manufacturers issue service bulletins on how to correct the problem in specific models. Generally, the first

## MOSLEY 3-WAY TV ANTENNA SWITCH

For Multiple


### UHF and VHF ANTENNA INSTALLATIONS

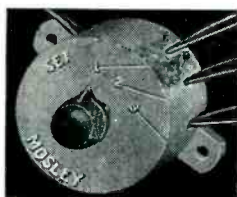

Cat. No. F-20  
MOSLEY 3-Way  
TV Antenna Switch  
List Price .....\$3.75

- Install anywhere. Extension rod supplied for back of set mounting.
- Constant impedance—Low loss—Solderless.
- Sturdy rotary switch making silver-to-silver contact.
- In brown or ivory polystyrene case.
- Also available in Flush Wall Plate style.

At Radio Parts Jobbers

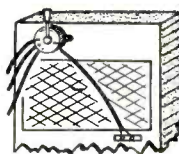

**MOSLEY Electronics, Inc.**

8622 St. Charles Rock Road

St. Louis 14, Missouri

**STOP  
BLACK BORDERS  
ON TV PICTURE**

use a  
**"B" Plus Booster**  
Model 5TV4 Replaces 5U4G

**Anytime!** Pulling a Tube beats  
Pulling a Chassis

WHEN YOU NEED • More Height • More Width  
• More Gain • Better Overall Performance

Built-in Time Delay to Protect TV Set

Write for **free** information



THE  
**5TV4**  
GETS RESULTS

- SUPPLIES EXTRA 30-40 VOLTS TO LOW VOLTAGE SUPPLY
  - GIVES FULL SIZE PICTURE WHEN LOW LINE VOLTAGE OR WEAK TUBES CUT PICTURE SIZE.
  - GIVES EXTRA GAIN NEEDED IN FRINGE AREA
- STANDARD R.T.M.A. GUARANTEE PAT. APPLIED FOR

**WORKMAN**

Sold Through  
Authorized  
Distributors  
Only.

List Price \$6.60.

TEANECK, NEW JERSEY

## TECHNICAL ARTICLES WANTED on

TV, AM RADIO, FM RADIO, PHONO MECHANISMS, HI-FI AUDIO, AUTO RADIO, TEST EQUIPMENT, ANTENNAS

pertaining to their

**Theory, Installation, Application, Service & Maintenance**

submit manuscripts to Managing Editor

**RADIO-TELEVISION SERVICE DEALER**

67 West 44th Street

New York 36, N. Y.

step is to determine, by the methods noted above, whether the tweet is originating in the video or sound detector. One or more of the following remedies is then applied to the corresponding circuit:

- Carefully check the lead dress—
  - Keep the leadin from the antenna terminals to the front end as far from the affected *if* strip as possible. Move the lead while watching the effect on the screen.
  - Keep the antenna leadin away from the 115-volt power line.
  - Keep *ac* and *dc* power leads from the *if* and detector as far away from the front end and antenna leadin as possible. No soldered components—resistors, condensers, coil wires in the *if* strip should be moved since this may affect the tuning.

2. Make sure the *if* and detector tubes are shielded.

3. Bypass the hot filament line going to the last *if* and detector stage with a filament choke and bypass condenser.

4. For tweets originating in the video detector, a tweet trap has been found effective in some cases (Fig. 10). This is obtainable from the manufacturer and is a series-resonant circuit placed across the detector load, to short out the load for the tweet harmonic. While observing the screen pattern, the trap is tuned for minimum interference.

In a few instances, manufacturers have recommended an *if* and *rf* realignment at new frequencies.

Double conversion interference, which is most common in fringe areas is counteracted by one or more of the following: stubs and switches (see below); reorientation of the antenna; returning the *rf* amplifier grid to ground instead of to the *age* line.

4.5 *mc* interference can be caused by incorrect positioning of the fine tuning control in split sound sets, incorrect tuning of the sound takeoff coil in intercarrier sets, or incorrect tuning of 4.5 *mc* trap in the video amplifier stage (if the set has one). In some cases, it is necessary to install such a trap if the set has none.

Eliminating interference caused by 60-cycle (120-cycle) hum and arcing simply requires finding the defective component. *RF* power supply interference is caused by poor shielding or a defect in the supply.

The remedies for external interference depend on how it comes into the receiver. The following remedies are available:

- For interference coming in from the power line—a low-pass filter between line cord and power outlet.
- For interference coming directly to the chassis—a bottom pan on the chassis, and copper screening inside the

cabinet well-grounded to the chassis and to external ground (provided the chassis is not "hot").

3. For interference coming in by way of the antenna-transmission line—

- At the *if* or other frequency below the TV spectrum—a high-pass filter;
- At TV or higher than TV frequencies—tuned traps (stubs);
- At all frequencies—reorientation and/or relocation of the antenna-transmission line.

For antenna-borne interference, it is desirable to know the frequency of the interfering signal. A mobile communications receiver is generally used both to check the frequency and to locate

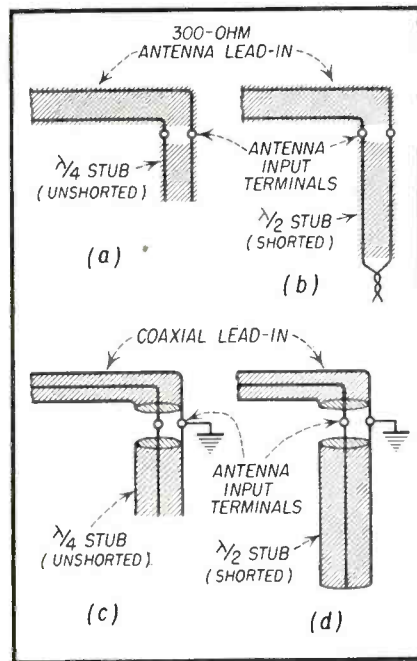


Fig. 11—300 ohm and coaxial cable stubs.

- (a & c) Quarter wave unshorted.  
(b & d) Half wave shorted.

the interference source by organizations specializing in interference problems. This is not generally available to a serviceman working on an occasional interference trouble. However, the problem can be solved on the basis of simple checks and general information. First, a high-pass filter is tried at the antenna terminals to determine the effect of the lower radio frequencies. Then tuned stubs are tried for frequencies in or above the TV bands.

Good low-pass and high-pass filters are commercially available or can be made by servicemen from data supplied in manuals.

Tuned traps can be easily constructed by the serviceman from lengths of transmission line, similar to the type already used in the receiver installa-

## Latest Books for TV "KNOW-HOW"!



### TV MANUFACTURERS' RECEIVER TROUBLE CURES VOL. 1, VOL. 2, VOL. 3 and VOL. 4

Positive cures for TV troubles! Gives you exact directions for correcting TV receiver performance "bugs". Each cure is official, factory-authorized, direct from the receiver's manufacturer. Listings by manufacturer and model or chassis number. Helps correct the most difficult faults—picture jitter, hum, instability, buzz, tearing, etc.

- Vol. 1, 115 pages (5¼ x 8¼").....\$1.80  
Covers 12 brands, Admiral through Dumont  
Vol. 2, 117 pages (5¼ x 8¼").....\$1.80  
Covers 11 brands, Emerson through Jackson  
Vol. 3, 119 pages (5¼ x 8¼").....\$1.80  
Covers 16 brands, Kaye-Halbert through Philco  
Vol. 4, over 115 pages (5¼ x 8¼").....\$1.80  
Covers 10 brands, Philharmonic through Shaw TV

VOLUME 5 COMING SOON!  
Prominent manufacturers not in first 4 volumes  
ONE SERVICE JOB WILL MORE THAN PAY  
THE COST OF THIS SERIES OF BOOKS!

### OBTAINING AND INTERPRETING TEST SCOPE TRACES

by J. F. Rider

Over 500 actual photographs of test scope traces. Shows how to use scopes and what traces mean. Valuable for servicing TV receivers, FM and AM radio receivers, audio systems and test equipment. Specific test equipment set-ups shown with each application. No other book like it! Over 140 pages... Only \$2.40

### HOW TO USE METERS

by J. F. Rider

Panel type, volt-ohm-milliammeters, vacuum tube voltmeters for servicing radio and TV receivers, audio amplifiers, power supplies; for use and repair of ham transmitters. Written for the service technician, the TV and Radio student and hams.  
Over 140 pages..... Only \$2.40

### TV SWEEP ALIGNMENT TECHNIQUES

by Art Liebscher, Test Equipment Specialist

Never before has there been a book such as this on TV sweep alignment! An expert gives you accurate time-saving methods—and tells you how they work. Introduces the new Supermark method. Chock-full of sweep curve pictures. Valuable for servicing in UHF signal areas. 123 (5½ x 8½") pp., illus.....\$2.10

### HOW TO USE SIGNAL AND SWEEP GENERATORS

By J. R. Johnson

First book on all types of signal and sweep generators. Gives test uses and discusses problems and their solutions in using this equipment. Applications of all signal and sweep generators in AM, FM radio and TV servicing.  
Over 120 (5½ x 8½") pages.....\$2.10

### GUIDE TO AUDIO REPRODUCTION

By David Fidelman

A to Z explanation of the reproduction of sound. Design, construction, assembly and testing of sound systems and their components. Valuable for service technicians, engineers, amateurs.  
Over 250 (5½ x 8½") pp., illus.

### RADIO TROUBLESHOOTING GUIDEBOOK

By J. F. Rider and J. R. Johnson

Here is a troubleshooting guidebook that covers the more than 100 million radio receivers now in use! Explicit information about troubles and possible causes. Completely practical for the radio service technician and student. Over 140 (5½ x 8½") pages.

Write for information on all RIDER books.

Buy these books now from your jobber... bookstore... If not available from these sources, write to:

**JOHN F. RIDER**

Publisher, Inc.

480 Canal Street, New York 13, N. Y.

# TOP TV SERVICE REQUIRES TOP Quality COMPONENTS

and for TOP QUALITY ask for

## Elmenco Paper Tubulars



That white, ceramic-cased paper tubular is appearing in more and more TV circuits as new models roll off the lines . . . your assurance that this unit excels those which preceded it.

Follow the lead of these manufacturers by offering your customers complete satisfaction with components which will require no further replacement during the life of their sets . . .

**Air-Tight, Water-Tight, Yet Reasonably Priced**

Just Wire In and Forget.

And you can keep a stock of Elmenco Capacitors on hand without worry of deterioration on the shelf. They have unlimited shelf life.

Contact your local jobber for full information and ask him about our handy paper tubular kits.



### STANDARD PAPER KIT

5 Each of 25 Capacities

.001 to .1—600V; .25—400V & .5—200V  
List Price \$37.50

WRITE FOR OUR DESCRIPTIVE CATALOG OF COMPLETE ELMENCO LINE

**ARCO ELECTRONICS INC.**  
103 LAFAYETTE ST., N. Y. 13, N. Y.

tion. Twin-lead or coax line is used, depending on the leadin to the receiver. The stubs act as tuned circuits which will attenuate a given frequency. Quarter-wave stubs are equivalent to series-resonant circuits and have open ends; half-wave stubs act like parallel resonant circuits and have shorted ends (Fig. 11). A length is cut longer than needed according to the formulas:

300-ohm twin-lead:

Length of half-wave stub =  $4840/f (mc)$   
(in inches)

Coax:

Length of half-wave stub =  $3880/f (mc)$   
(in inches)

The stub is attached to the antenna terminals of the set. A razor blade or sharp knife is used to short across the end of the twin lead stub, without cutting the wire. This is done at approximately quarter-inch intervals until the interference is cut down the most. For coax stubs, a medium-size safety pin can be pressed into the wire until the inner conductor is shorted against the outer one. The transmission line is then cut. If the interference is not a TV station, the line can be cut and the leads shorted together. If the interference is from a TV channel, a switch is needed to disconnect the stub when that channel is tuned in.

To minimize the effect of the stub on desired channels, it is usually advisable to connect a small carbon resistor of from 20 to 150 ohms across the ends instead of shorting the stub. No smaller value of resistance should be used than necessary to cut down the interference. In all cases when traps are installed, all the active channels should be checked to make certain the signals have not been adversely affected.

When indicated, the antenna should be checked to make certain the maximum signal is being picked up compared to the interference. If necessary the antenna should be reoriented or relocated for maximum signal with minimum interference. In cases of ignition interference, the antenna lead-in should be the maximum possible distance from the street where the noise is originating. The leadin should be twisted to cancel noise pickup—at least one twist every 1/2 feet. For difficult problems, coax may be necessary.

Oscillator radiation from another TV receiver can be reduced greatly by installing a booster at the offending receiver. This, however, requires the cooperation, financial and otherwise, of the owner and is not always a practical solution. At the receiver subjected to this interference, the usual solutions are antenna reorientation, a more directional antenna, and stubs.

This Space

Reserved for


**DAVIS ELECTRONICS**

4313 West Magnolia Blvd

Burbank, California

## South River NEWS

### CHIMNEY CORNER GUARD

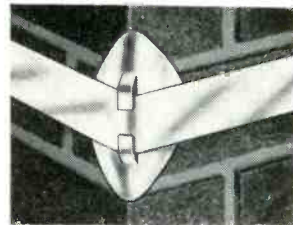

Box of Six . . . . . 49c

An exclusive South River device for protecting, strengthening, and safeguarding chimney and strapping. Prevents chipping of chimney. Permits uniform tightening of banding. Safeguards mounting equipment. South River Antenna Mounting Accessories are carried by every leading TV Parts Jobber from coast to coast.

Write for your copy of our new 1953 catalog.

In Canada A. T. R. Armstrong Co., Toronto

**SOUTH RIVER METAL PRODUCTS CO., INC.**  
SOUTH RIVER, N. J.

PIONEER AND OUTSTANDING PRODUCER OF FINEST LINE OF ANTENNA MOUNTS



# SAVE Up to \$1.00 each.

## Form a Group,

### Subscribe to "RTSD" -

"The Professional Radio-Television man's Magazine"—published monthly. All articles are exclusive and timely. Practically every issue is worth what an entire 1 year subscription costs.

The more in a group the bigger the savings. 6 men in a group save \$1.00 each; 4 men groups save 80c per man. Present "RTSD" subscribers may participate in or form a group with co-workers, or even competitors. Still active subscriptions are automatically extended 2 years. Start a Group today! The timely and exclusive technical data appearing in future issues of "RTSD" will make this the best investment you ever made. The special Group Rate offer may be withdrawn at any time—so hurry.

#### Use This Coupon For Convenience

(The coupon below can be used for from 1 to 6 subscription orders. Use it today!)

**RADIO-TELEVISION SERVICE DEALER**  
67 West 44th Street, New York 36, N. Y.

Please enter 2 years subscription orders for the names given below. Our remittance is enclosed.

NOTE: If you do not wish to tear this order blank out, just print or type the information on a single sheet of paper, following the style given. Each subscriber's occupation must be clearly described.

<input type="checkbox"/> One 2-year subscription	In U.S.A. <b>\$3.00</b>
<input type="checkbox"/> Two 2-year subscriptions each	2.50
<input type="checkbox"/> Three 2-year subscriptions, "	2.30
<input type="checkbox"/> Four 2-year subscriptions, "	2.20
<input type="checkbox"/> Five 2-year subscriptions, "	2.10
<input type="checkbox"/> Six 2-year subscriptions, "	2.00

#### TEAR OUT — MAIL TODAY

Name ..... Address ..... City ..... Zone ..... State ..... Describe Title or Position and Type of Business ..... <hr/> State whether a New Subscriber <input type="checkbox"/> or Renewal Order <input type="checkbox"/>	Name ..... Address ..... City ..... Zone ..... State ..... Describe Title or Position and Type of Business ..... <hr/> State whether a New Subscriber <input type="checkbox"/> or Renewal Order <input type="checkbox"/>
Name ..... Address ..... City ..... Zone ..... State ..... Describe Title or Position and Type of Business ..... <hr/> State whether a New Subscriber <input type="checkbox"/> or Renewal Order <input type="checkbox"/>	Name ..... Address ..... City ..... Zone ..... State ..... Describe Title or Position and Type of Business ..... <hr/> State whether a New Subscriber <input type="checkbox"/> or Renewal Order <input type="checkbox"/>
Name ..... Address ..... City ..... Zone ..... State ..... Describe Title or Position and Type of Business ..... <hr/> State whether a New Subscriber <input type="checkbox"/> or Renewal Order <input type="checkbox"/>	Name ..... Address ..... City ..... Zone ..... State ..... Describe Title or Position and Type of Business ..... <hr/> State whether a New Subscriber <input type="checkbox"/> or Renewal Order <input type="checkbox"/>



**OXFORD**

## Speakers



There is an application for every Oxford Speaker . . . and an Oxford Speaker for every application.

**OXFORD ELECTRIC CORPORATION**

3911 S. Michigan Ave.  
Chicago 15, Illinois

EXPORT: ROBURN AGENCIES  
NEW YORK CITY

Preferred for original equipment . . . Proven for replacement!

## CIRCUIT COURT

[from page 52]

switch *S101* is used to determine the point at which the diode can be cut off.

### Capehart-CX 37—

#### Horizontal Oscillator and AFC.

In the receiver under consideration automatic control of the horizontal oscillator is accomplished by a single triode phase detector circuit which uses  $\frac{1}{2}$  of a 12AU7. The plate of this tube is pulsed by a 15.75 kc pulse which is coupled from the plate of the *age* amplifier. Before being applied to the plate of V403B, the pulse is fed to an RC network consisting of R507, R502, C510 and C509. It is integrated and reduced in amplitude by this network and appears as a sawtooth pulse of approximately 20 volts peak to peak.

In the grid-cathode circuit we find two 82K resistors which act as a balanced network. When a positive going sync signal is applied to the grid, current flows through these resistors. The circuit time constants are so arranged that if the sync and sawtooth are in step the pulse arrives at the midpoint of the sawtooth and the voltage at the midpoint of the two resistors is zero.

If the oscillator should drift an out of phase situation occurs. As a result the potential difference between plate and grid causes changes in the plate current. This variation in turn causes the voltage at the mid-point of R503 and R504 to be less than or greater than zero. The voltage at this point is then applied to the oscillator.


The *dc* return for V403B is through R506. C505 feeds a negative going pulse to the cathode of V403B. This provides a certain amount of noise immunity to the circuit. Another feature of this network is that in the event of a momentary interruption of the sync signal there will be no grid current flow and no spurious control voltage is applied to the horizontal oscillator.

The horizontal oscillator V503, is a sine-stabilized multi-vibrator of the cathode coupled multivibrator type. An LC circuit is in the plate circuit in series with R509 the plate load resistor. The *dc* control voltage developed at the midpoint of R503 and R504 is applied to the grid of the first section of the multivibrator. Variations of bias on this grid determines the conduction time of the tube and this in turn determines the oscillator frequency.

LIFE quotes:

## "HIGH FIDELITY Simplified"

by H. D. WEILER

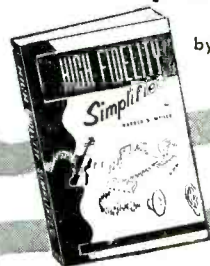

Radio and TV service technicians . . . familiarize yourself with high fidelity components, terminology and problems. High fidelity is booming! LIFE magazine's June 15, 1953 issue told over 15,000,000 people about the amazing difference Hi-Fi makes in sound reproduction . . . and LIFE reported enthusiastically how "High Fidelity Simplified"—the only book quoted—explains the complete Hi-Fi story. "High Fidelity Simplified" gives complete answers to all questions about Hi-Fi record players and changers, amplifiers, loudspeakers, tuners, tape recorders, etc. The best way to learn about this fast growing field is to read this best selling book which will pave the way for a profitable "extra" to your TV and radio servicing income. Order your copy from your parts jobber or bookstore today! If unavailable from these sources send \$2.50 to:

John F. Rider, Publisher, Inc.  
Dep't. SD, 480 Canal Street  
New York 13, N. Y.



free

268-PAGE  
1954  
**ALLIED**  
ELECTRONIC  
SUPPLY  
CATALOG

Everything in Electronics  
For Service Technicians and Engineers

You'll want the complete, up-to-date ALLIED Catalog. It's packed with the world's largest selection of TV and radio parts and accessories, test instruments, amplifiers, P.A. systems, tubes, tools—everything for service work and industrial electronic application. Depend on ALLIED for quick shipment from the world's largest stocks—save time and money. Send today for your FREE 268-page Catalog.

## ALLIED RADIO

ALLIED RADIO CORP., Dept. 26-J-3  
100 N. Western Ave., Chicago 80, Ill.  
 Send FREE 1954 ALLIED Catalog.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_



### 3—SPEED CHANGER CONVERSION

[from page 28]

trying to replace the obsolete changer only. A drawer can be constructed using the cabinet door as its front and "drawer slides" utilized to provide smooth in and out movement of the entire drawer assembly which will mount the new unit. Such a drawer is illustrated in Fig. 6.

**Pan Mounted Changers:** This type of mounting is not common in older consoles. However, should it be necessary to consider a replacement of this type, two courses can be followed:

1. Modify the pan by relocating the mounting brackets or use new brackets. This is usually quite difficult and is time consuming.
2. The more practical method is to replace the entire assembly (space permitting) with a modern disk-changer incorporating a base pan mount. The matching units will make a more attractive installation in addition to simplifying the con-

version. Specifications for Webcor base pan models are given in Fig. 7.

**Hum Problems:** Should initial test reveal the presence of a serious hum, reverse the leads to the diskchanger motor. If this does not help, the radio and changer chassis should be commonly grounded by a separate lead. The changer chassis is not originally grounded because of shock hazard involved in possible connection to *ac/dc* equipment. When straight *ac* equipment is used, the pickup cable shield terminal of the standoff on the underside of the changer can be grounded directly to the changer chassis. A separate ground lead from radio to changer chassis will be more effective, however. Often both connections will give best results. When a pre-amplifier is used, it may be necessary to find a mounting location in the cabinet that will provide a minimum of hum.

### Q MEASUREMENTS & METERS

[from page 31]

and its calibration will hold, provided the signal generator output always is adjusted to a predetermined reference value. A thermocouple-type *rf* ammeter is provided for this purpose and is shown in the circuit in Fig. 3A.

#### Boonton "Q" Meters

The familiar Boonton Types 100-A and 160-A Q-meters employ the Q-voltmeter method, using the resistor method of injecting the test signal into the Q-measuring circuit.

In the complete Q-meter of this type utilizing the principles just explained, the signal source is a self-contained, self-powered, variable-frequency *rf* oscillator with adjustable output. A pair of binding post terminals is provided for plugging-in a coil at L. A similar pair of terminals is provided in parallel with tuning capacitor C (a dial-calibrated unit) for connecting a capacitor to be tested. Also connected in parallel with C is a small dial-calibrated air trimmer capacitor, usually reading from -3 to +3 micromicrofarads.

In the Boonton Type 160-A instrument, the dial for capacitor C is direct-reading in micromicrofarads from 30 to 450. The 100-megohm-input v. t. voltmeter (a 0-5 v. instrument) reads 0-250 Q on the basis of 0.02 volt developed across an 0.04-ohm coupling resistor—a radio-frequency current of ½ ampere flowing through the resistor. When the basic 0-250 Q range is used, the oscillator output is adjusted to

deflect the pointer of the thermoammeter to its X1 reference point. Higher Q ranges are available by setting the ammeter to X1.5 (full-scale Q = 375) or to X2 (full-scale Q = 500). The internal oscillator supplies test voltages at frequencies from 50 kc to 75 mc.

#### Checking Q of Coils

When checking coil Q by the Q-voltmeter method, the coil under test is connected into the circuit in position L (see Fig. 3A). The oscillator is set to the desired test frequency, and capacitor C adjusted for resonance as indicated by peak deflection of the v. t. voltmeter. The oscillator output is adjusted to deflect the thermoammeter to its X1 reference point. The coil Q then is read directly from the meter scale. If the Q value is beyond the limit of the meter, the ref-X1.5 or X2 point and the indicated Q are then read directly from the meter scale. If the Q value is beyond the limit of the meter, the ref-X1.5 or X2 point and the indicated Q are then read directly from the meter scale. If the Q value is beyond the limit of the meter, the ref-X1.5 or X2 point and the indicated Q are then read directly from the meter scale.

When checking capacitor Q, the LC circuit is resonated at the desired test frequency first with a standard high-Q coil a position L and with only the tuning capacitor, C, in the circuit. Oscillator output is adjusted to bring the reference current meter deflection to its X1 point. The corresponding setting of the tuning capacitor is recorded at C<sub>1</sub>, and the Q-voltmeter deflection at Q<sub>1</sub>. The test capacitor next is connected to terminals in parallel with tuning capacitor C. The setting

### HOW TO SELL A

# hi-fidelity DISKCHANGER

When selling a record changer to your Hi-Fi customer, you'll find him most interested in accurate turntable speeds, balanced tracking and swift, gentle changing. A WEBCOR DISKCHANGER EXCELS IN THESE THREE QUALITIES. So you enhance your reputation by recommending a Webcor Diskchanger.



#### 1 Accurate Turntable Speeds.

Webcor's own powerful motor maintains constant speed and low "hum." "Step-Drive" mechanism translates power into three different speeds so accurately that "wow" is eliminated. Fly-Wheel action turntable is made of extra-heavy steel and is ball-bearing mounted. The result: constant, accurate turntable speed with a minimum of "wow," "hum" or "rumble."



#### 2 Balanced Tracking.

A result of the elimination of mechanical drives and gears. The Webcor balanced tone arm "floats" in the record groove without any undue pressure. No excess wear on delicate sidewalls or records. Grooves themselves guide carefully weighted arm.



#### 3 Swift, but Gentle Changing.

A Webcor exclusive, the famed "Push-Off" system that has proved itself in close to a million installations. Records slide gently from spindle step to thick, resilient carpet on turntable formed by exclusive Webcor electrostatic flocking.

Webcor "HF" Diskchangers are available with or without handsome base pan. Choose crystal or G. E. Triple Play cartridge. Will also take standard magnetic cartridges.

# Webcor®

by WEBSTER-CHICAGO


© w/c 1953

Chicago 39, Illinois

4135

**FASTER  
STURDIER**

**Lower Installed Cost**

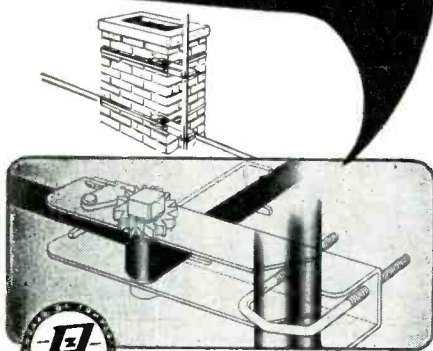


**SPEE-DEE**

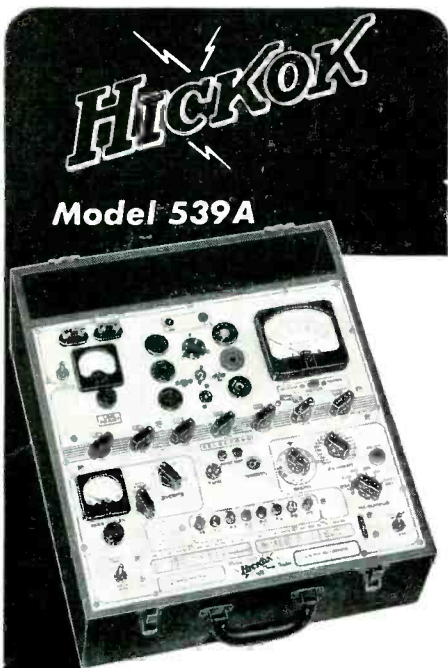**CHIMNEY MOUNT**

**Model AK 85** The fastest-installed chimney mount ever devised for TV antennas! Rugged in design—simple to install. Simply thread strapping through ratchet, around chimney and back through ratchet—wind up ratchet tight—and the job's done! Heavy gauge, zinc-plated steel with large "U" bolt for up to 1 3/4" O.D. mast and full length galvanized steel strapping.

**THE RADIART CORPORATION**  
CLEVELAND 13, OHIO



**HICKOK**

**Model 539A**

**Most Accurate  
LABORATORY PORTABLE  
TUBE TESTER**

- Accurately tests all Receiver tubes including high-gain types.
- Choice of 3 AC Signals and 3 micromho ranges.
- The leading tube tester in the industry.
- Write for technical details...

**THE HICKOK ELECTRICAL INSTRUMENT CO.**

10533 Dupont Ave., Cleveland 8, Ohio

of  $C$  now must be decreased in order to restore resonance. The new  $C$  and  $Q$  readings both are lower than before and are recorded as  $C_2$  and  $Q_2$ . The true  $Q$  of the capacitor under test then is determined from the four readings, as follows:

$$(9) Q_x = \frac{C_1 - C_2}{C_1(Q_1 - Q_2)} (Q_1 Q_2)$$

**Measuring Inductance with a Q Meter**

A Q-meter using the Q-voltmeter scheme may be used to measure inductance by the method described in connection with Equation (5) and capacitance by the method described in connection with Equations (6) and (7).

Inductance ( $L_s$ ), measured directly with the Q-meter is *apparent* inductance, which differs from true inductance ( $L_x$ ) because of the effects of distributed capacitance in the coil under test. True inductance is:

$$(10) L_x = L_s \left( \frac{C_1}{C_1 + C_d} \right)$$

Where,  $L_x$  and  $L_s$  are in microhenrys, and:

$C_1$  and  $C_d$  are in  $\mu f$

$C_1$  is the resonant setting of the Q-circuit tuning condenser, and  $C_d$  the distributed capacity of the coil.

**Measuring Distributed Capacity**

The following procedure should be followed in measuring distributed capacitance: (1) Resonate the Q-circuit containing the unknown coil. Have the tuning capacitor set to any convenient value  $C_1$  between 50 and 100  $\mu f$ . (2) Next, set the oscillator to 1/2 of the initial test frequency, and re-resonate the circuit by tuning the Q-circuit capacitor to a higher value,  $C_2$ . (3) Calculate the distributed capacitance by means of the following relationship:

$$(11) C_d = \frac{C_2 - C_1}{3}$$

Another circuit for checking Q values by the Q-voltmeter method is illustrated in Fig. 3. Here, the input signal voltage is developed across a padder capacitor,  $C_2$ , instead of across a low-ohmage resistor. As in the previous example, inductor  $L$  and tuning capacitor  $C_3$  in the Q-measuring circuit are in series with the input signal source, and a radio-frequency v. t. voltmeter shunts the tuning capacitor. The series trimmer,  $C_1$ , is set during the initial calibration of the instrument to give a predetermined voltage across  $C_2$ . The v. t. voltmeter may be switched temporarily to terminals X and Y for adjustment of the oscillator (generator section) output voltage to a reference value.

**UHF and THE KLIPZON  
CRYSTAL PROBE**



**solves your  
UHF ... VHF**

**ANTENNA PLACEMENT  
and ORIENTATION problems**

No more roof-top shouting—No phones—  
No expensive field strength measuring  
equipment!

Use a KLIPZON Type C PROBE  
We show you how. Maximum picture guaranteed in a jiffy! **SAVE TIME AND MONEY**  
Many other uses described in FREE  
4-page illustrated bulletin.

Ask for KLIPZON Type C at your local distributor; if not stocked, send \$6.95 check or M. O. direct to:

**UNITED TECHNICAL LABORATORIES**  
BOX 425E MORRISTOWN, N. J.

**Advertising  
Index**


Admiral Corporation	55
Allied Radio Corp.	70
American Television & Radio	8
Argos Products Co.	3
Astron Corporation	57
Arco Electronics, Inc.	68
Audio Fair	60
Bussmann Manufacturing Co.	51
Channel Master Corp.	4, 5
Copperweld Steel Co.	64
Davis Electronics	68
Duotone	24
Federal Telephone & Radio Corp.	33
Fairchild Recording & Equip. Corp.	63
Guardian Elec. Mfg. Co.	64
Hickok Electrical Instrument Co.	72
Hytron Radio & Electronics Co.	16, 17, 25
(IRC) International Resistance Co.	Cover 2
JFD Manufacturing Co., Inc.	11
Kester Solder Company	60
LaPointe Plascomold Corp.	27
Littelfuse, Inc.	18
P. R. Mallory & Co., Inc.	1
Mosley Electronics	66
Ohmite Manufacturing Co.	10
Oxford Electric Corp.	70
Philco Corporation	14, 15
Radiart Corporation	2, 72
Radio City	59
RCA Tube Dept.	Cover 4
Raytheon Mfg. Co.	9
Regency	22
Rider, John F. Publisher, Inc.	67, 70
Sams, Howard W. & Co., Inc.	6
Sangamo Electric Company	12
Schott, Walter L. Co.	35
Simpson Electric Company	7, 13
Snyder Manufacturing Co.	Cover 3
South River Metal Products Co.	68
Sylvania Electric Products Inc.	53
United Technical Laboratories	72
Vaco Products Co.	61
Webster-Chicago Corp.	71
Workman TV, Inc.	66

**Snyder**  
PHILADELPHIA

**2 NEW WAYS TO PROFITS**

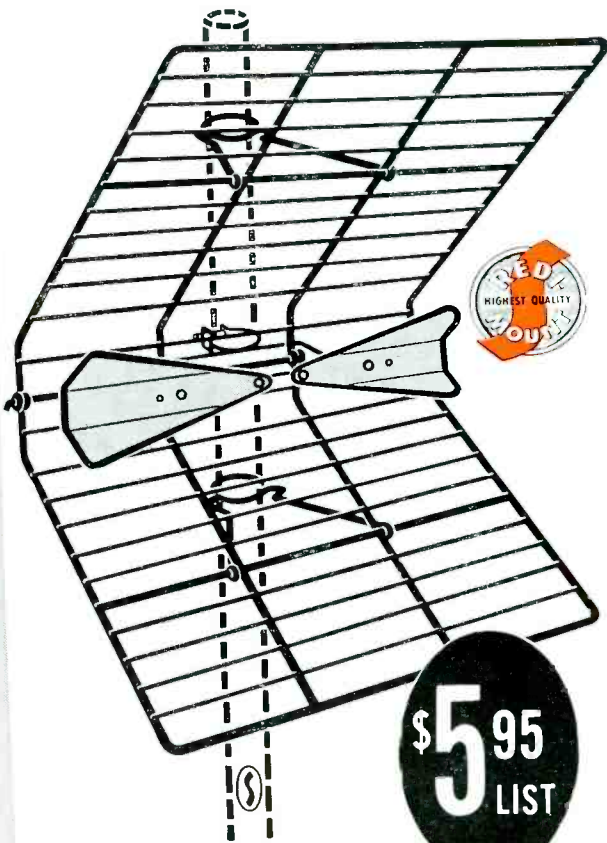**QUICKER**


**NEW UHF-6**  
BOW-TIE  
W/CORNER REFLECTOR



**\$5.95**  
LIST

**NEW UHF-5**  
BOW-TIE  
W/REFLECTOR

**\$2.95**  
LIST

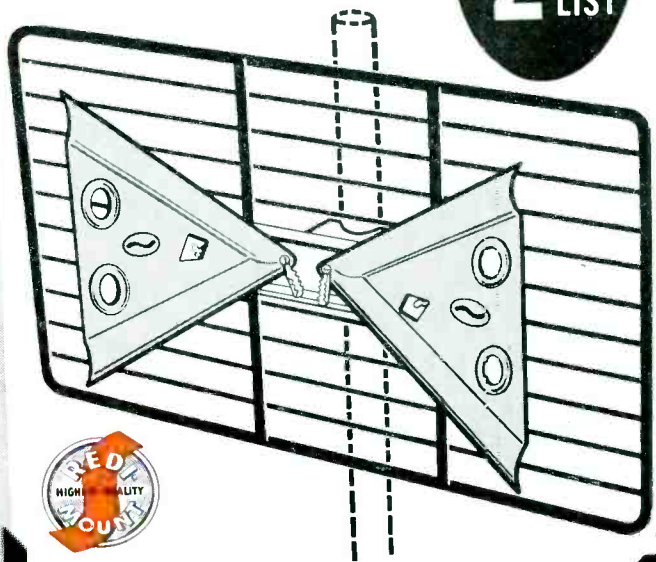

**UHF-5 & UHF-6**  
**FEATURES**

- Factory Pre-Assembled
- Hi-Tensil Aluminum Bows
- Universal U-Clamps; All-Welded Steel Screens; All-Weather Zinc Plated

*Unfold - Tighten - Erect*

**SNYDER MFG. CO.**

**ANTENN-GINEERS®**  
PHILADELPHIA, U.S.A.

BELLEVUE TUBE MILL, INC., PHILADELPHIA, A *Snyder* AFFILIATE  
SNYDER ANTENN-GINEERS LTD., TORONTO, CANADA, A *Snyder* AFFILIATE  
WORLD EXPORT: ROBURN AGENCIES, INC., NEW YORK 7, N.Y.



# Have you hung up

# *your shingle?*

IT PAYS TO KEEP GOOD COMPANY . . . and it's good business to advertise the good company you keep.


Thousands of dealers and servicemen are using the sales-magic in the RCA name to instill confidence in their customers. Identifying *your* name with RCA pays off in dollars and cents.

And it's so easy to do . . . because RCA's new Dealer Identification Program provides you with a handsome "shingle" with your name on it, that you'll be proud to display in your shop. When a customer sees this Dealer Identification Plaque he *knows* you are using the best tube products available.

So, we ask . . . "Have you hung up *your* shingle yet?" If not, be sure to see your **RCA Tube Distributor** today and learn how *you* can qualify for a Registered Dealer Plaque at no extra cost.
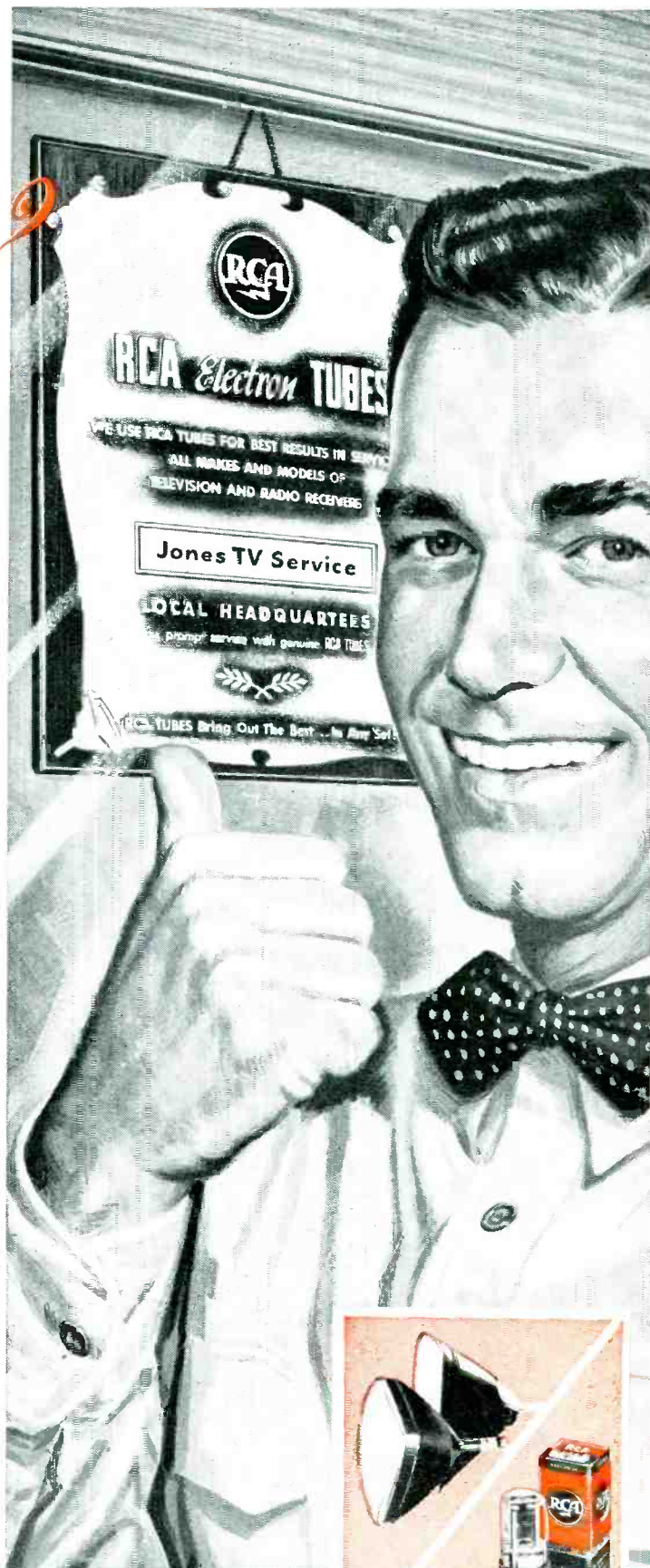
### Unlock the door to bigger profits

Here's *your* key to better business . . . RCA's dynamic Dealer Identification Program. Ask your *RCA Tube Distributor* for your copy of the colorful, 16-page booklet "A Magic Pass-Key to Customer Confidence." It tells you how — for the first time — you can become a Registered Dealer . . . and get *extra* sales benefits.



**RADIO CORPORATION of AMERICA**  
ELECTRON TUBES

HARRISON, N. J.