


May, 1955



*Radio-Television*  
**SERVICE  
DEALER**

TV-AM-FM-RADIO-ELECTRONICS


# PA in supermarkets

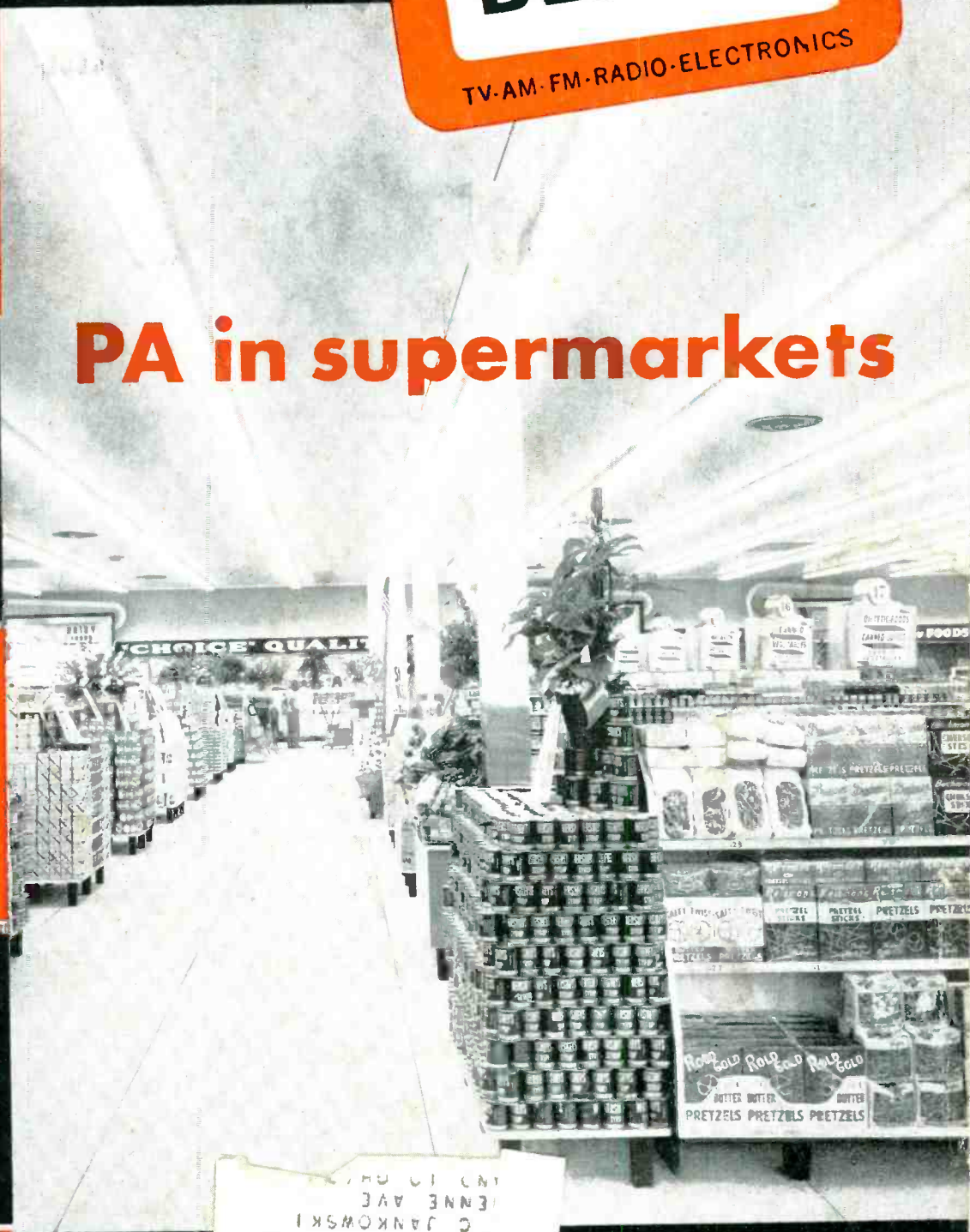

284 14 JAN 56  
C JANKOWSKI  
ENNE AVE  
AND 10 RHT



# Preferred for modern set servicing

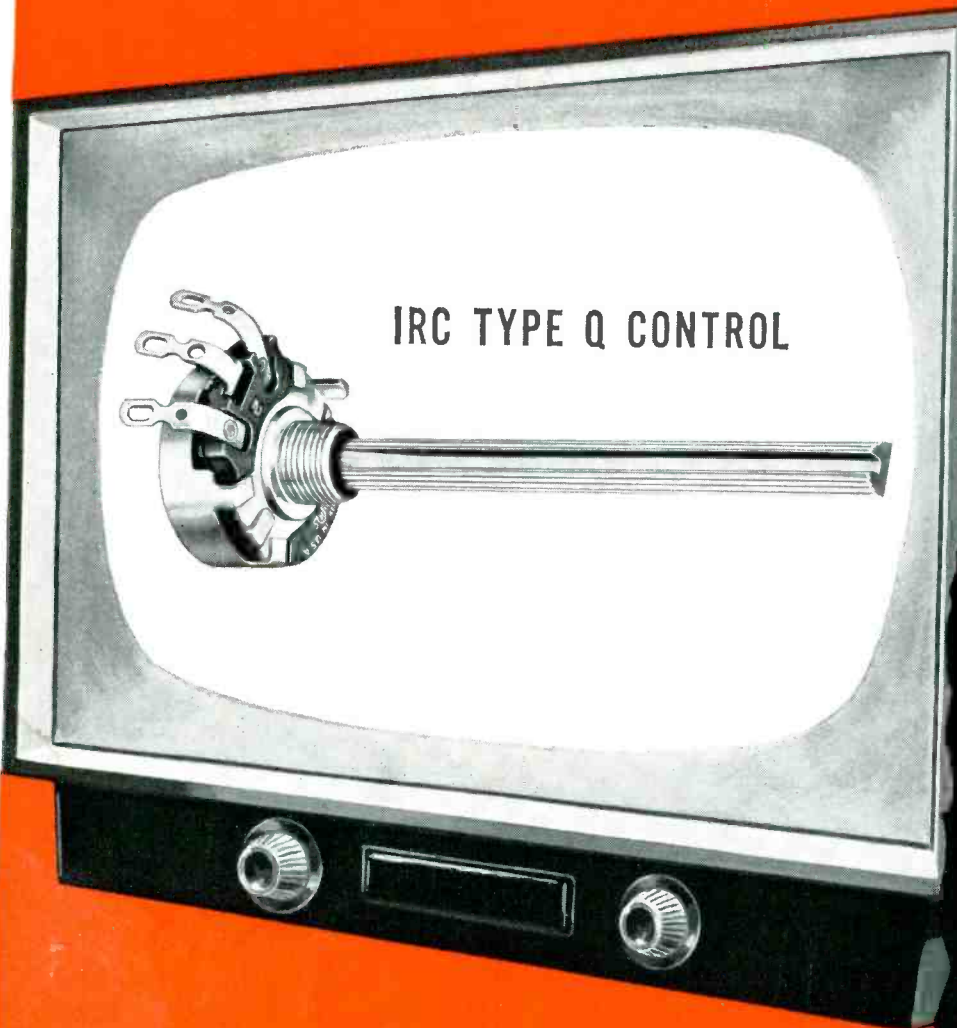

Service technicians get greater coverage with less investment; more practical service features; and easier, faster installation with the IRC Type Q Control. Here's a dependable, basic control that is directly designed for modern set servicing. For appearance, performance and price... there's none better. So why settle for less? Tell your Distributor you want Q Controls... most servicemen do.



This 8 page catalog gives you all the facts... Send for your free copy now—

## INTERNATIONAL RESISTANCE CO.

Dept. 492, 401 N. Broad St., Phila. 8, Pa.

In Canada: International Resistance Co., Ltd., Toronto, licensee

Send me Q Control Catalog DC1D.

Name \_\_\_\_\_

Company \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_

### KNOBMASTER FIXED SHAFT

Q Control standard shaft is knurled, flatted and slotted — fits most knobs without alteration.

### INTERCHANGEABLE FIXED SHAFTS

Exclusive IRC convenience feature — provides fast conversion to "specials", with FIXED shaft security. 15 types available.

### 1/4" LONG BUSHING

Accommodates all small sets, yet handles large set needs perfectly.

### 7 STANDARD TAPERS

Full coverage of all taper requirements is provided in the Q Control.

### 94 RESISTANCE VALUES

For TV, AM and FM coverage, 94 values of plain and tapped controls are furnished.

### QUALITY APPEARANCE

The handsome professional appearance of IRC Q Controls lets you point to your work with pride.

### CUSHIONED TURN

The smooth, quality of "feel" of a Q Control contributes to customer confidence.

### TYPE 76 SWITCHES


Either of two type IRC switches attached as quickly and easily as a control cover — meets all your requirements.



Wherever the Circuit Says

# SETTING THE PACE . . .

in **ALL-CHANNEL**  
fringe antennas!

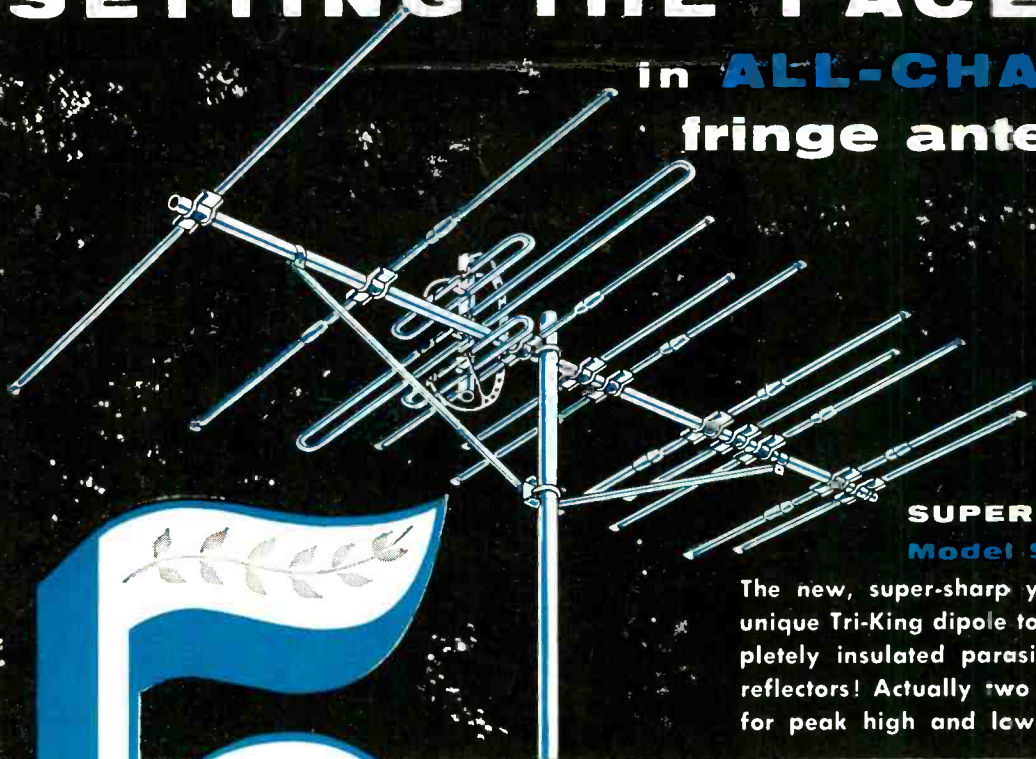

**SUPER SUN BEAM**  
Model SB662


The new, super-sharp yagi utilizing the unique Tri-King dipole together with completely insulated parasitic directors and reflectors! Actually two antennas in one for peak high and low band reception.



Clear Beam's **5** peak performers solve all fringe problems\* . . .


**TRI-KING**  
Model TK1500

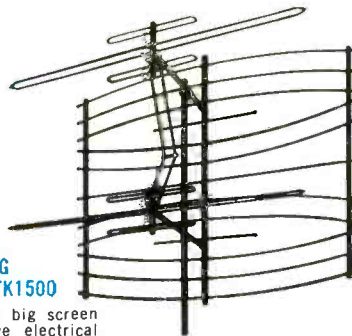Highest gain of the big screen antennas! Half wave electrical spacing. Eliminates ghosts and co-channel interference. Full radar screen - wind tunnel tested!



**BIG CHIEF**  
Model BC12-2

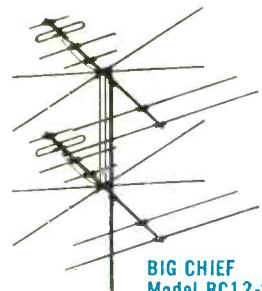An advanced conical-Yagi with element diameters varied for precision tuning, matched sensitivity and peak performance on high and low band!



**SKY SWEEP**  
Model MYS80

A deep fringe yagi incorporating the new magnetic "Focal-Sharp" design for concentrating signal strength!



**HUNTER** Model MYH50

New wave trap principle gives extremely high gain, sharp directivity, in-phase tuning on all channels. New, flat design for low wind resistance!



\*Spectrum-tested for balanced color reception!

affiliated with  
TEMPO TV products




**CLEAR** ANTENNA CORP.  
**BEAM** Canoga Park, Calif. • Chicago, Ill.

Warehouses in Seattle, Portland, San Francisco, Honolulu, Dallas, Kansas City, Chicago, Detroit, Baltimore


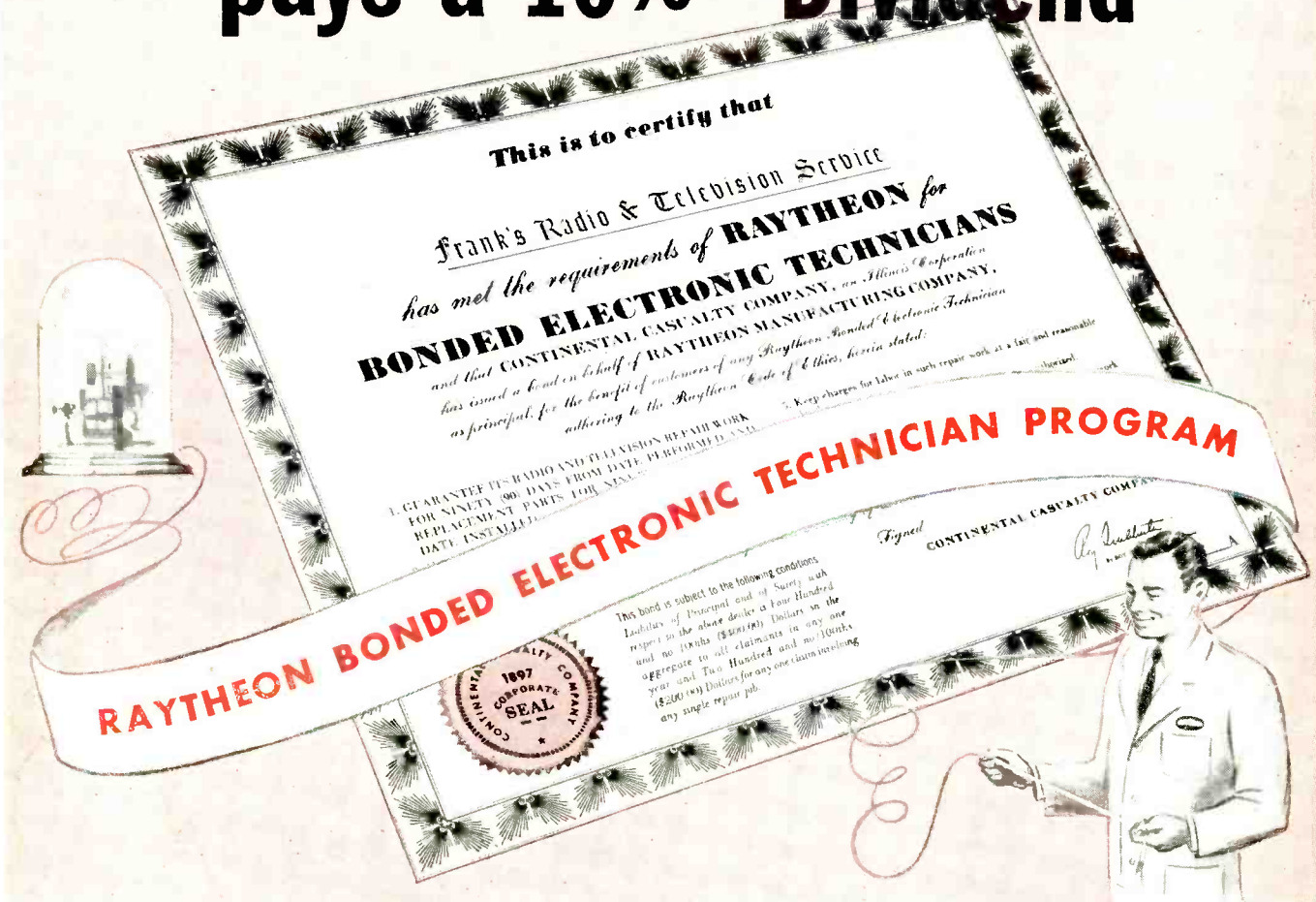
# this **RAYTHEON** "Bond" .... pays a 10% "Dividend"\*



If you are interested in increasing your Radio & TV Service business and profits 10% or more call the Raytheon Tube Distributor in your area right now.

Ask him to tell you how the Raytheon Bond gives you a national backing of your 90 day guarantee, increases customer confidence in you and your shop.

Ask him to show you the many free business builders — Creed Displays, Decals, Certificate, Identification Cards, ad mats, etc. — that Raytheon makes available to you to help you tell your customers and prospects you're "Bonded".

Ask him about the Raytheon national advertising that makes it easy for you to get more business and then ask him if you can qualify for this exclusive Raytheon business builder. If you can, it costs you nothing — it's Raytheon's investment in your future.

\*Recent surveys prove the Raytheon Bonded Program improves business by at least 10 per cent.



**RAYTHEON MANUFACTURING COMPANY**  
Receiving and Cathode Ray Tube Operations  
Newton, Mass. • Chicago • Atlanta, Ga. • Los Angeles, Calif.

Raytheon makes all these: Receiving and Picture Tubes • Reliable Subminiature and Miniature Tubes • Semiconductor Diodes and Transistors • Nucleonic Tubes • Microwave Tubes





**EVERY SERVICE FIRM OWNER IN THE U.S.A.  
Receives SERVICE DEALER Monthly  
Distribution of this Issue over 71,000**

Member **EPA**—Circulation Statement sent on request

**COWAN PUBLISHING CORP., 67 West 44th Street, New York 36, N. Y.**

VOL. 16, NO. 5

MAY, 1955

**EDITORIAL STAFF**

*Publisher*

**SANFORD R. COWAN**

*Editor*

**SAMUEL L. MARSHALL**

*Editorial Production*

**ROBERT CAMPBELL**

*Contributing Editors*

**ROBERT T. DARGAN**

**PAUL GOLDBERG**

**OSCAR FISCH**

**SAN D'ARCY**

*This month's front cover was made possible by the cooperation of the following firms: University Loudspeakers, Inc., David Bogen Co., Inc., Lowell Mfg. Co., Inc., Shure Brothers, Inc., and Magnecord, Inc.*

**BUSINESS STAFF**

*Advertising Manager*

**HARRY N. REIZES**

*Advertising Sales*

**LAWRENCE STEINER**

*Production Manager*

**DAVID SALTMAN**

*Circulation Manager*

**HAROLD WEISNER**

*Ass't Circ. Mgr.*

**C. J. BINDERMAN**

**BRANCH OFFICE**

**LOS ANGELES**

**TED E. SCHELL**

**2700 West Third Street**

**Dunkirk 2-4889**

**FEATURE ARTICLES**

<b>Series Filaments, by Steve Travis</b> .....	7
<i>A significant step in modern tube development</i>	
<b>Servicing with the Square Wave Generator, Part 3, by Oscar Fisch</b> .....	11
<i>Simplified waveform analysis related to square wave measurements</i>	
<b>P.A. in Supermarkets, by Gene Hessel</b> .....	23
<i>An opportunity for profits in a non-seasonal and specialized radio-TV field</i>	
<b>Broad Band Antenna Systems, by Douglas H. Carpenter</b> .....	29
<i>The design of all-channel antenna systems yielding high single-channel performance on every vhf channel</i>	
<b>Chrominance Systems in Color TV Receivers, part 6, by Bob Dargan and Sam Marshall</b> .....	32
<i>Explanation of high level 2-triode demodulation</i>	
<b>Microphonic and Sound Bar Problems, by Paul Goldberg (a Work Bench Feature)</b> .....	35
<i>Techniques involved in the elimination of sound bars in TV receivers</i>	
<b>Circuit Analysis, by the RTSD Technical Staff</b> .....	36
<i>Admiral 21A3Z—Voltage distribution</i>	
<b>Peak to Peak VTVM, by Harry C. Ashley and Philip Portnoy</b> .....	44
<i>For efficient peak to peak measurement of complex and sine wave forms</i>	
<b>TV Service Information Sheets</b> .....	65-72
<i>Complete preliminary service data for Stromberg Carlson 625 series</i>	

**CIRCUIT AND SERVICE FORUM**

<b>The Work Bench</b>	
Du Mont RA 109: Sound Bars in Pix .....	35
Admiral 19E1: Microphonic .....	35
<b>Circuit Analysis</b>	
Admiral 21A3Z—Voltage distribution .....	36
<b>Video Speed Servicing Systems</b>	
Emerson Model 680D, ch. 120140-B .....	37
Motorola ch. TS-525 .....	39
<b>Rider TV Field Manual Service Data Sheets</b>	
Sentinel Model 1U-581,-582,-584,-585 .....	41
<b>Answer Man</b>	
6BQ7 replacement in Standard Coil Tuner .....	46
Frequency response of Oscilloscope .....	46
19R20 Zenith—Noise .....	47

**DEPARTMENTS**

<b>Editorial</b> .....	4	<b>Circuit Analysis</b> .....	36
<b>Trade Flashes</b> .....	9	<b>Answer Man</b> .....	46
<b>Association News</b> .....	20	<b>New Products</b> .....	48
<b>Work Bench</b> .....	35	<b>Trade Literature</b> .....	49
<b>Advertising Index</b> .....		<b>64</b>	

RADIO-TELEVISION SERVICE DEALER is published monthly by Cowan Pub. Corp., 67 West 44th St., New York 36, N. Y. Subscription price: \$1.00 per year in the United States, & U.S. Poss. Elsewhere \$1 per year additional. Single Copies 25c. Second Class mail privileges authorized at New York, N.Y. Copyright 1955, Cowan Publishing Corp.

POSTMASTER: SEND FORM 3579 TO RADIO-TELEVISION SERVICE DEALER, 67 WEST 44th ST., NEW YORK 36, N. Y.





# EDITORIAL...

by S. R. COWAN  
PUBLISHER

## Color TV Outlook

Those of us who are privileged to watch and compare color TV programs with their black and white counterparts acknowledge that color is finer in every way. For pleasurable viewing black and white is third rate compared to color. That being so, why is color so slow in coming?

Interrogation of leading manufacturers about their 1955 color TV production schedules discloses conflicting opinions; but none at great variance. Estimates are that from 30 to 80 thousand color TV sets will be produced this year—unless—something unforeseen at the moment occurs shortly.

Frankly, say most "TV experts", the biggest deterrent to mass color TV set production is the picture tube problem; primarily its cost.

Picture tube makers are fully cognizant of what's expected of them. Their engineering and research staffs are working "all out" on the project. Success may be hours, days or months away. Honestly, no one knows at this minute when the problems will be solved. Your guess is as good as mine.

## Tube Tester Innovation

For years we have urged service dealers to charge customers, who come into their shops with a bag of tubes, a nominal sum for each tube tested. The charge is justified. It helps pay for the cost of tube testers. Also, it pays in part for the time the service dealer devotes to his customer. Most service dealers followed our recommendation about charging for this service, some preferred not to do so.

Now an instrument manufacturer has put on the market a "Test-It-Yourself" type of tube checker which service dealers can buy and place in a location convenient for their customers to use themselves. In this age of "do-it-yourself" merchandising we believe the instrument manufacturer in question has hit upon an excellent idea. Human nature is such that many customers would prefer to do their own tube testing, and abide by their own findings. Be that as it may, we like the Test-It-Yourself idea for an entirely different reason. We feel that some "doubting Thomas" species of human will, after setting numerous knobs and levers on the checker, come to appreciate more fully the complex nature of electronic equipment design and the skill required by servicemen. And as a net result, henceforth they will hold servicemen in higher esteem. Besides, they'll buy more tubes—especially when they themselves find tubes which an impartial checker shows as being "weak."

## Service Field Magazines

According to the latest reports issued by firms that are engaged to audit the paid circulation and gross distribution figures of magazines, proudly we announce that "Service Dealer" has many more paid subscribers and thousands more servicemen readers than our contemporary publications.

Since the inception of "Service Dealer" over 16 years ago our prime goal has been to improve the financial position of all radio-TV service dealers and to enhance their recognition and public acceptance. We hope to improve the service profession's living standard in every respect. It has not been an easy task—and as a task—it is far from being finished.

But it is truly gratifying to know that month after month more professional full time servicemen and owners of established firms that do servicing are readers of this magazine than any other. Our entire staff's efforts are solely pointed to the serviceman's and service profession's welfare. Its a comforting thought that upwards of 60,000 full-time professionals are part of our family.

## Technical Courses By Manufacturers

Many leading manufacturers have conducted seminars for servicemen in all parts of the country. Many of these courses are streamlined to such an extent that they are not of optimum effectiveness.

Rarely does a clinic include instruction on servicing other electronic apparatus such as FM tuners, phonograph record players, Hi-Fi equipments, automobile or 2-way communications receivers, etc. For example, how many lecturers have you heard discourse on servicing *any* of the myriad types of industrial electronics equipment? Thousands of G. M. cars have headlights controlled by autronic eyes. Could you service such an electronic device? Probably not, unless you took the Delco Radio Course, given free by United Motor Service.

Believe it or not, all around every service shop there are millions of electronic tubes functioning in devices that are not home radio or TV receivers. Hundreds of millions of dollars worth of potential service income on non-radio-TV items are bypassed annually by the average service firm. The bulk of this business, and it's mighty profitable business too, goes to a limited number of astute firms that have had the foresight not to rely solely on radio-TV. They don't have "all their eggs in one basket." We'll cover this broad subject in the months ahead.

MODEL TR-11  
MODEL TR-12

MODEL TR-4

the MOST  
COMPLETE  
LINE

MODEL TR-2

MODEL AR-1  
MODEL AR-2

**C·D·R**  
**R O T O R S**

*featuring the SHARPEST tuning  
Automatic Rotor*

with the **GREATEST TURNING POWER**

Here is everything anyone — distributor . . . dealer . . .  
serviceman — could ask for in rotors . . . all in the ONE line  
. . . the CDR ROTOR LINE! A model for every need . . . ALL  
FIELD TESTED AND PROVEN to be dependable and  
superior in every respect!



*Pre-Sold* for you to millions every week  
with regular announcements in every leading  
rotor market across the nation.



**CORNELL-DUBILIER**  
SOUTH PLAINFIELD, N. J.



**THE RADIART CORP.**  
CLEVELAND 13, OHIO





**“I WANT  
THE TUBES WITH  
THE GOOD  
HOUSEKEEPING  
GUARANTY SEAL!”**

“TV and radio tubes are mysterious things to me, but that Good Housekeeping Seal is a tried and true friend. I trust any product that has earned it. So when you replace tubes in my sets, be sure they’re CBS tubes . . . the tubes with the Good Housekeeping Guaranty Seal.”



**Check and Remember**

- 1** It's a *women* you talk to on most service calls.
- 2** CBS is addressing its national advertising especially to women.
- 3** 53% of *all women* are influenced in their purchases by the Good Housekeeping Guaranty Seal.
- 4** CBS tubes have that Seal.

*Use CBS tubes . . . the tubes in which women have confidence.*



Millions will see or hear about CBS tubes on TV and radio . . . and in national magazines throughout 1955.

**GET YOUR NEW  
CBS Tube SALES PROMOTION KIT**

*Ask your CBS tube distributor for special offer . . . or mail \$2.00 direct for complete Kit.*



**CBS-HYTRON**, Main Office: Danvers, Massachusetts  
A Division of **CBS** . . . the Columbia Broadcasting System, Inc.

A member of the CBS family: CBS Radio • CBS Television • Columbia Records • CBS Laboratories • CBS-Columbia • CBS International • and CBS-Hytron



# SERIES

# SERIES

# SERIES

# SERIES

# SERIES

# filaments

using the new 600 ma. tubes

by Steve Travis

WITHIN the past few months a significant step has been taken in television receiver design that will have a far reaching affect upon future circuitry. It is the purpose of this article to present the information concerning this advancement.

The improvement referred to has been brought about by the introduction of a new group of vacuum tubes. These tubes are similar to previously common prototypes but for one very distinct difference, that is, they are designed to allow the same amount of filament current to flow through all of them. Thus, although they use various voltage values across their filaments such as 3.15, 4.7, 6.3, 7, 12.6, and 25.2 volts, they are engineered to pass 600 ma through the heaters. These tubes are referred to as the 600 ma group.

Before delving into service information concerning these 600 ma tubes a greater appreciation of their purpose will be gained by a knowledge of the situation before their advent on the TV scene. In the design of ac/dc radios the connecting of vacuum tube filaments in series has been a common practice. The voltage across each tube filament is that required by the tube, and the total voltage across the series string should be the sum of the voltages across all the filaments plus the voltage drop across the voltage dropping filament resistor if one is used. This total adds up to the line voltage of 115 volts. With an arrangement of this type it is evident that there is no need for a power transformer winding since all the filaments of the tubes in the radio are connected in series across the power line.

Television receivers have been designed using this arrangement, but these receivers have not been too common because of the problems arising

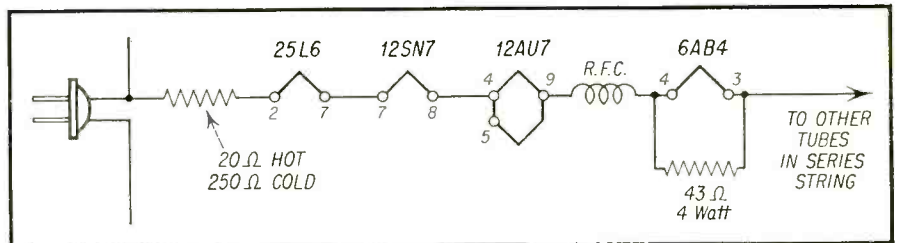


Fig. 1—Partial schematic of conventional series group. Series resistor on left is a thermistor the resistance of which is higher when cold.

from the differences in heater current ratings and the variations in heater warm-up time. Furthermore, as shown in Fig. 1, when connecting up tubes drawing 300, 450 and 600 ma of filament current in series additional provisions are required such as paralleling resistors or other tubes to bypass the proper portion of the heater current from those tubes that cannot carry the full current.

Figure 1 indicates that if a 600 ma tube is in the string there must be 600 ma flowing through the whole series circuit. Tubes which require less than 600 ma must have a shunt to bypass the remainder of the current around them. As an example, a tube which uses 450 ma filament current generally has a 42 or 43 ohm resistor in parallel with it ( $6.3V/.15A = 42$  ohms) to allow the balance of 150 ma to flow so that the total current will be the amount that flows through the entire series circuit. As can readily be seen, if this tube is removed from the socket for checking purposes while the set is in operation additional trouble is introduced. The shunt resistor usually becomes overheated and burns out. Thus, the problems of servicing receivers of this type are generally more difficult.

One of the more important reasons

for the unpopularity of series filament receivers is caused by improper voltage distribution which occurs while the heaters are warming up. This is the direct result of the warm-up periods of television circuit tubes not being equal. When a tube is cold the heater resistance is low. This resistance increases during the initial period to several times the cold value when it reaches its proper operating condition. The heating period or the time required to reach normal operating temperature is a function of the design of the heater. Because of the different cathode designs of various tubes, different physical forms or windings of heaters are required. As one example, the area of the emitting material that is to be heated in a picture tube is a spot 35/1000 of an inch on the face of the cathode element. This requires a type of filament winding different from that employed for other tubes such as a 5U4 or a 6BQ7 tube to bring the material on the cathode to its proper emitting temperature.

The voltage distribution across a string of filaments is determined by the resistance of the individual filaments. As stated previously, the resistance of the heaters increases as the tube warms up. But all tubes don't warm up or reach the proper operating temperature

Table One — The New 600 Milliampere Tubes

600 Ma. TUBE	PROTO-TYPE	Filament Voltage	TYPE	CONSTRUCTION	CIRCUIT EMPLOYMENT
2AF4	6AF4	2.35	7 Pin Miniature	Triode	UHF Osc.
3AL5	6AL5	3.15	7 Pin Miniature	Twin Diode	FM Detector
3AU6	6AU6	3.15	7 Pin Miniature	Pentode	IF Amp.
3AV6	6AV6	3.15	7 Pin Miniature	Twin Diode, Triode	Detector, Audio Amp.
3BC5	6BC5	3.15	7 Pin Miniature	Pentode	IF Amp.
3BE6	6BE6	3.15	7 Pin Miniature	Pentagrid	Converter
3BN6	6BN6	3.15	7 Pin Miniature	Pentode	FM Discriminator
3BZ6	6BZ6	3.15	7 Pin Miniature	Pentode	High Freq. Amp.
3CB6	6CB6	3.15	7 Pin Miniature	Pentode	High Freq. Amp.
3CF6	6CF6	3.15	7 Pin Miniature	Pentode	IF Amp.
3CS6	6CS6	3.15	7 Pin Miniature	Pentagrid	Sync. Sep.
3BY6	6BY6	3.15	7 Pin Miniature	Pentagrid	Amplifier
4BQ7A	6BQ7A	4.2	9 Pin Miniature	Twin Triode	RF Amp.
4BZ7	6BZ7	4.2	9 Pin Miniature	Twin Triode	RF Amp.
5AM8	6AM8	4.7	9 Pin Miniature	Diode, Pentode	Video Det., IF Amp.
5AN8	6AN8	4.7	9 Pin Miniature	Triode, Pentode	Video Det., IF Amp.
5AQ5	6AQ5	4.7	7 Pin Miniature	Pentode	Video Amp.
5AT8	6AT8	4.7	9 Pin Miniature	Triode, Pentode	Osc. Mix.
5BK7A	6BK7A	4.7	9 Pin Miniature	Twin Triode	RF Amp.
5J6	6J6	4.7	7 Pin Miniature	Twin Triode	Osc., Mix.
5T8	6T8	4.7	9 Pin Miniature	Triple Diode, Triode	FM Det., Audio Amp.
5U8	6U8	4.7	9 Pin Miniature	Triode, Pentode	Osc., Mix.
5V6GT	6V6GT	4.7	8 Pin Octal	Pentode	Low Freq. Amp.
5X8	6X8	4.7	9 Pin Miniature	Triode, Pentode	Osc., Mix.
5AS8	6AS8	4.7	9 Pin Miniature	Pentode	Detector, Video Amp.
6AX7	12AX7	3.15	9 Pin Miniature	Twin Triode	Sync. Amp., Sep.
6AU7	12AU7	3.15	9 Pin Miniature	Twin Triode	Hor. Osc.
6AW8	6AW8	6.3	9 Pin Miniature	Triode, Pentode	Sync. Sep., Video Amp.
6S4A	6S4	6.3	9 Pin Miniature	Triode	Vertical Output
6SN7GTB	6SN7GTA	6.3	8 Pin Octal	Twin Triode	Hor. and Vert. Osc.
7AU7	12AU7	7	9 Pin Miniature	Twin Triode	Hor. and Vert. Osc.
12B4A	12B4	6.3	9 Pin Miniature	Triode	Vertical Output
12BH7A	12BH7	6.3	9 Pin Miniature	Twin Triode	Vertical Osc.
12BY7A	12BY7	6.3	9 Pin Miniature	Pentode	Video Amp.
12AX4GTA	12AX4GT	12.6	6 Pin Octal	Diode	Damper
12BK5	6BK5	12.6	9 Pin Miniature	Pentode	Audio Output
12BQ6GTA	6BQ6GTA	12.6	7 Pin Octal	Pentode	Hor. Output
12CU6	6CU6	12.6	8 Pin Octal	Pentode	Hor. Output
12L6GT	25L6GT	12.6	8 Pin Octal	Pentode	Audio Output
12W6GT	6W6GT	12.6	7 Pin Octal	Pentode	Vertical Output
25CD6GA	25CD6G	25	6 Pin Octal	Pentode	Hor. Output

at the same time because of their inherent designs and purposes. It is only when the tubes have attained proper filament temperature that the resistances are correct and produce the desired voltage drops across them. Therefore, during the warm-up period the line voltage divides across the series line according to the instantaneous values of tube resistances. Since the IR drop (voltage drop) across any filament is proportional to its resistance, one tube may have more voltage impressed on it than another. This is one of the reasons for tube burnouts in circuits of this type.

One of the devices used to prevent premature burnouts is the thermistor (See Fig. 1). The latter is a negative temperature coefficient resistor, that is, its maximum resistance occurs when it is cold and its minimum resistance when it is hot. This property compensates for the opposite manner in which tube heaters behave. However, expense and long warm-up considerations have forced the tube industry to come up with a better answer.

### The New 600 Milliamperes Tubes

Very recently there has been introduced a complete line of 600 ma filament current tubes for all of the functions required in a TV receiver. With these 600 ma tubes the series circuit will certainly become the more common means of connecting vacuum tube filaments just as printed wire panels are fast becoming common in modern TV receivers. Only two major TV receiver manufacturers have not changed to the new 600 ma filament series string as yet. These companies, no doubt, are contemplating their use and will probably have versions available soon. A further important advantage obtained through the use of these new tubes is that it does away with parallel networks completely and permits the tubes to be lined up in series without paralleling the filaments with resistors or other tubes.

To insure dependable performance in these new 600 ma tubes the heater-cathode voltage breakdown rating has been increased; also the tolerance of the 600 ma string tube has been brought to a much closer level concerning the filament current it is designed to conduct. Where formerly, in manufacturing, the tubes were permitted a variation of plus or minus 50 ma, this has been reduced to plus or minus 25 ma in those tubes designated for series filament use. In addition, the use of larger filament wire size provides an added ruggedness to the new group.

Perhaps the most important feature that has been designed into the 600

[Continued on page 61]



# TRADE FLASHES



Directors of Daystrom, Inc. and Weston Electrical Instrument Corp., have signed an agreement of merger under the terms of which Weston would be merged into Daystrom. The merger calls for the issuance of one share of Daystrom stock for each share of Weston. It is planned that the business and assets acquired from Weston will be transferred to a wholly-owned Daystrom subsidiary to be named "Weston Electrical Instrument Corporation." According to the announcement, the Weston operations will be continued under the same management and personnel as at present, and the Weston name will be retained on its products.

Alpha Wire Corporation, 430 Broadway, New York 3, N. Y., have announced their ALPHLEX line of in stock extruded plastic tubing. It is available in a wide range of sizes and colors, from  $\frac{1}{8}$ " through 2½" diameter, in long lengths and cut to order. It conforms to MIL specs and UL standards, and is competitively priced.

To aid in the selection of the type of linearity which the application of a potentiometer demands while remaining consistent with economic considerations, the Engineering Dept. of Clarostat Mfg. Co., Inc. presents its definitions of four commonly accepted types. These types of linearities are listed, with illustrations, in ascending order of difficulty of manufacture and cost; the brochure is available from the concern at Dover, N. H.

Emerson Radio and Phonograph Corporation has completed its move of the company's administrative headquarters and plant located in the Port Authority Building, 111 Eighth Avenue, New York City. The executive offices have been transferred to the three-story building which was added last year to the Emerson manufacturing plant in Jersey City, New Jersey. The New York factory facilities will also be relocated in the Jersey City plant.

In the belief that nothing is so vital to a television serviceman as accurate information and field-proven servicing techniques, RAM Electronics Sales Company, Irvington, N. Y., has inaugurated a series of TV Forums to be held in every major television area in the

## for servicing *color* **YOU NEED SOMETHING EXTRA**

For instruments actually *ahead* of today's circuitry... ready for the day when color TV becomes as general as today's black-and-white sets... look at the Hycon line, designed with the electronic serviceman in mind. Accurate enough for critical work in the shop, you'll also find these test instruments rugged, compact, lightweight... just what you need for those money-making house calls.

### MODEL 617 3" OSCILLOSCOPE

Designed both for color TV servicing and laboratory requirements. Features high deflection sensitivity (.01 v/in. rms); 4.5 MC vertical bandpass, flat within  $\pm 1$  db; internal 5% calibrating voltage. Small, lightweight... but accurate enough for the most exacting work. SPECIAL FLAT 3" CRT PROVIDES UNDISTORTED TRACE FROM EDGE TO EDGE. **\$269<sup>50</sup>**




### MODEL 614 VTVM

Convenience at unprecedented low cost sums up this rugged, serviceable instrument. Hycon *plus* features include: 21 ranges (28 with p-p scales); large 6½" meter; 3% accuracy on DC and ohms, 5% on AC; AC frequency response to 250 MC (with accessory crystal probe). AND TEST PROBES STOW INSIDE CASE, READY TO USE **\$87<sup>50</sup>**
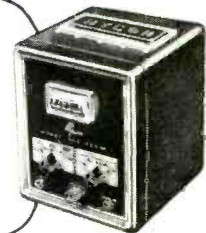
### MODEL 615 DIGITAL VTVM

Ideal for production-line testing and the laboratory, this new VTVM gives *direct* readings, without interpolation. Features illuminated digital scale with decimal point and polarity sign... 12 ranges (AC, DC, ohms)... response (with auxiliary probe) to 250 MC... accuracy: 1% on DC and ohms; 2% on AC. **\$374<sup>50</sup>**




See these latest Hycon money-makers—all in matching, bench-stacking cases—at your local electronic parts jobber.

**Hycon Mfg. Company**  
2961 East Colorado Street  
Pasadena 8, California

"Where accuracy counts"

ORDNANCE · ELECTRONIC TEST INSTRUMENTS  
ELECTRONIC SYSTEMS · AERIAL SURVEYS  
BASIC ELECTRONIC RESEARCH · AERIAL CAMERAS  
GO NO-GO MISSILE TEST SYSTEMS

# THE *American* IDEA

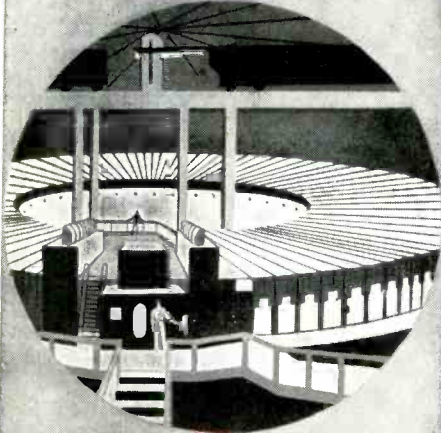

**"To find and follow the better way"...** Gigantic offspring of the cyclotron, the Bevatron—world's greatest magnet—can send masses of protons hurtling around its 135'-diameter race track at almost the speed of light. "Idea", to penetrate deep into the atomic nucleus, where lie secrets of matter and energy.

With us, the "American Idea" is, by directed effort and applied know-how, to continue to lead in bringing you electronic products of the highest quality.



Replacement Phonograph Cartridges

Complete line of  
"Full Vision"  
Microphones  
D-33 Broadcast  
D-22 Public Address



INSIST ON AMERICAN FOR QUALITY

Send for FREE Catalog 47



**American** microphone co.

370 South Fair Oaks Ave. • Pasadena, 1, Calif.

U. S. At the latest of these in New Orleans, La., Mr. Albert Friedman, RAM product development engineer, discoursed and conducted a question-and-answer period on trouble-shooting high voltage sweep and deflection circuits, theory and application of sweep circuits, relation of monochrome sweep circuits to color, and repair and service techniques and hints. More than 250 TV servicemen attended this forum. For details when a RAM forum will be held in your area, write directly to RAM, address above.

A series of 12 television dealer service schools on printed circuits and automation production techniques were held in the Atlanta, St. Louis and Columbia, S. C., distributors' territories during April, it was announced today by Max Schinke, national service manager of Admiral Corporation. Admiral's color motion picture on AUTOMATION was shown at these meetings. In addition, factory technicians demonstrated the servicing and repair of a printed circuit television chassis.

A new replacement flyback transformer, model EFR-148, for early Zenith television models has just been developed by the Rogers Electronics Corporation, 43 Bleecker Street, New York City. The EFR-148 flyback transformer installs easily, without the need for drilling on for further fusing. Every unit is packaged individually with complete schematic wiring diagrams.

The 1955 Electronic Parts Distributors Show officially opens its doors at the Conrad Hilton Hotel here Monday, May 16th at 10:00 A.M., with 289 exhibitors in 203 booths in the Exhibition Halls and 174 display rooms on the hotel's fifth and sixth floors. The Show runs through Thursday, May 19th. Exhibitors from all forty-eight states and nearly a score of other countries are pre-registered for what promises to be one of the most rewarding shows in the industry's history.


Harry G. Burnett, advertising manager of CBS-Hytron, a Division of Columbia Broadcasting System, Inc., has announced the appointment of William O. Hamlin as Supervisor of Technical Information Service. Born at East Orange, N. J., in 1922, and a former resident of Stratford, Conn., Hamlin came to CBS-Hytron from Sylvania, where he was technical editor of Sylvania News.

An experimental transistorized automobile radio that operates directly from a 6-volt car battery and requires only about one-tenth of the power used by a conventional car radio has been describ-

[Continued on page 53]



## NEW TRIAD CATALOGS

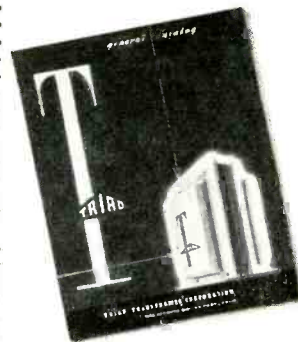

GENERAL CATALOG TR-55  
listing 84 new items



TV-GUIDE TV-155  
giving latest recommendations  
on correct television replacements

Contact your local distributor for these 2 new catalogs or write ...




**TRIAD**  
TRANSFORMER CORP.



4055 Redwood Ave. • Venice, Calif.



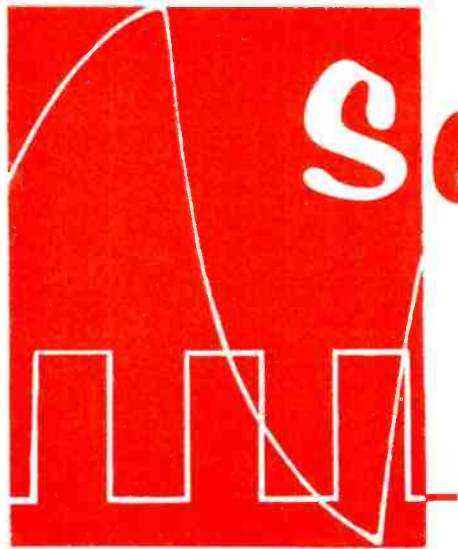

# Servicing

with the

# SQUARE - WAVE GENERATOR

## Part 3—Concluding Installment

by **Oscar Fisch**

**I**N the preceding installment, (April 1955), it was shown that a square wave generator can be useful in localizing trouble to the video amplifier area of the TV receiver. In this connection it was pointed out that before an intelligent diagnosis can be made, the serviceman must know what waveforms to expect when the amplifier is operating normally. A block diagram of the bench setup was given previously Fig. 1 shows a schematic of a typical video amplifier and indicates the manner in which the square wave generator and the scope are connected. Here are a few suggestions which may prove helpful:

1. Remove the video detector tube from its socket. This prevents the possibility of interference from noise or stray pickup signals via the video *if* amplifier.
2. If the receiver uses a germanium diode as a detector, remove the last video *if* tube instead, since the crystal is not easily removed.
3. Remove the horizontal output tube from its socket. This avoids stray pickup of pulses at the horizontal frequency which may interfere with the pattern observed on the scope.
4. Use a low capacity probe in conjunction with the oscilloscope when checking at the higher frequencies. If this is not done rounding of the corners may be observed because of the bypassing effect of the scope leads on the high frequency harmonics components of the wave.

5. Keep the output of the generator as low as possible consistent with a good readable pattern on the scope. This avoids distortion due to overloading either the video amplifier stages or the scope's vertical amplifier.

6. If the scope amplifier introduces too much distortion of its own, connect point "B" of Fig. 1 directly to one of the vertical deflection plates of the scope. The other vertical plate should be grounded. Terminals for this purpose are usually provided at the rear of the scope. You can tell whether the scope amplifier is introducing objectionable distortion by feeding the square wave output of the generator directly into the vertical terminals of the scope, and observing the waveform. A fairly good square wave indicates little distortion by the scope amplifier.

Once these details have been taken care of we can proceed with an observation of wave forms. At the outset, it should be realized there is no substitute for experience, and the technician using a square wave generator should make it a practice, whenever he can, to observe wave forms and correlate them with picture quality. The waveforms shown in following illustrations should be of help for comparison purposes. Fig. 2 shows the output waveform when a 40 cycle square wave was fed into the input of a normally operating video amplifier. At first glance it might seem that this is a seriously distorted wave. However, this is a normal response at this frequency for the average video amplifier. Fig. 3A represents the normal response at 100 cps. Both of these patterns were obtained using an ordinary

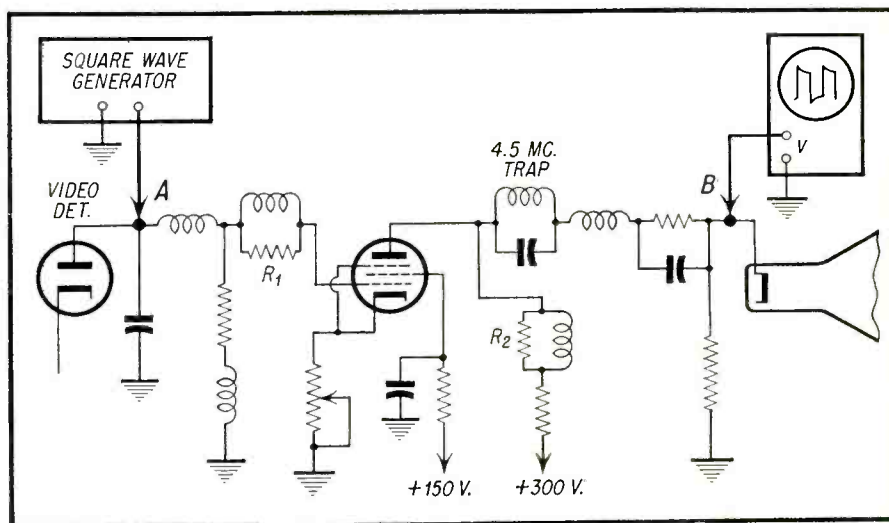


Fig. 1—Typical video amplifier circuit.

when it  
really blows...



YOU CAN STAKE  
YOUR REPUTATION


## on a **TACO** antenna!

*For Color as well as Black and White*


Proved in hurricanes Carol, Edna and Hazel along the East Coast and in many storm areas last year, the Taco spring-loaded assembly is recognized by the trade as the most rugged construction employed in any antenna — at any price! Both Trapper and Super Trapper are high-gain, broad-band antennas, unexcelled in gain across the entire VHF band. These antennas provide phenomenal picture clarity — combined with the most compact and streamlined design.

Get the facts on these two great antennas today. Write or see your Taco distributor.


**WORLD LEADER IN  
TV ANTENNA DESIGN**

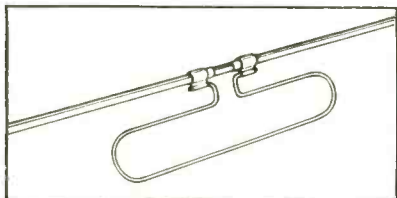

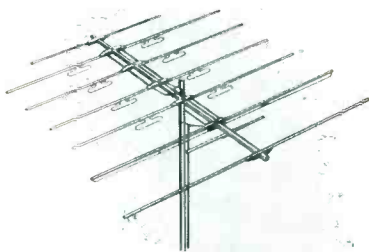The Taco trap\* provides the means whereby streamlined Trappers outperform bedspring type antennas.



**Super TRAPPER**

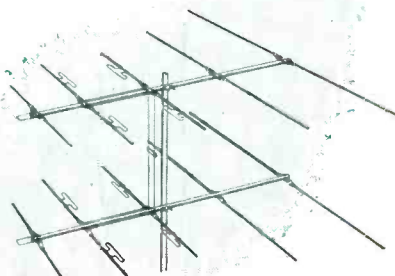

**TRAPPER**

© 1955 \*U.S. Pat. No. 2,705,283

TECHNICAL APPLIANCE CORPORATION • SHERBURNE, N. Y.

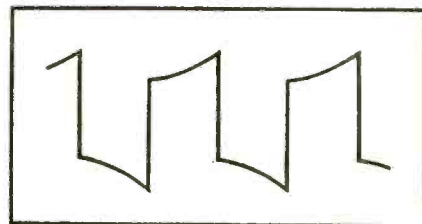


Fig. 2—Waveform of normal amplifier using a 40 cps square wave input signal.

isolating probe for the oscilloscope. (50,000 ohm resistor in series with the vertical test prod of the scope). Using a low capacity makes no observable difference in these two waveforms.

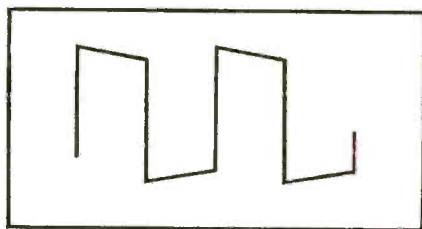


Fig. 3A—Waveform of normal amplifier using a 100 cps square wave input signal.

Figs. 3B, 4, and 5 were the patterns obtained for the normal amplifier at frequencies of 50 kc, 100 kc, and 250 kc respectively, using the resistive isolating probe with the oscilloscope. Figs. 6, 7, and 8 show the waveforms obtained at

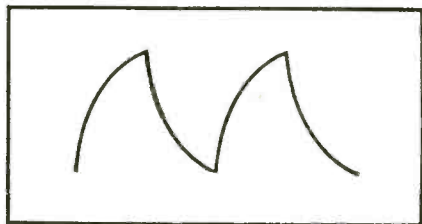


Fig. 3B—Normal amplifier, 50 kc; using a simple resistive isolating probe.

the same frequencies but using a low capacity probe. A comparison of these waveforms with those of Figs. 3A, 4, and 5 shows very strikingly the importance of using this probe. The wave forms of Figs. 3, 4, and 5 are badly distorted,


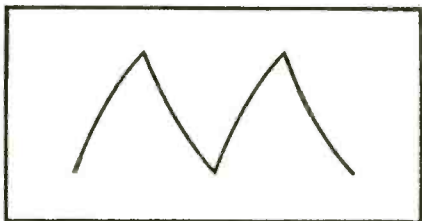


Fig. 4—Normal amplifier, 100 kc; resistive isolating probe is used with the scope.

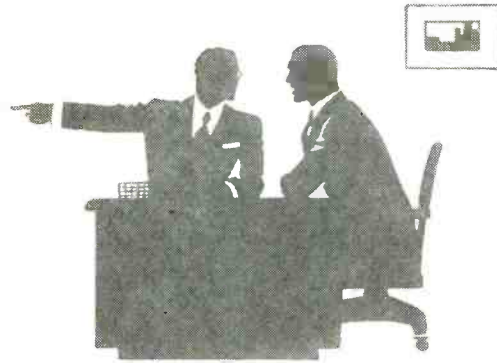

# YOU CAN RELY ON BUSS...



## for Fuses of Unquestioned High Quality

*Here's why*—Millions upon millions of BUSS fuses have given dependable electrical protection in homes, on farms and in industries over the past 40 years, thus establishing the unquestioned high quality of BUSS fuses.


With a reputation like this, BUSS can't afford to take a chance with faulty fuses that could injure its business and yours.

That's why every BUSS fuse, normally used by the Electronic Industries, is tested in a sensitive electronic device that automatically rejects any fuse not correctly calibrated, properly constructed and right in all physical dimensions.

Fuses that give you double protection against loss of user goodwill are the result. Not only are users guarded against damaged equipment when there is trouble on the circuit, but they are also protected against irritating shut-downs caused by needless blows.

Then why not be sure your buying and stock records specify BUSS and FUSETRON fuses . . . you'll save time and trouble by using BUSS as the one source for all your fuse needs.

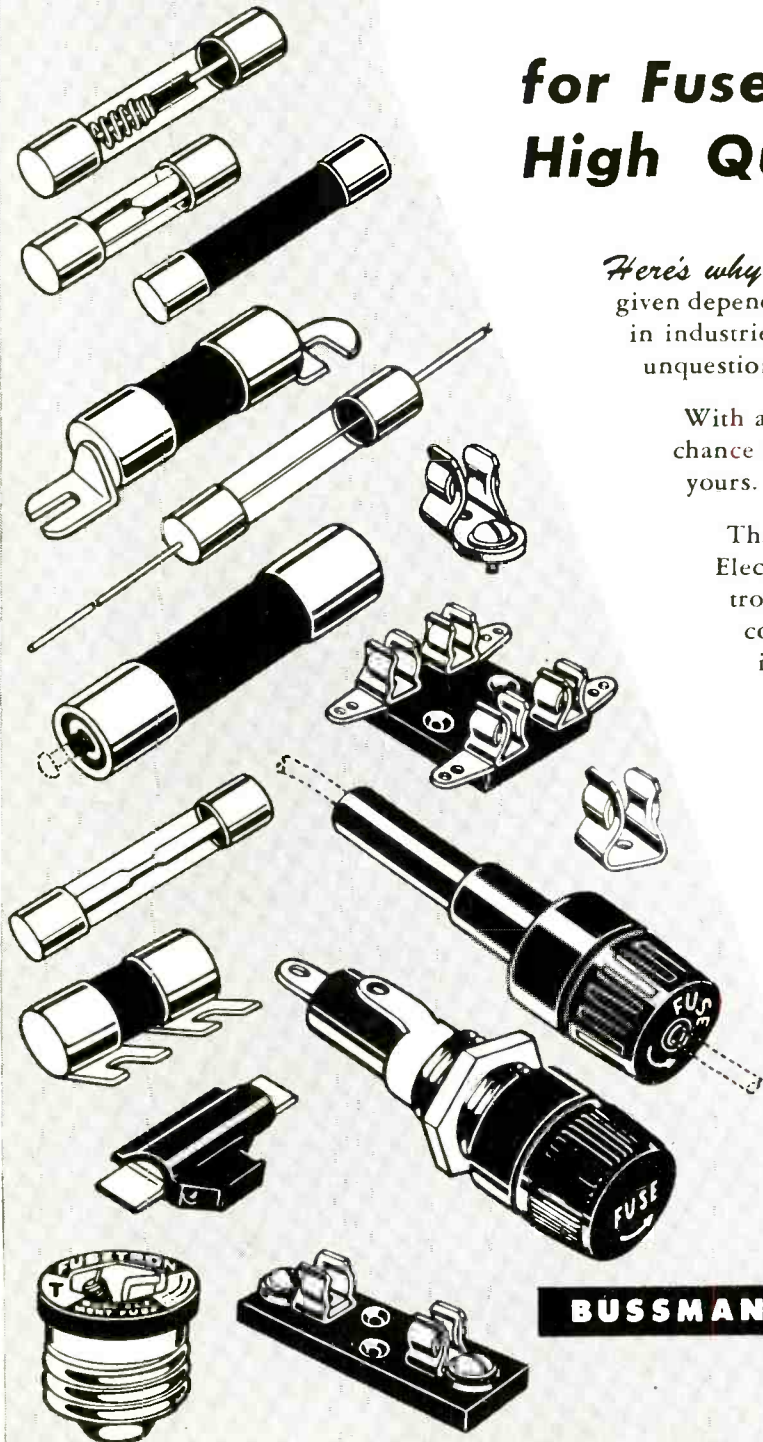Makers of a complete line of fuses for home, farm, commercial, electronic and industrial use.



**BUSSMANN MFG. CO.**



Div. of McGraw  
Electric Co.

University at Jefferson,  
St. Louis 7, Mo.



**\$55.80**  
No extra charge for metal cabinet (suggested net price)

## The P.E.C. you need is at your fingertips

— in this handy, four-drawer  
**Centralab Metal Shop-Pak No. PCK-110**

It's easy to find the P.E.C. you're looking for, when you have a Centralab PCK-110 Kit. There, within easy reach, you have 110 Centralab Printed Electronic Circuits\* — five each of 22 widely used types.

All are packaged in air-tight, sealed plastic envelopes — clearly marked. They are arranged in neat, businesslike order in a four-drawer metal cabinet. So there's no fumbling around to find just the P.E.C. you need.

This handy Centralab assortment is equivalent to a stock of 255 ceramic-based resistors and 305 ceramic capacitors. You have fewer parts to carry — and have less money tied up in inventory.

So save time — and cut your parts investment. Get a Centralab Shop-Pak No. PCK-110 from your Centralab distributor now.

Send coupon for Centralab Printed Electronic Circuit Guide No. 3. It shows circuit schematics to help you install P.E.C.'s.

### One single Centralab P.E.C. replaces several old-style individual components

Trying to locate a shorted or intermittent component in an old-style circuit? Quit wasting your valuable time — replace an entire section with a single Centralab P.E.C. You not only replace the one, worn-out component — you replace all the components of the same age. That way, you make another set-owner happy in the long run and save yourself a costly call-back.

# Centralab

\*Trademark

A Division of Globe-Union Inc.  
944 E. Keefe Ave., Milwaukee 1, Wisconsin  
Send me free copy of Centralab  
Printed Electronic Circuit Guide No. 3.

Name \_\_\_\_\_  
Company \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

Y-1255

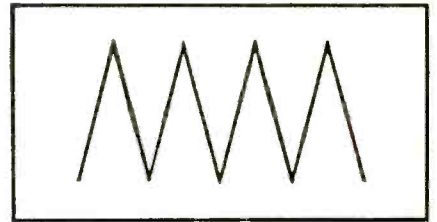


Fig. 5—Normal amplifier, 250 kc; resistive isolating probe is used.

but through no fault of the amplifier under test. In this case the input capacity of the scope plus the capacity of the

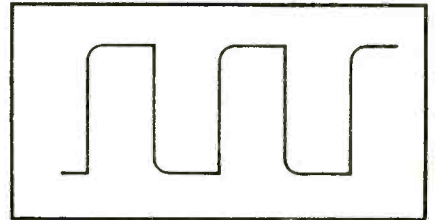


Fig. 6—Same as Fig. 3, but using a low capacity probe with scope.

leads are the offenders. To carry the procedure one step further, waveforms were observed at the same three fre-

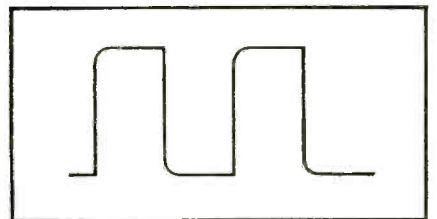


Fig. 7—Same as Fig. 4, but using a low capacity probe with scope.

quencies of 50 kc, 100 kc, and 250 kc, with the video amplifier output connected directly to the vertical deflection

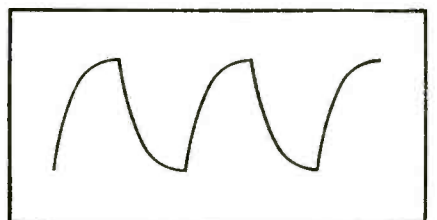


Fig. 8—Same as Fig. 5, but using a low capacity probe with scope.

plates of the oscilloscope. The waveforms observed were essentially the same as those of Figs. 6, 7, and 8 indicating that the scope amplifier was sufficiently good for this purpose.

Figs. 9 and 10 are examples of patterns observed when trouble occurs which seriously affects low frequency response. Possible causes of such trouble



*ask your jobber  
for the whole story  
of the...*

**1st NEW DESIGN  
of selenium rectifiers  
in over 20 years**


because the new Pyramid  
Kool-sel design is so revolutionary

and because its features  
themselves sell so immediately

Pyramid has prepared this  
hand-sized flip chart, which  
tells at a glance all about such

features as No Center  
Mounting and the Secret  
Barrier Layer of Pyramidium  
and explains the principles

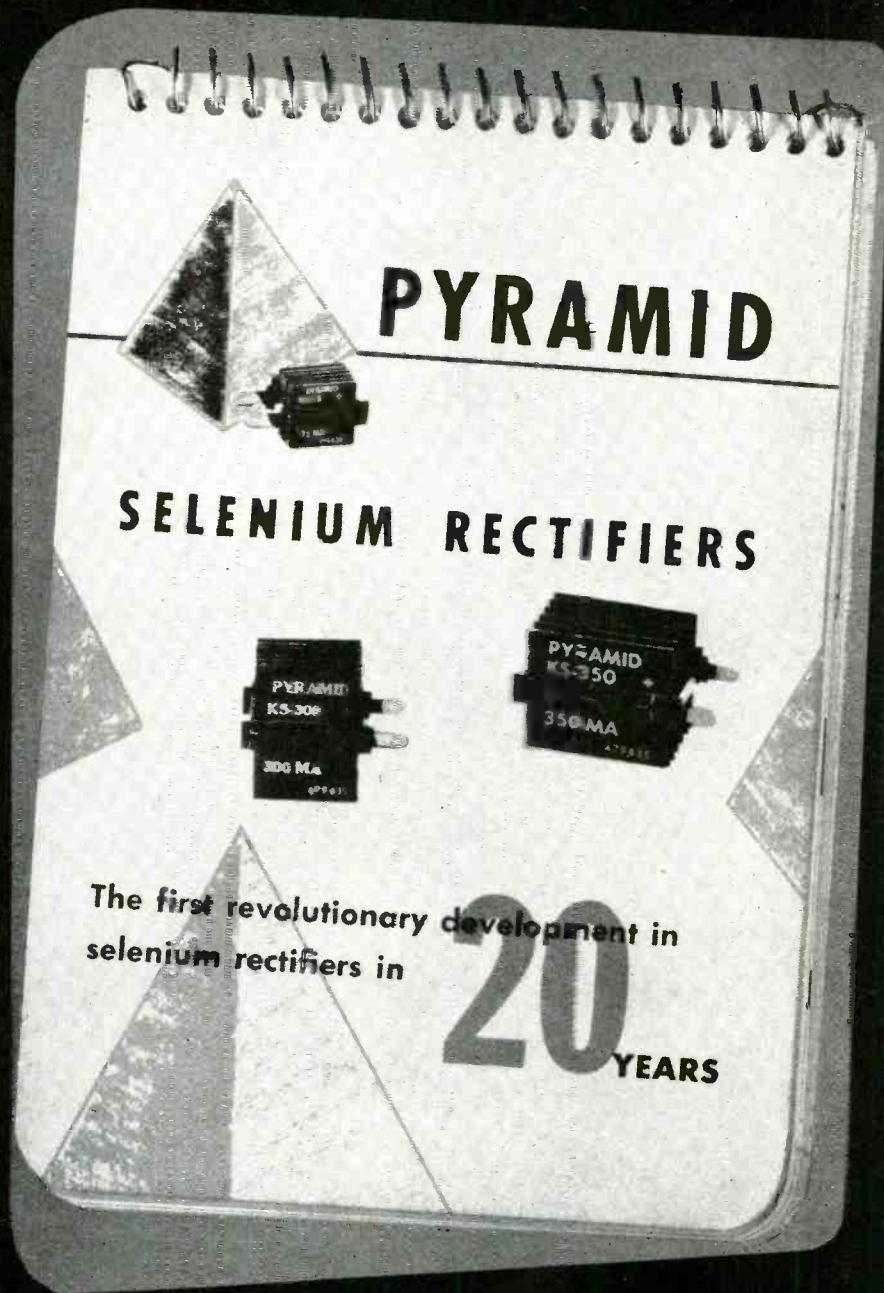that make Kool-sel rectifiers  
superior to any on the market.



DISTRIBUTOR DIVISION

**PYRAMID**

ELECTRIC COMPANY

1445 Hudson Blvd. • North Bergen, N. J.





# AMPHENOL

antennas & accessories for clearer, sharper pictures...
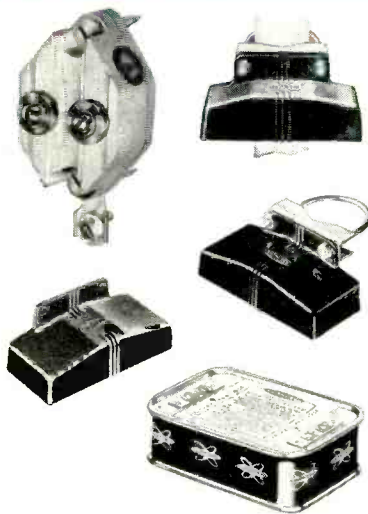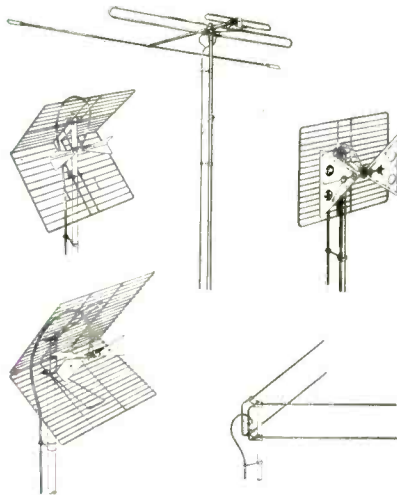
## ANTENNAS

A complete selection of high-gain, top-quality VHF and UHF antennas is offered by AMPHENOL. The color-tested INLINE (Reissue U.S. Pat. 23,273) is still the outstanding VHF antenna today, features high, level gain and stay-up construction. The Corner Reflector, installer's model Lightweight Corner Reflector and the Bo-Ty are superior UHF antennas—exceptionally sturdy, exceptionally high gain. The Stacked-V is a quality VHF/UHF all-channel antenna.




## ACCESSORIES

Every accessory needed for the quality tv antenna installation is available from AMPHENOL. Lightning Arrestors (with and without pipe-mounting strap); Isolating Networks: Isonet for VHF and UHF, Duonet for Hi-VHF and Lo-VHF, and the Trisonet for Hi-VHF, Lo-VHF and UHF—all three of these accessories effectively isolate antennas for different frequencies, couple them into a single lead-in. The Tele-Couplers, in two and four set models, couple up to four tv sets to a single antenna lead-in. The new High Pass Filter effectively eliminates tv interference by passing only signals at frequencies above 50 mc.
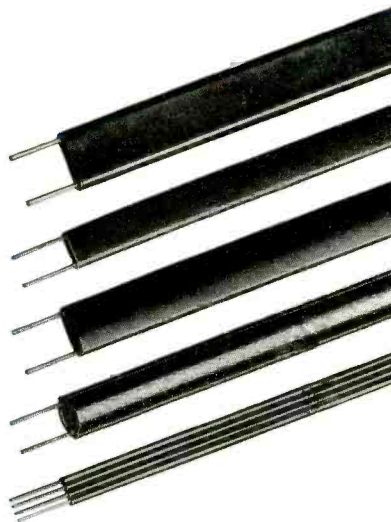
## LEAD-IN

Dependable standard Flat Twin-lead and unique AIR-CORE Tubular Twin-lead have been joined by several new lead-ins to make the AMPHENOL line the most complete available. New Century and Heavy-Duty Twin-Leads are deluxe VHF lead-ins; AIR-CORE transmitting Tubular Twin-Lead has been reinstated, as has Four Conductor Rotator Cable.



AMERICAN PHENOLIC CORPORATION

chicago 50, illinois

# AMPHENOL

In Canada: AMPHENOL CANADA LIMITED, Toronto

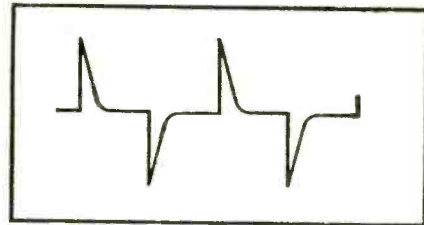


Fig. 9—Extremely poor low frequency response; 40 cps.

might be defective coupling condensers, screen or cathode bypass condensers, screen or grid resistors, and low frequency compensation circuits. Poor low frequency response may show up on

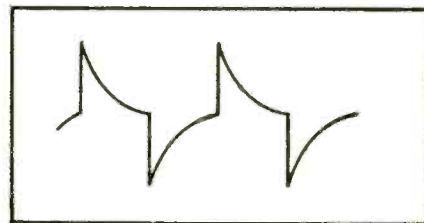


Fig. 10—Same trouble as in Fig. 9; 100 cps.

the screen as a change in shading from the top to the bottom of the raster or the "paint brush" effect, where large objects appear smeared. Picture syn-

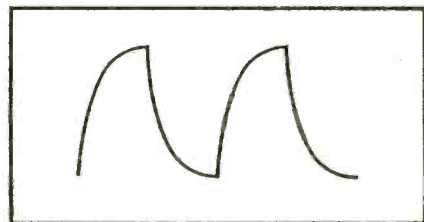


Fig. 11—Poor high frequency response; 100 kc.

chronization may be affected due to excessive distortion of the rectangular sync pulses.

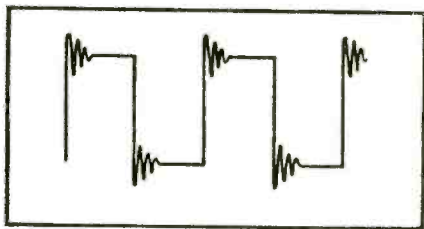


Fig. 12—Poor transient response; poorly damped peaking coils.

Figure 11 indicates the amount of distortion observed on a 250 kc fundamental square wave when the picture detail began to get fuzzy. This may be used as a rough guide, and any wave form considerably worse than this would

[Continued on page 56]



# DOUBLE YOUR SALES

## SNYDER

### Directronic®

#### INDOOR TV ANTENNAS

### 3-D

9<sup>95</sup>

### 5-D

12<sup>95</sup>

BLACK
WHITE
COLOR
AM/FM
VHF/UHF

6-POSITION  
BEAM  
SELECTOR


8-POSITION  
PUSH BUTTON  
BEAM SELECTOR

# SNYDER


SNYDER MFG. CO., PHILADELPHIA 40, U.S.A.  
BELLEVUE TUBE MILL, INC., PHILADELPHIA  
SNYDER ANTENN-GINEERS, LTD., TORONTO 14, CANADA  
WORLD EXPORT: ROBURN AGENCIES, INC., N.Y.  
VAN DER HOUT ASSOC., LTD., NEW TORONTO, CANADA



# NOW...

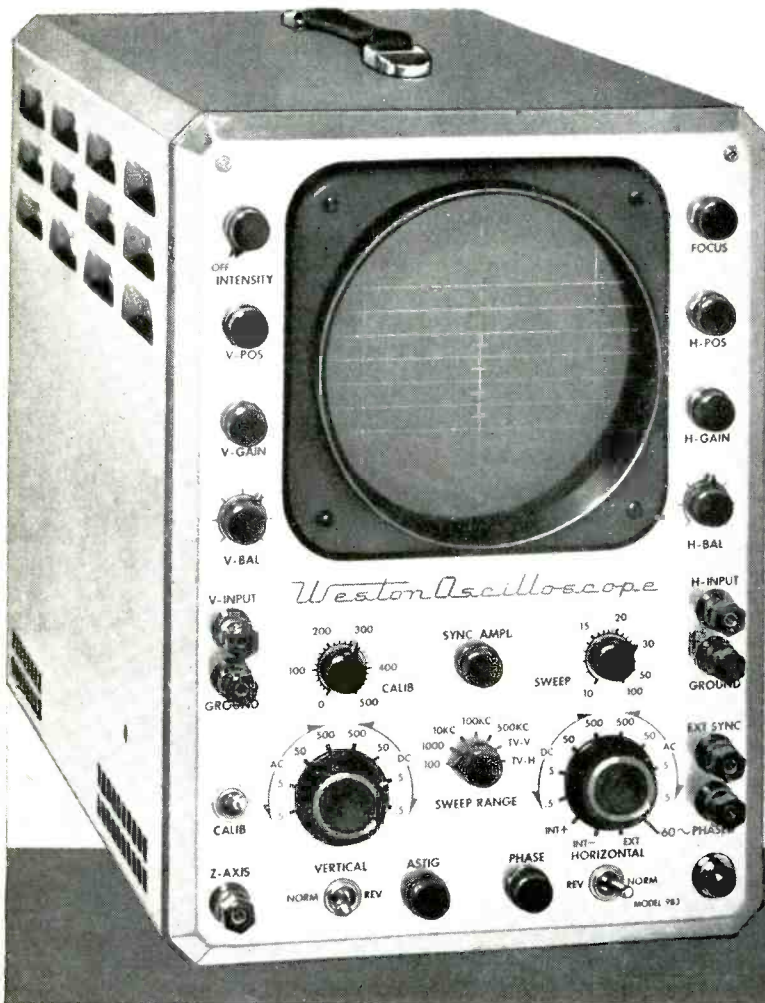

## WAVEFORM ANALYSIS

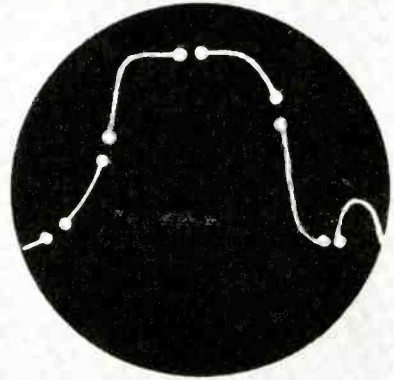

Response curves accurately displayed. Ideal for use with Weston intensity marker display. A fast, retrace sweep circuit with cathode follower output prevents pattern distortion.

# WESTON

The Model 983 is a high gain, wideband Oscilloscope designed to accurately reproduce waveforms comprising a wide band of frequencies. High sensitivity of 15 millivolts per inch RMS makes this Oscilloscope ideal for—SETTING RESONANT TRAPS... SIGNAL TRACING IN LOW LEVEL STAGES ... AS A GENERAL NULL INDICATOR... for PHASE CHARACTERISTIC MEASUREMENT IN INDUSTRIAL APPLICATIONS... and for SWEEP FREQUENCY VISUAL ALIGNMENT OF TV RECEIVERS.

The scope contains identical vertical and horizontal push-pull amplifiers with a choice of AC or DC coupling without affecting either sensitivity or bandwidth. Both amplifiers have compensated step attenuators and cathode follower input.

*It has excellent square wave reproduction with overshoot of only 2 to 5% with a rise time of 0.1 microsecond. The scope response is essentially flat throughout the specified range of 4.5 mc and is usable to 6 mc.*

The unit has provisions for internal calibration, internal phased sine wave, and Z-axis intensity modulation. Reversal of polarity of both horizontal and vertical signals is easily accomplished by means of toggle switching. *Tube replacements are non critical, and etched circuitry facilitates quick and rapid maintenance.*

The Model 983 Oscilloscope is now available through local distributors. For complete literature, return the coupon today. WESTON Electrical Instrument Corporation, 614 Frelinghuysen Avenue, Newark 5, New Jersey.


Price ... \$329.50






# the All-purpose Scope!

## SQUARE WAVE RESPONSE

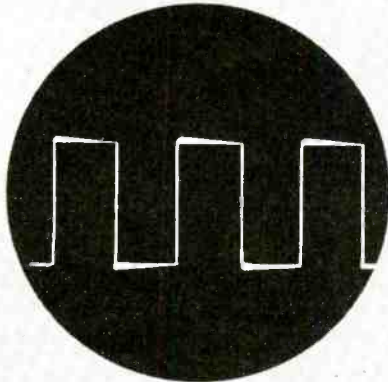


Overshoot is only 2 to 5%. Rise Time is 0.1 Microsecond. Square wave depicted 250 kc.

## PHASE MEASUREMENTS

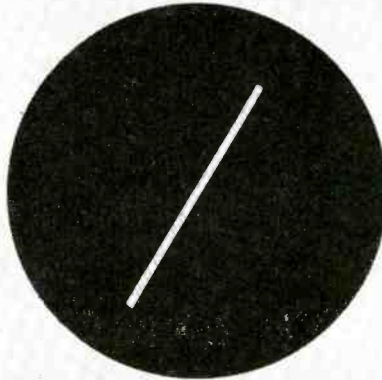

Phase shift between horizontal-vertical amplifiers, 0-100 kc-0°, to 1 mc within 2°; by internal adjustment with gain controls at max 0° phase shift possible on any specific frequency to 6 mc.

## RESPONSE CHARACTERISTIC

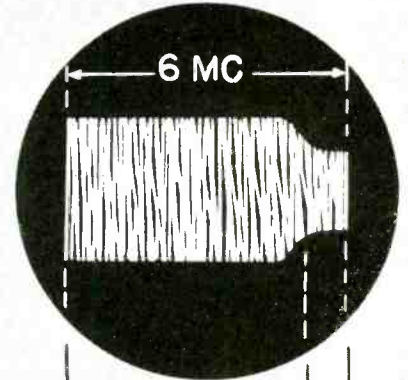

Note flatness throughout specified range; usable to 6 mc.

# 980

## LINE OSCILLOSCOPE

### SPECIFICATIONS: MODEL 983 OSCILLOSCOPE

**Wide Band Frequency Response:** Flat within 1.5 db from 0-3.58 mc and within -3 db to 4.5 mc on both vertical and horizontal amplifiers. Transient response: overshoot 2 to 5%. Rise time: 0.1 microsecond.

**High Deflection Sensitivity:** 15.0 millivolts per inch, RMS, on both vertical and horizontal amplifiers.

**Phase Shift:** Between horizontal-vertical amplifiers, 0-100 kc-0°, to 1 mc within 2°; by internal adjustment with gain controls at max 0° phase shift possible on any specific frequency to 6 mc.

**Calibrating Voltages:** 500 millivolts, 5 volts, 50 volts, 500 volts, peak to peak. Readily available and adjustable by front panel controls.

**Z-Axis Modulation:** Input terminal mounted on front panel.

**Sweep Frequencies:** 10-500,000 cps, variable. Preset TV/V position—30 cps. Preset TV/H Position—7875 cps. Retrace Time—better than 2% to 100 kc; at 500 kc less than 10%.

**Internally Phased Sine Wave:** Adjustable through 170°.

**Vertical and Horizontal Polarity:** Reversible.

**Input Impedance:** Vertical Amplifier (without Shielded Cable), 1 meg shunted by 60 mmf. Vertical Amplifier (with Shielded Cable), 1 meg shunted by 120 mmf. Vertical Amplifier (with Low Capacitance Probe), 10 meg shunted by 12 mmf. Horizontal Amplifier (without Shielded Cable), 1 meg shunted by 60 mmf.

**Power Supply:** 105/125 volts, 50/60 cycles.

**Tube Complement:** (1)-1V2, (1)-5U4-GA, (6)-6BQ7A, (4)-12BY7A, (4)-6AH6V, (1)-6UB, (1)-5UP1, (1)-0D3, and (1)-5NO60T.

**Case:** Grey hammertone finished steel.

**Panel:** Aluminum finish with etched, black markings.

**Size:** 10" x 14" x 19.5"

**Approx. Weight:** 40 lbs.

### OTHER WESTON 980 LINE INSTRUMENTS

- 980 Volt-Ohm-Milliammeter
- 981 Tubechecker
- 982 Vacuum Tube Voltmeter
- 984 Sweep Generator
- 985 Calibrator

### SEND COUPON FOR COMPLETE DETAILS

WESTON Electrical Instrument Corporation  
614 Frelinghuysen Avenue  
Newark 5, New Jersey

Please send literature on the 983 Scope and other 980 Line Instruments.

NAME \_\_\_\_\_


ADDRESS \_\_\_\_\_

## QUESTION:

# Why buy TWO when ONE will do?

## ANSWER:
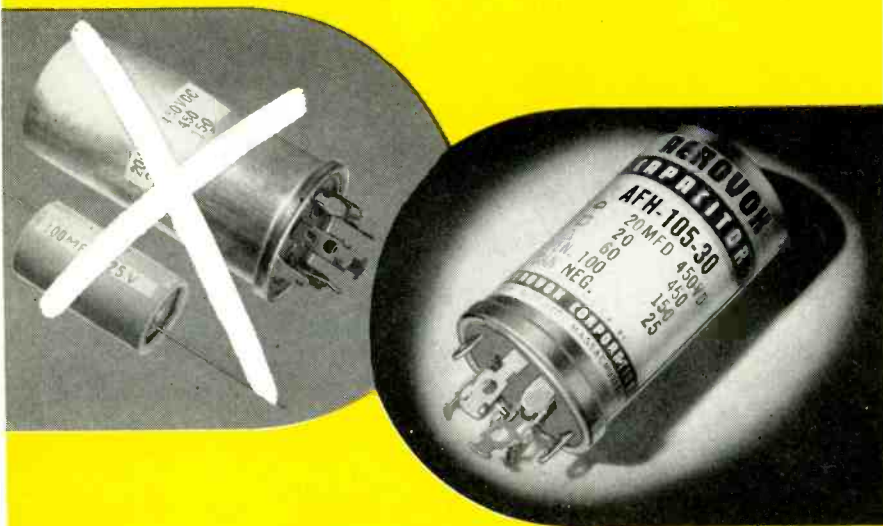
# Insist on **AEROVOX** TWIST-PRONG ELECTROLYTICS



Here's the reason: A popular TV replacement calls for a 4-section unit rated at 20-20/450, 60/150, 100/25. In the absence of such a number, some capacitor lines recommend TWO units in combination — 20-20/450 60/350, list price \$5.05, plus a tubular electrolytic 100/25, list price \$1.35, for a total of \$6.40.

By contrast, AEROVOX offers the identical part number — an AFH-105-30, rated at 20-20/450, 60/150, 100/25, list price \$4.25. Why buy TWO when ONE will do? Why \$6.40 list when you can get a single-unit replacement for \$4.25 — and cut your labor by half? Lastly, you avoid trouble in TV chassis where tight fits are a problem.

With more extensive listings (actually 290 to 345 more numbers than those of any one of five competing brands\*), AEROVOX Type AFH Twist-Prong Electrolytic Capacitors meet more requirements with single, economical units in place of multiple-unit makeshifts.

### Consult AEROVOX Listings!

Take full advantage of those more extensive listings of ALL types of capacitors. Ask your AEROVOX distributor — or write us.

*\*Details on written request.*

## AEROVOX CORPORATION

DISTRIBUTOR SALES DIVISION,  
NEW BEDFORD, MASS.

In Canada: AEROVOX CANADA, LTD., Hamilton, Ont.

Export: Ad. Auriema., 89 Broad St., New York, N. Y. • Cable: Auriema, N. Y.

# ASSOCIATION NEWS

by Samuel L. Marshall, Editor

## Radio Television Guild of Long Island (N.Y.)

In a recent meeting at the State Capitol in Albany Governor Averill Harriman heard various members of the Industry express their views on licensing.

The service technician was represented by Mr. Joseph B. Forman, representing The Empire State Federation of Electronic Technicians Associations (ESFETA) as well as The Radio Television Guild of Long Island. He was instructed to take a positive stand for licensing provided the technician could sit in on its formation. Forman also attacked bait ads as detrimental not only to the consumer but a blot on the character of the legitimate serviceman. He cited examples of gyp operations and strongly urged legislation to eliminate these practices.

## Long Island Electronics Technicians Assn. Inc. (N.Y.)

A very interesting "1954-1955 Annual Report of Board of Directors" can well be emulated by other associations who want to bring to the forefront a review of their year's activities and accomplishments.

## National Alliance of Television & Electronic Service Ass'ns.

In the March issue of the NATESA Scope, Frank Moch minces no words editorializing on "factory service at retail". Following is an excerpt of his thoughts on the subject:

"Any independent who purchases the products and/or services of any manufacturer, distributor or jobber who has not proved, beyond doubt, his willingness to cooperate with independent service in the fulfillment of its destinies, is digging his own grave. This is particularly true of component producers who stand to lose as much as we, should independents be squeezed out.

"As far as set producers are concerned, remember that the best set in the world cannot be sold without advertising. Most manufacturers spend millions to sell their sets and yet every single independent, every single day, has rendered what the public accepts as favorable expert opinion on sets without ever receiving one cent compensation.

*[Continued on page 26]*



# NEW BETTER WAY

## To Stock, Sell and Service

### PHONO-CARTRIDGE REPLACEMENTS



## NOW SEALED-IN-PLASTIC

This is a big step ahead in cartridge merchandising and servicing! For greater protection and convenience, E-V Replacement Cartridges now come in individual new sealed-in-plastic Blister-Paks, with full model identification, interchangeability chart, and instructions—in colorful display box.

### \$70,000,000 CARTRIDGE REPLACEMENT MARKET

The exclusive new Blister-Pak in the E-V Basic 6 Preferred Types makes it easier to take E-V cartridges along on a service call for immediate replacement. Advanced engineering by E-V assures finer reproduction, longer record and needle life, easy installation, and more satisfied customers.

### NEW E-V MODEL 47 DUAL-SLIDE CARTRIDGE FOR 78, 33-1/3, 45 RPM

Here is a unique new innovation in replacement cartridges! The dual-slide, dual needle Model 47 shown on the Blister-Pak at right makes it possible to replace hundreds of different specialized types with a single general-purpose cartridge—with design and operating features found only in wide range custom built cartridges.



### NEW PACKAGING... NEW MERCHANDISERS

**Make Cartridge Replacements Easier and More Profitable than Ever!**

Colorful new 2-drawer metal display-dispenser makes it easier for service-dealers to stock and sell phono-cartridge replacements. Your E-V Distributor is ready to supply you with these merchandisers and other E-V sales aids.

SIZE  
6x13x9 3/4"




## FREE HANDY NEW QUICK-ANSWER Cartridge Interchangeability Guide

This complete, up-to-date cartridge interchangeability guide SA9 is available FREE to service-dealers. A simple turn of the wheel gives you the exact replacement for all current cartridges. Get it now from your E-V Distributor or write to Electro-Voice.

# Electro-Voice



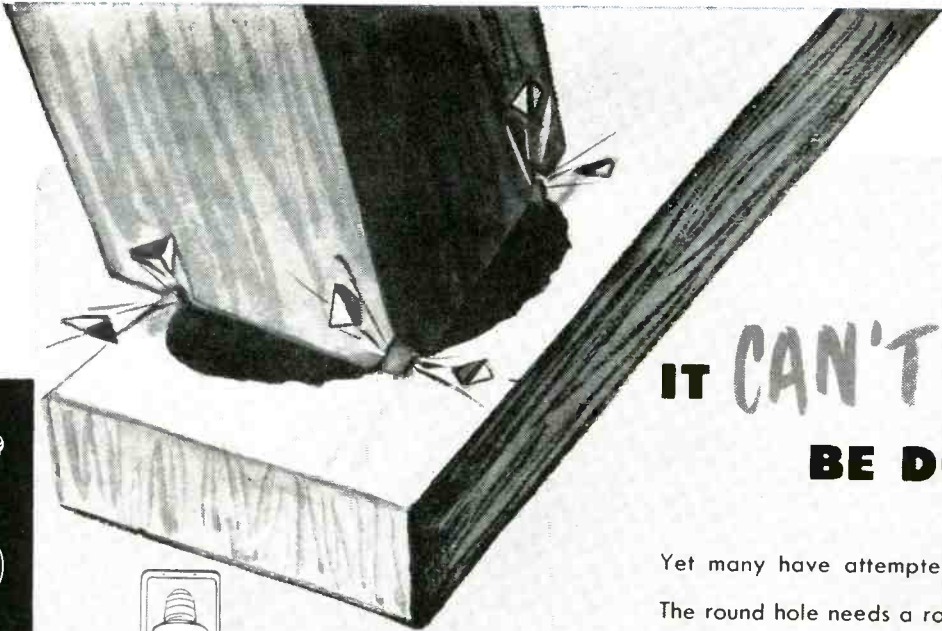


# IT CAN'T BE DONE!

Yet many have attempted to try it.


The round hole needs a round peg—custom-fit to meet the need. In the choice of a speaker, just as in the choice of the peg, the point of application should be the governing factor.

So why waste loudspeaker capacity and amplifier power using the wrong speaker for the job? University makes available over 50 different models of speakers, each designed to meet a particular requirement most efficiently. University loudspeakers are *application engineered* to provide optimum performance with maximum economy—technically and cost-wise.

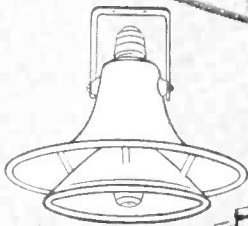Whether the need is for music or voice, or both—for either indoor or outdoor use; whether in a fixed position in a factory or for mobile use on a vehicle, boat, train or airplane... there's a University speaker that can do the job best. *Don't spend more for more than you need... CHECK UNIVERSITY FIRST!*



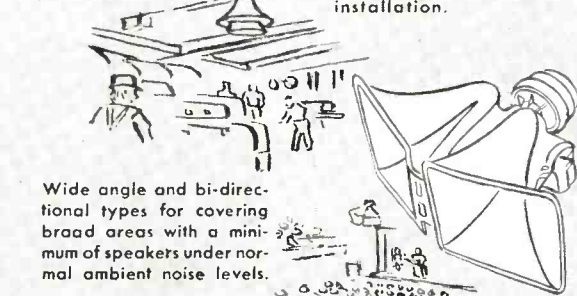Radial type projectors and paging speakers with 360° dispersion for maximum coverage at lowest cost and ease of installation.



Wide angle and bi-directional types for covering broad areas with a minimum of speakers under normal ambient noise levels.



Reflex trumpets in various sizes for incomparable efficiency, distance and noise penetration.



**FREE** Write Desk 77 for copy of University Technilog • Complete up-to-date manual of sound theory, application and installation requirements • SEND for your copy today.



**UNIVERSITY LOUDSPEAKERS • INC.**  
80 SOUTH KENSICO AVENUE WHITE PLAINS, N. Y.





# P.A. in Supermarkets

by | Gene Hessel

**P**UBLIC address paging and background music systems are reaching unprecedented peaks of popularity and there is a big reason—public demand. There is hardly a place where the public gathers where such a system is not in use. Families dining out take the soft and dignified music they enjoy for granted. Theatres, churches, schools, factories and department stores are enjoying the benefits resulting from careful installation of Public Address paging and background music systems. These installations provide an ideal opportunity for increased earnings in a non-seasonal and specialized radio-TV field for the Service Dealer.

## Supermarkets—Natural Prospects

Growing up with the Public Address Paging and Background music system is the Supermarket or Self-Service Food Market—a spot where a good sound system is almost a "MUST". In such a location a system of this type performs

a threefold duty: (1) it supplies background music for both customer and employee; (2) it is used for paging either customer or employee; and (3) it makes possible announcements of store specials or features, or any different store promotion throughout the store at any desired time. This latter practice is really efficient as has been proven by experience. If the music is suddenly terminated and is replaced by a voice over the public address system announcing that, "At counter #3 a free air ship balloon will be given with every purchase of Mrs. Kornfruits Krispy 'Krackers' Counter #3 will be surrounded in a very short time by many customers.

In the following paragraphs a typical Address Paging and Background Music system is described. The market selected is of the Self-Service type and has a main shopping area of 45,000 sq. ft. A lunch counter is provided for patrons where an inter-com system from counter to kitchen has been installed. This device aids greatly in the expediting of orders. Inter-communication to the various utility and store rooms from the Manager's office is effected with two new types of University Cobra Horn Paging speakers. Model CIB and CMIL, see Fig. 1. Two of the CIB units are installed in the general storeroom which comprises a fairly large area. The CIB speakers will handle 12 watts and mount quite easily with a universal bracket. The triangular base of the speaker bracket is fastened to the top of the University CTR-20 matching transformer with three screws, the mounting bracket of the CTR-20 then supports

both the transformer and the speaker. The CMILs which are 3 watt speakers are used in the meat cutting room and in the fruit and vegetable room where less power is required.

The control equipment necessary for this particular sound installation is in the manager's office and is mounted in a small conventional type of relay rack. Music for this store is supplied by a continuous tape playing mechanism which employs a double track fourteen-inch pre-recorded tape running at three and three-quarter inch per second. This gives a total of eight hours of program material after which time the program repeats itself. The chances are remote that any customer would stay around long enough to hear the same program twice. If the store manager desires, announcements, advertisements for the various commodities handled by the store etc., can be interspersed throughout the music. The music selected is of a popular vein and can be pre-recorded by a recording studio, a radio station, or is available in commercial tapes.

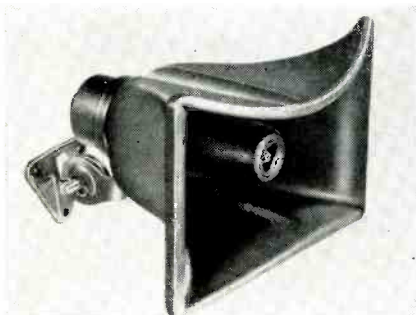


Fig. 1a—University Cobra horn paging speaker Model CIB.

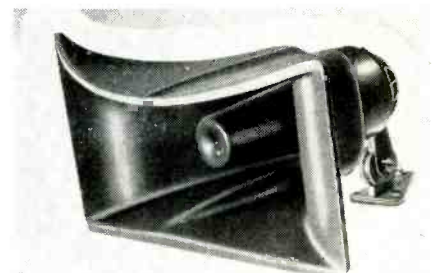


Fig. 1b—University Cobra horn paging speaker Model CMIL.

The tape playing mechanism is fed into the low level input of a 30 watt power amplifier of good quality as shown in Fig. 2. The tape playing mechanism used is a Magnecord 814 which has a 500 ohm zero level output. This is fed through a line matching transformer to the input of the 30 watt amplifier. A microphone is used for paging employees or emergency announcements to the public, should this be necessary. The microphone stand is equipped with a push-to-talk switch which silences the microphone when it is not in use. When the switch is depressed the music is temporarily silenced. The advantages of this arrangement are quite evident.

A most important consideration is the selection of suitable loudspeakers and their placement. In general, the architectural structure of buildings such as Super Markets make them very poor acoustically. It is therefore necessary to use as many speakers as possible to insure keeping the over-all sound level at a minimum with a maximum of coverage. In this installation 12 University Model #6200 12" cone speakers are used with excellent results. The phys-



Fig. 2—Bogen Model J330 amplifier has three mike inputs.

ical size of the 6200 is especially desirable since it is of a shallow design (4 1/4" deep) making it ideal for mounting into a ceiling type installation (see Fig. 3). It has power handling capacity of 30 watts and a frequency response of from 45 to 10,000 cps. Each of the 6200s is equipped with a good quality line matching transformer, whose primary impedance is 2500 ohms. The speakers are laid out in three rows of 4, effecting excellent objective coverage throughout the shopping area.

Lowell type baffles (Fig. 4) are used to flush mount the cone speakers into the ceiling. They are constructed completely of spun aluminum and therefore are very light in weight. The Lowell enclosure consists of a steel "High Hat" can which is lined with a sound absorbing material. This can is attached directly to the overhead I beams from which the ceiling itself is supported. The baffle section of the Lowell enclosure is similar in appearance to the average air

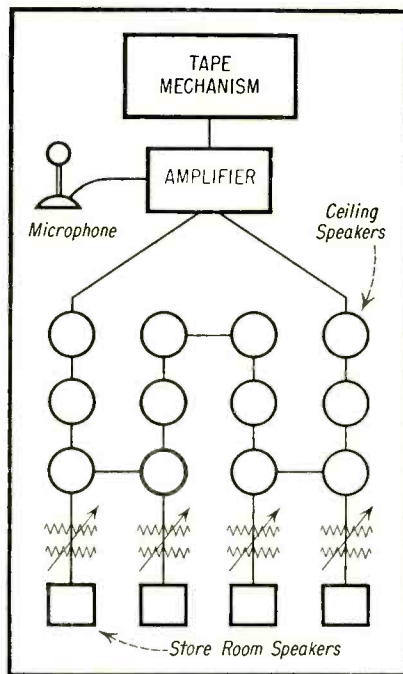


Fig. 5—Hookup of various components and speakers used in supermarket installation.

conditioning ducts normally installed into ceiling. The clean aluminum surface blends with the general styling of the store fixtures and counters. The speakers are wired in a loop from the amplifier through the speakers and returning to the amplifier. See Fig. 5.

It is important to make certain that all speakers are connected in phase with each other. Before these speakers were installed they were checked and the terminals color coded on the bench. In order to insure having no interruption of sound (due to a break in the wiring system) the wire from the amplifier is fed through all the speakers and returned from the last speaker to the



Fig. 3—University Model 6200.

amplifier. For purposes of paging and supplying background music for employees working in the store room and the meat cutting areas, loudspeakers in convention type of wall baffles have been installed in these locations. Because it is impossible to pre-determine the volume needed in these areas, each speaker is equipped with an individual L pad. It is possible of course to increase or decrease the over-all store volume as desired, at the main amplifier itself, depending on the number of people in the store.

Including the store room speakers, a total of 16 loudspeakers are used in the system. As mentioned previously, each is equipped with a line matching transformer with a primary impedance of 2500 ohms. This gives us a line impedance of 160 ohms which can be connected to the 250 ohm terminal on the power amplifier without too serious a mismatch. The amplifier which is used has a separate treble and bass control for proper tone balance. Number 14 stranded outdoor transmission line is used for loudspeaker cable connections.

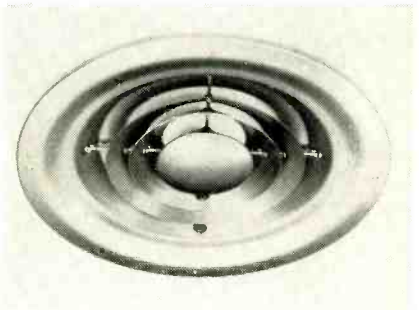


Fig. 4—Lowell diffusion baffle.

For a smaller market, in the interest of economy, a standard good quality automatic record player employing long playing records can do a good job of supplying the necessary background music. Other components of the system would be the same in all respects. While the initial cost of this type of installation would be less, it must be remembered that in the long run, constant replacement of records might prove to be more expensive than purchasing an automatic tape playing machine.

Since it is very easy to forget to shut off the automatic system over the weekend when the store is closed, an automatic time switch has been installed. This means that the system starts up and shuts off automatically at a pre-set time. The advantages of this time clock system are apparent. Availability is no problem since they are made by several manufacturers.

While the system just described is completely adequate for the market described, there are many more elaborate  
[Continued on page 61]





## Another Great Instrument in Philco's Complete Line of Test Equipment



MODEL 7300


# PHILCO®

## Precision Alignment Generator for Better Television and FM Radio Service

Speed up work on the bench or in the field . . . handle jobs more efficiently and make more profits! Every service man needs the Philco Precision Alignment Generator. A portable unit, versatile in application, it gives fast, accurate information for better TV and FM Servicing.

All necessary signals for servicing FM and TV receivers are supplied by this compact instrument. Intermediate frequencies and channel frequencies are covered in two ranges by the sweep generator. Three ranges, from 3.2 MC to 260 MC may be tuned in with the Marker Generator, and this function can be used to supply marker pips for use with the sweep generator or as an AM generator with 400 cycle modulation.

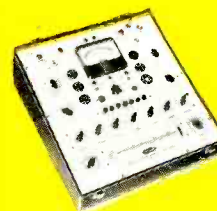Philco builds a complete line of high quality test equipment. See it at your Philco Distributor's now!



Philco Dynamic Mutual Conductance Tube Tester—Model 9100.




Philco 3" oscilloscope—Model S-8200. Portable or for use on the bench.



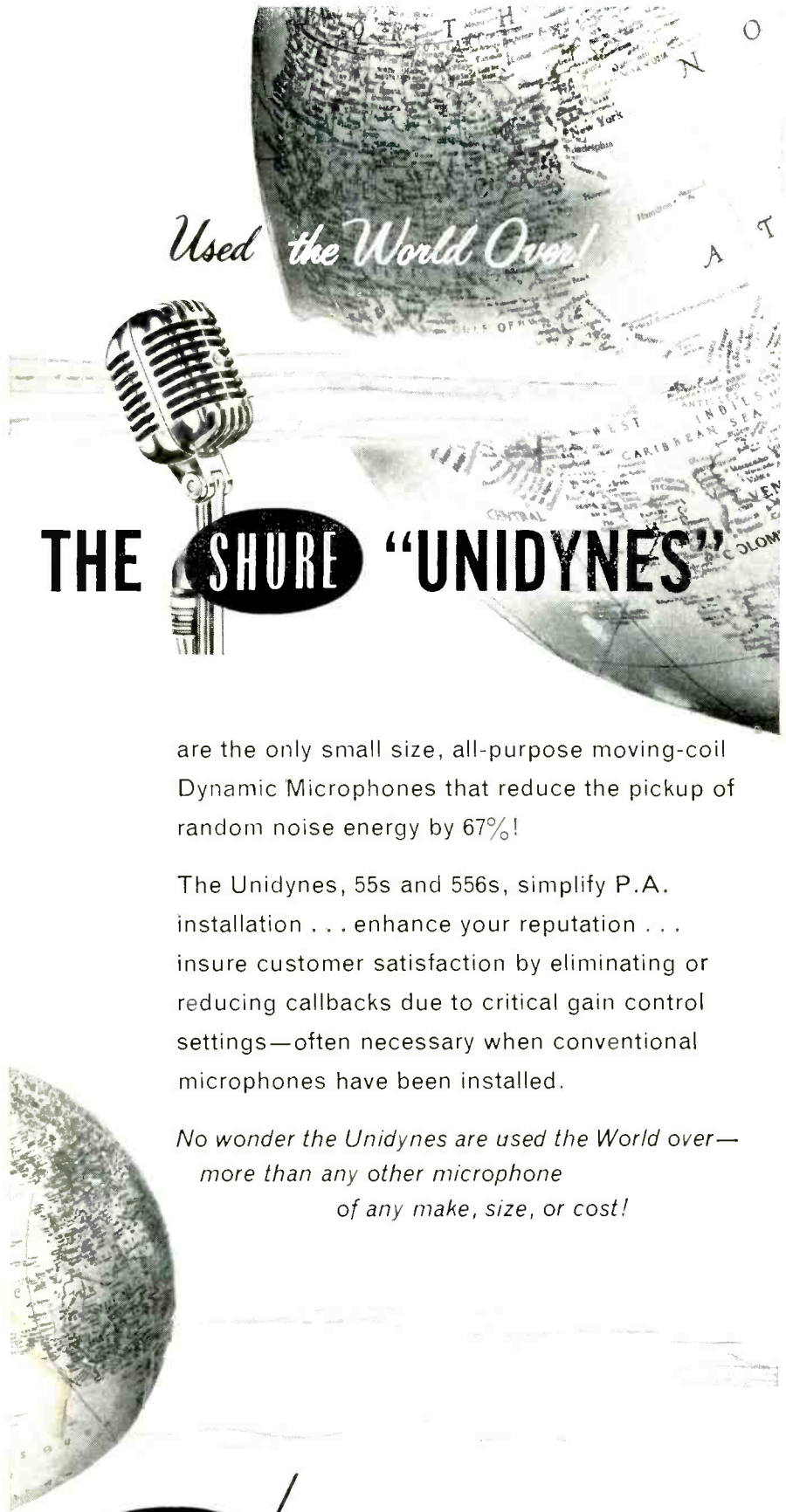**PHILCO CORPORATION**  
Accessory Division  
Philadelphia 34, Pa.





**THE SHURE "UNIDYNES"**

are the only small size, all-purpose moving-coil Dynamic Microphones that reduce the pickup of random noise energy by 67%!

The Unidynes, 55s and 556s, simplify P.A. installation . . . enhance your reputation . . . insure customer satisfaction by eliminating or reducing callbacks due to critical gain control settings—often necessary when conventional microphones have been installed.

*No wonder the Unidynes are used the World over—more than any other microphone of any make, size, or cost!*

**SHURE SHURE BROTHERS, Inc.**  
 Microphones and Acoustic Devices  
 225 W. Huron St., Chicago 10, Illinois  
 Cable Address: SHUREMICRO

**ASSOCIATION NEWS**

[from page 20]

This practice may have been reasonably sane as long as the very people for whose products you did such a tremendous sales job believed and practiced a live and let live philosophy."

**Television Service Association of Michigan**

Alexander Weiss was re-elected president of the Television Association of Michigan at the annual election March 8. New officers elected were Charles Judd, first vice-president; Karl Heinzman, second vice-president; Ray Cobble-dick, secretary; and Malcomb Wright, treasurer. The group also elected six directors: Edward Brown, Wm. Mattingly, Clayton Hibbert, Vernon Eberhardt, Harold Chase, and Jack Barton.

**Associated Radio & Television Servicemen—Illinois**

ARTS scheduled an open house lecture on April 26. Speaking this evening were Harry Alter, President, The Harry Alter Company, Chicago. The Topic: "Keeping Marketing Within Bounds." Also heard was Paul H. Wendel, who spoke on "YOU—the Service Man." The guest Chairman and Moderator was Mr. Leonard Maher, Field Secretary, NARDA—Chicago.

**Radio & Television Electronic Technicians Assn.—N.Y.**

R.A.T.E.T. announces a complete color TV series of lectures. Following is the date and subject schedule: May 5—Color Fundamentals; May 12—Color Circuitry; May 19—Troubleshooting and CRT; May 26—Alignment and Test Equipment.

**Associated Radio-Television Service Dealers—Columbus, Ohio**

Congratulations to the above from Yours Truly (SLM) on the 11th year birthday of ARTSD News. The March 9th meeting was a Technical one, with James Parent and Robert Kerzman of Hickock Electrical Instrument Co. conducted the meeting. Application of test instruments as applied to Color TV and general alignment of B&W TV sets. A question and Answer period followed their interesting talk.

**Federation of Radio Servicemen's Associations of Penna.**

At the March 20th meeting of the Pennsylvania Federation held in the Hotel Harrisburger, in Harrisburg, by unanimous decision the Federation of [Continued on page 55]



from

# DELCO RADIO...

One of the Largest Makers  
of High Quality


## SPEAKERS

for Home and Auto Radios,  
Phonographs and Television

Product of combined Delco Radio and General Motors engineering skills, manufactured in plants devoted exclusively to electronic parts, the Delco speaker line embraces 14 standard models for home and auto radios, phonographs, and television—plus the model 8007, a superior Hi-Fi dual-purpose speaker for replacement in AM, FM, TV and phonograph sets, and for use with custom-built high-fidelity audio systems. It's plain to see that here's the speaker line to fill your needs...products of uniformly fine design and construction, *all* of them competitively priced!

*Standard Speaker Features:* Designed and built to R.E.T.M.A. standards; cones uniform in response over operating frequency range; fully dustproofed with drawn brass magnet covers and felted cones; Alnico-V magnets; heavily plated metal parts.

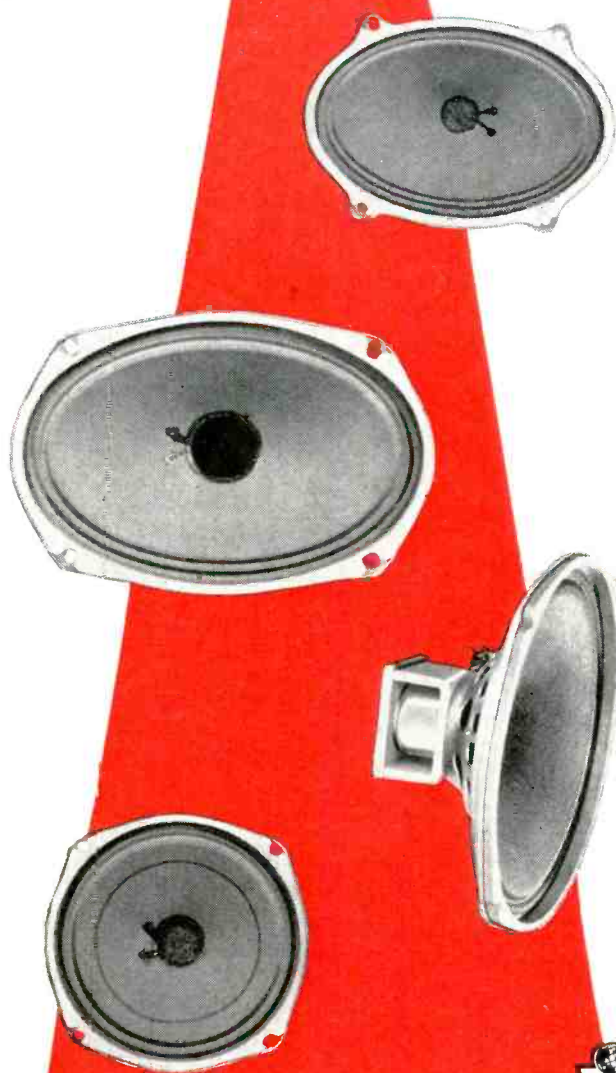*Model 8007 Hi-Fi Speaker Features:* Size 8"; 50 to 12,500 CPS frequency range; Alnico-V magnet; 10-watt power rating; 4.1 input impedance;  $1\frac{3}{16}$ " voice coil.



### DELCO RADIO

DIVISION OF GENERAL MOTORS, KOKOMO, INDIANA


A GENERAL MOTORS PRODUCT  A UNITED MOTORS LINE

DISTRIBUTED BY ELECTRONIC DISTRIBUTORS EVERYWHERE

Order these quality products of a volume electronics manufacturer through your UMS Electronic Parts Distributor today.
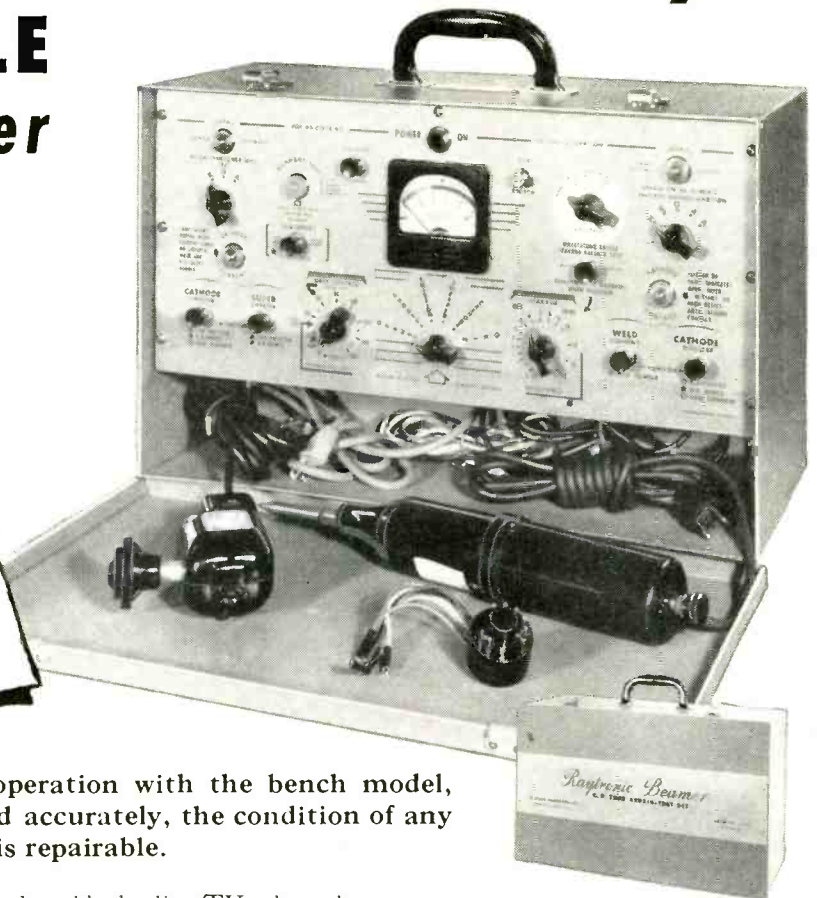
# a CHALLENGE by NEW PORTABLE Raytronic Beamer

*to ANY instrument  
for commercial  
TV CR Tube  
service work —  
for a  
COMPARATIVE  
DEMONSTRATION*



This portable instrument, identical in operation with the bench model, will make 8 tests to show, positively and accurately, the condition of any TV picture tube—and whether or not it is repairable.


The exclusive Cum-o-tron improved Raytronic Gas Test is now the only circuit for commercial use that employs the same circuitry and voltages used in picture tube laboratories, giving direct readings in fractions of one micro amp.

The Raytronic Beamer makes 5 repairs capable of restoring up to 85% of repairable tubes to satisfactory service. Endorsed

and used by leading TV tube and set manufacturers and their distributors, after exhaustive tests.

Thousands of users have verified every claim made for this instrument. They are reaping a new harvest of extra volume, extra profits, attracting new customers, winning loyalty and boosting endorsements from old customers.

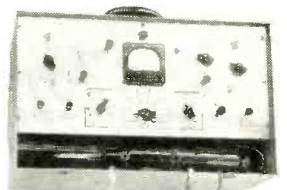Compact carrying case contains instrument and accessories—and is light weight, too.



Case cover removed for bench work in horizontal position; rubber base lugs.

## Read What They Say!

*(from hundreds of  
written statements)*

Raytronic Beamer is the best piece of test equipment I ever used, and will do more for the shop owner. It is actually worth many times its price and is so simple to operate.

J. S. ROHERSON,  
ROHERSON ELECTRIC SUPPLY  
Pontotoc, Miss.

The first day we used the Raytronic Beamer we repaired 20 CRTs—1 27", 4 21", 9 17", 4 16", 1 12", and 1 10". We save at least one CRT per day with this instrument and can't think of anything I would hate to part with more.

A. GLASER  
ALL AMERICAN TV  
Chicago 18, Ill.


**See Raytronic Beamer demonstrated — TODAY!**
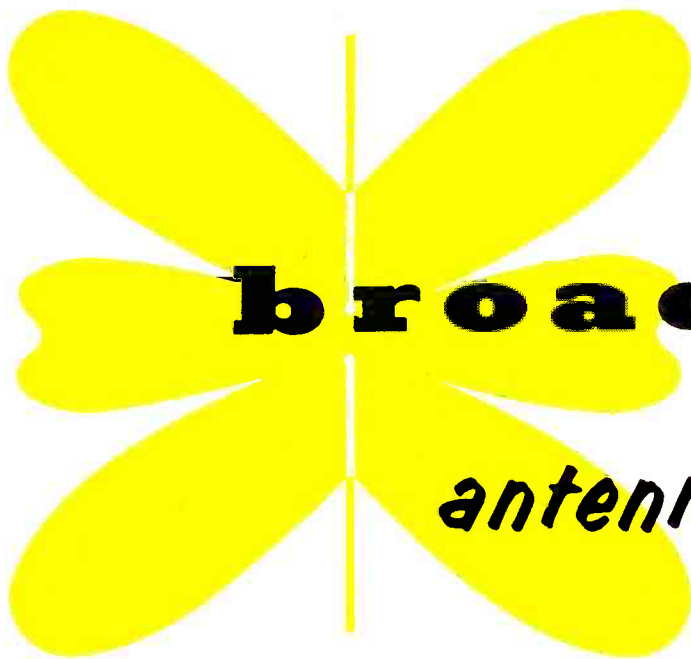
## RAYTRONIC LABORATORIES, INC.

Export Representative:  
International Standard Electric Corp.,  
Capehart Division,  
Box 420, Ft. Wayne 1, Ind.

General Offices:  
9701 Reading Rd.  
Cincinnati 15, Ohio





# **broad band**

## *antenna systems*

by **Douglas H. Carpenter**  
Chief Engineer, JFD Mfg. Co.

**D**URING the past few years there has been a gradual change in the nation's antenna requirements. Higher power grants, and finalized *vhf* frequency allocations have partially obsoleted the single channel antenna. Areas that were formerly serviced by one television transmitter now have several networks available. This process is still continuing, and has created a demand for all-channel antennas having characteristics equal to the single channel yagi on every *vhf* channel.

As a result, manufacturers of television antenna systems have concentrated on supplying and improving broad band arrays. When we discuss antenna systems we are speaking of passive networks or non-electronic circuitry. The limitations imposed upon the designer of such equipment are much greater than those in the general electronic field due to the fact that no secondary elements are available. There has been a great deal of interest expressed at dealer service meetings as to the actual electrical operation of the broad band antenna, and it is the purpose of this article to show how the most popular forms employ the same basic electrical principle to achieve performance on TV channels 2 through 13.

Three broad band antenna types manufactured by the JFD Manufacturing Co., Inc. are shown in the photograph of Fig. 1 and are representative of the design trend followed to attain all channel reception. In order of their illustration they are the Star Helix Rainbow, Dodo, and Jet Helix Rainbow, trade name models. The same exact electrical principle of operation is em-

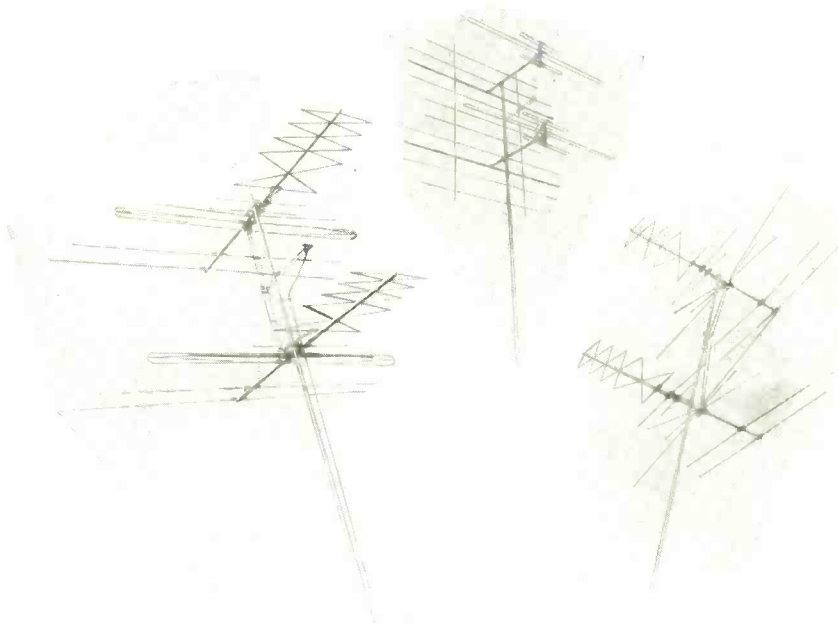


Fig. 1—Three broad band antenna types discussed in this article. Left: Star Helix Rainbow. Center: Dodo. Right: Jet Helix Rainbow.

ployed in each antenna although the physical configuration is different. The gain curves, horizontal polar patterns and so forth are different, of course, because of the number and type of parasitic elements employed.

If we wanted to design an antenna system for Channels 2 through 6 the problem would be greatly simplified, as here we are dealing with a continuous frequency range of 54 to 88 mc. There are many antennas that are used where only low channels are available, and generally they consist of a double driven element with a reflector and

several directors to peak the high end of the low channels. This antenna or similar types cannot be used for reception of Channels 7 through 13, however, as here the pattern splits up into several lobes. Fig. 2 shows the polar pattern of any resonant element operating at three times its fundamental half wave design frequency. This would be typical of a resonant element or antenna designed for Channel 3 operating on Channel 9.

Figure 3A shows the current distribution of a half wave element, and the direction of current flow. Fig. 3B shows

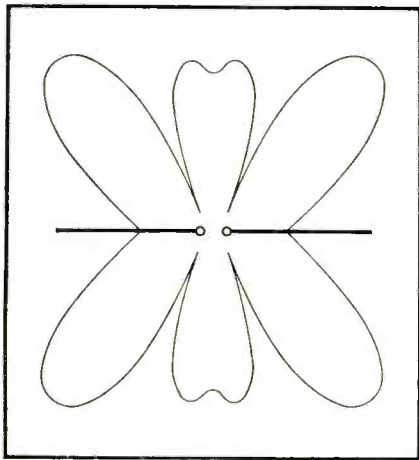


Fig. 2—Pattern obtained with 3/2 wavelength antenna.

this same element at three times this frequency and the current distribution that occurs. It can be seen that the antenna is divided into three parts; the center and two ends. The polarity or phase of the *center section* is exactly the same as that of Fig. 3A and the direction of flow is identical. The polarity of the two end sections are opposite, however, and the direction of current flow opposed to that of the center section. The net result is that we have a bucking current field resulting in the polar pattern of Fig. 2 where the energy transmitted by such an antenna would be scattered and not concentrated into a single usable lobe.

The thought has probably already presented itself that a solution could be found if the center section could be removed. In this case, we would be left with the two in-phase end components resulting again in our single lobe pattern. Unfortunately, *physical* elimination of the antenna center would resonate the half wave point at the high end of the low TV channels, and the antenna would be full wave type on the high channels with a center im-

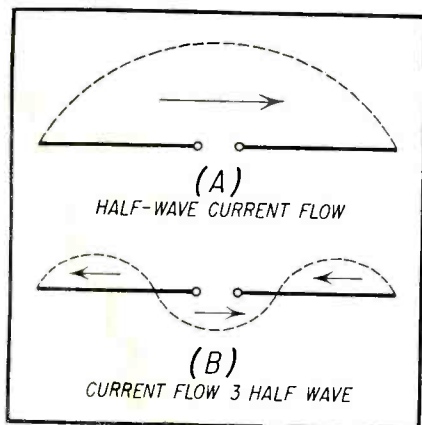


Fig. 3A—1/2 wave current flow.  
Fig. 3B—3/2 wave current flow.

pedance of approximately 1200 ohms. The ideal way to accomplish operation in both bands is to *electrically* eliminate the center component on Channels 7 through 13 and to substitute for it a component that is in phase with the end components. This condition would allow the current flow in the same direction along the entire dipole.

First let us consider the basic elements employed in the JFD Jet Helix Rainbow to accomplish this. Fig. 4A shows the three sections of the antenna that are important: the flat plane conical used for reception of Channels 2 through 6, and the high channel phasing element reflector and the high chan-

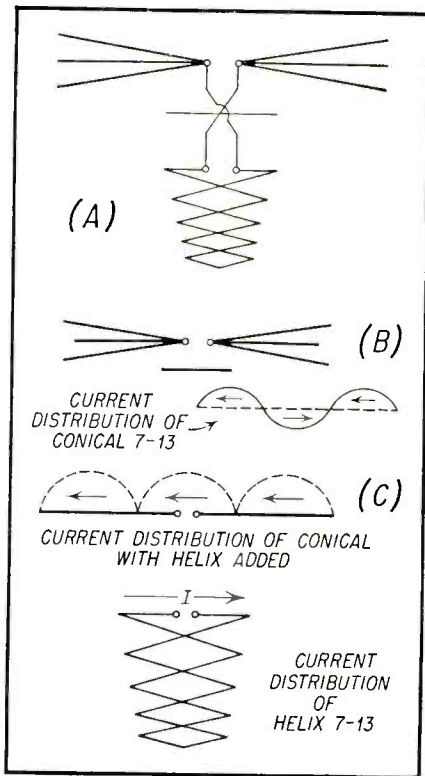


Fig. 4A—Jet Helix schematic. Fig. 4B—Current distribution of conical, channels 7-13. Fig. 4C—Current distribution of conical with helix added.

nel receiving element. It will be noted that the harness that connects the high channel element to the flat plane conical is transposed 1/2 turn. On Channels 2 through 6 the conical operates independently as the phasing element is short at these frequencies, and the length of harness plus the first crossover point of the helix have been so designed to act as a stub reflecting a high impedance at the conical terminals. On Channels 7 through 13 however, the phasing element serves to block energy normally received by the center of the conical, if we consider these two elements alone we would have the condition of Fig. 4B. It will be noted that the amplitude of the center current node has been greatly reduced. The

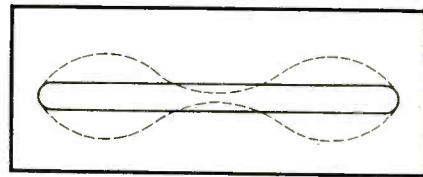


Fig. 5—Current distribution on a folded dipole.

direction of current flow in the high channel helix section is exactly the same as that of the undesired center component, but it is located in front of the conical at a definite spacing. Since the helix current flow is in the same direction as that of the undesired center section it is only necessary to transpose the interconnecting harness in order to change its phase 180 degrees at the conical terminals, and to re-insert it in phase with two end components. Fig. 4C shows the electrical result of this combination.

The Star Helix Rainbow employs exactly the same elements with the addition of one extra phasing element. The current distribution on a folded dipole is shown in Fig. 5. Here we have a closed circuit and the current reverses itself on the top half. The second phasing element is used to further reduce the amplitudes of both center components before inserting the desired component from the helical section.

Another form of this principle is employed in the JFD Dodo where a second high channel dipole is used instead of the phasing element. Instead of reducing the amplitude of the undesired center component by blocking action the component from one dipole is used. It can be seen in Fig. 6 that the harness from both small dipoles are transposed to a common take-off point, and that the harness from the large dipole is run straight. This, as in the case of the Jet Helix Rainbow and Star Helix Rainbow, is to insert the two components from the small dipoles in the correct phase; one to reduce the amplitude of the undesired component and one to substitute for it.

[Continued on page 60]

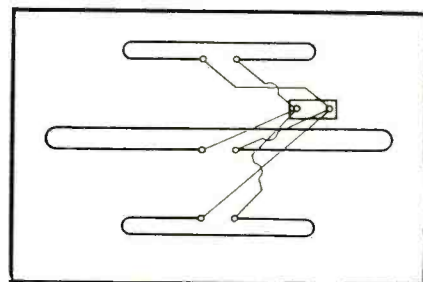


Fig. 6—Harness connections of JFD Dodo.



# More Professional Servicemen Subscribe To "SERVICE DEALER" Than Any Other Technical Magazine Because Its Feature Articles and Regular Departments Have Proven To Be The Most Helpful, Accurate and Timely. 24 Issues Cost Only \$2.



## You may subscribe if you are a:

- ★ Serviceman employed by a Service Organization.
- ★ Serviceman employed by a radio/TV Dealer.
- ★ Serviceman employed in industrial electronic service firms.
- ★ Independent serviceman who does not have a business establishment.
- ★ Employee of a Distributor.
- ★ Student enrolled in accredited Radio/TV Schools, Colleges, etc.
- ★ Hobbyists or experimenter.

- Video Speed Servicing Systems
- Rider's "TV Field Service Manual" data sheets
- Latest TV Installation and Maintenance Techniques for VHF and UHF
- Auto Radio Installation and Service

## A TYPICAL ISSUE COVERS

- Advanced Data on New Circuitry
- Production Changes and field service data on receivers
- New Tubes
- New Test Equipment, operation and application
- Hi-Fi Installation and service
- New developments, such as transistors, color, UHF, etc.
- News of the trade
- Service Short Cuts & Shop Notes
- Explanation of difficult circuits

**"Service Dealer" does not have field subscription salesmen calling on the trade.**

**You must order your subscription direct from us or from your magazine agency.**

Subscription rates: \$2.00 for 2 years

\$1.00 for 1 year

RADIO-TV SERVICE DEALER

67 W. 44 St., New York 36, N.Y.

NEW  RENEWAL

Gentlemen: Here is \$2.00 for which enter my 2 year subscription. (This rate applies in USA only. Elsewhere add \$1 per year)

Name .....

Address .....

City ..... Zone ..... State .....

Employed by (Name of firm) .....

Firm's business address .....

City ..... Zone ..... State .....

Your Position or Title .....

Check whether firm is:  Service Organization or  Dealer having Service Dept.

If some other type of company describe: .....

IF STUDENT, Name of School .....

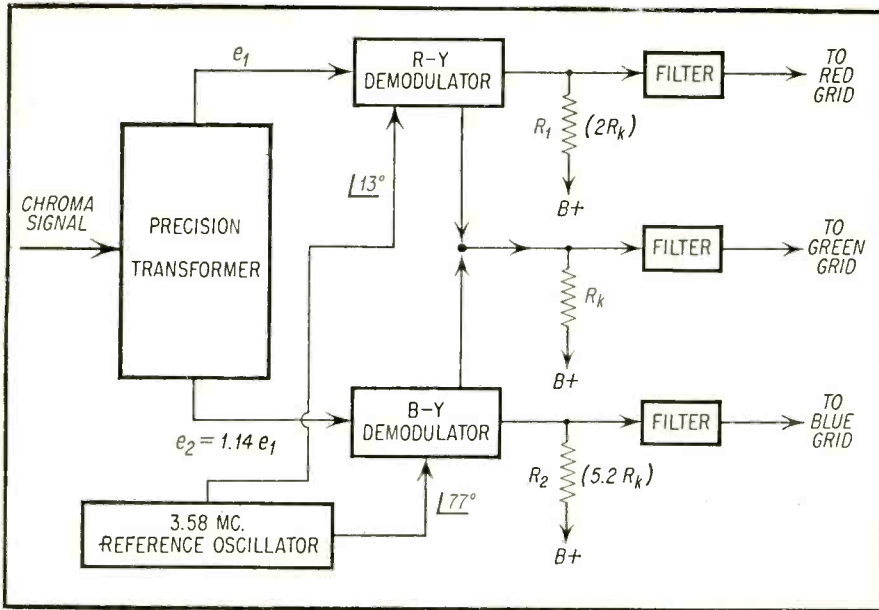


Fig. 1—Block diagram of high-level 2-triode demodulator system.

# CHROMINANCE Systems

by **BOB DARGAN**  
and **SAM MARSHALL**

Part 6

## in Color TV Receivers

In the previous installment we introduced high level 2-triode demodulation and pointed out that the 3.58 mc reference signal is required at 13 and 77 degrees for R-Y and B-Y respec-

tively or 64 degrees apart. This is shown in the block diagram of Fig. 1, and the circuit diagram of Fig. 2.

We will now proceed to derive the reasons for these unique demodulation angles, unique from the point of view that we have hitherto been accustomed to demodulate with the 3.58 mc axes displaced 90 degrees from one another. We will begin with a simplified diagram of Fig. 2 from which we will develop the complete two triode demodulation circuit. It might be pointed out that Fig. 2 as a circuit will work provided we matrix the R-Y and B-Y outputs to obtain G-Y.

At the outset, let us assume that the chrominance signal enters the transformer  $T_1$ , which feeds two secondary windings,  $S_B$  and  $S_R$ .  $S_B$  feeds the B-Y demodulator and  $S_R$  feeds the R-Y demodulator. Under these conditions the vectorial diagram will be as represented in Fig. 3. It is important to emphasize that there is an exact correspondence between the phase of the 3.58 mc in-

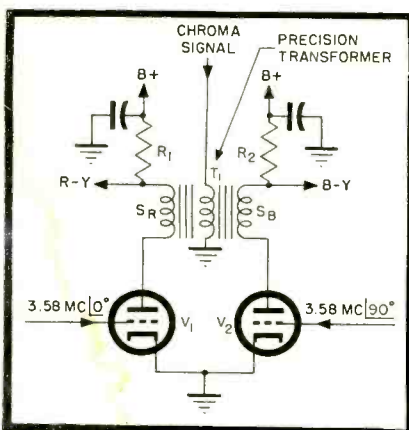


Fig. 2—Simplified circuit diagram of high-level 2-triode demodulator.

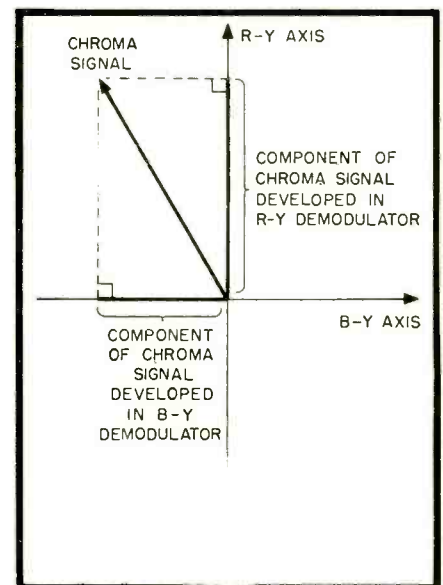


Fig. 3—Chroma signal is demodulated along R-Y and B-Y axis in R-Y/B-Y demodulator.



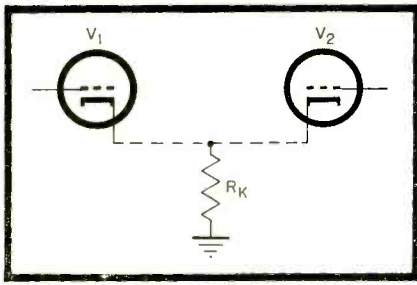


Fig. 4— $R_K$  inserted in cathode.

ected on the grid and the demodulated information between the plate and cathode.

Let us now alter Fig. 2 to include a small resistor in the cathode circuit as shown in Fig. 4. Doing so will result in a small voltage being developed across it which will be a combination of the R-Y signal in  $V_1$  and the B-Y signal flowing in  $V_2$ . We are assuming here that the plate current through each tube is of such a nature that the voltage across each plate resistor is still maintained as R-Y and B-Y.

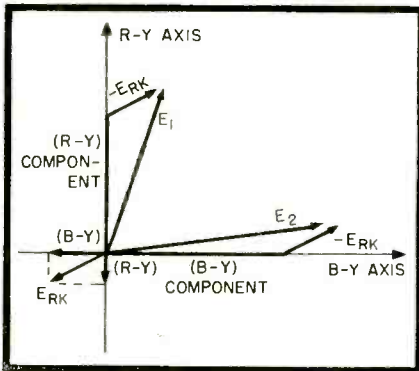


Fig. 5—Altered vector diagram.

Under these conditions we will have to alter the vector diagram of Fig. 3 to accommodate the small voltage drops in the cathode circuit. This is shown in Fig. 5 where we show the voltage  $E_{RK}$  as the vector sum of the negative B-Y and R-Y voltage drops. Now, the voltage between the plate and cathode of the R-Y demodulator ( $E_1$ ) will no longer be just R-Y but rather the difference of R-Y and  $E_{RK}$ . Therefore, we add a voltage at the top of R-Y in an opposite direction to  $E_{RK}$  and the resultant of R-Y and  $-E_{RK}$  is the voltage  $E_1$ . By a similar analysis the resultant of the voltage B-Y and  $-E_{RK}$  is equal to the voltage  $E_2$ .

Observe, now, that the demodulation voltages from plate to cathode,  $E_1$  and  $E_2$ , are no longer 90 degrees apart as was customary in previous demodulator circuits and assumed at the outset. This dictates that the angles of zero and 90 degrees on the grids of both tubes must be modified so that they are strictly in correspondence with the phase requirements of  $E_1$  and  $E_2$ . Again, it must be

emphasized that the difference between  $E_1$  and R-Y is that  $E_1$  is the voltage between plate and cathode and R-Y is the voltage between plate and ground.

By properly selecting the relative voltage on  $S_B$  and  $S_R$ , the resistors  $R_1$ ,  $R_2$  and  $R_K$ , and the phase angle at the grids as shown in Fig. 1, the system can be made to produce R-Y and B-Y at each plate resistor and G-Y across the cathode resistor  $R_K$ . These requirements are again listed below for emphasis.

- (1)  $E_1 : E_2 = 1 : 1.4$
- (2) Phase of  $E_1$  is  $13^\circ$
- (3) Phase of  $E_2$  is  $77^\circ$
- (4)  $R_1 = 2R_K$
- (5)  $R_2 = 5.2R_K$

It would be instructive at this point to assume a transmitted signal such as a red bar, and to examine the various voltages developed at both demodulators. Let us assume that the incoming signal is such as to produce a one volt signal on the grid of the red gun. Under these conditions the following signal magnitudes must be present:

- Y = .3 volt
- R-Y = .7 volt
- B = 0
- B-Y = -.3 volt
- G = 0
- G-Y = -.3 volt

We will assume one of the above conditions, that is R-Y = .7 volt, and show how the other values are caused to be established in the circuit. At the outset Y must equal .3 volt by reason of the expression:

$$Y = .3R + .59G + .11B$$

where G and B are both equal to zero.

Reference to Fig. 6 indicates that demodulation of the red signal is entirely along  $E_1$ , and because of the right angle relation of the signal with  $E_2$  it has no component along the  $E_2$  axis. Therefore the demodulating action will be restricted entirely to  $V_1$ .

An equivalent version of the demodulator circuit is shown in Fig. 7 for the specific case under discussion. Here we observe that  $V_1$  and  $V_2$  are replaced

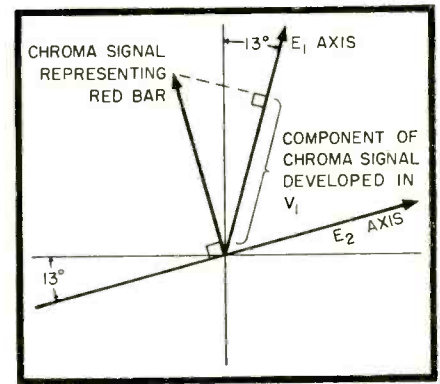


Fig. 6—Signal developed in  $E_1$ .

by equivalent switches conducting for a very short period of time during each 3.58 mc cycle at such times as to correspond to the phase angle of the 3.58 mc signal on the grid.

Note that  $R_2$  is in parallel with  $R_K$  by virtue of the switch action of  $V_2$ . Therefore B-Y has the same magnitude

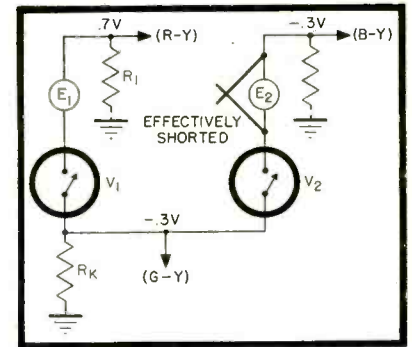


Fig. 7—Equivalent circuit.

as G-Y. Referring to the relationship for G-Y given in previous installments:

$$G-Y = -.51(R-Y) - .19(B-Y)$$

we obtain by substitution of G-Y for B-Y,

$$1.19(G-Y) = -.51(R-Y)$$

$$(G-Y) = \frac{-.51 \times (.7)}{1.19} = -.3 \text{ volt}$$

Since in the above case G-Y and B-Y are in parallel, B-Y is also equal to -.3 volt.

[Continued on page 60]

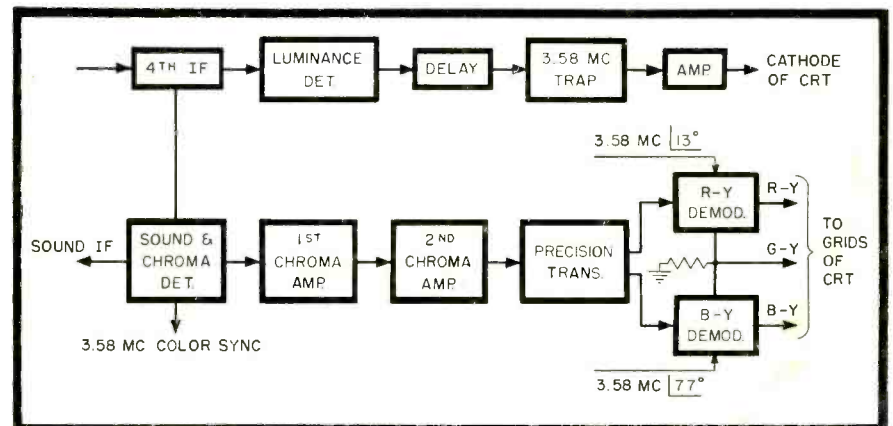


Fig. 8—Block diagram of high level 2-triode demodulator.

# SPECIAL OFFER TO OUR READERS!

By special arrangement with John F. Rider Publisher, Inc., RADIO-TV SERVICE DEALER now brings you a COMPLETE diagram service to help you do a faster, easier servicing job!

**ALL COMPLETE!**

**ALL FACTORY PREPARED!**

**ALL FACTORY AUTHORIZED!**

- ✓ Just \$1.25 for COMPLETE SERVICING INFORMATION on any TV receiver . . . any year, any make, any model . . . from 1946 on!
- ✓ Just 75¢ for COMPLETE SERVICING INFORMATION on any radio . . . any year, any make, any model . . . from 1941 on!

**TAKE ADVANTAGE OF THIS SPECIAL OFFER . . . MAIL THE COUPON TODAY!**

Radio-TV Service Dealer, 67 W. 44 Street, New York 36, N. Y.

Please RUSH me the following diagrams:

RADIO DIAGRAMS @ 75¢ EACH		
CHASSIS #	MAKE	MODEL #

TV DIAGRAMS @ \$1.25 EACH		
CHASSIS #	MAKE	MODEL #


MAKE ALL CHECKS & MONEY ORDERS PAYABLE TO Radio-TV Service Dealer  
(For all New York City orders, please submit additional 3% sales tax.)

Name .....

Address .....

City ..... State .....



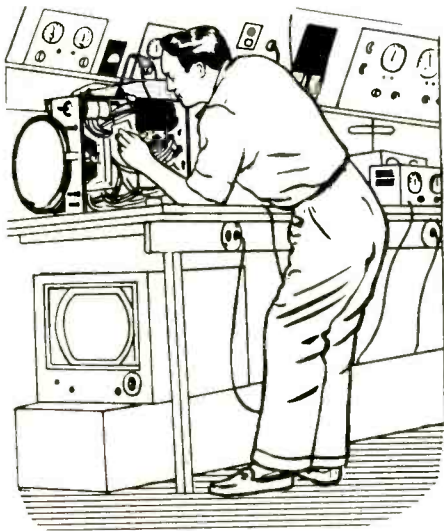

# The Work Bench

by PAUL GOLDBERG

This Month:

## MICROPHONIC & SOUND BAR PROBLEMS

### Du Mont RA 109

The receiver was turned on and sound bars were noted in the picture, but only at and above normal volume control settings. Before replacing any tubes it had to be determined whether the trouble was caused by microphonic action or by inadequate filtering in the plate or cathode of the audio output stage. The speaker was next disconnected and the receiver was turned on again. The sound bars once more appeared at a high volume setting and disappeared at a low volume setting. As a more positive check a dummy load resistance of about 5 ohms was connected in place of the speaker. This was done to simulate normal conditions while eliminating the microphonic effect. Nevertheless, sound bars again appeared at a high volume control setting. Thus, the trouble was in the filtering.

First a new filter was shunted across C222A, the plate load filter condenser. This cut down the intensity of the sound bars to some extent. Next, a filter was placed across C222B, the plate load filter of the first and second audio amplifiers. This action decreased the intensity of the sound bars even more. A filter was then shunted across C222D, the audio output cathode filter. This eliminated the sound bars in the picture completely. It was noted, moreover, that C222A, B, or D, individually would not eliminate the sound bars. It was therefore decided that the entire can, C222A, B, C, and D be replaced. This was done and the receiver now functioned properly.

Let us see now how sound bars were produced in this case. Sound bars are horizontal bars that vary in step with the modulation of the signal of the station. The number of bars varies with the frequency of the audio signal. At moments when the sound frequency is 300 cycles, there are five horizontal dark

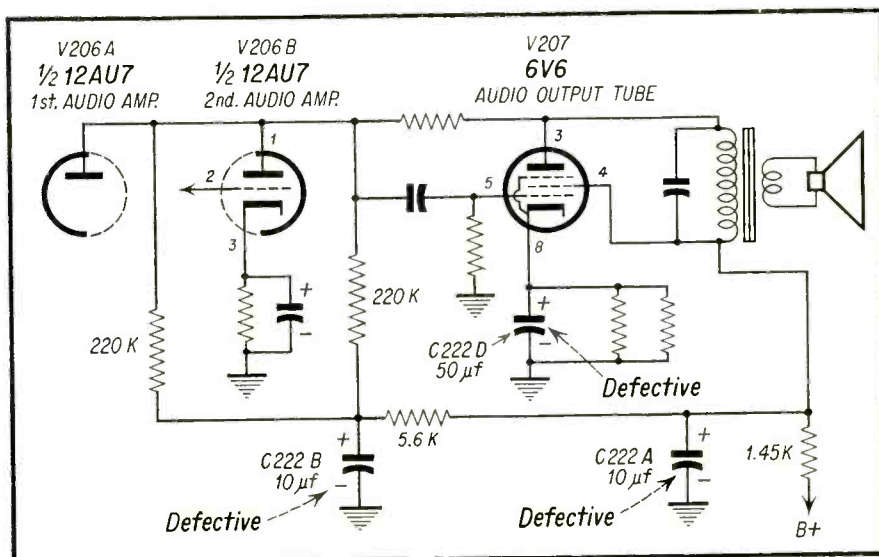


Fig. 1—Partial schematic of Du Mont RA 109

bars; when the sound frequency is three thousand cycles there are fifty horizontal dark bars (one dark bar per 60 cycles). The intensity of the bars varies with the strength of the audio signal. When a receiver is operated at a high volume level, there are large audio frequency variations of current in the plate and cathode circuits of the audio output stage. These current variations impose a varying drain on the "B" supply. If the plate and cathode supply circuits are not adequately filtered the current variations in the audio output stage may produce an appreciable amplitude of audio frequency ripple in the "B" supply voltages. This ripple can affect the operation of various sections of the receiver, producing audio frequency variations in picture signal gain, in width, and in horizontal sync phasing. The general effect is the appearance of sound bars in the picture. The bars are not present at a low volume level because the voltage regulation is better at reduced loads.

### Admiral 19E1

The receiver (in cabinet) was turned on and as the volume was turned up a microphonic whistle was heard from the speaker. The rf oscillator was then replaced with a number of new 6J6 tubes but still the microphonic whistle remained. It might be added that at low volume the whistle disappeared.

The speaker mounting screws and nuts were then removed and the speaker was suspended by hand in approximately the same location, but away from the cabinet; but this did not solve the problem. The receiver was next removed from the cabinet. Again at above normal volume the microphonic whistle was heard.

Suspecting a vibrating component in the tuner which usually causes this condition the side cover was then removed from the tuner to provide recess to the rf oscillator circuit. A long plastic

[Continued on page 59]

# Circuit

by Radio Television  
Service Dealer  
Technical Staff

This Month's Circuit:  
Admiral 21A3Z  
Voltage Distribution

# Analysis

Suppose you answered a call for service and found that very common combination of symptoms, namely, raster but no sound and no picture. Nine chances out of ten the wheels upstairs would turn and you would conclude that there was trouble somewhere in the tuner or in the video strip somewhere before sound take-off. You could be wrong though if you happened to run into a circuit similar to that used in many Admiral receivers.

Figure 1 is a partial schematic of the Admiral 21A3Z chassis. Because of the unusual arrangement used for the distribution of B+ voltage, a failure at V204, the audio output tube would result not only in the loss of sound, but loss of picture as well. Notice that the power supply delivers 265 volts at the filter choke L501. This is fed to the plate of the 6W6 audio output tube via the fuse, R502, and the primary of the audio output transformer. The cathode of the audio output tube, however, does not return to B-, or ground, through the usual cathode bias resistor. Instead, it is connected so that it supplies plate voltage for a number of other stages. Fig. 2 is a partial block diagram showing how these stages receive their B+ from the cathode of the audio output tube. In effect the audio output tube in this case acts as a dropping resistor, dropping the voltage from 265 at the plate to 145 at the cathode.

The advantages of this system of B+ distribution are twofold. First, by placing tubes in series, as is done here, the current handling requirement of the high voltage winding on the power transformer is reduced, thereby cutting costs. Secondly, as will be explained later, the audio output tube is made to serve still another function, namely, that of a voltage regulator for the 145 volt supply line.

Figure 1 is a partial schematic which corresponds to that part of Fig. 2 shown

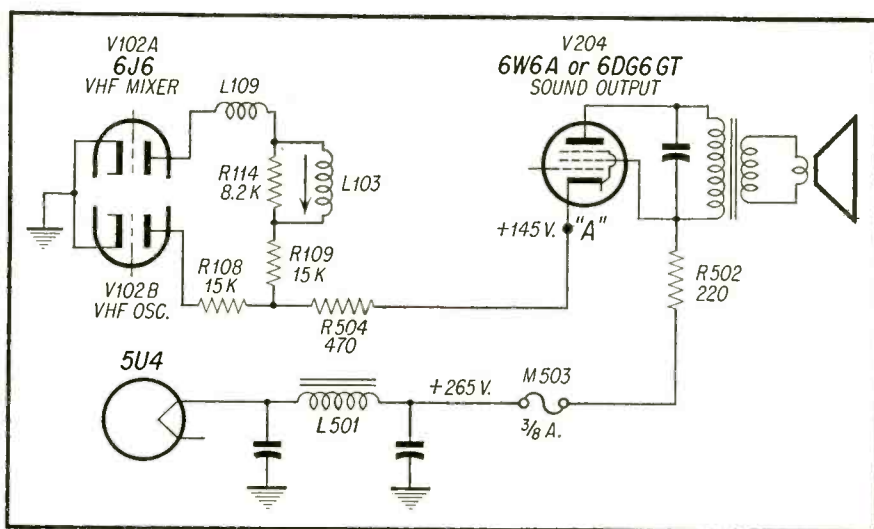


Fig. 1—Partial schematic showing B+ distribution in Admiral 21A3Z.

in heavy lines. Actually, it is only one of the many parallel paths from the cathode of V204 to ground shown in Fig. 2. We are concerned here with this path because it is the one involved

in producing the symptoms mentioned at the outset.

Figure 3 is a simplified equivalent circuit corresponding to the schematic of [Continued on page 52]

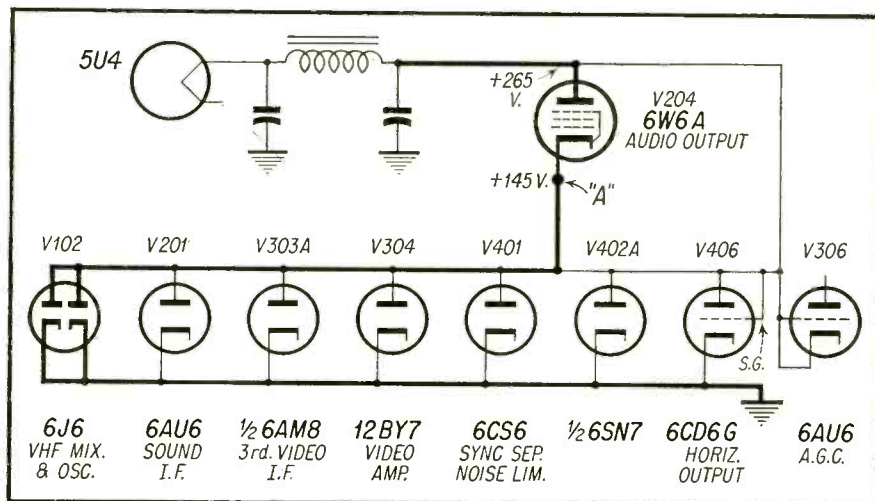


Fig. 2—Simplified diagram of B+ distribution in Admiral 21A3Z.



Mfr: Emerson Chassis No. 120140-B

Card No. EM 140-1 Model No. 680D


Section Affected: Sync

Symptom: Critical horizontal and vertical hold

Cause: Leaky condenser

What to Do:

Replace: C56 (.047  $\mu$ f)

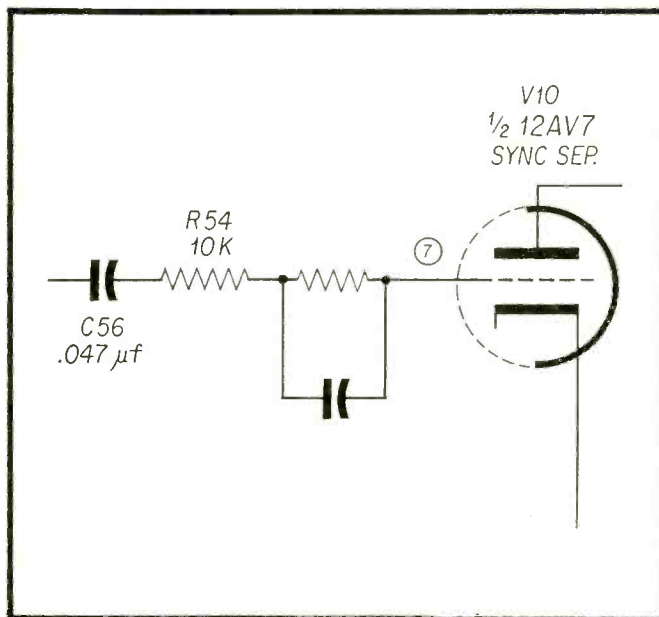

Mfr: Emerson Chassis No. 120140-B

Card No. EM 140-2 Model No. 680D


Section Affected: Pix and sound

Symptom: No pix or sound

Cause: Open resistor

What to Do:

Replace: R52 (1K)

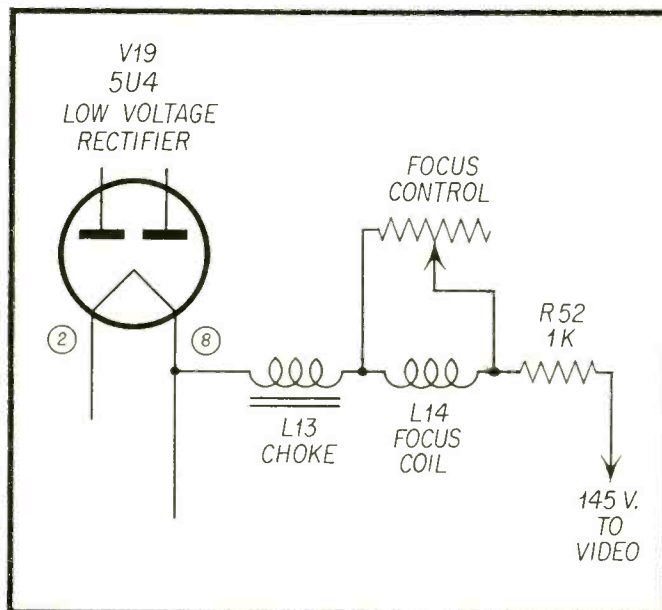

Mfr: Emerson Chassis No. 120140-B

Card No. EM 140-3 Model No. 680D


Section Affected: Raster


Symptom: Flashes in pix

Cause: Arcing condenser

What to Do:

Replace: C91 (18  $\mu$ f)

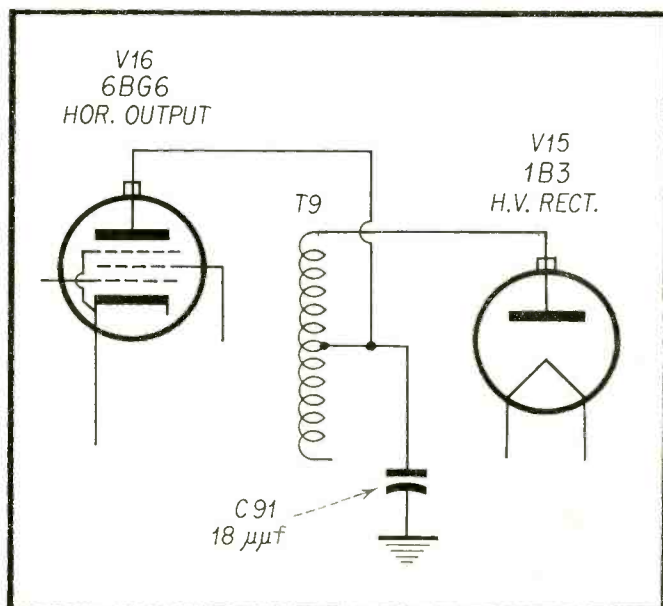

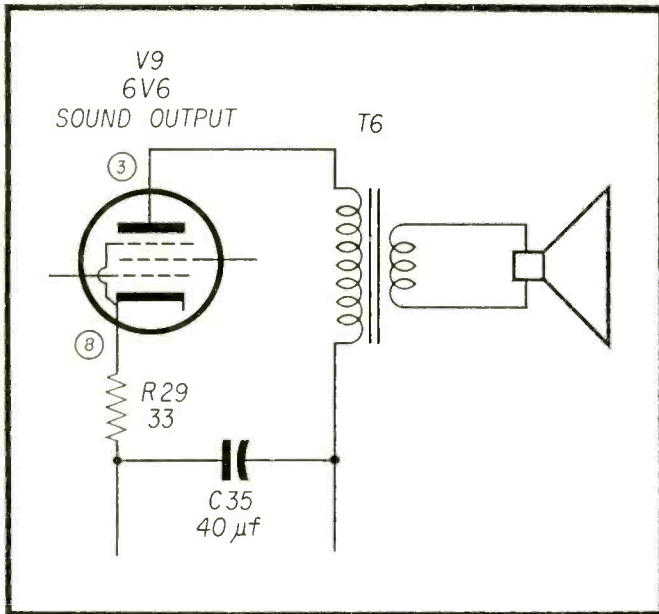

Mfr: Emerson Chassis No. 120140-B

Card No. EM 140-4 Model No. 680D


Section Affected: Pix

Symptom: Sound bars in pix

Cause: Leaky filter condenser

What to Do:

Replace: C35 (40  $\mu$ f)

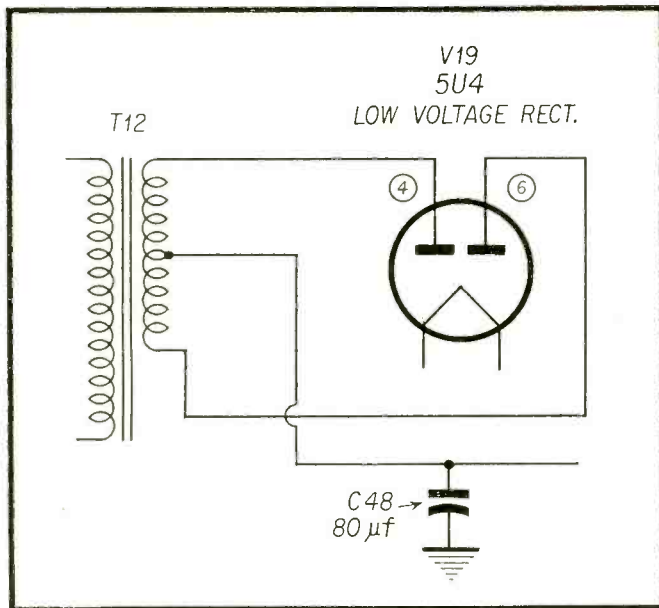

Mfr: Emerson Chassis No. 120140-B

Card No. EM 140-5 Model No. 680D


Section Affected: Sync

Symptom: Critical vertical hold and horizontal wiggle

Cause: Leaky filter condenser

What to Do:

Replace: C48 (80  $\mu$ f)

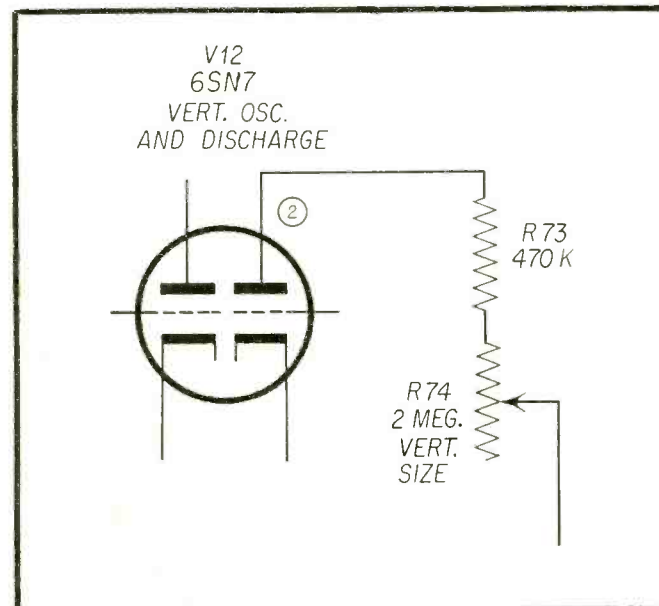

Mfr: Emerson Chassis No. 120140-B

Card No. EM 140-6 Model No. 680D

Section Affected: Pix

Symptom: Cannot reduce height properly

Cause: Vertical control changed in value

What to Do:

Replace: R74 (2 meg.)



Mfr: Motorola Chassis No. TS-525

Card No: MO525-1


Section Affected: Pix and Sound

Symptoms: Excessive TVI

Reason for Change: Circuit improvement

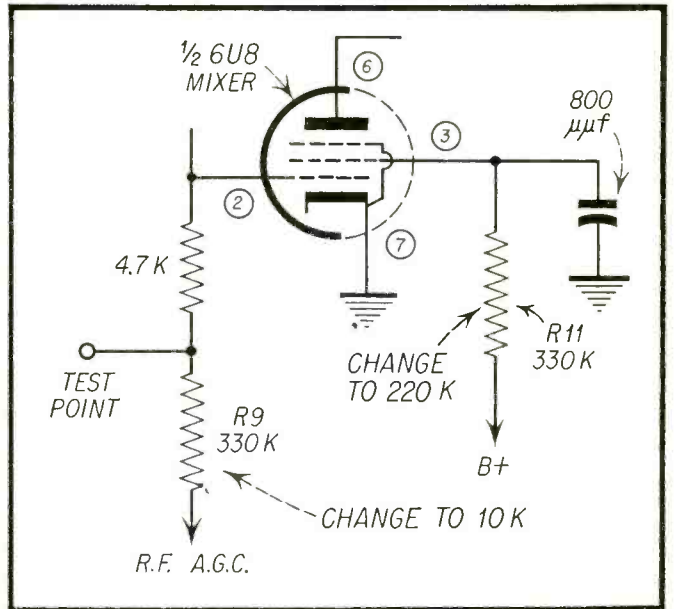**What to Do:**

Change: R9 from 330K to 10K also, R11 from 330K to 220K



Mfr: Motorola Chassis No. TS-525

Card No: MO525-2


Section Affected: Pix

Symptoms: Horizontal Pulling

Cause: Component Failure

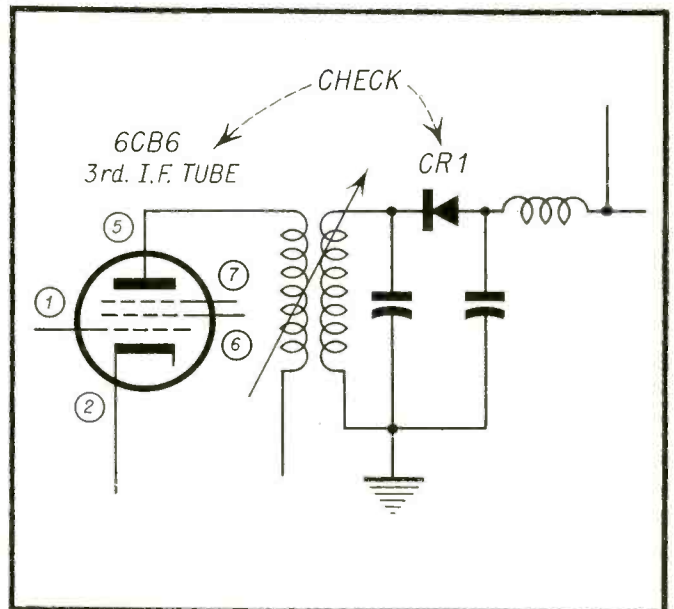**What to Do:**

Change: 3rd if tube (6CB6) or video detector crystal (CR1)



Mfr: Motorola Chassis No. TS-525

Card No: MO525-3


Section Affected: Pix


Symptoms: Picture Pulling

Cause: Coupling between horizontal hold control and brightness control leads

**What to Do:**

Add: .01 μf at brightness control

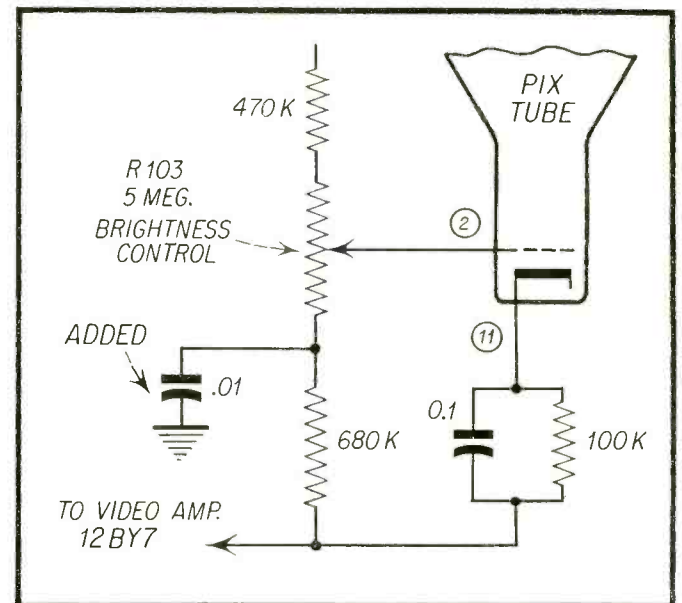

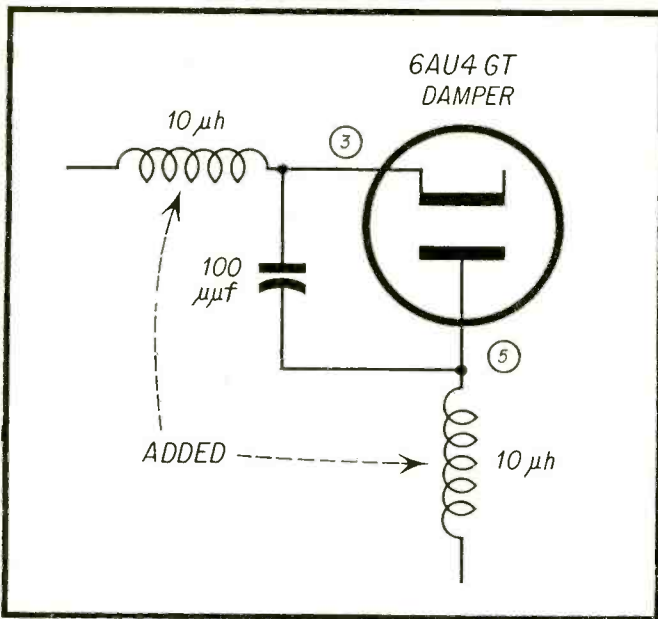

Mfr: Motorola Chassis No. TS-525

Card No: MO525-4


Section Affected: Pix

Symptoms: Horizontal Jitter

Reason for Change: Circuit Improvement

What to Do:

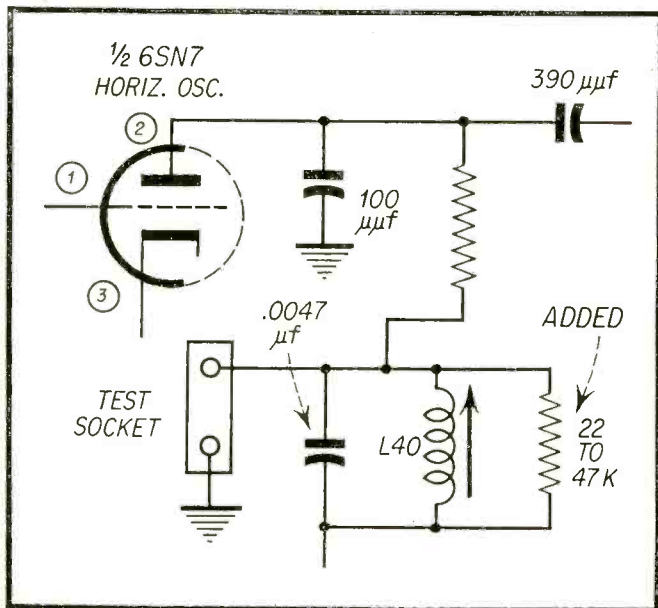Add: 10 microhenry chokes in plate and cathode leads of damper tube



Mfr: Motorola Chassis No. TS-525

Card No: MO525-5


Section Affected: Pix

Symptoms: Horizontal jitter and hunting

Reason for Change: Circuit improvement

What to Do:

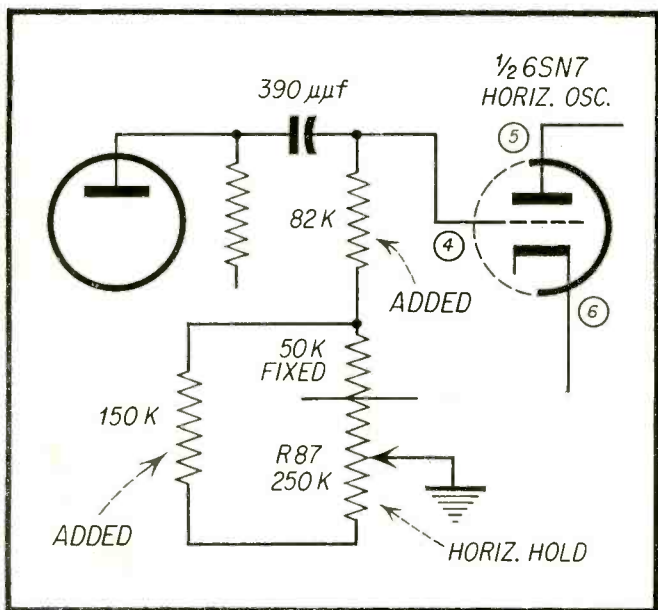Add: 22K to 47K across horizontal osc. coil



Mfr: Motorola Chassis No. TS-525

Card No: MO525-6

Section Affected: Pix

Symptoms: Critical horizontal lock-in

Reason for Change: Circuit improvement

What to Do:

Check: Horizontal hold control

Add: 82K in series with hor. hold control

Also: 150K in shunt with hor. hold control




# SENTINEL

Model No.

1U-581, -582, -584, -585

## TUBE LIST

SYMBOL	TUBE	CIRCUIT FUNCTION
	6AF4	UHF Oscillator
V1	6BZ7	VHF RF Ampl
V2	6X8	VHF Converter
V3	6CB6	Video IF Ampl
V4	6CB6	Video IF Ampl
V5	6CB6	Video IF Ampl
V6	6CB6	Video IF Ampl
V7	12BY7	Video Ampl
V8	6AU6	1st Sound IF Ampl
V9	6AU6	2nd Sound IF Ampl
V10	6AL5	Ratio Detector
V11	6AV6	Audio Ampl & Bias Clamp
V12	6K6GT	Audio Output
V13	12AU7	Sync Ampl & Phase Splitter
V14	6BE6	Noise Gate
V15	6AU6	Sync Ampl
V16	6AU6	AGC Keyer
V17	6AL5	Phase Detector
V18	6SN7GT	Horizontal Oscillator
V19	6RG6GT	Horizontal Output
V20	1B3GT	High Voltage Rectifier
V21	6W4GT	Horizontal Damper
V22	21FP4A	21" Picture Tube
V23	5U4C	Electrostatic Focus
		Low Voltage Rectifier
V24	5Y3GT	Low Voltage Rectifier
V25	6SN7GT	Vertical Oscillator
V26	6BL7GT	Vertical Amplifier

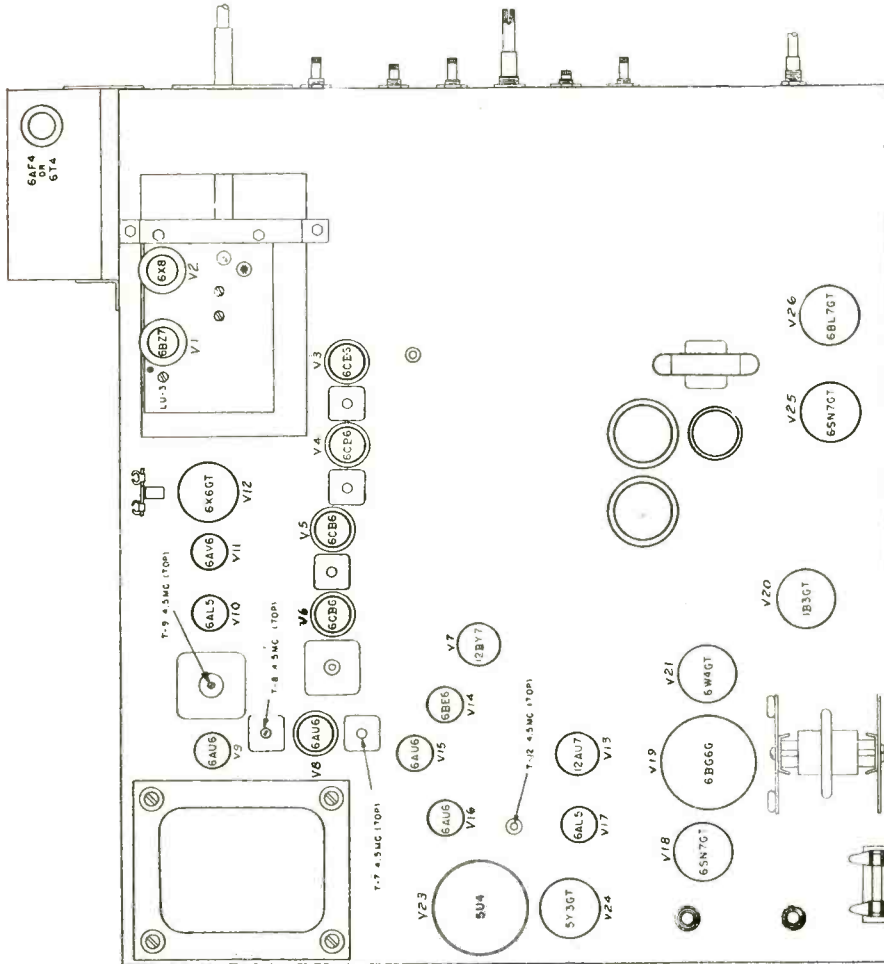


TOP VIEW



## KEY VOLTAGES

B+, plate of damper, V21	pin 5	300 vdc
Plate(s) of VERT. OSC., V25	pin 2	145 vdc
	pin 5	135 vdc
Plate of Vert. Out., V26	pins 2 and 5	280 vdc
Plate(s) of Hor. Osc. V18	pin 2	250 vdc
	pin 5	180 vdc
Grid of Hor. Out., V17	pin 5	-85 vdc

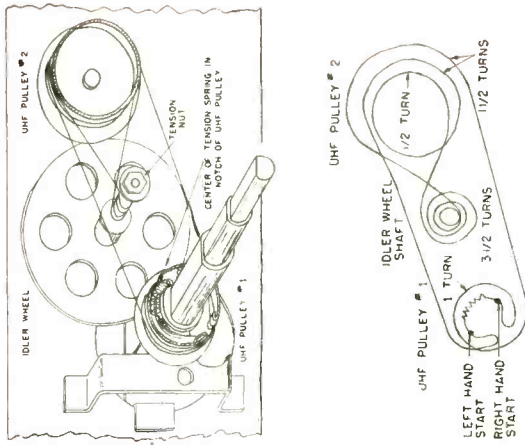(All voltages are measured with a VTVM connected between the tube pins and chassis.)



DIAL STRINGING

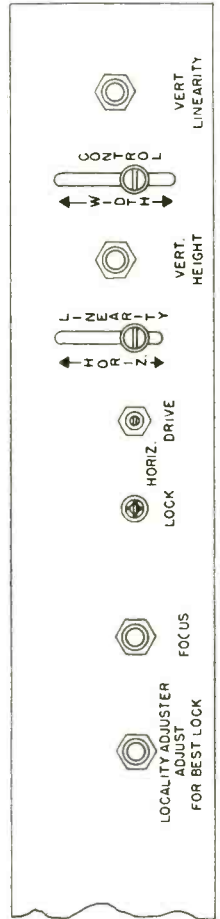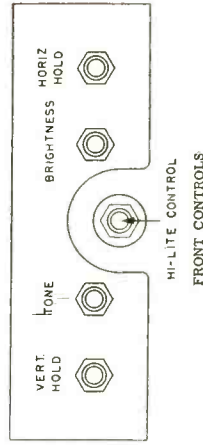

REAR CONTROLS

# TV FIELD SERVICE

Pre-published from Rider "TV Field Service Manual."

by Rider & Alsberg

Copyright 1954, John F. Rider Publisher, Inc.

**GENERAL INSTALLATION INSTRUCTIONS**

While each receiver is correctly aligned at the factory rough handling in transit, drift, etc., may throw the receiver off, so we suggest that the proper oscillator trimmers, ratio detector, and rear panel controls be checked for correct adjustment with a transmitted television pattern, in the customer's home at the time of installation. Be sure to have the receiver operating for one-half hour before making these adjustments. Listed below is the correct procedure to follow in making these adjustments.

- (A) Check all operating channels, using FINE TUNING CONTROL for best picture detail. (See paragraph PEAKING THE VHF OSCILLATOR TRIMMERS.)
- (B) Check LOCALITY ADJUSTER CONTROL located on back of chassis for proper setting.
- (C) Set AGC LEVEL control.

**PEAKING THE VHF OSCILLATOR TRIMMERS**

- (A) Set channel selector knob to the highest VHF operating channel.

**NOTE:** If highest VHF operating channel is channel 6 or below disregard step (E).

- (B) Remove channel selector and fine tuning knobs. This will expose the oscillator adjustment screws.
- (C) Set fine tuning to center position (when white painted line on fine tuning pulley is centered on fine tuning shaft pulley).
- (D) Use a non-metallic screwdriver such as polyesterene or nylon.
- (E) **FOR CHANNELS 7 THRU 13.** Adjust trimmer screw located at right of fine tuning pulley for best picture detail.
- (F) **FOR CHANNELS 2 THRU 6.** Set channel selector to highest operating channel between 2 and 6. Adjust trimmer screw located below fine tuning shaft pulley for best picture detail.

**FRONT REMOVABLE SAFETY GLASS**

To remove safety glass for cleaning purposes, remove screws from strip holding top of safety glass. Tilt top of safety glass forward and lift out.

**PIN CUSHION DISTORTION**

When distortion or non-linearity at the left and/or right sides of the picture tube occurs: Adjust the anti-pin cushion magnet assemblies held by wing nuts on the deflection yoke mounting bracket and extending on both sides of the picture tube for least distortion and for best linearity.

**HORIZONTAL LOCK**

If it is impossible to keep the test pattern or picture from continually moving or breaking up in a HORIZONTAL DIRECTION with the HORIZONTAL HOLD CONTROL, adjust the HORIZONTAL LOCK CONTROL, BY:

1. Set HORIZONTAL HOLD CONTROL to its mid position.
2. Turn the HORIZONTAL LOCK SCREW until pattern or picture locks in.
3. **PATTERN** or picture should now lock in evenly from either side of the HORIZONTAL HOLD CONTROL. An additional adjustment of the HORIZONTAL LOCK may be necessary to bring the locking into the center of the HORIZONTAL HOLD CONTROL.

**HORIZONTAL DRIVE**

The correct procedure for setting the HORIZONTAL DRIVE CONTROL is as follows:

1. Set HORIZONTAL WIDTH CONTROL for maximum picture width. Control in upper-most position.
2. Set HORIZONTAL LINEARITY CONTROL to bottom position.
3. Turn HORIZONTAL DRIVE paddler in until drive lines appear (bright vertical lines near center of screen).
4. Turn HORIZONTAL DRIVE paddler out until drive lines disappear.
5. Reset HORIZONTAL WIDTH AND HORIZONTAL LINEARITY to their correct position.

**ADJUSTMENT FOR STATION BUZZ**

If station buzz is excessive, adjust the ratio detector secondary adjustment screw located on top of the ratio detector for minimum buzz. **MAKE SURE THAT THIS POSITION IS BETWEEN THE TWO MAXIMUM buzz peaks** that will be noticed when adjustment screw is turned to the right or left of the minimum buzz position.

**ENGRAVED EFFECT IN PIX**

Tuner fine tuning  
Contrast con.  
V2, V3, V4, V5, V6, V7, V16, V22  
AGC Level and Vid. Load con.  
Check Vid. Det. xtal IN60 (Part of T6)  
Check 0.047  $\mu$ f cap. connected to pin 2 of V7  
Check Vid. Det. and Amp peaking coils

**VERT. BARS**

Hor. Drive con.  
V19, V21  
Check 56  $\mu$ mf cap. connected to yoke terminals  
Defl. yoke ringing

**PIX BENDING**

Hor. Hold and Freq. con.  
V16, V17, V18, V19  
Locality and AGC Level con.  
Check 0.0047 and 0.047  $\mu$ f caps. connected to pin 1 of V18

**WEAK OR NO PIX—SOUND WEAK—RASTER OK**

Tuner fine tuning  
V1, V2, V3, V4, V5, V6  
Check Vid. Det. xtal IN60 (Part of T6)  
RF and IF alignment

**INSUFFICIENT BRIGHTNESS**

Ion trap  
Brightness and Hor. Drive con.  
V19, V20, V21, V22, V23, V24  
Low line voltage

**RASTER BLOOMING**

Hor. Drive con.  
V19, V20, V21, V22  
Check HV Filter cap.  
Check 1.2 Meg. Res. connected to HV Filter cap.

**NO RASTER—NO SOUND**

Power input circuit  
V23, V24  
Check line fuse F1 (3 Amps)  
Check filter choke

**NO RASTER—SOUND OK**

Brightness con.  
Check HV Fuse F2 (0.2 Amps.)  
Ion trap  
V18, V19, V20, V21, V22  
HV trans. Hor. yoke CRT connections

**WEAK PIX—SOUND AND RASTER OK**

Tuner fine tuning  
Contrast con.  
V3, V4, V5, V6, V7, V8, V16  
Check Vid. Det. xtal IN60 (Part of T6)  
AGC Level, and Vid. Load con.

**POOR VERT. LIN.**

Vert. Size and Lin. con.  
V25, V26  
Check 0.1  $\mu$ f cap. connected to pin 1 of V26  
Check 100  $\mu$ f Elec. cap. connected to pin 6 of V26  
Vert. Out. trans.

**PIX JITTER UP & DOWN**

Vert. Hold and Contrast con.  
Locality and AGC Level con.  
V13, V16, V25, V26  
Check 0.0047  $\mu$ f cap. connected to pin 3 of V25

**SMEARED PIX**

Tuner fine tuning  
Contrast con.  
V3, V4, V5, V6, V7, V16  
Check Vid. Det. and Amp. peaking coils  
AGC Level and Vid. Load. con.  
Check 0.017  $\mu$ f cap. connected to pin 2 of V7  
IF and RF alignment  
Check Vid. Det. xtal IN60 (Part of T6)

**SOUND BARS IN PIX**

Tuner fine tuning  
V1, V2, V3, V4, V5, V6  
Check adjustment of T7  
IF and RF alignment

**INSUFFICIENT RASTER HEIGHT**

Vert. Size and Lin. con.  
V23, V24, V25, V26  
Check 0.1  $\mu$ f cap. connected to pin 1 of V26  
Vert. Out. trans.  
Low line voltage

**NO VERT. DEFL.**

V25, V26  
Check 0.1  $\mu$ f cap. connected to pin 1 of V26  
Vert. Defl. coils (yoke)  
Vert. Out and Osc. trans.

**NO VERT. SYNC.—HOR. SYNC. OK**

Vert. Hold con.  
Vert. Int. network  
V25, V26  
Check 0.0047  $\mu$ f cap. connected to pin 3 of V25


**NO HOR. OR VERT. SYNC.—PIX SIGNAL OK**

V13, V14, V15, V16  
Check 0.047  $\mu$ f cap. connected to pin 7 of V13

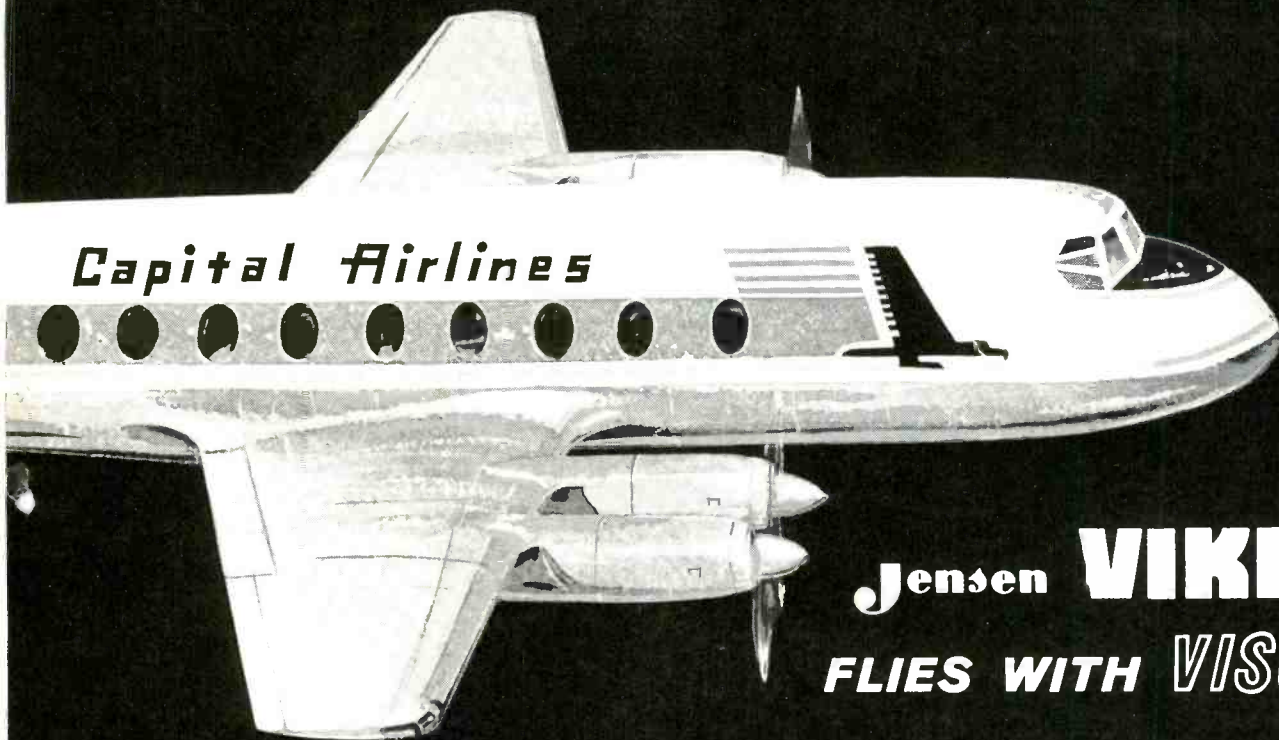**NO HOR. SYNC.—VERT. SYNC. OK**

Hor. Hold and Freq. con.  
V13, V18, V19  
Check 600  $\mu$ mf cap. connected to pin 4 of V18





Jensen **VIKING**  
**FLIES WITH VISCOUNT**

**AN OUTSTANDING AVIATION ACHIEVEMENT!**

With the purchase of forty Vickers Viscounts, Capital Airlines culminates an extended search for the type of aircraft to best serve its millions of loyal passengers. These outstanding four propeller turbine engine aircraft will add new and important pages to aviation history.

**AN OUTSTANDING SPEAKER ACHIEVEMENT!**

Jensen Manufacturing Company is proud of Capital's selection of Viking Speakers for the audio system of this new modern aircraft. This system makes use of 22 Jensen Viking 4J6 type speakers mounted in the thin cabin walls between the windows on both sides of the cabin.

Leading parts distributors and service dealers know VIKING by Jensen as a stand-out economical replacement speaker line with compactness and efficient performance that universally qualifies VIKING for all radio and TV speaker replacements. And when you sell or install a VIKING, you get the same locked-in alignment, the same precision construction and the same dependability that led Capital to specify them for their Viscount fleet.



**Jensen**

MANUFACTURING COMPANY • 6601 S. Laramie • Chicago 38, Ill.  
Division of the Muter Company  
IN CANADA: Copper Wire Products, Ltd. Licensee

**WORLD'S QUALITY STANDARD FOR MORE THAN A QUARTER CENTURY**

peak  
to peak

VTVM



by **Harry C. Ashley**  
**and Philip Portnoy**  
Chief Engineers, EICO Mtg. Corp.

Expressly designed for TV servicing, the EICO Model 232 (249) peak-to-peak vtvm features a full-wave, high frequency rectifier circuit that responds to and measures the peak-to-peak voltage value of complex and sine waveforms even when *dc* is present. It also reads the *rms* voltage of sine waves (on a separate scale), *dc* voltage values, and resistance values. For consistently high accuracy, there are seven non-skip ranges on all functions to provide a uniform 3 to 1 scale ratio between adjacent ranges.

All *rms* scales are in black with full-scale values of 1.5, 5, 15, 50, 500, and 1500 volts. All peak-to-peak scales are in red with full-scale values 4, 14, 42, 140, 420, 1400, and 4200 volts. When the instrument is set at the 1.5 volt

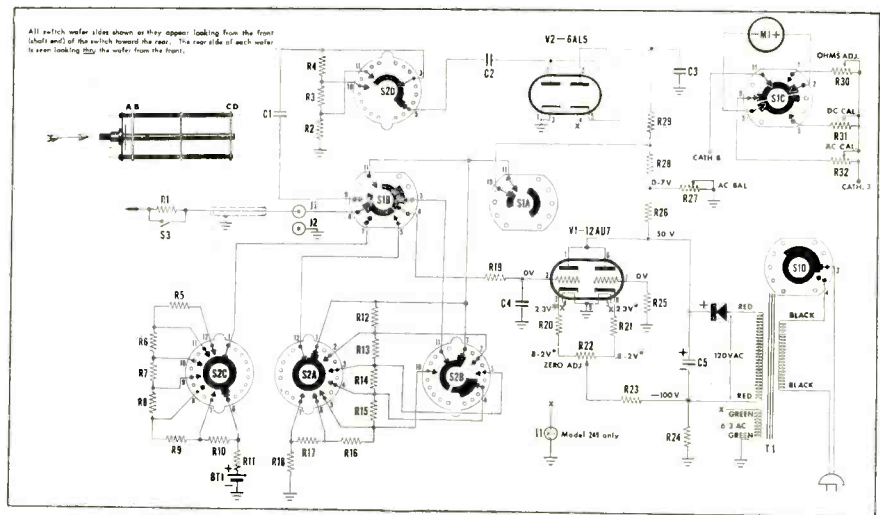


Fig. 1—Complete circuit diagram of EICO Model 232 (249) peak-to-peak VTVM.

Sym.	Description	Sym.	Description
B1	battery, 1 1/2V	R14	res., 700K $\Omega$ , 1/2W, 1%
C1	cap., .1mf - 1000V	R15	res., 200K $\Omega$ , 1/2W, 1%
C2, C3	cap., .025mf - 400V	R16	res., 70K $\Omega$ , 1/2W, 1%
C4	cap., .003mf - 400V	R17	res., 20K $\Omega$ , 1/2W, 1%
C5	cap., elec. 10mf - 150V	R18	res., 10K $\Omega$ , 1/2W, 1%
CR1	rect., .35 ma	R19	res., 3.3M $\Omega$ , 1/2W
I1*	bulb, #47	R20, 21	res., 680 $\Omega$ , 1/2W
M1	meter, 400 $\mu$ a	R22, 30	pot., 2K $\Omega$ , linear
R1	res., 1M $\Omega$ , 1/2W	R23	res., 47K $\Omega$ , 1/2W
R2	res., 150K $\Omega$ , 1/2W, 1%	R24	res., 68K $\Omega$ , 1/2W
R3	res., 325K $\Omega$ , 1/2W, 1%	R25	res., 4.7M $\Omega$ , 1/2W
R4	res., 900K $\Omega$ , 1W, 1%	R26	res., 33K $\Omega$ , 1/2W
R5	res., 9M $\Omega$ , 1/2W, 1%	R27	pot., 10K $\Omega$ , linear
R6	res., 900K $\Omega$ , 1/2W, 1%	R28	res., 82M $\Omega$ , 1/2W
R7	res., 90K $\Omega$ , 1/2W, 1%	R29	res., 18M $\Omega$ , 1/2W
R8	res., 9K $\Omega$ , 1/2W, 1%	R31, 32	pot., 2K $\Omega$ , linear
R9	res., 900 $\Omega$ , 1/2W, 1%	S1	switch, function
R10	res., 90 $\Omega$ , 1/2W, 1%	S2	switch, range
R11	res., 9.7 $\Omega$ , 1/2W, 1%	V1	tube, 12AU7
R12	res., 7M $\Omega$ , 1W, 1%	V2	tube, 6AL5
R13	res., 2M $\Omega$ , 1/2W, 1%		

Rotary on all switch wafers shown in extreme counter-clockwise position.

FUNCTION SWITCH S1		RANGE SWITCH S2	
Position	Setting	Position	Setting
1	OFF	1	1.5V, R X 1
2	AC VOLTS	2	5V, R X 10
3	-DC VOLTS	3	15V, R X 100
4	+DC VOLTS	4	50V, R X 1000
5	OHMS	5	150V, R X 10K
		6	500V, R X 100K
		7	1500V, R X 1M

Fig. 2—Parts list of VTVM

range, the *rms* or p-p scales on the lowest arc (designated as LOW-AC) are read; on higher ranges, the scales on the two center arcs are read. It should be noted that the fixed ratio of 2.83 to 1 between corresponding peak-to-peak and *rms* scales is derived from the relationship between the peak-to-peak and *rms* values of a sine wave. Therefore, while peak-to-peak readings are valid regardless of whether the waveform is complex or sine, *rms* readings are valid only for sine waves. Note also that the time delay between the instant the leads are removed from the source being measured and the instant the meter pointer returns to zero is normal and is the result of circuit constants selected to permit accurate measurement of recurrent pulses with low repetition rates.

### Operation

The central circuit in the operation of this instrument is a vacuum-tube bridge circuit using a 12AU7 twin-triode. When the bridge is balanced, the voltages at the two cathodes will be equal and the meter connected across them will read zero.

**DC Voltmeter Operation:** Referring to Fig. 1, when a positive *dc* voltage is applied, a fraction (depending on the range setting) is taken from the range voltage divider (*R12-R18*) and applied to the grid of *V1a*. This causes the current through *V1a* to increase and consequently the cathode voltage of *V1a* to increase. Concurrently the voltage on the arm of *R22* tends to increase,  
[Continued on page 58]



# WHAT'S YOUR SERVICE PROBLEM?

# PHOTOFACT HELPS YOU SOLVE IT

**FASTER, EASIER, BETTER, MORE PROFITABLY!**

## THE WORLD'S FINEST SERVICE DATA

PHOTOFACT Service Data is the *only* service information based upon first-hand examination of the actual production-run receivers and equipment. It is authentic, uniform data developed through actual study and analysis by service engineers in the Howard W. Sams Laboratories. PHOTOFACT is the *only* data prepared from the practical point of view of the Service Technician.

Thousands of Service Technicians use PHOTOFACT daily for time-saving, profit-boosting service operations. If you've never used PHOTOFACT, you've never realized your full earning power—you've never given such complete customer satisfaction. So get the proof for yourself. Try PHOTOFACT—use it on any job. Your Parts Distributor has the Folder Sets you need for any of the 17,000 TV and radio receivers, changers, recorders, etc., covered in PHOTOFACT. Once you use this great service, we know you'll want the complete PHOTOFACT Library.



THESE GREAT FEATURES ARE EXCLUSIVE IN PHOTOFACT—THEY HELP YOU EARN MORE DAILY, HELP INSURE CUSTOMER SATISFACTION

### FULL SCHEMATIC COVERAGE

1. Famous "Standard Notation" uniform symbols are used in every schematic.
2. The same standard, uniform layout is used for each schematic.
3. Diagrams are clear, large, easy to read, easy to handle.

4. Wave forms are shown right on the TV schematics for quick analysis by 'scope.
5. Voltages appear on the schematics for speedy voltage analysis.
6. Transformer lead color-coding is indicated on the schematic.
7. Transformer winding resistances appear on the schematic.
8. Schematics are keyed to photos and parts lists.

### FULL PHOTOGRAPHIC COVERAGE

9. Exclusive photo coverage of all chassis views is provided for each receiver.
10. All parts are numbered and keyed to the schematic and parts lists.
11. Photo coverage provides quicker parts identifications and location.

### ALIGNMENT INSTRUCTIONS

12. Complete, detailed alignment data is standard and uniformly presented in all Folders.
13. Alignment frequencies are shown on radio photos adjacent to adjustment number—adjustments are keyed to schematic and photos.

### TUBE PLACEMENT CHARTS

14. Top and bottom views are shown. Top view is positioned as chassis would be viewed from back of cabinet.
15. Blank pin or locating key on each tube is shown on placement chart.
16. Tube charts include fuse location for quick service reference.

### TUBE FAILURE CHECK CHARTS

17. Shows common trouble symptoms and indicates tubes generally responsible for such troubles.
18. Series filament strings are schematically presented for quick reference.

### COMPLETE PARTS LISTS

19. A complete and detailed parts list is given for each receiver.
20. Proper replacement parts are listed, together with installation notes where required.
21. All parts are keyed to the photos and schematics for quick reference.

### FIELD SERVICE NOTES

22. Each Folder includes time-saving tips for servicing in the customer's home.
23. Valuable hints are given for quick access to pertinent adjustments.
24. Tips on safety glass removal and cleaning.

### TROUBLE-SHOOTING AIDS

25. Includes advice for localizing commonly recurring troubles.
26. Gives useful description of any new or unusual circuits employed in the receiver.
27. Includes hints and advice for each specific chassis.


### OUTSTANDING GENERAL FEATURES

28. Each and every PHOTOFACT Folder, regardless of receiver manufacturer, is presented in a standard, uniform layout.
29. PHOTOFACT is a *current* service—you don't have to wait a year or longer for the data you need. PHOTOFACT keeps right up with receiver production.
30. PHOTOFACT gives you complete coverage on TV, Radio, Amplifiers, Tuners, Phonos, Changers.
31. PHOTOFACT maintains an inquiry service bureau for the benefit of its customers.

**ONLY \$25 DOWN**

Puts a Photofact Service Data Library in Your Shop. Ask Your Photofact Distributor—He Has the Full Easy-Pay Details.

## FREE PHOTOFACT CUMULATIVE INDEX

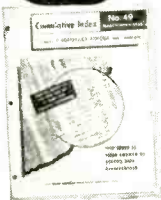

Send for it! Your guide to virtually any model ever to come into your shop; helps you locate the proper PHOTOFACT Folder you need to solve any service problem on any model. Once you have the make and chassis number, it takes just 60 seconds to find the applicable PHOTOFACT Folder. Send coupon now for your FREE copy of the valuable Cumulative Index to all PHOTOFACT Folders.

## HOWARD W. SAMS & CO., INC.

Howard W. Sams & Co., Inc., Dept. 4-E5  
2201 E. 46th St., Indianapolis 5, Ind.


Send FREE Photofact Cumulative Index.

Name.....

Address.....

City.....Zone...State.....

**HELPS YOU EARN MORE DAILY**

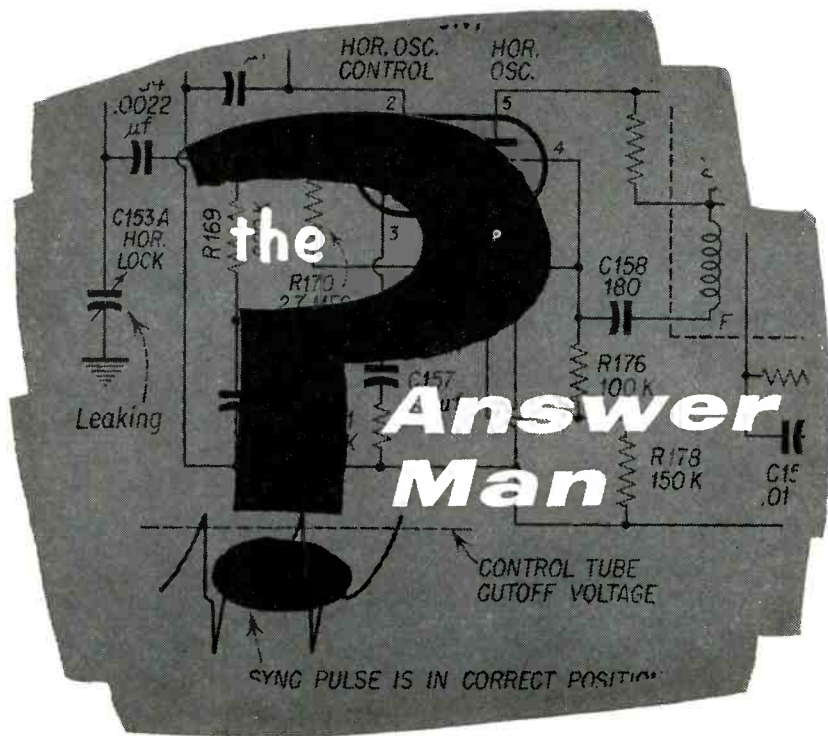

by Bob Dargan

**Do you have a vexing problem on the repair of some radio or TV set? If so, send it in to the Answer Man, care of this magazine. All inquiries acknowledged and answered.**

*Note: Only communications with Radio-TV Service Firm letterheads will be considered and answered. Please indicate make, model, and chassis number of receiver.*

Dear Mr. Answerman:

I have a Cascode Standard Coil Tuner in a TV receiver in which I have had to replace the 6BQ7 rf amplifier tube very frequently. In fact, I have had to put a new one in three times in the past week and I wonder if you can give me some indication as to what is killing these tubes. I use name brand tubes, not seconds or cheap ones.

L. C.  
Montreal, Canada

Most probably, the B plus feed resistor to the rf stage, 1500 ohms, has burned and the resistance is much less than this value. This results frequently when a 6BQ7 tube shorts and the damage to the resistor is generally such that the resistor is reduced to a much lower resistance in many instances. On the other hand, it can also burn open, but in this case it is easily located as faulty as it provides no B plus to the rf stage.

If the resistor has burned and become lower in value, the additional B plus voltage applied to the plates of the 6BQ7 tube will cause it to become weak after a short period of operation. What most TV servicemen do is replace the

weak tube with a new one. However, after another abnormally short period the tube fails again. This can occur in almost any tuner that employs the 6BQ7, 6BZ7 variety of rf amplifier tube. Since both triodes are connected in series, the cathode of the upper triode is connected to the plate of the lower triode (See Fig. 1) and the output

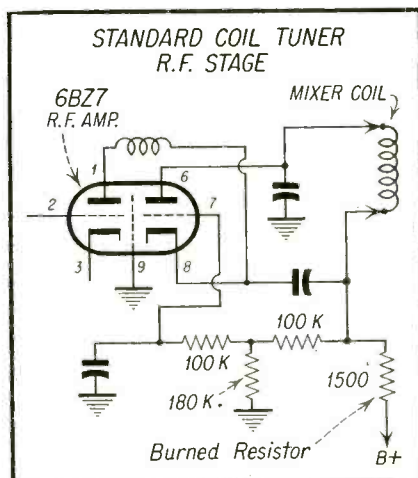


Fig. 1—Short between pin 8 and internal shield overheats 1.5K.

triode will have at least 110 volts potential applied to the cathode. The tube frequently breaks down between this cathode and filament or between this cathode and the shield, pin 9. As pointed out, this difficulty can occur in any cascode tuner, not just the Standard Coil Tuner. When the resistor is replaced it is suggested that a resistor with a dissipation rating of one watt be used instead of the 1/2 watt value generally found. It is certainly advisable in those receivers where repeated failure of the rf amplifier has occurred to examine the resistor or even replace it with a one watt size. Of course, this hinges upon the available space for the resistor.

Dear Sir:

Some years ago, I think I read in your pages of a case in New York City, where the owner of a small radio took it to a shop for test. He called for it later, didn't want the work done, and refused to pay the fee for testing. As I remember, he used every legal procedure available to obtain the set, and I believe it was carried to a high court, which ruled that the technician, or shop, was entitled to collect, but, that he should notify the customer of his intentions to charge for testing.

It made an impression on me to the extent that I had a line printed on my claim checks as follows: A FEE WILL BE CHARGED FOR TESTING AND DIAGNOSIS.

Now, a parallel case has arisen here.

A customer brought in a radio for test. She didn't want to spend more than \$3.50 for repairs. Our test showed a defective filter, and we substituted a new one to make sure. As the job would run over \$3.50, we waited for her to call, before going ahead. When she came in to get it, she decided not to have it done, and wanted to take the set, refusing to pay the \$1.00 testing charge. Her husband, an accountant, came in later and demanded it, threatening to go to the police. As they had established no credit with me, I refused to let them have the radio until the charge was paid.

Today, I am served with a summons to Small Claims Court, to pay \$7.50, plus costs.

What can I do?

This is a small town and we have no servicemen's organization here.

J. M.  
Chico, Calif.

We believe that in all instances where the customer was advised that a fee for labor will be charged for any work done, the laborer, artisan or mechanic is entitled to an artisan's or mechanic's Lien.

We are positive that the Justice of



the Peace or the Judge in the Small Claims Court of Chico, California will sustain your position that you do not have to return the set until you are paid for your labor; to wit; the \$1.00 for testing. This is a general and recognized principle of law and we are so advised by our lawyers. It is our lawyer's opinion that this matter will be dismissed and you will be able to retain possession until your fees are paid.

Dear Mr. Answerman:

Why does the vertical sync pulse of a composite video signal stand up higher than the horizontal sync pulse as seen on my scope when I know that the tops of the vertical pulses are supposed to be even with the tops of the horizontal pulses?

L. S.  
New York City

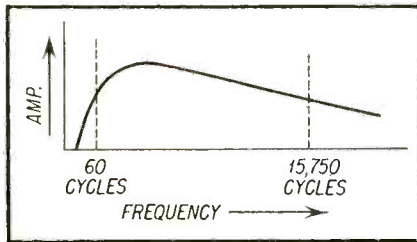


Fig. 2—Frequency response of vertical amplifier on some scopes.

This is because of the frequency response of the vertical amplifiers of your oscilloscope. A typical oscilloscope response is shown in Fig. 2. The vertical amplifiers have a greater output for the 60 cycle vertical pulses than

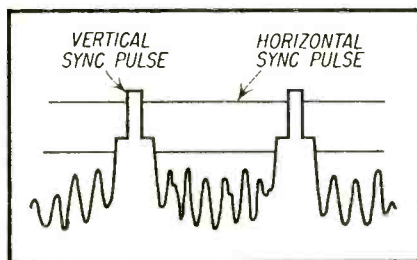


Fig. 3—Presentation of composite video on scope with poor response.

the 15,750 cycle pulses because of this drop off in vertical amplifier gain at the higher frequencies. Therefore, they present the vertical sync pulse as greater in amplitude than the horizontal as shown in Fig. 3.

Dear Answerman:

I have a 19R20 Zenith chassis that exhibits a little hiss or background noise in the audio. I have tried the buzz control but this is no help. Is there any-  
[Continued on page 56]

# PROTECTION...

Safeguarding radio and TV sets has long been a Clarostat responsibility. Clarostat ballast resistors, line-voltage regulators and fuse-type resistors are found in many sets and installations today. Necessarily expendable in providing protection, these items should be included in your parts inventory. Refer to the latest Clarostat catalog for details.

Handy plug-in regulators prevent line-voltage surges from reaching set—for full protection.



Tube-type plug-in ballasts provide voltage-dividing network—and protection.



Plug-in fuse-type Fuzohm® resistors provide protection from overloads.



**CONTROLS and RESISTORS**

CLAROSTAT MFG. CO., INC. DOVER, NEW HAMPSHIRE  
In Canada: Canadian Marconi Co., Ltd., Toronto 17, Ont.

# NEW

# products

## for better sales and service



### ETI Tester

Electronic Test Instrument Corp., 13224 Livernois Avenue, Detroit, Michigan, announces the availability of the VITAMETER. This instrument is designed to maintain, improve and vitalize the operation of a Cathode Ray Tube. Reactivation of the cathode of a picture tube is accomplished by a dynamic sweep between cathode and grid thus removing gas ions and stale emitting material from the surface of the cathode.




### Superex CRT Tester

Superex Electronics Corporation, 4-6 Radford Place, Yonkers, N.Y. has recently announced an addition to its line of a CRT Rejuvenator-Tester for all servicemen who own a tube tester. The unit will test and rejuvenate any picture tube 10" to 30" electrostatic or magnet focus without the necessity of the removal of the tube from the chassis or cabinet. The unit is supplied with settings and full instructions for its use.



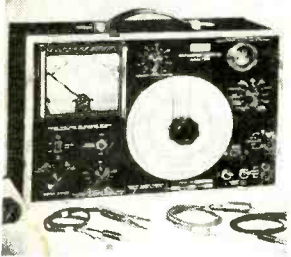
### Kay-Townes Antenna

Many months ago Kay-Townes engineers anticipating this condition started experiments on a completely new design of antenna. It was engineered to select signals from practically a pin point, and thus eliminate any co-channel interference from sides or rear. Tests on all bands have shown up to a 100-1 ratio. Arrays are available to correct most interference problems.


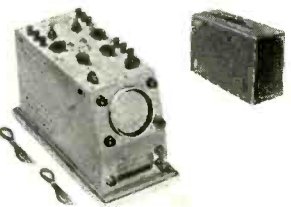
### Pyramid Analyzer

A new capacitor-resistor analyzer, model CRA-1, is now in production at the Pyramid Electric Co., 1445 Hudson Blvd., N. Bergen, N. J. The unit is designed with a built-in quick-check stage that permits the technician to test a suspected capacitor, while in the circuit, without disconnecting the capacitor. Tests may be performed for shorts, opens and intermittants, tests for capacitance, resistance, power factor, leakage current and insulation resistance.



### Hickok Portable 'Scope

Availability of a new lightweight 3" portable oscilloscope is announced by the Hickok Electrical Instrument Company. This 'scope features a new 6-section unitized circuit construction for minimum interaction between amplifiers and sweeps, as well as provides for replaceable circuit sections as individual units. Slightly larger than a normal sized telephone, the Model 385 provides a new high in dependable accuracy.


### Self Service Tube Tester

The American Scientific Development Co., 334-336 S. Main St., Ft. Atkinson, Wis., has developed a self-service tester which saves the serviceman's valuable time and empowers for himself the condition of that the customer be allowed to judge for himself the condition of his tubes, and to set up the tester himself, thus relieving him of any suspicions he may have about the counter salesman.



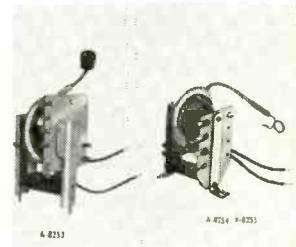
### Stancor Flybacks

Three new Admiral exact replacement flybacks have been added to the Stancor line, Chicago Standard Transformer Corporation, Addison and Elston, Chicago 18., Ill. They are A-8253, A-8254, and A-8255, replacing Admiral parts 79D48-1, 79C60-1, and 79C60-2 respectively. These flybacks are exact electrical and physical duplicates of the units they are designed to replace.



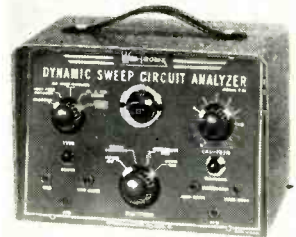
### Win-Tronix Analyzer

A new T.V. test instrument for color or monochrome, designed to troubleshoot horizontal and vertical deflection circuits. Manufactured by Winston Electronics, Inc., 4312 Main Street, Philadelphia 27, Pa., the Model 820 Dynamic Sweep Circuit Analyzer provides 60 cycles vertical sawtooth, 15 KC horizontal sawtooth and deflection transformer drive for both vertical and horizontal sweep circuit troubleshooting by speedy signal substitution.


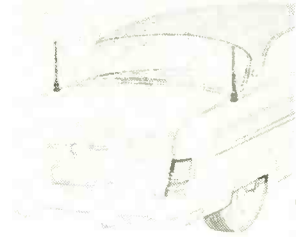
### Snyder Rear-Deck Antennas

A rear-deck dual auto antenna which provides the driver with maximum vision through its rear deck position, is being marketed by Snyder Mfg. Co., of Philadelphia. The two three-section staffs are 13 1/4 inches high when collapsed, and 27 inches high when extended. They are easily mounted on the rear fenders and are adjustable to 180°. They are available in the swivel or the ball and socket type.



### R.C.P. Modified Tube Checker

Radio City Products, Inc. Tube Checker—Modified Model 322 P Portable Tube Tester to provide for testing the new series tubes, announced by Walter Jablon. The unit includes the addition of a special power transformer and switch to insure correct testing conditions for series tube, CR Tubes including color as well as a reactivator for black and white tubes. All other current electronic tubes can be tested on Model 322 P.





# TRADE LITERATURE



## New Books

Audio Amplifier Manual (Howard W. Sams and Co., Inc.) 352 pages, \$3.95.

The fifth of the Audio Amplifier Series, the complete Photofact treatment includes data on 37 audio amplifiers, 12 preamplifiers and 14 AM-FM tuners. The data on each device is complete with copyrighted adjustment and maintenance data, parts lists, Standard Notation Schematics and all other information necessary for the service on the equipment.

Picture Book of TV Troubles, by Rider Laboratories Staff (John F. Rider Publisher, Inc.) 5½ x 8½, 96 pages, \$1.80.

This publication makes the diagnosis of troubles in the vertical and horizontal sweep and deflection circuits of television receivers a very simple matter. Every type of sweep and deflection circuit is shown schematically; then the results of defects in the components of these circuits are illustrated by picture tube patterns, and resultant incorrect waveforms, as well as the correct waveform.

Bigger Profits in TV, by Ray A. Snyder and Donald B. Shaw (Howard W. Sams and Co., Inc.) 132 pages, \$1.50.

The practical guide toward better business records, customer relations and increased profits in TV Servicing will prove helpful to every shop owner. It is written in simple and direct form with many sample problems and examples of accounting procedures, business records, shop tickets and labor costs. The many excellent technicians whose business difficulties come from lack of attention to business methods will be helped immeasurably by this work.

"Basic Electronics" (John F. Rider Publisher, Inc.) The use of over 800 pictures throughout the 560 pages in this series represents a completely revolutionary method of subject presentation. Every page covers one complete idea; on that same page, at least one big "show-how" illustration explains that idea. Anyone with an understanding of DC and AC electricity and electrical circuits can effectively use this course. The five-volume "Basic Electronics" course covers: Diodes, power supplies, amplifiers, oscillators, transmitters and receivers. The set retails for \$9.00 and is available at parts jobbers and bookstores.

Tape Recorder Manual (John F. Rider Publisher, Inc.) 8½" x 11", 312 pages, \$4.50.

In addition to the complete electronic information, this volume contains complete mechanical details in the form of step-by-step adjustment information, exploded views of the assembly, and service guide to both electrical and mechanical troubles. The manual is cross-indexed for easy reference to manufacturer, trade name and model numbers.

"How To Install TV Antennas," by Samuel L. Marshall (John F. Rider Publisher, Inc.) 5½" x 8½", 128 pages, \$2.50.

Devoted wholly to the practical aspects of this activity, it deals with every facet of the installation as related to VHF and UHF antennas. The subject matter covers from the simplest installation of a television antenna to the pouring of a concrete base for a tower; calculating the kind of mast required to accept different amounts of ice and wind loading; the steps necessary in the raising of a tall mast, etc.


Color TV Dictionary, by J. Richard Johnson (John F. Rider Publisher, Inc.)

The basis of the book are the terms which originated in the National TV Systems Committee (NTSC) and which formed the basis

# Gives your customers brilliant results ...pays off for you!

## NEW SONOTONE 1P CERAMIC CARTRIDGE

CUTAWAY VIEW  
(Actual size 1" long)

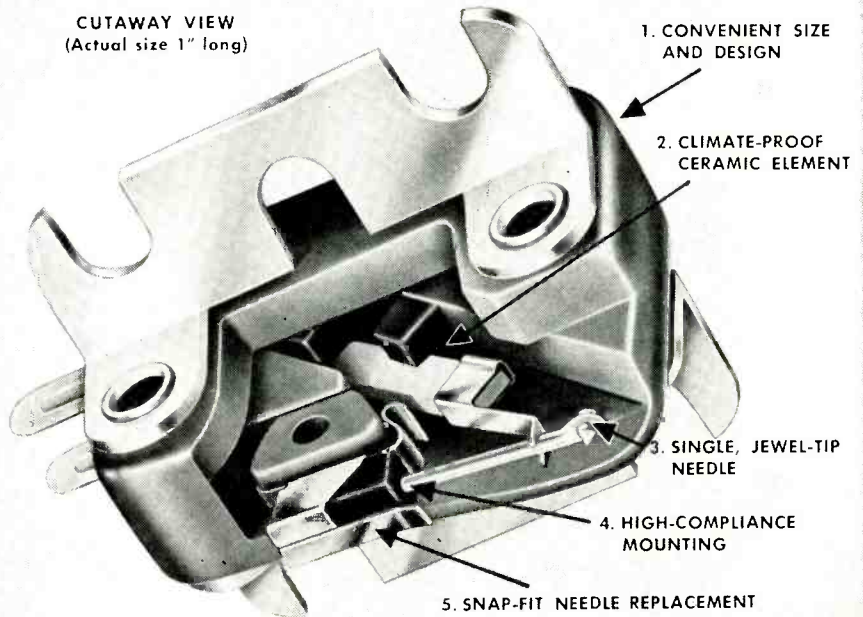


1. Easy to install. Just two models fit most arms now in use. Cartridge is less than 1" long, 8/10" wide with bracket. Time-saving hardware included.
2. Ceramic element gives flat response (see curve) —requires no preamplification or equalization. No deterioration problems as with other types...virtually immune to hum pickup.
3. Replaceable needle, diamond or sapphire. Models for 33-45 rpm, or 78 rpm.
4. Extreme lateral compliance and low-mass design give superior tracking, low wear.
5. Needles snap in, snap out easily.

### Tap the Huge 33-45 RPM Replacement Market!

Install this new Sonotone 1P, and give your customers exciting, true, wide-range response. At one stroke, you make a good sale, cut installation time, avoid problems found with other types of cartridges...and build your reputation for quality work and professional advice. No other cartridge has all the advantages this 1P gives you! With sapphire, \$8.50; with diamond, \$30.

RESPONSE 30-15,000 ± 3 DB!

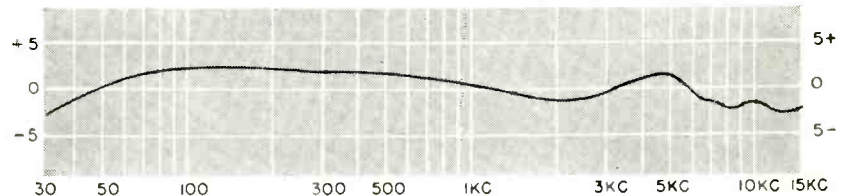


Response to new industrywide RIAA characteristic shows how 1P ceramic cartridge self-equalizes, because it works on "amplitude" rather than "velocity" principle. Here's startlingly improved performance for your customers' phonos!

# SONOTONE CORPORATION

ELMSFORD, N. Y.

Write Dept. CD-55 for free Phono Modernization Manual

# FOR GREATER PROFITS

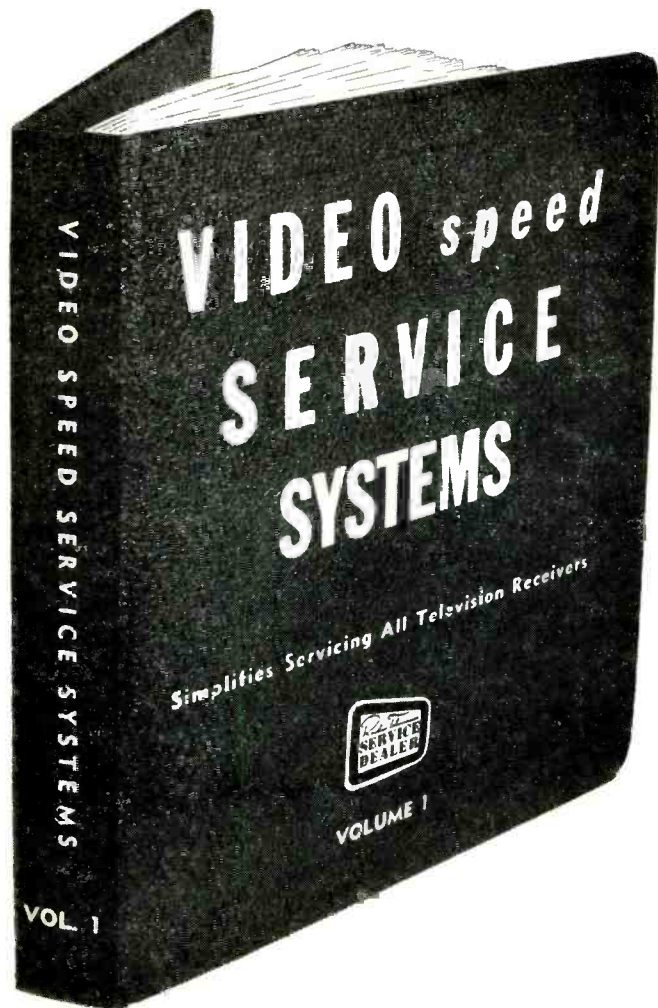

## SPEED UP YOUR SERVICING with THIS NEW BOOK

which shows you how to take care of and repair in the quickest possible time:

- Common troubles characteristic of certain receivers
- "Bugs" which might take you hours to find
- Factory and field service changes

SET UP SO THAT YOU CAN MAKE THESE REPAIRS IN THE SHOP OR IN THE FIELD WITHOUT REFERENCE TO ANY OTHER SOURCE.

Contains over 600 Service Items representing over 1000 of the most-serviced Television models now in use. Over 25 different manufacturers' lines are covered.

**\$4.95** postpaid

(Add 3% Sales Tax in New York City)

**DISTRIBUTORS—ORDER YOUR SUPPLY NOW!**

Service Dealers—get your copy of VSSS from your Distributor. If he can't supply you, order direct by mail from us.

Video Speed Servicing Systems IS GUARANTEED to Simplify Servicing All TV sets. A number of new Data Items are published in every issue of "Radio-Television Service Dealer" as a regular monthly feature.

### TEAR OFF AND MAIL NOW

RADIO-TELEVISION SERVICE DEALER

67 West 44th Street, New York 36, N. Y.

Please send me post-paid VIDEO SPEED SERVICING SYSTEMS Volume 1. Enclosed herewith is


my  check  money order for \$\_\_\_\_\_ for \_\_\_\_\_ copies at \$4.95 each. (Add 3% Sales Tax in New York City)

Name .....

Address .....

City ..... Zone ..... State .....



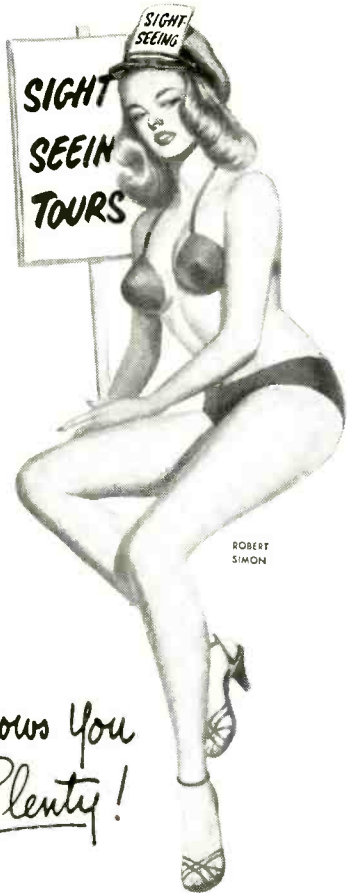

Shows You  
Plenty!

Best of all, Walco shows you how to make money — *real money* — with your replacement needle business! Walco starts you off *right* — with a needle inventory that's light in the right places, and heavy just where it *ought* to be — and then follows through with the most realistic price and discount policy in the industry. To top it off, Walco backs you up with the strongest needle merchandising program anywhere. You haven't seen anything, till you see the deal you'll get from Walco. Call your Walco distributor today — *he'll show you plenty!*

Write for a full size print of Hazel, the Walco cutie above, plus vital needle profit information.

NEEDLES FOR EVERY  
PHONOGRAPH BY

# Walco

Trade Name of Electrovox Company, Inc.  
60-SD Franklin Street East Orange, N. J.

of present color TV. The dictionary defines more than 263 names and terms and contains 45 illustrations. 70 pages. Price: \$1.25.

"Obtaining and Interpreting Test Scope Traces," by John F. Rider (John F. Rider Publisher, Inc.) 5½" x 8½", \$2.40.

A 192-page book containing more than 1000 waveforms; almost every illustration (exclusive of test set-up schematics) is an actual photograph, taken of waveforms right off the test scope screen. It is a treatment which explains the make-up of waveforms of all kinds in practical easy-to-understand language, and shows numerous examples of each type of distortion. Most important of all, it explains the reasons for the distortion seen in the waveform.

Rider Television Manual, Vol. 14. (John F. Rider Publisher, Inc.)

In order to present properly the true output of the receiver manufacturers, Rider Manuals include all the schematics, chassis views, circuit descriptions, voltage data, alignment information, and other data which apply to all the production runs of each receiver, including color receivers. Volume 14 contains the equivalent of more than 2,300 (8½" x 11") pages, loose-leaf bound with Fabrikoid covers, and sells for \$24.00.

Sonics, by Theodor F. Hueter and Richard H. Bolt (John Wiley and Sons, Inc.) 6 x 9¼, 456 pages, \$10.00.

A sound, useful, easy-to-read presentation of the principles and practices of the rapidly expanding field of *sonics*. Techniques and devices ranging from a few cycles per second to hundreds of megacycles per second are covered. Material is drawn from the fields of physics, engineering, and electronics. The reader is given a clear and authoritative account of: fundamental physics of vibration and sound, design principles of electroacoustic and fluid-dynamic transducers, choice of sonic variables for systems engineering, and special techniques for testing and processing. All information is given in a framework of basic physics, so that common features of seemingly unrelated techniques are made apparent.

National Electrical Code Handbook, by Arthur L. Abbott, revised by Charles L. Smith (McGraw-Hill Publishing Co.) \$7.50.

The handbook explains the NEC rules in brief, easy-to-understand language. It gives the general plan, scope, and intent of the Code requirements, and discusses them in simple fashion to aid electrical contractors, electricians and others in making and planning electrical installations that are in conformity with the National Electrical Code.

Radio-Television Service Pricing Guide (Oerlich Publications) \$2.95.

The "Guide" shows price and description of all the flat rate services such as: service calls, pick-up and delivery, pix tube replacements, alignment estimates, etc., and is supplied with extra flat rate sheets that do not show price so that the dealer can type in his own prices and substitute pages if desired. It also contains the standard rate system showing average time periods for each specific defect so that the entire service job may be priced. The "Guide" also contains ten pages for pricing merchandise such as radio, TV and appliances, and is bound in a loose leaf binder for easy page removal or addition.

Transistor Audio Amplifiers, by Richard F. Shea (John Wiley and Sons, Inc.) 6 x 9¼, 219 pages, \$6.50.

A short, lucid volume which should enable the audio engineer to design practically audio amplifier for which transistors can be used componentially. The inclusion of all specifications and specific design data enables you to take a commercial transistor specification, and knowing the requirements of your overall design, develop the necessary circuit of your amplifier.

TV Service Timesavers, by Milton S. Kiver (Howard W. Sams and Co., Inc.) 124 pages, 5½" x 8½", \$1.50.

Prepared in 5 sections entitled *general servicing timesavers*, *sectional servicing timesavers*, *test instruments and alignment*, *timesaver tips on servicing tools*, and *odds and ends for quicker servicing*, this handy reference summarizes

Get this  
Cabinet FREE

Sprague Ceramikit



WITH A BASIC ORDER OF  
CERAMIC CAPACITORS

● NOW . . . stock ceramics so you can find 'em when you want 'em . . . have your own neat and complete cabinet . . . at the cost of the capacitors alone.

● Sprague has pre-stocked these handsome, blue, heavy-gauge steel CERAMIKIT cabinets with its famous Ceramite capacitors. Ratings and quantities are based on popularity. No dogs! Stand-up indexes separate reusable plastic boxes. Catalog numbers and ratings can be seen at a glance.

● Whether you use many ceramics, or just a few, there's a Ceramikit sized and priced just right for you. Kit CK-2 is a two-drawer model holding 150 capacitors in 27 different ratings. Kit CK-3 is a single-drawer unit holding 75 capacitors in 12 different ratings. Remember there's not a dog in either Ceramikit.

● Kits interlock so you can build with Sprague as you buy your Ceramikits. Use the extra cabinets for handy indexed stocking of all your small parts.

● See your distributor *now* about Ceramikits, or get complete information in Sheet M-711 from the Sprague Products Company, Marshall Street, North Adams, Massachusetts.



CK-2  
150 Assorted  
Capacitors  
\$38.00 LIST

CK-3  
75 Assorted  
Capacitors  
\$19.25 LIST

don't be vague . . . insist on

# SPRAGUE

Sprague Products Co. is the Distributors'  
Division of the Sprague Electric Co.

many service techniques found profitable from actual experience. A total of 97 photographs and drawings are used to illustrate the 51 "Timesaver Tips," a few of which are: "Causes and Cures for the Narrow Picture"; "Tuner Sensitivity—How to Increase It"; "Vertical Retrace Blanking"; "Checking Horizontal Output Transformers"; "Touch-up Alignment"; "Remedy to a Corona Problem."

Basic Electricity (Howard W. Sams and Co., Inc.) 264 Pages, 8½" x 11", \$5.00.

This book presents the Student and Instructor with a practical approach to beginning studies in the intriguing and complex field of Electricity. The text material is laid out in 35 logical and easily understood lessons. Each lesson is profusely illustrated and explained. Many questions and problems are presented to aid the student in grasping the fundamental laws and relationships which will guide him throughout his further studies.

## CIRC. ANALYSIS

[from page 36]

Fig. 1. The series nature of this circuit can be seen clearly from this diagram. The encircled resistors are not actually resistors, but they represent the effective resistance values of the tubes involved. Thus, R-V204 is the effective resistance between the plate and cathode of V204, the audio output tube. Looked at in this way, the entire arrangement is nothing more or less than an elaborate voltage divider across the power supply output.

Starting with 265 volts at the power supply, we go through R502 which

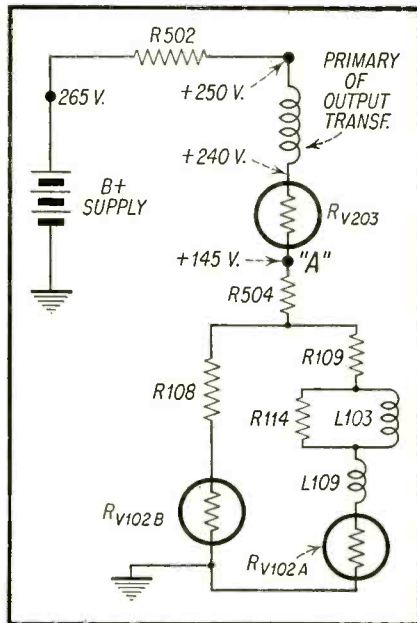


Fig. 3—Simplified equivalent circuit corresponding to Fig. 1. Note RV203 shown as equivalent resistance.

produces a 15 volt drop, then through the primary of the output transformer which produces a 10 volt drop resulting in a voltage between the plate of V204 and ground of 240 volts. The tube resistance itself (R-V204) then

causes a 95 volt drop, resulting in 145 volts appearing at its cathode. It is from this point, "A" of Fig. 3, that the various circuits shown in Fig. 2, receive B+.


It is apparent, that if V204, the sound output tube fails, the effect is the same as if the resistor R-V204 opened, thus depriving all the circuits shown in Fig. 2 of B+ voltage. Since the rf mixer and oscillator receive plate voltage from this point, they would become inoperative in the event of such a failure. An open primary in the output transformer, or an open R502 would have the same effect. This then results in the misleading symptoms of raster but no sound or picture, as previously mentioned.

In the particular model discussed here, an additional clue would be that the raster would be dimmer than normal, since the screen grid of the horizontal output tube would also lose its voltage. (See Fig. 2). The Admiral 19K1 chassis, which uses a somewhat similar arrangement, does not tie the horizontal output tube into the same line so that the brightness of the raster is not affected.
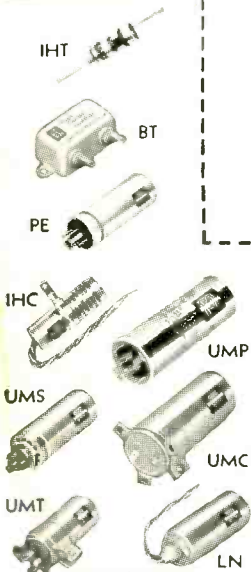
### Voltage Regulating Action

In Fig. 4 it will be seen that the control grid of the audio output tube is

**NEW!**  
Miniature and Sub-miniature Electrolytic Capacitors  
SMT & IMT



FAMOUS FOR "Time Tested Quality"

EXPORT  
15 Moore Street  
New York 4, N. Y.  
Cable "Minthorne"

# ILLINOIS the Capacitor Line of Time Tested Quality

## NOW PRESENTS

### "HANDEE-PAK" Capacitor Kits


- ELECTROLYTIC CAPACITOR KITS
  - CERAMIC CASED PAPER CAPACITOR KITS
- IN POPULAR CAPACITY AND VOLTAGE RANGES

Here are the new "ILLINI HANDEE-PAK" Assortment Kits now on display at your jobber. Attractively and conveniently packaged on cards and sealed in transparent polyethylene bags, each of the kits contains the most popular capacity and voltage ranges in use by the service industry.

Each of the ELECTROLYTIC "HANDEE-PAK" kits consists of five popular assorted capacitors. The paper capacitor kits are made up of ten assorted of the new type ITC oil impregnated ceramic cased capacitors, de-

### "STE-TITE" TYPE ITC CERAMIC CASED PAPER CAPACITORS

- |                              |                              |
|------------------------------|------------------------------|
| Capacity Ranges              | • Excellent Power Factor     |
| From .0005 to 1.0 mfd.       | • Accurate Capacity          |
| 200-400-600 & 1600 WVDC      | • High Insulation Resistance |
| • Hermetically Sealed        | • Overload Tested            |
| • High Temperature Operation | • Oil Impregnated            |

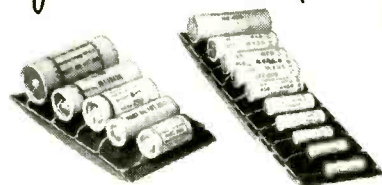


Kits Are Packaged In Polyethylene Bags

scribed below.

These capacitors lead the field in advanced design, superior quality and workmanship and are the ultimate in packaging and convenience. "HANDEE-PAKS" simplify storage, banish shelf-life problems.

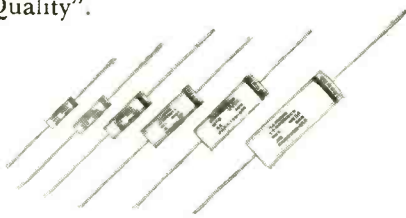A few "HANDEE-PAKS" in your service kit take up little room, serve you by being factory fresh and easily identified. Use them with confidence — millions of capacitors produced to date are your assurance of "Time Tested Quality".



If your jobber cannot supply you, write for catalog and information on the new "HANDEE-PAK" kits.



**ILLINOIS CONDENSER COMPANY**  
1616 N. THROOP STREET CHICAGO 22, ILLINOIS



kept at a fixed bias of 130 volts through the voltage divider action of R214 and R215 which are connected from the ground to the 250 volt point on the supply line. The grid is connected to the junction of these two resistors through R216. If the current through the tube should change because of tube variations, age fluctuations, etc., the voltage at the cathode of audio output tube would also change. This is true because a change in current through the tube means that the value of "R" in Fig. 4, which represents the effective resistance of all the circuits tied to the cathode changes resulting in redistribution of voltage between the audio output tube and the remainder of the circuit.

Suppose the change is such that the cathode voltage increases. Since the grid is held fixed at +130v, the bias would become more negative. This in turn

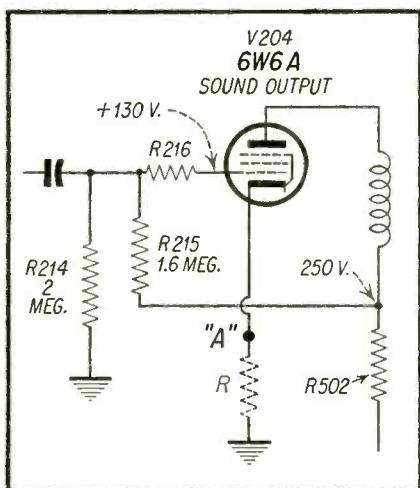


Fig. 4—Partial schematic illustrating voltage regulator action of the audio output tube.

would reduce the current through the tube (by increasing its effective resistance). The reduced current then tends to drop the cathode voltage back to its normal value. In this manner then, V204 acts as a series regulator, tending to maintain the voltage at its cathode at a constant level of 145 volts.

## TRADE FLASHES

[from page 10]

ed by scientists of the Radio Corporation of America. The new radio, employing nine transistors in place of electron tubes, is equal in performance to standard car radios, the RCA scientists said. Emphasizing its low power consumption, they pointed out that more than half the small amount of current required by the radio is used to light the two small pilot lights that illuminate its dial.

[Continued on next page]

# -THE All New Gun

## DESIGNED FROM SCRATCH FOR SERVICE MAN'S REQUIREMENTS

#199

**WEN**

Ideal for 90% of your work

**"Quick-Hot" Electronic Soldering Gun**

WORKING  
IN 2-3  
SECONDS

GET THE FEEL OF IT

**HEFT IT—TRY IT**

*You'll know at once*

that here is a "right" product—built to work well for years.

- Lightest
- Smallest
- Longest reach
- Longest life
- Most dependable

### OF ALL TRANSFORMER TYPE SOLDERING GUNS

You have the satisfaction of knowing when out on the job with this gun that it won't burn out. There'll be no "down" time—no return to the shop for repairs.



### LIGHT, HANDY *New Model #199*

New patented design delivers AMPLE heat fast on 110-120 V. A.C. 60 cycle, 1.1 Amp. Max. Cools quickly too. It's light, (1½ lbs.)—handy, beautifully balanced and smaller—to slip readily into tool kit or pocket. Molded red plastic handle and case. Gun made to withstand

### HUNDREDS OF HOURS CONTINUOUS OPERATION

Almost indestructible in ordinary use. New type, steel, extra long reach tips readily replaceable and interchangeable with special purpose tips. Gun fully guaranteed. And that PRICE

**Only \$7.95** LIST

FOR HEAVY DUTY you want

the famous **WEN** MODEL #250

Retails \$12.95.

WEN PRODUCTS EXHIBITED BOOTH #7 ELECTRONIC PARTS SHOW  
CONRAD HILTON HOTEL, CHICAGO—MAY 16th - 19th

**WEN**

**PRODUCTS, INC. CHICAGO 31, ILL.**

(Export sales, Scheel International, Inc., Chicago)

**NEW!**



**a Volt-Ohmmeter  
you can carry in  
your shirt pocket!**



**Simpson  
MIDGETESTER**  
MODEL 355

**SELF  
SHIELDED!**

The world's first practical shirt-pocket volt-ohmmeter. Rugged and accurate. Not affected by any outside magnetic influences. 10,000 Ohms per volt AC and DC! Fourteen ranges: 5 for AC voltages, 5 for DC voltages, and 4 for DC resistances.

**See your Parts Distributor**

**Simpson  
ELECTRIC COMPANY**  
WORLD'S LARGEST MANUFACTURER  
OF ELECTRONIC TEST EQUIPMENT

5204 W. Kinzie St., Chicago 44, Ill.  
ESTebrook 9-1121

IN CANADA: Bach-Simpson, Ltd., London, Ontario

**\$29<sup>95</sup>**  
including  
probe leads



A new idea in phonograph cartridge packaging has been introduced by Electro-Voice, Inc., Buchanan, Mich. Each E-V replacement phono-cartridge is now sealed-in-plastic in a unique "Blister-Pak." Full identification interchangeability chart and instructions are printed on the package.

Mr. Charles Weyl, president of international Resistance Company, Mr. William I. Elliott, president of Hycor Companies, and Mr. Kenneth T. Eckardt, president of the Hycor Sales Company, announce the acquisition of the Hycor Companies of California and Puerto Rico, by the International Resistance Company. Management of the Hycor Companies will continue operations independently.



Astron Corp. of N.J. is offering a metal "Swing Bin" which contains 90 capacitors of 18 different values, with a maximum of 5 of each type. It has clear plastic construction for easy visual stock control; attaches on the wall or under bench, and each of 6 bins swing out 180° for easy access.

Production of radio and television receivers in February increased from the output rate of both January and the same month a year ago, the Radio-Electronics-Television Manufacturers Association reported. During February, 702,514 television receivers were produced. This compares with 654,582 sets manufactured in January and 426,933 units turned out in February 1954. The radio production in February totaled 1,089,724 units, compared with 1,068,-

Still Time for You to Win


**A FREE TRIP**

to Bermuda or Trinidad

in Jersey Specialty's

**TIME-OF-YOUR-LIFE**

**Contest!**

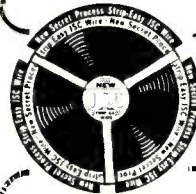

Visit Jersey Specialty Co. at Booth No. 101 at the Electronic Parts Show.

• THOUSANDS OF ENTRIES pouring in from all parts of the country!

• DISTRIBUTORS REPORT tremendous interest shown by dealers!

• DISTRIBUTORS' ORDERS for No. 2080 hundred foot TV wire coils flooding JSC plant now running full blast to meet orders from all over the country.

Trip to Tobago (Robinson Crusoe Island) Trinidad via Airplane "New Viscount" of British West Indian Airways (B.W.I.A.)

Trip to Bermuda via "Queen of Bermuda" Ocean Liner—Furness Bermuda Line

**DEALERS!**

**DEALERS!**

Rush Your Letter to JSC Today! Coupon mailed to you on receipt of your letter for free wire. Important, coupons redeemed at your wholesale distributor. Write today (your distributor has full details).

**Jersey Specialty Co., Inc.**

Burgess Place  
Mountain View, N. J.





146 receivers produced in January. During February 1954, radio set production had totaled 769,232.

A new brand featuring the well-known letters "CBS" for its radio and television tubes and semiconductor products has just been unveiled by CBS-Hytron, a Division of Columbia Broadcasting System, Inc. Charles F. Stromeyer, President of CBS-Hytron, said: "We have changed our brand name from CBS-Hytron to CBS because we wish to take full sales advantage of the nationally recognized and respected letters CBS . . ."



Guests at the cocktail party given by the Pyramid Electric Co. of N.J. during the I.R.E. show listen to Service Dealer publisher Sandy Cowan (second from left) recount one of his many anecdotes. Left to right: Art Cerf, Pyramid representative; Mr. Cowan; Mrs. Jack Poff, wife of Pyramid's sales manager; Bob Elliot, jobber sales manager of Erie Resistor Corp.; and Richard Kaiser.

Free portable batteries and advertising aids are the rewards for dealers and servicemen participating in Philco's nationwide "Rocket to Profit" promotion, one of the most flexible programs in parts and accessories history, according to General Manager James J. Shallow, Philco Accessory Division. Based on the theme that 87 per cent of all portable battery sales are produced by six "best seller" models, the promotion enables Philco Dealers and Servicemen to earn free quantities of "best sellers" with their regular purchase of these six most popular style batteries.

## ASSOCIATIONS

[from page 26]

Radio Servicemen's Associations passed the following resolution.

**RESOLUTION:** Resolved that Glenn McDaniels, President of R.E.T.M.A. and Wm. H. Parkinson, Chairman of R.E.T.M.A. Committee on technical education furnish satisfactory proof to the Federation that licensing of technicians would increase cost of service to the consumer, as stated before various legislative bodies.

## Television Service Association of Connecticut, Inc.

Held their 1st Annual Meeting on Feb. 20th. Chapters represented were from Hartford, New Britain, Waterbury, Meriden, and Manchester. Guests from Middletown, New Haven, Portland, and Haddam were also present. In my humble opinion the "Minutes and Proceedings" of this first meeting is one of the finest compilations of "Association" material ever to be collated in 10 pages. I would suggest other associations to write for copies of this brochure as a shining guide to what could be done by a wide awake group.

## Radio & Television Servicemen's Assn. of Pittsburgh, Penna.

B. A. Bregenzer, Editor of the R&TSA Video Scope, official organ of the above association, says, in part, on the subject of manufacturers setting up their own service companies:

"In our humble opinion, the task of supplementing the independent service profession with captive service will not be a profitable one for the general public, as no large operators ever can compete with the smaller independent on even terms and make a profit. So we think that the independent TV service profession must sell their customers on

Better sound from OXFORD SPEAKERS . . . complete line from 2" to 15" . . . for all replacement needs . . . ORDER TODAY!

**OXFORD**

**OXFORD ELECTRIC CORPORATION**  
3911 South Michigan Avenue • Chicago 15, Illinois

EXPORT — ROBURN AGENCIES, NEW YORK CITY — IN CANADA — ATLAS RADIO CORP. LTD. TORONTO

**NEW!**  
 READY FOR USE  
 IN SECONDS

**SNYDER**

*"Mike"*  
**Stand**

**FLOOR MODEL  
 MS-2**

**Sure-Grip Lock  
 WITH  
 VELVET ACTION**

**PORTABLE  
 COLLAPSIBLE  
 SPACE SAVING**

**HEAVY CAST IRON  
 GREY CRACKLE FINISH**

**SNYDER**  
 SNYDER MFG. CO., PHILADELPHIA 40, U.S.A.  
 BELLEVUE TUBE MILL, INC., PHILADELPHIA  
 SNYDER ANTENNA-ENGINEERS LTD., TORONTO 14, CANADA  
 WORLD EXPORT. ROBURN AGENCIES, INC., N.Y.

personalized ethical service at prices comensurate with an honest profit. Thus by lending that personal touch, coupled with the know how to give the best possible service, we think we can weather the storm."

**Western N.Y. Electronics Guild**

In a release by the above Guild licensing is opposed on the grounds that: 1. The present laws are sufficient to prevent malpractices and fraud; 2. It would be better to set up a local investigating committee to study charges of malfeasance practices, etc.; 3. It would impose an undue burden on part-time technicians and one-man shops and stifle competition.

**ANSWER MAN**

[from page 47]

thing that may be tried before I remove the chassis and perform a complete alignment. I have made normal checks such as tube substitutions, etc.

H.S.  
 Albany, N. Y.

The hiss that you are experiencing is undoubtedly due to a slight misadjust-

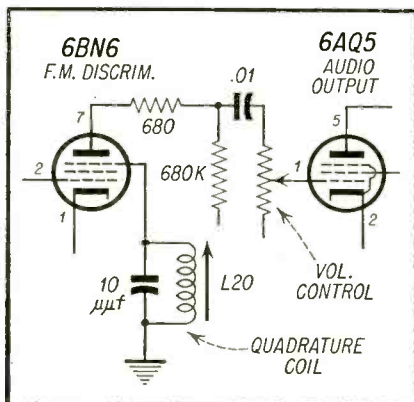


Fig. 4—Partial schematic of 6BN6 Gated Beam Detector.

ment of the quadrature coil in the 6BN6 Gated Beam Detector circuit shown in Fig. 4. This coil may easily be touched up by tuning it for the clearest sound with minimum hiss or buzz without employing alignment equipment.

**SQUARE WAVE GENERATOR**

[from page 16]

indicate poor high frequency response of the amplifier. Poor high frequency response makes itself evident as poor detail in the picture.

Figure 12 is a characteristic waveform which is associated with ringing


**6  
 CONNECTOR  
 TYPE SERIES  
 for  
 LOW LEVEL  
 SOUND**

*Cannon Corp.*

**UA**



**XL**

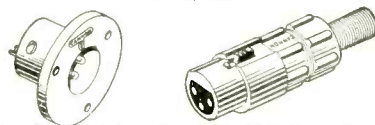


**P**



**O**



**X**

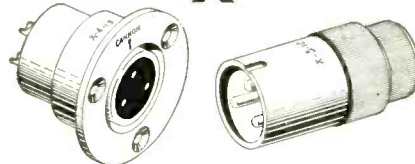

**XK**



Since 1915

CANNON ELECTRIC COMPANY,  
 3209 Humboldt St., Los Angeles,  
 Calif. • Factories in Los Angeles,  
 East Haven, Toronto, Canada;  
 London, England. Representatives  
 and distributors in all  
 principal cities.

Please Refer to Dept. 127

**CANNON ELECTRIC**



in high frequency peaking coils. This may be caused, for example, by open damping resistors across peaking coils such as  $R1$  and  $R2$  in Fig. 1. The effect on the picture is to produce a series of closely spaced, alternate black and white "shadows", directly to the right of objects which have sharp changes of shading.

When the cause of trouble has been localized to the video amplifier by any of the above or similar checks, conventional methods may then be used to pinpoint the source of trouble.

### Square Wave Checking of High Fidelity Audio Amplifiers

All that has been said in the preceding portion of this article (except where direct reference is made to TV circuits) applies equally well to the checking of high fidelity audio amplifiers by means of the square wave technique. With increased skill and experience in the use of the generator, the technician can discover in short order whether the frequency response, phase distortion, and transient response are within acceptable limits.

### Adjusting Horizontal and Vertical Linearity With the Square Wave Generator

While the square wave generator is not primarily designed for this purpose, it can be used to solve what is sometimes an annoying problem. In the home, or in the shop it is often necessary to adjust both horizontal and vertical linearity controls. In most cases, the station pattern is not on the air, and the adjustment is not too easily made. By setting the square wave generator to a frequency of 250 kc and feeding the signal into the grid of the video amplifier, 16 vertical pairs of black and white lines will be produced on the screen. The horizontal linearity and the width controls are then adjusted to space these lines equally, or as close as possible to equality.

In a similar way, if the generator is set for a multiple of 60 cps, horizontal pairs of black and white lines will be produced. At 1200 cps, for example, 20 pairs of horizontal lines would be produced. The vertical linearity and vertical size controls are then adjusted for equal spacing of these lines.

To facilitate this type of adjustment in the home, an adapter plug may be inserted into the socket of the video amplifier tube, and connections made to the readily available terminals on this adapter. The video amplifier tube, of course, is placed in the adapter socket during this operation.

### Sine Wave Applications

Most square wave generators have the facilities to provide sine waves over

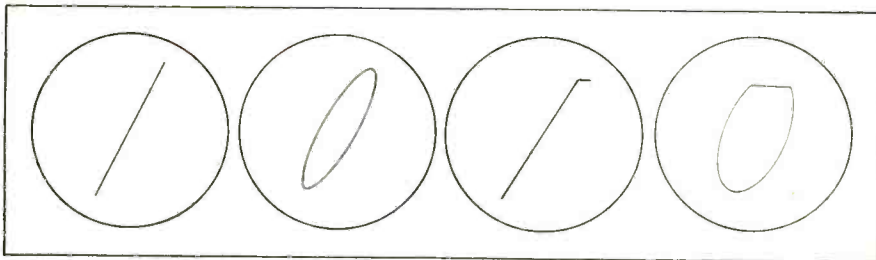


Fig. 13 — Various scope traces observed under different conditions of phase shift.

the same frequency range as that provided for square waves. This of course adds to the versatility of the instrument

and greatly extends its usefulness. By using this feature, we have in effect another instrument, namely, an audio

**TAKE THE ROAD TO  
EXTRA PROFITS...**

**REPAIR  
AUTO RADIOS**  
*quickly, easily with*  
**STANCOR**  
**EXACT REPLACEMENT  
AUTO VIBRATOR  
TRANSFORMERS**

*free!*

You can increase your auto radio repair profits by reducing installation time with STANCOR exact replacement vibrator transformers. Like STANCOR flybacks, STANCOR auto vibrator transformers are faithful duplicates of the originals they are designed to replace.

P-6481, PHILCO  
Exact Replacement

P-6480, MOTOROLA  
Exact Replacement

P-6482, DELCO  
Exact Replacement

P-6473, ZENITH  
Exact Replacement

**CHICAGO STANDARD TRANSFORMER CORPORATION**  
3586 ELSTON AVENUE • CHICAGO 18, ILLINOIS  
Export Sales: Roburn Agencies, Inc., 431 Greenwich St., New York 13, N.Y.

**ON THE JOB IT'S #99**

# RECOTON

## SERVICEMAN'S PHONEEDLE KIT

*for Profit-plus Business!*

**YOUR COST FOR NEEDLES ONLY \$9.90**  
SERVICEMAN'S NET  
Everything else included free

**LIST PRICE \$20.50**

**Included Free!**

- High powered jeweler's eye loupe
- Forceps, screw driver, wrenches, mirror
- Assorted nuts for RCA and Shure cartridges
- Condensed, simplified reference guide
- Plus a set of Redi-Stik labels to fill in with catalog number of replaced needle, and your name, address and phone number.

Here at last is a simple, easy to carry, convenient kit that taps your vast potential market of needle buyers where they can be sold most convincingly . . . in their own homes! It's here, while you are on a service call, that the consumer can be educated to buy the needles his phonograph sorely needs.

The **RECOTON #99 KIT** is so compact, it fits into your regular tool box. The transparent case measures only 7" x 3 1/4" x 1 3/4", yet holds approximately 25 needles. This profit-making kit contains 12 of the most popular ones (Nos. 303, 311, 315, 316, 318, 319, 336, 338, 355, 356, 385, 2712R), an efficient assortment that will fill about 95% of your "on the job" needs!

**RECOTON CORPORATION**  
52-35 BARNETT AVENUE • LONG ISLAND CITY 4, N.Y.

SEE US AT PARTS SHOW—RECOTON BOOTH 414

signal generator having a range well beyond the highest audio frequencies. As such it finds its greatest usefulness for such procedures as:

1. Determining accurate point by point frequency response curves for audio amplifiers.
2. Determining the extent of phase shift at any particular frequency. Fig. 14 shows some scope tracers observed under different conditions of phase shift.
3. Determining the undistorted power output of an audio amplifier.
4. Observing and tracing the cause of distortion.

## PEAK-TO-PEAK VTVM

[from page 44]

which since it tends to make the cathode of V1b more positive, causes a decrease in the plate current and hence in the cathode voltage of V1b. This push-pull action permits a large value of cathode resistance with negligible degeneration and, consequently, greatly increased stability of operation. The meter circuit is connected across the two cathodes and the difference in potential across the meter causes current to flow through the meter from the cathode of V1a to the cathode of V1b.

**AC Voltage Measurements:** The applied voltage is first rectified by the twin-diode V2, which serves as a full-wave peak-to-peak rectifier. The operation of this circuit is as follows: On the positive swing of the ac signal, diode V2a conducts and a negative dc voltage equal to the positive peak value builds up on the plate-connected side of C2. As the ac signal voltage swings negative, diode V2a ceases to conduct (and so prevents any discharge of C2) while diode V2b begins to conduct. The negative dc voltage on C2 is added in series to the signal voltage on the negative swing and is applied to the cathode of V2b. As a result, a negative dc voltage equal to the sum of the positive and negative peaks of the ac signal voltage is built up on the plate-connected side of C3 through conduction of diode V2b and is maintained because of the relatively long time constants of the circuit. To offset the contact potential within V1, an exactly adjusted positive voltage is taken from the junction of R26 and R27 and applied to the V1 rectifier circuit through isolating resistor R28. The peak-to-peak voltage across C3 is attenuated by R29 before application to the range voltage divider and thereafter the operation is similar to dc voltage measurement.

**IT PAYS FOR ITSELF FAST!**

# the VITAMETER

AN INSTRUMENT DESIGNED TO MAINTAIN, IMPROVE and VITALIZE OPERATION OF CATHODE RAY TUBES

Unique reactivator function is accomplished by dynamic sweep between cathode and grid . . . removing gas ions and stale emitting material from surface of cathode tube.

**IT'S PORTABLE**  
**WEIGHT ONLY 10 LBS.**

**only \$6995**

**the VITAMETER**

- analyzes performance characteristics
- locate and remove inter-element shorts
- repairs open elements
- welds open filaments
- restores or improves emission quality
- estimates tube life expectancy

**Write for bulletin.**

**ELECTRONIC TEST INSTRUMENT CORP.** 13224 LIVERNOIS AVENUE  
DETROIT 38, MICHIGAN



**Ohmmeter Operation:** The applied resistance determines the current through the battery and the section of the ohms range network (R5-R11) selected by the range switch. With nothing connected across the input terminals, no current is drawn, and consequently there is no voltage drop across the ohms network. As a result, the entire battery voltage is applied to the grid of V1-a. Potentiometer R30 in the meter circuit is adjusted to produce full-scale deflection (infinity reading) in this condition. A short across the input terminals produces a voltage drop in the ohms range network equal and opposite to the battery voltage and effectively places the grid of V1a at ground potential for a zero reading. Intermediate values of resistance produce voltage drops exceeded by the battery voltage and the difference in voltage is applied to the grid of V1a. This voltage causes an intermediate deflection on the meter which has an ohms scale calibrated to read the applied resistance.

## WORKBENCH

[from page 35]

probe (or stick) was then pressed against each component in the oscillator circuit. This is what is known as a vibration check. If the microphonic whistle is diminished by the pressure of the probe on the component then we have found the vibrating component. Resoldering of the component, replacement, or just the addition of solder on the component's pigtails can cure the trouble.

After pressing many components on the oscillator circuit with no results,

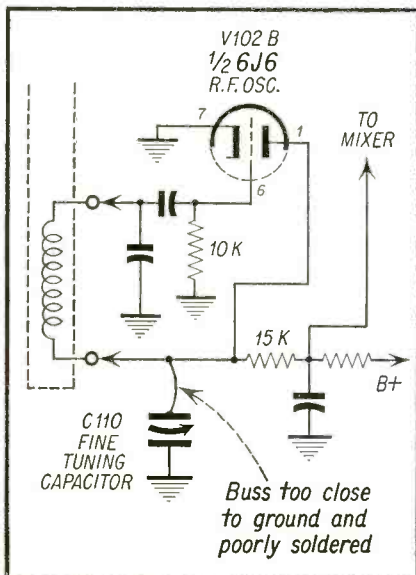


Fig. 2—Partial schematic of rf stage showing point of trouble.

they were next lightly tapped. Tapping produces momentary vibration and frequency modulation which results in a "pinging sound" from the speaker. The component producing the strongest "pinging sound" is the trouble maker. The loudest "pinging sound" was heard when the fine tuning condenser, C110 was tapped. Moreover, by pressing the plastic probe against the lead (or buss) connected to C110, the microphonic whistle completely disappeared. It was noted upon examination that this lead was very close to ground. The lead was then moved away from ground and then resoldered at both ends. This of course detuned the oscillator. Therefore, each station, as this

was a standard cascade tuner, was retuned by adjusting the oscillator slug. The volume control was then turned up to maximum and no microphonic whistle could now be heard on any station.

It may be interesting to describe how this microphonic whistle occurs. First the sound waves from the speaker set up mechanical vibrations in one or more of the wires, components or tube elements in the rf oscillator circuit. This mechanical vibration produces slight variations in inductance and capacity of the oscillator circuit which causes corresponding frequency modulation of the rf oscillator signal. This produces corresponding frequency modulation of the

## LIFE'S "LITTLE" PROBLEMS

ARE EASILY  
SOLVED  
WITH

### LITTLE SPACE

QUAM has a full line of shallow speakers, covering all popular applications.

### LITTLE TIME

QUAM speakers mount quickly and easily in the most difficult installations because of QUAM's unusual mounting bracket.

### LITTLE MONEY

QUAM speakers cost no more—and frequently cost less—than other speakers of the same size and magnet weight.

# QUAM

*Adjust-a-Cone*

# SPEAKERS

*ask for QUAM, the quality line for all your speaker needs*

Quam speakers are listed in Photofact Folders, Counterfactors, File-O-Matic, and Radio's Master.

A FREE copy of the latest QUAM catalog, listing over 100 replacement speakers, is available from your distributor, or from the Quam-Nichols Company.


## QUAM-NICHOLS COMPANY

238 East Marquette Road Chicago 37, Illinois

Use the complete line...
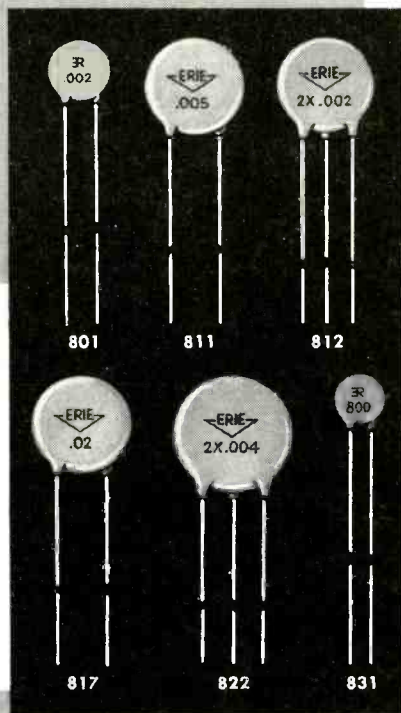
# ERIE DISC CERAMICONS®

Erie Disc Ceramicons are available at Distributors in four classes as standard stock:—High Stability General Purpose Ceramicons in a wide range of values, (5mmf to 1800 mmf) with 10% capacity tolerance,—Hi-K By-Pass and Coupling Ceramicons from 470 mmf to .02 mfd GMV,—Hi-K Dual Ceramicons,—High Voltage Ceramicons rated at 1500, 3000, and 6000 Volts, DC. Working. Characteristic of all classes is smallness of size graduating with increase in capacity value. For complete listing of styles and values available write for D-54 Catalog which includes all Erie Distributor products, or ask your nearest Erie Distributor.



ERIE ELECTRONICS DISTRIBUTOR DIVISION

ERIE RESISTOR CORPORATION  
Main Offices: ERIE, PA.


Factories: ERIE, PA. • LONDON, ENGLAND • TRENTON, ONTARIO

LABORATORY DESIGNED for  
UHF and VHF1 ... It's NEW!

## MOSLEY 2-WAY TV ANTENNA SWITCH

- Extremely low Standing Wave Ratio — by actual test!
- Positive rotary action!
- Silver-to-silver contactst
- Compact size!
- Solderless — easy to install!
- Low cost!

Cat. No. F-40  
List Price  
\$1.95

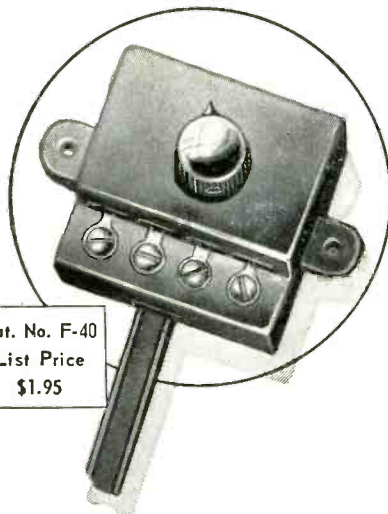

**Mosley**  
Electronics, Inc.  
8622 ST. CHARLES ROCK ROAD  
ST. LOUIS 14, MISSOURI

Another PREMIUM QUALITY MOSLEY Accessory  
for BETTER TV INSTALLATIONS!

### MOVING?

Be sure to advise the Circulation Department of RADIO-TELEVISION SERVICE DEALER, 67 West 44 St., New York 36, N. Y., of your NEW and OLD address so that we can keep your copies coming regularly. Or better yet, tear off the mailing label and send it to us with your new address.



sound if signal which is detected in the sound discriminator, and which produces audio frequency in its output. This is amplified in the audio amplifier and produces speaker cone motion. The speaker cone motion produces sound waves which tend to increase the vibrations in one or more of the wires, components or tube elements in the rf oscillator. The action is then repeated with reinforcement on each cycle. The net result is an audible whistle.

### ANTENNAS

[from page 30]

The reason that the transmission line is taken off the common harness termination point rather than the main dipole is due to transmit time considerations. If the harnesses from the two small dipoles were transposed and terminated at the main dipole the phase of the small dipole components would be changed in proportion to the length of the harness. Three equal lengths are used for this reason. It is interesting to note, however, that the transmission line could be taken off the main dipole if all harnesses were run straight. The individual harnesses happen to be ¼ wavelength long, so a phase change of 90 degrees would occur from the small dipoles to the present take off point and an additional 90 degrees from this point to the large dipole or the desired 180 degrees. The placement of the dipoles or phasing elements can be physically changed but the basic electrical operating principle is exactly the same.

This same principle was employed in the popular JFD Superjet and earlier antenna types.

### COLOR

[from page 33]

From these values we can easily prove that G and B are both zero. Thus:

$$G = Y - (G-Y) = .3 - .3 = 0$$

$$B = Y - (B-Y) = .3 - .3 = 0$$

which is what we set out to prove.

Figure 8 illustrates a partial schematic of the system around the 2-triode demodulator under discussion. The economy of potentiometers required for this type of demodulator is evident when we realize that this type of demodulator requires some five to seven tube envelopes less than previous designs. This economy of parts has the remarkable additional feature that the phasing and relative amplitude of the color signals produced is free from areas of drift and instability; it also has a minimum of adjustable elements (tuned coils and potentiometers), and is practically independent of variations of demodulator tube characteristics.



**P. A.**

[from page 24]

systems which in addition to the necessary speakers, amplifiers, microphones, automatic time switch and automatic tape playing mechanisms, incorporate additional tape recording and tape playing mechanisms. In this way the store manager can record on a standard seven inch reel of tape, the store specials, advertisements and store promotions for the week, leaving a minimum of 10 seconds of space between commercials. The main music reel is then recorded with intervals of 10 second breaks. With a sound operated relay the music reel shuts off and a standard tape playing mechanism plays one commercial. When the commercial is terminated the relay reverts and the music reel is brought into play. The frequency of commercials can be controlled by merely putting the necessary spaces in the recorded music. The 7 inch reel with the one minute commercial on it is also recorded at three and three-quarter inches per second. As can be seen, it is very simple to record enough commercials for at least two days.

When the tape has been fully played it is merely rewound, put back in operation and needs no further attention for two more days. The most important part of this system is that the same unit can be used, with the use of the store microphone, to record the commercials. This enables the store manager to change the commercials as often as he sees fit.

**600 MA TUBES**

[from page 8]

ma tube is that of providing a controlled warm-up time of about 10 seconds. This reduces to nil any possible unbalance or improper voltage distribution across the filament line during the starting period. It means that in 10 seconds the filament for all the tubes are at their constant operating value. Every 600 ma type tube will warm up in exactly the same time as every other one.

Of course, this does not mean that the receiver will be in operation in 10 seconds inasmuch as it takes a somewhat longer time to transfer the heat from the filament to the cathode material for adequate electron emission. In certain cases, such as damper tubes, it can take as long as 35 to 75 seconds before the receiver comes up to normal operation and high voltage is provided to develop the raster.

As is indicated in Table 1, the new 600 ma tubes have prototypes that correspond physically and electrically with each other except for filament voltages,


# How you can make \$50 or more a day in extra profits...with Bogen Complete Public Address Systems



Cash in on PA rentals to clubs, sports events, dances, church bazaars


Almost every day some activity in your area rents a public address system at a cost of twenty-five to fifty dollars or more. Are you letting this business get away from you? Maybe it's because you think installing PA systems presents too many problems...

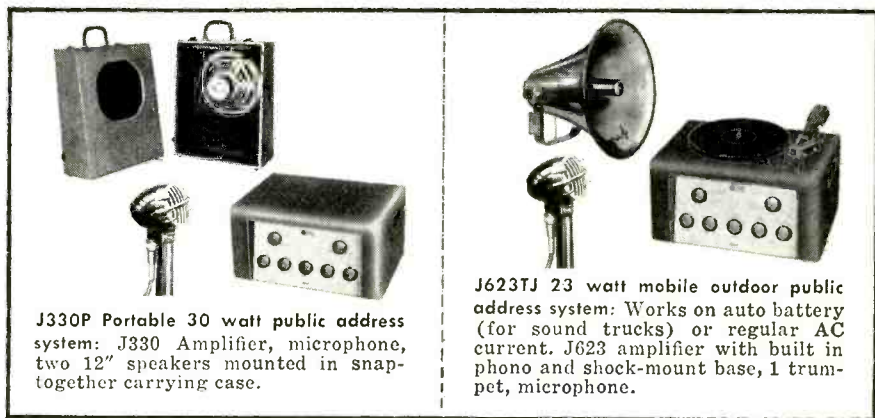You don't have to be a 'sound engineer' with Bogen PA. Bogen complete PA systems are the ultimate in easy installation. All you do is connect the microphone, amplifier and speakers and the system is ready to go. Keep both an indoor and outdoor Bogen Complete Public Address System on hand...and start rolling up those extra profits.



J330P Portable 30 watt public address system: J330 Amplifier, microphone, two 12" speakers mounted in snap-together carrying case.

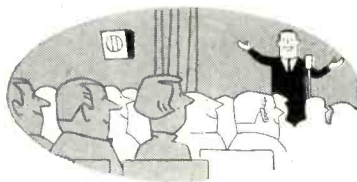J623TJ 23 watt mobile outdoor public address system: Works on auto battery (for sound trucks) or regular AC current. J623 amplifier with built in phono and shock-mount base, 1 trumpet, microphone.



Cash in on permanent PA installations, too—we'll do all the work!

Bogen engineers are ready to help you draw up plans and specifications for any type job—at a moment's notice... and the Bogen PA catalog can tell you at a glance which system goes where for most installations. Also, don't overlook the profit possibilities in servicing existing PA and intercom installations in your community.

**Start getting those extra profits now!**



Send for the Bogen complete public address system catalog. Mail this coupon today!

David Bogen Co., Inc., Dept. MP  
29 Ninth Ave., New York 14, N. Y.

Send me the Bogen Complete Public Address System catalog right away.

name \_\_\_\_\_  
company \_\_\_\_\_  
address \_\_\_\_\_  
city \_\_\_\_\_ zone \_\_\_\_\_ state \_\_\_\_\_

**Bogen**

"BECAUSE IT SOUNDS BETTER"

current ratings, and warm-up time characteristics.

With the 600 ma series string tube the negative temperature coefficient resistor will not be necessary to absorb voltage surges since the resistance in the whole series line will increase at a constant rate for all tubes. Therefore, an inexpensive resistor can be employed to furnish any additional voltage drop necessary to provide the proper voltage distribution across the whole series circuit. In fact, tube manufacturers suggest that these series filament resistors have a positive temperature coefficient.

### Typical Receivers

Two chassis employing the 600 ma filament circuit are shown in Fig. 2 and 3. These new receivers are a far cry from the series filament types produced by the TV industry in the past. The Admiral chassis 17XP3 is shown in Fig. 2 and in this diagram it can be noted that each filament terminal connects to the next and that all the tubes are in series with a voltage dropping resistor of 47 ohms, 20 watts. This circuit will do every bit as good a job as the power transformer type.

Figure 3 shows the Zenith series filament system. Here, the feature of providing accessible filament test points shown as J, K and L in Fig. 3. This permits rapid servicing of the series

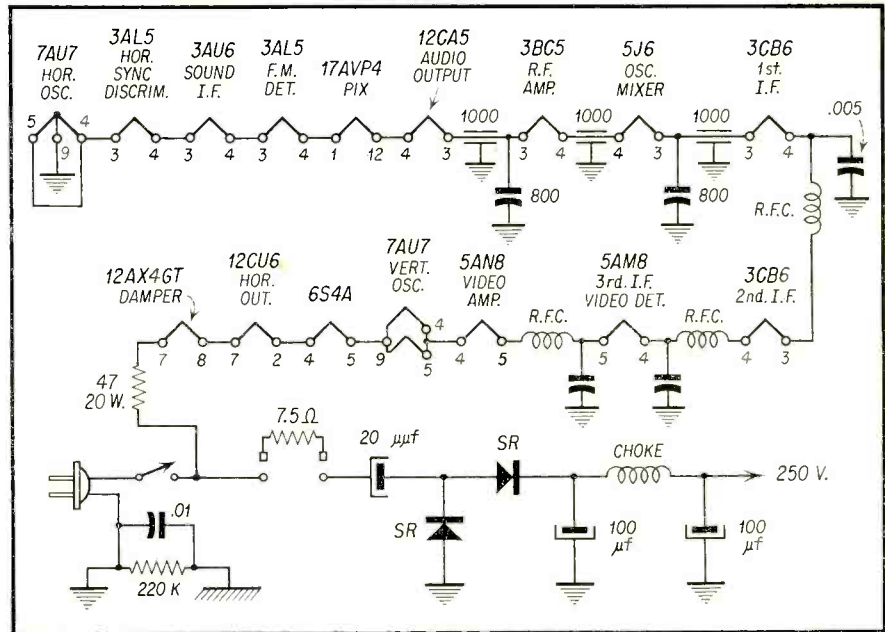



Fig. 2—Admiral chassis 17XP3 B plus and filament circuit.

string circuit without getting under the chassis. The most tubes that will be found in any portion of the line is five. Five tubes are the greatest number that need be removed from the chassis for test purposes of ascertaining which tube filament is open.

A point of interest to the serviceman concerning the Zenith chassis is that

all tubes except the 6SN7GTA horizontal oscillator tube may be substituted for while the receiver is hot and in operation. This is brought about only because the replacement of the horizontal oscillator tube with one that is cold that will not immediately provide the horizontal output with a signal from this cold tube. This lack of drive at the
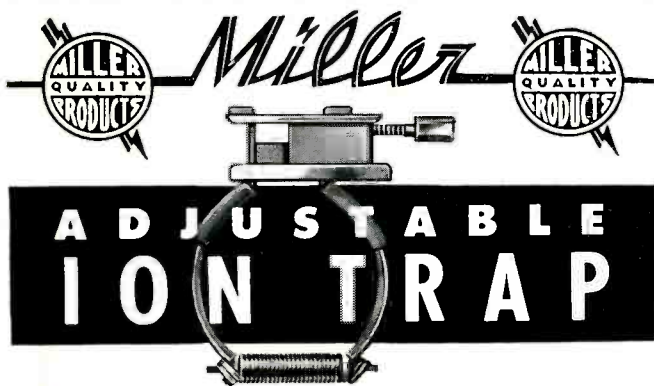
## BETTER PICTURES FROM OLD PICTURE TUBES



The Miller #6295 Adjustable Ion Trap is made to replace any single ion trap with gausses from 32 to 55. Most old picture tubes would give better pictures if the old ion traps were replaced and adjusted to proper gauss.

This Miller #6295 Adjustable Ion Trap, like all 850 Miller television and radio replacement parts, is unconditionally guaranteed. These adjustable ion traps may be bought singly or in an attractive counter display carton of 24 units.

Catalog No.	Description	Net Price
6295	Adjustable Ion Trap	.75

SOLD BY ALL LEADING RADIO AND TELEVISION PARTS DISTRIBUTORS  
Write for General Catalog 56

**J. W. MILLER COMPANY**  
5917 South Main Street • Los Angeles 3, California


Canadian Representative Atlas Radio Corp. Ltd. 50 Wingold Ave. Toronto 10, Ont. Canada

## NEW EASE IN HANDLING TV CHASSIS

TELE-SCOPIC PRODUCTS INC.

**Tele-Toter**  
N. Y.

### CHASSIS HOLDERS

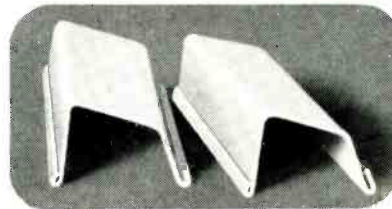

NO MORE  
CUT FINGERS



NO MORE  
ACHING BACKS



**\$1.00**  
PER PAIR  
SERVICEMAN'S NET

#### • SAFER—EASIER—FIRMER CHASSIS HANDLING

6-inch smooth, round finger rail permits instant grip adjustment for proper balance in lifting and carrying.

#### • IDEAL FOR SERVICE SHOP AND FACTORY

When storing chassis, leave TELE-TOTERS attached. Chassis is then ready for quick handling without digging fingers under sharp edges.


Send Checks or Money Orders Only  
No C.O.D. Orders Accepted.

**TELE-SCOPIC PRODUCTS, INC.**

215 W. 33rd St.

New York 1, N. Y.



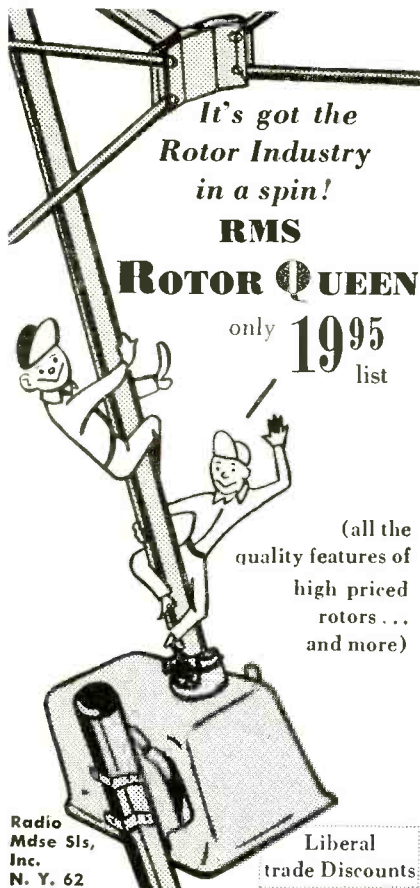

It's got the  
Rotor Industry  
in a spin!

**RMS**  
**ROTOR QUEEN**

only **1995**  
list

(all the  
quality features of  
high priced  
rotors...  
and more)

Radio  
Mds Sls,  
Inc.  
N. Y. 62

Liberal  
trade Discounts

SEE US AT THE CHICAGO SHOW  
BOOTH 128

**TUBES**  
70% to 90% DISCOUNT

Government, manufacturers, jobbers, etc. surplus.  
Guaranteed 1 year. Free catalog on request.

**CADILLAC TRADING**

Dept. AB, 231-07 Linden Blvd., Jamaica 11, N.Y.

**Capcon Printed-Circuit  
High-Pass Filter**  
18 PACKAGE DISPLAY



Stops TV or FM interference below 45 mc.  
—Signals above 54 mc. pass through filter without loss. Eliminates ghosts, herring bones, jitters, sound bars, snow, etc. Easy to install. The Capcon High Pass Filter is GUARANTEED to stop your picture interference problems.

A bargain package to stimulate impulse counter sales.  
List Price **\$18.00**  
Your Price **10.80**  
Your Profit **\$ 7.20**  
on 18 packs

Send check or money order (No C.O.D.'s please.)  
10 day money-back guarantee. Shipped postpaid.  
Complete line of more than 75 filters and wavetraps.  
Send for free literature.

**CAPCON INC.** Dept. D-5 25 Willett Street  
N. Y. 2, N.Y.

**JOIN**  
**+**  
**RED CROSS**

grid of the horizontal output tube and therefore lack of grid bias during a period that may be as long as 20 seconds will permit too much plate current to flow through the horizontal output tube. The excessive plate current will generally open the high voltage fuse. To prevent this, remove the high voltage fuse and permit the 6SN7GTA tube to warm up for about 30 seconds. The fuse can then be inserted without danger of it popping due to this cause. At the time of replacement of the high voltage fuse

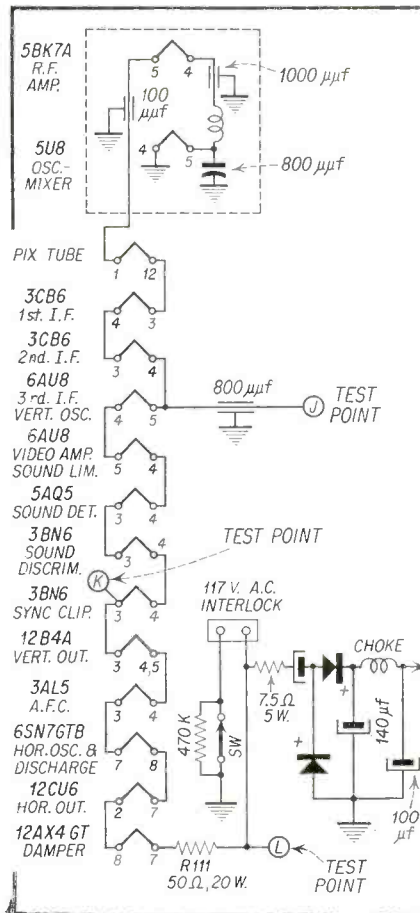



Fig. 3—Partial schematic of Zenith chassis 16T20 showing B plus and filament circuit. Notice use of test points for purposes of easy servicing on the part of the service technician.

it is recommended that the receiver be momentarily switched off.

**Replacement Tubes**

A point concerning the purchase of tubes must be made in closing. Care must be exercised for the present in buying tubes as replacements for the new receivers. As an example, there are three possible tubes that can be obtained in ordering the 6SN7 variety. Only the 6SN7GTB has the close tolerance, controlled warm-up filament. The same applies to the 12B4 type. Only the 12B4A should be used in the series filament as the other does not heat up properly for a series filament line.

**COMING  
IN MAY...**

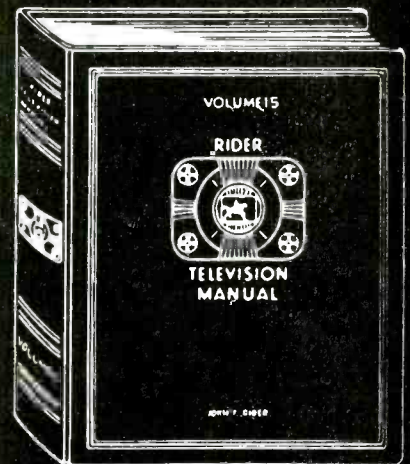

**RIDER'S  
TV 15!**


**LIMITED PRINTING-**

tell your jobber to  
reserve your copy now!

only \$24.

ask the  
**"Man-on-the-Roof"**  
 why he prefers

*South River*

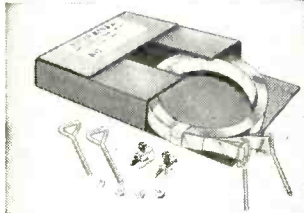

**NOW! Banding Kits NEW!  
 for EXTRA LARGE CHIMNEYS**

KIT XL "ST": (Consists of)  
 2—18' x 3/4" STAINLESS STEEL  
 STRAPS with eyebolts attached  
 2—Eyebolts Unattached  
 4—Nuts to Fit Eyebolts  
 2—KWIK KLIP Strapping Fasteners  
 Also available, KIT XL "G", same as  
 above with 18' GALVANIZED  
 STRAPS.  
 Universal—may be used with any  
 chimney antenna mount.

**SOUTH RIVER**  
 METAL PRODUCTS CO., INC.  
 South River, New Jersey

pioneer &  
 outstanding  
 producer of  
 finest line  
 of antenna  
 mounts

In Can.: A. T. R. Armstrong Ltd., Toronto



**EVERYTHING'S NEW  
 IN THE NEW iE CATALOG**

From the new Line-Lok UHF Stand-off to the New Telescoping Mast—iE offers a complete, expanded line of the industry's finest TV antenna hardware and accessories. *Quality Controlled* to best meet your needs. See your supplier or write iE for your free copy of iE's brand-new, 32-page buyer's catalog.

Exhibiting at the  
**ELECTRONIC PARTS SHOW**  
 BOOTH 24



325 NORTH HOYNE AVENUE, CHICAGO 12, ILLINOIS

## Advertising Index

Aerovox Corporation .....	20
American Microphone Co.....	10
American Phenolic Corp.....	16
Bogen, David Co., Inc.....	51
Bussmann Manufacturing Co.....	13
Cadillac Trading .....	63
Cannon Electric Co.....	56
Capcon, Inc. ....	63
CBS-Hytron .....	6
Centralab .....	14
Chicago Standard Transformer Corp...	57
Clarostat Mfg. Co., Inc.....	47
Clear Beam Antenna Corp.....	1
Cornell-Dubilier Elec. Corp.....	5
Delco Radio, Div. of General Motors Corp.....	27
Electronic Test Instrument Corp.....	58
Electro-Voice, Inc.....	21
Erie Resistor Corp.....	60
Hycon Manufacturing Co. ....	9
iE Manufacturing .....	64
Illinois Condenser Co.....	52
International Resistance Co.....	Cover 2
Jensen Industries .....	64
Jensen Manufacturing Co.....	43
Jersey Specialty Co.....	54
Miller, J. W. Co.....	62
Mosley Electronics .....	60
Mueller Electric Company .....	64
Oxford Electric Corp.....	55
Philco Corporation .....	25
Pyramid Electric Co.....	15
Quam-Nichols Co. ....	59
Radiart Corporation .....	5
Radio Merchandise Sales .....	63
Raytheon Manufacturing Co.....	2
Raytronic Laboratories, Inc.....	28
RCA Tube Dept.....	Cover 4
Recoton Corporation.....	58
Rider, John F. Publisher .....	63
Sams, Howard W. & Co.....	45
Shure Brothers, Inc.....	26
Simpson Electric Co.....	54
Snyder Manufacturing Co.....	17, 56
Sonotone Corporation .....	49
South River Metal Products Co.....	64
Sprague Products Company.....	61
Technical Appliance Corp.....	12
Tele-Scopic Products .....	62
Telrex, Inc. ....	Cover 3
Triad Transformer Corp.....	10
University Loudspeakers .....	22
Walco .....	61
Wen Products, Inc.....	53
Weston Laboratories, Inc.....	18, 19




*"Bless these smugglers!  
 JENSEN NEEDLES."*

**NOT VERY BIG!**

in fact... the one  
 truly miniaturized clip  
 in this age of miniaturization! The new

**MUELLER**

**MINI-GATOR**

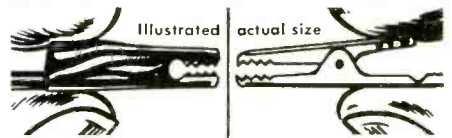

Separate skin-tight vinyl  
 plastisol insulator covers  
 right down to the nose.  
 Will not tear. Slotted "lip  
 action" tip permits full  
 jaw opening without  
 "baring" teeth.

Steel (cadmium plated)  
 or solid copper. 1-1/16"  
 long. Jaws open 3/16".  
 Solder connection. Clinch-  
 ing ears for cord strain  
 relief. For No. 20 or  
 smaller wire.

Simply stated in Electronic terms, it's



(Mini-gator : Alligator :: Transistor : Tube)

**SIMPLIFIES TESTING OF ALL MINIATURIZED AND  
 SUB-MINIATURIZED EQUIPMENT.**

Provides the quick convenience of a test clip  
 in spots that are otherwise inaccessible.

**FREES THE HAND THAT HELD THE PROD!**

**WRITE TO FACTORY FOR FREE SAMPLES!**

*Mueller Electric Co*  
 1568Y E. 31st STREET  
 CLEVELAND 14, OHIO



#### ALIGNMENT PROCEDURE

Apply A.G.C. bias of approximately -2 V to A.G.C. line (across C-202). Maintain the output level of the sweep generator such that the second detector output is 2 volts peak to peak. Scope Cal. 1-V per inch.

**NOTE—USE A NON-METALLIC ALIGNING TOOL AND LIGHT PRESSURE ON ALL SLUGS.**

Signal Generator Connection

Oscilloscope or VTVM Connection

Adjustments

- Output of 40mc. Sweep Generator to grid of 3rd I.F. Tube, pin 1 of 6CB6 V-12 thru 100 MMF isolating capacitor.

- Adjust top and bottom of T-11 for marker positions as shown on curve Figure 1.

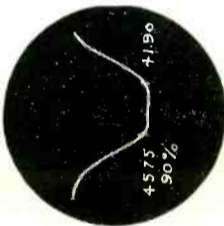


FIG. 1

- Output of 40mc. Sweep Generator to grid of 2nd I.F. Tube, pin 1 of 6CB6 V-11 thru 100 MMF isolating capacitor.

- Adjust top and bottom of T-10 for marker positions as shown on curve Figure 2.

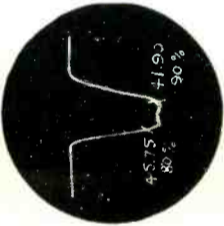


FIG. 2

- Output of 40mc. Sweep Generator to grid of 1st I.F. Tube, pin 1 of 6CB6 V-10 thru 100 MMF isolating capacitor.

- Adjust top of T-9 for marker position of 47.25mc.
- Adjust bottom of T-9 for marker positions at 41.25mc.
- Adjust bottom of T-6 for marker position at 39.75mc.
- Adjust bottom of T-7 and T-8 to produce curve as shown on Figure 3.

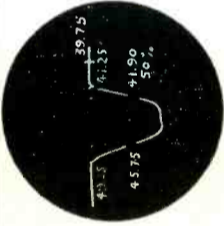


FIG. 3

- Raise converter tube shield from ground and connect output of 40mc. sweep generator to the shield.

Same as Step #1.

- Adjust top of T-6 and L-4 on tuner (L-14 on standard coil tuner) assembly to produce a curve as shown on Figure 4.

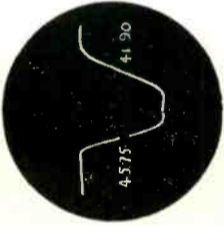


FIG. 4

- Connect a 400 cycle modulated 4.5mc. signal to the junction of video detector M-13 and C-130. Adjust generator output to a level to indicate 1.5 Volts on VTVM.

- Adjust L-21, T-15 and bottom slug of T-16 for maximum indication.

- Same as Step #5.

Connect — VTVM ground lead to the junction of the 2-100K resistors (see 5 above). Connect VTVM D.C. lead to the junction of C-183 and R-182.

- Adjust the secondary (top slug) of T-16 for zero volts between the positive and negative excursions. (Increase Generator output for good deflection).

#### Alternate Trap Alignment

**IF THIS METHOD IS USED, IT SHOULD BE PERFORMED BEFORE THE I.F. CURVE ALIGNMENT**

- | Signal Generator Connection                                                                             | Oscilloscope or VTVM Connection | Adjustments                                            |
|---------------------------------------------------------------------------------------------------------|---------------------------------|--------------------------------------------------------|
| 1. Connect a modulated (400 cycle) 39.75mc. signal to grid, pin 1 of the 1st video I.F. Tube—V-10.      | Same as Step #1.                | 1. Adjust bottom of T-6 for minimum response on scope. |
| 2. Connect a modulated (400 cycle) 41.25mc. signal to the grid, pin 1 of 1st video I.F. Tube 6CB6—V-10. | Same as Step #1.                | 1. Adjust bottom of T-9 for minimum response on scope. |
| 3. Connect a modulated (400 cycle) 47.25mc. signal to grid, pin 1 of 1st video I.F. Tube 6CB6—V-10.     | Same as Step #1.                | 1. Adjust top of T-9 for minimum response on scope.    |

#### PARTS LIST

##### COILS

Circuit Symbol	S-C Part No.	Description
L-1	171271	Matching Coil
L-2	171272	44Mc Input from UHF Tuner
L-3	171273	Neutralizing Coil
L-4	171274	VHF Tuner I.F. Output Adjust
L-5	171275	Filament Choke
L-6		
L-7		
L-8		
L-9		
L-10	171800	Antenna Input
L-11	171801	UHF Tuning
L-12	171802	UHF Tuning
L-13	171803	Filament Choke
L-14	171804	Filament Choke
L-15	171805	Crystal Pickup Loop
L-16	171806	Crystal Diode Load
L-17	171807	44Mc I.F. Adjust
L-18	171808	Oscillator Coupling Loop
L-19		
L-20	114747	40Mc Rejection
L-21	114400	1st Audio I.F.
L-22	114748	Peaking Coil
L-23		
L-24	114749	Peaking Coil
L-25	114750	Peaking Coil
L-26	114751	Peaking Coil
L-27	114415	4.5Mc Trap
L-28	114132	Horizontal Oscillator
L-29	114125	Horizontal Linearity
L-30	114129	Horizontal Size
L-31	161030	Filter Choke
L-32	114746	Deflection Yoke
L-33	114693	2.2 uh Choke
L-34		
L-35		

Circuit Symbol	S-C Part No.	Description
L-502 thru L-508	171253 thru 171259	VHF Oscillator Coils
L-509	171296	VHF Low Channel Osc. Adjust
L-510 thru L-513	171260 thru 171263	VHF Osc. Coil

##### TRANSFORMERS

Circuit Symbol	S-C Part No.	Description
T-1	171276	VHF Antenna Input
T-2		
T-3		
T-4		
T-5		
T-6	171246	Converter Secondary and 39.75Mc Trap Coil
T-7	171247	1st Video I.F. Output
T-8	171248	2nd Video I.F. Input
T-9	171249	41.25 and 47.25Mc Trap
T-10	171250	3rd Video I.F.
T-11	171251	4th Video I.F.
T-12		
T-13		
T-14		
T-15	114401	2nd Audio I.F.
T-16	114375	Ratio Detector
T-17	See M-8	Audio Output
T-18	161254	Vertical Blocking
T-19	161266	Vertical Output
T-20	161045	Horizontal Output
T-21	114127	Sawtooth Transformer
T-22	161444	Power Transformer
T-23		

##### MISCELLANEOUS

Circuit Symbol	S-C Part No.	Description
M-1	128200	Circuit Network
M-2	128003	Fuse, 1/4 Amp.
M-3	158037	Slide Switch
M-4	128007	Fuse, 5 Amp.
M-5		
M-6	34421	Phono Jack
M-7	128203	I.F. Strip
M-8	155734	Speaker Assembly
M-9		
M-10		
M-11	164023	VHF Tuning Unit
M-12	164024	UHF Tuning Unit
M-13	162157	1N64 Crystal Diode
M-14	171252	K-3 (Kemtron) Crystal Diode

##### RESISTORS

Circuit Symbol	S-C Part No.	Resistance	Watt	Tol.
R-1	28172	15K ohms	1/2 W	10%
R-2	28154	470 ohms	1/2 W	10%
R-3	171297	1 Megohm	1/2 W	5%
R-4	149315	750K ohms	1/2 W	5%
R-5	28165	3.9K ohms	1/2 W	10%
R-6	28158	1K ohms	1/2 W	10%

# RADIO-TELEVISION SERVICE DEALER COMPLETE TV SERVICE INFORMATION SHEETS


## STROMBERG-CARLSON


### 625 SERIES

An exclusive service of Cowan Publishing Corp. by special arrangement with John F. Rider, Publisher

Circuit Symbol	Part No.	Resistance	Watt	Tol.	R-194	149075	680 ohms	2 W	20%	Circuit Symbol	Part No.	Capacity	Type	Voltage	C-150	110724	.1 MF	Tubular	400
R-7	28183	220K ohms	1/2 W	10%	R-200	149384	22K ohms	1/2 W	10%	C-1	171298	800 MMF	Disc Ceramic	450	C-151	110459	.68 MMF	Ceramic	500
R-8	28158	1K ohms	1/2 W	10%	R-201	28189	680K ohms	1/2 W	10%	C-2	171299	22 MMF	Ceramic	450	C-152	110743	.1 MF	Tubular	600
R-9	28172	2.2K ohms	1/2 W	10%	R-202	149113	100K ohms	1/2 W	20%	C-3	110402	47 MMF	Ceramic	450	C-153	110724	.1 MF	Tubular	400
R-10	28150	15K ohms	1/2 W	10%	R-203	28187	47K ohms	1/2 W	10%	C-4	171300	3.9 MMF	Ceramic	450	C-154	110586	.005 MF	Disc Ceramic	450
R-11	28166	220 ohms	1/2 W	10%	R-204	149115	220K ohms	1/2 W	20%	C-5	171233	1000 MMF	Disc Ceramic	350	C-160	110586	.005 MF	Disc Ceramic	450
R-12	28158	1K ohms	1/2 W	10%	R-205	28187	47K ohms	1/2 W	10%	C-6	171301	1000 MMF	Ceramic	350	C-161	110586	.005 MF	Disc Ceramic	450
R-13	28158	1K ohms	1/2 W	10%	R-206	149111	47K ohms	1/2 W	10%	C-7	171498	470 MMF	Disc Ceramic	400	C-162	110703	.047 MF	Tubular	200
R-14	28158	1K ohms	1/2 W	10%	R-207	28186	390K ohms	1/2 W	10%	C-8	171499	.33 MMF	Ceramic	400	C-163	110486	.047 MF	Ceramic	400
R-15	28158	1K ohms	1/2 W	10%	R-208	149115	220K ohms	1/2 W	20%	C-9	171500	.39 MMF	Ceramic	400	C-170	110672	.01 MF	Disc Ceramic	450
R-16	28158	1K ohms	1/2 W	10%	R-209	149114	150K ohms	1/2 W	20%	C-10	110402	2 MMF	Ceramic	400	C-171	110486	.01 MF	Disc Ceramic	450
R-17	28158	1K ohms	1/2 W	10%	R-210	149114	150K ohms	1/2 W	20%	C-11	171299	47 MMF	Ceramic	450	C-172	111093	.01 MF	Electrolytic	50
R-18	28158	1K ohms	1/2 W	10%	R-211	28185	330K ohms	1/2 W	10%	C-12	171299	.75 MMF	Ceramic	450	C-180	110586	.005 MF	Disc Ceramic	450
R-19	149282	4.7K ohms	1 W	10%	R-212	149121	2.2 Megohms	1/2 W	20%	C-13	171233	1000 MMF	Disc Ceramic	350	C-181	110465	.0033 MF	Tubular	400
R-20	28172	15K ohms	1/2 W	10%	R-213	28162	2.2K ohms	1/2 W	10%	C-14	171301	1000 MMF	Disc Ceramic	400	C-182	110715	.01 MF	Tubular	400
R-30	149048	2.2K ohms	2 W	10%	R-214	28158	1K ohms	1/2 W	10%	C-15	171498	470 MMF	Disc Ceramic	400	C-183	110718	.01 MF	Tubular	400
R-31	149048	2.2K ohms	2 W	10%	R-215	28158	1K ohms	1/2 W	10%	C-16	171499	.33 MMF	Ceramic	400	C-184	110718	.01 MF	Disc Ceramic	450
R-32	149048	2.2K ohms	2 W	10%	R-216	149114	150K ohms	1/2 W	20%	C-17	171500	.39 MMF	Ceramic	450	C-185	110586	.005 MF	Tubular	400
R-33-39	28170	10K ohms	1/2 W	10%	R-217	149113	100K ohms	1/2 W	20%	C-18	110402	2 MMF	Ceramic	400	C-187	110735	.0047 MF	Tubular	600
R-40-49	28142	47 ohms	1/2 W	10%	R-218	See M-1	22K ohms	1/2 W	10%	C-19	171599	.75 MMF	Ceramic	400	C-190	110737	.01 MF	Tubular	600
R-100	28142	47 ohms	1/2 W	10%	R-219	See M-1	8200 ohms	1/2 W	10%	C-20	171298	800 MMF	Disc Ceramic	600	C-191	110737	.01 MF	Tubular	600
R-101	149103	2.2K ohms	1/2 W	20%	R-220	See M-1	8200 ohms	1/2 W	10%	C-21	171264	1.5 MMF	Ceramic	450	C-192	110707	.22 MF	Tubular	200
R-102	28159	1.2K ohms	1/2 W	10%	R-221	149121	2.2 Megohms	1/2 W	20%	C-22	171264	1.5 MMF	Disc Ceramic	200	C-200	110533	.47 MF	Tubular	200
R-103	28159	1.2K ohms	1/2 W	10%	R-222	149039	390 ohms	2 W	10%	C-23	171233	1000 MMF	Disc Ceramic	100	C-202	110823	.005 MF	Tubular	100
R-104	149103	2.2K ohms	1/2 W	20%	R-223	149149	1000 ohms	2 W	10%	C-24	171265	1.5 MMF	Ceramic	450	C-203	110586	.005 MF	Disc Ceramic	450
R-105	171238	24K ohms	1/2 W	5%	R-224	145146	50K ohms	1/2 W	10%	C-25	171233	1000 MMF	Disc Ceramic	450	C-210	110705	.1 MF	Tubular	200
R-106	149384	22K ohms	1/2 W	10%	R-225	149107	10K ohms	1/2 W	20%	C-26	171266	1.6 MMF	Ceramic	400	C-211	110718	.01 MF	Tubular	400
R-110	28142	47 ohms	1/2 W	10%	R-226	28191	1 Megohm	1/2 W	10%	C-27	171266	1.6 MMF	Disc Ceramic	400	C-212	See M-1	.0022 MF	Electrolytic	450
R-111	28159	1.2K ohms	1/2 W	10%	R-227	28177	47K ohms	1/2 W	10%	C-28	171288	82 MMF	Disc Ceramic	400	C-220	See M-1	.0047 MF	Electrolytic	50
R-112	28159	1.2K ohms	1/2 W	10%	R-228	145100	6 Megohms	1/2 W	10%	C-29	171289	Variable—RF Tuning	Disc Ceramic	400	C-221	See M-1	.0047 MF	Electrolytic	50
R-113	28170	10K ohms	1/2 W	10%	R-229	28167	5.6K ohms	1/2 W	10%	C-30	171289	Variable—RF Tuning	Disc Ceramic	400	C-222	110718	.01 MF	Tubular	400
R-120	28145	82 ohms	1/2 W	10%	R-230	149121	2.2 Megohms	1/2 W	20%	C-31	171290	Variable—RF Tuning	Disc Ceramic	400	C-223	110745	.22 MF	Tubular	600
R-121	28159	1.2K ohms	1/2 W	10%	R-231	149039	390 ohms	2 W	10%	C-32	171290	Variable—RF Tuning	Disc Ceramic	400	C-224	110560	.068 MF	Tubular	600
R-122	28159	1.2K ohms	1/2 W	10%	R-232	145149	1000 ohms	2 W	10%	C-33	171286	1.5 MMF	Trimmer	600	C-225	110557	.022 MF	Tubular	600
R-123	28164	3.3K ohms	1/2 W	10%	R-233	149075	680 ohms	2 W	20%	C-34	171233	1000 MMF	Disc Ceramic	450	C-226	110561	.1 MF	Tubular	600
R-130	28164	3.3K ohms	1/2 W	10%	R-234	149385	100K ohms	1/2 W	10%	C-35	171298	800 MMF	Disc Ceramic	450	C-232	111105	.20 MF	Electrolytic	450
R-131	28162	2.2K ohms	1/2 W	10%	R-240	149385	100K ohms	1/2 W	10%	C-36	171285	82 MMF	Disc Ceramic	400	C-233	110534	.001 MF	Tubular	400
R-132	28162	2.2K ohms	1/2 W	10%	R-241	149385	100K ohms	1/2 W	10%	C-37	171285	82 MMF	Disc Ceramic	400	C-240	110534	.001 MF	Tubular	400
R-133	149404	33K ohms	1 W	10%	R-242	149117	470K ohms	1/2 W	20%	C-38	171288	82 MMF	Disc Ceramic	400	C-241	110716	.0047 MF	Tubular	400
R-134	149012	33K ohms	1 W	10%	R-243	149117	470K ohms	1/2 W	20%	C-39	171288	82 MMF	Disc Ceramic	400	C-242	110716	.0047 MF	Tubular	400
R-135	149012	33K ohms	1 W	10%	R-244	149117	470K ohms	1/2 W	20%	C-40	171288	82 MMF	Disc Ceramic	400	C-243	110716	.0047 MF	Tubular	400
R-136	149119	1 Megohm	1/2 W	20%	R-250	149123	4.7 Megohms	1/2 W	20%	C-41	171291	Variable—Osc. Tuning	Ceramic	400	C-250	110722	.047 MF	Tubular	400
R-137	149121	2.2 Megohms	1/2 W	20%	R-251	28189	680K ohms	1/2 W	10%	C-42	171291	Variable—Osc. Tuning	Ceramic	400	C-251	110309	.390 MMF	Mica	500
R-138	28175	33K ohms	1/2 W	10%	R-252	149387	1.5K ohms	1/2 W	10%	C-43	171286	1.5 MMF	Trimmer	500	C-252	110262	.390 MMF	Mica	500
R-139	28179	68K ohms	1/2 W	10%	R-253	149184	5.6K ohms	1/2 W	10%	C-44	171233	1000 MMF	Disc Ceramic	450	C-253	110260	.270 MMF	Mica	500
R-140	149117	470K ohms	1/2 W	20%	R-254	149386	150K ohms	1/2 W	10%	C-45	171233	1000 MMF	Disc Ceramic	450	C-254	110262	.390 MMF	Mica	500
R-141	145140	1K-100K ohms	Dual Pot.	20%	R-255	145150	40K ohms	1/2 W	10%	C-46	171287	22 MMF	Ceramic	400	C-255	110737	.01 MF	Tubular	600
R-142	149134	220 ohms	1 W	20%	R-256	28177	47K ohms	1/2 W	10%	C-47	171288	82 MMF	Disc Ceramic	400	C-260	111093	.01 MF	Electrolytic	50
R-143	149094	68 ohms	1/2 W	20%	R-257	28170	10K ohms	1/2 W	10%	C-48	171288	82 MMF	Disc Ceramic	400	C-261	111093	.01 MF	Electrolytic	50
R-144	149411	2K ohms	7 W	20%	R-258	149103	2.2K ohms	1/2 W	10%	C-49	171289	Variable—RF Tuning	Disc Ceramic	400	C-262	110548	.22 MF	Tubular	400
R-145	149075	680 ohms	2 W	20%	R-259	149434	250 ohms	1/2 W	10%	C-50	171290	Variable—RF Tuning	Disc Ceramic	400	C-263	110722	.047 MF	Tubular	400
R-146	149109	22K ohms	1/2 W	20%	R-260	149111	47K ohms	1/2 W	10%	C-51	171240	1500 MMF	Ceramic	400	C-270	110722	.047 MF	Tubular	400
R-147	149119	1 Megohm	1/2 W	20%	R-261	145147	500K ohms	1/2 W	20%	C-52	171240	1500 MMF	Ceramic	400	C-271	110722	.047 MF	Tubular	400
R-148	149119	1 Megohm	1/2 W	20%	R-262	149094	68 ohms	2 W	10%	C-53	171240	1500 MMF	Ceramic	400	C-272	110743	.1 MF	Tubular	600
R-149	149119	1 Megohm	1/2 W	20%	R-263	149017	68 ohms	2 W	10%	C-54	171240	1500 MMF	Ceramic	400	C-273	110562	.001 MF	Tubular	1KV
R-150	28185	330K ohms	1/2 W	10%	R-264	149017	68 ohms	2 W	10%	C-55	171240	1500 MMF	Ceramic	400	C-274	110548	.22 MF	Tubular	400
R-151	149107	10K ohms	1/2 W	20%	R-265	149094	68 ohms	2 W	10%	C-56	171240	1500 MMF	Ceramic	400	C-275	110825	180 MMF	Ceramic	3KV
R-152	149107	10K ohms	1/2 W	20%	R-266	149051	4.7K ohms	2 W	10%	C-57	171240	1500 MMF	Ceramic	400	C-276	110311	120 MMF	Mica	500
R-153	149094	68 ohms	1/2 W	20%	R-267	149051	4.7K ohms	2 W	10%	C-58	171243	5 MMF	Ceramic	400	C-277	110291	100 MMF	Mica	500
R-160	149094	68 ohms	1/2 W	20%	R-268														



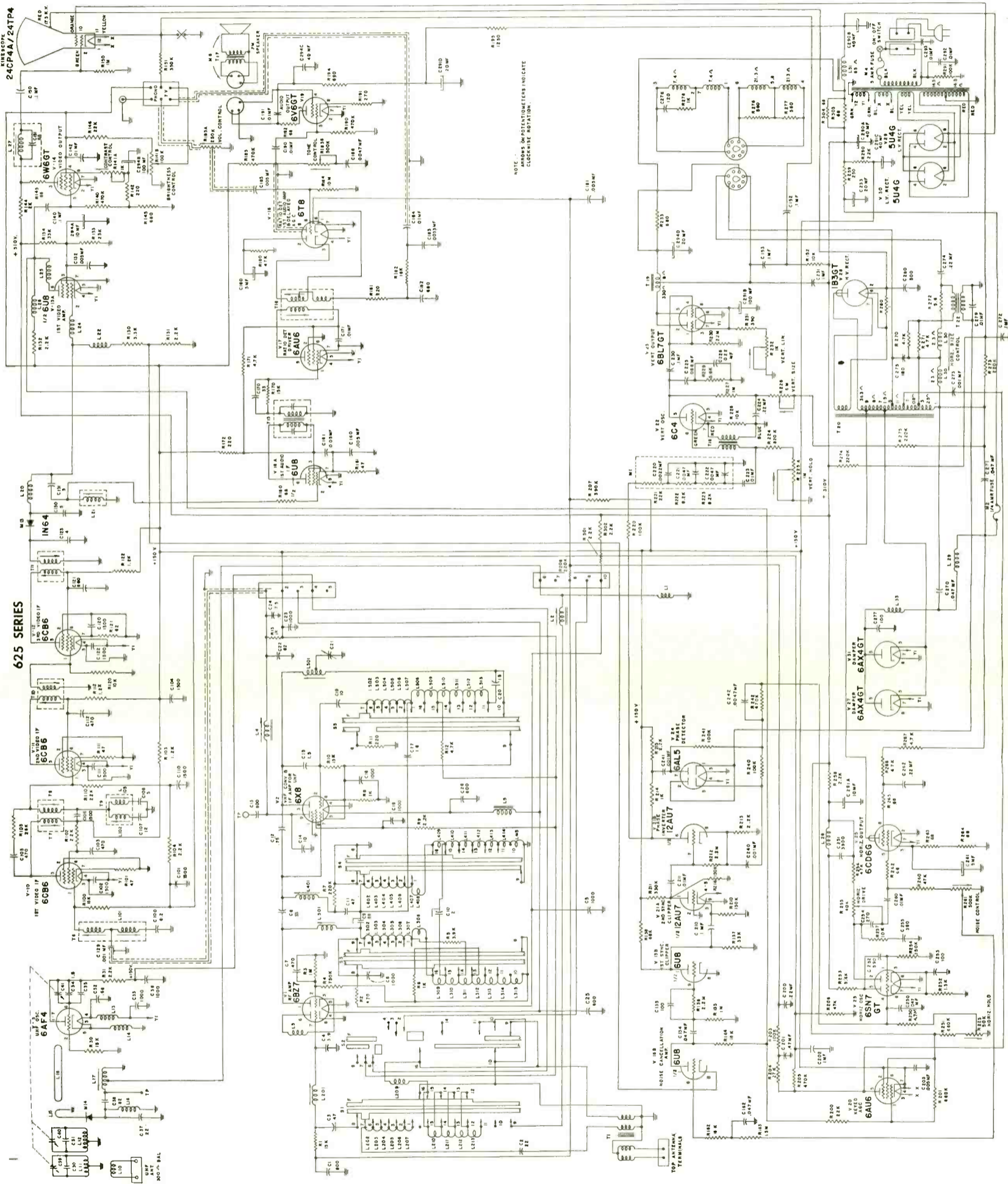

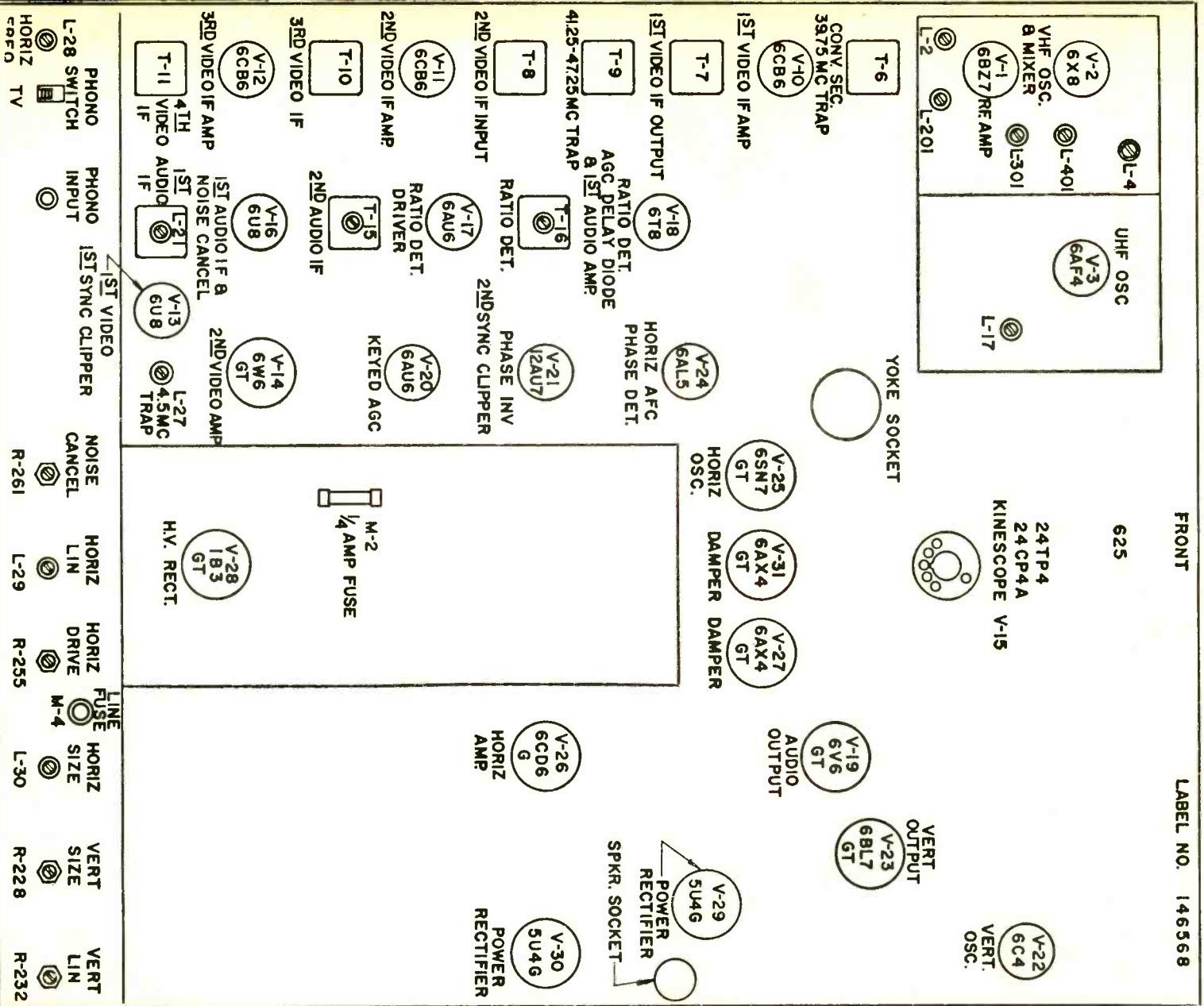

**TUBE VOLTAGE CHART**

1. Measurements are made at 117 Volts line using vacuum tube voltmeter. All voltages are D.C. and are positive with respect to chassis ground except where noted.
2. Contrast and brightness controls set at minimum, antenna disconnected.

	PIN 1	PIN 2	PIN 3	PIN 4	PIN 5	PIN 6	PIN 7	PIN 8	PIN 9	
V-10 6CB6 1st VIDEO I.F.	.0	.65	AC 6.3	AC 6.3	97	90	Gnd.			
V-11 6CB6 2nd VIDEO I.F.	.0	.65	AC 6.3	AC 6.3	95	96	Gnd.			
V-12 6CB6 3rd VIDEO I.F.	.0	.9	AC 6.3	AC 6.3	97	99	Gnd.			
V-13 6U8 1st VIDEO AMP & 1st SYNC. CLIPPER	32	—25	86	AC 6.3	Gnd.	92	Gnd.	Gnd.	—1.8	
V-14 6W6 2nd VIDEO AMP	8.2	AC 6.3	265	112	7.8	425	Gnd.	23		
V-16 6U8 1st AUDIO I.F. & NOISE CANCEL	91	.0	110	Gnd.	6.3	106	.6	—1	—7	
V-17 6AU6 RATIO DET. DRIVER	—46	Gnd.	Gnd.	AC 6.3	75	83	Gnd.			
V-18 6T8 RATIO DET.	—43	—1.65	—58	Gnd.	AC 6.3	.0	Gnd.	.13	47	
V-19 6V6 AUDIO OUTPUT	NC	Gnd.	225	245	.0	NC	AC 6.3	13		
V-20 6AU6 KEYED A.G.C.	97	112	110	112	2.4	300	112			
V-21 12AU7 PHASE INV. & 2nd SYNC. CLIPPER	38	Gnd.	6.0	AC 6.3	AC 6.3	91	10	15	Gnd.	
V-22 6C4 VERT. OSC.	NC	NC	Gnd.	AC 6.3	180	—43	.0			
V-23 6BL7 VERT. OUTPUT	.0	278	18	0	278	18	AC 6.3	Gnd.		
V-24 6AL5 PHASE DET.	.0	.0	Gnd.	AC 6.3	12	NC	—5.7			
V-25 6SN7 HORIZ. OSC.	—15	190	13	4.8	290	13	AC 6.3	Gnd.		
V-26 6CD6 HORIZ. OUTPUT	NC	Gnd.	20	135	7.2	7.2	AC 6.3	135		
V-27 6AX4 DAMPER	NC	NC	565	NC	255	255	AC 6.3	Gnd.		
V-29 5U4 L.V. RECTIFIER	NC	335	NC	Plate	NC	Plate	NC	335		
V-30 5U4 L.V. RECTIFIER	NC	335	NC	Plate	NC	Plate	NC	335		
V-31 6AX4 DAMPER	NC	NC	565	NC	255	NC	AC 6.3	Gnd.		
DEFLECTION SOCKET										
TUNER TERMINAL STRIP VOLTAGES:										
V.H.F. TUNER (V.H.F. POS.)	110	113	AC 6.3	—1.0	.0	.0	0	—5	.0	225
UHF POSITION	110	112	AC 6.3	110	.0	.0	AC 6.3	—5	.0	225
V 15 24CP4A KINESCOPE	Gnd.	.0	440	94	6.3					




AGAIN *telrex* OFFERS  
MORE BECAUSE...

# THERE IS A MATERIAL DIFFERENCE!

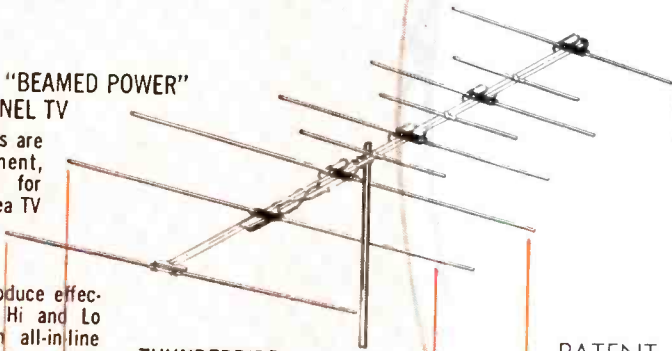
## NEW "THUNDER BIRD" "BEAMED POWER" ARRAYS FOR ALL-CHANNEL TV

"THUNDER BIRD" Antennas are loop phased, multi-element, "Beamed Power" Arrays for fringe and "sub-fringe" area TV reception. Element functions are duplexed by means of variable impedance phasing loops to produce effective high gain Yagis for Hi and Lo channel VHF Bands in an all-in-line array which actually produces superior gain and directivity — element for element — than equivalent separate units.




THUNDERBIRD  
MODEL T120


PATENT  
PENDING \*

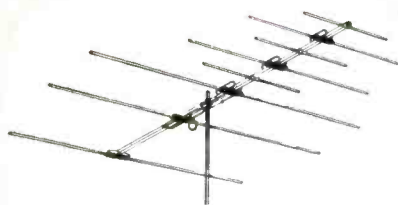


MODEL T110 THUNDERBIRD

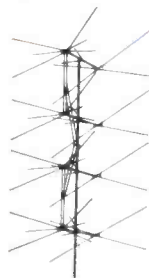

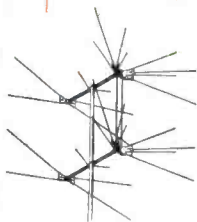
"8X-TV"—the  
Finest Fringe  
Area All-Channel  
Array ever  
Produced



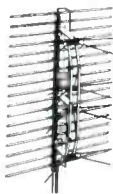"DUO-BAND"  
offers Sensational  
In-line  
Directivity and  
Gain on VHF  
and UHF



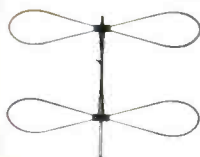"MODEL 84"  
covers Full  
UHF Range at  
Highest Signal-  
to-Noise Ratio  
and Maximum  
F/B Ratio



"CLOVER-V-BEAM"  
a Real Per-  
former, Low  
Cost and Incon-  
spicuous, Con-  
figuration Ideal  
for Second Set  
Installations

Producers of famous "BEAMED  
POWER" Communication Rotaries.  
Call or write for new catalogs  
on TV Antennas, Commercial  
Arrays or Amateur Rotaries.

• Top quality materials and construction plus superior performance is the TEL-REX watchword. Superb engineering combined with exhaustive laboratory and field testing assures reception quality that surpasses factory ratings. Over 100 different models are available to solve every installation problem, whether it be low cost or extra performance. Best quality materials assure peak performance rain or shine.

• See the new TELREX Exhibit at the Parts Show! Visit us at Booth 223, Electronic Parts Show Conrad Hilton Hotel, Chicago, May 16th to 19th inclusive.



AMERICA'S  
OUTSTANDING  
TELEVISION  
BEAM

ASBURY PARK 5  
NEW JERSEY, U.S.A.  
Tel. PRospect 5-7252

Canadian Distributor:  
DELHI METAL PRODUCTS,  
LTD., Delhi, Ontario

"Conical-V-Beams" are produced under U. S. Patent No. 23,346, Canadian Patent No. 500,436 and British Patent No. 691,485 — other patents pending. Sold only through authorized distributors.

# BATTERY BUSINESS IS PROFITABLE BUSINESS


Here's  
the **DOLLAR\$**  
and **CENT\$**  
of it

It stands to reason that the man who knows portable radios best, is the man who knows portable radio batteries best!

You are that man. Your customers look to you for fresh, full-power, long-life radio batteries to keep their portables going strong—that means RCA Batteries, of course.

With over 15,000,000 portables in the country, and with RCA Batteries available to power every leading model, you can profit from regular battery replacement business all year long, but especially now and in the months immediately ahead. It's clean, easy, rapid-turnover business—and it's profitable. Be sure your battery stock is complete. See your RCA distributor, and ask him for your free copy of "This Business of Selling Batteries" (Form 4F303)—your handbook of sales tips and promotional ideas for doing a big battery business.

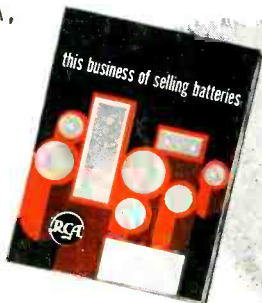Or write to RCA,  
Commercial  
Engineering,  
Section E42N,  
Harrison, N. J.



**RADIO CORPORATION  
of AMERICA**  
RADIO BATTERIES HARRISON, N. J.

