

THIRD ANNUAL VACATION NUMBER

June 6 1925

15 Cents

RADIO WORLD

Title Reg. U.S. Pat. Off.

Vol. 7. No. 11. ILLUSTRATED Every Week

155-167

SMOKESTACK PORTABLE
A FINE 5-TUBE SET

By Neal Fitzalan

HOW TO ELIMINATE BOTH
"A" AND "B" BATTERIES

By P. E. Edelman

OFFICIAL LIST OF STATIONS

A STROLL DOWN RADIO LANE

With Herman Bernard





Summer Static

Now Overcome by Volume!

Enjoy Radio All the Year Around—This Way!

How often have you heard it said, "Well, the warm weather is coming on, I had better put my radio on the shelf. It will be of no use until Fall."

There is absolutely no way to eliminate all static from your radio reception, but today there is a way, to reduce it to a point where it ceases to annoy.

This new way to overcome static is by volume. And volume can best be obtained by using transformers that will amplify weak signals to their greatest strength.


Here are the Kellogg audio and radio frequency transformers. Kellogg transformers give volume with clarity of tone.

The Kellogg radio frequency transformer is of the low-loss, high-efficiency type, incorporating important new features. It will operate at all broadcast wavelengths with standard .00035 to .0005

variable condenser. For best results, however, we recommend the Kellogg .0005 low loss variable condenser. Kellogg R. F. transformers at all radio dealers—\$2.35 each.

Kellogg audio frequency transformers give maximum volume with clear reproduction. They will build up the volume of any receiving set. This is due to the high quality materials used, expert workmanship employed and the special Kellogg process of manufacture. Kellogg

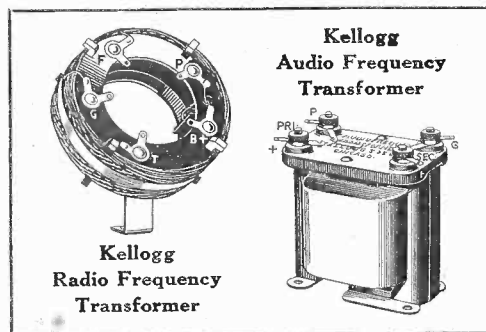audio frequency transformers are made in both shielded and unshielded types ranging in price from \$3.50 to \$4.50.



Kellogg transformers may be obtained at all radio dealers.

Kellogg Switchboard & Supply Co.

**1066 West Adams Street
Chicago, Ill.**


BARAWIK MONEY SAVING SPECIALS For JUNE

EACH MONTH the top of this page shows the newest and best standard radio parts and apparatus—at prices far lower than the same goods can possibly be obtained for elsewhere. Watch for this page! Make it and our big new catalog your buying guide. You will save a great deal of money and at the same time be assured of complete satisfaction with every purchase.


All Orders Filled Day Received

Low Loss Tuners
B-T—Green silk wound on low loss bakelite form.
200-550 meters \$4.45
50-225 \$4.45

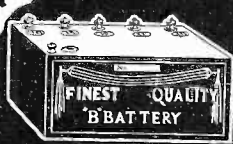
Ambassador
Silk wound on new type skeleton form. Covers whole broadcast band. \$5.95



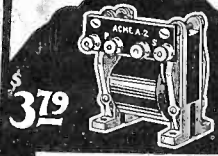Supercharge "B" Batteries
45 VOLT SIZE. Extremely long life. Stock always fresh. Special for this month.
45 volt.....\$2.80
2 1/2 volt.....1.20
Postage extra.



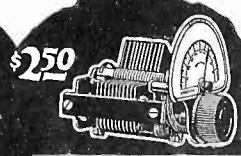
Armo Audio Transformer
One of the best known A. F. transformers. Specially priced—\$3.75. Postage paid.




Signal Low Loss Variable Condenser. Laboratory type.
11 plate 2.80 17 plate 2.80
22 plate... 2.70
48 plate 2.90
Postage paid.



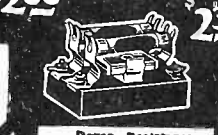Electric Drill Outfit
Usually sells for \$25 to \$35. Only \$17.95 this month. Order now. Postage extra.



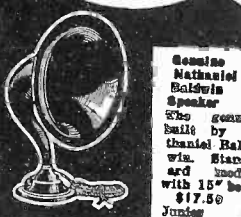Devo Resistance Coupled Audio—1st Stage, complete \$2.30
2nd \$2.45
3rd \$2.45
Post paid



Genuine Nathaniel Baldwin Speaker
The genuine, built by Nathaniel Baldwin. Standard model with 15" bell \$17.50
Junior model \$13.75



REMLER SUPER-HET KIT
One oscillator, one tuned stage transformer with condenser mountings attached and three intermediate transformers. For this month \$21.25 only

\$25.00 FOR YOUR OLD SET

No Matter What Kind It Is or What Condition It Is In Yes, we mean it! We will allow you \$25 for your old set if you will sit down right now and mail us your check or money order for \$35 balance in full payment for one of our 5 tube \$60 Marvelo Receivers. Never before in the history of radio merchandising has such an offer been made and we make it purely as an advertising proposition to introduce this wonderful new set.


Newest Type of Tuned Radio Frequency
Years ahead of the present standard types of tuned radio frequency receivers because its specifications and essential parts are of a far advanced superior design. The Marvelo V will give you clear, clean, undistorted, long distance, loud speaker reception with

WONDERFUL SELECTIVITY

without howls or squeals and with a degree of freedom from interference never before attained by a commercial radio receiver.

ACT QUICK!

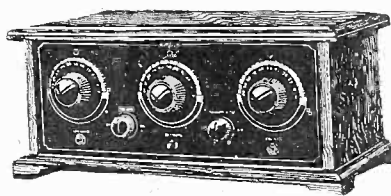This special advertising offer is positively limited. Pack up your old set now and ship it in to us. At the same time mail us your check or money order for \$35 and we will send you a Marvelo set at once. Get busy now—before this offer is withdrawn.



COMPLETE OUTFIT \$35.00
5 Type 201A Tubes 32.50
1—Antenna Equipment 86c
1—Loud Speaker 70c
Total \$67.50

Limited Offer


This \$60.00 **MARVELO** 5 Tube Receiver for only **\$35.00** and Your Old Set

Has finest low loss condensers; new type fieldless R. F. transformers; genuine bakelite panel, white silver engraved. An exceptional value. Order now before offer is withdrawn.



Marvelo Audio Transformer
The equal of any transformer, regardless of price. Produces the finest tone quality possible with satisfactory volume.
W1119—Shielded 6 -1 \$2.65
W1120—Shielded 3 1/2 -1 2.40
W1121—Shielded 2 -1 3.25
W1122—Unshielded 6 -1 2.25
W1123—Unshielded 3 1/2 -1 1.95
W1124—Unshielded 2 -1 2.85

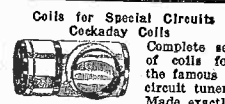All American A. F. Transformers
Another good standard transformer. Well built, beautifully finished. A quality product throughout.
W533—3 to 1.....\$4.05
W532—5 to 1.....4.25
W581—10 to 1.....4.25
Thornderson A. F. Transformer
One of the best standard A. F. Transformers. Used by most set manufacturers.
W589—2 to 1.....\$8.95
W587—3 1/2 to 1.....3.30
W586—6 to 1.....3.70




Coils for Special Circuits
Cockeyde Coils
Complete set of coils for the famous 4 circuit tuner. Made exactly according to L. M. Cockeyde's specifications. Each \$1.65
W298—Low loss. Each \$1.65
Harkness Reflex Coils
Green silk windings on genuine bakelite tubes. Complete with mounting brackets.
W295—Set of 2.....\$1.90

Wave Trap Coil
Spider web wound with loose coupled primary and secondary. Print and instructions included.
W170—Each.....\$1.05

Coll for Reimartz Circuit
Improved type. Covers whole wave band.
W296—Each.....\$1.05

Henninger Aero-Coils
The low loss, inductance system for tuned R. F. space wound on air. Very selective.
W1244—Per set of S.....\$9.45

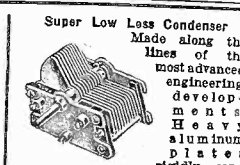AMPERITES
The Self-Adjusting Rheostat
W221—For UV201A.....98c
W222—For UV200.....98c
W223—For UV199.....98c
W224—For WD12.....98c



Super Low Loss Condenser
Made along the lines of the most advanced engineering developments in aluminum plates rigidly constructed.
W1231—11 plate.....\$1.65
W1232—17 plate.....1.85
W1233—23 plate.....2.05
W1234—43 plate.....2.85

American Brand
With 100 to 1 worm driven vernier.
W715—00025, 13 plate \$2.95
W716—00035, 17 plate 3.10
W717—0006, 23 plate 3.25

Aemo Lowest Loss Condenser
Enclosed in dust proof transparent case. Friction vernier. Requires 3 inch dial. Compactity .0005.
W810—Each.....\$4.95

Cardwell Condensers
King Quality. The original low loss condenser of patented design. Grounded rotor.
0.0025—\$2.98 0.005—\$3.50
0.0035—3.33 .001—4.20

ALL ORDERS SHIPPED POSTAGE PAID UNLESS OTHERWISE SPECIFIED

De Luxe Rheostats
As fine a rheostat as is possible to make. Genuine bakelite base. Large attractive black knob. One hole mount. Smooth and quiet.
W147—6 ohm.....62c
W148—10 ohm.....64c
W149—20 ohm.....86c
W149—30 ohm.....70c

Finest Quality Bakelite Sockets
Moulded of genuine brown bakelite. Reinforced slot and screw holes. Phosphor bronze contact springs.
Binding posts marked.
W140—Standard Base.....80c
W141—UV199 Base.....30c

SUPERIOR LIGHTNING ARRESTER
Air gap type. Absolutely dependable. Porcelain base. Brass binding posts and points. Approved by Underwriters. Easily installed.
W932—Each.....39c

Get This Big FREE Catalog OF ALL THE NEWEST PARTS BIG SAVINGS

Keep posted! The most complete radio catalogue ever compiled. Illustrates and describes all the newest parts, kits, cabinets, complete standard sets, and apparatus, and offers them at big reductions in price! Also many instructive books on radio. Every set builder needs our catalogue; the guide to the newest and best in radio and to big worth-while savings. Send for it at once. Absolutely free. Simply fill in and mail the coupon. Do it NOW!



De Luxe Charger
One of the finest chargers built. Maximum charging rate 7 amperes. Has accurate meter. Entirely enclosed. Neat appearing. Approved by Underwriters. For 110 volt 60 cycle A. C. current. Charges batteries overnight for a few cents. Guaranteed.
IW201—For 6 volt battery. \$12.95

STANDARD KITS AT BARGAIN PRICES

Every part of the last bolt and screw, is included in this wonder kit of finest quality parts.
IW858—Complete set parts (without cabinet).....\$33.50
ERLA REFLEX
IW876—Complete parts, 1 tube set.....\$15.60
IW877—Complete parts, 2 tube set.....23.60
IW878—Complete parts, 3 tube set.....31.60
AMBASSADOR 3 TUBE LOW LOSS
Everything necessary to complete this powerful low-loss set.
IW822—Complete, including high grade cabinet.....\$28.95
B. T. NAMELESS
One of the most popular circuits ever brought out. Extremely efficient. Genuine parts. No cabinet included.
W661—Complete for 5 tube set.....\$33.50
ACME 4 TUBE REFLEX
The loop set that makes 4 tubes do the work of 6.
IW883—Parts with loop and tools (no cabinet).....\$44.50



NEWSTYLE BAKELITE PLUG
Cord tips insert in end and cannot be loosened until proper side pull is made. One of the best plugs ever designed, and exceptional value at our

BARAWIK COMPANY,
102 S. Canal Street, Chicago.

Send me my copy of your latest Radio Catalog showing newest parts, kits, sets, apparatus, etc., at money saving prices.
Name.....
Address.....

Now Hear Radio Music Better Than Ever Before

By the end of this year, we expect to see the beautiful new Crosley Musicone replace at least half a million of the best of present-day radio reproducing devices.

For the Crosley Musicone, designed and built on entirely new principles, covered by *basic patents* issued and pending, reproduces music and the speaking voice true to life—

Without distortion, extraneous overtones, resonance vibrations or other horn noises;
Over the *entire* musical scale, from lowest to highest notes, on *any* instrument;
Without overloading; and without chattering, because its diaphragm is a floating cone;
Without adjustments or additional batteries;
Without directional properties or a horn;
And at a price that is revolutionary.

Sound from it fills the entire room, the notes clear and round and mellow. No need to cluster round. Every note comes in at its true musical value—in solo, duet, chorus, orchestra and drums.

Your own radio set—no matter what circuit nor how many tubes—needs the Crosley Musicone; and until it has this instrument, it can never give you the best that its maker built into it.

Ten thousand radio dealers are now displaying and demonstrating the beautiful Crosley Musicone.


By all means hear it, and know for the first time what real radio music is. Then equip your set with this beautiful, compact reproducer and no other. Write for complete description.

The Crosley Radio Corporation, Cincinnati
Powel Crosley, Jr., President
6401 Sassafras St.

Guarantee

Dealers are authorized to sell the Crosley Musicone on five days' trial in your home. Satisfaction guaranteed or money refunded upon return.

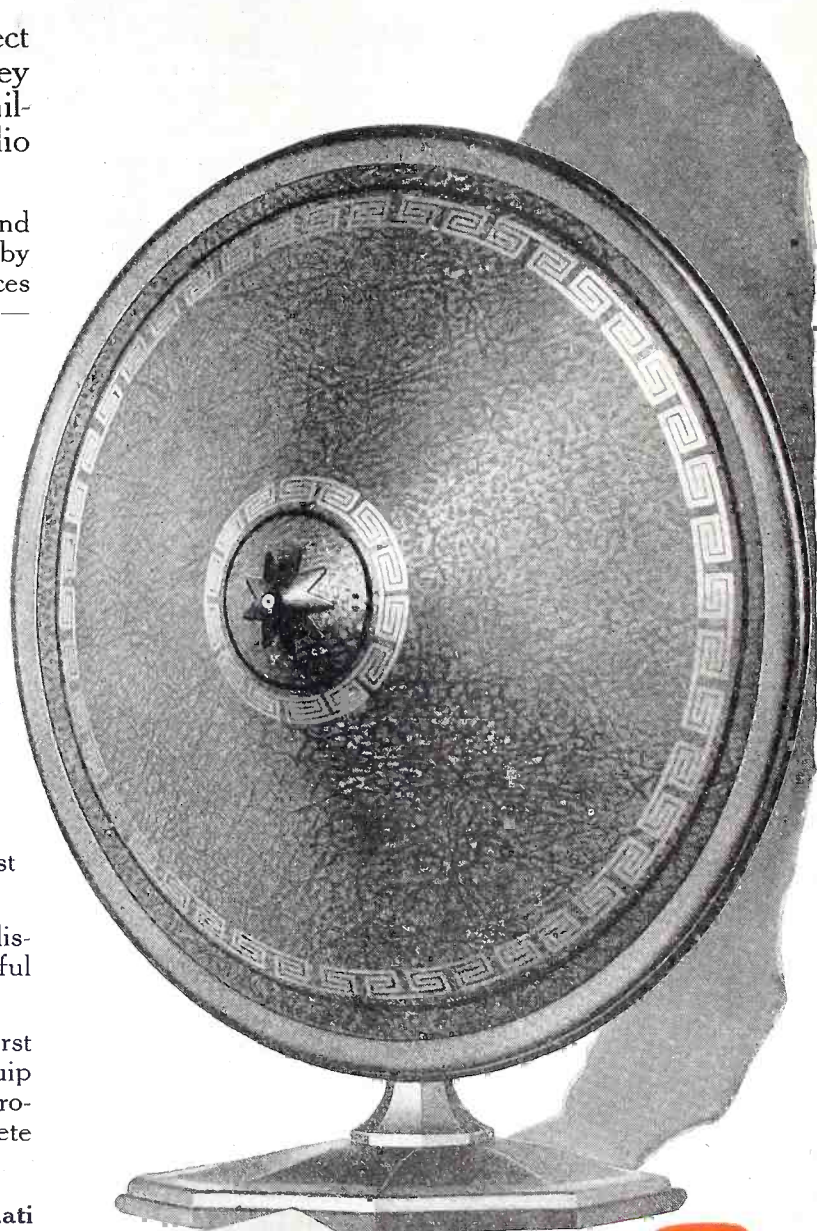Crosley manufactures receiving sets which are licensed under Armstrong U. S. Patent No. 1,113,149, and priced from \$14.50 to \$65, without accessories.



17⁵⁰

Add 10% West of Rocky Mountains.
The Crosley Musicone is artistically beautiful—an ornament in any home.
Crosley owns and operates station WLW, Cincinnati, the first remotely controlled super-power broadcasting station.

RADIO WORLD

[Entered as second-class matter, March, 1922, at the post office at New York, N. Y., under the Act of March 3, 1879]

A Weekly Paper Published by Hennessy Radio Publications Corporation from Publication Office, 1493 Broadway, New York, N. Y. Phones: Lackawanna 6976 and 2063

Vol. VII. No. 11. Whole No. 167.

June 6, 1925

15c per copy, \$6.00 a year

The Smokestack Portable A Fine Set for Use on Vacation

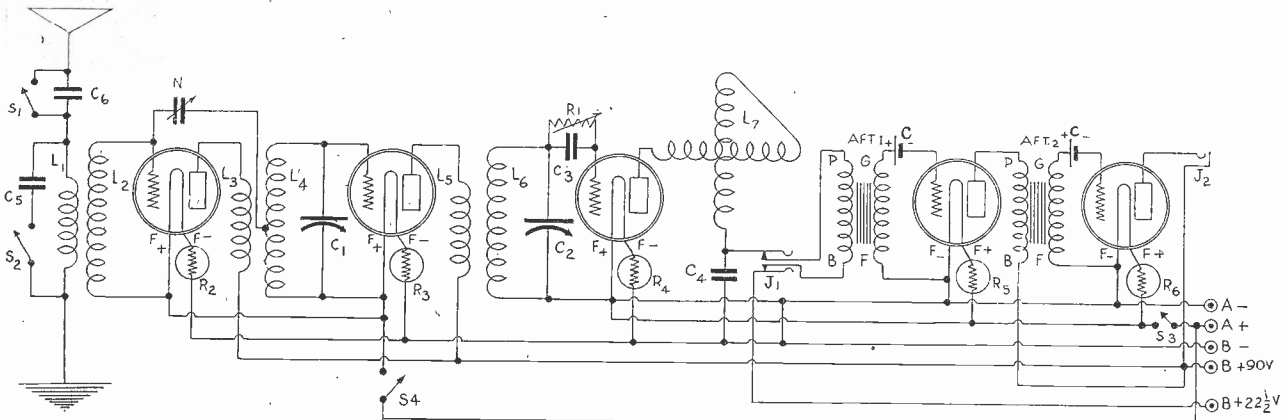


FIG. 1—The diagram of the Smokestack Portable. DV3 tubes (using 4½ volt A battery) are used in standard sockets. The grid return of the two RF stages worked fine to positive as shown, instead of the usual negative, but both ways should be tried.

By Neal Fitzalan

RECENTLY I received the following letter from a friend:

My Dear Neal:

I shall soon go on my vacation. You know last year I had a portable radio set but the reception was not very good. I didn't know much about radio then, but I have studied since and now can build almost any set. Of course you understand that I do not know the theoretical part of radio, but enough to put a set together. Now here is where you come in the boat. I would like you to give me a hook-up and complete description of a portable radio receiver, one that can get all the New York stations, and also some greater distance, with good quality. I don't want to spend much. Also put the least amount of controls on the panel that you can, and try and do away with rheostats.

Your friend,

PHILIP KRAMER.

The set (Fig. 1) is not expensive or difficult to build.

Parts to Purchase

The first things to buy are the five tubes, DV3 being used here, five standard sockets being next in line. Two Heghog audio-frequency transformers, 5 Amperites (to match the tubes that you purchase), three .001 mfd. Dubilier fixed condensers, .005 mfd. variable condensers, one X-L Variometer (type N), one variometer, 7x24" panel (hard rubber), 1 lb. of number 22 DCC wire, two pieces of hard rubber or other tubing 8" in length and 1½" in diameter, another piece of hard rubber tubing, 3" in diameter and 4" in length, a .00025 mfd. Dubilier fixed condenser for the grid, a 2-megohm grid leak, one double-circuit jack (anti-capacity) one single-circuit jack (anti-capacity) one terminal strip, one portable cabinet 15" x 24" four Cutler-Hammer single-circuit switches, two small Eveready C batteries (4½ volts apiece), three dry cells 1½ volts apiece, four small B batteries (22½ volts apiece), screws, nuts, etc. No. 18 bell wire for wiring up set. Don't use bus bar.

Wind all coils with number 22 double cotton covered wire. L1 and L2 are wound on a 3" tubing, L1 having 10 turns.

Leave ¼" and wind 45 turns for the secondary L2 and terminate. Leave the beginning and the end of the primary of the coil sticking out and the beginning and the end of the secondary winding likewise. This winding should take about 4". Cover the entire length of the tubing. L3L4L5L6 are wound on the smokestack forms, the forms being 8" in length and 1½" in diameter.

Leave the beginning of coil (L) sticking out and wind 20 turns No. 22 DCC wire on one form 8" in length and 1½" in diameter. Leave the end of wire out as a lead. Leave ¼" at space on form. Begin winding L4, which has a tap at the 50th turn, and is continued 30 turns more, leaving an end out as a lead. Total wire on secondary, 80 turns No. DCC.

L5 is wound in same fashion as L4 on same kind of tubing. Terminate. Leave ¼" and wind in straight fashion 80 turns (no tap). Be sure to leave an excess at the beginning and end of L5 and L6 (four leads) for interval set connection purposes. Do not put any shellac or varnish on coils. If you want coil to hold, put a drop of collodion on the ends of coils. Preferably bunch pinholes for wire anchorage.

The smokestack coils are placed on the end of the baseboard, 3½" from ends and ¾" in from ends. Strike an arc, and saw out the semicircle (see Fig. 2). This is done on both ends.

The two audio-frequency transformers are placed at right angles to each other and right next to their respective sockets. The same applies to the radio-frequency transformers, that is, they are placed close to their respective sockets also. This is all done so as to have very short leads and to prevent losses, as this is a portable set and you will not be right on top of a station, therefore must conserve all the energy that is necessary to receive loud signals. Exactly in the center of the baseboard place the antenna RFT, the only long leads here being the antenna and the ground. Place the Amperites one end at the socket, near the filament

Loop Used As Open Antenna

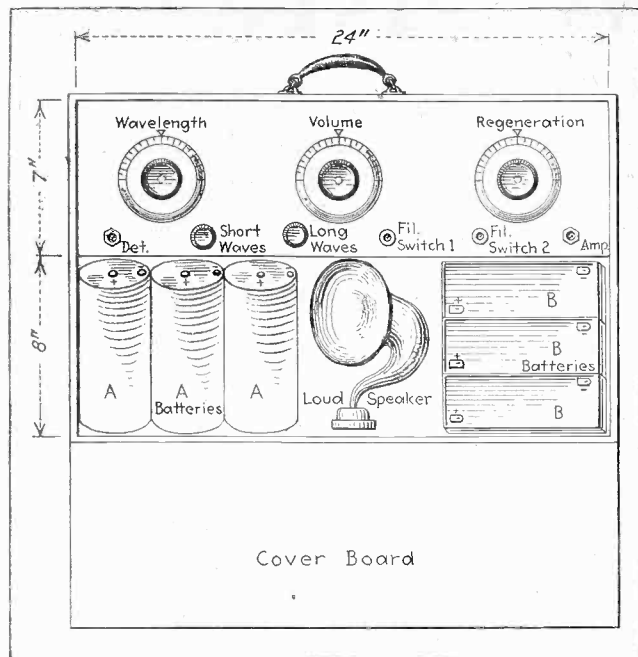


FIG. 2—How the front of the panel looks when completed. Note the small loud speaker between the A and B batteries. The whole case weighs 12 pounds. Four-inch dials are used.

posts. The other instruments are placed according to the discretion of the builder.

Six inches from the end of the panel and $2\frac{1}{2}$ " from the top and the bottom of the panel drill a $\frac{1}{4}$ " hole for the variable condenser dial. Six inches away from this hole and $2\frac{1}{2}$ " from the top and the bottom of panel drill another hole for the other condenser 6 " away from this hole and $2\frac{1}{2}$ " from the top and the bottom of the panel, drill the last hole for the variometer. Three inches from the left of the panel and 1 " from the bottom drill a hole for the jack. Four inches away from this hole and on the same line from the bottom of the panel drill another hole for the switch; 4 " away from this hole drill another for the other switch; 4 " away from this hole, and while still working on the same line drill another hole for the switch; 4 " away from this hole drill another hole for the last switch, and 4 " away from this hole drill the final hole for the last jack, this being 3 " away from the right-hand side of the panel. The total length of the cabinet as you see in the picture is 15 ". The cover board is of the same dimensions, that is 15 " width and 24 " length. The A battery takes up about 9 " of the space in the bottom of the cabinet. The loud speaker (the Amplion was used here, which is 3 " in diameter) will take up the same amount of space. The B batteries will take up the other 12 " of the space in the cabinet. The leads from the batteries may be led up from the back of the panel from the terminal strip.

The Wiring of the Set

First connect the coils up, as they are the most important instruments in the set. The beginning of L1 goes to the ground and not to the antenna, the end of the coil going to the antenna. The secondary winding of the same coil goes to the grid and the end of the winding of this coil goes to the filament switch S4, the other end of the filament switch going to the A plus. This connection which goes to the grid also goes to the X-L Vario-Denser (neutralizing condenser), the end of this condenser going to the 30th tap of L4. The beginning of the L3 goes to the plate post of the socket, the end going to the B plus 90 volts and to the end of L5. The beginning of L4 goes to the grid post of the socket, also connecting to the stationary plates of the variable condenser, the rotary plates going to the end of

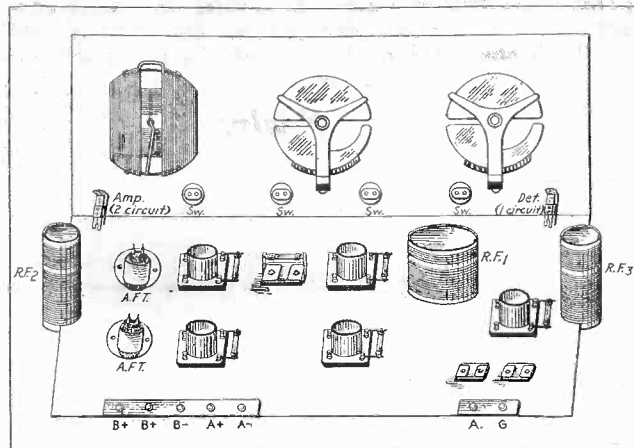


FIG. 3—A complete layout of back of the panel and the baseboard. Note the semi-circle cut in on each end to accommodate the Smokestack Coils. The diameter of the semi-circle is $1\frac{1}{2}$ " and from circumference to panel edge $\frac{1}{8}$ ".

L4, not to the tap, but to the last turn on the coil. This turn also goes to S4. The beginning of L5 goes to the plate and the end to the B plus 90 volts. The beginning of L6 to C3 and to R1, also to the stationary plates of the variable condenser. The variable plates of the condenser go to the end of L6 and to the filament plus. One end of the variometer goes to the plate post of the socket, the end of the variometer going to the top of the double circuit jack and also to the .001 mfd. condenser, the other end of this condenser going to the B minus which is connected to the A minus. All the Amperites are placed in the positive lead, except the ones in the AFT stages, which are placed in the negative leads of the A batteries. This way worked best on the set I built, although not according to formula. S1 is connected across the fixed condenser, with a capacity of .001 mfd., which is connected in series with the antenna. One end of S2 goes to the beginning of the coil L1, the other end of the switch going to C5, which also has a capacity of .001 mfd. The other end of this condenser goes to the end of the coil. This is so arranged that the condenser can be cut in or out. S3 is placed in the amplifier filament leads so that the filament current may be turned off and on.

We will now connect up the audio amplifier. Connect the post marked P to the second terminal of the double-circuit jack and the post B to the third terminal of the same jack, the end of the jack going to the B plus $22\frac{1}{2}$ volts. From the G post of the AFT, bring the plus of the C battery to this post and the negative post to the grid post of the socket, connecting the G post of the other AFT in the same fashion. The F post of the AFT goes to the filament minus. Connect the other transformer up in exactly the same fashion. Connect the plate post of the second AFT to the top terminal of the single-circuit jack, the end of the jack going to the B plus 90 volts. That completes the wiring of the set.

How to Tune the Set

By rough adjustments tune in any station (local, with plenty of volume), and take out tube number 1, this being the first from the left in Fig. 1. Turn the little knob on the neutralizing condenser in or out until the signal disappears entirely. This completes the neutralization. Leave the switches S1 and S2 in and turn the two variable condensers at approximately the same point, that is 30-30, and turn the variometer to the right until the tube is just about to spill over. The condenser C4 helps the regeneration a great deal, and it may be that this condenser is either shorted or blown if you do not get a lot of oscillatory action out of the tube. The detector filament needs no careful
(Concluded on page 28)

A and B Battery Eliminators

[This is the first of a series of articles on how to construct apparatus for obtaining filament and plate current from the lighting mains. Part II will be published next week.]

By P. E. Edelman

Electrical Engineer

PART I

HOW can I use the ordinary house lighting line as a current supply for operating my vacuum tube radio set? What apparatus and wiring are necessary? These questions are often asked, so I will answer them.

Requirements

For operating just one tube or possibly two, especially when these are of dry cell type, the use of dry cells is favored, but when a multi-tube set is to be operated a substitute is sometimes sought.

A substitute must afford reasonably constant supply and be quiet in practical operation. Considering an average 5-tube set using type 201A tubes suitable outputs will be as follows:

For Amplifier Tubes

Plate output supply, D. C. 100 volts, 25 milliamperes.

For Detector Tubes

Plate output supply, D. C. 20 volts or 40 volts, 4 milliamperes.

Total plate watts, four amplifier tubes, 2.5 watts; one detector tube, 40 volts; plate, .16 watts.

For each tube, filament supply, 6 volts $\frac{1}{4}$ ampere, or $1\frac{1}{2}$ watts per tube. Total for five tubes, $7\frac{1}{2}$ watts.

For 199-type tubes, filament requirements are much less, on basis of .07 ampere per tube. Five 199 tubes, $5 \times .07 = .35$ ampere.

Further requirements are absolute safety of operation, separation for loop set supply, of tube current source from ground lighting mains, absence of noises and large amount of heat, small space taken, and low cost. To be popular the initial cost should not be high. The upkeep cost must be low, preferably with absence of renewable parts, bulbs, chemicals, etc. A further requirement for popular use is absolute simplicity and fixed adjustment, so that no special wiring nor changes in standard types of sets are needed. Universal operation of A. C. or D. C. line is desirable, but special types, one for each kind of lighting circuit, are permissible when clearly labelled accordingly.

Kinds of Substitutes Considered

The following kinds of substitutes will be considered. First there is the use of direct current line. For filament supply this requires a series resistance. For plate supply this requires a filter trap, to remove commutator ripples. Other ways are to use the generator, or similarly to operate a vacuum tube oscillator to obtain high frequency current suitable for use on both filament and plate circuits via transformers.

Then there is the A. C. (alternating current) line. Here an obvious combination is the transformer, rectifier and filter. The rotary converter is worth consideration.

For either D. C. or A. C. line, thermic convertors using thermopiles are worth consideration along with rotary convertors and high frequency tube oscillators.

Then there are the battery combinations using continuously charged storage batteries of small size. I will show how this is practically done. Also there are the

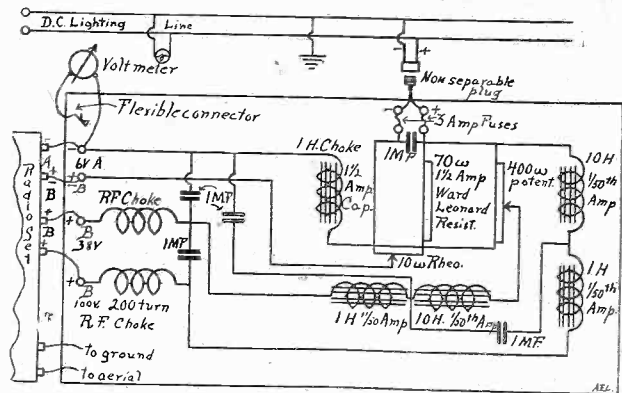


FIG. 1—A filtering system which employs the Campbell method. This method is used for cutting out the hum, which usually comes from the commutator of the DC generator.

more cumbersome large type batteries and separate charger outfits.

The use of high frequency current for filament supply and also for self-rectifying plate current supply will be considered as well as the use of thermocouple batteries energized by nichrome wire heaters. Practical filter circuits for cutting down hum and audio pulsating currents to negligible value will be shown.

Then there are special set circuits permitting direct A. C. feed from transformers. The necessary windings and middle tap connections will be shown. Also the use of ordinary 201A tubes as rectifier will be shown as well as use of special tubes, S tubes, and ordinary double filament incandescent auto lamp substitute for making an inexpensive home-made unit.

Brief mention will be made of chemical convertors or colloid rectifiers and electrolytic condensers, but all chemical devices are handicapped by undesirable messy liquid chemicals which are far from neatly handled in sets in parlors, etc.

Operation of tubes from filament current only, without separate plate current supply, will also receive mention with circuits suitable therefor.

Thus, while special attention is to be given to supply suitable for the average set, the same principles can be extended to fit requirements of any practical radio set using up to ten tubes of any type. Also, a unit suitable for a 5-tube set can be employed without change for a set of only four or three or even two tubes.

Because A. C. is the lighting current found in most homes and apartments, arrangements for its use will receive the main notice.

What Kind of Current?

First find out what kind of lighting circuit you have. One way is to telephone the lighting company. The fan motor you use may tell on its name plate, if it is not a universal type. Tests that can be made to determine this are omitted owing to the danger that novices may cause short circuits and blow fuses.

The usual house current will be 110 volts A. C. 60 cycle, or 110 volts D. C. Direct current will only be found in buildings having separate power supply or in certain downtown districts or business loops of cities.

One thing to remember is that usually one side of the line is grounded. Universal units insulated from ground are specially desirable, but where an arrangement is used in which there is a direct connection from the radio set to the lighting circuit, special care must be taken to have the ground wire on the correct side, else the current may run through the set and to the

How to Use the 110-volt Line

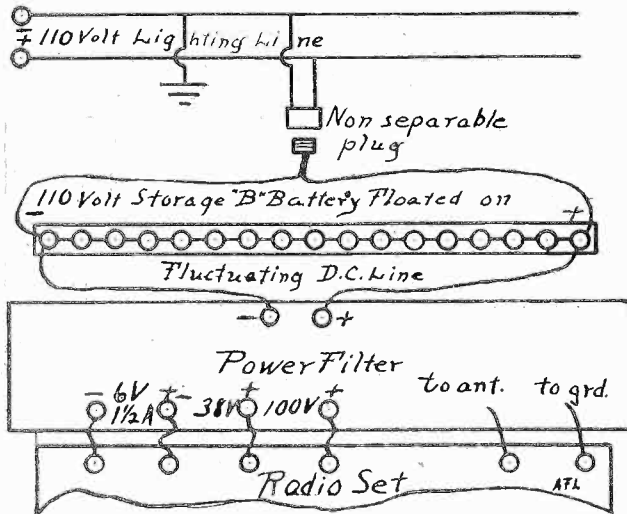


FIG. 3—How a floating B battery is hooked up in the line, in case the Campbell method does not cut out hum.

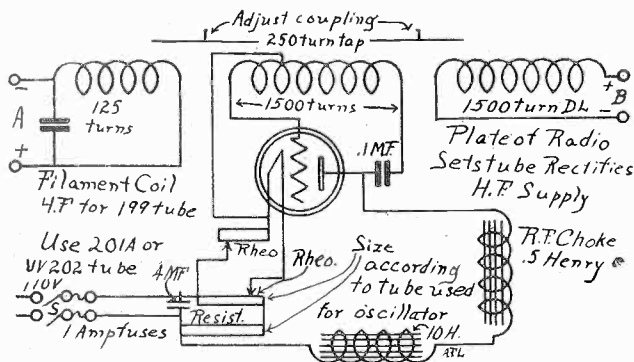


FIG. 3—How a 5-watt electron tube is hooked up in an oscillating system to supply A and B battery current.

ground via ground post of set, burning out the radio circuit. Every arrangement in which this can happen by wrong connection will be restated as a precaution and that is why further favor may be given to units in which this danger is wholly avoided.

In a unit employing a vacuum tube as a high frequency oscillator, the output can be used as plate current feed, also for supplying filaments of tubes having low current consumption, such as 199 type. Each kind of substitute is further to be considered from initial cost and upkeep standpoint.

From the general statements made thus far it may be evident that there will always be some capacity effect between the substitute and the ground. For filaments this does no harm, but requires attention in loop-operated sets. For plate circuit supply, the capacity effect of the substitute with respect to the ground must be reduced to a minimum in radio-frequency circuits to avoid bypass losses.

Comparative Results

Based on operation during two years it can be stated that battery substitute arrangements of proper design are economical.

City lighting mains are today very dependable in most localities with regard to continuity of supply and maintenance of characteristics of voltage and frequency. In some localities, where heavy power motors are operated on the same circuits as the lighting is taken from, this is not true, and wide fluctuations will not make substitutes operate smoothly as desired. A simple test is to watch the incandescent lamp in a socket burning. If it gives a steady light, the circuit can be used. If it flickers or fluctuates often, it is useless to

attempt to employ the source, except possibly with a sluggish-acting heater unit operating a thermocouple.

Use of Direct Current Lighting Line and Universal Units

The use of a direct current lighting socket as tube current supply source requires a device to control or change the lighting current to suitable form. Direct current will be found only in limited localities, usually downtown districts of cities and private plant-operated buildings. Ordinarily 110 volts direct current will be found, but a few buildings will have 220 volts or other voltage for lighting, so determine this by looking at label of a lamp socket used, or inquire of the power company.

Direct current usually comes from a generator but in some places a storage battery is kept floating on the line by the power plant. The latter case affords a good steady supply but the use of generator only is likely to give considerable commutator hum. To design a filter to cut out this hum is simple for a given case but the pitch of hum or commutator pulsating frequency will differ for various localities from different dynamos, so that a filter for general use will be preferably of the Campbell type, capable of cutting out a considerable band of audio frequencies. See Fig. 1.

An essential is the use of a fuse in each circuit, not larger than six amperes in main line connection and not over one ampere size in tap for plate supply. While lamps can be impressed into service as series resistors, the manufactured units such as G. E. or Ward Leonard come in suitable sizes and are preferable. The condensers are preferably of mica type such as Micadon, Freshman, etc., though some of the telephone condensers, as Mansfield or Western Electric types, may be economically used for the large sizes. The coils must have sufficient current carrying ability so as not to heat up, and this requires ordinarily, No. 18 wire or larger for filament circuit and No. 30 or larger for plate circuit. The resistance values of resistors used must be made to fit the type of tubes and number of tubes used, in size and current carrying capacity.

In first arranging a current feed circuit, as in Fig. 1, a voltmeter is a handy device to have around in making adjustments and determining plus and minus connections. Makeshifts such as noticing the bubbles from the negative wire inserted in a glass of water to show polarity, or noting brightness of a ten-watt 110-volt lamp for rough voltage guess, are not recommended.

The arrangement of Fig. 1 usually will be grounded via one side of line, so it is necessary to determine this and label wires correctly. A separable plug connector should be taped together so as not to get the polarity of connection reversed. Care should be used to keep the ground post of radio set and the ground of line connection on the same polarity side of the wiring as it is not desirable to have lighting current flow through the radio set wiring and down the radio set ground wire connection. There have been devices manufactured along lines of Fig. 1, but this method is properly considered experimental and requires care in use owing to usual ground on line wire. By making adjustments initially the proper voltages may be had, and thereafter the operation will be very satisfactory in most instances. The precautions are essential, to avoid burn-outs. If the arrangement of Fig. 1 is tried and there are still undesirable audio hums or wide fluctuations in current due to varying generator supplying the lighting line, it is nevertheless possible to get good results by adding a small B battery storage cell unit, continuously charged or floated on the circuit, Fig. 2. But this is not strictly a non-battery plan. In this case the stor-

Different Types of Rectifiers

age B battery can be used for both A and B battery supply, with suitable tubes.

Universal Methods

The universal methods will be discussed along with the alternating current supply arrangements as they can be used equally well on either kind of prime current supply. The thermopile or assembled heater and thermocouple series units are of this class. Thermopiles cannot be relied on for heavy currents but may be used as B battery substitute with satisfaction. The voltage from one thermocouple is usually very small, so a great many have to be assembled in series. By using an electric heater at one terminal and the air at room temperature at the other junction, it is possible with such combinations as nickel or german silver against zinc or an alloy of zinc and antimony to obtain as much as .04 volt per couple conveniently, and of course, there are no chemicals to renew as in batteries. 40 volts would require 1,000 junctions, usually arranged in plate form, heated at center and cooled outside.

Similarly, the direct current supply can also be used to energize a separate vacuum tube oscillator from which high-frequency current output suitable for operating the radio set tubes may be taken.

Vacuum Tube Oscillator on Direct Current Line

Fig. 3 indicates use of a 5-watt vacuum tube as oscillator. The coils may be chosen to give any frequency output which will not interfere with usual operation of set. This can be very high to keep below broadcasting wavelengths or made very low to be above both the broadcast and intermediate wavelength bands. For plate supply only, it is possible to use even a 201A type tube, but the UV202 or equivalent tube is best. Suppose that an ordinary radio set is to be used. Then honeycomb or D. L. coils 1500 can be used for the oscillator tube. The high-frequency output should come in the supersonic range but may be just at the high limit of audibility. The plate of the regular set tubes can rectify this high-frequency current, so this means is suitable for plate voltage supply. For filament operation, 199 tubes must be used and a separate step down coupling coil used. Units of this kind are difficult of initial adjustment for the home experimenter but can be made up in proper adjusted sizes in any equipped laboratory or factory, and may even be elaborated on with addition of filter or bypass trap condenser and smoothing choke coil.

Use and Size of Choke Coil

You will notice a radio-frequency choke coil mentioned in all cases where there can be a direct leak of plate to filament via the plate current supply source. It can be made simply by winding 200 turns of 22 DCC wire on a spool or form one inch in diameter, Fig. 4. This will choke back the radio-frequencies in the broadcast waveband.

Commercial Units

Units of this kind which have been marketed or are made or announced for early placing on market are known under several names. There is one comprised for direct current use only; on lines of Fig. 1. Another for universal use employs thermopile, called a Thermofomer. A different unit employs condensers and coils, as in Superducon. Then there is the "nobatte" rotary convertor device. Also in this class may be considered the assembled storage battery and charger devices such as Gould Unipower. Another way in which lighting circuits may be used directly requires special form of vacuum tube. Several kinds of these tubes have been made but not as yet marketed. Usual-

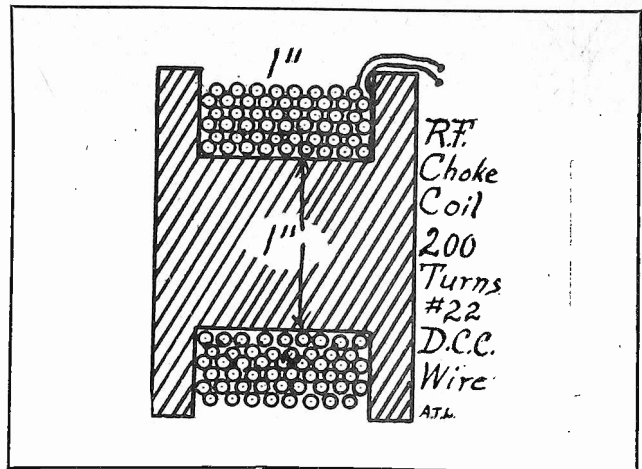


FIG. 4—How the radio-frequency choke coil is wound.

ly the lighting current is used to operate a heater which gives heat energy to an electron-emitting surface according to the types. A, uninsulated (Nicholson); B, separable (Torrissi); C, renewable, separated (Edelman). There is no technical reason why radio sets using such tubes and operating simply and directly from lighting mains without requiring somewhat complicated convertor devices, should not be marketed. For alternating current power amplifier plate and filament supply, there is the Western Electric A. C. 2-tube unit.

As should now be evident, there is little need for using battery substitutes in case of one or two tube sets employing 199 type tubes, and it is only in the large multitube sets that batteries become less desirable. That is where substitutes are practicable, using 201A and 200 type tubes. The use of small size storage cells of B battery type as A battery supply for 199 type tubes is quite practical, especially when a continuous charging arrangement is used, and this plan gives considerable competition to some of the battery substitute arrangements.

[Part II, of this article, to be published next week, June 13 issue, will deal with AC current mains used for supplying filament and plate potentials. The article will be concluded with Part III, June 20.]


Mount the Condenser Back from Panel

IF a variable condenser without a metal end plate, or one with a grounded rotor, is used, capacity effects can be cut down by spacing the condenser away from the panel. That is, mount the condenser about one-half inch from the back of the panel with spacing washers. Then make sure that the shaft is long enough to take the dial set screw.

Wedge Will Keep Tube in Place

VERY often a tube will not fit properly in its socket. If too loose it must be held down to make contact with the springs of the socket. To temporarily offset this condition a toothpick or a match whittled down to form a wedge and placed between socket and tube will hold the tube tightly in place.

A Saunter Down Radio Lane

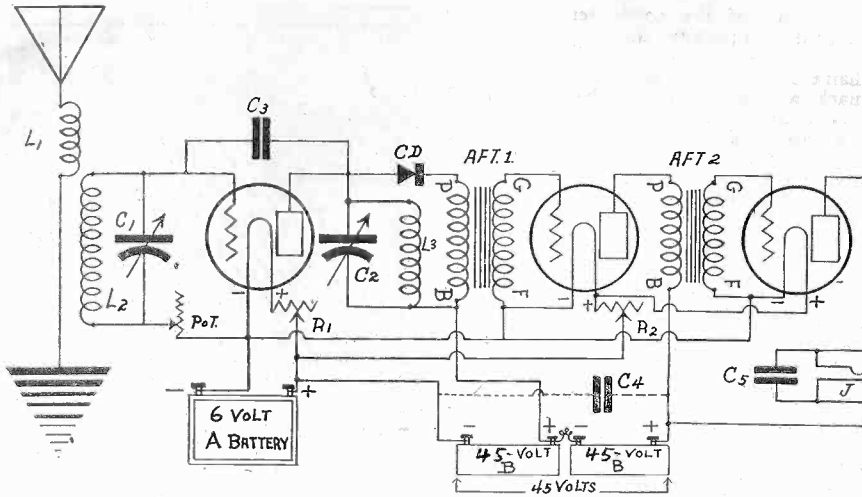

A FAN may build a circuit like this one, which ought to be (and is) selective, and yet will not get selectivity, because of improper aerial. Read what Herman Bernard says of the solution of this problem.

THE PRIMER

By Herman Bernard

Associate, Institute of Radio Engineers

IN THE Big City there are streets of great magnitude, such as Railroad Street and Garment Street. As no city has thirty-two great thoroughfares—New York has only three, Broadway, Fifth Avenue and Park Avenue—radio, as the thirty-second greatest industry in the United States, rates a lane. That is something less than rating a salute, as the ranks of highways are reckoned, but there are other and greater days ahead.



Herman Bernard

I LOOKED over the thoroughfares in the Big City and decided that the most interesting one to me would be Radio Lane. It held forth greater allurements, despite some bucolic aspects, for within its confines resided greater mysteries. Here and there was a Super-Heterodyne mansion, but for the most part the domiciles were not so dignified as to deny every pretense of welcome to an inquiring stranger. It bespoke the radio condition throughout the land, where unpretentiousness and modesty are the earmarks of the majority of receivers. Unlike Automobile Row, where every house was the product of the skilled trades, shacks and cabins in Radio Lane were built by those who lived within as shelter from the monotony to which radio abstinence condemns all hookup agnostics. But there were mansions enough, by way of hopeful interspersal, to remind one that the shack-dweller would not long remain content with his humble abode. There was enough moving in progress from the humbler to the handsomer to stir enthusiastic hopes even in a set manufacturer's breast amid the uncertainty of business in declining Spring.

It struck me, however, that even the humbler places could be made much more like the statelier abodes, and with little work, at that. Therefore I looked over a

patch of aerials and found something there that could be improved. A storage battery here, an inductance there—something was to be said about each in the interests of betterment.

* * *

LET US look at one aerial. From one insulator to the other, this stretch of 7-strand copper wire measures almost 100 feet. Near one insulator some No. 14 insulated wire is scraped and soldered to the aerial, trailing into a window on the ground floor of the house. A wooden arm projects at the cornice and at the tip of this bracket is a round porcelain insulator, "a circle with a hole in it, this serving to keep the No. 14 wire, called the lead-in, from touching the roof. The precaution is an excellent one from a service viewpoint. Also, the rules of the Board of Fire Underwriters require that the lead-in be not nearer than 1 foot from the house, and thus insulated.

A glimpse at the ground wire shows that it connects from a cold-water pipe in the kitchen, up beside a door jamb, around to another room, thence behind a moulding and finally to the set, a total distance of 32 feet. The wire between the corrugated insulators on the roof is 100 feet, the lead-in is 25 feet, and the ground wire measures 32 feet. Total, 157 feet. Now, what does that represent? The length of Hascom Flower's aerial! Nobody ever recommended an aerial of 157 feet for broadcast reception, not even a radio expert. The mistake Mr. Flower made was to consider that the size of one's aerial is the length of wire used for that part of the antenna system most commonly referred to as the aerial. Indeed, if we desired to split hairs, we might even include the pick-up qualities of the very coils in the set, and give them a rating in modified terms of feet, adding that to the aerial length. But at least, whenever anybody recommends a 100-foot aerial, be sure to include the aerial *per se*, and also, and by all means, the length of the lead-in and the lead from ground to set. All that wire helps pick up energy, the ground lead with that sweet gentleness characteristic of the indoor antenna, the outside wire with the grasping spirit and energetic endeavor that leads most of us to employ the exposed type.

Mr. Flower, therefore, had better mend his aerial ways. He had been complaining, neighbors said—for there are gossips along Radio Lane as well as along the Rialto and among the officers of secret societies—that his set was not selective.

His receiver probably was as selective as anyone with reason might hope it to be, and quite as selective as the needs of the day or night required. But he had saddled this inefficient aerial system on it. He had chained the horse to the barn and shouted, "Giddap!"

What should he do, therefore? Tear down part of his aerial? Preferably he should bring the lead from the cold water pipe outside the kitchen window and introduce it through the same window where his aerial lead-in is placed, thus confining to 12 feet a lead that measures 32. If that piece of electrical carpentry takes more time than he can spare from reading the Sunday newspaper comic sheets, then he might safely halve the 100-foot stretch, or even reduce it to 40 feet. He will be overjoyed at the resulting selectivity.

The aerial and ground leads are like respective plates of a physically large condenser, and by their length is largely determined the capacity of that condenser as well as the strain placed upon the grid of the tube. The charging and discharging of this condenser, if the capacity is too high, robs the grid of its effectiveness, and forces one to operate the tubes so far below the point of oscillation as to destroy the inherent advantage of tube employment.

In addition to either of the previously-mentioned ways, he should insert a small fixed condenser in series with the aerial or the ground connection to the set. The condenser may be .00025 mfd., as that is most likely to be the smallest fixed condenser Mr. Flower will have around the house. But if any purchasing is to be done, he should get a .0001 mfd. fixed condenser. The instrument is inserted by cutting the wire between the aerial antenna post and the coil lead that connects thereto, one side of the condenser being soldered to the antenna post, the other to the severed coil terminal. The insertion of this condenser accomplishes electrically what would result from reduction of the actual physical length of the wire on the roof. By the law of condensers, when you insert one in parallel it raises the capacity (hence also the natural wavelength of the system) and if you connect it in series it reduces the capacity. The lessened capacity restores the antenna system efficiency and allows the grids to approach the oscillation point, most easily distinguished as that crucial stage where the tube begins to squeal or contributes total inaudibility.

The physical reduction of the antenna length is to be preferred, for not only does that automatically reduce the capacity, but it also safeguards against the delivery of an overload of signal to the set. The antenna system is an agency for picking up energy, hence while the series condenser may avoid the harmfully excessive discharge, the unnecessary wire on the roof may be regarded as so many extra fielders, picking up balls batted from other diamonds and causing only confusion in one's own game.

* * *

MR. MONTAGUE ASTORFIELD, as you might have guessed, lived in one of the mansions. He personally didn't have any trouble, because he never concerned himself with any of the duties attendant on raising a radio to productive manhood. But his butler, Jukes—butlers are almost invariably called Jukes, though born Smith—was rebuked by his employer on one occasion for radio remission.

Mr. Astorfield, after hard hours at the
(Concluded on page 22)

How to Make a Wavemeter

By Lewis Winner

Radio Engineer

OF all the many radio instruments, the wavemeter plays the most important part in an experimental laboratory. One of the instances when a meter of this type comes into use is before you have completely wired the set with stiff wire so that you will know to just what wavelength your receiver will reach without going to the trouble of adding to or subtracting turns. Then after you have completely wired up your receiver in good fashion, the wavelength to which your receiver will respond can be marked in accordance with the numbers on your dial. There are a great many more ways that one may use the wavemeter, such as for resonance testing, crystal testing and finally finding the wavelength of the open and the closed oscillating circuits. There are many types of wavemeters, including the wavemeter with a galvanometer in series with the coil instead of the buzzer, and the plain wavemeter with a coil in series with the calibrated variable condenser. I am going to discuss the wavemeter with buzzer for excitation purposes, this one being the most practical for receiving set work, and the unilateral wavemeter for the transmitting set.

What to Buy

All the material which is purchased for this instrument should be of the very best. The first thing to purchase is a buzzer, which should be of the Century high-frequency type (Federal Company, Buffalo, N. Y.). A variable .005 mfd. straight line frequency condenser is used, or any other .0005 variable condenser. A dial should be bought for the condenser. On some dials the stations can be marked down with pencil or India Ink (as on the Lacault), so that you will have no trouble in finding the station on your receiver after you have once calculated it with the wavemeter. See Fig. 1. Two dry cells (1½ volts apiece), a piece of bakelite or hard rubber tubing, ¼ lb. of number 18 DCC, a panel 7x10", and finally a cabinet 7x10" inches, or one as the picture shows which will have to be built and be 9" long, 8½" wide, and 8¼" high, which includes the cover, 1" in height. The panel for this cabinet is 5x8½".

Layout of Panel.

The panel is very simple to drill. On the left hand of the cabinet place the two batteries, therefore there is nothing seen on the outside of this part of the panel. Six inches from the left edge of the panel and 3" down from the top of the panel drill a 3/16" hole for the condenser shaft. Lay the template of the condenser over this hole and drill the three other holes for holding the condenser. After this is done and the condenser fits snugly, place the dial on the shaft of the condenser. You will note that on the Lacault dial there are two holes which keep the dial in place. Put the dial on so that the set screws do not hit the set screws of the condenser proper. That will be at an angle of about 67½ degrees away. Drill two holes through the dial holes, using the dial as a template, the holes being ⅛" diameter. One-quarter inch from the top of the panel and 1¼" from the right-hand side of the panel drill a ¼" hole for the binding post, leaving ¼" and drill another hole with the same dimensions for the other binding post. That completes the drilling of the top of the panel. Two holes still having to be drilled for the buzzer which is on the inside of the panel. Mount the condenser. Then turn the panel "inside out" so that you will see

the plates of the condenser. One inch diagonally opposite the second binding post from the right drill a hole ⅛" in diameter, fit the buzzer in its place, and mark another hole for the purpose of holding the buzzer firmly, being sure that the buzzer does not hit the condenser plates, which it will if placed too close. Looking at the condenser with the back facing you and the piece of hard rubber (with 3 set screws) at the bottom, the first screw that you drilled for the buzzer should be 1" away from the center of the last screw on the end plate and the other post will be 2¼" away from the same place. There are seven holes to drill in the top of the panel. After you have placed all the instruments the next thing to do is to wind the excitation coil.

How to Wind the Coil.

Take a piece of tubing 3" in diameter and wind 50 turns of 18 DCC wire in one direction. After winding these turns, which will take up about 2¼" on the form, leave ⅛" and drill a ¼" hole for the binding post, leave 1½" and drill another hole of same dimensions. Put the posts in their respective places and attach the ends of the winding to the posts. DO NOT PUT ANY HOLDING MATERIAL ON THE COIL. That is all there is to the winding of the coil. We are now ready to wire the instrument up.

Study the picture and the schematic diagrams carefully. Holding the buzzer with the adjustment knob towards you, shunt the terminal attached to the frame and the terminal to the right of it with a 1 mfd. Dubilier fixed condenser. Connect the right-hand terminal to the positive end of the battery, and the other end of the battery, which is the negative, to the stationary plates of the variable condenser, the same end going to one binding post. The rotary plates go to the free terminal of the buzzer and to the other binding post. Across the binding posts shunt the coil. See Fig. 1. After finishing the above, we are ready to put the instrument into operation.

The Theory of the Operation of Set

Place the coil in inductive relation to the ground system (Fig. 1), so that radio-frequency oscillations will flow from the coil through the ground to the secondary of the set, which is tuned in resonance with the primary. Set the buzzer going at a very high pitch, which can be done

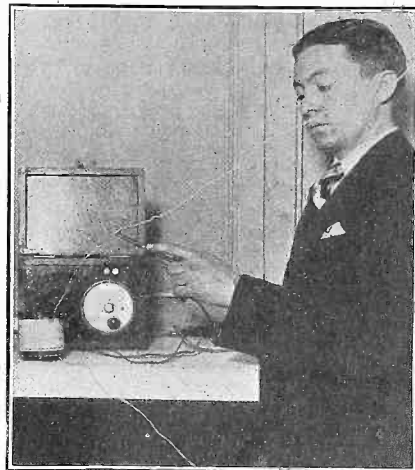


FIG. 1—Joseph Kramer, of 939 Longwood Avenue, Bronx, N. Y. C., showing how to place the wavemeter coil in inductive relation to the ground. The ground wire is seen running through the coil. The wavemeter is in the background. Note the dial on the wavemeter condenser.

by simply moving the little knob of the buzzer to you or away from you. The oscillations given out by the buzzer are transmitted by electromagnetic coupling to the open oscillation circuit through the ground wire. The greatest height of these oscillations will be heard when the tuning devices of that specific circuit are manipulated so that the same constant of oscillation will be had, e. g., the same wavelength in the set as that of the meter. The telephone diaphragm will be actuated greatest when the detector or secondary circuit is in exact resonance with the antenna system. The reason that we use the 1 mfd. condenser across the terminals of the buzzer (magnets of buzzer) is to absorb the counter-electromotive force of the windings and thus prevent sparking at the vibrator, which would cause an uneven tone in the telephones when adjusting for the specific wavelength, and which would make adjustment very difficult. Put your receiver into operation and adjust your tuning elements until you hear the same note in your headphones. The following data are given with relation to the setting of the condenser dial and to the wavelengths thereby obtained, on a 25-foot outdoor antenna, no ground, using

Blind War Veteran Honored on Opening Own Radio Shop



"BLIND JOE" ALONZO, world war veteran, who made a success as a radio expert and received a loving cup and bouquets from admirers when he opened a shop on the East Side, New York City. (Kadel & Herbert).

Testing Receiver's Cycle Range

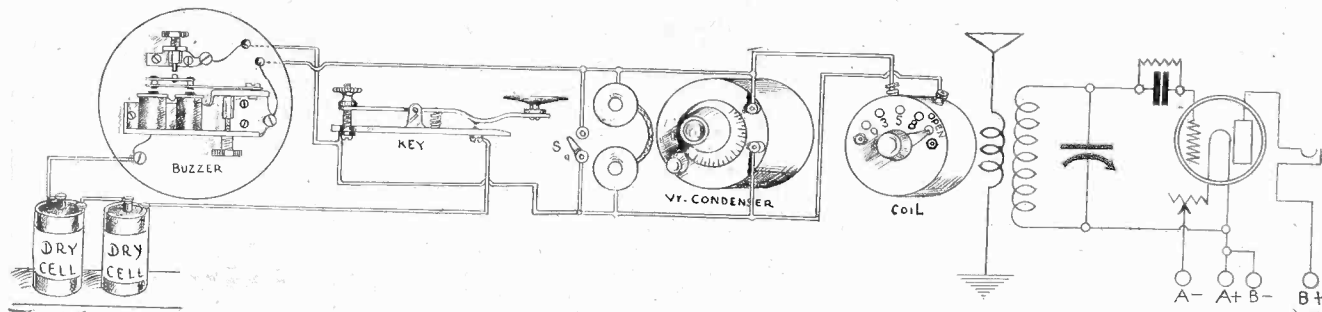


FIG. 4—A picture diagram of the wavemeter for receivers and transmitters. The switch is for closing the circuit. The key is for using the wavemeter as a miniature code transmitter, when using the absorption method of transmission by placing the coil in inductive relation to the antenna. This has a range of about five miles and is called the ICW method of transmission.



THE AUTHOR with the portable wavemeter described his article. Note that the only thing that was carried outside the meter was the special wavemeter coil.

the Lacault condenser and the described coil:

DIAL NUMBER OF CONDENSER OF WAVEMETER	WAVELENGTH IN METERS
0	250
10	275
20	300
30	325
40	350
50	375
60	400
70	425
80	450
90	475
100	500

Adjust condenser dial of wavemeter to 10 and turn dials of receiver until you hear the high-pitched note of buzzer in


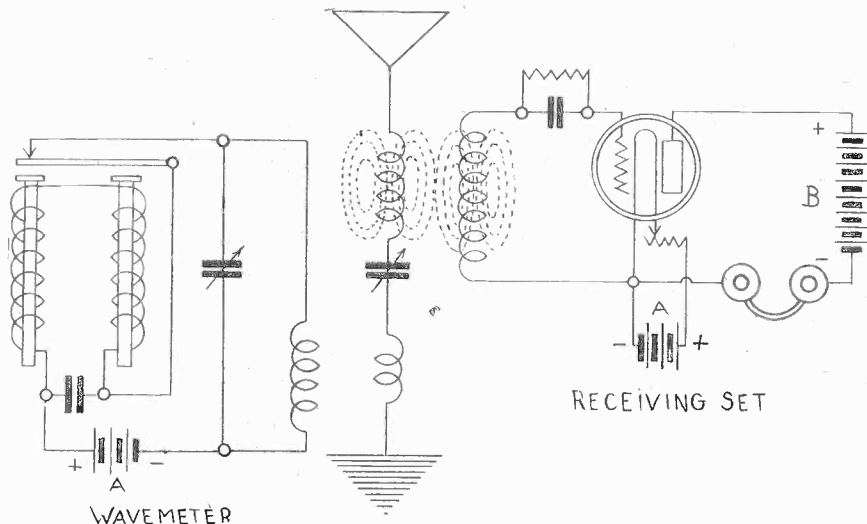


FIG. 5—An electrical diagram of a wavemeter for receivers only. The excitation coil is placed in inductive relation to ground of an ordinary receiving set. Note the fixed condenser (1 mfd.) shunted across buzzer magnets.

telephones. Say at 20 on the wavemeter and 30 on the receiver you hear the note. This is one wavelength. If you think that your set tunes below 250 meters, e. g., if you do not hear buzz at point where you receive your lowest wavelength, take three turns off the wavemeter coil. This will get it down to 220 meters, and so on for the lower waves (to 100 meters). If you tune your set to a point where, say, KYW (536 meters) should come in and you do not hear a buzz, put 8 turns on the meter coil. For the intermediate waves the procedure first mentioned is followed.

How to Calibrate a Transmitter

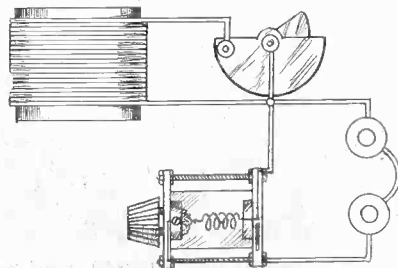The meter just described was for the calibration of receiving instruments only. For transmitting sets, however, we have a very simple arrangement of instruments employing only a crystal, pair of phones and a condenser, the same as used in the wavemeter just described, connected up in unilateral fashion (Fig. 3). Use a 20-turn coil. A crystal used here is a fixed type. DO NOT PLACE COIL TOO



UNILATERAL wavemeter hookup, a crystal detector being used, for transmission only.

NEAR THE TRANSMITTER, AS YOU WILL BURN OUT YOUR CRYSTAL IF THERE IS TOO MUCH ENERGY BEING TRANSMITTED FROM THE SET. Place the coil about a foot away from the ground system, and set the transmitter going. When you hear the note (CW, spark, or ICW) in the telephones of the wavemeter, you may calculate your transmitter to specific wavelengths. The following data are given for the purpose of calibrating your transmitter:

DIAL READING OF THE METER CONDENSER	WAVELENGTH IN METERS
0	100
10	110
20	120
30	130
40	140
50	150
60	160
70	170
80	180
90	190
100	200

Add turns for higher waves; decrease turns for lower waves.

The calibration of your transmitter is very important as the United States Government gives every amateur a specific wavelength to operate on and if the Radio Inspector (R. I.) ever comes up to your house when you least expect it and tests your transmitter with his wavemeter, finding out that you are not toperating at the wavelength assigned, your license is taken away and you have lots of trouble getting another.

Fig. 4 gives the wiring diagram of the wavemeter. (Concluded next week)

Official List of Stations

Complete, Accurate, Up-to-Date

Corrected and revised up to May 26

Station	Owner and Location	Meters	Station	Owner and Location	Meters	Station	Owner and Location	Meters
KDKA	Westinghouse E. & M. Co., E. Pittsburgh, Pa.	309	KFOJ	Moberly High School, Moberly, Mo.	246	KLS	Warner Bros Radio Co, Oakland, Cal.	242
KDLR	Radio Elec. Co., Devils Lake, N. D.	231	KFOL	L. M. Schabfuch, Marengo, Iowa.	234	KLX	Tribune, Oakland, Cal.	508
KDPM	Westinghouse E. & M. Co., Cleveland, Ohio	250	KFON	Echophone Radio Shop, Long Beach, Cal.	234	KLZ	Reynolds Radio Co., Denver, Col.	266
KDYL	Newhouse Hotel, Salt Lake City, Utah	250	KFOO	Latter Day Saints University, Salt Lake City, Utah	261	KMJ	San Joaquin Corp., Fresno, Cal.	234
KDZB	F. E. Seifert, Bakersfield, Cal.	210	KFOR	David City Tire & Elec. Co., David City, Neb.	226	KMO	Love Elec. Co., Tacoma, Wash.	250
KFAB	Nebraska Buick Auto Co., Lincoln, Neb.	240	KFOT	College Hill Radio Club, Wichita, Kan.	231	KNX	Express, Hollywood, Cal.	337
KFAD	McArthur Bros. Merc. Co., Phoenix, Ariz.	360	KFOX	Technical High School, Omaha, Neb.	248	KOA	General Electric Co., Denver, Col.	322
KFAE	State College, Pullman, Wash.	349	KFOY	Beacon Radio Service, St. Pau, Minn.	252	KOB	College of Agri, State College, N. M.	349
KFAF	Western Radio Corp., Denver, Colo.	278	KFPG	Oliver S. Garretson, Los Angeles, Cal.	252	KOP	Detroit Police Department, Detroit, Mich.	278
KFAJ	University of Colorado, Boulder, Colo.	261	KFPL	C. C. Baxter, Dublin, Texas	238	KPO	Hale Brothers, San Francisco, Cal.	429
KFAN	University of Idaho, Moscow, Idaho.	231	KFPM	New Furniture Co., Greenville, Texas.	242	KPPC	Pasadena Presbyterian Church, Pasadena, Cal.	229
KFAU	Boise High School, Boise, Idaho.	275	KFPR	Forestry Department, Los Angeles, Cal.	331	KPRC	Houston Print Co, Houston, Tex.	297
KFAW	Radio Den, Santa Ana, Cal.	214	KFPV	Heintz & Kohlmoos, San Francisco, Cal.	236	KQV	Doubleday Hill Elec. Co., Pittsburgh, Pa.	275
KFBB	F. A. Buttrely Co, Havre, Mont.	275	KFPW	St. John's Church, Cartersville, Mo.	268	KRE	Gazette, Berkeley, Cal.	258
KFBC	W. K. Azbill, San Diego, Cal.	278	KFPY	Symonds Investment Co., Spokane, Wash.	266	KSAC	Kansas State Agricultural College, Manhattan, Kans.	341
KFBE	Horn & Wilson, San Luis Obispo, Cal.	216	KFQA	The Principia, St. Louis, Mo.	261	KSD	Post Dispatch, St. Louis, Mo.	545
KFBG	1st Presbyterian Church, Tacoma, Wash.	250	KFQB	Searchlight Publishing Co., Ft. Worth, Texas	254	KSL	Radio Service Corp., Salt Lake City, Utah	300
KFBK	Kimball Upson Co., Sacramento, Cal.	248	KFQC	Kidd Bros., Taft, Cal.	231	KTHS	New Arlington Hotel, Hot Springs, Ark.	375
KFBL	Leese Bros., Everett, Wash.	224	KFQD	Southern Calif. Radio Ass'n, Los Angeles, Cal.	229	KTW	1st Presbyterian Church, Seattle, Wash.	454
KFBU	Bishop N. S. Thomas, Laramie, Wyo.	270	KFQE	National Guard, Denison, Tex.	252	KUO	Examiner, San Francisco, Cal.	346
KFBC	Nielson Radio Co., Phoenix, Ariz.	238	KFQF	G. S. Carson, Jr., Iowa City, Ia.	224	KUOM	State University of Montana, Missoula, Mont.	245
KFCB	1st Congregational Church, Helena, Mont.	248	KFQG	W. L. Ellis, Oklahoma City, Okla.	210	KWG	Portable Wireless Tel. Co., Stockton, Cal.	248
KFCF	F. A. Moore, Walla Walla, Wash.	256	KFQH	Radio Service Co., Burlingame, Cal.	231	KYW	Westinghouse E. & M. Co., Chicago, Ill.	535
KFCY	Western Union College, Lemars, Iowa.	252	KFQI	W. Riker, Holy City, Cal.	234	KZKZ	Electric Supply Co., Manila, P. I.	270
KFCZ	Central High School, Omaha, Neb.	258	KFQJ	F. C. Knerim, North Bend, Wash.	216	KZM	Western Radio Inst., Oakland, Cal.	241
KFDD	St. Michael's Cathedral, Boise, Idaho.	273	KFQK	Farmer's State Bank, Belden, Neb.	273	KZRQ	Far Eastern Radio, Inc., Manila, P. I.	222
KFDH	University of Arizona, Tucson, Ariz.	268	KFQL	Radio Co., Hollywood, Cal.	226	WAAB	V. Jensen, New Orleans, La.	273
KFDJ	Oregon Agricultural College, Corvallis, Ore.	254	KFRB	Hall Bros. Beverly, Texas.	248	WAAC	Tulane University, New Orleans, La.	275
KFDM	Magnolia Petroleum Co., Beaumont, Texas.	316	KFRC	Paris Dry Goods Co., San Francisco.	268	WAAD	Ohio Mech. Institute, Cincinnati, Ohio	259
KFDX	1st Baptist Church, Shreveport, La.	250	KFRH	The Radio Shop, Grafton, N. D.	268	WAAE	Drovers Journal, Chicago, Ill.	278
KFDY	State College of Agriculture, Brookings, S. D.	273	KFRJ	Men's Club, Grand Forks, N. D.	240	WAAM	I. R. Nelson Co., Newark, N. J.	263
KFDZ	H. O. Iverson, Minneapolis, Minn.	231	KFRK	J. F. Boland, Ft. Sill, Okla.	263	WAAW	Omaha Graft Exchange, Omaha, Neb.	384
KFEC	Meier & Frank Co., Portland, Ore.	248	KFRP	Trinity Church, Redlands, Cal.	211	WABA	Lake Forest University, Lake Forest, Ill.	227
KFEL	Winner Radio Corp., Denver, Colo.	254	KFRQ	Radio Service Co., Portland, Ore.	213	WABJ	Bangor Ry. & Elec. Co., Bangor, Me.	240
KFEQ	J. L. Scroggin, Oak, Neb.	268	KFRU	Etherical Studio, Bristow, Okla.	395	WABL	Agricultural College, Storrs, Conn.	275
KFER	Auto Elec. Service Co., Ft. Dodge, Ia.	231	KFRV	United Churches, Olympia, Wash.	220	WABM	F. E. Doherty Radio Co., Saginaw, Mich.	261
KFEY	Bunker Hill & Sullivan, Kellogg, Idaho.	233	KFRX	J. G. Klemgard, Pullman, Wash.	217	WABN	Ott Radio, Inc., La Crosse, Wis.	244
KFFP	1st Baptist Church, Moberly, Mo.	256	KFRY	College of Agriculture, State College, N. M.	256	WABO	Lake Avenue Baptist Church, Rochester, N. Y.	278
KFFV	Graceland College, Lamoni, Iowa.	250	KFRZ	Tege, N. M. Shop, Hartington, Neb.	222	WABQ	Haverford College Radio Club, Haverford, Pa.	261
KFGC	Louisiana State University, Baton Rouge, La.	268	KFRZ	The Electric Shop, Hartington, Neb.	222	WABR	Scott High School, Toledo, O.	263
KFGD	College for Women, Chickasha, Okla.	252	KFSY	The Van Blaricom Co., Helena, Mont.	248	WABU	Victor Talking Machine Co., Camden, N. J.	226
KFGH	Leland Stanford Junior University, Stanford University, Cal.	270	KFUJ	Hoppert P. and H. Co., Breckenridge, Minn.	242	WABW	College of Wooster, Wooster, O.	207
KFGQ	Crary Co., Boone, Iowa.	226	KFUL	T. Goggan & Bro., Galveston, Tex.	258	WABX	H. B. Joy, Mt. Clemens, Mich.	254
KFHA	Western State College, Gunnison, Colo.	252	KFUM	W. D. Corley, Colorado Springs, Colo.	242	WABY	John Magaldi, Philadelphia, Pa.	242
KFHL	Penn College, Oskaloosa, Iowa.	240	KFUV	Concordia Theo. Seminary, St. Louis, Mo.	545	WABZ	Coliseum Place Baptist Church, New Orleans, La.	275
KFI	E. C. Anthony, Inc., Los Angeles, Cal.	469	KFVU	Leandro, Cal.	224	WADC	Allen Theatre, Akron, Ohio.	258
KFIF	Benson Institute, Portland, Ore.	248	KFVW	G. P. Ward, Springfield, Mo.	252	WADF	A. B. Parfet Co., Port Huron, Mich.	238
KFIO	North Central High School, Spokane, Wash.	265	KFVX	Irvine H. Bouchard, Butte, Mont.	254	WAHG	A. H. Grebe Co., Richmond Hill, N. Y.	316
KFIQ	1st Methodist Church, Yakima, Wash.	256	KFVY	Y. M. C. A., Virginia, Minn.	248	WAIB	A. H. Waite & Co., Taunton, Mass.	229
KFIU	Alaska Elec. Co., Juneau, Alaska.	226	KFVZ	G. J. Bensberg, Camden, Ark.	242	WAIC	Hubbard & Co., Minneapolis, Minn.	244
KFIZ	Daily Commonwealth, Fond du Lac, Wis.	273	KFVD	Chas. & W. J. McWhinnie, San Pedro, Cal.	205	WAID	American Radio Res. Corp., Medford Hillside, Mass.	261
KFJB	Marshall Elec. Co., Marshalltown, Ia.	248	KFVE	Film Corp., St. Louis, Mo.	240	WAIA	Purdue University, West Lafayette, Ind.	273
KFJC	R. B. Fegan, Junction City, Kan.	219	KFVF	Clarence B. Juneau, Hollywood, Cal.	208	WAIB	State Police, Harrisburg, Pa.	276
KFJD	National Radio Co., Oklahoma City, Okla.	261	KFVG	1st Meth-Epis. Church, Independence, Kan.	236	WABJ	Star Telegram, Fort Worth, Tex.	476
KFJI	Liberty Theatre, Astoria, Ore.	246	KFVH	Herbert Wham, Manhattan, Kans.	219	WBAV	Erner Hopkins Co., Columbus, O.	294
KFJM	University of N. D., Grand Forks, N. D.	278	KFVI	56th Cav. Brigade, Houston, Tex.	248	WBAW	J. H. Stenger, Jr., Wilkes-Barre, Pa.	256
KFJR	Ashley C. Dixon & Son, Portland, Ore.	253	KFVJ	First Baptist Church, 2nd and San Antonio St., San Jose, Cal.	226	WBB	Plymouth Congregational Church, Newark, O.	226
KFJX	State Teachers College, Cedar Falls, Ia.	268	KFVK	Sacramento Chamber of Commerce, cor. 10th and J. Sts., Sacramento, Cal.	248	WBBG	I. Vermilya, Mattapoisett, Mass.	248
KFJY	Funwall Radio Co., Ft. Dodge, Iowa.	254	KFVL	Richard F. Lussier, 1st Lt. Hd. 5th Inf. Brigade, U.S.A., Vancouver Barracks, Vancouver, Wash.	231	WBBL	Grace Covenant Presbyterian Church, Richmond, Va.	229
KFJZ	W. E. Branch, Ft. Worth, Tex.	246	KFVO	F. M. Henry, Kirksville, Mo.	226	WBBM	H. T. Atass, Chicago, Ill.	226
KFKA	State Teachers College, Greeley, Colo.	273	KFVW	Moonlight Ranch, Denver, Colo.	246	WBBP	Petoskey High School, Petoskey, Mich.	238
KFKB	Brinkley Jones Hospital, Ass'n, Milford, Kans.	273	KFWA	Browning Bros. Co., Ogden, Utah.	214	WBBR	Peoples Pulpit Ass'n, Rossville, N. Y.	273
KFKQ	Conway Radio Laboratory, Conway, Ark.	273	KFWB	Warner Bros. Pictures, Inc., Hollywood, Cal.	252	WBBT	1st Baptist Church, New Orleans, La.	252
KFKU	University of Kansas, Lawrence, Kans.	275	KFWC	L. E. Wall & C. S. Myers, Upland, Cal.	211	WBBU	Jenks Motor Sales Co., Monmouth, Ill.	224
KFKX	Westinghouse E. & M. Co., Hastings, Neb.	288	KFWD	Art Light Co., Arkadelphia, Ark.	266	WBBV	Johnstown Radio Co., Johnstown, Pa.	248
KFLB	Signal Elec. Mfg. Co., Menominee, Mich.	248	KFWF	St. Louis To. Center, Lindell St., St. Louis, Mo.	214	WBBW	Ruffner City High School, Norfolk, Va.	222
KFLP	Eyervette M. Foster, Cedar Rapids, Ia.	256	KFYN	Carl E. Bagley, Welcome, Minn.	227	WBBY	Washington Light Infantry, Charleston, S. C.	268
KFLR	University of N. M., Albuquerque, N. M.	254	KFZ	The Ledger, Tacoma, Wash.	250	WBBZ	N. B. Watson, Indianapolis, Ind.	238
KFLU	Ro Grande Radio Sup. Co., San Benito, Texas	236	KGO	General Electric Company, Oakland, Cal.	361	WBCN	Southtown Economist, Chicago, Ill.	266
KFLV	Swedish Evangelist Church, Rockford, Ill.	229	KGU	M. A. Mulrony, Honolulu, Hawaii.	270	WBDC	Baxter Laundry Co., Grand Rapids, Mich.	256
KFLX	George R. Clough, Galveston, Texas.	229	KGV	The Oregonian, Portland, Ore.	492	WBES	Bliss Electrical School, Takoma Park, Md.	222
KFLZ	Atlantic Auto Co., Atlantic, Iowa.	273	KGY	St. Martin's College, Lacey, Wash.	246	WBOQ	A. H. Grebe & Co., Richmond Hill, N. Y.	236
KFMB	Christian Churches of Little Rock, Little Rock, Ark.	254	KHJ	The Times, Los Angeles, Cal.	405	WBR	State Police, Butler, Pa.	203
KFMO	University of Ark., Fayetteville, Ark.	301	KHQ	Louis Wasmser, Seattle, Wash.	273	WBRE	Baltimore Radio Ex., Wilkes-Barre, Pa.	231
KFMR	Morningside College, Sioux City, Iowa.	261	KJBS	J. Brunton & Sons Co., San Francisco, Cal.	236	WBSD	P. W. May, Inc., Newark, N. J.	252
KFMT	Dr. G. W. Young, Minneapolis, Minn.	263	KJR	Northwest Radio Co., Seattle, Wash.	384	WBTE	Southern Radio Co., Charlotte, N. C.	275
KFMW	M. G. Sataren, Houghton, Mich.	266	KJS	Bible Institute, Los Angeles, Cal.	294	WBZ	Westinghouse E. & M. Co., Springfield, Mass.	333
KFMX	Carleton College, Northfield, Minn.	337	KLDS	Reorganized Church of Jesus Christ of Latter Day Saints, Independence, Mo.	268	WCAD	St. Lawrence University, Canton, N. Y.	263
KFN	Henry Field Seed Co., Shenandoah, Iowa.	266				WCAE	Kaufman & Baer, Pittsburgh, Pa.	461
KFNG	Wooten Radio Shop, Coldwater, Miss.	254						
KFNJ	Teachers College, Warrensburg, Mo.	234						
KFNL	Union High School, Paso Robles, Cal.	240						
KFNV	L. A. Drake, Santa Rosa, Cal.	227						
KFNY	Montana Phono Co., Helena, Mont.	248						
KFOA	Rhodes Company, Seattle, Wash.	455						
KFOC	1st Christian Church, Whittier, Cal.	236						

Station	Owner and Location	Meters
WCAG	C. R. Randall, New Orleans, La.	268
WCAH	Entreklin Electric Co., Columbus, O.	266
WCAJ	Norwalk Wesleyan University, Norwalk, Conn.	275
WCAL	St. Olaf College, Northfield, Minn.	337
WCAO	Sanders & Stayman, Baltimore, Md.	275
WCAP	C. & P. Tel. Co., Washington, D. C.	469
WCAR	Southern Radio Corp., San Antonio, Texas	263
WCAT	School of Mines, Rapids City, S. D.	240
WCAU	Durham & Co., Philadelphia, Pa.	278
WCAX	University of Vermont, Burlington, Vt.	250
WCAY	Civic Broadcasting Ass'n, Milwaukee, Wis.	266
WCAZ	Carthage College, Carthage, Ill.	246
WCBA	Queen City Radio, Allentown, Pa.	254
WCBC	University of Michigan, Ann Arbor, Mich.	229
WCBD	W. G. Vollva, Zion, Ill.	345
WCBE	Uhalt Radio Co., New Orleans, La.	263
WCBG	H. S. Williams, Mayfield, Ky.	268
WCBH	University of Mississippi, Oxford, Miss.	242
WCBJ	Nicoll, Duncan & Rush, Bemis, Tenn.	240
WCBK	J. C. Mans, Jennings, La.	244
WCBL	Northern Radio Mfg. Co., Houlton, Me.	266
WCBM	Hotel Chateaux, Baltimore, Md.	229
WCBQ	1st Baptist Church, Nashville, Tenn.	242
WCBR	C. H. Messter (Portable), Providence, R. I.	205
WCBU	Arnold Wireless Co., Arnold, Pa.	220
WCBV	Forks Electrical Shop, Buck Hill Falls, Pa.	231
WCBZ	Neutrowound Radio Mfg. Co., Chicago Heights, Ill.	217
WCCO	Washburn Crosby Co., Minneapolis, Minn.	416
WCEE	C. E. Erbstein, Elgin, Ill.	275
WCKE	Stix Beer & Fuller Co., St. Louis, Mo.	273
WCM	Texas Market Department, Austin, Texas	268
WCOS	Wittenberg College, Springfield, Ohio	248
WCST	C. T. Sherer Co., Worcester, Mass.	268
WCUX	Clark University, Worcester, Mass.	238
WCW	Detroit Free Press, Detroit, Mich.	517
WDAE	Tampa Daily News, Tampa, Fla.	273
WDAF	Kansas City Star, Kansas City, Mo.	366
WDAG	J. L. Martin, Amarillo, Tex.	263
WDAH	Trinity Methodist Church, El Paso, Texas	268
WDAY	Radio Equipment Corp., Fargo, N. D.	244
WDBE	Kirk, Johnson & Co., Lancaster, Pa.	258
WDBF	Gilham-Schoen Elec. Co., Atlanta, Ga.	278
WDBP	R. G. Phillips, Youngstown, O.	222
WDBJ	Richardson Wayland Elec. Co., Roanoke, Va.	229
WDBK	M. F. Broz, Furn., Cleveland, O.	227
WDBL	Department of Markets, Stevens Point, Wis.	278
WDBO	Rollins College, Winter Park, Fla.	240
WDBP	State Normal School, Superior, Wis.	261
WDBQ	Morton Radio Supply Co., Salem, N. J.	234
WDBR	Tremont Temple Baptist Church, Boston, Mass.	261
WDBS	S. M. K. Radio Corp., Dayton, O.	275
WDBW	Radio Den, Columbia, Tenn.	268
WDBX	Dyckman Radio Shop, New York, N. Y.	233
WDBY	North Shore Congregational Church, Chicago, Ill.	258
WDBZ	Boy Scouts of America, Kingston, N. Y.	233
WDM	Church of the Covenant, Washington, D. C.	270
WDOD	Chattanooga Radio Co., Chattanooga, Tenn.	256
WDRG	Doolittle Radio Corp., New Haven, Conn.	268
WDWF	Dutee Wilcox Flint, Inc., Cranston, R. I.	440.9
WDZ	J. L. Bush, Tuscola, Ill.	278
WEAA	F. D. Fallain, Flint, Mich.	234
WEAF	A. T. & T. Co., New York, N. Y.	492
WEAH	Wichita Board of Trade, Wichita, Kans.	268
WEAI	Cornell University, Ithaca, N. Y.	254
WEAJ	University of South Dakota, Vermillion, S. D.	278
WEAM	Borough of North Plainfield, N. Plainfield, N. J.	261
WEAN	Shepard Co., Providence, R. I.	270
WEAO	Ohio State University, Columbus, O.	294
WEAR	Goodyear T. and R. Co., Cleveland, O.	389
WEAU	Davidson Bros. Co., Sioux City, Ia.	275
WEAY	Iris Theatre, Houston, Texas	270
WEBA	The Electric Shop, Highland Park, N. J.	233
WECB	W. C. Bridges, Superior, Wisc.	242
WEDB	Elec. Equipment & Service Co., Anderson, Ind.	246
WEEB	Roy W. Waller, Cambridge, Ohio	234
WEEF	Edgewater Beach Hotel, Chicago, Ill.	370
WEBJ	Third Avenue R. R. Co., New York, N. Y.	273
WEBK	Grand Rapids Radio Co., Grand Rapids, Mich.	242
WEBL	Radio Corp. of Ama. (Portable)	226
WEBM	Radio Corp. of Ama., Portable Mobile Station	226
WEBP	E. B. Peardon, New Orleans, La.	280
WEBQ	Tate Radio Co., Harrisburg, Ill.	226
WEBR	H. H. Howell, Buffalo, N. Y.	240
WEBT	Dayton High School, Dayton, Ohio	256
WEBW	Beloit College, Beloit, Wisc.	268
WEBZ	Savannah Radio Corp., Savannah, Ga.	234
WEEI	Wilson Electric Illuminating Co., Boston, Mass.	476
WEMC	Emma. Missionary College, Berrien Springs, Mich.	286
WENN	Al-Amer. Radio Corp., Chicago, Ill.	266
WEW	St. Louis University, St. Louis, Mo.	248
WFAA	Dallas News & Journal, Dallas, Texas	476

Station	Owner and Location	Meters
WFAM	The Times, St. Cloud, Minn.	273
WFAV	University of Nebr., Lincoln, Nebr.	275
WFB	Eureka College, Eureka, Ill.	240
WFB	1st Baptist Church, Knoxville, Tenn.	250
WFB	Gethsemane Baptist Church, Philadelphia, Pa.	234
WFBE	J. V. De Walle, Seymour, Ind.	226
WFBG	W. F. Gable Co., Altoona, Pa.	278
WFBH	Concourse Radio Corp., New York, N. Y.	273
WFB	Galvin Radio Supply Co., Camden, N. J.	236
WFB	St. Johns University, Collegeville, Minn.	236
WFB	Dartmouth College, Hanover, N. H.	256
WFB	Onondaga Hotel, Syracuse, N. Y.	252
WFB	Merchants Lighting Co., Indianapolis, Ind.	268
WFB	Radio Sales & Service Co., Bridge-water, Mass.	226
WFB	Wynne Radio Co., Raleigh, N. C.	252
WFB	Maryland National Guard, Baltimore, Md.	254
WFB	Signal Corps, Ft. Ben Harrison, Ind.	258
WFB	Knox College, Galesburg, Ill.	254
WFI	Strawbridge & Clothier, Philadelphia, Pa.	395
WFK	Francis K. Bridgman, Chicago, Ill.	217
WGA	Lancaster Elec. Supply Co., Lancaster, Pa.	248
WGA	W. G. Patterson, Shreveport, La.	263
WGA	The Tribune, South Bend, Ind.	275
WGB	Jones Elec. & Radio Co., Baltimore, Md.	254
WGB	H. H. Carman, Freeport, N. Y.	244
WGB	1st Baptist Church, Memphis, Tenn.	266
WGB	The Finke Furniture Co., Evansville, Ind.	217
WGB	Breitenbach's Radio Shop, Thrifton, Pa.	226
WGB	Fall River Herald Pub. Co. (New England States Portable)	210
WGB	Frank S. Megargee, Scranton, Pa.	240
WGB	L. W. Campbell, Johnstown, Pa.	248
WGB	Elyria Radio Ass'n., Elyria, Ohio	227
WGB	T. N. Saaty, Providence, R. I.	234
WGB	Hub Radio Shop, La Salle, Ill.	256
WGB	Dr. Rosa Artan, San Juan, P. R.	275
WGB	Stout Institute, Menomonie, Wis.	234
WGB	Marshfield Broadcasting Association, Marshfield, Wis.	229
WGB	Gimbel Brothers, New York, N. Y.	316
WGB	Furman University, Greenville, S. C.	236
WGB	Valley Theatre, Spring Valley, Ill.	256
WGB	University of Maine, Orono, Maine	252
WGB	Progress Sales Co., New Lebanon, Ohio	219
WGN	The Tribune, Chicago, Ill.	370
WGR	Federal Telephone Mfg. Co., Buffalo, N. Y.	319
WGS	Ga. School of Tech., Atlanta, Ga.	274
WGY	General Elec. Co., Schenectady, N. Y.	380
WHA	University of Wisconsin, Madison, Wis.	535
WHAD	Marquette University, Milwaukee, Wis.	275
WHAG	University of Cincinnati, Cincinnati, Ohio	233
WHAM	University of Rochester, Rochester, N. Y.	278
WHAP	Wm. H. Taylor Finance Corp., Brooklyn, N. Y.	240
WHAR	F. P. Cooks Sons, Atlantic City, N. J.	275
WHAS	The Courier Journal-Times, Louisville, Ky.	400
WHA	Wilmington Elec. Spec. Co., Wilmington, Del.	266
WHA	Reinscler Polytechnic Institute, Troy, N. Y.	380
WHB	Sweeney School Co., Kansas City, Mo.	366
WHB	Shaffer Music House, Oil City, Pa.	250
WHB	Hebal's Store, Stevens Point, Wis.	240
WHB	Rev. E. P. Graham, Canton, Ohio	254
WHB	Charles W. Howard, Bellefontaine, Ohio	222
WHB	Beardsley Specialty Co., Rock Island, Ill.	222
WHB	John S. Skane, Harrisburg, Pa.	231
WHB	Culver Military Academy, Culver, Ind.	222
WHB	Chesaning Electric Co., Chesaning, Mich.	227
WHB	Laver Auto Co., Ft. Wayne, Ind.	234
WHB	Franklin St. Garage, Ellsworth, Me.	231
WHB	J. H. Slusser, Logansport, Ind.	220
WHB	C. L. Carroll (Portable), Chicago, Ill.	233
WHB	1st Ave. Methodist Church, St. Petersburg, Fla.	258
WHB	Y. M. C. A., Providence, R. I.	231
WHB	Johnstown Auto Co., Johnstown, Pa.	256
WHB	St. John's M. E. Church, Memphis, Tenn.	233
WHB	Scientific E. & M. Co., Cincinnati, O.	216
WHB	E. W. Locke, Mechanicsburg, Ohio	208
WHB	Thos. W. Tizzard, Jr., Downers Grove, Ill.	207
WHB	B. L. Bing's Sons, Anderson, Ind.	219
WHB	Ray's Radio Shop, Columbus, Ga.	244
WHB	D. R. Kienzle, Philadelphia, Pa.	216
WHB	J. W. Bowers, Punxsutawney, Pa.	213
WHB	St. Norbert's Coll., West DePere, Wis.	250
WHI	Wm. Hood Dunwoody Ind. Inst., Minneapolis, Minn.	278
WHI	Hickson Elec. Co., Rochester, N. Y.	258
WHI	Radio Co., Cleveland, Ohio	273
WHI	George Schubei, New York, N. Y.	361
WHI	Bankers Life Co., Des Moines, Ia.	526
WHI	Radiophon Corp., Deerfield, Ill.	238
WHI	H. R. Miller, Philadelphia, Pa.	450
WHI	Journal Stockton Co., Omaha, Nebr.	278
WHI	Home Elec. Co., Burlington, Iowa	254
WHI	Capital Times, Madison, Wis.	236
WHI	L. M. Tate Post, V. F. W., St. Petersburg, Fla.	222

Station	Owner and Location	Meters
WIBH	Elite Radio, New Bedford, Mass.	210
WIB	Fredek. B. Zittel, Flushing, N.Y.	219
WIB	C. L. Carrell, Chicago (portable)	216
WIB	Univ. of Toledo, Toledo, O.	205
WIB	Nelson Bros., Chicago, Ill.	226
WIB	Elite Radio Stores, New Bedford, Mass.	210
WIL	Benson Radio Co., St. Louis, Mo.	273
WIP	Gimbel Brothers, Philadelphia, Pa.	508
WJAD	Jackson's Radio Elec. Co., Waco, Tex.	353
WJAG	Norfolk Daily News, Norfolk, Ind.	270
WJAK	Rev. C. L. White, Greentown, Ind.	254
WJAM	D. M. Perham, Cedar Rapids, Ia.	258
WJAR	The Outlet Co., Providence, R. I.	306
WJAS	Pittsburgh Radio Supply House, Pittsburgh, Pa.	275
WJAZ	Zenth Radio Corp., Chicago, Ill.	268
WJBC	Hummer Furniture Co., 2nd and Jolet Sts., La Salle, Ill.	234
WJBD	Ashland Broadcasting Committee, Ashland, Wis.	233
WJD	Dennison University, Granville, O.	317
WJJD	Loyal Order of Moose, Mooschoert, Ill.	303
WJY	Radio Corp. of Ama., New York, N. Y.	405
WJZ	Radio Corp. of Ama., New York, N. Y.	454
WKAA	H. F. Paar, Cedar Rapids, Iowa	278
WKAP	D. W. Flint, Cranston, R. I.	234
WKAQ	Radio Corp. of Porto Rico, San Juan, P. R.	341
WKAR	Mich. Agricultural College, Lansing, Mich.	285
WKAV	Laconia Radio Club, Laconia, N. H.	210
WKBE	K. & B. Electric Co., Webster, Mass.	231
WKRC	Kodel Radio Corp., Cincinnati, O.	336
WKY	WKY Radio Shop, Oklahoma City, Okla.	275
WLAL	1st Presbyterian Church, Tulsa, Okla.	250
WLAP	W. V. Jordan, Louisville, Ky.	275
WLAX	Greencastle Comm. Broad. Sta., Greencastle, Ind.	231
WLB	University of Minneapolis, Minneapolis, Minn.	278
WLBL	Wisconsin Department of Markets, Stevens Point, Wis.	278
WLIT	Lit Brothers, Philadelphia, Pa.	195
WLJ	Sears Roebuck Co., Chicago, Ill.	345
WLW	Crosley Radio Corp., Cincinnati, O.	422
WMA	C. B. Meredith, Cazenovia, N. Y.	275
WMA	Round Hills Radio Corp., Dartmouth, Mass.	360
WMA	Norton Laboratory, Lockport, N. Y.	266
WMA	1st Baptist Church, Columbus, Ohio	278
WMA	Chicago Daily News, Chicago, Ill.	448
WMA	Kings Highway Presbyterian Church, St. Louis, Mo.	248
WMA	Mercer University, Macon, Ga.	261
WMB	Trianon Ball Room, Chicago, Ill.	250
WMB	Fleetwood Hotel, Miami Beach, Fla.	384
WMC	The Commercial Appeal, Memphis, Tenn.	506
WMC	Hotel McAlpin, N. Y. C.	341
WMU	Doudeley, Hill Elec. Co., Washington, D. C.	261
WNAB	Shepard stores, Boston, Mass.	250
WNAC	Shepard Stores, Boston, Mass.	280
WNAD	University of Okla., Norman, Okla.	254
WNAL	Omaha Central High School, Omaha, Nebr.	258
WNAP	Wittenberg College, Springfield, O.	248
WNAR	1st Christian Church, Butler, Mo.	231
WNAT	Lenning Bros. Co., Philadelphia, Pa.	250
WNAX	Dakota Radio App. Co., Yankton, S. D.	244
WNJ	Radio Shop, Newark, N. J.	233
WNYC	Municipal Station, New York, N. Y.	526
WOAC	Page Organ Co., Lima, Ohio	261
WOAI	South East Equipment So., San Antonio, Texas	395
WOAN	Vaughan Con. of Music, Lawrenceburg, Tenn.	283
WOAW	Woodmen of the World, Omaha, Neb.	526
WOAX	F. J. Wolf, Trenton, N. J.	240
WOC	Palmer School of Chiro, Davinport, Ia.	484
WODA	Odea Radio, Paterson, N. J.	203
WOCL	Hotel Jamestown, Jamestown, N. Y.	275
WOI	Iowa State College, Ames, Iowa	270
WOO	John Wanamaker, Philadelphia, Pa.	508
WOQ	Unity School of Christianity, Kansas City, Mo.	278
WOR	L. Bamberger & Co., Newark, N. J.	405
WORD	Peoples Pulpit Assn., Batavia, Ill.	275
WOS	Mo. State Marketing Bureau, Jefferson City, Mo.	441
WPAK	N. D. Agricultural College, Agricultural College, N. D.	275
WPAZ	Dr. John R. Koch, Charleston, W. Va.	268
WPG	Municipality, Atlantic City, N. J.	300
WPSC	Penn State College, State College, Pa.	261
WQAA	H. A. Beale, Jr., Parkersburg, Pa.	228
WQAC	Gish Radio Service, Amarillo, Texas	234
WQAE	Moore Radio News Station, Springfield, Vermont	246
WQAM	Electric Equipment Co., Miami, Fla.	268
WQAN	The Scranton Times, Scranton, Pa.	250
WQAO	Calvary Baptist Church, New York, N. Y.	360
WQAS	Prince Walter Co., Lowell, Mass.	252
WQJ	Calumet Rainbo Broadcasting Co., Chicago, Ill.	448
WRAA	Radio Institute, Houston, Texas	256
WRAF	Radio Club, Inc., Laporte, Ind.	224
WRAG	Economy Light Co., Escanaba, Mich.	256
WRAL	Northern States Power Co., St. Croix Falls, Wisc.	248
WRAM	Lombard College, Galesburg, Ill.	244
WRAN	Black Hawk Elec. Co., Waterloo, Ia.	236
WRAP	Antioch College, Yellow Springs, O.	263
WRAW	Avenue Radio Shop, Reading, Pa.	238

[Concluded on page 22. Cut out strip on page 22 and paste here, for convenient 1-sheet station directory.]

THE RADIO UNIVERSITY

A QUESTION and Answer Department conducted by RADIO WORLD for its Readers by its Staff of Experts. Address Letters to The Radio University, RADIO WORLD, 1493 Broadway, New York City.

KINDLY ADVISE me if the Acme R2, R3 and R4 radio-frequency transformers, can be used in the "Powerful 3-Tube Reflex," described in the May 23 issue of RADIO WORLD.

No. This circuit called for variably-tuned coils.

KINDLY tell me if an Amperite for a WD11 will work three UV199s.—Frank Raphaelian, 54 Wadsworth Terrace, N. Y. C.

No. Use the 199 tube type (for 4½- or 6-volt sound, depending on your battery), one Amperite for each tube.

DURING THE period of Herman Bernard's broadcasting from WGBS, Friday, at 7 P. M., (316 meters), I switched off to WNYC and could distinctly hear the talk of Mr. Bernard. What is the cause of this?—Wm. H. Ewen, Vincetown, N. J.

That was a harmonic of WGBS, around 526 meters.

I HAVE made the loop as designed by Frank Freer in the May 16 issue of RADIO WORLD, and connected it to the antenna post of my set, finding that I do not get good results.—E. W. Link, 4914 Woodland Ave., Philadelphia, Pa.

Disconnect the coupling coil which is attached to the antenna and shunt the loop with a .005 mfd. variable condenser, connecting the both ends of the loop to the present antenna post of the set. Ground to the ground post.

WHENEVER I try to add radio-frequency to any set I always fail. Could you tell me how to obtain success when adding RF to any set?—A. Richardson, Conklingville, N. Y.

Follow Herman Bernard's directions for the Diamond of the Air (April 4, 11 and 25.)

I NOTE that in the 1925 I-A portable, published in the March 28 issue of RADIO WORLD, the dimensions on the rotor and the stator of the coil seem erroneous.—W. Lehman, Gibbon, Minn. Look at the template. Also see April 18 issue of RADIO WORLD.

PLEASE give a hook-up of a 2-step AF amplifier.—J. C. Carlton, Beacon, N. Y. Fig. 154 shows the diagram.

CAN THE loop as described by Frank Freer in the May 7 issue of RADIO WORLD be used with great success on the Diamond of the Air?—Geo. Sassman, 811 E. Russell St., Philadelphia, Pa. Yes.

I HAVE built the "Crystal Set That Gets DX" published in the Dec. 6 issue of RADIO WORLD, and get fine results on the high waves. Why can't I get the stations which are on low waves?—F. H. Quade, 706 Eashwood, Santa Ana, Cal.

In the May 16th issue the data that you requested was published.

WHERE CAN I get a good book on the fundamentals of radio?—Wm. J. Todd, Ogden, Utah. Send a note requesting all the pamphlets on the data that you want to the Superintendent of Documents, Government Printing Office, Washington, D. C., who will send you a list of the free pamphlets that they have, also the list of books for which charge is made.

I AM about to install a new antenna and would like to know if there is one that will reduce static and extraneous noises and also be simple to install.—B. C. Bohannan, Long Beach, Cal.

The Kane Antenna Co., Dept. W, Houquiam, Washington, makes just the thing you need. This can be purchased complete, with drawings and data as how to install, for \$14.

WHEN I put my finger on the plate and grid posts of the audio-frequency transformer I get a pronounced whistle. Could you please tell me how to cure this?—Louis Poster, 1070 Washington Ave., Bronx.

Place a .001 mfd. fixed condenser across the secondary of your first and second AFT.

THE CONDENSER which is shunted across the loop of my Super-Heterodyne is very broad in tuning.—Dr. F. Waitzfelder, 4224 Clayton Ave., Los Angeles, Cal.

Decrease the number of turns on your loop, also put a .001 mfd. fixed condenser across the loop.

I HAVE a milliammeter in the plate circuit and it does not show any current flowing. Is this the correct way in which the set should work?—D. M. Piyor, Muzquz, Cont.

No. If there is no current flowing through the plate circuit you may be sure that the tube is not in working order, as the flow of current in the plate circuit is the important factor in determining the amplification factor of the tube. If you have the same amount of B battery on all your tubes, and all the tubes are of the same type, there is no reason that the meter should not show a flow of current of nearly equal strength in all tubes. It cannot be equal because there are always some physical differences in the plate construction (plate a bit larger or smaller) which change the flow of current, but not enough sometimes to be noticed unless you detect the least wiggle of the needle on the meter.

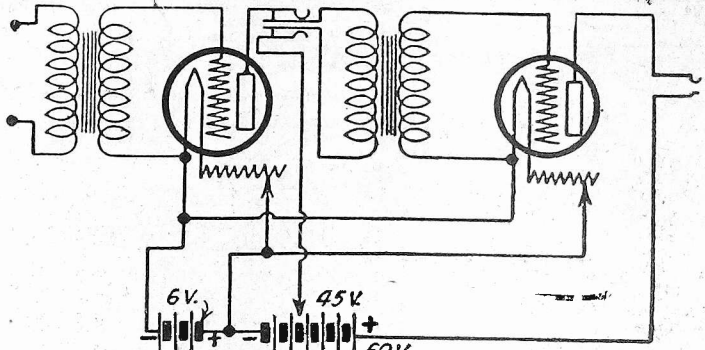


FIG. 154—The 2-step audio-frequency amplifier. The both AFT should be of the low ratio type and matched, or the first high, the second low. UV201As are used with 6-ohm rheostats. A double-circuit jack is used for first step and a single-circuit jack last step (second audio). Note that the F of AFT is connected to the A— and not to A+. If the amplifier distorts, shunt a .001 mfd. condenser across primary winding of either or both AFT.

I HAVE built the Benson Super-Heterodyne which was published in the March 7 edition, and have obtained good results as far as volume is concerned, but it is not selective. Could you help me out of this trouble?—A. A. Shore, 3216 Monument Ave., Philadelphia, Pa.

Reverse the secondary of the radio-frequency transformer. Decrease number of turns on loop or antenna. Ground the negative side of the A battery.

WILL YOU please give me the data on how to make a coupling coil for use with antenna in the Diamond of the Air, the circuit published in the April 4, 11 and 18 issues of RADIO WORLD?—P. Flynn, 2609-B. St. Urbain St., Montreal, Quebec, Canada.

Wind coil on a form 3" diameter tubing, with No. 22 DCC., 10 turns for primary, leave ¼", 50 turns for secondary, and shunt a .0005 mfd. variable condenser across secondary.

COULD YOU please state where I can purchase a complete list of parts for the Presley Super-Heterodyne, which was published in the April 18 issue of RADIO WORLD. How much will these parts cost?—Elza Powell, 330 N. Oakland Ave., Indianapolis, Ind.

Write to the Wallace Radio Company, Inc., 135 Liberty St., New York City, and to the Superadio Co.

REFERRING to the radio receiver described by Brewster Lec in the May 16 issue of RADIO WORLD, would you please answer following questions:—1. Will it cover all wavelengths? 2. Can 23 plate condensers be used? 3. Can a 3½" tubing be used (2½" for rotor)? 4. Can double cotton covered wire be used for winding coils? 5. Can this set be built on a 21" panel? 6. Give capacity of neutralizing condensers. 7. What should the ratio of the audio-frequency transformers be? 8. Can Pacant neutralizing condensers be used?—E. Crass, care Post Office, Paducah, Ky.

1, 2, 3, 4 and 5, the answers are yes. 6. Variable. 7. Both low, about 3-5 to 1. 8. Yes.


I BUILT the Diamond of the Air, and get no results. What is the trouble?—William Rossvelt, R.R. 3, Box 88, Santa Rosa, Cal.

Your question is too unspecific. There are at least 1,000 things that can be the matter with

any set. See results letters of those who get wonderful results on this set. Test your tubes, batteries, wiring (for broken connections) and your audio transformers for shorts.

The Weekly Rebus

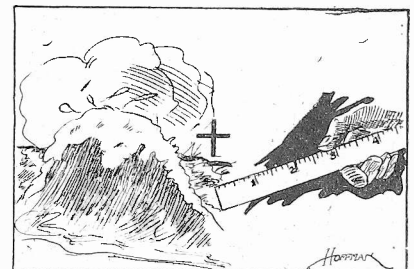WHAT does this Rebus represent? Send answer to Rebus Editor, RADIO WORLD, 1493 Broadway, New York



City. The names of those sending in the solution will be published.

- T. Heyward Brown, 1133 Euclid St., N. W. Washington, D. C.
- Max Greenhut, 99 Avenue C, N. Y. C.
- Gail Eaton, 231 Harvard St., Houston, Tex.
- Isidore Weiss, 608 East 9th St., N.Y.C.
- A. Saroky, P. O. Box 211, Station A, San Antonio, Tex.
- James Moran, 910 W. Pine, Enid, Oklahoma.
- V. T. Olson, 615 Florence St., Turlock, Cal.
- Harry Henderson, Macomb, Ill.
- T. B. Pinyown, 3846 Mayfield Rd., Cleveland Heights, O.

Join RADIO WORLD'S University Club

and we will enter your name on our subscription and University lists by special number. Put this number on the outside of your envelope addressed to RADIO WORLD (not the enclosed return envelope) and also put it in your queries and the questions will be answered the same day as received.

And Get Free Question and Answer Service for the Coming 52 Weeks.

RADIO WORLD, 1493 Broadway, New York City:

Enclosed find \$6.00 for RADIO WORLD for one year (52 Nos.) and also consider this an application to join RADIO WORLD'S University Club, which gives me free information in your Radio University Department for the coming year, and a number indicating my membership.



Name

Street

City and State

Call of the Great Outdoors

New Station

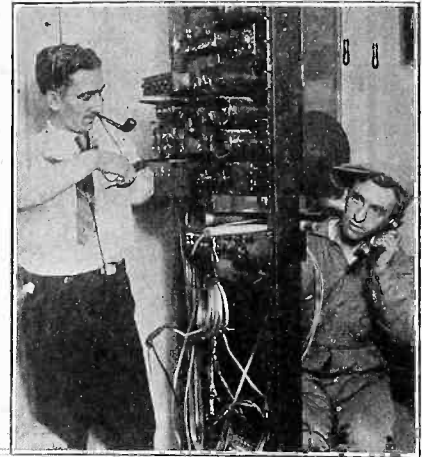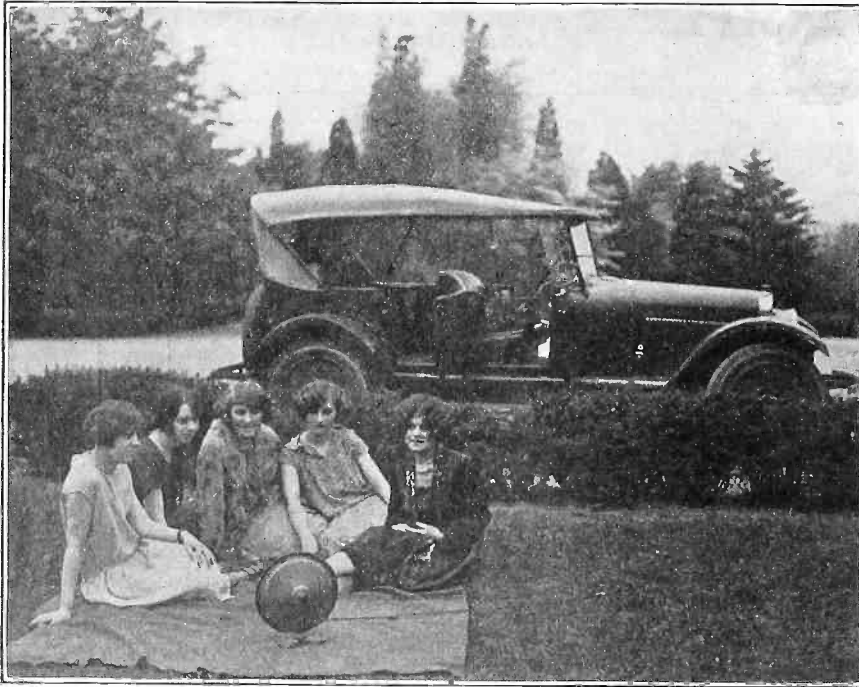

GETTING ready for WRNY, "Radio News" station, N. Y. C., sparring for shortest broadcast wavelength. (Foto Topics)



THIS 40-ounce bottle is a crystal set panel and cabinet. (Gilliams)


VACATION TIME raises the question of how best to employ a portable receiver. Top photo shows the storage battery of an auto used to light the tubes. A loop is in the lid, the batteries in the cabinet in the lower photo. (Foto Topics).

Sunlight Radio a Lure

ALTHOUGH sunlight reception is not as good as listening in at night, radio sets have advanced so far that they are very practical under the hottest sun. The light rays ionize the air, making it somewhat of a conductor, so that the energy of radio waves is partly dissipated. Therefore a successful portable should be a sensitive receiver for satisfactory results.

A loop will do very well, although at least four tubes must be used for successful speaker operation without reflex. This includes regeneration in the RF or detector stage. Otherwise six tubes are needed, else a reflex arrangement.

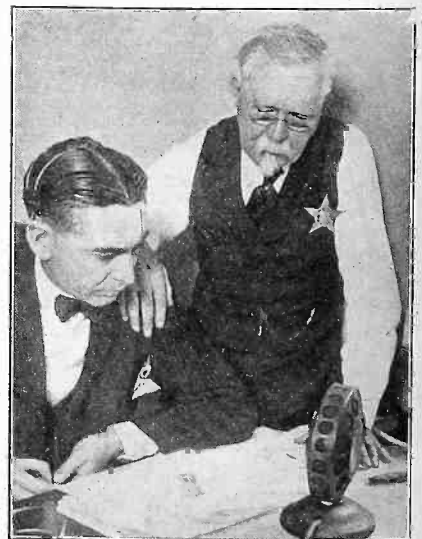A loop is handier than an outdoor open-end antenna for portable use.




EMMET EVANS and Capt. M. P. Evans of the Bureau of Identification, Police Department, Chicago, Ill., use the radio to catch criminals. (Underwood & Underwood)

Memorial to Victor Herbert

Russian Tower




ONE OF THE BEST radio programs in the four years of broadcasting was rendered by artists at the Ritz-Carlton Hotel, New York City, in a memorial one year after the death of Victor Herbert, America's greatest composer. Fritzi Scheff (center) sang, "Kiss Me Again" almost as well as a generation ago, when she and the song made a mutual hit. Graham McNamee, third from left, rear, announced at WEA. To his left is Paul Whiteman, whose orchestra played the Spanish suite specially composed by Mr. Herbert. Fred Stone (right, front) sang a song from "The Red Mill." Beside him is Dorothy Stone. Silvio Hein was master of ceremonies and Naham Franko directed his own orchestra in Herbert music. (Foto Topics)

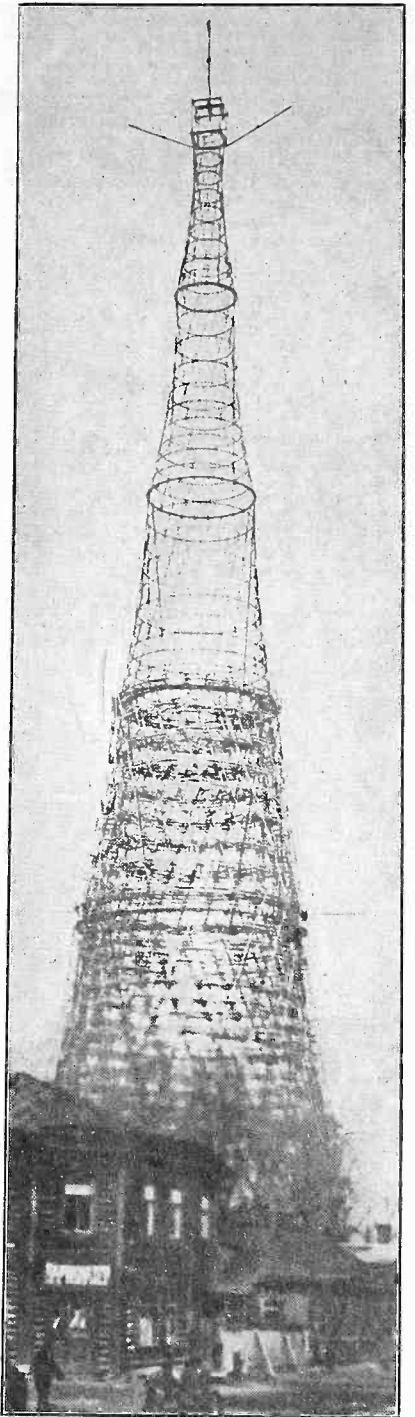

NOT a pagoda, but the tower of a broadcasting station in Moscow. (Wide World)



A DEMONSTRATION at Police Headquarters, New York City, connected by land line to station WNYC. The radio signalling device is shown in transmission work. When the key of the signalling device is closed a signal is flashed to all of the police stations and traffic booths throughout the city, which are equipped with receiving sets that are then tuned to WNYC's wave. This rapid means of communication is intended to help the police in watching and capturing automobile bandits. (International Newsreel)

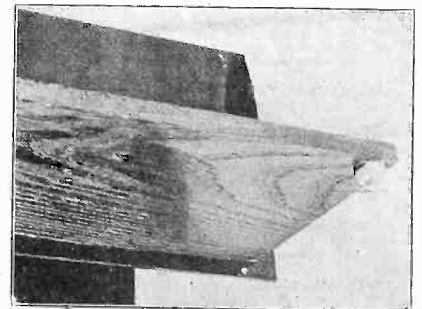

A FOOT under the baseboard prevents it from sagging. (Hayden)

THE KEY TO THE AIR

KEY

Abbreviations: E. S. T., Eastern Standard Time; C. S. T., Central Standard Time; M. S. T., Mountain Standard Time; P. S. T., Pacific Standard Time; D. S., Daylight Saving Time.

How to tune in a desired distant station at just the right time—Choose your station from the list published herewith. See what time division the station is under (E. S. T., C. S. T., etc.); then consult the table below. Add to or subtract, as directed from the table, as given on the PROGRAM. The result will be the same BY YOUR CLOCK that you should tune in, unless daylight saving time intervenes, as explained below.—The table:

If you are in	And want a station in	Subtract	Add
E. S. T.	C. S. T.	..	1 hr.
E. S. T.	M. S. T.	..	2 hrs.
E. S. T.	P. S. T.	..	3 hrs.
C. S. T.	E. S. T.	1 hr.	..
C. S. T.	M. S. T.	..	1 hr.
C. S. T.	P. S. T.	..	2 hrs.
M. S. T.	E. S. T.	2 hrs.	..
M. S. T.	M. S. T.	1 hr.	..
M. S. T.	P. S. T.	..	1 hr.
P. S. T.	E. S. T.	3 hrs.	..
P. S. T.	C. S. T.	2 hrs.	..
P. S. T.	D. S. T.	1 hr.	..

If you are under Daylight Saving Time, and the station you want is under that time, as if both are under Standard Time, the above table will hold.

If you are under Daylight Saving Time, and the stations operates under Standard Time, add one hour to the table result.

If the station uses Daylight Saving Time, and you are under Standard Time, subtract one hour from the table result.

FRIDAY

WAAM, Newark, N. J., 263 (E. S. T., D. S.)—11 A. M. to 12.
 WAHG, Richmond Hill, N. Y., 316 (E. S. T., D. S.)—12 to 1:05 P. M.; 8 to 12 P. M.
 WAMD, Minneapolis, Minn., 243.8 (C. S. T.)—12 to 1 P. M.; 10 to 12.
 WBBM, Chicago, Ill., 226 (C. S. T.)—8 to 10 P. M.
 WBBR, New York City, 272.6 (E. S. T., D. S.)—8 P. M. to 10.
 WBZ, Springfield, Mass., 333.1 (E. S. T., D. S.)—6 P. M. to 11.
 WCCO, St. Paul and Minneapolis, Minn., 416.4 (C. S. T.)—9:30 A. M. to 12 M.; 1:30 to 4; 5:30 to 10.
 WCAE, Pittsburgh, Pa., 461.3 (E. S. T., D. S.)—12:30 P. M. to 1:30 P. M.; 4:30 to 5:30; 6:30 to 11.
 WDAF, Kansas City, Kansas, 365.6 (C. S. T.)—3:30 to 7 P. M.; 8 to 10; 11:45 to 1 A. M.
 WDAF, New York City, 492 (E. S. T., D. S.)—6:45 A. M. to 7:45; 11 to 12; 4 P. M. to 5; 6 to 12.
 WEAR, Cleveland, O., 390 (E. S. T.)—11:30 A. M. to 12:10 P. M.; 3:30 to 4:10; 8 to 11.
 WEAQ, Ohio State University, 293.9 (E. S. T.)—8 P. M. to 10.
 WEEI, Boston, Mass., 476 (E. S. T., D. S.)—6:45 A. M. to 7:45; 2 P. M. to 3:15; 5:30 to 10.
 WEMC, Berrien Springs, Mich., 286 (C. S. T.)—9 P. M. to 11.
 WFAA, Dallas, Texas, 475.9 (C. S. T.)—10:30 A. M. to 11:30; 12:30 P. M. to 1; 2:30 to 6; 6:45 to 7; 8:30 to 9:30.
 WGBS, New York City, 316 (E. S. T., D. S.)—10 A. M. to 11; 1:30 P. M. to 4; 6 to 11.
 WGES, Chicago, Ill., 250 (C. S. T., D. S.)—5 P. M. to 7; 10:30 to 1 A. M.
 WGN, Chicago, Ill., 370 (C. S. T.)—9:31 A. M. to 3:30 P. M.; 5:30 to 11:30.
 WGR, Buffalo, N. Y., 319 (E. S. T., D. S.)—12 M. to 12:45 P. M.; 7:30 to 11.
 WGST, Atlanta, Ga., 270 (C. S. T.)—7 P. M. to 8.
 WGY, Schenectady, N. Y., 379.5 (E. S. T.)—1 P. M. to 2; 5:30 to 10:30.
 WHAD, Milwaukee, Wis., 275 (C. S. T.)—11 A. M. to 11:30; 6 P. M. to 8.
 WHAS, Louisville, Ky., 399.8 (C. S. T.)—4 P. M. to 5; 7:30 to 9.
 WHN, New York City, 360 (E. S. T., D. S.)—12:30 P. M. to 1; 2:15 to 5; 7 to 11; 12 to 12:30 A. M.
 WHO, Des Moines, Iowa, 526 (C. S. T.)—7:30 P. M. to 9; 11 to 12; 12:30 to 1:30; 4:30 to 5:30; 6:30 to 9:30.
 WIP, Philadelphia, Pa., 508.2 (E. S. T., D. S.)—7 A. M. to 8; 1 P. M. to 2; 3 to 4:50; 6 to 8.
 WJY, New York City, 405 (E. S. T., D. S.)—7:30 P. M. to 11:30.
 WJZ, New York City, 455 (E. S. T., D. S.)—10 A. M. to 11; 1 P. M. to 2; 4 to 6; 7 to 10:30.
 WLIT, Philadelphia, Pa., 395 (E. S. T.)—12:02 P. M. to 12:30; 2 to 3; 4:30 to 6; 7:30 to 1 A. M.
 WLW, Cincinnati, O., 422.3 (E. S. T.)—10:45 A. M. to 12:15; 1:30 P. M. to 2:30.
 WMCA, New York City, 341 (E. S. T., D. S.)—3 P. M. to 5; 6:30 to 7:30; 8:15 to 8:20; 9 to 10:15; 11 to 11:30.
 WNYC, New York City, 526 (E. S. T., D. S.)—3:45 P. M. to 4:45; 6:20 to 11.
 WOAW, Omaha, Neb., 526 (C. S. T.)—12:30 P. M. to 1; 5:45 to 7:10; 9 to 11.
 WOC, Davenport, Iowa, 484 (C. S. T.)—12:57 P. M. to 2; 3 to 3:30; 4 to 11.
 WOR, Newark, N. J., 405 (E. S. T., D. S.)—6:45 A. M. to 7:45; 2:30 P. M. to 4; 6:15 to 7.
 WPAK, Fargo, N. D., 283 (C. S. T.)—7:30 P. M. to 9.
 WPG, Atlantic City, N. J., 299.8 (E. S. T., D. S.)—7 P. M. to 8:30; 10 to 12.
 WOJ, Chicago, Ill., 448 (C. S. T.)—11 A. M. to 12M; 3 P. M. to 4; 7 to 8; 10 to 2 A. M.
 WRC, Washington, D. C., 469 (E. S. T.)—4:30 P. M. to 5; 6:45 to 12.

KDKA, Pittsburgh, Pa., 309 (E. S. T.)—6 A. M. to 7; 9:45 to 12:20 P. M.; 1:30 to 3:20; 5:30 to 11.
 KFAE, State College of Wash., 348.6 (P. S. T.)—7:30 P. M. to 9.
 KFDY, Brookings, S. D., 273 (M. S. T.)—8 P. M. to 9.
 KFI, Los Angeles, Cal., 467 (P. S. T.)—5 P. M. to 10.
 KFKX, Hastings, Neb., 288.3 (C. S. T.)—12:30 P. M. to 1:30; 9:30 to 12.
 KFNF, Shenandoah, Iowa, 266 (C. S. T.)—12:15 P. M. to 1:15; 3 to 4; 6:30 to 10.
 KFOA, Seattle, Wash., 455 (P. S. T.)—12:30 P. M. to 1:30; 4 to 5:15; 6 to 11.
 KGO, Oakland, Cal., 361.2 (P. S. T.)—11:10 A. M. to 1 P. M.; 1:30 to 3; 4 to 7.
 KGW, Portland, Oregon, 491.5 (P. S. T.)—11:30 A. M. to 1:30 P. M.; 5 to 11.
 KHJ, Los Angeles, Cal., 405.2 (P. S. T.)—7 A. M. to 7:15; 12 M. to 3:30 P. M.; 5:30 to 11:30.
 KNX, Hollywood, Cal., 337 (P. S. T.)—11:30 A. M. to 12:30 P. M.; 1 to 2; 4 to 5; 6:30 to 12.
 KOB, State College of New Mexico, 348.6 (M. S. T.)—11:55 A. M. to 12:30 P. M.; 7:30 to 8:30; 9:55 to 10:10.
 KPO, San Francisco, Cal., 429 (P. S. T.)—7:30 A. M. to 8; 10:30 to 12 M.; 1 P. M. to 2; 4:30 to 11.
 KSD, St. Louis, Mo., 545.1 (C. S. T.)—4 P. M. to 5.
 KTHS, Hot Springs, Ark., 374.8 (C. S. T.)—12:30 P. M. to 1; 8:20 to 10.
 KYW, Chicago, Ill., 536 (C. S. T., D. S.)—6:30 A. M. to 7:30; 10:55 to 1 P. M.; 2:25 to 3:30; 6:02 to 7:20; 9 to 1:30 A. M.
 CNRA, Moncton, Canada, 313 (E. S. T.)—8:30 P. M. to 10:30.
 CNRE, Edmonton, Canada, 516.9 (M. S. T.)—8:30 P. M. to 10:30.
 CNRS, Saskatoon, Canada, 400 (M. S. T.)—2:30 P. M. to 3.
 CNRT, Toronto, Canada, 357 (E. S. T.)—6:30 P. M. to 11.
 WAAM, Newark, N. J., 263 (E. S. T.)—7 P. M. to 11.
 WAHG, Richmond Hill, N. Y., 316 (E. S. T., D. S.)—12 M. to 2 A. M.
 WAMD, Minneapolis, Minn., 243.8 (C. S. T.)—12 M. to 1 P. M.; 10 to 12.
 WBBM, Chicago, Ill., 226 (C. S. T.)—8 P. M. to 1 A. M.
 WBBR, New York City, 272.6 (E. S. T., D. S.)—8 P. M. to 9.
 WBZ, Springfield, Mass., 333.1 (E. S. T., D. S.)—11 A. M. to 12:30 P. M.; 7 to 9.
 WCAE, Pittsburgh, Pa., 461.3 (E. S. T., D. S.)—10:45 A. M. to 12 M.; 3 P. M. to 4; 6:30 to 7:30.
 WCBD, Zion, Ill., 344.6 (C. S. T.)—8 P. M. to 10.
 WCCO, St. Paul and Minneapolis, Minn., 416.4 (C. S. T.)—9:30 A. M. to 12:30 P. M.; 2:30 to 5; 6 to 10.
 WDAF, New York City, 492 (E. S. T., D. S.)—6:45 A. M. to 7:45; 4 P. M. to 5; 6 to 12.
 WEEI, Boston, Mass., 476 (E. S. T., D. S.)—6:45 A. M. to 7:45.
 WEAR, Cleveland, O., 390 (E. S. T.)—11:30 A. M. to 12:10 P. M.; 3:30 to 4:10; 7 to 8.
 WEMC, Berrien Springs, Mich., 286 (C. S. T.)—11 A. M. to 12:30 P. M.; 8:15 to 11.
 WFAA, Dallas, Texas, 475.9 (C. S. T.)—12:30 P. M. to 1; 6 to 7; 8:30 to 9:30; 11 to 12:30 A. M.
 WGBS, New York City, 316 (E. S. T., D. S.)—10 A. M. to 11; 1:30 P. M. to 3; 6 to 12.
 WGN, Chicago, Ill., 370 (C. S. T.)—9:31 A. M. to 2:30 P. M.; 3 to 5:57; 6 to 11:30.
 WGR, Buffalo, N. Y., 319 (E. S. T., D. S.)—12 M. to 12:45 P. M.; 2:30 to 4:30; 7:30 to 8.
 WGY, Schenectady, N. Y., 379.5 (E. S. T.)—7:30 P. M. to 10.
 WHAD, Milwaukee, Wis., 275 (C. S. T.)—11 A. M. to 11:30; 6 P. M. to 8.
 WHAS, Louisville, Ky., 399.8 (C. S. T.)—4 P. M. to 5; 7:30 to 9.
 WHN, New York City, 360 (E. S. T., D. S.)—2:15 P. M. to 5; 7:30 to 10.
 WHO, Des Moines, Iowa, 526 (C. S. T.)—11 A. M. to 12:30 P. M.; 4 to 5:30; 7:30 to 8:30.
 WIP, Philadelphia, Pa., 508.2 (E. S. T., D. S.)—7 A. M. to 8; 10:20 to 11; 1 P. M. to 2; 3 to 4; 6 to 11:30.
 WJY, New York City, 405 (E. S. T., D. S.)—2:30 P. M. to 5; 8 to 10:30.
 WJZ, New York City, 455 (E. S. T., D. S.)—9 A. M. to 12:30 P. M.; 2:30 to 4; 7 to 10.
 WKRC, Cincinnati, O., 326 (E. S. T.)—10 to 12 M.
 WLW, Cincinnati, O., 422.3 (E. S. T.)—9:30 A. M. to 12:30 P. M.; 7:30 to 10.
 WMAK, Lockport, N. Y., 265.5 (E. S. T.)—10:25 A. M. to 12:30 P. M.
 WMC, Memphis, Tenn., 499.7 (E. S. T.)—7:30 P. M. to 10.
 WMCA, New York City, 341 (E. S. T., D. S.)—3 P. M. to 3:15; 3:30 to 5; 8 to 8:15; 8:30 to 8:45; 11 P. M. to 1 A. M.
 WNYC, New York City, 526 (E. S. T., D. S.)—1 P. M. to 3; 7 to 11.
 WOAW, Omaha, Neb., 526 (C. S. T.)—9 A. M. to 11; 2:15 P. M. to 4; 9 to 11.
 WOC, Davenport, Iowa, 484 (C. S. T.)—12:57 P. M. to 2; 5:45 to 7:10; 9 to 12.
 WOO, Philadelphia, Pa., 508.2 (E. S. T., D. S.)—11 A. M. to 1 P. M.; 4:40 to 5; 10:55 to 11:02.
 WOR, Newark, N. J., 405 (E. S. T., D. S.)—6:45 A. M. to 7:45; 2:30 P. M. to 4; 6:15 to 7:30; 8 to 11.
 WPG, Atlantic City, N. J., 299.8 (C. S. T.)—7 P. M. to 12.
 WOJ, Chicago, Ill., 448 (C. S. T.)—11 A. M. to 12 M.; 3 P. M. to 4; 7 to 8; 10 to 3 A. M.
 WRC, Washington, D. C., 469 (E. S. T.)—4:30 to 5:30 P. M.; 6:45 to 12.
 WWJ, Detroit, Mich., 357.2 (E. S. T.)—11 A. M. to 12:30 P. M.; 2 to 3; 7:20 to 10:30.
 KDKA, Pittsburgh, Pa., 309 (E. S. T.)—10 A. M. to 12:30 P. M.; 1:30 to 6:30; 8:45 to 10.
 KFI, Los Angeles, Cal., 467 (P. S. T.)—5 P. M. to 11.

KFKX, Hastings, Neb., 288.3 (C. S. T.)—12:30 P. M. to 1:30; 9:30 to 12:30.
 KFNF, Shenandoah, Iowa, 266 (C. S. T.)—12:15 P. M. to 1:15; 3 to 4; 6:30 to 10:30.
 KFOA, Seattle, Wash., 455 (P. S. T.)—Silent.
 KGO, Oakland, Cal., 361.2 (P. S. T.)—11 A. M. to 12:30 P. M.; 3:30 to 5:45; 7:30 to 9.
 KGW, Portland, Oregon, 491.5 (P. S. T.)—11:30 A. M. to 1:30 P. M.; 5 to 7; 10 to 11.
 KHJ, Los Angeles, Cal., 405.2 (E. S. T., D. S.)—7 A. M. to 7:30; 10 to 1:30 P. M.; 2:30 to 3:30; 5:30 to 2 A. M.
 KNX, Hollywood, Cal., 337 (P. S. T.)—1 P. M. to 5; 6:30 to 2 A. M.
 KOA, Denver, Colo., 322.4 (M. S. T.)—11:30 A. M. to 1 P. M.; 7 to 10.
 KPO, San Francisco, Cal., 429 (P. S. T.)—8 A. M. to 12 M.; 2 P. M. to 3; 6 to 10.
 KSD, St. Louis, Mo., 545.1 (C. S. T.)—7 P. M. to 8:30.
 KTHS, Hot Springs, Ark., 374.8 (C. S. T.)—12:30 P. M. to 1; 8:30 to 10:30.
 KYW, Chicago, Ill., 536 (C. S. T., D. S.)—11 A. M. to 12:30 P. M.; 4 to 5; 7 to 8.
 CKAC, Montreal, Canada, 411 (E. S. T.)—4:30 P. M. to 5:30.
 CNRO, Ottawa, Ontario, Canada, 435 (E. S. T.)—7:30 P. M. to 10.
 PWX, Havana, Cuba, 400 (E. S. T.)—8:30 P. M. to 11:30.

SUNDAY

WBBM, Chicago, Ill., 226 (C. S. T.)—4 P. M. to 6; 8 to 10.
 WBBR, New York City, 272.6 (E. S. T., D. S.)—10 A. M. to 12 M., 9 P. M. to 11.
 WCCO, St. Paul and Minneapolis, Minn., 416.4 (C. S. T.)—11 A. M. to 12:30 P. M.; 4:30 to 5:10; 7:20 to 10.
 WDAF, Kansas City, Kansas, 365.6 (C. S. T.)—4 P. M. to 5:30.
 WDAF, New York City, 492 (E. S. T., D. S.)—3 P. M. to 5; 7:20 to 10:15.
 WEAR, Cleveland, O., 390 (E. S. T.)—3:30 P. M. to 5; 7 to 8; 9 to 10.
 WGBS, New York City, 316 (E. S. T., D. S.)—3:30 P. M. to 4:30; 9:30 to 10:30.
 WGN, Chicago, Ill., 370 (C. S. T.)—11 A. M. to 12:45 P. M.; 2:30 to 5; 9 to 10.
 WGR, Buffalo, N. Y., 319 (E. S. T., D. S.)—3 P. M. to 4; 7:15 to 8.
 WGY, Schenectady, N. Y., 379.5 (E. S. T.)—9:30 A. M. to 12:30 P. M.; 2:35 to 3:45; 6:30 to 10:30.
 WHAD, Milwaukee, Wis., 275 (C. S. T.)—2 P. M. to 3.
 WHN, New York City, 360 (E. S. T., D. S.)—1 P. M. to 1:30; 3 to 6; 10 to 12.
 WIP, Philadelphia, Pa., 508.2 (E. S. T., D. S.)—10:45 A. M. to 12:30 P. M.; 3:30 to 4:30.
 WKRC, Cincinnati, O., 326 (E. S. T.)—6:45 P. M. to 11.
 WNYC, New York City, 526 (E. S. T., D. S.)—9 P. M. to 11.
 WPG, Atlantic City, N. J., 299.8 (C. S. T., D. S.)—3:15 P. M. to 5; 9 to 11.
 WOJ, Chicago, Ill., 448 (C. S. T.)—10:30 A. M. to 12:30 P. M.; 3 P. M. to 4; 8 to 10.
 KDKA, Pittsburgh, Pa., 309 (E. S. T.)—9:45 A. M. to 10:30; 11:55 to 12 M.; 2:30 P. M. to 5:30; 7 to 11.
 KFNF, Shenandoah, Iowa, 266 (C. S. T.)—10:45 A. M. to 12:30 P. M.; 2:30 to 4:30; 6:30 to 10.
 KOA, Denver, Colo., 322.4 (M. S. T.)—10:55 A. M. to 12 M.; 4 P. M. to 5:30 P. M.; 7:45 P. M. to 10 P. M.
 KGW, Portland, Oregon, 491.5 (P. S. T.)—10:30 A. M. to 12:30 P. M.; 5 to 9.
 KHJ, Los Angeles, Cal., 405.2 (E. S. T., D. S.)—10 A. M. to 12:30 P. M.; 6 to 9.
 KTHS, Hot Springs, Ark., 374.8 (C. S. T.)—11 A. M. to 12:30 P. M.; 2:30 to 3:40; 8:40 to 11.

MONDAY

WAAM, Newark, N. J., 263 (E. S. T., D. S.)—11 A. M. to 12 M.; 7 P. M. to 11.
 WAHG, Richmond Hill, N. Y., 316 (E. S. T., D. S.)—12 M. to 1:05 P. M.; 8 to 2 A. M.
 WAMD, Minneapolis, Minn., 243.8 (C. S. T.)—10 P. M. to 12.
 WBBM, Chicago, Ill., 226 (C. S. T.)—6 P. M. to 7.
 WBBR, New York City, 272.6 (E. S. T., D. S.)—8 P. M. to 9.
 WBZ, Springfield, Mass., 333.1 (E. S. T., D. S.)—6 P. M. to 11:30.
 WCAE, Pittsburgh, Pa., 461.3 (E. S. T., D. S.)—12:30 P. M. to 1:30; 4:30 to 5:30; 6:30 to 12.
 WCBD, Zion, Ill., 344.6 (C. S. T.)—8 P. M. to 10.
 WCCO, St. Paul and Minneapolis, Minn., 416.4 (C. S. T.)—9:30 A. M. to 12 M.; 1:30 P. M. to 6:15 to 10.
 WDAF, Kansas City, Kansas, 365.6 (C. S. T.)—3:30 P. M. to 7; 8 to 10; 11:45 to 1 A. M.
 WDAF, New York City, 492 (E. S. T., D. S.)—6:45 A. M. to 7:45; 4 P. M. to 5; 6 to 11:30.
 WEAR, Cleveland, O., 390 (E. S. T.)—11:30 A. M. to 12:10 P. M.; 3:30 to 4:10; 7 to 8.
 WEEI, Boston, Mass., 476 (E. S. T., D. S.)—6:45 A. M. to 8; 3 P. M. to 4; 5:30 to 10.
 WEMC, Berrien Springs, Mich., 286 (C. S. T.)—8:15 P. M. to 11.
 WFAA, Dallas, Texas, 475.9 (C. S. T.)—10:30 A. M. to 11:30; 12:30 P. M. to 1; 2:30 to 6; 6:45 to 7; 8:30 to 9:30.
 WGBS, New York City, 316 (E. S. T., D. S.)—10 A. M. to 11; 1:30 P. M. to 3:10; 7:30 to 8.
 WGES, Chicago, Ill., 250 (C. S. T., D. S.)—5 P. M. to 8.
 WGN, Chicago, Ill., 370 (C. S. T.)—9:31 A. M. to 3:30 P. M.; 5:30 to 5:57.
 WGR, Buffalo, N. Y., 319 (E. S. T., D. S.)—12 M. to 12:45 P. M.; 2:30 to 4:30; 7:30 to 11.
 WGST, Atlanta, Ga., 270 (C. S. T.)—9 P. M. to 10.
 WGY, Schenectady, N. Y., 379.5 (E. S. T.)—1 P. M. to 2; 5:30 to 8:30.
 WHAD, Milwaukee, Wis., 275 (C. S. T.)—11 A. M. to 11:30; 6 P. M. to 10:30.
 WHAS, Louisville, Ky., 399.8 (C. S. T.)—4 P. M. to 5; 7:30 to 9.

WHN, New York City, 360 (E. S. T., D. S.)—2:15 P. M. to 5; 6:30 to 12.
 WHO, Des Moines, Iowa, 528 (C. S. T.)—12:15 P. M. to 1:30; 7:30 to 9; 11:15 to 12.
 WIP, Philadelphia, Pa., 508.2 (E. S. T., D. S.)—7 A. M. to 8; 1 P. M. to 2; 3; 3 to 5.
 WJZ, New York City, 455 (E. S. T., D. S.)—10 A. M. to 11; 1 P. M. to 2; 4 to 5:30; 6 to 6:30; 7 to 11.
 WKRC, Cincinnati, O., 326 (E. S. T.)—8 P. M. to 10.
 WLIT, Philadelphia, Pa., 395 (E. S. T.)—12:02 P. M. to 1; 3 to 4:30 to 6; 7:30 to 11:30.
 WPAK, Fargo, N. D., 283 (C. S. T.)—7:30 P. M. to 9.
 WLW, Cincinnati, O., 422.3 (E. S. T.)—10:45 A. M. to 12:15 P. M.; 1:30 to 2:30; 3 to 5; 6 to 10.
 WMAK, Lockport, N. Y., 265.5 (E. S. T.)—8 P. M. to 12.
 WNYC, New York City, 526 (E. S. T., D. S.)—3:15 P. M. to 4:15; 6:30 to 11.
 WOAW, Omaha, Neb., 526 (C. S. T.)—12:30 P. M. to 1:30; 5:45 to 10:30.
 WOC, Davenport, Iowa, 484 (C. S. T.)—12:57 P. M. to 3 to 3:30; 5:45 to 6.
 WOO, Philadelphia, Pa., 508.2 (E. S. T., D. S.)—11 A. M. to 1 P. M.; 4:40 to 5; 7:30 to 11.
 WOR, Newark, N. J., 405 (E. S. T., D. S.)—6:45 A. M. to 7:45; 2:30 to 4; 6:15 to 11:30.
 WPG, Atlantic City, N. J., 299.8 (E. S. T., D. S.)—7 P. M. to 11.
 WQJ, Chicago, Ill., 448 (C. S. T.)—11 A. M. to 12 M.; 3 P. M. to 4.
 WRC, Washington, D. C., 469 (E. S. T.)—1 P. M. to 2; 4 to 6.
 KDKA, Pittsburgh, Pa., 309 (E. S. T.)—6 A. M. to 7:45 to 12:15 P. M.; 2:30 to 3:20; 5:30 to 10.
 KFAE, State College of Wash., 348.6 (P. S. T.)—7:30 P. M. to 9.
 KFI, Los Angeles, Cal., 467 (P. S. T.)—5 P. M. to 11.
 KFKX, Hastings, Neb., 288.3 (C. S. T.)—12:30 P. M. to 1:30; 5:15 to 6:15; 9:30 to 12:30.
 KFNF, Shenandoah, Iowa, 266 (C. S. T.)—12:15 P. M. to 1:15; 3 to 4; 6:30 to 10.
 KFOA, Seattle, Wash., 455 (P. S. T.)—12:45 P. M. to 1:30; 4 to 5:15; 6 to 10.
 KGO, Oakland, Cal., 361.2 (P. S. T.)—9 A. M. to 10:30; 11:30 A. M. to 1 P. M.; 1:30 to 6; 6:45 to 7; 8 to 11 A. M.
 KGW, Portland, Oregon, 491.5 (P. S. T.)—11:30 A. M. to 1:30; 5 to 8.
 KHJ, Los Angeles, Cal., 405.2 (P. S. T.)—7 A. M. to 7:15; 12 M. to 1:30 P. M.; 5:30 to 10.
 KNX, Hollywood, Cal., 337 (P. S. T.)—12 M. to 1 P. M.; 4 to 5; 6:30 to 12.
 KOB, State College of New Mexico, 348.6 (M. S. T.)—11:55 A. M. to 12:30 P. M.; 7:30 to 8:30; 9:55 to 10:10.
 KPO, San Francisco, Cal., 429 (P. S. T.)—10:30 A. M. to 12 M.; 1 P. M. to 2; 2:30 to 3:30; 4:30 to 5:30 to 10.
 KSD, St. Louis, Mo., 545.1 (C. S. T.)—7:30 P. M. to 10.
 KTHS, Hot Springs, Ark., 374.8 (C. S. T.)—12:30 P. M. to 1; 8:30 to 10:30.
 KYW, Chicago, Ill., 536 (C. S. T., D. S.)—6:30 A. M. to 7:30; 10:55 to 1 P. M.; 2:15 to 3:30; 6:02 to 7.

TUESDAY

WAAM, Newark, N. J., 263 (E. S. T., D. S.)—11 A. M. to 12 M.; 7 P. M. to 11.
 WAHG, Richmond Hill, N. Y., 316 (E. S. T., D. S.)—12 P. M. to 1:05 A. M.
 WAMB, Minneapolis, Minn., 243.8 (C. S. T.)—12 M. to 1 P. M.; 10 to 12.
 WBBM, Chicago, Ill., 226 (C. S. T.)—8 P. M. to 12.
 WBZ, Springfield, Mass., 333.1 (E. S. T., D. S.)—6 P. M. to 11.
 WCAE, Pittsburgh, Pa., 461.3 (E. S. T., D. S.)—12:30 P. M. to 1:30; 4:30 to 5:30; 6:30 to 11.
 WCCO, St. Paul and Minneapolis, Minn., 416.4 (C. S. T.)—9:30 A. M. to 12 M.; 1:30 P. M. to 4; 5:30 to 10.
 WDAF, Kansas City, Kansas, 365.6 (C. S. T.)—3:30 P. M. to 7; 11:45 to 1 A. M.
 WEAH, New York City, 492 (E. S. T., D. S.)—6:45 A. M. to 7:45; 11 to 12 M.; 4 P. M. to 5; 6 to 12.
 WEAR, Cleveland, O., 390 (E. S. T.)—11:30 A. M. to 12:10 P. M.; 7 to 10; 10 to 11.
 WEEI, Boston, Mass., 476 (E. S. T., D. S.)—6:45 A. M. to 8; 1 P. M. to 2; 6:30 to 10.
 WFAA, Dallas, Texas, 475.5 (C. S. T.)—10:30 A. M. to 11:30; 12:30 P. M. to 1; 2:30 to 6; 6:45 to 7; 8:30 to 9:30; 11 to 12.
 WGBS, New York City, 316 (E. S. T., D. S.)—10 A. M. to 11; 1:30 P. M. to 3; 6 to 11:30.
 WGES, Chicago, Ill., 250 (C. S. T., D. S.)—5 P. M. to 8; 10:30 to 1 A. M.
 WGN, Chicago, Ill., 370 (C. S. T.)—9:31 A. M. to 3:30 P. M.; 5:30 to 11:30.
 WGR, Buffalo, N. Y., 319 (E. S. T., D. S.)—11 A. M. to 12:45 P. M.; 7:30 to 11.
 WGY, Schenectady, N. Y., 379.5 (E. S. T.)—11 P. M. to 2:30; 5:20 to 7:30; 9 to 11:30.
 WHAD, Milwaukee, Wis., 275 (C. S. T.)—11 A. M. to 11:30; 6 P. M. to 8.
 WHAS, Louisville, Ky., 399.8 (C. S. T.)—4 P. M. to 5; 7:30 to 9.
 WHN, New York City, 360 (E. S. T., D. S.)—12:30 P. M. to 1; 2:15 to 3:15; 4 to 5:30; 7:30 to 10:45; 11:30 to 12:30 A. M.
 WHO, Des Moines, Iowa, 526 (C. S. T.)—12:15 P. M. to 1:30; 7:30 to 9; 11 to 12.
 WIP, Philadelphia, Pa., 508.2 (E. S. T., D. S.)—7 A. M. to 8; 1 P. M. to 2; 3 to 4:50; 6 to 11.
 WJY, New York City, 405 (E. S. T., D. S.)—7:30 P. M. to 1:30.
 WJZ, New York City, 455 (E. S. T., D. S.)—10 A. M. to 11; 1 P. M. to 2; 4 to 6; 7 to 11.
 WKRC, Cincinnati, O., 326 (E. S. T.)—8 P. M. to 12.
 WLIT, Philadelphia, Pa., 395 (E. S. T.)—11 A. M. to 12:30 P. M.; 2 to 3; 4:30 to 7.
 WLW, Cincinnati, O., 422.3 (E. S. T.)—10:45 A. M. to 12:15 P. M.; 1:30 to 2:30; 3 to 5; 6 to 10.
 WNYC, New York City, 526 (E. S. T., D. S.)—5:30 P. M. to 11.
 WOC, Davenport, Iowa, 484 (C. S. T.)—12:57 P. M. to 2; 3 to 3:30; 4 to 7:05; 9 to 11.
 WOR, Newark, N. J., 405 (E. S. T., D. S.)—6:45 A. M. to 7:45; 2:30 P. M. to 4; 6:15 to 12 M.
 WPAK, Fargo, N. D., 283 (C. S. T.)—7:30 P. M. to 9.
 WQJ, Chicago, Ill., 448 (C. S. T.)—11 A. M. to 12 M.; 3 P. M. to 4; 7 to 8; 10 to 2 A. M.
 WRC, Washington, D. C., 469 (E. S. T.)—1 P. M. to 2; 4 to 6:30.
 KDKA, Pittsburgh, Pa., 309 (E. S. T.)—6 A. M. to 7:45 to 12:15 P. M.; 2:30 to 3:20; 5:30 to 11.
 KFAE, State College of Wash., 348.6 (P. S. T.)—7:30 P. M. to 9.
 KFI, Los Angeles, Cal., 467 (P. S. T.)—5 P. M. to 11.
 KFKX, Hastings, Neb., 288.3 (C. S. T.)—12:30 P. M. to 1:30; 5:15 to 6:15; 9:30 to 12:30.
 KFNF, Shenandoah, Iowa, 266 (C. S. T.)—12:15 P. M. to 1:15; 3 to 4; 6:30 to 10.

WNYC, New York City, 526 (E. S. T., D. S.)—3:45 P. M. to 5; 6:50 to 11.
 WOAW, Omaha, Neb., 526 (C. S. T.)—12:30 P. M. to 1:30; 5:45 to 11.
 WOC, Davenport, Iowa, 484 (C. S. T.)—12:57 P. M. to 3; 3 to 3:30; 5:45 to 10.
 WOO, Philadelphia, Pa., 508.2 (E. S. T., D. S.)—11 A. M. to 1 P. M.; 4:40 to 5; 10:55 to 11:02.
 WOR, Newark, N. J., 405 (E. S. T., D. S.)—6:45 A. M. to 7:45; 2:30 P. M. to 4; 6:15 to 7:30.
 WPG, Atlantic City, N. J., 299.8 (E. S. T., D. S.)—7 P. M. to 11.
 WQJ, Chicago, Ill., 448 (C. S. T.)—11 A. M. to 12 M.; 3 P. M. to 4; 7 to 8; 10 to 2 A. M.
 WRC, Washington, D. C., 469 (E. S. T.)—1:30 P. M. to 5:30; 6:45 to 11.
 KDKA, Pittsburgh, Pa., 309 (E. S. T.)—9:45 P. M. to 12 M.; 1:30 P. M. to 3:20; 5:30 to 10:45.
 KFI, Los Angeles, Cal., 467 (P. S. T.)—5 P. M. to 11.
 KFKX, Hastings, Neb., 288.3 (C. S. T.)—12:30 P. M. to 1:30; 5:15 to 6:15; 9:30 to 12:30.
 KFOA, Seattle, Wash., 455 (P. S. T.)—12:30 P. M. to 1:30; 4 to 5:15; 6 to 11.
 KGO, Oakland, Cal., 361.2 (P. S. T.)—11:30 A. M. to 1 P. M.; 1:30 to 3; 4 to 6:45; 8 to 11 A. M.
 KGW, Portland, Oregon, 491.5 (P. S. T.)—11:30 A. M. to 1:30 P. M.; 5 to 11.
 KHJ, Los Angeles, Cal., 405.2 (P. S. T.)—7 A. M. to 7:15; 12 M. to 3:30 P. M.; 5:30 to 11.
 KNX, Hollywood, Cal., 337 (P. S. T.)—9 A. M. to 10; 1 P. M. to 3; 4 to 5; 6:30 to 12.
 KPO, San Francisco, Cal., 429 (P. S. T.)—7 A. M. to 7:45; 10 to 12 M.; 1 P. M. to 2; 3:30 to 11.
 KSD, St. Louis, Mo., 541.1 (C. S. T.)—6 P. M. to 9.
 KTHS, Hot Springs, Ark., 374.8 (C. S. T.)—12:30 P. M. to 1; 8:30 to 10:30.
 KYW, Chicago, Ill., 536 (C. S. T., D. S.)—6:30 A. M. to 7:30; 10:30 to 1 P. M.; 2:15 to 4; 6:02 to 11:30.
 CNRA, Moncton, New Brunswick, Canada, 313 (E. S. T.)—9:30 P. M. to 11.
 CNRR, Regina, Saskatchewan, Canada, 8 P. M. to 11.

WEDNESDAY

WAAM, Newark, N. J., 263 (E. S. T., D. S.)—11 A. M. to 12 M.; 7 P. M. to 11.
 WAHG, Richmond Hill, N. Y., 316 (E. S. T., D. S.)—12:30 P. M. to 1:05 A. M.
 WAMB, Minneapolis, Minn., 243.8 (C. S. T.)—12 M. to 1 P. M.; 10 to 12.
 WBBM, Chicago, Ill., 226 (C. S. T.)—8 P. M. to 12.
 WBZ, Springfield, Mass., 333.1 (E. S. T., D. S.)—6 P. M. to 11.
 WCAE, Pittsburgh, Pa., 461.3 (E. S. T., D. S.)—12:30 P. M. to 1:30; 4:30 to 5:30; 6:30 to 11.
 WCCO, St. Paul and Minneapolis, Minn., 416.4 (C. S. T.)—9:30 A. M. to 12 M.; 1:30 to 4; 5:30 to 11.
 WDAF, Kansas City, Kansas, 365.6 (C. S. T.)—3:30 P. M. to 7; 8 to 9:15; 11:45 to 1 A. M.
 WEAH, New York City, 492 (E. S. T., D. S.)—6:45 A. M. to 7:45; 11 to 12 M.; 4 P. M. to 5; 6 to 12.
 WEAO, Ohio State University, 293.9 (E. S. T.)—8 P. M. to 10.
 WEAR, Cleveland, O., 390 (E. S. T.)—11:30 A. M. to 12:10 P. M.; 3:30 to 4:10; 6:45 to 7:45.
 WEEI, Boston, Mass., 476 (E. S. T., D. S.)—6:45 A. M. to 8; 3 P. M. to 4; 5:30 to 10.
 WEMC, Berrien Springs, Mich., 286 (C. S. T.)—8:15 P. M. to 11.
 WFAA, Dallas, Texas, 475.5 (C. S. T.)—10:30 A. M. to 11:30; 12:30 P. M. to 1.
 WGES, Chicago, Ill., 250 (C. S. T., D. S.)—5 P. M. to 7; 10:30 to 1 A. M.
 WGBS, New York City, 316 (E. S. T., D. S.)—10 A. M. to 11 P. M.; 1:30 to 4; 6 to 7.
 WGN, Chicago, Ill., 370 (C. S. T.)—9:31 A. M. to 3:30 P. M.; 5:30 to 11:30.
 WGR, Buffalo, N. Y., 319 (E. S. T., D. S.)—12 M. to 12:45 P. M.; 2:30 to 4:30; 6:30 to 11.
 WGY, Schenectady, N. Y., 379.5 (C. S. T.)—5:30 P. M. to 7:30.
 WHAD, Milwaukee, Wis., 275 (C. S. T.)—11 A. M. to 11:30; 4 P. M. to 5; 6 to 10; 11:30 to 12:30 A. M.
 WHAS, Louisville, Ky., 399.8 (C. S. T.)—4 P. M. to 5; 7:30 to 9.
 WHN, New York City, 360 (E. S. T., D. S.)—2:15 P. M. to 5:30; 7:30 to 11; 11:30 to 12:30 A. M.
 WHO, Des Moines, Iowa, 526 (C. S. T.)—12:15 P. M. to 1:30; 6:30 to 12 M.
 WIP, Philadelphia, Pa., 508 (E. S. T., D. S.)—7 A. M. to 8; 10:20 to 11; 1 P. M. to 2; 3 to 4; 6 to 8.
 WJZ, New York City, 455 (E. S. T., D. S.)—10 A. M. to 11; 1 P. M. to 2; 4 to 6; 7 to 11:30.
 WKRC, Cincinnati, Ohio, 326 (E. S. T.)—8 P. M. to 10.
 WLIT, Philadelphia, Pa., 395 (E. S. T.)—12:02 P. M. to 12:30; 2 to 3; 4:30 to 6; 7:30 to 9.
 WLW, Cincinnati, O., 422.3 (E. S. T.)—10:45 A. M. to 12:15 P. M.; 1:30 to 2:30; 3 to 5; 6 to 10.
 WNYC, New York City, 526 (E. S. T., D. S.)—5:30 P. M. to 11.
 WOC, Davenport, Iowa, 484 (C. S. T.)—12:57 P. M. to 2; 3 to 3:30; 4 to 7:05; 9 to 11.
 WOR, Newark, N. J., 405 (E. S. T., D. S.)—6:45 A. M. to 7:45; 2:30 P. M. to 4; 6:15 to 12 M.
 WPAK, Fargo, N. D., 283 (C. S. T.)—7:30 P. M. to 9.
 WQJ, Chicago, Ill., 448 (C. S. T.)—11 A. M. to 12 M.; 3 P. M. to 4; 7 to 8; 10 to 2 A. M.
 WRC, Washington, D. C., 469 (E. S. T.)—1 P. M. to 2; 4 to 6:30.
 KDKA, Pittsburgh, Pa., 309 (E. S. T.)—6 A. M. to 7:45 to 12:15 P. M.; 2:30 to 3:20; 5:30 to 11.
 KFAE, State College of Wash., 348.6 (P. S. T.)—7:30 P. M. to 9.
 KFI, Los Angeles, Cal., 467 (P. S. T.)—5 P. M. to 11.
 KFKX, Hastings, Neb., 288.3 (C. S. T.)—12:30 P. M. to 1:30; 5:15 to 6:15; 9:30 to 12:30.
 KFNF, Shenandoah, Iowa, 266 (C. S. T.)—12:15 P. M. to 1:15; 3 to 4; 6:30 to 10.

KFOA, Seattle, Wash., 455 (P. S. T.)—12:30 P. M. to 1:30; 4 to 5:15; 6 to 10.
 KGO, Oakland, Cal., 361.2 (P. S. T.)—11:30 A. M. to 1 P. M.; 1:30 to 2:30; 3 to 6:45.
 KGW, Portland, Oregon, 491.5 (P. S. T.)—11:30 A. M. to 1:30 P. M.; 5 to 10.
 KHJ, Los Angeles, Cal., 405.2 (P. S. T.)—7 A. M. to 7:15; 12 M. to 1:30 P. M.; 5:30 to 12.
 KNX, Hollywood, Cal., 337 (P. S. T.)—1 P. M. to 2; 7 to 12.
 KOB, State College of New Mexico, 348.6 (M. S. T.)—11:55 A. M. to 12:30 P. M.; 7:30 to 8:30; 9:55 to 10:10.
 KPO, San Francisco, Cal., 429 (P. S. T.)—7 A. M. to 8; 10:30 to 12 M.; 1 P. M. to 2; 4:30 to 11.
 KSD, St. Louis, Mo., 545.1 (C. S. T.)—7 P. M. to 10.
 KTHS, Hot Springs, Ark., 374.8 (C. S. T.)—8:30 P. M. to 10.
 KYW, Chicago, Ill., 536 (C. S. T., D. S.)—6:30 A. M. to 7:30; 10:55 to 1 P. M.; 2:15 to 4; 6:02 to 11:30.
 PWX, Havana, Cuba, 480 (E. S. T.)—8:30 P. M. to 11:30.
 CNRO, Ottawa, Ontario, Canada, 435 (E. S. T.)—7 P. M. to 11.

THURSDAY

WAAM, Newark, N. J., 263 (E. S. T., D. S.)—11 A. M. to 12 M.; 7 P. M. to 11.
 WAHG, Richmond Hill, N. Y., 316 (E. S. T.)—12 P. M. to 1:05 A. M.
 WAMB, Minneapolis, Minn., 243.8 (C. S. T.)—12 M. to 1 P. M.; 10 to 12 M.
 WBBM, Chicago, Ill., 226 (C. S. T.)—8 P. M. to 10.
 WBZ, Springfield, Mass., 333.1 (E. S. T., D. S.)—6 P. M. to 11:45.
 WCAE, Pittsburgh, Pa., 461.3 (C. S. T., D. S.)—12:30 P. M. to 1:30; 4:30 to 5:30; 6:30 to 11.
 WCCO, St. Paul and Minneapolis, Minn., 416.4 (C. S. T.)—9:30 A. M. to 12 M.; 1:30 P. M. to 4; 5:30 to 10.
 WDAF, Kansas City, Kansas, 365.6 (C. S. T.)—3:30 P. M. to 7; 8 to 9:15; 11:45 to 1 A. M.
 WEAH, New York City, 492 (E. S. T., D. S.)—6:45 A. M. to 7:45; 11 to 12 M.; 4 P. M. to 5; 6 to 12.
 WEAR, Cleveland, O., 390 (E. S. T.)—10:30 A. M. to 12:10 P. M.; 3:30 to 4:15; 7 to 11.
 WEEI, Boston, Mass., 476 (E. S. T., D. S.)—6:45 A. M. to 7:45; 1 P. M. to 2; 2:30 to 10.
 WFAA, Dallas, Texas, 475.5 (C. S. T.)—10:30 A. M. to 11:30; 12:30 P. M. to 1; 2:30 to 6; 6:45 to 7; 8:30 to 9:30; 11 to 1 A. M.
 WGBS, New York City, 316 (E. S. T., D. S.)—10 A. M. to 11; 1:30 P. M. to 4; 6 to 7:30.
 WGES, Chicago, Ill., 250 (C. S. T., D. S.)—5 P. M. to 8; 10:30 to 1 A. M.
 WGN, Chicago, Ill., 370 (C. S. T.)—9:31 A. M. to 3:30 P. M.; 5:30 to 11:30.
 WGR, Buffalo, N. Y., 319 (E. S. T., D. S.)—12 M. to 12:45 P. M.; 2 to 4; 7:30 to 11.
 WHAD, Milwaukee, Wis., 275 (C. S. T.)—11 A. M. to 11:30; 6 P. M. to 7:15; 8:30 to 11.
 WHAS, Louisville, Ky., 399.8 (C. S. T.)—4 P. M. to 5; 7:30 to 9.
 WHN, New York City, 360 (E. S. T., D. S.)—2:15 P. M. to 5; 7:30 to 11; 11:30 to 12:30 A. M.
 WHO, Des Moines, Iowa, 526 (C. S. T.)—7:30 P. M. to 9; 11 to 12 M.
 WJY, New York City, 405 (E. S. T., D. S.)—7:30 P. M. to 11:30.
 WJZ, New York City, 455 (E. S. T., D. S.)—10 A. M. to 11 P. M.; 1 to 2; 4 to 6; 7 to 12 M.
 WLIT, Philadelphia, Pa., 395 (E. S. T.)—12:02 P. M. to 12:30; 2 to 3; 4:30 to 6; 8:30 to 9.
 WLW, Cincinnati, O., 422.3 (E. S. T.)—10:40 A. M. to 12:15 P. M.; 1:30 to 5; 6 to 8; 10 to 11.
 WMAK, Lockport, N. Y., 265.5 (E. S. T.)—11 P. M. to 1 A. M.
 WNYC, New York City, 526 (E. S. T., D. S.)—3:15 P. M. to 4:15; 6:50 to 11.
 WOAW, Omaha, Neb., 526 (C. S. T.)—12:30 P. M. to 1:30; 5:45 to 11.
 WOC, Davenport, Iowa, 484 (C. S. T.)—12:57 A. M. to 2 P. M.; 3 to 3:30; 4 to 7:10; 8 to 9.
 WOR, Newark, N. J., 405 (E. S. T., D. S.)—6:45 A. M. to 7:45; 2:30 P. M. to 4; 6:15 to 7:30.
 WPG, Atlantic City, N. J., 299.8 (E. S. T., D. S.)—7 P. M. to 11.
 WQJ, Chicago, Ill., 448 (C. S. T.)—11 A. M. to 12 M.; 3 P. M. to 4; 7 to 8; 10 to 2 A. M.
 WRC, Washington, D. C., 469 (E. S. T.)—1 P. M. to 2; 4 to 6:30.
 KDKA, Pittsburgh, Pa., 309 (E. S. T.)—9:45 A. M. to 12:15 P. M.; 2:30 to 3:20; 5:30 to 10:15.
 KFAE, State College of Wash., 348.6 (P. S. T.)—7:30 P. M. to 9.
 KFI, Los Angeles, Cal., 467 (P. S. T.)—5 P. M. to 11.
 KFKX, Hastings, Neb., 288.3 (C. S. T.)—12:30 P. M. to 1:30; 5:15 to 6:15; 9:30 to 12:30.
 KFNF, Shenandoah, Iowa, 266 (C. S. T.)—12:15 P. M. to 1:15; 3 to 4; 6:30 to 10.
 KFOA, Seattle, Wash., 455 (P. S. T.)—12:30 P. M. to 1:30; 4 to 5:15; 6 to 7.
 KGO, Oakland, Cal., 361.2 (P. S. T.)—11:30 A. M. to 1 P. M.; 1:30 to 3; 4 to 6:45; 7:15 to 10.
 KGW, Portland, Oregon, 491.5 (P. S. T.)—11:30 A. M. to 1:30 P. M.; 5 to 11.
 KHJ, Los Angeles, Cal., 405.2 (P. S. T.)—7 A. M. to 7:15; 12 M. to 3:20; 5:30 to 11:30.
 KNX, Hollywood, Cal., 337 (P. S. T.)—11 A. M. to 12:05 P. M.; 4 to 5; 6 to 12.
 KPO, San Francisco, Cal., 429 (P. S. T.)—7 A. M. to 8; 10:30 to 12 M.; 1 P. M. to 2; 3:30 to 11.
 KSD, St. Louis, Mo., 545.1 (C. S. T.)—7:30 P. M. to 9.
 KYW, Chicago, 536 (C. S. T., D. S.)—6:30 A. M. to 7:30; 10:55 to 1 P. M.; 2:25 to 3:30; 6:02 to 11.
 CNRC, Calgary, Canada, 430 (M. S. T.)—7 P. M. to 10.
 CNRM, Montreal, Canada, 411 (E. S. T.)—8:30 P. M. to 10:30.
 CNRW, Winnipeg, Canada, 384.4 (C. S. T.)—8 P. M. to 10.

A THOUGHT FOR THE WEEK

IN other years a vacation usually meant a sort of stop-brain process—and no news from the front of the world's activities. Radio in 1925 means that a vacation, no matter how far removed from so-called civilization, is punctuated by news from the diamond, from Washington, from almost every place where folk are busy doing things. Radio certainly has changed the habits of our people to a startling degree.

RADIO WORLD

Radio World's Slogan: "A radio set for every home."

TELEPHONES: LACKAWANNA 676 and 2063 PUBLISHED EVERY WEDNESDAY (Dated Saturday of same week) FROM PUBLICATION OFFICE HENNESSY RADIO PUBLICATIONS CORPORATION ROLAND BURKE HENNESSY, President M. B. HENNESSY, Vice-President FRED S. CLARK, Secretary and Manager 1493 BROADWAY, NEW YORK, N. Y. (Putnam Bldg., Times Square and 43rd Street) European Representatives: The International News Co., Breains Bldg., Chancery Lane, London, Eng., Paris, France, Brentano's 33 Avenue de l'Opera.

EDITOR, Roland Burke Hennessy MANAGING EDITOR, Herman Bernard

SUBSCRIPTION RATES

Fifteen cents a copy. \$6.00 a year. \$3.00 for six months. \$1.50 for three months. Add \$1.00 a year extra for foreign postage, Canada, 50 cents. Receipt by new subscribers of the first copy of RADIO WORLD mailed to them after sending in their order, is automatic acknowledgment of their subscription order. Changes of address should be received at this office two weeks before date of publication. Always give old address also. State whether subscription is new or a renewal.

ADVERTISING RATES

Table with 2 columns: Ad type and Rate. Includes General Advertising and Times Discounts.

CLASSIFIED ADVERTISEMENTS

Ten cents per word. Minimum, 10 words. Cash with order. Business Opportunities, 50 cents a line; minimum, \$1.00.

Entered as second-class matter, March 28, 1922, at the Post Office at New York, New York, under the act of March 3, 1879.

JUNE 6, 1925

Crosley Copyright Suit Goes to Highest Court

CINCINNATI.

THE United States Circuit Court of Appeals here granted a stay in the suit over broadcasting as a "public performance" under the copyright law. This halts the test litigation between the owner of the Crosley Radio Corporation's broadcasting station here and Jerome H. Remick & Co., of New York and Detroit, pending a hearing before the United States Supreme Court.

The Crosley Corporation won a decision in the court of first instance, that broadcasting a song was not a "performance," but the Appellate court reversed the finding of the court of first instance. Now the case is before the United States Supreme Court and proceedings are stayed pending appeal.

BERNIE HOLDS POPULARITY CONTEST LEAD

BEN BERNIE and his orchestra still lead in the voting by RADIO WORLD readers to determine the most popular radio entertainer of 1925. The Happiness Boys stand second. Roxy and Karl Bonawitz (WIP) are tied for third place. These four have a substantial lead over all others, for the time being. Nils T. Granlund, announcer, WHN, New York City, made a substantial gain, and is well ahead of those outside the first four.

Some of the other artists in the popularity fight are: Alvin E. Hauser, of WFBH; the Gold Dust Twins, of WEAF; the Harmony Girls, of WLS; Leo Reisman and Orchestra, of WBZ; Major J. Andrew White, of WJZ; Hotel Commodore Orchestra, under the direction of Bernard Levitow, of WJZ; Walter Peterson, of WLS, and Ford and Glenn, WLS.

Contest Rules

1. The votes in RADIO WORLD'S 1925 contest to determine the radio entertainer entitled to the popularity gold medal may be cast by filling out the coupon as published weekly in RADIO WORLD. One coupon entitles the sender to one vote. The coupon should be properly filled out and mailed. Anybody subscribing to RADIO WORLD (a new subscriber or one renewing an existing subscription), may cast as many votes as are represented by the total number of weeks of the new or renewed subscription. In addition, as the coupons are published, the subscriber may use them for sending in one vote on each such coupon. When subscribing, cast your total subscription votes by specifying the candidate in the subscription order.

2. This contest closes July 31. The last coupon will be published in the July 25 issue.

3. In case of a tie, a gold medal will be awarded to each contestant so tied.

FOG SIGNAL PUT UNDER TEST AS A LIFE-SAVER

WASHINGTON.

"FOG, the greatest menace of the sea, may be overcome by radio," J. Walter Drake, Assistant Secretary of Commerce, believes. Mr. Drake is sending two of his best radio engineers to Detroit to equip the Huron Lightship, at the entrance of the St. Clair River, with the necessary apparatus to "defeat the white death of the lakes." This will be the first station on the Great Lakes, to be followed by six more installations this season.

Estimating that over 95 per cent. of the \$20,000,000 loss in property and about the same percentage of the hundreds of lives lost just on the Pacific from 1918 to 1923 were due to accidents resulting from fog, Mr. Drake said that the Lighthouse Service system of fog signals "for the first time in maritime history affords a practicable means by which a navigator may obtain accurate bearings on invisible objects." It also enables vessels to locate each other in fog when approaching or needing assistance, he said. The mechanism is installed on a radio fog beacon on shore to guide ships.

Bill For Irish Station Will Go Before Dail

WASHINGTON.

ALTHOUGH Ireland is without a broadcasting station and is still dependent on British broadcast stations, radio is gaining in popularity in the Emerald Isle and approximately 3,000 receiving sets had been licensed up to April 1, according to reports to the Department of Commerce.

The government's plan for the erection of a broadcasting station has been postponed for the time being following consideration of a clause in the Anglo-Irish treaty by which the Free State has agreed not to establish wireless stations except by agreement with the British government. A bill providing for the establishment of a broadcasting station under State control has been completed and will be introduced in the Dail as soon as the necessary agreement has been reached with the British government.

THE DIAMOND OF THE AIR AS A 2-CONTROL SET, by Herman Bernard. This is the circuit that is sweeping the country. Four tubes; loop or aerial. Send 30c for May 23 and 30 issues of RADIO WORLD, 1493 Broadway, New York City.

THE SHORT-WAVE RECEIVER REINARTZ WILL USE IN ARCTIC. Full wiring directions. Send 15c for May 16 issue, RADIO WORLD, 1493 Broadway, New York City.

RADIO WORLD'S POPULARITY CONTEST

To Determine the Gold Medal Radio Entertainer for 1925 Popularity Editor, RADIO WORLD, 1493 Broadway, N. Y. C.

I hereby cast one ballot for:

(Name of Entertainer).....

(Entertainer's Station).....

(Voter Sign Full Name Here).....

(Street and Number).....

(City)..... (State).....


No. 8-6-0

FILL OUT THIS COUPON AND MAIL NOW!

MR. DX HOUND

A Character Created by RADIO WORLD Artist

By HAL SINCLAIR

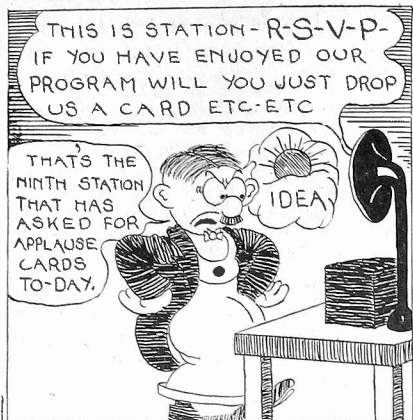

THE RADIO TRADE

Radio World Picked as Fan's Favorite

DON'T you feel terrible when, after you have told a credulous friend that your receiver obtained some very distant station, and you turn the dials in his presence next night to the number where you think you received the station, and it isn't there, even though the station is on the air? Your set no doubt can get the station, but you cannot locate the exact numbers on the dials to get the station. However, this difficulty can be done away with by using a logging chart so that every station that you receive will be marked down permanently. Such a device is put out by the Radio Chart Bureau, Patterson Building, Fresno, Cal., called the Find-Me-Quick Radio Chart. Jack L. Draper, of 501 Main Street, Ligonier, Ind., won a prize of one year's subscription to any magazine for having completed two Find-Me-Quick radio charts containing complete data for 100 different American and foreign stations logged on the Radio Chart. The magazine is to be picked out is absolutely up to the winner, and Mr. Draper selected RADIO WORLD, sending his selection to Felix M. Locher, of the Radio Chart Bureau.

Supertron's Guarantee

A GUARANTEE that really means something, and that is real protection and satisfaction for the consumer, dealer and jobber is being issued by the Supertron Manufacturing Company with every tube made by them. This guarantee certificate accompanies every tube of all types bearing a serial number, which serial number appears on each tube, the certificate and the tube corresponding, so that the consumer has the privilege of adjustment, exchange and service and knows that a substantial corporation stands squarely behind the tube. This is a sensible guarantee and is good news to the jobber and dealer; the jobber knowing that he takes no risk in handling, and the dealer knowing that he is absolutely protected on all angles of his transaction and that he is justified in recommending this tube not only to the experienced radio fan but also to the "cranky" customer who is always looking for trouble on every purchase, consequently, the slogan behind Supertron is, "The Tube with the sensible guarantee."

(Tested and Approved by RADIO WORLD)

Business Opportunities Radio and Electrical

Rates: 50c a line; Minimum, \$1.00

RADIO BATTERY ELIMINATOR, that can be retailed for less than \$20 and make good profit; manufactured on contract if desirable. Box A, Radio World.

RADIO AND MUSIC STORE; established over 5 years; busy cross-town thoroughfare; reasonable rent. 451 West 125th St., New York City.

MACHINE SHOP, fully equipped for making tools, dies, special machines and parts, metal stamping; suitable accommodations for inventors. Link Manufacturing Co., 151 Lafayette St., New York City.

WANTED—Automotive or Radio Product. Established manufacturer with large factory and sales organization and successful experience in manufacturing and marketing automotive and other metal products is open to add article of proven merit to his line; please give full particulars. Box 2, Radio World

Coming Events

- JUNE 4 to 6—Conference of Electrical Jobbers' Assn., Homestead Hotel, Hot Springs, Va.
- JUNE 7 to 13—Music Industries, Chamber of Commerce Convention, Drake Hotel, Chicago, Ill.
- JUNE 8 to 11—Annual meeting, Associated Manufacturers of Electrical Supplies, Homestead Hotel, Hot Springs, Va. Radio Section meets June 10.
- JUNE 15 to 18—Radio Display Show, Hotel Chase, St. Louis, Mo.
- AUG. 22 to 28—3d Annual Pacific Radio Exposition, Civic Auditorium, San Francisco. Write P. R. E., 905 Mission St., San Francisco.
- SEPT. 5 to 12—Third annual National Radio Exposition, Ambassador Auditorium, Los Angeles, Cal. Address Waldo K. Tupper.
- SEPT. 6 to 12—National Radio Exposition Grand Central Palace, N. Y. C. Write American Radio Exp. Co., 322 Fifth Ave., N. Y. C.
- SEPT. 14 to 19—Second Radio World's Fair, 25th Field Artillery Armory, Kingsbridge Road and Jerome Ave., N. Y. C. Write Radio World's Fair, Times Bldg., N. Y. C.
- SEPT. 14 to 19—Pittsburgh Radio Show, Motor Square Garden. Write J. A. Simpson, 420 Bessemer Bldg., Pittsburgh, Pa.
- SEPT. 21 to 23—International Radio Exposition, Steel Pier, Atlantic City, N. J.
- SEPT. 23 to OCT. 4—International Wireless Exp., Geneva, Switzerland.
- SEPT. 28 to OCT. 3—National Radio Exposition, American Exp. Palace, Chicago. Write N. R. E., 440 S. Dearborn St., Chicago, Ill.
- OCT. 5 to 10—Second Annual Northwest Radio Exposition, Auditorium, St. Paul, Minn.
- OCT. 5 to 11—Second Annual Radio Show, Convention Hall, Washington, D. C. Write Radio Merchants' Association, 233 Woodward Bldg.
- OCT. 12 to 17—St. Louis Radio Show, Coliseum. Write Thos. P. Convey, manager, 737 Frisco Bldg., St. Louis, Mo.
- OCT. 17 to 24—Brooklyn Radio Show, 23d Regt. Armory. Write Jos. O'Malley, 1157 Atlantic Ave., Brooklyn, N. Y.
- OCT. 19 to 25—Second Annual Cincinnati Radio Exposition, Music Hall. Write to G. B. Bodenhorf, care Cincinnati Enquirer.
- NOV. 19 to 25—Milwaukee Radio Exp., Civic Auditorium. Write Sidney Neu, of J. Andrae & Sons, Milwaukee, Wis.
- NOV. 17 to 22—4th Annual Chicago Radio Exp., Coliseum. Write Herrmann & Kerr, Cort Theatre Bldg., Chicago, Ill.
- DEC. 1 to 6—Boston Radio Show, Mechanics' Hall. Write to B. R. S., 209 Massachusetts Ave., Boston, Mass.

Literature Wanted

THE names if readers of RADIO WORLD who desire literature from radio jobbers and dealers are published in RADIO WORLD on request of the reader. The blank below may be used, or a post card or letter will do instead. Trade Service Editor, Radio World, 1493 Broadway, New York City. I desire to receive radio literature.

Name

City or town.....

State

Are you a dealer?.....

If not who is your dealer?.....

His name

His Address

- T. H. Leonard, c/o Remington Typewriter Co., Cedar Rapids, Ia.
- C. M. Donahan, Portland, Me.
- A. H. Curtin, 512 East Taylor St., Syracuse, N. Y.
- W. H. Workman, 4518 14th St., East, Vancouver, B. C.
- Thomas McGlove, 955 6th Ave., Astoria, L. I., N. Y.
- G. R. Hawks, 8 Pearne Ave., Cortland, N. Y.
- I. C. Smith, Saco, Montana.

SOME RECENT SPECIALS

THE DIAMOND OF THE AIR AS A 2-CONTROL SET, by Herman Bernard. This is the circuit that is sweeping the country. Four tubes; loop or aerial. Send 30c for May 23 and 30 issues of RADIO WORLD, 1493 Broadway, New York City.

BABY PORTABLE SET
How to make it. See RADIO WORLD, dated May 16, 15c per copy, or start your subscription with that number. RADIO WORLD, 1493 Broadway, New York City.

A 3-TUBE REFLEXED NEUTRODYNE, by Percy Warren. Send 15c for May 16 issue, RADIO WORLD.

A DX TRANSMITTER, by C. H. West, May 23 issue, RADIO WORLD, 15c.

IS THE JOBBER DOOMED?

CHARLES FRESHMAN has decided to place his Fall line direct with authorized agents, cutting out the jobber and distributor entirely. The reason is obvious. A strong undercurrent of shiftiness flows through the jobbing sea. Too many a jobber goes in business on credit and will pay "if he can." This type would recklessly cut prices almost down to production cost. He thinks nothing of his principal, the firm that has put many, many thousands of dollars into research, production and advertising. He will secretly rebate discounts to dealers or even sell retail, until the erstwhile jobber is a trade ploylot. He cheats his main backer—the manufacturer—but not for long. There are, of course, reputable jobbers, most of them banded in associations, but unless the back-stabber is eliminated the jobbing industry will disappear from radio. Freshman is not the first to cut out jobbers.

Weapons to Use Against Static

By Percy Warren



PERCY WARREN

HOW many hundreds of kinks have come out, all supposed to get rid of static entirely! It is yet impossible to rid the air of such strays. All that can be done is to reduce static to some extent and even then you may have to reduce the actual volume of the radio signals. By inserting a crystal in your set you reduce static but you also reduce the total volume.

What is static? Static consists of strays or electrical disturbances in the atmosphere. Some say that it is caused by lightning (when two clouds are supposed to hit each other). One of the most common questions is: Why is it that the stray is received all over the dials? When a spark transmitter emits a radio-frequency wave, which is tuned to a specific wavelength, the spark can be tuned out, but with some difficulty on account of the high decrement, but when static is transmitted there is no specific wavelength on which it is sent out, the decrement being tremendously high. This is a natural cause and cannot be eliminated, although it can be reduced. Since we can reduce static with a crystal detector, let us do so, as the ratio of the static to the signal strength can be reduced, in other words, the signal can be given the better of the argument.

The following is a list of devices that help in reducing the strays in any radio receiver: a potentiometer in series with the antenna, which is really a resistance in the antenna; a 1" gap shunted across the antenna and the ground; a special clarifier (nothing more than some inductances and capacities connected in series and in parallel, so as to reduce the total flow of current in the antenna system), and the old crystal, which may either be placed in series with the antenna or used in place of the detector vacuum tube.

A crystal detector is the best static reducer of the whole batch, because it does not cost much and it improves the quality of the signals, since it cannot amplify, therefore cannot distort. The crystal detector only rectifies signals. It has no plate on which B battery current can be loaded and that is why it absolutely refuses to distort.

There is mechanical static, usually called "man-made static," that is caused by proximity of the receiver to leaky power lines, static machines, X-ray machines, telephone lines, cable lines, trolley lines, power houses and telegraph lines. Static of this nature usually cannot be done away with, unless the cause is removed. Place the antenna at right angles to the lines or shield the antenna with some copper tubing 6" in diameter, which should be placed around the lead-in all the way down from where the lead-in begins until it ends.

International Parley

To Be Held In 1927

WASHINGTON.

WHILE no action has yet been taken on the recommendation of the League of Nations that the International Radio Conference called by the United States to meet in Washington this fall be postponed until 1927, officials in a position to know are inclined to believe the request will be granted.

14 STATIONS ON HIGHER POWER

PERMISSION to use higher power has been granted by the Department of Commerce to the following stations:

KFAB, Lincoln, Neb., to increase to 500 watts; KFKX, Hastings, Neb., 2,000; WBZ, Springfield, Mass., 2,000; WDBS, Dayton, Ohio, 500; WEAJ, New York, 2,500; WGAQ, Shreveport, La., 250; WGY, Schenectady, 2,000; WHA, Madison, Wis., 750; WKAR, East Lansing, Mich., 750; WLW, Harrison, Ohio, 5,000; WOC, Davenport, Iowa, 2,000; WOAI, San Antonio, Texas, 1,000; WRC, Washington, D. C., 1,000, and WSAI, Mason, Ohio, 5,000.

List of Stations

(Concluded from page 14)

Station	Owner and Location	Meters
WRAX	Flexon's Garage, Gloucester City, N. J.	268
WRBC	Immanuel Lutheran Church, Valparaiso, Ind.	278
WRC	Radio Corp. of Am., Washington, D. C.	469
WREO	Reo Motor Co., Lansing, Mich.	286
WRHF	Radio Hospital Fund, Washington, D. C.	256
WRK	Doron Bros. Elec. Co., Hamilton, O.	270
WRM	University of Illinois, Urbana, Ill.	273
WRR	Dallas Police and Fire Dept., Dallas, Texas	261
WRW	Tarrytown Research Laboratory, Tarrytown, N. Y.	273
WSAB	S. E. Mo. State Teachers' College, Cape Girardeau, Mo.	275
WSAC	Clemson Agricultural College, Clemson College, S. C.	337
WSAD	J. A. Foster Co., Providence, R. I.	256
WSAG	Gospel Tabernacle, St. Petersburg, Fla.	266
WSAI	U. S. Playing Card Co., Cincinnati, O.	326
WSAJ	Grove City College, Grove City, Pa.	229
WSAN	Allentown Call, Allentown, Pa.	229
WSAP	City Temple, New York, N. Y.	263
WSAR	Doughty & Welch Elec. Co., Fall River, Mass.	254
WSAX	Chicago Radio Laboratory, Chicago, Ill.	268
WSAZ	Chase Electric Shop, Pomeroy, Ohio.	244
WSB	The Atlanta Journal, Atlanta, Ga.	428
WSKC	World's Star Knitting Co., Bay City, Mich.	261
WSL	J. & M. Elec. Co., Utica, N. Y.	242
WSMB	Saenger Amuse. Co., New Orleans, La.	319
WSOE	School of Engineering, Milwaukee, Wisc.	246
WSRF	Harden Sales & Service Co., Broadlands, Ill.	233
WSR	Radio Co., Hamilton, Ohio.	253
WSUI	State University of Iowa, Iowa City, Iowa	484
WSY	Alabama Polytechnic Institute, Auburn, Ala.	250
WTAB	Fall River Daily Herald, Fall River, Mass.	266
WTAC	Penna. Traffic Co., Johnstown, Pa.	266
WTAL	Toledo Radio & Elec. Co., Toledo, O.	253
WTAM	Willard Storage Battery Co., Cleveland, Ohio	389
WTAP	Cambridge Radio Elec. Co., Cambridge, Ill.	243
WTAQ	S. Van Gordon & Son, Osseo, Wis.	254
WTAR	Reliance Radio & Elec. Co., Norfolk, Va.	261
WTAS	Charles E. Erbsstein, Elgin, Ill.	303
WTAT	Edison Elec. Ill. Co. (Portable), Boston, Mass.	242
WTAU	Ruggs Battery & Elec. Co., Tecumseh, Neb.	244
WTAW	Agricultural & Mech. College, College Station, Tex.	276
WTAX	Williams Hardware Mfg. Co., Streator, Ill.	231
WTAY	Oak Leaves Broadcasting Assn., Oak Park, Ill.	250
WTAZ	T. J. McGuire, Lambertville, N. J.	261
WTG	Kansas State Agricultural College, Manhattan, Kas.	273
WTIC	Travelers Insurance Co., Hartford, Conn.	347
WWAD	Wright & Wright, Inc., Philadelphia, Pa.	250
WWAE	Alama Ballroom, Joliet, Ill.	242
WWAO	College of Mines, Houghton, Mich.	244
WWI	Ford Motor Co., Dearborn, Mich.	266
WWJ	Detroit News, Detroit, Mich.	517
WWL	Loyola University, New Orleans, La.	275

THE SHORT-WAVE RECEIVER REIN-ARTZ WILL USE IN ARCTIC. Full wiring directions. Send 15c for May 16 issue, RADIO WORLD, 1493 Broadway, New York City.

RADIO PRIMER

(Concluded from page 10)

office, motored home just a little earlier than usual, to be greeted at the porte cochere by the strains of luncheon music from the Waldorf-Astoria. The butler proudly explained he had just finished charging the A battery. This was Mr. Astorfield's pet battery, for anything designated "A-1" or simply "A" struck a favorite pitch in his bonded bosom. For once Mr. Astorfield evidenced at least a semi-technical interest in radio. Asked he:

"Jukes, how does one charge a battery?"

The butler explained that a battery charger was connected to the lighting main, through two leads to the wall plug, and that two other leads from the charger were connected to the terminals of the battery.

"Let me see where this was done," commanded Mr. Astorfield. His tone of voice was not rough, yet it suggested nothing of that solicitude which accompanies announcement of a bonus untimed with cancellation of the Summer vacations.

Down to the cellar they went, the cellar being a place unfrequented by Mr. Astorfield; Jukes was in fact the chief bottle totter.

"I smell something," said the master of the house.

"Nothing," the servant of the house had the temerity to contradict. He thought to himself: "I wonder if he means a rat?"

"Jukes!" said Mr. Astorfield sharply. His voice was most upraising. A calling-down from Sir Hubert was rebuke indeed. "When I say a thing I am not to be contradicted—in this house. I smell fumes of sulphuric acid. Jukes, when you charged the battery you did not remove the vent caps. Those round screw-knobs over the apertures through which the distilled water is poured are the vent caps, Jukes. When charging a battery you must take them off, otherwise the concentration of fumes may prove disastrous. Mr. Finkelwroth, the president of the Quicksale Storage Battery Company, a \$1,000,000 Delaware corporation, paying 7 per cent., had a visiting chat with me at the office today."

* * *

HAVING heard enough of this phase of trouble in Radio Lane, I dropped softly from my uncomfortable perch at the cellar window of the house of unwelcome, and sauntered on to patches of things home-made. In one shack I found a heated discussion in progress on the advisability of grounding the A battery, the effect it has on oscillations, tuning, etc. Although Prof. Marius Latour claims a patent on this, nobody has been able to prevent oscillations by this method, nor affect tuning, nor produce any noticeable alteration, in derogation or improvement of the more conventional system. But there was nothing to be said authoritatively against the practice.

Much confusion attends the connections to the coil in the aerial circuit on such occasions when minus A is grounded. If a radio-frequency transformer—a coil of two windings, one smaller than the other—is regarded as upside-down, with the primary or small coil on bottom, the connections may be made as follows: top terminal of coil, beginning of secondary, to grid; end of secondary, connected to adjoining beginning of primary and to ground and minus A; end of primary, bottom terminal of the RFT, to aerial. Thus, the coil may be made in a single winding having one tap, the common connection of minus A and ground going to this tap.

Resistance AF in a RF Set That Gets DX on 2 Controls

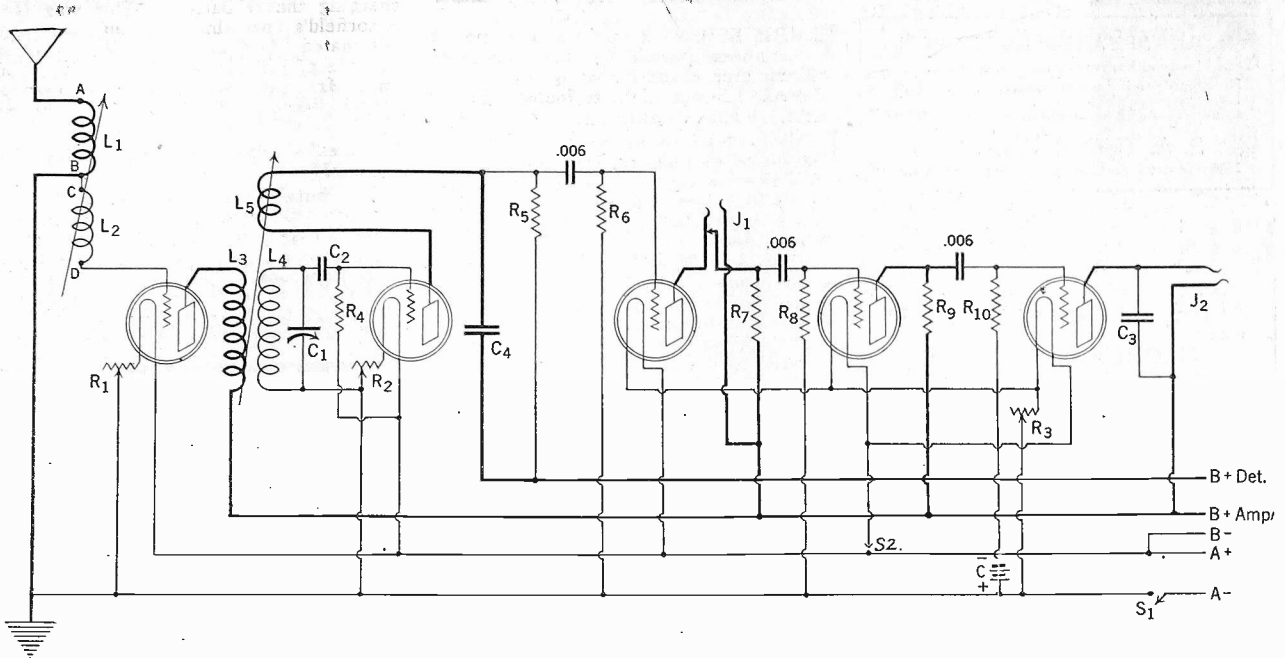


FIG. 1. A 5-tube set, comprising a stage of untuned RF, a regenerative detector and three stages of resistance-coupled AF. If a home-made coil is to be used for L1L2, or a standard variometer, tapped at midpoint, a third control may be included, but it is not necessary. The tone quality from this set, when using good resistors, is superb. R5, R7 and R9 are .1 meg.; R6, 1 meg.; R8, 5 meg.; R10, 25 meg.

By Capt. P. V. O'Rourke

USING both the "peak" transformer, of the so-called untuned type, as well as a tuned transformer (with tickler) in a 2-tube receiver, and adding three stages of resistance-coupled audio-frequency amplification, you have a circuit which is simple to tune and produces excellent signal quality. The volume is enough to satisfy anybody, and the use of resistance coupling in the audio stages gives a higher degree of audibility than the AF transformer method. Where the transformer on the AF side is louder than the resistance, it is less distinct, hence resistance is a net overall gain for those who are particular about quality.

The only coil necessary to make is L3 L4L5, a 3-circuit coupler, or a commercial product may be used. If home-made, the coil may consist of ten turns of No. 24 double silk covered wire for the aperiodic primary L3, 43 turns of the same kind of wire, wound in the same direction, for L4, and 26 turns of No. 26 single silk covered wire for the tickler L5. The stator form windings, L3L4, are on a 3 1/2" diameter tubing. The primary is begun near the top circumference, then terminated after the tenth turn. The secondary is begun right where the primary ended. The form for the tickler is 2 1/2" diameter and 2 1/2" high. The stator form may be 3/2 or 4" high. No particular attention need be paid to the direction in which the tickler is wound, as the connections thereto should be made one way, then the other, to see which works better.

The transformer in the aerial circuit is

the "fixed" one and should be a commercial product. As such is often used for interstage coupling it may have the binding posts at the terminals marked P, B, G and F, in which case P would correspond to A in Fig. 1, B would be B, C would be F and D would be G. The manner of connection is to secure the aerial lead to the P post (which may be marked A in some types) and connect the ground to the B post (which may be Grd. on some transformers). Now connect a wire from the end of the primary (B or Gnd, shown as B in Fig. 1) to the end of the secondary (F, shown as C in Fig. 1). That leaves the remaining secondary connection, G, (or, in Fig. 1, D) to be joined to the grid of the radio-frequency tube, at left, Fig. 1. This method of conductive coupling sometimes gives more volume and does not affect the tuning.

Optional Home-made Coil

The use of the fixed type of transformer, L1L2, eliminates one control. An arrow is shown in Fig. 1, indicating that this coil may be variable, and that is for those who care to make an inductance at home that will serve the purpose. The commercial product is simpler and preferable, however, those desiring to make a coil which may be regarded as a substitute may use No. 24 double silk covered wire, winding 33 turns on a spider-web form and 33 turns on another spider-web form, mounting both coils on the baseboard in close inductive relationship. One end of one coil is joined to one end of the other. This is a variometer effect. Put a horseshoe magnet, about 3" high, right behind the coils, in upright position. A piece of tin may be used for fastening the magnet to the baseboard. From the foregoing instructions as to wiring the fixed RFT the connections may be followed quite easily, since the common joint of the two coils goes to ground and minus A, the other terminals to aerial and grid respectively. If L1L2 is a home-made

(Continued on page 26)

This Nameplate FREE



A BEAUTIFUL colored nameplate to put on the panel of the Diamond of the Air will be furnished free to all. Send in your request now, if you haven't done so before.

Directions For Use

Take the nameplate and immerse it for two minutes in a glass of water, making sure that the entire nameplate is covered with the water. When you insert it in the water, the paper will coil up and only after it starts to uncoil, take out and place on a piece of blotting paper. Take a pin and lift off the nameplate gently, to get it transferred to the blotter. Do not injure the nameplate. You won't if you take care. On your panel draw a line representing where the top of nameplate is to go. By coiling back the blotter or other piece of absorbant paper you can see the nameplate top sufficiently to justify it with the line on the panel. Press firmly and nameplate will stick to panel. Allow to dry.

All nameplate requests received up to May 26 have been complied with, so if you didn't get your nameplate, please write to Nameplate Editor, RADIO WORLD, 1493 Broadway, New York City.

The nameplate is of the decalcomant or transfer type.

Rules for Aerial Safety

By Feodor Rofpatkin

EVERY fan who is contemplating installing an antenna out of doors should know the rules and regulations as

laid down by the National Board of Fire Underwriters. They follow:

The outside antenna shall not pass over or under electric light or power wires of any circuit carrying current of more than 600 volts, or railway or feeder wires, nor shall it be located so that a failure of either antenna or of the above mentioned electric light or power wires can result in a contact between the antenna and such electric light or power lines.

The antenna shall be so constructed and installed that a wind will not allow the wire to sag and swing and thereby touch the electric light and power lines.

All splices and joints in the antenna, unless made with approved clamps or splicing devices, shall be soldered.

All insulation on the antenna shall be of the highest grade, the material being of mica or of porcelain.

The lead-in wire shall be of copper, approved copper-clad steel or other approved metal which will not corrode excessively, and in no case shall they be smaller than No. 14 B. & S. gauge except that approved copper-clad steel not less than No. 17 B. & S. gauge may be used.

The lead-in wires on the outside of buildings shall not come nearer than four (4) inches to electric light or power wires, unless separated therefrom by a continuous and firmly fixed non-conductor that will maintain permanent separation. The non-conductor shall be in addition to any insulation on the wire.

The lead-in wires shall enter the building through a non-combustible, non-absorptive insulating bushing.

Each lead-in shall be provided with an approved device properly connected and located (inside or outside, preferably outside) as near as is practicable to the point where the wire enters the building. The protector shall not be placed in the immediate vicinity of ignitable stuff, or where exposed to inflammable gases, or dust, or flying of combustible materials.

The protective device shall be an approved lightning arrester which will operate at a potential of 500 volts for the receiver and at least 1000 volts for a 5 watt transmitter.

LOUD SPEAKER RECEPTION

from either coast on three tubes.

- Blueprint and instructions.....\$1.00
- Necessary low loss coil.....\$2.50
- Beautiful finished instrument.....\$35.00

S. A. TWITCHELL CO.

1930 Western Avenue Minneapolis, Minn.

KITS

- We carry all standard kits in stock.
- Freshman Masterpiece Kit.....\$9.50
- Baldwin-Pacific Super Kit.....8.95
- Aemo Reflex S Kit.....59.50
- Ultradyne Kit.....25.50
- Bremer-Tully Kit.....21.25
- Harkness Counterflex.....31.50

SAVE MONEY
Send Money
Order Now

GEORGE C. SPROULS


5739 N. SIXTH ST. PHILADELPHIA, PA.

The Five Tube Set which startled the World!

FRESHMAN MASTERPIECE

Line of New and Improved Radio Frequency Receiving Sets.

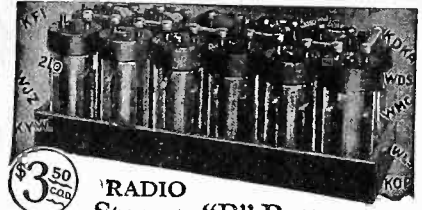For Sale by Authorized Freshman Dealers Only



RADIO Storage "B" Battery

12 Cells 24 Volts
Economy and performance unheard of before. Recharged at a negligible cost. Approved and listed as Standard by leading Radio Authorities, including Pop. Radio Laboratories, Pop. Sci. Inst., Standard, Radio News Lab., Lefax, Inc. and other important institutions. Equipped with Solid Rubber Case, an insurance against acids and leakage. Extra heavy glass jars. Heavy rugged plates. Order yours today!
SEND NO MONEY Just state number of batteries wanted and we will ship day order is received. Extra Offer: 4 batteries in series (96 volts), \$15. Pay expressman after examining batteries. 5 per cent discount for cash with order. Mail your order now!

WORLD BATTERY COMPANY
1219 So. Wabash Ave., Dept. 82, Chicago, Ill.
Makers of the Famous World Radio "A" Storage Battery
Prices: 6-volt, 100 Amp. \$15.00; 120 Amp. \$18.50; 140 Amp. \$26.00.
All equipped with Solid Rubber Case.

World FOR STORAGE BATTERIES RADIO

OPERATONE RADIO TUBES



Guaranteed the Best
Type 201A
Type 200
Type 199
199 with Standard Base EACH \$1
Type WD12 \$1.25
Mail Orders Filled. Dealers, Jobbers, Write for Discounts

OPERATONE TUBE CO.
Room 411
324 West 42nd Street, New York City

The LARGEST RADIO STORES IN AMERICA

Hook-ups!

All the latest and best Kits in our new RADIO CATALOG



FREE
NO other Radio Catalog includes such a complete assortment of the best and latest Knock-Down Kits, Parts and Accessories. You need this book—Write for your FREE copy today!

We Save You Money!
Our business is to buy up manufacturers' and government surplus stocks, jobber and dealer bankrupt stocks—but only brand-new, fully guaranteed, nationally advertised apparatus. Our catalogue crammed with bargains.



509 So. State St., CHICAGO, ILL., Dept. R.W.6
THE DIAMOND OF THE AIR AS A 2-CONTROL SET, by Herman Bernard. This is the circuit that is sweeping the country. Four tubes; loop or aerial. Send 30c for May 23 and 30 issues of RADIO WORLD, 1493 Broadway, New York City.

THE SHORT-WAVE RECEIVER REINARTZ WILL USE IN ARCTIC. Full wiring directions. Send 15c for May 16 issue, RADIO WORLD, 1493 Broadway, New York City.

A SIMPLE 1-TUBE DX SET FOR THE NOVICE, by Percy Warren. Send 15c for May 23 issue, RADIO WORLD.

\$2.00 ALL TYPES

A GUARANTEED Guarantee!

Identified by a serial number on each SUPERTRON tube

A GUARANTEE WITHOUT MEANS OF IDENTIFICATION MEANS UNASSURED SATISFACTION—IT MEANS NOTHING MORE OR LESS THAN "MAY-BE"—THINK IT OVER.

BUY SUPERTRONS WITH ABSOLUTE ASSURANCE

A Guarantee Certificate bearing a Serial Number accompanies each SUPERTRON tube which has a number that corresponds with the Guarantee Certificate.

SUPERTRON is all a tube can possibly be.

At the Public Demand Price \$2.00 All Types

SUPERTRON MFG. CO., Inc.
32 UNION SQUARE NEW YORK

EXPORT DIVISION
The M. Simons & Son Co., 220 B'way, N. Y.


REG. U.S. PAT. OFF.
SUPERTRON
A GOOD TUBE.

Sets In N. S. Wales Schools Officially Approved

WASHINGTON.
AFTER successful experiments, wireless apparatus will be permitted in public schools for the use of parents and citizens' associations by the New South Wales minister for education. It is expected that such a course will bring isolated country centers in touch with Sydney, and the country schools will thus become important social centers, especially in the evenings.

The DAVEN SUPER AMPLIFIER

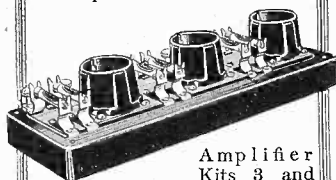will give to your receiver ample volume of wonderful quality. Completely assembled, easy to attach, low "B" Battery consumption.




Amplifier Kits 3 and 4-stages.

The Resistor Manual at your Dealer 25 cents. Post-paid 35 cents.

The Sons of Mars
DAVEN RADIO CORPORATION
"Resistor Specialists"
NEWARK, N. J.

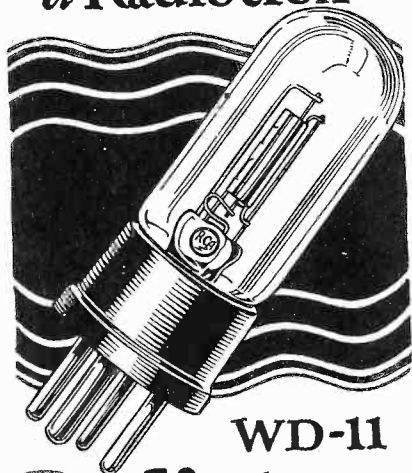It isn't a genuine WD-11 unless it's a Radiotron



WD-11 Radiotron

THE BABY PORTABLE, by Herbert E. Hayden. A 1-tube DX set on a 7 1/2 x 5 1/4" panel. Send 30c for May 16 and 23 issues to RADIO WORLD, 1493 Broadway, New York City.

A 3-TUBE REFLEXED NEUTRODYNE, by Percy Warren. Send 15c for May 16 issue, RADIO WORLD.

JOIN THE A. B. C.

A B. C. stands for the American Broadcast Club. Join it today. It involves no dues or payment of any kind, and no obligations. It was founded by RADIO WORLD simply to unite the broadcast listeners and radio fans in general in a common bond to promote their welfare as occasion requires. Send your name and



Famous for Quality and Service
Amplatron Tubes
Bonded to Give Service \$3
List Price
Send in your old and burnt out Tubes—We will send you now AMPLATRON—any model—at \$2.50
Dealers and Jobbers—Write for Discounts
Pennant Radio Laboratories
Dept. R. W., 28 Central Ave., Newark, N. J.

address to A. B. C. Editor, RADIO WORLD, 1493 Broadway, New York City.



For Battery, Antenna and Ground Leads—

Jones MULTI-PLUG

THE STANDARD SET CONNECTOR

HOWARD B. JONES

618 S. CANAL STREET CHICAGO

The THREE BLESSINGS OF RADIO CAN ONLY BE OBTAINED WITH A KANE ANTENNAE

- Blessing No. 1—The Kane Antennae absolutely eliminates all power noises.
- Blessing No. 2—The Kane Antennae cuts re-radiating squeals at least 50 per cent.
- Blessing No. 3—The Kane Antennae will reduce Static at least 50 per cent.

Now that Old Man Static is beginning to get in his usual summer work of ruining radio reception with his discordant, crackling noises, wouldn't you like to rap his fingers and make him let up a whole lot?

Static and Re-radiating squeals both cut 50 per cent—Power Interference absolutely cut out. Figure it out for yourself! Can you afford to be without a Kane Antennae? Then why not order one today?

"I had no idea that an aerial could make so much difference in a set," writes Mr. George C. Pratt, Secretary of the Beaver Cove Lumber & Pulp Co., Ltd., Vancouver, B. C. "I will be glad to recommend this aerial to anyone in this vicinity as the best on the market, and I have tried every kind I have heard of," Mr. Pratt also states.

And What About Old Man Static?

Are You Getting All the Distance You Want?

We will sell you working drawings with instructions for erecting this wonderful Antennae for a dollar bill. If after looking over the drawing you decide you would rather have a factory-built Antennae than build one yourself, we will take back the drawing and allow you full purchase price on an order for an Antennae.

The Special Kane Antennae for Radiola Super-Hets..... \$6.50
The Regular Kane Antennae for all other sets that use a ground connection..... 13.00
Working Drawings with Instructions for Erecting..... 1.00
(Stamps not accepted)

Postpaid to any part of the United States or sent C. O. D. when 25% of purchase price accompanies order.

Canadian orders filled by The Kane Antennae Company of Canada, 1220 Seymour Street, Vancouver, B. C.

"Hear As You Have Never Heard Before"

THE KANE ANTENNAE COMPANY Dept. W, HOQUIAM, WASHINGTON

The enormous volume of business we are now doing has compelled us to purchase our own factory with over half an acre of floor space in Hoquiam (Indian name, meaning "Hungry for wood"), the most westerly city in the United States.

Vancouver, B. C., May 16, 1925.
Gentlemen:

I have received the Kane Antennae shipped a couple of weeks ago, and have installed same as per your instructions.

I had no idea that an aerial could make so much difference in a set, as I thought I was getting excellent reception with the old single aerial, but there is no comparison in the present reception of the set with the new aerial, as with the old one.

I have been informed by several radio friends of mine that the static has been so bad for the past ten days that they were unable to tune in any except local stations, but outside of a very few instances I have not heard static since your Antennae was installed.

The antennae is about 45 feet from the ground with the lead-in facing southeast. The counterpoise is about 25 feet beneath the antennae. I have had no difficulty in tuning in KDKA, WCCO, WOC, WEBB; in fact, I am getting all the distance I want with very little interference.

I will be glad to recommend this aerial to anyone in this vicinity as the best on the market, and I have tried every kind I have ever heard of.

Yours very truly,
GEO. C. PRATT.

The 2-Control Resistance Set

(Continued from page 23)


inductance, the variometer setting is varied after the set is complete until the coupling is best for the whole wavelength band. This will be found to be the coupling which gives loudest signals around

GLOBE Low-Loss Tuners

Always give best results

Globe Radio Equipment Co.

217 West 125th Street New York

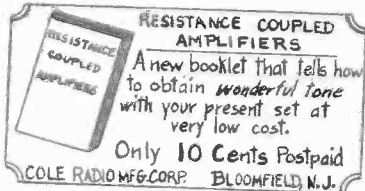

Static

"HOW TO KEEP STATIC OUT OF YOUR RADIO"

New Copyrighted Plans, \$1.00

LEON LAMBERT
WICHITA, KANSAS

List of Parts

- One untuned RF transformer, L1L2
- One 3-circuit tuning coupler, L3L4L5.
- Two 20-ohm rheostats, R1 and R2
- One 6-ohm power rheostat, R3.
- One detector grid leak, 2 meg., R4
- Two fixed condensers, .002, C3, C4
- One fixed grid condenser, .00025 mfd., C2
- One .0005 mfd. variable condenser (23 plates), C1.
- Three plate resistors and three grid leaks for the audio stages, as described in text, R5, R6, R7, R8, R9 and R10.
- Two push-pull or toggle A battery switches, S1, S2.
- One single closed circuit jack or double open circuit jack, J1.
- One single open circuit jack, J2.
- One 4½-volt C battery.
- Two or three 45-volt B batteries.
- One A battery.
- Five standard sockets.
- Five tubes, 6-volt storage battery type preferred.
- Two 4" dials, one with vernier.
- One 7x18" panel.
- One 17x9" baseboard.
- One cabinet.
- Aerial, leadin wire, internal connecting wire, ground clamp, lightning arrester, jack plug, earphones, speaker.

450 meters, or a little lower. Although this coil is variable, once the setting is obtained it remains permanent, unless, of course, the constructor wants to put the set in the 3-controls class.

Parts Used

R1 and R2 are rheostats to suit the type of tubes used. R3 is a power rheostat, 6 ohms, since it controls three tubes at once (the audio circuit). It is just like any other rheostat, except that the wire is stronger, so that the instrument will not heat up under the comparatively heavy current. Most rheostats of the general run will heat up on three tubes.

C4 is important in this or any other regenerative circuit followed by resistance AF. It, like C3, is .002 mfd., a fixed condenser. R4 is a 2 megohm leak, C2 a .00025 mfd. fixed grid condenser.

The resistors used in the set throughout are standard products. R5, R7 and R9 are all of the same value, 100,000 ohms (.1 meg.) R6, R8 and R9 are grid leaks, respectively 1,000,000 ohms (1 meg.);

When in Philadelphia Stay at the

HOTEL WALTON

BROAD AND LOCUST STREETS

PHILADELPHIA

Half square from everywhere, in the heart of the shopping and theatrical districts. Close to all Railroad Terminals.

Rooms

Without Bath, \$3.00

With Bath, \$3.50 up

Special Luncheon, 85c
Unusual Dinner, \$1.50

As well as a la carte service

EUGENE G. MILLER, Mgr.
H. C. CROWHURST, Asst. Mgr.

500,000 ohms (.5 meg.) and 125,000 (25 meg.). These values proved best over a long period of experimenting. The isolating condensers are .006 mfd. They keep the plate potentials off the grid and afford capacitative interstage coupling.

S1 and S2 are push-pull or toggle switches. S2 cuts off the last two audio tubes, since the earphones are to be used on the first resistance AF stage, a single closed circuit jack being used (J1) or, if one isn't handy, the more usual double open circuit jack. J2 is a single open circuit jack.

The C battery is inserted in the last stage for better effects and for economy.

WRITE FOR NEW CATALOGUE

Home of Semi-Assembled Kits
THE RADIO SHACK

55 Vesey Street Dept. E-156 New York

ULTRA-VERNIER TUNING CONTROL

A VERNIER DIAL ON WHICH YOU CAN PENCIL RECORD THE STATIONS. GEARED 20 TO 1. SILVER FINISH \$2.50 - GOLD FINISH \$3.50

PHENIX RADIO CORP., 116 E. East 25 St., N.Y.C.

"HOW TO MAKE—"

The following constructional articles have appeared in recent issues of RADIO WORLD:

- Sept. 6, 1924—A simplified Neutrodyne with Grid-Biased Detector, by J. E. Anderson.
- A Low-Loss Wave Trap, by Brewster Lee.
- Nov. 15—A Sturdy Low-Loss Coil, by Lieut. P. V. O'Rourke.
- An Ultra 1-Tube Receiver, by Bryt C. Caldwell.
- Dec. 6—A 4-Tube Super-Heterodyne Using a Variometer, by J. E. Anderson.
- A \$1 Coil Winder, by Herbert E. Hayden.
- Dec. 13—The World's Simplest Tube Set, by Lieut. P. V. O'Rourke.
- Dec. 20—A 1-Tube DX Wonder, Rich in Tone, by Herman Bernard.
- An Interchangeable Detector, by Chas. M. White.
- Dec. 27—A 2-Tube Variometer Set, by Lieut. P. V. O'Rourke.
- Jan. 3, 1925—A 3-Tube Portable That Needs No Outdoor Aerial, by Abner J. Gelula.
- Jan. 10—A Low-Loss DX Inductance, by Herbert E. Hayden.
- Jan. 17—A \$25 1-Tube DX Wonder, by Abner J. Gelula.
- Jan. 24—A Selective \$15 Crystal Set, by Brewster Lee.
- A Variometer-Tuned Reflex, by Abner J. Gelula.
- An \$18 1-Tube DX Circuit for the Beginner, by Feodor Koppatkin.
- Jan. 31—A Transcontinental 3-Tube Set, by H. E. Wright.
- An Experimental Reflex, by Lieut. P. V. O'Rourke.
- Feb. 7—The Bluebird Reflex, by Lieut. P. V. O'Rourke.
- A \$5 Home-Made Loudspeaker, by Herbert E. Hayden.
- Feb. 14—A Super-Sensitive Receiver, by Chas. H. M. White.
- A Honeycomb EFT for DX, by Herbert E. Hayden.
- Feb. 21—A 1-Tube Reflex for the Novice, by Feodor Koppatkin.
- A Set for Professional Folk, by Lieut. P. V. O'Rourke.
- A Honeycomb Crystal Receiver, by Raymond B. Wallis.
- Feb. 28—A Set That Does the Most Possible With 6 Tubes, by Thomas W. Benson.
- Three Resistance Stages of AF on the 3-Circuit Tuner, by Albert Edwin Sonn.
- March 7—Storage B Battery, by Herbert E. Hayden.
- Benson's Super-Heterodyne.
- March 14—The Reflexed 3-Circuit Tuner That You Can Log, by Herman Bernard.
- March 21—A Variable Leak, by Herbert E. Hayden.
- A 4-Tube, 3-Control Set That Gets the Most DX, by Lieut. P. V. O'Rourke.
- March 28—The Improved DX Dandy Set, by Herbert E. Hayden.
- A 3-Tube Reflex for the Novice, by Feodor Koppatkin.
- April 4—The Diamond of the Air, by Herman Bernard.
- What the New Rodion Tube Is, by Sidney E. Pinkstein.
- Sets for the DX Devotee, by Lieut. P. V. O'Rourke.
- April 11—Audio Hookups for Fine Volume and Quality as Well, by Brewster Lee.
- The Oils for the Diamond, by Herman Bernard.
- 1-Tube Distance-Getting Sets, by Lieut. P. V. O'Rourke.
- May 2—The Triplexer, by J. E. Anderson.
- May 9—A Set to Cut Static, by Feodor Koppatkin.
- Toroid Circuit with Resistance AF, by H. I. Sidney.
- A Push-Pull AF Amplifier, by Lt. Peter V. O'Rourke.
- May 16—A 3-Tube Reflexed Neutrodyne, by Percy Warren.
- The Baby Portable, by Herbert E. Hayden.
- One Tube More for Quality, by Brewster Lee.
- May 23—Powerful 3-Tube Reflex Receiver, by H. E. Wright.
- The 3-Control Diamond, by Herman Bernard.

Any copy, 15c. Any 7 copies, \$1.00. The whole 25 copies for \$2.50, or start subscriptions with any issue. Radio World, 1493 Broadway, N. Y. City.

Oh boy!

KESTER
Rosin Core
Radio SOLDER

Sure! is Safe and Simple

APPROVED BY
RADIO ENGINEERS
A GENUINE SOLDER

CHICAGO SOLDER COMPANY
4242 Wrigwood Ave. Chicago, U.S.A.

Originators and World's Largest Manufacturers of Self Fluxing Solder
YOUR DEALER CAN SUPPLY YOU

THE DIAMOND OF THE AIR AS A 2-CONTROL SET, by Herman Bernard. This is the circuit that is sweeping the country. Four tubes; loop or aerial. Send 30c for May 23 and 30 issues of RADIO WORLD, 1493 Broadway, New York City.

O'Rourke's Set

(Concluded from preceding page)

It is not a vital adjunct, although a refinement. C plus goes to A minus and C minus connects to that end of R10 (25 meg.) other than the terminal thereof that went to the grid of the last tube. About 4½ volts will suffice.

Voltage on Plates

The B battery voltage may be higher than usual for the resistance AF stages, up to 135 working very well, but 90 will perform nicely. The detector B voltage normally will have to be higher than otherwise, nearly double, in fact. About 45 volts worked excellently. However, on the B battery voltages, always try out different voltages in any set or circuit, despite any one's advice, although not going beyond the maximum called for.

Vernier Needed For C1

The variable condenser C1 is .0005 mfd., normally 23 plates, and should have vernier dial or other fine control, to facilitate tuning in stations on the lower waves.

As said before, the quality will be superb, due to the use of resistance-coupled AF and accurate resistors. Mountings are procurable commercially, and the AF stages may be placed conveniently in back of the RF and detector tubes. My favorite manner of constructing this set is to have the RF run from left to right (looking at front of panel) and the AF from right to left, so that the speaker jack, J2, is at extreme left on panel and the other jack to the right, between the condenser and tickler dials. The condenser dial should be to the left of the other dial. This system enables one to use even a 7x18" panel, although the baseboard, 17" wide long, should be more than the conventional 7" deep. About 9" would be better, for then the terminal strip can be mounted on the rear of the baseboard, too.

What the RF Tube Does

The set is as selective as the 3-circuit tuning sets which are so popular, but has greater reaching-out power. The RF tube accounts for this. On local reception, however, the presence of the RF tube is scarcely notable. This holds for all sets that have a stage of RF ahead of a regenerative detector.

AUTO RACE BROADCAST

FROM FIELD BY WGN

ON MEMORIAL DAY the Indianapolis 500-mile Sweepstakes Auto Races were broadcast by WGN, the Chicago Tribune station on the Drake Hotel. Using numerous microphones about the track and with a corps of announcers and reporters on the air, WGN brought every sound and color of the big race into fan's homes.

IN THE WEST it's "RADIO"

For Seven Years the Best
Practical Radio Magazine.

A Free Sample Copy
for the asking

PACIFIC RADIO PUB. CO.
Pacific Bldg. San Francisco

NAIL IN TREE A FINE AERIAL, SAYS SQUIER

A NAIL in a tree makes a good aerial for your portable set on your vacation. Maj. Gen. George O. Squier, former chief signal officer of the army, after many experiments, said:

"At this season of the year, when static is more pronounced and thousands of people are going into the open spaces on auto tours and camping expeditions, it is highly desirable that this very simple and efficient type of antenna should be tried out practically in the field.

"We have found in short that a living vigorous tree becomes an efficient antenna for a receiving set by driving a nail about three inches into the tree at an optimum point, usually about two-thirds of the total height of the tree, from the ground, and well within the tree top, and attaching the antenna binding post of the set to the nail by a piece of wire, the other terminal of the set being connected to the earth, or sometimes without any earth.

The resistance between the nail and the tree through the trunk and root system may be high, but this is thought to be an advantage since it retards the escape of

the varying potential of the nail due to the broadcast message and diverts it along the wire to the receiving set. Such an aerial gives a louder signal than wire alone, and one apparently free in a large measure from external disturbances. There is no definite theory to put forward at present, as many more data would have to be obtained from experience in the field.

"From a practical standpoint it makes it very simple to take radio in the auto, or into camp anywhere, by merely carrying along a piece of insulated wire and a nail to drive into the tree."

PANELS

RADION and HARD RUBBER
RETAIL ANY SIZE WHOLESALE
PRICE LIST MAILED ON REQUEST

**HARD RUBBER
SHEETS—RODS—TUBING**

Special Hard Rubber Parts Made to Order.
Send Sample or Sketch for Quotation.

NEW YORK HARD RUBBER TURNING CO.
212 CENTRE ST. NEW YORK

PANELS

FOR PRESSLEY,
SUPERDYNE,
"DIAMOND OF THE AIR,"
ETC.

CUT, DRILLED
ENGRAVED
CORTLANDT PANEL
ENGRAVING CO.

81 Cortlandt Street New York City

S-U-P-E-R-D-Y-N-E

SPECIALISTS

The Famous Wallace Low-Loss Coil for Superdyne, \$7.50
The Flawless Condenser for Superdyne, \$9.00
Superdyne Advice Free. Mail Orders Solicited.

WALLACE RADIO COMPANY, Inc.
135 LIBERTY STREET NEW YORK CITY

S. HAMMER RADIO CO.
303 Atkins Avenue, Brooklyn, N. Y.
Please send me FREE, Your NEW
RADIO CATALOG

Name
Address
City State

FILL OUT AND MAIL

"A THING OF
BEAUTY AND A
JOY FOREVER."

TYPE SA \$50
5-TUBE

American Interstate Radio
183 Greenwich St., N. Y. C.

SUMMER SPECIALS

Roberts 4-Tube Knockout Kit.....	\$42.50
Well-known 5-Tube T. R. F. Set.....	29.50
Hammerlund .0005 Condensers.....	4.00
Acme D. Coils.....	9.75
Ekko Stamp Albums.....	0.95
Brach Soldering Irons.....	1.65
Crosley Musicone Loud Speaker.....	13.95
Jewett Superspeaker.....	21.95
Little Gem Head Set.....	2.50

Send for our free summer special folder on sets and parts. Real bargains on standard parts and sets. Your opportunity to save money.

LIBERTY MAIL ORDER HOUSE
Dept. S-106 108 LIBERTY STREET, NEW YORK, N. Y.

FILL OUT AND MAIL NOW
SUBSCRIPTION BLANK

RADIO WORLD

1493 Broadway, New York City

Please send me RADIO WORLD for months, for which
please find enclosed \$.....

SUBSCRIPTION RATES:

Single Copy	\$.15
Three Months	1.50
Six Months	3.00
One Year, 52 Issues.....	6.00
<small>Add \$1.00 a Year for Foreign Postage; 50c for Canadian Postage.</small>	

SMOKESTACK PORTABLE SET

(Concluded from page 6)

adjustment. If the set does not respond to the higher wavelengths pull out the

FREE BOOKLET FOR INVENTORS

IF YOUR INVENTION is new and useful it is patentable. Send me your sketch. Z. H. POLACHEK, 70 Wall St., New York.

Reg. Patent Attorney-Engineer

NEUTRODYNE KIT \$19.75

Complete kit of licensed Neutrodyne parts, including panel, tube sockets, rheostats, jack, fixed condensers and grid leak. Neutroformers complete with variable condensers and neutrons. Every part included even to screws and wire. Easy read plans.

Send No Money Order by Postcard
Pay the Postman
RADIO SURPLUS STORES
HELENA MONTANA

For Maximum Amplification Without Distortion and Tube Noises use the well known

Como Duplex Transformers

Push-Pull
Send for Literature
COMO APPARATUS COMPANY
448 Tremont Street Boston, Mass.

WANTED IN EVERY LOCALITY

An agent to sell Biltmore Master Reflex Receivers to dealers, on our plan which allows the dealer to make summer profits equal winter profits.

The receiver with the "Guaranteed Best Tone"
BILTMORE RADIO COMPANY
Boston 30, Mass. Dept. R.W. 94 Green St.

ACME POWR-BEE

Better Than "B" Battery

NO HUM NO NOISE
Reduces the cost of radio. At your dealer's or write.

THE ACME ENGINEERING CO.
Dept. 8 LOUISVILLE, KY.
Dealers write for big sales proposition.

EVERY SET BUILDER
NEEDS
THIS




"Morsing Bus-Bar Union"

Makes for quick assembling. Repairs can be made by using Morsing Bus-Bar Union without taking set apart.

Assemble round or square Bus-Bar and solder three wires at a time. Order No. 1 for No. 14, No. 2 for 12 wire. Send 25 cents for enough for building one set, or ten dozen for \$1.00.

Newark Watch Case Material Co.
15 Ward Street Newark, N. J.

DISTRIBUTORS WANTED

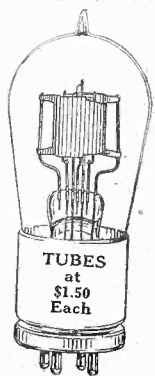

SAVE \$1.50
ON COST OF NEW
TUBES BY HAVING YOUR OLD
TUBES REBUILT


AT \$1.50 EACH

Guaranteed equal to new. Send us your tubes by parcel post. We return them parcel post, C.O.D., and try to maintain 24-hour service.

400 Old Colony Ave.
Boston, Mass.

HARVARD RADIO
LABORATORIES

USE TEMPLATE RIGHT

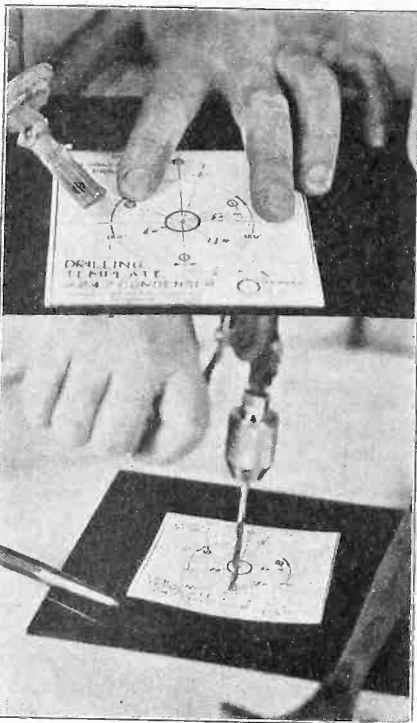

How to paste the template of a variable condenser over the central hole, which has been already drilled (top photo). If the template is laid on panel and central hole drilled from the template, the paper is subject to tear. The lower photo shows how template will move around if not securely pasted to panel. Do not on the front, where you will have the dials. Note the pencil pointing to coiling up of template on account of poor pasting.

switch S2, which automatically puts a condenser across the antenna and the ground, and if you do not get the low waves, push in S2 and pull out S1, which automatically cuts in C6, which is connected in series with the antenna. When you are not using the audio stages, push in S3, which cuts off the filaments from the A batteries.

If the set tunes broadly, reverse the secondaries of the radio-frequency transformers L6 L4 and L2. If the set distorts, increase the C battery voltage to about 8 volts instead of the conventional 4½ volts, also ground the cores of the AFT. If the signals are weak reverse the A battery leads and increase the B battery voltage of the audio-frequency amplifier tubes.

Around the cover of your portable case wrap 22 turns No. 22 SCC spaced ¼" away from each other. This is a loop. For a ground a 5" iron pipe in the wet ground where ever you may stop, connected to the Gnd. post of the set will be just right. The loop is used as the open-end antenna pictured in Fig. 1. Hence, one end of the loop is not connected, the other end going to C6. The directional effect not very great is obtained by turning the whole case.

FAHNESTOCK CLIPS

"Popular Wherever Radio Is Used"

14 Sizes in Beautiful Display Case
Dealers, write for big money-making proposition.

FAHNESTOCK ELECTRIC CO.
Long Island City, L. I.

THE DIAMOND OF THE AIR AS A 2-CONTROL SET, by Herman Bernard. This is the circuit that is sweeping the country. Four tubes; loop or aerial. Send 30c for May 23 and 30 issues of RADIO WORLD, 1493 Broadway, New York City.

EASILY-MADE CRYSTAL SETS. Send 15c for May 16 issue, RADIO WORLD.

THOUSANDS OF BARGAINS
FACTORY GUARANTEED MDSE. BY MAIL
Genuine New Radiotron or Cunningham Tubes
UV-199—200—301A—WD-11—12..... \$2.39
C299—300—301A—C11—12.....
Fresh Burgess or Eveready "B" Batteries
22 ½ Volt large size \$1.68—45 Volt \$5.00 size \$3.38
Write for Free new Complete Catalog on
Sets and Parts
STONE ELECTRIC CO., 714 Pine St., St. Louis, Mo.
All Mdse. F.O.B. St. Louis, Mo. Dept. W

Radio Tubes Exchanged



Send us your old tube—any make—any condition—and we will send you a Brand New Guaranteed Tube, of whatever type you require (except WD11), for \$1.75. All shipments by insured Parcel Post C. O. D. Send no money—order today.

\$1.75
C.O.D.


D-R-C RADIO CO.
331 S. LaSalle St. Chicago, Ill.



Federal Telephone & Telegraph Co.
Buffalo, N. Y.

Over 130 standard radio parts, each bearing the Federal iron-clad performance guarantee.

Write for Catalog

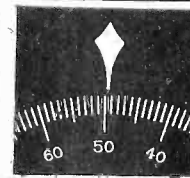

EUREKA DIAL POINTER

10c Each—Nickel Finish
Dealers Display Card.
\$3.25 Net

Obtain at your dealer's or sample mailed upon receipt of stamps.
C. W. BUTTS, INC.
42 Herden Place
East Orange, N. J.

EVEREADY

Radio Batteries

—they last longer

GEM TUBE

A Guaranteed Radio Tube

Within Reach of All

Every tube guaranteed. A tube for a dollar of \$2 value. A trial order will convince you as it has thousands of others. Send your orders at once.

Orders sent C.O.D. parcel post.

Type...201A
Type...200
Type...199
Type...199A

\$1.00

EACH

(with standard base)
Dealers. Write for Discounts
GEM TUBE CO.
Dept. W, 260 Broadway
New York City



RADIO MAILING LISTS

15870 Radio Dealers	Per M \$7.50
970 Radio Dealers in Mexico	Per List 10.00
1808 Radio Mfrs.	Per List 15.00
2324 Radio Jobbers	Per List 20.00
1125 Radio Jobbers, rated \$5,000 and up	Per List 15.00
714 Radio Jobbers, rated \$50,000 and up	Per List 10.00
597 Radio Mfrs. making complete sets	5.00
128 Radio Battery Mfrs.	2.50
125 Radio Cabinet Mfrs.	2.50
60 Crystal mounters for Wireless apparatus	2.50
25000 Radio Amateurs	Per M 7.50
625 Photograph and Music Radio Dealers	5.00
7400 Radio owners	Per M 7.50

Guaranteed 98% correct. Ask for Price List and all other lists.

A. F. Williams, Mgr., List Dept.
Established 1880
166 W. Adams Street Chicago, Ill.

A SET FOR REDUCING STATIC

with diagrams; in RADIO WORLD, dated May 9, 15c. per copy, or start your subscription with that number. RADIO WORLD, 1493 Broadway, New York City.

A POWERFUL 3-TUBE REFLEX, by H. E. Wright. Send 15c for May 23 issue, RADIO WORLD.

Tested and approved by Radio World
"TRI-TUNER"



Build Your Own Set!
 Use Arc Rad Products.
 A Three-Circuit Coil, all
 Litz wound on natural
 bakelite.


SENT **\$3.00**
 POSTPAID
 Panel shield and hook-
 ups included. Fahne-
 stock clips used.

Eliminate Soldering


ARC RAD PRODUCTS

48 South 7th Street Newark, N. J.
 EVERY PRODUCT GUARANTEED

BETTER CONTACT

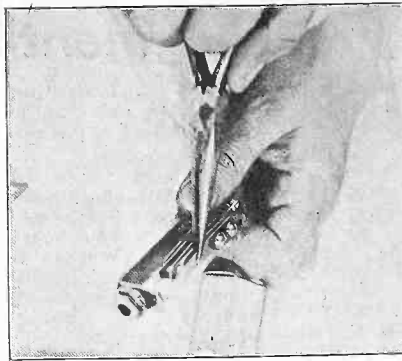

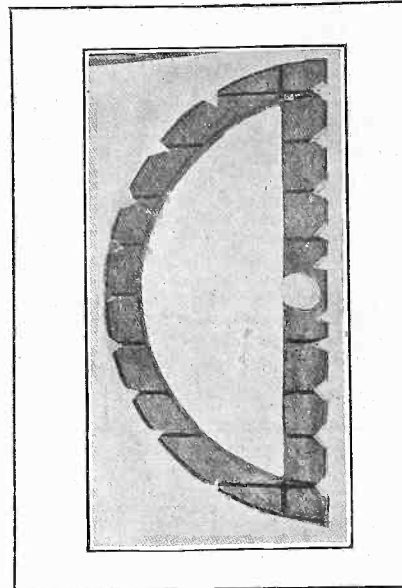LIFT the jack spring with round-nosed pliers if
 the contact is stiff; bend the spring toward its
 neighbor if the contact is poor.



ONE of the most successful substitutes for a
 variometer is the D coil the form for which is
 pictured above. It consists of a stationary coil
 and a rotor coil, wound on a D shaped piece of
 hard rubber on cardboard.

**Every Radio Fan
 should have
 this book**



**JUST OUT
 514 PAGES**

Compiled by
**HARRY F. DART,
 E.E.**

Formerly with the
 Western Electric Co.,
 and U. S. Army In-
 structor of Radio.

Technically edited by
F. H. Doane

NO MORE need you turn from book to book,
 hoping to find what you want. It is all here,
 in 514 pages crammed full of every possible radio
 detail. Written in plain language, by engineers
 for laymen. More than 100,000 sold.

IT EXPLAINS: Electrical terms
 and circuits, antennas, batteries,
 generators and motors, electron
 (vacuum) tubes, many receiving
 hook-ups, radio and audio frequency
 amplification, broadcast and com-
 mercial transmitters and receivers,
 super-regeneration, codes, etc.

Send \$1 today and get this 514-page I. C. S. Radio
 Handbook—the biggest value in radio today.

International Correspondence Schools
 Box 8791-E, Scranton, Penna.

I enclose One Dollar. Please send me—post-
 paid—the 514-page I. C. S. Radio Handbook.
 It is understood that if I am not entirely satis-
 fied I may return this book within five days and
 you will refund my money.

Name.....
 Address.....
 Check here and enclose \$1.50 if you wish the
 de luxe edition, bound in Leatheroid.

**Buy Tubes
 by Name**



WD-11

Radiotron
REG. U. S. PAT. OFF.

**THE SHORT-WAVE RECEIVER REIN-
 ARTZ WILL USE IN ARCTIC.** Full wiring
 directions. Send 15c for May 16 issue, RADIO
 WORLD, 1493 Broadway, New York City.

**A SIMPLE 1-TUBE DX SET FOR THE
 NOVICE,** by Percy Warren. Send 15c for May
 23 issue, RADIO WORLD.

A POWERFUL 3-TUBE REFLEX, by H. E.
 Wright. Send 15c for May 23 issue, RADIO
 WORLD.

A DX TRANSMITTER, by C. H. West, May 23
 issue, RADIO WORLD, 15c.

EASILY-MADE CRYSTAL SETS. Send 15c
 for May 16 issue, RADIO WORLD.

**NO STATIC
 NO DANGER
 OF LIGHTNING**

THE Antennaphone
REPLACES THE AERIAL

IMPROVES RECEPTION

Easy to install. Not attached to,
 but merely placed under the tele-
 phone. Sold with a money-back
 guarantee. AT YOUR DEALER or sent
 by mail complete with insulated wire
 upon receipt of One Dollar.
 Antennaphone Co., 90 West St., N. Y. C.

**THE ASTON CARD INDEX
 RECORD YOUR RADIO STATIONS**

Copyright
 1924 by
 S. T. Aston
 & Son



\$3.00
 Complete
 Postpaid

Telephone
 Franklin
 2159

100 Cards, Mahogany Finish or Oak Cabinet, and
 Index Dividers. A Useful Accessory to Any Set.
 Give Name of Set and Sketch of Dial Arrangement.
 Postpaid on Receipt of Cash or Money Order.
 Dealers Write for Terms.

S. T. ASTON & SON

114 WORTH STREET NEW YORK CITY

BABY PORTABLE SET. How to make it.
 See RADIO WORLD dated May 16. 15c per copy,
 or start your subscription with that number.
 RADIO WORLD, 1493 Broadway, N. Y. C.

A 3-TUBE REFLEXED NEUTRODYNE, by
 Percy Warren. Send 15c for May 16 issue,
 RADIO WORLD.

Two-For-Price-of-One Subscription Blank
For NEW RADIO WORLD Subscribers Ordering NOW

Radio World has made arrangements

This is the way to get two publications

- To offer a year's subscription for any one of the following publications
- with one year's subscription for RADIO WORLD
- RADIO NEWS or
- POPULAR RADIO or
- RADIO BROADCAST or
- WIRELESS AGE or
- RADIO DEALER or
- RADIO JOURNAL or
- RADIO (San Francisco) or
- BOYS' LIFE

- for the price of one!
- Send \$6.00 today for RADIO WORLD
- for one year (regular price
- for 52 numbers)
- and select any one of the other
- eight publications for twelve months.

- Add \$1.00 a year extra for
- Canadian or Foreign postage.
- Present RADIO WORLD subscribers
- can take advantage of this offer by
- extending subscriptions one year
- if they send renewals NOW.

RADIO WORLD'S SPECIAL TWO-FOR-PRICE-OF-ONE SUBSCRIPTION BLANK

RADIO WORLD, 1493 Broadway, New York City.

Enclosed find \$6.00, for which send me RADIO WORLD for twelve months (52 numbers), beginning.....
 and also without additional cost, Radio News, or Popular Radio, or Radio Broadcast, or Wireless Age, or Radio Dealer, or Radio Journal, or \$10.00
 for two yearly subscriptions.

Indicate if renewal
 Offer Good Until
 June 10, 1925

Name.....
 Street Address.....
 City and State.....

Total Power of All Stations Called Merely a Fragment

COMBINE all the power used by the broadcasting stations in every land and it is virtually nothing, electrically speaking, when estimated in conjunction with the total consumption of electrical power the world over. No less than 125,000,000,000 kilowatt hours of electricity are consumed each year. Of this the

United States produces and uses just about half. About eighty per cent. of this power is used in industry, the rest for homes.

There are in the United States and Canada 106 lighting, power and electric railway companies, having a yearly output each of 100,000,000 kilowatt hours. The Niagara Falls Power Company in 1924 reached the enormous figure of 2,858,482,674 kilowatt hours, with an average load of 325,419 kilowatts. The Commonwealth Edison Company and the Edison United Companies, New York, give peak loads in kilowatts of 717,000 and 615,283 respectively.

"It will thus be seen," said Joseph D. R. Freed, "that we are far away from the era of super-power in broadcasting.

"There are no really super-power stations as yet. What we have now are stations with increased power, up to five kilowatts, and we are watching with great interest the experiments being made at 1500 to 5000 watts. Power is not the only determining factor in the efficiency of broadcasting, entirely eliminating atmospheric conditions, but when it is accompanied by proper modulation and all other methods that pertain to transmission, power assumes vast importance, just as it does in the leading commercial code stations of the world.

"Suppose we have 500 broadcasting stations using an average of 500 watts, which is far ahead of the average which actually exists to-day in this country. We have

only a total of 250 kilowatts to be multiplied by the hours of broadcasting. As can be easily seen, this is very very small indeed, as compared with the other figures showing the use of power in the service of mankind.

"Suppose we used the energy of Niagara for broadcasting. The imagination must run riot in contemplating the effect!"

Vacation Specials

Federal 65 and 65A Transformers.....\$4.55
Daven Resistances 25% off list price.
General Instrument .0005 Low Loss Cond.\$2.95
Timmons A.C. B-liminator Kits.....\$16.00
Accurate 4" Vernier Dials.....\$2.65
Eastern Superdyncs Low Loss Coils.....\$3.95
Bruno Condenser for 1 Dial Neutrodyne.\$4.75
Brownlie Vernier Detectors.....\$1.50
McCullough A.C. Tubes.....\$5.75

Bruno Parts in Stock. Lowest Prices on All Standard Parts.

George's Radio Shop

214 St. Nicholas Ave. New York City



Sterling Five

Highest quality five tube tuned radio frequency set in a solid mahogany cabinet. List Price.

\$60.00

Write for free Log Book. Gibson-Sears Radio Corp. 48 W. Broadway, New York

Reg. Trade Mark

The New Type 54

SLEEPER MONOTROL

Reg. U. S. Pat. Off.

Has the extraordinary power of six stages of amplification, 3 of radio and 3 of audio. The utmost simplicity of tuning. Flawless tone quality. Exceptional selectivity. Write for Booklet "W." It's FREE.

Write for booklet "W." It's FREE.

SLEEPER RADIO CORPORATION
434 Washington Ave. Long Island City, N. Y.

**BUY THE
FILKO LIGHTNING
ARRESTER**
SCIENTIFICALLY CORRECT
with the **100% Guarantee**

Warranted to protect your radio from lightning, with a guarantee to pay you \$100 or to repair your set, should it be damaged by lightning through any fault of the arrester.

Listed as **STANDARD** under the re-examination service of the National Board of Fire Underwriters. If your dealer has none, send his name with remittance direct to Dept. RW66.

DX INSTRUMENT CO.
Harrisburg, Pa.

\$2.25 IN CANADA

**STATIC REDUCED
TO A MINIMUM**
REDUCED BATTERY
CONSUMPTION

**Welty's DeLux
Crystector**

Welty's Crystector fits in standard tube socket instead of detector tube in neutrodyne and radio frequency sets. No trouble to install. Wiring not changed—distance and volume only slightly reduced. The difference in natural tone and lack of static is wonderful. Summer reception is a pleasure as compared with tube detector.

LET US PROVE IT
If the Crystector does not function in your set, money cheerfully refunded.

Price, \$4.00 Prepaid

WM. A. WELTY & COMPANY
36 S. STATE STREET, CHICAGO, ILL.

RADIO TUBES DIRECT

NO DEALER PROFIT

Postage Prepaid—Satisfaction Guaranteed

ONE—"Goode" Two-o-one A Tube.....\$1.89
THREE—"Goode" Two-o-one A Tubes..... 5.00
The above is a five volt quarter-ampere tube for use on storage batteries and can be used either as a Detector or an Amplifier.

THE GOODE TUBE CORP., Inc.
OWENSBORO (Dept. B), KENTUCKY

RADIO WORLD'S QUICK-ACTION CLASSIFIED ADS.

10 CENTS A WORD. 10 WORDS MINIMUM

ELLCITE SUPER RADIO RECEIVER. No tubes, A or B batteries. Operates speaker. Clarity. Distance. Write Elccite Radio Co., Box 193, Buffalo, N. Y.

FOR SALE—New Kodak 3-tube set, \$15.00; Belmont Speaker, \$5.00; some new Erla parts, half price. Willie E. Hunter, Prosperity, S. C.

SALESMAN CALLING ON RADIO DEALERS WANTED to handle Radio Tubes as a side line. Thoria Tube Company, Dept. W, Middletown, Ohio.

RADIO BARGAINS GALORE. Big sale of sets and parts. We're also headquarters for portable radios, for less. Before you buy, get our prices. They're free. Just address Paul Stanton, Vermillion, Kansas.

GETTING BETTER QUALITY FROM AUDIO, by Brewster Lee. Last AF stage connected to two tubes in parallel. Send 15c for May 16 issue to RADIO WORLD, 1493 Broadway, New York City.

THE BLUEBIRD REFLEX 2-tube earphone marvel by Capt. Peter V. O'Rourke. Send 15c for February 7 issue. RADIO WORLD, 1493 Broadway, New York City.

THE SHORT-WAVE RECEIVER REIN-ARTZ WILL USE IN ARCTIC. Full wiring directions. Send 15c for May 16 issue. RADIO WORLD, 1493 Broadway, New York City.

RECENT BACK NUMBERS

of RADIO WORLD, 15 cent each, or any seven for \$1. Address Circulation Manager, RADIO WORLD, 1493 Broadway, New York City.

2650 MILES DISTANCE with one tube. We send complete understandable instructions with panel layout, picture diagrams, etc., for 25c. Or **BIG BOOKLET FREE.** VESCO RADIO CO., Box 117-RW, Oakland, California.

WANT TO MAKE MONEY? Of course, you do! Fast selling new invention; write quick for territory. Have own business. Konkle, 192 Market St., Newark, N. J.

RADIO HOSPITAL Specialists in Neutrodyne and Superheterodyne. Radio Central, Abilene, Kansas.

HOW TO MAKE IDEAL COILS, for tuning with .0025 and .001 mfd. condensers. Described by J. E. Anderson in March 7 and 14 and April 11 issues. Send 45c for all three. RADIO WORLD, 1493 Broadway, New York City.

A SIMPLE 1-TUBE DX SET FOR THE NOVICE, by Percy Warren. Send 15c for May 23 issue, RADIO WORLD.

A SET FOR REDUCING STATIC, with diagrams, in RADIO WORLD dated May 9. 15c per copy, or start your subscription with that number. RADIO WORLD, 1493 Broadway, N. Y. C.

A 3-TUBE REFLEXED NEUTRODYNE, by Percy Warren. Send 15c for May 16 issue, RADIO WORLD.

THE DIAMOND OF THE AIR AS A 2-CONTROL SET, by Herman Bernard. This is the circuit that is sweeping the country. Four tubes; loop or aerial. Send 30c for May 23 and 30 issues of RADIO WORLD, 1493 Broadway, New York City.

EARN \$5-10 WEEKLY, addressing, mailing circulars. Send stamped envelope for particulars. Palace Mail Co., Toledo, Ohio.

DINING AND SLEEPING CAR CONDUCTORS (White). Exp. unnecessary. We train you. Send for book of Rules and application. Supt. Railway Exchange, Sta. C, Los Angeles.

AGENTS—WRITE FOR FREE SAMPLES. Sell Madison "Better-Made" Shirts for large Manufacturer direct to wearer. No capital or experience required. Many earn \$100 weekly and bonus. Madison Mfrs., 501 Broadway, New York.

RADIOLA SUPER-HETERODYNE (new) — \$169.00 prepaid. G. Simms, Lake, New York.

HOW TO BUILD A NEUTRALIZED LOOP, by Frank Freer. Send 15c for May 2 issue, RADIO WORLD.

EASILY-MADE CRYSTAL SETS. Send 15c for May 16 issue. RADIO WORLD.

A DX TRANSMITTER, by C. H. West, May 23 issue, RADIO WORLD, 15c.

A PUSH-PULL AF AMPLIFIER with diagrams, in RADIO WORLD dated May 9. 15c per copy, or start your subscription with that number. RADIO WORLD, 1493 Broadway, N. Y. C.

PATENTS—Write for free Guide Books and "Record of Invention Blank" before disclosing inventions. Send model or sketch of your invention for our inspection and instructions free. Terms reasonable. Radio, Chemical, Mechanical, Electrical and Trademark experts. Victor J. Evans & Co., 924 Ninth, Washington, D. C.

A DX TRANSMITTER, by C. H. West, May 23 issue, RADIO WORLD, 15c.

Radio University Planned; All Teaching Via Ether

By Thomas Stevenson
WASHINGTON.

THERE is reason to believe that within the near future there will be inaugurated a radio university which will specialize in courses to put on the air for the benefit of those who would like to study at home.

It is understood that a group of New York people are now considering the organization of such a university and that within a short time they will seek to raise money enough through popular subscriptions to put the proposition over.

It is the opinion of officials of the Government that there is a definite place for a radio university. They believe that the experiment of the Kansas State Agricultural College has proven the public would take advantage of such an opportunity to increase general knowledge.

The Kansas State Agricultural College tried out the proposition of teaching by radio during the winters of 1923 and 1924. Lectures lasting 25 minutes each were broadcast five nights a week on agricultural development, engineering, rural architecture, farm mechanics, interior decorating and other subjects. By the time

the broadcasting of courses had begun, over four hundred persons, located in several states, had registered. At the end of ten weeks registrations had been made from all but nine states, and from Canada, and at the time of the completion of the courses 967 persons had enrolled while 311

took examinations in 488 courses and were awarded certificates.

So successful was the first experiment that in the fall of 1924 a more extensive course was projected. It included agriculture, engineering, home economics and general science. For this course there was enrolled 830 persons.

If the radio university is started, it may resort to the endowment plan as a means of obtaining sufficient funds. At the present time million dollar endowments are possessed by 121 U. S. universities. (Copyright, 1925, by Stevenson Radio Syndicate)



Write us for our
FREE
Catalogue
NEW YORK

B-C-L RADIO SERVICE CO.
220 FULTON ST.

HERCULES AERIAL MAST

20 Ft. Mast \$10
40 Ft. Mast \$25
60 Ft. Mast \$40

All steel construction, complete with guy wires and masthead pulley. We pay the freight.
S. W. HULL & CO., Dept. E3
2848 E. 7th St., Cleveland, O.

Write for literature and **FREE** Blueprint

Used in 80% of all receiving sets in Great Britain.
Eliminates tube noises. Pulls in inaudible stations.

The "BRETWOOD"



Range 300,000 to 10,000,000 ohms

Variable Grid Leak

Bretwood, Ltd., London, Eng., Sole Patentees and Owners

The Bretwood Variable Grid Leak used in a detector tube circuit, strengthens weak signals, makes DX easier, eliminates tube noises and internal howling, due to incorrect leakage from the grid of the tube.

By simply turning the knob the carrier wave may be tuned from the silent point to maximum audibility. The Bretwood is absolutely noiseless in operation and will hold any given setting indefinitely. It is a single-hole panel mount leak.

The Bretwood Variable Grid Leak, tested in the National Physical Laboratory (the official laboratory of Great Britain) and by RADIO WORLD'S Laboratory, proved to be a scientifically accurate instrument. The total range, 9,700,000 ohms, produced by 25 turns of the knob, make a minute adjustment very simple.

The Bretwood Variable Grid Leak is constructed on a different principle and produces better results than any other grid leak. In its specially-constructed barrel is a patented plastic, non-drying resistance material, in which there is a small movable plunger which again moves freely in an absorbent cartridge which gives the setting of the instrument great stability, making it far superior to the graphite, carbon or fibre, compressed or decompressed, resistance elements. It can be used in the most critical circuits with the greatest success.

The North American Bretwood Company

Sole Distributors for United States and Canada
1505 BROADWAY
NEW YORK CITY

Sent You on a Money Back Absolute Satisfaction Guarantee

NOTE TO RADIO MANUFACTURERS

Upon request, we will send any known radio manufacturer a sample of the Bretwood Variable Grid Leak, which will often double the DX value of a receiver and lessen by half a manufacturer's complaints.

A set with a FIXED Grid Leak may work perfectly where tested, while it needs a VARIABLE Grid Leak so that set may be adjusted to the locality where used.

The Bretwood Variable Grid Leak will often bring in distant stations on a loud speaker that can only be heard faintly with a phone.

The North American Bretwood Co.,
1505 Broadway, New York City,
Room 326

Gentlemen:

Enclosed find \$1.50 for which you will please send me one Bretwood Variable Grid Leak prepaid. Satisfaction guaranteed or my money back after trial within ten days of receipt by me.

NAME

STREET

CITYSTATE



Charted
Matched

Bring Your Super Up To Date

—with a set of Silver-Marshall Two-Ten (Inter-stage) and Two-Eleven (Filter) Transformers and a Silver Oscillator Coupler. Regardless of your super's previous efficiency, you can increase its amplification and general efficiency 1 1/2 to 2 1/2 times with this remarkable equipment! Each transformer is supplied with its characteristic curve on a tag. Set of matched and charted transformers and oscillator—Price **\$26.50**

Plans for the "Silver-Super"

are now available. This is the set described in last week's "Radio World." Designed by McMurdo Silver, Assoc. I.R.E. Complete working blueprints, baseboard layout, wiring plans, etc..... **50c**

Silver-Marshall, Inc.
112 S. WABASH AVENUE, CHICAGO



Mailing Lists

Will help you increase sales. Send for FREE catalog giving counts and prices on classified names of your best prospective customers—National, State, Local—Individuals, Professions, Business Firms.

99% Guaranteed by refund of 5¢ each

ROSS-Gould Co. 525 N. 10th St. St. Louis


A PUSH-PULL AF AMPLIFIER with diagrams; in RADIO WORLD, dated May 9, 1925, per copy, or start your subscription with that number. RADIO WORLD, 1493 Broadway, New York City.

THE BABY PORTABLE, by Herbert E. Hayden. A 1-tube DX set on a 7 1/2 x 5 1/4" panel. Send 30c for May 16 and 23 issues to RADIO WORLD, 1493 Broadway, New York City.

THE BLUEBIRD REFLEX 2-tube earphone marvel by Capt. Peter V. O'Rourke. Send 15c for February 7 issue. RADIO WORLD, 1493 Broadway, New York City.

THIS SHOWS HOW
SOUND CAN BE
DISTORTED BY
A TRANSFORMER

Sound wave amplified
with distortion.

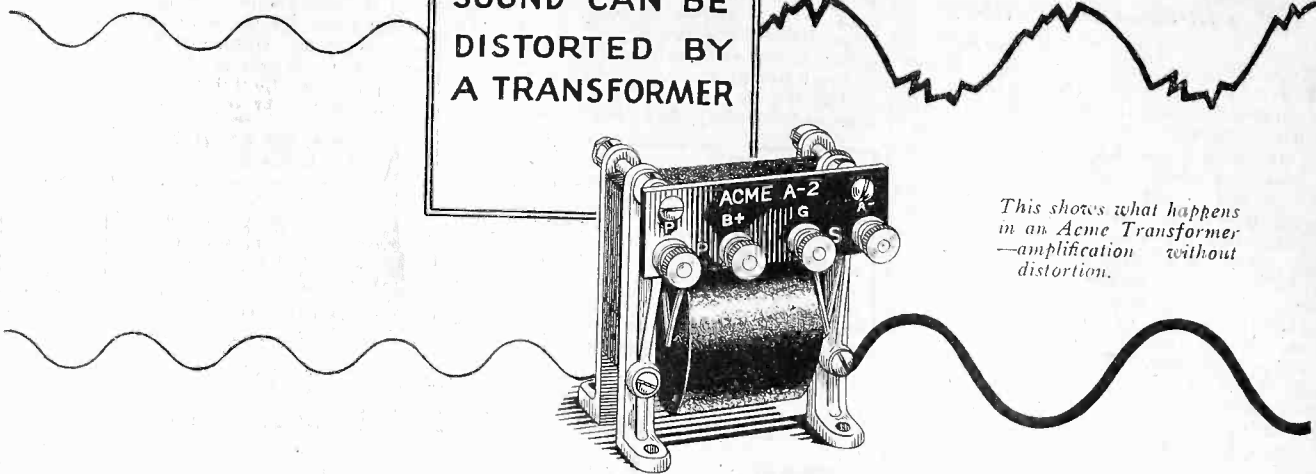

With ACME transformers you get Amplification *without distortion*

WHEN you put a lot of time and money into a radio set you want to be sure that it will give the best results. You want to know that you can bring in the distant stations loud and clear, so that a roomful of your friends can enjoy it. You want amplification, but above all you want Amplification without Distortion. To do this, use amplifying transformers that increase the sound without spoiling the quality.


The Acme A-2 Audio Frequency Amplifying Transformer is the result of five years of research by Acme Engineers. Whether you have a neutrodyne, superheterodyne, regenerative or Reflex, the Acme A-2

Audio Transformer will make your set better.

If you are not getting loud, clear, undistorted radio, change to Acme Transformers and note the difference.

Each Acme Transformer is tested in our factory and bears a guarantee tag; there are no Acme "seconds." Use Acme Transformers in the set you build. Insist on them in the set you buy. One of the big reasons why the Acmeflex Kitset gives such excellent results is that it uses Acme Transformers.

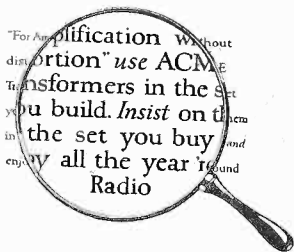Send the coupon today for our 40-page book, "Amplification without Distortion," which shows how to get the best results out of your set through proper amplification and also contains a number of valuable wiring diagrams that will help you build a set. Enclose 10c. with coupon.



The transformer is the magnifying glass of radio

Acme Transformers are sold by all radio dealers.

ACME APPARATUS COMPANY
Transformer and Radio Engineers and Manufacturers
Dept. L2, Cambridge, Mass.

ACME

for amplification

ACME APPARATUS CO.,
Dept. L2, Cambridge, Mass.

Gentlemen: I am enclosing 10 cents, (U. S. coin or stamps), please send me a copy of your book, "Amplification Without Distortion," which please send to:

Name

Street

City State