

September 7th, 1929

15 CENTS

RADIO

REG. U.S. PAT. OFF.

WORLD

The First and Only National Radio Weekly


389th Consecutive Issue—EIGHTH YEAR

Reactivation
of Tubes
Explained

**LIST OF STATIONS
BY CALL LETTERS**

Tuning
the HB
Compact

FOREIGN STATIONS ON SHORT-WAVE ADAPTER!

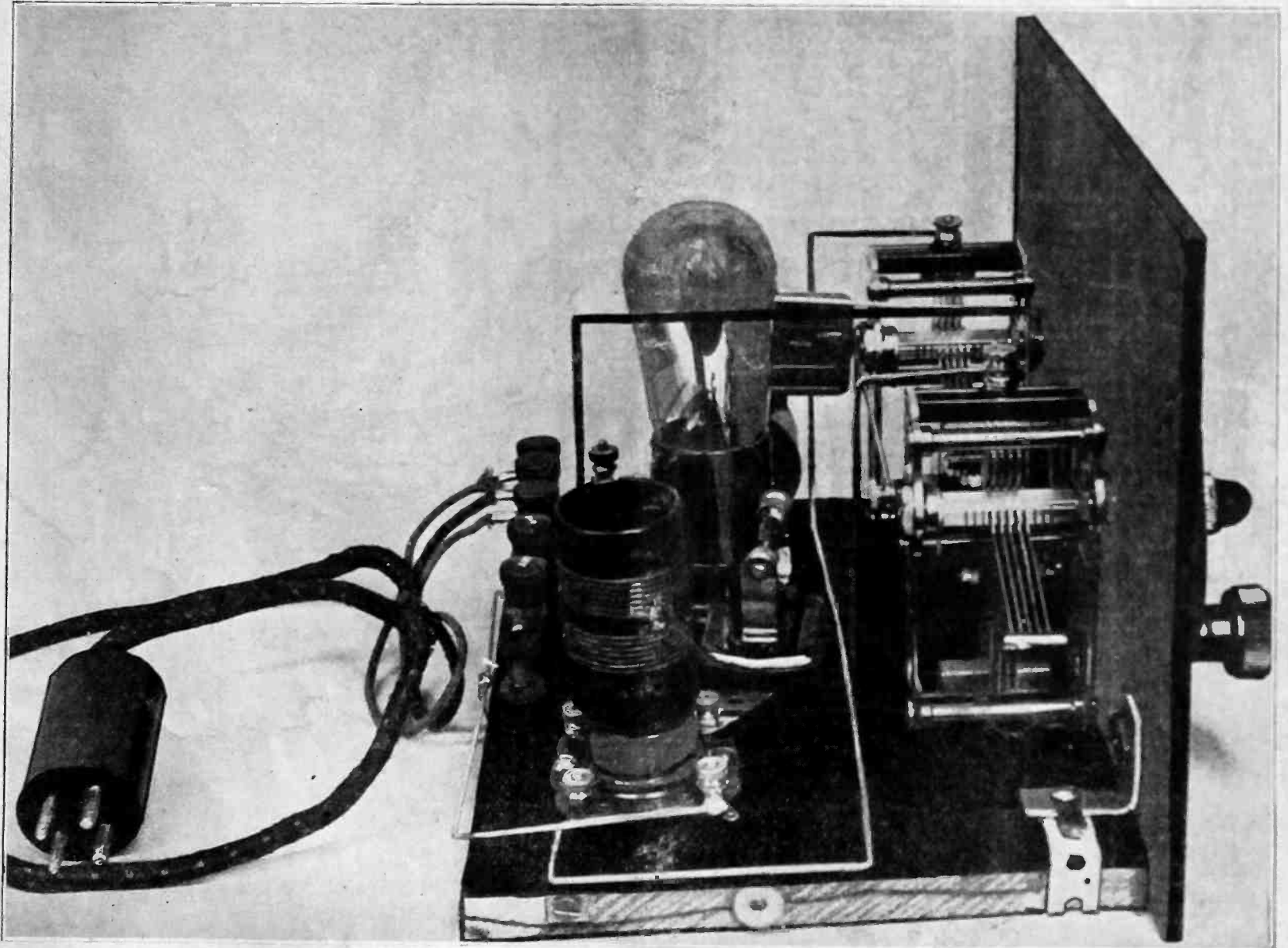

See Article on this Adapter on pages 3 and 4.

New A C
High Mu
Tube Analysis


Extension
of the Range
of Meters

How to Use
Phonograph
Pick-ups

Ten Questions
You Ought to
Answer Easily

A NEW IDEA IN COILS!

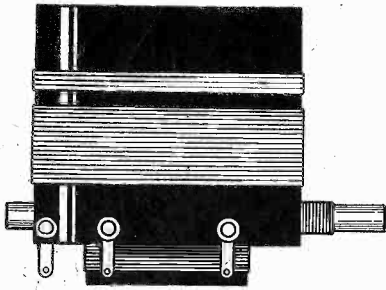The Bernard Tuner Works Screen Grid Tubes Up to the Hilt!




Cat. No. BT5A—\$2.50
FOR .0005 MFD. CONDENSERS
 Bernard Tuner for antenna coupling, the primary being fixed and the secondary tuned. This coil is used as input to the first screen grid radio frequency tube. The double-action tuning method invented by Herman Bernard is employed. Adjust an equalizing condenser across the tuning condenser so that exactly the same dial settings prevail through all circuits. This equalizer, 90 mmfd., once set, is left thus.
 Cat. No. BT3A for .00035 mfd.\$2.55

FOR the first time in radio a coil has been designed that permits working the screen grid tube up to the enormous amplification level that theory long promised but practice long denied.

The secret lies in tuning the plate circuit of the screen grid tube, and still covering the entire broadcast band. Herman Bernard, noted radio engineer, invented the solution—a tuned coil consisting of a fixed and a rotating winding in series, the moving coil turned by the same dial that turns the tuning condenser. An insulated link physically unites condenser shaft and moving coil. Thus when the condenser plates are entirely in mesh the moving coil is set for maximum inductance. That is, it aids the other part of the tuned winding. As the condenser is turned to lower capacity setting the moving coil aids less and less, until at the middle of the dial it acts as if fixed. From then on the moving coil bucks the fixed winding, greatly reducing the total effective inductance, and thus nullifying the effect of the high starting capacity.


The Bernard Tuner is a two-winding coil for interstage coupling, working out of a screen grid tube, 222 or 224, and into any type tube. The tuned primary has coupled to it a still larger inductance, on separate inside form, for step-up, thus greatly increasing an already enormous amplification! This is Cat. No. BT5B for .0005 mfd., BT3B for .00035 mfd. Use BT5A or BT3A for antenna coupler, tuning the secondary, with an equalizing condenser across the antenna tuning condenser, so that the high minimum capacity of the tube's output will be duplicated at the input.

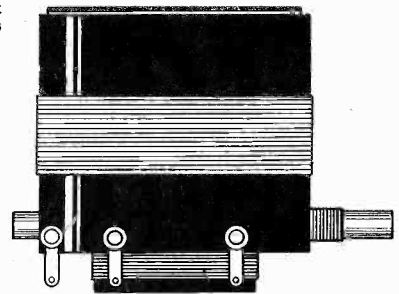


Cat. No. BT5B—\$2.50
FOR .0005 MFD. CONDENSERS
 Bernard Tuner for working out of a screen grid tube, consists of a rotary coil in series with a fixed coil, the two constituting a tuned primary, for tuning the combined rotary and fixed windings to exceed the broadcast band of wavelengths. The condenser shaft and rotary coil shaft are physically coupled so one motion turns both. Develops the highest possible amplification from the screen grid tube.
 Cat. BT3A for .00035 mfd.\$2.55

The Diamond Pair

Since 1925 the Diamond of the Air has been an outstanding circuit. It has undergone few changes. When power tubes and screen grid tubes appeared these were included. When AC operation became practical, the model was described for such use. Whether battery-operated or AC-operated, the Diamond of the Air is a dependable and satisfactory circuit. It uses a screen grid RF stage, tickled detector and two stages of transformer coupled audio. The same coils are used for both models, battery or AC. The secondaries are tuned. They are matched with fine precision, to permit ganged tuning.

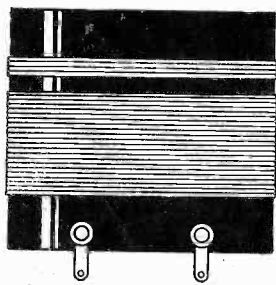

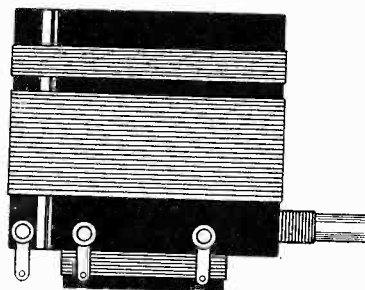
Cat. No. RF5—\$0.75
FOR .0005 MFD. CONDENSER
 Antenna coil for any standard circuit, and one of the two coils constituting the Diamond Pair. The secondary is carefully wound to match the inductance of the companion coil's secondary, so equality of tuning prevails.
 Cat. No. RF3 for .00035...\$0.80



Cat. No. SGT5—\$1.25
FOR .0005 MFD. CONDENSER
 Interstage 3-circuit coil for any hook-up where an untuned primary is in the plate circuit of a screen grid tube. This primary has a large impedance (generous number of turns), so as to afford good amplification. Used in the Diamond of the Air.
 SGT3 for .00035 mfd.\$1.30


The Diamond Pair of coils for .0005 mfd. tuning are Cat. Nos. RF5 and SGT5. A circuit of excellent stability, extremely high selectivity and good sensitivity, the Diamond of the Air should be built with coils that permit full capitalization of the virtues of the circuit. Not only is the number of turns correct for this circuit on each coil, but the spacing between aperiodic primary and tuned secondary is exactly right. Note that the 3-circuit coil SGT5 (or SGT3) has a high impedance primary. This means good amplification from the screen grid tube, obtained in a manner that guarantees selectivity attainment.

ANTENNA COUPLER

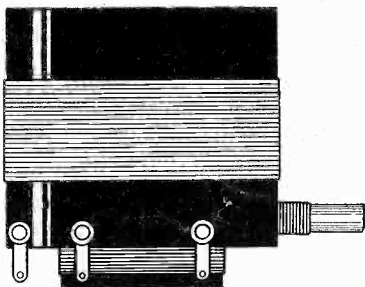


Cat. No. VA5—\$1.10
FOR .0005 MFD. CONDENSER
 Moving primary and fixed secondary, for antenna coupling, adjustable from a knob at the front panel, thus providing volume control.
 Cat. No. VA3 for .00035 mfd.\$1.15

SG TRANSFORMER

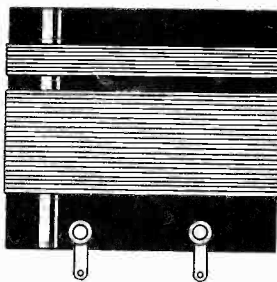

Cat. No. SGS5—\$0.75
FOR .0005 MFD. CONDENSER
 Interstage radio frequency transformer, to work out of a screen grid tube, where the generous-sized primary is in the untuned plate circuit.
 Cat. No. SGS3 for .00035 mfd.\$0.80

STANDARD TUNER

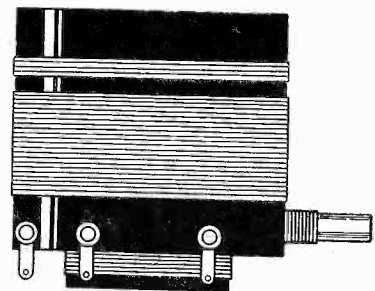

Cat. No. T5—\$1.25
FOR .0005 MFD. CONDENSER
 Standard three-circuit tuner, for antenna stage, or interstage coupling where primary is in the plate circuit of any tube except a screen grid. Provides abundant selectivity and gives smooth tickler action.
 Cat. T3 for .00035 mfd.\$1.30

SCREEN GRID COIL COMPANY, 143 West 45th St., New York, N. Y.

Just East of Broadway

Enclosed please find \$..... for which please ship at once, parcel post prepaid, the following coils:

Quantity	Cat. No.	Price	Quantity	Cat. No.	Price	Quantity	Cat. No.	Price	Quantity	Cat. No.	Price
<input type="checkbox"/>	BT5A	@\$2.50	<input type="checkbox"/>	RF5	@\$0.75	<input type="checkbox"/>	VA5	@\$1.10	<input type="checkbox"/>	SGSF	@\$0.75
<input type="checkbox"/>	BT3A	@\$2.55	<input type="checkbox"/>	RF3	@\$0.80	<input type="checkbox"/>	VA3	@\$1.15	<input type="checkbox"/>	SGS3	@\$0.80
<input type="checkbox"/>	BT5B	@\$2.50	<input type="checkbox"/>	SGT5	@\$1.25	<input type="checkbox"/>	T5	@\$1.25	<input type="checkbox"/>	FL1	@\$0.35
<input type="checkbox"/>	BT3B	@\$2.55	<input type="checkbox"/>	SGT3	@\$1.30	<input type="checkbox"/>	T3	@\$1.30	<input type="checkbox"/>	EQ80	@\$0.85

NAME


ADDRESS

CITY..... STATE.....

5-DAY MONEY-BACK GUARANTEE!

Insulated Link

A flexible coupling device to unite two independent $\frac{1}{4}$ " shafts for single dial operation of a tuning condenser and a Bernard Tuner. If the condenser has shaft protruding from the rear, then the condenser may be power mounted and the coil shaft coupled by the link to either extension shaft of the condenser. If the condenser has no shaft protruding at rear, mount the Bernard Tuner on the front panel. It has shaft protruding at rear for coupling by the link to the condenser's front shaft. To make sure of insulated protection do not force the receptacles of the link together when mounting.

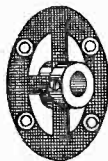

FL4. \$0.35

Data on Construction


The coils are wound by machine on a bakelite form $2\frac{1}{2}$ " wide, and the tuned windings have identical inductance for a given capacity condenser, i. e., .0005 mfd. or .00035 mfd. Full coverage of the wave band is assured. The wire is silk insulated.

All coils with a moving coil have single hole panel mounting fixture. All others have base mounting provision. The coils should be used with connection lugs at bottom, to shorten leads.

Only the Bernard Tuners have a shaft extending from rear. This feature is necessary so that physical coupling to tuning condenser shaft may be accomplished by the Insulated Link.

[Note: Those desiring the 80 mmfd. equalizing condenser for use with the antenna model Bernard Tuner, BT5A or BT3A, should order EQ80 at \$0.85.]

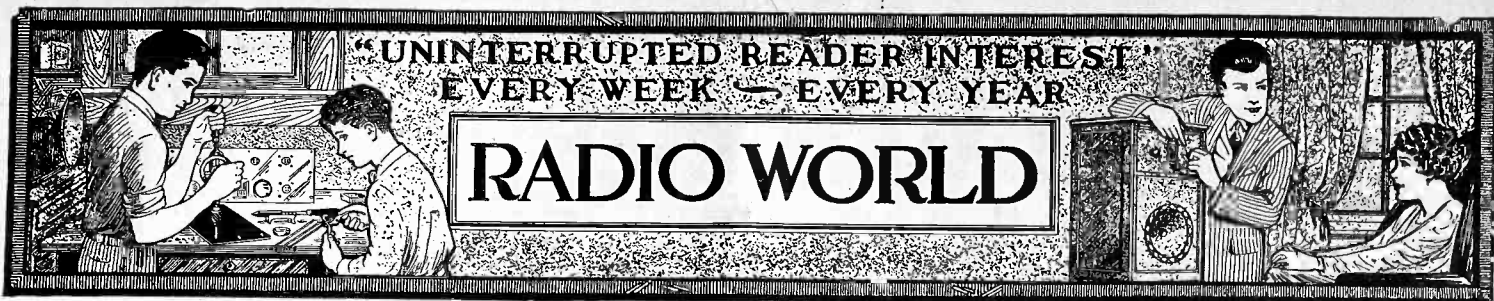SCREEN GRID COIL COMPANY
 143 West 45th Street, New York City



Vol. XV, No. 25 Whole No. 389
 September 7th, 1929
 15c per Copy, \$6.00 per Year
 [Entered as second-class matter, March, 1922, at the Post Office at New York, N. Y., under act of March, 1879.]

Technical Accuracy Second to None
 Latest Circuits and News

EIGHTH YEAR

A Weekly Paper published by Hennessy Radio Publications Corporation, from Publication Office, 145 West 45th Street, New York, N. Y. (Just East of Broadway) Telephone, BRyant 0558 and 0559

I GET ABROAD

On My Little Short-Wave Adapter

By John F. Barry

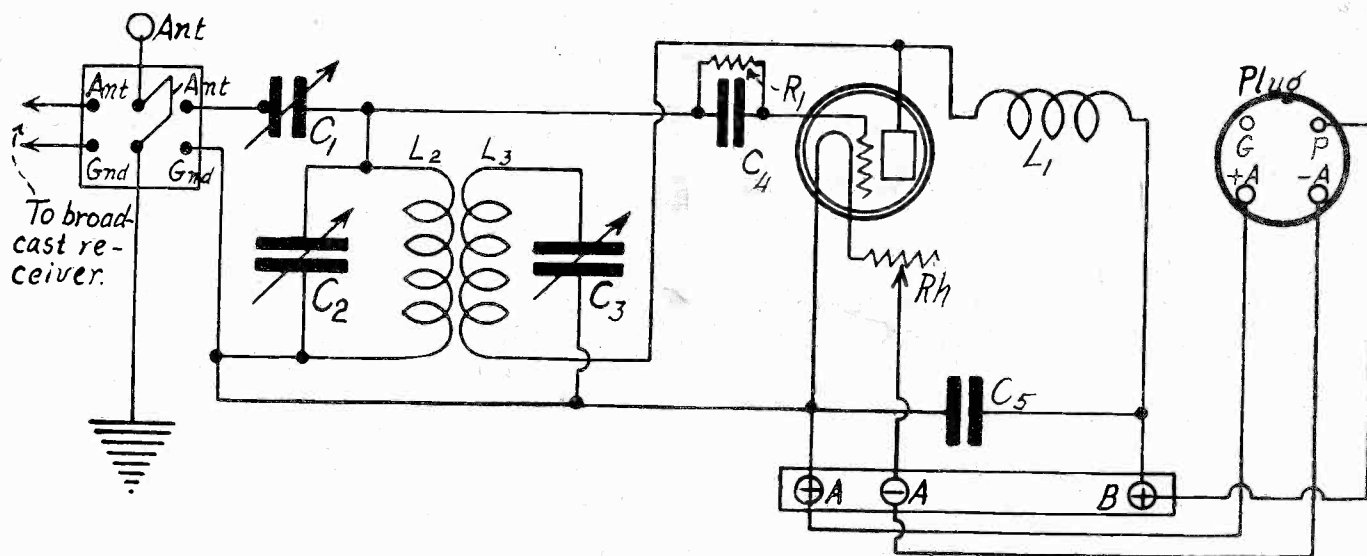


Fig. 1
 CIRCUIT DIAGRAM OF BARRY'S ADAPTER

RADIO fans who have built short wave receivers or adapters without any success are skeptical about the claims of others who report consistent reception of remote stations. Indeed, they are more than skeptical; they are convinced that those who report reception of stations on the other side of the earth are endowed with fertile imaginations.

It is, indeed, easy to discount the claims of others after a few failures with replicas of the very receivers upon which the claims are based. It is easier to reach adverse conclusions about the other fellow's claims than to admit superior skill on his part, or a more enduring patience.

Yet it is a fact that while the tribe or skeptics doubt and scoff at claims, there is another tribe of fans that is daily enjoying the thrills that come with the reception of stations located abroad. There is no denying that there is a thrill in hearing an announcer speak in German, Dutch, Spanish, Russian, Chinese, even if the announcements mean nothing except the certainty that they emanate from a remote station. There is no denying that there is a thrill in hearing music played by foreign musicians in their home lands while you yourself are comfortably seated at your own fireside. There is no denying there is a thrill in hearing the sounds of Big Ben tolling the midnight hour while you are eating your dinner in the evening, or in hearing the ticking of a clock in Eindhoven, Holland, many, many ticks ahead of your own parlor clock.

There is a general impression in radio circles that short wave adapters in general are not successful. There are many reasons why this view has gained wide circulation. One is that many adapters put on the market were not up to the standard required for short wave reception. Another is that many good adapters were not adaptable to the great variety of receivers in use. Still another is that many fans did not have the patience to make the adaptation properly, nor to tune properly the short wave combination after the adaptation was properly made.

There is no technical reason why short wave adapters should not work well. That it is so attested by the fact that many who have made adapters and the adaptation to their broadcast receivers

have had phenomenal success. One of these fans is the author, who is just a radio experimenter living in White Plains, New York, and who listens to European short wave stations as if they were local broadcasting stations. He brings them in whenever they are on the air and whenever it pleases him to tune them in. Moreover, he does not keep the reception to himself, but he invites his neighbors and friends to share the enjoyment of the entertainments from abroad.

Not only have I proven my claims by local witnesses but I have secured confirmation from several European stations of their reception. Thus I have a letter from Funk-Stunde Aktiengesellschaft, Berlin, Germany, confirming the reception of their 25.5 meter station, another from N. V. Philips' Radio, Eindhoven, Holland, confirming reception of programs from PCJ, on 30.2 meters and still another from World-Radio, London, England, confirming reception of programs from 5SW, Chelmsford, England, 24 meters. Please note that Eindhoven signs itself FCJ, not PCJJ as listed in most short wave directories.

Some one of the skeptical tribe might suggest that I am using

LIST OF PARTS

- L1—One 85-millihenry choke coil
- L2, L3—One set of short wave coils, as described
- C1—One 50 mmfd. midget condenser (about 13 plates)
- C2, C3—Two .00014 mfd. variable condensers
- C4—One moulded mica condenser, capacity .00015 mfd., with clips
- C5—One .001 mfd. condenser
- R1—One 10 megohm grid leak
- Two cushion type standard sockets
- One double pole, double throw switch
- One binding post strip with three binding posts
- One adapter plug, or plug made of old tube base
- One 112A tube
- One 7x10 panel
- One 7x9 baseboard
- Two dials, vernier type

HAS VERIFICATIONS

To Prove He Gets Foreign Stations

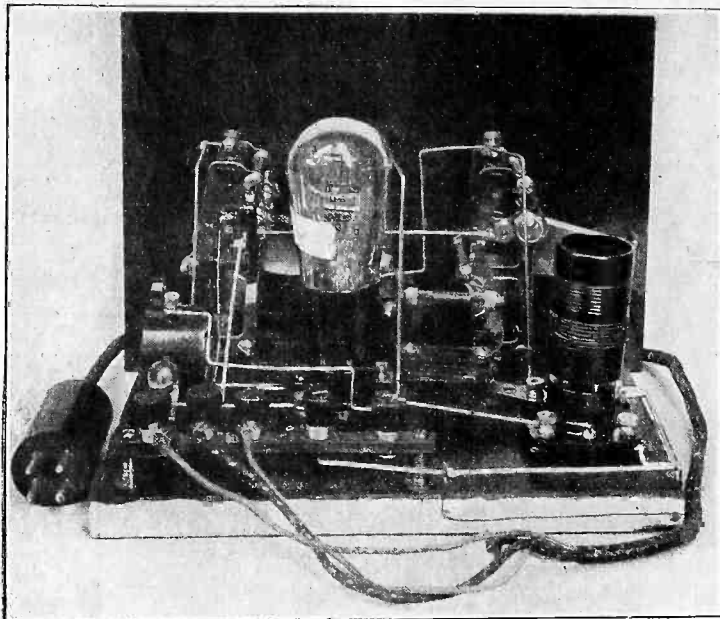


Fig. 2

A VIEW OF THE ADAPTER FROM THE REAR

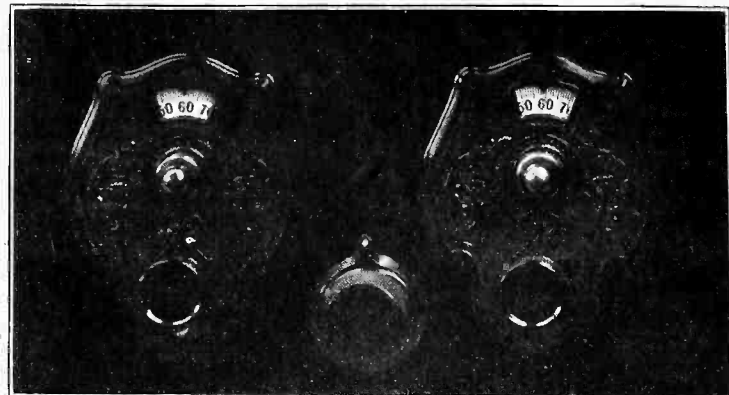


Fig. 3

THE APPEARANCE OF THE FRONT PANEL IF THE 7-INCH HEIGHT IS CUT DOWN, WHICH IS OPTIONAL

an adapter with an extraordinary array of amplifier tubes. But such is not the case. There is only one tube in the adapter, and I plug it into the detector socket of my broadcast receiver, thus using the amplifier in that circuit. As a matter of fact, there is nothing unusual about the circuit diagram of his adapter. The secret, if there be one, is in the use of first class parts, put together in the proper way, and handled by one who has learned how to tune. A glance at the circuit diagram, Fig. 1, will show the simplicity of the adapter.

In the antenna circuit is a double throw, double pole switch by means of which either the broadcast wavelengths or the short wave adapter may be selected, or rather by means of which the antenna may be thrown to one or the other.

Much depends on the antenna for the success of short wave receivers, so it is well to describe the antenna used in my set. It consists of 100 feet of No. 14 solid enameled copper wire erected in the form of an inverted L with the horizontal portion running North and South, the lead-in being taken off at the South end. Naturally, it is well insulated so that no part of the short wave signal is frittered away in insulation leakage. The ground lead goes to the cold water system of the house. That is the type of antenna and ground that can be recommended for almost any radio installation.

Starting with the antenna lead when the switch is thrown to the short wave adapter we first come to a midget condenser C1 which is in series with the antenna and the tuned circuit. This condenser is for the purpose of "shortening" the antenna and to make it suitable for the short waves. It is a thirteen-plate variable condenser.

One side of this condenser connects with the top of the tuned circuit and with the grid leak R1 and stopping condenser C4. The leak has a value of 10 megohms and the condenser .00015 mfd.

The tuned circuit consists of a straight line frequency condenser C2 of .00014 mfd. and a short wave coil L2. The tickler circuit is of the shunt type and consists of the coil L3 and another .00014 mfd. condenser C3. The rotors of both C2 and C3 are grounded, which explains the reason why there is no body capacity effects in the circuit even when critical regeneration is used.

In order to force the radio frequency currents through the tickler a radio frequency choke coil L1 is connected in the plate circuit of the tube. Also, a .001 mfd. by-pass condenser C5 is connected across the output to prevent any radio frequency currents from wandering into parts of the circuit where they don't belong.

Best results are obtained with a 112A tube in the adapter. Any other tube, including a screen grid tube, gave poorer results. A necessary condition for optimum results is that a rheostat be used in the filament circuit of the tube. The rheostat, Rh, is put in the negative leg of the filament circuit and its maximum resistance is 6 ohms. The socket used for the tube is of the cushioned type to minimize mechanical vibration of the elements.

The filament and plate leads of the adapter terminate on a binding post strip marked A plus, A minus and P. This is used for convenience and to provide an anchor for the leads. To this binding post strip are connected the flexible leads to the plug which is inserted into the detector socket of the broadcast receiver. A view of this plug is shown at the right in the drawing with the leads run-

ing to proper prongs. The view is taken from above the plug as it would be inserted. Note that the two filament leads are reversed from the usual connection. This happened to be the proper connection for the broadcast amplifier used with this adapter. If the broadcast amplifier is wired in the usual manner these two leads should be reversed. Of course, the essential thing is that plus goes to plus and minus to minus regardless of the manner in which the receiver has been wired. Before connecting the leads to the plug the polarity of the detector socket springs in the broadcast receiver should be tested to avoid any mistake.

The tuning coils L2 and L3 are wound on a small form 1.25 inches in diameter and are provided with a standard tube base prong which fits into a cushion type socket. Thus change of coils from one wavelength range to another is done in a moment.

Batteries should be used both for the filament current and the plate voltage. Eliminators are not recommended. The plate voltage on the tube is 45 volts, supplied, however, through a variable resistance located in the broadcast receiver and not shown in the adapter diagram. A resistance having a maximum value of 50,000 ohms is suggested.

In addition to using batteries not only on the adapter tube but also on the broadcast receiver used in conjunction with it, I strongly recommend individual rheostats on all the tubes used in preference to automatic filament control or fixed ballast resistors.

In order to eliminate all body capacity effects the entire adapter is shielded. The box containing the adapter is lined with phosphor bronze screening such as is used for windows, and this screen is connected to ground, or to A plus on the adapter. The bottom side of the shielding is attached to the subpanel rather than to the box, but in such a manner that it touches no conductor except the A plus lead and the screening in the sides and top of the containing box. Contact between the subpanel screen and the screening on the box is made automatically when the adapter is slipped into the box.

5SW, Chelmsford, broadcasts daily except Saturdays and Sundays, from 12.30 p.m. to 1.30 p.m., and from 7 p.m. to midnight, British Summer or Greenwich Mean time, according to the season; and PCJ every Thursday from 6 p.m. to 8 p.m., and from 11 p.m. to midnight, every Friday from midnight to 3 a.m., and from 6 p.m. to 8 p.m., and Saturday from midnight to 6 a.m., all Greenwich Mean time. The German station is not on a regular schedule.

British Summer time bears the same relation to Greenwich Mean time as Daylight Saving time bears to standard time in this country. Greenwich Mean time is five hours faster than Eastern Standard time, six hours faster than Central Standard time, seven hours faster than Mountain Standard time, and eight hours faster than Pacific Standard time.

Construction of Coils

Those wishing to construct their own coils can do so by following the following specifications:

Wave length range meters	L2		L3	
	Wire	Turns	Wire	Turns
16-32	Litz	7	No. 24 enameled	7
29-58	Litz	15	No. 28 enameled	10
54-110	Litz	25	No. 28 enameled	20
103-210	No. 28 enam.	47	No. 28 enameled	29

All are space-wound in threaded groove. Diameter of all 1.25 inches.

[The designer of this adapter, John F. Barry, Box 18, White Plains, N. Y., has kindly consented to answer questions regarding this circuit to those who write him enclosing a self-addressed stamped envelope for reply.—EDITOR.]

RANGES OF METERS

How Scale May Be Increased

By J. A. Dowie

National Radio Institute

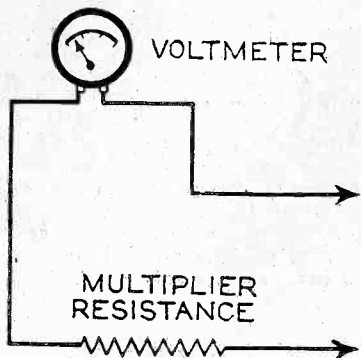


FIG. 1.

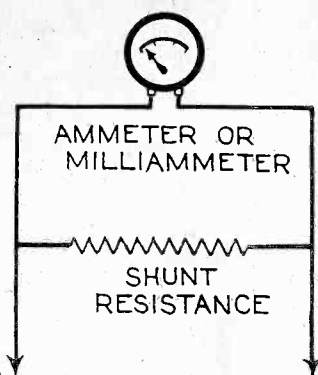


FIG. 2.

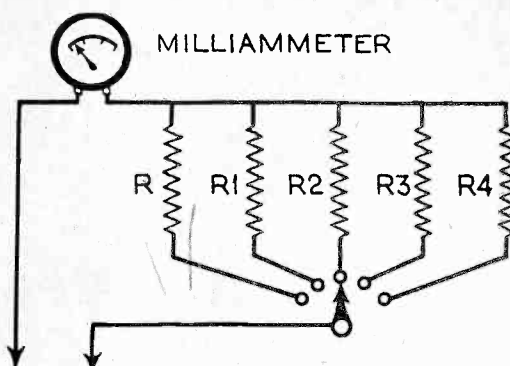


FIG. 3.

A SERIES RESISTOR INCREASES THE VOLTAGE SCALE OF A VOLTMETER (FIG. 1). A SHUNT RESISTOR INCREASES THE SCALE OF A CURRENT METER (FIG. 2). A MILLIAMMETER IS SHOWN AS A MULTI-RANGE VOLTMETER (FIG. 3).

POSSESSION of the knowledge required to increase the range of indicating instruments, such as voltmeters and ammeters, permits the utilization of a device for some purpose which otherwise would necessitate a new instrument. Occasions frequently arise where current indicating devices at hand do not afford the operating range necessary for the test being conducted or measurement to be made.

A voltmeter may be used to measure voltages higher than its maximum scale reading by connecting a suitable resistance in series with the instrument. Such series resistances are known as multipliers. Similarly, the range of an ammeter or milliammeter may be increased by using an appropriate resistance, which is connected in shunt or in parallel.

To increase the range of a voltmeter, it is necessary to place a resistance of the proper ohmic value in series with the instrument. This arrangement is shown in Fig. 1. The series resistance will have a value depending upon the maximum scale reading required of meter and upon the internal resistance of the meter itself. The internal resistance value may be obtained from the maker of the meter.

The application of the following formula when the internal resistance of the meter is known will make actual calculation very simple:

- $R1 = R (E1 - E) / E$
- R1 = Resistance connected in series with voltmeter.
- R = Internal resistance of voltmeter.
- E1 = Highest reading of voltmeter desired.
- E = Highest present reading of voltmeter.

Thus, if we have on hand a voltmeter the maximum scale reading of which is 100 volts, with an internal meter resistance specified by its manufacturer as being equal to 100,000 ohms, and we wish to extend its range to indicate voltages up to 400 volts—

$$R1 = 100,000 \times \frac{400 - 100}{100} = 300,000 \text{ ohms.}$$

$$\text{Series resistance} = 300,000 \text{ ohms.}$$

To obtain the scale readings with this extended range voltmeter, multiply the indicated meter reading by 4 (400 ÷ 100) which gives the difference of potential across both the voltmeter and added series resistance.

To increase the range of an ammeter or a milliammeter, a shunt (parallel) resistance must be connected across its terminals, according to what maximum scale reading we desire. Fig. 2 illustrates how the shunt resistance is connected.

The value of the shunt resistance is determined from the following formula:

- $Rs = Ia \times Ra / Is$
- Rs = Shunt resistance.
- Ra = Internal resistance of meter.
- Ia = Original highest reading of meter.
- Is = Current to flow through shunt.

The application underlying this formula is, however, possible only if and when the internal resistance of the meter is known.

The principle underlying this formula is that the total resistance of a path consisting of two or more resistances in shunt or in parallel is always less than the resistance of either one of the

individual resistances. The current flow divides between the two branches, the sum of all the branches being the total circuit current. If we add in shunt to the internal resistance of the meter another resistance of equal value, the total resistance of the meter circuit consisting of the meter and the shunt resistance as shown in Fig. 2 is halved.

If the value of Rs is equal to Ra, the meter scale is doubled.

For determination of the shunt resistance let us assume Rs to be the required shunt resistance. Ra is the internal resistance of the meter. Ia is the meter current scale, I is the total current flow in the circuit and Is is the current which is to flow through the shunt resistance. As an example, let us assume a DC milliammeter rated at 0-30 milliamperes (.03 of an ampere) and 1.2 ohms resistance, the operating scale of which we wish to increase to 150 milliamperes (.15 of an ampere). Since the meter is capable of only passing 30 milliamperes, 120 milliamperes (.12 of an ampere) must flow through the external shunt resistance.

Applying formula No. 2.

$$Rs = Ia \times Ra / Is$$

$$I = .15 \text{ ampere}$$

$$Ia = .03 \text{ ampere}$$

$$Is = .12 \text{ ampere}$$

If we consider Ra as the internal resistance of the meter and Rs as the resistance of the shunt, we determine the value of the shunt resistance by solving the following formula:

$$Ra \times Ia / Is$$

Substituting our values, this formula reads $Rs = 1.2 \times (.03 \div .12)$, or .3 of an ohm. In other words, a shunt resistance of .3 of an ohm will increase the range of the above mentioned instrument to 150 milliamperes.

With a known value of meter resistance and a known value of shunt resistance, the multiplying factor or the increase in current range is determined by applying the following formula:

$$(Rs + Ra) / Ra$$

$$Rs = \text{Shunt resistance}$$

$$Ra = \text{Meter resistance}$$

Applying this formula to our problem and substituting our values, we obtain

$$(3 + 1.2) / 1.2 = 5$$

In other words, the meter range is multiplied by 5.

By connecting an accurate fixed resistance in series with milliammeters, it is possible to make very useful voltmeters. For example, a standard milliammeter having a scale of 0 to 1 milliamperes can be used as a very efficient voltmeter having convenient ranges from 1 to 1,000, or even more volts by simply connecting in series with it multiples of suitable resistance and "calibrating" or simply reading the scale in volts instead of in amperes.

Fig. 3 shows a diagram with five external resistance connected to a 0 to 1 DC milliammeter. R is 1,000 ohms in series, and affords a voltage scale from 0 to 1 volt; R1 is 10,000 ohms resistance and extends the range of the meter to 0 to 10 volts:

- R2 = 100,000 ohms; 0 to 100 volts
- R3 = 200,000 ohms; 0 to 200 volts
- R4 = 500,000 ohms; 0 to 500 volts
- R5 = 1,000,000 ohms; 0 to 1,000 volts

HAS VERIFICATIONS

To Prove He Gets Foreign Stations

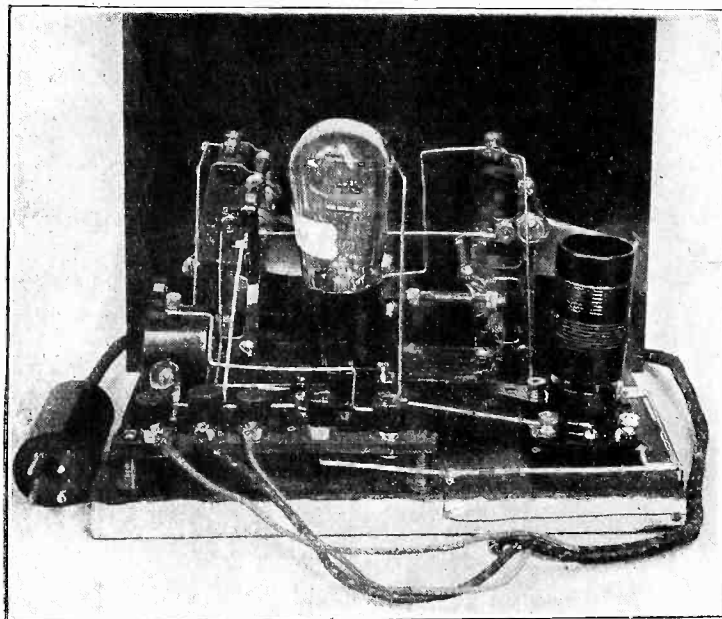


Fig. 2

A VIEW OF THE ADAPTER FROM THE REAR

an adapter with an extraordinary array of amplifier tubes. But such is not the case. There is only one tube in the adapter, and I plug it into the detector socket of my broadcast receiver, thus using the amplifier in that circuit. As a matter of fact, there is nothing unusual about the circuit diagram of his adapter. The secret, if there be one, is in the use of first class parts, put together in the proper way, and handled by one who has learned how to tune. A glance at the circuit diagram, Fig. 1, will show the simplicity of the adapter.

In the antenna circuit is a double throw, double pole switch by means of which either the broadcast wavelengths or the short wave adapter may be selected, or rather by means of which the antenna may be thrown to one or the other.

Much depends on the antenna for the success of short wave receivers, so it is well to describe the antenna used in my set. It consists of 100 feet of No. 14 solid enameled copper wire erected in the form of an inverted L with the horizontal portion running North and South, the lead-in being taken off at the South end. Naturally, it is well insulated so that no part of the short wave signal is frittered away in insulation leakage. The ground lead goes to the cold water system of the house. That is the type of antenna and ground that can be recommended for almost any radio installation.

Starting with the antenna lead when the switch is thrown to the short wave adapter we first come to a midget condenser C1 which is in series with the antenna and the tuned circuit. This condenser is for the purpose of "shortening" the antenna and to make it suitable for the short waves. It is a thirteen-plate variable condenser.

One side of this condenser connects with the top of the tuned circuit and with the grid leak R1 and stopping condenser C4. The leak has a value of 10 megohms and the condenser .00015 mfd.

The tuned circuit consists of a straight line frequency condenser C2 of .00014 mfd. and a short wave coil L2. The tickler circuit is of the shunt type and consists of the coil L3 and another .00014 mfd. condenser C3. The rotors of both C2 and C3 are grounded, which explains the reason why there is no body capacity effects in the circuit even when critical regeneration is used.

In order to force the radio frequency currents through the tickler a radio frequency choke coil L1 is connected in the plate circuit of the tube. Also, a .001 mfd. by-pass condenser C5 is connected across the output to prevent any radio frequency currents from wandering into parts of the circuit where they don't belong.

Best results are obtained with a 112A tube in the adapter. Any other tube, including a screen grid tube, gave poorer results. A necessary condition for optimum results is that a rheostat be used in the filament circuit of the tube. The rheostat, Rh, is put in the negative leg of the filament circuit and its maximum resistance is 6 ohms. The socket used for the tube is of the cushioned type to minimize mechanical vibration of the elements.

The filament and plate leads of the adapter terminate on a binding post strip marked A plus, A minus and P. This is used for convenience and to provide an anchor for the leads. To this binding post strip are connected the flexible leads to the plug which is inserted into the detector socket of the broadcast receiver. A view of this plug is shown at the right in the drawing with the leads run-

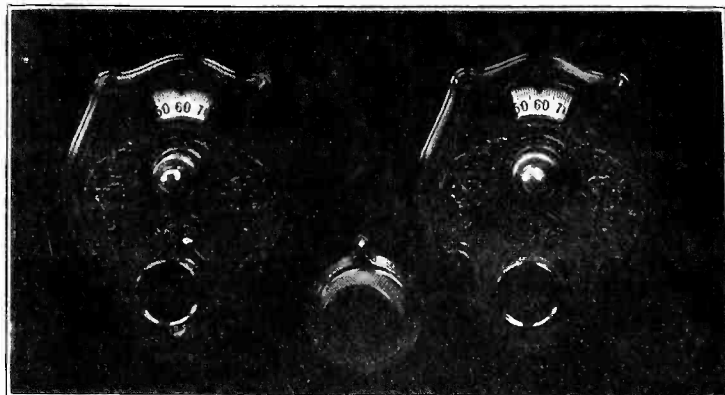


Fig. 3

THE APPEARANCE OF THE FRONT PANEL IF THE 7-INCH HEIGHT IS CUT DOWN, WHICH IS OPTIONAL

ing to proper prongs. The view is taken from above the plug as it would be inserted. Note that the two filament leads are reversed from the usual connection. This happened to be the proper connection for the broadcast amplifier used with this adapter. If the broadcast amplifier is wired in the usual manner these two leads should be reversed. Of course, the essential thing is that plus goes to plus and minus to minus regardless of the manner in which the receiver has been wired. Before connecting the leads to the plug the polarity of the detector socket springs in the broadcast receiver should be tested to avoid any mistake.

The tuning coils L2 and L3 are wound on a small form 1.25 inches in diameter and are provided with a standard tube base prong which fits into a cushion type socket. Thus change of coils from one wavelength range to another is done in a moment.

Batteries should be used both for the filament current and the plate voltage. Eliminators are not recommended. The plate voltage on the tube is 45 volts, supplied, however, through a variable resistance located in the broadcast receiver and not shown in the adapter diagram. A resistance having a maximum value of 50,000 ohms is suggested.

In addition to using batteries not only on the adapter tube but also on the broadcast receiver used in conjunction with it, I strongly recommend individual rheostats on all the tubes used in preference to automatic filament control or fixed ballast resistors.

In order to eliminate all body capacity effects the entire adapter is shielded. The box containing the adapter is lined with phosphor bronze screening such as is used for windows, and this screen is connected to ground, or to A plus on the adapter. The bottom side of the shielding is attached to the subpanel rather than to the box, but in such a manner that it touches no conductor except the A plus lead and the screening in the sides and top of the containing box. Contact between the subpanel screen and the screening on the box is made automatically when the adapter is slipped into the box.

5SW, Chelmsford, broadcasts daily except Saturdays and Sundays, from 12.30 p.m. to 1.30 p.m., and from 7 p.m. to midnight, British Summer or Greenwich Mean time, according to the season; and PCJ every Thursday from 6 p.m. to 8 p.m., and from 11 p.m. to midnight, every Friday from midnight to 3 a.m., and from 6 p.m. to 8 p.m., and Saturday from midnight to 6 a.m., all Greenwich Mean time. The German station is not on a regular schedule.

British Summer time bears the same relation to Greenwich Mean time as Daylight Saving time bears to standard time in this country. Greenwich Mean time is five hours faster than Eastern Standard time, six hours faster than Central Standard time, seven hours faster than Mountain Standard time, and eight hours faster than Pacific Standard time.

Construction of Coils

Those wishing to construct their own coils can do so by following the following specifications:

Wave length range meters	L2		L3	
	Wire	Turns	Wire	Turns
16-32	Litz	7	No. 24 enameled	7
29-58	Litz	15	No. 28 enameled	10
54-110	Litz	25	No. 28 enameled	20
103-210	No. 28 enam.	47	No. 28 enameled	29

All are space-wound in threaded groove. Diameter of all 1.25 inches.

[The designer of this adapter, John F. Barry, Box 18, White Plains, N. Y., has kindly consented to answer questions regarding this circuit to those who write him enclosing a self-addressed stamped envelope for reply.—EDITOR.]

RANGES OF METERS

How Scale May Be Increased

By J. A. Dowie

National Radio Institute

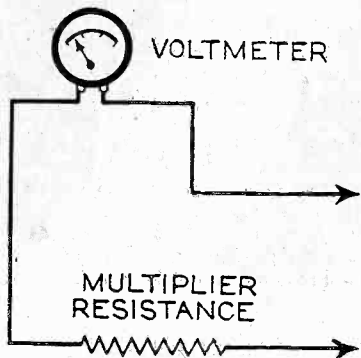


FIG. 1.

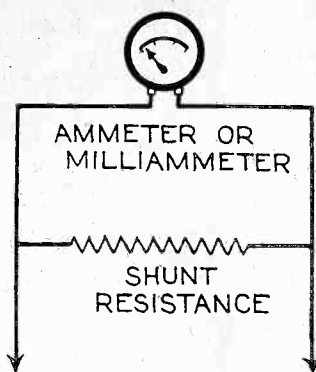


FIG. 2.

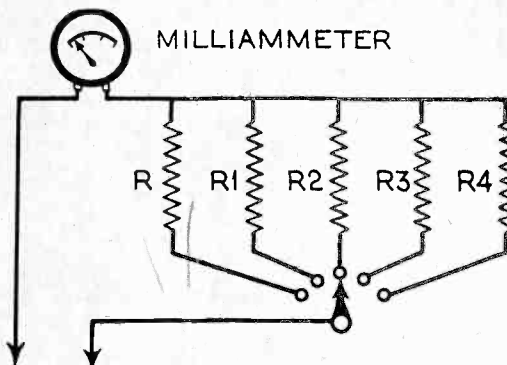


FIG. 3.

A SERIES RESISTOR INCREASES THE VOLTAGE SCALE OF A VOLTMETER (FIG. 1). A SHUNT RESISTOR INCREASES THE SCALE OF A CURRENT METER (FIG. 2). A MILLIAMMETER IS SHOWN AS A MULTI-RANGE VOLTMETER (FIG. 3).

POSSESSION of the knowledge required to increase the range of indicating instruments, such as voltmeters and ammeters, permits the utilization of a device for some purpose which otherwise would necessitate a new instrument. Occasions frequently arise where current indicating devices at hand do not afford the operating range necessary for the test being conducted or measurement to be made.

A voltmeter may be used to measure voltages higher than its maximum scale reading by connecting a suitable resistance in series with the instrument. Such series resistances are known as multipliers. Similarly, the range of an ammeter or milliammeter may be increased by using an appropriate resistance, which is connected in shunt or in parallel.

To increase the range of a voltmeter, it is necessary to place a resistance of the proper ohmic value in series with the instrument. This arrangement is shown in Fig. 1. The series resistance will have a value depending upon the maximum scale reading required of meter and upon the internal resistance of the meter itself. The internal resistance value may be obtained from the maker of the meter.

The application of the following formula when the internal resistance of the meter is known will make actual calculation very simple:

- $R1 = R (E1 - E) / E$
- R1 = Resistance connected in series with voltmeter.
- R = Internal resistance of voltmeter.
- E1 = Highest reading of voltmeter desired.
- E = Highest present reading of voltmeter.

Thus, if we have on hand a voltmeter the maximum scale reading of which is 100 volts, with an internal meter resistance specified by its manufacturer as being equal to 100,000 ohms, and we wish to extend its range to indicate voltages up to 400 volts—

$$R1 = 100,000 \times \frac{400 - 100}{100} = 300,000 \text{ ohms.}$$

100
Series resistance = 300,000 ohms.

To obtain the scale readings with this extended range voltmeter, multiply the indicated meter reading by 4 (400 ÷ 100) which gives the difference of potential across both the voltmeter and added series resistance.

To increase the range of an ammeter or a milliammeter, a shunt (parallel) resistance must be connected across its terminals, according to what maximum scale reading we desire. Fig. 2 illustrates how the shunt resistance is connected.

The value of the shunt resistance is determined from the following formula:

- $Rs = Ia \times Ra / Is$
- Rs = Shunt resistance.
- Ra = Internal resistance of meter.
- Ia = Original highest reading of meter.
- Is = Current to flow through shunt.

The application underlying this formula is, however, possible only if and when the internal resistance of the meter is known.

The principle underlying this formula is that the total resistance of a path consisting of two or more resistances in shunt or in parallel is always less than the resistance of either one of the

individual resistances. The current flow divides between the two branches, the sum of all the branches being the total circuit current. If we add in shunt to the internal resistance of the meter another resistance of equal value, the total resistance of the meter circuit consisting of the meter and the shunt resistance as shown in Fig. 2 is halved.

If the value of Rs is equal to Ra, the meter scale is doubled.

For determination of the shunt resistance let us assume Rs to be the required shunt resistance. Ra is the internal resistance of the meter. Ia is the meter current scale, I is the total current flow in the circuit and Is is the current which is to flow through the shunt resistance. As an example, let us assume a DC milliammeter rated at 0-30 milliamperes (.03 of an ampere) and 1.2 ohms resistance, the operating scale of which we wish to increase to 150 milliamperes (.15 of an ampere). Since the meter is capable of only passing 30 milliamperes, 120 milliamperes (.12 of an ampere) must flow through the external shunt resistance.

Applying formula No. 2.

$$Rs = Ia \times Ra / Is$$

$$I = .15 \text{ ampere}$$

$$Ia = .03 \text{ ampere}$$

$$Is = .12 \text{ ampere}$$

If we consider Ra as the internal resistance of the meter and Rs as the resistance of the shunt, we determine the value of the shunt resistance by solving the following formula:

Substituting our values, this formula reads $Rs = 1.2 \times (.03 \div .12)$, or .3 of an ohm. In other words, a shunt resistance of .3 of an ohm will increase the range of the above mentioned instrument to 150 milliamperes.

With a known value of meter resistance and a known value of shunt resistance, the multiplying factor or the increase in current range is determined by applying the following formula:

$$(Rs + Ra) / Rs$$

$$Rs = \text{Shunt resistance}$$

$$Ra = \text{Meter resistance}$$

Applying this formula to our problem and substituting our values, we obtain

$$(3 + 1.2) / 3 = 5$$

In other words, the meter range is multiplied by 5.

By connecting an accurate fixed resistance in series with milliammeters, it is possible to make very useful voltmeters. For example, a standard milliammeter having a scale of 0 to 1 milliamperes can be used as a very efficient voltmeter having convenient ranges from 1 to 1,000, or even more volts by simply connecting in series with it multiples of suitable resistance and "calibrating" or simply reading the scale in volts instead of in amperes.

Fig. 3 shows a diagram with five external resistance connected to a 0 to 1 DC milliammeter. R is 1,000 ohms in series, and affords a voltage scale from 0 to 1 volt; R1 is 10,000 ohms resistance and extends the range of the meter to 0 to 10 volts:

- R2 = 100,000 ohms; 0 to 100 volts
- R3 = 200,000 ohms; 0 to 200 volts
- R4 = 500,000 ohms; 0 to 500 volts
- R5 = 1,000,000 ohms; 0 to 1,000 volts

TUNING THE

By Herman

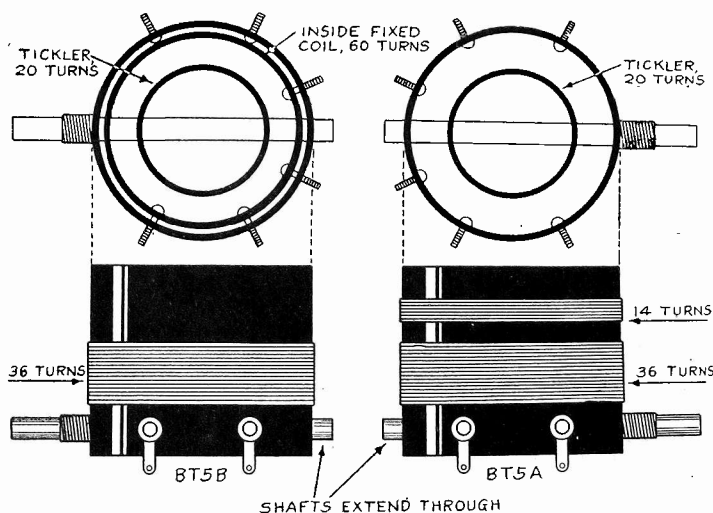


FIG. 1.

THE WINDING DATA FOR .0005 MFD. CONDENSERS, FOR COILS ON A 2½" OUTSIDE DIAMETER FOR THE MAIN FORM, ARE INDICATED.

[The main constructional features of the HB Compact, a four-tube battery model receiver, using two screen grid tubes, one 240 high mu and a 112A output tube, were published in the August 24th and 31st issues. In the August 31st (last week) the full-sized picture diagram of the wiring was printed. The circuit, using the new Bernard dynamic tuners for working the screen grid radio frequency amplifier up to the hilt, and for making the dials track, is exceptionally sensitive, provides adequate selectivity, and is wonderful on tone. Its construction is highly recommended, as this circuit has proved to be one of the best of the sets using few tubes so far designed.—Editor.]

THE details on construction of the HB Compact have been published, and some questions have been received from readers, but it is not quite time to answer all these questions, as it was promised that this week tuning would be discussed, and next week, issue of September 7th, the topic would be trouble-shooting. Nevertheless, if you will turn to pages 14 and 15 you will see some questions answered, because it was deemed these were especially urgent.

Lest the reader has not read any of the foregoing articles a few words on the theory and design of the circuit will be written, and the coil winding data given.

The circuit consists of a screen grid radio frequency amplifier, with the grid and plate circuits of the same tube tuned; a 240 high mu detector, worked on the negative bias principle; a screen grid first stage audio amplifier, and a 112A output tube. Those desiring a 171A output tube may make the substitution, but must increase the last stage plate voltage to 180, use a filter and provide 40.5 volts negative bias for the 171A.

High-Gain Audio, Also

The two-stage audio amplifier is resistance-coupled, and the gain is at least as great as that provided by a pair of audio transformers, while the tone is second to nothing ever produced in radio. The first audio stage screen grid tube accounts for the high volume, despite the use of only two stages of resistance coupling, where three stages were the previous rule with ordinary tubes or modestly high mu tubes.

In the radio tuner a new system is used, embodying the dynamic RF coil invented by the author, where the secondary is a single coil in two series-connected parts. One (dynamic) winding is on a rotatable form, and is connected in series with a fixed (static) winding, which is on the outside form. The tuning condenser is connected across the entirety, that is, across the combination of the static coil and the dynamic coil. The variometer effect of the moving coil or dynamic segment works in the same direction as does the tuning condenser which has its shaft coupled to the shaft of the moving coil. The same tuning motion turns both moving coil and condenser rotor simultaneously. Thus the frequency range is extended.

But in this particular circuit a very large starting capacity appears in the tuned plate circuit, and the dynamic coil system is used to enable covering the entire broadcast band with usual condensers, .0005 mfd. or .00035 mfd., despite this high-minimum-capacity handicap. The dynamic achievement is absolutely a solution of the difficulty, and is the only way to cover the full band while

still working the screen grid tube up to its practical maximum of amplification, a degree of sensitivity that will prove utterly astonishing.

Doubter Turns Booster

The circuit diagram is republished this week as Fig. 2 so that readers who are getting their first view of the diagram, and reading about the circuit for the first time, may have a clear picture of the electrical requirements. As a further aid, coil data will be given again.

Regarding those who have read previous articles on the subject of this new system of tuning, with full-gain screen grid amplification, it will be recalled that preliminary articles were published late in July and early in August, and that they immediately evoked letters by the armful. Some few wrote in wondering whether the circuit worked at all, as they had read glowing accounts of other circuits (not of my design, and not in RADIO WORLD) and had considered themselves stung. I mentioned some of these letters in a previous article, and gave new assurances that the HB Compact, battery model, is indeed all that I said it was, though secretly believing it was more.

It so happens that last Saturday afternoon a young man visited me at my office and identified himself as the writer of one of the doubting letters, one I singled out for special reply. He had read my published answer and thereupon had built the circuit.

"I want to take back what I said," he apologized. "I saw only four tubes in the circuit, and some system of tuning I was not familiar with, therefore doubted, and noted the absence of regeneration from the detector, so I wondered if the circuit could be all that you said it was. Well, after reading your reply I built the circuit, and I've come all the way from Camden, New Jersey, to New York City, to tell you that this circuit is the wonder of wonders, the dream of dreams, and the quintessence of what-have-you. Besides, its ten times, all of that, and ten times again!"

Sympathetic Toward Doubters

It was indeed gratifying to receive this enthusiastic report especially from one who had been the gloomiest of disbelievers, and most especially from a young man who travelled ninety miles to make an unnecessary apology, for set constructors who doubt the rosy descriptions of circuit performance have me on their side, rather than against them, because I, too, have read no end of articles on circuits, where the enthusiasm must have come only from the hands, and not from the head, most certainly not justified by the ordinary circuit that was touted to the skies. Any praise sung for the present circuit comes from the head, and from the heart.

Moreover I have received some letters from impatient readers who have built the circuit and who will take my place in the ballyhoo. Some of these letters will be published soon in RADIO WORLD, so if there is one last lingering doubter on the list, let him read these letters and make his peace with his imaginary enemy.

The coil winding is not a job, but the material with which to work has to be available. This consists of the odd requirement of a tickler form with a shaft protruding from front and rear. That is, the tickler shaft goes all the way through. This is necessary so that the panel-mounted coils may present a rear-extending shaft for connection by flexible coupler or link to the shaft of the tuning condenser. Note, therefore, that condensers with extending rear shafts are not required, since the coils afford this connection facility.

However, if pressed on this point, you may mount on the front panel tuning condensers that do have rear shaft protruding, and connect the rear of the condenser shaft to the front and only shaft of a modified home-constructed tuner. The picture diagram is not schemed out that way and you will have to improvise the slight difference in making connections.

Data on Coils

If an outside form of 2½" diameter is used for L1L2, this form may be 2½" high. See Fig. 1. The number of turns on the antenna coil primary, L1, is 14. A space of ¼" or ⅜" is left and another winding put on, separately. This has 36 turns. The tickler form should be small enough to rotate inside the other without striking the inside wall of the outside form. An outside diameter of 1¾" for the tickler will provide this safety. Wind 20 turns on the tickler, 10 on each side of where the tickler shaft pierces the moving coil's form. Connect one end of the dynamic or moving coil to one end of the 36-turn winding. Connect the tuning condenser to the remaining terminals of the series-connected coils. The wire may be No. 24 silk covered throughout.

HB COMPACT

Bernard

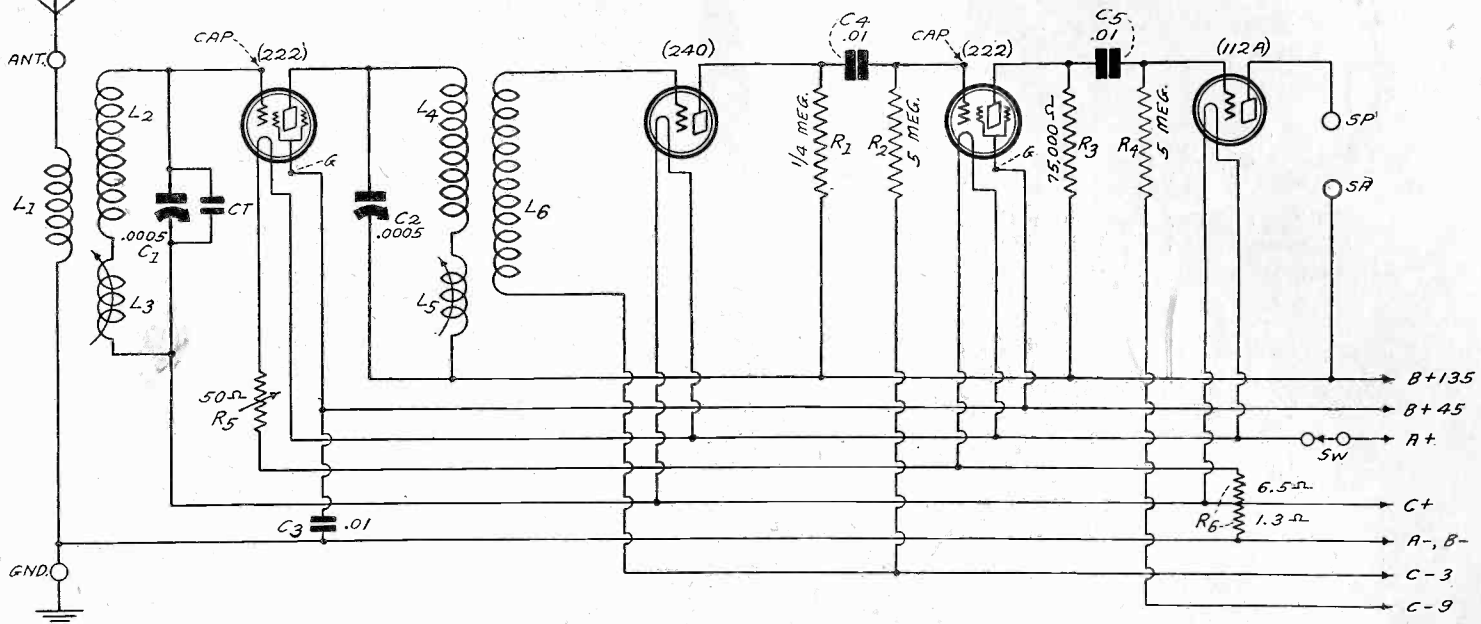


FIG. 2.

THE REDUCTION IN VOLTAGE ON THE FIRST TUBE BY THE RHEOSTAT R5 INCREASES THE VOLTAGE ON THE OTHER TUBES A TRIFLE. THIS IS PERMISSIBLE.

The inductance described is Cat. BT5A, made by the Screen Grid Coil Company, for .0005 mfd., and is shown at right in Fig. 1.

The other coil, BT5B, for interstage coupling, is different. The same size forms are used for outside stationary and inside moving coil, but there is a third form, slipped inside the other fixed form, and this third form has 60 turns on it. The data are: 20 turns on tickler, 36 turns on outside stationary winding, as in previously-discussed model, then 60 turns on a $2\frac{1}{8}$ " diameter tubing, to constitute L6. The interconnection of the 20-turn tickler and the 36-turn outside fixed winding leaves in reality two coils—the combination static and dynamic windings for tuning the plate circuit, L4L5, and the pickup coil to feed the 240 detector.

The Parallel Capacity

The large pickup coil, establishing a step-up ratio, helps the amplification tremendously, and as the Bernard tuner compensates for the distributed capacity arising, there is every reason to use this step-up.

The foregoing data are for .0005 mfd. If .00035 mfd. is used, add 10 turns to the 36-turn winding and 20 to the 60-turn.

The circuits will not tune alike unless compensated, because of the difference in starting capacities. Therefore a condenser has to be placed in parallel with the first tuning condenser, C1, to provide an amount of capacity equal to that developed in the succeeding plate circuit by the high-amplification device. What this capacity should be can not yet be accurately foretold for all installations, but 80 or 90 mmfd. was suggested, although it is known that in some instances more capacity than this will be required. The only difference, of course, is that where the capacity added to the first tuned circuit is not large enough, the dials will not track. Tune in a low wavelength station. The dials will read differently. Turn the first dial until it reads the same as the second. This tunes out the station. Do not molest the second dial. Now add the capacity across the first tuning condenser. A small fixed condenser, .0001 mfd., may be tried, and for finer adjustment the 80 or 90 mmfd. condenser may be placed across that, until the station comes in again. But at all hazards some definite capacity value will give you the same dial settings for both tuned circuits.

The Function of the Rheostat

Not enough receivers have been built so far to permit of specifying an average capacity that would mean something, but after about twenty or thirty receivers have been tested in the laboratory in that way, an average will be struck, and probably a fixed capacity will be specified. Meanwhile an adjustable one is advised, and it may as well be a high capacity, or two small ones in parallel, as two 80 mmfd. The only difference, as was stated before, is dissimilarity of dial settings, if the proper capacity is not put in parallel. No difference in the sensitivity, selectivity or tone obtains, and moreover the whole broadcast spectrum will be tuned in

even without any equalizing capacity across the first stage. It is the Bernard tuner in the plate circuit that guarantees full coverage of broadcast frequencies.

In tuning the receiver it will be found that the volume control has not much effect when only part of its resistance is thrown into circuit. This is due to the very high amplification. You can attenuate the signal so much that an ordinary receiver would suffer utter loss of signal, yet this receiver still brings in the signal loud as you would want, and more and more of the resistance has to be cut in. Therefore a rheostat of 60, 75 or 100 ohms should be used, not one of 20 or 30 ohms. The specifications call for a 75-ohm resistor, but some resistance more or less will not make a material difference.

The rheostat serves also to get rid of any regenerative effects produced in tuning in lower wavelengths. When the rheostat is turned to full a position of greatest resistance, the tubes other than the RF tube will light a little more brightly. It is just a little, and no harm results. The reason is the common resistance that serves all four tubes.

As the current through the first tube's filament is reduced, because of increased use of resistance in R5, the current through this common resistor, between A minus and C plus, is lowered, and the voltage drop in that section is therefore less, hence the applied voltage is higher on the three other tubes. The increase is so small that if the first tube were turned off entirely the higher voltage on the rest would rise only one-seventh, and, mind you, the first tube never is turned off unless all tubes are turned off. The switch on the rheostat prevents turning off only the first tube and leaving the others heated.

The first tuned circuit will seem to tune "more broadly" than the detector circuit, but this is scarcely a fact, merely an appearance. The first circuit tunes in a certain frequency and some other frequencies incidentally, as it alone has to select as best as possible from the full band. This is true of any circuit. The next stage, however, has the benefit of pre-selection by the first tuner, hence seems to tune more sharply. Appearances should not be counted at all, only the actual result, and it will be found that the stations will be tuned in satisfactorily without crosstalk interference.

The values of the resistors in the audio channel should be followed, except that in some instances motorboating may be experienced, whereupon a 50,000 ohm resistor should be used for R3 instead of 75,000 ohms, or across the 75,000-ohm resistor a leak should be connected, 1 or 2 meg. or thereabouts.

[Last week's constructional article was a textual description of building the HB Compact, battery model, illustrated with a full-size picture diagram that occupied two full pages. Therefore the diagram had to be on different pages than the text, although on the succeeding two pages. References to the diagram were many, and it is suggested you obtain two copies of the August 31st issue, so you can also have the picture diagram before you while you read the textual wiring instructions.—Editor.]

TABLE II.
Average Characteristics of Rectifier and Voltage Regulator Tubes

Type	Use	Filament supply	Filament terminal voltage	Filament current (amperes)	Filament Resistance (ohms)	Maximum voltage per plate, R.M.S.	Maximum rectified current (milliamperes)
UX 280	Full Wave Rectifier	A.C.	5.0	2.0	2.5	350	110
UX 281	Half Wave Rectifier	A.C.	7.5	1.25	6.0	700	85
UX 274	Voltage Regulator	Rated voltage, 90 D.C. Starting voltage, 125 D.C. Max. direct current, 50 MA.					
UX 276*	Ballast Tube	Current rating, 1.7 amps. Voltage range 40-60					
UX 286*	Ballast Tube	Current rating, 2.05 amps. Voltage range, 40-60					

* Standard mogul type screw base.

TABLE III.

Grid Voltage, Plate Current Characteristics of the 220 Tube

Eg	Ep 45	90	135	180
0	4.4	12	20.5	27.0
-5	2.5	9	17.5	24.0
-10	1.0	6.3	14.2	21.0
-15	0	3.7	11.2	18.0
-20		.7	8.5	16.8
-25		0	5.7	13.7
-30			3.5	10.5
-35			1.7	7.8
-40			.5	5.3
-45			0	3.0
				1.4

TABLE IV.

Grid Voltage, Plate Current Characteristics of the 201A Tube

Eg	Ep 45	90	135
0	1.7	5.7	13.0
-2	.7	3.7	9.1
-4	.2	2.3	7.2
-6		1.2	4.8
-8		.3	3.3
-10		0	1.8
-12			1.0

TABLE V.

Grid Voltage, Plate Current Characteristics of the 112A Tube

Eg	Ep 45	90	135	180
0	2.8	14	24	34
-2.5	1.5	8.6	19	29
-5	0	4.5	14.5	24.5
-7.5		1.5	9.0	19.3
-10		0	4.5	15.5
-12.5			1.6	10.3
-15			0	5.7
-17.5				2.2
-20				.5
-22.5				
-25				

TABLE VI.

Grid Voltage, Plate Current Characteristics of the 171A Tube

Eg	Ep 45	90	135	180	220
0	13	38.5	70	102	134
-10	2	20.0	48	77	102
-20	0	6	29	58	77
-30		0	12	38	66
-40			2	20	44
-50			0	6.5	26
-60				0	10
-70					1
-80					0

TABLE VII.

Grid Voltage, Plate Current Characteristics of the 222 Screen Grid Tube
Screen Grid Voltage +45 volts.

Eg	Ep 90	135	180
0	1.90	1.98	2.05
-1.5	1.45	1.48	1.51
-3.0	.90	.95	1.00
-4.5	.55	.60	.61

PICK-UP

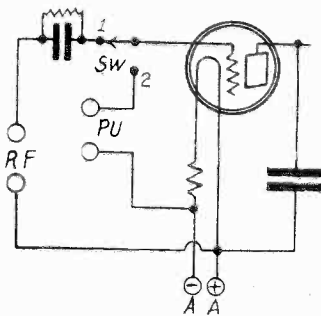


FIG. 78

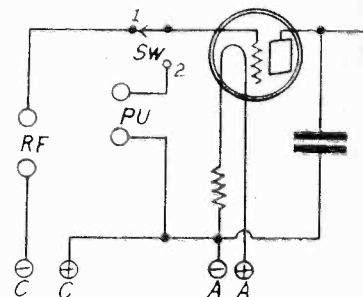


FIG. 79

TABLE VIII.

Grid Voltage, Plate Current Characteristics of the 240 Tube

Eg	Ep 45	90	135	180
0	.24	.63	1.55	2.47
-1	.04	.30	.92	1.54
-2	0	.09	.48	1.22
-3		0	.22	.69
-4			.05	.34
-5			0	.20
-6				0
-7				0

TABLE IX.

Grid Voltage, Plate Current Characteristics of the 227 Heater Tube

Eg	Ep 45	67.5	90	112.5	135	157.5	180
0	5.4	7.0	10.2	13.6	17.0	20.4	23.8
-2	2.4	4.8	7.65	11.0	14.15	17.3	20.45
-4	1.0	2.95	5.35	8.35	11.55	14.7	17.85
-6	.1	1.4	3.4	5.95	8.9	12.05	15.20
-8		.4	1.9	3.95	6.55	9.55	12.70
-10			.75	2.3	4.45	7.05	10.2
-12			.1	1.1	2.80	5.00	7.75
-14				.3	1.45	3.20	5.45
-16					.62	1.9	5.7
-18					.1	.95	2.25
-20						.30	1.24
-22							.57
-24							.10

TABLE X.

Grid Voltage, Plate Current Characteristics of the 245 Tube

Eg	Ep 90	180	250
0	40	97	142
-10	22	74	119
-20	7.0	52	97
-30	.5	32	74
-40		15	52
-50		4.0	32
-60		1.0	15
-70			4.0
-80			1.0

TABLE XI.

Grid Voltage, Plate Current Characteristics of the 224 Heater Type Screen Grid Tube. Screen Voltage +75 Volts.

Eg	Ep 135	180
0	5.45	5.55
-1.5	3.875	4.00
-3.0	2.55	2.65
-4.5	1.45	1.5
-6.0	.4	.7

[Herewith is fifteenth consecutive weekly instalment of J. E. Anderson's and Herman Bernard's book, "Power Amplifiers," which is being printed serially. The tables referring to tubes are a direct continuation of last week's article, while the connections for phonograph pickups and microphones introduces a new subject. Another interesting instalment will be published next week. Power detection will be the topic.—Editor.]

Playing Phonograph Records

In modern broadcast receivers provision is often made for connecting a phonograph pick-up unit to the circuit so that the audio

CONNECTIONS

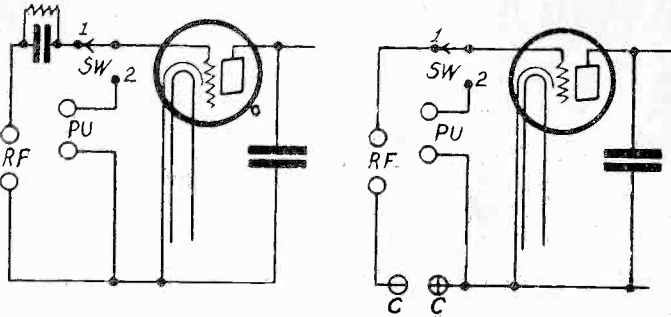


FIG. 80

FIG. 81

amplifier may be used for playing records electrically. There are many different ways in which the pick-up unit can be connected, but not all those which have been used are suitable.

The most common method used when the amplifier was not originally designed for record playing is to plug the pick-up unit into the detector socket so that the pick-up terminals make contact with the plate spring and one of the filament springs on the socket. This put the pick-up unit in series with the primary of the first audio transformer and also with the plate battery. This connection should never be used because a current is continually flowing in the circuit, and this current changes the characteristics of both the audio transformer and the pick-up unit. Moreover, it drains the battery when no current is necessary.

The pick-up unit should be connected either in the grid circuit of the detector tube in such a manner that the detector tube becomes an amplifier or else in series with the primary of the first audio transformer in such manner that the plate voltage source is excluded from the circuit. If either of these connections gives so much amplification that the volume control on the pick-up unit, or the volume control in the amplifier, if any, does not have sufficient range to limit the output to desired values, then the pick-up unit can be connected in the grid circuit of the tube following the detector, or in series with the primary of the second transformer.

Fig. 78 illustrates a proper connection of the pickup unit in the grid circuit of a detector employing grid condenser and leak. The pick-up unit is connected across the terminals marked PU. One of these terminals is connected to minus A below the ballast resistor. The other is connected to one point of a single pole, double throw switch SW. When the amplifier following the detector is to be used for radio reception the switch is turned to point (1), thus picking up the tuned circuit and disconnecting the pick-up unit. The tube is then adjusted for detection. When the pick-up unit is to be used the switch is turned to point (2), disconnecting the tuner and converting the detector to an amplifier having a negative grid bias equal to the drop in the ballast resistor.

Fig. 79 illustrates the same connection when the detector operates on the grid bias principle. The return of the PU is now made so that the greater portion of the grid bias battery is excluded from the circuit when the tube is to be used as an amplifier. As in the preceding case the only bias retained is the drop in the ballast resistor. This is sufficient because the signal voltage from the pick-up unit will be much less than the bias thus provided.

When the detector tube is of the heater type, the pick-up unit can be returned directly to the cathode as in Fig. 80. This does not provide any bias. None is really necessary because the signal voltage is very small. However, it is a simple matter to provide bias by returning the pick-up unit to a point of lower potential than the cathode, for example, to the point where the grid return of the first audio amplifier is made. It is assumed that the cathode of the detector tube is connected to the cathode of the following tube.

Another way of providing a small bias is to insert a low value resistor between the cathode and the point where the pick-up unit is returned. This can be done without appreciably changing the detecting efficiency of the tube.

If the heater type detector is operated on the grid bias principle, the pick-up unit can be connected as in Fig. 81. While the pick-up unit is here connected to the cathode, it may be connected as suggested in Fig. 80 to get a small negative bias.

If the grid bias for detection is obtained from a battery, the pick-up unit may be returned to a point on this battery about 1.5 volts from the cathode, thus making the bias 1.5 volts negative for amplification. A small resistance also may be inserted in the cathode lead above the pick-up return point to provide a small bias. It makes no difference whether the negative bias for detection is obtained from a voltage drop in a resistance or from a battery.

One reason why it is not essential to have a negative bias on the tube when it is used as an amplifier for phonograph signals is that the impedance of the pick-up unit is relatively small, so that any grid current that will flow will not produce a great drop in the signal voltage impressed on the tube.

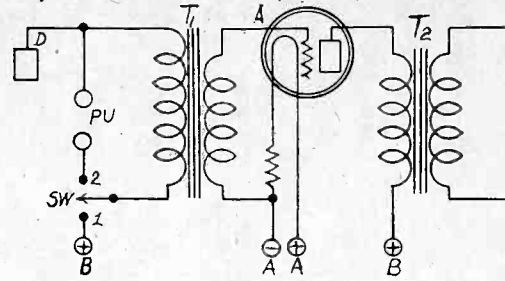


FIG. 82

THE PROPER METHOD OF CONNECTING THE PICK-UP UNIT IN SERIES WITH THE TRANSFORMER PRIMARY.

If it is desired to connect the pick-up unit in series with the primary of the first transformer, it may be done as in Fig. 82. One side of the pick-up unit is connected permanently to the plate of the tube and the top of the transformer. The other side of the unit is connected to a point on the double throw, single pole switch SW. When the pick-up unit is to be connected to the transformer the switch is thrown to point (2). This disconnects the plate voltage so that no direct current can flow either in the tube or in the pick-up and transformer circuit. When the amplifier is to be used with the tuner, the switch is set on point (1). This disconnects the pick-up unit and puts the tube and the transformer primary on the battery.

Sometimes a matching transformer is used between the pick-up unit and the audio coupling transformer to get a louder signal and improved quality. The method of connecting this transformer is shown in Fig. 83, T1 being the matching transformer and T2 the audio coupling transformer. The primary of T1 is provided with a number of taps for adjusting the impedance of the primary to the impedance of the pick-up unit. The secondary of T1 is supposed to have the same impedance as the primary of T2.

The switch SW2 is for selecting either the radio signal or the signal from the pick-up unit. The B battery may be connected permanently to the junction of T1 and T2 because when the switch is set on point (2) no direct current can flow in the circuit formed by the secondary of T1 and the primary of T2. When the switch is set on point (1), the matching transformer is thrown out of the circuit and the plate circuit of the detector tube is established through the primary of T2.

The coupling transformer can be used with any of the connections illustrated in Figs. 78 to 82 inclusive. It is necessary only to connect the secondary terminals of T1 to the points labeled PU in these circuits and leaving the terminals of the pick-up unit on the primary of T1.

The use of the matching transformer in any case is of doubtful advantage. The matching is based on the assumption that best results will be obtained when the pick-up unit delivers maximum power. What is desired is the maximum voltage on the grid of the amplifier, and this is obviously not obtained when one-half of the voltage generated in the pick-up unit is wasted in the impedance of the unit, which is the condition for maximum power output. The use of the matching transformer changes the quality somewhat. Whether this change is an improvement or a loss depends largely on personal taste as to what constitutes good quality.

While the pick-up unit has been put either in the grid circuit of the detector or in the primary of the first audio transformer in all the circuits shown in Figs. 78 to 83, inclusive, it may be better in some instances to put it in the grid circuit of one of the amplifier tubes or in series with the primary of the second transformer. Just where it should be put in any given amplifier depends on the amplification, the sensitivity of the pick-up unit, the volume desired, and on the effectiveness of the volume control built in with the pick-up unit. In most instances sufficient volume will be obtained if the unit is connected in the grid circuit of the amplifier ahead of the power tube.

Use of Microphone

Some experimenters often have occasion to use a microphone with their amplifiers, either for telephonic communication or for measuring sound intensities. The connection of a microphone to a power amplifier is essentially the same as the connection of a phonograph pick-up unit, and the terminals marked PU in the circuits in Figs. 78 to 81, inclusive, may be used for connecting the microphone output. What is meant by the output terminals is indicated in Figs. 84 to 87, inclusive.

The carbon button microphone operates on the principle of varying resistance. The sound waves exert a pressure on the diaphragm D, Fig. 84, and this in turn exerts a varying pressure on the carbon granules. The resistance of the carbon is lower, the greater the pressure. As long as the pressure on the carbon remains constant, a steady current flows from the battery E through the carbon and the primary of transformer T. As sound falls on the diaphragm, the resistance varies and therefore the current varies. This varying current flows through the primary of transformer T and induces a corresponding varying electromotive force in the secondary. The induced emf is alternating and can be impressed on the grid of an amplifying tube.

A push-pull carbon microphone is essentially two equal microphones placed back-to-back. A single diaphragm, D, Fig. 85, is

MICROPHONE USES

How to Hook Up the Four Main Types

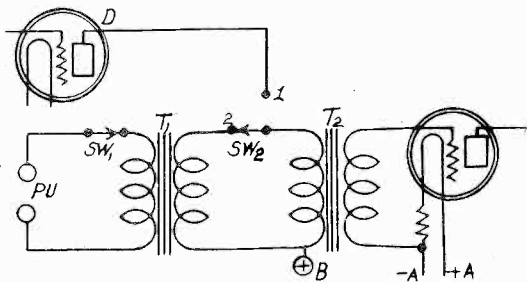


FIG. 83

placed between two equal carbon buttons C,C. Two equal circuits are formed by the two sides of the microphone, the battery E, and the two equal sides of the primary of transformer T. As the diaphragm vibrates, the resistance in one circuit is increased and that in the other decreased by the same amount. The current through the battery remains substantially constant, but that through the transformer primary alternates in the same manner as the sound that falls on the diaphragm. There is a DC component in each of the sides of the primary, but the component in one side neutralizes that in the other so that only the alternating component is effective. An alternating emf is induced in the secondary of the transformer, and this varies as the sound waves that fall on the diaphragm. The output emf can be impressed on the grid circuit of an amplifying tube.

Single and push-pull carbon microphones can be obtained at widely varying prices, depending on the accuracy with which they have been constructed. Transformers suitable for these transformers are also available. The manufacturers of the microphones specify what transformer should be used as well as what the value of the voltage E should be.

Where exceptional fidelity is required, condenser microphones are used. A condenser microphone consists essentially of a high grade condenser of very small capacity, of which one plate is rigid and the other is a tightly stretched diaphragm. It operates on a different principle from that of a carbon microphone. A high voltage polarizing battery E, Fig. 86, is used to charge the condenser through a very high resistance R1. When sound waves fall on the diaphragm of the microphone condenser M, the capacity changes. When it increases current flows into the condenser through R1, and when it decreases current flows out through the same resistance. That is, when the diaphragm vibrates an alternating current flows through R1. The alternating voltage drop in R1 is impressed on the grid of an amplifying tube, either directly or through a condenser C and a grid leak R2. R3 in this circuit is a ballast which maintains the grid of the tube negative.

Extreme precautions must be taken to prevent any leakage current through the insulation of the microphone. If there is considerable leakage the low notes will not be reproduced in their true proportion. The resistance connected across the microphone must also be exceedingly high if the low notes are to be picked up as efficiently as the high. In practice the total effective resistance may be as high as 50 megohms, which indicates that the insulation of the condenser must be of a very high order.

Because of the necessity of a high resistance across the microphone it may be better to omit C and R2 and couple the microphone by means of R1 alone. The grid of the tube must be kept negative because any grid current would indicate a comparatively low resistance shunted across the microphone.

It is customary to mount the first amplifier tube as near the microphone as possible in order that leakage between leads may be reduced to a minimum.

While the output in the case illustrated in Fig. 86 is a transformer, this could well be a resistance coupler.

Condenser microphones also come in push-pull. A circuit for such a microphone is illustrated in Fig. 87. All precautions men-

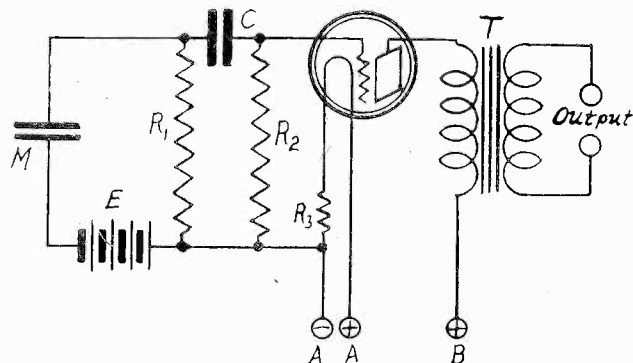


FIG. 86.

tioned in connection with the single microphone in Fig. 86 apply with equal force to this circuit. It is clear that the stopping condensers and the grid leaks can be omitted if the negative terminal of the grid bias battery E2 is connected to the positive terminal of the microphone polarizing battery E1.

Photo-Electric Input

In many amplifiers the input signal is derived from a photo-electric cell. This is the case wherever the signal at one stage consists of light intensity variations, as in talking motion pictures in which the sound signal is recorded on the film, in certain types of phonographs in which the sound is also recorded on a film, in the transmission of still and moving pictures, in the transmission of television images, and in photo-telephony.

The connection of the photo-electric cell to the amplifier is not unlike the connection of the condenser microphone. A polarizing battery on the photo-electric cell is necessary, which serves the same purpose as the B battery in ordinary amplifier tubes. Indeed, the B battery can be used for the photo-electric cell at the same time it is used for amplifier tubes.

In Fig. 88 is shown one connection of a photo-electric cell to an amplifier tube. PC is the photo-electric cell into which the signal-modulated light enters. E is the polarizing battery and R1 is the load resistance. The fluctuating light produces a fluctuating current through this resistance and the resulting voltage drop is impressed on the grid of an amplifier tube, in this instance through the stopping condenser C and the grid leak R2. The use of C and R2 is for the purpose of establishing a definite grid bias on the tube, which in this case is the drop in the ballast resistance R3.

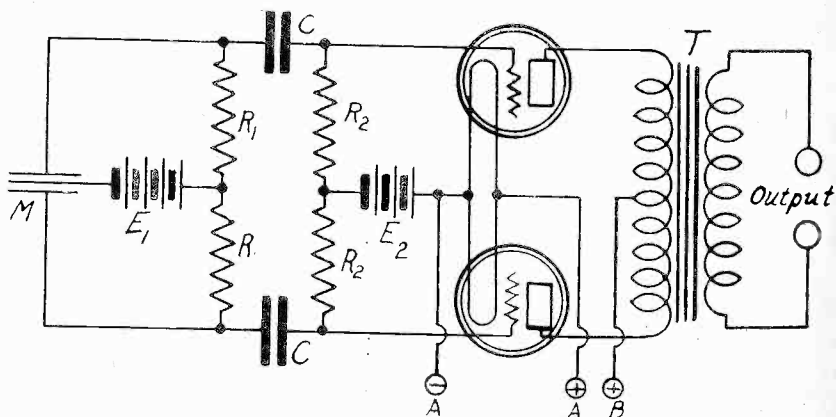


FIG. 87.

THE CONNECTION OF A PUSH-PULL CONDENSER TYPE MICROPHONE TO A PUSH-PULL AMPLIFIER.

It is not necessary, however, to use C and R2, as shown in Fig. 89. In this circuit the grid is maintained at a suitable negative potential with respect to the filament by means of a grid battery E. In this circuit, also, the B battery is used for polarizing the photo-electric cell, but a separate battery could be used just as well.

Resistance couplers follow the circuits in Figs. 88 and 89 because in nearly all cases where a photo-electric cell is used it is necessary to amplify low frequencies as well as the high. Indeed, in some cases it is necessary to amplify so-called direct current. Where telephonic frequencies only are involved a transformer could follow the amplifier tube in either of the circuits in Figs. 88 and 89.

The output binding posts in Figs. 88 and 89 can be connected to PU terminals in Figs. 78 to 81, inclusive.

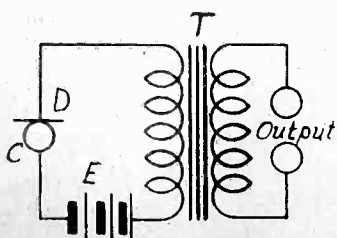


FIG. 84

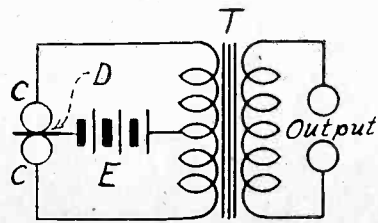


FIG. 85.

NEW 228 TUBE

Additional Curves for High Mu AC Valve

By J. E. Anderson

Technical Editor

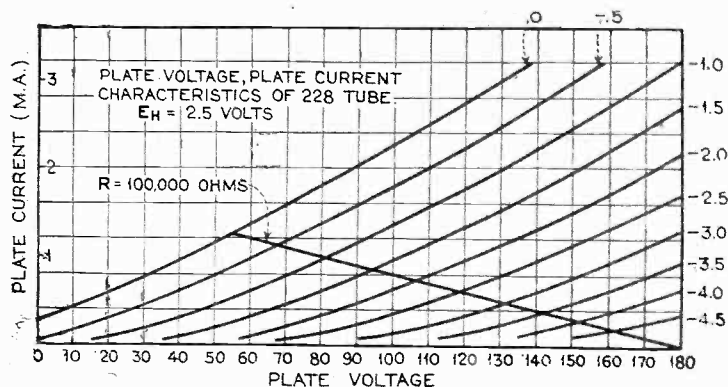


FIG. 1.

PLATE CURRENT, PLATE VOLTAGE CHARACTERISTICS OF THE 228 HIGH MU HEATER TUBE.

LAST week was published for the first time announcement of the new 228 heater type high mu tube, with characteristic curves. The two curves then given were for no load on the tube and for a load resistance of 100,000 ohms, and both curves gave the relationship between grid voltage and the plate current.

It is now customary to give also a family of plate voltage, plate current curves to show the performance of the tube under varying conditions; because from such a family of curves it is possible to obtain the plate current for different effective plate voltages, grid voltages and plate load resistances. These curves also provide a quick method of obtaining the voltage amplification for any given load resistance.

Because of the usefulness of these curves we herewith publish a family of plate voltage, plate current curves for a range of grid voltages from zero to 4.5 volts negative and a plate voltage range from zero to 180 volts positive.

Amplification Factor Varies

As was pointed out last week, the amplification factor varies to some extent, a fact which is true for all tubes. The family of curves herewith also shows this variation of the amplification factor. Take, for example, the line representing a current of 2.8 milliamperes and note the plate voltages where the various curves cross this line. The zero bias line crosses the selected current line at 123 volts. The -0.5 line crosses the current line at 143 volts. The difference is just 20 volts. Since this change was produced by a grid voltage change of $\frac{1}{2}$ volt, the amplification factor is 40. The -1.0 line crosses the same current line at 163.5 volts. The difference between the two voltages is now 163.5-143, or 20.5, giving a value of 41 for the amplification constant. That these values should be smaller than the values obtained for small changes of plate voltage is to be expected. Last week the amplification "constant" was given as 45, which was a mean value obtained by changing the plate voltage by 7.5 volts.

The amplification factor itself is not so important as the voltage amplification that can be obtained from the tube in a given circuit. This amplification can be obtained very simply from the family of curves. The load line drawn across the curves is for a resistance of 100,000 ohms, as indicated, and a plate battery voltage of 180 volts. What is the voltage amplification between zero bias and a bias of 4.5 volts? The load line crosses the zero bias line at 54 volts effective plate voltage. It crosses the curve for 4.5 volts bias at 161.5 volts. The difference, which is the drop in the resistor, is 107.5 volts. Since this is produced by a grid voltage change of 4.5 volts, the amplification is 23.9.

If necessary it would be possible to use a bias as great as 5 volts without much distortion. While the curve for a bias of 5 volts is not given, it crosses the load line at 171 volts. Therefore between zero bias and 5 volts the amplification is 23.4. There is evidently some distortion or the two values would have been the same, but as they do not differ much, the distortion is small.

If the tube is to be operated under these conditions the fixed grid bias should be 2.5 volts. At this point the plate current is nearly .6 milliamperes, and the effective plate voltage is 119 volts. While this would allow a signal amplitude of 2.5 volts, it would be better not to use more than 2.25 volts. This would make the amplitude of

the signal drop in the load resistor 53 volts, which is ample to load up a 245 tube. Now if grid bias detection is used it is possible to get more than 2.25 volts out of the detector, so that only one amplifier tube is needed between the detector and the power tube.

If somewhat better quality is desired a plate load resistance of .2 or .25 megohms should be used. If .2 megohm be used the amplification will be raised to nearly 28 times. The maximum voltage amplitude in the coupling resistor will be nearly 70 volts. This is more than enough to load up a 245 tube. A negative bias of 2 volts would be sufficient in this case. This would give a steady current of about .5 milliamperes.

If the plate load resistance be .25 megohm, the amplification will be 29, with a smaller percentage of distortion than when the load is 100,000 or 200,000 ohms.

Used Ahead of a 250

When the tube is used ahead of a 250 power tube, 180 volts in the plate circuit are not enough. It should be raised to at least 225 volts and be applied through a load resistance of .25 megohm. This will allow loading up the power tube to the maximum without appreciable distortion. The negative bias in this instance should be slightly less than 3 volts. Even when the 228 tube precedes a 250 power tube, a grid bias detector will deliver sufficient signal voltages to load up the circuit provided that 225 volts or more are used on the 228 and the load resistance is .25 megohm or higher. Hence it is not necessary to use more than two tubes in the amplifier.

As an amplifier having three plate circuits on the common voltage supply is very unstable, exceptional precautions must be taken to minimize feedback through the common impedance. For a discussion of this subject the reader is referred to the August 10th issue of RADIO WORLD.

Used as a Detector

The performance of this tube as a grid bias detector is not shown in the family of plate voltage, plate current curves published herewith, because detection depends on the departure of the curves from straight lines, especially near the plate voltage axis. The detection effect is shown much better on the grid voltage, plate current curves last week. There it appears that best detection is obtained when the grid bias is 4 volts negative. This is for a load resistance of 100,000 ohms and a plate battery voltage of 135 volts.

Taking the amplification factor into consideration, the best bias for detection when the plate battery voltage is 180 volts would be 5 volts negative. Likewise when the plate battery voltage is 220, the bias for detection would be 6 volts negative.

The bias does not depend appreciably on the value of the load resistance, either for detection or amplification.

Too Much Bias in First Stage

AFTER having installed a 171A power tube in my battery-operated receiver, where the last tube formerly was a 201-A, I find the tone is not nearly as clear. My receiver has a radio frequency amplifier, condenser-and-leak detection, and two stages of transformer-coupled audio.—J. H. D.

The wiring of receivers of the type of yours usually provides a common C minus lead for the first and second audio stages. Therefore, although you retained a 201A as first audio amplifier at the usual plate voltage, say, 90 volts, the change in the last-stage bias for the new power tube, to about 40.5 volts negative, biased the first audio tube to the same extent. This is enormously wrong. Cut the C lead that is common to the grid circuits of the two audio stages, so that the first stage can go to 4.5 volts negative, as formerly, while the last stage alone gets the high bias. Then the tone will be clear.

WORTH THINKING OVER

THE person who can listen in on the radio these times and not get some better understanding of the culture that comes with good music must be like the girl who, when shown the tempestuous beauty and inspiring grandeur of Niagara Falls remarked gleefully: "How cute!"

REACTIVATION OF T

Flashing, with No Plate Voltage, Restore

By Gush

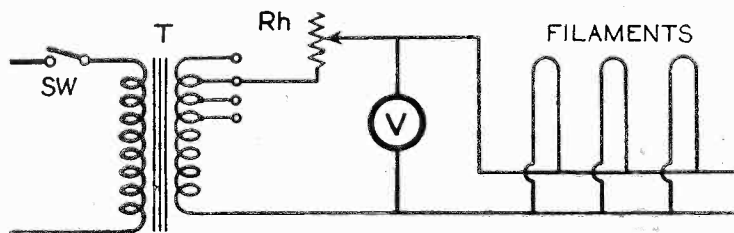


FIG. 1
A CIRCUIT FOR FLASHING TUBE FILAMENTS DURING REACTIVATION.

Although new vacuum tubes are comparatively inexpensive, there is a great deal of interest in reactivation of "paralyzed" tubes. In most instances a "paralyzed" tube is simply a dead tube, and any attempt to revive it is usually wasted time and effort. However, there are cases in which the tube is only suffering from suspended activity, and in such cases the reactivation process may restore the tube to another period of usefulness. Only the thoriated tungsten filaments can be reactivated under any conditions.

The thoriated tungsten filament is made of a mixture of pure tungsten and a small quantity of thorium oxide. The heating of the filament reduces the thorium oxide near the surface of the conductor to pure thorium, the thickness of the layer of thorium being only about one molecule. The presence of the thorium has the property of releasing electrons more readily than tungsten, and it is for this reason that filaments of this type are operated at a much lower temperature than filaments of pure tungsten.

The metallic thorium on the surface of the tungsten continually evaporates as the tube operates. The thorium that is thus liberated is replaced by the reduction of the supply of thorium oxide in the interior of the filament, that is, by the conversion of the oxide to the pure metal. Normally this process is gradual. When all the oxide has been reduced and all the thorium evaporated, the tube is dead beyond the possibility of reactivation.

A Paralytic Stroke

Sometimes a tube is subjected to abuse, for example, the application of an excessive plate voltage. This may cause the surface layer of thorium to be evaporated without any replacement from within. The tube is then apparently dead or paralyzed. If the "paralyzing" shock was not too great, it is possible to revive the tube in this case, for there is still a quantity of thorium oxide in the filament which can be reduced to metallic form on the surface of the tungsten provided the proper process be applied.

The following tubes have thoriated filaments: UX-199, UX-120, UX-200A, UX-201A, UX-222, UX-240, UX-171 and UX-210, and the corresponding tubes of the CX type. In addition to these amplifier tubes, the two rectifiers 213 and 216-B have thoriated filaments.

The reactivation process consists of two parts, the flashing and the burning. Both of these are required in reactivating a tube which has been abused greatly; only the second need be applied if the tube has been overloaded but slightly.

The purpose of the flashing is to clean the surface of the tungsten filament, to remove all impurities on the surface. This is done by operating the filament for a period of from 10 to 20 seconds at a high temperature so that any impurities, including any thorium, is actually boiled off. In effect this completely paralyzes the filament, but leaves it in a condition for the formation of a new and clean thorium layer from the thorium oxide that is still left in the interior. The filament terminal voltage for flashing depends on the normal terminal voltage of the tube in question, and is approximately three times as great. The actual values for the various tubes are given in the table herewith.

The Burning Process

The burning process consists of operating the filament for a certain period at a terminal voltage about 20 per cent. higher than the normal operating voltage. The exact burning voltage for each tube is also given in the table. The length of the

Type of tube	Emission test	Filament
199	3.3	4
120	3.3	4
222	3.3	4
201A	5.0	7
201B	5.0	7
200A	5.0	7
240	5.0	7
171	5.0	7
210	6.0	9
213	4.0	6
216B	5.0	9

burning period depends on the tube and on its condition. It is first burned for a period of 30 minutes. Then a test is made of its filament emission. If the emission current is less than the minimum current given in the attached table for the tube in question, the filament is burned for another period of 30 minutes and another emission test is made. It may require a total of 1.5 hours for complete reactivation, or the first period of 30 minutes may be sufficient. If no improvement in the emission current is shown after a few thirty-minute periods of burning, the tube can be considered dead.

If the burning was done without first flashing the tube and no improvement is shown with the continued burning, the filament should be flashed before abandoning hope of reactivation.

Emission Test

During the emission test the tube is operated as a rectifier, the grid and the plate being tied together. The rectifier 213 has two filaments which may be in different conditions. Therefore

Right or

[Herewith are ten questions. They are propounded from articles published in last week's issue, August 31st. If you read that issue carefully, then you should be able to answer all ten questions accurately. Read this week's issue from cover to cover and you will know the answers to next week's questions even before the questions are put.—Editor.]

* * *

(1).—When a screen grid tube is operated in a resistance coupled circuit, the applied plate voltage should be increased to offset the voltage drop in the coupling resistor and the screen voltage should be decreased.

(2).—An electrolytic condenser of large capacity should be connected across the output of a rectifier next to the tube for best results.

(3).—A screen grid tube in an amplifier is of no advantage because only a small fraction of the amplification factor can be utilized.

(4).—If a high mu tube has a low internal plate resistance it is feasible to couple it to the next tube by means of a transformer.

(5).—If a family of plate current, plate voltage curves is available for a power tube it is possible to calculate the amount of second harmonic distortion which will result when a given signal is impressed on the tube.

(6).—The grid bias on a tube can be determined by measuring the plate current in the tube with a known voltage on the plate.

(7).—In a screen grid tube the plate current flows in the same direction for all plate voltages just as in a three-element tube.

(8).—In a screen grid tube the screen current remains constant and is always less than the plate current.

(9).—Grid current never flows in a tube when the grid is negative with respect to the filament of the cathode.

(10).—When a vacuum tube is used as a grid bias detector for large signals the detected signal is substantially proportional to the radio frequency signal and not proportional to the square of the carrier amplitude.

THORIATED FILAMENTS

Most Emission—Over-Heating Also Used

Quirk

Flashing	Plate voltage	Minimum emission	Filament Resistance
	emission test	current (ma)	(Ohms)
12.0	50	6	50
12.0	50	15	25
12.0	Test as amplifier		25
16.0	50	25	20
16.0	50	25	20
16.0	50	12	20
16.0	50	25	20
16.0	50	50	20
16.0	100	100	10
16.0	100	50 (per filament)	2.5
16.0	125	100	6

of the filaments should be reactivated and tested independently of the other. That is, the tube is tested as if it were different tubes.

The source of the flashing and burning voltages may be either a battery or a transformer. For flashing a B battery of the required voltage might well be used since the duration of the flash is very short, and hence very few milliampere-hours will be taken from the battery. For burning it is necessary to use storage batteries or a suitable transformer, except that the filament of dry cell tubes may be burned with dry cells.

Whenever it is possible to use a transformer for flashing and burning this is recommended. Inexpensive toy transformers having the required voltages are available and can be purchased in almost any electrical store. If the voltage taps are not exactly those required for a given operation and a given filament, a rheostat can be inserted in series with the filament or a transformer for adjusting the voltage to the required value. Fig. 1 shows the circuit for the flashing operation, using a transformer as the voltage source and Fig. 2 shows the connection

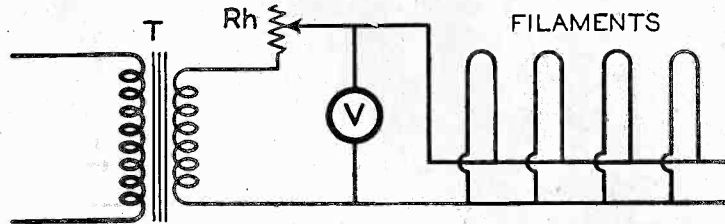


FIG. 2
AN ARRANGEMENT OF CIRCUIT FOR BURNING THE FILAMENT DURING REACTIVATION.

for the burning operation. Essentially the two circuits are the same, differing only in the voltage indicated by the voltmeter across the filament line. Fig. 3 shows the emission test circuit, V being the voltmeter which measures the emission test filament voltage and ma the milliammeter which indicates the emission.

To make the process of reactivation clear, let us take a UX-120 tube as an example. The test circuit is arranged as in Fig. 1, with a 25-ohm resistor in place of the filament. Turn on the power and adjust the taps on the transformer and the setting of the rheostat until the reading of the AC voltmeter is 12 volts, the flashing voltage given in the table. Then open the switch, remove the 25-ohm resistor and put the filament of the 120 tube in its place. Get a watch ready for timing the flash. Turn on the power for 10 or 20 seconds. A longer flash will probably vaporize the filament and end the operation.

If the filament survives the flashing operation readjust the circuit so that the voltage indicated by the AC voltmeter is 4 volts, the burning voltage given in the table for the tube in question. Leave it burning at 4 volts for 30 minutes.

At the expiration of this burning period, put the tube in circuit shown in Fig. 3 and measure the emission current. The filament voltage now should be 3.3 volts and the plate voltage should be 50 volts. If now the emission current, that is, the combined grid and plate current, is more than 15 milliamperes, the tube may be considered reactivated. If it is less than this, return the tube to the burning circuit, Fig. 2, for another 30-minute period. Test again on circuit in Fig. 3. Continue until the total burning period is 1.5 hours, or until the emission current is greater than 15 milliamperes.

Burn-out Danger

As some of the filaments may burn out completely during the flashing process, it may be well to attempt to restore a tube first to the burning operation alone. If it cannot be restored by this method alone, it has been greatly damaged and very little is lost if the filament does go during a flashing operation.

The last column in the table gives the hot resistance of the filament of the tube. This is included in order that a resistor of the indicated value may be connected across the filament line while the flashing volt is adjusted.

The taking of an emission test with the circuit in Fig. 3 should be done quickly, for nothing is gained by letting current flow for a considerable period. It only shortens the life of the tube, and may defeat the purpose of the reactivation. In order to shorten the time that current flows, the battery E should be left disconnected until everything is ready for a reading. Then contact should be made just long enough to observe the reading on the meter MA.

Whenever it becomes necessary to buy a new tube because an old one cannot be reactivated, it is best to get one which cannot be reactivated at all. It has a longer life. Of course, there are a few tubes which cannot be had except in the thoriated tungsten filament. When a new tube of this type is purchased it is well to remember that it can readily be "paralyzed" by abuse, that is, by the application of too high plate voltages and too low grid voltages.

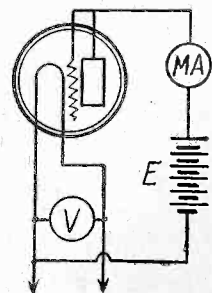


FIG. 3
WHEN TAKING AN EMISSION TEST ON THE TUBE THE PLATE AND THE GRID SHOULD BE CONNECTED TOGETHER.

Wrong?

Right. This is correct for a screen grid tube, for this will not function properly if the effective voltage on the plate is less than the screen grid voltage. In a three-element tube it is necessary to increase the battery voltage, unless the amplitude of the signal demands it.

Wrong. If the condenser next to the rectifier tube is too small the tube is subjected to heavy strains. Also, the filtering will be much poorer than if a smaller condenser is used.

Wrong. The main object of using a tube is not to get maximum amplification that tube is capable of but to get a certain amount of amplification from the tube and the circuit. The screen grid will yield a higher amplification than any other tube, even if a small fraction of its amplification constant is utilized.

Right. The mu of the tube has nothing to do with the coupling that follows the tube. If the internal impedance of the tube is so low that it is small compared with an audio transformer primary impedance, it is all right to use a transformer.

Right. The output power can be calculated from the curves by assuming the curves are straight lines. The second harmonic distortion can be calculated by taking into account the fact that the curves are not straight.

Right. The tube can be used as a vacuum tube voltmeter.

Wrong. For certain voltages on the plate the plate current is negative, a fact which can be seen from the family of curves in Fig. 77, page 14, August 31st issue of RADIO WORLD.

Wrong. The screen grid current varies and is in opposite phase to the plate current. This also can be seen from the curves in Fig. 77.

Wrong. For low values of negative grid bias there is a large grid current, but this decreases rapidly as the negative bias is increased. If the tube is gaseous, there may be considerable grid current.

Right. That is the reason modern receivers are said to have linear detection. The linearity of the response is better, the more the signal up to a certain limit which is usually not met in practical cases.

A Question and Answer Department conducted by Radio World's Technical Staff. Only Questions sent in by University Club Members are answered. The reply is mailed to the member. Join now!

RADIO UNIVERSITY

Annual subscriptions are accepted at \$6 for 52 numbers, with the privilege of obtaining answers to radio questions for the period of the subscription, but not if any other premium is obtained with the subscription.

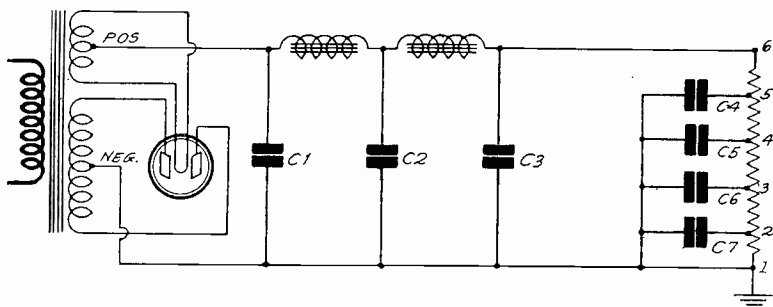


FIG. 782

DIAGRAM OF SIMPLE B SUPPLY.

Summary of HB Compact Advice

PLEASE summarize the mechanical and electrical precautions for the construction of the HB Compact, battery model, described in the August 24th and 31st issues.—H. R.

The precautions are: (1) Mount the coils on the front panel. If Screen Grid Coil Company's models are used no insulation is necessary between the shaft and the front panel, where the steel cabinet is used, but if National Company coils are used, insulation is necessary. If an insulation front panel is used, e.g., hard rubber or bakelite, no other insulation at all is necessary. (2) Put a flexible coupler on the shaft protruding at rear of each coil, and mount the tuning condenser so that its shaft points toward the front panel, but fits into the open side of the flexible coupler or link. (3) Insulate the rheostat if a metal panel is used, otherwise not. (4) If a metal subpanel is used with metal cabinet, use these as grounded A minus, and pick up the A minus lead for circuit connections at the most convenient points from the subpanel, otherwise (as where a baseboard is used), be sure to connect all leads calling for grounded A minus, to the ground binding post, which you start off with as A minus and ground. (5) If the aluminum subpanel is used with steel cabinet, and the socket hardware protrudes downward from bottom a little more than room allows, due to lugs pointing straight down, bend back the lugs with fingers or pliers, so they will clear the half-inch space allowed. The lugs are so constructed as to facilitate this bending. (6) Insulate two main condenser brackets and six auxiliary condenser brackets.

* * *

His Radiator a Good Aerial

IN my home I may use the outdoor aerial and radiator ground, or I may ignore the aerial, and connect the radiator lead to the antenna post of the receiver. In either instance I get about the same results in reception. I wonder if it would be all right, therefore, to use the radiator as aerial and dispense with any ground connection.—D. E. R.

Yes. In some locations this condition prevails, due to the ground lead being at a relatively high radio frequency potential. It is a common occurrence in apartment houses, particularly on the upper floors, and in taller buildings.

* * *

Lining Up a Gang Condenser

PLEASE explain an easy way to line up a gang condenser where there is an equalizing condenser across each tuning section of the main condenser.—H. F.

The ear test, or listening test, is one often used. A station is tuned in and the equalizers are adjusted until volume is greatest. Preferably a low wavelength station should be tuned in. The human ear does not appreciate changes in volume unless they exceed 25 per cent., but as wrong adjustment of the equalizers will decrease the volume much more than that, approximately correct adjustment will be possible by the listening test. A better way is to put a 0-25 or similar milliammeter in series with the detector plate lead, just as a precautionary determination of how much plate current is flowing, and then substitute a milliammeter of greater sensitivity, one that reads at a maximum deflection somewhat more than the reading provisionally obtained. This meter should not be more than 0.5 ma. Then the equalizer adjustments may be made on the basis of the detector plate current reading. If negative grid bias detection is used, the plate current will

increase as the signal increases, while by the leak-condenser method the plate current will decrease as the signal increases. Hence the adjustments are correct when the plate current reads highest by the negative grid bias method and lowest for the leak-condenser method.

* * *

AC Power for 3.3 Volt Tubes

IS it possible to power a receiver using 199 and 120 tubes, omitting batteries at present in service?—G. D.

Yes. Use a 4.5-volt A eliminator, and a 135-volt B eliminator that has suitable intermediate B voltage taps. Usually C batteries serve biasing purposes even in an electrified installation like this one. It is assumed you have AC house lighting supply. Be sure the supply is 110 volts, 50-60 cycles. If the A and B eliminators are designed for such primary voltage and frequency, as nearly all of them are.

* * *

Cure for Motorboating

A RESISTANCE-COUPLED audio amplifier in a receiver that I built motorboats, and therefore I am considering using some factory made radio frequency coils designed for the circuit, instead of home-made coils at present in use.—U. T.

The radio frequency coils have nothing to do with this condition of audio oscillation or audio regeneration called motorboating. Try reducing the values of the plate coupling resistors and grid leaks, particularly the grid leaks. Also use a large capacity, as afforded by Mershon condensers, to bypass the B plus voltages, both intermediate voltages and power tube voltage. These two remedies almost always cure the ill. The only common exception is where the choke coils used in the filter circuit of an AC type B supply have too high a resistance. If yours is an AC circuit, try using only one choke coil, and put a 2 mfd. paper dielectric condenser next to the rectifier, and a large capacity, 18 mfd. or more, even 36 mfd., at the other side of the choke coil.

* * *

Why I^2R Equals the Wattage

IHAVE studied Ohm's law, and understand it so far as it has come under my observation, but I do not understand why the current squared, times the resistance, equals the wattage.—G. H.

It is simply a statement in substituted terms of the definition that the current times the voltage equals the wattage. Thus, as $i \times e = \text{wattage}$, by Ohm's law you can substitute for the voltage e , the expression $i \times r$. Hence $i \times e$, representing wattage, becomes $i \times (i \times r)$ or $i^2 r = \text{wattage}$. It is customary to use small letters, i, r, e , etc., to designate variable voltages, while capital letters, I, R, E , are used if effective voltages are under discussion.

* * *

A Simple B Supply

PLEASE show a diagram of a simple B supply, using 280 tube, and give data on voltage divider.—F. J. R.

The diagram is published herewith as Fig. 782. A 5-volt winding heats the rectifier tube. The other winding is high voltage, about 350 to 375 volts across each half of the secondary, 700 to 750 across entirety. C1 is 2 mfd., C2 is 2 mfd. or higher capacity, C3 is as high as you can get. The output voltage divider points (1) to (6), may be a 10,000-ohm 50-watt resistor with four sliders, so you can get what voltage values you desire. The by-pass condensers are 2 mfd., except whatever one you use for bypassing the last audio biasing resistor. This capacity should be 4 mfd.

* * *

Use of Different Types of Cabinet

WHERE a metal cabinet is prescribed for a receiver, is it just as well to use a wooden cabinet, with a bakelite front panel, or must one use the steel cabinet?—H. G. S.

The type of cabinet is immaterial. You may use what you have or what you prefer. Where a metal cabinet is prescribed it is usually because of its compactness and physical suitability for the receiver, as well as for economical reasons, since the front panel is a part of the cabinet.

High or Low Ratio for RF?

WHAT ratio do you propose for coupling a tuned primary screen grid circuit to a detector, where the secondary is untuned?—K. H. D.

The ratio must be determined on the basis of the circuit design and this ratio has much to do with the performance. If you want more volume of course use a higher ratio than otherwise, say 1-to-1½ tuned primary to untuned secondary, with close coupling. For greater selectivity a stepdown ratio may be used or looser coupling. The capabilities of the screen grid tube are best proved by a tuned primary, with step-up ratio to the next stage, and the circuit design should be good enough to enable this to be done, even where few tubes are used. In multi-tube circuits, of course, the overall gain is so great that individual stage gain need not be so high. See the HB Compact for battery operation, described in this issue, as an example of a high-gain circuit of the type that interests you.

* * *

Interested in HB Compact

MY attention was attracted to the HB compact as a four tube receiver design for battery operation that promises to excel. I therefore ask you kindly to inform me where I can get a template of the layout of parts or, preferably, a blueprint. I should like to build this tempting receiver at once.—E. W. S.

See the pictorial wiring diagram, published full size, on pages 12 and 13 of last week's issue. Also read the second instalment of the constructional article, published on pages 12 and 13 of that issue. You will not need a blueprint, of course, as the pictorial diagram is, so to speak, a "blueprint printed in black."

* * *

Coil Efficiency Discussed

PLEASE clear up some points on coils for radio frequency. Is it true that coils with a small field, such as doughnut or toroid coils, are more efficient? What is the most suitable diameter for any coil? Is there any advantage in space winding?—H. S. A.

The subject of coil design can not always be dissociated from the particular circuit in which the coils are to be used, as sometimes a less efficient coil solves problems that arise only if a more efficient coil were used. It is certainly untrue that coils with smaller external fields, like toroids, are more efficient. Indeed, it is exactly true to state that the measure of a coil's efficiency is the extent and strength of its field. The only positive asset a coil has is its field, hence the field is its figure of merit, much more so, by the way, than the mutual conductance is a tube's figure of merit. Toroids require much more wire to attain a given inductance than do solenoids, hence toroids have a higher radio frequency resistance, and this effect is sometimes capitalized to produce stability. But it is resistance directly in the tuned circuit, so has little to commend it, grid suppressors with more efficient coils being preferable. In general, there is no known type of coil superior to the solenoid. What the diameter should be depends on the number of turns of a given type of wire and insulation, since the axial coil length should be about one-and-a-half times the diameter. But variations from this formula are entirely permissible even small-diameter, long length coils being acceptable, especially in modern circuits where the sensitivity of cascaded RF stages is very high, and the selectivity adequate, due to the number of stages. Space winding reduces the distributed capacity, hence is valuable where circuit constants and design may make it otherwise difficult to cover a given band of frequencies, as the broadcast band, using a small capacity condenser (.00025 mfd.) Another advantage is that space winding, being usually done in grooved forms, makes possible greater uniformity of inductance in quantity production.

* * *

Listens In to Television

ONCE in a while on my short-wave set I pick up television signals. These I recognize by their peculiar grinding sounds, a grind produced as if from some whirling motor. Please let me know what it is I hear.—F. S.

You hear the sounds to which the vision has been converted, plus the sound of the motor driving the scanning disc. This motor sound is extraneous and is a form of interference, although it need not necessarily have any bad effect upon the picture. When a moving object is televised, the image is scanned, and the resultant intermittent and graduated light is impressed on a photo-electric cell. This has the property of producing changes in current values equivalent to changes in light values. These changing current values are amplified and many of them are audible. The changes are impressed on a radio frequency wave, this constituting the act of modulation, and the modulated wave is transmitted in the usual way. At the receiving end a set is tuned to the signal frequency, and the transmission process is reversed, so the image can be seen. That is, the radio wave is tuned in, the carrier eliminated, by detection, the audio component amplified in the AF channel, the

output fed into a kino lamp which produces values of light corresponding to the values of current, and these light values a scanning disc picks up. Concentration of this controlled light, through the disc holes to a small screen, completes visibility.

* * *

Voltage Divider for B Supply

I AM in doubt as to what type and wattage of voltage divider to use in my B supply.—G. H.

The problems of output voltages are easily solved by using a resistor with adjustable taps. Then with the aid of a high resistance voltmeter, 1,000 ohms per volt, you can establish the desired voltages by moving the taps and finally tightening the moving part. For ordinary purposes, using a B supply for 245 tube, single-sided output, a 10,000 ohm resistor would be satisfactory, rated at 50 watts. If push-pull is used either the wattage of the entire resistor should be raised, say 50 per cent., or the wattage of the biasing section, through which flows the current of the last audio push-pull tubes, should be 75 watts. It is this section that carries the extra current due to push-pull. The rating, of course, is higher than the actual wattage, but this is as it should be. The resistance of the total voltage divider determines the bleeder current at specified voltage. Hence at 300 volts, with 10,000 ohms total, the bleeder is 30 ma. It is well to have a substantial bleeder like this, to stabilize the output voltages, making them stand up better as more plate current is drawn, due to the extra number or different type of tubes and couplings used.

* * *

Reason for Selectivity Difference

THE short-wave receiver I built, to cover the broadcast band as well. I find enough selectivity on the short wavelengths but not enough selectivity on the higher wavelengths (broadcast spectrum). I am satisfied with the receiver, as it was built primarily for short-wave reception, and the broadcast wave feature is purely incidental, and welcome as that much extra service. But I would like to know the reason for this phenomenon of differentiated selectivity. I use plug-in coils. Two coils for the broadcast band require throwing a switch to increase the tuning capacity by parallel condenser connection.—T. Y.

The reduced selectivity on the broadcast band is due to the reduced ratio of inductance to capacity. For best results the ratio of inductance to capacity should be high. This high ratio is not quite feasible in such a receiver as yours, hence the results on the broadcast band must be accepted as they are, merely fair, while reliance for best work is placed on the receiver when it is functioning on the short waves.

Join

Radio World's

UNIVERSITY CLUB

And Get Free Question and Answer Service for the Coming 52 Weeks. This Service for University Subscribers Only

Subscribe for RADIO WORLD for one year (52 numbers). Use the coupon below. Your name will be entered on our subscription and University Club lists by special number. When sending questions, put this number on the outside of the forwarding envelope (not the enclosed return envelope) and also put it at the head of your queries. If already a subscriber, send \$6 for renewal from close of present subscription and your name will be entered in Radio University.

NO OTHER PREMIUM GIVEN WITH THIS OFFER

[In sending in your queries to the University Department please paragraph and number them. Write on one side of sheet only. Always give your University Club Number.]

RADIO WORLD, 145 West 45th Street, New York City. Enclosed find \$6.00 for RADIO WORLD for one year (52 nos.) and also enter my name on the list of members of RADIO WORLD'S UNIVERSITY CLUB, which gives me free answers to radio queries for 52 ensuing weeks, and send me my number indicating membership.

Name

Street

City and State

If renewing subscription, put cross here.

REACTIVATION OF T

Flashing, with No Plate Voltage, Restore

By Gust

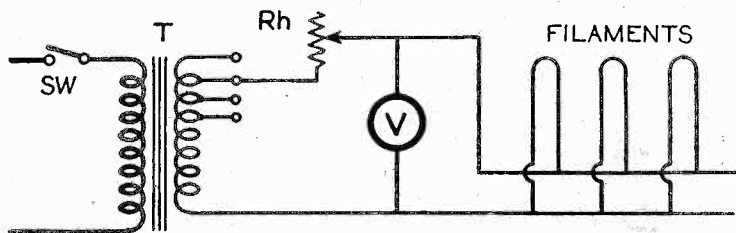


FIG. 1
A CIRCUIT FOR FLASHING TUBE FILAMENTS DURING REACTIVATION.

Although new vacuum tubes are comparatively inexpensive, there is a great deal of interest in reactivation of "paralyzed" tubes. In most instances a "paralyzed" tube is simply a dead tube, and any attempt to revive it is usually wasted time and effort. However, there are cases in which the tube is only suffering from suspended activity, and in such cases the reactivation process may restore the tube to another period of usefulness. Only the thoriated tungsten filament tubes can be reactivated under any conditions.

The thoriated tungsten filament is made of a mixture of pure tungsten and a small quantity of thorium oxide. The heating of the filament reduces the thorium oxide near the surface of the conductor to pure thorium, the thickness of the layer of thorium being only about one molecule. The presence of the thorium has the property of releasing electrons more readily than tungsten, and it is for this reason that filaments of this type are operated at a much lower temperature than filaments of pure tungsten.

The metallic thorium on the surface of the tungsten continually evaporates as the tube operates. The thorium that is thus liberated is replaced by the reduction of the supply of thorium oxide in the interior of the filament, that is, by the conversion of the oxide to the pure metal. Normally this process is gradual. When all the oxide has been reduced and all the thorium evaporated, the tube is dead beyond the possibility of reactivation.

A Paralytic Stroke

Sometimes a tube is subjected to abuse, for example, the application of an excessive plate voltage. This may cause the surface layer of thorium to be evaporated without any replacement from within. The tube is then apparently dead or paralyzed. If the "paralyzing" shock was not too great, it is possible to revive the tube in this case, for there is still a quantity of thorium oxide in the filament which can be reduced to metallic form on the surface of the tungsten provided the proper process be applied.

The following tubes have thoriated filaments: UX-199, UX-120, UX-200A, UX-201A, UX-222, UX-240, UX-171 and UX-210, and the corresponding tubes of the CX type. In addition to these amplifier tubes, the two rectifiers 213 and 216-B have thoriated filaments.

The reactivation process consists of two parts, the flashing and the burning. Both of these are required in reactivating a tube which has been abused greatly; only the second need be applied if the tube has been overloaded but slightly.

The purpose of the flashing is to clean the surface of the tungsten filament, to remove all impurities on the surface. This is done by operating the filament for a period of from 10 to 20 seconds at a high temperature so that any impurities, including any thorium, is actually boiled off. In effect this completely paralyzes the filament, but leaves it in a condition for the formation of a new and clean thorium layer from the thorium oxide that is still left in the interior. The filament terminal voltage for flashing depends on the normal terminal voltage of the tube in question, and is approximately three times as great. The actual values for the various tubes are given in the table herewith.

The Burning Process

The burning process consists of operating the filament for a certain period at a terminal voltage about 20 per cent. higher than the normal operating voltage. The exact burning voltage for each tube is also given in the table. The length of the

Type of tube	Filament Emission test
199	3.3
120	3.3
222	3.3
201A	5.0
201B	5.0
200A	5.0
240	5.0
171	5.0
210	6.0
213	4.0
216B	5.0

burning period depends on the tube and on its condition. It is first burned for a period of 30 minutes. Then a test is made of its filament emission. If the emission current is less than the minimum current given in the attached table for the tube in question, the filament is burned for another period of 30 minutes and another emission test is made. It may require a total of 1.5 hours for complete reactivation, or the first period of 30 minutes may be sufficient. If no improvement in the emission current is shown after a few thirty-minute periods of burning, the tube can be considered dead.

If the burning was done without first flashing the tube and no improvement is shown with the continued burning, the filament should be flashed before abandoning hope of reactivation.

Emission Test

During the emission test the tube is operated as a rectifier, the grid and the plate being tied together. The rectifier 213 has two filaments which may be in different conditions. Therefore

Right on

[Herewith are ten questions. They are propounded from articles published in last week's issue, August 31st. If you read that issue carefully, then you should be able to answer all ten questions accurately. Read this week's issue from cover to cover and you will know the answers to next week's questions even before the questions are put.—Editor.]

* * *

(1).—When a screen grid tube is operated in a resistance coupled circuit, the applied plate voltage should be increased to offset the voltage drop in the coupling resistor and the screen voltage should be decreased.

(2).—An electrolytic condenser of large capacity should be connected across the output of a rectifier next to the tube for best results.

(3).—A screen grid tube in an amplifier is of no advantage because only a small fraction of the amplification factor can be utilized.

(4).—If a high mu tube has a low internal plate resistance it is feasible to couple it to the next tube by means of a transformer.

(5).—If a family of plate current, plate voltage curves is available for a power tube it is possible to calculate the amount of second harmonic distortion which will result when a given signal is impressed on the tube.

(6).—The grid bias on a tube can be determined by measuring the plate current in the tube with a known voltage on the plate.

(7).—In a screen grid tube the plate current flows in the same direction for all plate voltages just as in a three-element tube.

(8).—In a screen grid tube the screen current remains constant and is always less than the plate current.

(9).—Grid current never flows in a tube when the grid is negative with respect to the filament of the cathode.

(10).—When a vacuum tube is used as a grid bias detector for large signals the detected signal is substantially proportional to the radio frequency signal and not proportional to the square of the carrier amplitude.

THORIATED FILAMENTS

Lost Emission—Over-Heating Also Used

Quirk

Plate voltage	Minimum emission current (ma)	Filament Resistance (Ohms)
Flashing 12.0	50	50
12.0	50	25
12.0	Test as amplifier	25
16.0	50	20
16.0	50	20
16.0	50	20
16.0	50	20
16.0	50	20
16.0	100	10
16.0	100	50 (per filament)
16.0	125	6

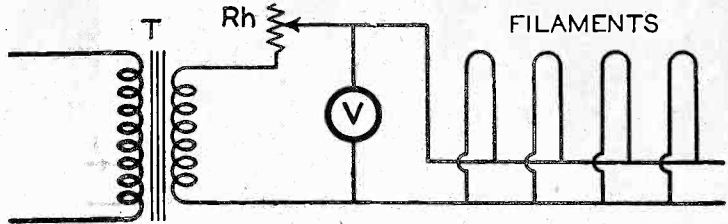


FIG. 2
AN ARRANGEMENT OF CIRCUIT FOR BURNING THE FILAMENT DURING REACTIVATION.

for the burning operation. Essentially the two circuits are the same, differing only in the voltage indicated by the voltmeter across the filament line. Fig. 3 shows the emission test circuit, V being the voltmeter which measures the emission test filament voltage and *ma* the milliammeter which indicates the emission.

To make the process of reactivation clear, let us take a UX-120 tube as an example. The test circuit is arranged as in Fig. 1, with a 25-ohm resistor in place of the filament. Turn on the power and adjust the taps on the transformer and the setting of the rheostat until the reading of the AC voltmeter is 12 volts, the flashing voltage given in the table. Then open the switch, remove the 25-ohm resistor and put the filament of the 120 tube in its place. Get a watch ready for timing the flash. Turn on the power for 10 or 20 seconds. A longer flash will probably vaporize the filament and end the operation.

If the filament survives the flashing operation readjust the circuit so that the voltage indicated by the AC voltmeter is 4 volts, the burning voltage given in the table for the tube in question. Leave it burning at 4 volts for 30 minutes.

At the expiration of this burning period, put the tube in circuit shown in Fig. 3 and measure the emission current. The filament voltage now should be 3.3 volts and the plate voltage should be 50 volts. If now the emission current, that is, the combined grid and plate current, is more than 15 milliamperes, the tube may be considered reactivated. If it is less than this, return the tube to the burning circuit, Fig. 2, for another 30-minute period. Test again on circuit in Fig. 3. Continue until the total burning period is 1.5 hours, or until the emission current is greater than 15 milliamperes.

Burn-out Danger

As some of the filaments may burn out completely during the flashing process, it may be well to attempt to restore a tube first to the burning operation alone. If it cannot be restored by this method alone, it has been greatly damaged and very little is lost if the filament does go during a flashing operation.

The last column in the table gives the hot resistance of the filament of the tube. This is included in order that a resistor of the indicated value may be connected across the filament line while the flashing volt is adjusted.

The taking of an emission test with the circuit in Fig. 3 should be done quickly, for nothing is gained by letting current flow for a considerable period. It only shortens the life of the tube, and may defeat the purpose of the reactivation. In order to shorten the time that current flows, the battery E should be left disconnected until everything is ready for a reading. Then contact should be made just long enough to observe the reading on the meter MA.

Whenever it becomes necessary to buy a new tube because an old one cannot be reactivated, it is best to get one which cannot be reactivated at all. It has a longer life. Of course, there are a few tubes which cannot be had except in the thoriated tungsten filament. When a new tube of this type is purchased it is well to remember that it can readily be "paralyzed" by abuse, that is, by the application of too high plate voltages and too low grid voltages.

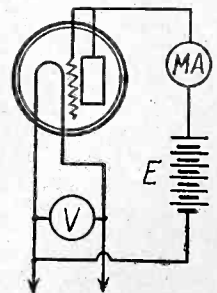


FIG. 3
WHEN TAKING AN EMISSION TEST ON THE TUBE THE PLATE AND THE GRID SHOULD BE CONNECTED TOGETHER.

each of the filaments should be reactivated and tested independently of the other. That is, the tube is tested as if it were two different tubes.

The source of the flashing and burning voltages may be either a battery or a transformer. For flashing a B battery of the required voltage might well be used since the duration of the flash is very short, and hence very few milliampere-hours will be taken from the battery. For burning it is necessary to use storage batteries or a suitable transformer, except that the small dry cell tubes may be burned with dry cells.

Whenever it is possible to use a transformer for flashing and burning this is recommended. Inexpensive toy transformers having the required voltages are available and can be purchased in almost any electrical store. If the voltage taps are not exactly those required for a given operation and a given tube, a rheostat can be inserted in series with the filament or filaments for adjusting the voltage to the required value. Fig. 1 shows the circuit for the flashing operation, using a transformer as the voltage source and Fig. 2 shows the connection

Wrong?

- (1).—Right. This is correct for a screen grid tube, for this tube will not function properly if the effective voltage on the plate is less than the screen grid voltage. In a three-element tube it is not necessary to increase the battery voltage, unless the amplitude of the signal demands it.
- (2).—Wrong. If the condenser next to the rectifier tube is large the tube is subjected to heavy strains. Also, the filtering may be much poorer than if a smaller condenser is used.
- (3).—Wrong. The main object of using a tube is not to get the maximum amplification that tube is capable of but to get a high amplification from the tube and the circuit. The screen grid tube will yield a higher amplification than any other tube, even if only a small fraction of its amplification constant is utilized.
- (4).—Right. The μ of the tube has nothing to do with the type of coupling that follows the tube. If the internal impedance of the tube is so low that it is small compared with an audio transformer primary impedance, it is all right to use a transformer.
- (5).—Right. The output power can be calculated from the curves by assuming the curves are straight lines. The second harmonic distortion can be calculated by taking into account the fact that the curves are not straight.
- (6).—Right. The tube can be used as a vacuum tube voltmeter.
- (7).—Wrong. For certain voltages on the plate the plate current is negative, a fact which can be seen from the family of curves in Fig. 77, page 14, August 31st issue of RADIO WORLD.
- (8).—Wrong. The screen grid current varies and is in opposite phase to the plate current. This also can be seen from the curves referred to.
- (9).—Wrong. For low values of negative grid bias there is a small grid current, but this decreases rapidly as the negative bias increases. If the tube is gaseous, there may be considerable grid current.
- (10).—Right. That is the reason modern receivers are said to have linear detection. The linearity of the response is better, the larger the signal up to a certain limit which is usually not met in practical cases.

REACTIVATION OF T

Flashing, with No Plate Voltage, Restore

By Gush

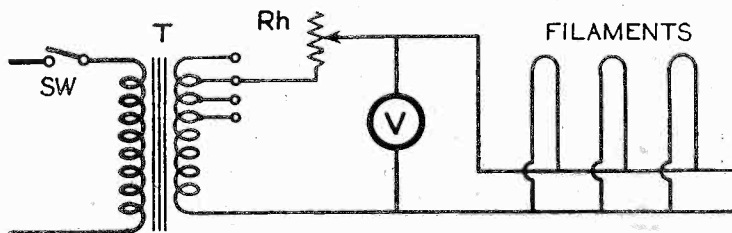


FIG. 1

A CIRCUIT FOR FLASHING TUBE FILAMENTS DURING REACTIVATION.

Although new vacuum tubes are comparatively inexpensive, there is a great deal of interest in reactivation of "paralyzed" tubes. In most instances a "paralyzed" tube is simply a dead tube, and any attempt to revive it is usually wasted time and effort. However, there are cases in which the tube is only suffering from suspended activity, and in such cases the reactivation process may restore the tube to another period of usefulness. Only the thoriated tungsten filament tubes can be reactivated under any conditions.

The thoriated tungsten filament is made of a mixture of pure tungsten and a small quantity of thorium oxide. The heating of the filament reduces the thorium oxide near the surface of the conductor to pure thorium, the thickness of the layer of thorium being only about one molecule. The presence of the thorium has the property of releasing electrons more readily than tungsten, and it is for this reason that filaments of this type are operated at a much lower temperature than filaments of pure tungsten.

The metallic thorium on the surface of the tungsten continually evaporates as the tube operates. The thorium that is thus liberated is replaced by the reduction of the supply of thorium oxide in the interior of the filament, that is, by the conversion of the oxide to the pure metal. Normally this process is gradual. When all the oxide has been reduced and all the thorium evaporated, the tube is dead beyond the possibility of reactivation.

A Paralytic Stroke

Sometimes a tube is subjected to abuse, for example, the application of an excessive plate voltage. This may cause the surface layer of thorium to be evaporated without any replacement from within. The tube is then apparently dead or paralyzed. If the "paralyzing" shock was not too great, it is possible to revive the tube in this case, for there is still a quantity of thorium oxide in the filament which can be reduced to metallic form on the surface of the tungsten provided the proper process be applied.

The following tubes have thoriated filaments: UX-199, UX-120, UX-200A, UX-201A, UX-222, UX-240, UX-171 and UX-210, and the corresponding tubes of the CX type. In addition to these amplifier tubes, the two rectifiers 213 and 216-B have thoriated filaments.

The reactivation process consists of two parts, the flashing and the burning. Both of these are required in reactivating a tube which has been abused greatly; only the second need be applied if the tube has been overloaded but slightly.

The purpose of the flashing is to clean the surface of the tungsten filament, to remove all impurities on the surface. This is done by operating the filament for a period of from 10 to 20 seconds at a high temperature so that any impurities, including any thorium, is actually boiled off. In effect this completely paralyzes the filament, but leaves it in a condition for the formation of a new and clean thorium layer from the thorium oxide that is still left in the interior. The filament terminal voltage for flashing depends on the normal terminal voltage of the tube in question, and is approximately three times as great. The actual values for the various tubes are given in the table herewith.

The Burning Process

The burning process consists of operating the filament for a certain period at a terminal voltage about 20 per cent. higher than the normal operating voltage. The exact burning voltage for each tube is also given in the table. The length of the

Type of tube	Emission test	Filament B
199	3.3	
120	3.3	
222	3.3	
201A	5.0	
201B	5.0	
200A	5.0	
240	5.0	
171	5.0	
210	6.0	
213	4.0	
216B	6.0	

burning period depends on the tube and on its condition. It is first burned for a period of 30 minutes. Then a test is made of its filament emission. If the emission current is less than the minimum current given in the attached table for the tube in question, the filament is burned for another period of 30 minutes and another emission test is made. It may require a total of 1.5 hours for complete reactivation, or the first period of 30 minutes may be sufficient. If no improvement in the emission current is shown after a few thirty-minute periods of burning, the tube can be considered dead.

If the burning was done without first flashing the tube and no improvement is shown with the continued burning, the filament should be flashed before abandoning hope of reactivation.

Emission Test

During the emission test the tube is operated as a rectifier, the grid and the plate being tied together. The rectifier 213 has two filaments which may be in different conditions. Therefore

Right on

[Herewith are ten questions. They are propounded from articles published in last week's issue, August 31st. If you read that issue carefully, then you should be able to answer all ten questions accurately. Read this week's issue from cover to cover and you will know the answers to next week's questions even before the questions are put.—Editor.]

* * *

(1).—When a screen grid tube is operated in a resistance coupled circuit, the applied plate voltage should be increased to offset the voltage drop in the coupling resistor and the screen voltage should be decreased.

(2).—An electrolytic condenser of large capacity should be connected across the output of a rectifier next to the tube for best results.

(3).—A screen grid tube in an amplifier is of no advantage because only a small fraction of the amplification factor can be utilized.

(4).—If a high mu tube has a low internal plate resistance it is feasible to couple it to the next tube by means of a transformer.

(5).—If a family of plate current, plate voltage curves is available for a power tube it is possible to calculate the amount of second harmonic distortion which will result when a given signal is impressed on the tube.

(6).—The grid bias on a tube can be determined by measuring the plate current in the tube with a known voltage on the plate.

(7).—In a screen grid tube the plate current flows in the same direction for all plate voltages just as in a three-element tube.

(8).—In a screen grid tube the screen current remains constant and is always less than the plate current.

(9).—Grid current never flows in a tube when the grid is negative with respect to the filament of the cathode.

(10).—When a vacuum tube is used as a grid bias detector for large signals the detected signal is substantially proportional to the radio frequency signal and not proportional to the square of the carrier amplitude.

THORIATED FILAMENTS

Lost Emission—Over-Heating Also Used

Quirk

Flashing	Plate voltage emission test	Minimum emission current (ma)	Filament Resistance (Ohms)
12.0	50	6	50
12.0	50	15	25
12.0	Test as amplifier		25
16.0	50	25	20
16.0	50	25	20
16.0	50	12	20
16.0	50	25	20
16.0	50	50	20
16.0	100	100	10
16.0	100	50 (per filament)	2.5
16.0	125	100	6

each of the filaments should be reactivated and tested independently of the other. That is, the tube is tested as if it were two different tubes.

The source of the flashing and burning voltages may be either a battery or a transformer. For flashing a B battery of the required voltage might well be used since the duration of the flash is very short, and hence very few milliampere-hours will be taken from the battery. For burning it is necessary to use storage batteries or a suitable transformer, except that the small dry cell tubes may be burned with dry cells.

Whenever it is possible to use a transformer for flashing and burning this is recommended. Inexpensive toy transformers having the required voltages are available and can be purchased in almost any electrical store. If the voltage taps are not exactly those required for a given operation and a given tube, a rheostat can be inserted in series with the filament or filaments for adjusting the voltage to the required value. Fig. 1 shows the circuit for the flashing operation, using a transformer as the voltage source and Fig. 2 shows the connection

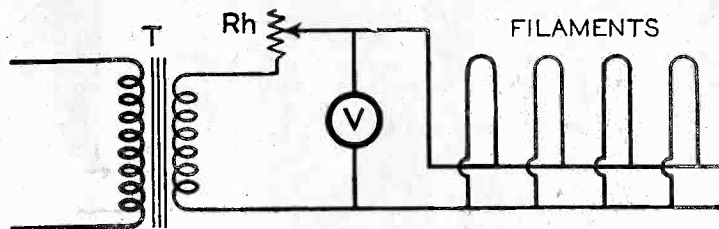


FIG. 2
AN ARRANGEMENT OF CIRCUIT FOR BURNING THE FILAMENT DURING REACTIVATION.

for the burning operation. Essentially the two circuits are the same, differing only in the voltage indicated by the voltmeter across the filament line. Fig. 3 shows the emission test circuit, V being the voltmeter which measures the emission test filament voltage and ma the milliammeter which indicates the emission.

To make the process of reactivation clear, let us take a UX-120 tube as an example. The test circuit is arranged as in Fig. 1, with a 25-ohm resistor in place of the filament. Turn on the power and adjust the taps on the transformer and the setting of the rheostat until the reading of the AC voltmeter is 12 volts, the flashing voltage given in the table. Then open the switch, remove the 25-ohm resistor and put the filament of the 120 tube in its place. Get a watch ready for timing the flash. Turn on the power for 10 or 20 seconds. A longer flash will probably vaporize the filament and end the operation.

If the filament survives the flashing operation readjust the circuit so that the voltage indicated by the AC voltmeter is 4 volts, the burning voltage given in the table for the tube in question. Leave it burning at 4 volts for 30 minutes.

At the expiration of this burning period, put the tube in circuit shown in Fig. 3 and measure the emission current. The filament voltage now should be 3.3 volts and the plate voltage should be 50 volts. If now the emission current, that is, the combined grid and plate current, is more than 15 milliamperes, the tube may be considered reactivated. If it is less than this, return the tube to the burning circuit, Fig. 2, for another 30-minute period. Test again on circuit in Fig. 3. Continue until the total burning period is 1.5 hours, or until the emission current is greater than 15 milliamperes.

Burn-out Danger

As some of the filaments may burn out completely during the flashing process, it may be well to attempt to restore a tube first to the burning operation alone. If it cannot be restored by this method alone, it has been greatly damaged and very little is lost if the filament does go during a flashing operation.

The last column in the table gives the hot resistance of the filament of the tube. This is included in order that a resistor of the indicated value may be connected across the filament line while the flashing volt is adjusted.

The taking of an emission test with the circuit in Fig. 3 should be done quickly, for nothing is gained by letting current flow for a considerable period. It only shortens the life of the tube, and may defeat the purpose of the reactivation. In order to shorten the time that current flows, the battery E should be left disconnected until everything is ready for a reading. Then contact should be made just long enough to observe the reading on the meter MA.

Whenever it becomes necessary to buy a new tube because an old one cannot be reactivated, it is best to get one which cannot be reactivated at all. It has a longer life. Of course, there are a few tubes which cannot be had except in the thoriated tungsten filament. When a new tube of this type is purchased it is well to remember that it can readily be "paralyzed" by abuse, that is, by the application of too high plate voltages and too low grid voltages.

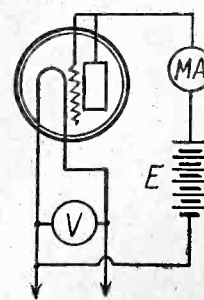


FIG. 3
WHEN TAKING AN EMISSION TEST ON THE TUBE THE PLATE AND THE GRID SHOULD BE CONNECTED TOGETHER.

Wrong?

- Right. This is correct for a screen grid tube, for this tube will not function properly if the effective voltage on the plate is less than the screen grid voltage. In a three-element tube it is not necessary to increase the battery voltage, unless the amplitude of the signal demands it.
- Wrong. If the condenser next to the rectifier tube is large the tube is subjected to heavy strains. Also, the filtering may be much poorer than if a smaller condenser is used.
- Wrong. The main object of using a tube is not to get the maximum amplification that tube is capable of but to get a high amplification from the tube and the circuit. The screen grid tube will yield a higher amplification than any other tube, even if only a small fraction of its amplification constant is utilized.
- Right. The mu of the tube has nothing to do with the type of coupling that follows the tube. If the internal impedance of the tube is so low that it is small compared with an audio transformer primary impedance, it is all right to use a transformer.
- Right. The output power can be calculated from the curves by assuming the curves are straight lines. The second harmonic distortion can be calculated by taking into account the fact that the curves are not straight.
- Right. The tube can be used as a vacuum tube voltmeter.
- Wrong. For certain voltages on the plate the plate current is negative, a fact which can be seen from the family of curves in Fig. 77, page 14, August 31st issue of RADIO WORLD.
- Wrong. The screen grid current varies and is in opposite phase to the plate current. This also can be seen from the curves referred to.
- Wrong. For low values of negative grid bias there is a small grid current, but this decreases rapidly as the negative bias increases. If the tube is gaseous, there may be considerable grid current.
- Right. That is the reason modern receivers are said to have linear detection. The linearity of the response is better, the larger the signal up to a certain limit which is usually not met in practical cases.

A Question and Answer Department conducted by Radio World's Technical Staff. Only Questions sent in by University Club Members are answered. The reply is mailed to the member. Join now!

RADIO UNIVERSITY

Annual subscriptions are accepted at \$6 for 52 numbers, with the privilege of obtaining answers to radio questions for the period of the subscription, but not if any other premium is obtained with the subscription.

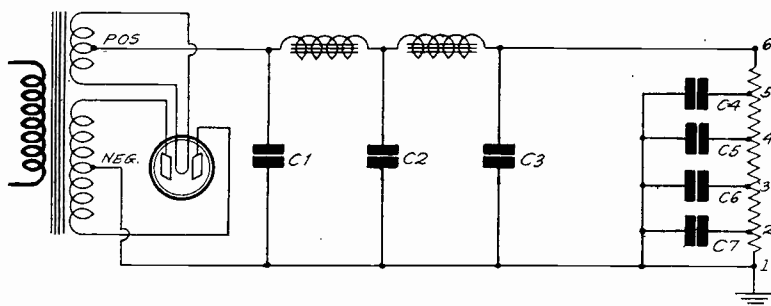


FIG. 782
DIAGRAM OF SIMPLE B SUPPLY.

Summary of HB Compact Advice

PLEASE summarize the mechanical and electrical precautions for the construction of the HB Compact, battery model, described in the August 24th and 31st issues.—H. R.

The precautions are: (1) Mount the coils on the front panel. If Screen Grid Coil Company's models are used no insulation is necessary between the shaft and the front panel, where the steel cabinet is used, but if National Company coils are used, insulation is necessary. If an insulation front panel is used, e.g., hard rubber or bakelite, no other insulation at all is necessary. (2) Put a flexible coupler on the shaft protruding at rear of each coil, and mount the tuning condenser so that its shaft points toward the front panel, but fits into the open side of the flexible coupler or link. (3) Insulate the rheostat if a metal panel is used, otherwise not. (4) If a metal subpanel is used with metal cabinet, use these as grounded A minus, and pick up the A minus lead for circuit connections at the most convenient points from the subpanel, otherwise (as where a baseboard is used), be sure to connect all leads calling for grounded A minus, to the ground binding post, which you start off with as A minus and ground. (5) If the aluminum subpanel is used with steel cabinet, and the socket hardware protrudes downward from bottom a little more than room allows, due to lugs pointing straight down, *bend back the lugs with fingers or pliers*, so they will clear the half-inch space allowed. The lugs are so constructed as to facilitate this bending. (6) Insulate two main condenser brackets and six auxiliary condenser brackets.

His Radiator a Good Aerial

IN my home I may use the outdoor aerial and radiator ground, or I may ignore the aerial, and connect the radiator lead to the antenna post of the receiver. In either instance I get about the same results in reception. I wonder if it would be all right; therefore, to use the radiator as aerial and dispense with any ground connection.—D. E. R.

Yes. In some locations this condition prevails, due to the ground lead being at a relatively high radio frequency potential. It is a common occurrence in apartment houses, particularly on the upper floors, and in taller buildings.

Lining Up a Gang Condenser

PLEASE explain an easy way to line up a gang condenser where there is an equalizing condenser across each tuning section of the main condenser.—H. F.

The ear test, or listening test, is one often used. A station is tuned in and the equalizers are adjusted until volume is greatest. Preferably a low wavelength station should be tuned in. The human ear does not appreciate changes in volume unless they exceed 25 per cent., but as wrong adjustment of the equalizers will decrease the volume much more than that, approximately correct adjustment will be possible by the listening test. A better way is to put a 0-25 or similar milliammeter in series with the detector plate lead, just as a precautionary determination of how much plate current is flowing, and then substitute a milliammeter of greater sensitivity, one that reads at a maximum deflection somewhat more than the reading provisionally obtained. This meter should not be more than 0-5 ma. Then the equalizer adjustments may be made on the basis of the detector plate current reading. If negative grid bias detection is used, the plate current will

increase as the signal increases, while by the leak-condenser method the plate current will decrease as the signal increases. Hence the adjustments are correct when the plate current reads highest by the negative grid bias method and lowest for the leak-condenser method.

* * *

AC Power for 3.3 Volt Tubes

IS it possible to power a receiver using 199 and 120 tubes, omitting batteries at present in service?—G. D.

Yes. Use a 4.5-volt A eliminator, and a 135-volt B eliminator that has suitable intermediate B voltage taps. Usually C batteries serve biasing purposes even in an electrified installation like this one. It is assumed you have AC house lighting supply. Be sure the supply is 110 volts, 50-60 cycles, if the A and B eliminators are designed for such primary voltage and frequency, as nearly all of them are.

* * *

Cure for Motorboating

A RESISTANCE-COUPLED audio amplifier in a receiver that I built motorboats, and therefore I am considering using some factory made radio frequency coils designed for the circuit, instead of home-made coils at present in use.—U. T.

The radio frequency coils have nothing to do with this condition of audio oscillation or audio regeneration called motorboating. Try reducing the values of the plate coupling resistors and grid leaks, particularly the grid leaks. Also use a large capacity, as afforded by Mershon condensers, to bypass the B plus voltages, both intermediate voltages and power tube voltage. These two remedies almost always cure the ill. The only common exception is where the choke coils used in the filter circuit of an AC type B supply have too high a resistance. If yours is an AC circuit, try using only one choke coil, and put a 2 mfd. paper dielectric condenser next to the rectifier, and a large capacity, 18 mfd. or more, even 36 mfd., at the other side of the choke coil.

* * *

Why I^2R Equals the Wattage

IHAVE studied Ohm's law, and understand it so far as it has come under my observation, but I do not understand why the current squared, times the resistance, equals the wattage.—G. H.

It is simply a statement in substituted terms of the definition that the current times the voltage equals the wattage. Thus, as $i \times e = \text{wattage}$, by Ohm's law you can substitute for the voltage e , the expression $i \times r$. Hence $i \times e$, representing wattage, becomes $i \times (i \times r)$ or $i^2 r = \text{wattage}$. It is customary to use small letters, i, r, e , etc., to designate variable voltages, while capital letters, I, R, E , are used if effective voltages are under discussion.

* * *

A Simple B Supply

PLEASE show a diagram of a simple B supply, using 280 tube, and give data on voltage divider.—F. J. R.

The diagram is published herewith as Fig. 782. A 5-volt winding heats the rectifier tube. The other winding is high voltage, about 350 to 375 volts across each half of the secondary, 700 to 750 across entirety. C1 is 2 mfd., C2 is 2 mfd. or higher capacity, C3 is as high as you can get. The output voltage divider points (1) to (6), may be a 10,000-ohm 50-watt resistor with four sliders, so you can get what voltage values you desire. The by-pass condensers are 2 mfd., except whatever one you use for bypassing the last audio biasing resistor. This capacity should be 4 mfd.

* * *

Use of Different Types of Cabinet

WHERE a metal cabinet is prescribed for a receiver, is it just as well to use a wooden cabinet, with a bakelite front panel, or must one use the steel cabinet?—H. G. S.

The type of cabinet is immaterial. You may use what you have or what you prefer. Where a metal cabinet is prescribed it is usually because of its compactness and physical suitability for the receiver, as well as for economical reasons, since the front panel is a part of the cabinet.

High or Low Ratio for RF?

WHAT ratio do you propose for coupling a tuned primary screen grid circuit to a detector, where the secondary is untuned?—K. H. D.

The ratio must be determined on the basis of the circuit design and this ratio has much to do with the performance. If you want more volume of course use a higher ratio than otherwise, say 1-to-1½ tuned primary to untuned secondary, with close coupling. For greater selectivity a stepdown ratio may be used or looser coupling. The capabilities of the screen grid tube are best proved by a tuned primary, with step-up ratio to the next stage, and the circuit design should be good enough to enable this to be done, even where few tubes are used. In multi-tube circuits, of course, the overall gain is so great that individual stage gain need not be so high. See the HB Compact for battery operation, described in this issue, as an example of a high-gain circuit of the type that interests you.

* * *

Interested in HB Compact

MY attention was attracted to the HB compact as a four tube receiver design for battery operation that promises to excel. I therefore ask you kindly to inform me where I can get a template of the layout of parts or, preferably, a blueprint. I should like to build this tempting receiver at once.—E. W. S.

See the pictorial wiring diagram, published full size, on pages 12 and 13 of last week's issue. Also read the second instalment of the constructional article, published on pages 12 and 13 of that issue. You will not need a blueprint, of course, as the pictorial diagram is, so to speak, a "blueprint printed in black."

* * *

Coil Efficiency Discussed

PLEASE clear up some points on coils for radio frequency. Is it true that coils with a small field, such as doughnut or toroid coils, are more efficient? What is the most suitable diameter for any coil? Is there any advantage in space winding?—H. S. A.

The subject of coil design can not always be dissociated from the particular circuit in which the coils are to be used, as sometimes a less efficient coil solves problems that arise only if a more efficient coil were used. It is certainly untrue that coils with smaller external fields, like toroids, are more efficient. Indeed, it is exactly true to state that the measure of a coil's efficiency is the extent and strength of its field. The only positive asset a coil has is its field, hence the field is its figure of merit, much more so, by the way, than the mutual conductance is a tube's figure of merit. Toroids require much more wire to attain a given inductance than do solenoids, hence toroids have a higher radio frequency resistance, and this effect is sometimes capitalized to produce stability. But it is resistance directly in the tuned circuit, so has little to commend it, grid suppressors with more efficient coils being preferable. In general, there is no known type of coil superior to the solenoid. What the diameter should be depends on the number of turns of a given type of wire and insulation, since the axial coil length should be about one-and-a-half times the diameter. But variations from this formula are entirely permissible even small-diameter, long length coils being acceptable, especially in modern circuits where the sensitivity of cascaded RF stages is very high, and the selectivity adequate, due to the number of stages. Space winding reduces the distributed capacity, hence is valuable where circuit constants and design may make it otherwise difficult to cover a given band of frequencies, as the broadcast band, using a small capacity condenser (.00025 mfd.) Another advantage is that space winding, being usually done in grooved forms, makes possible greater uniformity of inductance in quantity production.

* * *

Listens In to Television

ONCE in a while on my short-wave set I pick up television signals. These I recognize by their peculiar grinding sounds, a grind produced as if from some whirling motor. Please let me know what it is I hear.—F. S.

You hear the sounds to which the vision has been converted, plus the sound of the motor driving the scanning disc. This motor sound is extraneous and is a form of interference, although it need not necessarily have any bad effect upon the picture. When a moving object is televised, the image is scanned, and the resultant intermittent and graduated light is impressed on a photo-electric cell. This has the property of producing changes in current values equivalent to changes in light values. These changing current values are amplified and many of them are audible. The changes are impressed on a radio frequency wave, this constituting the act of modulation, and the modulated wave is transmitted in the usual way. At the receiving end a set is tuned to the signal frequency, and the transmission process is reversed, so the image can be seen. That is, the radio wave is tuned in, the carrier eliminated, by detection, the audio component amplified in the AF channel, the

output fed into a kino lamp which produces values of light corresponding to the values of current, and these light values a scanning disc picks up. Concentration of this controlled light, through the disc holes to a small screen, completes visibility.

* * *

Voltage Divider for B Supply

I AM in doubt as to what type and wattage of voltage divider to use in my B supply.—G. H.

The problems of output voltages are easily solved by using a resistor with adjustable taps. Then with the aid of a high resistance voltmeter, 1,000 ohms per volt, you can establish the desired voltages by moving the taps and finally tightening the moving part. For ordinary purposes, using a B supply for 245 tube, single-sided output, a 10,000 ohm resistor would be satisfactory, rated at 50 watts. If push-pull is used either the wattage of the entire resistor should be raised, say 50 per cent., or the wattage of the biasing section, through which flows the current of the last audio push-pull tubes, should be 75 watts. It is this section that carries the extra current due to push-pull. The rating, of course, is higher than the actual wattage, but this is as it should be. The resistance of the total voltage divider determines the bleeder current at specified voltage. Hence at 300 volts, with 10,000 ohms total, the bleeder is 30 ma. It is well to have a substantial bleeder like this, to stabilize the output voltages, making them stand up better as more plate current is drawn, due to the extra number or different type of tubes and couplings used.

* * *

Reason for Selectivity Difference

THE short-wave receiver I built, to cover the broadcast band as well, I find enough selectivity on the short wavelengths but not enough selectivity on the higher wavelengths (broadcast spectrum). I am satisfied with the receiver, as it was built primarily for short-wave reception, and the broadcast wave feature is purely incidental, and welcome as that much extra service. But I would like to know the reason for this phenomenon of differentiated selectivity. I use plug-in coils. Two coils for the broadcast band require throwing a switch to increase the tuning capacity by parallel condenser connection.—T. Y.

The reduced selectivity on the broadcast band is due to the reduced ratio of inductance to capacity. For best results the ratio of inductance to capacity should be high. This high ratio is not quite feasible in such a receiver as yours, hence the results on the broadcast band must be accepted as they are, merely fair, while reliance for best work is placed on the receiver when it is functioning on the short waves.

Join

Radio World's

UNIVERSITY CLUB

And Get Free Question and Answer Service for the Coming 52 Weeks. This Service for University Subscribers Only

Subscribe for RADIO WORLD for one year (52 numbers). Use the coupon below. Your name will be entered on our subscription and University Club lists by special number. When sending questions, put this number on the outside of the forwarding envelope (not the enclosed return envelope) and also put it at the head of your queries. If already a subscriber, send \$6 for renewal from close of present subscription and your name will be entered in Radio University.

NO OTHER PREMIUM GIVEN WITH THIS OFFER

[In sending in your queries to the University Department please paragraph and number them. Write on one side of sheet only. Always give your University Club Number.]

RADIO WORLD, 145 West 45th Street, New York City. Enclosed find \$6.00 for RADIO WORLD for one year (52 nos.) and also enter my name on the list of members of RADIO WORLD'S UNIVERSITY CLUB, which gives me free answers to radio queries for 52 ensuing weeks, and send me my number indicating membership.

Name

Street

City and State.....

If renewing subscription, put cross here.

FILMED SOUND TO BE USED BY WORLD CHAIN

The formation of an international sound-film radio program producing and distributing system was announced by Malcolm Strauss, president of the Cinema Vision Corporation, a newly organized company.

Films recording only sound will be made in English and foreign languages to be shipped to broadcasting stations throughout the world, to be used in place of personal entertainers.

Production and shipment films will begin in a few months, said Mr. Strauss. WMCA will be the New York transmitting unit.

Under the plan singers, entertainers and orchestras will perform before a microphone connected to a film recorder. The film used will be of sufficient width to accommodate the sound record only.

Seeks Advertisers

The films exposed in the recorder will be developed and a large number of prints will be made and sent to all the participating stations for simultaneous broadcasting. Programs will be made to order for business houses desirous advertising through the new medium. The use of films will eliminate the necessity of land wires (telephones) for connecting stations on a chain.

The Cinema Vision Corporation's personnel includes Donald Flamm, president of WMCA; Marion Gilliam of WPCB and Herman Halstead, vice-president of Paul Block, Inc.

73 Stations on List

Forty-three stations in this country and thirty abroad are said to be allied with the new system, but the entire list cannot be made public at present.

RADIOPHONE TO IRELAND

Transatlantic telephone service will be extended to Belfast, in Northern Ireland; to Dublin, in the Irish Free State and to the Isle of Man next Monday, the American Telephone and Telegraph Company has announced. The rate for conversation between New York and these points will be \$46.50 for the first three minutes and \$15.50 for each additional minute. The hours of service will be 6:30 A. M. to 10 P. M. Eastern Daylight Saving Time.

Calls from America to Ireland will be routed through New York to a radio transmitting station of the Bell system, across the Atlantic to a receiving station in Great Britain, and thence by wire to London. From London telephone wires will carry the calls to submarine cables running under the Irish Sea.

Penalty Proposed Over Call Letters

Washington.

Disciplinary action is threatened by the Federal Radio Commission against stations that disobey the regulation requiring the announcement of call letters every fifteen minutes except where a continuity would be interrupted.

Complaints that stations are more lax than ever have reached the Commission in impressive quantity. Some of the letter-writers say that announcers are so saturated with the idea of their own importance that they fail to consider the station or the listeners.

Commissioner Lafount proposed that offending stations have their licenses suspended pending a hearing on complaints of call-letter reticence.

4 TUBE FIRMS IN BIG MERGER

Four independent tube manufacturers have merged and formed a new \$10,000,000 corporation, with RCA affiliations. They are Sonatron, Televocal, Marathon and Magnatron, with a combined output of 75,000 to 100,000 tubes daily. Plants are in Hoboken, Union City and Newark, all in New Jersey, and in Chicago. The new entity is the Union Radio Corporation.

The Union concern will be licensed by RCA, General Electric and Westinghouse, and it is said RCA will take the corporation's note for \$2,000,000 with an option of cash at maturity or 50,000 shares of stock at \$40 a share.

The chairman of the board of directors of the new corporation is Joseph E. Davies, former chairman of the Federal Trade Commission. Lehman Brothers are the bankers.

The daily production capacity of these companies, it is said, is from 75,000 to 100,000 radio tubes, made in five plants located at Chicago, Newark, Hoboken and Union City, N. J. This is said to compare favorably with the tube capacity of the Radio Corporation of America and E. T. Cunningham, Inc. A representative of the new company said that this is just a beginning and that other independent tube manufacturers will be added.

A THOUGHT FOR THE WEEK

A MORE or less crudite editorial writer said in a New York newspaper recently that television is pretty nearly ready for everyday use, ending up his blurb with the assertion that "television is on its way."

It doesn't take great brilliancy to remark: and so is the millennium.

RADIO MUSEUM BEING FORMED; RELICS SOUGHT

Washington.

A movement for the creation of a radio museum embodying the display of historical apparatus from the first transmitter used by Marconi to present-day high-powered equipment, is being sponsored by a group of Government radio officials with representatives of private communications companies.

C. U. Mitman, representing the Smithsonian Institute, declared at a recent informal meeting that the Institution was anxious to obtain a brief historical exhibit of radio and would be glad to participate in any projects to procure the equipment. The Radio Corporation of America, which now has an extensive historical collection, through one of its officials, George Clark, expressed its willingness to participate.

Much Material

A conference was held at which it was agreed that a permanent committee should be formed to assume charge of the collection.

A general discussion of the need for a collection of historical apparatus in radio disclosed that a large amount of material was held by the Navy Department and would have to be disposed of within a short time, and that there was other historical equipment at Navy Yards, at various Army depots, at the Bureau of Standards, and in possession of the Radio Corporation of America. Mr. Mitman pointed out that, according to the law, historical apparatus held by various government departments could not be loaned or given to agencies outside the government unless approved by the Smithsonian Institution.

Smithsonian Institution Interested

He suggested that the Smithsonian Institution was anxious to obtain a brief historical exhibit of radio and would be glad to participate in any projects which had to do with the disposal of this equipment.

Mr. Clark pointed out that the Radio Corporation of America had for the past seven years displayed historical equipment at various radio shows throughout the country and now was anxious to preserve this equipment, and was willing to participate financially in its collection and storage until suitable display space could be obtained in a museum such as the National Museum in Washington, Museum of Peaceful Arts in New York, and any other recognized museums.

Reception Barrier Afflicts West Coast, Says Observer

(Chicago.)

Cities of the West Coast, including Los Angeles, San Francisco, Portland and Seattle, are isolated from the Middle West and East by an heretofore almost solid wall of resistance to radio reception, in the opinion of Prof. Paul G. Andres, vice-president of the Temple Corporation, in charge of engineering.

The principal need to overcome this isolation is more powerful broadcasting stations to raise the energy level at the point of reception, said Prof. Andres.

Among other causes for this isolation, Prof. Andres said was the close proximity of West Coast radio stations to the centers of population in the various cities. He added:

"This makes it very difficult for radio fans of these communities to tune out other local stations and bring in distant ones.

Because the energy of these stations is soaked up by numerous steel buildings, programs received from them in the Middle West and East come in very weak, if at all.

"Refinements in engineering work on receivers would help to step up the weak energy of stations in the West and help make programs audible to listeners far away."

The mineral content of the Rocky Mountains, together with a mysterious fissure in the earth East of the Rockies, probably plays an important part also in this isolation problem, according to Prof. Andres.

He discovered this fissure while riding by plane from Kansas City to Los Angeles. On the ground it would appear to be a deep, sloping ravine. From the air it looks like an abrupt drop into a deep crack in the earth which extends North and South for hundreds of miles.

Alphabetical List of Stations by Call Letters; Location and Frequency

[FROM FEDERAL RADIO COMMISSION LIST REVISED UP TO NOON, AUGUST, 27th.]

Table with 4 columns: Station, Location, Frequency, Station, Location, Frequency. It lists hundreds of radio stations across the United States and territories, including call letters, locations, and frequencies.

[IF YOU WANT TO CONVERT THE FREQUENCIES TO WAVELENGTHS, CONSULT PRECEDING PAGE]

Rider Lifts a BIG Load Off the Service Man's Chest!

In New Book Noted Radio Engineer Devotes 240 Pages to Trouble Shooting in All Receivers and Gives the Wiring Diagrams of Factory-Made Sets in 200 Illustrations—You Can Carry This Book Around With You—No More Torture Tracing Out Circuits.

“Trouble Shooter’s Manual” By John F. Rider JUST OUT!



JOHN F. RIDER
Member, Institute of Radio Engineers

The first comprehensive volume devoted exclusively to the topic uppermost in every service man's mind is "Trouble Shooter's Manual," just published. It is not only a treatise for service men, telling them how to overcome their most serious problems, and fully diagramming the solutions, but it is a course in how to become a service man. It gives all the details of servicing as they have never been given before. Finding the right mode of attack, applying the remedy promptly and obtaining the actual factory-drawn diagrams of receivers always have been a load on the service man's chest. But no more. Rider, expert on trouble shooting, has produced the outstanding volume on servicing, and has taken the load off the service man's chest!

This book is worth hundreds of dollars to any one who shoots trouble in receivers—whether they be factory-made, custom-built or home-made receivers. The home experimenter, the radio engineer, the custom set-builder, the teacher, the student,—all will find this new book immensely informative and absolutely authoritative.

Wiring Diagrams of All These Receivers!

Besides 22 chapters covering thoroughly the field of trouble shooting, this volume contains the wiring diagrams of models, as obtained direct from the factory, a wealth of hitherto confidential wiring information released for the first time in the interest of producing better results from receivers. You will find these diagrams as well

- R. C. A.** 60, 62, 20, 64, 30, 105, 51, 16, 32, 60, 25 A.C., 28 A.C., 41, Receptor S.P.U., 17, 18, 33.
- FEDERAL** Type F series filament, type E series filament, type D series filament, Model K, Model H.
- ATWATER-KENT** 10B, 12, 20, 30, 35, 48, 32, 33, 49, 38, 36, 37, 40, 42, 52, 50, 44, 43, 41 power units for 37, 38, 44, 43, 41.
- CROSLLEY** X1, Tridyn 3R3, 801, 401, 401A, 608, 704, B and C supply for 704, 704A, 704B, 705, 706.
- ZENITH** 39, 39A, 392, 392A, 40A, 35PX, 35APX, 352PX, 352APX, 37A, 35P, 35AP, 352P, 352AP, 34P, 342P, 33, 34, 35, 35A, 342, 352, 352A, 362, 31, 32, 333, 353A, power supply ZE17, power supply ZE12.
- MAJESTIC** 70, 70B, 180, power pack 7BP3, 7P8, 7P3 (old wiring) 8P3, 8P8, 7BP8.
- FRESHMAN** Mastpiece, squaphase, G, G-60-S power supply, L and LS, Q15, K, K-60-S power supply.
- FADA** 50/80A receivers, 460A Fada 10, 11, 30, 31, 10Z, 11Z, 30Z, 31Z, 16, 17, 32, 16Z, 32Z, 18, special, 192A-192S and 192BS units, R80A, 480A, and SF 80/80A receivers, 460A receiver and R80 unit, 7 A.C. receiver, 475 UA or CA and SF45-75 UA or CA, 50, 70, 71, 72, C electric unit for special and 7 A.C. receivers, ABC 6 volt tube supply, 86V and 82W, E180Z power plant and E 420 power plant.
- FRED-EISEMANN** NR5, FE14, NR70, 470, NR 5 7, 437, NR11, NR30 DC.

worth the price of the book. The wiring diagrams are of new and old models, of receivers and accessories, and as to some of the set manufacturers, all the models they ever produced are shown in wiring diagrams! Here is the list of receivers, etc., diagrams of which are published in this most important and valuable book:

- STEWART-WARNER** 300, 305, 310, 315, 320, 325, 500, 520, 525, 700, 705, 710, 715, 720, 530, 535, 750, 801, 802, 806.
- STROMBERG-CARLSON** 1A, 2B, 501, 502, 523, 524, 635, 636, 403AA power plant, 404 RA power plant.
- ALL-AMERICAN** 6 tube lectric, 8 tube 80, 83, 84, 85, 86, 88, 6 tube 66, 61, 62, 65, 66, 6 and 3 tube A.C. power pack.
- DAY FAN** OEMT, 4 tube, 5-5 tube 1925 model, Day Fan 3 A.C., power supply for 6 tube A.C., B power supply 5524 and 5525, motor generator and filter, 6 tube motor generator set, 6 tube 110 volt D.C. set, 6 tube 32 volt D.C. set.
- COLONIAL** 26, 31 A.C., 31 D.C.
- WORKRITE** 8 tube chassis, 6 tube chassis.
- AMRAD** 70, 7100, 7191 power unit.
- SPARTON** A.C. 89.
- MISCELLANEOUS** DeForest F5, D10, D17, Super Zenith Magnavox dial, Thermydync, Grimes 4DL inverse duplex, Garod neutrodyne, Garod EA, Ware 7 tube, Ware type T, Federal 102 special, Federal 59, Kennedy 220, Operadio portable, Sleeper RX1, Armad inductrel.
- PHILCO** Philco-electric, 82, 86.
- KOLSTER** 4-tube chassis used in 6 tube sets, tuning chassis for 7 tube sets, power amplifier, 7 tube power pack and amplifier, 6 tube power pack and amplifier, rectifier unit K23.

Some of the Questions Settled in Book:

Securing information from the receiver owner, list of questions, practical chart system of repairs, circuits and operating conditions. Repairs in the home, method of operation, spare tubes, the process of elimination, recognizing symptoms, examples of practical application, tracing distortion, tracing electrical disturbances; vacuum tube tests; neutralizing systems, filament circuits, grid circuits, methods of securing grid bias, plate circuits; long serials, short aerials, selectivity, imperfect contact, directional qualities, grounds; "A" operation, AC eliminators, DC eliminators; "A" eliminator hum, reasons, voltage, reasons, noise; full wave, half wave, B battery eliminators, filament rectifiers, gaseous rectifier, dry disc rectifier, wiring, parts used, design, voltage regulation, operating limitations, requirements for perfect operation, combination filament and plate voltage eliminators, AC and DC types; B battery eliminator output current and voltage, excessive hum, dead eliminator, poor design, reasons for defects, motorboating, punctured condensers, shorted chokes, voltage regulator tubes, function of filter system, C bias voltages, voltage divider systems, filter condensers, function condensers, voltages in the system; determining voltages in B eliminators, AC DC, voltage drop, effect of shorted filter system, defective rectifiers, defective transformer, defective chokes, defective by-pass condenser, design of filter system, defective voltage divider network, relation between hum and output voltage, isolation of troubles, external filters, noise filters; cone, dynamic, exponential speakers, troubles, dead, weak output, distorted output, rattle, continuity testing, windings, magnets, frequency filters, testing, chokes, condensers, hum eliminator; audio amplifier types, transformer, resistance, impedance, auto-transformer, combinations, requirements for perfect operation, operating limitations, tubes, forms of coupling, plate voltage, grid voltage, filament voltage, isolating condensers, voltage reducing resistances, noise, analysis of trouble, plate current, grid current.

“The Mathematics of Radio”

John F. Rider wrote two companion books grouped under the title "Service Man's Manual." The first was "Mathematics of Radio," the second "Trouble Shooter's Manual." The value of one of these books is more than doubled by the possession of the other. "The Mathematics of Radio," 128 pages, 8 1/2 x 11", 119 illustrations, bridges the gap between the novice and the college professor. It gives a theoretical background so necessary for a proper understanding of radio and audio circuits and their servicing.

See advertisement of "The Mathematics of Radio" on page 20.

Here are the 22 chapter headings:


- SERVICE PROCEDURE
- PRACTICAL APPLICATION OF ANALYSIS
- VACUUM TUBES
- OPERATING SYSTEMS
- AERIAL SYSTEMS
- "A" BATTERY ELIMINATORS
- TROUBLES IN "A" ELIMINATORS
- TROUBLE SHOOTING IN "A" ELIMINATORS
- "B" BATTERY ELIMINATORS
- TROUBLES IN "B" BATTERY ELIMINATORS
- TROUBLE SHOOTING IN "B" BATTERY ELIMINATORS
- TROUBLE SHOOTING IN "B" BATTERY ELIMINATORS
- TROUBLE SHOOTING IN "B" BATTERY ELIMINATORS
- TROUBLE SHOOTING IN "B" BATTERY ELIMINATORS
- TROUBLE SHOOTING IN "B" BATTERY ELIMINATORS
- TROUBLE SHOOTING IN "B" BATTERY ELIMINATORS
- TROUBLE SHOOTING IN "B" BATTERY ELIMINATORS
- TROUBLE SHOOTING IN "B" BATTERY ELIMINATORS
- TROUBLE SHOOTING IN "B" BATTERY ELIMINATORS
- TROUBLE SHOOTING IN "B" BATTERY ELIMINATORS
- TROUBLE SHOOTING IN "B" BATTERY ELIMINATORS
- TROUBLE SHOOTING IN "B" BATTERY ELIMINATORS

RADIO WORLD, 145 West 45th St., New York, N. Y. (Just East of Broadway)
Enclosed please find:
 \$3.50 for which please send me postpaid "Trouble Shooter's Manual," by John F. Rider, being Part II of "Service Man's Manual," 240 pages, 8 1/2 x 11", more than 200 illustrations, including wiring diagrams of commercial receivers as advertised; imitation leather cover, gold lettering.
 \$2.00 for which please send me postpaid "Mathematics of Radio," by John F. Rider, 128 pages, 8 1/2 x 11", 119 illustrations, flexible cover, this being Part I of "Service Man's Manual."

NAME
ADDRESS
CITY STATE

MERSHON

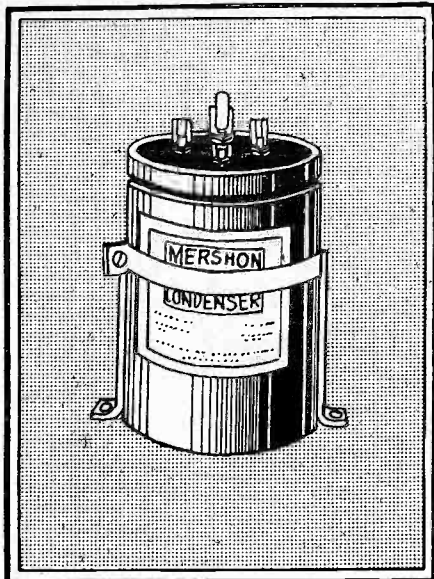Electrolytic Condensers
at Professional Discounts



Mershon Electrolytic Condensers for Filtering Circuits of B supplies, rated at 400 volts D.C., or for by-pass condensers, give enormous capacities in compact form. We offer, at attractive discount, genuine Mershons made by the Amrad Corporation.

Cat. No. Q 8 **\$4.67**
NET
Consists of four Condensers of 8 mfd each, all in one small copper case (less brackets), List Price, \$7.95.....
LIST PRICE, \$7.95
[Cat. Q 8B same as above, but includes mounting bracket. No brackets sold separately..... \$4.67]

Cat. Q 2-8, 2-18 **\$5.55**
NET
Consists of four Condensers, two of 8 mfd. each, and two of 18 mfd. each, all in one small copper case (less brackets), List Price, \$9.45.....
LIST PRICE \$9.45
[Cat. Q 2-8, 2-18B, same as above, but includes mounting bracket. No brackets sold separately..... \$5.75]

Mershon electrolytic condensers are instantly self-heating. They will break down only under an applied voltage in excess of 415 volts D.C. (commercial rating; 400 volts D.C.) but even if they do break down because of overvoltage, no damage to them will result, unless the amount of leakage current and consequent heating of the electrodes and solution cause the solution to boil. Voltages as high as 1,000 volts will cause no particular harm to the condenser unless the current is high enough to cause heating, or the high voltage is applied constantly over a long period.

High capacity is valuable especially for the last condenser of a filter section, and in bypassing, from intermediate B+ to ground or C+ to C-, for enabling a good audio amplifier to deliver true reproduction of low notes. Suitably large capacities also stop motor-boating.

Recent improvements in Mershons have reduced the leakage current to only 1.5 to 2 mills total per 10 mfd. at 300 volts, and less at lower voltages. This indicates a life of 20 years or more, barring heavy abuse.

How to connect: The copper case (the cathode) always is connected to negative. The lugs at top (anodes) are connected to positive. Where there are two different capacities the SMALLER capacity is closer to the copper case.

Mershons of equal capacity may be connected in series for doubling the voltage rating, or in parallel (any combination) to increase the capacity to the sum of the individual capacities, the rating remaining the same, 400 volts.

When series connection is used, the copper case of one condenser the anode of which goes to the high voltage should be connected to a lug or to lugs of the other condenser. The copper case of the second condenser goes to the negative.

In B supplies Mershons are always used "after" the rectifier tube or tubes, hence where the current is direct. They cannot be used on alternating current.

OTHER CAPACITIES OF MERSHONS

["S" stands for single condenser, "D" for double, "T" for triple and "Q" for quadruple. First figure between hyphens denotes quantity, second capacity per anode.]

- Cat. No. S-8, list price \$4.10; net, \$2.41
- Cat. No. S-9, list price \$4.25; net, \$2.49
- Cat. No. S-18, list price \$4.80; net, \$2.82
- Cat. No. S-40, list price \$5.40; net, \$3.17
- Cat. No. S-72, list price \$10.00; net, \$5.88
- Cat. No. D-8, list price \$5.25; net, \$3.08
- Cat. No. D-9, list price \$5.75; net, \$3.38
- Cat. No. D-18, list price, \$6.15; net, \$3.62
- Cat. No. T-8 list price \$6.30; net, \$3.70
- Cat. No. T-9, list price \$6.45; net, \$3.79
- Cat. No. T 1-8, 2-18, list price \$7.90; net, \$4.65
- Cat. No. 1-18, 2-9, list price \$7.50; net, \$4.41

[Note: Add 20c to above prices if bracket is desired. No brackets sold separately.]


No. C.O.D. orders on Mershon Condensers
GUARANTY RADIO GOODS CO.
143 West 45th Street, New York, N. Y.
(Just East of Broadway)

DO YOU LIKE

Dust in Your Eye?

HERE is a .0005 mfd. tuning condenser carefully encased in a housing consisting of metal front and back with transparent celluloid cross-piece sealed in between, all the way around, to keep out dust. The accumulation of dust on the stator and rotor plates of a condenser and about the bearings tends to build up a high resistance to radio frequencies. Keep out the dust and you keep the selectivity and sensitivity high, because of unimpaired efficiency.

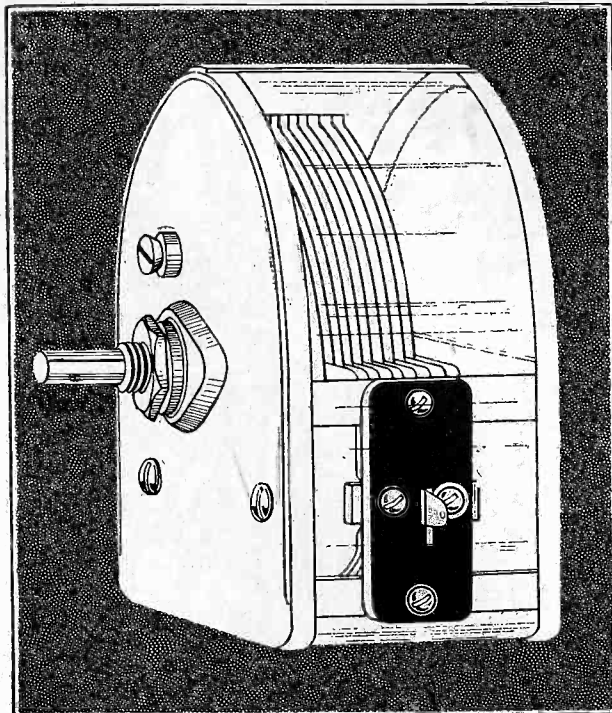Do you like dust in your eye? The condenser is the eye of the receiver, just as the tube is the heart.



Easy-Turning Rotor

MADE to last, and to work at highest efficiency from first to last, this condenser is sturdily constructed. The plates are accurately soldered in place to make best contact and permanent, lasting, accurate alignment. The contact is positive. The back and front metal housing pieces are connected to the rotor as a part of the construction of the condenser itself, and these metal pieces shield the built-in condenser from outside disturbances. The only dielectric insulation are two pieces of specially selected hard rubber, 1 1/8" x 3/8". This is a fine minimum, and it consists of the best insulator. Connection to stator plates is made from the receiver to a tinned lug protruding from one of the insulators. At rear another tinned lug is for rotor connection. Single hole panel mounting is provided with 3/4" shaft projecting. Two-hole mounting is optional. Sub-panel mounting, by means of brackets, is optional, the screws for this purpose being in tapped holes of the front and rear shields. The rotor turns so easily that you'll be delighted at the result. Moreover, the tension of the rotor is adjustable at rear.

Helps You Get DX

NOT only is the dust-protected condenser sturdy and dependable, but it is handsome as well. Those who want excellence surely can obtain it from this condenser. Because of the retained efficiency, you will find this condenser helps you to bring in distant stations.

Equip your set now with dust-protected condensers. Order Cat. No. DUP5 at \$2.50.

GUARANTY RADIO GOODS CO.,
143 West 45th Street, N. Y. City
(Just East of Broadway)
Gentlemen: Please ship at once.....
dust-protected .0005 mfd. condensers, Cat. DUP5, at \$2.50 each.
 Enclosed please find remittance. You are to pay cartage.
 Ship C.O.D. I will pay cartage.
NAME
ADDRESS
CITY..... STATE.....
5-DAY MONEY-BACK GUARANTY

Two for the price of One

- Get a FREE one-year subscription for any ONE of these magazines:
- CITIZENS' RADIO CALL BOOK AND SCIENTIFIC DIGEST (quarterly, four issues).
 - RADIO (monthly, 12 issues; exclusively trade magazine).
 - RADIO ENGINEERING (monthly, 12 issues; technical and trade magazine).
 - SCIENCE & INVENTION (monthly, 12 issues; scientific magazine, with some radio technical articles).
 - YOUTH'S COMPANION (monthly, 12 issues; popular magazine).
 - BOYS' LIFE (monthly, 12 issues; popular magazine).

Select any one of these magazines and get it FREE for an entire year by sending in a year's subscription for RADIO WORLD at the regular price, \$6.00. Cash in now on this opportunity to get RADIO WORLD WEEKLY, 52 weeks, at the standard price for such subscription, plus a full year's subscription for any ONE of the other enumerated magazines FREE! Put a cross in the square next to the magazine of your choice, in the above list, fill out the coupon below, and mail \$6 check, money order or stamps to RADIO WORLD, 145 West 45th Street, New York, N. Y. (Just East of Broadway).

Your Name
Your Street Address
City State.....

DOUBLE VALUE!

If renewing an existing or expiring subscription for RADIO WORLD, please put a cross in square at beginning of this sentence.

RADIO WORLD, 145 West 45th Street, New York, N. Y. (Just East of Broadway)

Component Parts

for

H. B. Herman's

245 Power Amplifier

for 5 x 17 1/2" Base

(Note: This will completely power MB29)

- T1, Ch1, Ch2—One Polo 245 power supply, consisting of one 12 amp. 2.5 volt winding, one 3 ampere 3 amp. 2.5 volt, one 5 volt, one 724 volt, all center-tapped; primary winding and two chokes; all in one cadmium-plated case\$10.00
- C1, C2, C7—Three 2 mfd. HV filter condensers, 550 volts rms working voltage, @ \$1.70 5.10
- C3, C4, C5, C6—One Mershon electrolytic condenser, consisting of two 18 mfd. anodes and two 8 mfd. anodes, with mounting bracket 5.75
- C8, C9—Two .01 mfd. mica dielectric condensers @ .3570
- C10—Two HV filter condensers, 550 volts rms working voltage, connected in parallel @ \$1.70 3.40
- R1—One voltage divider: (1) to (2) 8 ohms, (2) to (3), 40 ohms, (3) to (4) 775 ohms, (4) to (5) 4,400 ohms, (5) to (6) 2,500 ohms. 1.75
- R2—One .5 meg. metallized resistor..... .30
- R3—One 2 meg. metallized resistor..... .30
- R4—One 50,000 ohm (.05 meg.) metallized resistor40
- R5—One 5 meg. metallized resistor..... .30
- Ch3—One output impedance 3.00
- F—One 2 ampere cartridge fuse, with fuse holder40
- Mounting bracket for C1, C2, C7, C10..... .25
- Speaker—Two binding posts @ .1020

\$31.15

GUARANTY RADIO GOODS CO.

143 West 45th Street New York City

**A New Tube
228 AC,
High Mu**

**Amplification Factor, 45
Mutual Conductance, 1,000**

An Amazing Tube That Attains New Volume Levels in Resistance Audio and Greater Selectivity as a Detector of Bias or Leak—Condenser Type.

Heater Voltage, 2.5 v. AC. Plate Voltage, 180 Volts Grid Bias 2.5 Volts Negative for Amplifier; 6 Negative for Bias Detector.

Same Base, Same Prongs, Same Heater Voltage as 227, and, therefore, can be used to replace 227.


Order 228.....\$2.50

Kelly Tube Company

143 West 45th Street (Suite 1214)
NEW YORK, N. Y.

**ARISTOCRAT
FLOOR SPEAKER**

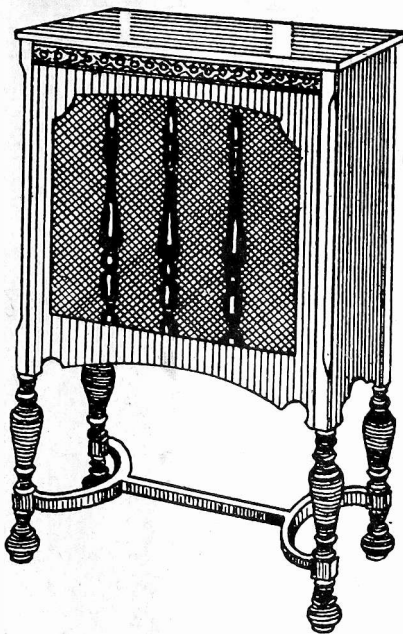With Melted Wood Horn of 8 ft. tone travel (exponential type) with baffle and horn motor built in. Extraordinary bargain. **\$20.00**



The speaker cabinet is walnut finish, 33" high, 24 1/2" wide, 17 1/2" deep, with carved, lega. Golden cloth grille covers front opening. Built inside is No. 595 molded wood horn with baffle and No. 203 driving motor unit that stands 25 volts without filtration. Horn and motor removable. Table alone is worth price asked. Remit with order and we pay cartage on Aristocrat Floor Speaker.

Acoustical Engineering Associates

143 WEST 45th STREET
NEW YORK CITY
(Just East of Broadway)

LYNCH
Manufacturers of LYNCH RESISTORS, EQUALIZERS, SUPPRESSORS, MOUNTINGS, RESISTANCE-COUPLED KITS, ETC.
Write for Booklet.
Lynch Mfg. Co., Inc., 1775 Broadway, N. Y.

Blueprint FREE!

Get a free blueprint of either circuit listed on the coupon below, by sending \$1.00 for eight weeks' subscription for RADIO WORLD, or send \$1.50 for 13 weeks' (quarter of a year) and get both blueprints free!

RADIO WORLD, 145 W. 45th St., N. Y. City

- Enclosed please find:
- \$1 for which send RADIO WORLD for 8 weeks and send free blueprint of the battery model 4-tube Screen Grid Diamond of the Air.
 - \$1 for which send RADIO WORLD for 8 weeks and send free blueprint of the 4-tube AC Screen Grid Diamond of the Air.
 - \$1.50 for which send RADIO WORLD for 13 weeks and send both blueprints free. (If renewing a subscription put cross here.)

NAME.....
ADDRESS.....
CITY..... STATE.....

**A Tube NECESSITY
-Not an Extra**

There is no choice. You MUST use AMPERITE to AUTOMATICALLY control fluctuations in the current supply to your tubes. A type for every tube—A.C. or D.C. \$1.10, with mounting (in U.S.A.) at all dealers.



Radiall Company
50 FRANKLIN ST., NEW YORK



FREE New "Amperite Blue Book"—brim full of useful radio pointers and circuit diagrams. Write Dept. R, W. 18

AMPERITE
The "SELF-ADJUSTING" Rheostat

Wholesale Prices

—for Dealers, Agents and Set Builders
RASCO HAS IT—PROMPT DELIVERY



Our huge Wholesale Radio catalog No. 19 (2ND EDITION) is a valuable encyclopedia—a liberal Radio education. Mailed immediately on request—absolutely

FREE

1500 Illustrations and 6000 articles

From many years in the Radio Mail Order Business, we have learned how an organization must be efficiently run to gain and retain the good will of our customers. Radio Specialty Co. ships orders promptly—offers you 100% quality merchandise on a strict money-back basis if not thoroughly satisfied and sells at rock-bottom net prices.

Our catalog contains the largest assortment of completely assembled all-electric AC Receivers at amazingly low prices, and other Radio Merchandise including such lines as Pilot—Silver—Marshall—Carter—Aero—Yaxley—Tobe—Hammarlund—Amer Tran—Cunningham—Dongan—Thordarson—Muter, etc., etc. The latest improvements in Radio are listed and thoroughly described in this great catalog: AC All-Electric Sets with self-contained ABC power supply—Public Address Amplifier systems—AC Set Converters—A and B eliminators—Dynamic Speakers and Units—Magnetic Speaker Chasses—250 Tube Amplifiers—Airplane Cloth Speakers—Push-Pull Power Amplifiers—Electric Phonograph Turn-Tables—Combination Radio and Electric Phonograph Consoles—Speaker Tables—Short Wave Sets and Adapters—Shield Grid Tube Kits—Television Parts—Electric Household Appliances, Vibrators, Tools, Workshops—Cameras, etc., etc. Logically, how can you afford to be without our catalog. Send for one now!

RADIO SPECIALTY CO.
100R Park Place New York, N. Y.
Radio's Oldest Mail Order House

**Component Parts for
Herman Bernard's**

H B Compact

(BATTERY MODEL)

The Circuit of Circuits!

Only Four Tubes

- Bernard Antenna Tuner BT5A.....\$2.50
- Bernard Interstage BT5B..... 2.50
- Two Dustproof .0005 cond. pair with 4 support brackets 5.00
- One 90 mmfd. equalizer35
- Three .01 mfd. at 40c each..... 1.20
- One .25 meg.30
- One 5.0 meg.30
- One .75 meg.40
- One 75-ohm rheo. with switch..... .80
- One 1.3 ohm..... .15
- One 6.5 ohm..... .30
- 4 binding posts at .10..... .40
- Drilled steel cabinet 7x9 1/2x15"..... 4.00
- Satin aluminum subpanel, socketed, bracket, insulators, 4 resistor clips..... 2.00
- Two dials at .70 ea..... 1.40
- Two dial pointers at .10 ea..... .20
- 7-lead cable50
- Two links at .35 ea..... .70

\$23.00

GUARANTY RADIO GOODS CO.

143 West 45th Street, New York, N. Y.
Just East of Broadway

FILL OUT AND MAIL NOW

SUBSCRIPTION BLANK

RADIO WORLD

RADIO WORLD

145 West 45th Street, New York City,
(Just East of Broadway)

Please send me RADIO WORLD for months, for which

please find enclosed

SUBSCRIPTION RATES:

- Single Copy.....\$.15
- Three Months..... 1.50
- Six Months..... 3.00
- One Year, 52 Issues..... 6.00
- Add \$1.00 a Year for Foreign Postage; 50c for Canadian Postage.

LET US PUT YOUR SPEAKER OR YOUR SET IN SHAPE!


If your receiver or amplifier, no matter of what kind, is not giving proper results, send it to us, prepaid. We will test it FREE and let you know what's wrong, telling you cost of repairs. Our charges are very reasonable. Six years' experience. Loudspeakers and units repaired. Burnt-out coils replaced. Jaynox Laboratories, 57 Dey Street, New York City.

"WHATB-ELIMINATOR SHALL I BUILD?"
 Send 10c to Dept. RW10 for this helpful construction book.
 175 Varick St., New York, N.Y.
ELECTRAD
INC.

P O L O

Transformer Block

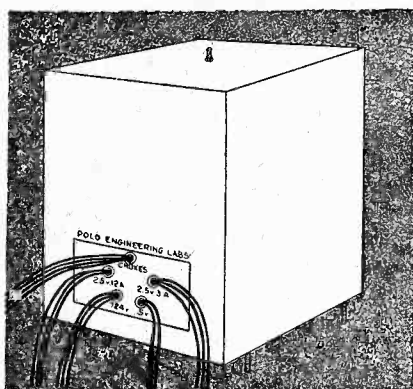2.5 v. at 3 amps., 2.5 v. at 12 amps.,
 5 v. at 2 amps., 724 v., CT; two
 chokes, all in one casing . . . **\$10**



HERE is a compact transformer block, enabling you to build an ABC supply of finest design, to furnish the required voltages to operate screen grid AC tubes, 227 AC tubes, and 245 power tubes in single or push-pull circuit. This transformer block is expertly engineered and properly voltaged. The high voltage secondary, for instance, is fully high enough, so that when the voltage drops in the choke coils, tube and other apparatus in the B supply are taken into consideration, the direct current output across the voltage divider is 300 volts when the maximum current flowing through a section of the divider is 80 milliamperes. This enables correct

[Center taps on all windings except primary.]

POLO ENGINEERING LABORATORIES

57 Dey Street, N. Y. City

Suite 6

Walter J. McCord, Manager

Equip Yourself Now With Necessary Meters!

To do your radio work properly you need meters. Here is your opportunity to get them at no extra cost. See the list of nine meters at left. Heretofore we have offered the choice of any one of these meters free with an 8-week subscription for RADIO WORLD, at \$1, the regular price for such subscription. Now we extend this offer. For the first time you are permitted to obtain any one or more or all of these meters free, by sending in \$1 for 8-week's subscription, entitling you to one meter; \$2 for 16 weeks, entitling you to two meters; \$3 for 24 weeks, entitling you to three meters; \$4 for 32 weeks, entitling you to four meters; \$5 for 40 weeks, entitling you to 5 meters; \$6 for 48 weeks, entitling you to six meters. Return this offer with remittance, and check off desired meters in squares at left.

RADIO WORLD will help you in your radio work, so you will be able to use the meters most valuably. Keep abreast of all the new circuits, intimate details on perfecting existing sets, and get inside track on sensitivity, distance reception, tonal quality, and news of radio, technical and non-technical. Enjoy the writings of Dr. Lee De Forest, McMurdo Silver, J. E. Anderson, Herman Bernard and a host of other radio engineers who contribute their knowledge to you through the medium of RADIO WORLD, the first and only illustrated national radio weekly. You can find no magazine that better caters to your needs than RADIO WORLD. Short waves? RADIO WORLD will tell you all about them. Extremely sensitive broadcast receivers? Their construction and operation are fully discussed with confident regularity. Power supplies—push-pull or otherwise? AC receivers? Screen grid tubes? Large receivers that give a super-abundance of performance—small, economical receivers that give performance out of all comparison to their size? Are you interested in these? Then you're interested in RADIO WORLD.


Present mail subscribers may renew their subscription under this remarkably generous offer. Put a cross in square.

RADIO WORLD

145 W. 45th St., N. Y. City—Published Weekly.
 All Newsstands, 15c per copy—\$3, six months—\$6 a year

O-600v, AC & DC

High Resistance Meter
ACCURATE TO 1%!

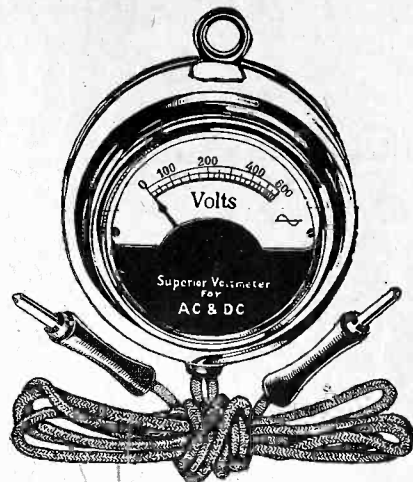

O-600 AC and DC Voltmeter—same meter reads both with 32" long flexible cords built in, and equipped with hanger. Extreme diameter (less hanger) 2 3/4".

MOST USEFUL!

Here is a meter that serves an abundance of uses, because it has a wide voltage range, 0 to 600 volts, and measures voltage of alternating current and direct current, and is accurate to 1%. In a meter it's accuracy that counts.

You can measure not only the DC voltages of B eliminators, power packs and B batteries, with easily legible readings of 20 volts per division of the scale, with wide divisions between 100 and 400 volts, so that you can easily see to within 5 volts, but you can also measure the AC voltage across high-voltage power transformer secondaries. If full-wave rectification is used, you measure each of the two sections of the transformer secondary and add the voltages. Thus up to 1,200 total volts across the secondary may be read. For half-wave rectification, a secondary up to 600 volts is read across the total winding. You find out at once whether this winding is open or shorted, since no reading then would be obtained, or find out whether the voltage is right, or too high or too low. In all instances the AC voltage across the secondary should read higher than the desired DC output, due to the voltage drop in the tube and to the current in the entire voltage divider and its sections. The normal deduction from the AC voltage, to obtain the DC voltage, is at least 10%.

A REQUISITE FOR SERVICING!

Often service men, experimenters and students must know not only the transformer high voltage, but also whether the AC line voltage is the rated 110 volts or not. This meter tells you. Connect it across the 110-volt line. By reading this voltage and the voltage of the high-voltage secondary you can also determine the step-up ratio, by dividing the smaller reading into the larger.

Because this is a high-resistance meter you can rely on the accuracy of the readings.

Only a high-resistance meter can accurately measure the DC voltage of a B eliminator. Other meters draw so much current that the reading may be 50 volts less than what it should be, or still more inaccurate, and you could almost guess the voltage more accurately than a low-resistance meter would read.

MONEY-BACK GUARANTY!

This meter is sold on a 5-day money-back guaranty. Buy one, try it, test it thoroughly, compare it with other meters in performance and appearance. If not fully satisfied, send it back and your money will be promptly refunded.

The meter is full nickel plated, highest possible polish, has green cords, with red (positive) and black (negative) moulded bakelite tip-holders, and sturdy tips. The positive and negative indications are for DC measurements. For AC the meter may be connected at random.

This meter, which is of the moving vane type, is made in Germany and represents finest workmanship.

Cat. M600 AC-DC\$6.00

SEND NO MONEY!

GUARANTY RADIO GOODS COMPANY,
 143 West 45th Street, New York, N. Y.
 (Just East of Broadway).

Please ship at once C.O.D. one O-600 voltmeter, reading both AC and DC, on 5-day money-back guaranty. This meter must be exactly as advertised in Radio World. Cat. M600, price\$6.00

NAME

ADDRESS

City State.....

5-DAY MONEY-BACK GUARANTY

FREE!

Your Choice of These Nine Meters FREE!

- | | | |
|--------------------------|-------------------------|---------|
| <input type="checkbox"/> | 0-5 Voltmeter D.C. | No. 328 |
| <input type="checkbox"/> | 0-50 Voltmeter D.C. | No. 337 |
| <input type="checkbox"/> | 0-Volt Charge Tester | No. 25 |
| <input type="checkbox"/> | 0-10 Amperes D.C. | No. 338 |
| <input type="checkbox"/> | 0-25 Milliamperes D.C. | No. 325 |
| <input type="checkbox"/> | 0-50 Milliamperes D.C. | No. 326 |
| <input type="checkbox"/> | 0-100 Milliamperes D.C. | No. 380 |
| <input type="checkbox"/> | 0-300 Milliamperes D.C. | No. 389 |
| <input type="checkbox"/> | 0-400 Milliamperes D.C. | No. 394 |

New Diamond

PARTS FOR BATTERY MODEL DIAMOND

C1—Aerovox .0005 moulded fixed.....	.25
C2—Hammarlund .0005 mfd Midline.....	3.30
C3, C4—Two Aerovox moulded .008 mfd. @ .50 ea.....	1.00
C5—Hammarlund .0005 mfd Midline.....	3.30
C6—Aerovox .0025 moulded fixed with clips.....	.30
C7—Aerovox .0005 moulded fixed.....	.25
A1—622 Amperite with mount.....	.85
A2, A3, A4—Three 1A Amperites, three mounts @ .85.....	2.55
R1—50-ohm Frost rheostat.....	1.00
R2—5-meg. Lynch metallized leak.....	.40
T1, T2—Two National A100 audios @ \$5.70 ea.....	11.40
Ant., Gnd., Sp. —, Sp. + posts @ .10 ea.....	.40
P1—Yaxley jewel window bracket .35 with pilot lamp .20.....	.55
Sw—Yaxley No. 10 A battery switch.....	.35
7 x 21-inch front panel.....	2.35
10 x 20-inch official battery Diamond subpanel, self-bracketing, with four sockets affixed; subpanel hardware, insulated bushings, washers.....	3.00
Front panel and subpanel together.....	5.00
Two dials with pointers.....	2.00
Two knobs @ .20.....	.40
One roll stranded Braidite.....	.30
Hammarlund 70 mmfd. Equalizer.....	.40
Four Kelly tubes: one 222, two 201A, one 112A or 171A.....	7.00

GUARANTY RADIO GOODS CO.

143 WEST 45th STREET
(Just East of Broadway)
NEW YORK CITY

LACAULT'S BOOK

GIVES YOU A FINE UNDERSTANDING OF the SUPER-HETERODYNE

R. E. LACAULT, E.E., I.R.E., who died recently, was one of the outstanding authorities on the Super-Heterodyne. He wrote a book, "Super-Heterodyne Construction and Operation," that explains in a non-technical manner the phenomena associated with a Super-Heterodyne. More, it gives a clear outline of the way such a receiver functions, and naturally gives the clues to solving virtually all the troubles that may arise in a Super.

So thoroughly did Lacault do his work that he covered associated topics, thus making his book a sidelight on radio in general, including advice on trouble-shooting.

Therefore the service man, the home experimenter, the custom set builder and the student will welcome this book.

It consists of 103 pages and includes 68 illustrations. It is bound in maroon buckram.

There are three valuable tables in the book, also. One classifies harmonics into groups, e.g., sound, radio, short waves, heat, light, chemical rays, X-rays and "unknown." Another is a trouble-shooting chart, classifying "trouble experienced" and "causes" and referring to the text for specific solutions. The third is a table for converting broadcast frequencies to wavelengths (accurate to .1 of a meter) or for converting the wavelength into frequency.

THE book begins with a comparison of alternating and direct current and proceeds to a discussion of the relation of wavelength to frequency. Then tuning is explained.

Condensers, coils, induction, vacuum tube operation and testing, earphones and speakers, rectification, oscillation, grid condenser action, modulation, grid bias detection, regeneration, beat notes, frequency changing, audio amplification, batteries, aeriads, loops, wiring, sockets, and shielding are only some of the other important topics covered.

Besides, there is an entire chapter on the construction of a Super-Heterodyne receiver, with list of parts, front, top and rear views of set, front panel layout, shield dimensional drawings, schematic diagram of wiring and picture diagrams of the top and bottom views of the subpanel.

You Can Get This Book At Once!

You will want this book not only for present reading but also for future reference. It is authoritative and highly informative. Send for it now! It's free with each order for an eight weeks' subscription for RADIO WORLD. Present subscribers may renew under this offer. Their subscriptions will be extended eight weeks. Please use coupon.

RADIO WORLD, 145 W. 45th St., N. Y. City
(Just East of Broadway)

Gentlemen: Enclosed find \$1.00. Please enter my subscription for RADIO WORLD for eight weeks at \$1.00 and send me at once one copy of R. E. Lacault's "Super Heterodyne Construction and Operation," FREE!

I am a subscriber at present. (Check off if true.)

Name


Address

City..... State.....

5-DAY MONEY-BACK GUARANTEE

CONE ASSEMBLY WITH DOUBLE MAGNET UNIT

\$6.00

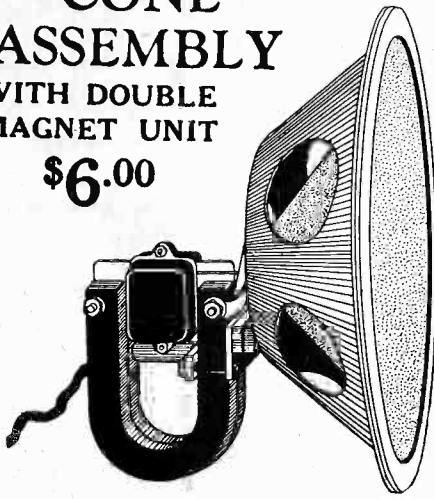

An excellent magnetic type speaker for installation in any cabinet. The unit is a double-magnet Paratone, with two magnet coils, for utmost sensitivity. Each horseshoe magnet is 3/4" thick. The magnet coils are forever protected against dust and other foreign, injurious substances, by special bakelite housings. The pin is reverse drive. The cone frame is metal. The 9" cone is specially treated buckram.


All assembled, with long cord, ready to play, Shipping weight 6 lbs. \$6.00 (Cat. CAS) Net

The unit alone (cord included). It will operate any type sounding surface, including paper, cloth, wood, etc. Shipping weight 4 lbs. (Cat. UA) Net

Guaranty Radio Goods Co.
145 West 45th St., New York City

AERIAL TUNER

Improves Summer Reception

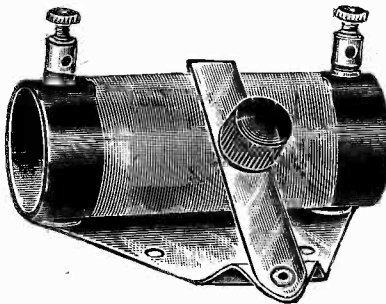

Remove aerial lead from set. Connect aerial instead to one of the binding posts of the Aerial Tuner. Connect the other binding post of the Aerial Tuner to antenna post of your set. Then move the lever of the Aerial Tuner until any weak station comes in loudest. The lever need not be moved for every different frequency tuned in. The Aerial Tuner acts as an antenna loading coil and puts the antenna's frequency at any frequency in the broadcast band that you desire to build up. It makes high wavelengths come in loud as low wavelengths. It helps separate stations and clear up reception. Makes great improvement in Summer reception. Price, \$1.00.

GUARANTY RADIO GOODS CO.

143 West 45th Street
New York City

(Just East of Broadway)

Please look at the subscription date stamped on your last wrapper, and if that date indicates that your subscription is about to expire, please send remittance to cover your renewal.

In this way you will get your copies without interruption and keep your file complete.

Subscription Department, Radio World, 145 West 45th Street, New York, N. Y.

CLAROSTAT

Not just the name of a product, but the name of a service dedicated to better radio results. CLAROSTAT stands for variable and fixed resistors, volume controls, automatic line voltage ballasts, socket antennas, etc.

CLAROSTAT MFG. CO.,
291 North 6th Street Brooklyn, N. Y.


FREE RADIO GUIDE

SEND FOR IT

This book tells about newest startling developments. How to take advantage of the new wrinkles in radio, television, short wave etc. Pictures and descriptions of thousands of new ideas. Shows new A-C Screen Grid tube and other sets, kits, parts, accessories and supplies at wholesale prices. Shows you how to save money on these and many more necessities besides. Now edition now ready. Send for it today—NOW BARAWIK CO., 139 Canal St., Chicago, U. S. A.



Horn Unit \$2.25

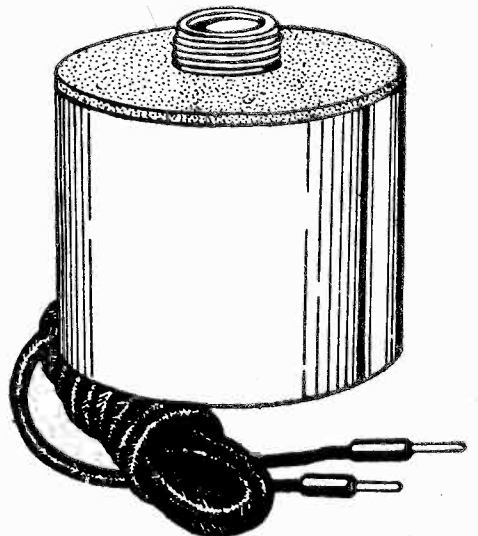

This unit is pre-eminent for horn-type speakers, such as the exponential horns or other long tone-travel horns. The faintest word from a "whispering tenor" or the tumultuous shout of the crowd or highest crescendo of the band is brought out clearly, distinctly. Stands up to 450 volts without filtering. Works right out of your set's power tube, requiring no extra voltage source. Standard size nozzle and cap are die-cast aluminum, one piece, with milled platinum-like finish. The casing is full nickel, of highest possible polish. Works great from AC set, battery set or any other set, push-pull or otherwise.

For Portable Use

This unit can be used in a portable without any horn attached and will give loud reproduction. Order Cat. 225, with 4 1/2 ft. cord attached . . . (Shipping weight, 2 lbs.) . . . \$2.25

Air-Column Horn

8-ft. tone travel molded wood horn (less unit No. 225) is obtainable already mounted in a baffle box. Outside overall dimensions of baffle box, 21 1/4" high, 18" wide, 15" front to back. Shipping weight, 27 lbs. Order Cat. 596 @ \$8.00. The 225 unit and 596 horn built into a ply-walnut table 33" high, 24 1/2" wide, 17 1/2" front to back. Shipping weight, 50 lbs. Cat. No. 597 . . . @ \$20.00

Acoustical Engineering Associates,
145 W 45th St., N. Y. City (Just E. of Bway).

Please ship C. O. D.
 Cat. No. 225 @ \$2.25 Cat. No. 596 @ \$8.00
 Cat. No. 597 @ \$20.00

Name

Address

City..... State.....

FIVE-DAY MONEY-BACK GUARANTEE

RADIO RECEIVING TUBES, by Moyer and Westrel, first edition just off the press. No radio service man, experimenter or student of radio should be without this authoritative book on the principles and applications of vacuum tubes. It answers all your questions relating to receiving, amplifying and rectifying tubes. Price postpaid, \$2.50 Radio World, 145 W. 45th St., New York.



**Professionals - Engineers
Radiotricians - Mechanics
Consultants - Designers
Service Men - Contractors
Manufacturers - Dealers**

An Invitation

- ¶ A recent survey among the readers of RADIO-CRAFT has disclosed the fact that our circulation is mostly among professional radio men.
- ¶ These men naturally want to read and talk "shop."
- ¶ Our Magazine, starting with the October issue, will be the romping ground of radio technicians.
- ¶ We want to publish your experiences, your wishes, your constructive ideas.
- ¶ Let the other fellow in the trade know what's going on, so that the whole radio fraternity may benefit from it.
- ¶ Send us your articles, letters, experiences, questions, stories, etc.
- ¶ We will pay you for every line published.

What Radio-Craft Readers Want

Articles giving the professional radio man's experience with radio sets, power amplifiers, talking sound film equipment, experience with tubes.

Service men, repair men, laboratory men and radiotricians very frequently develop and get up kinks and test sets that are short-cuts and are a great deal of help in their work. Your co-readers want to know about this equipment, these short-cuts and your novel kinks. Why not give them the benefit of your findings? RADIO CRAFT pays well for this work.

Send all contributions to:

Editor

RADIO-CRAFT

98 Park Place, New York

**A Courtesy to the
Professional Radio Man**

In order to make it possible for all Radio Technicians to read RADIO-CRAFT regularly, each month, we have put into effect a special subscription price.

The regular price of RADIO-CRAFT is \$2.50 per year (12 issues). The newsstand rate is 25 cents a copy.

Any radio professional, sending in a subscription on his letterhead, showing that he is engaged in some capacity in radio work will receive as a special courtesy

8 Issues for

RADIO-CRAFT

for \$1.00

Just pin a dollar bill to the coupon below and forward it with your letterhead or business card.

RADIO-CRAFT
RW-8, 98 Park Place,
New York, N. Y.

Enclosed find \$1.00 for which please enter my subscription to Radio-Craft for eight months.

Name

Address

City..... State.....

NATIONAL

Velvet B Eliminator \$16.13
180 Volts (280 Tube Free)



Latest Model National Velvet-B, Type 3580, in handsome crackle finish black metal casing, for use with sets up to and including six tubes. Input 105-120 volts AC, 50 to 60 cycles. Output 130 volts maximum at 35 milliamperes. Three variable output intermediate voltages. (Det., RF, AF). Eliminator has excellent filter system to eliminate hum, including 80 henry choke and 18 mfd. Mershon condenser. No motorboating! (Eliminator Licensed under patents of the Radio Corporation of America and associated companies.)

Guaranty Radio Goods Co.

143 W. 45TH STREET
(Just East of Broadway)
NEW YORK CITY

MORECROFT

New second edition of "Principles of Radio Communication," by Prof. John H. Morecroft, of the Electrical Engineering Department of Columbia University and past president of the Institute of Electrical Engineers. This is an outstanding and authoritative book on the subject.

This large book on radio principles and practice is something that you must not be without. Every set builder, every designer, every engineer, every service man, simply must have this book. Ready reference to all intricate problems makes this volume invaluable. Set builders, experimenters, distributors, dealers, salesmen and teachers, students and operators, all find Morecroft their standby, and now the new second edition awaits you. 1,001 pages and 831 illustrations in this cloth-bound volume.

Price \$7.50

RADIO WORLD

145 West 45th Street
New York City
(Just East of Broadway)

PANELS



BAKELITE AND HARD RUBBER
Also Bakelite Tubing and Rods
Any Size or Quantity
CORTLANDT PANEL ENGRAVING CO.
165 Greenwich St., New York City

Quick Action Classified Ads

Radio World's Speedy Medium for Enterprise and Sales

10 cents a word — 10 words minimum — Cash with Order

LEADING CIRCUITS

DIAMOND OF THE AIR, SCREEN GRID MODEL, battery operation, four tubes described in February 9th, 16th, 23d and March 2d issues, 1929. Send 50c for these four copies. Blueprint free with 8 weeks' subscription to RADIO WORLD at \$1.

AC DIAMOND, screen grid, 4 tubes, published in March 23d and 30th issues. Send 25c for these two numbers. Blueprint free with 8 weeks subscription for RADIO WORLD at \$1.

If you are renewing a present subscription please so state.

RADIO WORLD, 145 W. 45th St., N. Y. City

ARTISTS and Art Students are printing 250 signs or pictures an hour without machinery. Sample and particulars, 10c. Straco, 1014 Mulberry, Springfield, Ohio.

EVERYTHING IN RADIO

At attractive Prices Sets or parts
Orders shipped exactly as ordered. Prompt service. Write for prices. Inquiries invited Send your address.
ALL RADIO CO., 417 North Clark St., Chicago

HELP WANTED

WANTED a radio engineer to assist an inventor. Must be a good mechanic, capable of designing and doing his own machine work and with inventive ability and vision to develop the idea. Address P. O. Box 530, New Haven, Conn.

AGENTS WANTED


CARTER WINDOW WASHER. Exclusive Distributor wanted. **BIG PROFITS.** Cleans, Dries, Polishes, one operation. Territory closing fast. Act quick. **CARTER PRODUCTS, 985 1/2 Front Street, Cleveland, Ohio.**

HAVE AN EXPERT PUT YOUR SPEAKER IN SHAPE!

If your present speaker, no matter of what kind, is not giving proper results, send it to us, prepaid. We will test it **FREE** and let you know what's wrong, telling you cost of repairs. Our charges are very reasonable. Six years' experience. Loudspeakers and units repaired. Burnt-out coils replaced. **Jaynron Laboratories, 57 Dey Street, New York City.**

New Style DeLuxe Leatherette Carrying Case FREE with each Jiffy Tester!

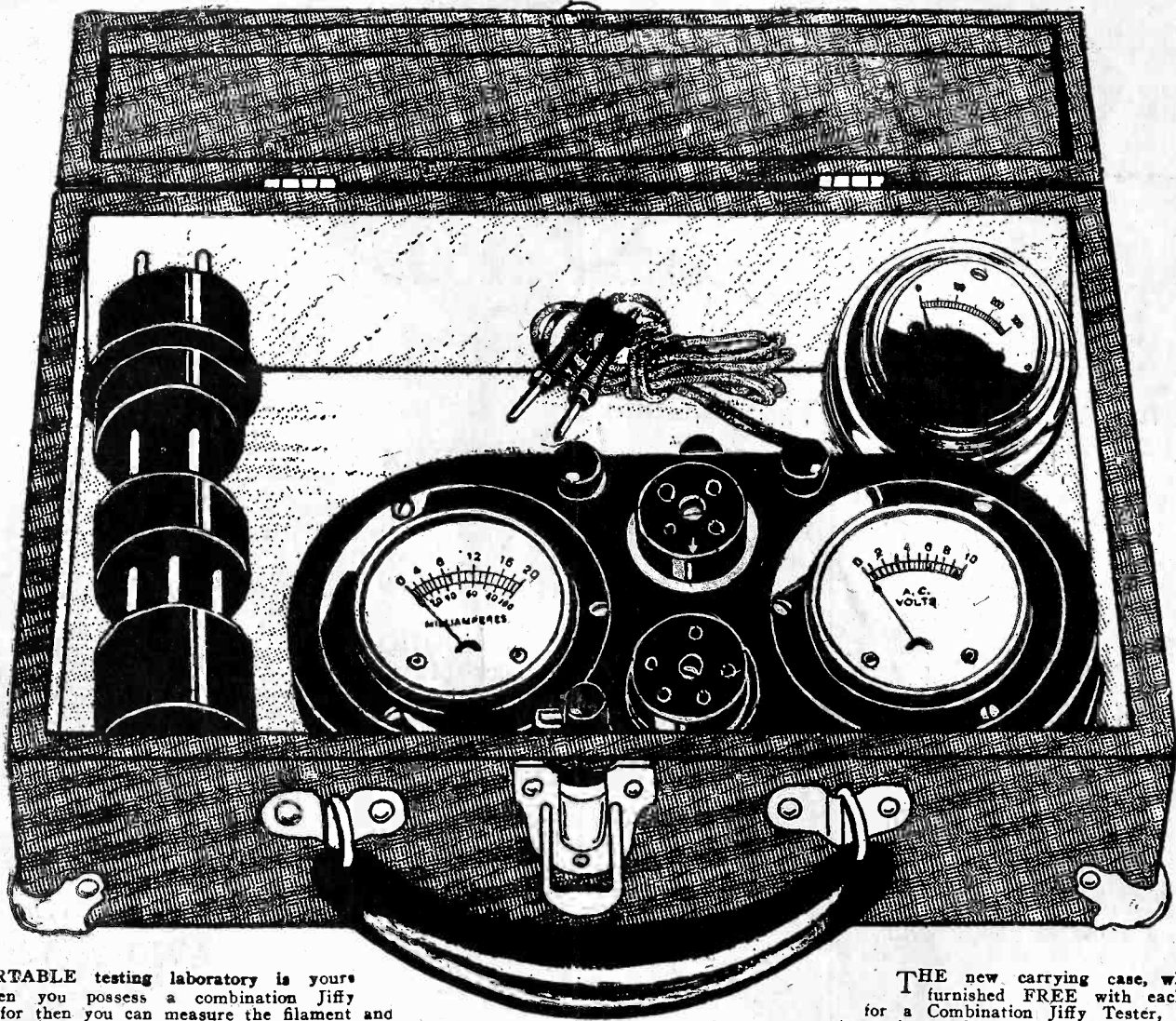This combination of meters tests all standard tubes, including the new AC screen grid tubes and the new 245 tube, making thirteen tests in 4½ minutes! Instruction sheet gives these tests in detail.



A PORTABLE testing laboratory is yours when you possess a combination Jiffy Tester, for then you can measure the filament and plate voltages of all standard tubes, including AC tubes, and all standard battery-operated or AC screen grid tubes; also plate voltages up to 500 volts on a high resistance meter that is 99% accurate; also plate current.

The Jiffy Tester consists of a 0-20, 0-100 milliammeter, with change-over switch and a 0-10 volt AC and DC voltmeter (same meter reads both), with two sockets, one for 5-prong, the other for 4-prong tubes; a grid bias switch and two binding posts to which are attached the cords of the high resistance voltmeter; also built-in cable with 5-prong plug and 4-prong adapter, so that connections in a receiver are transferred to the Tester automatically. Not only can you test tubes, but also opens or shorts in a receiver, continuity, bias, oscillation, etc. The instruction sheet tells all about these tests.

In addition you can test screen grid tubes by connecting a special cable, with clip to control grid (cap of tube) and other end of special cable to the clip in the set that went to the cap before the tube was transferred to the tester.

THE new carrying case, which is furnished FREE with each order for a Combination Jiffy Tester, contains the entire outfit, including the three meters, cable and plug, and three adapters (one for 4-prong tubes, two for 199 tubes). This case is 10½ x 7¾ x 3½" and has nickel corner pieces and protective snap-lock. The case is made of strong wood, with black leatherette overlay.

To operate, remove a tube from the receiver, place the cable plug in the vacant receiver socket, put the tube in the proper socket of the Tester, connect the high resistance meter to the two binding posts, and you're all set to make the thirteen vital tests in 4½ minutes!

The Combination Jiffy Tester is just the thing for service men, custom set builders, experimenters, students, teachers and factories. Order "Jiffy 500." The price is only \$14.50.

If a 0-600 AC and DC high resistance meter (99% accurate) is desired, so house electricity line voltage and power transformer voltages can be measured, as well as plate voltage, instead of the 0-500 DC voltmeter, order "Jiffy 600" at \$15.50.

GUARANTY RADIO GOODS CO., 145 W. 45 St., N. Y. City. (Just East of Broadway).


- Please ship at once on 5-day money-back guaranty one "Jiffy 500," at \$14.50, consisting of
- (1) One Two-in-One 0 to 10 voltmeter for AC and DC. Same meter reads both. Scale especially legible at 1½ to 7½ volts. This meter reads the AC and DC filament voltages.
- (2) One DOUBLE reading DC milliammeter, 0 to 20 and 0 to 100 milliamperes, with change-over switch. This reads plate current.
- (3) One 0-500 volts high resistance voltmeter, 99% accurate; with tipped 30" cord to measure B voltages.
- (4) One 5-prong plug with 30" cord for AC detector tubes, etc., and one 4-prong adapter for other tubes.
- (5) One grid switch to change bias.
- (6) One 5-prong socket.
- (7) One 4-prong socket.
- (8) Two binding posts.
- (9) One handsome moire metal case.
- (10) One instruction sheet.
- (11) One de luxe carrying case.
- (12) One screen grid special cable.
- If 0-300 DC high resistance 99% accurate voltmeter is preferred to 0-500, put check here. Price is same, \$14.50.
- Same as above, except substitute a 0-600-volt AC and DC high resistance 99% accurate voltmeter (same meter reads both) for the 0-500 DC meter. Price \$15.50.

NAME

ADDRESS

CITY STATE

FIVE-DAY MONEY-BACK GUARANTY

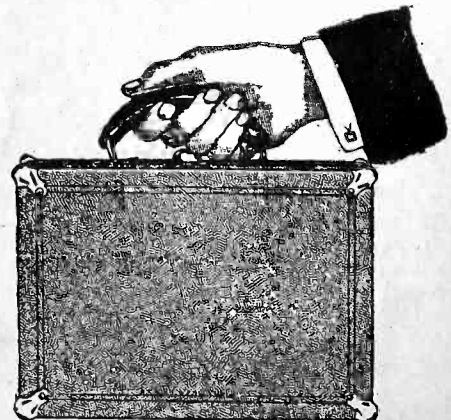

The new de luxe leatherette carrying case is compact and handy. Size 10½" long, 7¾" wide, 3½" deep.