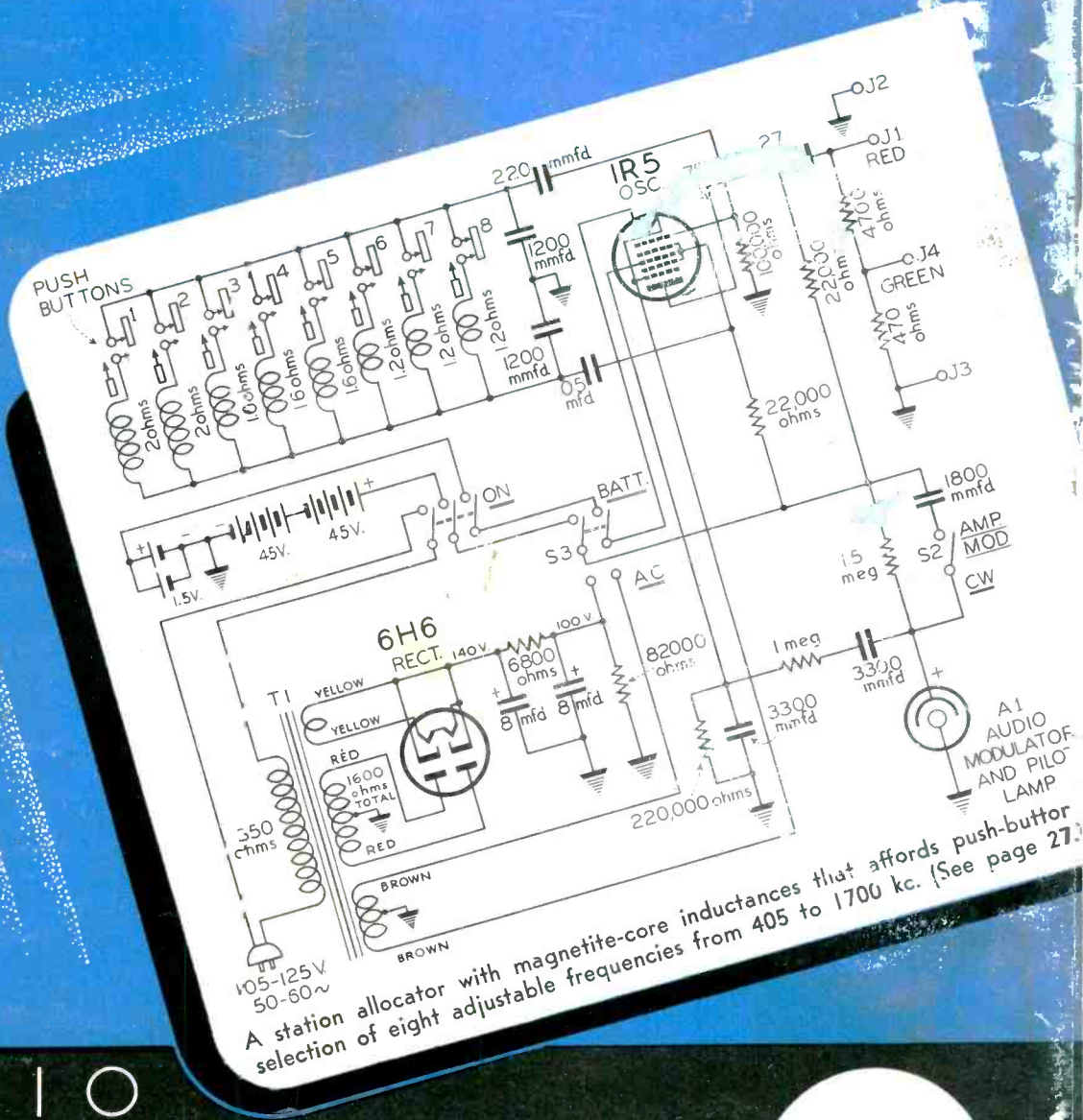


# SERVICE

A MONTHLY DIGEST OF RADIO AND ALLIED MAINTENANCE



★ RADIO  
 ★ TELEVISION  
 ★ ELECTRONICS

December  
 1943





*"In recognition of Service beyond the call of duty . . ."*

In this grim business of war, the men in uniform take the risks; they deserve the decorations.

We tube manufacturers don't expect medals. When, however, credit does come our way . . . and when it comes from such a man as Paul V. Galvin, President of RMA . . . it makes us mighty proud and happy.

"Let me take a moment for special mention of the tube engineers. Too often they are not fully recognized. We see fine accomplishments in apparatus, but we fail to appreciate the important work that has been done be-

hind the scenes by the tube engineer. Hats off to you—your accomplishment has been most extraordinary. But you, also, you cannot as yet rest upon your oars. The job is not finished, and new and additional accomplishments are required before we are finished with this war." \*

Hytron engineers realize fully that "the job is not finished", and they continue to strive for "new and additional accomplishments" needed to win the war. Their aim is to develop better tubes to make possible better fighting equipment—let the decorations fall where they may.

\* Excerpt from address of Paul V. Galvin, president of the Radio Manufacturers Association at the Institute of Radio Engineers' Rochester Fall Meeting, November 9, 1943.



OLDEST EXCLUSIVE MANUFACTURER OF RADIO RECEIVING TUBES

**HYTRON**  
CORPORATION ELECTRONIC AND RADIO TUBES

SALEM AND NEWBURYPORT, MASS.



**BUY  
ANOTHER  
WAR BOND**

# SPRAGUE TRADING POST



## A FREE Buy-Exchange-Sell Service for Radio Men

**WILL TRADE**—Will swap back issues of Radio-Craft, Short Wave Craft, Radio & Television, Service and Radio News for tubes or what have you. Some magazines date back as far as 1932. Eslick Radio Co., 2825 E. 13th St., Wichita, Kans.

**EQUIPMENT FOR SALE**—Precision #832 V-O-M; Supreme #450 radio tester; Supreme #501 tube tester; Jewell 199 set analyzer; Rider chalanyst; Rider's manuals 4 to 11 incl.; Hickok 188 signal generator. M. W. Shellhamer, 224 Pitt St., Tamaqua, Penna.

**TUBES TO SWAP**—Will sell or trade radio tubes: 2A5; 2A7; 77; 2A3; 33; 1F5G; 1B5; 6G5; 57; 58; and others for other tubes or eqpt. My list for yours. Jack Grant, Olney, Okla.

**URGENTLY NEEDED**—Hall-crafter S-29 or Echophone EC-1. State price and condition in first letter. Lieut. E. E. Grubb, Hq. Co., 2nd Bn., 513th Parachute-Infantry, Fort Bragg, N. C.

**WANTED**—3" or 5" oscilloscope; Supreme 561 or any modern oscillator; and condenser tester. Name price and describe. Radio Maintenance Service Co., 841 So. Vermont Ave., Los Angeles 5, Calif.

**WANTED**—All-wave signal generator, late model tube tester, Rider chalanyst and other test eqpt. Walt's Radio Service, RFD 1, Box 52, Norfolk, Va.

**FOR SALE OR TRADE**—Weston #301 D-C milliammeters, voltmeters, ammeters. Also Readrite #430 tube tester; Weston model 506 D-C milliammeters 0-100, 0-200. Want Rider's manuals 8-13 incl. also condenser tester. C. F. McCracken, Hughes Park, Bridgeport, Pa.

**WANTED**—Webber Mod. 500 radio laboratory in good condition. Must be a bargain. Quote price. Radiodell Radionics Labs., 1112 E. Carson St., San Antonio, Texas.

**WANTED**—For war plant jobs, jobs, model 55-C Shure dynamic microphone or #725 Electro-voice-Cardak. Must be hi-impedance. H-K Amplifier Service, 250 Walnut St., Waterbury 27, Conn.

**WANTED**—Six 1H5GT tubes and three A-B power packs (A 1½ volts and B 190 volts). Wilmer O. Houze, Rt. 1, Box 67, Allen, Alabama.

**WANTED**—A good multimeter and a signal generator. Herman Crammer, 1328 Bancroft Ave., Anniston, Alabama.

**FOR SALE**—I. Guthman diversity coupler, never used. Will sell for cash or trade for Triplett #1200A. H. A. McElroy, 7055 Shirley Drive, Oakland 11, Calif.

**WANTED**—14-watt amplifier to use with guitar pick-up. Name price and describe fully. T. W. Gasnell, Route 1, Box 110, Leesville, La.

**FOR SALE**—One #302 Bendix tube tester and volt ammeter in hardwood carrying case. A-1 condition. \$25 cash f.o.b. Want to buy a good multimeter with ohmmeter handling 10 megs., battery-operated type. Robert W. Gorseline, 6 Ocean Green S.W., Washington, D. C.

**WILL TRADE**—Dark room photo equipment worth \$60, incl. Sun Ray enlarger 13.5 lens 35mm—½ V.P. like new. Want late tube checker and equipment worth about this sum. Julius Werner, 410 W. Berks St., Philadelphia, Penna.

**URGENTLY NEEDED**—Rider chalanyst and Jr. Voltomyst or similar equipment. Lowenstein's, 228 N. Broadway, Santa Ana, Calif.

**FOR SALE**—Six 6', four 4½' Fox aluminum trumpets; 22-6-volt field Western Electric, Fox and Racon horn units. Need Rider's manuals, Supreme audolyzer or vedolyzer, and Supreme #561 A-F, R-F oscillator. Lester G. Poague, 7007 Nebraska Ave., Tampa, Fla.

**WANTED**—A good signal generator and set analyzer or multi-tester. Will pay good price for good units. Philip D. Hows, Patten, Me.

**FOR SALE**—RCA voltomyst Jr., practically new. Best cash offer takes it. James Acheson, 1286 Mulvane Ave., Topeka, Kans.

**FOR SALE**—Triplett tube tester #327A with complete, up-to-date tube chart. Perfect condition. Sam Bloom, c/o Kaplans, Vidalia, Ga.

**FOR SALE**—Foote-Pierson tape recorder, double pen. Brush VP-1 vibration pick-up, brand new. Astatic lapel mike #218, also new. Have a number of tuning forks of various pitches—also a list of other desirable items. A. F. Toth, 3608-29th St., Long Island City 1, N. Y.

**WANTED**—Echophone EC-1 or other inexpensive communications

receiver for use by radio students. Gus Petropius, 918 St. Charles Road, Maywood, Ill.

**WANTED**—A complete set of Rider's manuals, also a record changer and pick-up arm. Will pay cash or trade test eqpt. Ted Solarz, 3033 S. Pulaski Rd., Chicago 23, Ill.

**WANTED**—High quality output transformer with 500 ohm sec. for P-P 6L6's. State price, make, type. Have audio and power transformers and following tubes for sale, 43, 45, 56, 58, 75, 2B7, 25Z5, 6A7 and BH. C. L. Goebel, 221 West 233rd St., New York 63, N. Y.

**WILL TRADE**—Have 8 assorted Weston & Triplett 2" and 3" meters; two special 5" Weston meters; 1 Thordarson T-50W12 6-volt, 12-watt amplifier brand new; 100 new radio tubes of std. makes in needed numbers; 2 IRC ladder type L-pad 50-ohm attenuators; assortment of 7 hi-fidelity low-level output, input and mixing transformers, also dozens of odd radio and sound parts. Write for details on any. Want late model all-wave signal generator and/or tube checker, Rider's Manuals, etc., incl. Perlex 44 or similar 35 mm. miniature or 2¼ x 3¼ speed graphic camera. Al Olson, 2915 Ave Q½, Galveston, Texas.

**WANTED**—New or used signal generator, 60-cycle. C. J. Courneya, Tweed, Ontario, Canada.

**WANTED**—A good test oscillator, new or used. William Hill, 14 St. Clair St., Willoughby, Ohio.

**FOR SALE**—At 25% off list, plus postage: 2-1A4G; 1-25Z5G; 2-36; 1-56; and 1-71A tubes; also one power transformer (new) 110 v., 60 cy., H.V. at 70 ma. 350 v. plate; 5 v. at 3 A. for rect., 6.3 v. and 2.5 v. fil. In original box with diagram. Also Triplett 1220-A free-point tester, \$10. Banks Radio Service, Crowder, Okla.

**FOR SALE**—Have large quantity of tubes, some old types, some new; also audio and power transformers; condensers and resistors of all types;

40-meter crystals; small dry rectifier, and many other items. Write for list. What have you? Al. Lovato, 17155 Wildemere, Detroit, Mich.

**WILL TRADE**—Will swap Hickok #110 VTVM with acorn tube, prod and inst. sheet for any of the following, cash difference to be supplied, if any: Simpson #329 Tube Tester, Supreme #589 tube tester with 9" meter, ditto #599; ditto #561 AF and RF oscillator; or Supreme Vedolyzer, M. Chertock, 1591 West 6th St., Brooklyn, N. Y.

**URGENTLY NEEDED**—Hickok 19X signal generator for police radio. G. W. Swartzlander, Fremont Police Radio, Fremont, Ohio.

**SWAP OR SELL**—32 V. d-c to 110 V. a-c inverter, like new. Also Briggs-Stratton ¼ h.p. gas engine, in good shape. Want record changer, 0-1 d.c. milliammeter, or what have you? E. L. Hallgren, Inland Air Lines, Cheyenne, Wyoming.

**FOR SALE**—RCA velocity microphone MI4000, type PB90, \$25; 30-watt amplifier, perfect condition; 12" P.M. speaker in wall baffle; 2-12" dynamic speakers in portable case, 2500 fields; electro-voice microphone #600; Shure mike; 879, 1852, 1853, and 718 tubes; also B&S and Starrett calipers, rules, micrometer, dividers, etc. H. Tanaka, 600 W. 187th St., New York 33, N. Y.

**WANTED**—A good ohmmeter and a condenser tester, also radio test equipment. Floyd Beach, Route 6, Harrison, Ark.

**FOR SALE**—Webster-Chicago 25-watt amplifier, perfect condition; 12" P.M. speaker in wall baffle; 2-12" dynamic speakers in portable case, 2500 fields; electro-voice microphone #600; Shure mike; 879, 1852, 1853, and 718 tubes; also B&S and Starrett calipers, rules, micrometer, dividers, etc. H. Tanaka, 600 W. 187th St., New York 33, N. Y.

**WANTED**—Webber #230 signal tracer and #210 service estimators. Give full details. Albion W. Gamage Radio Service, So. Bristol, Maine.



## CASH WAITING for your unused parts and equipment

Going into the Army or Navy? Giving up your service work for a war job? Or, even if you have remained in servicing work and have unused parts and equipment lying around, you can still render a patriotic service by advertising these for sale through the Sprague Trading Post. We'll gladly run your ad free.

Radio equipment of all types is badly needed today—and the Trading Post will help you dispose of it quickly. It is a golden opportunity to do your bit in keeping radios working on the home front and, at the same time, turn unused materials into cash, and avoid the possibility of obsolescence when the war is won and new, up-to-the-minute equipment is again available.

### YOUR AD RUN FREE!

Send in your ad today. "Equipment for Sale" and "Equipment Wanted" ads of an emergency nature will receive first attention. Sprague reserves the right to eliminate any ads which do not fit in with the spirit of this special wartime advertising

service. Different Trading Post ads appear regularly in Radio Retailing—Today, Radio Service-Dealer, Service, Radio News, and Radio Craft. Please do not specify any certain magazine for your ad. We'll run it in the first available issue.

Dept. S-312, SPRAGUE PRODUCTS CO., North Adams, Mass.



# SPRAGUE CONDENSERS KOOLOHM RESISTORS

Obviously, Sprague cannot assume any responsibility, or guarantee goods, services, etc., which might be exchanged through the above advertisements



“WHEN this war ends, we shall be on the threshold of a new era in radio . . . an era in which man will see, as well as hear,” said David Sarnoff, president of RCA, in a recent talk before the American Association for the Advancement of Science.

“Radio vision will have many uses,” he explained.

“It will be used to prevent collisions on highways and railroads, on sealanes, and on the airways of the world. Radio will be the new eye of transportation and commerce.”

An important prediction for the Service Man to think about!

THE restrictions on the sale of blank recording discs and recording needles are off. Through a WPB amendment to limitation order L-265, consumers will again be able to secure the familiar varnish coated non-metal discs.

The Service Man was given a bit more relief, too, in ruling CMP Reg. 9A, which liberalizes restrictions on controlled materials. Service Men can now purchase \$150 worth of copper wire, or 1/8 of the amount used in 1941, using the rating of AA-3 and the allotment symbol V-3.

WHEN the opening night performance at the New York City Center of Music and Drama was concluded, a prominent drama critic said . . . “All that is needed at the City Center for play productions is a sound-engineering genius.”

For because of sound problems, it was impossible to know who was who, he said. Most of the cast, he explained, were at the mercy of some badly placed microphones.

Paging p-a experts!

SAVE waste paper. It's an important war job. Paper production has been curtailed. And waste paper is needed to make up for the shortage. Do your part by saving every box, newspaper, magazine, etc. Tie them up and be sure your salvage depots gets every package. Save waste paper!

**ALFRED A. GHIRARDI**

Advisory Editor

**F. WALEN**

Managing Editor

**LEWIS WINNER**

Consulting Editor

**BARRY KASSIN**

Assistant Editor

	Page
An Analysis of Grid-Bias Circuits. By Alfred A. Ghirardi . . . . .	5
Application of Special Photocontrols. By S. J. Murcek . . . . .	8
Ser-Cuits. By Henry Howard . . . . .	10
The Audio Chanalyst (Part III) . . . . .	28
 Annual Index . . . . .	 15
 Circuits	
Audio Chanalyst . . . . .	28
Hallicrafters SX-28 . . . . .	10
Philco 42-762 . . . . .	14
Philco 42-788 . . . . .	14
RCA Station Allocator, 171 (Cover) . . . . .	27
 Cover	
Station Allocator (RCA 171) . . . . .	27
 Index to Advertisers . . . . .	 32
 Manufacturers	
New Products . . . . .	26
News . . . . .	30
Jots and Flashes . . . . .	32

Copyright, 1943, Bryan Davis Publishing Co., Inc.

Published monthly by Bryan Davis Publishing Co., Inc.  
19 East 47th Street, New York, 17, N. Y. Telephone PLaza 3-0483

**Bryan S. Davis, Pres.**  
**F. Walen, Secretary**



**Paul S. Weil, General Manager**  
**A. Goebel, Circulation Manager**

James C. Munn, 10515 Wilbur Avenue, Cleveland 6, Ohio  
Pacific Coast Representative: Brand & Brand, 816 W. Fifth St., Los Angeles 13, Calif.



Entered as second-class matter June 14, 1932, at the Post Office at New York, N. Y., under the Act of March 3, 1879. Subscription price: \$2.00 per year in the United States of America and Canada; 25 cents per copy. \$3.00 per year in foreign countries; 35 cents per copy.




# RAYTHEON DISTRIBUTION

**B**efore the war, tubes made by RAYTHEON were used by the majority of important receiver manufacturers . . . because RAYTHEON tube developments kept pace with the latest engineering thinking . . . aiding RAYTHEON set customers in keeping at the top of the art in receiver designs.

During the war, there has been a 1000% increase in RAYTHEON technical achievements in protecting the vast requirements of our Army and Navy.

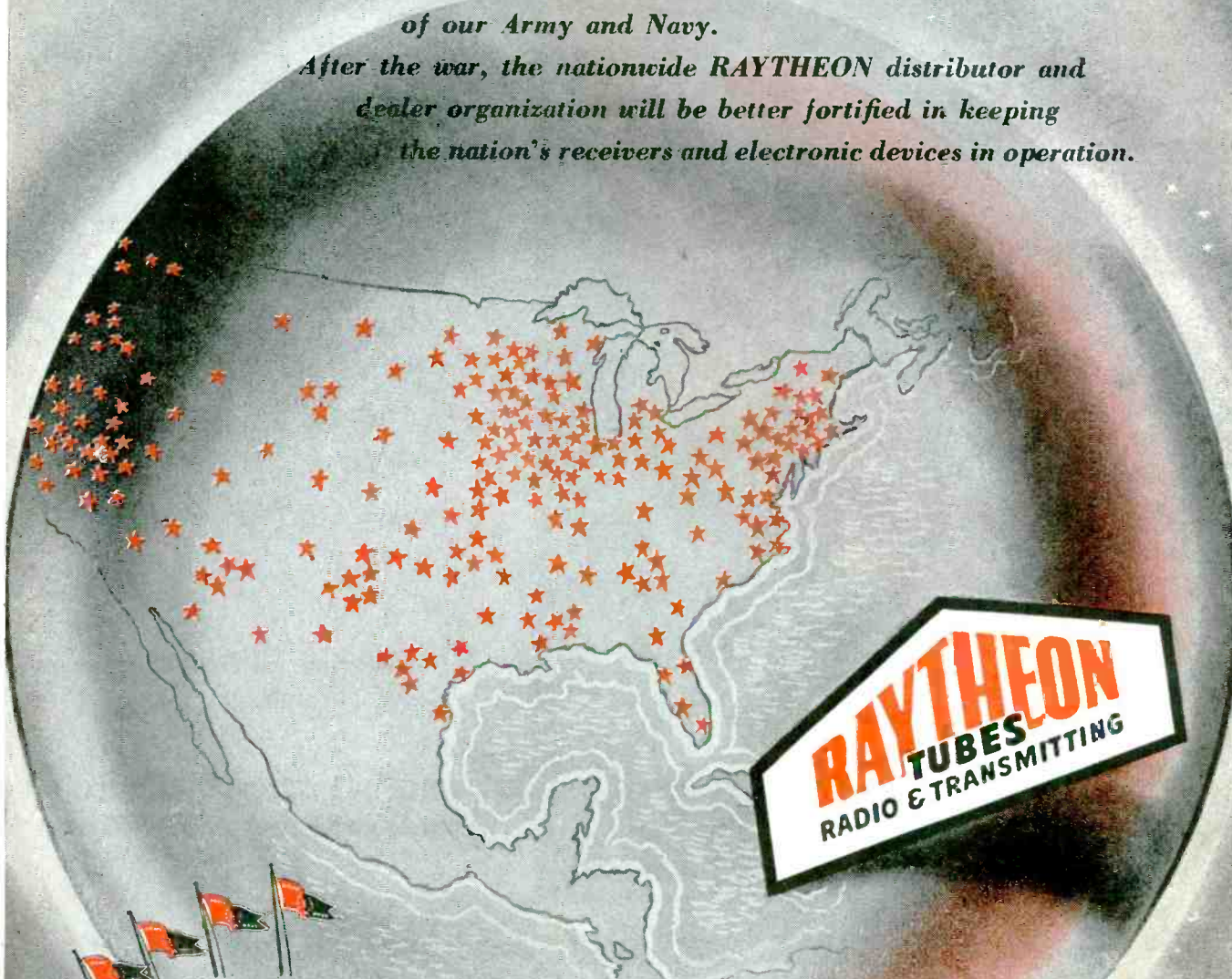After the war, the nationwide RAYTHEON distributor and dealer organization will be better fortified in keeping the nation's receivers and electronic devices in operation.



FOUR "E" AWARDS

Each Division of Raytheon has been awarded the Army and Navy "E"

**RAYTHEON PRODUCTION CORPORATION**

NEWTON, MASS.; LOS ANGELES, NEW YORK, CHICAGO, ATLANTA


DEVOTED TO RESEARCH AND THE MANUFACTURE OF TUBES FOR THE NEW ERA OF ELECTRONICS


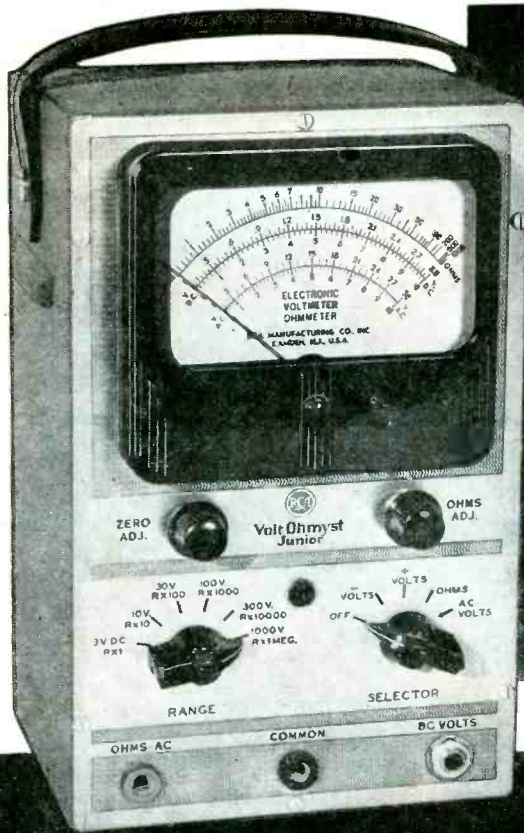
# RCA JUNIOR VOLTOHMYST

TYPE 165-A

*For testing DC  
and AC voltages  
and resistances*



**EXTREMELY WIDE RANGE**

**PROTECTED METER CIRCUIT**

**SCALES NEED NO RE-SETTING  
WHEN RANGES ARE CHANGED**

**HIGH INPUT RESISTANCE**

**PERMITS DYNAMIC VOLTAGE  
MEASUREMENTS IN SIGNAL-  
CARRYING CIRCUITS WITHOUT  
INTERFERING WITH THEIR  
ACTION**

## **SOME TYPICAL APPLICATIONS:**

- ★ For Testing Oscillator Strength
- ★ For Testing DC Supply Voltages
- ★ For Testing Bias Cell Voltage
- ★ For Testing Automatic Volume Control Voltage
- ★ For Testing FM Discriminator Voltage
- ★ For Checking "Gassy" Tubes
- ★ For Testing All Radio Receiver AC Voltages
- ★ For Testing All Radio Receiver Resistor Values

**WRITE FOR DESCRIPTIVE BULLETIN**



## **RCA TEST AND MEASURING EQUIPMENT**

RCA Victor Division • RADIO CORPORATION OF AMERICA • Camden, N. J.



**BUY MORE WAR BONDS**



## AN ANALYSIS OF GRID-BIAS CIRCUITS

By ALFRED A. GHIRARDI

Advisory Editor

**G**RID bias is a voltage applied to the grid of a vacuum tube to obtain a particular type of performance from the tube, which may be closely predicted from the manufacturer's data and a family of static characteristic curves for the particular tube type in question. It is not the purpose of this discussion to go into the theory of operation of vacuum tubes. Suffice it to say that the bias determines the no-signal operating potential of the grid, the r-f or audio signal voltage causing the grid potential to vary above and below this value in exact accordance with the envelope of the signal. Taking the most common illustration of characteristic curves, the grid voltage versus plate current curve of a triode which is of the familiar elongated "S" shape, the most nearly distortionless amplification would be obtained by selecting the grid-bias voltage so that the operating point would occur at the center of the straight portion. Also, the amplitude of the signal voltage would have to be limited so that the peaks would remain on the straight portion. This is the principle of operation of the most used type of amplifier, the *Class A amplifier*.

By increasing the grid bias, with other conditions unchanged, the operating point moves down on the curve until at approximately twice the Class A value, the plate current is nearly zero. This is the Class B operating point, very useful in a number of electronic applications but of only limited value in the popular variety of radio receivers. Several years back, a few receivers made use of Class B audio amplifiers. In large console sets operating from a-c, Class B was used especially to obtain a high power output at a high efficiency. In a series of battery portables, Class B was used to obtain a sufficient power output together with considerable battery economy, taking advantage of the high efficiency of such an amplifier. The introduction of beam power tubes eliminated the need for Class B amplifiers

for obtaining high audio power, thus eliminating their attendant disadvantages. Consequently, this discussion will deal almost entirely with Class A amplifiers.

### Fixed-Source Grid Bias

In the early days of radio when only batteries were used for supplying the required filament and plate power, grid bias or *C bias* as it was usually called, was used only in the first and second audio stages. One reason for this was the expense of *B* batteries which limited the plate voltages employed in the preceding r-f stages to some 45 or 67½ volts. With such low voltages on the plates of early triodes no *C* voltage was really required. Also, the advantages of using *C*-bias voltage was not very widely known. Most early audio amplifiers were transformer coupled, using a bias battery, connected as shown in Fig. 1(a), which usually consisted of a few flashlight cells. This provided a *fixed source* of *C*-bias voltage. Several years later when high- $\mu$  tubes were brought out, resistance-coupled amplifiers came into the picture with the bias battery connected as shown in Fig. 1(b). Then, with the coming of a-c receivers, the use of batteries for supplying the voltages and currents needed to operate the tubes of a receiver declined for about a decade, except for portable work and for farm receivers. But, history repeats itself—and so with radio, *C* batteries came back for use in some of the amplifier stages, but in a new compact, convenient form known as *bias cells*, brought out by Mallory. These cells, diagrammed in Fig. 1(c) are miniature no-drain cells delivering about 1¼ volts for Class A grid bias or any similar application where no current greater than the order of a microampere flows through the cell. The metal case itself is the *negative* electrode, and the black center disc is the *positive* electrode. Special holders have been designed to accommodate from one to several of these


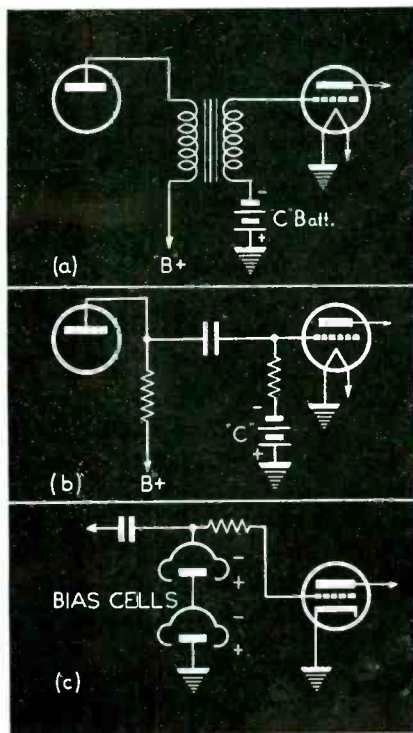


Fig. 1. Circuit arrangements for obtaining grid-bias voltage by means of a fixed source of bias voltage.

Fig. 2. Grid-leak bias methods of detection; also commonly used in oscillators to prevent distortion and to aid frequency stability.

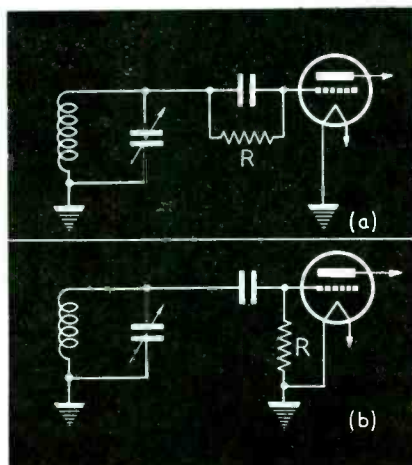



cells. They have a long life and may be connected in series when higher voltages are required.

### Grid-Leak Resistor Bias Method

Another early method of obtaining grid bias which is still used in special equipment is shown in Fig. 2(a). This is the grid-leak detector which is really a diode detector combined with an audio amplifier. The grid-leak resistor  $R$  and grid condenser serve the same purpose as the familiar resistor and bypass condenser, now used in all sets of the superheterodyne type, in the diode detector. An a-f voltage is built up across the grid-leak signal and

this voltage is applied between grid and cathode, more clearly shown in Fig. 2(b). It is then amplified the same as in a Class A audio amplifier except, perhaps, that the bias voltage is less negative. In the early days, the grid leak consisted of a pencil line drawn across a paper type grid condenser using the circuit arrangement Fig. 2(a). Later more stable grid-leak resistors in metallized form were employed.

The grid-leak detector is not a high-quality demodulator because the functions of detection and amplification are, to a considerable extent, incompatible. However, for low modulation factors, such as were used in the early days of broadcasting, the results were not so bad. Super-regenerative receivers used at frequencies of 50 mc and above, commonly used grid-leak detection arranged as shown in Fig. 2.

Grid-leak bias is also commonly used in oscillators of all types, including those in superhet receivers. The action obtained is self-biasing which limits the amplitude of oscillation, preventing excessive distortion and improving frequency stability. The initial bias is zero but, as soon as oscillation starts, the grid is driven positive which causes grid current to flow. The grid current creates an  $IR$  drop in the grid-leak resistor, applying negative bias to the grid, which prevents further build-up of oscillation amplitude. The grid-leak bias method has the advantage of simplicity and of automatically biasing the grid in proportion to the excitation voltage available. Because of this automatic action, the bias voltage developed across the grid-leak resistor is not critically dependent on the value of the grid-leak resistance. The value of the grid-

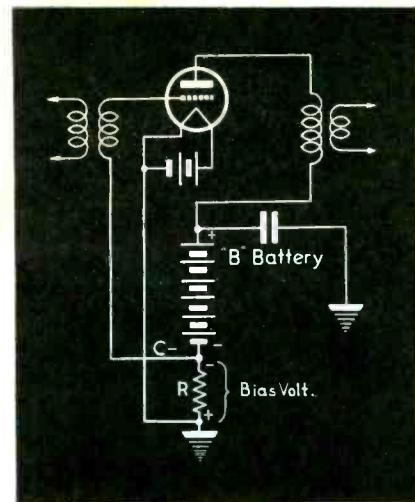


Fig. 5. Cathode circuit bias resistor method used in battery portables.

leak resistor, while not critical, should be kept within certain limits or some undesired effects may occur, such as motorboating or parasitic oscillation as well as super-regenerative action.

### Cathode-Resistor Bias Method

Self-biasing of a single tube is most easily accomplished by any one of the several simple cathode-resistor bias methods illustrated in Fig. 3. The arrangements shown at (a), (b) and (c) are for heater-type tubes. That shown at (d) is for filament type audio or power tubes. In each case a grid bias resistor,  $R$ , is connected in the cathode circuit. The cathode current flowing through  $R$  causes a voltage drop across it, which makes the cathode positive with respect to the ground. Since the grid circuit is returned to ground potential in each case so it is at ground potential with respect to all d-c voltages, the grid is biased negatively with respect to the cathode.

The cathode current for triodes is the sum of the d-c plate current and the d-c grid current (if any). For tetrodes and pentodes, the screen current and other grid currents must also be added to this. The correct value of the bias resistor  $R$  (in ohms) is equal to the required bias (volts) divided by the total cathode current (amperes). The grid bias resistor value is not particularly critical—the nearest commercial value is usually used.

Where a grid-bias resistor alone (without a bypass condenser) is used, as at Fig. 3(a), the signal voltage developed across the bias resistor is being applied to the grid in opposite phase to the signal voltage; hence, a reduction in net input signal voltage takes place and, therefore, a reduction in signal output. This is called current degeneration and has some beneficial effects which are well known to

Fig. 3. Simple cathode-resistor bias arrangements.


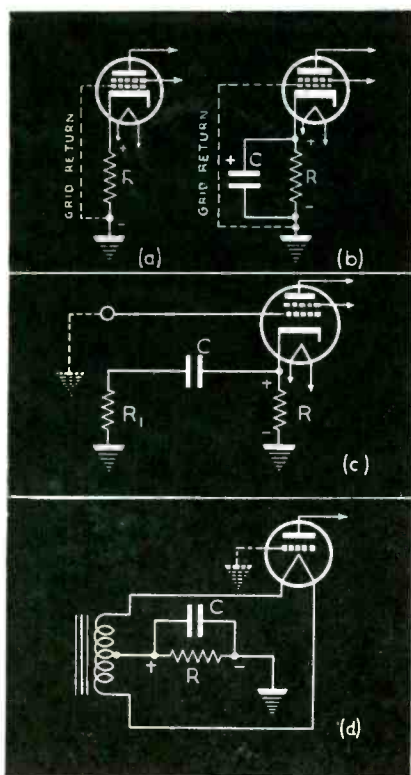


Fig. 4. Cathode-resistor bias arrangements for obtaining one or several bias voltage values.

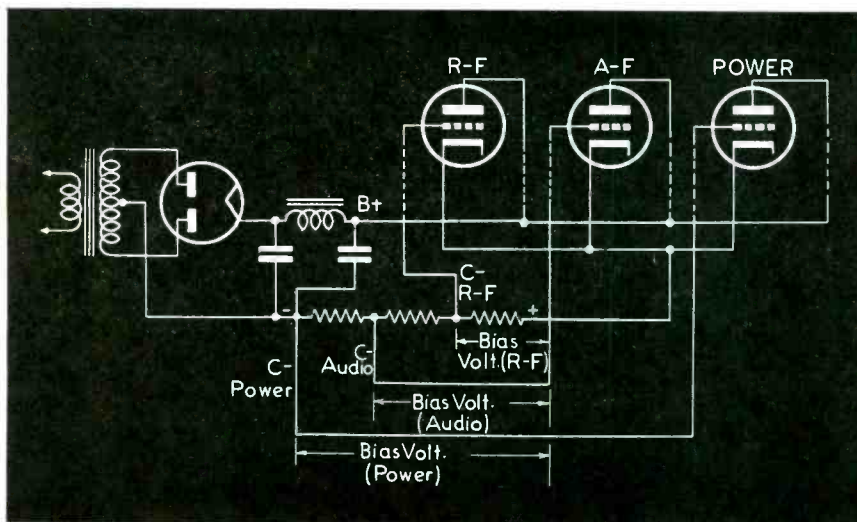



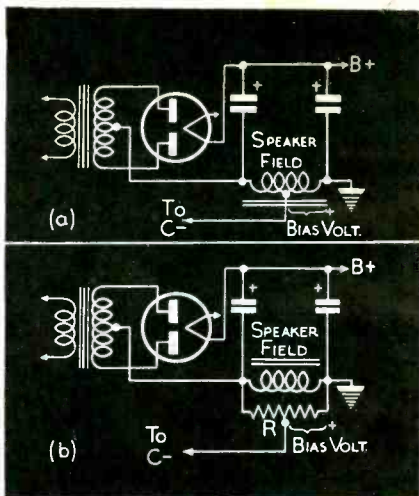


Fig. 6. Tapped speaker field arrangements for obtaining C bias.

Service Men. When maximum amplification is desired, the resistor is bypassed with a condenser,  $C$ , as in Fig. 3(b), large enough to have negligible reactance at the lowest important frequency to be reproduced. This calls for a 25- or 50-mfd electrolytic condenser in audio applications where a full bass is required.

The circuit of Fig. 3(c) shows an alternate method of preventing degeneration without the use of a high capacity. The resistance of  $R_1$  must be high compared to the reactance of the condenser  $C$  at the lowest important frequency.  $R$  is the normal cathode bias resistor. Taking a typical example; let us assume that 60 cycles is the lowest bass note to be reproduced and a 0.1-mfd condenser is used. Its reactance at this frequency is 26,000 ohms. If we make  $R_1$  ten times this value, the degeneration will be insignificant. But that is only about  $\frac{1}{4}$  megohm. We can usually use up to 1 megohm for  $R_1$  in an a-f amplifier so the stunt is an excellent one.  $R_1$  and  $C$  constitutes a *decoupling filter*. The grid-bias circuit arrangement shown at Fig. 3(d) is commonly used for obtaining proper grid bias for a-c operated filament-type audio or power tubes. Connection is made to the electrical center of the filament winding by either a center-tap on the winding as illustrated, or a center-tapped resistor shunted across it. The cathode current flows through the bias resistor  $C$  in this cathode-return circuit, producing the bias voltage.

#### Variations of the Cathode-Resistor Bias Circuit

Several more complicated variations of the cathode-resistor bias arrangements just explained, are illustrated in Figs. 4, 5, and 6.

Where a number of different bias voltages are required for the various

tubes of an a-c operated amplifier or receiver, the circuit arrangement indicated in Fig. 4 is often used. A series of *drop* resistors, or a voltage divider, is connected in the negative high-voltage leg of the rectifier-filter  $B$  supply. Plate and screen currents for the entire set pass through this divider; hence the voltages developed are very stable and fairly independent of signal voltage except in the case of violent audio overloading. Resistance-capacity filters are often used in the  $C$ -leads to prevent common coupling caused by the divider resistors. Since an appreciable current is carried, the resistors in the filter are wire-wound and are of fairly low resistance values.

Applying the same technique to battery portables, a resistor,  $R$ , is connected between the negative terminal of the  $B$  battery and ground, bias being obtained by the voltage drop in this resistor. This arrangement is shown in Fig. 5. The negative terminal of the  $B$  battery is actually the  $C$ -terminal, which is more negative than *ground potential*. Note that the  $B+$  terminal must be bypassed to ground by a condenser, because of the added resistance in the  $B$  circuit.

Another method for obtaining negative bias is illustrated in Fig. 6. Here, the field coil of the speaker is connected in the negative high-voltage return circuit so that the voltage drop

Fig. 8. Bias arrangements for avc circuits.

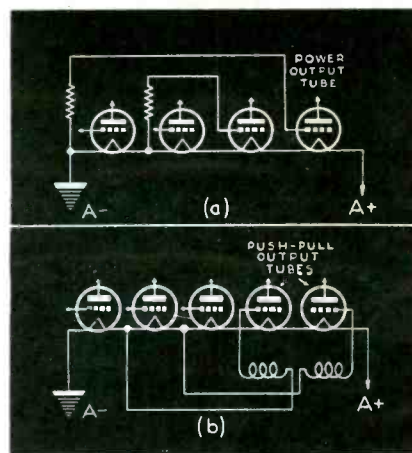
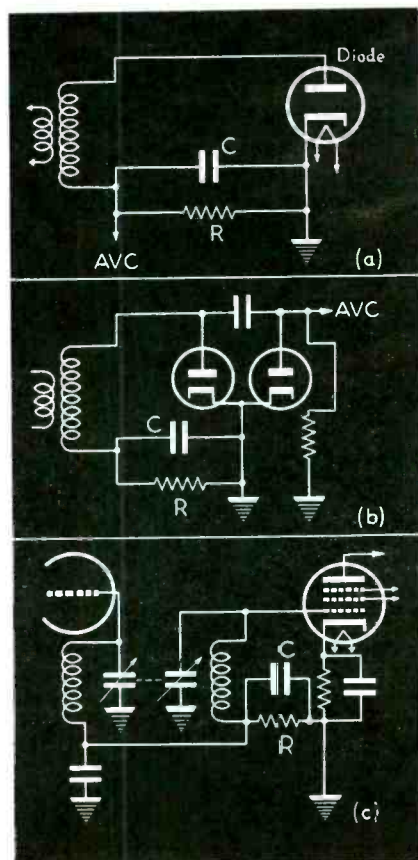


Fig. 7. Bias voltage circuits used in d-c sets or a-c/d-c series-filament portables.

across the field, or any part of it, may be utilized as  $C$  bias. Fig. 6(a) shows the arrangement when a tapped field is employed; Fig. 6(b) shows how the same effect may be obtained when replacement speakers not having a proper tap must be employed. The high-resistance potentiometer  $R$  provides the electrical tap. These connections make it necessary to use a dual electrolytic filter capacitor with a common positive terminal, as shown.

In d-c sets or a-c/d-c series-filament portables, bias voltage is obtained by using the filament string as a voltage divider as illustrated in Fig. 7. If a transformer-coupled push-pull output stage is used, a split secondary must be provided on the push-pull input transformer so that equal  $C$  bias voltage will be applied to both of the push-pull tubes, as shown in Fig. 7(b). Adequate bypassing with decoupling resistors are employed where necessary.

Fig. 8 illustrates the fundamental circuit of the well-known automatic volume control system widely used in receivers. This system produces a bias voltage proportional to the signal strength, the bias being applied in whole or part to r-f, converter and i-f tubes to keep the overall gain constant over a wide range of incoming signal voltages. There is an initial small negative bias voltage, independent of any signal, developed by the *contact potential* diode. This results from the flow of grid current through a high value of grid resistor,  $R$ , connected in the grid-return lead in each circuit shown. This grid current results from the bombardment of the grid by electrons when there is no applied negative voltage to repel the electrons. This potential is known as *contact potential*. Signal voltage is rectified and added to this basic voltage. The bias resistor  $R$  in Fig. 8(a) is some-

(Continued on page 20)

# APPLICATIONS OF SPECIAL PHOTOCONTROLS

By S. J. MURCEK

**E**LECTRONIC control of certain manufacturing processes is most readily accomplished through visual observation of the process under control. Visual observation, in turn, is provided with a form of the photoelectronic camera, usually associated with an appropriate form of the photocontrol.

Actual process control, in such installations, is provided in the greatest part by the electronic system of the photocontrol itself.

Manufacturing processes for various end products differ widely. Thus, the photocontrol system intended for control of a given process in a textile plant is not suitable for direct application to a similar operation in a steel plant. The fundamental reason for this lack of equipment interchangeability lies in the nature of the electronic system end operation. In a given instance, the camera may suit an application specifically, but not another in a similar category. Again, the electronic system incorporated in the photocontrol may operate relays, where direct manipulation would be the most desirable end operation.


The demand for photocontrols suited to the control of only a particular operation has given rise to a distinctly new group of photoelectronic controls, termed *special photocontrols*. These new photocontrols may be of either the *static* or *dynamic* type. Thus, where the operation to be controlled is characterized by a relatively slow change in illumination level, a specific variation of the static photocontrol is used. Where the operation gives rise to a series of rapid or periodic variations of the accompanying illumination level, special dynamic photocontrols are the rule.

A special photocontrol of relatively simple nature, and, incidentally, easy to service and maintain, is a device which is designed to the specific purpose of controlling artificial illumination. This unit is shown in Fig. 1. Great savings of power, which would otherwise be uselessly consumed by a given artificial lighting system, become possible through the application of this photocontrol. A good example of such an installation is the control of lighting on an airway beacon. Here

the beacon lighting is controlled automatically by the photocontrol, dispensing with the necessity for other than occasional personal attention.

This particular photocontrol is of

Fig. 1. A special photocontrol unit designed to control illumination. Among its uses are airway beacon lighting control. This is known as the static type control. (Courtesy United Cinephone)

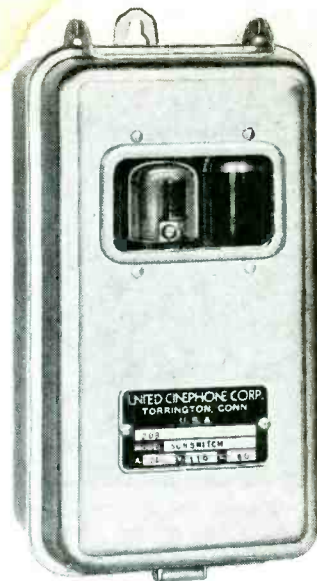

the static type, responding to changes in the natural illumination level by the illumination of the beacon with the approach of nightfall, and extinguishing it with the approach of full daylight. Since provision is incorporated into the photocontrol to cause operation at two differing light levels, the unit is not directly suited to any other operation. Thus it is placed in the special classification embracing such devices.


The circuit for a special photocontrol of this type is shown in Fig. 2. In this circuit, the a-c supply line, connected to terminals 1 and 2, powers the photocontrol. A full-wave rectifier tube 17, affords rectification. The resulting continuous current is filtered by capacitors 14 and 15, in combination with resistor 16. It should be observed that resistor 16, by virtue of the developed voltage drop, absorbs the peaks of the rectified a-c appearing across capacitor 15, and effectively limits the return current from capacitor 14 to capacitor 15 when the a-c supply voltage is at the zero instant between alternations. This effects a pronounced smoothing, or fil-

tering action on the rectified a-c supplied by the rectifier tube.

The d-c voltage appearing across capacitor 14 is in parallel with the voltage divider consisting of resistors 11 and 12, and control potentiometers 10 and 21. Each of these resistance elements is selected so that the proper operating voltage appears on the associated phototube and pentode 9, electrodes.

In normal daylight, the conductance of phototube 5 is high, resulting in the flow of a comparatively large current through the phototube and its load resistor 6. Since, under these conditions, the resistance of the resistor 6 is large with respect to that of the phototube, the voltage across this tube is less than that appearing between the slide contact of potentiometer 10, the *night* adjustment, and the negative terminal of the voltage divider. The cathode of pentode 9 is common with the night potentiometer slide contact. Therefore the voltage between the cathode of this tube and

Fig. 2. Circuit of the light control photocontrol, illustrated above.

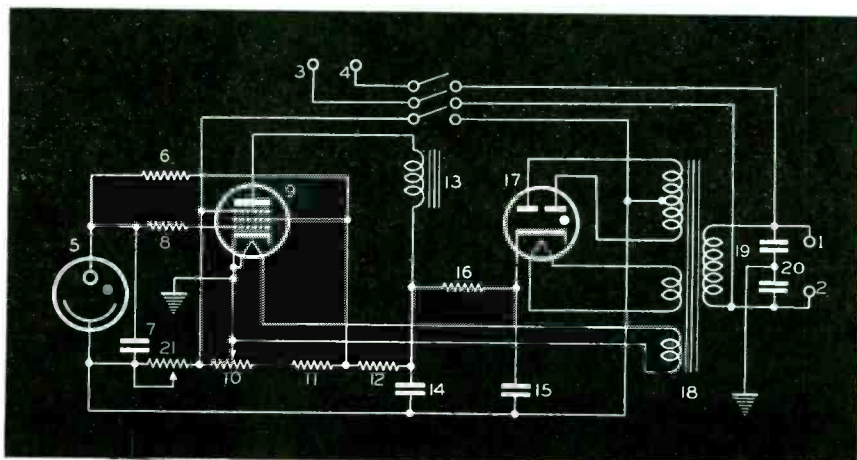



the negative terminal of the voltage divider is identical with the last mentioned voltage. Thus, the grid of tube 9 is negative with respect to its cathode, and the tube plate current is very small. As a result, relay 13 does not seal, and the a-c voltage across terminals 3 and 4, which energize the artificial lighting system, is zero.

With the approach of nightfall, the illumination on phototube 5 is reduced considerably. This reduction in illumination causes the tube resistance to rise, decreasing the current in the phototube circuit. Here, the voltage across the phototube increases. Less of the circuit supply voltage appears across resistor 6, since the resistance of the phototube now approaches that of this resistor.

The rise of the voltage across the phototube places the grid of pentode 9 positive with respect to the cathode, since the voltage across the phototube, under dark conditions, is greater than that appearing between the cathode of the pentode and the negative terminal of the d-c voltage divider. When the grid of the latter tube is positive with respect to its cathode, its plate resistance decreases, the plate current rising sharply as a result. Thus, the coil of relay 13 is energized and the relay seals, closing its make contacts. Power is now supplied to the artificial lighting system, and the day potentiometer 21 is short-circuited.

Closure of the relay contacts which short-circuit the day potentiometer reduces the voltage existing between the cathode of the pentode and the d-c supply negative terminal.

Increase in phototube illumination with the approach of daylight restores the phototube conductivity to a level which is too low to maintain closure of relay 13, de-energizing the arti-

cial lighting system, and reconnecting potentiometer 21 in series with the voltage divider.

Consideration of the circuit action reveals that the illumination level required to unseal relay 13 is less than that to effect its closure. This is due to the reduction of the pentode cathode to d-c negative terminal voltage with relay closure, which in turn insures the presence of artificial illumination with the actual decline of daylight, and the extinguishing of such illumination with sunrise. Briefly, the photocontrol is more sensitive during the night hours than at sunset. This mode of operation also prevents the operation of the control during small changes of daylight illumination, such as would occur during the passage of a cloud above the site of the photocontrol.

In Fig. 2, capacitor 7 serves to bypass small a-c modulation voltages, due to electromagnetic induction, which are present on the phototube voltage. Resistor 8 limits the pentode grid current in the event the grid of this tube becomes highly positive with respect to its cathode. This would be true if direct sunlight should strike the cathode of the phototube. Capacitors 19 and 20 bypass a-c line noise impulses between ground and the line itself, preventing the impression of these voltage surges across the phototube circuit.

The photocontrol of Fig. 1 should be so mounted that the phototube is not subject to direct illumination from direct sun or moonlight.

A static photocontrol which terminates in a reversible end-motor instead of an end-relay has been specifically designed for the purpose of holding the edge of a moving strip of paper in a given constant position. The complete operation involves the reeling of paper strip from a rough reel to one suitable for shipment. The function the light beam, then results in a provide a finished roll with uniform

edges. Thus, if the control maintains the edge of the paper strip in a given position, as the paper is being re-wound, then the roll edges must certainly be uniform. In Fig. 3, 11 represents the edge of this paper strip. The photocontrol is termed, for this reason, an edging control.

In the circuit of Fig. 3, a-c is supplied to the circuit power transformer 5. This transformer is provided with two primary windings, enabling operation of the device from either of two a-c supply voltages. Low voltage operation is possible through the parallel connection of these windings. In series, the operation is from an a-c source having twice this voltage. Thus, for example, the control may be operated from either a 115 or 230-volt a-c line.


The phototube exciter lamp 6 is heated to operating color temperature from the low voltage winding 7 on transformer 5. Light rays from the exciter lamp filament are converged into a tight beam of parallel rays by lens 8, in such a manner that the entire surface of the phototube viewing lens 9 is under its illumination. These rays are converged further by lens 9 into a spot having a diameter no larger than the phototube 10 cathode width, on which they are focussed. Thus the intrusion of the paper edge into the light beam obstructs an amount of light which is directly proportional to the area of strip obstructing the beam. Partial obstruction of the light beam, then results in a proportional reduction of the phototube conductivity.

When the light beam is unobstructed, the phototube conductivity is at a maximum, and the voltage across the phototube load resistor 12 is, as a result, also at a maximum. This voltage will then exceed that appearing between the cathode of pentode 18 and the ground return 34, causing the grid of this tube to become positive with respect to its cathode. Under these conditions, the tube 18 plate current is high, and the voltage between the anode and cathode is correspondingly low. That is, a large voltage appears across pentode 18 plate load resistor 19-35. This places the pentode anode negative with respect to its shield grid.

The cathodes of the rectifier thyratrons 23 and 24 are common with the shield grid of pentode 18. Under the previously described conditions obtaining, the control grid of thyatron 23 is negative with respect to its cathode, and this tube does not, as a result, conduct.

However, the cathode of the inverter triode 20 is connected by means of the

Fig. 3. Circuit of a photocontrol system for holding edge of moving strip of paper in constant position.

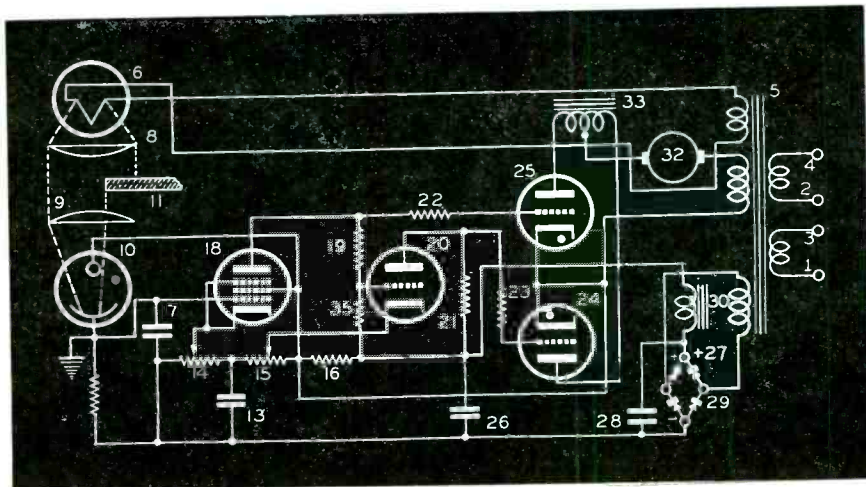

(Continued on page 22)

# SER-CUITS

By HENRY HOWARD

**T**HE unusual services that a communications receiver must afford, demands a highly specialized form of circuit design. The Hallcrafters SX-28 (Fig. 1) illustrates this design feature quite effectively.

The receiver is a 5-band affair covering .55 to 43 mc. The r-f amplifier, or preselector, has two 6SK7 tubes in cascade on bands 3, 4, 5 and 6. On bands 1 and 2 more than one stage is unnecessary to obtain the required image ratio and reduction of spurious interference. With two r-f stages using three preselection circuits, the band width would be narrowed to such an extent that even expanding the i-f amplifier to its utmost would still not provide high-fidelity reception. The modern communications receiver requires two stages of preselection on the higher frequencies to accomplish only one primary object—satisfactory image rejection.


The i-f amplifier is designed for maximum stability. The first two i-f transformers are permeability tuned. In comparing this type of transformer with one having compression mica tuning condensers, it must be remembered that it takes many more turns of the adjusting screw to cause the equivalent change in tuning of the

No.	Value	Voltage or Purpose	Type	No.	Value	Voltage or Purpose	Type
C 1	Band No. 1 Tuning Condenser			C44	10. mfd	300	Electrolytic
C 2	Main Tuning Condenser			C45	.05 mfd	400	Tubular
C 3	1/2 Plate Bandspread Condenser			C46	.05 mfd	400	Tubular
C 4	1/4 Plate Bandspread Condenser			C47	40. mfd	25	Electrolytic
C 5	3/4 Plate Bandspread Condenser			C48	30. mfd	400	Electrolytic
C 6	50 mmf		Variable Air	C49	30. mfd	450	Electrolytic
C 7	2,160 mmf	Band No. 6 Pad	Mica	C50	.02 mfd	400	Tubular
C 8	2,962 mmf	3 Pad	Mica	C51	.01 mfd	600	Tubular
C 9	2,376 mmf	4 Pad	Mica	C52	.01 mfd	600	Tubular
C10	1,600 mmf	3 Pad	Mica	C53	500. mmf	400	Mica
C11	876 mmf	2 Pad	Mica	C54	.05 mfd	400	Tubular
C12	515 mmf	1 Pad	Mica	C55	50. mmf	400	Mica
C13	Temperature Compensated	Condenser		C56	.02 mfd	400	Tubular
C14	.02 mfd	400	Tubular	C57	.02 mfd	400	Tubular
C15	.02 mfd	400	Tubular	C58	.05 mfd	200	Tubular
C16	.02 mfd	400	Tubular	C59	.05 mfd	200	Tubular
C17	.05 mfd	200	Tubular	C60	100. mmf	400	Mica
C18	.02 mfd	400	Tubular	C61	250. mmf	400	Mica in T.
C19	.02 mfd	400	Tubular	C62	.05 mfd	200	Tubular
C20	.02 mfd	400	Tubular	C63	.05 mfd	200	Tubular
C21	.05 mfd	200	Tubular	C64	100. mmf	400	Mica
C22	.02 mfd	400	Tubular	C65	.02 mfd	400	Tubular
C23	.02 mfd	400	Tubular	C66	.05 mfd	200	Tubular
C24	.02 mfd	400	Tubular	C67	.02 mfd	400	Tubular
C25	.02 mfd	400	Tubular	C68	50. mmf	400	Mica
C26	.05 mfd	200	Tubular	C69	50. mmf	400	Mica
C27	.02 mfd	400	Tubular	C70	2000. mmf	400	Mica
C28	.02 mfd	400	Tubular	C71	100. mmf	400	Mica
C29	20. mmf	Trimming Condenser		C72	25. mmf	BFO Control	Air
C30	20. mmf	Trimming Condenser		C73	500. mmf	400	Mica in T.
C31	20. mmf	Trimming Condenser		C74	.01 mfd	600	(Braided Leads)
C32	20. mmf	Trimming Condenser		C75	2. mmdid	200	Twisted Leads
C33	.02 mfd	400	Tubular	C76	2000. mmf	400	Mica
C34	.05 mfd	200	Tubular	C77	.02 mfd	400	Tubular
C35	.02 mfd	400	Tubular	C78	10. mfd	200	Tubular
C36	.02 mfd	400	Tubular	C79	5. mmdid	400	Ceramic
C37	100. mmf	400	Mica	C80	5. mmdid	400	Ceramic
C38	100. mmf	400	Mica	C81	2. mmdid	400	Twisted Leads
C39	.02 mfd	400	Tubular	C82	10. mmdid	400	Ceramic
C40	50. mmf	400	Mica	C83	5. mmdid	400	Ceramic
C41	10. mfd	25	Electrolytic	C84	5. mmdid	400	Ceramic
C42	.02 mfd	400	Tubular	C85	2. mmdid	400	Twisted Leads
C43	5000. mmf	400	Mica	C86	5. mmdid	400	Ceramic

No.	Value in Ohms	Wattage or Purpose	No.	Value in Ohms	Wattage or Purpose
R 1	100,000	1/2	R34	1,000	1/2
R 2	10,000	RF Gain Control	R35	500,000	1/2
R 3	300	1/2	R36	100,000	Tone Control
R 4	1,000	1/2	R37	100,000	1/2
R 5	3,000	1/2	R38	50,000	1/2
R 6	15,000	1/2	R39	200,000	1/2
R 7	100,000	1/2	R40	250,000	1/2
R 8	300	1/2	R41	250,000	1/2
R 9	1,000	1/2	R42	200	1/2
R10	3,000	1/2	R43	20,000	1/2
R11	100,000	1/2	R44	5,000	10
R12	400	1/2	R45	20,000	1/2
R13	1,000	1/2	R46	30,000	1/2
R14	3,000	1/2	R47	100,000	1/2
R15	100,000	1/2	R48	100,000	1/2
R16	300	1/2	R49	100,000	1/2
R17	1,000	1/2	R50	3,000	1/2
R18	3,000	1/2	R51	1,000	1/2
R19	100,000	1/2	R52	50,000	1/2
R20	500,000	1/2	R53	50,000	1/2
R21	400	1/2	R54	600	ANL Control
R22	1,000	1/2	R55	500,000	1/2
R23	3,000	1/2	R56	1,000	1/2
R24	30,000	1/2	R57	100,000	1/2
R25	250,000	1/2	R58	200	1/2
R26	250,000	1/2	R59	250,000	1/2
R27	500,000	1/2	R60	250,000	1/2
R28	100	1/2	R61	500,000	1/2
R29	500	1/2	R62	500,000	1/2
R30	30,000	1/2	R63	3,000	1/2 Inside T.
R31	11,000	1/2	R64	500,000	1/2
R32	4,000	1/2	R65	50,000	1/2
R33	500,000	1/2	R66	50,000	1/2

Fig. 1. This circuit diagram and table of capacitor and resistor values for Hallcrafters SX-28, a five-band receiver, covering the .55 to 43 mc bands.



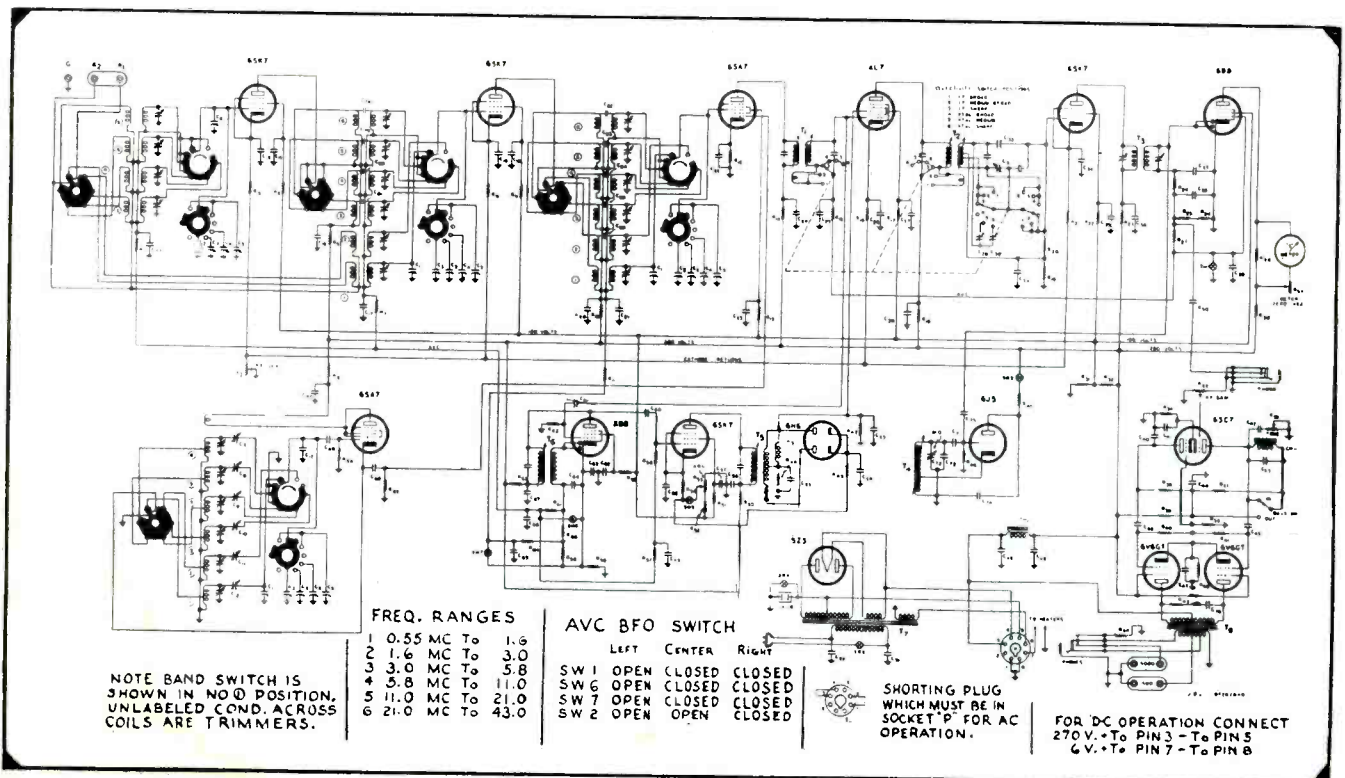



## Is he on your Christmas list?

*There are many ways in which you can remember him now and in the months ahead.*

**V**ISIT your blood bank—not just once, but as often as you can. Blood plasma may save his life—on some battle-torn field.

Buy War Bonds every payday—as many as possible—dollars are needed to give him the weapons he requires to achieve Victory.

Give generously to the USO, the Red Cross and other agencies. They can make the difference between a lonely soldier and a happy one.

**PARTS FOR RADIO, ELECTRICAL AND ELECTRONIC DEVICES, INCLUDING SPEAKERS, TRANSFORMERS, VIBRATORS, VITREOUS ENAMELED RESISTORS, WIREWOUND CONTROLS, PLUGS, JACKS, SWITCHES, ELECTRIC MOTORS**

**CABLE ADDRESS: UTARADIO, CHICAGO**

Co-operate with Civil Defense authorities—a nation is only as strong as its home front.

And do your job—no matter what it is. Work—and work hard for Victory.

That's what you can do for this soldier—what you can do to help bring him home sooner to really enjoy the many merry Christmases to come.

UTAH RADIO PRODUCTS COMPANY, 816 Orleans St., Chicago, Ill. Canadian Office: 560 King Street West, Toronto. In Argentine: UCOA Radio Products Co., S. R. L. Buenos Aires.



SERVICE, DECEMBER, 1943 • 11



For those extra-severe-service applications, particularly in communications-grade radio equipment, fine electronic assemblies, and tough industrial applications, these extra-good Aerovox oil capacitors are now the No. 1 choice. Available on high-priorities, of course, for applications essential to the war effort.

### OIL-FILLED CAPACITORS

Available in wide range of cans, mountings, terminals, capacities, voltages, combinations.

The popular 'bathtubs' normally have terminals on one side of case, but terminals can be placed on both sides, on top or on bottom. Mounting lugs arranged for flat or upright mounting. Also rectangular-can units. Voltages up to 1000.

Round-can transmitting capacitors in voltages up to 7500. Rectangular units up to 5000.

Large, high-voltage capacitors in voltages up to 50,000. X-Ray type units up to 150,000 each.

- Consult our local jobber regarding your capacitor requirements. Ask for latest Aerovox catalog. Or write us direct.

**AEROVOX**  
Capacitors  
INDIVIDUALLY TESTED

AEROVOX CORP., NEW BEDFORD, MASS., U. S. A.  
In Canada: AEROVOX CANADA LTD., HAMILTON, ONT.  
Export: 100 VARICK ST., N. Y. C. • Cable: 'ARLAB'

permeability tuned type. Hence a slight change in the position of the screw will have negligible effect upon the tuning. The adjusting screw is under spring tension thereby making it impossible to turn under vibration.

The diode transformer is air-tuned with two variable condensers, each with a lump capacity of 50 mmfd and a variable capacity of 50 mmfd. These air trimmers are also under spring tension so that they can withstand considerable vibration.

Variable selectivity is also afforded. Six ranges of selectivity are available, from broad high fidelity i-f to crystal sharp, which is used for c-w reception only.

A double AVC system is used. The r-f and mixer tubes are operated by the broadly tuned carrier coming through only three tuned i-f circuits. The final signal however passes through six-tuned i-f circuits. As a result, when the signal is slightly detuned, the receiver output has dropped considerably while the AVC action has dropped but very little. This results in a reduction of between-station noise and a more sharply defined aural tuning action.

The receiver also features an S or signal intensity meter. There is also an automatic noise limiter which chops off the peaks where they extend above the signal level.

A micrometer scale dial is used. This is turned by a large handwheel, which has a locking clutch allowing the dial to be locked in position. The clutch disengages the handwheel so that the receiver cannot be detuned.

The receiver also has a separate r-f gain control and tone control, and a stand-by socket, which is provided for remote relay operation of the receiver.

#### Philco 42-762

This 6-volt battery receiver, Fig. 2, covers broadcast and two short-wave bands. It has a 3-gang condenser in a bandspread band for wide-range tuning and a separate permeability tuned system for bandspread. A 9-point, 15-circuit switch controls tuned circuits in the antenna input, tuned r-f plate, first detector grid, oscillator and the phono connection. The detailed switching functions are . . . antenna input to various r-f transformers; grounding and shorting of non-used transformers; two sections for handling the r-f grid; trimmer selection; r-f amplifier output to one of four r-f transformers; grounding of idle transformers; two sections in the detector grid, selection of trimmers and oscillator grid; grounding of idle oscillation transformers; condenser tuning; oscillator plate and phono selection.

A shunt-fed oscillator circuit is used

# WANTED

## For the PHILCO ENGINEERING STAFF

### ● RADIO TECHNICIANS

Ham operators and radio service men familiar with test equipment.

### ● RADIO-ELECTRONICS-ELECTRICAL ENGINEERS

Men with degrees in electrical engineering or comparable experience in radio and television.

### ● MECHANICAL ENGINEERS

Men with college degrees or comparable experience in the engineering aspects of electrical appliances, and in designing small machinery.

### ● DESIGN ENGINEERS — DRAFTSMEN

Men with experience in mechanical designing, especially of small metal parts and of the automatic machinery to mass-produce them.

### ● MODEL MAKERS

First class precision workers and all-round mechanics capable of starting with blueprints, making the parts required and assembling the finished models.

**W**E expect the men who qualify for these positions to become permanent members of our staff and take an important part in our post-war program.

To maintain the Philco tradition of progressive research and development, is first and foremost in our minds. In such an atmosphere of encouragement most engineers find they do their best work. To aid them, we provide the finest of technical equipment. But often, even more helpful is the inspiration and personal assistance they gain here at Philco in working with men who have done so much for the advancement of Radio, Television, Refrigeration and Air-Conditioning.

### WRITE US TODAY

Qualified men not now engaged in work requiring their full talents, are invited to write us in detail as to their experience, education, family and draft status, and salary. Letters will be treated in strict confidence.

*Hiring subject to local W. M. C. rulings.*

WRITE TO MR. GEORGE DALE

# PHILCO

## CORPORATION

Philadelphia 34, Penna.



with a 4700-ohm resistor and an r-f choke in the power lead. To prevent coupling to the remainder of the tubes through the *B* supply, a decoupling filter is used (10000 ohms and 5 mfd). A 100-ohm resistor is inserted in the oscillator grid to prevent parasitics.

Full avc voltage is supplied to the 7B7E r-f amplifier control grid and suppressor grid and similar i-f elements. A portion of the avc bias is also fed to the converter signal grid. A delayed avc action (superimposed negative bias) is obtained from the negative 6-volt storage battery terminal which also supplies bias to the driver and Class *B* output stage. To accomplish this, the A+ terminal must be grounded.

There are several interesting features in the audio amplifier. Three stages are used to supply grid power to the class *B* stage and maintain sufficient audio gain. The 7C6 detector-first a-f is conventional, using a 3.3-megohm grid leak for bias. A tapped 2-megohm volume control in combination with a 6-megohm tone control provides for bass compensation and treble or bass reduction. The *B* supply to this stage is fed through an individual filter. The second audio, or driver stage, contains a 6G6EG pentode feeding a grid input transformer. Note the 2.2-megohm degeneration resistor from the driver plate to first audio plate. Note also that the cathode receives the entire voice coil voltage for feedback. Most receivers use only a part of this voltage. One reason for the large amount of degeneration used is the need for reducing distortion due to the Class *B* stage, particularly at low levels.

A pair of 49s (2 volt, 120-mil tubes) have parallel filament connection to provide equal bias and prevent coupling due to audio currents in the filament circuit. Note the .01-mfd grid-to-grid capacitor and .004-mfd plate-to-plate capacitor.

In the power unit, a synchronous self-rectifying vibrator supplies 140 volts *B*. A dual battery switch minimizes noise coupling due to the use of a common battery for vibrator, filament and bias supply. It does this by eliminating the IR voltage drop which occurs across the vibrator switch from the other circuits.

#### Philco 42-788

Fig. 3 shows a high gain, high fidelity 115-230 volt a-c receiver, with a t-r-f stage, two i-f stages and three audio stages. The tuning system with the separate bandsread iron core tuning system and the bandswitch, are similar to those in the foregoing battery set. A triple tuned i-f transformer



## INTEGRITY OF DESIGN

... a phrase that tells  
the story of a business

The phrase, *Integrity of Design*, has come to typify that "lengthened shadow" behind the business of creating Jackson Instruments. Like Topsy, it "just grewed" into our thinking and into our work. Today it constitutes our inspiration—and our constant challenge, permeating every phase of anything we do.

The very *naturalness* of this phrase, as applied to Jackson Instruments, has kept forcing itself forward—until *Integrity of Design* has become the hallmark of Jackson Instruments. It represents that unseen *plus* that comes from "hidden" care. It means that Jackson products are conceived, designed, developed and built—not for low price—but for *high performance*.

And that is why on all fronts Jackson Instruments are measuring up to the demanding tests of war. It is why, too, in the peacetime "tomorrow" to come they will emerge better than ever—from having had to meet the tests of today's raging world conflict.

All Jackson employees—a full 100%—are buying War Bonds on a payroll deduction plan. Let's ALL go all-out for Victory.




# JACKSON

*Fine Electrical Testing Instruments*

JACKSON ELECTRICAL INSTRUMENT COMPANY, DAYTON, OHIO

SERVICE, DECEMBER, 1943 • 13

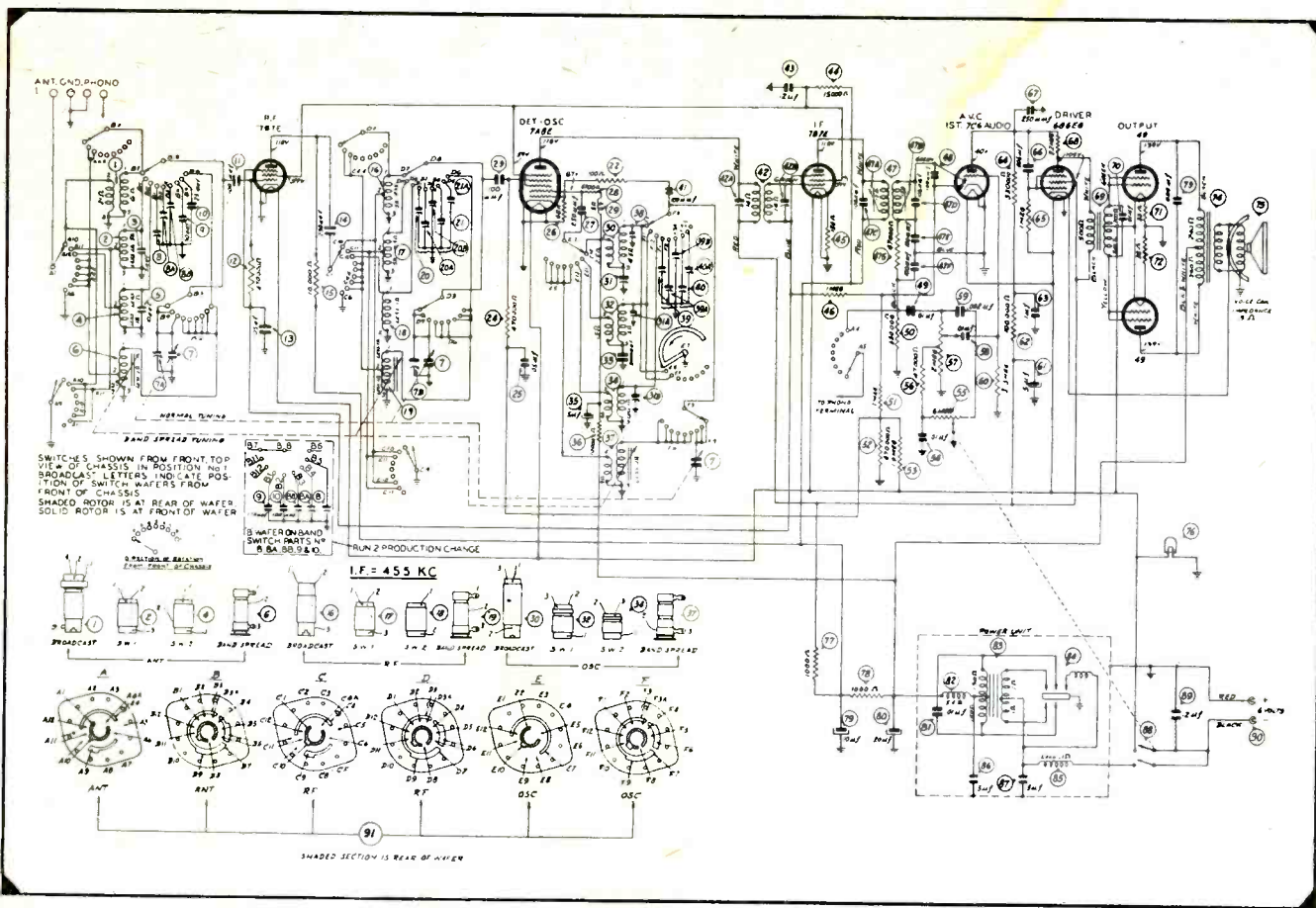

is used in the first i-f, a standard double-tuned unit in the second i-f and an iron core single-tuned unit in the detector. The first i-f cathode has a bias sensitivity control.


Fig. 3. Philco 42-788 high-fidelity receiver with iron-core tuning in the band-spread system.

Separate diodes are used for detection and avc, allowing more flexible avc, arranged in a delaying system. This is accomplished by impressing negative bias from the power unit voltage divider. Maximum avc is impressed upon the first i-f and r-f control grid. A smaller voltage is im-

Fig. 2. Philco 42-762 six-volt battery receiver with shunt-fed oscillator circuit.

pressed on the converter grid. A fixed negative bias is applied on the control and suppressor grid of the second i-f and on r-f and i-f suppressors and

(Continued on page 31)

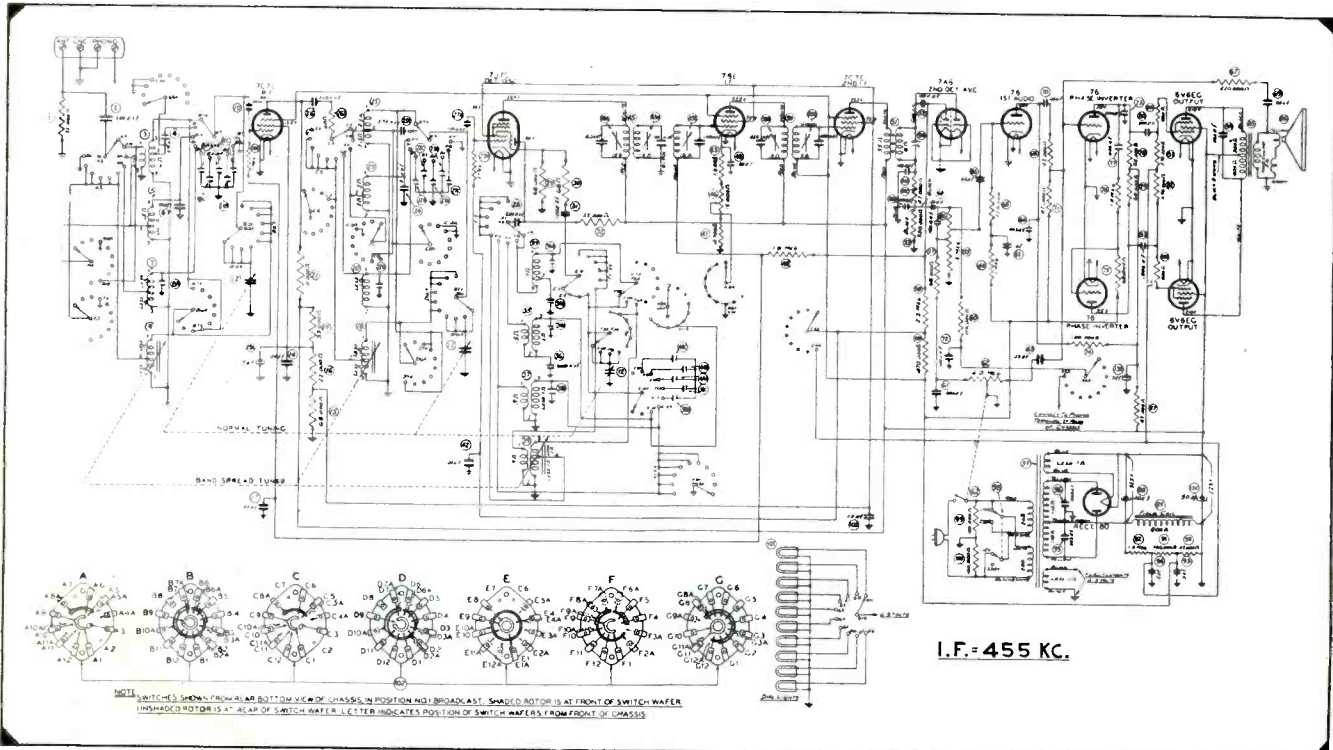



JANUARY, 1943 — DECEMBER, 1943

An asterisk preceding a listing indicates that a partial or complete circuit accompanies the text.

AMPLIFIERS

\*An Analysis of Low Power Phono and A-F Amplifiers. *By Alfred A. Ghivardi*..... July 5

\*Automatic Radio 265 A-C Phono Amplifier..... July 6

\*Microphone and Pick-up Pre-amplifiers (Wilcox-Gay Recorder Combination)..... March 25

\*Knight Expander-Compressor Adapter Unit..... Sept. 20

\*Knight 3-Tube Amplifier (for phono use)..... Sept. 18

\*Knight 5 Tube, 3-Stage Amplifier..... Sept. 18

\*Silvertone 2341 7-Tube Guitar Amplifier..... Aug. 16

\*Silvertone 7356 7-Tube Phono Amplifier..... Aug. 16

\*Silvertone 8922 Phono Amplifier..... Aug. 16

\*Silvertone 12856 Amplifier and Record Player..... Aug. 16

\*Silvertone 12860-12862 Phono Amplifier and Record Player..... Sept. 18

\*Silvertone 12870 or 7984 Phono Amplifier..... Aug. 16

ANTENNAE

\*Admiral C6 Receiver Using Loop Antenna..... May 22

\*Airline 14BR-523A..... Mar. 19

\*Airline 14WG-808 Receiver Using a Foil Type Antenna..... Apr. 15

\*An Unique Aligning Aid for Loop Receivers. *By John T. Willard*..... July 9

\*An Analysis of Radio-Frequency Input Circuits. *By Alfred A. Ghivardi*..... Apr. 5

\*Antenna Coupling Methods..... Apr. 5

\*Antenna-Oscillator Circuit Design..... Feb. 18

\*Arvin RE-90 Auto Radio Antenna Coupling..... July 16

\*Belmont 11AE2 4-band Receiver (with high-pass filter in antenna system)..... Mar. 20

\*Belmont 671B..... Mar. 19

\*Detroit 386 and 3861 (with high impedance capacity coupled antenna)..... July 13

Foil Antenna Uses..... July 25

\*Knight 6CH5 (with high or low antenna capacity coupling)..... June 17

\*Philco 42-350 (with low impedance loop, iron core auto-transformer antenna connection)..... June 18

\*Philco 42-365 (with rotatable low impedance loop, antenna auto-transformer)..... Mar. 23

\*Silvertone 7070 (with low impedance loops)..... Feb. 12

\*Stromberg Carlson 925 A-M/F-M (14-tube receiver with low impedance tapped loop antenna, and dipole for f-m)..... Nov. 16

AUTO RADIO

\*Arvin RE 90 Auto Radio..... July 16

\*Firestone Air Chief S-7350-1 Auto Radio..... Mar. 20

\*Knight 6CH5..... June 17

\*Philco Auto (AR10)..... Jan. 8

\*Reducing Auto-Radio Noise. *By Barry Kassin*..... June 25

\*The Repair of Auto Radio Control Cables. *By Burton V. Selle*..... July 18

AUTOMATIC TUNING

\*A Study of Automatic Tuning Devices. *By Alfred A. Ghivardi*..... May 5

BOOK REVIEWS

Basic Electricity for Communications. *(By William H. Timbie)*..... July 24

Radio Trouble Shooters Handbook. *(By Alfred A. Ghivardi)*..... July 24

What You Should Know About The Signal Corps. *(By Harry M. Davis)*..... July 25

CONDENSERS

Electrolytic Condenser Applications..... Jan. 13

\*Electrolytic and Paper Condenser Test Methods. *By T. R. Cunningham*..... Apr. 20

\*Faulty Compensator Condensers. Solving Electrolytic Condenser Replacement Problems. *B. M. E. Heller*..... Nov. 5

..... Jan. 13

CONVERTERS

\*RCA 164 U-H-F Converter..... July 10

CASE HISTORIES†

†This material is obtained from our readers and is representative of the actual experiences of the Service Man in the field.

Foil Antenna Uses..... July 25

Hum Cures..... July 25

\*Output Transformers as Filters. *By T. R. Cunningham*..... April 33

Philco Auto Radio AR10. *By A. Knickiner*..... Jan. 8

Philco Beam-of-Light Models. *By A. Knickiner*..... Jan. 8

Philco PT-2, 3, 10 and 12. *By A. Knickiner*..... Jan. 8

Philco PT-26 and 28. *By A. Knickiner*..... Jan. 8

Philco PT-87. *By A. Knickiner*..... Jan. 8

Philco PT-89. *By A. Knickiner*..... Jan. 8

Philco PT-91 to 96. *By A. Knickiner*..... Jan. 8

Philco 322. *By A. Knickiner*..... Jan. 8

Philco 350. *By A. Knickiner*..... Jan. 8

Philco 395. *By A. Knickiner*..... Jan. 8

Philco 350, 490, 1012, 1015, and 1016. *By A. Knickiner*..... Jan. 8

Philco 640. *By A. Knickiner*..... Jan. 8

Philco 1001, 1002, and 1003. *By A. Knickiner*..... Jan. 8

Philco 1002. *By A. Knickiner*..... Jan. 8

Philco Chrysler 1908. *By A. Knickiner*..... Jan. 9

Philco 40-185, 195, 41-255, 265, 287, 296. *By A. Knickiner*..... Jan. 8

RCA Victor 121. *By Willard Moody*..... Feb. 21

RCA RP-360. *By A. Knickiner*..... Jan. 20

Silvertone 4462. *By L. Roeshot*..... Sept. 31

Spartan 516. *By Willard Moody*..... Feb. 21

Stewart Warner 206FA, 386 and 358. *By M. Trakes*..... Mar. 25

Stewart Warner 208C. *By M. Trakes*..... Mar. 39

Volume Controls. *By T. R. Cunningham*..... Apr. 28

Westinghouse WR-336. *By Willard Moody*..... Feb. 21

Zenith 5R303. *By Willard Moody*..... Feb. 21

Zenith 8S463, 7S487 and 10S589. *By L. Roeshot*..... Sept. 31

CHARTS

An Analysis of Radio Interference Phenomena..... Apr. 25

\*Electrolytic Condenser Applications..... Jan. 13

\*Instrument Trouble Shooting Chart..... Sept. 12

"V" Line Parts..... Mar. 2, 33

COVER DIAGRAMS

\*A Five Channel Code Practice Oscillator (Silvertone 100)..... Aug. 29

\*Antenna-Oscillator Switching System (RCA Victor V-209)..... Feb. 18

\*A 32-Volt, 7 tube, two-band receiver (Wells Gardner 775)..... Apr. 27

\*Beat Frequency Oscillator (RCA 68-B)..... June 30

\*Pre-amplifier and Two-Speed Recorder Combination (Wilcox-Gay A-113-114-115)..... Mar. 25

\*RCA Audio Channel 170..... Oct. 32

\*Station Allocator (RCA 171)..... Dec. 27

\*Two-Side Record Player (RCA Victor RP-151)..... Jan. 8

\*Unique Detector Systems (Farnsworth CC-90, CK-91, 93)..... May 22

\*Zenith S6622 Wireless Record Player..... Sept. 26

Zenith 12A6..... Nov. 22

EDITORIALS

Aircraft Communications Servicing..... Apr. 2

Copper Wire Restrictions..... Sept. 2

Frequency Modulation..... Nov. 2

Lifting of Transfer of Sale Restrictions by Amendment to Limitation order L-265..... June 2

Limitation Order L-265..... May 2

Materials Shortage..... Oct. 2

Need For Test Instruments..... Mar. 2

P-A Systems..... Nov. 2

Paper Conservation..... Nov. 2

Receiver Maintenance..... Aug. 2

Remodeling and Conversion of Receivers..... Feb. 2

Service Man Deferment..... Jan. 2

Service Rationing..... Jan. 2

Taxicab Radio Service Needs..... Mar. 2

Television..... Oct. 2

Test Instrument Repairs..... Aug. 2

Training Programs for Repair Work..... Jan. 2

"V" Line Parts..... Apr. 2

"W" Line Parts..... Mar. 2

Vacuum Tube Distribution for Civilian Consumers..... May 2

Vacuum Tube Distribution..... July 2

Wartime Shortage Substitutions..... Sept. 2

ELECTRONIC APPLICATIONS

Application of Special Photo-controls. *By S. J. Murcek*..... Dec. 8

\*Audio Channelist (RCA No. 170—Part 1)..... Oct. 32

\*Audio Channelist (RCA 170—Part 2—Electronic Volt-Ohmmeter)..... Nov. 26

\*Audio Channelist (RCA 170—Part 3)..... Dec. 28

\*Controlled Rectifiers. *By S. J. Murcek*..... Oct. 9

Electronics and Ionics (Part 1). *By Dr. Joseph Slepian*..... Mar. 28

Electronics and Ionics (Part 2). *By Dr. Joseph Slepian*..... Apr. 36

\*Electronic Timer Troubles. *By S. J. Murcek*..... Sept. 7

\*Peculiarities of Electronic Circuits. *By S. J. Murcek*..... Nov. 8

\*Photocontrol Servicing. *By S. J. Murcek*..... June 12

\*Solving Photocontrol Application Problems. *By S. J. Murcek*..... Aug. 8

\*Square-Wave Generators. *By John Kane*..... Nov. 24

The Electron and Electronics. *By W. C. White*..... May 10

FEATURES

A "B" Eliminator Welder. *By Burton V. Selle and Corporal Hubert W. Meredith*..... Nov. 7

\*A Spare Parts Tester. *By Harry A. Leeper*..... Nov. 7

\*An All-Wave Oscillator. *By Frederick U. Dillon*..... Apr. 18

An asterisk preceding a listing indicates that a partial or complete circuit accompanies the text.

\*An Analysis of A-M and F-M Receivers. *By S. J. Thompson* June 5

\*An Analysis of Filament Switching in A-C/D-C Battery Portables. *By Barry Kassin* Mar. 12

An Analysis of Grid-Bias Circuits. *By Alfred A. Ghirardi* Dec. 5

\*An Analysis of Low Power Phono and A-F Amplifiers. *By Alfred A. Ghirardi* July 5

\*An Analysis of Radio-Frequency Input Circuits. *By Alfred A. Ghirardi* Apr. 5

An Analysis of Radio Interference Phenomena Apr. 25

\*An Unique Aligning Aid for Loop Receivers. *By John T. Willard* July 9

\*An U-H-F-Converter That Extends Test Instrument Range. *By William Carroll* July 10

\*A Versatile Power Supply. *By M. E. Heller* Oct. 7

\*A Study of Automatic Tuning Devices. *By Alfred A. Ghirardi* May 5

\*A Study of Vibrators (Part 1). *By M. E. Heller* Aug. 12

\*A Study of Vibrators (Part 2). *By M. E. Heller* Sept. 14

Design Characteristics of "V" Line Power and Audio Transformers and Reactors. Apr. 30

\*Applications of Special Photo Controls. *By S. J. Murcek* Dec. 8

\*Electrolytic and Paper Condenser Test Methods. *By T. R. Cunningham* Apr. 20

\*Electronic Timer Troubles. *By S. J. Murcek* Sept. 7

\*"First Aid" to Test Instruments (Part 1). *By Alfred A. Ghirardi* Aug. 5

\*"First Aid" to Test Instruments (Part 2). *By Alfred A. Ghirardi* Sept. 10

\*"First Aid" to Test Instruments (Part 3). *By Alfred A. Ghirardi* Oct. 13

Highlights of G. E. 90 Television Receiver. July 20

\*Instantaneous Sound Recorder. *By Alfred A. Ghirardi* Jan. 16

\*Peculiarities of Electronic Circuits. *By S. J. Murcek* Nov. 8

\*Power Transformer Checks. *By T. R. Cunningham* May 24

\*Practice Code Oscillators (Silvertone 100). Aug. 29

\*Repairing Speakers Today. *By Barry Kassin* July 22

\*Replacing Screen Grid Tubes with Variable-Mu Types. *By Frederick E. Bartholy* Mar. 5

\*Ser-Cuits. *By Henry Howard* Jan. 9

\*Ser-Cuits. *By Henry Howard* Feb. 10

\*Ser-Cuits. *By Henry Howard* Mar. 19

\*Ser-Cuits. *By Henry Howard* Apr. 12

\*Ser-Cuits. *By Henry Howard* May 14

\*Ser-Cuits. *By Henry Howard* June 16

\*Ser-Cuits. *By Henry Howard* July 12

\*Ser-Cuits. *By Henry Howard* Aug. 16

\*Ser-Cuits. *By Henry Howard* Sept. 18

\*Ser-Cuits. *By Henry Howard* Oct. 18

\*Ser-Cuits. *By Henry Howard* Nov. 16

\*Ser-Cuits. *By Henry Howard* Dec. 10

\*Servicing Bandswitches. *By Alfred A. Ghirardi* Feb. 5

Servicing Today (An Analysis of the State of the Industry) June 10

\*Solving Electrolytic Condenser Replacement Problems. *By M. E. Heller* Jan. 13

\*Solving Photocontrol Application Problems. *By S. J. Murcek* Aug. 8

\*Some Practical Wartime Service Expedients. *By Howard J. Fohr* May 12

\*Square-Wave Generators. *By John Kane* Nov. 24

Station Allocator (RCA 171) Dec. 27

The Audio Chanalyst (Part III) The Electron and Electronics. *By W. C. White* May 10

\*The Repair of Auto Radio Control Cables. *By Burton V. Selle* July 18

\*Wartime Servicing of I-F Transformers. *By Alfred A. Ghirardi* Nov. 5

FREQUENCY MODULATION

\*A-M and F-M Receiver Analysis Frequency Modulation (Editorial) June 5

\*Knight D 182-197 A-M/F-M Receiver Nov. 2

\*Knight D-360-361 A-M/F-M 16 Tube Receiver May 20

\*Philco 42-350 A-M/F-M Combination Receiver Oct. 18

\*Stromberg Carlson 925 A-M/F-M (14-tube; loop and dipole antennae) June 18

\*Zenith 12A6 (12-tube, 4-band A-M/F-M with automatic tuning on both a-m and f-m). Nov. 16

Nov. 22

HUM

An Analysis of Radio Interference Phenomena. Apr. 25

Hum Cures July 25

Hum Cure for Farnsworth AC55 *By Henry D. Morse* Nov. 14

Stewart Warner 206FA, 386 and 358 (intermittent hum) Mar. 25

INTERCOMMUNICATORS

Intercommunication Speeds War Industry. *By F. D. Wilson* Apr. 10

MOTORS

\*Instantaneous Sound Recorder. *By Alfred A. Ghirardi* Jan. 16

Wartime Servicing (Part 4). *By Alfred A. Ghirardi* July 20

Phono-Motor Lubrication (General Industries K, L, and 17) Oct. 22

Phono-Motor Lubrication (Magnavox, Universal Motor) Oct. 22

Phono-Motor Lubrication (Presto J5 Recorder) Oct. 22

Phono-Motor Lubrication (RCA RP-139A) Oct. 22

Phono-Motor Lubrication (RCA RP-145 and RP-152) Oct. 22

Phono-Motor Lubrication (RCA RP-152 Motor No. 91706-1) Oct. 22

Phono-Motor Lubrication (RCA RP-153) Oct. 24

Phono-Motor Lubrication (RCA RP-155) Oct. 24

Webster - Chicago Model 11 Phono-Motor Lubrication. Oct. 24

NOISE

An Analysis of Radio Interference Phenomena. Apr. 25

Auto Radio Noise Reduction. June 25

\*Eliminating Electric Sign Radio Interference. *By Frederick U. Dillon* Mar. 10

OSCILLATORS

\*An All-Wave Oscillator. *By Frederick U. Dillon* Apr. 18

\*An Analysis of A-M and F-M Receivers. *By S. J. Thompson* June 5

An Analysis of Grid-Bias Circuits. *By Alfred A. Ghirardi* Dec. 5

\*Practice Code Oscillators (Silvertone 100). Aug. 29

\*RCA 68-B Beat Frequency Oscillator June 30

\*RCA Victor V-209 (antenna-oscillator switching system) Feb. 18

\*Square-Wave Generators. *By John Kane* Nov. 24

\*Station Allocator (RCA 171) Dec. 27

PARTS

\*A Spare Parts Tester. *By Harry A. Leeper* Nov. 7

Copper Wire Restrictions (Editorial) Sept. 2

Electrolytic Condenser Replacement Jan. 13

\*Flashlight Cells for "C" Supply. Limitation Order L-265 (Editorial) Nov. 23

Limitation Order L-265 Amendment (Editorial) May 2

Materials Shortage (Editorial) June 2

\*Repairing Speakers Today. *By Barry Kassin* Oct. 2

\*The Repair of Auto Radio Control Cables. *By Burton V. Selle* July 22

Tone Control Replacements. July 18

\*Tube Substitutions. Oct. 22

"V" Line of Replacement Parts Approved. Nov. 23

"V" Line Parts (Editorial) Mar. 9

Wartime Shortage Substitutions (Editorial) Apr. 2

Sept. 2

PHOTOCELLS

Applications of Special Photocontrols. *By S. J. Murcek* Dec. 8

\*Photocontrol Application Troubles and Their Solution. Aug. 8

\*Photocontrol Servicing. June 12

PHONOGRAPHS, PICKUPS, RECORD PLAYERS, ETC.

\*Admiral N6, 6-Tube A-C Phono Radio Nov. 16

\*Airline 14WG-808 4-Band Receiver and Record Changer. Apr. 15

\*Firestone S7401-6 Record Player Sept. 20

\*Knight Expander - Compressor for Phono Use. Sept. 20

\*Record Player, (Silvertone 12860-12862) Sept. 18

\*Silvertone 12856 Record Player and Amplifier. Aug. 16

\*Silvertone 8922 Phono., Mixer, and Amplifier. Aug. 16

\*Zenith 5G484 Radio-Phono Portable Battery Combination. Oct. 18

\*Zenith S-6622 Record Player. Sept. 26

POWER SUPPLIES

\*A Study of Vibrators (Part 1). *By M. E. Heller* Aug. 12

\*A Study of Vibrators (Part 2). *By M. E. Heller* Sept. 14

\*A Versatile Power Supply. *By M. E. Heller* Oct. 7

\*Barrier Rectifier Units in A Full-Wave Bridge for Power Supplies Nov. 10

\*Belmont 7H31 (May be operated from any one of three power supplies) Mar. 23

\*DeWald 764 (Uses auto-transformer for power booster) Feb. 12

Design Characteristics of "V" Line Power and Audio Transformers and Reactors. Apr. 30

\*Flashlight Cells for "C" Supply. Nov. 23

\*Output Transformers as Filters. *By T. R. Cunningham* Apr. 33

\*Power Transformer Checks. *By T. R. Cunningham* May 24

PUSH-BUTTON TUNING

\*Admiral A10 Push-Button Tuning May 20

\*Arvin RE-90 Auto Radio Push-Button Tuning July 16

\*Firestone S-7350-1 Push-Button Control Mar. 20

\*Knight D-360-361 16 Tube A-M/F-M Oct. 13

\*RCA Victor V-225. *By Alfred A. Ghirardi* May 6

\*Setchell-Carlson 501 (Push-button, aviation, battery operated) Mar. 25



An asterisk preceding a listing indicates that a partial or complete circuit accompanies the text.

**RECORDING**

- \*Instantaneous Sound Recorder  
Wartime Servicing (Part 4).  
By *Alfred A. Ghivardi*.....
- \*Knight D174 Radio-Recorder.....
- \*Knight 390 8-tube Recorder-  
Radio.....
- \*RCA Victor VHR 212 Recorder  
Unit.....
- \*Silvertone 7072 Phono-Radio-  
Recorder.....
- \*Wilcox-Gay A-113-114-115 (Pre-  
amplifiers and two-speed re-  
corder combination).....

Jan. 16  
May 20  
June 18  
Apr. 24  
Feb. 10  
Mar. 25

**RECEIVERS**

- \*Airline 14BR-523A.....
- \*Airline 14 WG-575 A-C/D-C.....
- \*Airline 14WG-808 (4-band re-  
cord changer receiver, using  
a foil antenna).....
- \*Admiral A10 (push-button tun-  
ing receiver).....
- \*Admiral C6 Loop Receiver.....
- \*Admiral C7 (5-bands with 2-  
position selectivity).....
- \*Admiral N6, 6-Tube A-C Phono-  
Radio.....
- \*Admiral P6-XP6 (single band  
t-r-f).....
- \*Admiral P6XP6 Portable.....
- \*Arvin RE 90 Car Receiver.....
- \*Automatic Radio P77 A-C/D-C  
Portable.....
- \*Automatic Radio 202-206 Loop  
Receiver.....
- \*Automatic Radio 215-220 (broad-  
cast and shortwave).....
- \*Automatic Radio 245-351 Radio-  
Phono.....
- \*Belmont 6P11 A-C/D-C Port-  
able.....
- \*Belmont 7H31 (with three pow-  
er supply operation).....
- \*Belmont 11AE2 (multiple ganged  
permeability tuner, t-r-f, 4  
s-w bands).....
- \*Belmont 671B, 2-band Phono-  
Radio.....
- \*Clarion D110 Bandswitching  
Receiver.....
- \*Detrola 360 A-C/D-C Combina-  
tion.....
- \*Detrola 386 and 3861.....
- \*De Wald 675 Radio-Phono Re-  
ceiver.....
- De Wald 764 Radio-Phono (with  
auto-transformer power boost-  
er).....
- \*De Wald 814 (8-tube, 3-bands,  
with multi-tap power trans-  
former).....
- \*Farnsworth CT-60 Portable.....
- \*Farnsworth CT-63 and 64 Dual-  
band A-C/D-C.....
- \*Farnsworth CC-90, CK-91, 92  
and 93 Phono Radio.....
- \*Farnsworth CK-111 Phono-  
Radio.....
- \*Farnsworth DK-73 and 75.....
- \*Firestone S-7350-1.....
- G. E. 90 Radio and Television  
Receiver.....
- Hallcrafters Super Skyrider  
SX28.....
- \*Knight 6CH5 Auto Radio.....
- \*Knight D174 Radio-Recorder  
Receiver.....
- \*Knight D 182-197 A-M/F-M  
Receiver.....
- \*Knight D-155, 156, 157 Three-  
Way Portables.....
- \*Knight D-360-361, 16-Tube A-M  
/F-M Phono Receiver (with  
push-button tuning).....
- \*Knight 390 8-Tube Radio-Re-  
corder.....
- \*Pal Marine A-C/D-C Portable.....
- \*Philco 42-350 F-M/A-M Com-  
bination.....
- \*Philco 42-365.....
- \*Philco 42-762.....
- \*Philco 42-788.....
- \*Pilot T-186 A-C/D-C Portable.....
- \*RCA 26BP A-C/D-C Battery  
Portable.....
- \*RCA Victor 36X.....

Mar. 19  
June 16  
Apr. 15  
May 20  
May 22  
May 14  
Nov. 16  
June 16  
Nov. 16  
July 16  
Apr. 13  
Apr. 13  
Apr. 13  
Apr. 13  
Mar. 16  
Mar. 23  
Mar. 19  
Mar. 19  
May 18  
July 16  
July 13  
Feb. 12  
Feb. 12  
Mar. 23  
June 17  
June 18  
May 22  
May 21  
May 20  
Mar. 20  
July 20  
Dec. 10  
June 17  
May 20  
May 20  
July 16  
Oct. 18  
June 18  
Mar. 14  
June 18  
Mar. 23  
Dec. 14  
Dec. 14  
July 16  
Mar. 12  
Jan. 9

- \*RCA Victor 55X Speaker Con-  
versions.....
- \*RCA Victor CV-112X Power  
Supply Converter.....
- \*RCA Victor RP-151 Automatic  
Record Changer.....
- \*RCA Victor V-209 and V-210.....
- \*RCA Victor 211K.....
- \*RCA Victor V-225 (with im-  
pedance coupled r-f stages).....
- \*RCA Victor V-225 (electric  
push-button tuning).....
- \*Setchell-Carlson 501 (aviation  
push-button battery-operated  
receiver).....
- \*Silvertone 7070 (loop antenna  
selection by push buttons).....
- \*Silvertone 7072 (two-band, phono-  
radio-recorder).....
- \*Silvertone 7167 Phono-Radio  
Automatic Changer (2-band  
combination, with tuned pre-  
selection).....
- \*Stromberg Carlson 925 14-Tube  
A-M/F-M.....
- \*Traveler TB-512 A-C/D-C Port-  
able.....
- \*Ward Airline 12-Tube Receiver.....
- \*Westinghouse WR-12X4.....
- \*Westinghouse 12X14 (push-but-  
ton loop tuning).....
- \*Westinghouse WR-12X14 (elec-  
tric push-button tuning).....
- \*Westinghouse WR-42K11 5-  
Tube Radio Phono.....
- \*Westinghouse WR-62K1 and  
62K2 A-C/D-C.....
- \*Westinghouse WR-62K3 A-C/  
D-C Portable.....
- \*Westinghouse M-102 and M-111  
(with simple bandswitching  
and dual pri. power trans-  
former).....
- \*Zenith 5G01 Universal portable.....
- \*Zenith 5G484 Battery Phono  
and Portable Combination.....
- \*Zenith 6B14.....
- \*Zenith 7G605 S-W Portable  
(with band-spread tuning).....
- \*Zenith 12A6 12-tube, 4-Band  
A-M/F-M (with automatic  
tuning on both a-m and t-m).....

Jan. 10  
Jan. 9  
Jan. 8  
Feb. 18  
Feb. 14  
Feb. 14  
May 6  
Mar. 25  
Feb. 12  
Feb. 10  
Jan. 12  
Nov. 16  
Jan. 12  
May 14  
Jan. 12  
Feb. 13  
May 6  
Feb. 12  
Mar. 23  
Mar. 38  
Mar. 23  
Oct. 18  
Oct. 18  
July 13  
Oct. 21  
Nov. 22

**RECTIFIERS**

- \*A Study of Vibrators (Part 1).  
By *M. E. Heller*.....
- \*A Study of Vibrators (Part 2).  
By *M. E. Heller*.....
- \*A Versatile Power Supply. By  
*M. E. Heller*.....
- \*Barrier Rectifiers Units Used in  
A Full-Wave Bridge for  
Power Supplies.....
- \*Controlled Rectifiers. By *S. J.  
Murcek*.....
- \*Removing Oxide Film from Vi-  
brator Points.....

Aug. 12  
Sept. 14  
Oct. 7  
Nov. 10  
Oct. 8  
Oct. 31

**SERVICE HINTS AND KINKS**

- A "B" Eliminator Welder.....
- \*An I-F Wavetrap.....
- \*Faulty Compensator or Condens-  
ers.....
- \*Flashlight Cells for "C" Supply.  
Foil Antenna Uses.....
- G. E. 90 Servicing (danger  
precautions).....
- Hum Cures.....
- Hum Cure for Farnsworth AC55  
Instrument Trouble Shooting  
Chart.....
- \*An Unique Aligning Aid for  
Loop Receivers. By *John T.  
Willard*.....
- Lubrication of Phono Motors.....
- \*Improving Vibrator Operation.....
- \*Output Transformers as Filters.  
By *T. R. Cunningham*.....
- \*Power Transformer Checks. By  
*T. R. Cunningham*.....
- \*Repair of Open I-F Coils.....
- \*Replacing Sapphire in RCA Vic-  
tor 211K Receivers.....

Nov. 7  
Nov. 22  
Nov. 5  
Nov. 23  
Nov. 25  
June 19  
July 25  
Nov. 14  
Sept. 12  
July 9  
Oct. 22  
Oct. 24  
Apr. 33  
May 24  
Nov. 5  
Feb. 15

- \*Resistor for R-F Chokes. By  
*T. R. Cunningham*.....
- Slipping Dial Cords.....
- Stewart Warner 208C, Open  
Speaker Field Coil.....
- \*Stopping I-F Oscillations.....
- Tactical Radio Service Needs  
(Editorial).....
- \*Tube Substitutions.....
- \*Volume Controls. By *T. R.  
Cunningham*.....
- \*Volume Control Maintenance.  
By *Barry Kassir*.....

Nov. 28  
Apr. 31  
Mar. 39  
Nov. 6  
Mar. 2  
Nov. 23  
Apr. 28  
May 28

**SOUND**

- \*Are You Overlooking Industrial  
Sound? By *F. D. Wilson*.....
- Intercommunications in War In-  
dustries.....
- \*Phono and Audio Frequency  
Amplifier Analysis. By *Alfred  
A. Ghivardi*.....
- \*Repairing Speakers Today. By  
*Barry Kassir*.....
- Sound Recorder Wartime Ser-  
vicing.....

Feb. 8  
Apr. 10  
July 5  
July 22  
Jan. 16

**SPEAKERS**

- \*RCA Victor 1X, 12X, and 14X  
Speaker Conversions.....
- \*Repairing Speakers Today. By  
*Barry Kassir*.....

Jan. 10  
July 22

**TELEVISION**

- Highlights of G. E. 90 Tele-  
vision Receiver).....
- Television (Editorial).....

July 20  
Oct. 2

**TEST EQUIPMENT**

- \*All-Wave Test Oscillator. By  
*Frederic U. Dillon*.....
- \*A Spare Parts Tester. By *Har-  
ry A. Leeper*.....
- \*An U-H-F-Converter That Ex-  
tends Test Instrument Range.  
By *William Carroll*.....
- \*Audio Chanalyst (RCA No. 170-  
Part 1).....
- \*Audio Chanalyst (RCA 170,  
Part 2 — Electronic Volt-  
Ohmmeter).....
- \*Audio Chanalyst (RCA 170—  
Part 3).....
- \*Electrolytic and Paper Condens-  
er Test Methods. By *T. R.  
Cunningham*.....
- \*"First Aid" to Test Instruments.  
By *Alfred A. Ghivardi*.....
- \*"First Aid" to Test Instruments  
(Part 2). By *Alfred A.  
Ghivardi*.....
- \*"First Aid" to Test Instruments  
(Part 3). By *Alfred A.  
Ghivardi*.....
- \*Instrument Trouble Shooting  
Chart.....
- Station Allocator (RCA 171).....
- Test Instrument Repairs (Edi-  
torial).....

Apr. 18  
Nov. 7  
July 10  
Oct. 32  
Nov. 26  
Dec. 28  
Apr. 20  
Aug. 5  
Sept. 10  
Oct. 13  
Sept. 12  
Dec. 27  
Aug. 2

**TOPE COMPENSATION**

- \*Tone Compensation for Pickup  
Circuits.....
- \*Tone Control Replacements.....

Feb. 16  
Oct. 22

**TRANSFORMERS**

- Design Characteristics of "V"  
Line Power and Audio Trans-  
formers and Reactors.....
- \*Power Transformer Checks. By  
*T. R. Cunningham*.....

Apr. 30  
May 24

An asterisk preceding a listing indicates that a partial or complete circuit accompanies the text.

**TUBES**

*An Analysis of Grid-Bias Circuits. <i>By Alfred A. Ghirardi</i>	Dec.	5
*Characteristics of Two-Element Rectifier Tubes	Nov.	12
*Controlled Rectifiers, Using Thyatron Tubes	Oct.	8

*Tube Substitutions	Nov.	23
Vacuum Tube Distribution (Editorial)	July	2
Vacuum Tube Distribution for Civilian Consumers (Editorial)	May	2
*Replacing Screen-Grid Tubes with Variable-Mu Types. <i>By Frederick E. Bartholy</i>	Mar.	5

**TUNING INDICATORS; TUNING MECHANISMS**

*Admiral A10 Push-button Tuning	May	20
*A Study of Automatic Tuning Devices. <i>By Alfred A. Ghirardi</i>	May	5
*Firestone S-7350-1 (with rotary switch and magnetic plunger)	May	8
*RCA Victor V-225. <i>By Alfred A. Ghirardi</i>	May	6
*Silvertone 7072 (electric switching)	May	5
Slipping Dial Cords	Apr.	33
*Zenith 12A6 12-tube, 4-Band A-M/F-M (full automatic tuning on both a-m and f-m)	Nov.	22

**VIBRATORS**

*A Study of Vibrators (Part 1). <i>By M. E. Heller</i>	Aug.	12
*A Study of Vibrators (Part 2). <i>By M. E. Heller</i>	Sept.	14
*Improving Vibrator Operation	Oct.	24

**VOLUME CONTROLS**

*The Maintenance of Volume Controls. <i>By Barry Kassin</i>	May	28
*Volume Controls. <i>By T. R. Cunningham</i>	Apr.	28

**WARTIME SERVICING**

Aircraft Communications Servicing (Editorial)	Apr.	2
An Analysis of Grid-Bias Circuits. <i>By Alfred A. Ghirardi</i>	Dec.	5
Copper Wire Restrictions (Editorial)	Sept.	2
Hum Cure for Farnsworth AC55	Nov.	14
Instantaneous Sound Recorder Wartime Servicing (Part 4). <i>By Alfred A. Ghirardi</i>	Jan.	16
Materials Shortage (Editorial)	Oct.	2
Paper Conservation (Editorial)	Nov.	2
P.A. Systems (Editorial)	Nov.	2
*Photocontrol Servicing. <i>By S. J. Murcek</i>	June	12
Receiver Maintenance (Editorial)	Aug.	2
*Repairing Speakers Today. <i>By Barry Kassin</i>	July	22
*Resistor for R-F Chokes	Nov.	28
*Servicing Bandswitches. <i>By Alfred A. Ghirardi</i>	Feb.	5
Service Man Deferment (Editorial)	Jan.	2
Service Men Declared Essential in Deferment Ruling. <i>By Elliott Marshall</i>	Jan.	5
Service Rationing (Editorial)	Jan.	2
Servicing Helms. <i>By Barry Kassin</i>	Oct.	22
Servicing Today (An Analysis of the State of the Industry)	June	10
*Some Practical Wartime Service Expedients. <i>By Howard J. Folt</i>	May	12
Taxicab Radio Service Needs (Editorial)	Mar.	2
Test Instrument Repairs (Editorial)	Aug.	2
*The Repair of Auto Radio Control Cables. <i>By Burton V. Selle</i>	July	18
Training Programs for Repair Work (Editorial)	Jan.	2
*Tube Substitutions	Nov.	23
"V" Line of Replacements Parts Approved	Mar.	9
"V" Line Parts (Editorial)	Apr.	2
*Wartime Servicing of I-F Transformers. <i>By Alfred A. Ghirardi</i>	Nov.	5
Wartime Shortage Substitutions (Editorial)	Sept.	2

"THE HELP SITUATION" by Lariat



HERE'S HELP THAT'S "Hep!"

**RIDER MANUALS (Thirteen Volumes)**  
 Volumes XIII to VII.....\$11.00 each volume  
 Volumes VI to III..... 8.25 each volume  
 Abridged Manuals I to V (one volume)...\$12.50  
 Automatic Record Changers and Recorders, 6.00

**OTHER RIDER BOOKS YOU NEED**

The Cathode Ray Tube at Work Accepted authority on subject	\$3.00
Frequency Modulation Gives principles of FM radio	1.50
Servicing by Signal Tracing Basic method of radio servicing	3.00
The Meter at Work An elementary text on meters	1.50
The Oscillator at Work How to use, test and repair	2.00
Vacuum Tube Voltmeters Both theory and practice	2.00
Automatic Frequency Control Systems —also automatic tuning systems	1.25
A-C Calculation Charts Two to five times as fast as slide rule. More fool-proof, 160 on 2 colors	7.50
Hour-A-Day-with-Rider Series— On "Alternating Currents in Radio Receivers"— On "Resonance & Alignment"—On "Automatic Volume Control"—On "D-C Voltage Distribution"	90¢ each

**JOHN F. RIDER PUBLISHER, INC.**  
 404 Fourth Avenue (16) N. Y. City  
 Export Division: Roeco-International Electric Corp.  
 13 E. 40th Street, New York City Cable: ARI-LAB

Tired of training help that's either too young or too old to know the latest in high-speed servicing techniques? — What radio serviceman isn't?

That's why more and more of them are turning to *Rider Manuals* and *Rider Books* for up-to-the-minute information to speed the diagnosis of faulty radio receivers.—And to help in turning out the huge volume of work they have today. You can depend upon the help that *Rider Books* offer you.

Every book listed at the right should be in your library or on your service bench today. Available at all good radio jobbers throughout the world these *Rider Publications* will be augmented during 1944 by *Rider Manual Volume XIV*. Exact date of publication will be announced shortly.

Check the list at the right carefully and place your order, today!

**RIDER MANUALS**  
 GIVE YOU THE HELP YOU NEED!







# What happens when a Shadow meets an RCA Electron Tube

**J**UST by itself, it's hard enough to measure to an accuracy of 1/10,000 of an inch. But on a production line, where tens of thousands of wires have to measure up to this accuracy, it's next to impossible—unless you want to spend more time measuring than producing.

However, with a simple electronic device, built around an RCA Electron Tube, thousands of small lead wires for radio tubes are now being checked for such accuracy at the rate of 5 to 8 a minute!

How is it done? Like this . . .

The wire passes before a light. As it does, it casts an enlarged shadow on a sensitive phototube whose output is meas-

ured on a meter. If the wire is 1/10,000 of an inch off, the difference is recorded on the meter and the offending wire can be rejected. If desired, the wire can be rotated to measure out-of-roundness.

This is electronics — the so-called "dream science" of tomorrow—in action today at RCA!

Many of you Distributors and Servicemen can remember when radio, too, was just a "dream." But *you* helped that dream "come true."

Much of the electronic equipment you may be helping to sell, install, or service tomorrow will be built around tubes, circuits, and parts already familiar to you

from your radio days! *Yes, the magic brain of all electronic equipment is a tube...and the fountain-head of modern tube development is RCA!*

#### TUNE IN "WHAT'S NEW?"

RCA's great new show, Saturday nights, 7 to 8, Eastern War Time, Blue Network.



This machine, while used at RCA to measure the diameter of tungsten wires by an electronic method, embodies a basic principle for measuring any critical dimension of any component that can be made to cast a shadow directly proportional to the dimension to be checked.



## RADIO CORPORATION OF AMERICA





# CINAUDAGRAPH SPEAKERS

*— bring 'em in*



**Cinaudagraph Speakers, Inc.**

3911 S. Michigan Ave., Chicago

*"No Finer Speaker Made in all the World"*



## Sound Control

★ For distortionless control of loudspeaker volume, Clarostat offers the Series CIB constant-impedance output attenuator. Constant input and output impedance because of compensated ladder-type resistance network. Individual loudspeaker volume can be controlled in an extensive sound system, without upsetting the general setup. Rated at 10 watts. ★ Ask your Clarostat jobber about Clarostat sound-system controls. ★ Or write us.



## MUELLER



## CLIPS

*For Quick Temporary Connections*

- Made in 10 sizes—from the tiny wee-pee-wee to the 300 ampere Big Brute.
- Offered in both steel and solid copper.
- Red and black rubber insulators to fit each size.
- A complete line with

### A CLIP FOR EVERY PURPOSE

Stock deliveries on practically all items.

Send for free samples and catalog 810

**Mueller Electric Co.**

1565 E. 31st St. - Cleveland, Ohio


## GRID BIAS

(Continued from page 7)



what critical in value for best results. Fig. 8(b) shows a more versatile circuit using two diodes in which a larger avc bias resistor may be used with a gain in bias voltage produced. Fig. 8(c) uses this principle for a detector overload circuit in inexpensive t-r-f receivers. When the detector is overloaded with a strong signal, avc is applied to the r-f stage which limits the blasting that would otherwise occur.

Fig. 9 illustrates a grid leak self-adjusting bias circuit that is often used in high-mu first audio stages with 6SQ7, 6SF5, or similar tubes, and can be used wherever low input voltages (approximately 1 volt) are handled. Usually, a grid-leak bias resistor  $R$  of 10 megohms is employed, but it may be any value between about 5 to 15 megohms. This method eliminates troublesome hum which often appears in the conventional cathode-resistor bias system of Fig. 3.

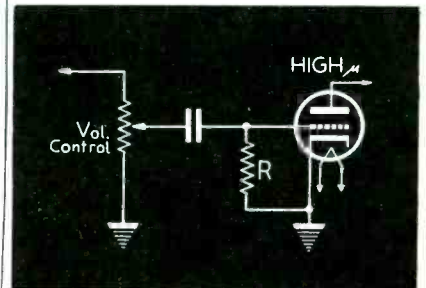
There are still some t-r-f sets to be serviced which use  $C$ -bias volume control in the first r-f stage as shown in Fig. 10(a). If the control obtained



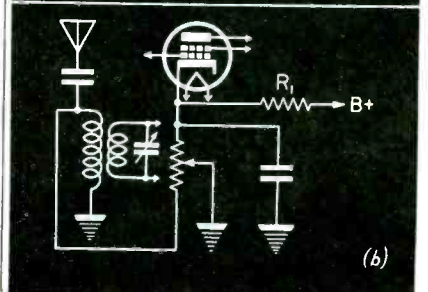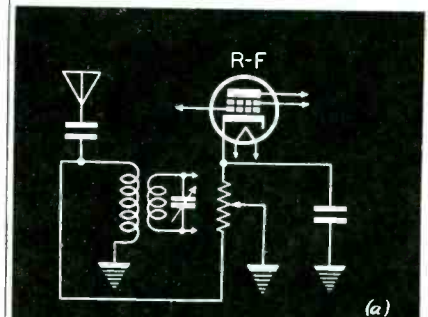
Figs. 9 (above) and 10 (below). Fig. 9, grid-leak type self-adjusting bias circuit. Fig. 10, C-bias volume control circuits.





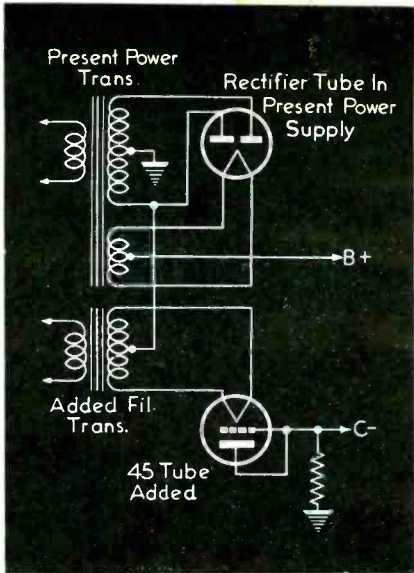

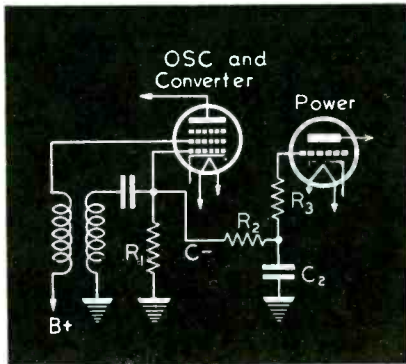Figs. 11 (top) and 12 (below). Fig. 11, an auxiliary C-bias voltage source where high C bias is required. Fig. 12, a "trick" bias circuit that conserves B voltage.



is inadequate (insufficient attenuation), more bias can be obtained with the circuit of Fig. 10(b) where a resistor,  $R_1$ , is connected from cathode to  $B+$  to bleed some steady current through the control, independent of the tube's plate and screen current.

High-power equipment often requires large negative voltages for control devices as well as for C bias. By simply adding another rectifier tube to the standard power supply as shown in Fig. 11, these voltages may be obtained. The use of a type 45 tube with grid tied to plate produces a low-impedance negative bias voltage supply.

A trick circuit which conserves valuable B voltage in a portable receiver is shown in Fig. 12. The source of negative bias voltage is the oscillator grid where the potential exists as rectified r-f, developed across  $R_1$ , the oscillator grid leak. This voltage is filtered by  $R_2$ ,  $C_2$  and  $R_3$  and is applied to the power tube grid as pure d-c bias. One of the troubles encountered is the fact that the oscillator grid voltage is somewhat dependent upon the frequency, so the bias is subject to a certain amount of change as the set is tuned. With care, this change may be minimized.

# These 2 GHIRARDI BOOKS

## Will help you to Diagnose, Locate and Repair Receiver Troubles

### EASIER • BETTER and FASTER



Price only \$5 each

#### Ghirardi's Famous MODERN RADIO SERVICING

Ghirardi's MODERN RADIO SERVICING is a 1300-page, hard-hitting, intensely practical course in radio service work that is literally worth its weight in gold to both beginners and experienced servicemen alike. It answers your questions—shows you short cuts—explains the theory and operation of instruments—shows how to use your time to best advantage—helps solve your daily servicing problems as they arise.

#### A THOROUGH SERVICE COURSE

In brief, MODERN RADIO SERVICING is the only single, inexpensive book giving a thorough explanation of the workings of all Test Instruments; Receiver Troubleshooting Procedure; Circuit Analysis; Testing and Repair of Component Parts; Installation, Adjustments, Maintenance, etc. It clearly explains HOW to do everything and explains WHY!

"It contains enough servicing information for six books and is written in an interesting, easy-to-understand manner," writes T/Sgt. Charles Leuthold of the Army. To which William Hermann, serviceman of New York adds: "The best book on servicing ever written. Improved my servicing knowledge 75% after reading it."

The 1300 pages of this big volume include 706 illustrations, 720 self-testing review questions to make study easy—and the book covers a total of 766 different servicing topics. Sold singly for only \$5 (\$5.50 foreign)—OR save money by buying it in conjunction with Ghirardi's TROUBLE SHOOTER'S HANDBOOK. See special Combination Offer below.

FEATURED BY LEADING RADIO JOBBERS!

### 5-DAY MONEY BACK GUARANTEE

RADIO & TECHNICAL Division of MURRAY HILL BOOKS, INC.  
Dept. S-123  
232 Madison Ave., New York 16, N. Y.


Enclosed find \$— for books checked, or  send C.O.D. for this amount plus postage (sent C.O.D. in U.S.A. only). If not fully satisfactory, I may return the books within 5 days and receive my money back.

- SPECIAL MONEY-SAVING COMBINATION—Both books \$9.50 (\$10.50 foreign)
- RADIO TROUBLESHOOTER'S HANDBOOK \$5 (\$5.50 foreign)
- MODERN RADIO SERVICING \$5 (\$5.50 foreign)

Name.....

Address.....

City (and Dist. No.).....State.....

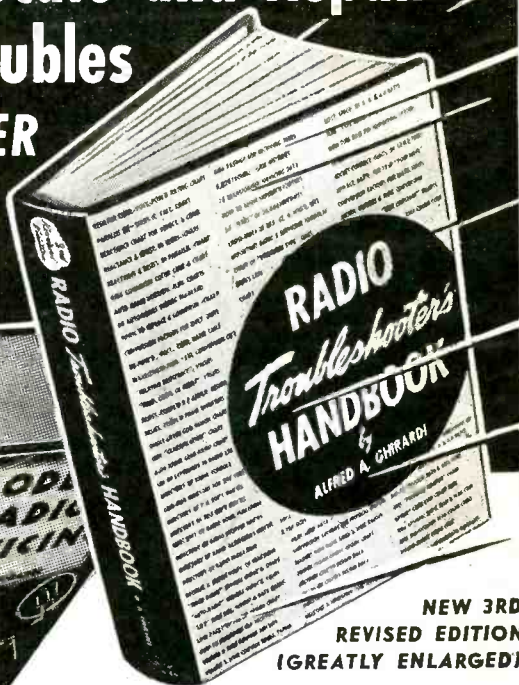

NEW 3RD REVISED EDITION (GREATLY ENLARGED)

**RADIO TROUBLESHOOTER'S HANDBOOK**  
Don't waste time in the complicated troubleshooting of every receiver! First look up the model No. in the big "Trouble" Case History section of this new Handbook. Nine times out of ten, you'll find exactly the clue you need to repair it—often without any testing at all!

Don't let work pile up while you fuss around for a hard-to-get replacement tube or part. Turn to the big Data sections of the Handbook—and you may be surprised to learn that some easy-to-get component can be substituted—and this big Handbook tells you how to do it!

#### HOW TO TEST A RADIO IN 2 MINUTES OR LESS!

The Handbook isn't a "study book." You simply refer to it when you want specific servicing information about a specific set or job. Its data will pay for itself in time saved the very first time you use it!

And remember! This 3rd Edition is completely revised, over 40% larger, and contains NINE MORE SECTIONS OF VITAL NEW MATERIAL. It includes the trouble symptom and remedy "Case Histories" of over 4,800 receivers and automatic record changers! 50-page tabulation of IF peaks of 20,173 superhets and alignment data for practically every superhet known! 60 pages of auto radio charts and data! Covers 1,250 portable radio models! 20-page tube chart! Loads of other information covering manufacturer's names, data on ballasts, pilot lamps, tube testing magnet wire, tuning coils, grid bias resistors, condensers, transformers, parallel and series networks, decibels, volume and tone controls, filters, conversion factors, reactance charts—plus a wealth of graphs, charts, and other data that will help you do every job better—AND A LOT FASTER!

RADIO TROUBLESHOOTER'S HANDBOOK has 710 big, manual-size pages. It's yours for only \$5 complete (\$5.50 foreign)—and you buy it on our unreserved 5-DAY MONEY-BACK GUARANTEE. You cannot lose!

#### SPECIAL MONEY-SAVING COMBINATION OFFER


Both books for only \$9.50 (\$10.50 foreign).

A total of Over 2000 Pages of the world's finest service data!

MAIL THIS NOW!



# FLEXIBLE

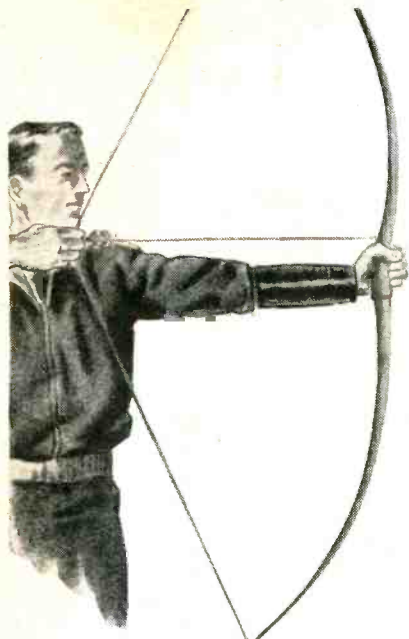

**FLEXIBILITY** in application is one of the many features of the new General Electric SERVICE TESTING EQUIPMENT. You are given a wide choice of portable, compact apparatus—direct from the famous G-E electronic laboratories—designed for accurate, rapid maintenance and testing work by radio service men, service dealers and others.

The units include: G-E unimeters, tube checkers, audio oscillators, oscilloscopes, condenser resistance bridges, signal generators and other utility instruments for testing radio electronic circuits and component parts.

These sturdy, dependable units are now in production principally for the Armed Forces. But they may be purchased on a priority if you are engaged in war work. After the war, of course, the full line will again be available to everybody. . . . *Electronics Department, General Electric, Schenectady, N. Y.*

**FREE CATALOG**



**ELECTRONICS DEPARTMENT  
GENERAL ELECTRIC CO.**  
Schenectady, N. Y.

Please send, without obligation to me, the General Electric Testing Instrument Catalog, S-1 (loose-leaf), for my information and files.

Name \_\_\_\_\_  
Address \_\_\_\_\_  
Company \_\_\_\_\_

**GENERAL ELECTRIC**  
Electronic Measuring Instruments

## PHOTOCONTROLS

(Continued from page 9)

register zone width potentiometer 15 slider to a voltage level between that of the pentode shield grid and cathode. Since the plate of the pentode is negative with respect to the shield grid, the grid of the triode inverter is negative with respect to its cathode. The voltage across its plate loading resistor 21 therefore is zero. Thus, the control grid of the thyatron 24 is at the voltage level of the positive terminal of the d-c voltage divider, and positive with respect to its cathode. Now, thyatron 24 conducts.

The resulting current flow is through one-half of the differential field winding 33 in the series register motor 32. It is then directed through the motor armature and the anode supply winding 31 on the power transformer core, causing the motor armature to rotate. The rotation of the motor shaft is in such a direction that the paper strip edge guides move the paper edge 11 into the path of the light beam between the optical lenses 8 and 9.

As the motor shaft continues to rotate, due to continued conduction by the thyatron 24, the paper edge obstructs an increasing proportion of the

light beam, thus reducing the phototube conductivity.


Eventually, the positive bias on the pentode control grid decreases as a result, to a level wherein the grid of the inverter triode is near zero voltage level. The triode begins to conduct in limited amount, the resulting voltage drop across the triode plate loading resistor 21 thus being increased. This places the plate of the triode, and therefore the grid of thyatron 24, negative with respect to the pentode shield grid, this electrode then being negative with respect to the cathode. Thyatron 24 now no longer conducts and the shaft of the register control motor ceases to rotate.

At this juncture, the edge of the paper strip obstructs perhaps half the light beam area, which places the paper edge near the center of the phototube objective lens, 9.


If, by reason of irregularity in the warp of the paper strip, the paper edge should continue to move across the light beam in such a manner as to obstruct a greater portion of the light beam, the phototube conductivity decreases to a lower value.

The current flow through the register motor field is in a direction opposite to that prevailing when thyatron 24 conducts. Therefore, the shaft of

Fig. 4. A dynamic type photocontrol circuit. This is a pinhole detector used to detect and eliminate sections of steel strip which are perforated by small holes.

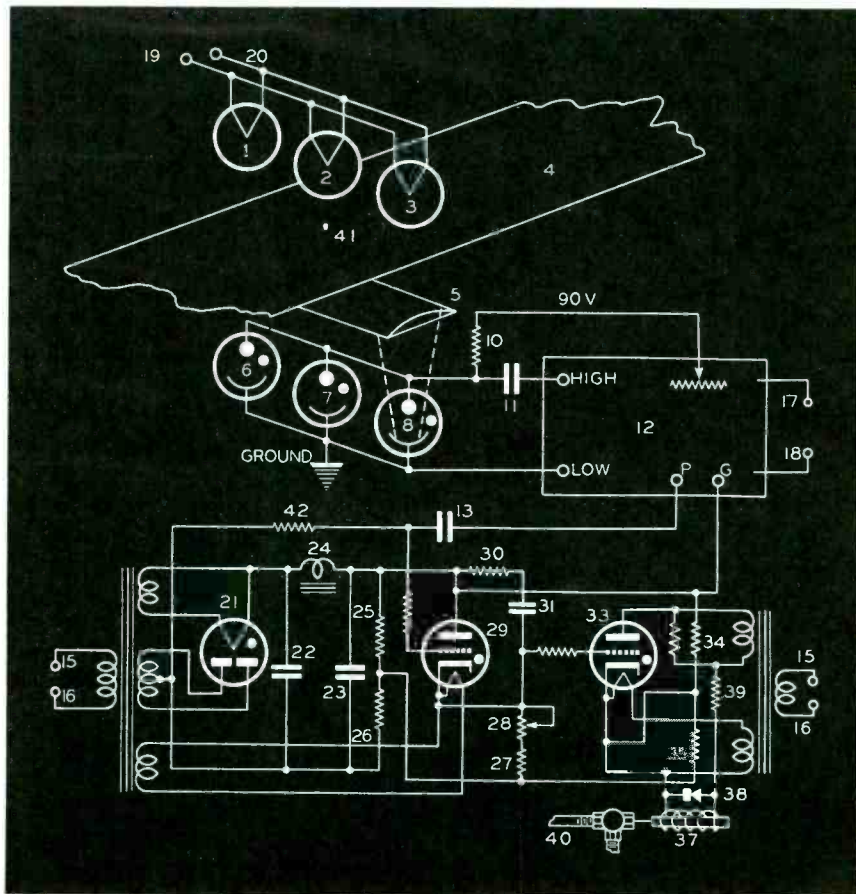



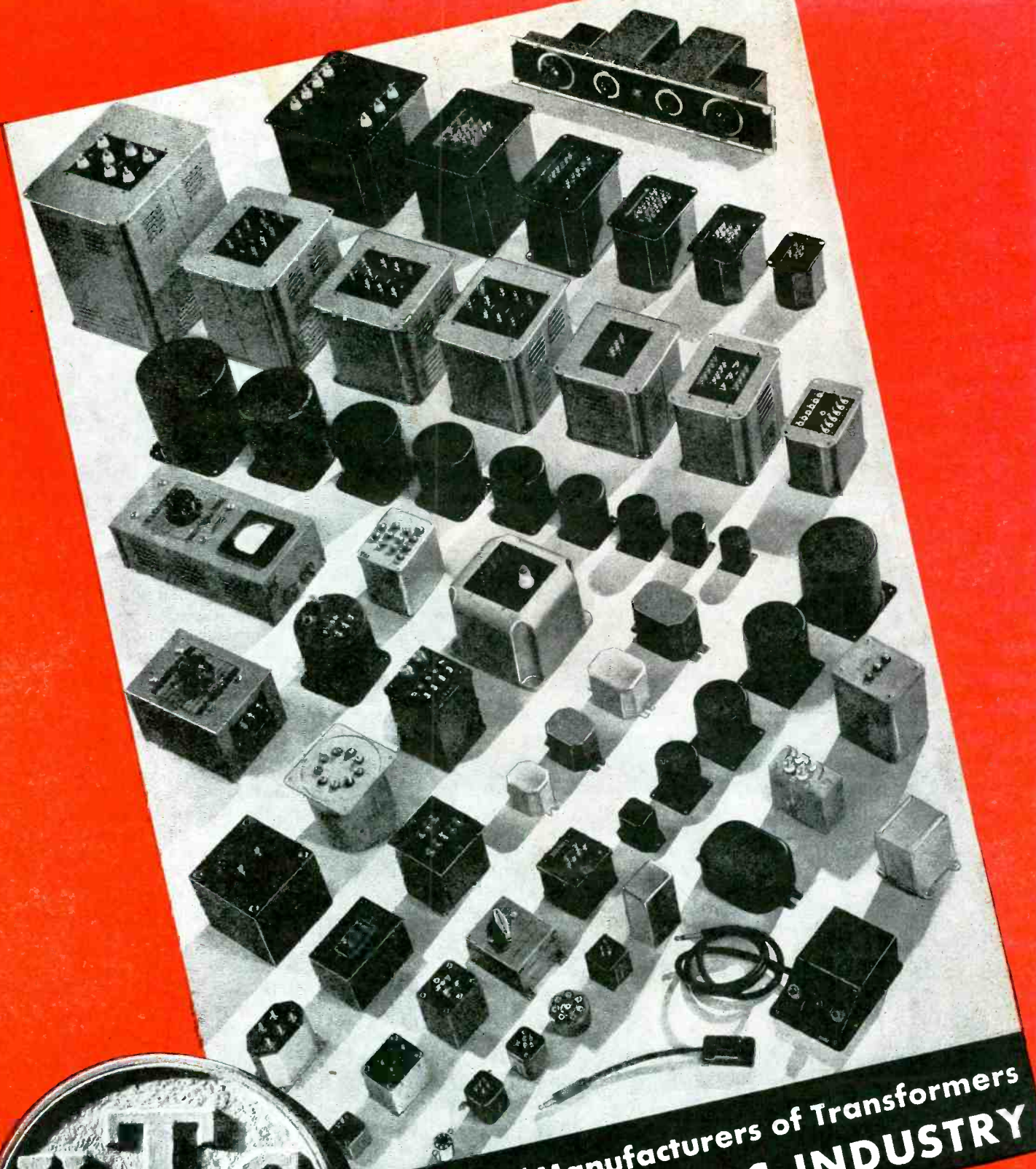

Foremost Manufacturers of Transformers  
to the **ELECTRONIC INDUSTRY**

*United Transformer Co.*

150 VARICK STREET • NEW YORK 13, N. Y.  
EXPORT DIVISION: 13 EAST 40th STREET, NEW YORK 16, N. Y., CABLES: "ARLAB"



**H**allicrafters has the honor of being the first exclusive radio manufacturer to receive the Army-Navy Production Award for the third time! This third award adds a second White Star to Hallicrafters' flag—and stands as a symbol of their great contribution to the cause of freedom.



**hallicrafters**

The World's Largest Exclusive Manufacturer of Short Wave Radio Communications Equipment

the register motor now rotates in a direction opposite to that caused by the conduction of the rectifier thyatron. This causes the paper strip to be drawn in such a direction as to move the strip edge out of the light beam.

Meanwhile, the inverter grid of the inverter triode is positive with respect to its cathode, the plate of this tube now swinging negative with respect to the shield grid of pentode 18. Therefore, the thyatron does not conduct at this time.

Continuing increase in the conductivity of the phototube through the gradual withdrawal of the paper edge out of the light beam finally causes the voltage between the grid and cathode of the pentode to swing to approximately zero volts. This causes the pentode plate current to rise to a slight degree, causing the plate to become slightly negative with respect to its shield grid. Thyatron 23 then is dark, its grid now negative with respect to its cathode. Here, the register motor shaft ceases to rotate, leaving the paper edge again near the center of the light beam.

It is obvious, from the discussion of Fig. 3, that the paper edge is automatically maintained in such a position that it is near the center of the light beam at all times, since a small change in the illumination incident on the cathode of phototube 10 is sufficient to cause operation of the register correction motor. The significance of this operation is evident when it is known that the speed of the paper strip thus held in register approaches 2,000 feet per minute.

Register position, or the position in the light beam where the paper edge comes to rest, is determined by the position of the slider arm of the position control potentiometer 14.


Zone width potentiometer 15 functions to increase or decrease the static positive bias on the triode cathode, thus determining the pentode plate current at which the triode will conduct, by reason of the variable voltage drop across resistor 35. Capacitors 13 and 17 function to bypass undesired voltage ripples, due to electromagnetic modulation of the sensitive phototube circuits.

The circuit of a special photocontrol in the dynamic group is shown in Fig. 4. This device is known as a pinhole detector, being utilized to detect and eliminate sections of steel strip which are perforated by small holes. Such steel strip is a raw material in the manufacture of metal food containers. Obviously, perforated material would result in a leaky container.

In the diagram of Fig. 4, the strip is shown passing under a battery of reflector type lamps, 1, 2 and 3. These

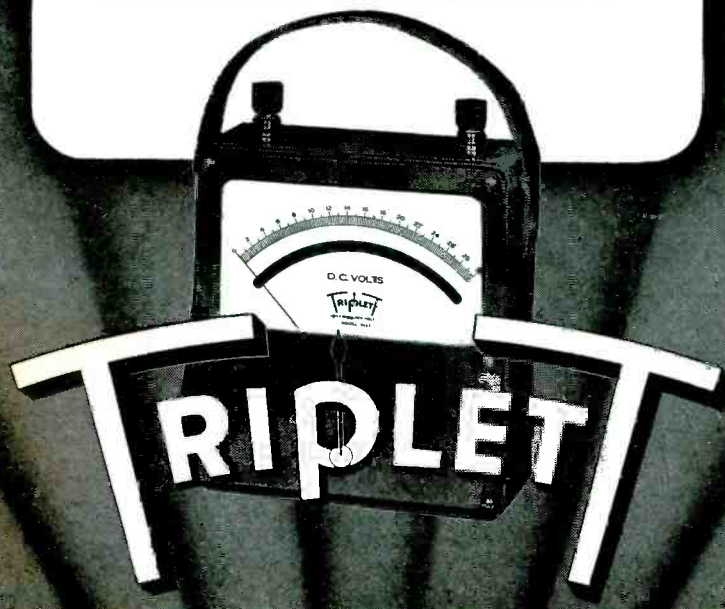**MODEL 625—0-30 D.C. VOLT METER**

This is one of today's most popular portables. The new design has a hinged dial cover for added protection; insulated molded case and hand calibrated mirror scale 4.58" in length. Furnished to an accuracy within one-half of 1%. THE TRIPLETT ELECTRICAL INSTRUMENT COMPANY, BLUFFTON, O.





are so arranged that a continuous path of light bathes the moving strip surface. Terminals 19 and 20, connected with the a-c power supply line, furnish the power required by each lamp.

The photoelectric camera, consisting of a semi-cylindrical lens 5 and the phototubes 6, 7 and 8, is suspended beneath the moving strip so that the light beam from one of the lamps above the sheet will strike the lens should a perforation be present.

A conventional high gain amplifier 12, is utilized to increase the small voltage developed across the phototubes to a magnitude suitable for the manipulation of the thyatron tube grid circuits. To accomplish this operation, it is necessary to tap the d-c voltage divider within the amplifier at a point approximately 90 volts positive with respect to ground or negative d-c potential level. This voltage is impressed across the phototubes in series with the phototube loading resistor 10. Dynamic coupling between the camera and the high gain amplifier is effected by means of capacitor 11.

As the strip moves over the electronic camera lens, often at rates of speed approaching 2,500 feet per minute, a perforation in the strip will cause one of the phototubes to be illuminated, momentarily. The phototube resistance decreases momentarily as a result, the voltage across the bank of phototubes thus being decreased similarly. Capacitor 11 then discharges through the phototubes, quickly recharging in series with resistance 10 when the voltage across the phototubes returns to normal.

It is obvious, then, the *HIGH* input terminal of the amplifier is momentarily impulsed in negative polarity with respect to the negative or ground input terminal marked *LOW*, in Fig. 4.

The width of the phototube cathode, in each case, is one inch. The strip travels at a nominal rate of 1,800 feet per minute, or 30 feet per second. The time elapsed during which the strip moves a distance of one inch is 0.002783 second. Since the photocathode width is one inch, then this time is the duration of the phototube voltage impulse for the detection of a small hole. This corresponds to a frequency of


1

or 357 cps.

.002783


Associated with the thyatron tube 29 is a delay timer, to which is coupled a high gain amplifier output. This delay timer obtains its d-c operating power from the power supply consisting of gaseous rectifier 21, filter capacitors 22 and 23, and filter reactor 24. Voltage divider (25, 26) subdivides the d-c output voltage, ap-

**TODAY in WAR . . . TOMORROW in PEACE**



**BRACH**

**MARINE ANTENNAS and MOUNTS**

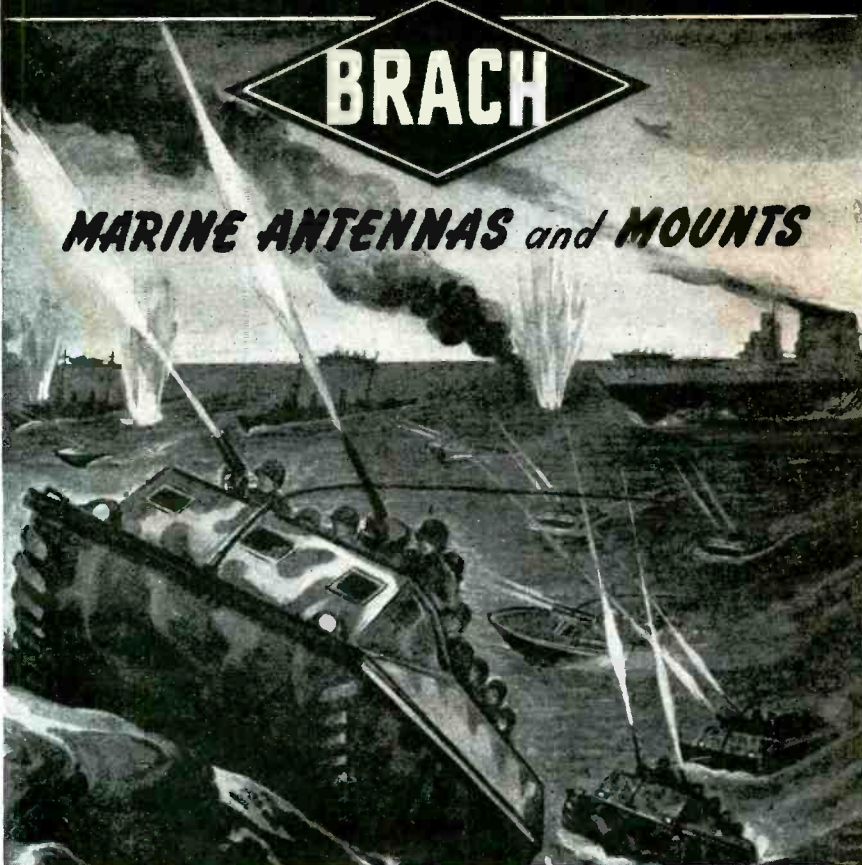

Brach Marine Antennas and Mounts are now manufactured 100% for the service of Uncle Sam's amphibian tanks, PT boats, etc. But with the dawn of Victory we shall be ready and able to utilize our enhanced experience and wartime "know how" in supplying the civilian requirements for antenna equipment for ship-to-shore communication.

**L. S. BRACH MFG. CORP.**

World's Oldest and Largest Manufacturers of Radio Antennas and Accessories  
55-65 DICKERSON STREET • NEWARK N. J.

pearing across capacitor 23, into proper proportions for the operation of the timer.

Thyatron 29 cannot normally fire, even though timing capacitor 31 charges to the maximum voltage value existing between the positive terminal and the tap on the voltage divider. This is due to the fact that the grid of this tube is connected to the negative terminal of the voltage divider. Thus, the tube cathode is still positive with respect to the grid when timing capacitor 31 is fully charged.

However, when the detection camera is excited by the passage of a

perforation, terminal *P* of the amplifier becomes positive with respect to the negative terminal of the voltage divider. Coupling capacitor 13 momentarily charges in series with the *P* terminal of the amplifier and the grid circuit resistor 42, causing a momentary voltage pulse to appear across the latter. The grid end of this resistor is positive, the voltage across this resistor exceeding that across resistor 26 in the voltage divider, swinging the grid of thyatron 29 positive with respect to its cathode. Thyatron 29 then fires, discharging timing capacitor (Continued on page 31)





Supreme's New "Hairline Accuracy" Meter

**ALLIED LIVES**... Allied victories... depend upon the Communication waves and wires. These channels of contact **must** be kept open. Our fighting men rely on the accuracy, dependability and ease of operation of Supreme Instruments and Meters, assured by Supreme's 15 years of experience. **Supreme Radio Testing Equipment Keeps Communications Open.**



Supreme 504-A Tube and Set Tester

**SUPREME**


SUPREME INSTRUMENTS CORP.  
GREENWOOD, MISSISSIPPI, U. S. A.

**ALLIED COIL-WINDING CALCULATOR**

A new slide-rule type rapid calculator for inductance, capacitance, and frequency components of series or parallel tuned r-f circuits as well as inductance, turns-per-inch, wire type, wire size, coil diameter and coil length for single layer-wound solenoid type r-f coils has been prepared by Allied Radio Corporation, 833 West Jackson Boulevard, Chicago 7, Illinois.

All values, in either case, are found with a single setting of the slide and are said to be accurate to within approximately 1% for coils ranging from 1/2" to 5 1/2" in diameter and 1/4" to 10" in length. All possible combinations within these limits are shown. Wire types and sizes include 11 to 35-gauge plain enamel, 11 to 36-gauge ssc, dsc, and scc, and 12 to 36-gauge dcc.

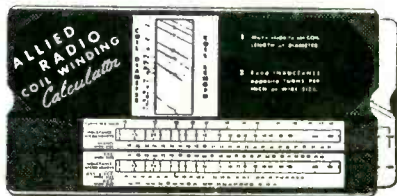The rule is also engineered to indicate turns-per-inch from 10 to 160; inductance from 0.1 to 15 microhenrys; capacitance



from 3 to 1,000 micromicrofarads; frequencies from 400 kilocycles to 150 megacycles with equivalent wavelengths in meters. Priced at 25c each.

\* \* \*

**RCA R-F AMPLIFIER AND PHOTOTUBE**

Two new tubes, the 829-B push-pull r-f beam power amplifier and 931-A multiplier phototube (9-stage electrostatically focused type), have been developed by RCA.

The 829-B is an improved design of push-pull r-f beam power amplifier having a total maximum plate dissipation of 40 watts. It is recommended especially for use in r-f power amplifier equipment. Having the same size and general appearance as the RCA-829 which it replaces, the new 829-B differs in that it has not only a higher plate-voltage rating (750 volts) but also an improved mechanical structure to permit use of the tube in applications involving considerable vibration.

The 931-A has the same size and general appearance as the 931 which it supersedes, but differs in that its current amplification has a minimum value 6 times higher, and an average value more than 3 times higher for the same voltage per stage. At 3,750 angstroms, the 931-A has a sensitivity of 1,800 microamperes per microwatt of radiant flux at 100 volts per stage, whereas the 931 had a corresponding value of 532 microamperes per microwatt, an improvement of over 3 times.

\* \* \*

**G. E. MYCALEX BOOKLET**

An eleven-page publication describing properties and applications of G. E. mycalex has been published by the Specialty Division of the General Electric Company's Electronics Department, Schenectady, New York.

G. E. mycalex is used as an insulator and is produced in plates, rods, strips and disks from which parts are machined to finished shapes. It also can be compression-molded into simple shapes with and without metal inserts.



**KEN BURCAW NOW CAP FLYER**

Ken Burcaw, jobber sales manager of Radiart Corporation, Cleveland, Ohio, has become a flyer in the Civil Air Patrol.

\* \* \*

**WARTIME SERVICE BOOK**


A 20-page manual with 250-tube substitution suggestions, methods of changing farm radios for electric operation and data on repairing burned out tubes, has been published by City Radio Company, 506 E. Washington Street, Phoenix, Arizona.

The manual, titled *Wartime Radio Service* by Charles and H. A. Middleton, is based on actual applications developed in the shop.

The tube substitution data is prepared in a very effective manner. The tube, substitute, and the circuit changes necessary are presented in column form. It thus becomes quite simple to find the data required to make the change.

Schematic information is also provided to show how farm radio changes can be made and how tube filaments can be repaired.

The price of the book is \$3.00.

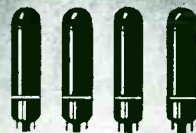

**4 STANDARD TYPES**

of Amperite Regulators replace over 400 types of AC-DC Ballast Tubes now in use.

Amperites are real REGULATORS... have patented Automatic Starting Resistor which prevents initial surge and saves pilot lights... Ask Your Jobber.

**AMPERITE**

THE *Simplest* WAY TO REPLACE

**BALLASTS**

WRITE FOR REPLACEMENT CHART

AMPERITE CO. 561 BROADWAY, NEW YORK, N. Y.



# STATION ALLOCATOR


(See Front Cover)

ON the cover this month we have the circuit of the RCA station allocator, 170. It is a modulated oscillator and was designed for rapid, accurate push-button alignment and tuning of r-f and i-f stages within the frequency range of 405 to 1,700 kc. It may be operated from either a 105-125-volt a-c supply or from self-contained batteries. Eight push-buttons provide eight frequency channels with .05% stability. Magnetite-core variable inductors and polystyrene coil forms and dielectric serve to provide this high stability factor.

The instrument and case is isolated from the power line, since a self-contained power transformer is used. This transformer draws only 5 watts. Battery operation for *A* supply is provided for by two Burgess No. 2 or Eveready No. 950 flashlight cells. Two Burgess No. W30P1 or Eveready No. 733 or 455 are used for *B* supply. The *A* drain is 50 mils at 1.5 volts; the *B* drain 2.6 mils at 90 volts.

A  $\frac{1}{4}$ -watt neon lamp serves the dual purpose of modulator and pilot lamp and also serves as a warning of dead *B* batteries by its failure to glow. When the modulation switch calls for modulated output the neon lamp acts as a relaxation type oscillator with a distinctive note of approximately 400 cycles. The exact frequency depends upon the supply voltage, and will, therefore, change somewhat in switching from line to battery operation. Two r-f output voltages are available, 2 or 0.2 volts with or without modulation.

For accurate setting of the allocator a beat method is used between the local broadcast station and the unmodulated allocator. If the beat is not picked up at once, the oscillator may be modulated to help bring the carrier very close to the station frequency. Then, when the modulation is removed, the beat will be heard. The recommended procedure for Service Men is to make a list of the eight most popular stations in your locality in order of frequency, allow at least a 10-minute warm-up period and then proceed to set the buttons in order of frequency. In operation, the output lead is placed close to the loop or antenna lead of the receiver and the receiver is tuned for the distinctive signal. After a preliminary tuning, the coupling of the antenna is reduced and a final adjustment made. An avc voltmeter or standard a-c output meter (with avc inoperative) should be used when available for greatest

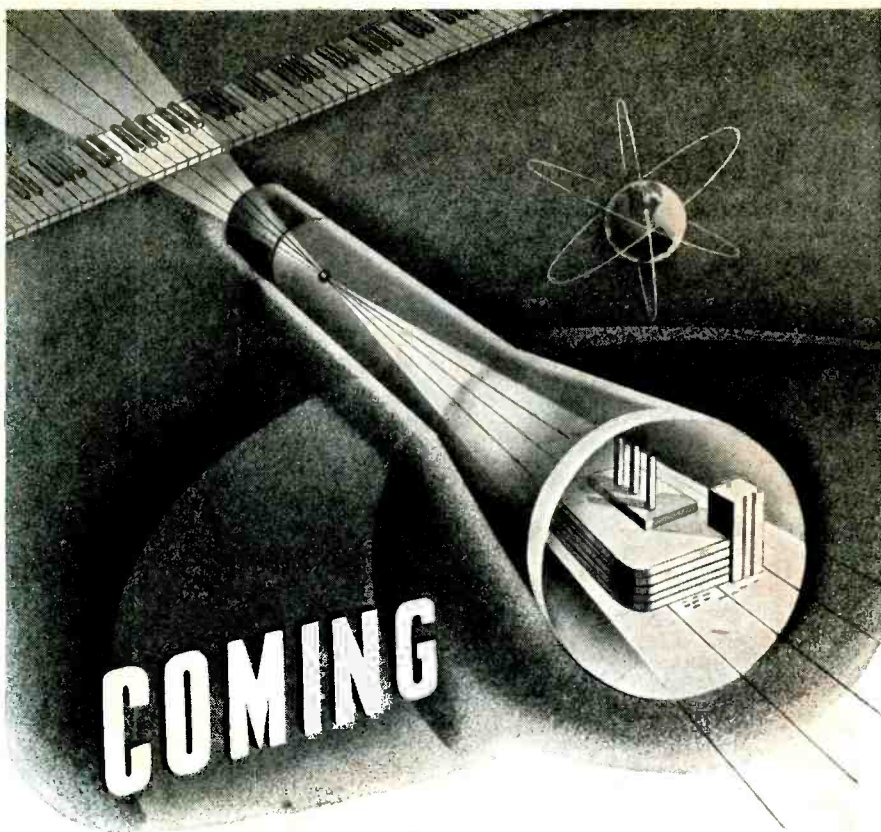

The utilization of the electron through the agency of the vacuum tube is one of Ken-Rad's many contributions to the science of Electronics in war. These electronic discoveries will be at the disposal of industry—in hundreds of developments—immediately after the Peace

## KEN-RAD

TRANSMITTING TUBES  
CATHODE RAY TUBES

INCANDESCENT LAMPS  
FLUORESCENT LAMPS

METAL AND VHF TUBES  
SPECIAL PURPOSE TUBES

OWENSBORO

KENTUCKY

U S A

accuracy. A final check is made on the receiver by comparing push-button with manual tuning of the local station.

Now for some circuit details. The 1R5 is designed as a pentagrid converter but is used here to provide isolation of the oscillator from the output circuit. This is accomplished by electron coupling. It is also well adapted to low level modulation which is applied from the neon lamp to the signal grid (3). Grid 1 serves as the usual oscillator grid and 2 as the oscillator anode in a Colpitts oscillator with an untapped coil and a tapped capacitor, or capacity voltage divider. Two

1,200-mmfd condensers are grounded at the junction. The circuit is chosen for use with single, untapped variable inductors for the push buttons.

The audio oscillator circuit is unusual. The power circuit consists of 1.5-megohm resistors shunted with a 1,800-mmfd capacitor, all in series with the lamp. Combined resistance-capacity coupling delivers audio voltage to the modulating grid. Note the 220,000-ohm grid leak. The 1R5 filament is returned to A— by way of the filament winding on the transformer. The output circuit consists of a resistance-attenuator coupled to the plate through a small condenser (27 mmfd).

# THE AUDIO CHANALYST

## Part III

**T**HIS, the final installment, considers the low gain channel *B* amplifier, the audio oscillator, speaker and power supply—all sections not previously covered. Some typical applications of the chanalyst are also considered.

### Amplifier Channel B

Amplifier *B* is a single stage resistance coupled 6SJ7 pentode amplifier, the output of which is rectified by one of the diodes of 6H6 and impressed upon a 6E5 indicator. The output is also brought out to two jacks, *OUTPUT VM* and *OUTPUT AF*. The former is for voltmeter measurements; the latter for audio output arranged particularly for oscillograph measurements. A two-circuit jack disconnects the rectifier and *magic eye* when a standard phone plug is inserted, preventing the clipping effect which would occur with the diode load and the consequent cathode-ray image distortion.

The amplifier has a sensitivity of 0.1 volt maximum, input resistance of 1 megohm, frequency characteristic essentially flat to 10,000 cycles and an attenuation ratio of 60 db (1,000 to 1). Two attenuators, *Coarse* and *Fine*, are located in the a-f input circuit to the

amplifier grid. The *Coarse* control consists of a 3-point switch labelled 1, 10 and 100, and provides a voltage step-down of 100 to 1, equivalent to 40 db attenuation. The *Fine* control consists of a 1-megohm potentiometer in series with a ¼-megohm resistor and provides 10 to 1 (20 db) smooth attenuation. The maximum gain of the amplifier is adjustable by means of a 1,000-ohm cathode resistor where the amount of current degeneration is controlled. The 40-mfd bypass is connected to the potentiometer arm so the gain is proportional to the percentage of the resistance bypassed.


The output impedance is approximately 0.1 megohm (the value of the plate load resistor) so care must be exercised not to load the amplifier with high capacity shielded cable, particularly when working with high audio frequencies. Channel *B* is not calibrated to a particular zero reference level as in channel *A*, the high gain amplifier. In checking gain and in signal tracing, the sensitivity and attenuation ratio must be observed so as not to overload the amplifier or false measurement and distortion will result.

Circuit of the complete RCA audio chanalyst.
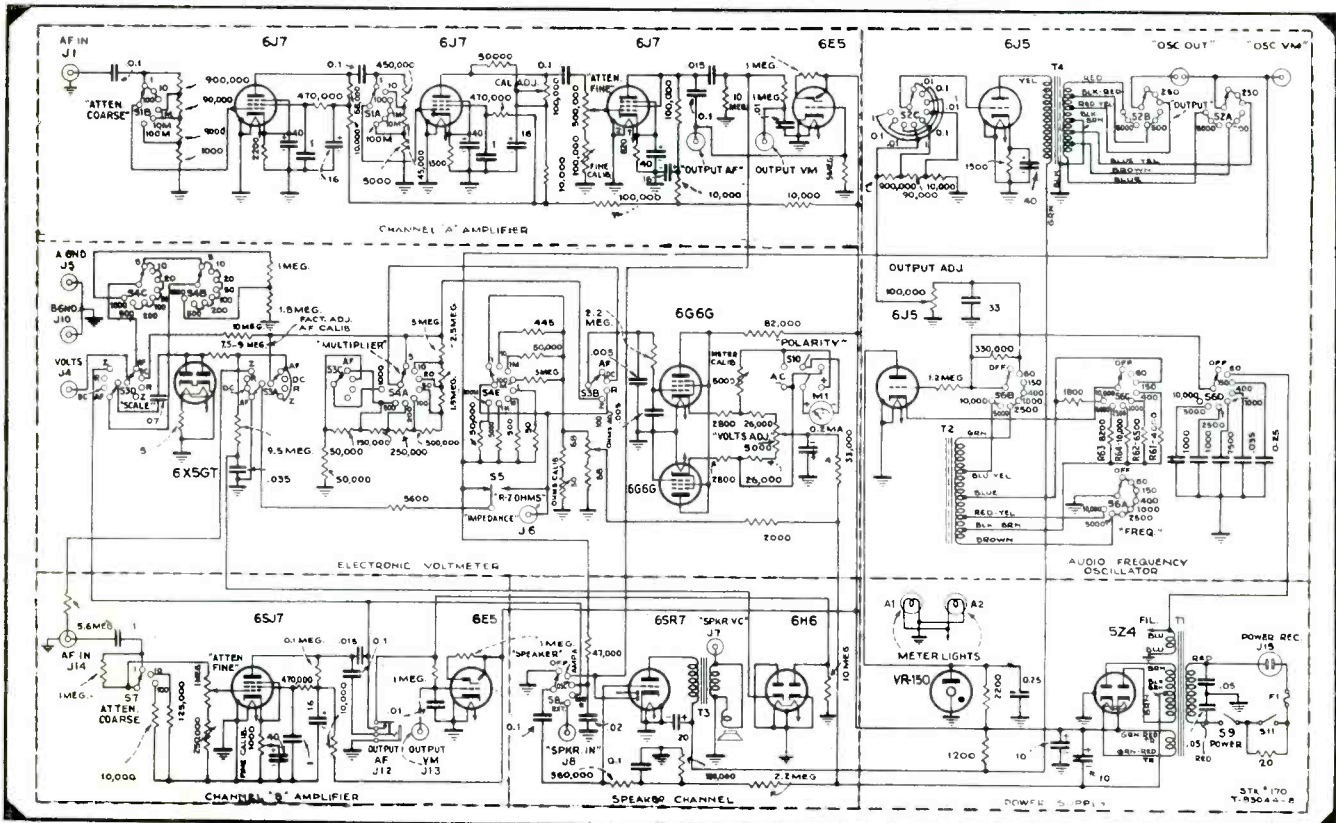
### Audio Oscillator Channel

This channel consists of a hot cathode Hartley oscillator with the plate grounded through a ¼-mfd bypass condenser providing seven spot frequencies from 60 to 10,000 cycles. The frequency is governed by a tapped choke or autotransformer, five different capacitors and five different cathode resistors. It is stabilized by a regulated power supply. Isolation of the load circuit is provided by a buffer amplifier.

The oscillator tube is a 6J5 and is operated in an unusual manner with 1.2 megohms in series with the grid. The output voltage is taken from the low potential side of this resistor, being applied to the 6J5 buffer grid through a 330,000-ohm isolating resistor and a two-stage attenuator. A 33-nmfd shunt condenser, in combination with the resistor, acts as a low-pass filter to reduce harmonic distortion and as an equalizer to attenuate high frequencies slightly. The following frequencies are provided: 60, 150, 400, 1,000, 2,500, 5,000 and 10,000. The 60-cycle point is a dummy as far as the oscillator is concerned. It is provided by the 6.3-volt filament winding directly to the buffer amplifier. Note the method of applying this voltage to the oscillator out-





put tap while the oscillator is cut off by opening the cathode. The cathode resistors limit the dynamic operating range of the oscillator to maintain a good waveform and to limit the output voltage to approximately 6.3, the same as the 60-cycle source.

The buffer input voltage is controlled by a nine-point step-by-step attenuator and a 0.1-megohm potentiometer for continuous adjustment. The output transformer has a multi-tapped secondary which is grounded at the center to provide output impedances of 250, 500 and 5,000 ohms balanced to ground, and grounded output impedance of a fourth of these values, namely, 62.5, 125 and 1,250 ohms. The undistorted power output is 80 milliwatts.

#### Speaker Channel

This channel consists of a p-m speaker transformer coupled to a 6SR7 triode, a switch being provided to connect the grid circuit to the output of amplifier A, amplifier B, the internal oscillator or an external source. The input impedance is approximately 560,000 ohms, the value of the grid leak. Bias is obtained from a voltage divider, the cathode being directly grounded. This channel may be used to supply a sound pressure field for testing and comparing microphones as well as for the more obvious functions normally associated with audio systems such as checking hum, distortion, operation of equalizers and filters, and trouble shooting.

The speaker is very useful in checking noisy amplifiers, starting at the input and proceeding through the amplifier until the point is reached where noise is noticed. An examination of components and connections at this point should readily reveal the fault. In checking phonograph pickups the speaker channel is used in conjunction with amplifier B.

#### The Power Supply

Because no power tubes are used in the chanalyst a large power unit is not

required. A 5Z4 and resistance-capacitance filters take care of all the sections except the oscillator which has a VR-150 voltage regulator supplying it. The gas type regulators have a considerable filtering action. Individual decoupling filters are used in all stages of the audio amplifiers and these filters are real *brute force* networks with 16-mfd condensers and, usually, 10,000-ohm resistors. This insures stability and freedom from hum, important when dealing with the bass frequencies.

A 20-ohm resistor with a shorting switch is placed in the primary of the power transformer to prevent voltage overload when encountering high line voltages. The primary circuit also includes a fuse and a pair of .05-mfd bypass condensers from line to chassis. These capacitors serve to minimize the induction of hum and prevent line disturbances into the amplifiers.

#### Applications

The prime application of the audio chanalyst is, of course, audio signal tracing. It serves to check a-f units; diagnosing troubles that such equipment is likely to experience including dead or weak operation, distortion, noise, hum, intermittent operation and oscillation. It is also suitable for gain measurement and checking frequency response. The testing and balancing of push-pull circuits including inverter performance is also an important function. Besides being noticed in the speaker output, hum is also indicated by a fuzzy pattern on the 6E5 indicator. The hum voltage may be measured by the electronic voltmeter in connection with one of the amplifier channels.


Principal causes of hum are due to a defective power supply but others are also quite common. Among these are defective tubes, leaky coupling condensers, overloaded power supply due to shorts, poor ground connections,

(Continued on page 31)

# DUMONT

## OIL-FILLED Ceramic SEALED CAPACITORS

For  
Dependable  
Service  
Work

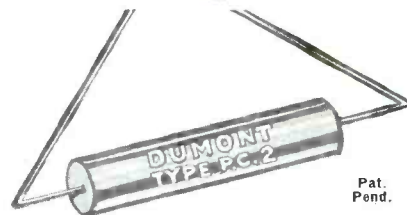

Pat. Pend.

For long life in repairs for those expensive high-class service jobs on amplifiers, public address, police and school systems and all good electronics equipment.

All capacitors from .0001 to .25 from 600 volts to 2000 volts.

It is your duty to buy war bonds

Literature and prices on request

DUMONT  
ELECTRICO.  
MFR'S OF  
CAPACITORS FOR EVERY REQUIREMENT  
34 HUBERT STREET  
NEW YORK, N. Y.

# 14<sup>NEW</sup> STANCOR Victory Model

## TRANSFORMERS AND CHOKES

ARE NOW AVAILABLE FROM STANCOR JOBBERS!



If your present supplier is unable to supply your requirements for VICTORY MODEL Transformers and Chokes, contact your nearest STANCOR Jobber today. A nation-wide distribution system is maintained for your convenience. If you don't know your nearest STANCOR jobber, write us.

STANDARD TRANSFORMER CORPORATION  
1500 NORTH HALSTED STREET CHICAGO



### NEWS OF "THE REPRESENTATIVES"

At the November meeting of the Mid-Lantic chapter a planning committee under the chairmanship of S. K. Macdonald was formed. This committee working with the chapter's president, L. D. Lowery, will consider not only postwar possibilities of the chapter, but will make immediate recommendations regarding publicity for the local organization and a new buyer's guide which will be a revised edition of the *Classified Index* published last year.

A membership committee was appointed by Norman M. Sewell, vice president L. D. "Doc" Lowery. It consists of chairman Roy Bengé, John McKinley, and Robert Williams. Bob Williams and Don Gawthrop were accepted as new members at this meeting.

A combined dinner and meeting sponsored by the Representatives Wolverine chapter and the Michigan chapter of the National Electronic Distributors Association was recently held in Lansing, Michigan. Distributors from Detroit, Pontiac, Flint, Saginaw, Muskegon, Grand Rapids, Kalamazoo, Lansing, Jackson and Ann Arbor attended. Postwar planning was discussed.

R. T. Perron, 80 Davenport Street, Taunton, Mass., was elected chairman of the New England chapter at a recent meeting. Vice chairman of the chapter is T. Coakley, 11 Beacon Street, Boston, Mass. H. Gerber, 94 Portland Street, Boston 14, Mass., is secretary.

F. A. Emmet, 2837 West Pico Blvd., Los Angeles 6, Calif., was recently elected a member of the Los Angeles chapter.

J. Maquire of the Mid-Lantic chapter has joined the Armed Forces.

B. Whan has moved to 679 N. Wells Street, Chicago, Illinois.

### LAND PURCHASED FOR SYLVANIA RESEARCH CENTER

A tract of land on Long Island has been purchased by Sylvania Electric Products, Inc., for the building of a research center. Because of wartime restrictions there will be no immediate building program, although two structures now on the property will be renovated for use by a small research group.

### HALLICRAFTERS CELEBRATE 10TH ANNIVERSARY

The Old Timers' Club of the Hallcrafters Company celebrated the tenth anniversary of the company recently with a surprise dinner in honor of W. J. Halligan, president and founder.

### CONNECTOR WALL CHARTS

Two wall charts showing insert, size and identification details of AN plugs have been prepared for all branches of the Army, Navy and industry using standard Army-Navy specifications electrical connectors, by Cannon Electric Development Company, Los Angeles, Calif.

### SYLVANIA ENGINEER'S BOOK ON ELECTRONICS TO APPEAR SOON

A book entitled *A Primer of Electronics*, written by Don P. Caverly, commercial engineer of Sylvania Electric Products, Inc., will appear soon. McGraw-Hill is the publisher.

The new book is a primer and omits complex technicalities.

### CENTRALAB TRIMMER CATALOG

An 8-page bulletin, 695 revised, on trimmers, has been released by Centralab, division of Globe-Union, Inc., 900 East Keefe Avenue, Milwaukee 1, Wisconsin. The construction principles and data on four styles in current production are provided. Helpful drawings and actual photographs also appear.

### N. U. VISUAL AID VACUUM TUBE CHART

A visual aid vacuum tube chart for instruction purposes has just been published by National Union Radio Corporation, Newark, N. J.

The chart, 30" x 45", shows all parts of a typical radio tube individually and in relation to the final construction. It also contains element classifications and symbols for diodes, triodes, tetrodes, pentodes and multi-element and multi-unit types including diode triode, double triode, diode pentode and pentagrid converters. Sketches of base pin arrangements and numbering systems for vacuum tubes are also included.

Copies of the chart are available through National Union distributors, free of charge to recognized universities, colleges and Signal Corps instruction centers, or at \$1.00 each to individuals outside of recognized institutions conducting fully accredited radio courses.

### UNIVERSAL MICROPHONE TO MAKE LIP MIKES

Herbert Baumgarten, materials engineer and coordinator for the Universal Microphone Co., Inglewood, Cal., conferred with Signal Corps engineers in the East recently relative to production on the new lip model microphone.

### ILLINOIS INSTITUTE ELECTS SIEGEL OF OHMITE TO BOARD

David T. Siegel, founder and president of the Ohmite Manufacturing Company, Chicago, was elected to the board of trustees of Illinois Institute of Technology recently.

Mr. Siegel was one of five new members named to the Institute's board. He was elected as an alumni representative to the board, having been nominated by the Illinois Tech Alumni Association.

### IRC WINS SECOND WHITE STAR

For the second time the International Resistance Company has been awarded a white star for their "E" flag.

### DIAL LIGHT CATALOG

A 24-page catalog describing an assortment of pilot light assemblies and accessories has been released by the Dial Light Company of America, Inc., 90 West Street, New York 6, New York.

Data on incandescent lamps, socket assemblies, jewels, and numbers, letters and trade marks available for pilot light assemblies, are included in this catalog.

### MECK ANNOUNCES POSTWAR PLANS

A postwar merchandising policy has been announced by John Meck Industries, Plymouth, Ind.

In this policy according to John Meck, president, the jobber will be retained for distribution.

In describing the importance of the jobber, Mr. Meck said:

"We are well aware that many economic planners, seeking to change our time-proved distribution system, have evolved glamorous methods of direct selling which may influence postwar merchandising to some extent. Nevertheless, it cannot be established that radio parts jobbers, in the long run, either add to distribution costs from the dealer's standpoint or perform functions which are not essential to a smooth flow of goods from manufacturer to consumer, with maximum profit to the dealer.

"The stock-carrying and service facilities of radio parts jobbers unquestionably add to convenience and speed with which dealers can conduct their businesses."

## WARTIME RADIO SERVICE

This booklet includes the following—  
Nearly 300 Tested Substitutions for All the  
Hard to Get Types of Tubes

Gives instructions for Building Inexpensive Apparatus for Repairing Open Heaters in 150 Mil Heater Type Tubes and How to Use It. About 40% of These Tubes Can Be Made to Give Additional Service.

Tells How to Change the Late Farm Radios for Electric Operation. Diagram and Text Eliminate the Bugs.

The only book of its kind—it saves you valuable time, enables you to increase your sales and satisfy your customers. You can't afford to figure it out yourself.

\$3.00 per copy, postpaid

### CITY RADIO COMPANY

The RADIO CITY of Phoenix, Arizona  
504-6 E. Washington Street

## WHEN YOU CHANGE YOUR ADDRESS

Be sure to notify the Subscription Department of SERVICE at 19 E. Forty-seventh St., New York 17, N. Y., giving the old as well as the new address, and do this at least four weeks in advance. The Post Office Department does not forward magazines unless you pay additional postage, and we cannot duplicate copies mailed to the old address. We ask your cooperation.



## PHOTOCONTROLS

(Continued from page 25)

tor 31, becoming non-conductive when the voltage across this capacitor is so low that the tube fails to conduct an ionization current.

Once discharged, the voltage across capacitor 31 is near zero, but rising relatively slowly as the capacitor is charged by the current conducted through the delay control and limit resistors 28 and 27, respectively. At this time, the voltage across the capacitor is less than that across resistor 25 in the voltage divider. This causes the control grid of power thyatron 33 to assume a positive polarity with respect to its cathode, the latter electrode being connected to the tap on the voltage divider. This thyatron now conducts, energizing solenoid coil 37 of hydro-electric valve 40. The rectified a-c passed by the thyatron through coil 37 is limited by limit resistor 39. Rectifier unit 38 functions to short-circuit the coil self-induced voltage between pulses of rectified a-c, thus effectively maintaining a relatively constant field flux through the coil, holding the valve, 40, open.

Operation of the hydro-electric valve causes a deflector guide to remove the perforated strip section, the latter falling into a scrap bin.

Valve 40 is held open until capacitor 31 voltage exceeds that across resistor 25. Then the grid of thyatron 33 assumes a voltage polarity negative with respect to its cathode. Since the capacitor charging period is dependent on the resistance values of resistor 28 and 27, adjustment of resistor 28 varies the time interval during which the valve remains opened. Resistor 27 merely functions to prevent a short-circuit condition if the resistance of the rheostat 28 is reduced to zero. Thus, rheostat 28 may be adjusted to the length of time necessary for the passage of the perforated strip section from the strip shear blade, over roll conveyor to scrap removal guide.

(To be continued)

\* \* \*

## SER-CUITS

(Continued from page 14)

second i-f control grid.

A field coil shunted by a divider resistor in the negative high voltage supplies two bias voltages; for 6V6 power output, and the foregoing avc system, and first and second audio. Ample decoupling filters are provided. The output push-pull tubes have 680 ohms in the grid leads to suppress parasitics. Inversed feedback from the voice coil is fed direct to the second a-f grid through an equalizer consist-



Your Meissner distributor will advise you on the Meissner replacement parts now available... while keeping our facilities devoted to the manufacture of vital electronic parts for war needs we have been doing our utmost to keep a replacement parts stock in the hands of Meissner distributors... a service which we, here at Meissner, are doing to help keep 'em playing.

See your Meissner distributor today... he will tell you just what parts are available now.



PRECISION-BUILT ELECTRONIC PRODUCTS

ing of a 220,000-ohm resistor and a .05-mfd capacitor. The power transformer has a dual primary. A dual 150,000-ohm potentiometer is run to ground, supplanting the usual paper condensers. However, a .003-mfd by pass condenser is applied across each half of the high voltage secondary to limit disturbances coming from the a-c line.

\* \* \*

## AUDIO CHANALYST

(Continued from page 29)

induction hum, shorted or reversed hum bucking coils in speakers and defective or improperly adjusted hum

balancers in amplifiers with filament type tubes.

Oscillation problems can be checked, too. Incidentally common form of oscillation, motor-boating, is generally caused by defective filter or decoupling circuits in the plate or screen power circuits, open grid circuits or some kind of feedback that shouldn't be! One way to tackle this one is to apply a large paper condenser from grid to ground of each stage until the culprit is found. Then the grid and power supply circuits of that stage should be checked using the electronic voltmeter channel.





# Voice Communication Components

Universal Microphones, as well as Universal Plugs, Jacks, Cords, and Switches, are vital voice communication components today in the War Effort. When peace comes, they will continue to fulfill their role in a postwar world surmounting the barriers of distance with Radio and Aircraft.

**UNIVERSAL MICROPHONE CO., LTD.**

INGLEWOOD, CALIFORNIA

CANADIAN DIV: 560 KING ST. WEST, TORONTO 2  
FOREIGN DIV: 301 CLAY, SAN FRANCISCO 11, CAL.



## JOTS & FLASHES


**C**ONGRATULATIONS to this month's Army-Navy "E" winners for outstanding production . . . they include KenRad Tube and Lamp Corp., Utah Radio Products Co., Electronic Enterprises, Inc., Delco Radio Division of General Motors. . . . Aircraft-Marine Products, Inc., now located at 1523 N. 4th St., Harrisburg, Pa. . . . Stromberg-Carlson appoints F. Leo Granger as Radio Service Manager . . . All credit to KenRad for the star shaped Christmas Card sent to all former employees now in the Armed Services . . . it's signed by the boys and gals who are keeping production lines rolling. . . . Burt Browne, well known Chicago advertising authority on radio and electronics, back on the job after Arizona vacation. . . . Lucius E. Packard in charge of General Radio's new Chicago office at 920 S. Michigan Ave. . . . Lester Via, with 10 years' radio experience, appointed to engineering department of John Meck Industries to undertake special crystal research. . . . J. W. Whiteside appointed buyer in tube division of General Electric's Electronic Department. . . . Frank W. Warner named chief engineer of that company's plastic divisions. . . . Radio Service Men in all parts of the country report very favorably on Sprague's Trading Post Program . . . claim that it has helped them get equipment they need badly and also to dispose of material they no longer require . . . Thanks to all you Servicers for your Holiday Greetings . . . they're much appreciated and sincerely reciprocated . . . Don't forget the 4th War Bond Drive gets underway in January . . . be ready to do your share and more . . . your Uncle Sam still needs plenty \$\$\$ to wind up this war in a hurry. . . . Robert C. Berner joins Emerson Radio as assistant to president Ben Abrams . . . Regret to report death of Frank A. Ross, senior vice-president of Stewart-Warner. . . . Universal Microphone appoints Ted Pockrandt as supervisor of production on new lip microphones for Signal Corps . . . Employee publications received and enjoyed this month include *Raytheon News*, *Hallcrafters Tuner* and *Universal Micro-Topics* . . . better start studying up on television . . . there will be plenty of activity in this field shortly after hostilities are concluded . . . looks like a profitable year ahead for radio Service Men . . . Read all available technical material carefully . . . start planning now for the postwar readjustment period . . . here's wishing you all a most prosperous New Year.

## ADVERTISERS IN THIS ISSUE

SERVICE, DECEMBER, 1943

AEROVOX CORP. . . . .	12
Agency—AUSTIN C. LESCARBOURA & STAFF	
AMPERITE CO. . . . .	26
Agency—H. J. GOLD & Co.	
L. S. BRACH MFG. CORP. . . . .	25
Agency—UNITED ADVERTISING AGENCY	
CINAUDAGRAPH SPEAKERS, INC. . . . .	20
Agency—MICHAEL F. MAYGER	
CITY RADIO CO. . . . .	30
CLAROSTAT MANUFACTURING CO., INC. . . . .	20
Agency—AUSTIN C. LESCARBOURA & STAFF	
DUMONT ELECTRIC CO. . . . .	28
Agency—A. ROTHSCHILD	
GENERAL ELECTRIC CO. . . . .	29
Agency—N. W. AYER & SON, INC.	
HALLICRAFTERS CO. . . . .	24
Agency—BURTON BROWNE, ADVERTISING	
HYTRON CORP. . . . .	Inside Front Cover
Agency—HENRY A. LOUDON, ADVERTISING	
JACKSON ELECTRICAL INSTRUMENT CO. . . . .	13
Agency—KIRCHER, LYTTLE, HELTON & COLLETT, INC.	
KEN-RAD TUBE & LAMP CORP. . . . .	27
Agency—ALLEN, HEATON & McDONALD, INC.	
MEISSNER MANUFACTURING CO. . . . .	31
Agency—BURTON BROWNE, INC.	
MUELLER ELECTRIC CO. . . . .	20
NATIONAL UNION RADIO CORP. . . . .	Back Cover
Agency—SAYRE M. RAMSDELL ASSOCIATES, INC.	
PHILCO CORPORATION . . . . .	12
Agency—SAYRE M. RAMSDELL ASSOCIATES, INC.	
RCA VICTOR DIV., RADIO CORP. OF AMERICA . . . . .	4, 19
Agency—KENYON & ECKHARDT, INC.	
RADIO & TECHNICAL DIV. MURRAY HILL BOOKS, INC. . . . .	21
Agency—THE HARRY P. BRIDGE CO.	
RAYTHEON PRODUCTION CORP. . . . .	3
Agency—BURTON BROWNE, ADVERTISING	
JOHN F. RIDER PUBLISHER, INC. . . . .	18
Agency—LANSFORD F. KING	
SOLAR MANUFACTURING CORP. . . . .	Inside Back Cover
Agency—O. S. TYSON & Co., INC.	
SPRAGUE PRODUCTS CO. . . . .	1
Agency—THE HARRY P. BRIDGE CO.	
STANDARD TRANSFORMER CORP. . . . .	29
Agency—BURNET-KUHN ADVERTISING CO.	
SUPREME INSTRUMENTS CORP. . . . .	26
Agency—O'CALLAGHAN ADVERTISING AGENCY, INC.	
TRIPLETT ELECTRICAL INSTRUMENT CO. . . . .	24
Agency—WESTERN ADVERTISING AGENCY, INC.	
UNITED TRANSFORMER CO. . . . .	23
Agency—SHAPPE-WILKES INC.	
UNIVERSAL MICROPHONE CO., LTD. . . . .	32
Agency—RALPH L. POWER AGENCY	
UTAH RADIO PRODUCTS CORP. . . . .	11
Agency—THE BUCHEN Co.	



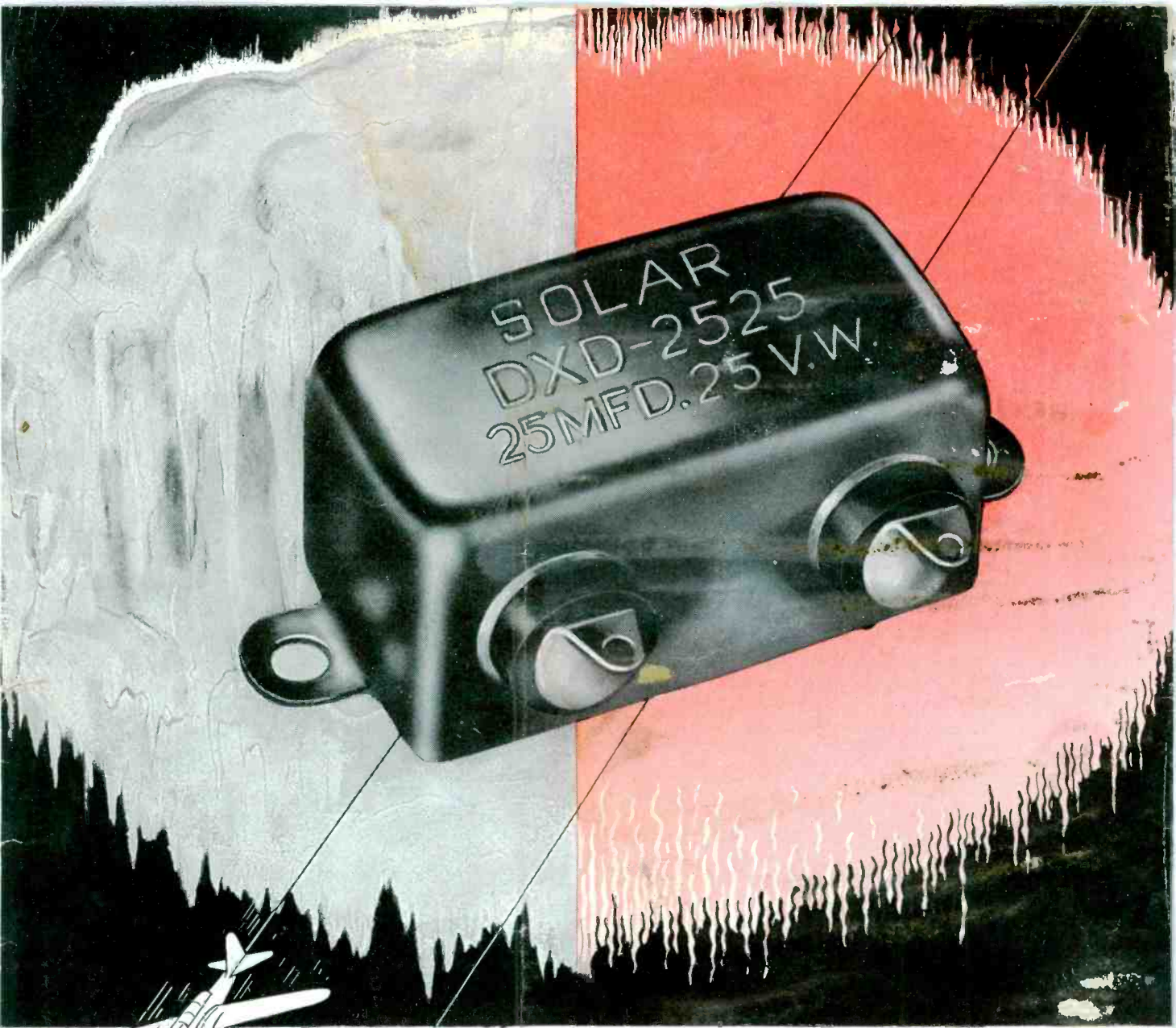

## **FREEZE 'EM OR FRY 'EM**

• Global war means airplanes in the Arctic. It means tanks in the tropics. For fighting machines of all kinds, combat conditions call for freezing or frying — and sometimes both!

Solar is building capacitors which meet these extreme conditions. If "freezing or frying" is part of your capacitor problems — call on Solar's "temperature-engineering" services.

*Facts and more facts. Complete capacitor data describing and illustrating the entire Solar line is now available to design engineers on request.*



# Solar

**SOLAR**

SOLAR MANUFACTURING CORP., 285 MADISON AVE., NEW YORK 17, N. Y.

## — **CAPACITORS** —

CAPACITORS: ELECTROLYTIC • MICA • PAPER • TRIMMER • TRANSMITTING

[www.americanradiohistory.com](http://www.americanradiohistory.com)





## QUAKE-PROOF CONSTRUCTION



In a few cubic inches of space National Union tube designers plan and build their electronic skyscrapers. Many fragile parts of these intricate mechanisms are precisely balanced, buttressed and welded fast.

For N. U. engineers well know the *rough sailing* that's ahead for these tubes—the shocks, concussion, vibration—relatively far more shattering than the impact of an earthquake on a modern steel and masonry building. So their war job is to build tubes which will stand up and take what comes—whose parts will *stay* in precise alignment—whose exact

clearances will not be altered—whose air seal will not be broken.

To master this complicated construction problem calls for precision engineering of the first order—and a minute knowledge of the strength, rigidity and other characteristics of many metals. The point is—modern electronic tubes are scientific instruments. For post-war tubes of highest character, teamed-up with service assistance to match, service engineers can *count on* National Union.

**NATIONAL UNION RADIO CORPORATION, NEWARK, N. J.**  
Factories: Newark and Maplewood, N. J., Lansdale and Robesonia, Pa.

# NATIONAL UNION RADIO AND ELECTRONIC TUBES



Transmitting, Cathode Rays, Receiving, Special Purpose Tubes • Condensers • Volume Controls • Photo Electric Cells • Panel Lamps • Flashlight Bulbs