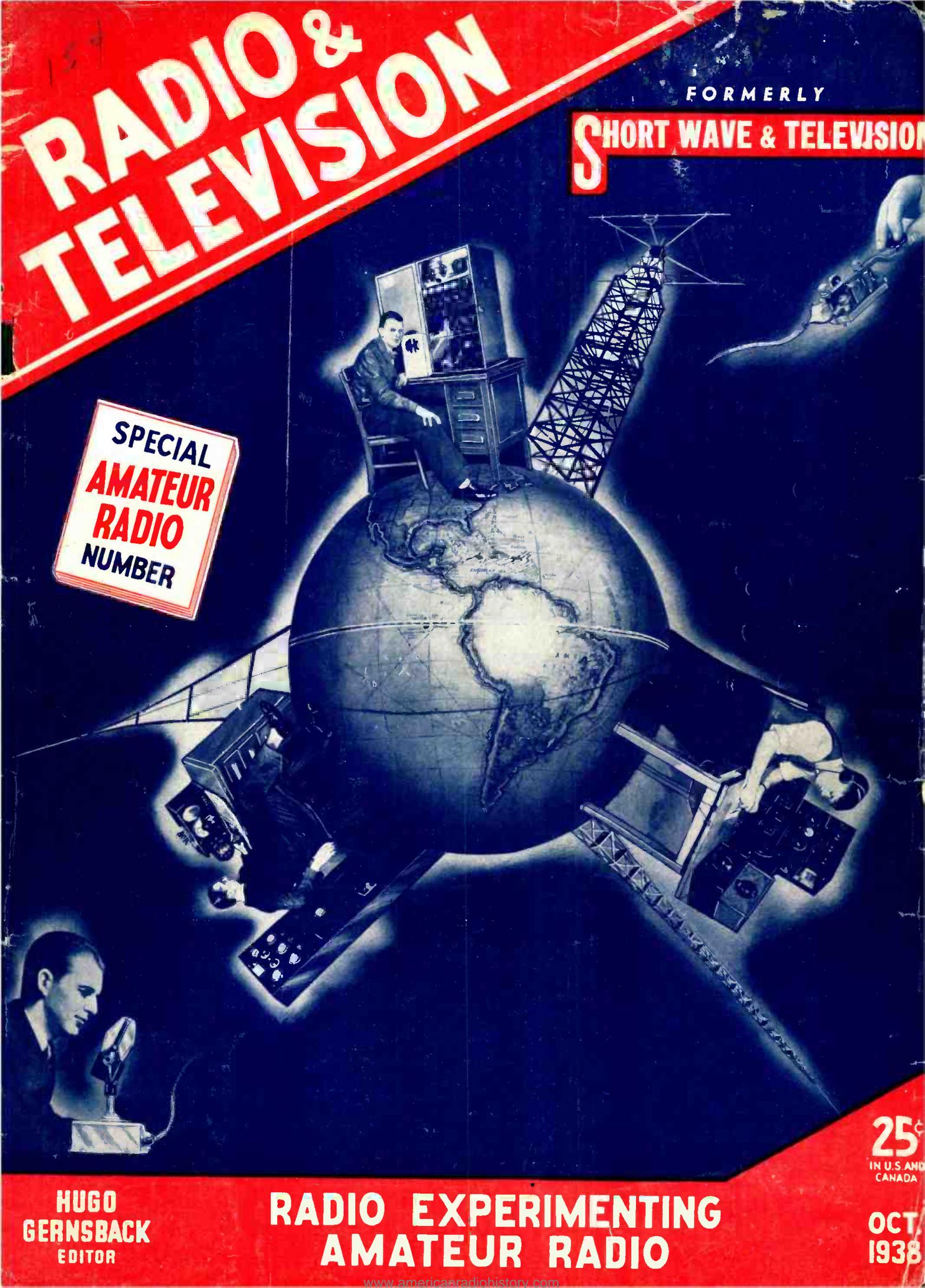


RADIO & TELEVISION

FORMERLY

SHORT WAVE & TELEVISION

**SPECIAL
AMATEUR
RADIO
NUMBER**



**HUGO
GERNSBACK
EDITOR**


RADIO EXPERIMENTING AMATEUR RADIO

25¢
IN U.S. AND
CANADA

**OCT
1938**

You can't lose! A money-back guarantee protects you!

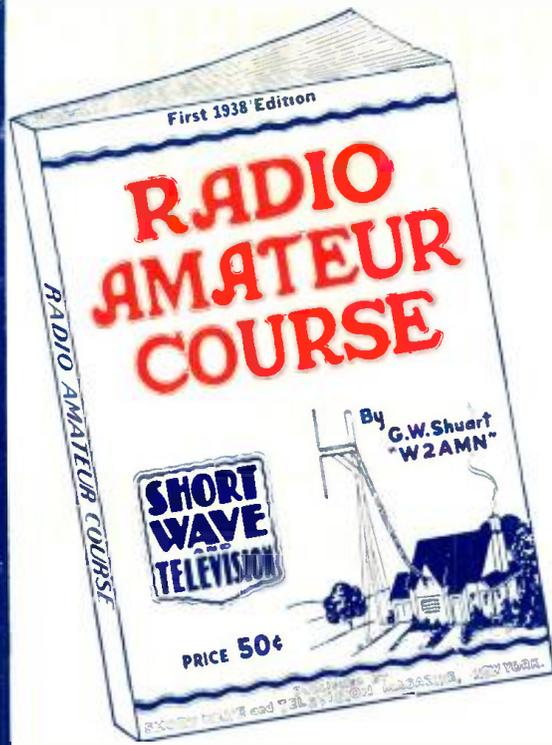THE RADIO AMATEUR COURSE REPRESENTS THE GREATEST BOOK VALUE EVER OFFERED TO RADIO "FANS" FOR 50c



TO convince you that there isn't a better book buy today the publishers of the RADIO AMATEUR COURSE make the sensational offer of a money-back guarantee on such a low-priced book. Stop in at any of the many dealers listed below and examine this volume. See for yourself if the RADIO AMATEUR COURSE isn't just the book you've always wanted.

**148 PAGES . . . 6 1/4 x 9 1/2 INCHES
OVER 150 DIAGRAMS AND PHOTOGRAPHS**

Printed on the finest quality paper—well illustrated— attractive 4-color cover—complete with radio information you must have. It contains a step-by-step program for obtaining a short-wave radio education.

Written by George W. Shuart, W2AMN, foremost short-wave authority

ON SALE AT THE FOLLOWING DEALERS

- ARIZONA**
Sam's Cigar Store,
127 N. First Ave., Phoenix.
- CALIFORNIA**
Scott Wholesale Radio Co.,
344 E. Fourth Street, Long Beach.
Offenhach Electric Co., Ltd.,
1452 Market Street, San Francisco.
Zack Radio Supply Co.,
1426 Market Street, San Francisco.
- COLORADO**
Auto Equipment Co.,
14th at Lawrence, Denver.
- CONNECTICUT**
Radio Inspection Service Co.,
297 Asylum Street, Hartford.
Stern Wholesale Paris, Inc.,
210 Chapel St., Hartford.
- GEORGIA**
Wholesale Radio Service Co., Inc.,
430 W. Peachtree St., N. W., Atlanta.
- ILLINOIS**
Allied Radio Corporation,
823 West Jackson Blvd., Chicago.
Newark Electric Company,
226 W. Madison Street, Chicago.
Wholesale Radio Service Co., Inc.,
901 W. Jackson Blvd., Chicago.
- INDIANA**
Van Sickle Radio, Inc.,
31 West Ohio Street, Indianapolis.
- MASSACHUSETTS**
Greater Boston Distributors,
40 Waltham St., Boston.
H. Jappe Co., 46 Cornhill, Boston.
Wholesale Radio Service Co., Inc.,
110 Federal Street, Boston.
Springfield Radio Co.
387 Dwight Street, Springfield.
H. Jappe Co.,
37 Mechanic Street, Worcester.
- MICHIGAN**
Rissi Brothers, Inc.,
5027 Hamilton Ave., Detroit.

- MISSOURI**
Modern Radio Company,
409 No. Third Street, Hannibal.
Bustein Applebee Co.,
1012-14 McGee Street, Kansas City.
Van Sickle Radio Co.,
1113 Pine Street, St. Louis.
- NEBRASKA**
Radio Accessories Company,
2506 Farnam Street, Omaha.
- NEW HAMPSHIRE**
Radio Service Laboratory,
1187 Elm Street, Manchester.
- NEW JERSEY**
Arco Radio Co.,
227 Central Avenue, Newark.
Wholesale Radio Service Co., Inc.,
219 Central Avenue, Newark.
- NEW YORK**
Wholesale Radio Service Co., Inc.,
742 E. Fordham Rd., Bronx.
Wholesale Radio Service Co., Inc.,
90-08 166th Street, Jamaica, L. I.
Plan, The Radio Man, Inc.,
64 Dey Street, New York City.
Eagle Radio Co.,
84 Cortlandt Street, New York City.
Federated Purchaser, Inc.,
25 Park Place, New York City.
Harrison Radio Co.,
12 West Broadway, New York City.
Sun Radio Co.,
212 Fulton Street, New York City.
Terminal Radio Corp.,
89 Cortlandt Street, New York City.
Thor Radio Corp.,
65 Cortlandt St., New York City.
Try Mo Radio Co., Inc.,
85 Cortlandt Street, New York City.
Wholesale Radio Service Co., Inc.,
100 Sixth Avenue, New York City.
Radio Parts & Equipment Co.,
241 Clinton Avenue No., Rochester.
M. Schwartz & Son,
710 712 Broadway, Schenectady.

- OHIO**
News Exchange,
51 So. Main Street, Akron.
Canton Radio & Supply Co.,
1110 Tuscarawas Street, W. Canton.
United Radio, Inc.,
1103 Vine Street, Cincinnati.
The Hughes-Peters Electric Corp.,
178-180 N. Third Street, Columbus.
Standard Radio Parts Co.,
135 East Second Street, Dayton.
- OREGON**
Portland Radio Supply Co.,
1300 W. Burnside Street, Portland.
- PENNSYLVANIA**
Radio Distributing Co.,
1124-26 Market Street, Harrisburg.
M. & H. Sporting Goods Co.,
512 Market Street, Philadelphia.
Camcardio Co.,
963 Liberty Ave., Pittsburgh.
- RHODE ISLAND**
W. H. Edwards Co.,
32 Broadway, Providence, R. I.
- UTAH**
O'Loughlin's Wholesale Radio Supply,
315 South Main Street, Salt Lake City.
Radio Supply, Inc.,
46 Exchange Place, Salt Lake City.
- WASHINGTON**
Spokane Radio Co., Inc.,
611 First Avenue, Spokane.
- WISCONSIN**
Radio Parts Co., Inc.,
536-538 W. State Street, Milwaukee.

- TEXAS**
Amarillo Electric Co.,
111 East 8th Avenue, Amarillo.
- AUSTRALIA**
McGill's Agency,
183-181 Elizabeth Street, Melbourne.
- CANADA**
The T. Eaton Co., Ltd.,
Winnipeg, Manitoba.
Canadian Electrical Supply Co., Limited,
285 Craig Street W., Montreal, Que.
Metropolitan News Agency,
1248 Peel Street, Montreal, Que.
- CUBA**
The Diamond News Co.,
Palacio Asturiano, Por San Jose,
Habana.
- ENGLAND**
Gorrings American News Agency,
9a, Green Street, Leicester Square,
London, W.C.2.
- HOLLAND**
Radio Peeters, Van Woestraat, Amsterdam, Z.
- INDIA**
Empire Book Mart,
Box 631, Bombay.
- MEXICO**
American Book Store, S. A.,
Avenida Madero 25, Mexico City.
Central De Publicaciones,
Avenida Juarez 4, Apartado 2430,
Mexico, D. F.
- NEW ZEALAND**
Te Aro Book Depot, Ltd.,
64 Courtenay Place, Wellington.
- SOUTH AFRICA**
Technical Book Co.,
147 Longmarket Street, Cape Town.

If this book is not at your dealer's, send your order directly to us. We will credit your dealer with the sale of this book. To order your copy of RADIO AMATEUR COURSE, fill in coupon below and mail.

RADIO AND TELEVISION, 99 HUDSON STREET, NEW YORK, N. Y.
Gentlemen: I enclose herewith my remittance of Fifty Cents (50c) for which please send me POSTPAID, my copy of the RADIO AMATEUR COURSE. (Remit by check or money order; register letter if you send cash or unused U.S. Postage Stamps.)

Name

Address

City State
R&T-1038

Be sure to see all future copies of RADIO AND TELEVISION for additional listings of dealers handling the RADIO AMATEUR COURSE.

RADIO AND TELEVISION
99 HUDSON ST., NEW YORK CITY



J. E. SMITH
President
National Radio
Institute
Established 1914
The man who has
directed the
home study train-
ing of more men
for the Radio In-
dustry than any
other man in
America.

I WILL TRAIN YOU TO START A SPARE TIME OR FULL TIME RADIO SERVICE BUSINESS WITHOUT CAPITAL

**HERE ARE A FEW EXAMPLES
OF THE KIND OF MONEY
I TRAIN MY MEN TO MAKE**

**\$200 TO \$300 A MONTH
IN OWN BUSINESS**

"For the last 18 months I have been in business for myself, making between \$200 and \$300 a month. I have N.R.I. to thank for my start in this field."—**ARLIE J. FROBNER**, 224 W. Texas Ave., Goose Creek, Texas.



\$10 TO \$25 A WEEK IN SPARE TIME

"I am making from \$10 to \$25 a week in spare time while still holding my regular job as a machinist. I owe my success to N. R. I."—**WM. F. RUPP**, 203 W. Front St., West Conshohocken, Pa.



**CHIEF OPERATOR BROADCASTING
STATION**

"When I completed 20 lessons, I obtained my Radio Broadcast Operator's License and immediately joined Station WMLP, where I am now Chief Operator."—**HOLLIS F. HAVES**, 85 Madison St., Lober, Mich.



**EARNINGS TRIPLED BY
N.R.I. TRAINING**

"I have been doing nicely, thanks to N.R.I. Training. My present earnings are about three times what they were before I took the Course. I consider N.R.I. Training the finest in the world."—**BERNARD COSTA**, 952 Manhattan Ave., Brooklyn, N. Y.



OVER \$1,000 BEFORE GRADUATING

"Before completing half the N.R.I. Course I was servicing sets, and I made \$1,000 to \$1,200 before graduating. I am doing Radio service work for myself now."—**ASHLEY G. ALDRIDGE**, 1228 Shepherd St., Petersburg, Va.



**Get My LESSON on Radio
Servicing Tips FREE**

I want to prove my Training gives practical, money-making information, that it is easy to understand—what you need to master Radio. My sample lesson text, "Radio Receiver Troubles—Their Cause and Remedy," covers a long list of Radio receiver troubles in A.C., D.C., battery, universal, auto, T. R. F., superheterodyne, all-wave, and other types of sets. And a cross reference system gives you the probable cause and a quick way to locate and remedy these

set troubles. A special section is devoted to receiver check-up, alignment, balancing, neutralizing, testin'. You can get this lesson Free by mailing the coupon.



**The Tested WAY
to BETTER PAY**

Do you want to make more money? The world-wide use of Radio has made many opportunities for you to have a spare time or full time Radio service business of your own. Four out of every five homes in the United States have Radio sets which regularly need repairs, new tubes, etc. Servicemen can earn good commissions selling new sets to owners of old models. Even if you have no knowledge of Radio or electricity, I will train you at home in your spare time to sell, install, fix, all types of Radio sets; to start your own Radio business and build it up on money you make in your spare time while learning. Mail coupon for my 64-page book. It's Free—it shows what I have done for others—what I am ready to do for you.

**Many Make \$5, \$10, \$15 a Week Extra
in Spare Time While Learning**

The day you enroll I start sending you Extra Money Job Sheets. They show you how to do Radio repair jobs, how to cash in quickly. Throughout your training I send you plans and ideas that have made good spare time money—from \$200 to \$500 a year—for hundreds of fellows. I send you special Radio equipment, show you how to conduct experiments, build circuits, illustrating important Radio principles. You get PRACTICAL EXPERIENCE while learning.

**There's a Real Future in Radio
for Well-Trained Men**

Radio today is young—yet it's one of our large industries. More than 28,000,000 homes have one or more Radios. There are more Radios than telephones. Each year millions of Radios get out of date, need replacing or new tubes, repairs. Millions are spent each year for Radio repairs. More than 5,000,000 auto Radios are in use; more are being sold every day, offering more profit-making opportunities for Radio experts. And RADIO IS STILL YOUNG—GROWING. Radio is expanding into other fields. The few hundred \$30, \$50, \$75 a week jobs of 20 years ago have grown to thousands. Yes, Radio offers opportunities—now and in the future!

**Get Ready Now for Your Own Radio Business
and for Jobs Like These**

Radio broadcasting stations employ engineers, operators, station managers and pay up to \$5,000 a year. Fixing Radio sets in spare time pays as much as \$200 to \$500 a year—full time repair jobs with Radio jobbers, manufacturers and dealers, as much as \$30, \$50, \$75 a week. Many Radio Experts open their own full time or part time Radio sales and repair businesses. Radio manufacturers and jobbers employ testers, inspectors, foremen, engineers, servicemen, paying up to

\$6,000 a year. Automobile, police, aviation, commercial Radio, loud speaker systems are newer fields offering good opportunities. Television promises to open many good jobs soon. Men I have trained are holding good jobs in these branches of Radio. Read their statements in my 64-page book. Mail the coupon.

**I ALSO GIVE YOU A
PROFESSIONAL
SERVICING
INSTRUMENT**



Here is the instrument every Radio expert needs and wants—an All-Wave, All-Purpose, Set Servicing Instrument. It contains everything necessary to measure A.C. and D.C. voltages and current; to test tubes, resistance; adjust and align any set, old or new. It satisfies your needs for professional servicing after you graduate—can help you make extra money fixing sets while training.


**Save Money—Learn At Home
Money Back Agreement Protects You**

I am sure I can train you at home successfully. I will agree in writing to refund every penny you pay if you are not satisfied with my Lessons and Instruction Service when you finish. You get a copy of this agreement with my Book.

**Find Out What Radio Offers You
Get My 64-Page Book Free Now**

Act Today. Mail the coupon now for my Free Lesson and my book, "Rich Rewards in Radio." Both are free to anyone over 16 years old. My book points out Radio's spare time and full time opportunities and those coming in Television; tells about my Training in Radio and Television; shows you letters from men I have trained, telling what they are doing and earning. Find out what Radio offers YOU! MAIL THE COUPON in an envelope, or paste it on a penny post card—NOW!

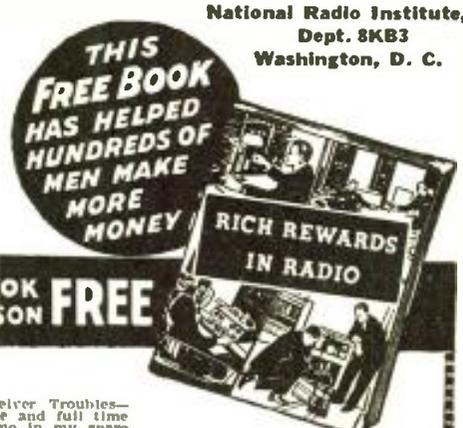**J. E. SMITH, President
National Radio Institute,
Dept. 8KB3
Washington, D. C.**



**GOOD FOR BOTH 64 PAGE BOOK FREE
SAMPLE LESSON FREE**

**J. E. SMITH, President, National Radio Institute,
Dept. 8KB3, Washington, D. C.**

Without obligating me, send your Lesson "Radio Receiver Troubles—Their Cause and Remedy," and free book about spare time and full time Radio opportunities and how I can train for them at home in my spare time—about the N.R.I. Set Servicing Instrument. I am particularly interested in the branch of Radio checked below.

- Radio Service Business of My Own
- Spare Time Radio Repair Work
- Retail Sales of Radio Sets and Equipment
- Service Expert for Retail Stores
- Broadcasting Station Operator
- Aviation Radio Operator
- Loud Speaker Systems, Installations and Service
- Auto Radio Installation and Service
- Television Station Operator
- Service Expert with Radio Factory
- Commercial Radio Station Operator
- All-around Servicing Expert

(If you have not decided which branch you prefer—mail coupon now, for information to help you decide.)

NAME AGE

ADDRESS 14X1

HUGO GERNSBACK, Editor
 H. WINFIELD SECOR, Manag. Editor
 M. HARVEY GERNSBACK, Assoc. Editor

In This Issue

FEATURES

"Radio & Television"—Hugo Gernsback.....	325
Famous Radio Experts Salute the Amateur	326
The Phone HAM and What He Does—Llewellyn Bates Keim, W2IKV	328
Back in the Days of Crashing Spark-Gaps—E. T. Jones	330
Radio Amateurs Record Bird Calls.....	332
Metal Horn Focuses Ultra Short Waves	332
Dem Was the Happy Days—Austin C. Lescarboursa	333
How HAM Radio Saved Shawneetown!—Robert T. Anderson's Own Story	334
The "YL" in Amateur Radio—Beatrice Holman, WIKTG	335
The World Comes to My Room—via HAM Radio—John "Pop" Garvey	336
A Day in the Life of a Busy HAM—E. E. C. England, VE3QL	338
Want to Learn Foreign Languages? Michael Norton, B.A.	341

S-W STATIONS—HOW TO FIND THEM

Short Wave League—On the Ham Bands	342
World Short Wave Stations	346
Let's Listen In with Joe Miller	347

CONSTRUCTOR

An Advanced High-Frequency Receiver—Howard G. McEntee, W2FHP.....	352
Five Meter Super-Regenerative Receiver—Herman Yellin, W2AJL	356
Modulator for the 35 Watt Transmitter—Harry D. Hooton, W8KPX	360

MISCELLANEOUS

What Price HAM Radio?—H. W. Secor	337
Rapid Growth of Radio Amateurs	340
Local HAM Gossip—Lee R. Kemberling.....	343
What Do You Think?	344
Fourth Silver Trophy Award for Best HAM Station Photo	345
Radio "Kinks"—Monthly Prizes	349
Question Box	351
New Short-Wave Apparatus	354

Cover composition by H. Gernsback and Thomas D. Pentz. Photos: HAM Stations, top—C. A. Kowalski, W9KHC; right—Max Otto; left—Eric W. Vogeler, WIJXV. Antennas, top—W. S. Burkhardt, W4DLH; others—C. A. Kowalski.

RADIO & TELEVISION—Published monthly on the tenth of the month. Entered as second-class matter Feb. 15, 1938, at the post office at Springfield, Mass., under the act of March 3, 1879. Trademarks and copyrights by permission of H. Gernsback. Text and illustrations are copyright and may not be reproduced without permission. Subscription price \$2.50 a year in the United States and possessions and Canada, \$3.00 in foreign countries. Make all subscription checks payable to Popular Book Corporation.

Published by Popular Book Corporation. Publication Office—29 Worthington St., Springfield, Mass. Editorial and Executive Offices—99 Hudson St., New York, N.Y. HUGO GERNSBACK, President; H. W. SECOR, Vice-President; EMIL GROSSMAN, Director of Advertising. European Agents: Atlas Publishing and Distributing Co., Ltd., 18 Bride Lane, Fleet St., London, England; Brentano's—London and Paris. Australian Agents: McGill's Agency, 179 Elizabeth St., Melbourne.

Copyright 1938 by H. Gernsback

In the Nov. Issue

- A 110 Volt D.C. Transmitter—Herman A. Yellin, W2AJL.
- A Versatile Cathode-Ray Monitor for the HAM Station—A De Luxe Instrument of Low Cost—C. Walter Palmer, E.E.
- A DX Aerial for Short-Wave Fans—Tom Aso.
- A 5 to 50 Meter 6-Tube Super—Harry D. Hooton, W8KPX.
- One Meter Transmitter—Nelson G. Haas and Carl A. Erbacher.
- Reception with the Flat-Top Beam Antenna—John D. Kraus, W8JK.



Here's a glimpse of the cathode-ray de luxe monitor to be described in the next issue by C. Walter Palmer, E.E. A demonstration proved that it is indeed an instrument of many uses.



Certified Circuits

When you see this seal on a set it is a guarantee that it has been tested and certified in our laboratories, as well as privately in different parts of the country. Only construction—experimental sets are certified.

You need not hesitate to spend money on parts because the set and circuit are bona fide.

This is the only magazine that renders such a service.

TRAIN FOR RADIO IN 12 WEEKS

BY MY QUICK, EASY "LEARN BY DOING" METHOD



Prepare today to enter a real money-making field by my quick, easy way to learn Radio. Here in my school you are trained in **12 weeks** for your start for a better job and a real future. You do actual work on a great outlay of Radio equipment. The remarkable "**Learn-By-Doing**" methods used in the great Coyne Shops train you in **Radio, Television** and sound equipment servicing. Not by books . . . Not by Correspondence . . . But all under the individual guidance of skilled instructors, and only on similar kind of work you will meet out on a real job. My methods make it **easy to learn**—First you are **told how** to do a thing—then you are **shown how** to do it—then you **do the work yourself**. WHERE ELSE CAN YOU FIND SO QUICK AND EASY A WAY TO GET PRACTICAL TRAINING IN THIS GIANT INDUSTRY?

I'LL FINANCE YOUR TRAINING

DON'T LET LACK OF MONEY keep you from sending in the Coupon TODAY. Learn how you can get training first and take more than a year to pay for it after graduation. Make your first payment 60 days after your regular 12 weeks' training period ends. Then take over a year to pay the balance of your tuition in easy monthly payments. Hundreds of ambitious fellows have used this method to get Coyne Training. **FILL IN THE COUPON AND MAIL IT TODAY.** It will bring you the details of this amazingly quick and easy way to get your start towards a good pay job.



H. C. Lewis

Radio—Television—Sound Equipment

Your training at Coyne is in wonderful, modern daylight shops on the finest kind of RADIO, TELEVISION and SOUND EQUIPMENT. Television is sure to come as a commercial industry, whether this year or next. Talking Picture and Public Address Systems offer opportunities for the trained man. Everything possible has been done to make your stay at Coyne happy and healthful as well as profitable.

Electric Refrigeration Training Included at No Extra Cost

This combination Training (Radio and Refrigeration) can be of great value to you. Whether you go into business for yourself or get a job working for a Radio Sales and Service organization, the fact that you are trained in servicing Electric Refrigerators should be profitable to you. Many Radio Manufacturers also make Electric Refrigerators and men with this combination training are much more valuable to these employers. You can NOW get this training without extra cost.

No Advanced Education or Previous Experience Needed

If you can read and write simple English and are ambitious you can be trained the Coyne way—by actual experience on a wide variety of up-to-date Superheterodyne sets, oscillators, analyzers, and test instruments. You learn how to operate television receiving and transmitting equipment and how to install, test and service public address systems and sound picture equipment. Coyne training also helps prepare you to qualify for a government license examination as Amateur Broadcast or Telegraph Radio Operator and to know Code and Department of Commerce rules. Send coupon for all details.

Part Time Work While Learning Employment Service after Graduation

If you need part time work to help pay living expenses while training, my Employment Department will help you get it. They will also give you Life-time Employment Service after you graduate.

Mail Coupon Today I'll Send You All the Facts

Get the new "Coyne Opportunity Catalog," giving all facts about Coyne Training. Photographs of Shops showing students at work on modern radio equipment under the personal supervision of Coyne Expert Instructors. Also details of my Part Time Employment Offer, Pay After Graduation Plan and Graduate Employment Service. Yours without cost. Simply Mail the Coupon.



H. C. LEWIS, President,
Radio Division, Coyne Electrical School,
500 S. Paulina St., Dept. 78-2K, Chicago, Ill.

Send me your big FREE Book about Coyne Training and give me all details regarding your "Part Time Employment Offer" and "Pay After Graduation Plan" of easy, monthly payments.

NAME.....AGE.....
ADDRESS.....
CITY.....STATE.....

H. C. LEWIS, President RADIO DIVISION Founded 1899
COYNE ELECTRICAL SCHOOL
500 S. Paulina St., Dept. 78-2K, Chicago, Ill.

Please say you saw it in RADIO & TELEVISION



HUGO GERNSBACK, EDITOR

H. WINFIELD SECOR, MANAGING EDITOR

"RADIO & TELEVISION"

HUGO GERNSBACK, Editor

● WHEN in June, 1930, I published the first issue of this magazine under the name of *SHORT WAVE CRAFT*, the short wave art had just gotten under way and its wonders attracted many thousands of individuals. Particularly was this true of the radio experimenters and constructors who were intensely interested in building one and two tube short wave receivers, with which it was perfectly possible, even in those days, to receive radio programs from foreign countries.

As the art progressed, during the next few years, the incentive to build short wave receivers by private individuals slowed down, for the reason that commercial sets were appearing in ever increasing numbers and it became possible to buy such sets at constantly lower prices.

When a few short years ago the all-wave radio receivers made their appearance, the incentive to build one, two and three tube short wave sets was still further diminished, while today practically all radio sets that you may purchase in the open market are built for broadcast and short wave reception.

History repeated itself in this respect, duplicating the pioneer days of broadcasting. In the early 20's when you could not buy a complete radio set, the experimenter and builder had a paradise of his own. Then about 1925 the commercial radio sets made their appearance, which spelled the doom of over one million home radio set-builders—except for a group of about 100,000 builders who still continued to construct radio sets for the mere enjoyment of it. It was this class who, about 1930, graduated into Short Waves and who were kept busy constructing receivers up to the past few years, when again the commercial sets overtook them and reduced the incentive for building purely short wave sets.

By all this I do not mean that there are no radio set-builders left in the United States today. Quite to the contrary I believe their name is still legion and I know there are even today between 75,000 and 100,000 individuals left who are interested in radio building and radio experimentation.

Changing times and changing conditions naturally influence these builders. Many go into other lines, become engineers, engage in the manufacture of radio material themselves, become servicemen, etc. But in their place you

will find every year a new crop of radio enthusiasts, who as yet have not had a taste of radio experimentation and to whom the entire field is still new.

During the past few years we have not had a vital reduction in radio enthusiasts, but to the contrary there has often been a healthy increase. This may best be shown by the continuous and steady growth of those radio experimenters called *radio amateurs*, who now have rolled up **A GREATER TOTAL THAN HAS EXISTED AT ANY TIME IN THE HISTORY OF AMATEUR RADIO IN THIS COUNTRY.**

Changing conditions in radio make necessary other changes within the industry. One of the minor changes—in order to keep abreast of the times—has been the change of the name of this magazine.

For some time we felt that the name *SHORT WAVE & TELEVISION* was not broad enough to cover this fast growing industry. Moreover, the distinction between short waves and other radio waves is no longer as marked as it was eight years ago when this magazine was launched. For this reason it was felt that the change of the title to *RADIO & TELEVISION* would be more in keeping with the changing times and would not impede the progress of the magazine.

On the other hand, the new title will broaden the field of the magazine, particularly the field of radio experimentation and amateur radio.

No radical change of editorial policy is contemplated in *RADIO & TELEVISION*. The magazine will continue to serve the thousands of radio experimenters and radio amateurs and particularly the new-comer in radio experimentation, as well as the man who hopes to break into amateur radio.


Particular attention will be paid, as of old, to the radio beginner, that is the young man who knows nothing of radio today and who will be one of the countless thousands of radio experts of tomorrow.

There is no other magazine today in the United States which serves the radio beginner and *RADIO & TELEVISION* will continue in helping to shape the radio destiny of those serious-minded young people, who are just getting under way in radio and who, ten years hence, will be the backbone of the radio industry itself.

October, 1938

FAMOUS RADIO EXPERTS

DR. LEE DE FOREST, Ph.D., Sc.D.

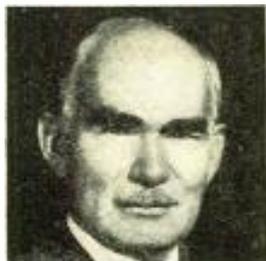

Dr. de Forest—world-famous for his invention of the audion, which included a grid in the vacuum tube. This made possible our present marvelous V.T. amplifiers, modulators and transmitters. He was also a pioneer in radio telephony.


● AT this time it is fitting to recall briefly the part played by the "Ham" and amateur in Radio's development. The early amateurs, between 1906 and '12, were usually considered by all "professional" operators, commercial

and naval, simply as unmitigated pests, to be legislatively suppressed. How often was a ship operator told by some small boy (location unknown) whom he had just asked to "Shut up"—"G.T.H. this is a free country. Ain't the air free?" Then came the Radio Act of 1912, the irksome license requirements, and all Hams thrust tyrannically into the cellar (or attic) below 200 meters, considered then as a bleak and unprofitable ethereal Siheria.

The World War first demonstrated the priceless value to the nation of the radio amateur, as has every crisis of flood, storm, or earthquake since. While the "commercials" were struggling for dependable trans-oceanic communication with cumbersome alternators, arc generators, and even spark transmitters, using thousands of watts of power on the "very valuable" wavelengths from 600 to 20,000 meters, (Continued on page 358)

DR. FRANK CONRAD

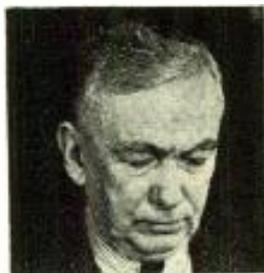Assistant Chief Engineer, Westinghouse Electric & Manufacturing Co.



Dr. Conrad—the "father of short waves" in America. He carried out extensive tests in the early days of short waves which laid the groundwork for our present structure.

● LIKE many others, my first experiences in radio came when I was an amateur. The first call letters assigned me in 1915 were 8XK. I worked under this call for many years.

My first radio set was hand-built so that I might obtain, for my own personal information, Arlington Time Signals. After this first set was constructed and ready to operate, instead of getting Washington, I actually received the signals from another amateur, John Coleman, who lived a few squares distant from me in Pittsburgh.

Later as my experience in radio grew and equipment became more extensive, I corresponded with many amateurs in various parts of the country. Some of the pioneering testing was reported by these correspondents. They aided the art in those early days by keeping in touch with those who were engaged in trying out new ideas, many of them revolutionary at the time.

I remember, too, that after broadcasting began and the commercial stations became powerful, that the amateurs whose spark sets often blasted early programs were quick to respond to requests that they shift their hours of operation to wavelengths bands that did not interfere.

Many executives, prominent in radio today, began their careers as amateurs whose experience became their springboard to commercial jobs with broadcasting concerns and radio manufacturers.

I feel even today a strong bond of fellowship with all radio amateurs who now, just as in the old days, carry on their own individual experimenting and their communications, not only in this country but with other amateurs in all parts of the world.

One of the most important developments of radio has been in the so-called short-wave field. Prior to 1921 it was believed that these high frequencies could carry only a few miles as the skip-distance effect had not, at that time been thoroughly investigated. The common wavelength for radio communication was somewhere around 300 meters, except for government stations such as Arlington.

Now these short waves, in which the modern amateur operates, carry to every part of the globe and in this band are the future possibilities for an expansion of radio's service.

There will always be a definite place in radio for the amateur. As an individual and as a group my experience with him has been worthwhile. My heartiest wishes are that long may he continue to be a part of the radio world.

DR. E. F. W. ALEXANDERSON

Consulting Engineer, General Electric Company



Dr. Alexanderson—famous radio research engineer and one of America's radio pioneers. Designed early high frequency generators and basic antennas. Demonstrated "large screen" television ten years ago.

● THE amateur has always been a pioneer exploring the latest developments in radio. When we did our first experimental broadcasting from Schenectady in 1916, we received many letters from amateurs reporting on the quality of the reception. Radio telephony was then new and these reports served us both as a guide in our technical endeavor and as encouragement in our efforts along new lines. Later, when broadcasting was well established, the amateurs were among the first to explore the use of short waves over long distances; thus again when we broadcast television regularly from Schenectady in 1928 we had to depend largely upon the amateur for forming an opinion on the value and practicability of long distance television. Among the amateurs who sent us regular reports were one in Los Angeles and another in Germany. The fact that clear images could be received occasionally was interesting and encouraging, but we concluded that the results were too unreliable for regular broadcasting and these tests were discontinued.

It is my sincere hope that the amateurs will continue their pioneer work. The wavelengths below one meter is a large and unexplored field and even if it is found that reliable communication is limited to the visual horizon, there are interesting possibilities for amateurs to form chains to relay such waves over long distances. The amateurs may also do valuable work in popularizing new developments in radio transmitters and receivers, such as the Armstrong system of frequency modulation.

RALPH R. BEAL

Research Director, Radio Corporation of America

Ralph Beal holds the important post of Research Director of RCA and he has had an extensive career in American radio. As a practical engineer, his word to the American radio amateur is very welcome.



● THE American radio amateur occupies a position that is fast becoming unique in the field of world radio. Here, we look upon the radio amateur as an American institution, and it is apparent that in a comparatively short time he will be limited almost completely to the Americas. An indication of this is to be found in estimates which show that out of a world total of 70,000 licenses, the United States has approximately 48,000.

The American amateur's status is based upon two fundamentals. He has at his disposal the knowledge and the material with which he performs a service of value to himself, to the public, and to the radio industry; and he has the personal freedom to perform this service, privately or publicly. He lives under a democratic form of government that recognizes the right to individual freedom, while in other sections of the world the amateur is permitted to exist only under restricting regulations, if at all.

Both the public and the radio industry owe debts of gratitude to the American amateur. He stands (Continued on page 358)

O. B. HANSON

Vice-president and Chief Engineer, National Broadcasting Company



Mr. Hanson—chief engineer of the NBC, is responsible for the many new and valuable engineering achievements put into practice over the vast network operated by his company.

● MOST of us who now control the technical operations of radio broadcasting began our careers as "hams." Some of us still tinker in the amateur hands, trying our hands at new circuits and testing the (Continued on page 358)

SALUTE THE AMATEUR

JOHN V. L. HOGAN

Consulting Engineer



Allied News-Photo.

Mr. Hogan is well known to American amateurs for his work in radio, particularly in television and facsimile. Also his "high fidelity" transmitting station now in operation near New York City, marks a new departure in broadcasting.

- IT seems to me that the present status of the radio amateur is vastly improved, in comparison to his standing in "the old days," and that there is little or no uncertainty as to his future. Because the radio amateur

is one who loves radio, and who works in a communication field closely parallel to that of commercial radio, he generally is able to contribute usefully to the service of radio. His contribution may be in his experienced and skilful work, it may be by way of invention, or it may simply be the use of his own equipment to provide a valuable communication link in some emergency. In any event, amateur radio operations always have been (and always should be) encouraged, for they are good for the science, the art and the business of radio. Better yet, they are good for the amateur himself.

Looking back to my own amateur days, from 1904 to 1909, I feel that what I then learned by practical experience in the use of radio apparatus has been of inestimable value in my later professional work. There is perhaps no better way to learn what radio is about and how it works than to study the literature of the art and to apply its teachings in one's own amateur station. Today the amateur has the benefit of finer apparatus, better books and periodicals, and greater communication opportunities than existed in the early 1900's. In those days one could not find hundreds of fellow hams to talk with over the air, and we had no radiotelephony and no vacuum tubes. There were so few stations that no licensing system was needed to limit interference, and, while we had almost infinite opportunity to copy messages from nearby or distant ship and shore stations, we usually could find only a few friends to whom we might transmit.

Amateur conditions have changed for the better since those times, but the old excitement of improving one's apparatus and the old romance of receiving over great distances remain the same. And so does the opportunity for the progressive amateur to move forward into a successful professional career.

C. W. HORN

Director of Research & Development, National Broadcasting Company

Mr. Horn, like Dr. Conrad, has been responsible for a great deal of our short-wave engineering triumphs. Thousands of tests were made with transmitters, receivers and antennas by Mr. Horn when short waves were believed to be practically useless.



- THE average person thinks of the radio amateur as something of a "bug" who loves to operate his station to communicate with his friends both far and near. In doing so he sometimes causes some interference to broadcast reception, which results in occasional letters to broadcasting stations or the United States Radio Supervisor. I feel that the true worth of the amateur is not usually understood, sometimes even by the amateur himself.

In the old days when the amateurs were using spark sets, they caused a great deal of interference to broadcast reception, but when the problem became serious the amateurs cooperatively undertook to cure the evil, and succeeded almost 100 per cent. As a pioneer in the broadcasting game, I received many complaints, and there was even action taken to restrict the amateur. Instead of forwarding these complaints to the governmental authorities, I usually referred them directly back to the amateur, and frequently to the Amateur Radio Relay League, because I knew that many of the complaints were unjustified, and also that the amateurs themselves would correct their apparatus and eliminate the difficulty. I am happy to state that not one of the thousands of complaints that I received was ever forwarded to a government inspector.

Perhaps my attitude was due to my having been one of the old pioneer amateurs.

(Continued on page 358)

JAMES MILLEN

"Jim" Millen, as he is known affectionately to thousands of "hams," is well known for his development of high-class "ham" transmitting and receiving equipment. He has also written many valuable articles and books on short waves, and his personality and engineering ability have been a powerful factor in amateur radio development.



- IT seems to me that many of the present day amateurs are missing one of the most important benefits to be derived from amateur radio, in confining their contacts with other hams to a standardized description of their rigs, type of antennas, and the weather. Amateur radio affords too great an opportunity for the exchange of opinions, information, and ideas on worth-while subjects of mutual interest. If one's hobby is amateur radio, and he wants to confine his transmissions to a discussion of amateur equipment, certainly there is ample material for worth-while discussion other than the endless repetition of a highly condensed station description.

On the other hand, amateur radio affords such an unusual opportunity to discuss other hobbies and subjects such as photography, stamp collecting, model airplane construction, gardening, etc., that it is a shame that more of us do not use this modern communication system as an entering medium to other new, interesting, and educational fields.

R. A. HEISING

Bell Telephone Laboratories

The name of Heising is known to every radio amateur. The famous Bell Telephone Laboratories are to be congratulated on having associated with them a man of such far-sighted engineering introspection as Mr. Heising. His researches have greatly benefited American radio development.



- IT has been said that the radio amateur has made many of the important technical advances in radio. That certainly is true. It is very often the man who can bring a new point of view into a problem who can find a successful answer.

But who is an amateur? It might surprise one to think of the Bell System being a radio amateur at one time, but that is the case. In 1914 the American Telephone and Telegraph Company put into commercial use as wire telephone amplifiers the high vacuum tubes that had been developed in its laboratory. Telephone executives began to think they might experiment in radio to see what there was to it. They hired a number of young men right out of college, including the writer, and began active work. None of the new men, nor the directing engineers, were radio men, nor did they have any practical knowledge of radio. They were all rank amateurs in that respect.


They worked in the laboratory first. They built a transmitter at Montauk and a receiver at Wilmington and made their first radio telephone tests. They built a transmitter at Arlington and sent out receivers to remote places and made longer radio telephone tests. Then they made other sets at the request of the Navy Department for experimental use. All this time there was no plan for commercial exploitation. It was all to see what could be done.

But, like all amateurs, their experience was valuable to the government when we got into the war. The radio telephone experience of the Bell System was called upon immediately to provide something of military value and use. As a result, radio telephones were made for submarine chasers to give instant communication in convoy service, and radio telephones were made for airplane spotting service and formation flying. These were the first practical radio telephones in history. They contained new circuits that were so much more efficient than those in previous radio telephones and so much simpler in construction and operation, that they were instantly adopted and continued to be used for many years. Because the engineers who developed them had a substantial background of telephone principles and practices, the purely radio part was backed up by the important wire part of properly designed telephone accessories for satisfactory reproduction of speech. It was the happy combination of the fresh viewpoint of the amateur backed up by the seasoned judgment of the expert that made the radio telephone possible, and which brought the broadcasting art to its present high quality.

(Article by Comdr. R. H. G. Matthews appears on page 358)

The PHONE HAM and What He

Llewellyn Bates Keim,

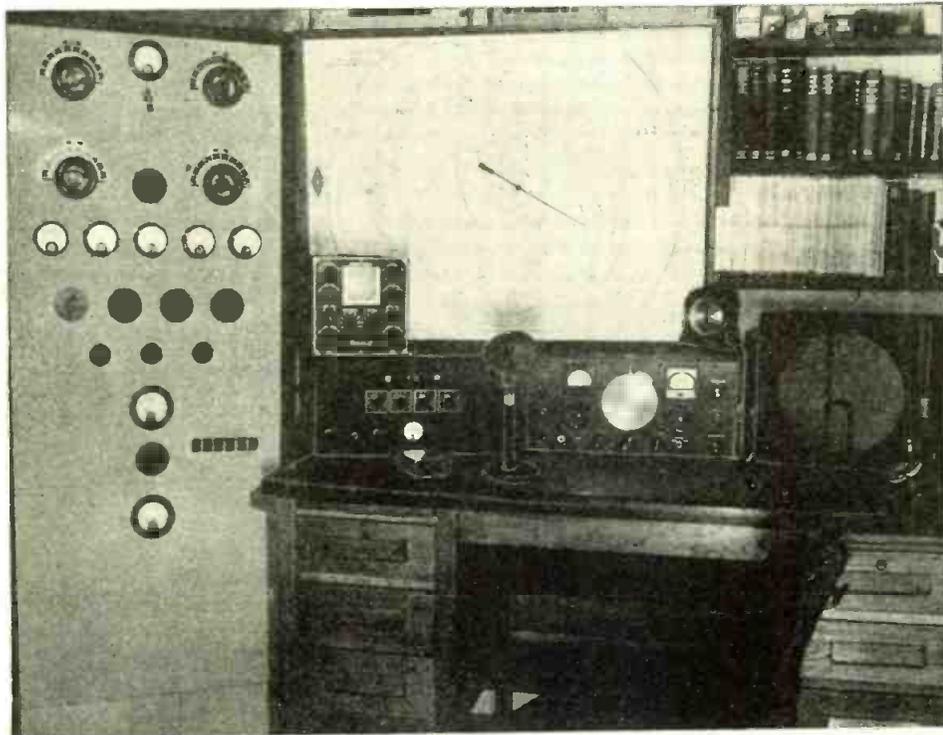

W2BTP. A neat and effective 20 meter station, particularly interesting because of the rotating antenna installation. The large map pointer turns with the antenna, indicating the direction in which the signal is traveling.

Many people ask — "What does a *phone ham* do?" Mr. Keim is an outstanding American radio amateur who carries on phone contacts with stations both in this country and abroad; he here tells many unusual things about the "phone ham".

and hundreds of others like them, have by their interest and devotion to their hobby, made possible this whole thing known as *broadcasting*, and it will ever be a lasting tribute to the amateur, that hardly a broadcast station exists in this or any other country which does not number at least one amateur on its staff. The so-called short waves were once considered useless for commercial use, so the amateur was told to play there, and, to the consternation of his more learned elders, he turned this part of the ether spectrum into the most valuable of all the com-


● HAVE you ever stopped to wonder, while tuning on the short wave bands of your broadcast receiver, just what sort of "Genus Homo" is this thing known as a *radio amateur*, and just why is he there? Though the amateur fraternity is divided into two groups, those who communicate by the Continental Morse code and its language of dots and dashes, and those who use telephony, this latter group—although smaller in number—is the more important. Important, I repeat, for it is through them that the public has largely learned of this vast army of experimenters with Hertzian waves.

Popular misconception has associated the radio amateur with a performer on a broadcast hour involving non-professional talent as its entertainment vehicle. But the genuine "ham" dates back many years before the war, when the amateurs gave the Brooklyn Navy Yard keen competition, before the days of licensing authorities or the Federal Communications Commission. The art of wireless communication has made great strides in the last thirty years, and ever in the vanguard of this march of progress has been the *amateur*, with his omnipresent tubes, coils, and condensers.

Early Phone Hams Gave Us Broadcasting

Lest you may wonder why there is a spot on the dials of your receiver, devoted to this activity, instead of providing an operatic or educational program, for your entertainment, let me trace a little of the history of the *phone ham* as a class. All of our present-day broadcasting is due directly to the activities of some of the earliest *hams*, and among them the names of de Forest, Cannon and Conrad are ranked as the *pioneers*. These,

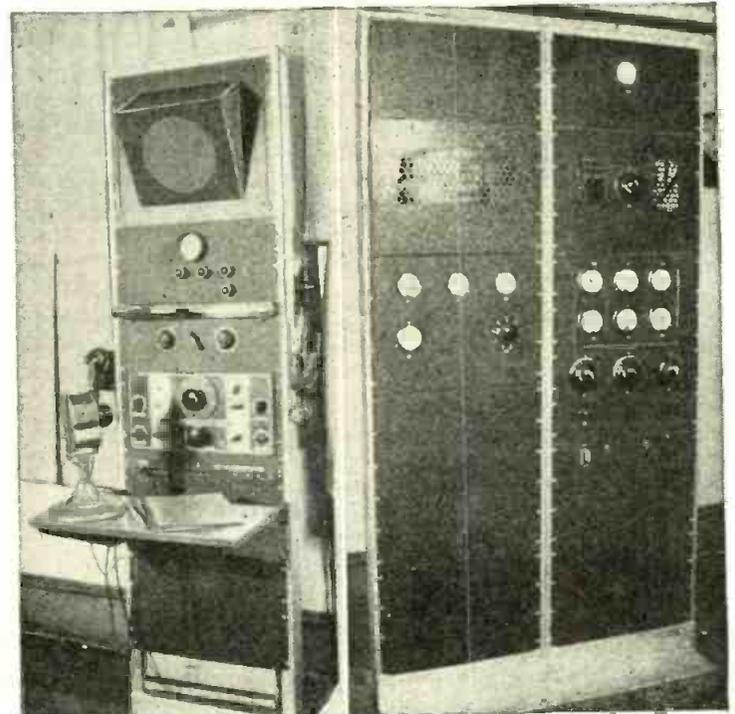Below—Radio Amateur Station, W8KXN, Plattsburgh, New York. Located deep in the Adirondack Mountains, Mr. Lambert is well known on 75 meters, throughout the Eastern part of the U.S. and in England.




Does

W2IKV

Boy, what an amateur phone station! The call letters are W5HDK and the equipment includes professional type receivers and a transmitter designed and built by W5JC.

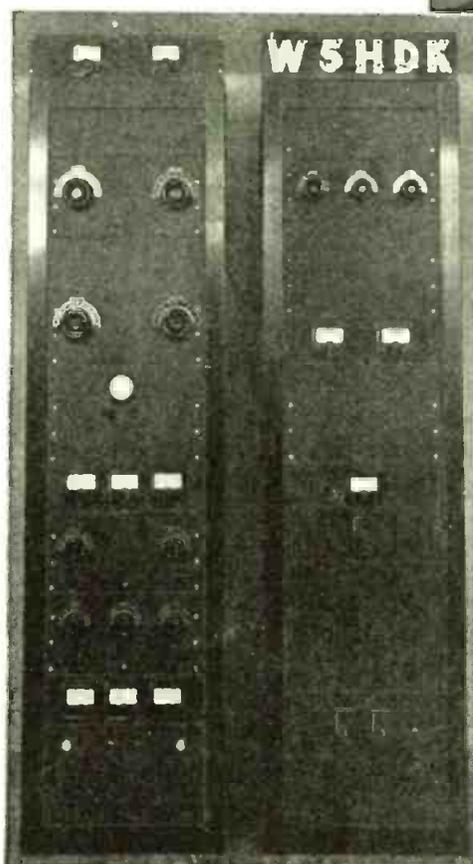In the photo below of the transmitter, note the neon call letters above the modulator rack. The r.f. rack contains two transmitters of one kilowatt each, for operation on 10 and 160 meters.



munication frequencies. As a pioneer, *the radio amateur has no master.*

As we mentioned above, there are telegraph devotees, and those to whom the radio telephone is the more interesting. It is with this latter group that we are more concerned for the moment.

Phone Ham May Be 16 or 60

Let us never lose sight of the fact that all *phone hams* are also telegraphers, and the amateur who follows along this track

is an equally important part of the fraternity, providing a great number of skilled operators ever ready to serve their country in time of emergency. But the general public knows little of them and their activities, since the average household receiver is not equipped to render code signals intelligible, and even fewer average householders can read the dots and dashes. This does not hold true of the daily conversations of the phone ham, and it is this fellow in whom we are interested.

Statistics show that he may be sixteen or sixty, a wealthy corporation executive or a young lad striving hard to save enough to acquire that new piece of apparatus so badly needed in his rig, yet all of them meet on one common ground—they are brother hams. The friendships they make over the air are far, wide and lifelong, and all that each knows of his friend is the way he handles his key, or the sound of his voice, and the personality behind the microphone.

Ranging from the amateur who has purchased his equipment completely assembled, to the lad who builds his all, there is every possible stage in between. To each one the hobby holds forth a different interest. Some wish constantly to try out a new circuit by arranging their available gear into a new combination, claimed by a brother ham to give more power and a louder signal at the far end; others wish only to develop their operating ability and prowess at contacting the more elusive of dx stations. Still others are chiefly interested in the way the several hands available for amateur communications behave throughout the year, experimenting with various antennas until they can foretell what type of conditions to expect. This study of the propagation of electric waves is perhaps the most interesting of problems an amateur

can set for himself, the field is the largest and least crowded, and in the end, the results may be the most interesting. No matter what else he may be doing, however, the true phone ham is constantly delving into some problem, and the desire for knowledge is enormous.

5 Bands Open to Phone Hams

What goes on inside of a ham station during a typical day's operating would be hard to relate, as there are so many activities that a short article could hardly do them all justice. There are five bands open to radiotelephone operation, provided the amateur holds the Class A license, and each of these has its devotees, but this does not say that an amateur may not operate on all bands. Many do, and advisedly so, thereby covering the widest scope of activity and making the most of their hobby. The wise amateur selects his operating frequency to cover the distance he wishes to work, and, transmitting conditions being favorable, he contacts his station with the least interference to his brother hams. Local contacts, those within a radius of about twenty-five miles, now take place mostly on five meters, a beehive of phone activity in the metropolitan centers, and at times this band, too, offers signals from surprisingly great distances.

One never knows what thrills lie in store in this great indoor pastime. Because of the simpler nature of equipment needed to set up a station on five meters, many newcomers make their bow to the air waves here, and even the more seasoned amateur finds pleasure in outfitting his auto or even his boat, if he is fortunate enough to own one, with a complete station, so that he may try his skill in mobile operation. This

(Continued on page 364)

Back in the CRASHING

E. T. Jones



Experimenter-Amateur 5QW (until 1915). Author, Inventor, Engineer, Chief Radio Operator "WNU"—signed "Z." First Editor "Radio News"—Member Institute Radio Engineers, Sales Executive and presently Manager, Advertising and Sales Promotion—Engineering Products, RCA Manufacturing Co., Camden, N. J.

● AFTER I tell you that I have been searching twenty-nine years for the radio bug that bit me during the latter part of 1909, you'll be disappointed when you fail to find me hiding behind a set of long gray whiskers. While I have not as yet seen this strange yet fascinating creature, he must look something like an octopus with about forty times the number of tentacles because once he grabs you there is no "letting go." It was during the autumn of 1909 when I first felt its pleasant bite. I had just listened to telegraph signals coming from apparently nowhere—right out of the air—without the aid of connecting wires between the point of transmission and reception. Unbelievable—but there the signals were, loud and clear. My hair stood on end—it was like receiving a great shock—it registered a long-lasting impression that is just as realistic today as it was then—29 years ago.

The "First"
The only book on the subject available to me at the time was Hugo Gernsback's MODERN ELECTRICS. I read each issue at




What's the duster for? Don't ask! Anyhow, it's an honest-to-goodness "ham" station—vintage of 1910—and it appeared in the "Wireless Telegraph" contest department in the December 1910 issue of "Modern Electrics" magazine. (Published and edited by Hugo Gernsback; first issue May, 1908!)

least *one dozen times*, while waiting patiently for the next issue to arrive. I read interesting accounts of extremely successful Amateurs who were able to copy ships and radio stations *from tremendous distances* up to and including 75 miles! Of course they employed super receiving stations—especially the antennae—4 to 8 wires, 200 to 300 feet in length, supported by two 80 foot masts. Then I would gaze on their pictures—garbed in white coats (for scientific atmosphere, I guess)—comfortably perched in front of their equipment with their noses pointed skyward, as though they had Steinmetz, Edison and Marconi in the palms of their hands. For one most distinguished pose I refer you to page 527, December issue 1910 of MODERN ELECTRICS.

When the modern hams of today learn from the following, how I constructed my first radio receiving set, they'll probably page Mr. Ripley, but it's the truth! Fortunately in those days even the electric street cars employed dry cells to ring the bell announcing your desire to "take leave" of the contraption (and it was a relief, I assure you). I resided but three squares from a central car-barn where these crates were overhauled. That barn became the most important building in the U.S.A. insofar as I was concerned. It supplied me with numerous partially dead dry cells. In those days flat carbons were used for the *positive* electrodes in dry cells. By removing the carbon strips, cutting and drilling them as required, an excellent *carbon detector* was constructed with the aid of a sewing needle, a porcelain knob, and a few pieces of hardware. (See figure No. 1.) Another of the partially dead dry cells furnished the small amount of current required for the proper operation of the detector, in series with the highly sensitive (???) 75 ohm watch-case telephone receiver. Diagram of connection is shown in figure No. 2.

The rig appeared to work perfectly. Stations were coming in from all over the world, so it seemed. This belief continued until I finally reached the point where I could copy 25 words per minute, at which time I discovered, *to my great embarrassment*, that most of these supposed signals were nothing more than mechanical vibrations being picked up by the ultra sensitive (or should I say *ultra microphonic?*) carbon detector. At least it proved one thing—it worked! Believe it or not, I was picking up signals from a 25 kw. station located about 2 miles from my home! Station HB—United Fruit Company, New Orleans, La. I made another great discovery which was as embarrassing as the microphonic re-

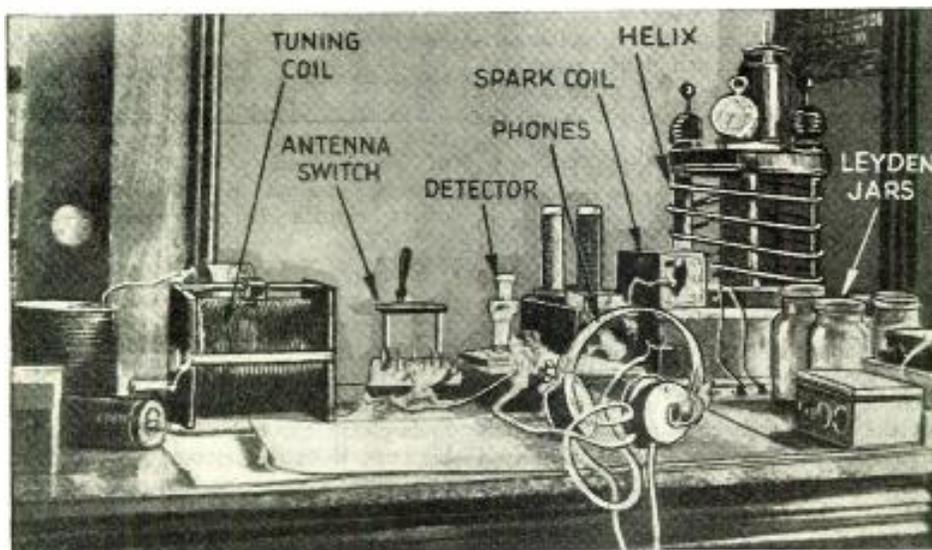E. T. Jones' first real attempt at building a "ham radio station."




Days of SPARK-GAPS

Says E. T. J.—"When the radio 'ham bug' bites you, you stay bit!"

ceptions. I found that I could read the signals from that station without the aid of a radio receiver—when the wind was blowing in the right direction—by merely sticking my head out of the window. (And I didn't get Chile—Bah!) Station HB was using a 25 kw. Fessenden 500 cycle rotary gap, *without mufflers*, which—at the station proper—sounded like an earthquake every time a spark jumped the gap. Some fun, eh keed? Ask good old "Dot" how loud it was!

of both ends of the primary tubing, and would have tried another if we could have gotten it out of the side.

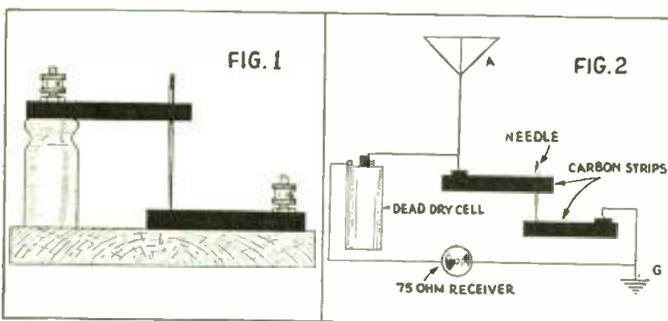It is this kind of so-called shennanigans which was and still is happening daily and deep into the night in thousands of homes in America that stamps Amateurs as the *real pioneers* of the radio industry. Without their spirit of stick-to-itiveness and their dogged determination to succeed under the most trying and heart-rending conditions, I doubt very much if the radio art would



The extremely simple carbon-steel needle microphone detector used back in those palmy days by E. T. Jones.

We Strike "Pay Dirt"!

We amateurs had been hearing strange rumors about a mysterious crystal which would supplant the carbon (microphonic) detector. This precious crystal was known as *Silicon*. From what little information we gathered, it appeared as though it would cost a king's ransom to take even as much as a peek at it under lock and key. It was soon learned that a local iron foundry used great quantities of this material in the treatment of metals. I won't take up valuable space telling you about the tremendous problem this company had on their hands from that time on. Sooooo—to make a long story short—they gave us enough of the crystals to last us a life-time in order to get rid of us. This marked the beginning of all future nervous breakdown cases—the *cat-whisker era* I call it. This ancient art was revived in 1922—remember?


With the aid and encouragement of Hugo Gernsback, the *Father of Amateur Radio*, we tried everything under the sun, from sticking needles in a spud (potato to you, Oswald) to the use of carbide enclosed in glass tubes. We made *permanently adjusted* crystal detectors, sealed in beeswax, that when dropped on the floor would retain their precious adjustments! We made loose couplers with secondaries coming out

have progressed to the lofty heights it has reached today.



Wavelength—An Unknown Quantity

Then began the era of *all-wave* transmitters—from 10 to 40,000 meters—all at the same time!! Nice coverage—if you can get it today. Better see F.C.C. first though. Our transmitters were about as wide open as Tony Galento is when he approaches his opponent. Wavelength?—let me see—what on earth could that have been at that time? No one paid any attention to it—the amateur who had the longest and largest antenna and the largest tuning helix was the nertz. The race was on, loose couplers that could have tuned to 100,000 meters were built and the champion of them all was Johnny Dobbins—now at WNU, New Orleans—who used a hat shipping container for the primary of his loose coupler! It measured about two feet in diameter and four feet in length—wound full of No. 22 DCC wire with a double slider—*E. I. Co.'s famous ball bearing sliders*.

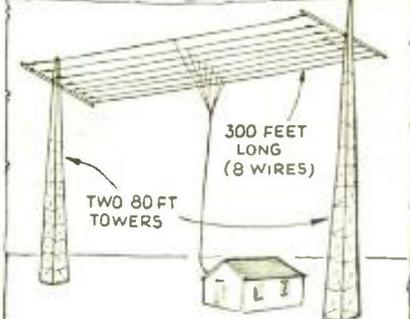
Then came the race for POWER (did I hear anyone paging a broadcast station in the lobby of the F.C.C. office?). My contribution consisted of a One Kilowatt OPEN CORE transformer floating in a bath of oil to prevent FIRE! The boiling oil came in handy during the winter months—it kept the shack warm. With
(Continued on page 370)



IN 1909 HAMS HEARD SHIPS 75 MILES AWAY!

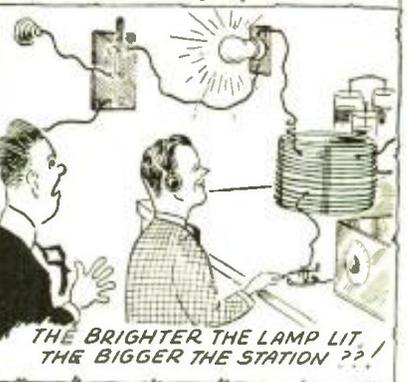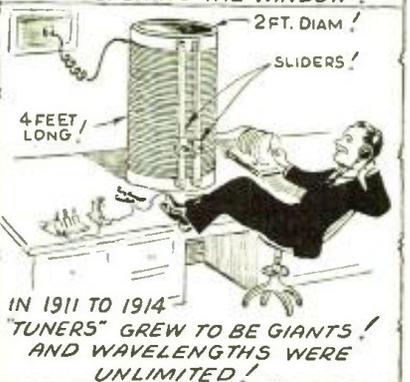

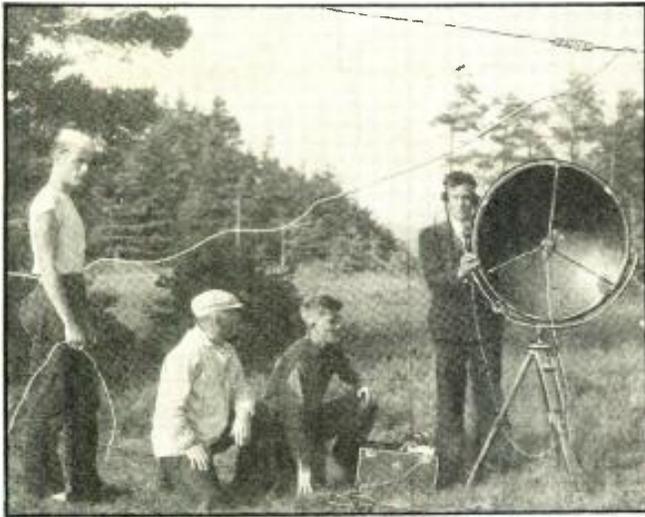¹W. E. Beakes—who signed "E"—now Vice-President and General Manager, Tropical Radio Tel. Co., Boston, Mass.



One of the radio amateurs who helped to trap wild bird calls is seen standing beside the parabolic microphone. Speech amplifier and standard "mike" used by the expedition are seen at the right.

● ONE of the unique projects attempted at Kent's Island (by the Bowdoin Scientific Expedition) was the recording of bird songs by means of radio. The recordings were made possible by the cooperation of Mr. Albert R. Brand of the Laboratory of Ornithology, Cornell University, Ithaca, New York.

Since it was impracticable to transport the heavy Ford sound truck to Kent's Island, it was driven to Eastport, thence carried by steamship to Grand Manan, the nearest accessible point to Kent's Island. From Kent's Island the bird songs were transmitted by the Station's *short wave* amateur radio and picked up by the sound truck stationed at Seal Cove, Grand Manan, eight miles distant.


To the pet raven "Croaky" went the distinction of being the

Radio Amateurs Help to Record *Bird Calls*

first bird to transmit his harsh sonorous voice over the air to be permanently recorded. Calls from the gull colony nearly a *mile* away were also picked up with the aid of a parabolic reflector in the focus of which a microphone was placed.

The recordings of the petrel presented a more difficult problem. It was necessary to set up a sensitive microphone very near the burrows of the nesting colony. The petrel utters its song at very uncertain and irregular intervals. The best performances are given only at night between ten in the evening and three o'clock in the morning. Furthermore, the birds are most active when the

(Continued on page 380)

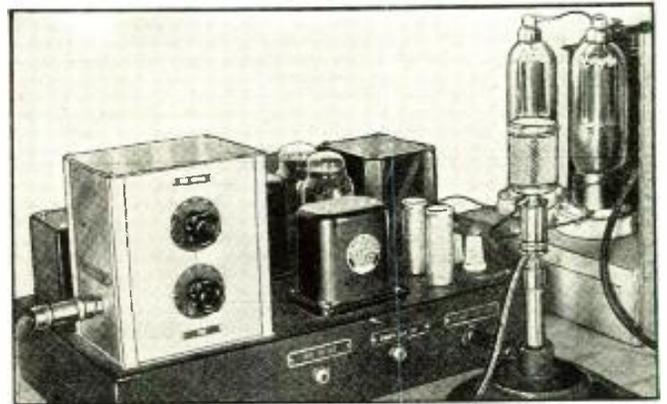

Metal Horn Focuses Ultra Short Waves

● A SIMPLE and efficient means of producing a beam of ultra-high frequency radio waves in which a flared metal horn is used as an antenna to project the waves into space in much the same manner as acoustical horns can concentrate sound waves into a beam, has been developed in the communication laboratories of the Massachusetts Institute of Technology by Dr. Wilmer L. Barrow. This new development in directive "antennas" was described by Dr. Barrow in a paper presented at the joint meeting of the Institute of Radio Engineers and the International Scientific


Radio Union and aroused great interest.

The electromagnetic horn or trumpet should find early application to micro-ray communication, in which the intelligence is sent over a narrow pencil-like radio beam at wavelengths only about a tenth of a meter long. Other applications may be to airplane and ship navigation, and similar problems to which these very short waves are adapted. This range of wavelengths, roughly below one meter in length, is rapidly being explored and being put to practical use. For example, several micro-wave communication channels have been

in use in Europe for three or four years. The one across the English Channel is perhaps the best known. These micro-waves and the horn antenna appear to be almost ideally suited for application to the "blind" landing of airplanes under conditions of fog, snow or rain, although a further increase in the reliability and ruggedness of the sending and receiving apparatus is needed before the shorter micro-waves can be safely employed here.


The possibilities of radiating waves from electromagnetic horns was first described

(Continued on page 380)

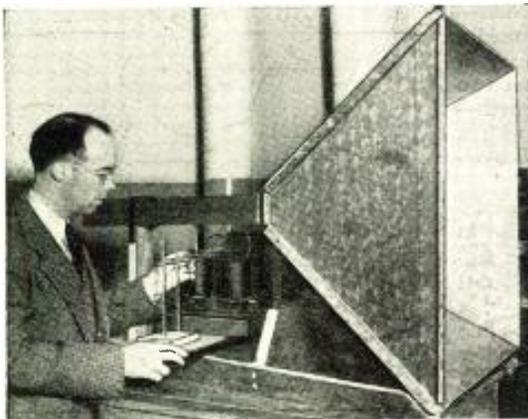

Left—Metal horn recently devised and successfully used by Prof. Wilmer L. Barrow in focusing ultra short waves; waves in the region of 300 to 4300 megacycles (wavelengths of from 1 meter to 7 centimeters).

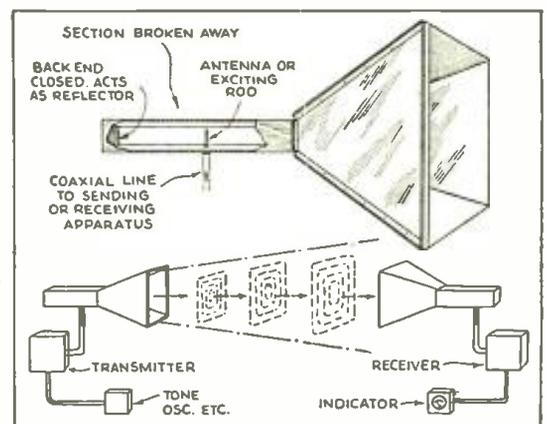Right—Detail of wave focusing horn developed by Prof. Barrow at the Massachusetts Institute of Technology. The receiver may be fitted with a corresponding focusing horn.



Dem was the HAPPY DAYS

Austin C. Lescarboua

Mr. Lescarboua, one of the real early "hams" in this country, gives us some very interesting side-lights on the experiences he encountered while operating one of the first "spark-coil" and "crystal-detector" stations.

● IF that Marconi operator hadn't made such an impression on my young mind as he sat before a huge spark coil emitting its dazzling sparks, this story wouldn't have been written. However, upon the occasion of the first electrical exposition in New York City back in 1907, which featured a Marconi wireless demonstration from one end of the old Madison Square Garden to the other, Yours Truly decided then and there upon an amateur wireless career.

There wasn't much choice of equipment in those early days, thirty years ago. The commercial stations, particularly ship installations, were using spark coils mainly, although power transformers were beginning to be used at the leading shore stations. The coherer-decoherer had already given way to the carbon-granule coherer and earphones, as well as the Marconi

Worked with Hugo Gernsback



Years passed. 1910. My meagre spending money went into a 2-inch spark coil, purchased at the inside factory price because I happened to be working for dear old Mesco at the time. Meanwhile, I had been serving as assistant engineer of the Telefunken Wireless Telegraph Company of America, learning much about the more practical side of wireless. Also, I had worked with Hugo Gernsback in the pioneer days of the old E. I. Co. But, not getting enough wireless during working hours, I spent most of my evenings rigging up a lofty aerial on the apartment-house roof, and wiring and rewiring the spark coil, key, condensers made of ordinary window glass and tinfoil, changeover switch, two-slide tuning coil, silicon detector, and earphones.

The power problem was really the main hitch. The two-inch coil drew at least 6 amperes. My early efforts with dry battery proved very costly, for a set of cells wouldn't last more than a week. And so I turned to a storage battery, bought, painfully, cell by cell. Being blessed with D.C. supply, and having an old-fashioned link-fuse panel board available in the kitchen, I proceeded to connect my storage battery in series with our electric lights, so that the more lights used by the family the greater the charging rate. In this way I obtained a good source of power at no extra cost.

Later came a Wehnelt electrolytic interrupter, so that the two-inch coil could be operated directly off the 110 volts D.C. This interrupter consisted of a piece of heavy glass tubing with bottom end fused about a length of platinum wire. The inside of the tube was filled with mercury to make contact between the platinum wire and the lead wire. Rapid interruption of the current produced a steady spark or really an arc from the coil secondary, resulting in a great step-up in transmitting power. Also a higher pitched signal which was so much more "professional" than the ragged buzz I had been using.

But whom to talk to? That was the question. There were other amateurs on the air, some of the fellows whose names

(Continued on page 365)

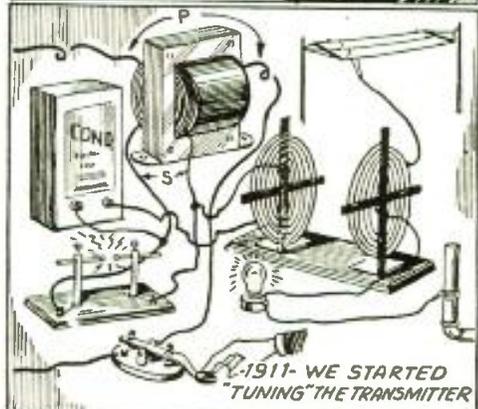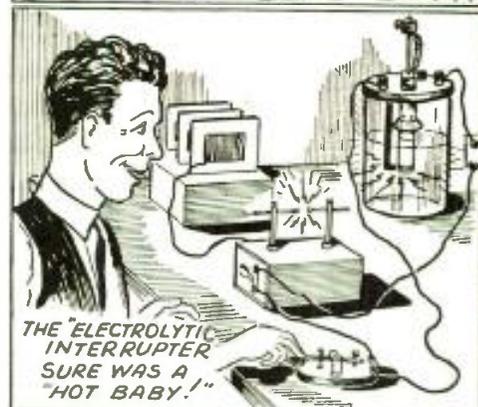

The November issue of RADIO & TELEVISION

will be an "Advanced Radio Amateur Number." It will contain valuable articles for the beginner as well as the advanced HAM.

magnetic detector, but the latter, with its elaborate spring motor, grooved wheels and moving belt of iron wire, was too ambitious for the amateur to tackle. So the choice was usually the carbon-granule auto-coherer, soon to be replaced by the electrolytic detector, the needle resting on knife-edge carbons, and the various forms of crystal detectors.

Late in 1907 I began receiving signals on a carbon-granule detector, connected with a couple of dry cells and an ordinary 75-ohm watch-case telephone receiver. For an aerial, I used the fire-escape of our apartment house. On several occasions I was rewarded by very weak dots and dashes. The whole family had to listen in on this wonder of the ages. My reputation was duly established as another Marconi in the making.

How HAM RADIO Saved Shawneetown!

Robert T. Anderson's
Own Story

Mr. Anderson was awarded the second Paley trophy for an outstanding radio amateur performance. The exciting events which led to this award are described in this exclusive article.



Many times Mr. Anderson and his short wave radio equipment were nearly thrown overboard by the rough water encountered during the flood period in Illinois.

● JANUARY 20, 1937, one of the early days of the flood, nearly caught me without a transmitter. I had just built a rack and panel job consisting of a L6 tritet, 10 buffer driving P P 10's operating on 3920

was still heavy, principally in the form of sleet, with some rain and snow.

An Urgent Message

When I arrived at the shop the next morning I found an urgent telephone call waiting for me from the authorities wanting to know how soon I could leave for Shawneetown, 23 miles away, with enough "gear" to establish and maintain communication. Since I had no emergency equipment ready, and had to obtain supplies, arrangements were made to leave at noon.

At 12:30 p. m. we loaded my equipment consisting of the exciter unit, a Crosley Model 636 allwave, 6V battery receiver; a set of spare tubes for transmitter and receiver; an adequate tool kit; a flashlight, 6 Eveready 486 B-batteries, a box of incidental parts and a tent.

By this time the road between Harrisburg and Shawneetown was flooded and impassable in four places. We were able to detour around the first flooded area, and crossed the second in a small boat over water so rough that the men had refused to take a reporter over an hour before at any price! Since I had a radio set they took me across for nothing.


A Hazardous Trip

A three mile ride in a farm wagon took me to the third gap at a coal mine within

nine miles of Shawneetown. I found the telephone at the mine still working to Shawneetown, contacted the authorities there and prepared to set up and handle messages. However, the authorities insisted that I continue across the next gap by boat and promised to meet me in a boat and take me across the last gap. They told me of their plight: that provisions of all kinds were low and they were entirely out of bread. At this time I joined forces with a bread salesman who was trying to deliver several hundred loaves of bread and some meat to Shawneetown. About dark we secured a small boat and pushed off.

We were so badly overloaded that we would have been swamped immediately if the man nearest the bank had not jumped overboard. The water was not deep but the temperature was about 20° Fahr. and the blizzard was at its height. We later found another boat, split our load and reached the railroad crossing and the last gap of water. Here we found ourselves unable to go farther or return. Our motorboat failed to arrive, the current in the last gap was terrific, and it would have been suicidal to have attempted crossing in our small boats without oars. Since we had no adequate oars it was impossible to return to the mine against the northwest gale. So we "set up" by light from the

(Continued on page 373)

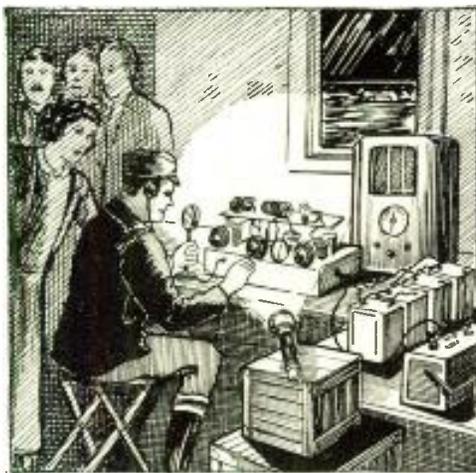

Finally arriving at the scene of operations, Mr. Anderson proceeded to "set up" his transmitting and receiving equipment, the only illumination being furnished by a flashlight.

kc., but the final had a bad case of parasitic oscillation, and I had never tried the outfit. However, I had remarked that it should be easy to use the exciter as a portable, and considered building up power supplies to enable me to do so, but put it off until the main rig was working satisfactorily.

My emergency work actually started at noon Thursday, Jan. 21, 1937, when K. E. Schonert, W9HQD, and I discussed the situation, decided it looked serious and placed our stations at the service of the Red Cross and other relief agencies.

At 3 p. m. when the heavy rain began changing to sleet and freezing on suspended wires, we realized that conditions were becoming very serious and that communications would be disrupted by morning, so I took the rest of the day off and went home to start work on the "rig." By midnight the rig was on the air. By this time there was considerable ice on the ground as well as suspended objects, and the precipitation

●
Exclusive photo showing Mr. Anderson and the emergency short wave transmitter and receiver which he used in calling help to rescue the inhabitants of Shawneetown.
●



The "YL" in Amateur Radio

Beatrice Holman
W1KTG



Photo by Boris

▲ Beatrice Holman, W1KTG, licensed radio amateur of Belmont, Mass. The number of young lady "Ham" operators is increasing each year.

◀ A dandy Ham station we'll say! It is operated by the author of the accompanying article. If you're a Ham, you've probably heard this station "on the air".



Photo by Chandler

● THE YL in amateur radio leads a charmed existence. She is a mystery to her other YL friends, a problem to her family and the delight (she hopes) of her brother amateurs. She would rather wear ear-phones than a Paris hat; she would rather stay up till three QSO-ing her boy friend in Sydney or Brisbane than dance at the Ritz; she subscribes to radio magazines and would rather read Terman on antennas than the latest novel about the younger set. She may live in a pent-house in a big city, with the latest type commercial equipment under her control, or she may have her shack in a lonely outpost with battery or windmill power and a make-shift rig; in any event, *the world is at her feet!* So is the postal service, for her daily mail in time is likely to become a major item in the carrier's routine.

Hams Are Gallant

She likes the friendly spirit of amateur radio, finding it one of the best influences in the world today. It breaks down borders and barriers; it spans the high seas and the long trek to make communication possible between people who would otherwise never know each other; it creates pleasant and lasting friendships; it knows no distinctions of nationality, politics or class.

Because women radio operators are still in the minority, the YL in amateur radio has an unusually interesting time. If she needs assistance in putting up masts or rhombics, she gets it promptly through the gallantry of her brother hams; in the same

way, any technical advice which she requests is promptly and freely offered. (In the case of my own station, I speak from experience, because one amateur has not only given his time, help and advice but actually built my transmitters as well.)

Sweet Voice—Quick Response

Probably there are more YL amateurs who operate phone than cw. transmitters. Their voices become as well known on the

larily of Eileen, the XYL at G6DH, whose cheery greeting on ten meter phone is *known to hams the world over!* Then in this country on ten and twenty meters there are many outstanding YL personalities, including *Eunice* at W5ZA and *Jean* at W4DGO.

Although I enjoy phone contacts very much indeed, I prefer to operate cw. In many countries today phone operation is forbidden; there amateurs are allowed to use only code transmitters. The YL who can handle a key or bug, then, has an almost unlimited possibility of contacts in every continent, all over the globe, from the Arctic circle through all the zones. In some cases, owing to atmospheric difficulties or interference, the QSO's may be short—a mere exchange of greetings and reports on signal strength; more often, however, they are an interesting exchange of facts and the beginning of many schedules.

Your Geography Begins to "Live"!

Places on the map that were just memories of school geography become very real when one establishes contact with them by air. And the wonder and speed of radio are all the more impressive when the resulting QSL or letter arrives with the foreign stamps after a long journey by boat or plane. I have learned interesting facts about people and places in my own country through radio contacts—about the oil industry in Oklahoma, farming in the South and West, the occupations and ideas of

(Continued on page 363)

The November issue of RADIO & TELEVISION

will be an
"Advanced Radio Amateur Number."
It will contain valuable articles, both
general and constructional, for the beginner as well as the advanced HAM.

air as the broadcasting stars. In fact, amateur radio activities are good preparation for broadcasting. For DX phone work, one must think quickly and speak clearly in order that the foreign contact may be complete. Familiarity with the operation of an amateur phone station helps develop confidence and poise; the operator knows that a pleasing voice brings a quick response, and that is where the YL has an advantage. In this respect, I think particu-

The WORLD COMES To My Room— *Via Amateur Radio*

John "Pop" Garvey, W8RID, tells
Michael Hrehocik all about it.



Amateur Radio brings the world to the bedside of "Pop" Garvey's room. The transmitter was built by "ham" friends.



"Pop" is in the coal business and he takes orders—via telephone. Note how the phone is "rigged" by a special bracket.

● ARE you looking for an inexpensive hobby that takes a comparatively short time to master? A hobby that will bring the outside world to your room—to your bedside. One that will create an outlet for your repressed feelings and one that will make it possible for you to make hundreds of friends. Smiling John "Pop" E. Garvey of Cleveland, Ohio, bed-ridden with arthritis for over ten years, was searching for one and found it—a short wave amateur station.

"CQ . . . CQ . . . CQ . . . W8RID, Cleveland, Ohio . . . calling CQ . . . CQ . . .," Pop sharply spoke into his "Mike" a second after I had entered his room. Pop, a jolly, round faced individual, with laughing blue eyes, pudgy nose and a big black cigar at a cocky angle, was lying in his bed—a portable bed equipped with balloon tire wheels. He had just snapped on a switch that is attached to his microphone line. This line leads to his transmitting cabinet that stands two or three feet to the side of the bed. Repeating the call CQ . . . —a general inquiry in the vernacular of the amateur operators indicating that he wished to contact someone—he got in touch with a chap in Michigan. After talking to him for a half hour, he signed off with a rousing 73—goodbye.

Not many of us relish the thought of not eating for a day. "But," comments Pop, "most amateurs will gladly pass up their victuals in order that they may put in a few more hours on the air. Why, the young fellow I just talked to is really a fanatic. He's up to three or four o'clock every morning chewing the rag. His wife doesn't permit him to stay up later than 11 or 12 o'clock. She believes that he abides by this ruling, for she can check up on him in his log book. Every amateur is required to keep a log book into which he records the station he contacts, the time he begins and signs off and various other details. But he fools her, for he keeps two log books—one for her to peer into and one for the government inspector. Yes sir, once you get this disease of being an amateur radio operator, it's less curable and more deadly than arthritis."

"I always thought that it took a radio engineer or someone in his category to run an amateur station. How did you ever get mixed up in this?" I questioned.


"Being a victim of arthritis, I was confined to my bed and had plenty of time on my hands. A larger portion of this time I devoted to listening to my short-wave set and this was the factor that led me into my thrilling hobby. I began corresponding with a few out of town amateurs and through them I became acquainted with a few hams in Cleveland. I was curious to get as much information about short wave as possible, and as these local amateurs would call on me I would pepper them with hundreds of questions. Seeing my interest develop rapidly, quite a number of the local hams formed a club at my home and decided to build me a set. When the boys had a few hours to spare they would work on it and in this way my transmitter was completed in six months.

Cost of Set Nominal

"While my set did cost more than the average, one can either buy or build a receiving set for about \$50 and a transmitter from \$75 to \$100. If one has the necessary background, he can build it
(Continued on page 378)



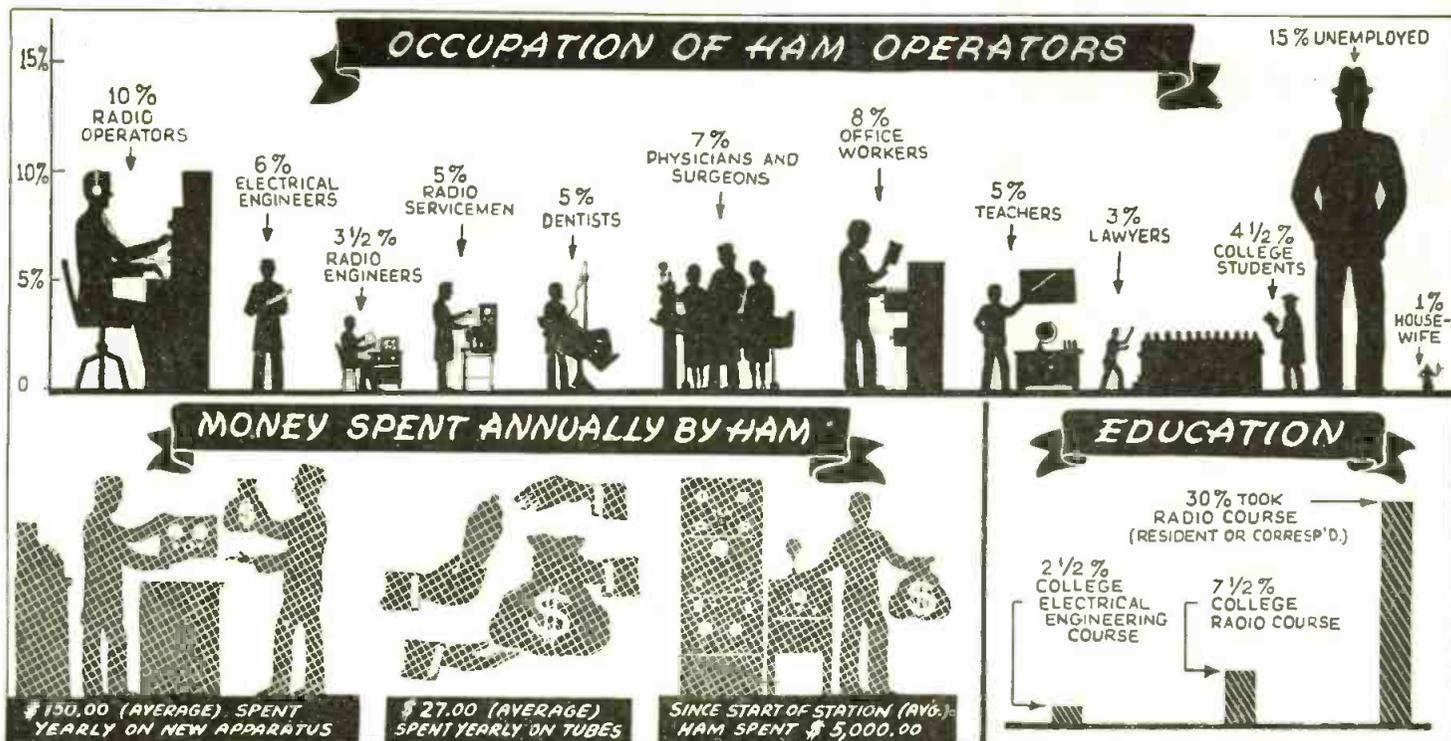Mr. and Mrs. John E. Garvey "at home." By means of a mirror, "Pop" can see what is going on all about him.



What Price HAM Radio?

How much money do American Hams spend annually for radio apparatus?
 Do they buy more ready-made receivers than they do transmitters?
 How many battery sets are used?
 How much do Hams spend for tube replacements?

● THE editors of this magazine were greatly interested in determining a number of interesting facts about the American Radio Amateur or "Ham," as he is more popularly called. There was only one way to find out and that was to mail questionnaires to a great number of leading Hams all over the United States—and this was done.

What Hams Do for a Living

Probably the most interesting fact about the average Ham station owner and operator concerns his occupation. The answers to the questionnaires disclosed that 10% of the amateurs are licensed radio operators, occupied either in the commercial field or as police and marine operators. Six per cent of the amateurs are graduate electrical engineers, while 3 1/2% are radio engineers. Radio service-men figured in the answers to the questionnaires to the extent of 5%. radio technicians 2 1/2%, telegraphers 3%, radio broadcast engineers 2%. Among the professional men who are licensed, according to the questionnaires, 2% are ministers, 3% writers, 5% dentists, 7% physicians and surgeons, 3% lawyers, and 1% musicians. Other interesting figures show 5% teachers, 5% business executives, 8% office workers, officers and salesmen, 5% merchants, 4 1/2% college students, 15% unemployed, and even the housewife showed up as 1%.

A further analysis of the occupations of radio amateurs indicates that quite a num-

H. W. Secor

ber occupy Government positions, either with the Army, Navy, Marines or in the Government service. Quite a few Hams are airplane pilots, 2% farmers, 1% newspaper reporters, while others are sprinkled through the various professions of optometrist, librarian, the advertising profession, statisticians, printers, bank tellers, restaurant workers, express messengers, time-keepers, telephone engineers, signal engineers, radio editors, radio communications experts, movie sound engineers, motion picture projection operators.

Education

A highly important factor in any profession, including data on the radio amateur, is education. The answers to the questionnaires disclosed that 2 1/2% of the Hams have taken a college *electrical engineering* course and 7 1/2% have pursued technical radio courses at some one of America's well-known colleges or universities. About 30% had taken, either resident or correspondent, courses in some one of the numerous radio schools that are scattered across the country. 51% had no formal radio training or background, but simply educated themselves by reading books and technical magazines such as RADIO & TELEVISION.

Money Spent Annually on Ham Stations

When it comes to the amount of money spent by the individual Ham annually on his station, either for new apparatus or for tube replacements, this, of course, varies a great deal and the figure obtained by checking an average of the amounts mentioned in the answers given to the questionnaires does not show what the amateur with the small station spent. Naturally, if he only has a small station and has been in the Ham game for only a short time, he will probably not spend as much annually for apparatus or tubes as would those who have been in the game for 5 or 10 years and who have built up elaborate stations.

The questionnaires were sent to representative amateur operators, as nearly as could be judged, and the average amount spent by this representative class of amateur operators on new equipment each year is \$150.00; for tube replacements, the average is \$27.00 per year.

The radio dealer or manufacturer should not take this as a representative figure for all operators, as the only way to reach such a figure bearing on the whole membership of 46,000 licensed Hams would be to send a questionnaire to every one of them. This must be understood for the very good reason that among some of the reports handed in by the radio amateurs, we find those who spent as much as \$3,000 during the past year on new equipment,

(Continued on page 374)



Here's the smiling face of VE3QL—E. E. C. England of Walkerville, Ont., Can., a real live "ham".

● THE following episode is taken from a day during the last amateur phone contest. The time, 7:00 P.M., E.S.T., Friday evening, March 18th. Everything was in readiness waiting for the one minute to roll around. Everything had been checked over and over to avoid disappointments. The beam antenna had been oiled, greased, and calibrated to make it twirl around at the touch of the wheel. The receiver was all tuned, waiting for the DX to roll in—one minute more—just sixty seconds—there—7:01 and just listen to the DX rolling in. A pair of earphones bought specially for the occasion were installed in case of too much QRM. At last through the jumble of voices came a CQ, fading a little, but at least readable; would he never sign his call, here it is—GM6WD—and on the other end of the band. Up from the chair and around the back of the transmitter to change crystals, just hoping he wouldn't "sign his call" and look over the band before I changed frequency.

Three Visitors—and What a Time!

My hope was granted and he later signed, listening for W stations. Well, I took the chance, and lo and behold, he came back to VE3QL the first GM station (Scotland) I had ever contacted. We exchanged our serial numbers and signed. I was off to a good start at least. Then came disaster. a knock at the door and in walked three short wave listeners (SWL's). Of all the times to pick, when DX was just pounding in, and me trying to listen to DX stations and answer their questions at the same time. It proved to be a bigger job than I had anticipated.

Silence once again and eight o'clock striking, one hour of good DX gone, and also a slight increase of QRM (interference). Another CQ—very faint—but the signal slowly climbing up. PAOFB—was I hearing right—the Netherlands calling CQ; so back I went to the old frequency. I gave him a long and bellowing call and back he came to VE3QL, with a 4R7 signal fairly good. I had just signed off

A Day in the of a

E. E. C. England, VE3QL

The accompanying article gives a new slant for the layman on what a busy "ham" can do with 24 hours. How does he eat, sleep and carry on "day" and "night" schedules?

Read on . . .

with him when QRM from one end of the band to the other just smothered the DX out of the picture. Somebody *would* put an electric razor on, as if he couldn't pick

flew by and no real difficulties had transpired, which was something to be thankful for. A few G (English) stations were worked and then time was called. Even hams have to eat, and with a big night ahead of me, I felt the need of something energizing.

Ten after ten, and back I went to the receiver, ready to call them when they called CQ. My DX included, up to this time, the West Indies, Netherlands, England, France and Scotland—not too bad. I only needed an Asiatic contact for my WAC (worked all continents), but so far I had heard nothing from that part of the world. Of course there was a whole week ahead of me, and a lot could happen before then. During the hour I got my French stations, five in all, plus a Belgian station.

The Family Retire

Ten forty-five, and the family having been in and out of the room since the contest started, they finally went to bed, leaving the house in silence and the cat and me to keep each other company. The CW (code) was starting to come through heavy

Another view of the rotary beam antenna tower; the operator is repairing one of the wires.




Mr. England is seen standing on the tower supporting his beam antenna. More than once he had to crawl up that ladder and see what was wrong with the antenna on a "dark and stormy night."

some other time to shave! It was only on about five minutes and I made up for lost time by working six G's and another GM which was the last up to nine o'clock. Not too bad, considering the delays.

French Contact

Another hour on its way and no idea of what it held. The French stations were beginning to come through—maybe I could work a couple to boost my score. I slowly tuned down the band and VP6MR calling CQ Canada, that sounded easy, and after a short call I finally *contacted* him. I got my number from him, but we still continued the QSO (contact). After a description of his "rig," he continued on the location of Barbados and a rough description of the West Indies—from the type of weather to his own kind of work. We had quite a QSO with no QRM for either of us. Time

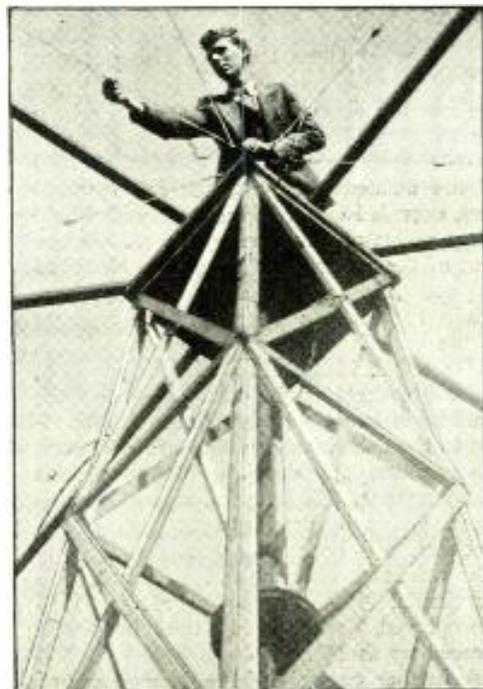

Life Busy HAM

but the earphones helped a little. The wind was coming up and the wheel of the beam antenna was beginning to turn back and forth slowly. A lot of local stations which were not in the contest signed off, sleep being the better proposition, and this also improved the listening part of my problem. I had the usual run of luck in contacting stations, but had heard nothing in the line of DX for ten minutes. The favorite pastime seemed to be tuning from one end of the band to the other, over and over. A path was worn from the chair to the back of the transmitter, from changing frequencies so often.

Down over the band again and T12AV was calling CQ with an R8 signal; success at last, if I could hook him.

Beam Antenna Out of Control!

A short call and back he came, but not receiving me so well, so I got up to turn the antenna and snap, *off came the chain*—a very unpleasant situation. The QSO was completed, with lots of tough listening at the other station. Then came the problem of climbing up on the roof and repairing the damage at eleven-thirty at night, a slight wind, and nobody to hold the light for me! Out came the ladder and up I went, fixing pulleys, straightening wires. Back to the room and exactly twelve o'clock, *Everything and everybody was on the air!* So far I hadn't heard an Asiatic—if it were only my luck to contact one.

I started off the hour with an HK (Colombia, S.A.) and an ON in Belgium. From twelve o'clock on to five o'clock in the morning I just sat in my chair and worked the stations on the average of four or five an hour.

A Fine "Log"



Five o'clock and quite a nice report "log" to show for my hours of patient listening and talking on the air. It became impossible to keep my eyes open, and the stations seemed to fade away as I slowly began to get drowsy. I shut off the transmitter and receiver, wound up the clock, set the alarm for eleven that morning, and dropped down on the couch, falling asleep immediately.

Eleven o'clock and the sun brightly shining, the sky was as clear as could be with no signs of rain for the present. I turned on the receiver and listened across the band, but there wasn't much on. Ten meters seemed to be quite alive, if only the antenna would work down there. It was worth a try at least. I got the rig all in working order after a few delays and tried to work somebody. I called CQ until I was hoarse and then tried calling other stations; but it just wouldn't work. I finally decided it was the antenna, and went outside to look over the problem. It wouldn't work no matter how hard I tried to fix it, so that meant keeping on twenty meters. By this time lunch was ready and I was summoned for it.

Foreign Contacts Galore!


Ten after one and I again went downstairs. The desk had to be cleaned up a little bit after the night before. Papers and books, pencils and pens, paper that had been torn into small pieces while trying to get a call letter through. Clear at last; now to try and work somebody. I began by working England, four in succession, followed by an HK, and then France. A couple of
(Continued on page 377)

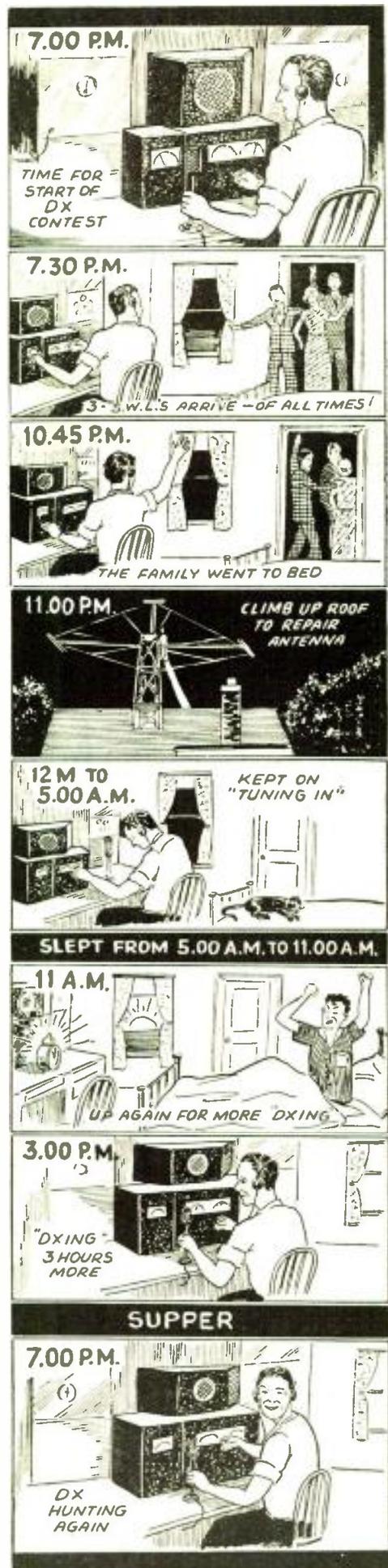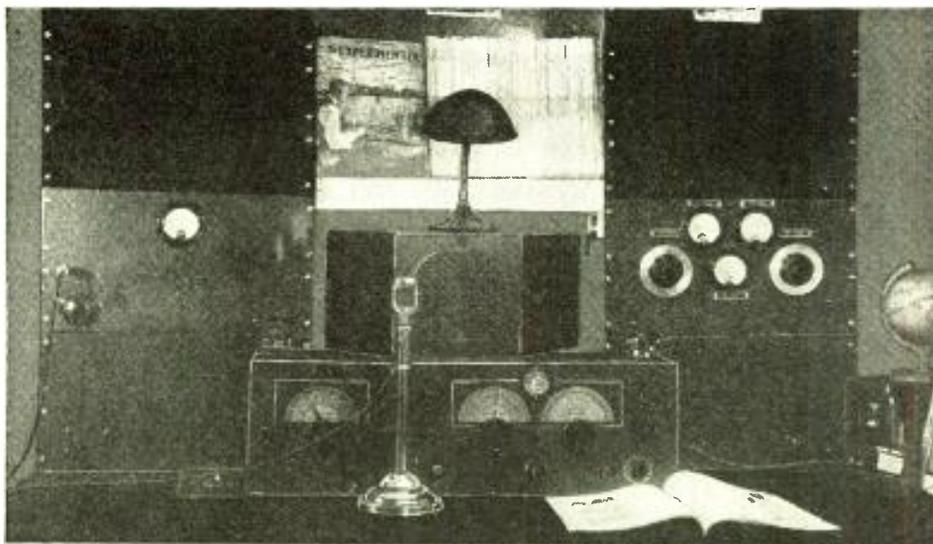The elaborate receiving equipment at station VE3QL, where stations roll in from all over the world.



Drawings above show some of the incidents in the daily life of a busy "ham".

Rapid Growth of Radio Amateurs

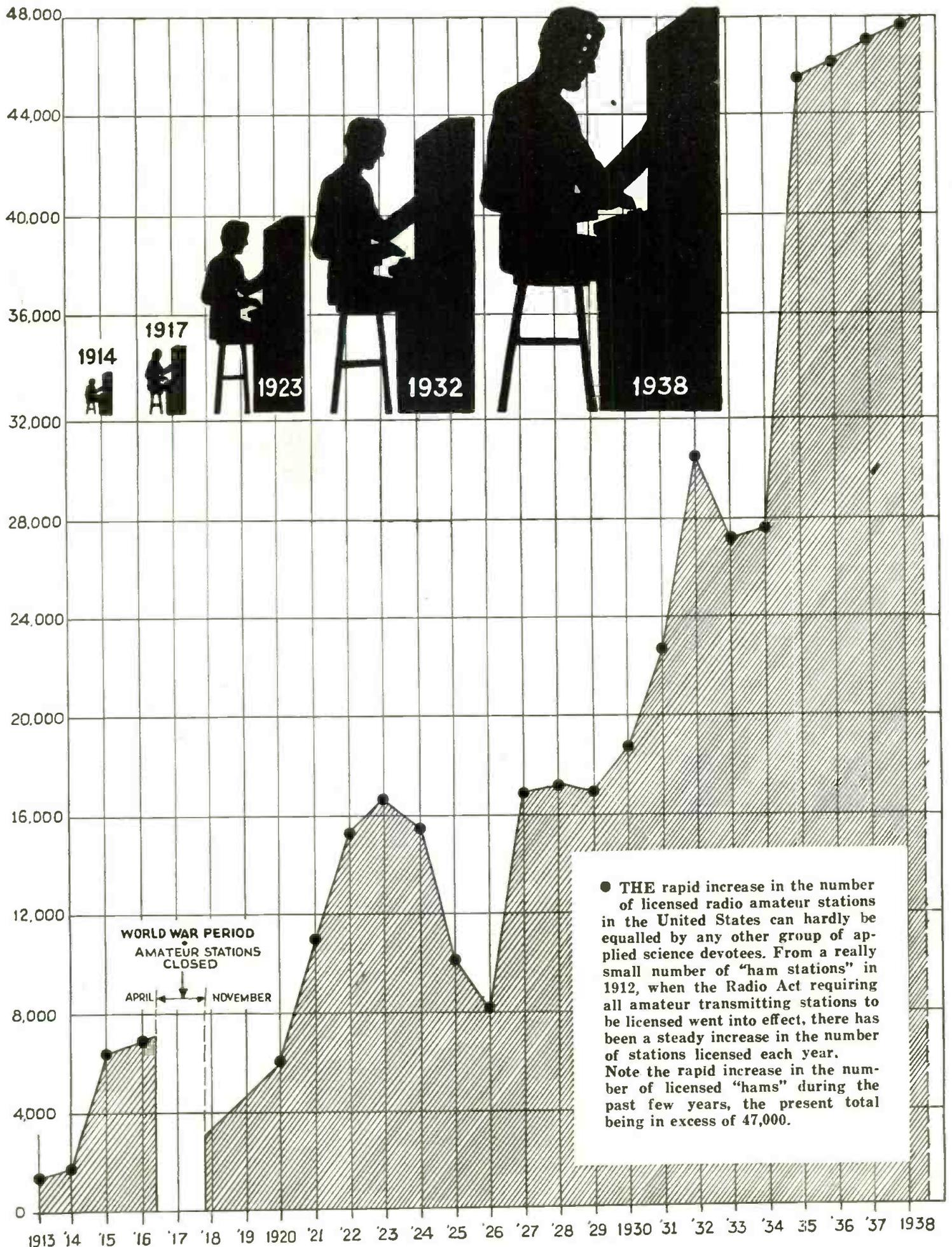

Want to Learn Foreign Languages?

Hon. Michael Norton, B. A.
(England)

Mr. Norton has worked out a system, which—when used in conjunction with a short-wave receiver—enables you to learn a foreign language easily.




● THE short waves are bringing many foreign language programs to the United States. The American citizen seems to be more enterprising than the European. He wants to learn *foreign* languages so that he will miss nothing.

Over here in Europe, we miss about 60 per cent of what is on the air, some of us even more. I have learned four *foreign* languages and have used various methods. The fourth language I learned was Italian, and I did this mostly by listening to radio programs from Italy. I feel sure that if you want to learn to speak a language and to understand it when spoken, then learn by radio. But learn by a system! In teaching myself, I have found the following method the soundest.

Spend the first week in just getting to know the *sound* of the language. Just listen to the language over the radio for as long a time as possible every day! Don't try and understand it at first, but try and imitate it as if you were a child mimicking a grown-up person. You will soon be able to repeat little words to yourself. You may not know what you are saying, but you will be saying it correctly, more correctly than others who have been learning much longer by other methods.

At this stage, you can begin to learn just the elementary rules of the language from a *self-tuition* book giving the imitated pronunciation. The grammar need not be closely studied, but a knowledge of the construction of the language will be a great help in guessing it from the radio. The first step in disentangling a language is to be able to identify the parts of speech. When you can do this, you will be able to use a dictionary. During the first week of listening, there will have been some words which you have heard several times. Those that you remember, you can look up in a dictionary. You can guess some of them. When you know a few words, you can guess a lot more.

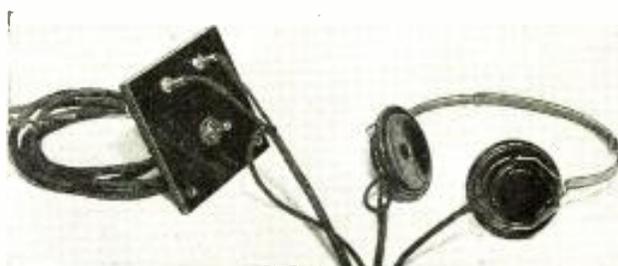The subject matter that you will have to deal with will be the weather forecast, the news and possibly advertisements. When you can understand a sentence here and there, try and get an idea of the subject matter, and don't bother about details. If you concentrate on any detail, you lose



By fitting a simple switch attachment to your receiver, headphone reception may be enjoyed and is a great aid in studying "foreign" languages.

Left—A pair of good headphones and a switch and cable like that shown provide "private" reception.

about three sentences that come after.

From the beginning practice repeating to yourself any sentences that you have remembered. You will soon be able to anticipate call signs, advertisements, and parts of the weather forecast. Now you should practice saying them over in unison with the announcer. When you can understand most of the news, you will be able to understand only some of the talks. Broadcast talks may be divided into two classes: elementary and advanced. When you have mastered all the news, you will be able to understand all the elementary talks, for they will be delivered slowly and with a good deal of explanation.

The talks which are not elementary are usually technical; though not so technical that you, as a student of the language, should ignore them. They deal with the topics most discussed in the country from

which they come. To understand these talks, you must read the language, but it is best if you read what is of current interest. After reading newspapers and then periodicals, a light novel need not prove too difficult, provided that you keep your mind on the plot and do not bother too much about details—just as you have been doing in your listening.


The reading of stories and novels will help you to master the abstract words that you will not have met much in the news. You should therefore pay special attention to these. Having learned to understand the different styles of different writers on various subjects, you will find that you can now follow the most difficult talks. When you can easily understand all the talks given by all the varying types of people, you can claim a very good knowledge of the language.

Some people might think that you could gain only a limited knowledge of a language from listening in. On the contrary, an extensive knowledge will be yours. Starting with the most simple and ordinary topics of the time and the weather, you progress step by step to the arts and to all sorts of branches of modern technical development. You will hear many different voices and accents. But remember that anyone speaking with the accent of an announcer is most likely to be understood by the largest number of people in the country to which the announcer belongs. You will have copied the *right* man.

Now you want to begin *listening*. Remember to turn up the volume control of your radio for foreign languages. You must do this because you want to copy what you hear. When an artist copies a picture, he

(Continued on page 372)

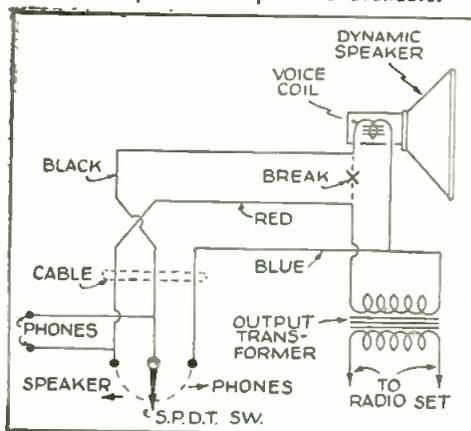The diagram below shows how to connect the simple switching system, whereby headphone or loudspeaker reception is available.



The Short Wave League



Hugo Gernsback, Executive Secretary

HONORARY MEMBERS

Dr. Lee de Forest
 D. E. Replogle
 John L. Reinartz
 Manfred von Ardenne
 E. T. Somerset
 Hollis Baird

On the Ham Bands (with the Listening Post Observers)

Edited by
Elmer R. Fuller

● WELL, another month has rolled by and here we are again with the second edition of this department. "Yours truly" is wondering just how this column is being received by the radio *hams* and *fans*; but I'll probably hear about it soon enough if it isn't what we intended it to be. About twenty-three reports on reception during

the past month (July) have been received. All of these, I regret to say, are not usable. On every report it is necessary to include certain things and many of you have not done this.

In every report include the station call, approximate frequency, readability, and signal strength. This is not hard to follow, but it is very important. I know that many have home-built and other types of receivers which are not calibrated as accurately as they might be. This need not stop you from giving the approximate frequency. You can certainly make a frequency graph to cover the ten and twenty meter amateur bands, and these are the ones most frequently used for getting real, good dx. LIST ONLY AMATEURS! This department does not care a thing about the commercial phones nor the short wave broadcast stations. We are interested only in the *amateurs* and matters concerning them and their stations.

Each month pictures of *Listening Post Observers* and their equipment will be published in these pages. Why not send in yours now? This month, because this is a new feature, we had to skip this procedure, but we do not wish to do it again. So, dig out the camera, get into the picture yourself, and then have someone else snap it for you. (Or trip the shutter with a string.—*Editor*) Let's see who will be the first to get his picture into print. First here, first served.

Now let's get down to the reports of the month. From them I find that conditions were about the same all over the country. During July it was very rare that any real good dx came

through. But from the reports, I find that there were some, and some that were rather good.

Harry Honda, out there on the Pacific coast, reports the following on twenty meter phone:—

Call	Freq.	R	S
VR6AY	14.35	—	—
VK2NS	14.02	—	—
AC4AN	14.20	5	5
TI1AF	14.09	5	7
HH5PA	14.05	5	8
ZS1AX	14.04	5	9
ZS5AW	14.08	5	5
ZS6AD	14.01	—	5
ZS2AZ	14.11	—	6
ZS6ED	14.005	—	6

E. H. Walker—Observer for England
 (All on 20 meter phone)

LU1Q1	5	7
LU8AB	5	7
VE5ACN	5	4
HK3LC	5	5
TI1AF	5	6
CO2RQ	5	5
CO2SV	5	5
PY1FR	5	7
PY2CK	5	7
PY2LM	5	6
PY4CT	5	5
SU1JM	5	6
SU1KG	5	9
W5BYS	5	4
W6AM	5	5
W6GRL	5	4
W6GVM	5	7
W6NTX	5	5
W7BVO	5	4

Roger Legge, Jr.—Observer for New York

LX1AI	14.03	5	6
HA4A	14.13	—	6
ZS1AX	14.03	—	7
TG9AA	14.06	—	7
GW2IP	14.03	—	7
GM6SR	14.02	—	8
G18UR	14.08	—	7
PK6XX	14.01	—	6
HA8Q	14.06	—	7
CN8AR	14.28	—	7
CN8AM	14.08	—	7
CN8MA	14.08	—	7
FA3QV	14.32	—	7
FA3HC	14.09	—	6
VP7NR	14.14	—	6
SM7UC	14.05	—	7
EA8AE	7.16	—	6
EA8AK	7.12	—	5
EA8AS	7.27	—	7
I1MY	14.32	—	6
VS2AE	14.37	—	5

Wally Hallgren—Observer for California

K6OQE	5	7
K6CMC	5	7
G61D	4	5

Stanley Clarke—Observer for Canada

U1FC	14.400	3	4
PY2CK	14.090	5	7
PY2GC	14.105	5	6
OK1PZ	14.405	5	6
PJ3CO	14.400	5	8
YR5CF	14.390	5	7
FM8AD	14.270	5	8
U1AD	14.420	5	5
SP1RG	14.400	3	5

Richard A. Rush—Observer for California

PY2AK	28.200	—	—
-------	--------	---	---

(Continued on page 377)

Three good examples of short wave listener cards; some are printed in colors.

Local HAM Gossip

A new Department—you can help make this a valuable and entertaining feature. Rush news of Ham club activities to "Local Ham Gossip" Editor, c/o this magazine.



Lee R. Kemberling, W8ESN, who tells the interesting story of the great 5-meter "Field Meet" held in Toledo, Ohio.

● THE Toledo Ultra High Frequency Ass'n is made up of a group of hams and DXers interested in ultra-high frequency work. This group held meetings at the homes of members until the membership passed 15. All this time, Lee R. Kemberling, W8ESN, was watching their progress and was building his new radio shack in the rear of his home. The size of this building is 22 x 27 ft. When the shack was about completed, he went to one of the meetings of the Association, and gave a long talk on getting one's license and just what had been done in the past on Ultra Hi Freq. He added that if the "gang" wanted to grow right and get some place, they should have a room in which to meet besides the homes of the members, as many fellows would come to a public meeting place, although they would not go to private homes. He offered the TUHFA his shack, as a meeting place; it will hold about 50 to 75 in the large room 18' x 22'.

The TUHFA held the first meeting there in October, with a membership of 12. In the first 2 months the membership went to 25, meeting every Tuesday night at 7 p.m. W8ESN talks on the F.C.C. laws and gives code lessons for one hour. This group grew until they had to put a limit on it! Now over half the members have licenses and more will be going up later this year. This is largely attributed to W8ESN's talks and code lessons. At W8ESN he has put 250 watts on 5 meters and, beginning the first of September, will be on the air every third night with code and talks on amateur radio for one hour at 7 p.m. Lee Kemberling is now an Honorary Member of the Association and Activity Manager of programs. At the close of the summer activities on July 12, the membership was 25, with 20 more

5-METER-5 FIELD MEET JULY, 10

OTTAWA PARK, 10A.M.

PRIZES HIDDEN 5 METER XMTR HUNT. PRIZES
FOR BEST HOME BUILT ULTRA HI FREQ RECEIVER, TRANS-RECEIVER
BRING YOUR LUNCH. LEMONADE FREE
SPONSORED BY TOLEDO ULTRA HI-FREQ. ASS'N. & TOLEDO RADIO CLUB
CALL CHAIRMAN W8ESN LEE R. KEMBERLING, FOREST 3695-J

Card announcing 5-meter "Field Meet" of the Toledo Hams. Live Stuff!

waiting on the list. The 5-Meter Field Meet closed the summer. The officials of the TUHFA are: Bernard Shonebarger, Pres.; Lawrence Gilsdorf, Vice-Pres.; Dean Seaman, Recording Sec'y; Stephen Petroll, Treas., and Lee R. Kemberling, Activities Manager. All mail is sent to the Radio Shack W-8-E-S-N, Box No. 3, Toledo, Ohio.

TUHFA & TRC Field Meet

Starting on Sunday July 10, the gang had a good start before 10 a.m. First the Receiver prizes were given for the best Ultra Hi home-made receiver, rated both for looks and operation. We had 18 receivers set up, and as we could not get a.c. at the park where we were going to hold the meet, the gang went over to W8ESN's Radio Shack and cleaned out the side yard and in the rear of the shack, this giving us room for over 100 cars to park and a place to hold the meeting. The Receiver prize was won by a Mr. C. H. Peters, with a set which would operate on a.c. or 6 volts d.c. Second prize, Ralph Kachenmeister, receiver both a.c.—6 volt d.c. portable. This took until noon—time out for lunch. We had 65 gallons of lemonade made up and kept a 10 gallon jug going all the time. By noon there were over 90 hungry guests. A half-hour talk on "Benefit of Ultra Hi Frequency to Mankind" was given by Lee R. Kemberling (W8ESN). This lasted over 1½ hours, as there were many questions asked. After this a talk on Ultra Hi Frequency Antennas was given by Dean Seaman and Stephen Petroff. They did a lot of drawing on the blackboard to show the

various types of "ultra high" antennas.

At 3 p.m., the 5-meter "Xmtr hunt" started. This Xmtr was hidden the day before by Burt Holmes, Ed Martin and yours truly, and was tested after midnight to make sure it would cover the city, which it did. This Xmtr is W8ESN's portable, and has an output of 10 watts crystal controlled on 5. There were 56 cars in this hunt and over 150 were at the meet. About 70 were from out of town, some coming over 200 miles. W8ESN put on the big 5-meter rig which has 250 watts and all the cars left the radio shack and started out to look for the hidden Xmtr. After 5 minutes on the air with the large rig, the gang got word to start to look for the small rig. B. Holmes and E. Martin heard the large rig sign off and at once put the hidden Xmtr on the air and placed a tone on the sig. Every 15 minutes they stopped and gave the call. At 3:35 p.m., C. H. Peters found the Xmtr, got his slip and reported back to the radio shack. At 4:10 p.m., A. M. Cooper (W8BHL) with Gail Griner (W8DPN) found the Xmtr and at 4:25 p.m. Hal Shafer was third. This ended the hunt and W8ESN went on the air with the large rig and called all the other cars into the shack. This hunt was one of the best that has been put on around this part of the country and the boys from out of town would like to have one later on. A hunt like this makes the gang get up on their toes and keeps them working on new rigs all the time.

At 5 p.m., the transceiver prize was called. Receivers were set up at the shack. We had three: Super-Skyrider, HRO and a Hammarlund Pro., all working on 5 meters. We would start the three cars out that had transceivers in them and would work them at given spots in and out of the city, a distance of over 5 miles, checking each car off in ¼; sixteen were in this. First prize went to Ray Lewis, Pres. Toledo Radio Club with L. Gilsdorf (W8RQ1) at the mike. Third prize to Dean and Richard Seaman with Ray Zeh (W8RQ1) at the mike. Third prize to C. H. Peters, with Paul Luckman (W8KPII) at the mike.

This took 2 hours and it was now 7 p.m.—time to sign off after a very interesting
(Continued on page 368)

WANTED

● Local correspondents, who are able to send us from time to time news items (with photographs, when possible) of the activities among Hams, DXers and amateur radio personalities.



Regular space rates will be paid for the most interesting items submitted by anyone, each month.

To avoid errors, please typewrite your copy.

The name of each correspondent will be printed at the bottom of the items sent in.

Address—"Local Ham Gossip" Editor,
RADIO & TELEVISION,
99 Hudson Street,
New York, N. Y.

What Do You Think?

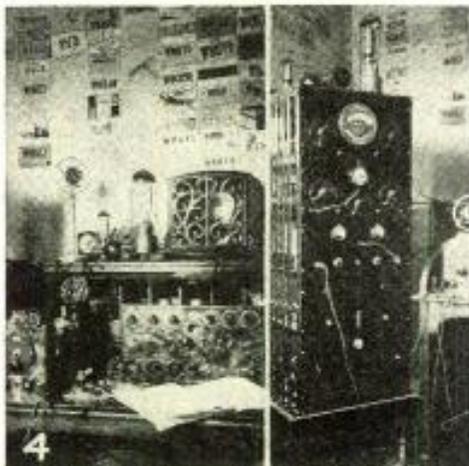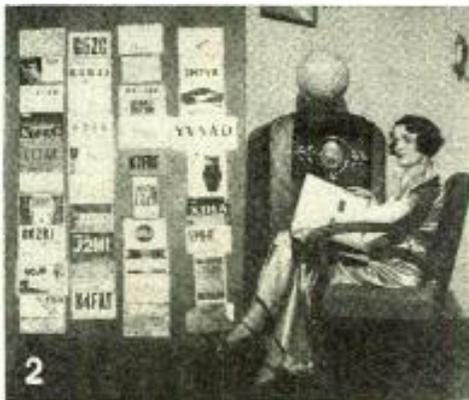

Hi! Fellers! Did You Send That QSL Card?

Editor,

There has been a lot of "pro and con" talk about this SWL-QSL business.

It seems like the hams, and I mean HAMS who are always belching about SWL's sending cards to them requesting a QSL, are about at the end of their rope; I believe that it would be a good idea for them to give up ham radio, before they find themselves in a state of nervous prostration.

I have been in the amateur game only 18 years now and feel that I still have enough reciprocity left to send a card to a SWL who requests one.

I also have a better feeling towards the SWL than I do a lot of hams. I have been trying here to make WAS on 20 meters and have asked the fellows (some are skunks) to pse QLS as I needed their state for WAS (worked all states) and believe it or not, I have gone to the trouble to write them a letter three times already, and do you think they QSL'd? Well, the truth is, they did *not!* Would you call this ham radio? If so, then the game is going to the dogs. The stations I refer to are—W9 in Willmar, Minn., a W9 in Emporia, Kans., a W5 in Kerrville, Tex., a W4 in Atlanta, Ga., a W9 in Louisville, Ky., a boy, oh boy, a hundred others. If you would like to publish their full call letters, I would be more than pleased to furnish them.

I know a W4 who receives an average of 200 SWL cards a month, *and he answers all of them;* I don't receive that amount but what I do receive. *I acknowledge.*

But these mugs, lugs or bugs, whatever they are, who do not QSL the stations they work when asked to, are not fit to be called *amateurs.*

I have had punks tell me over the air that I had better send my card first, if I wanted one of theirs. Suppose we all felt this way? Phew, the whole business is getting rotten, or is it the smell of these certain SKUNKS?

Then there are the hams and I mean *real ones* whom I have QSL'd, who make the other no-good punks look like the rankest of beginners. These fellows are worth their weight in gold, just to have their friendship.

These squawkers who complain about the SWL who puts R9 reports on their cards must be crazy. If they do not believe their signals to be that loud, they should do something about improving their efficiency or their antenna, so it would be that loud.

I am open for any comments or debate—come one, come all.

If I have stirred the gander in you punks out there, then this article has served its purpose. And do you want to hear more from me? If so, I will spill plenty.

But I believe a word to the wise (?) is sufficient. *An eye for an eye and a tooth for a tooth* is my motto. What? 73 es CUL.

LOUIS C. BREMER, W3LE,
130 S. Broadway,
Baltimore, Md.

Constructive Criticism

Editor,

I am about the very last person to throw brickbats but I just can't help throwing a few. I feel this way since the day I read the April 1938 issue.

What is the matter with 160 meter transmitters? Seems that the fellow with the class A ticket should get all of the gravy for 20 and 80 meter rigs.

In the receiver diagrams why not let the readers wind their own coils instead of buying them ready made and then tearing them apart later and removing turns of wire, etc.?

Your radio log is the most perfect I have ever seen. I have been trying to log one foreign station for 5 years and only succeeded after locking up the schedule and frequency in SHORT WAVE & TELEVISION.

The November issue of RADIO & TELEVISION

will be an

"Advanced Radio Amateur Number"

It will contain valuable articles for the beginner, as well as the advanced HAM. Transmitter and Receiver construction and other valuable information which you can't afford to miss.

I can't see why you are against S-W Adaptors. I have been using a five-tube superheterodyne converter with a very sensitive 9-tube broadcast receiver for 5 years; I really started logging stations a month ago when I started using an adaptor, plugged into a midget receiver which is home-made (the audio section consists of a single 27 and a single 47 and a 24 detector). When I use a 24 tube in the adaptor I get good results down to 19 meters; when I use a 27 tube I get down below 10 meters.

FRANK SAJ,
818 Carrol,
Buffalo, N. Y.

A Real S-W Fan

Editor,

Here's from a reader since 1932 April issue, and I still have the copy. I've missed some of course since then and having very limited means, financially, I expect to miss some copies in the future. But thanks to friendly hams, I've come smilin' through thus far. I've thought many times of writing to ye old "ed," but know you're busy as heck, so procrastination is the thief of time, etc. Say, the ex-YL says all radio men are nuts; how about it?

Oh yeah! Well she listened to S. & L. "ringside" via short wave. My hookup is from S. W. C. mag., how's that; we have three B.C. receivers, but SW phone and CW for me. I get the drowsy cheer from the ex-YL about three a.m., but what care I after 10 years "on the air." Now pardon a long note, but the air is quite rite now, so I'm scratching the Parker.

Glancing up at the chronometer, I see it's
(Continued on page 376)

(1) Listening post of Nicola Cannata, 1003 So. Halsted St., Chicago, Ill. (2) Prize Winner Zana Kandle, also from Chicago, 7953 Dobson Ave.; she uses a Midwest receiver. (3) Jim Groll, North Chicago St., Dwight, Ill. (4) Station VE4ACP, R. Peters, Jr., 356 Aikins St., Winnipeg, Man., Can.

Fourth Silver Trophy Awarded to

William Orr, W2HCE

Bronxville, N. Y.


For Best HAM STATION Photo of the Month

● THE transmitter rig is to the left and is working on 20 meter phone. The rig uses a 41 xtal oscillator on 7.088 kc., a RK39 doubler to 14.176 kc., link coupled to a 805 in the class "C" amplifier, running at 200 watts input. This R.F. equipment is contained in the two top panels. In the next panel, the third from the top, is the speech amp. This uses a 57 pentode, 57 triode, push-pull 56's, and push-pull 45's as drivers. The modulators, which consist of 4-46's in push-pull parallel are in the next panel, with the square meter. The bottom panel contains the 500 v. 0.5 amp. power-supply for the modulators, and the 1250 volt 0.3 amp. supply which supplies juice to the 805. The four 866's can be seen in the cut out. On the table to the right is the D-104 crystal microphone, electric clock, and the receiver.

The receiver is a home-built job. The line-up is 6K7 R.F. amp., 6A8, 1st det., 6C5 H.F. osc., 2 6K7's I.F. with three iron core 465 kc. I.F. transformers. A "R" meter is incorporated in the I.F. amp. in a Wheatstone bridge circuit. 6H6 2d det. and noise-silencer, 6C5 and 6F6 audios. The receiver uses a Tobe tuning unit which covers 20, 40, 80 and 160 vy fb. In front of the receiver are a pair of Brush xtal phones. To the right of the receiver is a small B.C.L. midget for use when 20 m. is flat. On the wall are the Phone "WAC" ticket and the six QSL's that brought it.

I have one of your "globe" lamps on the receiver. The doohickey to the right of the lamp is a tricky match stand. The whole station, from the antenna to the receiver, is home-made.

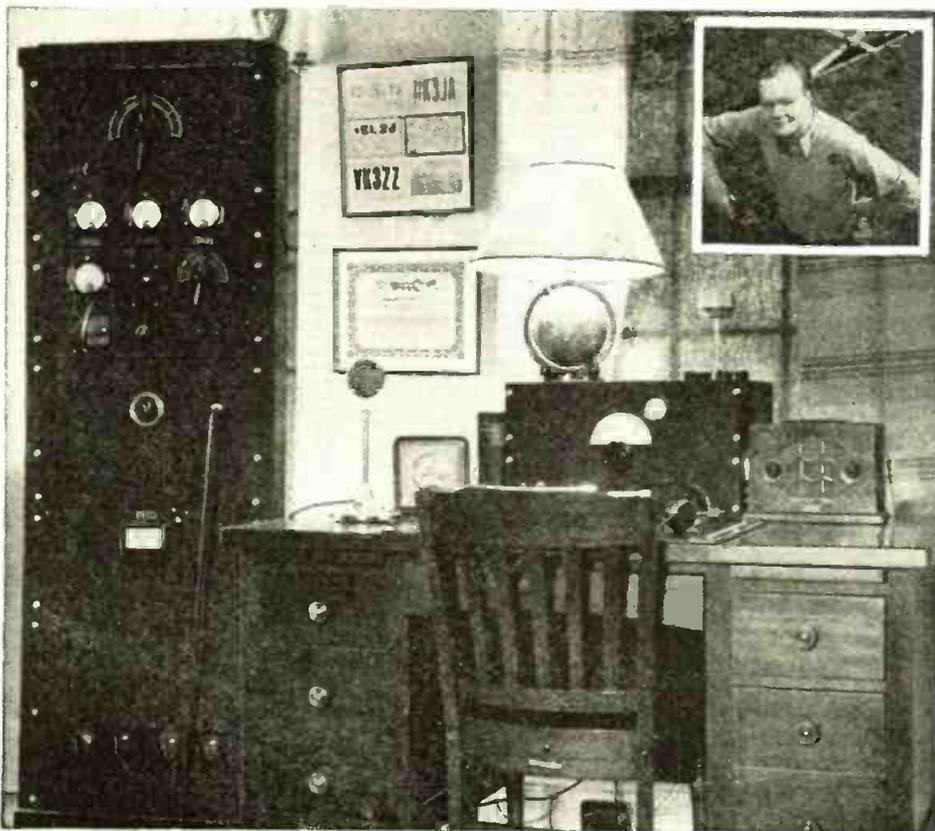Mr. Orr's first-rate Ham shack, located at 11 Sunny Brae Place, Bronxville, N. Y., has been the scene of much experimenting. Antennas and transmitters of every kind imaginable have been "given the works" at this station. He tells you about some of them in his very interesting description of the station.



This beautiful silver trophy stands 11 $\frac{3}{4}$ " high and is to be awarded monthly by RADIO & TELEVISION magazine for the best photo of a Ham station. The silver statue stands on a handsome bakelite base on which is a silver plate. The name of the winner will be engraved on this plate before the trophy is sent to him.

The antenna is a rotary beam supported on a 36 ft. telephone pole erected in the back yard. The antenna is 17' x 17' square and is bi-directional. It gives a 4R gain on receiving and a 1 $\frac{1}{2}$ R gain in transmitting over $\frac{1}{2}$ wave doublet. The antenna is fed with a quarter wave stub and 45 ft. of coaxial cable. It is extremely effective, as we have worked 55 countries on phone in all continents. WAC on phone was made with 120 watts in 1936. We worked VU2CQ several times and got reports ranging up to R8. The antenna is rotated by means of two ropes from the shack.

So much for the present rig. Hr's some other dope you might be interested in.

I'm 19 years old and am in the first year
(Continued on page 376)

World Short Wave Stations

Revised Monthly

Complete List of SW
Broadcast Stations

Reports on station changes are appreciated.

Mc.	Call	Mc.	Call	Mc.	Call			
31.600	WIXKA	BOSTON, MASS., 9.494 m., Addr. Westinghouse Co. Daily 5 am.-12 m., Sun. 7 am.-12 m. Relays WBZ.	17.800	TGWA	GUATEMALA CITY, GUAT., 16.84 m., Addr. Ministre De Fomento. Irregular.			
31.600	WIXKB	SPRINGFIELD, MASS., 9.494 m., Addr. Westinghouse Co. Daily 5 am.-12 m., Sun. 7 am.-12 m. Relays WBZ.	17.790	GSG	DAVENTRY, ENG., 16.86 m., Addr. B.B.C., London. 1 m.-3.15 am., 5.45 am.-12 n., 12.20-6, 6.17-8.30 pm.			
31.600	W3XEY	BALTIMORE, MD., 9.494 m., Relays WF8R 4 pm.-12 m.	17.785	JZL	TOKYO, JAPAN, 16.87 m. Irregular.			
31.600	W2XDV	NEW YORK CITY, 9.494 m., Addr. Col. Broad. System, 485 Madison Ave. Daily 5-10 pm.; Sat. and Sun. 12.30-5, 6-9 pm.	17.780	W3XAL	BOUND BROOK, N. J., 16.87 m., Addr. Natl. Broad. Co. 8 am.-8 pm.			
31.600	W9XHW	MINNEAPOLIS, MINN., 9.494 m. Relays WCCO 9 am.-12 m.	17.770	PHI2	HUIZEN, HOLLAND, 16.88 m., Addr. (See PHI, 11.730 mc.) Off the air at present.			
31.600	W3XKA	PHILADELPHIA, PA., 9.494 m., Addr. NBC. Relays KYW 9 am.-10 pm.	17.760	DJE	BERLIN, GERMANY, 16.89 m., Addr. Broadcasting House. 12.05-10 am.; also Sun. 11.10 am.-12.25 pm. Daily 4.50-10.45 pm.			
31.600	W5XAU	OKLAHOMA CITY, 9.494 m., Sun 12 n.-1 pm., 6-7 pm. Irregular other times.	17.760	W2XE	NEW YORK, N. Y., 16.89 m., Addr. Col. Broad. System, 485 Madison Ave. Irregular.			
31.600	W4XCA	MEMPHIS, TENN., 9.494 m. Addr. Memphis Commercial Appeal. Relays WMC.	17.755	ZBW5	HONGKONG, CHINA, 16.9 m., Addr. P.O. Box 200. 4-10 am. Irregular.			
31.600	W8XA1	ROCHESTER, N. Y., 9.494 m., Addr. Stromberg Carlson Co. Relays WHAM 7.30-12.05 am.	End of Broadcast Band		15.245	TPA2	PARIS, FRANCE, 19.68 m., Addr. 98 Bis. Blvd. Haussmann. "Paris Mondial" 5-10 am.	
31.600	W8XWJ	DETROIT, MICH., 9.494 m., Addr. Evening News Ass'n. Relays WWJ 6-12.30 am., Sun. 8 am.-12 m.	17.310	W2XG8	HICKSVILLE, L. I., N. Y., 17.33 m., Addr. Press Wireless, Box 296. Tests 9.30-11.30 am. except Sat. and Sun.	15.230	HS8PJ	BANGKOK, SIAM, 19.7 m. Irregularly Mon. 8-10 am.
31.600	W9XPD	ST. LOUIS, MO., 9.494 m., Addr. Pulitzer Pub. Co. Relays KSD.	15.550	CO9XX	TUINICU, ORIENTE, CUBA, 19.29 m., Addr. Frank Jones, Central Tuinicu, Tuinicu, Santa Clara. Broadcasts irregularly evenings.	15.230	OLR5A	PRAGUE, CZECHOSLOVAKIA, 19.7 m. Addr. (See OLR4A, 11.84) Sun., Wed., Sat. 5-5.10 pm.; Mon., Tues., Thurs., Fri. 6.55-9.55 pm.
26.450	W9XA	KANSAS CITY, MO., 11.33 m., Addr. Commercial Radio Eqpt. Co. Testing after August 1st.	15.370	HAS3	BUDAPEST, HUNGARY, 19.52 m., Addr. Radiolabor, Gyali Ut 22. Sun. 9-10 am.	15.220	PCJ2	HUIZEN, HOLLAND, 19.71 m., Addr. N. V. Philips' Radio Hilversum. Sun., Mon., Thurs., Fri., Sat. 6.25-9.30 am., Tues. 12.30-2 am., 6.25-9.30 am., Wed. 12.30-11 am.
26.400	W9XAZ	MILWAUKEE, WIS., 11.36 m., Addr. The Journal Co. Relays WTMJ from 1 pm.	15.360	DZG	ZEESEN, GERMANY, 19.53 m., Addr. Reichspostzenstralamt. Tests irregularly.	15.210	WBXK	PITTSBURGH, PA., 19.72 m., Addr. (See 21.540 mc.) 8 am.-6 pm.
26.300	W2XJ1	NEW YORK, N. Y., 11.4 m., Addr. Bamberger Broad. Service, 1440 Broadway. Relays WOR 8 am.-1 am.	19 Met. Broadcast Band		15.200	DJB	BERLIN, GERMANY, 19.74 m., Addr. (See 15.280 mc.) 12.05-11 am., 4.50-10.45 pm. Also Sun. 11.10 am.-12.25 pm.	
26.100	W9XJL	SUPERIOR, WIS., 11.49 m. Relays WEBC daily.	15.340	DJR	BERLIN, GERMANY, 19.56 m., Addr. B'rdcast'g House, 8-9 am., 4.50-10.45 pm.	15.190	LYZ4	LAHTI, FINLAND, 19.75 m. Addr. Oy Suomen Yleisradio, Ab., Lahten Yleisradioasema, Lahti. Irregular 12.30-1.30 pm.
25.950	W6XK6	LOS ANGELES, CAL., 11.56 m., Addr. B. S. McGlashan, Wash. Blvd. at Oak St. Relays KGFJ 24 hours daily.	15.330	W2XAD	SCHENECTADY, N. Y., 19.56 m., Addr. General Electric Co. Relays WGY 11.30 am.-6 pm.	15.190	ZBW4	HONGKONG, CHINA, 19.75 m., Addr. P. O. Box 200. Irregular. 11.30 pm. to 1.15 am., 3-10 am.
25.950	W9XUP	ST. PAUL, MINNESOTA, 11.56 m. Relays KSTP.	15.320	OLR5B	PRAGUE, CZECHOSLOVAKIA, 19.58 m. Addr. (See 11.840 mc.) Sun., Wed., Sat. 5-5.10 pm.; Mon., Tues., Thurs., Fri. 6.55-9.55 pm.	15.180	GSO	DAVENTRY, ENG., 19.76 m., Addr. (See 17.79 mc.) 4.15-6, 6.20-8.30 pm., 1-3.15 am.
21.550	GST	DAVENTRY, ENG., 13.92 m., Addr. (B.B.C., London) Irregular at present.	15.310	GSP	DAVENTRY, ENG., 19.6 m., Addr. (See 17.79 mc.) 4.15-6, 6.20-8.30 pm.	15.170	TGWA	GUATEMALA CITY, GUAT., 19.77 m., Addr. (See 17.8 mc.) Daily 10.45-11 am.; Sun. 10.45 am.-6 pm.
21.540	W8XK	PITTSBURGH, PA., 13.93 m., Addr. Grant Bldg. Relays KDKA 6.45-9 am. Also Sunday, 6 pm.	15.300	XEBM	MAZATLAN, SIN., MEX., 19.61 m., Addr. Box 78, "El Pregonero del Pacifico." Irregularly 9-10 am., 1-2, 8-10 pm.	15.160	XEWW	MEXICO CITY, MEXICO, 19.79 m., 12 n.-12 m., irregular.
21.530	GSI	DAVENTRY, ENG., 13.93 m., Addr. (See 21.550 mc.) 5.45 am.-12 n.	15.300	—	ROME, ITALY, 19.61 m., Addr. (See 2RO, 11.81 mc.) Relays 2RO to 9 pm. irregularly.	15.160	JZK	TOKYO, JAPAN, 19.79 m. 12.30-1.30 am., 2.30-4, 4.30-5.30, 8-8.30 pm., 12.30-1.30 am.
21.520	W2XE	NEW YORK CITY, 13.94 m., Addr. Col. Broad. Syst., 485 Madison Ave. Daily exc. Sat. and Sun. 6.30-9 am. Sat. and Sun. 7 am.-12 n.	15.290	LRU	BUENOS AIRES, ARG., 19.62 m., Addr. El Mundo. Relays LRI, 7-9 am.	15.160	VUD3	DELHI, INDIA, 19.79 m., Addr. All India Radio. 1.30-3.30 am., 6.30-8.30 am.
21.500	W2XAD	SCHENECTADY, N. Y., 13.95 m., General Electric Co., 7-11 am.	15.280	H13X	CIUDAD TRUJILLO, D. R., 19.63 m., Relays H1X Sun. 7.40-10.40 am. Weekdays 12.10-1.10 pm.	15.155	SM5SX	STOCKHOLM, SWEDEN, 19.79 m., Daily 11 am.-5 pm., Sun. 9 am.-5 pm.
21.470	GSH	DAVENTRY, ENG., 13.97 m. (See 21.550 mc.), 5.45 am.-12 n.	15.280	DJQ	BERLIN, GERMANY, 19.63 m., Addr. Broadcasting House. 12.05-10 am., 4.50-10.45 pm. Also Sun. 11.10 am.-12.25 pm.	15.150	YDC	BANDOENG, JAVA, 19.8 m., Addr. N. I. R. O. M. 6-7.30 pm., 10.30 pm.-2 am., Sat. 7.30 pm.-2 am., daily 5.30-10.30 am.
21.450	DJS	BERLIN, GERMANY, 13.99 m., Addr., Broadcasting House. 12.05-11 am.	15.270	W2XE	NEW YORK CITY, 19.65 m., Addr. (See 21.520 mc.) Daily except Sat. and Sun., 12 n.-5 pm., Sat. & Sun. 1.30-5 pm.	15.140	GSF	DAVENTRY, ENG., 19.82 m., Addr. (See 17.79 mc.) 5.45 am.-12 n.
19.020	HS8PJ	BANGKOK, SIAM, 15.77 m. Mondays 8-10 am.	15.260	GSI	DAVENTRY, ENG., 19.66 m., Addr. (See 17.79 mc.) 1-3.15 am., 12.20-4 pm., 9.20-11.25 pm.	15.130	TPB6	PARIS, FRANCE, 19.83 m., Addr. "Paris Mondial," 98 Bis Blvd. Haussmann. 6-8.15 pm.
18.480	HBH	GENEVA, SWITZERLAND, 16.23 m., Addr. Radio Nations. Sun., 10.45-11.30 am.	15.250	WIXAL	BOSTON, MASS., 19.67 m., Addr. University Club. Daily 1-2 pm., Sun. 10 am.-12 n. Tues., Thurs. 3.30-5.30 pm.	15.130	WIXAL	BOSTON, MASS., 19.83 m., Addr. World-Wide B'cast'g Foundation. University Club. 10-11 am., Mon.-Fri.
16 Met. Broadcast Band				End of Broadcast Band		15.120	HVJ	VATICAN CITY, 19.83 m., 10.30-10.45 am., Tues., Wed. & Thurs.
17.810	—	ROME, ITALY, 16.84 m., Addr. (See 2RO, 11.81 mc.) Relays 2RO to 6 pm. irregularly.				15.110	DJL	BERLIN, GERMANY, 19.85 m., Addr. (See 15.280 mc.) 12 m.-2, 8-9 am., 10.40 am.-4.25 pm., also Sun. 6-8 am.
17.810	TPB3	PARIS, FRANCE, 16.84 m. Addr. (See 15.245 mc.) 8.30-10 am.				15.080	RK1	MOSCOW, U.S.S.R., 19.87 m. Works Tashkent near 7 am. Broadcasts Sun. 12.15-2.30 pm. Daily 7-9.15 pm.
								End of Broadcast Band
						14.940	PSE	RIO DE JANEIRO, BRAZIL, 20.08 m., Broadcasts Wed. 3.45-4.15 pm.
						14.920	LZA	SOFIA, BULGARIA, 20.10 m., Addr. Radio Garata. Mon., Tues., Thurs., Fri. 11.30 am.-2.45 pm., Wed. 11.30 am.-4.45 pm., Sat. 11.30 am.-5 pm., Sun. 2 am.-5 pm. Daily except Sun. 5-6.30 am.
						14.600	JVH	NAZAKI, JAPAN, 20.55 m. Broadcasts irregularly 5-11.30 pm. Works Europe 4-8 am.

(Continued on page 348)

All Schedules Eastern Standard Time

Let's Listen In with

Joe Miller

"DX" Editor

● HERE 'tis, the October issue, and with it the end of our second year with **SHORT WAVE & TELEVISION**.

We can certainly look back over the past two years with pleasant memories of the many FB acquaintances we have made among our numerous readers.

As this article is being written, in the midst of the August heat wave, dx conditions are fairly good, but not dependable from day to day. The still high noise level mars many good dx signals, often being the difference between hearing or losing the call letters of the weaker fones.

By the time this article appears in print, the fall upswing in improved reception will definitely be evident, with continually lowering QRN and a pick-up in strength of many signals.

Begin tuning the 10 meter ham band as soon as you read this, if not yet, as this band begins its fall and winter peak during this month. Best times for good dx between 10 am.-1 pm., with a peak near noon.

During the past month, we realized a much-cherished and coveted objective, in our final realization of 100 VAC, which mark we have since comfortably passed. Never did we imagine, when we began SW dxing somewhat less than 5 years ago, that such an attainment was even within the realm of possibility!

To mind comes the occasion, 3 short years ago, when a well-known dxer's mark of all of 6 VAC was challenged by a then well-known dx writer as *impossible!* Impossible that any dxer could have amassed such a remarkable total, and this only 3 years ago!

And so short waves go on, with yesterday's impossibility today's reality in achievement.

As the world's first dxer to reach 100 VAC, we are moved to inaugurate a new dx organization, for which we hope some of you may eventually become eligible, i.e., the Century VAC Club, certainly the most exclusive dx organization one could imagine, hi, what with the *only* requirement being that one possess veris on fone totalling 100 VAC!

Now to DX:



FRENCH INDO-CHINA

Radio Boy-Landry, 9.76 mc., at Saigon, was well received one am. during July, despite QRN. The 31 meter band, year in and year out, is the most reliable SW dx band, and most anything on the air, no matter where it's located on this ever-shrinking little globe of ours, will sooner or later be logged, if one but perseveres, on this popular SW BC band. Boy-Landry transmits on 3 waves now, 6.20, 11.71, and on 9.76 mc. Look for Saigon on the 2 higher frequencies in September, in the early am. hours.

QRA: Ets. Boy-Landry, Dept. Radio, 17, Place A Foray, Saigon, French Indo-China. Rene Lebon, whose station card and photo we showed in our last article, operates in Hanoi as F18AC, a famous Asiatic amateur call. He sends us some news of new SW BC stations in Indo-China.

Radio Hanoi I, 9.51 mc., and Radio Hanoi II, 11.90 mc., using 15 and 150 watts respectively, and built personally by Rene, are now on the air daily, midnight, 2 am. and 6-10 am. EST. Rene adds that these stations are owned by the Radio Club de l'Indo-chine, and that all correct reports will be verified. Address the Radio Club de l'Indo-chine, Radio Hanoi, Hanoi, French Indo-China.

CHINA

XTJ, 11.69 mc., Hankow, was very well heard one morning while in contact with XTS, 11.44 mc., at Swatow, also a line signal. Both stations used inverted speech. This at 5:25 am.

XTJ daily broadcasts from 7-7:30 am. as "The Voice of China," and is very well heard on the West Coast, both while phoning at all hours of am. and broadcasting.

NGX, 9.20 mc., also at Hankow, which relays the powerful XGOW, BCB station at Hankow, is being well heard on the West Coast from 5-10 am, according to Ashley Walcott, W6. Tho the assigned frequency of NGX is 9.20 mc., the station varies this frequency inside the limits of 9-9.25 mc., to avoid interference, probably purposely created, by the enemy forces. XGX uses 150 watts. In a verification of XGX to Mr.

Left: J6DP (Photo) Here's a really FB DX shack, which RYUICHI proudly presents! FB, OM!

Below: An outstanding DX QSL card: white letters on blue background.



F88AB—A charming photo of "OM" Paul and the Junior "OP," all set in his FB DX shack to work some real DX. And Paul is some DXer!

Walcott, T. Y. Woo, Director, the Central Broadcasting Administration, Central Executive Committee of Kuomintang, Chungking, China, states that a powerful new 35 kw. transmitter is being installed, and will be broadcasting within a few months. Reports on XGX should be sent to Mr. Woo.

FINLAND

Lahti is now being reported by numbers of alert dxers throughout the U. S., mostly on the 31 meter band, where its signal is heard at 9.50 mc., its schedule being 12:15-5 pm. On 11.78 mc., the schedule is 1:05 am.-12:05 pm. This data is contained in a veri to Ed Goss, W2, N. Y. State manager for I. D. A., for the 9.50 mc. wave. Veri states power is 1 kw.

Lahti is also reported with an exceptional rating of R9 for the West Coast by Max Fisher, W6, on 15.189 mc., one morning, from 12:30 am. till after 3 am. Max adds that a woman makes announcements, these in English, on the hour, with often a 2-5 minute silence between annts. When heard in early am., this station broadcasts physical exercises, conducted by either a man or woman, accompanied by an organ. Watch for this new country to add to ur logs. Lahti QSLs promptly. QRA in last issue.

MADAGASCAR

Radio Tananarive, with its 3rd verification here (this for 10.95 mc.), has been, to put it aptly, "cleaned up," as we already had the 9.5 and 6 mc. veris of this ace catch. Look for this rare dx "sig" this fall and winter on frequencies of 9.38 and 10.95 mc. on a schedule of 12:30-12:45 am., 3:30-4:30 am., 10-11 am. wkdays; and 2:30-4 am. Sundays. Our luck has always held up on the Sunday transmissions between 2:30-4 am.

FED. MALAY STATES

ZGE, 6.21 mc. (now heard on 6.24) at Kuala Lumpur, at last QSL'd our hopeful reports of April, 1937, with its station card, which will be shown next month (conditions permitting). We had the ill-fortune to forget to write ZGE c/o the Malayan Amateur Radio Society, which organization operates the transmitter, the same one as used for commercial telephony under the call ZGB. However, a follow-up report, (Continued on page 379)

Mc.	Call	
14.535	HBJ	GENEVA, SWITZERLAND, 20.64 m., Addr. Radio Nations. Broadcasts Sun. 1.45-2.30 pm.
14.440	—	RADIO MALAGA, SPAIN, 20.78 m. Relays Salamanca 8.15-8.45 pm. Sometimes 2-4 pm.
14.166	PIIJ	DORDRECHT, HOLLAND, 21.15 m., Addr. (See 7.088 mc.) Sat. 12 n.- 12.30 pm.
14.004	EA9AH	TETUAN, SPANISH MOROCCO, 21.4 m. Apartado 124. News at 4.30 and 7.15 pm. Relays Sala- manca from 5.40 pm.
13.635	SPW	WARSAW, POLAND, 22 m. Daily 6-8 pm. Sat. & Sun. 6-9 pm.
12.862	W9XDH	ELGIN, ILL., 23.32 m. Press Wire- less, Tests 2-5 pm.
12.235	TFJ	REYKJAVIK, ICELAND, 24.52 m. Works Europe mornings. Broad- casts Sun. 1.40-2.30 pm.
12.200	—	TRUJILLO, PERU, 24.58 m., "Rancho Grande." Address Hacienda Chiclin. Irregular.
12.060	RNE	MOSCOW, U.S.S.R., 24.88 m. Daily 6-7 am., 12.15-1 pm., 8-9.15, 10- 11 pm., also Sun. 6 am.-1 pm.
11.970	H12X	CIUDAD TRUJILLO, D. R., 25.07 m., Addr. La Voz de Hispaniola. Relays HIX Tue. and Fri. 8.10- 10.10 pm.

25 Met. Broadcast Band

11.910	CD1190	VALDIVIA, CHILE, 25.2 m., P. O. Box 642. Relays C869 10 am.-1 pm., 11 am.-10 pm.
11.900	XEW1	MEXICO CITY, MEXICO, 25.21 m., Addr. P. O. Box 2874. Mon., Wed., Fri. 3-4 pm., 9 pm.-12 m. Tues. and Thur. 7.30 pm.-12 m., Sat. 9 pm.-12 m.
11.895	HP51	AGUADULCE, PANAMA, 25.22 m., Addr. La Voz del Interior. 7.30- 9.30 pm.
11.885	TPA3	PARIS, FRANCE, 25.24 m., Addr. (See 15.245 mc.) 1-4 am., 10.15 am.-5 pm.
11.885	TPB7	PARIS, FRANCE, 25.24 m. (See 15.245 mc.) 6-8.15, 8.30-11 pm.
11.870	W8XK	PITTSBURGH, PA., 25.26 m., Addr. (See 21.540 mc.) 6-8.45 pm.
11.860	YDB	SOERABAJA, JAVA, 25.29 m., Addr. N. I. R. O. M. Sat. 7.30 pm. to 2.30 am., daily 10.30 pm. to 2 am.
11.860	GSE	DAVENTRY, ENG., 25.29 m., Addr. (See 11.75 mc.)
11.855	DJP	BERLIN, GERMANY, 25.31 m., Addr. (See 15.280 mc.) Irregular 11.35 am.-4, 7-10.45 pm.
11.840	KZRM	MANILA, P. I., 25.35 m. Addr. Erlanger & Gallinger, Box 283. 9 pm.-10 am. Irregular.
11.840	CSW	LISBON, PORT., 25.35 m. Nat'l Broad. Station. 11.30 am.-1.30 pm. Irregular.
11.840	OLR4A	PRAGUE, CZECHOSLOVAKIA, 25.34 m., Addr. Czech Shortwave Sta., Praha XII, Fochova 16. Mon., Tues., Thurs., Fri. 6.55-9.55 pm.
11.830	W9XAA	CHICAGO, ILL., 25.36 m., Addr. Chicago Federation of Labor. Irregular 7 am.-6 pm.
11.830	W2XE	NEW YORK CITY, 25.36 m., Addr. Col. Broad. System, 485 Madison Ave., N.Y.C. 5.30-10 pm.
11.826	XEBR	HERMOSILLA, SON., MEX., 25.37 m., Addr. Box 68, Relays XEBH. 1-4 pm., 9 pm.-12 m.
11.820	GSN	DAVENTRY, ENG., 25.38 m., Addr. (See 11.75 mc.) Irregular.
11.810	ZRO	ROME, ITALY, 25.4 m., Addr. E.I.A.R., Via Montello 5. Daily 5-8.45 am., 10 am.-9 pm.
11.805	CO6F	MATANZAS, CUBA, 25.41 m., Addr. Gen. Betancourt St. Relays MGF. 2-3, 4-5, 6-11 pm.
11.805	OZG	SKAMLEBOAEK, DENMARK, 25.41 m. Addr. Statsradiofonien. Irreg.
11.800	JZJ	TOKYO, JAPAN, 25.42 m., Addr. Broadcasting Co. of Japan, Overseas Division. 7-7.30, 8-9.30 am., 2.30-4, 4.30-5.30 pm.
11.795	DJO	BERLIN, GERMANY, 25.43 m., Addr. (See 15.280 mc.) Off the air at present.
11.790	WIXAL	BOSTON, MASS., 25.45 m., Addr. (See 15.250 mc.) Mon., Wed., Fri. 3.30-5.30 pm., Sat. 5-5.30 pm., Sun. 2-4.30 pm.

Mc.	Call	
11.780	HP5G	PANAMA CITY, PAN., 25.47 m., Addr. Box 1121. Heard till 12 m.
11.780	LYZ3	LAHTI, FINLAND, 25.47 m. Addr. (See 15.190 mc., LYZ4) Irregularly after midnight.
11.770	DJD	BERLIN, GERMANY, 25.49 m., Addr. (See 15.280 mc.) 10.40 am.- 4.30 pm., 4.50-11 pm.
11.760	TGWA	GUATEMALA CITY, GUAT., 25.51 m. (See 17.8 mc.) Irregular 10- 11.30 pm. Sun. 6-11.30 pm., ir- regular.
11.760	OLR4B	PRAGUE, CZECHOSLOVAKIA, 25.51 m., Addr. (See 11.840 mc.) Irregular.
11.750	GSD	DAVENTRY, ENG., 25.53 m., Addr. B.B.C., London. 1-3.15, am., 12.20-4.00 p.m., 6.20-8.30, 9.20- 11.25 pm.
11.740	COCX	HAYANA, CUBA, 25.55 m. P. O. Box 32. 6.55 am.-1 am. Sun. till 12 m. Relays CMX.
11.740	HVJ	VATICAN CITY, 25.55 m. Testing irregular.
11.730	XETA	MONTEREY, MEX. 25.57 m., Addr. Box 203. Relays XET, 12 n.-2 pm.
11.730	PHI	HUIZEN, HOLLAND, 25.57 m., Addr. N. V. Philips' Radio.
11.730	WIXAL	BOSTON, MASS., 25.57 m., Addr. World-Wide B'cast'g. Founda- tion, University Club. Daily exc. Sat. and Sun. 8-10 pm.
11.720	CJRX	WINNIPEG, CANADA, 25.6 m., Addr. James Richardson & Sons, Ltd. Daily 6 pm.-12 m., Sun. 5- 10 pm.
11.718	CR7BH	LAURENCO MARQUES, PORTU- GUESE E. AFRICA, 25.6 m. Daily 12.05-1, 4.30-6.30, 9.30-11 am., 12.05-4 pm., Sun. 5-7 am., 10 am.- 2 pm.
11.715	TPA4	PARIS, FRANCE, 25.61 m., (See 15.245 mc.) 5-7.15 pm., 8.30-11 pm.
11.710	SBP	MOTALA, SWEDEN, 25.63 m., 1.20- 2.05, 6-9 am., 11 am.-1 pm., Sat. 1.20-2 am., 6 am.-1.30 pm., Sun. 3 am.-1.30 pm.
11.710	YSM	SAN SALVADOR, EL SALVADOR, 25.63 m., Addr. (See 7.894 mc.) Irregular 1.30-2.30 pm.
11.700	HP5A	PANAMA CITY, PAN., 25.65 m. Addr. Radio Teatro, Apartado 954. 10 am.-10 pm.
11.700	CB1170	SANTIAGO, CHILE, 25.65 m. Addr. P.O. Box 706. Relays C889 6 pm.-12 m.

End of Broadcast Band

11.530	SPD	WARSAW, POLAND, 26 m., Addr. 5 Mazowiecka St. 6-9 pm.
11.402	HBO	GENEVA, SWITZERLAND, 26.31 m., Addr. Radio Nations. Sun. 7-7.45 pm., Mon. 1-1.15 am.
11.040	CSW	LISBON, PORTUGAL, 27.17 m., Addr. Nat. Broad. Sta. 1.30-5 pm.
11.000	PLP	BANDOENG, JAVA, 27.27 m. Re- lays YD8. 6-7.30 p.m., 5.30-10.30 or 11 am. Sat. until 11.30 am.
10.960	—	TANANARIVE, MADAGASCAR, 27.36 m., Addr. (See 9.53 mc.) 12.30-45, 3.30-4.30, 10-11 am.
10.670	CEC	SANTIAGO, CHILE, 28.12 m. Irregular.
10.660	JVN	NAZAKI, JAPAN, 28.14 m. Broad- casts daily 2-8 am. Works Europe irregularly at other times.
10.600	ZIK2	BELIZE, BRIT. HONDURAS, 28.25 m., Tues., Thurs., Sat. 7.30-7.45 pm.
10.535	JIB	TAIHOKU, TAIWAN, 28.48 m. Works Japan around 6.25 am. Broadcasts, relaying JFAK 9.05-10 am., 1-2.30 am. Sun. to 10.15 am.
10.370	EAJ43	TENERIFFE, CANARY ISLANDS, 28.93 m. Relays Salamanca, Spain. 2-4, 5-9.45 pm.
10.350	LSX	BUENOS AIRES, ARG., 28.98 m., Addr. Transradio International. Tests irregularly.
10.330	ORK	RUYSELEDE, BELGIUM, 29.04 m. Broadcasts 1.30-3 pm. Works OPM 1-3 am., 3-5 pm.
10.290	DZC	ZEESEN, GERMANY, 29.16 m., Addr. (See 15.360 mc.) Irregular.
10.260	PMN	BANDOENG, JAVA, 29.24 m. Re- lays YDB 5.30-10.30 or 11 am., Sat to 11.30 am.
10.220	PSH	RIO DE JANEIRO, BRAZIL, 29.35 m., Addr. Box 709. Broadcasts 6-9 pm.

Mc.	Call	
10.042	DZB	ZEESEN, GERMANY, 29.87 m., Addr. Reichspostzentramt. Ir- regular.
9.980	COBC	HAVANA, CUBA, 30.04 m., Addr. P. O. Box 132. Relays CMBC 6:55 a.m.-12:30 a.m.
9.940	JDY	DAIREN, MANCHUKUO, 30.18 m. Relays JOAK daily 7-8 am. Works Tokyo occasionally in early am.
9.865	COCM	HAVANA, CUBA, 30.41 m., Addr. Transradio Columbia, P. O. Box 33. 7 am.-12 m. Relays CMCM.
9.860	EAQ	MADRID, SPAIN, 30.43 m., Addr. Post Office Box 951. 7.30-8, 8.40- 9 pm.
9.830	IRF	ROME, ITALY, 30.52 m. Works Egypt afternoons. Relays ZRO, 6-9 pm.
9.760	CSW	LISBON, PORTUGAL, 30.74 m. Addr. Nat. Broad. Sta. 5-8 pm.
9.760	—	SAIGON, INDO-CHINA, 30.72 m., Addr. 17, Place A. Foray, "Radio Boy-Landry." Heard 6-9.15 am.
9.720	COCQ	HAVANA, CUBA, 30.85 m. Addr. 25 No. 445, Vedado, Havana, 6.55 am.-1 am. Sun. till 12 m.
9.700	FZF6	FORT DE FRANCE, MARTINIQUE, 30.9 m., Addr. P. O. Box 136. 11.30 am.-12.30 pm., 6.15-7.50 pm.
9.690	T14NRH	HEREDIA, COSTA RICA, 30.94 m., Addr. Amando C. Marin, Apart- ado 40. Sun. 7-8 am. Tues., Thurs., Sat. 9-10 pm.
9.685	TGWA	GUATEMALA CITY, GUAT., 30.96 m. Daily 10-11.30 pm.; Sun. 6- 11.30 pm.
9.675	DZA	ZEESEN, GERMANY, 31.01 m., Addr. (See 10.042 mc.) Irregular.
9.660	LRX	BUENOS AIRES, ARG., 31.06 m., Addr. El Mundo. Relays LRI, 9.30 am.-11.30 pm.
9.650	CS2WA	LISBON, PORTUGAL, 31.09 m., Addr. Radio Colonial. Tues., Thurs. and Sat. 3.30-6 pm.
9.645	HH3W	PORT-AU-PRINCE, HAITI, 31.1 m., Addr. P. O. Box A117. 1-2, 7-8 pm.
9.640	CXA8	COLONIA, URUGUAY, 31.12 m., Addr. Belgrano 1841, Buenos Aires, Argentina. Relays LR3, Buenos Aires 7 am.-11 pm.
9.635	ZRO	ROME, ITALY, 31.13 m., Addr. (See 11.810 mc.) Off the air at present.
9.630	HJ7ABD	BUCARAMANGA, COL., 31.14 m. 10 am.-12 n., 4-11 pm.
9.625	JFO	TAIHOKU, TAIWAN, 31.16 m. Re- lays JFAK irreg. 4-10 am.
9.616	HJ1ABP	CARTAGENA, COL., 31.20 m., Addr. P. O. Box 37. 11 am.-1 pm., 5-11 pm., Sun. 10 am.-1 pm., 3- 6 pm.
9.615	ZRK	KLIPHEUYAL, SOUTH AFRICA, 31.2 m., Addr. P. O. Box 4559, Johannesburg. Daily, exc. Sat. 11.45 pm.-12.50 am. Daily exc. Sun. 3.20-7.20, 9-11.45 am., Sun. 3.30-4.30 or 4-5, 5.30-7, 9-11.45 am.
9.607	HP5J	PANAMA CITY, PANAMA, 31.23 m. Addr. Apartado 867. 12 n. to 1.30 pm., 6-10.30 pm.

31 Met. Broadcast Band

9.600	RAN	MOSCOW, U.S.S.R., 31.25 m. 7- 9.15 pm.
9.595	HBL	GENEVA, SWITZERLAND, 31.27 m., Addr. Radio Nations. Irregular.
9.590	VUD2 VUD3	DELHI, INDIA, 31.28 m. Addr. All India Radio, 1.30-3.30 am., 6.30-8.30 am., 7.30 am.-12.30 pm.
9.590	PCJ	HUIZEN, HOLLAND, 31.28 m., Addr. (See 15.220 mc.) Sun. 2-3, Mon. 7-8, 8.15-9.25 pm. Tues. 1.45-2, 2.10-3.40 pm., Wed. 7-8.30, 8.45-10.15 pm., Thurs. 7-9 pm.
9.590	VK6ME	PERTH, W. AUSTRALIA, 31.28 m., Addr. Amalgamated Wireless of Australasia, Ltd. 6-8 am. exc. Sun.
9.590	VK2ME	SYDNEY, AUSTRALIA, 31.28 m., Addr. Amalgamated Wireless of Australasia, Ltd., 47 York St., Sun. 12 m.-2 am.; 4.30-8.30 am.; 11.30 am.-1.30 pm.
9.590	W2XE	NEW YORK, N. Y., 31.28 m., Addr. CBS, 485 Madison Ave., Irregu- lar.

(Continued on page 850)


All Schedules Eastern Standard Time

Radio Kinks

Each month the Editor will award a 2 year subscription for the best kink submitted. All other kinks published will be awarded eight months' subscription to RADIO & TELEVISION. Look over these kinks; they will give you some idea of what is wanted. Send a typewritten or ink description with sketch, of your favorite to the Kink Editor.

Housing for Xmtr 1st Prize

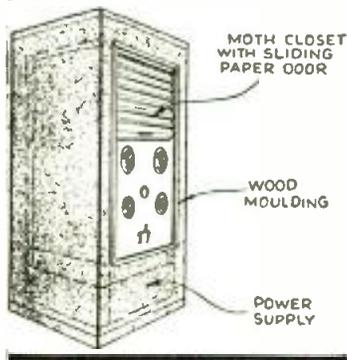
A sturdy moth-proof closet makes a first rate housing for a transmitter—and is very inexpensive. Those of the kind that are made with pressed wood panels on a wooden frame, and




which are equipped with sliding corrugated cardboard doors are excellent, for the framework will hold up to 150 lbs. weight. The heaviest unit—the power supply—rests on the floor inside the closet, so need not be included when calculating the weight of the apparatus. These cabinets are 2 feet deep by 3 feet wide, and may be had either 4 feet or 6 feet high.—George Nichols.

Power Supply

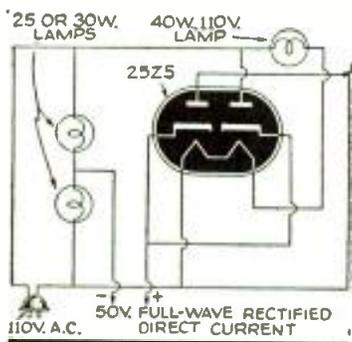A way of securing full-wave rectification of alternating current without the use of a power transformer is shown in the diagram. Two 25 or 30 watt incandescent lamps are connected in series across the 110 volt a.c. line, as shown, and the center point between them is used as the negative leg of the rectified voltage. The positive leg is




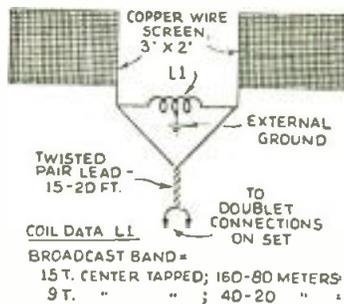taken from the two cathode terminals of the 25Z5 rectifier tube, as shown. The voltage output with this arrangement is about 50 volts at low current drains. The 40-watt lamp is used to reduce the filament voltage for the 25Z5 to its proper point.—Russell Yost.



Aerial Hint

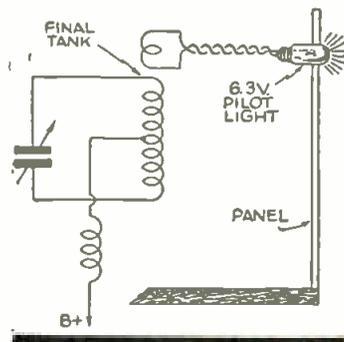I have had considerable interference with radio reception in my locality and finally hit on the scheme described for UHF reception. The coils specified are wound with No. 26 d.c.c. wire on a 1/4" diameter tube, suspended between the two legs of the antenna. I have had most gratifying results with this arrangement, the noise pick-up being very low and the signal pick-up high.—Frank Owens.




Carrier Indicator

A simple visual means of showing when a transmitter is on the air is to use a small wire loop coupled either to the final tank or to the oscillator coil of the transmitter. The ends of this loop are connected to a 6.3 volt pilot light on the front panel of the transmitter. When the transmitter is put on the air, the r.f. voltage induced in the loop will light up the 6.3 volt pilot bulb. Care must be taken that the coupling loop is not too close to the transmitter coils to prevent the bulb from being burned out.—Robert J. Ingelsby.

Even Bandspread

A particularly good way of assuring that any desired band is spread over an equal area on the tuning dial is shown here. A fixed condenser, C1, is mounted inside the plug-in coil form and connected as shown, in series with the bandspread tuning con-

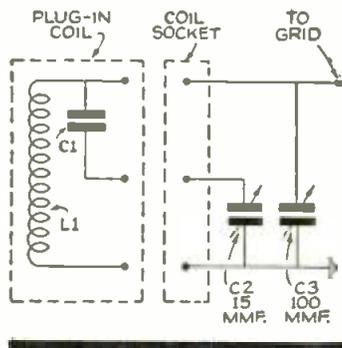
denser C2. If desired, C1 can be a variable condenser having a maximum capacity of 100 mmf. It should be adjusted so that the limits of any ham or broadcast band correspond to one complete rotation of band-



spread condenser C2. Without the use of condenser C1, it will be found that some bands will only cover a part of the rotation of the bandspread condenser while other bands will not be completely covered by one complete rotation of this condenser.—Homer Apple.

Phone & Speaker Kink

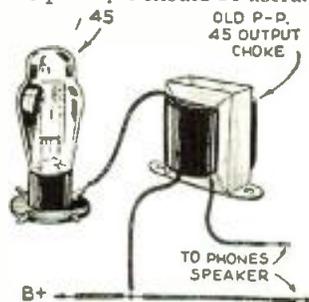
The diagram shows how I wired an output terminal for phones or loud speaker from a 45 tube. The inductance used is an old push-pull 45 output choke, and it works very well with phones or magnetic speaker. This principle should be useful in



sets using push-pull audio systems, by removing one of the power tubes and connecting the phones between the plate terminal on the socket of the tube removed and the B+.—M. P. McKay.

Low-Cost Chassis

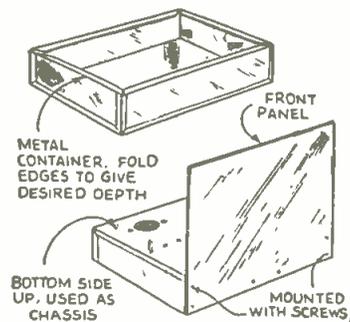
For experimental work a simple chassis may be fashioned at very little cost from tin containers such as are available from drug stores and garages. Baking pans will also serve for the purpose. With a pair of tins-



container so that it will be a 1/4" deeper than the desired chassis. Fold the extra 1/4" back to secure a smooth non-scratching edge. Holes for sockets, etc., can easily be cut with an old knife.—Jim Lattig, W9QJR.

Soldering Aids

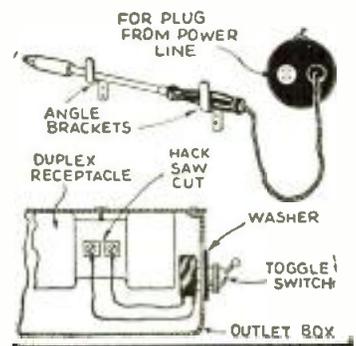
Two angle brackets mounted on the wall provide a resting place for the iron. If the iron is to be placed here while still warm, it is advisable to mount a piece of asbestos on the wall so



it will not be scorched. A duplex receptacle is needed, as shown in the sketch, and a toggle switch mounted on the side of a metal box provides a semi-permanent method of supplying power to the soldering iron. The toggle switch turns the iron on or off, as desired.—Lincoln Weeks.

Novel Condenser Shaft

It is frequently necessary to mount a condenser back of the metal panel on a transmitter or receiver and this arrangement requires the use of an insulated shaft. The drawing shows how an insulated section of shaft can be coupled to the condenser; the insulated section is made from the core of a pie-wound r.f. choke. The windings are cut off and the small metal caps on the ends are also removed. A shaft coupler completes the job.—Barnett Mitchell, W4EZI.

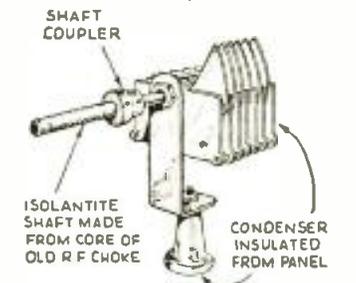


Mc.	Call	Mc.	Call	Mc.	Call
9.590	W3XAU	PHILADELPHIA, PA., 31.28 m. Relays WCAU Mon., Thurs., Sat. 12 n.-12 m.; Tues., Fri., Sun. 11 pm.-12 m.; Wed. 9 pm.-12 m.	9.500	LYZ2	LAHTI, FINLAND, 31.58 m., Addr. (See 15.19 mc. LYZ4) 2-5 pm.
9.580	G5C	DAVENTRY, ENGLAND, 31.32 m., Addr. B. B. C., Portland Pl., London, W. 1, 6.20-8.30, 9.20-11.25 pm.	9.500	HS8PJ	BANGKOK, SIAM, 31.58 m. Thursday, 8-10 am.
9.580	VLR	MELBOURNE, AUSTRALIA, 31.32 m. Addr. Box 1686, G. P. O. Daily 3.30-8.30 am. (Sat. till 9 am.) Sun. 3-7.30 am. Daily exc. Sat. 9.35 pm.-2.15 am.	9.488	EAR	MADRID, SPAIN, 31.6 m., Addr. (See 9.860 mc.) 7.30-8.30 pm. Mon., Tues., Thurs., Sat. at 9.30 pm, also.
9.580	OAX5C	ICA, PERU, 31.32 m. Radio Universal 6-10 pm.	End of Broadcast Band		
9.570	KZRM	MANILA, P. I., 31.35 m., Addr. Erlanger & Galinger, Box 283. Sun. 3-10 am. Daily exc. Sat. 4.30-7 pm., 11.15 pm.-12.15 am. Daily exc. Sun. 4-10 am.	9.445	HCODA	GUAYAQUIL, ECUADOR, 31.77 m. Irregularly till 10.40 pm.
9.570	W1XK	SPRINGFIELD, MASS., 31.35 m., Addr. Westinghouse Electric & Mfg. Co. Relays WBZ 6 am. to 12 m. Sun. 7 am.-12 m.	9.428	COCH	HAVANA, CUBA, 31.8 m., Addr. 2 B St., Vedado, 7 am.-1 am.
9.560	DJA	BERLIN, GERMANY, 31.38 m., Addr. Broadcasting House. 12.05-11 am., 7-10.45 pm.	9.380	—	TANANARIVE, MADAGASCAR, 31.96 m. Addr. Le Directeur des PTT, Radio Tananarive, Administration PTT. 12.30-12.45, 3.30-4.30, 10.11 am.
9.550	TPBII	PARIS, FRANCE, 31.41 m. Addr. (See 15.245 mc.) 1-3 am., 10.15 am.-5 pm.	9.355	HC1ETC	QUITO, ECUADOR, 32.05 m., Addr. Teatro Bolivar, Thurs. until 9:30 p.m.
9.550	W2XAD	SCHENECTADY, N. Y., 31.41 m., General Electric Co., 6.30-10 pm.	9.345	HBL	GENEVA, SWITZERLAND, 32.08 m., Addr. Radio Nations. Off the air at present.
9.550	OLR3A	PRAGUE, CZECHOSLOVAKIA, 31.41 m. (See 11.840 mc.) Irreg.	9.330	OAX4J	LIMA, PERU, 32.15 m., Addr. Box 1166, "Radio Universal." 12 n.-3 pm., 5 pm.-1 am.
9.550	XEFT	VERA CRUZ, MEX., 31.41 m. 10.30 am.-4.30 pm., 10.30 pm.-12.30 am.	9.290	HIG	CIUDAD TRUJILLO, D. R., 32.29 m., 7.10-8.40 am., 11.40 am.-2.10 pm., 3.40-8.40 pm.
9.550	YDB	SOERABAJA, JAVA, 31.41 m., Addr. N.I.R.O.M. Daily exc. Sat. 6-7.30 pm., 5.30 to 10 am. Sat. 5.30-11.30 am.	9.280	HC2CW	GUAYAQUIL, ECUADOR, 32.31 m., 11.30 am.-12.30 p.m., 8-11 pm.
9.550	VUB2	BOMBAY, INDIA, 31.41 m., Addr. All India Radio. 9.30-10.30 am., 1 am.-3.30 pm.	9.200	COBX	HAVANA, CUBA, 32.59 m. Addr. San Miguel 194, Altos. Relays CMBX 7 am.-12 m.
9.540	DJN	BERLIN, GERMANY, 31.45 m., Addr. (See 9.560 mc.) 4.50-10.45 pm.	9.125	HAT4	BUDAPEST, HUNGARY, 32.88 m., Addr. "Radiolabor," Gyali-ut, 22, Sun. and Wed. 7-8 pm., Sat. 6-7 pm.
9.540	VPD2	SUVA, FIJI ISLANDS, 31.45 m., Addr. Amalgamated Wireless of Australasia, Ltd. 5.30-7 am.	9.100	COCA	HAVANA, CUBA, 32.95 m., Addr. Galiano No. 102. Relays CMCA 9 am.-12 m.
9.535	JZ1	TOKYO, JAPAN, 31.46 m., Addr. (See 11.800, JZJ) Irregular.	9.020	COBZ	HAVANA, CUBA, 33.26 m., Radio Salas Addr. P. O. Box 866, 7:45 am.-12.10 am. Irreg. 12.30-2 am. Relays CMBZ.
9.535	HB9D	ZURICH, SWITZERLAND, 31.46 m., Addr. Radio Club of Zurich, Post Box Zurich 2. Sun. 9-11 am., Thur. 1-3 pm.	8.965	COKG	SANTIAGO, CUBA, 33.44 m. Addr. Box 137. 9-10 am., 11.30 am.-1.30 pm., 3-4.30, 5-6, 10-11 pm., 12 m.-2 am.
9.530	W2XAF	SCHENECTADY, N. Y., 31.48 m., Addr. General Electric Co. 3-11 pm.	8.841	HCJB	QUITO, ECUADOR, 33.5 m. 7-8.30 am., 11.45 am.-2.30 pm., 5-10 pm., except Mon. Sun. 12 n.-1.30 pm., 5.30-10 pm.
9.530	ZHO	SINGAPORE, MALAYA, 31.48 m., Mon.-Fri. 12.40-1.40 am., Sat. 12.25-1.40 am., 10.40 pm.-1.10 am. Irreg. 5.40-9.40 am.	8.700	HKV	BOGOTA, COLOMBIA, 34.46 m. Tues. and Fri. 7-7.20 pm.
9.526	XEDQ	GUADALAJARA, GAL., MEXICO, 31.49 m. Irregular 7.30 pm. to 12.30 am.	8.665	COJK	CAMAGUEY, CUBA, 34.64 m., Addr. Finlay No. 3 Altos. 5.30-6.30, 8-11 pm., daily except Sat. and Sun.
9.526	ZBW3	HONGKONG, CHINA, 31.49 m., Addr. P. O. Box 200. 11.30 pm. to 1 am., 3-10 am.	8.665	W2XGB	HICKSVILLE, N. Y., 34.64 m., Addr. Press Wireless. Mon. to Fri. News at 9 am. and 5 pm.
9.525	LKJ1	JELOY, NORWAY, 31.49 m. 5-8 am.	8.580	YNPR	MANAGUA, NICARAGUA, 34.92 m. Radiodifusora Pilot.
9.523	ZRH	ROBERTS HEIGHTS, S. AFRICA. 31.5 m., Addr. (See ZRK, 9.606 mc.) Daily exc. Sun. 5-7.30 am.; Sun. 5.30-7 am.	7.894	YSD	SAN SALVADOR, EL SALVADOR, 37.99 m., Addr. Dir. Genl. Tel. & Tel. 7-11 pm.
9.520	HJ4ABH	ARMENIA, COLOMBIA, 31.51 m. 6-10 pm.	7.870	HCIRB	QUITO, ECUADOR, 38.1 m. La Voz de Quito. 9-11 pm.
9.520	OZF	SKAMLEBOAEK, DENMARK, 31.51 m., Addr. Statsradionfoni, Heibergsgade 7, Copenhagen., 2-6.40, 8-11 pm.	7.854	HC2JSB	GUAYAQUIL, ECUADOR, 38.2 m. Evenings to 11 pm.
9.520	YSH	SAN SALVADOR, EL SALVADOR 31.51 m., Addr. (See 7.894 mc.) Irregular 6-10 pm.	7.797	HBP	GENEVA, SWITZERLAND, 38.48 m., Addr. Radio-Nations.
9.510	G5B	DAVENTRY, ENGLAND, 31.55 m., Addr. (See 9.580 mc.—G5C) 1-3.15 am., 1.30-4, 4.15-6, 6.20-8.30, 9.20-11.25 pm.	7.410	HCJ84	QUITO, ECUADOR, 40.46 m., 7-9.30 pm. irregularly.
9.510	HJU	BUENAVENTURA, COLOMBIA, 31.55 m., Addr. National Railways. Mon., Wed. and Fri. 8-11 pm.	7.380	XECR	MEXICO CITY, MEX., 40.65 m., Addr. Foreign Office. Sun. 6-7 pm.
9.500	VK3ME	MELBOURNE, AUSTRALIA, 31.58 m., Addr. Amalgamated Wireless of Australasia, 167 Queen St. Daily except Sun. 4-7 am.	7.220	HKE	BOGOTA, COL., S. A., 41.55 m. Tues. and Sat. 8-9 pm. Mon. and Thurs. 6.30-7 pm.
9.500	XEWW	MEXICO CITY, MEX., 31.58 m. Addr. Apart. 2516. Relays XEW. 6 pm.-12 m.	7.200	YNAM	MANAGUA, NICARAGUA, 41.67 m. Irregular at 9 pm.
			7.088	PIIJ	DORDRECHT, HOLLAND, 42.3 m., Addr. Dr. M. Hellingman, Technical College. Sat. 11.10-11.50 am.
			6.990	XEME	MERIDA, YUCATAN, 42.89 m., Addr. Calle 59, No. 517, "La Voz de Yucatan desde Merida." Irregular.
			6.977	XBA	TACUBAYA, D. F., MEX., 43 m. 9.30 am.-1 pm., 7-8.30 pm.
			6.805	HI7P	CIUDAD TRUJILLO, DOM. REP., 44.06 m., Addr. Emisoría Diaria de Comercio. Daily exc. Sat. and Sun. 12.40-1.40, 6.40-8.40 pm. Sat. 12.40-1.40 pm. Sun. 10.40 am.-11.40 am.
6.790	PZH	PARAMIRABO, SURINAM. 44.16 m., Addr. P. O. Box 18. Daily 6.05-8.36 am., Sun. 9.36-11.36 am. Daily 5.36-8.36 pm.			
6.775	HIH	SAN PEDRO DE MACORIS, DOM. REP., 44.26 m. 12.10-1.40 pm., 7:30-9 pm. Sun. 3-4 am., 4.15-6 pm., 4.40-7.40 pm.			
6.750	JVT	NAZAKI, JAPAN, 44.44 m., Addr. Kokusai-Denwa Kaisha, Ltd., Tokyo. Irregular.			
6.730	HI3C	LA ROMANA, DOM. REP., 44.58 m., Addr. "La Voz de la Feria." 12.30-2 pm., 5-6 pm.			
6.720	PMH	BANDOENG, JAVA, 44.64 m. Relays NIROM programs. 5.30-9 am.			
6.690	TIEP	SAN JOSE, COSTA RICA, 44.82 m., Addr. Apartado 257, La Voz del Tropico. Daily 7-10 pm.			
6.675	HBQ	GENEVA, SWITZERLAND, 44.94 m. Addr. Radio-Nations. Off the air at present.			
6.672	—	44:94 m., relays Salamanca, Spain, 7-9.45 pm.			
6.672	YVQ	MARACAY, VENEZUELA, 44.95 m. Irregular.			
6.635	HC2RL	GUAYAQUIL, ECUADOR, S. A., 45.18 m., Addr. P. O. Box 759. Sun. 5.45-7.45 pm., Tues. 9.15-11.15 pm.			
6.630	HIT	CIUDAD TRUJILLO, D. R., 45.25 m., Addr. "La Voz de la RCA Victor." Apartado 1105. Daily exc. Sun. 12.10-1.40 pm., 5.40-8.40 pm.; also Sat. 10.40 pm.-12.40 am.			
6.625	PRADO	RIOBAMBA, ECUADOR, 45.28 m. Thurs. 9-11.45 pm.			
6.558	HI4D	CIUDAD TRUJILLO, D. R., 45.74 m. Except Sun. 11.55 am.-1.40 pm.			
6.550	XBC	VERA CRUZ, MEX., 45.8 m. B.15-9 am.			
6.550	TIRCC	SAN JOSE, COSTA RICA, 45.8 m., Addr. Radioemisora Catolica Costarricense. Sun. 11 am.-2 pm., 6-7, 8-9 pm. Daily 12 n.-2 pm., 6-7 pm., Thurs. 6-11 pm.			
6.545	YV6RB	BOLIVAR, VENEZUELA, 45.84 m., Addr. "Ecos de Orinoco." 6-10.30 pm.			
6.520	YV4RB	VALENCIA, VENEZUELA, 45.98 m. 11 am.-2 pm., 5-10 pm.			
6.516	YNIGG	MANAGUA, NICARAGUA, 46.02 m., Addr. "La Voz de las Lagos." 8-9 pm.			
6.500	HIL	CIUDAD TRUJILLO, D. R., 46.13 m. Addr. Apartado 623. 12.10-1.40 pm., 5.40-7.40 pm.			
6.490	HIIL	SANTIAGO DE LOS CABALLEROS, D. R., 46.2 m., Addr. Pres., Trujillo 97, Altos., 5.40-7 pm.			
6.470	YNLAT	GRANADA, NICARAGUA, 46.36 m., Addr. Leonidas Tenoria, "La Voz del Mombacho." Irregular.			
6.465	YV3RD	BARQUISIMETO, VENEZUELA, 46.37 m. Radio Barquisimeto, irregular.			
6.450	HI4V	SAN FRANCISCO DE MACORIS, D. R., 46.48 m. 11.40 am.-1.40 am., 5.10-9.40 pm.			
6.440	TGQA	QUEZALTENANGO, GUATEMALA, 46.56 m. Mon.-Fri. 9-11 pm., Sat. 9 pm.-1 am., Sun. 1-3 pm.			
6.420	HIIS	SANTIAGO, D. R., 46.73 m. 11.40 am.-1.40 pm., 5.40-7.40, 9.40-11.40 pm.			
6.416	YV6RC	BOLIVAR, VENEZUELA, 46.73 m. Radio Bolivar.			
6.410	TIPG	SAN JOSE, COSTA RICA, 46.8 m., Addr. Apartado 225, "La Voz de la Victor." 12 n.-2 pm., 6-11.30 pm.			
6.400	YV5RH	CARACAS, VENEZUELA, 46.88 m. 7-11 pm.			
6.388	H18J	LAS VEGAS, D. R., 46.92 m., Irreg.			
6.384	VP2LO	STE. KITTS, B.W.I. 46.96 m. ICA Service Labs. Box 88. Daily 4-4.45 pm., Sun 10-10.45 am. and irreg. at other times.			
6.380	YV5RF	CARACAS, VENEZUELA, 46.92 m., Addr. Box 983. 6-10.30 pm.			
6.370	T18WS	PUNTARENAS, COSTA RICA, 47.07 m., Addr. "Ecos Del Pacifico", P. O. Box 75. 6 pm.-12 m.			
6.365	YVIRH	MARACAIBO, VENEZUELA, 47.18 m., Addr. "Ondas Del Lago." Apartado de Correos 261. 6-7.30 am., 11 am.-2 pm., 5-11 pm.			

(Continued on page 334)

All Schedules Eastern Standard Time

Question Box

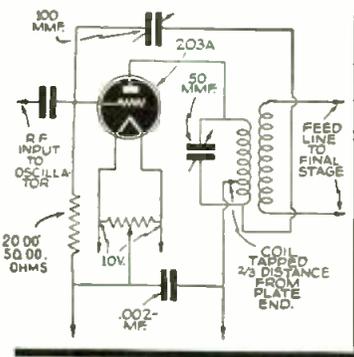

Circuit for a regenerative doubler —1154


Frequency Doubler

I have a 203A and an 800 and would like to use either as a frequency doubler. I intend to use either of these tubes at frequencies up to about 14 or 15 megacycles. Can you furnish me with a diagram of a doubler, using either of these tubes, and also state which tube I should use? I have seen many diagrams of frequency doublers in your magazine but none have appealed to me for my particular need.—G. H. Harris, Watertown, N. Y.

A 203A makes a wonderful frequency doubler at frequencies up to about 15 mc.; a single one in a regenerative doubler circuit will put out close to 100 watts on 20 meters, when excited by a 40-meter crystal oscillator. This is more than enough to "kick the pants off" a pair of 852's in push-pull when inductively coupled to them. Thus we can have over 750 watts in the antenna on 14 mc. with only three stages. The efficiency of the 03A stage could be increased either by increasing the excitation or by lowering the input, but we can sacrifice a little efficiency for the sake of the output, because a 03A will dissipate 80 or 90 watts without getting too warm. Thus if the efficiency of the 03A is only about 60%, we can still get about 100 watts out of it without exceeding the dissipation rating of the tube. The diagram of the frequency doubler is shown. There is much controversy as to whether the circuit is regenerative, degenerative or neutralized, but in any event, the output is greatly increased over that of a straight doubler. The grid resistor should be between 2,000 and 5,000 ohms and if over 1000 volts is placed on the tube, some protection in the form of battery bias in addition to the resistor bias is advisable.

By substituting an 800 for the 03A, the circuit will function nicely on 10 meters, but the output will be limited to about 25 watts because of the lesser allowable plate dissipation on the tube. With the 800, about 90 volts of battery bias should be used in addition to the grid-leak bias, for protection in the event that the tube should lose excitation.

A Low-Level Amplifier

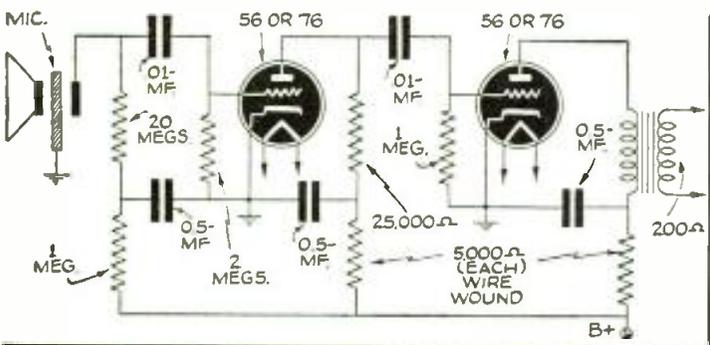

Hook-up for low-level amplifier with condenser microphone—1155

I have a large number of resistors on hand and would like to construct a high quality low-level audio frequency amplifier suitable for use with either a condenser or dynamic type microphone. This should be one for use with either the 56 or 76 type tubes. If possible could you publish a diagram of such an amplifier, giving list of parts?—Hiram Johnson, Harrisburg, Pa.


A number of inquiries have been received by this department requesting data for an amplifier, for use with either of the microphones mentioned. A diagram of such an amplifier is shown. With these microphones, an input transformer can be used, in which case the transformer secondary is connected directly from grid to ground across the 2 megohm grid-leak or resistor. With the use of an input transformer, we would eliminate the 20 and

1 meg. resistors and the .01 and .5 mf. conds. used to supply and isolate the d.c. polarizing voltage which places an initial charge on the "hot" plate of the condenser head.

Note that these tubes operate without bias. This is possible because of the small magnitude of the voltages involved. The output of the condenser head rarely exceeds 1/1000 volt. The gain of this amplifier is about 40 db, and the output can be connected to an amplifier designed to amplify the output of a double-button mike. This amplifier should be well shielded, especially if used in the vicinity of a transmitter, and should be kept far away from any power supply equipment, to avoid hum pickup. If a.c. is used on the heaters the heater circuit should be by-passed with 1 mf. condensers.

Photo-Cell Relay Circuit

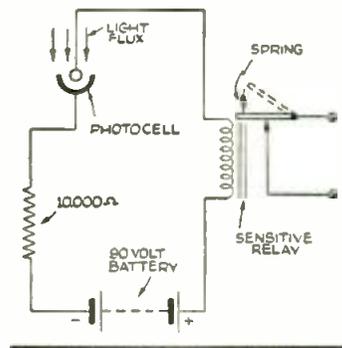Will you kindly publish a diagram of a simple photoelectric cell circuit, in which a sensitive relay can be made to operate. I would like to use this in connection with a circuit for a burglar alarm. I have the necessary apparatus on hand. All I would like is the diagram of the simplest relay system that I may use.—Harold M. Wilson, Cleveland, Ohio.




A simple photo-cell relay circuit —1156

There are any number of types of circuits that can be used in conjunction with photoelectric cells. However, one of the simplest photo-electric relay circuits is shown here. It is self-explanatory. A very sensitive relay should be used; one that will operate on about 30 microamperes. A very intense illumination or light source should be used.

A.V.C.-Fixed Bias Amplifier

I am constructing a super-het. receiver for all-wave operation but especially for reception on waves below 20 meters. In this receiver I wish to use a duplex-diode pentode of the 6B7 type as a half-wave rectifier and A.V.C., also as a fixed bias amplifier. Is it possible for me to secure a diagram showing how such a tube can be used as mentioned above? I intend to use all 6.3 volt heater tubes throughout the receiver.—Max Liebowitz, Montreal, Canada.

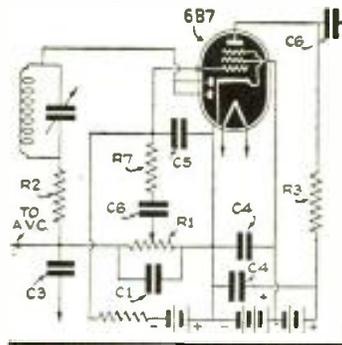

Simple A.V.C.-fixed bias amplifier —1157

The 6B7 is recommended for performing the simultaneous functions of A.V.C., detection and amplification. This 3-in-1 feature is important, allowing the constructor to choose whichever way he wishes to utilize the component units. Here is a diagram showing a half-wave detector, which utilizes both plates in parallel as the diode. The A.V.C. action is obtained by utilizing the voltage drop caused by the rectified current flowing through a resistor in the detector circuit.

A fee of 25c (stamps, coin or money order) is charged for letters that are answered by mail. This fee includes only hand-drawn schematics. We cannot furnish full-size working drawings or picture layouts. Letters not accompanied by 25c will be answered on this page. Questions involving considerable research will be quoted upon request. Names and addresses should be clearly printed on each letter.

An ADVANCED

Howard G. McEntee, W2FHP

High-Frequency Receiver

8-tube receiver covers 10, 20 and 40 meter bands. A high class set with bandspread, audio output meter, a built-in monitor, beat oscillator and a crystal filter.

● TO BEGIN with, the old receiver did not have sufficient "gimp" on the 20 meter band, and worse yet, it did not cover 10 meters at all. It was satisfactory, however, at 40 meters and the higher wavelengths. This led to the conclusion that the new job should be made to cover 40, 20 and 10 meters only. There is no reason why it cannot be used successfully on 5 meters, although no experiments have been conducted on this band. At this station, as at most others, a satisfactory 5 meter receiver was already at hand, and it was not desired to compromise the design too much. This receiver, then, is extra "hot" for 10 and 20, covers 40 in fine shape, and was designed with an eye to 5 meters.

Plug-In Coils Used

The highest efficiency called for plug-in coils, and being of a lazy type we did not care for the idea of lifting the cover and poking coils inside whenever a frequency shift was needed. Hence, a simplified means of inserting the coils through the front panel in one unit was worked out. The coil sets

when transmitting C.W., tuned the receiver to his own signal to improve keying or just to gloat over his own beautiful signal? The use of a *built-in* monitor has always seemed a fine solution to this problem, so such a unit is incorporated. Regeneration and tuning controls are right on the front panel, where they may be changed to suit. The monitor tube is also used as the beat oscillator, switching being accomplished by a relay as seen in the circuit diagram. This relay also has a set of contacts which open the B+ leads of the whole H.F. and I.F. portion of the receiver when the monitor is in operation. The relay operation is controlled by a switch incorporated in the monitor regeneration control. However, for ideal operation, the relay should be controlled by the same switch that turns on the transmitter, and for this purpose a pair of screw terminals are placed on the rear of the

chassis so that the monitor is turned on, and the B+ on all but tubes V5 and V6 turned off, when these terminals are closed. A separate volume control for the monitor makes it unnecessary to disturb settings of receiver controls in any manner when using the monitor. This latter control is mounted on the shield of the B.F.O. compartment, directly over the relay.

Standard plug-in coils are used for the monitor with the addition of a 50 mmf. trimmer condenser placed in each coil. This acts as the *tank* condenser while the monitor panel control provides *bandspread* tuning.


Audio Output Meter

Another unusual feature of the receiver is the addition of an *audio output meter*. This is very useful, particularly for radio-fone work, and some very useful data may be secured when the A.F. voltage is noted in conjunction with the carrier strength as shown by the "R Meter." Of course, since no attempt is made to match the impedance of the meter to that of the output circuit, the true A.F. output capabilities of the set are not registered, but the meter is useful mainly for comparative purposes. Possessing a basic range of 0-1 V. A.C., the 13,000 ohm resistor gives a rough multiplication of 10, which is a sufficient range in view of the existing impedance mismatch.


Crystal Filter

The balance of the receiver is more or less straightforward, with possible exception of the *crystal filter* circuit. An I.F. of 1600 kc. is employed, and the use of the conven-

(Continued on page 382)

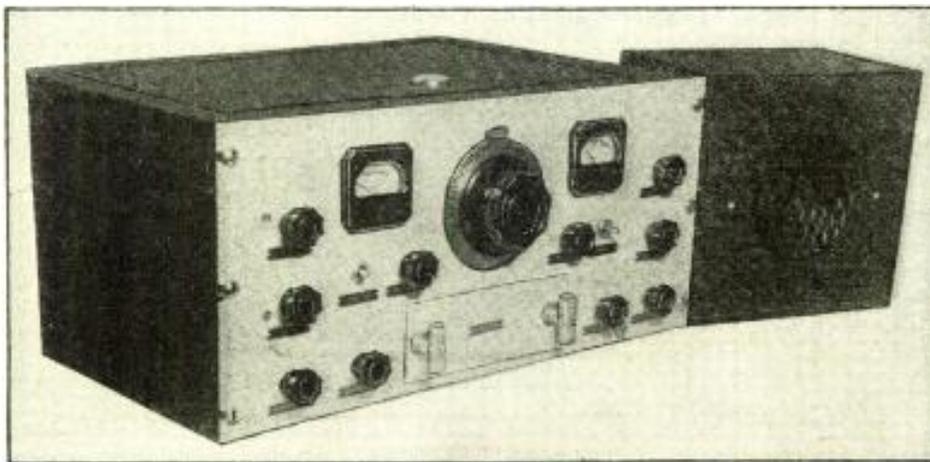

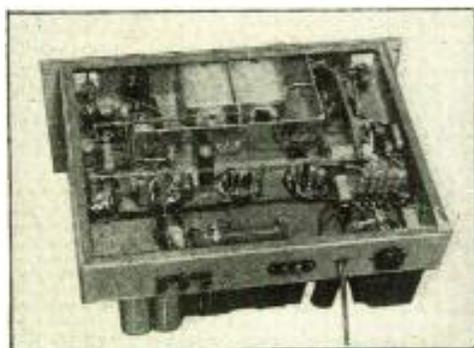are completely self-contained and protected. Several ideas in receiver features have long been attractive to us. Who has not,



Bottom view.

Note the handsome appearance of the Communications Receiver built by Mr. McEntee and shown above, together with loud-speaker, which is housed in the grilled cabinet at the right.

Rear view of the receiver, showing the power transformer and chokes.



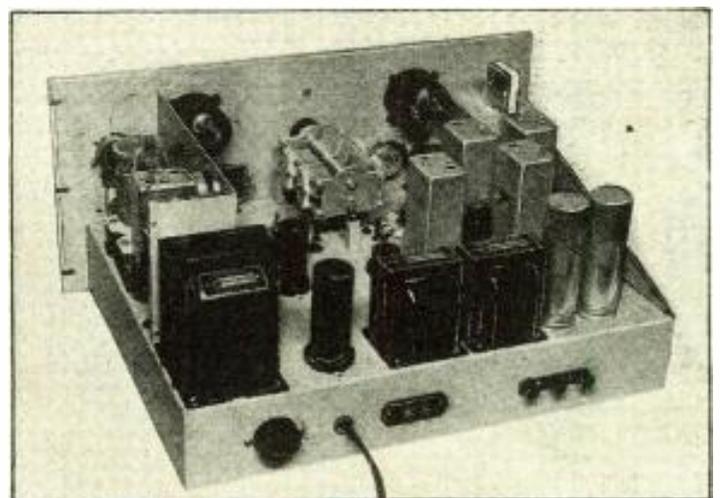


Diagram for Advanced H.F. Receiver

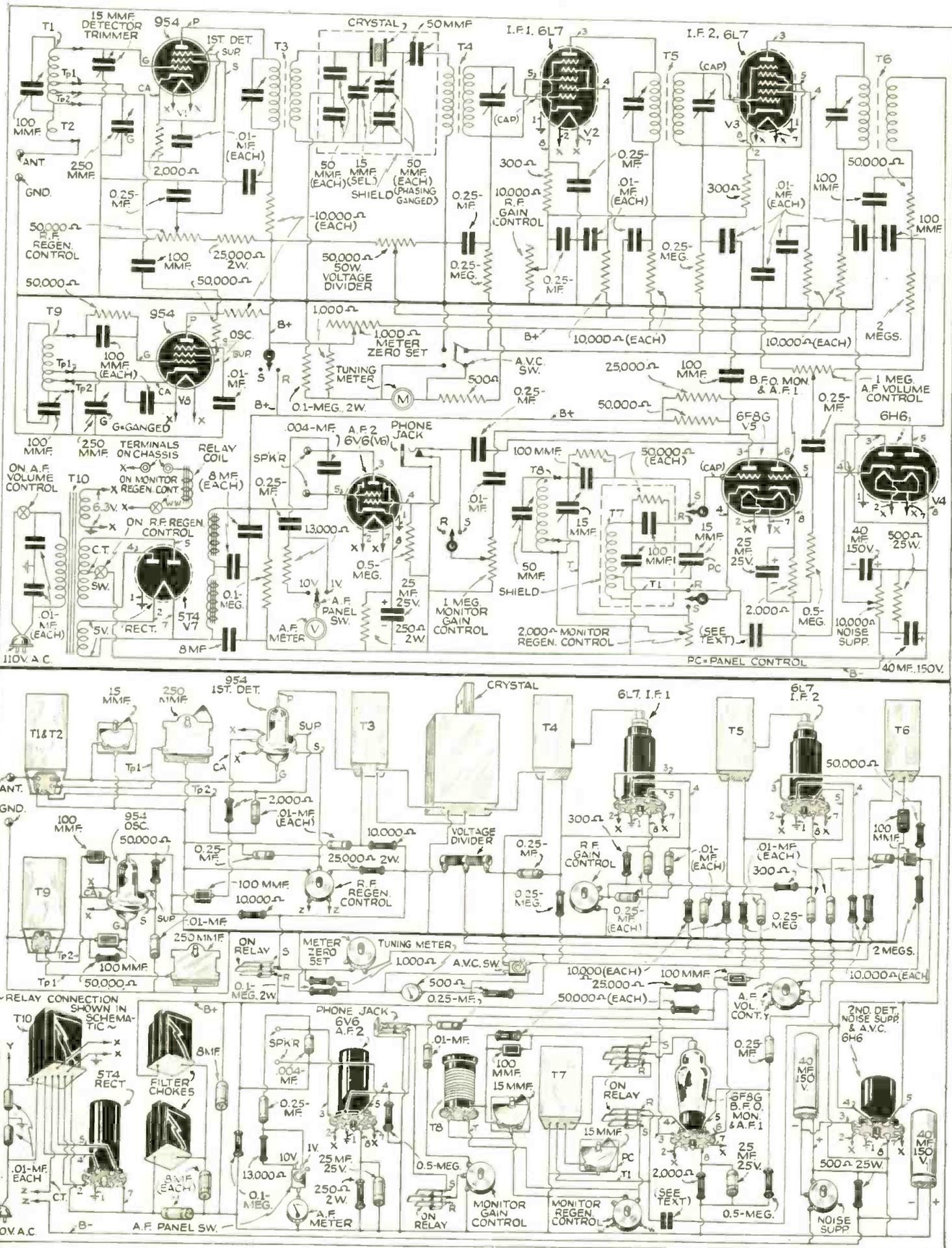

Both schematic and picture diagrams are given above for the construction of the Communications Type Receiver. The relay is not shown in the picture diagram; the relay terminals on the chassis connect with the transmitter. This set has a built-in monitor.

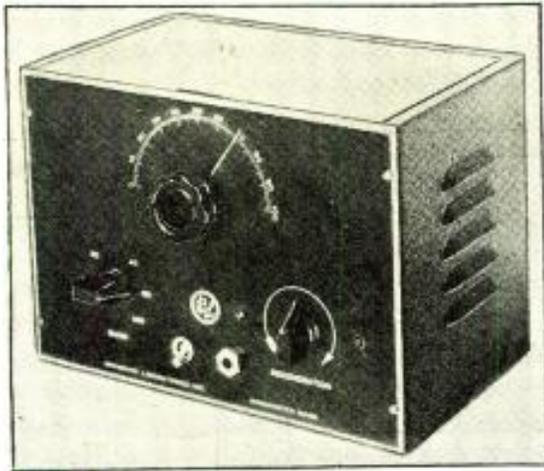

The 2-tube 5-band Amateur Receiver, complete in cabinet. The accurately calibrated tuning unit is factory-built.

An Efficient 5-Band Amateur Receiver

A dandy 2-tube receiver which operates from batteries or A.C. power. Band-spread; tunes 10, 20, 40, 80 and 160 meters.

F. J. Gaffney and E. P. Tilton, W1HDQ

designed with two fundamental considerations in view: First, to make available an efficient 5-band hand-spread amateur receiver at a fraction of the cost usually considered necessary for amateur requirements; Second, to design


this receiver so that it was readily portable and could be readily used in emergency cases.

More and more, amateurs are organizing and building their equipment (Continued on page 371)

● IN these days of high-powered communication receivers, the progressive amateur is apt to cast a disdainful glance at a receiver as simple as an autodyne detector and one stage of audio. The results obtained with the inexpensive receiver to be described will convince even the most skeptical that a tremendous amount of pleasure can be gained from the operation of a truly quiet receiver, especially after listening to the sizzle and crackle of a powerful superhet. This is especially true on the 10- and 20-meter bands where, in most cases, the autodyne receiver will compare most favorably with the 10-tuber.

The amateur set to be described was

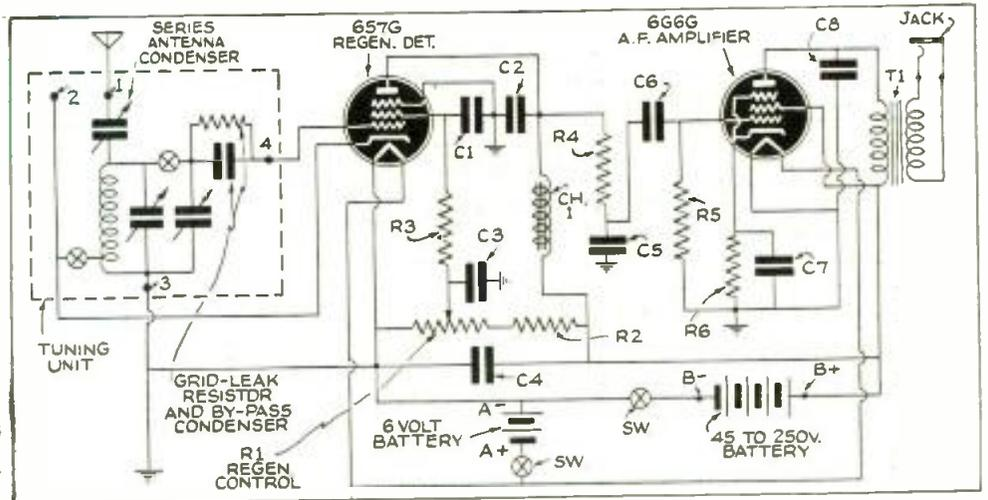Simple wiring diagram of the 5-band Receiver is shown at the right. Fig. 1.




Low Cost A.C. Transceiver

M. N. Beitman

● FIVE-METER, two-way radio communication still represents the simplest way for the beginner amateur to get started.


Diagram for constructing the Transceiver.

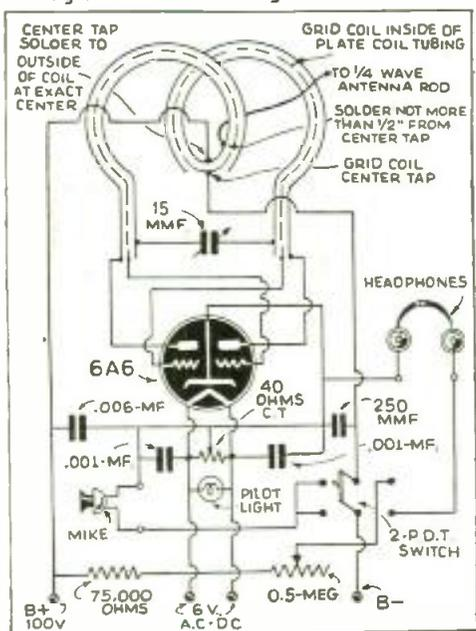

In the past, the majority of five-meter transceivers have been built for battery operation and have considerably inconvenienced the builder who had facilities for obtaining 110-volt A.C. power. The illustrated A.C. or battery operated transceiver, built in the familiar bread-board style, represents the simplest and least expensive unit that combines high efficiency and ease of operation. The unit, of course, may be constructed in other forms and may be mounted in a small portable case for specific applications.

Since the distance covered by an ultra high-frequency transmitter depends primarily on the height of the antenna above ground and very little upon the power, a simplified low-power single-tube circuit is used. The type 6A6 dual-triode operates as a push-pull oscillator for transmission and as a push-pull super-regenerative detector for reception. The double-pole, double-throw switch employed makes the necessary circuit changes from "transmit" to "receive."

Grid modulation is employed, and the

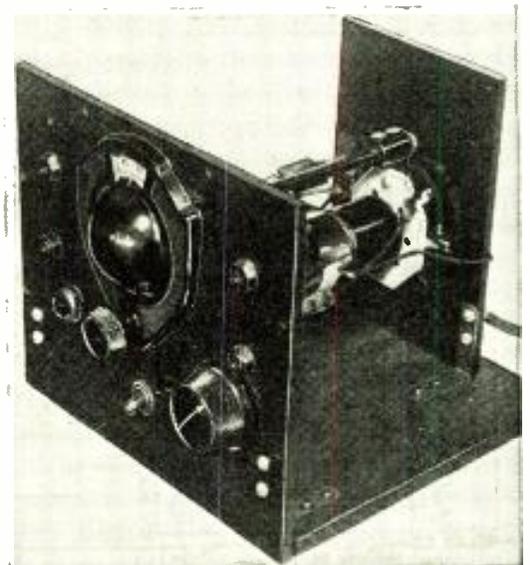

This A.C. Transceiver is available in kit form.

microphone varies the grid bias at the modulation frequency. The transmitter will not oscillate when the microphone is flat. This phenomenon may be illustrated by holding a single turn of wire attached to a pilot light near the tank coil. With the microphone in the upright position, the unit will oscillate, and the light will light brightly. On the other hand, when the microphone is lying flat, this will not take place.

The plate coil is made of two turns of (Continued on page 375)

DEALERS!

SERVICE MEN!

SOUND MEN!

AMATEURS!

SET BUILDERS!

SEE ALL THE NEW RADIO DEVELOPMENTS IN ALLIED'S 1939 CATALOG!

15,000 RADIO ITEMS AT LOWEST PRICES!

180 PAGES • SEND COUPON



EVERYTHING IN RADIO!

Write today for ALLIED's giant new 180-page Catalog for 1939! Whether you service, build, or sell radios, sell or rent sound equipment, or operate an Amateur station, you need this great book. It brings you Radio's most extensive listing of receivers, parts, kits, sound systems, test equipment, Amateur gear, books, tools, and accessories—over 15,000 items at the lowest prices in Radio!

COMPLETE STOCKS—FASTEST SERVICE LOWEST PRICES

ALLIED'S 50,000 square feet of floor space are required to carry our entire stock, which means that you get what you want when you want it. ALLIED's fast, dependable service saves you time and trouble. ALLIED's economical merchandising methods save you money. Thousands of radio men agree that it pays to make ALLIED your one dependable source of supplies, agree that, "Wherever high grade, low cost radio equipment is required, ALLIED is 1st choice!"

ALLIED RADIO

833 W. JACKSON BLVD., CHICAGO

FREE

SEND COUPON

ALLIED RADIO CORP.
Dept. 3-K-9, 833 W. Jackson Blvd., Chicago, Ill.

Send me your new 1939 Catalog—Free.


Name

Address

City State


NEW SETS!

62 new 1939 KNIGHT Radios—as low as \$7.95. 4 to 16 tubes, with latest 1939 features—3 kinds of Push-Button Tuning, new "Tiny Knight" models, new low drain battery sets with 1.4 tubes. Sets for AC, AC-DC, 6 Volt, 32 Volt, battery, and auto operation—and new phono-radios, record players, phonographs . . . all priced to bring you greater sales and profits! Send for the ALLIED Catalog . . . see why these 1939 KNIGHTS are the year's biggest values!

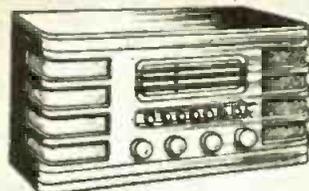

NEW KITS!

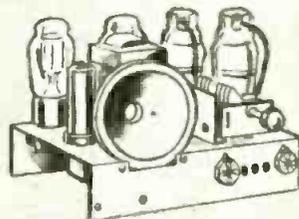Here's Radio's finest and largest Build-Your-Own selection! Many new exclusive ALLIED kits: Beginners' 1, 2, and 3 Tubers; 6 Tube Auto Set; Photo Cell Kit; Electric Fence Controls; 4 Tube Portable; low-cost transmitters—and diagrams and projects for building 100 others! We can supply matched kits for any circuit described in any construction article—write for Free Parts Lists!




NEW P. A. SYSTEMS!

You'll find a complete range of revolutionary new KNIGHT Public Address Systems—both standard and deluxe—from 8 to 65 watts. New Portable System, 30 Watt Mobile System, new Booster Power Stage, Electric Guitar Amplifier, etc. Also, the most complete line of recording equipment in any radio catalog: recorders, record players, record changers, microphones, amplifiers, discs and accessories.




NEW HAM GEAR!

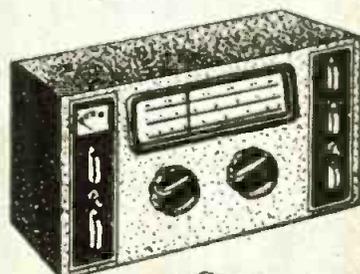Here's a giant new Ham section—an "Amateur Catalog" in itself! Shows new Hallicrafters Ship-to-Shore, National, Hammariund, Utah, and G.T.C. transmitters as low as \$15.95; new receivers: National NC-510 and NC-44, Hallicrafters "Dual Diversity" and "Marine", Sargent "Streamliner", Howard 450, etc.




NEW TESTERS!

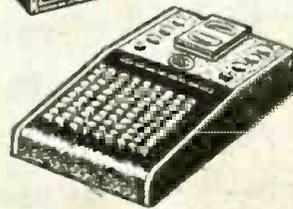A new, bigger Service Section, with Radio's most complete Test Equipment listing! All leading lines; new Push-Button type equipment, new Stark Rural Meter, new Rider's Chanalyst-Tube Checkers, Set Testers, Analyzers, Oscillographs, Signal Generators, Meters, etc.—and over 14,000 parts. Every servicing need at your finger tips—and all priced to save you money!



OVER 14,000 PARTS!

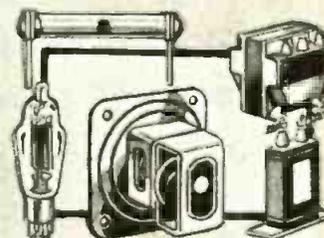ALLIED's new catalog shows more than 14,000 exact duplicate and replacement parts for repairing practically any radio. All leading lines are listed, including the famous KNIGHT brand of parts—they cost less, work better, and earn more! Also books, tools, accessories, etc.—everything in radio at lowest prices. The ALLIED Catalog is THE Buying Guide for radio men everywhere!





5-Meter Super-Receiver Uses

Herman

This 5-meter receiver will prove interesting to short wave Fans and Hams; it will pick up the television sound channel. It is a complete set with built-in power-supply and loud speaker.

It is easy to tune in stations on this 5-meter receiver, and the high quality of the voice is surprising.

● RECENT activity on five meters has taken a tremendous spurt upward. The reason for this has been twofold:—unusual conditions have enabled amateurs to maintain two-way communication over several hundred miles with ease, and in a few cases distances of 1500 miles have been covered. Naturally enough, such dx conditions have attracted many hams from the lower frequencies. A second incentive for 56 megacycle operation has been the operation of the NBC television station in New York City and the station in Los Angeles. Considering the complexities of the equipment necessary for adequate reception, a larger

number of amateurs than one would expect, have gone in for this latest phase of short-wave communication.

Before we go any further, it might be well to state that the five-meter receiver to be described is definitely *not* suitable for intercepting the television images. It is, however, a thoroughly practical and economical receiver for intercepting the sound accompanying the images.


The receiver, of the *super-regenerative* type, has nothing radically new in principle, but it does contain a number of novel features to recommend it to the ultra-high frequency enthusiast. It is completely self-contained except for its antenna, having a built-in power supply and a panel mounted

speaker actuated by an audio amplifier delivering approximately 2.75 watts. The built-in power supply operates on either alternating or direct current. On alternating current the 25Z6 rectifier acts as a voltage-doubler delivering 200 volts. When used on direct current, it is necessary to throw a toggle switch which disconnects the rectifier tube from the circuit. With the lower voltage available on d.c. there is little loss in sensitivity; the main difference in performance is in the output volume.

4 Tubes Used

The receiver uses a total of four octal base tubes, a metal 6K7 as a tuned R.F. amplifier, a 6C8G double triode tube as a combination self-quenched detector and

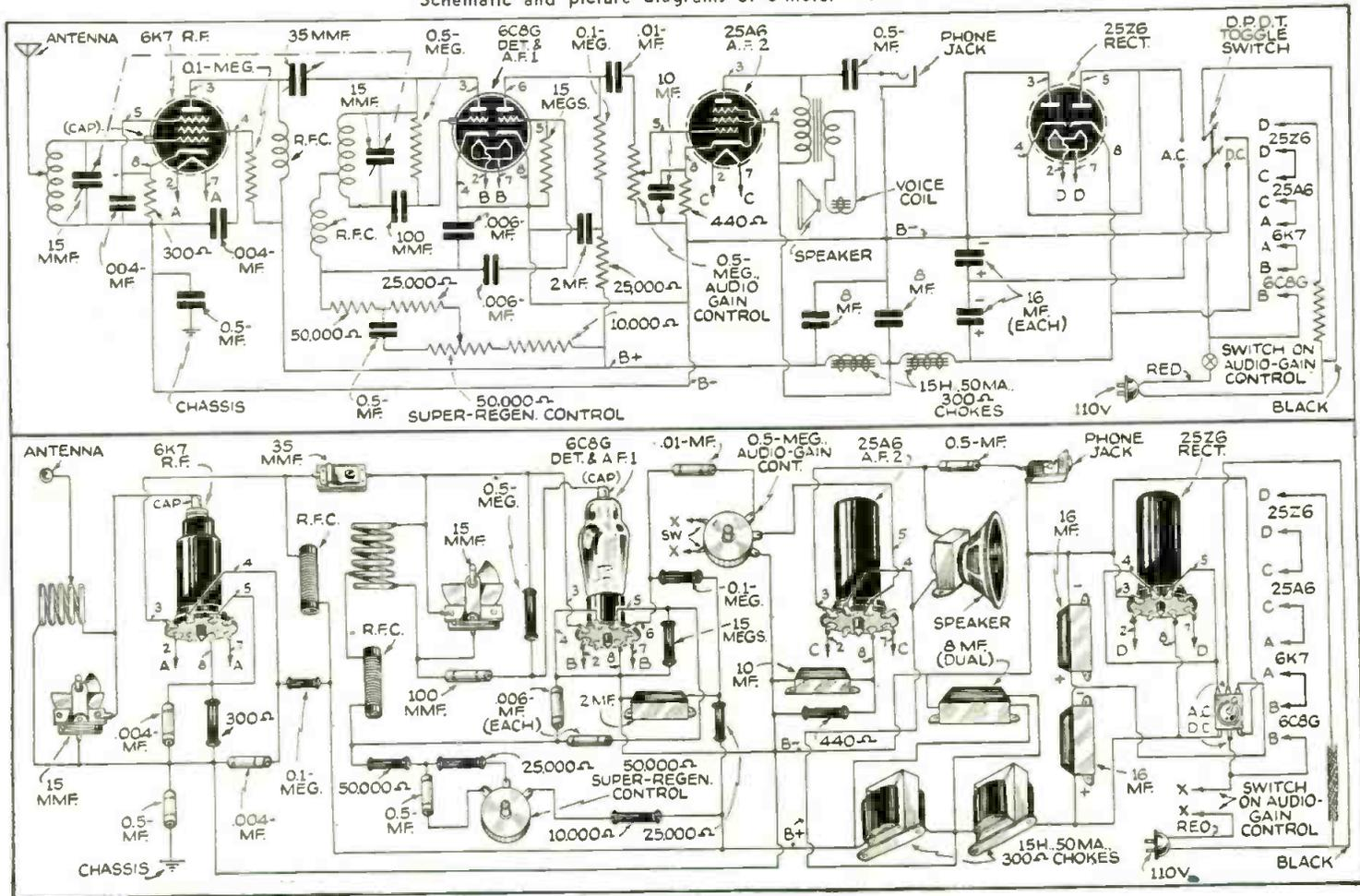Schematic and picture diagrams of 5-meter receiver.




Regenerative 4 Tubes

Yellin, W2AJL

audio amplifier feeding into a 25A6 power amplifier. A 25Z6 acts as a voltage doubler when the receiver is operated on A.C.

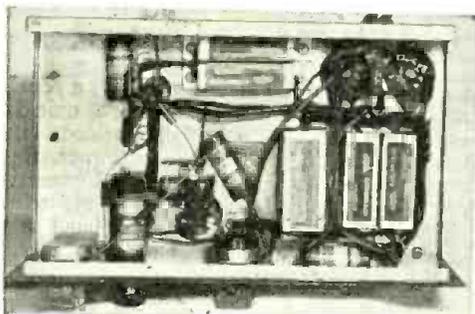The receiver was built around a 7 by 12 inch panel fastened to a 6½ by 11 inch chassis. The two potentiometers and the phone jack serve to hold the panel to the chassis quite firmly. A standard Bud 5½ by 7 inch interstage shield provided the shielding between the detector and R.F. amplifier. Before using it, the shield is



Note the neat appearance of the bottom of the receiver, as constructed by the author. The cost of building this job is nominal.

trimmed down to 5½ by 4¾ inches and drilled according to the dimensions shown in figure 2c. This shield serves as the mounting for the detector tuning condenser and also to support the detector tube socket holder. The socket holder, cut bent and drilled to the size shown in figure 2d, is made from the unused portion of the original shield. Figure 2a shows the placement and dimensions of all the holes on the chassis. Likewise figure 2b gives all the panel drilling dimensions, including the

The November issue of
RADIO & TELEVISION

will be an

**"Advanced Radio
Amateur Number"**

It will contain valuable articles for the beginner as well as the advanced HAM.

speaker opening. Some difficulty may arise in drilling the speaker opening. If a fly cutter and a drill press are available, the operation will be quite painless.

R.F. Isolating Stage Essential

Super-regenerative detectors have strong radiating properties, being much more prone to cause interference with neighbor-


(Continued on page 366)

**SAVE MONEY
WITH THIS
BRAND NEW
FREE
RADIO CATALOG!**



**188 PAGES
OF SUPER
VALUES**

**1939
EDITION**

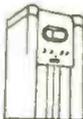	NEW 1939 LAFAYETTE RECEIVERS		PUBLIC ADDRESS EQUIPMENT
	50,000 PARTS AND TUBES		AMATEUR APPARATUS
	TELEVISION KITS		ELECTRICAL APPLIANCES
			CAMERAS

**SAVE ON EVERYTHING
YOU BUY IN RADIO**

Cover to cover, this book is the most valuable guide you ever saw in radio shopping — and saving. It's brand new and complete right down to the last RF Choke. If you're a radio servicer, you'll find extra profits in this big "silent partner." Over 50,000 profit-packed items listed! If you're a "ham" you'll want this FREE catalog because it has all the latest "wrinkles" in amateur reception. If you're a sound engineer, you'll be more than a little interested in Lafayette P.A. for 1939 — as modern as tomorrow! And if you're just John Q. Jones, American citizen, here's your chance in a lifetime to get that auto radio, that new Console, that camera you've wanted and thought you couldn't afford. Send for this eye-opening FREE catalog now! You'll thank us from this day on.

**VALU-BILL says —
I wouldn't lose any
time clipping it!**

WHOLESALE RADIO SERVICE CO. INC.

NEW YORK, N.Y. • CHICAGO, ILL. • ATLANTA, GA.
100 SIXTH AVENUE 901 W. JACKSON BLVD. 265 PEACHTREE STREET
BOSTON, MASS. • BRONX, N.Y. • NEWARK, N.J. • JAMAICA, L.I.

WHOLESALE RADIO SERVICE CO., INC.

100 Sixth Avenue

New York, N. Y.


Rush FREE 1939 Catalog No. 73-4K8

NAME _____

ADDRESS _____

CITY _____ STATE _____

PASTE COUPON ON PENNY POSTCARD

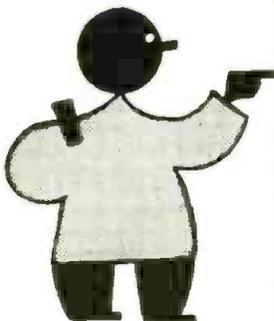

COMDR. R. H. G. MATTHEWS



Commander Matthews, radio amateur since 1909, has seen the rise of amateur radio to its present great magnitude. He has been active in the affairs of the American Radio Relay League, and through his broad experience in commercial as well as amateur radio, he speaks with authority.

● I HAVE had the rare opportunity of observing the development and growth of amateur radio since its inception. Having had my first amateur station in 1909, I have always been proud of the way the American amateur has maintained his position and privileges in contrast to the treatment received by amateurs of the other nations of the world. Looking back over this period, it is obvious that the amateur has never lost any frequencies or other privileges, with one exception, the importance of which time has minimized. I can well recall how sad I felt about the

Famous Radio Experts Salute the Amateur

(Continued from page 327)

prospects of amateur radio when the privilege of using 425 meters in connection with my special amateur license for station 9ZN was terminated, and we were told that amateur operation must take place thenceforth below 200 meters. That single loss, which no one certainly decries today, is, to my knowledge, the only curtailment of privilege which the American amateur has suffered.

I would like to pay tribute to the man whose imagination and breadth of vision made amateur radio possible, and laid the foundation for our present tremendous amateur operations. It was my privilege to have been associated, as Vice President of the *American Radio Relay League*, with its founder and first President, the late Hiram Percy Maxim. No publication commemorating the growth of amateur radio can do justice to its subject without paying tribute to this truly great man.

It has again been my privilege in recent years to serve the amateur as Central Division Director of the League. The problems confronting amateur radio now are different from those of its early days, but surely no greater or more dangerous. Our greatest danger is the infringement on amateur bands by the propaganda stations of certain European nations, whose respect for treaties is not too marked. Our government sustained the rights of the American amateur at the recent Cairo conference in a manner which has earned the gratitude of all amateurs acquainted with the proceedings. It is necessary for this government of ours to know that there is a solid phalanx of amateur radio standing behind it, and that American amateurs are anxious to lend their entire support to self-regulation and cooperation in every respect with American regulatory bodies.

With this type of close cooperation between the amateurs and the government, there is no reason why American amateur radio cannot continue its growth at the same rate it has maintained since its earliest days of thirty years ago.

Continuations of Radio Leaders' Opinions

RALPH R. BEAL

(Continued from page 326)

ready at all times to act for the people during public peril or emergency. His performance during the great floods in the Ohio Valley and in California will always be a testimonial to this fact. And he serves as a large-scale laboratory that has been of inestimable value to the radio industry. It is not too much to say that, without the amateur's work of testing new devices and equipment and his gathering of much important data, radio would not have so quickly reached its present high technical standards.

We in the radio industry recognize and appreciate the amateur's contributions to the development of radio. Today, we are facing an ever-widening horizon of discoveries and applications in the radio spectrum. We are penetrating the enchanting domain of ultra-short waves, out of which is coming television and facsimile; and we are examining the equally fascinating field of "micro-waves," which seems to hold infinite possibilities. Here are great opportunities for the amateur, and there is every reason to expect that his contributions in the future will be just as important as those in the past.

DR. LEE DE FOREST, Ph.D., Sc.D.

(Continued from page 326)

the lowly amateur with his vacuum tube oscillator and 5 or 10 watts, was consistently communicating over thousands of miles on the discarded waves below 200. By 1925 American amateurs, operating on wavelengths as short as 20 meters, were in daily communication with all parts of the world.

In 1929 I wrote to Hiram Percy Maxim: "What the technique of modern short-wave radio owes to our amateur, the world is never told, or is loath to admit. Discoveries which the paid commercial engineer would never dare attempt to make, simple and compact constructions which only poverty, necessity, and an untutored common-sense could ever evolve, have time and time again emanated from the 'ham's' work-bench, to confute and confound the professional into speedy confiscation. All these things, priceless in themselves, we owe to the amateur."

"But more than these material gifts we owe to him the invaluable spirit of discovery, of wide-awake experimentation not shackled by the book knowledge and predetermined notions of the engineer; of youthful enthusiasm, the tireless spirit of quest—that which was chiefly responsible for radio at its inception, and for its matchless rapidity of growth. This spirit alone is priceless.

"And little does the amateur ask in recompense for all this. Merely to be left alone in a now cramped cranny in the wide fields of higher frequencies which he discovered and gave to mankind."

But since this was written commercial, military, and aviation demands have encroached still further, until today we have a total in wave bands of only 38,854 meters available for more than fifty thousand amateurs! The resulting jam seems sufficient to take most of the old-time zest out of that Ace of Indoor Sports, ham "rag-chewing." But a vast amount of this present activity is, I believe, utterly unprofitable, at least for those hams who are gifted for invention and discovery.

To all such my earnest advice is to begin anew to investigate, this time in the quasi-optical frequency range which is left to you. Tubes are now available for 100 to 300 megacycle work. The remaining essential apparatus is cheap, easily assembled. Let Club members chip in, pool their resources, map out programs for attacking the new problems. Aim your sharp beams skyward and learn where they return to Earth, rotate your arrays, study shifting and fading. Such work will be no end of fun. And soon you will be discovering new principles and modalities invaluable to aviation, taking some of the dangers from blind-flying in fog and landing. For it is in your power, now as never before, to save human lives.

O. B. HANSON

(Continued from page 326)

qualities of a novel antenna array. All of us are still "hams" by what you might call remote control.

We find it profitable to take an occasional peek over the amateur's shoulder. In the "ham shack" the new device or method undergoes a quick, thorough and decisive

test. In no other laboratory is a dark region of the radio spectrum so quickly explored, its contours determined, its limits defined. I give a single instance. Recently at my home in Westport, Connecticut, I was amazed when I tuned my television receiver to the five-meter band and heard not one, but several, amateur stations in the Middle West.

Now, it has been understood generally that the range of the five-meter band was practically limited to the optical horizon. In our own laboratories we have speculated on the various qualities of ultra high frequencies. To try out our varied theories, however, we would have to scatter hundreds of men with appropriate equipment over large areas of the country, gather data under all sorts of conditions and then collate the mass. In commercial radio that, of course, is impossible.

But the blessed "ham" is always and everywhere on the air, gathering the stuff of radio progress. It matters little whether a new field seems to offer commercial possibilities; the "ham's" interest lies in doing the apparently impossible. Right now radio's technical men are deep in the problems of television, peering into a darkness that obscures many of the basic facts we must have before we send pictures through the air into the American home. I feel certain that before long the amateur will emerge from his shack with some of the answers.

C. W. HORN

(Continued from page 327)


I operated a station before there were licenses, and then obtained one of the very first licenses. My call letters in those days were "NH" and my station was located at Far Rockaway. My chief claims to amateur radio distinction are the interference that I caused the Navy station at Fire Island, and the fact that I heard the CQD sent out by Jack Binns when the *S.S. Republic* was rammed by the *S.S. Florida*.

The rapid growth of radio broadcasting can be credited to the fact that there were thousands of radio amateurs when broadcasting first began in 1920. These men were naturally the first to build receivers
(Continued on page 373)

IMITATED • COPIED • BUT NEVER DUPLICATED

CD
Capacitors
SINCE 1910

THE STANDARD OF QUALITY

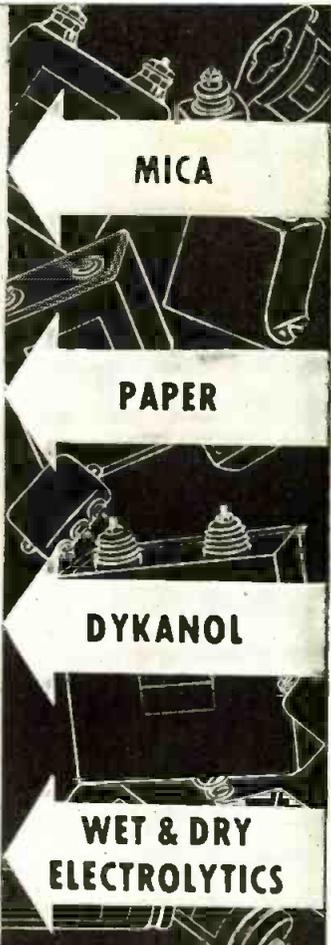

CORNELL-DUBILIER ELECTRIC CORPORATION
 1027 HAMILTON BLVD. SO. PLAINFIELD, N. J.

20 Meter Rotary Beam Works Wonders at W2AZ

New Type of Construction and Elements Produces Small Beam Which Now Does Work of Three Large Fixed Beams. Ideal for Congested Area.

An Interview with FRANK CARTER, W2AZ
 By H. WINFIELD SECOR


● WATCHING, as we do, for outstanding performances among the amateurs of the country, our attention was attracted by a report, in a recent number of QST, which indicated that some exceptional work was being done by Frank Carter, W2AZ, of East Rockaway, L. I. He was reported to have worked 36 zones, on twenty meters. The total number of zones is 40, so we figured that he was doing so well that a visit to his station would be of interest. It was, and how! We found that he had worked 75 different countries on twenty meter phone.

An outstanding feature, and one of great interest to every amateur who uses either *ten* or *twenty* meters—was the rotary beam used at W2AZ; it can be used on both frequencies, by the simple expedient of altering the connections from the transmission line to the matching stub.

Mr. Carter is the organizer and president of the very active organization which is doing so much to cut down all kinds of man-made interference, the *National Association for the Prevention of Radio Interference*. Amateur radio is his hobby, but he also obtains his livelihood from radio; he is the manager of the Service Department of the Ludwig Baumann Company, and it is his job to keep the owners of nearly 100,000 radios, purchased on the installment plan, happy.

The transmitter at W2AZ can be run with an input up to a full kilowatt, though it seldom is run above 800 watts. There are two


(Continued on page 362)

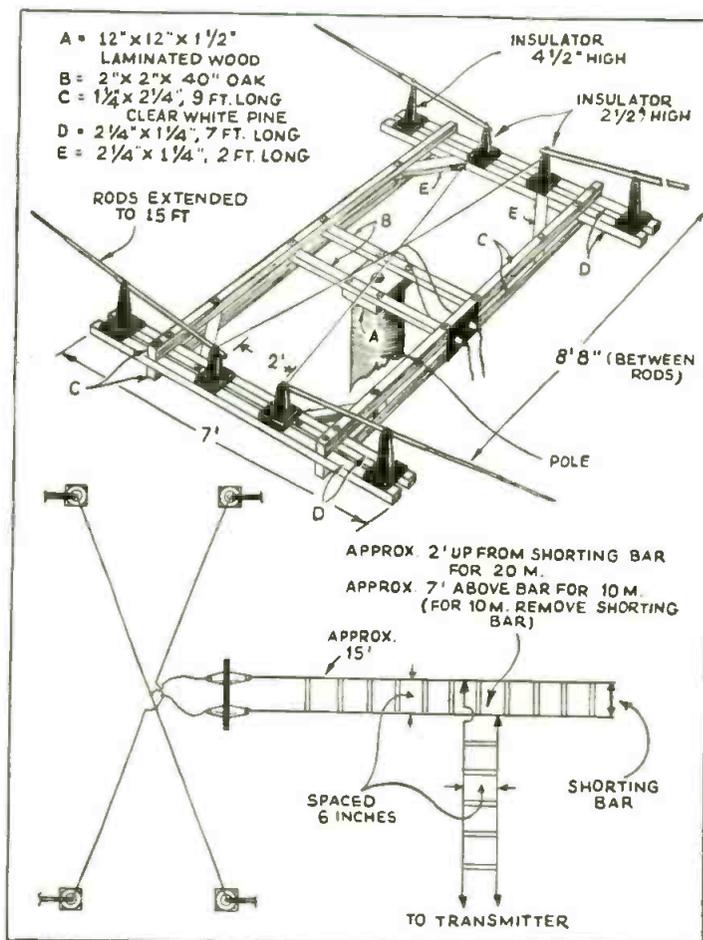

Construction of the rotary beam antenna at W2AZ.

Modulator for the 35 Watt Transmitter

HARRY D. HOOTON,
W8KPX

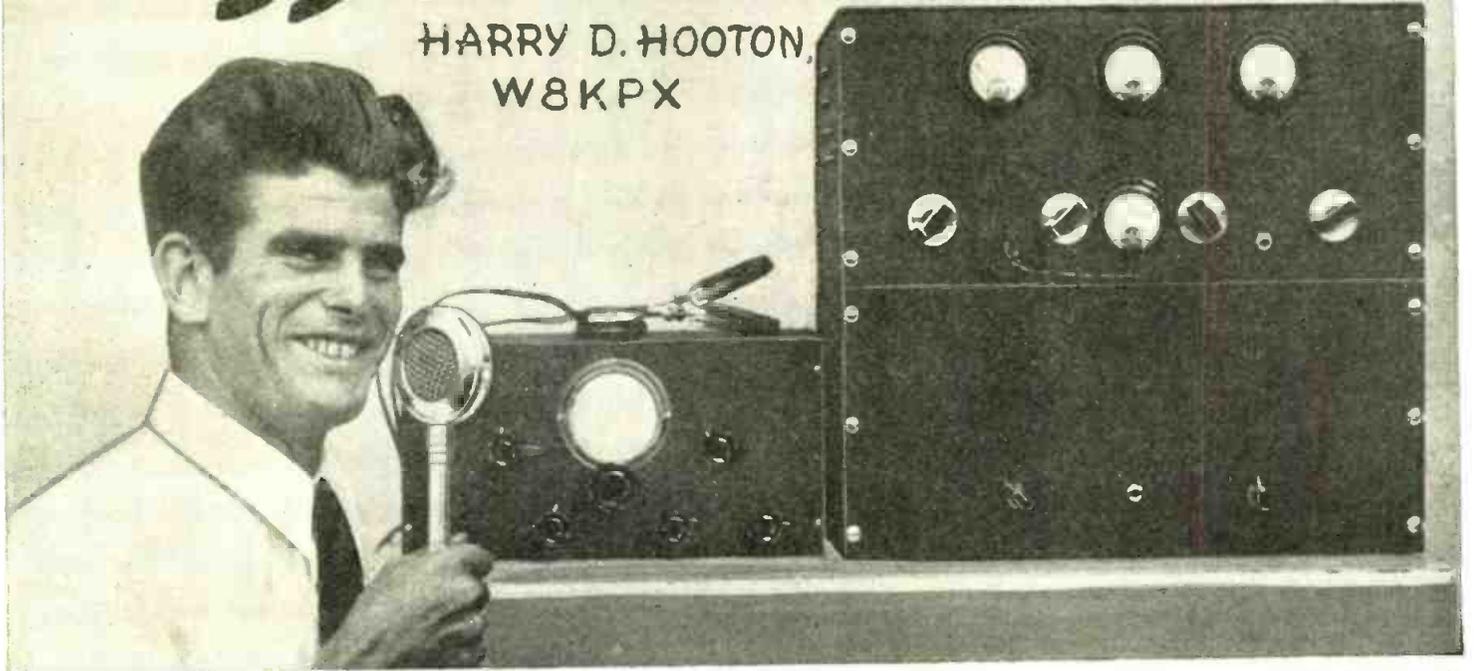


This picture shows the 35-watt transmitter at the top of the rack, while just below it appears the modulator. Cabinet seen at left of picture is the station receiver.

● RECENTLY we described the radio frequency portion of the 35-watt transmitter-exciter. The remaining standard chassis and panel section which will be described in this article, contains the power supply and the 15-watt audio unit used for plate and screen modulating the RK-39 final. All of the equipment, R.F. and A.F., has been installed in a standard, $17\frac{1}{2} \times 13 \times 20$ inch, crackle finished steel cabinet. This makes a snappy little table model rig—an ideal phone and C.W. transmitter for the 14 and 28 megacycle bands where only a very little power is required.

The modulator, as Fig. 1 "a" shows, consists of a double-button carbon microphone, transformer coupled to a 6F5G which is in turn resistance-capacity coupled to a 6F8G, with the two triode sections in parallel, driving a pair of 6L6Gs in push-pull class "A" audio. The output of the modulator is about 15 watts which is more than sufficient to 100% modulate the plate and screen of the RK-39 when running 35 to 40 watts input. The power unit shown at "b" is practically the same as that described in July issue, using a 5U4G as rectifier. The swinging choke is not absolutely necessary in a class "A" modulator circuit, but it does give better regulation under the varying load of C.W. work and is therefore very desirable. The two pairs of filter condensers are connected in series in order to eliminate any possibility of their breaking down under the normal load. The purpose of the 0.5 megohm resistors across the individual condensers is to equalize the voltage so that each condenser in the string

In the July issue, Mr. Hooton described a very interesting 35-watt transmitter for the "ham" beginner. The present article deals with the construction of a suitable phone modulator for that transmitter. The construction cost is very nominal.

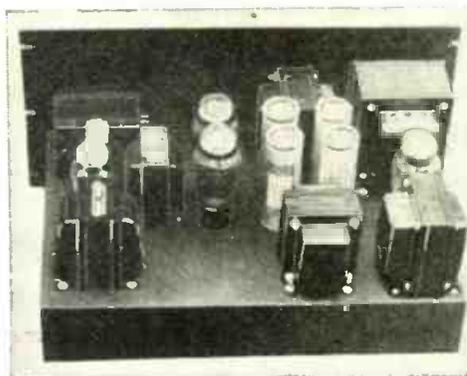will take a proportionate share; if the resistors are not used trouble may be encountered by having one condenser "blow out" repeatedly because of unequal voltage distribution across the electrolytics. The



Rear view of the modulator.

use of dry electrolytic condensers is not recommended; use wet, heavy-duty filter units with a working voltage rating of at least 550 or 600 volts. Two of the condensers must have their metal cans insulated from the chassis.

Placing the Parts

The construction of the modulator-power unit is quite simple and straightforward and no difficulty whatever should be encountered if the proper precautions are observed. The position of the various transformers, chokes, etc., is extremely important in any small, compact audio system if the A.C. hum level is to be kept down to the minimum. In the present unit each transformer and choke has been placed at right-angles with respect to its neighbor and if the specified components are used, the layout as shown in the photographs will be correct. If the constructor already has some parts of a different manufacture on hand, the following method of orientation may be used: Mount the high-voltage and filament transformers as shown and connect their primary windings to the 110 volt A.C. line. Be careful not to come in contact with the secondary terminals of the high-voltage transformer; the 800 volts will give a painful shock and is plenty high enough to be fatal in many instances. Connect a pair of headphones to the terminals of each filter choke and transformer in turn and rotate it about on the chassis until the position is found which gives the minimum hum in the phones. The use of cheap, "bargain sheet" or unshielded audio and

filter components should be avoided at all costs as these are almost certain to cause trouble in an installation of this kind. It is necessary to shield all of the leads from the microphone jack, the microphone transformer and the gain control, with copper braid suitably grounded at several points to the chassis, in order to eliminate any possibility of audio feedback or extraneous noise getting into the modulator circuit.

Tuning Up the Transmitter

The actual *tune-up* procedure of the phone transmitter is not at all complicated or difficult. Adjust the R.F. portion as outlined in July issue article, making sure that the RK-39 is receiving plenty of excitation (5 ma. grid current) but do not connect the antenna. Remove the microphone plug from its jack and turn on the modulator voltages. The 0-200 milliammeter is now plugged into the plate circuit of the 6L6G modulator tubes and the 200 ohm cathode resistor is adjusted until the plate current is about 110 to 120 milliamperes. Connect the antenna to its feed-through insulators and adjust the coupling until the RK-39 is drawing 80 milliamperes (400 volts divided by 80 milliamperes gives a 5,000 ohm load which matches the tap on the modulation transformer). Do not attempt to modulate the transmitter or operate the modulator without the proper load on the secondary of the modulation transformer; if no secondary load is presented, then the excess energy generated in the primary may cause it to either burn out or the insulation to break down. Turn up the gain

control while talking or whistling into the microphone until the RK-39 plate milliammeter needle moves slightly with the modulation. Adjust the gain to just below the point where the needle begins to move; this will give approximately 100% modulation.

If the use of a crystal or velocity type microphone is desired, it will be necessary to add another stage of pre-amplification, using a high-gain type of tube such as the 6S7G or 6J7, ahead of the 6J5G. It is also better to replace the 6J5G with either a 6C5 or a 6C5G. Because of the extremely high gain developed in such a circuit, all input and grid leads will have to be shielded carefully and a de-coupling filter must be used in the 6S7G or 6J7 plate lead. Unless the constructor has had some experience with high-gain audio equipment, it is best to stick to the double-button carbon microphone arrangement.


This is the concluding article in this low-power transmitter series. If the instructions have been carefully followed, no difficulty whatever should be experienced. If any additional advice or information is required, however, the author will be glad to correspond with readers who enclose a stamped, self-addressed envelope with their letter. Address all letters in care of RADIO & TELEVISION.

List of Parts

I.R.C. (Resistors)


- One volume (gain) control, 0.5 megohm
- One volume (tone) control, 1 megohm
- One metallized resistor, insulated type, 50,000 ohms, 1 watt

(Continued on page 369)

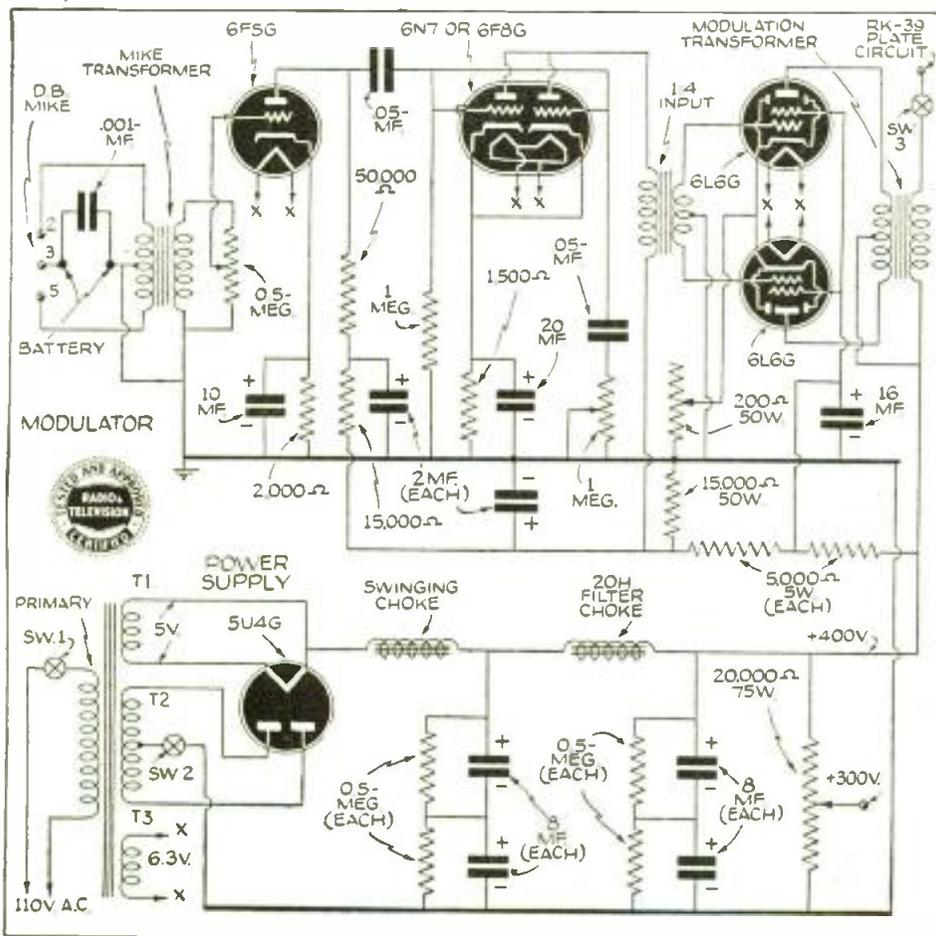

The hook-up of the modulator is shown above.

PROTECTION

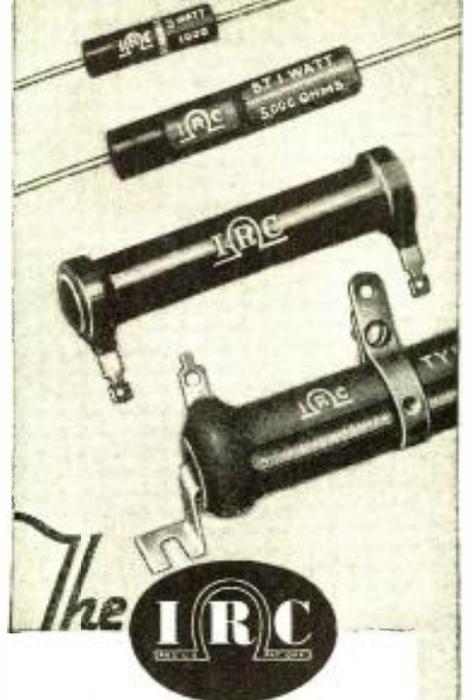

Secret of

TROUBLE-FREE RESISTORS

It is a matter of record that nine out of ten resistor breakdowns are caused solely by failure of the protective covering, either in its job of keeping moisture from the element, or in dissipating heat properly.

... It is also a matter of record that the outstanding popularity of IRC Resistors results in no small part from their perfection in this respect. Hand in hand with engineering improvements inside of the resistors themselves, IRC has pioneered and perfected BOTH Molded phenolic insulation for IRC BT Metallized Resistors and other types, as well as the famous Cement Coating for heavy duty power wire wounds.


By whatever test you choose to make—even boiling hot and freezing cold salt water immersion—you'll find these IRC protective coatings supreme.

"They Stay Put"

INTERNATIONAL RESISTANCE COMPANY

401 N. Broad St., Philadelphia, Pa.
In Canada, 187 Duchess St., Toronto, Ont.

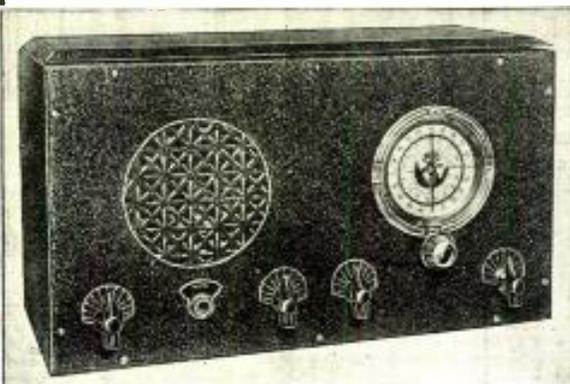OUR NEW SHORT WAVE LISTENER MODEL THE DOERLE MODEL D39



THE OUTSTANDING VALUE FOR 1939

Model D39 designed to have all the desirable features of our larger models but at a price within reach of all.

Uses a 6k7g tube as screen grid tuned R.F. amplifier, a 6j7g tube as tuned electron coupled screen grid regenerative detector, a 76g tube as a driver audio which is fed into the popular and efficient 2516g beam power audio output tube which delivers over two watts of undistorted audio power to the dynamic speaker.

A 25z6g tube is used as the rectifier and is fully capable of supplying the power requirements of the set. A type k92a tube is used as the ballast to drop the filament supply to the proper voltage.

Separate controls for volume, tone, regeneration and R.F. gain are used.

A headphone jack is incorporated to permit the use of phones when desired which automatically cuts off the speaker when phones are plugged in.

A carefully designed circuit is used so as to give maximum efficiency and output. The built-in power supply is well filtered to eliminate hum. Filter networks are incorporated in the audio amplifiers and a tuneable hum filter removes all traces of this condition common in many short wave sets. Operates from regular 110 volt house current. Covers from 9 to 600 meters with no skips which includes the standard broadcast band and all short wave bands except the amateur 5 meter band. Send stamp for circular D39.

Sold complete ready to use nothing else to buy with all tubes and coils 9 to 600 meters wired and tested

\$19.95

All parts needed to build and wire but less tubes, with all coils, cabinet, chassis and diagram. May be obtained in battery model or 220 volt model at same prices for portable or foreign use.

\$14.95

FLASH! SEND 10¢ FOR OUR NEW CATALOG containing CIRCUIT DIAGRAMS, and complete information on over 25 different types of short wave receivers and transmitters from \$2.50 and up. This catalog is chock full of schematic and picture diagrams, hook ups and short wave information. A book in itself. Well worth the dime, which will be refunded with your first order.

OSCAR B. KUSTERMAN 68 Barclay Street, Dept. 10
New York City

ASSURED STABILITY

WITH

BLILEY CRYSTAL UNITS

10-20-40-80-160
Meter Bands



TYPE B5—This low-drift crystal unit sets new standards for high-frequency crystals. Price 40 meters, \$4.80; 20 meters, \$7.50.


TYPE LD2—A precision low-drift crystal unit that is reliable, efficient and powerful. Price, 80 or 160 meters, \$4.80.

TYPE HF2—Simplifies the construction of 5-10 and 20-meter transmitters. Price, 10 or 20 meters, \$5.75.

TYPE BC3—A moderately priced mounted crystal with unusual activity and power output. Price 40, 80 or 160 meters, \$3.35.

BLILEY ELECTRIC CO., ERIE, PA.

SHORT WAVE CONVERTERS FOR CAR RADIOS

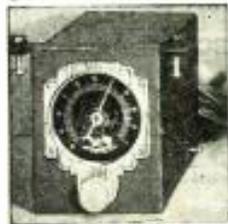

MODEL 600

Can be attached to any car radio.

MODEL 600 covers 49-31-25-20-15 and 16 meter bands. Designed for American and Foreign short wave broadcast. Distance range 5000 to 10000 miles. List Price\$24.95

MODEL 700 long wave covers 135 to 410 kc. Receives Gov. weather reports, etc. List Price\$24.95

POLICE UNITS
MODEL 100 with fixed condensers, covers 1800 to 2800 kilocycles. List Price\$11.95

Price
MODEL 800 Super Sensitive police converter with fixed condenser. Covers 1500 to 2800 kc. Two metal tubes, exceptional distance range. List Price\$15.95
MODEL 200 with variable condenser, covers 1550 to 6000 kilocycles. List Price\$17.95
MODEL 300 with variable condenser and illuminated dial. Very sensitive, has two metal tubes. Exceptional distance range. List Price\$21.95

ABC RADIO LABORATORIES 3334 N. New Jersey St., Dept. S-10, Indianapolis, Ind., U.S.A.

20 Meter Rotary Beam Works Wonders at W2AZ

(Continued from page 359)

receivers, a National HRO and a Hammarlund Super Pro. Mr. Carter is very enthusiastic about the National SW-3, which he uses for a two stage, regenerative pre-selector, as suggested on page 164 of *SHORT WAVE & TELEVISION* for July, 1938.

Mr. Carter lives in a section reasonably free from radio interference and he has a large piece of property—see sketch. And it is just this feature of his station which brought the value of his beam so forcibly to us, as we realized that very few amateurs would have space enough to duplicate his three "fixed" arrays, even if they could afford to buy the necessary telephone poles, etc. The accompanying pictures illustrate most of the major points which were brought home to us by this amateur, whose voice has been heard in nearly every corner of the globe, and who talks about his "skeds" with hams in Australia in much the same way as we talk about a phone conversation with someone a couple of blocks away. He talks with a somewhat Southern accent, which is very pleasant to hear. So picture him, sitting there, before his operating table, with you occupying the large over-stuffed chair in front of the loudspeakers, in the very large living room, which he has converted into his radio "shack." Said Mr. Carter:


"Before giving you the full details on the construction and operation of this rotary beam, we want you to know that we put it up very much against our will. We were talked into it, and it took a lot of talking. After all, we were getting out pretty well with the three fixed beams we were using and we couldn't see any excuse for going to the expense and the trouble of making

a rotary beam. You see that little SW-3 sitting there on the table? Well, that belongs to an old friend of ours, Arthur Lynch, W2DKJ. He told us that it would help us in getting some of the weak boys through. As you can see, we have very fine receivers, and we thought that the addition of the pre-selector was kind of silly. He brought it over, we hooked it up, and he hasn't been able to talk us out of it again.

"He told us about a new type of rotary beam that he had designed, which he thought was 'hot stuff,' and that he wished we would try it out, in comparison with the three fixed beams which we then had in operation. He came over one night and brought a small carton with him. The elements which now comprise our beam were in the carton. It was about four inches square and six feet long and weighed less than fourteen pounds—the elements themselves weigh less than nine pounds. We built up the framework, set the rods on the insulators and put the whole works on top of one of the lower poles which was near the house. It was very easy to tune the thing up. When we put it on the air, we got the shock of our life!

"The little rotary did everything that the three fixed beams, each of which was twice its size and twenty-five feet higher, would do. In addition, it brought signals to us, from directions not actually in a direct line with one of the fixed beams, with better strength and with less interference. Long periods of test—our beam has been up for several months—indicate that there have been only a few occasions when the signal from any of our fixed beams was any better anywhere than the signal from the little rotary. On these occasions, the increase of signal strength from our station, as reported in South Africa, for instance, has been just a slight change in the needle on the S meter of the HRO, used by the operator at the receiving station.

"A very important point, not generally considered when directional aerials are contemplated, has been very thoroughly demonstrated by our experience with these beams. As you have seen, all three of our fixed beams are quite a distance apart. Also, they are set at angles, with relation to each other, as far as the limits of our property will permit, so that parasitic excitation and reradiation from those which are not in use is cut to a minimum. However, when we pump full power into one of the fixed beams, we can measure plenty of current in the others. This indicates that it is impossible for us to get full efficiency out of any one of the three fixed beams, while the others are still in the air. Of course, we have made tests with stations in other parts of the

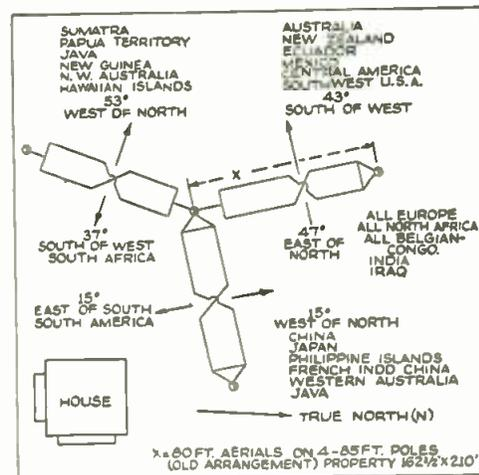

New rotary aerial does all the transmitting and receiving DX formerly accomplished by the 3 large aerials shown.

world and reception is possible in directions other than that covered by the beam which is being powered, until we lower the other beams; then transmission is limited to the desired direction. The same thing occurs when we are receiving. Therefore, we have found that better, all around results are obtained with our little rotary, both on transmitting and receiving.

"When our attention was first called to the telescopic, corrugated, copper-plated, steel tubing, used for beam elements, we would not believe that tubing could be made so light, with any degree of rigidity. We had tried many other types of solid and hollow elements, but had not been able to secure any which did not sag too much.

"That, we believe, Mr. Secor, along with your sketches, should enable any experienced amateur, who is a bit handy with carpenter tools and who knows something about beam antenna tuning, to get very

much better performance out of his present transmitter than would be possible with the ordinary type of antenna, or even with a group of rather elaborate arrays of the kind we used to think were really modern."

It will be seen that none of the mechanical measurements will have to be changed if operation on the "ten meter" band is desired. It is but necessary to open the shorting bar, at the base of the half-wave stub, and run the transmission line up to a point on the stub, where a correct impedance match is obtained, as indicated by the removal of standing waves on the transmission line. For full details regarding the adjustment of beams of this type for ten or twenty meter operation, we refer our readers to the various articles which have been written by John D. Kraus, W8JK, after whom this type of beam is sometimes called. Herewith is brief log of dx "worked" with this aerial.

DATE TIME	STATION CALLED	CALLED BY	STATION WORKED		IF QSO		RESULTED TIME OF ENDING QSO	REMARKS
			R	S	R	S		
637 P	KATEF	X	5	8	5	9	632 P	July 30 Philippine Is.
8 A	CQ	X	5	8	5	9	822 A	Aug. 7 Australia
822 A	X	VK3UM	5	6	5	9	828 A	Australia
838 A	VK4U	X	5	7	5	9	917 A	Australia
1125 A	CQ	X	5	6	5	9	1136 A	W9CTR
135 P	GM6RG	X	5	9	5	7	250 P	Scotland
758 P	CQ	X	5	9	5	9	831 P	CEIAD Chile
150 A	CQ	X	5	9	5	9	158 A	ON1NW Belgium
545 A	CQ	X	5	9	5	9	618	GM8CH Aug. 14 Scotland
618	X	G4BB	5	9	5	8	632 A	England
632	X	VK4U	5	9	5	9	718 A	Australia
726 A	VK21U	X	5	9	5	9	719 A	Australia
803 A	PK6XX	X	5	8	5	9	919 A	Dutch New Guinea
242 P	GSM1	X	5	9	5	9	330 P	England
351 P	R12L	X	5	8	5	8	128 P	Ireland

The "YL" in Amateur Radio

(Continued from page 335)

people in every section. Information obtained in this direct way is much more valuable because it is personal and true. *It is the next best thing to travel!*

Though most of the amateurs in foreign countries speak English, sometimes they prefer to write in their own language; we rather expected that, and can take care of French, German, Spanish and Italian nicely; letters in Esperanto were a puzzle at first, but YL curiosity can solve almost any difficulty.

The YL radio operator, like her brother ham, soon finds that she needs a systematic file for her correspondence, and scrap-books for her photographs of operators and their equipment. The compactness, neatness and efficient arrangement of apparatus in the photographs which I have collected speak very well for their owners. They range from the elaborate layout of OE3AH, the Archduke Anton of Hapsburg, to small portable outfits in gold-mining camps, or portable jobs for car, plane, or marine operation. One station is entirely contained in a packing-case; another uses a variety of transmitters for separate bands and looks like the control room of a broadcast station.

I Visit a Freighter

Not long ago I had the opportunity of visiting a freighter which I had worked during last winter on ten meter cw., while it was crossing the Atlantic. The operator, W6BOY, uses a low-powered transmitter and the ship's 600-meter antenna, with surprisingly good results. His pile of DX QSL's would be the envy of any shack. On his trip to Europe, he visited some of his European radio friends and had many pleasant times in stations which he had worked. His account of the ten meter DX which he was able to contact on the high seas in the night-time was very interesting, as he figured that darkness prevailed over three-quarters of the distance which he covered, and his description of the Aurora Borealis at sea was something to remem-

ber! He now has a ten meter phone transmitter for use in port, as the ship is on a coastwise run. After looking at W6BOY's log with its consistent record of fine operating, I decided that what I needed for DX was a shack on a ship in the North Atlantic and a 600-meter antenna—without the rough weather!

Other interesting contacts made at WIKTG include a phone QSO with Unalaska, one of the Aleutian Islands—in answer to a CQ! The Canal Zone, where many of the men in the service are amateur radio enthusiasts, is a source of many pleasant QSO's; the operators are real rag-chewers, have something to say and know how to say it, so that it is always fun to work a K5 or an NY.

SWL Cards Galore for YL's

The YL operator receives many more SWL cards as a rule than her brother hams. They arrive in all kinds and sizes, from the very technical report on a specially designed card to the hurried notation on a slip of paper. At this station, they are always welcome and always answered. Sometimes they give me exactly the information which I want and have been unable to get on the air because of lack of contacts with certain districts or sections. For example, we tried experiments with a twenty meter Zepp but had no QSO's with New Zealand. We discarded the antenna and later got a very fine report from a listener in Dunedin which was greatly appreciated.


The interest in amateur radio all over the world is greater than most people realize; and in no other country, as far as I know, has the amateur such opportunities to obtain the best equipment at a reasonable cost, in no other country is he so wisely controlled by the government, as in the United States.

The YL who handles traffic or even an occasional message finds the other stations on the air willing to go out of their way to help. The press contributes information accurately and without delay.

SLEEP SWEETLY



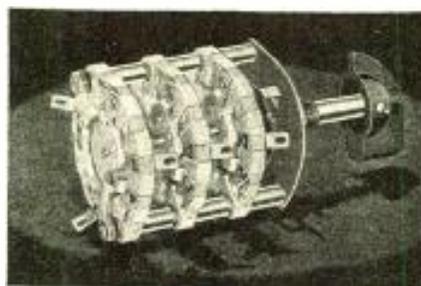Centralab comes to the rescue with its NEW ISOLANTITE SELECTOR SWITCH



When you fall asleep, dead to the world from fatigue, trying to dope out how in blazes you're going to change bands on that new rig . . . take it easy . . . CENTRALAB'S new Isolantite Selector Switch will solve your problem.

Switches for

TRANSMITTERS

- Crystal Frequency Selector from one band to another, or within the band to dodge QRM.
- Amplifying or Doubling Stages select the proper coil or tap on one coil, or correct tank coil on final stage.
- Antenna Coupling in series or parallel for matching antenna to given frequency.
- Transceivers send and receive switch.

RECEIVERS

In either preselectors or receivers wherever wave changes are required.

Send for bulletin 684, giving complete details. Dept. R

Centralab

Division of Globe Union Inc.

900 E. Keefe Avenue Milwaukee, Wis.

Your Inquiries Invited

When you need amateur equipment it is to your advantage to write to Bob Henry, W9ARA. You get personal attention; terms financed by myself so you buy with less cost and more convenience; fair trade-in value for your equipment; ten day trial of all receivers; and my cooperation in every way to see that you are 100% satisfied. No wonder Bob Henry's customers are boosters. You will be too. For the newest equipment, the latest information and technical help:

WRITE TO:
BOB HENRY,
BUTLER, MISSOURI

Compare Bob Henry's Terms with Others

Model and Receiver	Cash Price	Down Payment	12 Mo. Payments
The NEW NC-44.....	\$49.50	\$9.90	\$3.49
NC80X and NC81X ...	99.00	19.80	6.99
Improved NC101X...	129.00	25.80	9.11
The NEW NC100A.....	120.00	24.00	8.48
Latest RME-69.....	152.88	30.56	10.80
Sky Champion	49.50	9.90	3.49
Sky Challenger II	77.00	15.40	5.44
Super Skyrider	99.00	19.80	6.99


Also Super Pro, HRO, PRI5, Breting 9, Sargents, others.
Similar terms on Harvey, RCA, RME, Bassett, Temco transmitters and National, Progressive, Utah, Stancor kits.

Special Department for Export Orders

HENRY RADIO SHOP
211 North Main Street Butler, Missouri

THORNE'S RADIO COIL WINDER

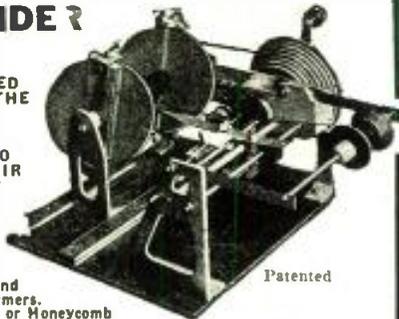DESIGNED FOR THE AMATEUR AND RADIO REPAIR SHOP



Will wind Transformers, Straight or Honeycomb coils and Ear Phone armatures. Revolution recorder. 14 Speed changes. Patented

Write for Illustrated Circular and Price.
MIAMI LABORATORIES, INC.
951 N. W. Third Street Miami, Florida

Steel Chassis Bases



Made of heavy gauge steel, BUD Chassis Bases are sturdily constructed and will last a lifetime. Send for Free catalog No. 1395W showing complete line of BUD products.

BUD

BUD RADIO, INC.
CLEVELAND, OHIO

The Phone HAM and What He Does

(Continued from page 329)

is most interesting in the summer months, when the desire for the "open road" beckons one forth from the shack, scene of home operations.

Talking on 10 Meters

Lower in frequency is ten meters, that elusive band, where power means nothing and conditions mean all, towards a successful contact or QSO, in the parlance of the ham. Ten meters is said to close up in summer, thus most of the activity takes place in the winter months, though W5HDK, whose new station on this band is illustrated, has been having some very successful summertime contacts with the Antipodes. Long distance operation is the main feature of this band, thus most hams who put in their time here can also be found talking on some other band, and 160 meters is the current second choice for "L L" as he gives his handle (Christian name, in amateur parlance).

Operating an amateur-built transmitter with an input of one kilowatt, the maximum legal power allowed, this station is an example of neatness and efficiency. Listen for him, and you will hear a true amateur talking with his fellows.

Around the World on 20 Meters

To talk of *twenty meters* is to talk of the amateur's dream of paradise on the air. Here the gang can gather and commune with the world, forgetting their cares for the time, and becoming a part of the universal society of mankind. If every country were as friendly toward the amateur as Uncle Sam, encouraging him onward, there would be less talk of war, for no one would wish to shoulder arms against his friend, even though that friend be of another nationality. These air friendships, unusual as they may seem to the outsider, are genuine, sincere good fellowships. The human voice can be a great factor in building friendship, and the personality of the man behind the microphone goes a long way to cement the bond, although the parties thereto may be separated by the seven seas.

Twenty meters offers just such an opportunity, day and night, almost any time of the year. Here is probably the height of activity for the phone man, for there is hardly an hour of the day that some distant nation is not audible on this band, together with many stations from one's own country. One moment you may talk with that elusive Filipino, about whom you have heard so much, or perhaps it will be an expedition to New Guinea, known to all the amateurs as PK6XX. As the clock runs on, stations from far and near fill the dial of the amateur's receiver, and it is his privilege and pleasure to talk with one and all. Schedules take up a good part of his operating hours, and these contacts are often as regular as the arrival and departure of an airplane. But it is not always possible to contact a distant station, and those located near at hand offer as much pleasure to the constant listener.

By no means do all of the activities of an amateur take place on the air, far from it. There are radio clubs, conventions, and hamfests, gatherings of the clan, and what gatherings these are! Here is where the great hobby shows its true side of friendship, for at long last you are afforded the opportunity of talking with and meeting in person the fellow whom you have known

for years. Memorable occasions these, and the phone men seem to be at the greater advantage, for they know and recognize the voices long before they are introduced to one another. Until you have attended a national amateur convention, such as was held in Chicago on the last Labor day, you cannot know all there is to the true amateur spirit.

"What It Takes" to Become a Ham

What does it take to become a ham? The will to learn, and the ability to be a good sport and to share with your fellows your problems and achievements. Any citizen can obtain his license and operate a station, but that does not say that he is a true ham. Nor is the desire to see one's call letters published in all the radio papers of the globe a true exemplification of the amateur spirit. Personal publicity can be far better acquired by a good public relations counsel than by operating an amateur station. Sad to relate, not all those possessing an amateur license have learned this fact, to the everlasting harm of this great hobby, especially when their eagerness to gain the spotlight assumes the proportions of an international diplomatic misunderstanding. But these unpleasanties,

Interesting articles to be found in the current issue of

Radio-Craft:

Construction Details of a 441-Line Teleceiver

New!—Anti-Noise Counterpoise Antenna System

New Circuits in Modern Radio Receivers—No. 13

Home-Built 11-Tube Set Introduces "Synchrotronic" Reproduction

How to make a Modern V-T. Voltmeter, Howard G. McEntee

This magazine is for sale on all newsstands.

though they do occur, are few and infrequent, and the loyal amateur is ever on the alert to avoid them.

Good Will Among Nations

The true ham spirit, which has bonded together this vast, cosmopolitan army of men and women, with a common interest in a scientific hobby, will go a long way towards cementing the good will among nations. The true amateur is humble, quiet, self-effacing, and desirous only of the opportunity to perfect his station and his equipment. He asks but the liberty to carry on his experiments which have benefited all mankind, the developments which have been rewarded, not with financial gain, but with that greatest of all payments, the satisfaction of completing a self-imposed problem. So, if you do happen to hear an amateur who may momentarily disturb your pleasure in listening to a broadcast, by interfering with your receiver, do not condemn him unjustly, but rather cooperate with him, for the interference may result from some experiment that will shortly bring you, his hearer, a more perfect form of entertainment, be it *sight* or *sound*, or something which we today dare not imagine possible.

Dem Was the Happy Days

(Continued from page 333)

have made radio history, including Armstrong, King, Burghard, Amy, Pacent, Dr. Hudson, Dr. Goldsmith, Cannon, Vermilye, and others, in the New York area alone. But for some reason I never seemed to get out to their receivers. Hence I found it necessary to establish a receiving station just for my own signals. A friend, George Barr, gladly consented to become partner in the ordeal, and purchased his own 2-inch spark coil, timer, phones and other paraphernalia, which we set up about two miles distant. Soon we had a nice communication system established, and dot-dashed back and forth each evening and most of Sunday.

Everything was swell for awhile. Then came an unwelcome intruder. A chap signing himself "HB" thundered in at both our stations like the proverbial ton of bricks. Indeed, HB simply swamped out everything on the local ether. We occasionally heard the Operator Pickered, who held forth at Station WA atop the old Waldorf-Astoria Hotel, coming back at HB, requesting him to stand by for awhile, so that WA might clear its traffic to DU, the station atop the Hotel DuPont in Wilmington, Del.

In time I was invited to visit HB. He turned out to be a doctor; his transmitter was a revamped X-ray outfit with rotary spark gap. This improvised transmitter was capable of packing a terrific wallop into the huge aerial on the roof.

By 1911 there were really serious attempts made to tune our signals. Instead of the plain aerial system, whereby the antenna was connected to one side of the spark gap and the ground to the other, we now made use of a closed oscillating circuit for the primary, and the antenna and ground connected to the secondary of the oscillation transformer. A small lamp bulb placed in the ground lead indicated by its dim glow whether we had the proper number of turns connected in the primary circuit.

Late in 1911 I had advanced to a quarter-kilowatt open-core, oil-bath transformer, a rotary spark gap, a large bank of condensers made of good window glass with tinfoil sheets shellacked in place, and a rotary interrupter. My call letters were JB, for no other reason than their delightful rhythm in the Morse code then used by American radio operators. How clumsy seemed the Continental code used by foreign ships in our harbors and off our coasts!

Miracle of the Ages

Perhaps the greatest thrill of those days was the occasional human voice picked out of the ether. I believe it was in 1908 when, one evening, I was startled to hear a voice standing out from the background of dots and dashes. The voice was counting numbers. Presently, it proved to be Dr. Lee de Forest, operating a radio telephone transmitter somewhere in New York City. The whole family came rushing into my room to see what had happened to me. I was shouting for the whole world to experience this miracle of the ages.

The greatest difficulty of early wireless days, at least for one living in a city apartment, was a good aerial. Our apartment house had a nice flagpole at one corner of the roof. I dared hitch a three-wire aerial on to the ropes of the flagpole and to hoist it high in the air. That evening I was thrilled by listening to many brand new call letters.

The joy was short-lived. Within a few weeks, the result of pulling the aerial wires taut, the flagpole developed a decided bend. Our building superintendent's attention was called to the fact by some not over-friendly neighbors. Whereupon he made his annual

A New Sargent Communication Super-Het!



Sargent Model 51

It is a real pleasure to announce a receiver of the calibre of Model 51. Although our receivers already enjoy a reputation for correct, careful design, we have surpassed any previous receiver in the ranked, life-time construction of Model 51. Built to last—out of the best obtainable materials—Model 51 will give stable operation, dependable service for years. In locations that are inaccessible, repair parts hard to obtain, Model 51 is the receiver for dependability.

Regenerative input, introduced in our Model 21 and outstandingly successful, is used on all bands on 51. Individual panel-operated trimmers on R.F. and detector stages insure perfect alignment at all times. 10 and 20 meter band performance is outstanding. High sensitivity, very low noise level—a pleasant superhet to listen to.

For extreme DX the regenerative input adds that extra punch that brings those very weak signals up to audibility. For maintaining a communication schedule, Model 51 has stability equalled by few receivers. A receiver you will be proud to own.

Streamliner '39

A sensational value in a communication receiver. 5-tube superhet, covers 10 meters, illuminated dial. 2 stages I.F., panel trimmer, Beat Oscillator, AVC. 4 tuning bands. Covers 9.5 to 550 meters. Uses hand switching—no plug-in coils. Net price, complete with tubes, speaker, \$33.90 power, ready to go.
Equals performance of receivers selling for many times the price.

Look At These Features

- Regenerative Input, all Bands
- High 10/20 Meter Efficiency
- 10 New Type Glass Tubes
- Equivalent Performance 13 Tubes
- Isolantite Insulation
- Shadow Tuning
- Iron Core I.F.
- Band Spread
- C.W. Pitch Control
- R.F. and Det. Panel Trimmers
- Break-in Switch
- Headphone Jack
- R.F. Input Control
- Manual Volume or AVC
- Tone Control
- Push-Pull Audio
- 8" Jensen Speaker
- A.C.-D.C. Circuit
- Full Wave A.C. Rectification
- Both Power Lines Filtered
- Lifetime Filter Condensers—no Electrolytics
- Shielded, Moisture-proof Bypasses
- Insulated, Moisture-proof Resistors

Model 51 Net Prices

Model 51-AK, 9.5 to 550 meters, 110 volts AC-DC \$157.00
Model 51-MK, 9.5 to 3750 meters, 110 volts AC-DC \$175.00
6 volt Battery Model on special order. Prices include R.C.A. tubes, speaker power, ready to go.

Sept. 15th Delivery
Orders filled in Rotation

9.5 to 20,000 Meters!

The greatest tuning range of any receiver built! Model 11-CA tunes this range. A popular, operator's type tuned R.F. regenerative receiver. Has hand spread, band switching, self-powered, built-in speaker, every important feature. \$77.00 net. Also sold for 9.5-3750 meters and 9.5-550 meters at lower prices. Built also for D.C. or battery. Write.

Write for Complete Data

E. M. SARGENT CO.

Cable Address "EMSCO"

212 9th Street Oakland, Calif.

visit to the roof, discovered the offending aerial, and promptly hauled it down.

We may have dreamed of the days when we might converse by voice; however, I for one feel that the memory of those early days still holds the greatest thrill for those who make radio their hobby.

R.C.A. INSTITUTE TELEVISION COURSES

● WITH the inauguration of television field tests, R.C.A. Institutes assigned two of its instructors to the engineering group in charge of the experimental work. These instructors have had immediate contact with development and have studied at first hand the many problems and vicissitudes with which the new art has been confronted. Concurrently other members of the school staff have been engaged in the preparation of lesson material and construction of special television demonstration equipment.

In addition, two volumes of significant papers were published in July, 1936, and October, 1937. These books, titled *Television*, Volumes I and II, are two of the most complete books available on the subject.

Feeling that the basic system of television is unlikely to undergo any immediate major change R.C.A. Institutes considers the time propitious for the inception of its *Television Courses*. These courses will begin with the fall term, convening September 6, 1938. For persons who have had no previous training in Radio Engineering, the course requires a period of two years in the day school or five years in the evening school. Special *Television Units* of six months' duration in the day school or one year in the evening school are available to applicants possessing adequate technical background.



ASTATIC

Now Ready!

MULTI-UNIT

Dual Diaphragm CRYSTAL MICROPHONE

SELF LOCKING TILTING HEAD

Brand new! For public address and night club use. Cannot be acoustically overloaded. Two models: MU-2 (\$29.50) with two dual diaphragm crystal units, and MU-4 (\$39.50) with four dual diaphragm crystal units. Black and chrome. Complete with socket and 25-ft. cable. See jobber or write for literature.

Astatic Microphone Laboratory, Inc.

Dept. J-3, Youngstown, Ohio
Licensed under Brush Development Co. Patents

—A Sure-Profit Field for Alert Radio Men!

HOME RADIO DIATHERMY

Hundreds of Radio Servicemen are now representing our Home Short wave diathermy line and acting as our agents in all parts of the country. We offer exclusive territory with absolute protection for all agents accepted by us. Our Short wave diathermy line is standard and has been definitely accepted as "fool-proof" by all who have made the most rigid tests possible on Diathermy equipment.

Our agents have averaged better than \$40.00 a week part-time. Full-time agents can easily do better. We show you how! Write for full particulars and details on making a real good income.


SCIENTIFIC DIATHERMY CORP.

200 West 34th Street, Dept. RT, New York, N. Y.

VERSATILITY PLUS!

THE ALL PURPOSE

HAM TUNER BL-5H

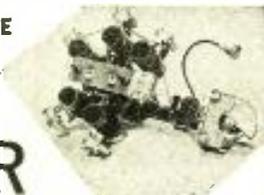

Designed to meet rigid amateur specifications. Use the 5-H whenever a quality high Q coil switching tuner is needed. Covers the 10- 20- 40- 80- and 160-meter amateur bands. Band spreads each of the five bands. A convenient band switch selects any of the bands at will.

BUILD

- A simple efficient 5-band Ham receiver.
- A 5-band preselector.
- A Ham band signal generator.
- A field strength meter.
- A frequency monitor.

Constructional details supplied with tuners.

HAVE YOU SEEN THE NEW 5P and 5G

BL EXCITER UNITS!

MAXIMUM EFFICIENCY AT MINIMUM COST
SEE YOUR PARTS DISTRIBUTOR

KITS and TUNERS
FOR THE AMATEUR AND EXPERIMENTER
BROWNING LABS., Inc. WINCHESTER, MASS

PYRO PANTAGRAPH



Size of Box: 12 1/2 x 8 1/2 inches

\$2.75

Shipping weight, 3 lbs.

THIS electrical outfit is especially designed for burning designs permanently on materials such as Leather, Wood, Cork, Bakelite, etc. Plug the Pyro-electric pencil in any 110 volt AC or DC outlet and it is ready to be used. Plug and cord furnished.

By the use of the Pantagraph included in the outfit, any design may be reproduced either in original, reduced or enlarged form.

Outfit consists of: one Pyro-electric Pencil; one Pantagraph; three hardwood plaques; one bottle of Varnish; one Brush; one tracing tip and four-page instruction sheet.

Size of box: 12 1/2 x 8 1/2 inches.

Outfit will be forwarded by Express Collect if not sufficient postage included with your order.

WELLWORTH TRADING CO.
658 W. Washington Blvd. Dept. SWT-1038 Chicago, Ill.

5-Meter Super-Regenerative Receiver

(Continued from page 357)

ing and distant receivers than even the old regenerative receivers. In order to eliminate this radiation, the detector should be isolated from the antenna by a stage of R.F. The R.F. grid coil and condenser are the same size as the detector tuning combination. Both condensers have a capacity of 15 mmfd.

Acorn Tube May Be Used for R.F.

Since the tube filaments were all connected in series, all tubes used would of necessity be of the 0.3 ampere type. Thus the choice of an R.F. tube fell quite naturally to the metal type 6K7. Use of the acorn type 954 would have resulted in much greater gain, but the cost would have been greater. However, the 954 can be used instead of the 6K7 with only minor changes. The filament of the 954 would have to be shunted with a 42 ohm resistor since it has a 0.15 ampere filament. All grounds are brought to one point for each stage and then connected together by a ground bus which is then connected to the chassis by a half microfarad paper condenser. Nothing is grounded to the chassis directly. The reason for this is to eliminate the possibility of shorting the 110 volt line with a reversed line plug or of the cabinet appearing hot on D.C. with the line plug reversed. The R.F. grid coil is mounted directly on the terminals of the 15 mmfd. tuning condenser. This condenser is insulated from the panel by a bakelite washer. It might even be desirable to mount this condenser on an angle bracket instead of directly on the panel. Provision has been made for an antenna with single wire feed. If it is desired to use a doublet type of antenna, a small coupling coil of two or three turns of number 12 bus bar can be suspended from the antenna posts on the


side of the cabinet. Coupling between the two coils should be varied for optimum results.

1 Tube Acts as Detector and 1st A.F.


The R.F. tube is coupled to a combination detector and first stage of audio. This tube is a 6C8G which has two separate triodes in one envelope. One triode section is employed as a self-quenching detector and the other half is used as an audio amplifier. The section having both its grid and plate terminals coming out at the base of the tube is used as the detector. The other section has its grid terminal at the top of the glass envelope. Having the grid and plate terminals close together makes for a minimum of wiring, there being practically no high frequency wiring at all. A material contribution to the shortness of leads was the method of mounting the 6C8G. This was mounted in a horizontal position parallel to the panel and close to the detector tuning condenser. The bracket holding the detector tube also serves to lend added rigidity to the interstage baffle shield. As stated before, this bracket is constructed from the remainder of the interstage shield.

The detector grid-leak is mounted directly on the socket between the grid and plate terminals, while the grid condenser is wired directly between the grid and the rotor of the tuning condenser. The leads in no case are more than a quarter of an inch long. Incidentally, a little experimenting with grid-leaks will amply repay the constructor. The writer uses a 15 meg-ohm leak, but the constructor should experiment with values from 10 to 20 meg-ohms.

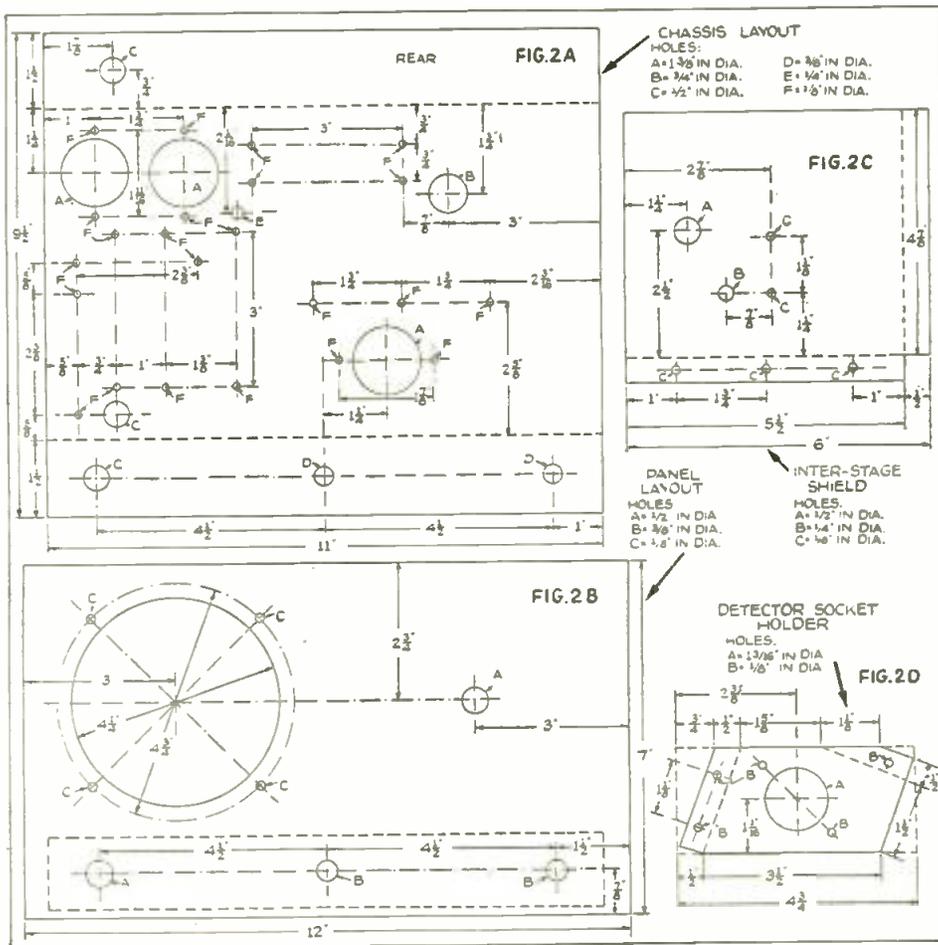Both the R.F. plate choke and the detector choke coils are of the same size and of the



Details of chassis and panel.

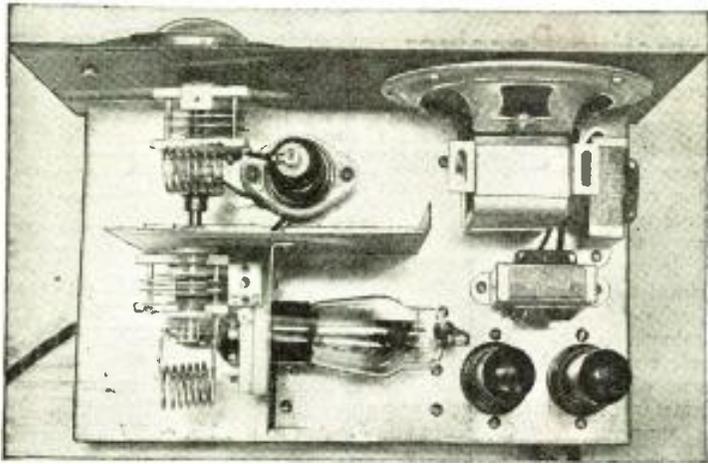

Top view of receiver.

manufactured type having an inductance of 5.7 microhenries. The .006 mf. mica condenser bypassing the detector choke coil should be connected directly to the cathode of the 6C8G. The detector choke is connected to the third turn from the plate end of the detector tuning coil. The method of mounting this choke coil is as follows: the end of the choke connecting to the detector coil is fastened to the unused prong (No. 1) of the detector socket and a half inch length of wire is run directly from the terminal to the coil. The tap can then be easily changed from one turn to another. The other end of the choke is mounted on a single terminal insulating strip mounted on the socket. As the photo shows, this results in the choke coil being at right-angles to the detector coil. As in the R.F. stage, all grounds are brought to one point and connected to the common ground bus.

Super-Regenerative Control

Super-regeneration is controlled by a 50,000 ohm potentiometer. The voltage from this control is passed through a resistance-capacity filter to prevent common coupling between the detector and the other tubes. When first tried out the receiver had a tendency to motor-boat, but the addition of the 25,000 ohm resistor in series with the regeneration control rotor effectively squelched any such tendencies.

The .006 mf. condenser which couples the detector section of the 6C8G to the audio section may seem rather small, but it is the correct value. The new and rather novel system of *automatic biasing* is used in this audio section. The cathode is grounded, thus resulting in a minimum of hum and the bias generated across the 15 megohm grid-leak. Most tubes draw grid current even with zero grid bias. The reason for this is that electrons are emitted from the cathode at so high a velocity that they reach the grid, even without any positive potential on the grid. By employing a very large value of grid-leak and grounding the cathode, the small drop across the leak due to the minute current will provide sufficient negative bias for proper operation. Using a larger coupling condenser than that shown, will result in a momentary *blocking* when tuning in a particularly loud signal.

The grid coupling condenser and leak were placed underneath the chassis at a point beneath the detector stage and a shielded wire run to the grid cap of the tube. The use of shielded wire obviated the possibility of any hum pickup. The plate resistor has a value of 100,000 ohms, while a 2 mf. condenser and a 25,000 ohm resistor comprise the R-C decoupling filter. These values were chosen so that the amplifier would work on both 100 volts as would be the case where D.C. is used and with the higher voltage available when the receiver

is operated on A.C. A .01 mf. paper condenser couples the first audio stage to the 25A6 power audio stage through a 500,000 ohm potentiometer. This audio gain control and the regeneration control are completely independent of each other. There is no interaction between them; varying the audio gain will not result in a variation of super-regeneration. The audio gain control contains the line switch for turning the receiver on and off.

Phones or Speaker May Be Used

Bias for the 25A6 is derived from a 440 ohm, 5 watt wire-wound cathode resistor, by-passed by a 10 mf. electrolytic condenser. The power stage furnishes sufficient audio power to actuate the loud speaker, even on weak signals. In addition, a *phone jack* was incorporated in the receiver. However, in actual practice the loudspeaker has been used exclusively. Although the photograph shows a standard dynamic speaker with field coil, it has since been replaced with a *permanent magnet* speaker which is strongly recommended. The field coil had been connected across the rectifier output. The additional drain of the field caused a 30 volt drop in voltage when the receiver was operated on A.C. Since it was desired to have the maximum signal possible, the change was made to the P.M. speaker with a slight rise in power output. On D.C. however, there is no voltage drop caused by the field, since it is connected across the D.C. line. For those desiring to use the field coil type of dynamic, one should be used having a field resistance of 5000 ohms.

Voltage Doubler Used with Rectifier

The power-supply consists of a 25Z6 rectifier used as a *voltage doubler* on alternating current. On D.C. the rectifier is cut out of the circuit. Briefly operation of the voltage doubler is as follows:—on one half of the A.C. cycle one of the 16 mf. condensers is charged up, and on the other half of the cycle the other 16 mf. condenser is charged. The two condensers being connected in series with respect to the load, the voltages across them become additive, resulting in an output voltage of twice the A.C. voltage. In actual practice the output voltage is slightly less than double the A.C. voltage because of the current drawn by the load. Two 15 henry choke coils and two 8 mf. electrolytic condensers comprise the filter circuit. The audio power stage receives its plate voltage at the junction of the two chokes, since it does not require such highly filtered voltage. The detector, R.F. and first audio stages make use of the full filter system.

All tube filaments are connected in series with the 200 ohm resistor cord. The tube filaments should be connected in the sequence shown on the diagram. The 6C8G filament is wired so that it is nearest to ground; then come the 6K7, 25A6 and 25Z6 in the order named. The 200 ohm series resistor is contained in the special line cord which has three leads. The thickest lead is the end of the resistor and connects to one

(Continued on following page)

**MORE
RECORD-
BREAKING
VALUES**

**NATIONAL
NC-44**



AMATEUR RADIO IS A THRILLING HOBBY—DISCOVER IT YOURSELF!

**\$49.50
COMPLETE**

Seven tubes in a superb circuit. Its performance is a sensation in the low price field. Full vision dial calibrated directly in frequency and a separate electrical bandspread dial makes accurate tuning easy. Separate controls for RF and Audio gain. 4 Bands from 550KC to 30 MC. Here is value far beyond price! See our FREE catalog.

**A VALUE BOMBHELL!
LAFAYETTE PHONO-COMBINATION**

Handsome 5 tube AC-DC table model FS-11—has all the extra-value features you expect to find only in combinations selling at three times the cost. The most in real entertainment for the least possible money!



★ 30-DAY FREE TRIAL ★
Try this or any one of the other 50 LAFAYETTE radios for 30 DAYS. If you're not satisfied we will cheerfully refund your money.

ONLY
\$19.95
Complete Ready to Operate

ALL IN THIS NEW 1939



**FREE
CATALOG**

Here you see only two of the 50,000 values in the greatest catalog in radio. Page for page, you can't beat it in quality stock and economy prices! Get your copy today.

**PIONEER IN
TELEVISION**

Flash! Featured in the new catalog—RCA licensed build-them yourself television kits! Complete with specifications and diagrams. Priced amazingly low.

FLASH!

List price P. A. Catalog available to servicemen. Write to Public Address Division for free copy.

WHOLESALE RADIO SERVICE CO. INC.
NEW YORK, N.Y. • CHICAGO, ILL. • ATLANTA, GA.
150 SIXTH AVENUE, 101 W. JACKSON BLVD., 245 PEACOCK STREET
BOSTON, MASS. • BRONX, N.Y. • NEWARK, N.J. • JAMAICA, L.I.

WHOLESALE RADIO SERVICE CO., INC.
100 Sixth Avenue, New York, N. Y.

Rush FREE 1939 Catalog No. 73-4KA

VALU-BILL says:
"It's a
reg'lar
encyclopedia!
DON'T MISS
IT!"

Name _____

Address _____

City _____

State _____

PASTE COUPON ON PENNY POSTCARD

5-Meter Super-Regenerative Receiver

(Continued from preceding page)

side of the 25Z6 filament, the red lead connects to the switch and the black lead runs to the plate and cathode terminals of the 25Z6. Since the resistor element is distributed evenly over the entire length of the line cord, *no attempt should be made to shorten the cord by cutting it.* The entire length must be used. In operation, the cord will become warm, but not too hot to touch.

Adjusting Set for Best Reception

Once the receiver has been completely wired, a few adjustments will result in efficient operation. The receiver is turned on by advancing the combination audio gain control and line switch and the gain control advanced to its maximum clockwise position. The regeneration control is then slowly advanced in a clockwise direction. At some point a slight click or smooth plop will be heard; this indicates that the detector is oscillating; the regeneration control is advanced another few degrees when a loud rushing noise will be heard. This indicates *super-regeneration*, and at this point, the receiver is in its most sensitive condition. The Audio gain control may now be retarded if the rushing noise is too loud for comfort.

When a signal is tuned-in the rushing noise will disappear or be reduced in intensity. On strong signals it will disappear entirely, while on weak signals the noise will still be heard in the background.

Once a signal has been tuned-in the r.f. and detector circuits can be brought into resonance. This is done by changing the inductance of the coils by either compressing or expanding the coils. Incidentally, the

frequency range of the receiver can be adjusted within small limits by this operation. Although the same size coils are used by the constructor and the receiver wired exactly like the photo, some adjustment of the coils may be necessary to cover the desired frequency range. It may even be necessary to *add or subtract* a turn.

By using different size coils different frequency ranges can be obtained. As built by the writer for 56 megacycle reception, both coils consist of seven turns of number 12 bus bar, wound on a diameter of $\frac{5}{8}$ inch. For the 112 mc. range approximately 3 turns wound to a diameter of $\frac{1}{2}$ inch will be required.

List of Parts

BUD

- 1—Metal Cabinet No. 994 (7x12")
- 1—Chassis 11x6 $\frac{1}{2}$ " No. 997
- 1—Interstage shield 5 $\frac{1}{2}$ x7" No. 1256
- 2—15 mmf. variable condensers No. 565
- 2—U.H.F. r.f. chokes No. 925
- 2—Octal isatex sockets No. 959
- 2—Octal bakelite sockets No. 1063
- 1—Ceramic flexible coupling No. 795
- 2—Metal tube grid caps No. 108
- 1—Phone jack No. 233
- 1—4" black bakelite dial (vernier) No. 103B
- 2—Knobs No. 183
- 1—35 mmf. coupling cond. adjustable No. 833

SPRAGUE (Condensers)

- 2—16 mf. 200 v. type BT-162
- 1—8x8 mf. 450 v. type PTM-88
- 1—10 mf. 25 v. type BII-10
- 1—2 mf. 200 v. type BT22
- 3— $\frac{1}{2}$ mf. 600 v. type TC-5
- 1—.01 mf. type SW-11
- 1—.0001 mf. mica type 1FM-31
- 2—.004 mf. mica type 1FM-24
- 2—.006 mf. mica type 1FM-26

I.R.C. (Resistors)

- 1—440 ohms type AA
- 1—50,000 ohm potentiometer

- 1—50,000 ohm pot. type 11-123
- 1—S.P.S.T. switch No. 21
- 1—300 ohms type BT $\frac{1}{2}$
- 1—50,000 ohms type BT $\frac{1}{2}$
- 2—100,000 ohms type BT $\frac{1}{2}$
- 2—25,000 ohms type BT $\frac{1}{2}$
- 1—10,000 ohms
- 2—15 megs.

RAYTHEON (Tubes)

- 1—6K7
- 1—6C8G
- 1—25A6
- 1—25Z6

OXFORD-TARTAK

- 1—5" P.M. or 5000 ohm field loud-speaker

STANCOR

- 2—15 henry chokes 50 ma. No. c-1277

Miscellaneous

- 1—D.P.D.T. toggle switch
- 2—Lengths No. 12 bus bar
- 1—200 ohm resistor line cord

Local HAM Gossip

(Continued from page 343)

day on 5 meters. With 65 gallons of lemonade and all the prizes gone, we QRT for the summer and closed the radio shack up until Sept. 1st. I am sure from what the gang had to say, they will want a "field meet" this fall. This one will be better and bigger than the last, *I hope*. One hundred and fifty-three attended—all free! The radio clubs paid for the lemonade and drinks; the prizes were given by Warren Radio Co., 1110 Madison Ave., Harry's Auto Supply Co., Adams St., Toledo Radio Spec. Co., on 10th St., and the Lifetime Mike Co., on Madison Ave. The total value of the prizes was \$30. Joe Solark was chairman of the group of TUHFA and TRC members that made the lemonade.



This MODERN DESK LAMP
Is Yours Absolutely FREE
 With a Year's Subscription to **RADIO & TELEVISION**

JUST THINK OF IT—you can get absolutely FREE, the beautiful desk lamp shown at the left. This attractive desk lamp is suitable for home, desk, den, office, laboratory, studio or workshop. It is sent to you by the publishers with their compliments for a one-year subscription to **RADIO & TELEVISION**. Look at the many fine features which this handsome desk lamp has. Read the list below.

LOOK AT THESE FEATURES!

- ⊛ Constructed of metal with attractive bronze finish.
- ⊛ Scientifically constructed to give glareless, diffused light.
- ⊛ Helmet-type shade can be tilted to any convenient angle.
- ⊛ Stands 13" high and has 10" metal shade.
- ⊛ 5-foot rubber insulated cord and plug.
- ⊛ Constructed to last for many years.

Clip Coupon Today — and Mail!

Send your subscription today to **RADIO & TELEVISION** for One Year (12 issues) and receive absolutely FREE one of these truly remarkable desk lamps. New subscribers are accepted or you may extend your present subscription another twelve months under this offer. Mail your remittance of \$2.50 (Plus 25c for shipping charges on lamp) to the publishers of **RADIO & TELEVISION**. (Canada and foreign \$3.25) You will promptly receive your FREE DESK LAMP by return mail. Use the coupon at the right to order your subscription.

RADIO & TELEVISION

99 Hudson Street

New York, N. Y.

RADIO & TELEVISION, 99 HUDSON ST., NEW YORK, N. Y.

Gentlemen: Enclosed you will find my remittance of \$2.50 for which enter my subscription to **RADIO & TELEVISION** for One Year (12 issues). Send me promptly my FREE DESK LAMP. (Canada and foreign \$3.25.) In U. S. add 25c additional to cover shipping charges of lamp.

() NEW SUBSCRIBER

() EXTEND PRESENT SUBSCRIPTION

Name

Address

City State

(Send remittance by check, money order or unused U. S. Postage stamps. Register letter if you send cash or stamps.)

R&T-103R

Modulator for the 35 Watt Transmitter

(Continued from page 361)

- One metallized resistor, insulated type, 15,000 ohms, 1 watt
- One metallized resistor, insulated type, 2,000 ohms, 1 watt
- One metallized resistor, insulated type, 1,500 ohms, 2 watts
- One metallized resistor, insulated type, 1 megohm, 1/2 watt
- Four metallized resistors, insulated type, 0.5 megohm, 1 watt
- One wire-wound resistor, 200 ohms, 50 watts; adjustable type
- One wire-wound resistor, 15,000 ohms, 50 watts
- Two wire-wound resistors, 5,000 ohms, 25 watts
- One wire-wound resistor, 20,000 ohms, 75 watts

AEROVOX (Condensers)

- One electrolytic condenser, 10 mf., 25 volts
- One electrolytic condenser, 25 mf., 25 volts
- One electrolytic condenser, 25 mf., 50 volts
- One electrolytic condenser, 16 mf., 450 volts
- Two electrolytic condensers, 2 mf., 450 volts
- Two paper dielectric condensers, 0.05 mf., 600 volts
- One mica condenser, .001 mf.

SOLAR (Condensers)

- Four electrolytic condensers, 8 mf., 600 volts, wet type

RCA (Tubes)

- One 6F5G tube
- One 6F8G or 6N7G tube
- Two 6L6G tubes
- One 5U4G tube

PAR-METAL (Cabinet, panel and chassis)

- One two-panel size steel cabinet, black crackle, 17 1/2 x 13 x 20"
- Two standard steel panels, 8 3/4 x 19"
- One standard steel chassis, 10 x 13 x 3", black crackle finish

JEFFERSON (Transformers)

- One microphone transformer, universal type
- One input transformer, One plate to p.p. grids
- One modulation transformer, Push-pull 6L6S in class "A" to 5,000 ohm class "C" load

STANCOR (Transformers)

- One "swinging" choke, 8-30 henries, 250 milliamperes
- One filter choke, 15 henries, 250 milliamperes
- One plate transformer, 800 volts, c.t., 300 milliamperes
- One filament transformer, 5 volts at 6 amperes and 6.3 volts at 6 amperes

Brush Announces New Models...

HEADPHONES — PICKUPS MICROPHONES

Featured in the complete and revised Brush line are new type microphones, headphones, and pickups. Special attention has been given to making these products widely adaptable for either amateur or commercial use. Also featured is the popular Brush Hushatone (pillow speaker) which brings new comfort and convenience to radio listeners.

Fill in and mail the coupon below for the new Brush catalog of the complete Brush line.

THE BRUSH DEVELOPMENT CO.

3326 Perkins Avenue
CLEVELAND, OHIO

Please send the new Brush catalog of the complete Brush line to:

NAME

STREET

CITY

STATE

WORLD'S GREATEST all around ELECTRIC TOOL

DRILLS • GRINDS • SANDS • SAWS
POLISHES • SHARPENS • CARVES

The new WHIZ ELECTRIC TOOL is the handiest, most useful power tool ever made. Not a delicate instrument but a real rugged tool, equally effective for both power and precision work. Drills through 1/4 inch iron plate in 32 seconds or engraves intricate designs on jewelry. Handles any material: Metals, Woods, Alloys, Plastics, Glass, Steel, etc. Saves time. Eliminates tedious labor. Plug into any socket AC or DC, 110 volts. Chuck 3/4 inch capacity. Ball bearing thrust. Powerful, triple-gear motor. "Worth its weight in Gold." To a mechanic or handy man. STANDARD MODEL with normal speed (uses 50 different accessories, instantly interchangeable). Special Introductory Price for limited time, only \$6.95.

Accessory outfit (Value \$2) includes set of drills, wheels, mounted brush, polishing wheel, carving bur, etc. FREE with each outfit ordered NOW. We pay postage on all shipments. Will send C.O.D. if desired.


10-DAY TRIAL—MONEY BACK GUARANTEE

Special "2-SPEED" MODEL combines Normal speed and High speed in one outfit (uses 200 accessories) only \$8.95 complete, with same accessory outfit (value \$2) FREE.

PARAMOUNT PROD. CO.

Dept. 10-SW, 48 W. 48th St. New York

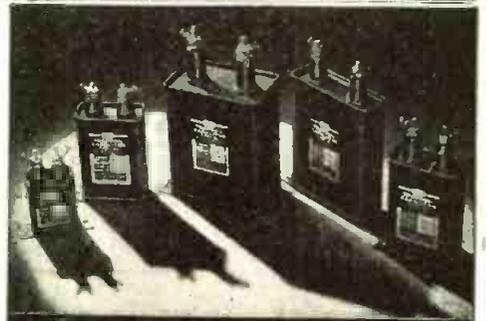Don't miss the November issue—chock full of HAM and FAN features.



TRANSOIL

for transmitting

HIGHEST QUALITY
OIL CAPACITORS

Ask for new complete
Transmitting Catalog
describing

TRANSOIL—SOLAR—TRANSMICA

SOLAR
MFG. CORP.



599 BROADWAY,
NEW YORK CITY

THE NEW EARCAPS

improve the quality of your headphone to give results of a dynamic speaker. Immediate delivery for Ambassador, Baldwin, Brandes, Cannonball, Globe, Kellogg, Murdoch, Radlocar, Solid, Trimm Featherweight and Professional, and Western Electric phones. Send for illustrated literature giving complete information. Inventor and Manufacturer Dept. S-10

PAUL JARNAK, 69 West 83rd St., New York City

WE HAVE The RADIO YOU WANT

How would you like to save up to 50% on Nationally advertised Radios, such as Stromberg Carlson, Philco, RCA, Zenith, G E, etc. etc. for home, farm and auto, over 400 models to choose from. Also hundreds of electric appliance items for the home. Write today for the new 1938 giant catalog FREE.


MODELL'S Dept. 60 Cortlandt St., N.Y.C.

HEADSETS

Amateurs! Check your requirements and don't forget the importance of your phones. Get new ones—get better ones—get Featherweights!

For information, write Dept. R-910

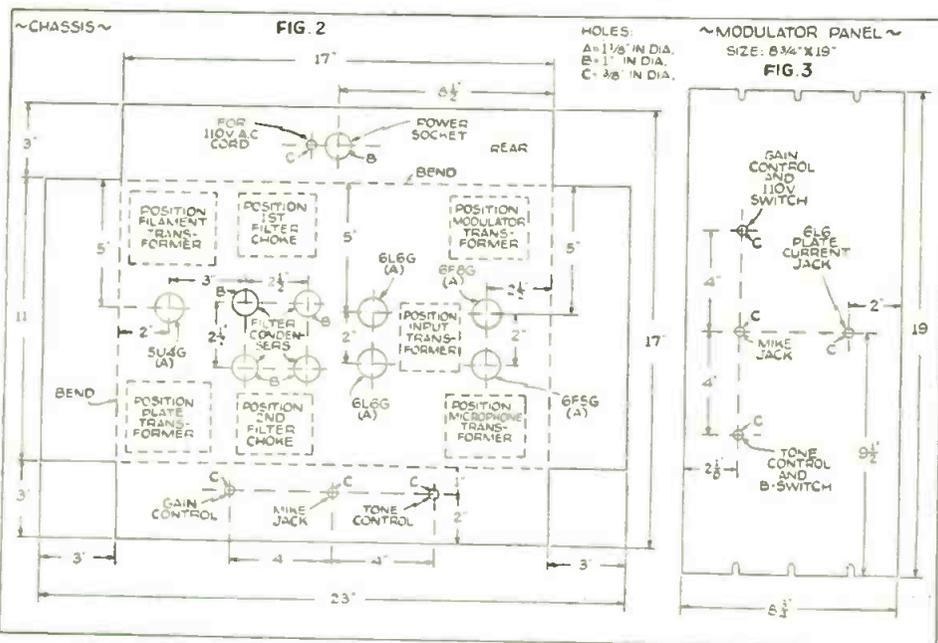TRIMM RADIO MFG. CO.
1770 W. Berteau Ave.,
Chicago, Illinois.



Drilling dimensions for chassis and panel of modulator.

STOP, LOOK & BUY!

Rockbottom Prices On Army and Navy and Surplus Merchandise

When prices are low we buy! They're low now—LOWER THAN THEY EVER WILL BE—hence this sale. Most of the merchandise is new—never used; some of it reconditioned. 100% satisfaction on each transaction or your money refunded.

ORDER FROM THIS PAGE. Use the convenient coupon below. Be sure to include sufficient extra remittance for parcel post charges, else the order will be shipped express, charges collect. Any excess will be refunded. C.O.D. shipments require a 20% deposit. If full remittance accompanies order deduct 2% discount. Send money order—certified check—new U. S. stamps. No C.O.D. to foreign countries.

ORDER TODAY QUANTITIES LIMITED QUICK SHIPMENTS ASSURED

EDISON 1/50TH H.P. UNIVERSAL MOTOR

Made by Edison Electric Co. for Dictaphone machines. Can be used on 110 volt D.C. or A.C. lines (any frequency on A.C.). Double shaft, 5/16" diam. Any speed obtainable with suitable rheostat. Size 9" x 4" high, x 3 1/2" wide overall. Sbp. Wt. 8 1/2 lbs.

ITEM NO. 10
Your price \$2.25

SPERRY GYROSCOPE LIQUID COMPASS

Made for U.S. Signal Corps; sensitive and accurate. Quick readings easily made from top; accurate readings of graduations through focusing magnifying lens on side of instrument. Complete with level sights and ratchet leather carrying case. Excellent for boats, boy scouts, campers, hikers, etc. A few turns of wire around its case makes it usable as a galvanometer. Sbp. Wt. 3 lbs.

ITEM NO. 12
Your price \$1.85

PORTABLE TELEGRAPH AND BUZZER FIELD SETS

Made for military use by Western Electric. A wonderful buy if only for the parts it contains. Never been used. Good for code practicing, signaling, communications, etc. Contains 2 used, high frequency buzzer with platinum contacts, telegraph key, telephone switches, earphone, condensers, transformers, chokes, etc. A \$50 value easily. Complete in wooden case with diagrams and instructions. Sbp. Wt. 12 lbs.

ITEM NO. 16
Your price \$5.45

PRISMATIC RIFLE SIGHT AND OBSERVERS' SCOPE

Made by Warner & Swasey. Consists of a prismatic ocular and objective lens (6 power), calibrated reticles with cross hairs, 2 highly polished lenses set in solid bronze frame with soft rubber eye cup. Micrometer adjustment for windage and elevation. Mount on Krag, Enfield, Savage, Remington, etc. With mount and leather case. Sbp. Wt. 4 lbs. Regular price \$38.00.

ITEM NO. 18
Your price \$8.95

TELEGRAPHIC TAPE RECORDER

A wonderful buy! Apparatus makes a written record of code and similar messages on paper tape. An ideal machine for learning code or teaching code to groups. Radio men can easily adapt it to short-wave receivers for taking permanent records of code messages. Double pen permits simultaneous recording of two messages. Pens are operated by battery and key while tape feeder is spring driven (hand wound). Case made of solid brass on heavy iron base. Completely reconditioned. (Less tape; easily obtained anywhere.) Original cost \$85.00. Sbp. Wt. 20 lbs.

ITEM NO. 20
Your price \$19.95

ARMY AIRCRAFT KEY

Type J-E Army aircraft solid brass transmitting key with large heavy duty tungsten contacts. Well balanced action—easy on the fist. Sbp. Wt. 2 lbs.

ITEM NO. 22
Your price \$1.90

VARIABLE SPEED UNIVERSAL MOTOR

FOR 110 VOLTS, A.C. OR C.C.
Made for Dictaphone machines by American Gramophone Co. Used, but in excellent condition. Special lever control permits variable speeds up to 3000 r.p.m., 1/2" shaft extends from both sides of motor. Measures 7 1/2" x 3 1/4" diam. overall. Sbp. Wt. 6 3/4 lbs.

ITEM NO. 11
Your price \$2.55

WESTERN ELECTRIC BREAST MIKE

A lightweight aircraft-type carbon microphone, with breast plate mounting. Can be adapted for home broadcasting or private communication systems. With cord and plug. Sbp. Wt. 4 lbs. (Illustrated at right.)

ITEM NO. 14
Your price \$2.45

Magnavox Anti-Noise Microphone, also good for home broadcasting etc. With cord and plug. Sbp. Wt. 2 lbs.

ITEM NO. 15
Your price \$1.80

NAVY PORTABLE SEARCHLIGHT

1/2 MILE RANGE
Cast aluminum and bronze housing. Mangin type parabolic glass reflector 5" diam. Trigger switch and handle for operating, tilting and focusing lamp. Made by General Electric and National X-Ray Co. for U.S. Navy. Measures 4" deep x 5 1/2" diam. overall. Focal length, 15 1/2". Approximate 100 candle power. Has threaded nipple for 1/2" pipe support. Complete with wooden carrying case. Excellent for camp trailers, barns and outdoor and indoor displays. Supplied with either 6 or 12 volt lamp. Sbp. Wt. 14 lbs. (Net 4 lbs.)

ITEM NO. 17
Your price \$6.65

AIRCRAFT GENERATOR PROPELLER

"DeSauriers" automatic pitch, controllable pitch. Operating speed 4,500 r.p.m. Made 11 1/2" x 2" sweep 23". All aluminum and bronze housing. Complete with streamlined housing (shown dotted). Fits 9/16" shaft. Net weight 5 1/2 lbs. Sbp. Wt. 7 1/2 lbs. Original cost \$200.

ITEM NO. 19
Your price \$5.25

NAVY FLOODLIGHT

Made to U.S. Navy rigid specification these sturdily constructed floodlights are now available at less than half of their original price of \$70.00. Brand new merchandise, never before used. Pittsburgh floodlight type FLC-500, 16" Durex aluminum reflector. Floodlight has double adjustments and is weatherproof. Takes 300 to 500 Watt Mogul base lamp. Measures 18" x 18" x 24" overall. Sbp. Wt. 35 lbs.

ITEM NO. 21
Your price \$29.70

ANTI-CAPACITY SWITCHES

Made by Western Electric. Double throw switch with 12 terminals—equivalent to two double-pole, double-throw switches. All contacts are of platinum plate. Original price \$3.50 each. Sbp. Wt. 1 lb.

ITEM NO. 23
Your price \$1.55

Back in the Days of Crashing Spark-Gaps

(Continued from page 331)

that kind of a "rig" it didn't matter how big you built your loose coupler tuner. You couldn't get away from my signals—two turns or 500 turns it was just as loud and persistent.

Antenna Radiation meter, did you say? Yes—a darned good strong 32 candle-power carbon lamp (and it had to be strong) made a good one. INSULATION??? Why worry about that when without it your lamp lighted brighter with most of the current going to ground via the antenna mast and guy wires—not to mention the lead-in! At least you thought you were getting plenty "into the air"—no one else could light up a 32 C.P. lamp as brightly. You were the "tops."

Then came the best friend the Amateurs of this country ever had. Mr. E. T. Cunningham who gave us the *audiotron* . . . first vacuum tube and the one gadget that really put Amateur radio here to stay. Unheard of distances were covered and soon everyone was in touch with one another . . . swapping experiences. This education led to the development of highly efficient amateur equipment and stations.

In fact Amateur radio has progressed so rapidly that it recently became necessary to ship a transmitting unit to Pitcairn Island, so that present day Amateurs might manufacture a new spot on the globe to conquer. After that—well, perhaps they'll take a shot at Mars, but I assure you that it will be the only spot not as yet touched by Amateur signals.

If you are capable of realizing the kick that Jules Verne would get from one little peek through the periscope of a modern submarine—then you will fully appreciate how I feel when I see a youngster busily engaged in the operation of his modern 1938 Ham rig—so great is the contrast between modern equipment and that which I had to make and use in the year 1909.

I could go on raving like this for months with great pleasure and without end—but Hugo has been kind enough to allot me sufficient space in which to jot down a small portion of my romantic reminiscences—which I deeply appreciate—so CUL.



Short Wave League

At a Directors Meeting held in New York City, New York, in the United States of America, the Short Wave League has elected

John F. Müller

a member of this League.

In Witness whereof, this certificate has been officially signed and presented to the above.

H. Winfield Secor
Club Secretary

This handsome certificate is presented FREE to all members of the SHORT WAVE LEAGUE. The full size is 7 1/4" x 9 1/2". See page 374.

WE HAVE NO CATALOG. ORDER FROM THIS PAGE.
HUDSON SPECIALTIES - 40-T West B'way - N.Y.C.
IT'S EASY TO ORDER—CLIP COUPON—MAIL NOW

HUDSON SPECIALTIES CO., 40-T, West Broadway, N. Y. C. 1038

I have circled below the numbers of the items I'm ordering. My full remittance of \$..... (include shipping charges) is enclosed.
OR my deposit of \$..... is enclosed. (20% required), ship order C.O.D. for balance. (New U.S. stamps check or money order accepted.)

Circle Item No. wanted: 10 11 12 14 15 16 17 18 19 20 21 22 23

Name Address

City State

Send remittance by check, stamps or money order; register letter if you send cash or stamps.

An Efficient 5-Band Amateur Receiver

(Continued from page 354)

so that it may be of service when other communication means fail.

The amateur set to be described covers the 10-, 20-, 40-, 80- and 160-meter bands. The heart of the receiver is the BL-5H Tuner, a 5-band coil switching arrangement so designed that the coils not in active use are *shorted*. Band-setting trimmers are rigidly mounted on each of the 5 coils, thus allowing the amateur bands to be *spread* over substantially all of the tuning range, as well as to allow adjacent channel reception in case this is desired.

Construction of the Receiver

The construction of the receiver is extremely simple as will be evidenced by the circuit diagram shown in Fig. 1. For simplicity, only *one* of the 5 sets of coils employed is shown. The components of the receiver are mounted on a small sub-base, details of which are shown in Fig. 2. A 6S7G is used for a *regenerative detector*, while a 6G6G is used for the *audio amplifier* (other tubes with similar characteristics may be used if desired). The filaments of these tubes may be either operated from a 6.3-volt filament transformer for station operation or may be heated either from a 6-volt storage battery or three dry cells connected in series when it is desired to

operate the receiver "portable." In any case, the total filament drain is only 300 milliamperes. *Regeneration* is accomplished by varying the screen voltage on the detector and, if the receiver is carefully constructed, this regeneration control will be found to be especially *smooth*, thus providing maximum gain and sensitivity. In this connection, it is especially important that the RF filter system in the plate circuit of the 6S7G be connected as indicated in Fig. 1. The 100 mmf. plate by-pass (C) condenser and the .002 mf. screen by-pass (C) condenser should be grounded to the same point, as indicated. It is advisable also to ground the BL-5H Tuner to this common ground. The filter system in the screen circuit consisting of the .002 mf. condenser, the 1000-ohm resistor and the .1 mf. condenser is essential for smooth regeneration. In order to prevent the regeneration control from being too critical, a 20,000 ohm resistor is placed in series with the 50,000 ohm potentiometer. The value of this resistor, in many cases, should be increased. It must be sufficiently low so as to allow regeneration over all of the 5 amateur bands, yet sufficiently high so that the control is not critical. If the antenna used with the receiver has a very low radio-frequency resistance, it will be found that this resistor may be increased to 50,000 or 75,000 ohms. However, if the antenna used is not well insulated, it may be necessary to employ as low a value as 10,000 ohms for this resistor.

The audio choke employed in the plate circuit of the detector has an inductance of approximately 100 henrys. A resistor can not be used in this position in place of the choke without increasing the B battery voltage very materially.

Wiring the Receiver


In wiring the receiver, all components should be so situated that the leads carrying radio frequency current are kept as short as possible. The tube positions indicated on the chassis layout shown in Fig. 2 have proven very satisfactory. The 6S7G tube must be shielded. As will be noted from the photograph of the receiver, the choke and the output transformer in the plate circuit of the 6G6G are mounted on top of the chassis, while the other component parts are mounted underneath. The output transformer should have an impedance rating of approximately 12,000 to 2,000 ohms, the 12,000 ohm side being connected in the plate circuit of the 6G6G, while the 2,000 ohms impedance approximately matches the phones or magnetic speaker, which are conveniently plugged into the jack provided.

If the receiver is to be completely operated from batteries, it is necessary to employ an on-and-off switch which opens both the -B battery lead as well as the A battery lead, as otherwise a constant drain on the B battery through the voltage dividing system on the screen of the detector tube will result. The B supply voltage may have any value between 45 and 250 volts; 90 volts is entirely satisfactory.


Adjusting Band-Setting Condensers on 5H Tuner

The antenna is connected either through a series antenna condenser or to the cathode tap on the coils of the 5H Tuner. Since


(Continued on following page)

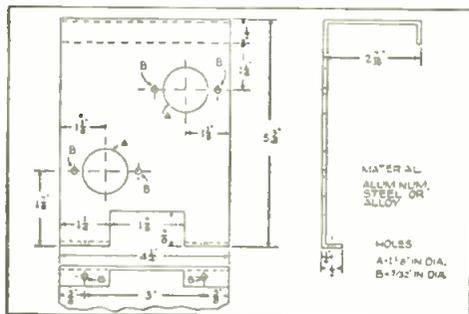

Chassis detail. Fig. 2.

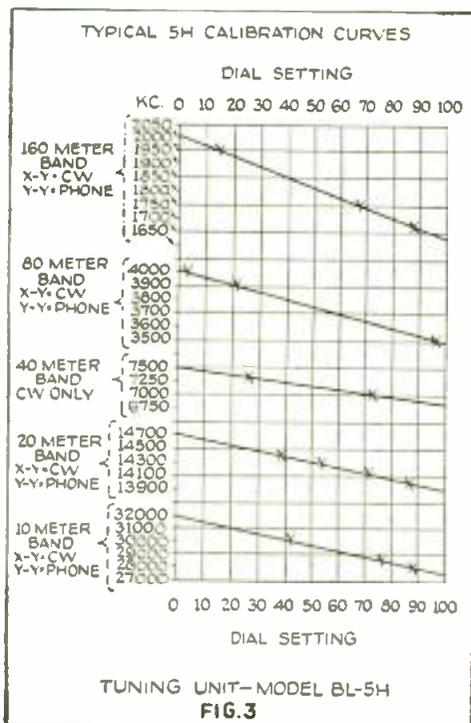

Calibration curves for 5 bands.

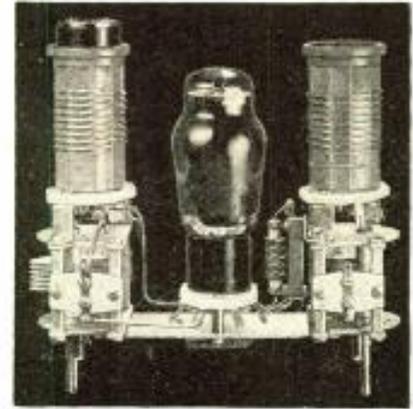

For Beginners!

Hammarlund's new "OD-10" oscillator-doubler "Foundation Unit" is ideal for beginners. Can be assembled in a few minutes time and provides a low power transmitter capable of up to 25 watts output on two bands with a single crystal. Designed to be used with other Hammarlund "Kits", it allows the beginner to start with low power and gradually build up a 300 watt "rig" simply by adding these inexpensive units. Write for folder!

HAMMARLUND MFG. CO., INC.
424-438 W. 33 St., N.Y. City SW&T-10
 Please send me "OD-10" folder.

Name

Address

City State



HAMMARLUND

Canadian Office: 41 West Ave. No., Hamilton, Ontario

CORNELL-DUBILIER OFFERS
THE MOST COMPLETE CON-
DENSER CATALOG IN RADIO

FREE

New data, new designs, new types... every week uncovers some new C.D. engineering development. Are you keeping abreast of capacitor progress? You'll find in this new catalog a wealth of information. Every one of its 40 pages illustrates and describes some new type capacitor. Cornell-Dubilier, world's oldest and largest exclusive manufacturer of capacitors, offers you this amazing catalog, thoroughly complete, representing the engineering experience of 28 years in the capacitor field at no cost. No amateur experimenter, serviceman or engineer should be without it! Mail coupon for **FREE** copy today.

Are you on the C.D. house organ mailing list? If not, check coupon for your copy.

CORNELL-DUBILIER ELECTRIC CORPORATION
1027 HAMILTON BOULEVARD
SOUTH PLAINFIELD, N. J.

CORNELL-DUBILIER ELECTRIC CORPORATION SW1030
1977 HAMILTON BOULEVARD, SOUTH PLAINFIELD, N. J.

Rush to me copy of Catalog 161
Put my name on list for house organ


Name

Address

City State

RADIO INSTRUCTION

36 BOOKS in 1

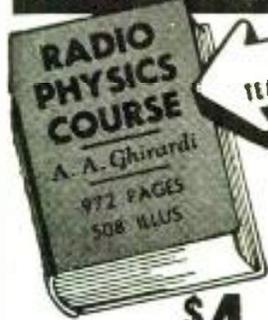

THIS 1 BOOK
TEACHES YOU EVERYTHING

only \$4

Ghirardi's great home-study course gives you EVERYTHING there is to learn about RADIO, ELECTRICITY, SOUND—and even Television and Cathode-Ray Tubes! This easy course makes everything as simple as A.B.C. That's why it is used by more radio schools and students than any other radio book in the world.

HERE'S WHAT YOU GET!

Sound—Electrical Theory and Principles—Electrical Currents—Electro-magnetism—Transformers—Inductance—Condensers—Measuring Instruments—Radioactivity—Broadcasting—Receiving—Vacuum Tubes—Amplification—Superheterodyne—Speakers—Receivers of all types—Short-Wave—Auto-Radio—Aircraft Radio—Public Address—Photoelectric Cells—Cathode-Ray Tubes—Television—Testing and Servicing—Sound Motion Pictures—Reference Tables—658 Review Questions for Self-Study—and DOZENS of other subjects.

TRY IT!

Master Radio the quick "Ghirardi way"—previous training and knowledge of mathematics are not necessary. Easy and speedy! Get started at once—order your book this simple way: write your name and address on this ad, and send it in with \$4 today (\$4.50 foreign) for your copy, more money back if not satisfied. Free circular—no obligation.

RADIO & TECHNICAL PUBLISHING CO.


45 Astor Place, New York.

Dept. SWT-108

COMPLETE in 1 Book

RAPID CALCULATOR

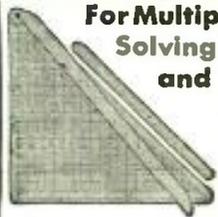For Multiplication, Division,
Solving Triangles, Stress
and Force Diagrams




THE "TRIGONOGRAPH" is a time-saving, indispensable "triangular slide rule" for: Solving Right and Oblique Triangles, Obtaining All Trigonometric Functions of an Angle by a Single Setting.

Multiplication, Division, Proportional Calculations, and Solution of Stress and Force Diagrams. A Combined Numerical Calculator and Trigonometric Function Table on a Single Page. Ideal for review. Instruction Book furnished. Celluloid "Trigonograph" \$1.50; Cardboard Model 50c. Money back guarantee. Descriptive Circular on Request.

CHEMICAL RUBBER PUBLISHING CO.
1908 W. 112th St. Cleveland, O.

LEARN CODE RIGHT

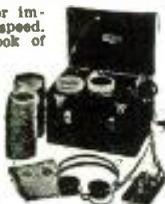It's easy and practical to learn or improve your radio or Morse Code, any speed. Senior model with 10 tapes and Book of Instructions—\$20.25. (Rented at low cost.) Junior model with 5 tapes and Book of Instructions—\$12.00. (Not rented.) Complete oscillator equipment, less battery, \$8.50. Send for details today to—



INSTRUCTOGRAPH CO.

Dept. SW-10
912 Lakeside Place, Chicago

BUY ON CASH OR TERMS; HALLICRAFTER and R.M.E. SHORT-WAVE RECEIVERS, SPEED-X and VIBROPLEXES

RADIO COURSES

RADIO OPERATING—BROADCASTING
For Gov't. License Preparation
● RADIO SERVICING—a practical course
● RADIO AMATEUR CODE ● TELEVISION ● ELECTRONICS—1 yr. day course, 2 yrs. eve.
Day and Evening Classes. Booklet Upon Request

New York YMCA Schools
6 W. 64th Street, New York City
TRADE AND TECHNICAL SCHOOL
Licensed by the State of New York

An Efficient 5-Band Amateur Receiver

(Continued from preceding page)

the capacitance of the antenna system alters the tuning position, it will be necessary for the amateur to adjust the band-setting condensers associated with each of the 5 coils. These condensers should all be set with the antenna connected to the receiver, although it is advisable before the final adjustment on these condensers are made to determine which connection gives better signal strength. On the 160 and 80 meter bands, antenna connection to the point marked No. 1 usually results in better reception, while on the 10-, 20-, and 40-meter bands connecting the antenna to point No. 2 is usually advisable. This however depends somewhat upon the antenna used. In fact when working portable with a "fish pole" antenna the series antenna condenser may be *shorted*. Having determined the antenna connections for the various bands, connect the antenna to its appropriate point and set the dial or pointer knob so that it is approximately 50 on the scale. With the series antenna condenser partially closed (this will depend upon antenna length) adjust the band-setting condenser on the 160-meter coil until phone reception is heard. If a signal generator is available place the output lead from the signal generator so that it closely parallels the antenna lead-in. With the pointer set at 50 on the scale, adjust the band-setting condenser on the 160-meter coil for 1.86 mc. A similar procedure is followed for each of the other coils, following the frequency calibration for the various bands given in Fig. 3 as a guide. Another method of adjusting the band-setting condensers is to tune in a station the frequency of which is known, set the pointer to the position on the scale which corresponds to this frequency (see Fig. 3), adjust the band setting condenser until this station is again tuned in.

This article prepared from data supplied by courtesy of the *Browning Laboratories*.

Parts List

BROWNING LABORATORIES, INC.

1—BL-5H Tuner
Etched and engraved panel—7" x 10"
1½" knob with 1½" pointer and two 1¼" pointer knobs

I.R.C. (Resistors)

R1—50,000 ohms, 1 watt Potentiometer (Type 11-123)
R2—20,000 ohm. ½ watt (BT-½)
R3, R4—1000 ohm. ½ watt (BT-½)
R5—.25 megohm. ½ watt (BT-½)
R6—500 ohm. ½ watt (BT-½)

CORNELL-DUBILIER (Condensers)

C1, C8—.002 mf. mica
C2, C5—.0001 mf. mica

BUD MFG. CO.

Cabinet—6" x 7" x 10"

YAXLEY OR UTAH

1—Phone Jack

U.T.C.

CH1—100 henry audio choke (S-24)
T1—10,000 to 2000 ohm impedance output transformer (S-18)

TOBE (Condensers)

C7—10 mf. 50 volt dry electrolytic condenser
C3, C6—0.1 mf. 400 volt paper condenser
C4—.05 mf. 400 volt paper condenser

MISCELLANEOUS

On-off switch
Tube shield

RADIO INSTRUCTION

RADIO ENGINEERING



RCA Institutes offer an intensive course of high standard embracing all phases of Radio and Television. Practical training with modern equipment at New York and Chicago schools. Also specialized courses and Home Study Courses under "No obligation" plan. Catalog Dept. SW-38.

RCA INSTITUTES, Inc.

A Radio Corporation of America Service

75 Varick St., New York, 1154 Merchandise Mart, Chicago

LEARN RADIO TELEVISION

500 LICENSED graduates placed in past 7 years in shipping, broadcasting, aviation, police, etc.; we also teach radio servicing and repairing; new beginners' class Sept. 12th, Nov. 7th.; 52-page catalog free; oldest, largest and best equipped.

MASS. RADIO SCHOOL

18 BOYLSTON ST., BOSTON

Est. 1899

GET AHEAD IN RADIO TELEVISION

What you should do to win good employment in Radio, Television and broadcasting is told fully in this fascinating free booklet. Write now: BWC-10, 4000 S. Figueroa St.

TELEVISION



BE A RADIO SERVICE EXPERT



Modern receivers require men with modern training for service work

LEARN AT HOME

Our home instruction method and service equipment offer starts you earning money almost at once. Up to \$9 an hour easy in a short time. Write for free book.

Radio Training Ass'n of America
Dept. SW-810
4525 Ravenswood Ave., Chicago

Want to Learn Foreign Languages?

(Continued from page 341)

stands nearer to it than if he were just looking at it to see and appreciate it.

By listening to loud reproduction, you will learn to shout. This *learning* to shout is a good thing. For when you repeat the language to yourself for practice, you may say it louder than normal, but when you come to speak it, you will instinctively speak no louder than the person with whom you are talking. Anyone who has already tried speaking in a *foreign* language will tell you that if ever they have to talk loud, they find pronunciation difficult. So it will be just the opposite with you. You learn to speak loud, and then when you come to talk at ordinary volume, any defect in pronunciation will be reduced.

Headphone Adapter for Any Radio

For greater sensitivity and for private listening at late hours, a headphone adapter permitting headphone reception with the speaker off is essential. The simplest adapter is illustrated. The single-pole double-throw switch and the two phone tip-jacks are mounted on a piece of bakelite two inches square. A three-conductor cable is wired according to the circuit diagram and is connected to the radio set dynamic speaker's voice coil. If a magnetic speaker is used the speaker coil is used instead.

Headphone Adapter Parts List

5 ft. 3-conductor cable*
1 S.P.D.T. toggle switch*
2 Tip-jacks*
1 Bakelite panel 2" x 2"

TRIMM

Featherweight headphones
*Most Radio mail order houses can supply this item if properly identified as to title of article, issue (month) of RADIO & TELEVISION and year.

How HAM RADIO Saved Shawneetown!

(Continued from page 334)

flashlight, in a farmhouse where we found eleven marooned refugees, and finally contacted Harrisburg and got out the first news from Shawneetown. By 3 a. m. my storage battery was exhausted and I was forced to suspend action.

Fortunately, a good friend, Jack Hatfield, arrived from the mine in a large boat propelled with a pair of oars, loaded us aboard and returned us to the mine.

When we reached the mine about daylight I set up and started relaying messages between Shawneetown and Harrisburg. In response to these messages, food, medicines, doctors and nurses were dispatched via the Ohio River and a large towboat, the *Patricia Barrett* left Memphis with a covered barge to assist in the possible evacuation.

While I handled messages, Jack went back into the backwater in a motor-boat he had secured, and broke a lane in the ice which had formed. It took all morning to reach Shawneetown, for by this time the water had covered the railroad track. He returned to the mine in the afternoon and took me to Shawneetown, arriving at 6 o'clock.

I set up the apparatus in the WPA office on the third floor of the oldest bank in the state of Illinois.

Conditions in Shawneetown were indescribably bad. It was not yet flooded, but the immediate danger was so great that the town was practically evacuated to the schoolhouse and every other possible shelter located out of the levee district.

Next morning we improvised an organization for rapid handling of messages. I improved the antenna systems, and "handled all messages." It was a big job and kept four of us busy all of the time. As I was the only operator, I was at the key at all times but since all incoming messages were by radio phone I had a stenographer take them in shorthand and transcribe them later.

At one time the power failed for several hours, but I hooked up the batteries and handled messages without interruption.

At 2 a. m. Monday it was apparent that it would be impossible to save Shawneetown and would be necessary to evacuate the inhabitants to a safer place. The *Patricia Barrett* had arrived and was capable of carrying everyone at one load, but there was no place to take them.

Early Monday morning everyone who wished to leave went aboard the *Barrett*. I set up my station in the pilot house and we left Shawneetown, tying up to some trees downstream until refugees from the High School could be brought aboard. At noon we received orders from the Red Cross to take refugees to Mt. Vernon, Ind., and Henderson, Ky. Shortly before the boat departed upstream I removed the gear and returned to Harrisburg where the situation had become critical.

During the rest of the emergency I helped operate W9HQD, which operated 24 hours a day. Too much praise cannot be given Kes Schonert, W9HQD, for the part he played in clearing the air and listening for my weak signals.

Famous Radio Experts Salute the Amateur

C. W. HORN

(Continued from page 358)

and gave us an immediate audience of many thousands. The amateurs were responsible for the construction of many of the home-made sets during the first years and for assisting their friends in the building of broadcast receivers. Many of the amateurs saw an opportunity of engaging in a profitable business, and, therefore, the industry had available many trained men upon whom to draw for engineering and service work. KDKA is generally thought of as a pioneer broadcasting station, and the men associated with this pioneer were mostly amateurs, such as Dr. Frank Conrad, Frank Falkner, John Coleman, and many others who have built a name and reputation in the industry.

As radio became a more complicated science, the big laboratories were naturally the source of new developments. The amateur could not afford the expensive laboratory equipment, but he did the next best thing, and immediately tried out every new tube and device that the laboratories produced. As a result the manufacturers had available an immediate field test of the newly developed devices, which saved time and resulted in a large amount of data that was helpful to the industry.

Today we are confronted with a new frontier in radio development in which we have to solve many problems in television and ultra high frequency transmissions. The television receiver is a highly complicated piece of mechanism as compared with the sound receiver. Therefore, even if television should become a reality today, and receivers be placed on the market, the industry would be faced with a tremendous shortage of trained personnel for installation and

service work. The only hope of meeting this demand for highly technical men is from the ranks of the amateurs. This was one of the reasons why the RCA decided to put kinescope tubes and other parts on the market. With thousands of experimenters building their own receivers, we can expect a fair percentage of them to enter the radio field, and these, to some extent, meet the demand for these specialists.

Consequently the amateur is making a valuable contribution to the welfare of his country. Because of the amateur the radio industry can more quickly get under way and make available to the public the latest advancements. This aids the national economic picture. In addition to this the amateur keeps himself in training and thus stimulates future advancements. In the event of war, the American people will be grateful to the amateur, because communication is probably the most vital factor for the national defense, particularly in view of the fact that modern warfare calls for rapid movement, and depends upon mobile units such as tanks and airplanes. The amateur as a class is patriotic, and many of them are members of the U.S. Army and U.S. Navy Reserves. It is unnecessary to repeat the good work that they do during times of disaster and floods. However, I feel that the amateurs' greatest contribution lies in the less spectacular and fundamentally more important service they play as yeomen in the advancement of radio and science, which benefits the country as a whole.

I am proud of the amateurs and proud that I was one myself.

More "Salutes" Next Month

Please say you saw it in RADIO & TELEVISION

RADIO INSTRUCTION

I CAN MAKE YOU A
RADIO EXPERT

Quicker, Easier with the New
SPRAYBERRY
Personalized
TRAINING IN RADIO



Get my
FREE BOOK




I ACTUALLY SET YOU UP FOR
A BUSINESS OF YOUR OWN

Here's the finest, most up-to-the-minute Radio Education available anywhere. Specially designed to give you intense, practical, quick training for a money-making career in the fast moving Radio Industry. All subjects covered, including Television, Electronics, Radio Set Repair, etc. Previous experience is unnecessary. You get my personal instruction every step of the way.

I equip you with BIG, PROFESSIONAL OUTFITS for doing interesting experiments and handling profitable share-time service jobs. I'll show you how to get these jobs while you're learning. My Course is Sold Under an Iron-Clad, Money-Back Agreement.

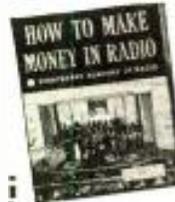SPECIAL SERVICEMAN'S COURSE. Complete details of this and fundamental Course features, etc., described in my 44-page FREE BOOK. Send for your copy today.



Mail Coupon Now

SPRAYBERRY ACADEMY OF RADIO,
F. L. Sprayberry, President
145-K University Place, N. W.,
Washington, D. C.

Please send me FREE copy of "How To Make Money in Radio"

Name Age
Address
City State
(Mail in envelope or paste coupon on postcard)

FASTEST WAY TO LEARN CODE

Easy, Fascinating, LEARN by EAR
To Be a GOOD OP.



The New All Electric Master Teleplex Code Teaching Machine is exactly what thousands are looking for. No experience needed. Ideal for beginners—steps up WPM for ALL Ops. There is no guess work

with Master Teleplex, because it records your sending in visible dots and dashes. You SEE and HEAR exactly how you are making your signals. You learn code the way you'll be using it—by SOUND. Complete course included at no extra charge. Used by many schools for teaching code. Low cost; easy terms. MONEY BACK GUARANTEE. Send now for booklet \$10, no obligation. Post card will do.

TELEPLEX CO.

72-76 Cortlandt St. New York, N.Y.

Be a TELEVISION EXPERT

First National's modernistic method of training is new and different. 75 profusely illustrated lessons in addition to COMPLETE APPARATUS for over 100 Radio and Television experiments will be given you—prepare you for employment in good pay Radio-Television field. You will also be qualified for the examination for your first class Radio-Telephone Operator's license. Get the facts! FREE—Write now for free 24-page booklet "Vision," describing this training.

FIRST NATIONAL TELEVISION (Training Division)
Dept. B-10 Fidelity Bldg. Kansas City, Mo.

RADIO ENGINEERING

broadcasting, aviation and police radio, servicing, marine radio telegraphy and telephony, Morse telegraphy and railway accounting taught thoroughly. Engineering course of nine months' duration equivalent to three years of college radio work. All expenses low. Catalog free. School established 1874.

Dodge's Institute, Turner St., Valparaiso, Ind.

RADIO INSTRUCTION

**THE Easiest WAY
THE Quickest WAY
THE Soundest WAY
TO LEARN CODE—**

THE CANDLER WAY!

Thousands upon thousands of operators—amateurs and commercial alike—have proved to their own satisfaction that the CANDLER SYSTEM for learning code is the easiest, quickest and soundest method. Why spend months in undirected practice when the Candler System will give you more real progress in a week? Candler teaches you the proper fundamentals, sound consciousness and mental coordination and in a short time you will find yourself receiving code as easily as you read print, and copying several words behind without conscious strain or effort.




Send for the FREE "Book of Facts" today, explaining the CANDLER SYSTEM, and containing many helpful hints on code. There is no obligation.

CANDLER SYSTEM CO.
Dept. S-10 ASHEVILLE, N. CAROLINA, U.S.A.



OMNIGRAPH CODE

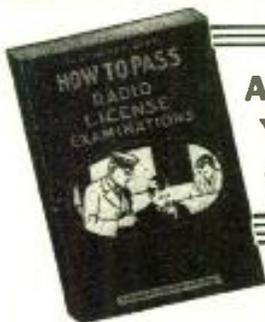Automatic sender teaches you easily. Thousands sold last 38 years. Metal Dials changed FREE. Models \$2 to \$25. Folder R. Omnigraph Mfg. Co., 810 East 39 St., Brooklyn, N. Y.



**Answers
YOUR
Questions**

DREW'S

HOW TO PASS Radio License Examinations

By CHARLES E. DREW, I.R.E., A.I.E.E.

This book is more than just a new edition of a famous work. It has been completely rewritten, and will serve as an excellent guide to all radiomen. Important phases of the subject are given thorough treatment, so that the man who understands the content of this book will be well qualified to pass the examination for his license.

Published March 1938 \$2.00

ON APPROVAL COUPON

John Wiley & Sons, Inc.
440 Fourth Avenue, New York, N.Y.

Kindly send me a copy of Drew's HOW TO PASS, on ten days' approval. If I decide to keep it, I will remit \$2.00; otherwise I will return the book postpaid.

Name

Address

City and State

Employed by

SWT10-38

What Price HAM Radio?

(Continued from page 337)

while one Ham operator spent \$900.00 on new tubes and tube replacements during the past year! So, between the two extremes of the well-financed Ham station owner and operator, and those in the lower brackets (the beginners and small station owners), there is a broad financial chasm.

Power of Average Transmitter

While the maximum power limit set by the Federal Communications Commission for amateur stations is 1000 watts, there are numerous small stations, such as those operated by beginners and others, that are rated at only 20 to 50 watts. Among the Hams who answered the questionnaire, 15% own 1000 watt transmitters; 1% each own 900 and 800 watt transmitters; 11% 500 watters; 3% 400 watters; 3% 300 watters; 7½% 250 watters; 10% 200 watters and 11% 150 watters. The balance is distributed over various values of transmitter power from about 20 watts up to 150.

Manufactured Versus Home-Made Apparatus

A surprising fact which the questionnaires showed was that the average Ham, if he can afford it, will purchase a good factory-made receiver. The tabulated answers showed that 60% own factory-built receivers. Of these, 35% own manufactured receiving sets costing \$175 or more apiece, while 8.6% have factory-built receiving sets which cost between \$200 and \$300 apiece; for sets costing \$100 to \$150 we find 36½%. The balance of the sets owned by station operators are the usual run-of-the-mill sets costing between \$30 and \$100.

When it comes to transmitters, 88% of the Hams questioned by the editors preferred to *build their own*, either by buying the parts separately or from kits; 8% own manufactured transmitters and the balance are of composite construction.

Antenna Kits—Phones—Test Equipment

Regarding antenna kits, 8% use transmitting antenna kits, such as the Johnson-Q. Most of the receiving aerials are home constructed and only about 1% use factory-made kits.

As to headphones, all of the leading makes are well represented in Ham stations. Leading with 22% are Baldwin phones. Trimm phones are next with 17%, Western Electric 11%, Brandes 10%, Brush 8%. (Of course this picture might be different, if all 46,000 Hams were questioned.—Ed.)

Only about half the Hams who answered the questionnaires own factory-built testing equipment (not forgetting the fact, of course, that most of the Hams probably own from one to a dozen meters which are "built into" their transmitters). Among the leading makes of measuring instruments used we find Triplett leading with 18½%, Weston 15%, Jewell 8%, General Radio 2½%, Supreme 2%, Westinghouse 1½%, RCA and Du Mont 1½% each, with a small percentage divided among the other well-known makes of testing instruments.

Battery Versus A.C. Operation

Ninety-four per cent of the Ham stations covered by the questionnaires are operated on 110 volt, A.C., while 6% are battery-operated.

Another interesting figure shows that 2½% of the Ham stations are shared by a YL (unmarried young lady); 7½% by an XYL (their wives); 13% share with another Ham, while 1% are "club" owned and operated stations.

All about the SHORT WAVE LEAGUE

A FEW WORDS AS TO THE PURPOSE OF THE LEAGUE

The SHORT WAVE LEAGUE was founded in 1930. Honorary Directors are as follows:


Dr. Lee de Forest, John L. Reinartz, D. E. Replegle, Hollis Baird, E. T. Somerset, Baron Manfred von Ardenne, Hugo Gernsback, Executive Secretary.

The SHORT WAVE LEAGUE is a scientific membership organization for the promotion of the short wave art. There are no dues, no fees, no initiations, in connection with the LEAGUE. No one makes any money from it; no one derives any salary. The only income which the LEAGUE has is from its short wave essentials. A pamphlet setting forth the LEAGUE'S numerous aspirations and purposes will be sent to anyone on receipt of a 3c stamp to cover postage.

FREE MEMBERSHIP CERTIFICATE

As soon as you are enrolled as a member, a beautiful certificate with the LEAGUE'S seal will be sent to you, provided 10c in stamps or coin is sent for mailing charges.

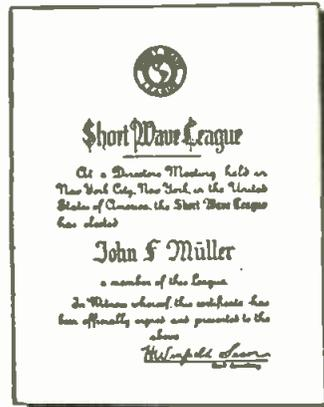Members are entitled to preferential discounts when buying radio merchandise from numerous firms who have agreed to allow lower prices to all SHORT WAVE LEAGUE members.



If you wish your name engraved on the Free membership certificate, as illustrated above, please send 25c to cover cost.

SHORT WAVE ESSENTIALS LISTED IN OPPOSITE COLUMN SOLD ONLY TO SHORT WAVE LEAGUE MEMBERS

They cannot be bought by anyone unless he has already enrolled as one of the members of the SHORT WAVE LEAGUE or signs the blank below (which automatically enrolls him as a member, always provided that he is a short wave experimenter, a short wave fan, radio engineer, radio student, etc.).

Inasmuch as the LEAGUE is international, it makes no difference whether you are a citizen of the United States or any other country. The LEAGUE is open to all.

Application for Membership SHORT WAVE LEAGUE

SHORT WAVE LEAGUE 10-38
89-101 Hudson Street, New York, N. Y.

I, the undersigned, herewith desire to apply for membership in the SHORT WAVE LEAGUE. In joining the LEAGUE I understand that I am not assessed for membership and that there are no dues and no fees of any kind. I pledge myself to abide by all the rules and regulations of the SHORT WAVE LEAGUE, which rules you are to send to me on receipt of this application.

I consider myself belonging to the following class (put an X in correct space): Short Wave Experimenter Short Wave Fan Radio Engineer Student

I own the following radio equipment:

Transmitting

Call Letters

Receiving

Name

Address


City and State

Country


I enclose 10c for postage and handling for my Membership Certificate.

FOUR NEW 10¢ RADIO BOOKS

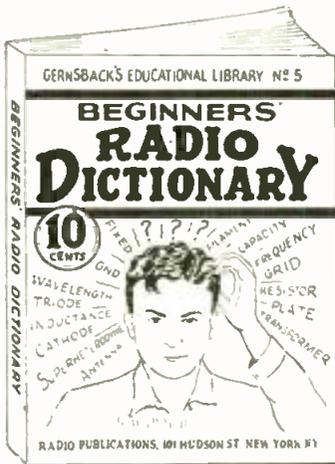RADIO FANS EVERYWHERE—these little ten cent text books give you an excellent foundation for the study of radio. They are clearly written, profusely illustrated and contain over 15,000 words in each book. You'll be amazed at the wealth of information these volumes have. They are handy for review or reference books.



**FAMOUS
GERNSBACK
EDUCATIONAL
LIBRARY**

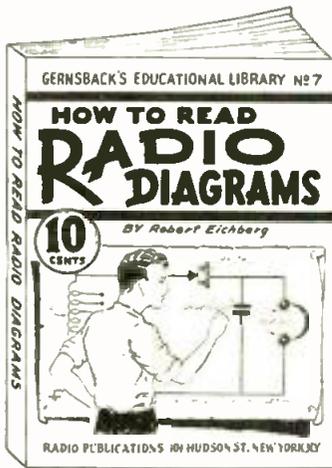


NO. 5—BEGINNERS' RADIO DICTIONARY

Are you puzzled by radio language? Can you define frequency? Kilocycle? Tetrode? Screen grid? Baffle? If you cannot define these very common radio words and dozens of other, more technical, terms used in all radio magazines and instruction books, you need this book in your library. It's as modern as tomorrow—right up to the minute. It tells you in simple language just what the words that puzzle you really mean. You cannot fully understand the articles you read unless you know what radio terms mean. This is the book that explains the meanings to you. Can you afford to be without it, even one day longer?

NO. 7—HOW TO READ RADIO DIAGRAMS

All of the symbols commonly used in radio diagrams are presented in this book together with pictures of the apparatus they represent and explanations giving an easy method to memorize them. This book, by Robert Eichberg, the well-known radio writer and member of the editorial staff of RADIO-CRAFT magazine, also contains two dozen picture wiring diagrams and two dozen schematic diagrams of simple radio sets that you can build. Every diagram is completely explained in language which is easily understood by the radio beginner. More advanced radio men will be interested in learning the derivation of diagrams, and the many other interesting facts which this book contains.

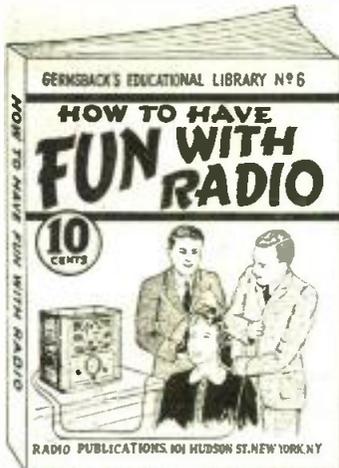

**ADDS
FOUR
NEW
BOOKS!**



NO. 6—HOW TO HAVE FUN WITH RADIO

Stunts for parties, practical jokes, scientific experiments and other amusements which can be done with your radio set are explained in this fascinating volume. It tells how to make a newspaper talk—how to produce silent music for dances—how to make visible music—how to make a "silent radio" unit, usable by the deafened—how to make toys which dance to radio music—sixteen clever and amusing stunts in all. Any of these can be done by the novice, and most of them require no more equipment than can be found in the average home. Endless hours of added entertainment will be yours if you follow the instructions given in this lavishly illustrated book.

NO. 8—RADIO FOR BEGINNERS

Hugo Gernsback, the internationally famous radio pioneer, author and editor, whose magazines, SHORT WAVE & TELEVISION and RADIO-CRAFT are read by millions, scores another triumph with this new book. Any beginner who reads it will get a thorough ground work in radio theory, clearly explained in simple language, and through the use of many illustrations. Analogies are used to make the mysteries of radio as clear as "2+2 is 4". It also contains diagrams and instructions for building simple radio sets, suitable for the novice. If you want to know how transmitters and receivers work, how radio waves traverse space, and dozens of other interesting facts about this most modern means of communication, this is the book for you!

Other Titles in This Series!

Four other volumes in this ten-cent radio book series—each on a popular subject—are available. The titles are:
No. 1—HOW TO BUILD 4 DOERLE SHORT-WAVE SETS
No. 2—HOW TO MAKE THE MOST POPULAR ALL-WAVE 1- AND 2-TUBE RECEIVERS
No. 3—ALTERNATING CURRENT FOR BEGINNERS
No. 4—ALL ABOUT AERIALS

BOOKS ARE ALL UNIFORM

Every book in the GERNSBACK EDUCATIONAL LIBRARY has 32 pages—with illustrations varying from 24 to 66 in number. Each title volume contains over 15,000 words. Positively radio's greatest book buys! If you do not think these books worth the price asked, return them in 24 hours and your money will be instantly refunded.

RADIO PUBLICATIONS
101 HUDSON STREET NEW YORK, N. Y.

MAIL COUPON TODAY!!

RADIO PUBLICATIONS, Dept. R&T-10-38
101 HUDSON STREET, NEW YORK, N. Y.

Gentlemen: Please send immediately, POSTPAID, the book numbers circled below. I am enclosing....cents—each book being 10c.

1 2 3 4 5 6 7 8

Send FREE listing of 48 new 10c publications.

Name

Address

City State

Remit by check or money order—register letter if you send cash or unused U. S. postage stamps.

Fourth Silver Trophy Award

(Continued from page 345)

at Columbia University taking an E.E. course. Got interested in radio about 10 years ago and progressed through the xtal sets, battery sets and the like. Got my ticket in 1934, and got on 160 phone with a pair of 59's, suppressor modulated. Since I was cursed with an experimental nature, the rig was rapidly rebuilt and torn down 19 times in one year! I tried suppressor, grid, and plate modulation, controlled carrier and tried out several antennas. I had the best luck with a 250 ft. center-fed job. We didn't use over 60 watts on 160. In 1935 I got my class A and stuck the rig on 14 mc. phone. As you can guess, the parallel 46's didn't put out much, so the rig was ripped down. I rebuilt it 9 times before I was satisfied! I tried 46's, an 825, 203A, 242A, 211, 852, and finally ended up with the 805. After this I got ideas on oscillators and tried all of 'em. After I blew up a couple of xtals with hi-powered oscillators, I decided the 41 pentode oscillator was best. I messed around with buffers, and finally stuck in a RK39 as a doubler with 600 v. on it. It works wonderfully, and I can drive the 805 to 50 grid mills. During this time I messed around on 56 mc. with W2HXD (he heard the five meter sigs of G5BY a few years ago). I also tried 20, 80, and 160 c.w.

The receiver has only been changed about five times, but it seems to be OK now.



That's about all there is about the station. I've handled a little flood tfc. (traffic) and took messages from the "Morrisey," W1OXDA, but I don't regularly do much tfc. handling. My main interest, when the rig is in working order, is to experiment with antennas and work DX on phone.

Just thought I'd let you know about S.W.&T. I've been reading it since it came out every other month. Remember?

What Do You Think?

(Continued from page 344)

2:17 a.m. PST so I'm hooking up with a Canadian friend, a 200 watter, who comes in here like a house afire! I take in my antenna when I have him out! (Say, a lot of us are fair liars too.) But I get good reception here year around; east is good too. We, my pardner and I, are busy day and nite; not much money, but boy we "go to town" anyway. We trade around quite a lot and borrow each other's stuff.

Say, "ed," pardon me taking your time to spill the ink, but I thought I should tell you what S.W.&T. has meant to us here on the west coast. Through your magazine, I've bought other publications too.

A photo of the shack soon—it's somewhat "tore up" at present, so the delay is necessary.

M. E. VAN NATTAN,
6151 Walnut Ave.,
N. Long Beach, Calif.

Prize of 1 year's subscription to *Radio & Television* given each month for best "listening post" photo.

Short Wave League — On the Ham Bands

(Continued from page 342)

Call	Freq.	R	S
James R. Wood - Observer for Minnesota			
V'S6AG	14.084	4	6
Howard Kemp - Observer for Connecticut			
EA9AH	13.99	4	6
K6KPM	14.22	3	4
F8FN	14.07	4	6
EI6G	14.40	3	4
VR6AY	14.34	4	5
F8MA	14.12	3	4
ZS1AA	14.09	3	4
F8VP	14.10	4	4
F8NT	14.08	4	6

Call	Freq.	R	S
M. J. Markson - Observer for Colorado			
CE1AG	14.040	5	4
CE1BC	14.350	5	5
KA1ME	14.230	5	4
KA2OV	14.230	4	5
KA1HF	14.225	5	5
K6OQE	14.230	5	6

Call	Freq.	R	S
L. F. Gallagher - Observer for New York			
FA8CC	14.120	5	6
FA3HC	14.280	4	7
XU8RB	14.080	4	6
OZ5G	14.300	5	7
OZ3U	14.340	4	6
PK1PK	14.030	3	7
SU1RK	14.330	4	6
SU1CH	14.390	5	8
ZT6P*	14.265	3	6
SM5SD	14.270	5	7
YR5KW	14.120	5	6
KA1MG	14.310	4	7
SP1CC	14.340	4	8
VR6AY	14.350	5	7
LA8C	14.125	5	7
SV1KE	14.300	4	7
HA8N	14.125	5	9
VU2LL	14.340	4	7
VU2CQ	—	5	7
HKN	14.360	4	7
J7CB	14.310	4	6
CN8AM	14.090	5	7
CN8AU	14.130	4	7

*The QRA of this station is in doubt in the mind of "yours truly." Will someone write and tell me where it is?

Call	Freq.	R	S
PK6XX	14.200	—	8
KA3AA	—	—	—
KA7EF	14.70	—	7
KA1CS	14.75	—	8
ZK1AA	—	—	—
J7CR	—	—	6

Excellent results on the five meter band have been reported by Owen Shepherd, Jr., who is Observer on five meters for the State of Connecticut. This is the only band which Owen is working under the call of W11J. During the month of July, he has reported as hearing every district in the United States except the 7th. In Canada, he has received stations in the 3rd and 9th districts. We wish to congratulate W11J upon his accomplishments on the five meter band, and we hope that he will continue to show reports like the one received here last month. Part of his report is as follows:

W4EDD	8.4	CSU	5
FLH	5	EKI	4
AUC	3	ML	4
W5ZS	4	W6DNS	7

"Yours Truly" - Observer for New York

W1OXDA	14.350	5	7
F3OX	14.155	3	5
PAODGA	14.200	4	9
K4ENT	14.255	4	5
OA4C	14.345	3	5
F3HM	14.165	4	7
EI2L	14.100	5	7
ON4AM	14.210	5	7
K4ENY	14.237	3	8
LU4AD	14.210	5	6

Charles H. Fuller - Observer for New York

HH2B	14.155	5	8
HK3LC	14.200	5	9
PY5BL	14.200	5	6
LU8AB	14.150	5	6

In order to reduce the reports to include only real, good dx, the following distances have been decided upon, to be considered in publishing these reports. There is no need in reporting stations which may be heard at almost any time of day or night. For the 160 meter band, 1000 miles has been set as the minimum distance, and for the 80 meter band, 1500 miles. For the 20 meter band, 2000 miles has been established and the same distance for the 10 meter band.

Once more, may I remind you to include the approximate frequency, readability, and signal strength in your reports.

The Life of a Busy Ham

(Continued from page 339)

the local hams dropped in about two o'clock, to find out how the "rig" had been working, and upon seeing the log from 7:01 p.m. to the present time, 2:05 p.m. they knew that the transmitter was at least working across the ocean!

Three o'clock and once again I was alone, ready to start all over again. Back over the band again, but many attempts to contact someone proved unsuccessful. I began to look over the rig, to make sure everything would be in order for this evening. A few slight alterations and everything was completed. Leaving instructions to wake me up for supper, I went to bed. Six o'clock and supper on the table. After a hurried meal I rushed downstairs and again put the transmitter and receiver on, got out the call book, log book and scrap pad, sharpened half a dozen pencils, and prepared for the evening ahead of me. I began by working Cuba, South America, Ireland and the Netherlands—all within the next hour.

Seven o'clock rolled around and with it the end of one of the busiest twenty-four hours of activity I had experienced for a long time.

Call	Freq.	R	S
Clarence Hartzell - Observer for Pennsylvania			
F8AF	14.075	3	5
F3OX	14.078	4	7
PAQMZ	14.038	4	5
VK4VD	14.148	5	7
VK2UC	14.134	4	6
EA9AH	13.996	5	9
FA3HC	14.105	3	6
PK1MX	14.300	2	4

Call	Freq.	R	S
Edmond H. Davenport - Observer for Vermont			
VK2ABK	—	4	6
CT1ZZ	14.050	4	6
SU1KG	—	3	4
VP3WA	14.150	5	7

Call	Freq.	R	S
Robert Hatcher - Observer for Virginia			
ZB1R	14.050	—	7
AC4AN	—	—	5
FA3HC	—	—	7
TF3C	—	—	6
FA8HT	—	—	6
AH2BU*	14.410	5	8
ZD2B	—	—	—
ZB1R	14.410	3	5
ZB1R	14.410	5	7
ZC6AQ	14.020	5	7

*This is also a new one to yours truly and I would like to have its QRA from someone.

for October, 1938

Please say you saw it in RADIO & TELEVISION

SPRAGUE ATOMS

"Mightiest Midgets of All"



SAVE
Time...
Money.
Space!

Actual size of an
8 mfd. 450 V. ATOM.
List price only 60c.
Others equally low.

Use Sprague ATOM Dry Electrolytic Condensers for those jobs where you've got to save space—where you've got to install a really good, honestly reliable condenser at a rock-bottom price. ATOMS are made by an exclusive Sprague etched-foil process that guarantees highest quality. No "blow-outs"—not a "firecracker" in a carload! Made in all std. capacities including DUAL COMBINATIONS. Just the thing for "duplicate" replacements. You save real money—and you get the finest, most dependable midget condensers on the market today. Featured by leading jobbers singly or in handy kits.

Write for Free Catalog

SPRAGUE
450 VOLTS

SPRAGUE
PRODUCTS CO.
North Adams, Mass.

CASH IN

ON YOUR SPARE TIME!

300 WAYS
TO MAKE
MONEY

ONLY
25c
Per Copy

68
PAGES

Cash In!

MAIL ORDER PLANS
TESTED MONEY MAKERS
BUSINESS SECRETS
SUCCESS SCHEMES

25
CENTS

SOLD ON A
MONEY-BACK
GUARANTEE!

BRAND
NEW
BOOK
40,000 WORDS
in TEXT!
In "CASH IN"
you get ALL
the real money-
makers — dozens
of profitable tested
mail order plans,
confidential business
secrets, dozens of prac-
tical tested formulas, suc-
cessful tested schemes—actual experiences
of men who have started on a shoestring
—with less than \$10 capital.

Buyers of This Book Tell Us—

... "Biggest value I've yet to see. Book is worth at least a dollar." S. BUDA, B'klyn, N. Y.
... "Your book is as good if not better than others selling at \$1.00."

GEORGE BRUNET, Montreal, Can.

... "CASH IN is the best value I have yet to see in the mail order field."

LAWRENCE FOX, Brooklyn, N. Y.

"CASH IN" contains only tested ideas covering every type of full—or spare-time enterprise—it's a "masterpiece" in business ventures. 25 CENTS per copy. Sent POSTPAID anywhere upon receipt of 25 cents U.S. stamps or coin.

NATIONAL PLANS INSTITUTE
246-T FIFTH AVENUE NEW YORK, N. Y.

himself; otherwise, he can contact almost anyone in the radio line to help, especially if you happen to be a shut-in."

"Even though arthritis has made it virtually impossible for me to move around," said Pop, "I still manage to work my fingers and with them I am able to press buttons. And so when I wish to go on the air I snap the button just below the microphone. Should anything go wrong with the set, it is so constructed that it shuts off automatically. There really isn't much to operating it, but never-the-less one needs a background for it. While all the building was taking place, in the meantime I was busy being taught the ABC's of shortwave. I listened intently to the boys whenever they made the slightest remark related to this field. I read several text books and after about 11 months of study I thought I was sufficiently prepared to take a test for a short-wave operator's license."

"They certainly must have had a swell time carrying your bed up the stairs leading to the Federal Communications Commissioner's office when you went to take your test," I commented.

"Why, no. I didn't even have to leave the house. I simply wrote to the Commission stating that I would like to take a test, but that I was a shut-in. And so I filled out a Class C application, which signifies that a person is unable to come down for the examination; therefore, the Commission sends an amateur out to your home to give you the test—that is if you live within a radius

The World Comes to My Room

(Continued from page 336)

of 100 miles. There is no expense involved in taking the test."

Continuing, he says, "And now you come to the point where you face the music. You have your set; you've been studying pretty hard, and now the test. Two sentinels guard the sacred entrance. They stop you and ask, 'Halt who goes there?' The first one is the code—which requires one to be able to take the Continental Morse Code at 13 words a minute. You must pass this in order to take the next step—a question and answer quiz to determine whether or not you are thoroughly acquainted with the mechanical parts of a transmitter. If you are successful in both, the sentinels step aside and cheerfully utter, 'You may pass.' But sometimes these tests are like big trailers out on a highway—you fail to pass them and I fell into this category. But shucks, after one waits three months, he can try again."

Conducts "Coal Business" by Telephone

Brring! Brring! It's Pop's telephone—a cradle type that is affixed to a bracket. When this bracket spreads out towards him, the receiver comes to rest at a point slightly over his ear and the mouthpiece at an angle below his chin. This eliminates the holding


of the telephone, which he is unable to do. The call happened to be an order—a coal order. For while radio is his hobby, he never-the-less keeps abreast in business. At first he used to sell post cards, automobile polish and several other items, but now a sign out on his porch reads, "Coal orders taken." During the past few years he has built up a lucrative business.

Thrilled by First "Out-of-Town" Contact

"And the stirring interest in getting your first out-of-town station; and then those from other states. I felt chills go up and down my spine. Here I was lying in bed, talking to a fellow away down in Texas hundreds of miles away, who perhaps may be a wealthy ranchman or just a cow rustler. A half hour later I tuned in a lad in Alabama, who earns his bread pickin' the little balls of cotton."

In addition to broadcasting over his amateur station, Pop has also been on the air over a commercial station WJAY (now WCLE), Cleveland.

Shut-ins and other listeners bombarded the station with letters and cards. They had found a leader. They liked to listen to his advice and all agreed that it was an inspirational program. Pop's card file has increased steadily and he has added people from all walks of life to his list, including such celebrities as Gene and Glenn, radio stars, Joe E. Brown, Tony Wons and many others.—Courtesy OUTWITTING HANDICAPS MAGAZINE.

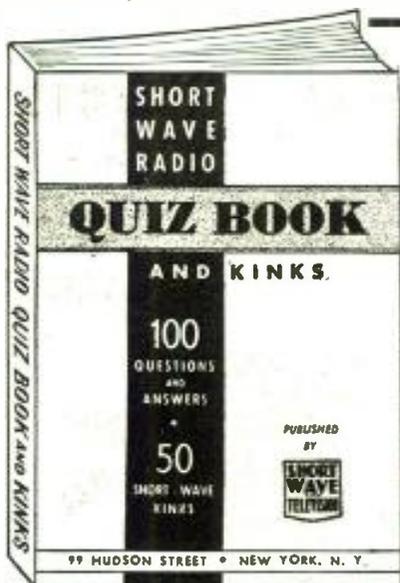

FREE BOOKS—AND HOW YOU

CAN GET THEM!

HERE is a brand new book—with an unusually interesting content. The text—prepared by the Editorial Staff of RADIO AND TELEVISION, contains a variety of material which only experts could select and incorporate in such an excellent volume.

"SHORT WAVE RADIO QUIZ BOOK AND KINKS" cannot be bought—it is sent to you absolutely FREE with your subscription to RADIO AND TELEVISION at the Special Rate of Seven Months for One Dollar. (Old subscribers may get this book by extending their subscription.)

The book contains 64 pages with a heavy flexible colored cover. It measures 5½ x 8½ inches, and includes hundreds of photographs and diagrams. The contents are outlined below.

Contents of the "QUIZ BOOK"

Questions and Answers Covering S-W transmitters.
Questions and Answers Covering S-W Receivers.
Ultra-Short-Wave Transmitters and Receivers.
S-W "Kinks"—Short-cuts and Practical Wrinkles, Coil Winding Data.
How to Add an Audio Amplifier to a Small S-W Receiver.

How to Connect an R.F. Stage Ahead of Your Present Receiver.

Dozens of Novel New Hook-Ups for the S-W Experimenter.

Clear diagrams showing how to connect the latest type tubes in place of your old tubes, so as to obtain greater DX.

HOW TO "HOOK UP"—

S-W Converters
Noise Silencers
Power supplies
Modulators
Beat Oscillators
Antennas
Pre-selectors
5-meter receivers

2 Other FREE Books

ABC OF TELEVISION



Contains latest material on Television developments. It covers theory of scanning; simple television receiver, how the eye sees; the photo-electric cell; neon lamps; need for broad channel width in transmission of high-fidelity television signals; cathode ray tube and television receivers; Farnsworth system of television transmission, and other important features.

SHORT WAVE GUIDE

Covers hundreds of Short-Wave questions and answers; illustrates popular Short-Wave kinks; gives instructions for building simple Short-Wave receivers; instruction on the best type of antenna to use; diagram and construction details for building a simple "ham" transmitter; practical hints on Short-Wave tuning.



RADIO AND TELEVISION • 99 Hudson Street • NEW YORK, N. Y.

RADIO AND TELEVISION, 99 Hudson Street, New York, N. Y.

Gentlemen: Enclosed you will find my remittance of \$..... for which enter my subscription to RADIO AND TELEVISION as checked below; also send me, postpaid, the book or books which I have marked at the right.

7 months—\$1.00—choice of any one of three (3) books. (Canadian and foreign—\$1.30)
 14 months—\$2.00—choice of any two (2) of the three (3) books. (Canadian and foreign—\$2.60)

21 months—\$3.00—all three books. (Canadian and foreign—\$3.90)

If you are a subscriber now, we will extend your present subscription.

New subscriber Old subscriber

Name..... Address.....

City..... State.....

Send your remittance by check or money order. If you send cash or unused U.S. postage stamps, please be sure to register your letter for your own protection.

- S.W. RADIO QUIZ BOOK AND KINKS
 ABC OF TELEVISION
 SHORT WAVE GUIDE

R&T-1038

Let's Listen In with Joe Miller

(Continued from page 347)

registered, with return receipt, elicited a reply from the commercial phone's offices, and we were assured our report would be passed on to the Amateur Society. Sure enough, 2 weeks later we received ZGE's card!

QSL states frequency is 6.135 mc. (tho now 6.24 mc.), and schedule is Tues., Fri. and Sun., 6:40-8:40 am. EST.

DX GOSSIP

ZHP, Singapore, has now changed to 9.68 mc., where it is heard almost daily up to 9:45 am. by Ashley Walcott, W6. Look for this catch.

JAPAN—JZL, 17.785 mc., Nazaki, is heard daily, 6-6:30 am., while **JVH**, 14.60 mc., is reported on Sats. at 11 pm. transmitting baseball.

PAPUA—VHPM, using freqs. of 8.08 mc. and 6.54 mc., at Port Moresby, has been reported testing between 5:30-6:30 am. Here is a real dx catch, and a new country for all, so keep a sharp watch for it, daily.

INDIA—VVX, 13.35 mc., Fort St. George, heard calling VVS, in Burma, with a very strong signal, at 6 am. but VVS, tho on, did not reply.

CHINA—LATE FLASH—Roy Myers, W6, reports a Shanghai fone on 15.46 mc., working in clear speech with JVE, 15.66 mc., 4-6 am. As speech from Shanghai is also Japanese, transmitter must be operated by Japanese occupants of Shanghai.



ASIA

Asiatic ham sigs died down during these hot months, but we look with the certainty of past experience to a very decided improvement for the PK's, VS's, and KA's, etc., beginning with Sept., and continuing throughout the cool months.

Many FB catches are reported from the West, where dxers log those rare 'uns, undaunted by varying seasons, due to their proximity to those coveted dx signals.

Those reported from Asia are:
BURMA: XZ2EX, "England-Xray," 14060; **XZ2PB**, "Portugal Boston," 14035; **XZ2DX**, "Denmark-Xray," 14045; **XZ2EZ**, 14350, by Roy Myers, Max Fisher, and Jas. Moore, W6.

CHINA: XU6TL, 14120; **XU8ET**, 14160; **XU8RJ**, 14110 and 14340; **XU8AM**, "America, Mexico," 14080; **XU8RB**, 14100; **XU6DL**, 14000. **XU8RB** QSLs here with 2 FB QSLs and a very courteous 6 page letter, relating his most interesting experiences in China, which we cert wish we could describe here, but would require far

more space than we could command. Many tnx, Reggie, OB, for ur FB reply, and best o' luck to you out there!

HONGKONG: VS6AG, 14090; and **VS6AF**, 14300, reported. In the Federated Malay States, **VS2AE**, 14360.

PHILIPPINES: KA1YL, H.F. 20 m.; **KA1MH**, 14200; **KA1FH**, 14100; **KA4LH**, 14100; **KA7EF**, 14150; **KA3DT**, 14228, last by Ye Ed.

JAVA: PK4JD, 14010, Sumatra; **PK3AA**, 14360; **PK1JR**, 14300; **PK2JN**, 14310; **PK1VY**, 14270, with a V-beam on America, and, of course, **PK6XX**, located at Hollandia, Netherlands New Guinea, which station is well heard all over the U. S., and uses a 1 kw. rig, which they may vary during tests, as on one occasion when power was altered between 25 watts and 1 kw.

A rotary beam is used, 1/2 wave long, and also a V-beam, 465 feet long, stretched over the water. Operator is **W2BVB**, Harold Ramm. Frequency ordinarily used is 14020, but also heard on 14190. Commercial frequency are 11.355 mc. and 6.425 mc.

The station is used by its sponsor, the *Archbold Expedition* of the American Museum of Natural History, to keep in constant communication with the museum "H.Q." in the U. S. QSL cards are not available, and anyone reporting them risks failure. Reports can be sent to ARRL "H.Q." or to **W2BVB's** home QRA, but no guarantee of a QSL is made.

French Indo-China offers **F18AC**, 14070. Straits Settlements: **VS1AI**, 14090; **VS1AF**, 14070; **VS1AB**, 14060.

Murray Buitekant reports a QSL from **VS7RF**, Ceylon, a FB "dx" catch for a **W2!** Congrats, OM!

7 MC.: Ashley Walcott reports some unusual dx in the way of Javanese 7 mc. fones, heretofore unreported by a U. S. dxer. Listed are: **PK3WI**, 7010; **PK3GD**, 7040, 7120, 7200, 7260; **PK1MO**, 7280; **PK1SK**, 7030-7070; **PK1PK**, 7020. All speak in Dutch only, on this band. Congrats, Ashley, on some FB "dx"!

NEW GUINEA: VK9WL, 7090, reported by Ashley, along with many other Aussie VK's on this band.

GILBERT & ELLICE ISLANDS: VRIAR and **VRIAS**, both located in this group of islands, reported by Ashley, working each other on 7.00 mc., often near 3 am.

3.5 MC.: From New Zealand, Ashley reports the following FB dx on this unusual dx band: **ZL2BN**, 3964; **ZL2BE**, 3900; **ZL2BT**, 4000; **ZL2NP**, 3830; **ZL3AY**, 3630; **ZL1GZ**, 3987; **ZL2JT**, 3780; **ZL3CV**, 3530. Ashley adds hearing several VKs on this band, and even a Russian fone. Some real dx there!

AFRICA


CR7MF, L.F. 20 m., variable freq., reported by Roy Myers, announcing as "Mexico France." This is a rare catch, from Mozambique.

From South Africa: **ZS5AW**, 14100; **ZS2DY**, 14360; **ZS1BL**, 14370; **ZS1AX**, 14250; **ZS2EF**, 14080; **ZS6ED**, 14010. From Southern Rhodesia, **ZE1JR**, 14350.

Not much from Africa this month. Asiatic and African reports are courtesy of: Ashley Walcott, Roy Myers, Max Fisher and Jas. Moore.

A new country on 20 m. fone is French Guiana, where **FY8AC** is located. Ye Ed was fortunate enough to log OM **FY8AC** on his very first fone QSO, and he is the first **FY8** to go on phone. The card illustrated this month was promptly mailed to us for our report.

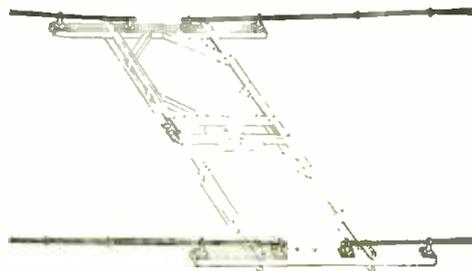PK4DG—SUMATRA—This FB Ham QSLs with a nice card, red lettering and border.



Rotary Beam Kits At a Price You Can Afford

PREMAX CORULITE ROTARY BEAM ANTENNA

FOR 10 AND 20 METERS


Tremendous gain in power transmitted in a given direction over ordinary type of antenna; marked increase in received signal; great reduction in unwanted signal; simplest construction; universal utility; better than average efficiency. Recommended because of outstanding performance at **W2AZ**, **W2GYL**, **W3CHO**, **W2DKJ**, **W8JK** and other stations.

Fully telescoping; meets all amateur requirements. Kit contains 4 17 1/2-ft. telescoping Corulite Elements, 8 combination mounting brackets and soldering lugs, complete drawings and a comprehensive bibliography of directional arrays, matching sections, transmission lines, etc. Length, collapse, 6 ft. Weight 10 lbs. See your jobber or write direct.

PREMAX PRODUCTS
DIV. CHISHOLM-RYDER CO., INC.
3854 HIGHLAND NIAGARA FALLS, N. Y.

Westinghouse Power Generator

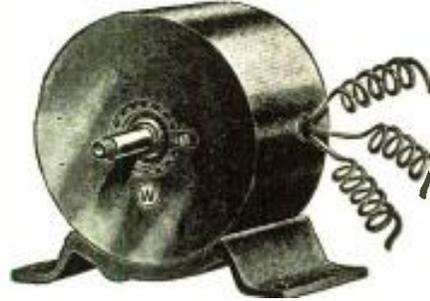Manufactured for U. S. Signal Corps
200 Watt. 110 V. AC



A. C. ELECTRICAL POWER

from a Windmill, from available Waterpower, from your Automobile, from your Motorcycle, from your Bicycle, Foot-Pedals or Handcrank (for transportable Radio Transmitters, Strong Floodlights, Advertising Signs); do you want to operate AC Radio sets from 32 V. DC farm light systems; operate two generators in series to get 200 V. AC; obtain two phase and three phase AC, etc., etc.

There Are Over 25 Applications

Some of which are:
A.C. Dynamo lighting from eight to ten 20 Watt 110 Volt lamps. Short Wave Transmitter supplying 110 Volts AC for operating "Ham" transmitter. Operating 110 V. AC 60 Cycle Radio Receiver in DC districts. Motor Generator. Public Address Systems. Electric Sirens on motor boats, yachts, etc. Camp Lighting. Short Wave artificial "fever" apparatus. Television. Pelton Waterwheel for lighting or other purposes. Airplane: for lighting strong searchlights or electric signs. Laboratory work, etc., etc. 1/4 to 1/2 H.P. needed to run generator.

BLUE-PRINT 22 x 28 in. and Four-Page 8 1/2 x 12 in. INSTRUCTION SHEETS FREE with Generator.

Generator, as described, including four replacement carbon brushes. Blue-print and instructions **\$7.90**

Send \$2.00 deposit, balance C.O.D. Shipping weight 18 lbs. (Replacement carbon brushes bought separate \$1.50 per set of four. Set of instructions bought separate \$1.00.) MONEY-BACK GUARANTEE

WELLWORTH TRADING COMPANY
560 West Washington Blvd. Dept. SW-1038 Chicago, Ill.

COMMERCIAL NOTICES 10¢ A WORD

Under this heading only advertisements of a commercial nature are accepted. Remittance of 10c per word should accompany all orders. Copy should reach us not later than the 10th of the month for the second following month's issue.

AGENTS WANTED
300% PROFIT SELLING GOLD Leaf Letters for Store Windows; Free samples. Metallic Co., 440 North Clark, Chicago.

CLUBS
JOIN NOW — MEMBERSHIP Card, Copy Membership Directory, Listing in next issue, 20c. Universal All-Wave League, P. O. Box 8393, Pittsburgh, Pa.

CORRESPONDENCE COURSES
500,000 USED CORRESPONDENCE Courses and Educational Books. Sold, Rented, Exchanged. All subjects. Satisfaction guaranteed. Cash paid for used courses. Complete details and bargain catalog free. Send name. Nelson Company, 3485 Manhattan Building, Chicago.

INSTRUCTION
RADIO ENGINEERING, BROADCASTING, aviation and police radio, servicing, marine and Morse telegraphy taught thoroughly. All expenses low. Catalog free. Dodge's Institute, Colt St., Valparaiso, Ind.

AMATEUR RADIO LICENSES. home study course in code and theory. Reasonable, efficient and thorough. Results guaranteed. American Radio Institute, 200 Broadway, New York, N. Y.

MISCELLANEOUS
3/4 INCH TR. 0-125 VT. A.C. Voltmeter, 0-10 A.C. Ammeter, \$2.75 each, Weston D.C. 0-7 and 0-140 Voltmeter, 2 1/2" with 9 pt. D.P. Switch \$2.75. Nat'l. MB27-4 Stg. T.R.F. chassis and Thord. 45 J.P. Pack, \$7.50. 10" MUTER DYN. SPKR. \$3.00. Victor 73" Hi-Fi Orthophonic Horn, Mag. and Acoustic Pick-ups, \$10.00, plus express. \$400.00 RCA battery Superhet—\$25.00. Harry Ackerson, Ramsey, N. J.

WE OFFER SUBJECT TO PRIOR sale 7 mm lacquered cable used by the Government. It is an ideal cable for high voltage, low current service, such as used in radio transmitters, amplifiers, etc. It is a special steel wire, 20 gauge, with very heavy rubber insulation. (Worth 12c a foot. Special price 50 ft. \$2.00, 100 ft. \$3.00. F.O.B. N. Y. Gold Shield Products, 350 Greenwich St., New York City.

PATENT ATTORNEYS
INVENTORS—PROTECT YOUR rights before disclosing your invention to anyone. Form "Evidence of Conception"; "Schedule of Government and Attorneys' Fees" and instructions sent free. Lancaster, Allwine & Rommel, 436 Bowen Building, Washington, D. C.

SONG POEMS WANTED
WANTED ORIGINAL POEMS, songs for immediate consideration. Send poems to Columbian Music Publishers, Ltd. Dept. K49, Toronto, Can.

QSL-CARDS-SWL
100 NEAT SWL CARDS PRINTED with your name and address sent post-paid for \$1. Bunch of samples and RST Chart for five cents in stamps. W1BEP, 16 Stockbridge Ave., Lowell, Mass.

SHORT WAVE LISTENER'S AT-tractive reply getting cards, QSLs Samples (Stamps). W-8-E-S-N, 1827 Cone, Toledo, Ohio.

RADIO EQUIPMENT
FOR SALE—ONE 60 WATT WEB-ster amplifier used four months \$110.00 Also transmitter and receiver parts of all kinds. Write us your needs. Keith Sound Service, Newton, Iowa.

RADIOS
BARGAINS—5 tube new radio complete with dynamic speaker \$3.95. 7 tube Superhet 12 1/2 to 35, 34 to 120 180-550 meters \$14.95. Values cannot be duplicated. Fully guaranteed. I. G. Young, 127 Liberty St., New York.

SHORT WAVE RECEIVERS
USED DOERLE'S, D-38, BS-5, 7C reconditioned by factory, 40% off. See January Short Wave & Television for description. Kusterman, 68 Barelay St., New York.

PLANS 18 DISTANCE RECORD Crystal Sets—with "Radiobuilder"—Year, 25c. Laboratorles, 7700-A East 14th, Oakland, Calif.

FOR SALE (NON COMMERCIAL) 3¢ A WORD

Under this heading we accept advertisements only when goods are offered for sale without profit. Remittance of 3c per word should accompany all orders. Copy should reach us not later than the 10th of the month for the second following month's issue.

USED C.T.S. AIR CONDITIONING Course for sale at \$2.95. Information gladly supplied. Wacker, 3727 West 13th, Chicago, Illinois.

SW3 \$9.00. SKY BUDDY \$17.50. Silver 5C \$29.00. Ireting 12 \$39.00. W9ARA, Butler, Missouri.

SELL BATTERY RADIO WITH two tubes and batteries \$6.25. Alfred Niemi, 220 East Spruce St., Chisholm, Minnesota.

FIRST \$30 TAKES EFFICIENT 60 watt transmitter, tubes, coils, power

supply, crystal. W3FLY, 3418 North 21 Street, Philadelphia, Pennsylvania.

2500 MILE CRYSTAL SET KIT \$1.00; metal tube receiver kit \$2.00. Information on request. Weingarten, Saugus, Calif.

BARTER AND EXCHANGE — FREE!

NO ADVERTISEMENT TO EXCEED 35 WORDS, INCLUDING NAME AND ADDRESS

Space in this department is not sold. It is intended solely for the benefit of our readers, who wish to buy or exchange radios, parts, phonographs, cameras, bicycles, sporting goods, books, magazines, etc. As we receive no money for these announcements, we cannot accept responsibility for any statements made by the readers. Use these columns freely. Only one advertisement can be placed. Copy should reach us not later than the 10th of the month for the second following month's issue.

accepted from any reader in any one issue. All dealings MUST be above board. Remember you are using the U. S. mail in all these transactions and therefore you are bound by the U. S. Postal Laws. Describe anything you offer accurately and without exaggeration. Treat your fellow men the way you wish to be treated. We welcome suggestions that will help to make this department interesting and helpful to our readers.

HAVE RADIO PARTS, MAGAZINES—Open Road, SW Craft, SW&T, Radio-Craft, Modern Mechanics, and stamps. Want receiver (3 or more tubes) or F. H. Frantz, 30 N. 4th St., Coaley, Pa.

HAVE 7J ELGIN POCKET WATN slightly used. Will trade for model gasoline engine. Have 8" Utah spkr. with rectifier, also radio parts and new tubes, what have you? Send description. Elthue Thompson, Kosciuszko, Miss.

TRADE PHONOGRAPH PLAYER, record container compartment, Webster pick-up, 20 meter Billye crystal, or what do you want for good dynamic microphone or small portable transmitter. Carl A. Kowalski, 1239 Kingsmoor Ave., Fort Wayne, Ind.

WANTED—FIVE METER TRANSCeiver, small 20 meter transmitter, 16mm projector, or photography equipment. Have complete NST taxidermy course, 10 copies Short Wave (craft), Television, new speaker unit, radio parts. John Antonio, Box 33, Elkland, Penna.

WILL SWAP WINCHESTER model 67—22 rifle, or Springfield 20 Gauge shotgun, both in A-1 condition, for good candid camera with fast shutter. Trade either or both. Ray Cecil, Winters Lane, Cold Springs, Kentucky.

HAVE CUSTOMBUILT CRYSTAL controlled transmitter; receivers; dynamic speaker; extra parts; coils; books; World War relics; other things. Want: World War relics, candid cameras, typewriter or 1st Lt. W. DeVere Johnson, 1115-68 St., Kenosha, Wis.

HAVE: 21" BAYONET, GEAR shift clock, pedometer, Sheffield hunting knife, electric table stove, cost \$12.00, burglar alarm for car, For: binoculars, Civil War sword, cap and ball Colt, no parts, stamps, coins. R. Linville, 147 Vienna Ave., Niles, Ohio.

WANTED: ALL KINDS OF MODERN test equipment. Buy or trade. Have 44 QST magazines from 1930 to 1934. Have DeVry model K-1 snapshot camera. Send full particulars. C. Fortler, 368 Besserer, Ottawa, Ont.

TRADE DOERLE 7C 5 TUBE receiver, 9 1/2-1500 meters, 2 months old; for a 4 or 5 tube 5 meter transceiver. Frank Hamill, Hixson, Tennessee.

TRADE—PATTERSON ALL WAVE projector for what. Trade 48 acres Michigan Lake land for Scott 30 tube or McMurdo Silver Masterpiece V.I. receiver. Don Newbold, 218 Locust St., Akron, Ohio.

TRADE: NEW 6" PHOTOELECTRIC cell complete in metal cabinet with power supply, tubes, and relay, cost \$40.00; 1907 to 1909 newspapers; stamp collection 1200 different; magazines; for crystal, xmitter, or parts. George Brown, Carnesville, Ga.

WILL TRADE KEYSTONE 16 MM projector, 15" dynamic speaker and over 2,000 U.S. and foreign stamps for a good complete 3 or 4 tube SW receiver. A. Conlin, 83 Westfield Rd., Holyoke, Mass.

NEW ZEISS IDEAL B 6" F:4.5 lens, tripod, filter, pan, tilt head, lights, changing bag, daylight tank, \$180.00. Want short wave receiver same value. Bert Kavanaugh, 516 West 136 St., N.Y.C., N.Y.

WANT—PORTABLE TRANSCeiver, power tools, 3x5 printing press. Have—Wollensack 250 power microscope, sporting goods, old U.S. coins, mounted specimens of Adirondack wildlife to offer. Vern A. Scharf, St. Regis Falls, New York.

FRESHMAN 5-TUBE MASTER-piece, Freed-Eisemann 0-tube set, 1-tube battery set. Freed-Eisemann speaker, headphones, tubes, parts, 4x5 printing press, 25 golf clubs. Trade for anything equal value. E. G. Bartlett, Atlanta, Mo.

HAVE WOOD AND METAL working tools, QST's, Radio News, Radio Eng., I.C.S. course in Radio, book Principles of Radio by Kinney. Want 8 or 16 mm movie apparatus. F. W. Johnson, Antwerp, Ohio.

WANTED: USED BILLEY CRYSTALS in perfect condition. State type, frequency, and lowest price. Also will swap 3 tube 5 meter receiver. Glenn Godwin, W8QHX, 5 Mildred Ave., Binghamton, N. Y.

WILL TRADE FULL SIZE VIO-lin, value \$65.00, original oil paintings by professional artist, for ham equipment. W9IMJ, 616 N. Central Ave., Chicago, Ill.

HAVE: WURLITZER GUITAR, boy's books, mounted pheasant. Want: Beagle rabbit dog or what have you? Joseph C. Kubik, 37 Pine Street, Gt. Barrington, Mass.

WANT HUNTING AND FISHING equipment, also camera and field glasses. Have books, typewriter, radio and other articles. Samuel Prokipschak, Box 77, Moscow, Pa.

WANTED TRANSMITTER, Prefer Utah kit ready assembled or any other make, will trade Loedy trap drum outfit complete. William Fletz, 1610 Mahan Ave., Bronx, N.Y.C.

LIKE TO SWAP SWL CARDS with all fellows all over the world. Will QSL 100%. Would also like to join all radio clubs the world over. Bob Larson, 618 North June St., Los Angeles, California, U.S.A.

SWAP 25 WESTERN OR LOVE story magazines for "The Book of Old Ships" by Culver and Grant. Want Indian head pennies. Ward E. Williams, 1414 10th Ave., Lake Charles, La.

SWAP: USED DRIVER TWELVE inch band saw for Sky Buddy or other good make short wave radio. Keith Neal, 115 Fifth Street, Clear Lake, Iowa.

(Continued on opposite page)

Amateurs Record Bird Calls

(Continued from page 332)

island is enshrouded in a dense fog. From the microphone the voice of the birds was run through a field amplifier constructed by Mr. Paul Kellogg of Cornell University. From the amplifier it was continued through an insulated cable to the amateur radio station a quarter of a mile away. The difficulties of preventing extraneous sounds and so-called "feed back" taxed the skill and ingenuity of the radio department.

Thomas A. Gross, W1JZM, gives an interesting account of the ham radio station on Kent's Island, in the third annual report of the Bowdoin Scientific Station (Bowdoin College, Brunswick, Me).

Metal Horn Focuses Ultra Short Waves

(Continued from page 332)

by Dr. Barrow in May, 1936, in connection with the transmission of telegraph, telephone and television signals through the inside of hollow metal pipes. The development of the horn was continued intensively from both experimental and theoretical angles, until it is now possible to design horns for particular applications with an engineering precision of perhaps higher degree than results for antennas of more conventional construction. One reason for the excellent agreement between calculations and experiment is that the waves, which start from a small rod placed in the throat of the horn, are forced to follow the guiding surfaces of the horn straight out into space and cannot easily go back on connecting wires, supports and the like to be radiated in unintended directions.

Prof. Barrows' experiments range in frequency from 300 mc. to 4,300 mc. (wavelengths from 1 meter to 7 cm., or 39" to 2.8").


Compared to other directive antennas that are used at micro wavelengths, the horn developed at M.I.T. is peculiarly easy to operate, since there is only one simple adjustment to make. The simplicity of construction of the horn, which can be made from sheet copper or galvanized iron, makes it an economical system to build. The fact that no insulators are used contributes to efficient operation and relatively permanent mechanical strength.

One feature of the electromagnetic horn of rectangular cross-section is that the sharpness of the beam in the two directions at right angles to its length can be controlled by varying the flares of the two sets of opposite sides. In this way, a fan-shaped beam may be sent out that is sharp in one plane and broad in another. By changing the shape of the horn a cigar-shaped beam can be radiated.

Waves may be started in the horn by locating a small rod antenna only a few inches long directly in the throat. Waves may also be started by connecting a hollow pipe carrying the ultra-short radio waves so that it opens into the throat, thus pouring the waves into the throat, where they broaden out through the horn and into the outer space. The first method may be likened to an old style phonograph, where the diaphragm and needle excited the sound waves directly in the throat of the now antiquated phonograph horn. The second method resembles a speaking tube connected to the small end of a horn.

Already this horn antenna is being applied to the "blind" landing of airplanes in a research carried on at the Massachusetts Institute of Technology for the Bureau of Air Commerce.

BARTER and EXCHANGE FREE ADS (continued)

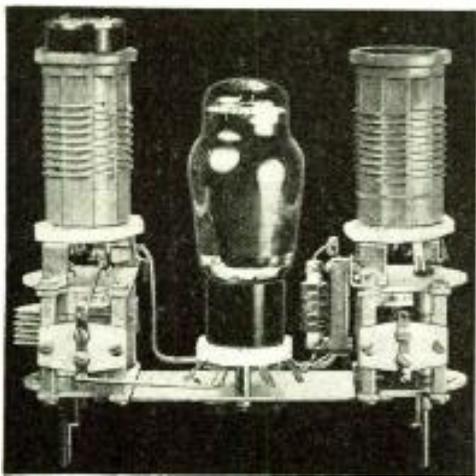


OSCILLATOR DOUBLER KIT

● CRYSTALS being rather expensive, for work on the higher frequencies, an oscillator doubler is an adjunct which affords efficiency with economy for almost any "ham" rig. Such a circuit, in foundation kit form, has just been brought out by Hammarlund Mfg. Co. under the designation of Model OD-10. The outfit is primarily designed for use with other of the manufacturer's units such as the B1-40 and PA-300 with which it forms a 300-watt all-band transmitter of modern design. It can also be used as a beginner's rig. In the latter instance, it is capable of producing outputs as high as 25 watts on two bands. Two hands are obtainable although a single crystal only is used. The manufacturer stresses the fact that the OD-10 is an excellent unit for the beginner; not only is he able to use it as a low-power transmitter in order to get on the air promptly and at moderate cost, but as his ability and finances enable him, he may add to it, making a more elaborate and powerful transmitter. The other units may be added without changing the unit.

All hardware is completely drilled and has a handsome satin finish.

The special isolantite crystal socket fits into the top of the coil form, so that both may be changed in a single operation. All connecting leads in the unit are short and direct, as the layout has been carefully engineered. The circuit shown in Fig. 1 is a standard "ham" circuit and uses any suitable pentode or tetrode, depending upon the power output desired. The unit, which measures 8 1/4" x 7 1/2" x 3 3/4" is entirely self-supporting and fastens directly to a panel with four mounting screws.

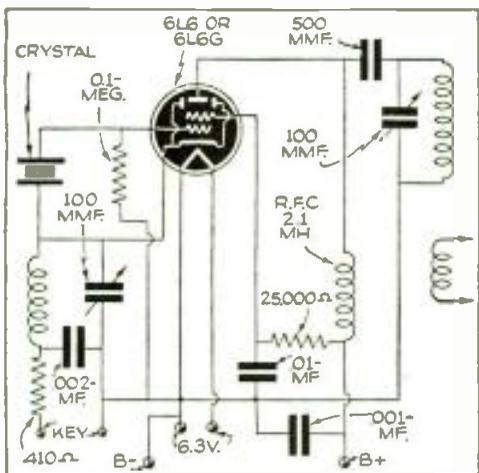This article prepared from data supplied by courtesy of Hammarlund Mfg. Co.



Hook-up of Oscillator Doubler.

SWAP USED HIGH SCHOOL mechanical drawing course and a Dietzen drawing compass. Want a one or two tube S.W. receiver or radio parts. Whatcha say? W. Morton, 1331 Flint St., Gastonia, N. C.

SHORT WAVE LISTENERS IN U.S.A. and foreign countries. Would like to exchange my SWL card for yours. I will QSL 100%. Edmund Brummer, 34-21, 84th Street, Jackson Heights, Long Island, New York.

20W. FONE-CW MASONITE RACK transmitter, SW15 complete, Thordarson T-5381, T-8322 modulation transformer, SW&T complete from December 1931, 80 issues. Low power transmitting parts, 21's. Want 35mm candid camera, tank, enlarger, W812S, 421 Wayne, Johnstown, Penna.

WANTED—COLLINS 30 DNB, 32B or other model transmitter. Hall-crafter Super Rider, Challenger II or National HHO. Trade Q3A's, new unused 809's for good candid camera, Eastman Bantam Special, Reomator or Retina, Radio W80QU, Wellsville, N. Y.

WILL TRADE FOR SMALL superhet, A.C. table model, one, SW3 complete set coils power pack (1 stage amp.) and speaker, Kenneth Torkeson, Box 67, Canby, Ore.

WANTED, A BICYCLE MOTOR for cash or trade. Send for list and describe motor, Raymond Zitta, 28-26 47 St., Long Island City, N. Y.

HAVE CIVIL WAR NEWSPAPERS, book, bayonet, gunband and sabre, Ice skates, Philco model 20 chassis, little repair, no tubes. Want Hall-crafter or Lionel Decker, 89 Lockman Ave., Marlers Harbor, New York, N. Y.

WILL TRADE ONE CRAFTSMAN combination wood plane, slightly used, with 23 cutters, for a 135 or 180 volt Carter Genemotor in good condition. Ben Wolf, Rt. one, Box 108, Burnet, Texas.

HAVE NEW \$10 PHILCO OUTPUT meter (model 012), 90 foreign stamps, 10 U.S. recent commems. and radio tubes. Want 4&6 trg. Hammarlund plug-ins. Offers? T. Smolar, Route No. 2, Box 21-M, New Brunswick, N. J.

WILL EXCHANGE A U. S. stamp book (new, unused) or many good carpenter tools for a 2 or 3 tube receiver or foreign stamps and radio parts. Will answer all letters. Charles Chapin, Crookston, Minnesota.

WANTED—GOOD SHORTWAVE electrical receiver or sender in trade for \$28 Gibson Kalamazoo guitar and case, good stamp collection in 37 Scott album, Everything Al, Frank Anderson, 49 Pershing Drive, Rochester, N. Y.

CATHOLIC BIBLE, ARC LAMP information on motion picture, merchants or roadshow, equipment, operation, starting on "shoe string." Wabi film, projection bulbs, P.E. cells, radio tubes, show equipment, motors. Harry Benson, Itoadshow, Chesterton, Indiana.

HAVE RADIO PARTS AND ALSO 22 rifle, 16 mm projector. Wanted: printing supplies of all kinds, Fred Word, P.O. Box 255, Falfurrias, Texas, for full list of parts and information.

WOULD LIKE TO EXCHANGE post cards, exchange one of my location for one of yours, in U. S. or foreign, exchange with girls and boys. Let's hear from you, 73. Burdett B. Trine, Sheridan, Ore.

USED AND UNUSED U. S. COM- memoratives to trade for other U. S. stamps, stamp for stamp, also trade radio parts and old Detective, Western magazines for U. S. stamps, or? Oscar E. Tanken, Greenbush, Minnesota.

WANTED TO BUY A JUNIOR Candler code course and a code sending machine, must be reasonable. Louis Edward Rothman, C.C.C. Co. 1299, Couch, Idaho.

ATTENTION, S.W. LISTENERS of the world, I will swap "shack" photos with anyone; will exchange SWL cards and correspondence with foreign listeners 100% here. QRA: L. M. Carling, 1601 S. 15th Avenue, Maywood, Illinois, U. S. A.

POSTCARD COLLECTORS, WILL exchange card for one from your locality. Please autograph picture side before sending. H. Van Deventer, Sioux Lookout, Ont., Canada.

TRADE RCA 8-INCH SPEAKER model A-100 in handsome metal cabinet, 48 issues Boys Life, Open Road for Boys for what have you, radio equipment, parts, etc. Clinton Slusher, Jr., 906 Stewart Ave., Roanoke, Va.

WILL TRADE 1937-38 ISSUES OF Popular Science and Modern Mechanics for radio magazines, books, or what have you? Louis Levine, Lake City, S. Car.

DO YOU HAVE A GOOD 5 AND 10 meter receiver you want to trade for a good All-Star Jr. Superhet? John Melvin, c/o Traffic Survey, 3731 Cedar Ave., Cleveland, Ohio.

WANTED: A GOOD TUBE TEST- er, Rider Manuals. Good phonograph motor and pickup. Used Radio tubes. Must be good also. What have you P.A. parts? Joseph Geviado, 159 Sabin St., Pawtucket, R. I.

TRADE DEVELOPING AND printing outfit, complete with practically new Eastman adjustable monel tank and chromium ferrotype plate, for code course, typewriter, test instruments. Will pay difference if necessary. Howard Doane, 151 Montclair, Knoxville, Tenn.

WANT 20 METER JOHNSON "Q," "bug" key, Xmitter meters, Have "A" and "B" F15 gc coils and other receiving equipment. Terence O'Rourke, 1832 Vancouver Drive, Honolulu, T.H.

WANT A-1 RADIO PARTS, micro-ammeter 4in2 controls for auto radio, etc. Swap elec. clipper for dry shaver. Have tools, typewriters, dozens of items, send your list. Geo. Keil, 418 1/2 W. Sprink, Freeport, Ill.

TRADE ANTENNA TRO L, straight line frequency variable condenser .0005 cap., voltage regulator 0-3 dc., A.C.H. sharp tuner vernier dial. All new parts. Want radio books, or what have you? Alexander Podstepny, 217 Pine St., Phila., Penna.

SWL'S AND HAMS, LET'S SWAP cards, I QSL 100%. Harry Link, 618 Academy Street, New York City, New York.

ATTENTION SWL'S, WOULD like to receive cards from any and all SWL's especially Tennessee and vicinity. QRA William Scott, 213 W. Holston Ave., Johnson City, Tenn., U.S.A.

TRADE 6L6 XTAL TRANSMITTER, volume controls, tubes, variable condensers, rest-tors. Write for list of hundreds of parts for trade. Want microphone transformer or? WILLIE, 913 Jefferson, Jonesboro, Ark.

WANT INSTRUCOGRAPH CODE machine with tapes. Will pay cash or give ham equipment for it. A. Morris Byrd, 119 N. Delsea Dr., Glassboro, N. J.

HAVE LEEDS 3564 KC. CRYSTAL with holder for 40 meter crystal, 5 meter equipment or what have you. Also have 35 diff. issues SWL and SW&T, Frank Zellavez, WILKE, 894 Rogers Pl., New York City.

I WANT TO EXCHANGE SWL cards, radio mags, and stamps. What say, O.M.'s? G-SWL R. G. Auckland, 69 Tottenham Lane, Hornsey-N8, London, Eng.

WANTED GOOD 5 AND 10 METER receiver. Will swap very good All Star Jr. Super-Heterodyne receiver, complete coils 13-565 M. special metal cabinet (16x12x8) less speaker. Edward Brooks, 1636 East 30th St., Cleveland, Ohio.

SWAP ONE TUBE 5 METER transceiver. Uses 53 tube. Complete with tube but less power supply. A small compact transceiver. For bug, crystal mike, or what have you? Raymond Twardzik, 41 Van Derveer St., Amsterdam, N. Y.

I HAVE A BROWNING "35" TO give in exchange for a good standard make and keyboard typewriter, portable preferred, or for a fast camera, Edward M. Weaver, 122 Tenth Avenue South, Seattle, Washington.

WANTED 5 METER TRANS- ceiver, also photographic equipment enlarger, etc. Trade for used radio tubes most types, power transformers, 2 6", 2 5", 1 14" dynamic speakers, etc. Anthony Ceracche, 103 Dryden Rd., Ithaca, New York.

SHORT WAVE LISTENERS IN U.S.A. and foreign countries. Would like to swap SWL cards with you, I QSL 100%. Will correspond in English and French. Frank Cole, Jr., 1249 Spruce St., Berkeley, Calif., U.S.A.

HAVE ARROWHEADS, SPEAR heads, small tomahawk, other Indian relics to trade for collectors' firearms, stamps or books. W. G. Conley, R.F.D. 4, Ozark, Ark.

HAVE CODE MACHINE, A VERY good transceiver 3 tube using 2-42s and 75 speech. Would like to trade for 10 meter crystal or some transmitter parts. Steve Fargo, Jr., 2374 River-view Ave., Dayton, Ohio.

SWL'S AND HAMS, LET'S SWAP cards, I QSL 100%. Want cards from all parts of U.S. and foreign countries. QRA—Bruce H. Stribling, N. Clemson Ave., Clemson, S. C., U.S.A.

TRADE BALTIMORE NO. 9 printing press, hand operated, assortment of type, for 2 or 3 tube A.C. or A.C.D.A. Sw set with tubes, coils, or what have you? Henry Botkin, Jr., 118 N. Main St., St. Marys, O., U.S.A.

HAVE A.C. SW3, 20, 40, 80 BAND spread coils, speaker, four tube dual band A.C. receiver, 16mm motor driven projector. All perfect condition. Trade for good communication super. Bill Sausen, 255 So. Syndicate, St. Paul, Minnesota.

ARGUS CAMERA, PERFECT CON- dition, only used for three rolls film, complete with leather case. Will trade for 6 1/2 x 9 centimeter film pack camera. Give full particulars. J. F. Newman, 1721 Milburn Ave., Cleveland, Ohio.

CANOE, STURDY, 16 FT., GREEN, arrangement for sail. Will trade for an oscilloscope, auto-radio of good make, Rider's manuals, Servicemen's or Candler's Code Course, or phone transmitter. H. William Propser, Solebury, Penna.

WANTED: RECORDING EQUIP- ment. Will trade transformers, speakers, auto radio, etc. I will answer all letters and cards. Seddon A. Strouse, 289 E. Bringham St., Germantown, Philadelphia, Pa.

MALAYA, ASIA, WANTED SWLS anywhere. Swap stamps, cards, and correspondence. All mails answered 100%. Tan Bin Hussain, Muntelbal, Ipoh, Perak, F.M.S.

WILL TRADE TEN LESSON course in taxidermy, good shape, for one tube plug coil radio, or Trimm phone 24,000 ohms. What have you? All letters answered. Abraham Blasonette, Tilbury Box 161, Ontario, Canada.

WILL TRADE FOR XMITTER, transmitter or xmitter parts. I have NRI \$100 radio course, 53 Radio News, 43 Radio-Craft, 20 SW&T, 13 Popular Science, etc. Write WBMNF, Madison, Wisconsin.

WANTED: TOY MOLDS, RADIOS, movie films and machines, etc., binoculars, testing instruments, windcharger, little radios, record changers, amplifiers, anything. Warren W. Wigner, 1220 Fairview, Fort Wayne, Ind.

WANT—2 TUBE U.I.F. PRODU- cts Ultra Air Rover, Buy or swap. Swap 2 W.E. 211, Weston switch-board voltmeter 0-15-150. Robert Leple, 3026 S. St. Louis Ave., Chicago, Ill.

WANTED—RADIO PARTS, SHORT wave revr., camera equipment or what have you. Have Junior Instructograph with two tapes, also stamps. All letters answered. Harold Tucker, Qrs. 342, West Point, N. Y.

WANTED FOR HOBBY COLLEC- tion—early type receiving tubes, Meyer cartridge, two clement diodes, Navy and Audion with candelabra base, etc. Let me know what you have. All correspondence answered. Charles Gosick, Fairfield, Iowa.

HAVE ONE 12" AND ONE 10" DYN- amics, power packs from ICA and Brunswick, radio parts and tubes. Want test equipment or what have you? M. H. Wells, 2090 Blvd. Dr., N. E., Atlanta, Ga.

WANT TO TRADE—HAM RADIO parts, good all wave Westinghouse, etc. Write—Walter D. Keith, Newton, Iowa.

WILL SWAP PICTURE POST- cards with anyone from U. S. or foreign countries. I will send you my card as soon as I receive yours. Bob Stratos, 3476 N. Holton St., Milwaukee, Wis., U.S.A.

WANTED: USED SMALL ONE cylinder gasoline engine in good working condition. Will pay cash. Send all particulars to K. Voss, 666 Onderdonk Ave., B'klyn, N. Y.

WILL SWAP KOLSTER POWER transformer for good short wave receiver. SWL's will exchange cards; with you from U.S.A. and foreign countries at 100%. Albert Braunan, South Acton, Mass.

HAVE SPRINGFIELD SINGLE shot, 22; metal tube ten meter converter; 4 tube midket T.R.F. receiver; 16mm projector and films. Want crystal, power transformer, other radio or photographic equipment. Saul Weingarten, Rt. 1, Box 94, Saugus, Calif.

TRADE TWO NEW \$8.00 RADIO bugs, 50 watt cw transmitter 53 xtal. dub., 6L6G final, Supreme 85PL tube, condenser and continuity tester, 8800 stamps. Want: receiver (SW3 or?) and other ham parts. Dawson, 1308-F, The Dalles, Oregon.

WILL SWAP 5 METER SUPER regen receiver complete with power supply and 5 meter transmitter complete with modulator for what have you. Columbus Emma, W60CQ, 6539 Gaviota Ave., Van Nuys, Calif.

SHORT WAVE LISTENERS OF the world. Swap cards. All QNL's answered promptly. Bob Liggett, 824 Passmore St., Philadelphia, Pa.

WILL SWAP TEN UNCUT ARIZO- na smoky tobaxes for milk, photo pickup, radio parts or what have you? Wayne Dickey, Wintersburg, Ariz.

HAVE SET OF 12 GAUGE RE- loading tools for paper shot shells Crimper, etc., fair used condition. Trade watsa? W. S. Crooks, W8LVG, Box 15, Stow, Ohio.

WILL EXCHANGE JIG SAW A condition, standard track with bridges, stamps, etc., for transceiver, reporter or what have you? Jack McCoullie, 26 Chestnut St., Salem, New Jersey. (Continued on following page)

(Continued from page 352)

I WISH TO HEAR FROM ALL stamp collectors wishing to exchange or swap. I will do typewriting or mimeographing for good used or mint stamps. Elvin W. Person, Esther, Alberta, Canada.

WANTED: SUPERSKYRIDER (1935 or later) will pay cash—or cash and trade a late model BCL Philco superb. Frank L. Garkus, 218 Wayland St., San Francisco, Calif.

TRADE—2 TUBE, 637-1247, AC-DC short wave set, coils, 2 General type 231-A amplifying transformers, new. Want volt-ohm-milliammeter or point to point tester or? J. A. Ketchum, Hamilton Place, Nashville, Tenn.

WOULD LIKE TO EXCHANGE SWL-QSL or fotos in U.S. or foreign countries. All cards received will be answered. All mail acknowledged. Frank Gregor, WBYK, 1921 W. 14 Ave., Gary, Ind.

TRADE 38/55 LEVER ACTION Marlin rifle (\$7), for radio parts, two tube aw battery receiver, 2 "955" tubes, carbon mike, what have you? Preferably parts or tubes. Vernon Preston, Rt. No. 2, Arlington, Wash.

301-A STEWART WARNER CON-verter swap for short wave receiver, power supply or parts. Write Dale Criderman, 13557 Vaughan, Detroit, Mich.

TRADE ANSCO-MEMO CAMERA f-6.3 lenses with one-hundredth shutter stop. With case and A1 condition for SW-3 receiver or other similar receiver. W3HLY, R. W. Sommers, 310 Ellis St., Glassboro, N. J.

SWAP—DRUM OUTFIT FOR high powered binoculars or crystal microphone or what have you? Will answer all mail. Frank J. Garone, 252 Navy St., Brooklyn, N. Y.

CORRESPONDENCE WANTED from all foreign countries. Will swap stamps, postcards, photos and nature specimens. All letters answered. Maylan Wilbur, Weld, Maine, U.S.A.

WANT USED NATIONAL DIAL type "BM" or "B" or Crowe 4 vernier dial. Will trade used 12A7 tube and 8-9 mfd filter condenser. John W. Creamer, 423 East Third, Chillicothe, Missouri.

SWAP:—COMPLETE PUBLIC AD-dress system with two speakers; B-eliminator, several small radios and many radio parts. What have you to offer? Richard Kelley, 1034 Elm St., Franklin, Pennsylvania.

WANTED AUTO AND TABLE model radios. Have stamps and all kinds radio parts. Terrence Gines, Box 14, Fort Lawn, S. C.

WOULD LIKE TO EXCHANGE SWL cards with any SWL in U.S. or foreign countries. All cards received here will be answered with our card. QRA John L. Ballin, 40 East 68 St., New York, N. Y.

WANTED, SMALL A.C. GENERA-tor around 20 to 50 watts, also gaso-line engine 1/2 to 2 H.P., suitable for driving generator. James N. Glass, R.R.1, Box 17, Eddyville, Ky.

SWL FOREIGN AND U.S. I SWAP cards 100%. Also want July and August 1938 issues of SW&T, will swap other radio magazines for same. Victor Samardza, 1044 Longfellow Ave., Bronx, N. Y.

HAVE SHOTGUN, 12-GAUGE, double barrel, Winchester, 38-40 carbine, Waltham 17-jewel, 16 size, cord watch. Want late model radio or? C. Moore, 211 East 103 Street, Los Angeles, Calif.

HAVE BRAND NEW UNIVEX camera and projector that have had but 2 rolls of film run through them. Anyone got a Skybuddy or Sky Chief or? R. E. Fuller, Ypsilanti, Michigan.

WILL SWAP COMPLETELY equipped communications superb; short-wave equipment; test equipment; radio books and magazines; tennis racket; kodak. Want a portable typewriter. Or what have you? John J. Vilkas, 1515 South 49th Court, Cicero, Illinois.

HAVE MOTOR DRIVEN 16MM projector to trade for electric trains and equipment or model airplane gas motor. Also have radios, amplifiers, transmitters, etc., to trade. Write Johnny Newsome, Box 725, Wake Forest, North Carolina.

HAVE ANGORA RABBITS, PIGE-ons, shortwave kit, radios, courses, firearms, stamps; want saxophone, xylophone, 22 rifles, cavies, lovebirds, pets? Hilary A. Munk, Somers, Conn.

HAVE RELOADING TOOL stereoscope with 100 views 35 years old camera, Simplex typewriter, books, radio parts, for cheap miniature cameras, value \$4.00, JIG saw, microscope, telescope, rifle scope, chromatic harmonica. Sofus Anderson, Lampkin, N. D.

HAVE THREE CHEAP CANDID cameras, back issues technical and fiction magazines in good condition. Want stamps, first day covers, radio parts, or? A. letters answered. Jack Towne, 1519 California St., Redding, Calif.

EXCHANGE RADIO PARTS. Bicycle parts and two 1/4 H.P. A.C. motors for any small radio sets or 35mm film equipment and films. Joseph Geraci, Jr., 3338 East 132nd St., Cleveland, Ohio.

SWL'S—I WOULD LIKE TO trade my SWL card for one of yours. I QSL 100%. QRA Roger Mais, 132 E. 8th St., Mishawaka, Indiana.

WANTED OLD AUTOMOBILE name plates and U.S. stamps in quantities of one to a hundred. Advise what you wish in exchange. Have large mimeographed swap list. Rudolph Zak, 2509 East 89th, Cleveland, Ohio.

ENGLAND CALLING. Wanted, small batches of foreign stamps, U.S.A., West Indies or South America. In exchange for English stamps uncommon values. Write S. Miles, 33 Freshwater Rd., Reading, England.

WILL SWAP MAGIC BOOKS which are in good condition for 40 or 80 meter crystal or other radio parts. Will answer all letters. Lloyd Geiser, 582 Beech St., Pottstown, Pa.

FOR TRADE—5 METER SUPER-regenerative receiver. Have heard Kenosha, Wisconsin, with it. 6C5 det.—76 audio—42 output. Want 40 meter stal. meters, xmitter parts, W2LJF, Curtis Purdy, 50 Cleveland St., White Plains, N. Y.

HAVE—B eliminators, speakers, tubes, SW-2 receiver, telescope, microscope, cartridges, plug-in coils. Want—electric razor, developing outfit, camera, photograph course, 16mm films, Hawaiian guide, movie camera or? Stanley, 2748 Meade, Detroit.

TRADE: NEW \$10-\$15 VALUE electric razors for—Radio physics course and Modern Radio Servicing, watchmakers tools, A.C. powerpack, s.w. receiver, test equipment, or? State condition, etc. All offers considered. Miner, Oakdale, Iowa.

HAVE 100 FICTION MAGAZINES (Western, detective, short stories, Blue-book, etc.) to swap. Want power supply for small set, SW receiver or what have you? Laurence Wolcik, 117 N. Spring Street, Bloomfield, New Jersey.

SWAP DETROLA 3 TUBE S.W. converter, two Zenith doublet antenna kits, Kodak Jiffy 6-20 camera, 600 volt power supply. All in A-1 condition. What am I offered in trade? Jack Israel, 319 Peshine Ave., Newark, N. J.

I WANT TO QSL WITH ANY SWL in the world as well as at home. So come on SWL I QSL 100%. William Slaughter, 1101 W. Cary St., Richmond, Virginia.

WILL SWAP A FIVE INCH DY-namo speaker, for a three inch magnetic speaker and a 3:1 ratio audio transformer. Warren Hardin Wilson, Glen Ullin, N. Dak.

I WILL EXCHANGE PRINTING for transmitter or receiver or parts for such. Please write printing orders carefully. Send to Warren Greene, 232 Grove Street, Woonsocket, Rhode Island.

WILL SWAP \$15 ELECTRIC razor for candid camera, Argus preferred. Also swap 35MM Super X 40 exposures on roll, on daylight loading cartridge. P. O. Box 36, Red Hook, New York.

HAVE THREE YEARS COMPLETE SW&T magazine '35, '36, '37. Also some Radio-Craft and Radio News mags. Want single button hand mike or transceiver hand set good condition. Jack Klein, 1983 Bryant Ave., Bronx, N. Y.

SWAP ALL-STAR SENIOR RE-ceiver complete (without cabinet) for factory-built short wave set. Cash extra if necessary. A. E. Kilmeldorf, 1487 Vyse Ave., Bronx, N. Y.

WANTED: 1/2, 2 OR 5 METER transceiver or transmitter also 3 or 4 tube S.W. receivers, trade about anything radio line, tubes, "B" supplies, parts, some photographic equipment. Paul Schulz, Jr., 431 45th Street, Moline, Illinois.

WILL SWAP STAMP COLLEC-tion value exceeds \$3.50 for a pair of Baldwin, Western Electric, or other type of good earphones. William John Paley, Jr., 39 Ontario Street, Albany, New York.

WANTED: S.W. SUPER-HETERO-dyna receiver. Must have 10 meter band; band-spread; beat oscillator and R.F. stage. Describe fully and state price. G. H. Thompson, 531 So. Main St., Pittston, Pa.

TRADE, 130 U.S. VALUABLE commemorative stamps, 4 rare Valtale crystals and others, for 40 or 80 meter crystal or key or what have you? Carl Waack, 323 Miami St., Piqua, Ohio.

SWL'S AND HAMS IN U.S.A. and foreign countries. Will exchange my SWL card for one of yours. I QSL 100%. (QRA) Joseph Ulling Jr., 1322 West Rush St., Phila., Pa., U. S. A.

SWAP SWL CARDS AND VIEW cards with foreign and U.S. listeners. Wanted photograph equipment. C. K. Guffey, 111 1/2 So. 15th St., Unionville, Mo.

WANT UNITED STATES COM-munications in blocks and first day covers. Have government postals, World War censored covers, T.B. seals, coins and stamps. Mervyn H. Reynolds, Assistant Educational Adviser, 158th Company CCC, Southwest Harbor, Maine.

WANTED: ANY KIND OF CAM-era equipment such as camera, enlarger or anything else. Will trade a \$35 Ukelin for equipment. Ukelin used very little, in good condition. All letters answered. Geo. Chaffield, Box 93, Wolcott, N. Y.

BUNDLE UP YOUR OLD OR NEW postcard views and send to me. For each one I'll forward one piece old Mexican money. (Not spendable now.) No two cards alike please. Harold Maniss, Colorado, Texas.

SHORT WAVE LISTENERS everywhere. I would like to exchange SWL cards with all. Foreign cards are especially wanted. Cyrus Will, 651 Briar Street, Kenilworth, Illinois.

WANTED—JEWELL ANALYZER type 1-665 and Jewell pattern 579 service test panel with remote control. Have microphones, meters, generators, telegraph, xmitter parts, gas engine, etc. Write Stanley J. Nicewicz, 79 Church St., Broad Brook, Conn.

HAVE 40 STOCK ORCHESTRAS-tions past song hits arranged for dance band. Also have solome, harmonium, plunger, cup miter for trumpet. Would like Pilot "Super Wasp" A.C. complete, or? James Birch, Box 141, Barstow, Calif.

HAVE ONE AND TWO TUBE radios, crystal sets, oil paintings. Want radio parts, riffs, good field glasses, etc. John Hayes, Doe Run, Mo.

TWENTY PIECE AMERICAN Fiber electric train set, 67 consecutive weekly Philatelic Gossips, many boys' books (Tom Swift, etc.), all A-1 condition. Want Candler course, "buk," radio technical course or books, transmitter. Byron Britt, Alliance, Nebraska.

HAVE STAMP COLLECTION value about \$50.00. Will trade for test equipment, battery operated. Also have parts for 6v. B Battery eliminator. S. S. Tyndall, Senlac, Saska., Canada.

I WILL TRADE A TWO TUBE Philmore battery set for a desk mike stand with a 5 or 6 inch ring with springs. Richard Kershaw, 846 University St., Springfield, Mo.

I HAVE AN 110 VOLT AC GAIN practice set and a good 8" dynamic speaker (will handle 6 or 8 watts). Am interested in transmitting crystals or other equipment or? Please wire to: Douglas Gates, Seguin, Texas.

WANT OLD TYPEWRITERS (such as Oliver, etc.) writ watch "Radio Amateur Course," printing press, SW radio, radio books and magazines. Send for list of swaps. M. Konon, 48 Edwards St., Patchogue, N. Y.

WILL TRADE ARGUS CAMERA 4.5 lens plus cash for Gross 3 tube Stand-by receiver complete with all coils. W2LZH, CCC No. 3205, Ashton, Idaho.

SWL'S—I WOULD LIKE TO EX-change SWL cards with any SWL in U.S. or in foreign countries. All cards received will be answered promptly. (QRA) Richard J. McCormick, 10 Bowman's, Mahanoy City, Pa., U.S.A.

HAVE GOOD AUDITORIUM guitar and new candid camera 16 pictures to roll. Trade for low power phone xmitter or 5 meter xmitter and receiver. Robert Taggart, 62 Orchard, Kansas City, Kansas.

WOULD LIKE TO TRADE FOR A 2 tube sw recr. a correspondence course in Radio. The recr. must be ac dc. Will answer all mail. A. Radeska, CCC 297 F-55, Lolo Creek, Missoula, Montana.

I WILL QSL 100% TO ANYONE in U. S. Canada and foreign countries who sends his or her card. Will join radio clubs. QRA—Alme Gros-louis, 1429 Main St., West Warwick, Rhode Island, U. S. A.

TRADE: RACK-PANEL POWER supply uses 2 R.C.A. 866's and has Weston 0-500 volt meter and variable voltage control. F.B. for class B work. Write W2TME, Chicago, Illinois, 2901 N. Kilbourn Ave.

HAVE MISC SERVICE MANUALS on Wells-Gardner (Airline), Crosley, and Zenith radios. Will trade for resistors, condensers, wire, etc. Paul Bahr, 1205 W. 10th St., Marion, Ind.

SWAP-POSTAL PRESLECTOR, complete course in Accounting from International Correspondence School, lots of radio parts. What am I offered in trade? Charles G. Hoffman, RR5, Box 300B, Terre Haute, Ind.


WILL SWAP SWL CARDS. Send your cards. We will send our cards. A. J. Schwartz, P. O. Box 695, Albany, N. Y.

tional crystal circuit at this frequency is not entirely satisfactory due to the large detuning effect experienced from the phasing control. In this circuit, a dual 50 mmf. condenser is used for phasing and is so altered that when one section is at full capacity the other is at minimum. This alteration is easily accomplished by sawing the rotor shaft in half between the two rotor sections and soldering the ends into a 1/2 inch length of tight-fitting tubing so that the sections are 180 degrees apart.

A shield can 2 1/2" x 4" x 3" deep houses the units indicated on the crystal circuit. The crystal holder plugs in at the top and the phasing condenser and the 15 mmf. unit (used as a selectivity control) project through the front and through suitable holes in the receiver panel. The 50 mmf. variable unit is reached through the side of the case; it is set at about 1/2 capacity and left there. The two 50 mmf. fixed units in series across the secondary of T3 are midget micas. Note that all these components are insulated from ground. Also be sure to disconnect the built-in tuning condensers on the secondary of T3 and the primary of T4, as they are not required.

TUBES

The 954 first detector is made regenerative, thus adding a tremendous amount of gain to the receiver and also aiding in image suppression. Bandspread of the H.F. coils is accomplished by tapping the main tuning condensers down toward the lower end of the coils. This makes it necessary to use small tank condensers across each secondary to set the bands properly. 100 mmf. units were used on the 40 and 20 meter coils and 50 mmf. units on the 10 meter coils. A 15 mmf. panel trimmer on the grid coil of V1 compensates for slight changes in antennas and the like. V8 is electron-coupled to the cathode circuit of V1 giving efficient mixing with no trace of detuning or pulling effects.

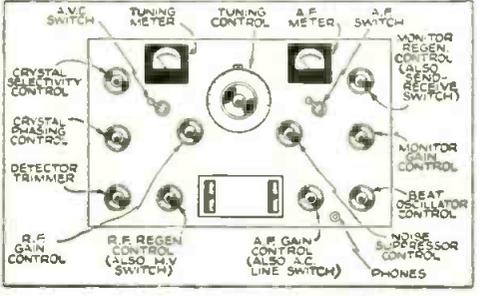

Front Panel "Controls."

Passing over the crystal filter which has already been described, we come to the two i.f. tubes, V2 and V3. These are 6L7's, chosen for their superior results as A.V.C. controlled tubes. With the grids connected as shown, less voltage is needed for A.V.C. than would be the case if 6K7's were used, while the gain is entirely adequate.

I.F. Gain Control: I.F. gain is varied by cathode voltage control of the 6L7's, while the tuning meter is operated by the plate current of these tubes. The meter is of the forward-reading bridge-type, and when the set is first placed in operation, must be adjusted to zero settings by means of the associated 1,000 ohm variable resistor. This resistor is mounted on the chassis below the "R" meter and must be adjusted when the tubes are warmed up and the R.F. gain control is set at the zero resistance setting, with no signal input to receiver. The A.V.C. switch shorts this meter when the A.V.C. circuit is grounded.

Tube V4 is the second detector. A.V.C. tube and noise-silencer and it certainly handles all its functions efficiently. The noise-silencer control is on the panel, of course.

Audio output from V4 goes through the A.F. volume control to the grid of one triode section of V5. The output of the triode goes through the fone jack to V6, the output tube. The second section of V5 is used as both B.F.O. and monitor, as previously noted. The B.F.O. is cut out by shorting the panel control, accomplished by bending one corner of a rotor plate. The B.F.O. is connected through a shielded lead to the 6H6 plate.

Coil Construction: The basis of each coil set is a 6 1/2" x 2 1/2" x 1/4" thick aluminum plate, which fits into a hole of this size in the front panel. The coil forms are 5-prong isolantite units, 1 1/2" diameter. These are held firmly with their tops against 2 1/2" x 1 1/2" pieces of bakelite or, preferably, Victrol. Brass rods 1/16" diameter are soldered into two of the coil form prongs, the upper ends being threaded and passing through the Victrol pieces, which No. 2-58 nuts hold them firmly. The Victrol pieces in turn are supported about 1 1/2" away from the 1/4" aluminum plates by screws run through bushings or sections of 1/4" brass tubing of the proper length. This leaves sufficient room between the Victrol piece and the aluminum plate to mount the tank condensers on brackets. Shield cans about 2 1/2" square and 3/8" high complete the assembly. A 1/4" hole in the top of the shield can allows the coil prongs to protrude, while a 1/8" hole in the side allows access to the tank condenser. A pair of knobs from the "5 and 10" facilitate handling the coil sets.

The sockets for the coils are simply mounted on another 3/4" piece of aluminum, screwed to the underside of the chassis. A triangular brace in the rear affords the required rigidity. The I.F. channel should be aligned using the crystal in a simple low power oscillator circuit, several of which were described in recent issues of SHORT WAVE AND TELEVISION.

DATA PRINTS

Only 33 $\frac{1}{2}$ c each
in orders of 3 at \$1

BUILD YOUR OWN—SAVE MONEY!



**RADIO CONTROL
FOR MODEL BOATS,
PLANES, ETC.**

Circuit data50c

**20 ELECTRIC LODGE &
PARTY TRICKS. Fun
Galore!**
"How to Do 'Em" Data 50c




**S-W DIATHERMY
(Artificial Fever)**

Dataprint giving Constructional
data for Small, Medium and
Large size App. (All 3)....50c

**Induction PIPE &
ORE LOCATOR**

Construction Data.....50c

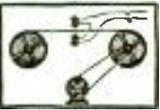


**RECORD VOICE OR
CODE on Steel Wire!**

Telegraphone Data, for
Voice or Code.....50c

TESLA COIL DATA:

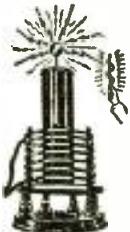Data Print—drawings and data for
building 36-inch spark Tesla...50c
Exciter—1 K.W. 20,000 Vt. Transf.
.....50c
3" Spk. Tesla Coil. Works on Ford
Coil50c
3" Spk. Oudin Coil. Works on 110
A.C.50c
20 "Tricks" with Teslas & Oudins
.....50c
8" Spk. Tesla Coil. 15,000 Volt
Exciter—1/4 K.W.50c
Transf.50c
Violetta—1" Spk. Oudin. Vibrator
type50c
How to Operate Oudins from V. T.
Osc.50c



More DATAPRINTS You Need!

Water Turbines "Re-winding" Armatures
Water Wheels Induction Balance
100 Mechanical Movements Telautograph
Motor Circuits (20) Einthoven String Galva-
nometer
Telephone Hookups (20) Magnets and Solenoids—
Polarized Relay. Ultra- Get our list
sensitive Wheatstone Bridge
Ring 4 bells on 2 wires Induction Coils—1 to 12
20 Simple Bell Hook-ups inch Spk data
Electric Chime Ringing fits Electric Pipe Thawer
any clock
Welding Trf. 2 K.W. 110 V. Prim. 18 V. Sec....50c
5 prints \$1.50 or 10 for \$2.00; single prints 50c

The DATAPRINT Co.

Lock Box 322 RAMSEY, N. J.

The shortwave listener will doubtless have no interest in the monitor but he should incorporate all the other features.

Coil Table							
T2	T1		T9				
Turns	Turns	BS	Cath.	BS	Cath.		
Turns	Turns	Tap	Tap	Tap	Tap		
40 M.	5	22	4	1 1/4	22	4	5
20 M.	4	10 1/4	2	1	10 1/4	2	2
10 M.	3	5	1	1/2	5	1	1 1/2

T1 and T9 spaced 1 1/4" long—No. 22 wire, bare or enameled.
T2 close wound No. 28 SSC.
Taps may need slight adjustments because of circuit and component variations.
BS—Bandspread.

List of Parts

- BLILEY**
1—CF1 crystal unit. 1600 kc.
- TRIPLETT**
1—227 R meter (0-1ma.)
1—227 rectifier type a.c. meter (0-1 V.)
(both with rear illumination)
- R.C.A.**
2—954 tubes (V1, V2) 1—6F8G tube (V5)
1—6H6 tube (V4) 1—6V6 tube (V6)
2—6L7 tubes (V2, V3) 1—5T4 tube (V7)

- PAR-METAL**
1—19" x 8 3/4" x 1/2" panel, No. 3722 (original painted French Gray)
1—Cabinet No. SC-128
1—Chassis No. 15215 (original painted French Gray)
1—Bracket No. SB-713 (original painted French Gray)
1—Speaker case No. SC-996

- HAMMARLUND**
4—HF15 trimmer condensers
6—CF5M coil forms
6—S8 sockets
2—S900 sockets
3—S5 sockets
1—S4 sockets
2—SWC-40 coils (monitor 10 and 20 meter bands)
1—SWC-41 coil (monitor 40 meter band)
1—MTCD-250C tuning condenser (main tuning)
6—APC50 padding condensers
4—APC100 padding condensers
1—HFD50 double 50 mmf. condenser (alter as per text)

- CORNELL-DUBILIER**
12—.01 mf. 600 V. paper condensers
7—.25 mf. 600 V. paper condensers
7—100 mmf. midget mica condensers
2—50 mmf. midget mica condensers
1—.004 mf. midget mica condenser
3—8 mf. 600 V. paper condensers, No. PE-B608
2—40 mf. 150 V. electrolytic condensers, No. BR4015
2—25 mf. 25 V. electrolytic condensers, No. BR252

- I.R.C. (Resistors)**
1—25M ohm BT 1/2 1—25M ohm BT2
2—2M ohm BT 1/2 2—100M ohm BT2
2—300 ohm BT 1/2 1—250 ohm BT2
2—.25 megohm BT 1/2 1—50,000 ohm type EPA
1—2.0 megohm BT 1/2 1—500 ohm type DHA
1—.5 megohm BT 1/2 1—50M ohm variable
4—50M ohm BT 1/2 1—1M ohm variable
1—1M ohm BT 1/2 2—10M ohm variable
1—500 ohm BT 1/2 2—1 meg. ohm variable
1—13M ohm BT 1/2 1—2M ohm variable
6—10M ohm BT1 3—SPST switches, No. 21

- ALADDIN**
1—G1601, 1600 kc. I.F. transformer (T3)
2—G1600, 1600 kc. I.F. transformer (T4, T5)
1—G1604, 1600 kc. I.F. transformer (T5)
1—S3729 1600 kc., B.F.O. oscillator (T7)

- GUARDIAN**
1—6.3 V. relay, series 110, 4 pole D.T.

- CROWE**
1—No. 296 vernier dial
10—No. 591 knobs with pointers

- JEFFERSON**
1—463-431 power transformer
2—466-430 shielded chokes

- CINAUDAGRAPH**
1—6" speaker No. MA6-8 with universal output transformer

- BLAN**
6—shield cans.


- YAXLEY**
1—Circuit-opening jack

- MISCELLANEOUS**
6—Handles for coil sets
1—SPDT center position off toggle switch (C-H)
1—DPST toggle switch (C-II)
1—Shield can 2 1/4" x 4" x 3" shield
3—Aluminum plates 6 1/2" x 2 3/8" x 1/8"
1 Set name plates (Gordon)
Hardware, etc.



**U. S.
ARMY
SIGNAL
CORPS
LAMPS**
The lamp
of 100 uses

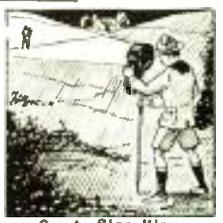- Scout Signalling
Night Bowling Alleys
Trailer Lamp
Night Motor Boat Races
Auto, Truck and Trailer
Camps
Tractor Light
Camp Light
Barnyard Lighting
Night Fishing
Radio Shacks
Bungalows
Picnics, etc.




Large size—12 1/2" wide, 5 3/4" deep, 1 1/2" high including socket, fitted with 10" silver blated reflector (no glass, nothing to break). Packed in portable box carrying case, with hinged cover, haup and handles. Every case contains weatherproof extension cord and Plug, 2 extra bulbs, selector key and signaling key and 16 page U.S. Army Instruction Manual. Shipping weight 18 lbs. Price... \$3.95 (Cost the Government about \$25.00) F.O.B. N. Y. 3 for \$10.00

Small size—6" wide, 5" deep, 1 1/2" high including socket. Lamp furnished with 6 volt bulb for A.C. current. One extra bulb furnished free. Additional bulbs, 15c each. Packed in a corrugated carton. Shipping weight 2 lbs. Price... \$1.95 (Cost the Government about \$10.00) F.O.B. N. Y. 3 for \$5.00

These lamps will make an attractive souvenir of the World War for your Club, Motor Boat, House, Den, Radio Shack or Country Home. They will also be an acceptable gift to any of your friends.

An Accurate, Eight Inch White Wood SLIDE RULE With A, B, C, D, C1 and K Scales

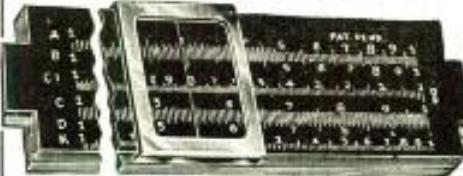Features
Nickel Silver Framed Indicator with integral friction spring. Scales calibrated directly on well-seasoned wood will retain accuracy regardless of temperature or humidity changes. Instructions and illustrations of primary operations clearly printed on back side of rule for ready reference or teaching. Each rule in a durable pocket carrying case for convenience and protection.



The extremely low price of these slide rules and their absolute accuracy makes them ideal for the student as well as the working man who has always wanted to use a slide rule.

Price 25c plus 5c postage.
20 Page Book of Instructions for using a slide rule. 5c each, plus postage
36 page Book of 300 Examples and Answers. 10c each, plus postage.



STOPPANI COMPASS

A Precision Instrument made in Belgium. Purchased by the U. S. Government at more than \$30.00 each. Ideal for Radio Experimenters Laboratory, also may be used as a Galvanometer for detecting electric currents in radio circuits. Rubly jeweled, solid bronze. 4 inches square, fitted in a hardwood case. Also used by hunters and surveyors. Our Price prepaid \$4.50 each

Send for catalog containing full descriptions of these items and many other unusually interesting and worthwhile merchandise.
GOLD SHIELD PRODUCTS
Dept. RT-10 350 Greenwich St. New York

A FREE BOOK FOR EVERYONE IN RADIO

1938 RADIO REFERENCE ANNUAL


RADIO-CRAFT

Remit ONE DOLLAR by check, money order or stamps for your FREE BOOK and Seven Months' Subscription to RADIO-CRAFT. 99T HUDSON STREET, NEW YORK, N. Y.

SHIPPING LABELS Size 2 1/2 x 4 \$1.50 per 1000

Printed in RED & BLUE with your name & address. Regular \$3.50 value. SAMPLES.

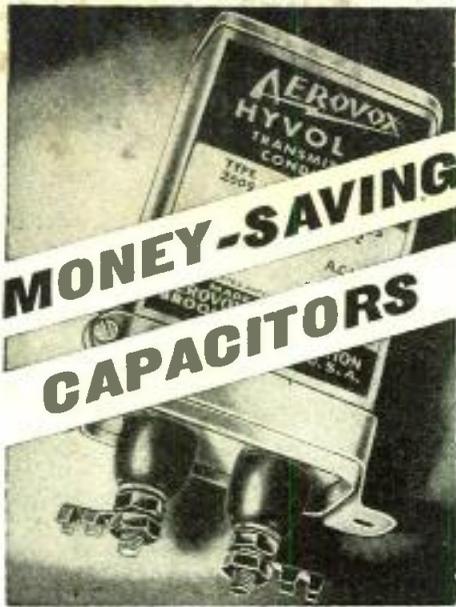SAMNICK 305 E. 45th St., New York City
Write for prices on printing.



● Mass-produced for new low prices, HYVOL capacitors for transmitting and other high-voltage applications are now available in oil-filled (heavy-duty) and wax-filled (normal-duty) types. ● Welded steel can. High-tension pillar terminals. Conservative ratings. 600 to 3000 v. D.C.W. ● Compare prices. Compare quality—at your local jobber's.



**CHASSIS — CABINETS
PANELS & CANS**
STANDARD SIZES ON HAND
SPECIAL SIZES MADE TO ORDER
KORROL RADIO PRODUCTS CO.
Dept. S-10
350 Greenwich St. New York City



**biggest
opportunities
still ahead**

In a decade radio has become a giant industry. The opportunities created are being enjoyed by trained men. The International Correspondence Schools Radio Course, prepared by leading authorities and constantly revised, WILL MAKE YOU A TRAINED MAN! A fascinating book — FREE.

INTERNATIONAL CORRESPONDENCE SCHOOLS
Box 2881-E Scranton, Penna.
Send me—free—information on subject checked:
 Radio Radio Service Man
 Radio Operator Electrical Engineer
Name.....
Address.....

World S-W Stations

(Continued from page 350)

Mc.	Call	Station
6.360	HRPI	SAN PEDRO SULA, HONDURAS, 47.19 m. 7.30-9.30 pm.
6.340	HIIX	CIUDAD TRUJILLO, D. R., 47.32 m. Sun. 7.40-10.40 am., daily 12.10-1.10 pm., Tues. and Fri. 8.10-10.10 pm.
6.335	OAXIA	ICA, PERU, 47.33 m., Addr. La Voz de Chiclayo, Casilla No. 9. 8-11 pm.
6.324	COCW	HAVANA, CUBA, 47.4 m., Addr. La Voz de las Antillas, P. O. Box 130. 6.55 am.-1 am. Sun. 10 am.-10 pm.
6.310	HIZ	CIUDAD TRUJILLO, D. R., 47.52 m. Daily except Sat. and Sun. 11.10 am.-2.25 pm., 5.10-8.40 pm. Sat. 5.10-11.10 pm. Sun. 11.40 am.-1.40 pm.
6.300	YV4RD	MARACAY, VENEZUELA, 47.62 m. 6.30-9.30 pm. exc. Sun.
6.295	OAX4G	LIMA, PERU, 47.63 m., Addr. Apartado 1242. Daily 7-10.30 pm.
6.290	HIG	TRUJILLO CITY, D. R., 47.67 m. 7.10-8.40 am., 11.40 am.-2.10 pm., 3.40-8.40 pm.
6.280	COHB	SANCTI SPIRITUS, CUBA, 47.77 m., Addr. P. O. Box 85. 9-11.30 am., 12.30-1.30, 4-7, 8-11 pm.
6.270	YV5RP	CARACAS, VENEZUELA, 47.79 m., Addr. "La Voz de la Philco." Daily to 10.30 pm.
6.255	YV5RJ	CARACAS, VENEZUELA, 47.18 m.
6.243	HIN	CIUDAD TRUJILLO, D. R., 48 m., Addr. "La Voz del Partido Dominicano." 12 n.-2 pm., 6-10 pm.
6.235	HRD	LA CEIBA, HONDURAS, 48.12 m., Addr. "La Voz de Atlántida." 8-11 pm.; Sat. 8 pm.-1 am.; Sun. 4-6 pm.
6.225	YVIRG	VALERA, VENEZUELA, 48.15 m. 6-9.30 pm.
6.210	—	SAIGON, INDO.CHINA, 48.28 m., Addr. Radio Boy-Landry, 17 Place A. Foray. 4.30 or 5.30-9.15 am.
6.210	TG2	GUATEMALA CITY, GUAT., 48.28 m., Addr. Dir. Genl. of Electr. Commun. Relays TG1 Mon.-Fri. 6-11 pm., Sat. 6 pm.-1 am. Sun. 7-11 am., 3-8 pm.
6.205	YV5RI	CORO, VENEZUELA, 48.32 m., Addr. Roger Leyba, care A. Urbina y Cia. Irregular.
6.200	H18Q	CIUDAD TRUJILLO, D. R., 48.36 m. Irregular.
6.200	ZGE	KUALA LUMPUR, FED. MALAY ST., 48.36 m. Sun., Tue. and Fri. 6.40-8.40 am.
6.185	HI1A	SANTIAGO, D. R., 48.5 m., Addr. P. O. Box 423. 7 am.-5 pm.
6.171	XEXA	MEXICO CITY, MEX., 48.61 m., Addr. Dept. of Education. 7-11 pm.
6.156	YV5RD	CARACAS, VENEZUELA, 48.71 m. 11 am.-2 pm., 4-10.40 pm.
6.153	HI5N	MOCA CITY, D. R., 48.75 m. 6.40-9.10 pm.
6.150	CJRO	WINNIPEG, MAN., CANADA, 48.78 m., Addr. (See 11.720 mc.) Daily 6 pm.-12 m., Sun. 5-10 pm.
6.150	ZPI4	VILLARRICA, PARAGUAY, 48.75 m. 5-6 pm.
6.147	ZRD	DURBAN, SOUTH AFRICA, 48.8 m., Addr. (See ZRK, 9.606 mc.) Daily exc. Sat. 11.45 pm.-12.50 am.; Daily exc. Sun. 3.30-7.30 am., 9 am.-3.45 pm.; Sun. 5.30-7.9-11.30 am., 12 n.-3.20 pm. Also 4-5 am., 3rd Sun. of month.
6.147	ZEB	BULAWAYO, RHODESIA, S. AFRICA, 48.8 m. Mon., Wed., and Fri. 1.15-3.15 pm.; Tues. 11 am.-12 n.; Thurs. 10 am.-12 n. Sun. 3.30-5 am.
6.145	HJ4ABE	MEDELLIN, COL., 48.79 m. La Voz de Antioquia. 11 am.-12 n., 6-10.30 pm.
6.140	W8XK	PITTSBURGH, PA., 48.83 m., Addr. Westinghouse Electric & Mfg. Co. Relays KDKA 11 pm.-12 m.
6.137	CR7AA	LAURENCO MARQUES, PORT. E. AFRICA, 48.87 m. Daily 12.05-1, 4.30-6.30, 9.30-11 am., 12.05-4 pm., Sun. 5-7 am., 10 am.-2 pm.
6.130	VP3BG	GEORGETOWN, BRIT. GUIANA, 48.94 m. From 5 pm. on.
6.130	COCD	HAVANA, CUBA, 48.94 m., Addr. Box 2294. Relays CMCD 7 am.-1 am.

Those interested in lower-frequency stations can refer to last month's list.

Please say you saw it in RADIO & TELEVISION

Index to Advertisers

Advertiser	Page
A	
ABC Radio Laboratories	362
Aerovox Corp.	384
Allied Radio Corporation	355
Astatic Microphone Laboratory, Inc.	365
B	
Barter & Exchange Free Ads.	380, 381, 382
Bliley Electric Co.	362
Browning Labs., Inc.	366
Brush Development Co., The	369
Bud Radio, Inc.	364
C	
Candler System Co.	374
Centralab	363
Chemical Rubber Publ. Co.	372
Commercial Notices	380
Cornell-Dubilier Electric Corp.	359, 371
Coyne Electrical School	323
D	
Dataprint Company	375, 383
Dodge's Institute	373
F	
First National Television	373
For Sale Ads.	380
G	
Gold Shield Products	383
H	
Hammarlund Manufacturing Co., Inc.	371
Henry Radio Shop	364
Hudson Specialties Company	370
I	
Instructograph Company	372
International Correspondence Schools	384
International Resistance Company	361
J	
Jarnak, Paul	369
K	
Korrol Radio Products Co.	384
Kusterman, Oscar B.	362
M	
Mass. Radio School	372
Miami Laboratories, Inc.	364
Modell's	369
N	
National Company, Inc.	Inside Back Cover
National Plans Institute	377
National Radio Institute	321
National Schools	372
New York YMCA Schools	372
O	
Omnigraph Mfg. Co.	374
P	
Paramount Prod. Co.	369
Premax Products	379
R	
Radio Amateur Course	Inside Front Cover
Radio & Technical Publ. Co.	372
Radio-Craft	383
Radio Publications	376
Radio Training Assn. of America	372
RCA Institutes, Inc.	372
RCA Manufacturing Co., Inc.	Back Cover
S	
Sammick	383
Sargent, E. M. Co.	365
Scientific Diathermy Corp.	365
Short Wave League	374, 375
Solar Mfg. Corp.	369
Sprague Products Co.	377
Sprayberry Academy of Radio	373
T	
Technifax	375
Telex Co.	373
Trim-Radio Mfg. Co.	369
Triplett Electrical Instrument Co.	375
W	
Wellworth Trading Company	366, 379
Wholesale Radio Service Co., Inc.	357, 367
Wiley, John & Sons, Inc.	374

(While every precaution is taken to insure accuracy, we cannot guarantee against the possibility of an occasional change or omission in the preparation of this index.)



THREE YEARS OLD—

and still a "Best Buy"

Three years brings obsolescence to most radios, but to the NC-100 it has brought increasing popularity. Time has proved the soundness of its design, its versatility, and its dependably high performance. As with other National products, details have been changed from time to time in line with our policy of constant improvement. There is a new direct-reading dial, a new meter. The cabinet is different. But there is never any change in the thoroughbred quality that has won so many friends, and held them.



NATIONAL COMPANY, INC., MALDEN, MASS.



Enjoy Foreign Reception At Its Best!

Here's a treat for short-wave listeners!

Listen in on this 16-tube receiver direct to stirring events happening in foreign countries. That's exactly what you can do with the ACR-111 Amateur Communication Receiver, and here are the reasons why: It's easy to operate—very selective—extremely sensitive and quiet in operation.

Judge for yourself what the ACR-111 has to offer. See it... Tune it... Examine it—at your nearest RCA Amateur Equipment Distributor, or write direct for full particulars. . . .

For maximum performance at minimum cost—use RCA radio tubes
RCA presents the Magic Key every Sunday, 2 to 3 P. M., E.S.T.
on the NBC Blue Network

RCA MODEL ACR-111 FEATURES:

- 16-tube superheterodyne circuit.
- Special broad band-spread tuning control.
- Ultra selective crystal filter for those hard to get station announcements when other station interference occurs.
- Noise Suppression eliminates most types of local noise.
- "Magic Eye" for accurate tuning. Indicates received signal strength thus determining reception conditions for your favorite stations.
- Beat Oscillator to locate the wave of weak stations.
- All popular wave lengths from 10 to 540 meters.
- Professional-like appearance.
- Connections for headphones to enjoy late programs.
- Complete with tubes, speaker—ready to operate, \$129.50 f.o.b. factory.



for Amateur Radio

RCA MANUFACTURING CO., INC., CAMDEN, N. J. • A Service of the Radio Corporation of America